

# HOW TO USE TV TEST PATTERNS


# POPULAR ELECTRONICS

JUNE  
1961

35  
CENTS
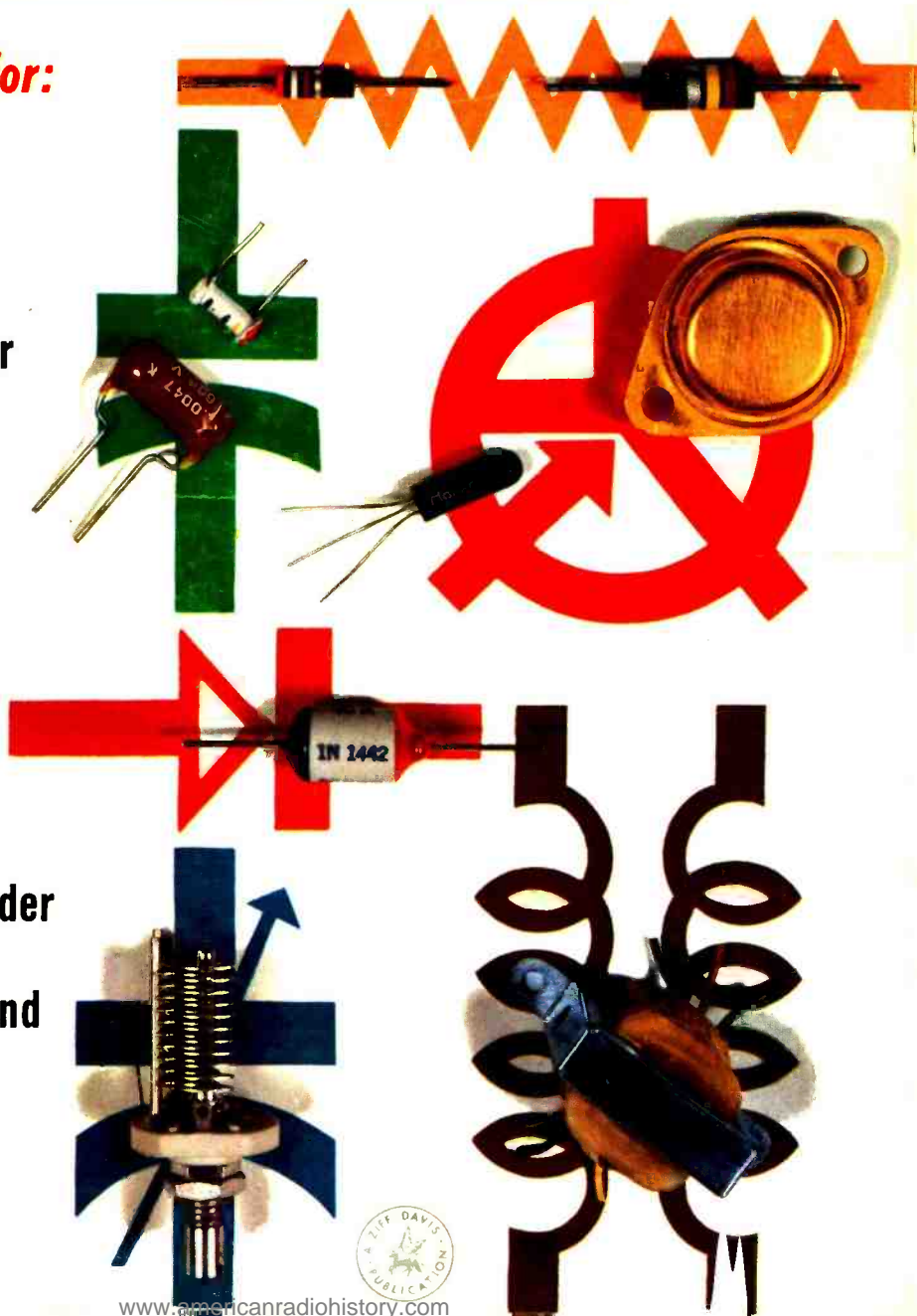
## Building Plans for:

- Transistorized Heart Monitor
- Moisture Meter for Gardeners
- Underwater Fish Caller
- Magnetic Coin Tossing
- Musical Telephone Holder
- CB to Ham Band Transceiver
- Loudspeaker Metronome



# This is CADRE 2-Way Radio

developed by **CADRE INDUSTRIES CORP.**  
for the 27 Mc **CITIZENS BAND OPERATION**


These CADRE units are built to the highest standards of the electronics industry, by a company that has been long established as a prime manufacturer of precision electronic research equipment and computer assemblies. CADRE transceivers are 100% transistorized — compact, lightweight . . . engineered for unparalleled performance and reliability.

The CADRE 5-Watt Transceiver, at \$199.95, for example, for offices, homes, cars, trucks, boats, aircraft, etc., measures a mere 11 x 5 x 3", weighs less than 6 pounds! Nevertheless, it offers 5 crystal-controlled transmit/receive channels (may be used on all 22), and a range of 10 miles on land, 20 over water!

The CADRE 100-MW Transceiver, \$124.95, fits into a shirt pocket! Weighs 20 ounces, yet receives and transmits on any of the 22 channels . . . efficiently, clearly . . . without annoying noise. A perfect "pocket telephone"!

For the time being, it is unlikely that there will be enough CADRE transceivers to meet all the demand. Obviously, our dealers cannot restrict their sale to the fields of medicine, agriculture, transportation, municipal services, etc. However, since these CADRE units were engineered for professional and serious commercial applications—and cost more than ordinary CB transceivers—we believe that as "water finds its own level," CADRE transceivers will, for the most part, find their way into the hands of those who really need them.

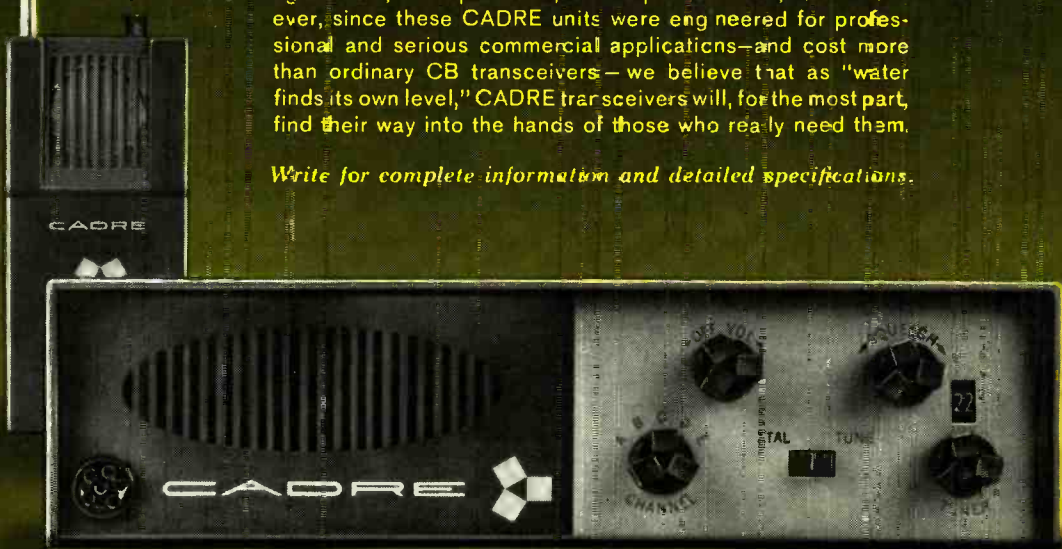*Write for complete information and detailed specifications.*



**CADRE INDUSTRIES CORP., Endicott, N. Y.**

*Prices appearing in this advertisement are suggested retail prices*

[www.americanradiohistory.com](http://www.americanradiohistory.com)

New G-E Profitable Service Management Course tells...

# HOW TO INCREASE YOUR BUSINESS, MAKE MORE MONEY BY PROVEN EFFECTIVE METHODS

Are you making as much money as you should? Charging enough for service calls? Paying more in taxes than you should? How can you protect against stock pilferage, overstocking, understocking? Overdue bills a problem? . . . Getting your share of new business? Is your personal selling and advertising as effective as it could be? How about special offers, seasonal promotions? How many TV and radio homes are in your county?

Find the answers to these and hundreds of other problems that affect your everyday business, in General Electric's new Profitable Service Management Course. A complete business management and development program specially prepared for TV and radio service dealers. Learn step by step how to assure a satisfactory profit margin, increase business with methods proved successful by service dealers from coast to coast. Four-part program includes:

**1 "Sound Business Practices,"** an 85-page manual which will help you set up a successful business or increase your present business. 17 topics in 4 chapters: Business For Profit • Planning Your Business • Organizing Your Business • Controlling Your Business

**2 "Selling Electronic Service,"** a 57-page guide to increased sales through modern advertising, sales promotion and merchandising techniques. 14 topics in 3 chapters: Attracting New Customers • Promoting Your Business • Keeping Customers Satisfied

**3 "Sounds of Success,"** 33 $\frac{1}{3}$  LP record reveals the secrets of operating a profitable electronic service center as told by successful dealers.

**4 Workbook** for checking your acquired knowledge, prior to receiving your Management Award Certificate.

This is not a get-rich-quick course—not an electronics course, but a down-to-earth guide for turning your technical skills into more business and profits. It's easy to study; complete; prepared by experts; handsomely packaged for your bookshelf.

**GENERAL  ELECTRIC**

— Send for your Profitable Service Management Course today! —

GENERAL ELECTRIC COMPANY, DEPT. B, 3800 N. Milwaukee Ave., Chicago 41, Illinois



Please ship prepaid:

ETR 2202 Profitable Service Management Course, \$12.50 each, or \$10.00 plus 10-GBQ6G-A or GTB G-E tube carton tops.

My check or money order is enclosed for the required amount plus any sales or use tax applicable in my area.

Name.....

Address.....

City..... Zone..... State.....

# POPULAR ELECTRONICS

VOLUME 14

NUMBER 6

JUNE

1961



POPULAR ELECTRONICS is indexed  
in the Readers' Guide  
to Periodical Literature

## Special Feature

The Zener Diode.....R. J. Shaughnessy 76

## Electronic Construction Projects

Listen to Your Heart.....Edward Lininger 47  
Heads . . . or Tails?.....Harold P. Strand 51  
Transistorized Metronome.....Norman Latner 54  
Musical Telephone Holder.....Herbert Friedman 71  
Electronic Fish Caller.....James J. Bucher 74  
Soil Moisture Meter.....Ronald Wilensky 85  
AC/DC Electronic Load.....Harold Reed 89  
Transistor Saver.....George E. Lang 90  
Storage Battery Tester.....J. C. Chapel 92  
Low-Power/High-Power Relay.....Herb S. Brier, W9EGQ 95

## Audio and High Fidelity

Hi-Fi Showcase.....18  
Tuner Kits Come of Age.....56  
Tape Speeds—Then and Now.....Richard A. Flanagan 67  
Your Connections are Important.....Jim Kyle, K3JKX/6 73  
First Mike Kit.....91

## Amateur, CB, and SWL

CB Rig Goes "Ham".....Edward M. Noll, W3FQJ 64  
On the Citizens Band.....Tom Kneitel, 2W1965 87  
Across the Ham Bands: How to Avoid Violating Regulations. Herb S. Brier, W9EGQ 93  
Short-Wave Report: False Reporting.....Hank Bennett, W2PNA 83  
Short-Wave Monitor Certificate.....84

## Electronic Features and New Developments

POP'tronics News Scope.....6  
They'll Fly Safely.....Ken Gilmore 41  
Interpreting TV Test Patterns.....J. K. Locke 59  
Space Electronics.....Oliver P. Ferrell 68  
Transistor Topics.....Lou Garner 96  
Carl and Jerry: First Case.....John T. Frye, W9EGY 99

## Departments


Letters from Our Readers.....10  
POP'tronics Bookshelf.....24  
New Products.....30  
Tips and Techniques.....36  
Index to Volume 14 (Jan.-June, 1961).....124

Copyright © 1961 by ZIFF-DAVIS PUBLISHING COMPANY. All rights reserved.



# THIS COULD HAPPEN TO YOU... UNLESS THE KIT YOU BUILD IS A PACO

COMPARE THESE PACO FEATURES:

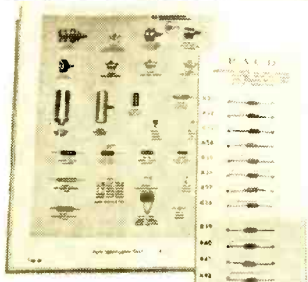

No mistaken identity or endless searching. Parts are clearly pictured and labeled; resistors are neatly mounted and identified!



Step-by-step instruction book makes assembling a Paco Kit foolproof! Paco gives you giant, fold-out diagrams on corresponding instruction pages so you can see both at the same time.



### PACO Model C-25 IN-CIRCUIT CAPACITOR TESTER KIT

Reveals dried out, shorted, or open electrolytics—in the circuit—with Paco's exclusive Capacity Dial. Instantly finds open or direct shorted capacitors without removing from circuit. Great time saver!

**Specifications:**

**SIMPLE SEQUENTIAL TEST:** reveals open or shorted capacitors, including electrolytic types.

**ELECTROLYTIC DIAL:** indicates actual electrolytic values while capacitor is in-circuit; any electrolytic which yields a capacity reading on Electrolytic Dial is automatically revealed as not open or shorted.

**ELECTROLYTIC TEST:** indicates in-circuit electrolytic capacity from 2 mfd to 400 mfd in two ranges; condenser is automatically proved non-shortened and not open if Capacity Reading can be obtained.

**Model C-25:** Kit, complete with PACO-detailed assembly-operating manual. **Kit Net Price: \$19.95**  
**Model C-25W:** Factory-wired, ready to operate. **Net Price: 29.95**



### PACO Model DF-90 TRANSISTORIZED DEPTH FINDER KIT

Protect your boat against shoals and underwater hazards with this compact, easy-to-read depth finder. Transistors prolong battery life, provide utmost accuracy and portability. A boon to fishermen—locates hard-to-find schools of fish. A low cost safety device for every boat owner.


**Specifications:**

**FULLY TRANSISTORIZED:** 5 transistors, with a low battery drain for extremely long battery life.

**HIGH INTENSITY INDICATOR:** for sensitive, accurate response under all conditions.

**FAST, EASY READINGS:** made possible by means of oversized scale calibrated at one-foot intervals from 0 to 120 feet.

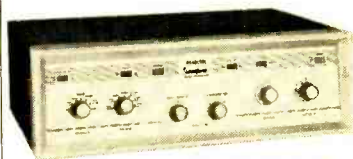**Model DF-90:** Kit, complete with PACO-detailed assembly-operating manual. **Kit Net Price: \$84.50**  
**Model DF-90W:** Factory-wired, ready to operate. **Net Price: \$135.50**



### PACO Model SA-40 STEREO PREAMP-AMPLIFIER KIT

Assemble a superb home music system with this true 40 watt stereo preamp-amplifier. Unmatched flexibility, less than 0.5% distortion, and handsome design make this the ideal component for music lover and audiophile alike!

**Specifications:**

**MUSIC WAVEFORM POWER OUTPUT:** 25 watts per channel (50 watts total).

**RESPONSE:** 30 cps to 90Kc.  $\pm 1.0\%$  db

**HARMONIC DISTORTION:** less than 0.5% at 20 watts per channel output.

**Model SA-40:** Kit, complete with black and gold case and PACO-detailed assembly-operating manual. **Kit Net Price: \$79.95**

**Model SA-40W:** Factory-wired, with black and gold case, ready to operate. **Net Price: \$129.95**

## FREE! COMPLETE ILLUSTRATED CATALOG

Mail this coupon for the complete Paco catalog of electronic equipment kits, including test instruments, measuring instruments, and high fidelity components.



Paco Electronics Company, Inc., Dept. PE6  
70-31 84th Street, Glendale 27, L. I., N. Y.  
Please send me your complete illustrated catalog.

Name .....

Address .....

City..... Zone..... State.....

©PACOTRONICS, INC. 1961

# POPULAR ELECTRONICS

World's Largest-Selling Electronics Magazine

Average Net Paid Circulation Over 357,000

This month's cover photo by Irv Dolin

**Publisher**  
PHILLIP T. HEFFERNAN

**Editor**  
OLIVER P. FERRELL, 2W1665

**Managing Editor**  
JULIAN M. SIENKIEWICZ  
WA2CQL

**Art Editor**  
JAMES A. ROTH

**Associate Editors**  
RICHARD A. FLANAGAN  
MARGARET MAGNA

**Assistant Editor**  
MARC E. FINKEL

**Editorial Assistants**  
MARY ANNE O'DEA  
MARIA SCHIFF


**Draftsman**  
ANDRE DUZANT

**Editorial Consultant**  
OLIVER READ, W4TWV

**Contributing Editors**  
H. BENNETT, W2PNA  
H. S. BRIER, W9EGQ  
J. T. FRYE, W9EGV  
L. E. GARNER, JR.  
T. KNEITEL, 2W1965

**Advertising Manager**  
WILLIAM G. McROY, 2W4144

## COMING NEXT MONTH

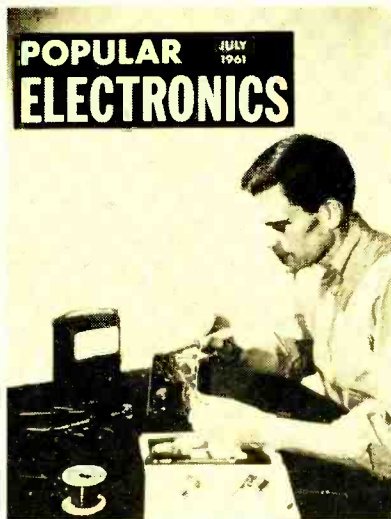

(ON SALE JUNE 27)

- **SHORT-WAVE LISTENING**  
Learn the best times to listen to short-wave broadcasts from Asia and the Pacific islands. Call letters, locations, and frequencies are given for all English-language stations in this area heard in the United States.
- **TRANSISTORS IN HI-FI**  
Will transistors ever edge out tubes in hi-fi as they have in other areas? Here's an informative look at some of the advantages transistors offer the hi-fi field as well as some of the problems they pose.
- **CB POWER METER**  
With maximum input on CB rigs limited to 5 watts, operating at peak efficiency is a "must." For about \$10, you can build a meter which makes measuring CB power as easy as 1-2-3, and gives an SWR reading as well.

ZIFF-DAVIS PUBLISHING COMPANY,  
One Park Ave., New York 16, N. Y.  
William B. Ziff, Chairman of the Board  
(1946-1953); William Ziff, President;  
W. Bradford Briggs, Executive Vice  
President; Hershel B. Sorbin, Vice  
President and General Manager;  
Michael Michaelson, Vice President  
and Circulation Director; M. T. Bir-  
mingham, Jr., Vice President and  
Business Manager; Richard Kislik,  
Treasurer; Charles Housman, Finan-  
cial Vice President.



**BRANCH OFFICES:** Midwestern Office,  
434 S. Wabash Ave., Chicago 5, Ill.,  
Jim Weakley, Advertising Manager;  
Western Office, 9025 Wilshire Blvd.,  
Beverly Hills, Calif., William J. Ryan,  
Western Manager.

**Foreign Advertising Representatives:**  
D. A. Goodall Ltd., London; Albert Mil-  
hado & Co., Antwerp and Dusseldorf.

**SUBSCRIPTION SERVICE:** Forms 3579 and all subscription correspondence should be addressed to Popular Electronics, Circulation Department, 434 South Wabash Avenue, Chicago 5, Illinois. Please allow at least four weeks for change of address. Include your old address as well as new—enclosing if possible an address label from a recent issue.

**CONTRIBUTORS:** Contributors are advised to retain a copy of their manuscripts and illustrations. Contributions should be mailed to the New York Editorial Office and must be accompanied by return postage. Contributions will be handled with reasonable care, but this magazine assumes no responsibility for their safety. Any copy accepted is subject to whatever adaptations and revisions are necessary to meet the requirements of this publication. Payment covers all author's, contributor's and contestant's rights, titles, and interest in and to the material accepted and will be made at our current rates upon acceptance. All photos and drawings will be considered as part of material purchased.

**MEN 17 to 55**



# DeVry Tech's Electronic Training

*has helped Men like these Get Better Jobs or Shops of their own...*

# How about YOU?



**No Advanced Education Required**

## **NO PREVIOUS TECHNICAL EXPERIENCE NEEDED!**

Men from practically every walk of life have won better jobs or businesses of their own through DeVry Tech's program. Many of these men, like thousands of others, had no previous technical experience. They prepared either in our well-equipped Toronto or Chicago laboratories, or at home in their spare time without interfering with their regular jobs.

The "Electronic Age" is here! Opportunities for men 17 to 55 are great! Fill in coupon below for FREE details! Act now!


### **LIVE-WIRE EMPLOYMENT SERVICE**

DeVry Tech's Placement Department is in contact with some of the best-known employers in the Electronics field. The service is free to all graduates — and DeVry Tech's record in helping to place men has been outstanding.

**Get FREE Facts!**



**GET 2 FREE BOOKLETS**

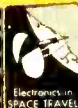

We'll give you free copies of interesting booklets, "Pocket Guide to Real Earnings" and "Electronics in Space Travel." See for yourself how you may take advantage of the opportunities in this growing field.

**DRAFT AGE?** We have valuable information for every man of draft age; so if you are subject to military service, be sure to check the coupon.

Accredited Member of National Home Study Council

### **MAIL COUPON TODAY!**

**DEVRY TECHNICAL INSTITUTE**  
4141 Belmont Avenue • Chicago 41, Illinois • Dept. PE-6-R

Please give me your two free booklets, "Pocket Guide to Real Earnings" and "Electronics in Space Travel"; also include details on how to prepare for a career in Electronics. I am interested in the following opportunities (check one or more):

- Space & Missile Electronics
- Television and Radio
- Microwaves
- Radar
- Automation Electronics
- Communications
- Computers
- Broadcasting
- Industrial Electronics
- Special "Short Courses"

Name \_\_\_\_\_ Age \_\_\_\_\_  
 Please Print  
 Address \_\_\_\_\_ Apt. \_\_\_\_\_  
 City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

Check here if you face military service.  
 Canadian residents: Write DeVry Tech of Canada, Ltd.,  
 970 Lawrence Avenue West, Toronto 19, Ontario

Here are some of the many Electronic opportunities DeVry Tech's program will fit you for:

- COMMUNICATIONS • TELEVISION • RADIO • GUIDED MISSILE CONTROL
- COMPUTERS • RADAR • MICRO-WAVES • INSTRUMENTATION
- AUTOMATION ELECTRONICS

"One of North America's Foremost Electronics Training Centers"



**DeVRY TECHNICAL INSTITUTE**  
CHICAGO • TORONTO



**UNDERWATER VTVM**—Specially constructed to meet military conditions aboard Polaris-firing submarines, the VR-2100 voltmeter is equally at home under water as on shore. Designed by the Cubic Corporation of San Diego, it has been explosion-proofed, can withstand 50G shock, and can operate in highly volatile acid atmospheres usually considered off-limits for such delicate electronic equipment. Incidentally, television repairmen will be able to combine pleasure with business when Scuba diving.



**ELECTRONIC SPIDER**—Raytheon engineers have come up with a unique spider-like packaging idea. Three diodes, a coupling network, a transistor and two resistors—comprising a basic computer building block—are squeezed into a case which would normally contain only a transistor. One such block, a logic unit, has seven leg-like leads to join it to other electronic elements in a modern data processing machine. So the next time you want to step on a spider, first make sure it's a logical step.



**WHEELED MISSILE**—The U. S. Air Force has taken to the nation's highways in order to transport its potent Minuteman ICBM to "hardened" underground sites. Minuteman, a three-stage solid-propellant missile capable of carrying a nuclear warhead, is moved from the assembly plant to the launching site in a motorized transporter. At the site, the missile in its 63'-long, 8500-pound container is raised to a vertical position by means of two erector actuators which can lift 108,000 pounds. Then the missile is gently lowered into the well-like concrete-lined tube from which it will be launched in the event of an emergency. After the emplacement of the missile, the container is lowered back on the transporter. The transporter-erector-emplacment system was developed by the Bendix Corporation.



**TOASTING A NEW POWER SOURCE** drives a small electric motor and its propeller. The power is derived from two thin plates which are heated like pieces of bread in a toaster. Even though removed from the heat source, these plates continue to produce electricity as long as the stored heat remains. It's been tabbed the "Austin effect"—after its discoverer, a Westinghouse engineering consultant. The power source is rechargeable in the same way as the battery in your car.

*More on page 8*

POPULAR ELECTRONICS



# Do you WISH you were EMPLOYED in ELECTRONICS?

## F.C.C. LICENSE—THE KEY TO BETTER JOBS

An F.C.C. *commercial* (not amateur) license is your ticket to higher pay and more interesting employment. This license is Federal Government evidence of your qualifications in electronics. Employers are eager to hire *licensed* technicians.

## WHICH LICENSE FOR WHICH JOB?

The **THIRD CLASS** radiotelephone license is of value primarily in that it qualifies you to take the second class examination. The scope of authority covered by a third class license is extremely limited.

The **SECOND CLASS** radiotelephone license qualifies you to install, maintain and operate most all radiotelephone equipment except commercial broadcast station equipment.

The **FIRST CLASS** radio telephone license qualifies you to install, maintain and operate every type of radiotelephone equipment (except amateur) including all radio and television stations in the United States, its territories and possessions. This is the highest class of radiotelephone license available.

## GRANTHAM TRAINING PREPARES YOU

The Grantham course covers the required subject matter completely. Even though it is planned primarily to lead directly to a first class FCC license, it does this by **TEACHING** you electronics. Some of the subjects covered in detail are: Basic Electricity for Beginners, Basic Mathematics, Ohm's and Kirchhoff's Laws, Alternating Current, Frequency and Wavelength, Inductance, Capacitance, Impedance, Resonance, Vacuum Tubes, Transistors, Basic Principles of Amplification, Classes of Amplifiers, Oscillators, Power Supplies, AM Transmitters and Receivers, FM Transmitters and Receivers, Antennas and Transmission Lines, Measuring Instruments, FCC Rules and Regulations, and extensive theory and mathematical calculations associated with all the above subjects explained simply and in detail.

## OUR GUARANTEE

If you should fail the F. C. C. exam after finishing our course, we guarantee to give additional training at **NO ADDITIONAL COST**. Read details in our free booklet.

# GET your first class commercial F.C.C. LICENSE QUICKLY!

Learn by Correspondence or in Resident Classes

Grantham training is offered by correspondence or in resident classes. Either way, we train you quickly and thoroughly---teach you a great deal of electronics and prepare you to pass the F. C. C. examination for a first class license. Get details now. Mail coupon below.

**This booklet FREE!**

This free booklet gives details of our training and explains what an F. C. C. license can do for your future. Send for your copy today.



## Upgrade Your Income

To get ahead in electronics—first, you need the proper training; then, you need “proof” of your knowledge. Your first class commercial F. C. C. license is a “diploma” in communications electronics, awarded by the U. S. Government when you pass certain examinations. This diploma is recognized by employers. Grantham School of Electronics specializes in preparing you to earn this diploma.

Grantham training is offered in resident classes or by correspondence. Our **free** booklet gives complete details. If you are interested in preparing for your F. C. C. license, mail the coupon below to the School's **home office** at 1505 N. Western Ave., Hollywood 27, California—the address given in the coupon—and our free booklet will be mailed to you promptly. **No charge—no obligation.**

# Grantham School of Electronics

HOLLYWOOD  
CALIF.

SEATTLE  
WASH.

KANSAS CITY  
MO.

WASHINGTON  
D. C.

RESIDENT CLASSES  
HELD IN FOUR CITIES

If you are interested in attending day or evening classes mail the coupon for free information to our home office in Hollywood, Calif.



(Mail in envelope or paste on postal card)

To: GRANTHAM SCHOOL OF ELECTRONICS  
1505 N. Western Ave., Hollywood, Calif.

Gentlemen:

Please send me your free booklet telling how I can get my commercial F.C.C. license quickly. I understand there is no obligation and no salesman will call.

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

I am interested in:  Home Study,  Seattle classes  
 Hollywood classes,  Kansas City classes,  Washington classes

MAIL COUPON NOW—NO SALESMAN WILL CALL →

13G

# NEWS SCOPE

*Continued*



UPI


◀ **ON THE AIR**—Filled with helium, this small blimp-shaped balloon carries a radio antenna wire some 55 feet above the ground as part of a lightweight and compact radio rescue beacon to help locate downed aircraft. Developed by the Crosley Division, Avco Corporation, in Cincinnati, the beacon sends out a signal—for 24 hours—that can be picked up thousands of miles away. It can be released by the pilot of the stricken aircraft or propelled free by the jar of a crash landing. The beacon, including the parachute, balloon, radio transmitter, antenna gear and catapult mechanism, is packaged in a container 36" long and 5½" in diameter. Total weight—40 pounds.



◀ **SPACE AIR SAMPLER**—Ionization gauges intended to sniff the thin atmosphere in near space and to measure its density have been designed and built by Westinghouse for the National Aeronautics and Space Administration. Tested in an Aerobee Hi Rocket launched from Wallops Island, Va., one of these gauges provided direct measurements of pressures and densities at altitudes from 70 to 125 miles up. Until this experimental flight, efforts to adapt high-sensitivity ionization gauges to space probes had met with little success due to problems of bulk and susceptibility to vibration. The new gauges can survive the high G's at blast-off while not taking up too much room in a rocket's limited pay load. They are expected to be useful in gathering atmospheric data all the way up to 450 miles.



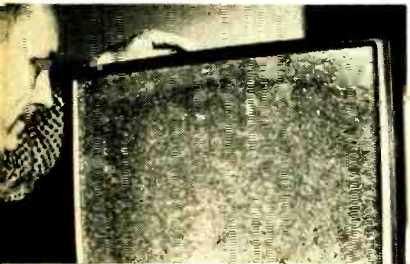◀ **SPACE CHIMP DIGS TECHNOLOGY**—Jerry, space-age research chimp for International Rectifier Corp., monkeys with one of the 20,000-volt rectifiers used in high-power radar missile warning systems and nuclear research. Jerry's main job is to assist scientists in studying the whole human physiological system in space and on earth.




UPI

◀ **IT'S A TOUGH BREAK** for Sam Castle, Jr., shown gazing at his mysteriously damaged television set. Awakened from sleep by a crackling sound he was afraid meant a fire in the house, Castle found that the noise actually came from the glass pane front of his TV set. With each "pop," new cracks appeared in the glass, until it began to look like an ice-frosted window. Thus far, no explanation is in the offing for this phenomenon, or for similar events involving car windshields which occurred a few years ago. Mr. Castle's big problem is whether he should call in a TV repairman or a glazier.

# BREAK THROUGH TO HIGHER PAY

# in ELECTRONICS

# TV-RADIO

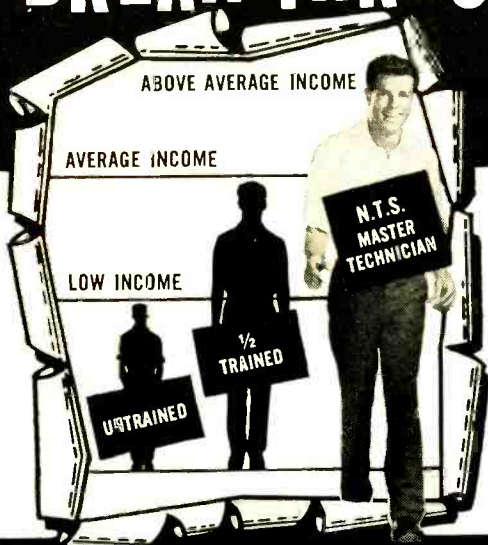

**START NOW!** Break through the Earning Barrier that stops half-trained men. N.T.S. "All-Phase" training prepares you — at home in spare time — for a high-paying CAREER in Electronics — TV — Radio as a **MASTER TECHNICIAN**. One Master Course at One Low Tuition trains you for unlimited opportunities in All Phases: *Servicing, Communications, Preparation F.C.C. License, Broadcasting, Manufacturing, Automation, Radar and Micro-Waves, Missile and Rocket Projects.*

A more rewarding job... a secure future... a richer, fuller life can be yours! As an **N.T.S. MASTER TECHNICIAN** you can go straight to the top in industry... or in your own profitable business.


You work on actual job projects



## SUCCEED IN MANY HIGH-PAYING JOBS LIKE THESE...

- TV-Radio Sales, Service and Repair
- Profitable Business of Your Own
- Communications Technician — F.C.C. License
- Hi-Fi, Stereo & Sound Recording Specialist
- TV-Radio Broadcasting Operator
- Technician in Computers & Missiles
- Electronics Field Engineer
- Specialist in Microwaves & Servomechanisms
- Expert Trouble Shooter
- All-Phase Master Technician

## 19 BIG KITS YOURS TO KEEP

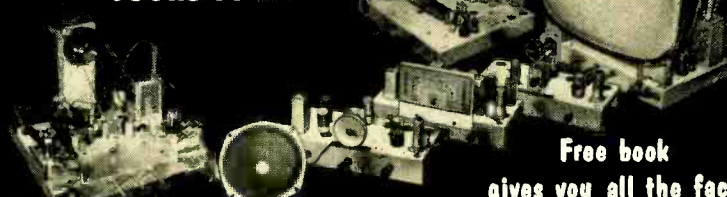

Free book gives you all the facts

## NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905

4000 SO. FIGUEROA ST., LOS ANGELES 37, CALIF., U. S. A.

Write Dept. R2G-61



N.T.S. Shop-Tested HOME TRAINING is **Better, More Complete, Lower Cost**... and it is your key to the most fascinating, opportunity-filled industry today!

### YOU LEARN QUICKLY AND EASILY THE N.T.S. SHOP-TESTED WAY

You get lessons, manuals, job projects, unlimited consultation, graduate advisory service.

You build a Short Wave-Long Wave Superhet Receiver, plus a large-screen TV set from the ground up, with parts we send you at no addi-

tional cost. You also get a Professional Multitester for your practical job projects.

### EARN AS YOU LEARN... WE SHOW YOU HOW!

Many students pay for entire tuition — and earn much more — with spare time work they perform while training. You can do the same... we show you how.

**SEND FOR INFORMATION NOW... TODAY! IT COSTS YOU NOTHING TO INVESTIGATE.**

### RESIDENT TRAINING AT LOS ANGELES

If you wish to take your training in our Resident School at Los Angeles, the world's TV capital, start NOW in our big, modern Shops, Labs, and Radio-TV Studios. Here you work with latest Electronic equipment — professionally installed — finest, most complete facilities offered by any school. Expert friendly instructors. Personal attention Graduate Employment Service. Help in finding home near school — and part time job while you learn.

WRITE FOR SPECIAL RESIDENT SCHOOL CATALOG AND INFORMATION



ACCREDITED MEMBER

... the only nationally recognized accrediting agency for private home study schools.

### N.T.S. HOME TRAINING is

- Classroom Developed
- Lab-Studio Planned
- Shop-Tested
- Industry-Approved
- Specifically Designed for Home Study

### ACTUAL LESSON



**MAIL COUPON NOW** for **FREE BOOK** and **ACTUAL LESSON**

**NO OBLIGATION! NO SALESMAN WILL CALL**

## NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905

Mail Now To National Technical Schools, Dept. R2G-61 4000 S. Figueroa St., Los Angeles 37, Calif.

Please rush **FREE** Electronics-TV-Radio "Opportunity" Book and Actual Lesson. No Salesman will call.

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

Check here if interested **ONLY** in Resident Training at Los Angeles.

**VETERANS:** Give date of discharge \_\_\_\_\_

TIME TO CLEAN UP  
YOUR SYSTEM...

# Norelco®

T-7 LOUDSPEAKERS  
with voice coil magnets of  
Ticonal-7 steel (30% more  
efficient\* than Alnico V)

\*... 30% more efficient  
response to the full signal range  
of your amplifier... **WHETHER  
ITS RATED OUTPUT is  
10 WATTS or a HUNDRED...**  
at any listening level from a  
whisper to a shout!

GUILD-CRAFTED BY PHILIPS OF  
THE NETHERLANDS TO GIVE YOU


## THE CLEANEST SOUND AROUND



Ask for a  
demonstration  
wherever  
good sound is  
sold or write to:

**NORTH  
AMERICAN  
PHILIPS  
CO., INC.**

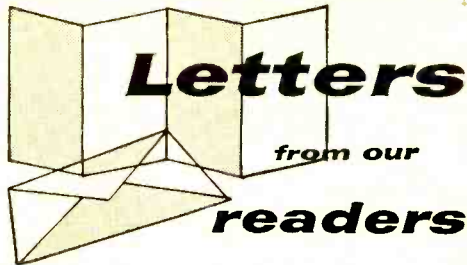High Fidelity Products Division,  
230 Duffy Avenue,  
Hicksville, L.I., N.Y.



### More "Sweet Sixteens"

■ I've just finished building the "Sweet Sixteen" speaker system which appeared in your January 1961 issue, and it was really worth the effort. The quality is outstanding for such a low-cost unit; highs as well as rich lows are reproduced wonderfully. I think I'll try another one for stereo.

MORRIS MADURO  
Panama, Rep. of Panama

■ I built a speaker system based on the one described in your January issue under the title "Sweet Sixteen." Instead of 16 speakers, I used 18—and built them into a cabinet already containing two 12" coaxial units. The resulting sound is equal to or far exceeds that of much more expensive installations. Some listeners prefer the added "boom" of the coaxial speakers, but more and more I am beginning to find that the small speakers alone provide the clear crisp tones which are such a pleasure to hear.

C. R. DAVENPORT  
Indianapolis, Ind.

*These are just a couple of the hundreds of letters that continue to pour in on the "Sweet Sixteen." We would also like to hear from readers who have added a tweeter to the original unit ("Sweeter with a Tweeter," April, 1961).*

### Audio Analgesia

■ I have some questions concerning the audio analgesia apparatus described by Charles Fowler in "The Noise That Banishes Pain" in the January



1961 issue. Any information you can give me will be appreciated.

- (1) Must the system be stereo?
- (2) Why does the author recommend Emory Cook records?
- (3) What is the source of the white noise?

(Continued on page 14)

Always say you saw it in—POPULAR ELECTRONICS

# AT LAST!

# RADIO-TV and ELECTRONICS TRAINING

## .... AT A PRICE YOU CAN AFFORD!



\*21 INCH Receiver Kit included

Yes, this great course costs far less than any training of its kind given by other major schools! Radio-Television Training School will train you for a good job in Television or Industrial Electronics — **AT HOME IN YOUR SPARE TIME.**

Think of it—a complete training program including over 120 lessons, Fourteen Big Radio-Television Kits, Complete Color-TV Instruction, Unlimited Consultation Service... **ALL at a really big saving to you.** How can we do this? Write to us today... and find out!

And what's more — you can (if you wish) **OPEN YOUR OWN RTS-APPROVED AND FINANCED RADIO-TV SERVICE SHOP**

**We Want Many More Shops This Year**

This 38 year old training organization — called RTS, that's Radio-Television Training School — wants to establish a string of Radio-TV Repair Shops in principal cities throughout the U. S. So far, a great many such shops are **NOW IN BUSINESS AND PROSPERING.** We are helping and training ambitious men to become future owners and operators of these shops in all areas.

**FOR UNSKILLED INEXPERIENCED MEN ONLY — WE TRAIN YOU OUR WAY!**

We must insist that the men we sign up be trained in Radio-TV Repair, Merchandising and Sales by our training methods—because **WE KNOW** the requirements of the industry. Therefore, we will **TRAIN YOU**... we will show you how to earn **EXTRA CASH**, during the first month or two of your training period. **YOU KEEP YOUR PRESENT JOB. TRAINING TAKES PLACE IN YOUR OWN HOME, IN YOUR SPARE TIME!**

**COMPLETE COLOR TV INSTRUCTION INCLUDED**

*you build these and other units*



**RADIO-TELEVISION TRAINING SCHOOL**  
815 EAST ROSECRANS AVENUE  
LOS ANGELES 59 CALIFORNIA

Est. 1922



**ACT NOW!**

**CUT OUT AND MAIL — TODAY!**

**RADIO-TELEVISION TRAINING SCHOOL**  
815 EAST ROSECRANS AVE Dept. PE-61  
LOS ANGELES 59 CALIFORNIA

**SEND ME FREE** — all of these big opportunity books — "Good Jobs in TV-Electronics," "A Repair Shop of Your Own" and "Sample Lesson." I am interested in:

Radio-Television       Industrial Electronics (Automation)

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City & State \_\_\_\_\_  
ZIP \_\_\_\_\_

**Mail This Coupon Now — No Salesman Will Call**

**RTS APPROVED SERVICE SHOP**

Get your free book on the **FAMOUS RTS BUSINESS PLAN** find out how you can open **A REPAIR SHOP OF YOUR OWN**

*We supply and finance your equipment*

When you are ready and qualified to operate one of our RTS-Approved TV Repair Shops **WE WILL SUPPLY AND FINANCE EVERY BIT OF EQUIPMENT YOU NEED TO GET STARTED** plus an inventory of parts and supplies. In other words we will stake you... **AN OFFER NEVER MADE BEFORE BY ANY TRAINING ORGANIZATION.** Under the RTS Business Plan you receive:

1. An electric sign for the shop front.
2. Complete laboratory of test equipment.
3. Letterheads, calling cards, repair tickets, etc.
4. Basic inventory of tubes, parts, supplies.
5. Complete advertising and promotional material.
6. Plans for shop arrangement.
7. Instructions on how to go into business.
8. Continuous consultation and help.
9. The right to use RTS Seal of Approval, and the RTS Crest.
10. The right to use the Famous Trade Mark.



**ALL THESE FREE!**

RTS' Membership in The Association of Home Study Schools is your assurance of Reliability, Integrity, and Quality of Training.



**MODEL 100**  
Available after June 15



**MODEL 10**  
Available after June 15

**MODEL 50**  
Available after April 15



**INTERNATIONAL'S**

*new*  
*series* **Executive**

**for SUPERIOR Citizens band communication**

**INTRODUCING THREE SYSTEM-ENGINEERED TRANSCEIVERS**

**MODEL 100**

The ultimate in Executive Citizens transceivers. NEW crystal filter which minimizes adjacent channel interference in the receiver. NEW built-in receiver calibration circuit. NEW International NR squelch. NEW 12 position crystal control transmit channel selector. NEW front panel microphone jack. NEW provision for connecting external speaker and S meter. Dual conversion superheterodyne receiver. Push-to-talk operation. Three way power supply for 6/12 vdc, 115 vac. Complete with 1 transmit crystal, 1 receive crystal, new style ceramic microphone and coil cord. . . . . **\$199.50\***

**MODEL 10**

International's exciting NEW Compact transceiver for the budget minded customer who desires quality workmanship and engineering plus the best possible circuit for the money invested. Field tested full 5 watt transmitter contained in the higher price Executives. Tunable superheterodyne receiver covering all 23 channels. Three position crystal control transmit channel selector. Manual transmit-receive control. Noise limiter. Available accessories include four separate power supplies — 6 vdc, 12 vdc, 24 vdc or 115 vac, push-to-talk relay kit, squelch kit, and 12 position transmit channel selector. Complete with 1 transmit crystal, matching microphone and external speaker, but less power supply. . . . . **\$59.50\***

**MODEL 50**

A precision engineered transceiver featuring push-to-talk operation. Three position crystal control transmit channel selector. Dual conversion superheterodyne receiver tuning all 23 channels. Series Gated automatic noise limiter. NEW International NR squelch. Three way power supply — 6/12 vdc, 115 vac. Additional features of Model 100 are available as accessories, and may be added at any time. Complete with 1 transmit crystal, matching microphone . . . . . **\$149.50\***

*\*Suggested Price*

**SEE THE EXECUTIVE SERIES AT YOUR AUTHORIZED INTERNATIONAL DEALER**



**INTERNATIONAL CRYSTAL MANUFACTURING CO., INC.**

18 NORTH LEE • OKLAHOMA CITY, OKLAHOMA

# Letters

(Continued from page 10)

- (4) Is it possible for the volume of the white noise in the 'phones to cause ear damage?
- (5) Would the system work as well if music were recorded on one channel of a stereo tape recorder and white sound on the other channel?

Since reading the article, I have rigged a turntable and FM tuner to play through separate amplifiers, using the tuner between stations to produce the white noise. I had to give supplementary local anesthetic to only two of the ten patients on whom I tried this apparatus.

R. S. DAVIDSON, D.D.S.  
Pikeville, Tenn.

We will attempt to answer your questions in the order in which you presented them.

(1) It is necessary to have a stereo system in order that the volume of the white sound and that of the music can be controlled separately. Ideally, the patient should adjust the white sound so that the volume is loud, but comfortable—then bring in the music to a barely audible level.

(2) The Emory Cook records were recommended because they are a very convenient stereo source—white sound on one channel, music on the other.

(3) White NOISE is made up of all the frequencies in the audible spectrum, each present at the same intensity; white SOUND is white noise

which has been "tailored" so that the intensity of each frequency is proportional to the sensitivity of the ear at the frequency.


(4) Ear damage is unlikely if the white sound volume is kept below the "uncomfortable" level.

(5) There's no reason why a stereo tape system wouldn't work, but for best results you should use white sound rather than white noise.

For further information, write to Cook Laboratories, Inc., 101 Second St., Stamford, Conn., and ask for their booklet entitled "Audio Analgesia." Include 25 cents to cover cost of handling and mailing.
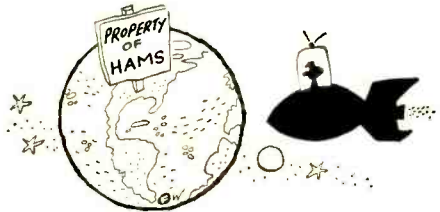
## "It's a Ham's World"


■ I found the article entitled "It's a Ham's World" (February 1961 issue) very interesting, particularly the listings of clubs conducting courses in amateur radio code and theory. In our organiza-



tion, the Taft Junior High School Radio Club (Oklahoma City, Okla.), we are currently studying code and plan to tackle theory soon.

I'd like to take this opportunity to recommend
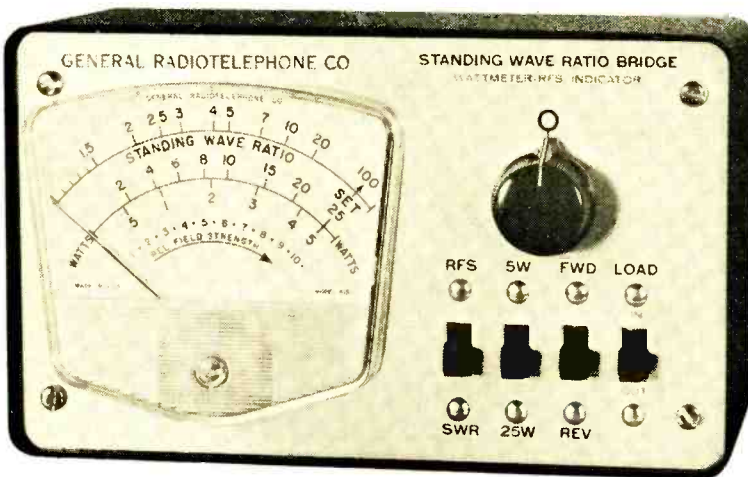
## Now for the first time—A single precision instrument that measures TRUE POWER • STANDING WAVE RATIO • RELATIVE FIELD STRENGTH



Your Dealer or Write:  
**GENERAL RADIOTELEPHONE COMPANY Dep't. P6**  
2806 West Burbank Blvd., Burbank, California, U.S.A.

### General Radiotelephone presents the new Model 615 Multi Function Bridge.

**Functions:** Direct readings of forward and reverse power for VSWR. Reads true power to 52 ohm load in two ranges of 5 and 25 watts. Shows relative field strength using telescoping antenna.

**Specifications:** Self contained 52 ohm, 30 watt, GLOBAR dummy load. Flat loading within 3db. to 50Mc. Meter 1 Mil. movement with 4 scales for all functions. Couplings are Silver plated SO-239 Coax connectors. Unit may be left in line during operation at all times. Accurate transmitter adjustments and continuous monitoring of power.

**Ranges:** VSWR- 27 to 54Mc. Scaled 0 to 100 with Calibrate -Set mark. Watts- Two separate scales for 5 and 25 watts.

**RFS- Relative Field Strength Meter** Calibrated 0 to 10 with sensitivity control.

**Mechanical:** Size-7"W x 4 1/8"H x 3 3/4"D. WT-4 lbs. Shpg Wt. 6 lbs. Cabinet-Black wrinkle finish. Panel-Gold anodized solid aluminum. Controls-4 Slide-switch functions and one Rotary Control. Warranted for 90 days against defects. FOB Burbank. Net Price - \$39.95. Adapter Cable for connecting SO-239 and Motorola Type Plugs: \$1.95 each.





# Are You Interested In Electronics - TV - Radio?

CARL E. SMITH  
E. E., President

then you will want to know

## What IS The FCC?

It's amazing what the future holds for you in this modern world of electronics. Let me send you the entire story—FREE!

- How to pass the FCC Exam
- Successful Electronic Training

I can train you to pass the Valuable FCC exam in a minimum of time if you have any practical experience and a fair knowledge of mathematics.  
CARL E. SMITH, E.E., President

**Get  
All 3  
FREE**



**GET THIS HANDY POCKET  
ELECTRONICS DATA GUIDE**

**Free...**

Puts all the commonly used conversion factors, formulas, tables, and color codes at your fingertips. Yours absolutely free if you mail the coupon today. No further obligation!

**TO GET THIS FREE GIFT, MAIL COUPON TODAY!**

## Not For Beginners

Please inquire only if you really want to get ahead and to add to what you have already learned in school, in the service, or on the job. Some previous schooling or experience in electronics, electricity, or related fields is necessary for success in Cleveland Institute programs.

**Cleveland Institute of Electronics**

1776 E. 17th St. Desk PE-78 Cleveland 14, Ohio

June, 1961

**Investigate Our  
NEW  
Training Program  
in Computers,  
Servo-Mechanisms,  
Magnetic Amplifiers,  
and Others**

## Your FCC Commercial License —or Your Money Back

Completion of the Master Course (both Sections) will prepare you for a First Class Commercial Radio Telephone License with a Radar Endorsement. Should you fail to pass the FCC examination for this license after successfully completing the Master Course, you will receive a full refund of all tuition payments. This guarantee is valid for the entire period of your enrollment agreement.

**Cleveland Institute of Electronics**

1776 E. 17th St. Desk PE-78 Cleveland 14, Ohio

Accredited by the

National Home Study Council



Please send Free Career Information Material prepared to help me get ahead in Electronics and a free copy of your "Pocket Electronics Data Guide." I have had training or experience in Electronics as indicated below.

- |   |   |
|---|---|
| <input type="checkbox"/> Military           | <input type="checkbox"/> Broadcasting       |
| <input type="checkbox"/> Radio-TV Servicing | <input type="checkbox"/> Home Experimenting |
| <input type="checkbox"/> Manufacturing      | <input type="checkbox"/> Telephone Company  |
| <input type="checkbox"/> Amateur Radio      | <input type="checkbox"/> Other: _____       |

In what kind of work are you now engaged? \_\_\_\_\_  
In what branch of Electronics are you interested? \_\_\_\_\_

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

PE-78

fastest, easiest way  
to learn math  
**BASIC MATHEMATICS**

(A PICTURED-TEXT COURSE)  
by Norman H. Crowhurst

*New approach and pictorial technique makes it easier than ever before possible to learn all the math you need to get ahead.*

This remarkable 4-volume course takes you in easy stages from counting through algebra, geometry, trigonometry to calculus so that you will understand easily, quickly, all the math you will need to get ahead—regardless of your previous education! It employs an exciting new technique wherein basic mathematics is presented as one continuous development of mathematics. The individual branches of mathematics are not divided into separate and unrelated subjects. Algebra, geometry, trigonometry, calculus are interwoven at progressively rising levels in the different volumes. Each volume reinforces your understanding as you penetrate more deeply into the subjects. Selected illustrations create clear images of mathematical ideas formerly difficult to understand or imagine through words alone.

**NOW AVAILABLE VOLUME I—FIRST STEP TOWARD MASTERY OF MATHEMATICS**—In Volume I you gain the self-confidence you need to master mathematics! You build a solid foundation in mathematics without realizing that you are being introduced to subjects usually considered dry and difficult-to-master. You learn addition, subtraction, multiplication, division, taking of roots, decimals, areas, angles, distance/time, rate of growth, ratios, percentages, etc. All subjects follow one another so easily that learning is 'painless'. Imagine a dedicated teacher sitting next to you and very patiently and painstakingly explaining step by step the processes of mathematics in each subject area... This is Basic Mathematics.

**WHY A KNOWLEDGE OF MATH SPEEDS YOUR PROGRESS IN ELECTRONICS**—No matter what your plans are in electronics—mathematics plays a vital role. The more math you know, the easier it is to learn electronics. And, if you've set your sights on being an advanced technician or an engineer, you must have a firm foundation in mathematics to achieve your goal. This course will speed you towards your goal.

**4 VOLUMES TAKE YOU FROM COUNTING TO CALCULUS—**

**NOW AVAILABLE**

VOL. I—Arithmetic as An Outgrowth of Learning to Count #268-1, \$3.90. VOL. II—Introducing Algebra, Geometry, Trigonometry, Calculus as Ways of Thinking in Mathematics #268-2, \$3.90.

**AVAILABLE IN LATE 1961**

VOL. III—Developing Algebra, Geometry, Trigonometry, Calculus, as Working Methods in Mathematics VOL. IV—Developing Algebra, Geometry, Trigonometry, Calculus as Analytical Methods in Mathematics.

At book stores, parts distributors, or direct.

No matter where you buy these books, we guarantee satisfaction or your money back within 30 days.



**JOHN F. RIDER PUBLISHER INC.**  
116 West 14th Street, New York 11, N. Y.  
Canada: Chas. W. Pointon, Ltd., 66 Racine Rd., Rexdale, Ont.  
Export: Acme Code Company, Inc., 630 9th Ave., N. Y.

## Letters

(Continued from page 14)

another manual for the would-be novice: "Steps to a Ham License," published by American Basic Science Club, Inc., 501 E. Crockett St., San Antonio 6, Texas. Copies are 50 cents each.

DAVID GEESEKA  
Oklahoma City, Okla.

### Help Wanted

■ I would like to get some information on the Masterpiece VI, a short-wave receiver manufactured by the McMurdo-Silver Corporation of Chicago—which went out of business about 1939 or 1940. If any of the P.E. readers can help me, I would appreciate hearing from them.

STEPHEN A. LABAN, WPE2DXH  
2676 Grand Concourse  
New York 58, N. Y.

■ If any of your readers have circuit data on the Breting 45 receiver and would lend it to me, I would be very grateful and would return it promptly.

STEPHEN T. BEMIS  
16 Williams St.  
West Medway, Mass.

### "Dirty" DX

■ I've just read "How to Get DX" by Fred E. Ebel, WOPXA, in the August issue, and I think that using a YL to make contacts is the dirtiest trick one amateur can play on another. I don't



know if there is any law against this in the States but there is in Canada.

The following is a quotation from "The Radio Amateur Licensing Handbook (Canada)" by Jim Ketchin, Regional Supervising Radio Inspector, Department of Transport, Canada. "Any person without a Certificate of Proficiency may take part in radiotelephone transmissions provided the licensee retains physical control of the equipment and does the calling and signing off."

I think that if an amateur can't raise DX by himself he shouldn't use trickery to do so.

RICHARD DILLEY  
Pointe Claire, Quebec, Canada

*We're sorry you are so upset, Richard, but we meant it all in fun. As for violating the FCC Regulations, here in the U. S. anyone can transmit a message provided "a duly licensed amateur operator maintains actual control over the emissions, including turning the carrier on and off for each transmission and signing the station off after communication with each station has been completed."*

-30-



## snap!

Recall when sound . . . almost any sound . . . was fun? Pure, clear, fresh sounds are part of the fountain of memory.

Nothing can ever equal that first awareness of rain on a window, or a distant train whistle, or the silence of falling snow.

But there are some special delights reserved for adult ears. Audiotape, for example.

Audiotape gives you greater clarity and range, less distortion and background noise. Make it your silent (but knowledgeable) partner in capturing memorable moments in sound

. . . from junior's nonstop chatter . . . to the spirit-soothing music of Schubert.

Remember: if it's worth recording, it's worth Audiotape. There are eight types . . . one exactly suited to the next recording you make.



**audiotape**  
TRADE MARK

*"it speaks for itself"*

**AUDIO DEVICES, INC.**, 444 Madison Ave., N. Y. 22, N. Y.  
Hollywood, 840 N. Fairfax Ave., Chicago: 5428 N. Milwaukee Ave.

RESIDENT SCHOOL COURSES IN  
LOS ANGELES AND NEW YORK CITY

# START YOUR CAREER IN ELECTRONICS NOW AT RCA INSTITUTES... Choose from this list

	Course	Qualifications	Length of Course
A	Advanced Electronic Technology (T-3)	High School grad, with Algebra, Physics or Science	Day 2¼ yrs. Eve. 6¾ yrs. (N.Y.) 4½ yrs. (L.A.)
B	Television and General Electronics (V-7)	2 yrs. High School, with Algebra, Physics or Science	Day 1½ yrs. Eve. 4½ yrs. (N.Y.) 3 yrs. (L.A.)
C	Radio and Television Servicing (V-3)	2 yrs. High School, with Algebra, Physics or Science	Day 9 mos. Eve. 2¼ yrs. (N.Y.) 1½ yrs. (L.A.)
D	Transistors	Radio background	Eve. 3 mos.
E	Electronic Drafting (V-11 V-12)	2 yrs. High School, with Algebra, Physics or Science	Eve. Basic: 1 yr. Advanced: 2 yrs.
F	Color Television	Television background	Eve. 3 mos.
G	Audio-Hi Fidelity	Radio background	Eve. 3 mos.
H	Computer Programming (C-1)	College Graduate or Industry sponsored.	Eve. 24 weeks
I	Technical Writing (V-10)	High School Graduate	Eve. 2¼ yrs. (N.Y.) 1½ yrs. (L.A.)
J	TV Studio Production (S-1)	High School Graduate	Day 15 weeks Eve. 45 weeks
K	Digital Computers	Electronics background	Eve. 3 mos. (L.A.)
L	Preparatory Math & Physics (P-0)	1 yr. High School	Day 3 mos.
M	Preparatory Mathematics (P-0A)	1 yr. High School	Eve. 3 mos.
N	Home Study Courses	Choose from: Radio and Electronic Fundamentals, TV Servicing, Color TV, Transistors, and Automation Courses. Catalog free on request.	

RCA Institutes is one of the largest technical institutes in the United States devoted exclusively to electronics. Free Placement Service. Applications now being accepted for next term classes in Los Angeles and New York.



The Most Trusted Name  
in Electronics  
RADIO CORPORATION OF AMERICA



Send to the school nearest you!

RCA Institutes, Inc., Dept. PER-61

Pacific Electric Building 350 West Fourth Street  
610 S. Main St., L.A. 14, Calif. New York 14, N. Y.

Please send me your FREE catalog. I am interested in the courses circled below.

A B C D E F G H I J K L M N

Name \_\_\_\_\_ (please print)

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

For Home Study Courses See Ad On Opposite Page

# Hi-Fi



## Showcase

A quick look at  
new products in the  
stereo/hi-fi field\*

IN CASE you're thinking of adding a tape deck or deck/preamp combination to your hi-fi system, the new "Series 500" units from *American Concertone* should fill the bill admirably—every member of the series is intended for professional and studio use. The basic transport (Model M-506) is furnished with three fully shielded heads (it has space for a fourth) and three hysteresis motors. Produced in speeds of 3¾-7½ ips and 7½-15 ips, the transport sells for \$349.50; the Model M-508 is equipped with a monaural preamp and sells for \$520; and the Model M-507, priced at \$645, includes stereo preamps. . . . From *Allied Radio* comes a stereo tape record/play preamp kit suitable for use with any quality 3-head tape deck. Although erase and record bias voltages are preset to match Allied's new KN-4000 stereo tape deck, both are adjustable to match heads on other quality transports. The Knight-Kit preamp permits stereo and monophonic recording and playback as well as "echo chamber," "sound-on-sound," and other special effects. Twin VU meters indicate recording and playback levels, and a 3¾-7½ ips equalization switch functions in both record and playback. Price of the 83 YX 929 kit is \$79.95; factory-assembled unit (KN-4001) sells for \$129.95.

Another new product from Allied is the Knight KN-850 12" hi-fi speaker. A 3-way unit built in England to Allied's specifications, the KN-850 has a mechanical crossover at 2000 cycles, an electrical crossover at 5000 cycles, and an L-pad for precise adjustment of the high-frequency level to suit your taste. The 12" model sells for \$79.50; a 15" version, the KN-815A, is priced at \$89.95. . . . From *Burgess Battery* comes a product that has been over five years in the

\*Write to the manufacturers listed at the end of this column for more data on products mentioned

Always say you saw it in—POPULAR ELECTRONICS




# LET RCA TRAIN YOU IN ELECTRONICS

RCA Institutes, one of the world's leading electronic technical schools, offers Home Study Courses in . . .
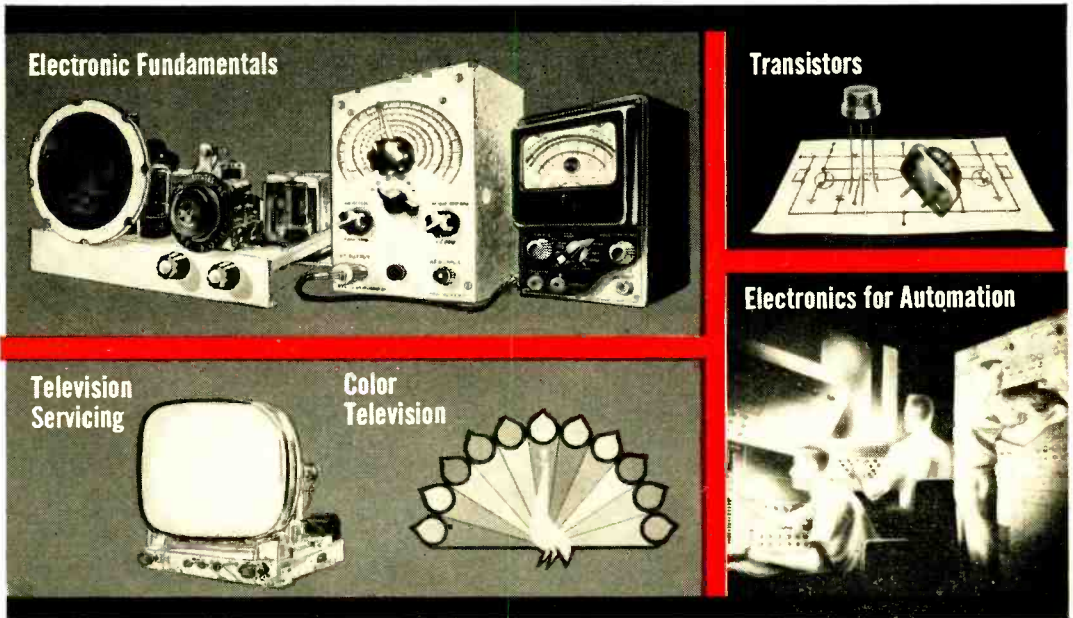
## RADIO, TV, TRANSISTORS, AUTOMATION

. . . Now you have five comprehensive courses for your electronic training. Practical work with the very first lesson. With the new Voluntary Tuition Plan, you pay for each study group only when you order it. If you interrupt the course at any time, for any reason, you don't pay until you resume the course.

Even if you have not completed high school, you can begin your electronic career training at RCA Institutes. Choose from any of these courses. .



Send for our 64 page Home Study Catalog

**FREE!**

RESIDENT SCHOOLS in New York City and Los Angeles offer Technical Institute and Vocational School Courses in Electronics. Day and Evening classes start 4 times each year. Resident School Catalog sent free on request.



### RCA INSTITUTES, Inc. Home Study School, Dept. PE-61

A Service of Radio Corporation of America

350 West Fourth Street, New York 14, N. Y.

Please rush me your FREE illustrated 64-page book "Your Career in Electronics," describing your home training programs. No obligation. No salesman will call.

Name  Age

Address

City  Zone  State

Veterans: Enter discharge date

**CANADIANS** — Take advantage of these same RCA courses at no additional cost. No postage, no customs, no delay. Send coupon to:

RCA Victor Company, Ltd., 5581 Royalmount Ave., Montreal 9, Quebec

To save time, paste coupon on postcard.

FOR RESIDENT SCHOOL COURSES SEE AD ON OPPOSITE PAGE

## Showcase

(Continued from page 18)

making—high-quality recording tape. With the stress on tape uniformity, Burgess uses a special iron oxide powder and acetate or Mylar base to produce a tape with a micro-finished surface. In addition, a lubricant built into the coating is said to last the life of the tape, minimizing flake-off and keeping heads clean. Prices vary with reel size and tape thickness.


Two integrated stereo amplifiers are available from **EICO** in either kit or factory-wired form. Built to handle virtually any stereo program source—FM/AM; multiplex; tape heads; magnetic, crystal, or ceramic cartridges—both amplifiers include a variety of controls. The ST40 develops 20 watts per channel and is priced at \$79.95 in kit form, \$124.50 fully wired. The ST70 contains dual 35-watt amplifiers as well as a speaker phase-reversal switch, and sells for \$94.95 in kit form, \$144.95 factory-wired. . . . A fully integrated

FM/AM tuner and stereo amplifier/pre-amplifier combination from **Fisher** follows the same general lines as the company's more expensive 600 and 800 stereo receivers. There's plenty of power in the 500-S's 45-watt stereo amplifier, and there are 13 inputs and 5 outputs on the rear panel, including a center-channel output for a composite stereo signal. Needing only a pair of speakers and a tape head or phono cartridge to form a complete stereo setup, the 500-S is priced at \$349.50. . . . New from **Harman-Kardon** are a 50-watt stereo preamplifier/amplifier and an FM tuner, two companion pieces designed for custom installations. Features of the A500 amplifier include a front-panel ambiance control for regulating volume of a third-channel amplifier or reverberation device; blend control indicator lamps to show the exact degree of blend; and a tape monitor switch which permits monitoring tape while recording. On the F500 tuner, controls include an FM/multiplex switch with indicator lights, an inter-channel muting defeat switch, and a local/long-distance range switch. Both

# NEW ANTENNAS
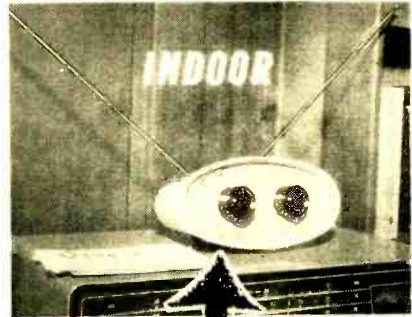
## Short Wave Listening

Amazing new indoor short wave antenna system reaches out for those far away signals and greatly increases the performance of any short wave receiver. Covers frequencies from 5 through 30 megacycles including all the important short wave and amateur bands . . . Easy to operate—simply attach cable (6 foot furnished) to receiver, extend telescoping ears and adjust "match" and "tune" controls for maximum signal strength. Attractively housed in unbreakable modernistic plastic case with chrome plated antennas. Completely factory wired.



MODEL SW1

Price \$14<sup>75</sup>

Peaked for  
11-13-16  
19-24-31  
40m

### OUTDOOR

### HIGH EFFICIENCY


High efficiency outdoor antenna. Only 40 feet long. Mounts quickly and easily under eaves, in attic space, etc. Peaked for top performance on the important short wave bands with 8 trap assemblies. Complete kit includes 100 feet of lead in cable.

MODEL SWO

**hy-gain**  
antenna products

1135 No. 22nd St.

Lincoln, Nebr.

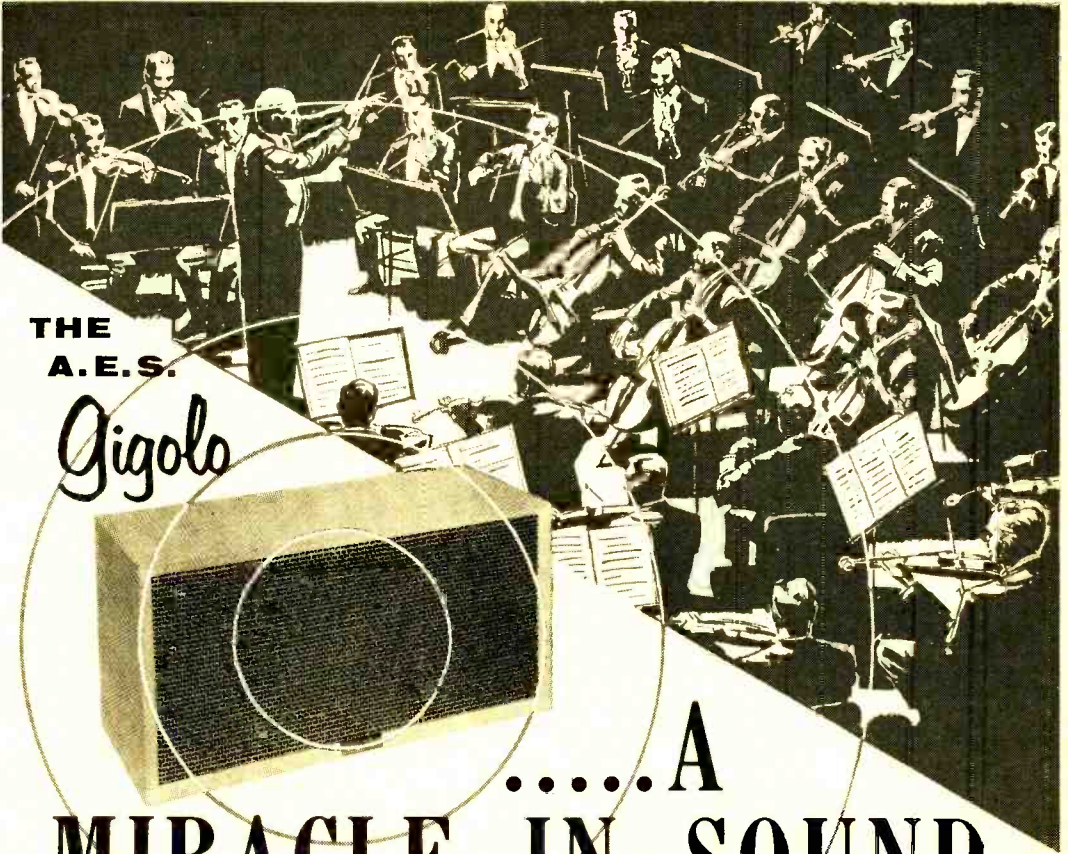

**THE  
A. E. S.**

*Gigolo*

.....A  
**MIRACLE IN SOUND**


After two years of research and development, a speaker system we can offer to the public on a 100% MONEY BACK GUARANTEE. Compare the A. E. S. Gigolo, to any bookshelf speaker, regardless of price and if you do not feel that the Gigolo is the most outstanding unit you have heard, you may return it for a full purchase price refund.

Thousands of these gigolos are now in use all over the country. The acceptance has been unbelievable. Never before a sound so realistic to so many people in so many different homes! These are the facts that enable A.E.S. to make this bold offer.

Size —  
24" wide, 12" high, 9½" deep.  
Power Handling Capacity —  
The Gigolo is extremely flexible. May be used with small economy amplifiers of very low wattage, as well as with the highest power component amplifiers with satisfactory results.

Frequency Response —  
The Gigolo will reproduce both high and low frequencies in excess of the requirements of even the most critical home listener.

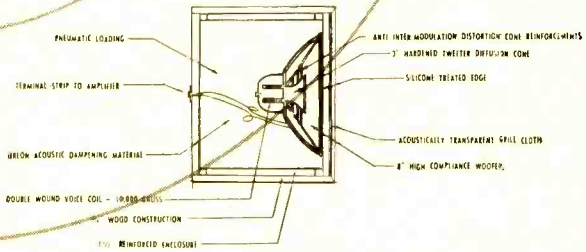Order now to insure prompt delivery  
Price — \$15.00, F.O.B. factory  
Unfinished only  
Price subject to change within thirty days of the issuance of this magazine



**ORDER BLANK**

A.E.S., Inc.  
3338 Payne Avenue, Cleveland, Ohio

Gentlemen please ship ..... GIGOLOS.

I understand these units are guaranteed and if I am not satisfied I may return for a full refund of sales price, \$15.00 each.

Name .....

Address .....

City and State .....

Enclosed find check ..... money order .....

# EARN \$10,000 A YEAR

- DIESEL       ELECTRONICS  
 AUTO         AUTOMATION

The average starting salary of students, completing our FCC License, Electronics Technician Course, and those completing our Diesel Automotive Training, is \$4,300 per year.

After becoming familiar with the industry, their salary usually increases to \$6,000 or \$7,000 per year.

After they become senior technicians, or master mechanics, they can earn \$8,000 to \$10,000 per year.

When they become specialists, or a part of management . . . or start their own business . . . they can earn considerably more.

**RESIDENT SHOP TRAINING** is easier and costs less than you may think! We provide you with housing and part-time jobs while in school, plus free nation-wide placement service for graduates.

Check subject above in which you are interested and mail for

◀ **FREE BOOKLET** ▶

Your Future  
IN  
ELECTRONICS  
AND  
AUTOMATION

## BAILEY

### Technical Schools

Veteran Approved  
1626 S. Grand, Rm. 28, St. Louis 4, Mo.

Your Future  
in  
DIESEL and  
AUTO  
MECHANICS

Name \_\_\_\_\_ Age \_\_\_\_\_  
 Street \_\_\_\_\_  
 Town \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

## TV PICTURE TUBES AT LOWEST PRICES

### ALL ALUMINIZED GLASS TYPES

Tube Type	Price With Old Tube	Tube Type	Price With Old Tube	Tube Type	Price With Old Tube
10BP4	7.95	17B1P4	11.50	21CEP4	21.00
12LP4	8.95	17CDP4	11.50	21CX4	15.75
14A1P4	14.00	17CK/CA/BZ/		21DEP4	21.00
14ATP4	14.00	BRP4	17.00	21DFP4	21.00
14B/E/CP4	10.00	17DLP4	17.00	21DLP4	21.00
14HP4	11.00	17H/RP4	12.50	21DSP4	21.00
14QP4	11.00	17L/VP4	12.50	21EP4	14.25
14RP4	11.00	17OP4	11.50	21FP4	14.50
14W/ZP4	11.00	20C/DP4	13.50	21WP4	16.00
14XP4	11.60	20H/MP4	14.50	21XP4	16.50
16DP4	12.00	21AC/BS/AMP4	14.50	21YP4	16.00
16K/RP4	9.95		15.75	21ZP4	15.50
16LP4	12.50	21AL/ATP4	16.75	24C/VP4	23.50
16TP4	9.95	21AU/AVP4	15.75	24AEP4	24.50
16WP4	12.00	21AWP4	15.75	24AHP4	26.50
17AT/AVP4	12.50	21BTP4	16.75	24DP4	24.50
17BP4	9.95	21CBP4	16.75	27EP4	39.95
				27RP4	39.95
				27SP4	40.95

### METAL TYPES

12UP4	12.00	16GP4	14.50	19AP4	16.00
16AP4	13.50	17CP4	17.00	21AP4	19.75
16EP4	14.00	17GP4	17.60	21MP4	20.75
		17TP4	17.60		

### TEST TUBES

8XP4	16.07	8YP4	16.07
------	-------	------	-------

### 1 year warranty

Prices include the return of an acceptable similar tube under vacuum. These tubes are manufactured from reprocessed used glass bulbs. All parts and materials including the electron gun are brand new.

**ALL PRICES FOB CHICAGO, ILLINOIS.** Deposit required, when old tube is not returned, refundable at time of return. 25% deposit required on COD shipments. Old tubes must be returned prepaid. Tubes shipped Rail Express. Shipped only to Continental U.S. and Canada.

### WRITE FOR COMPLETE LIST

**—PICTURE TUBE OUTLET—**  
**2922 MILWAUKEE AVE., CHICAGO 18, ILLINOIS**  
**Dickens 2-2948**

## Showcase

(Continued from page 20)

units measure 5 7/16" x 15 1/4" x 12", excluding knobs; prices are \$159.95 and \$129.95, respectively.

An inexpensive, wide-range speaker system ideal for use as part of a stereo pair, **Jensen's Model TF-3** is a four-speaker, three-way unit incorporating a 10" woofer, two special mid-range speakers, and a single tweeter. Prices are \$99.50 (oiled walnut) and \$79.50 (unfinished gum hardwood). . . . A lightweight version of the **Norelco "Continental"** tape recorder is a monaural record/stereo playback unit specially designed for hi-fi. Operating at 7 1/2 ips only, the "Continental" 200 (Model EL3541) incorporates a narrow-gap 4-track record/playback head for playing back 4-track stereo tapes through an external hi-fi system or for recording and playing back 4-track monaural tapes. Furnished complete with microphone, the "200" also includes an output jack for monitoring purposes. The unit operates from any 117-volt a.c. source and is priced at \$179.50.

A compact stereo preamp/amplifier/receiver combination measuring 16 1/4" x 14" x 4 1/2", **Sherwood's S-7000** requires only the addition of speakers and a record changer to form a complete home stereo music system. With 19 front-panel controls and 9 inputs for maximum flexibility, the S-7000 incorporates an AM/FM receiver, two preamps, and two amplifiers delivering 24 watts per channel. As a bonus feature, two cathode-follower outputs and a front-panel tape monitoring switch equip the unit for stereo tape-recording setups. Price is \$299.50; \$307.00 in brown leatherette case.

*American Concertone, Inc., 9449 W. Jefferson Blvd., Culver City, Calif.*  
*Allied Radio Corp., 100 N. Western Ave., Chicago 80, Ill.*  
*Burgess Battery Co., Div. of Servel, Inc., Freeport, Ill.*  
*Electronic Instrument Co., Inc. (EICO), 33-00 Northern Blvd., Long Island City 1, N. Y.*  
*Fisher Radio Corp., 21-21 44th Drive, Long Island City 1, N. Y.*  
*Harman-Kardon, 520 Main St., Westbury, N. Y.*  
*Jensen Manufacturing Co., 6601 S. Laramie Ave., Chicago 38, Ill.*  
*North American Philips Co., Inc. (Norelco), High Fidelity Products Div., 230 Duffy Ave., Hicksville, L. I., N. Y.*  
*Sherwood Electronic Laboratories, Inc., 4309 N. California Ave., Chicago 18, Ill.*

Always say you saw it in—POPULAR ELECTRONICS



# LAFAYETTE is America's Citizens Band Headquarters

Complete Portable Communications for Everyone



Ship to Shore



On the Farm



Construction Work

NO LICENSES, TESTS OR AGE LIMITS


HE-29



LAFAYETTE  
**9** TRANSISTOR  
CITIZENS  
BAND  
"WALKIE TALKIE"

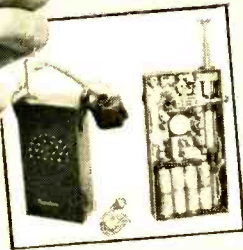**49.95**  
2.00 Down  
**2 for 96<sup>50</sup>**

PORTABLE—  
POCKET SIZE  
Only  
6 3/4 x 3 1/4 x 1 5/8"



- Completely Wired—Ready to Operate
- Fully Transistorized—9 Transistors plus 1 Diode
- Uses Inexpensive Penlight Batteries
- No License, Tests or Age Limits
- Comes with Leather Carrying Case, Earphone, Antenna, Batteries and Crystals

As simple and easy to use as the telephone—and twice as handy. Receives and transmits up to 7 miles under favorable conditions, or 1.5 miles under average conditions. Weighs only 18-oz. and slips into your pocket. Push-to-talk button operates built-in speaker as sensitive microphone.

LAFAYETTE HE-20A  
DELUXE  
Citizens Band  
TRANSCEIVER

**109<sup>50</sup>** 5.00 Down

Now With Added Deluxe Features—

- Pi-Network for Greater Power Output
- Calibrated "S" Meter
- 14 Tube Performance, 3 Diodes
- Built-in 12 Volt Power Supply for Mobile Use
- Complete with Matched Crystals for Channel 9
- Highly efficient 2-way communications system operating over a distance of up to 20 miles or more depending on terrain. Features



Made in U.S.A.

4 crystal-controlled transmit positions and 4 crystal-controlled receive positions. Tuneable superhet receiver covers all 23 assigned channels. Other highlights include dependable ceramic mike & relay, adjustable squelch control, automatic series gate noise limiter and illuminated dial.

LAFAYETTE HE-15A

Made in U.S.A.



ONLY  
**57<sup>50</sup>**  
5.00 Down

SUPERHET

CITIZENS BAND TRANSCEIVER

NOT A KIT

- Completely Wired—Not A Kit
- 5 Crystal-Controlled Transmitting Positions
- Tuneable Receiver Over Full 23 Channels
- High Output Crystal Microphone
- Complete with Transmitting Crystal for Channel 9

A compact, precision transmitter and receiver covering up to a 20 mile or more radius, depending upon conditions. The HE-15A features an effective full-wave variable noise limiter, RF jack on front panel, planetary vernier tuning, 5-prong microphone jack for easy relay addition, and 12 tube performance from 4 dual-function tubes, 2 single-function tubes, 2 rectifiers.

- HE-19 Telescoping Whip Antenna ..... Net 3.95
- HE-16 Power Supply for 12 Volts ..... Net 10.95
- HE-18 Power Supply for 6 Volts ..... Net 10.95

LAFAYETTE All-in-One  
CITIZENS BAND  
MOBILE ANTENNA

HE-800WX  
**6.95**

- Chrome Swivel Base
- Stainless Steel Spring
- 102 1/2" Stainless Steel Whip for Optimum 11-Meter Performance

Chrome swivel ball mount base designed for mounting on any surface. Stainless steel spring holds rod in properly adjusted position and prevents rod damage from shocks and blows. Stainless steel whip for maximum resiliency and strength.



NEW! LAFAYETTE  
RADIO FIELD INDICATOR

TM-14  
**6.95**

- Continuously Indicates Transmitter Output
  - Rugged 200 u Meter Movement
  - Requires No Electricity, Batteries or Transmitter Connection
- Check the performance of marine, mobile or fixed transmitter. Features a 200 u meter movement with variable sensitivity control. Earphones can be plugged in for an aural check of output. Antenna extends from 3 1/4" to 10 3/4". Magnet on bottom plate allows easy mounting on car dash or metal surfaces. Size, less antenna, 3 3/8 W, 2 1/4 H, 2" D.



**LAFAYETTE**  
RADIO

PLEASE INCLUDE SHIPPING CHARGES WITH ORDER

165-08 LIBERTY AVENUE, JAMAICA 33, N. Y. • OTHER LOCATIONS:

NEW YORK, N. Y.  
100 6th Avenue

NEWARK, N. J.  
24 Central Avenue

BRONX, N. Y.  
542 E. Fordham Rd.

PARAMUS, N. J.  
182 Route 17

BOSTON, MASS.  
110 Federal Street

PLAINFIELD, N. J.  
139 W. 2nd Street

# PURCHASING A HI-FI SYSTEM?

TIME PAYMENTS AVAILABLE  
Up to 2 Years to Pay!

Send Us  
Your List of  
Components  
For A Package  
Quotation

YOU CAN BUY WITH  
CONFIDENCE AT AIREX

All merchandise is brand new,  
factory fresh and guaranteed.

Free Hi-Fi Catalog

## AIREX RADIO CORPORATION

85-PE Cortlandt St., N. Y. 7


WO 4-1820

Jim Lansing\*  
Altec Lansing  
Electrovoice  
Jensen • Hartley\*  
University • Viking  
Acoustic Research  
Janszen • Superscope  
Wharfedale  
USL Citizen Band  
Gonset • Hollicrafter  
Texas Crystals  
Concertone  
Bell • G.E.  
Weathers  
Harman-Kardon  
Eico • Pilot • Fisher  
ESL • Roberts  
Bogen • Leak • TEC  
Dynakit • M. H. Scott  
Thorens\* • Sherwood\*  
Dual Changer  
DeWald  
Sony • Challenger  
Wollensak • Pentron  
Garrard • Quad\*  
Mirocord • Pickering  
Glaser-Steers  
Components  
Rek-O-Kut • Tandberg\*  
Audio Tape • Conrac  
Norelco • Magnecord\*  
Fairchild • Gray  
Artizan Cabinets  
Rockford Cabinets  
\*Fmr Traded

# POP'tronics Bookshelf
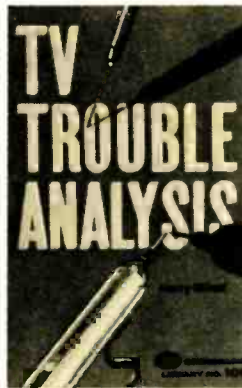
## TV TROUBLE ANALYSIS by Harry Mileaf

This book is intended to help the TV technician cut down his servicing time



and increase his ability to pinpoint troubles on unfamiliar sets. After giving the reader a brief refresher course on current TV theory, the author explains the "theory of trouble": the reasons for component and circuit failure are analyzed, and these failures are discussed in terms of

their effects on key waveforms and on the sound and picture of the receiver itself.

Published by Gernsback Library, Inc.,  
154 W. 14th St., New York 11, N. Y.  
224 pages. Soft cover, \$3.20. Hard cover, \$4.95.



## ALTERNATING CURRENT ELECTRICITY by Alexander Efron, E.E., Ph.D.

Volume 10 in the Rider Basic Science Series, this book contains a complete treatment of alternating current theory. Techniques for generating alternating electromotive force are covered first, and concepts of the sine wave, cycle, frequency and period are carefully developed. Resistance, capacitance, and inductance—the components of a.c. circuits—are discussed next. The vector diagram approach is used, emphasizing the geometrical nature of the relationships. Chapters on a.c. measuring equipment, polyphase power, the transformer, a.c. motors and rectification complete the text, and an appendix is devoted to the "j" operator and complex numbers. Prob-



LEADS AGAIN WITH  
CITIZENS "RADIO-PHONE"  
BAND TR-910 TRANSCEIVER



Amazing at only

# 99.95

LIST

- Push-to-talk with foolproof relay
- Full Squerech control
- Built-in "S" and Plate current meter
- 5 channel Transmit
- 22 channel Vernier controlled receive
- Automatic noise limiter

Furnished with Ceramic Microphone and one Transmitting Crystal

Write for Brochure and Name of Your Nearest Dealer

UNITED SCIENTIFIC LABORATORIES, INC.

35-09 37th AVE., LONG ISLAND CITY 1, N. Y.

Also Mfr's of DeWald Hi-Fi Stereo Components and FM Radio

**For serious-minded men desiring higher income and status-**

CREI has developed a program of home study that is comparable in technological content to advanced residence courses in electronics. The program was developed hand-in-hand with leading companies and Government agencies contributing to the Nation's efforts in electronics, communications, missiles, and space exploration.

This CREI program in Electronics Engineering Technology may be completed in 2 to 4 years, depending on how much of your spare time you can devote to study. The courses are presented in easy-to-understand form. Our instructors will give you personal attention and assist you when you need help.

To qualify CREI graduates for advancement to key technical positions, CREI offers a complete program in electronics, including—

- Automation • Instrumentation • Industrial Electronics
- Aeronautical Electronics • Guided Missiles • Radar
- Servo-mechanisms • Computers • Astronautics • Telemetering • Communications • Electronics Manufacturing • Field Engineering • Nuclear Engineering

# A COLLEGE-LEVEL EXTENSION PROGRAM IN ELECTRONICS

There is a drastic need in the electronics industry for well-educated engineers and technical personnel. Although the great majority of students find ample opportunity for advancement with their present companies, CREI maintains a Placement Bureau to assist graduates and advanced students in finding more desirable positions. For many years, the demand for CREI graduates and advanced students has far exceeded the supply.

A few of the private companies and government agencies whose officials approve CREI for their own personnel:

- U. S. Navy (5,240 enrolled in extension program)
- Army, Air Force, Marine Corps, Coast Guard
- Columbia Broadcasting System
- National Broadcasting Company
- Federal Electric Corporation
- Florida Power & Light
- Pan American Airways
- United Airlines
- The Martin Company
- All America Cable & Radio
- Voice of America
- ... and many others

**QUALIFICATIONS FOR CREI.** You qualify if you have a high school diploma or equivalent, and if you have had basic electronic training and practical experience in electronics. Available to Veterans.

**CREI's Extension Division offers you a college-level home study program in electronics comparable in technological content to advanced residence courses.**

**Mail this coupon . . . today!**

**CAPITOL RADIO ENGINEERING INSTITUTE**

ECPD Accredited Technical Institute Curricula • Founded 1927  
 Dept. 1206-H, 3224 16th St., N.W., Washington 10, D.C.  
 England: CREI London, Granville House, 132-135 Sloane Street, London S.W. 1, England

Please send me your course outline and FREE 56-Page Book "Your Future in Electronics and Nuclear Engineering Technology" . . . describing opportunities and CREI home study courses in Advanced Engineering Technology.



Check field of greatest interest

- Radar, Servo and Computer Engineering Technology
- Electronic Engineering Technology
- Communications Engineering Technology
- Television Engineering Technology
- Aeronautical Electronic Engineering Technology
- Automation and Industrial Electronics Engineering Technology
- Nuclear Engineering Technology

Name \_\_\_\_\_ Age \_\_\_\_\_  
 Street \_\_\_\_\_  
 City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

Check:  Home Study     Residence School     Korean Veteran

To obtain fast, immediate service and to avoid delay, it is necessary that the following information be filled in:

Employed by \_\_\_\_\_

Type of Present Work \_\_\_\_\_

Education: Years of High School \_\_\_\_\_

Other \_\_\_\_\_

Electronics Experience \_\_\_\_\_

Get Into One Of Today's  
TOP OPPORTUNITY FIELDS

# ELECTRICITY — ELECTRONICS TELEVISION RADIO · ELECTRONICS

**COYNE** Train in the New Shop-Labs of Oldest,  
Best Equipped School  
of Its Kind in U. S.  
Founded 1899

in Chicago—Electrical and Electronic Center. Prepare for a better job and a successful future. Train on real equipment — no advanced education or previous experience needed. Lifetime employment service to graduates. Part time employment help to students. Finance Plan—enroll now, pay most of tuition later.

**FREE BOOK**—Mail Coupon or write to address below for Big Free Illustrated Book—"Guide to Careers."

Information comes by mail. No obligation  
and **NO SALESMAN WILL CALL.**

**COYNE ELECTRICAL SCHOOL**  
Chartered as an Educational Institution Not for Profit  
1501 W. Congress Pkwy., Chicago 7, Ill., Dept. A1-2C

**COYNE ELECTRICAL SCHOOL, Dept. A1-2C**  
1501 W. Congress Pkwy., Chicago 7, Ill.

Send **FREE** Book, "Guide to Careers" and details of all training you offer. I am especially interested in

Electricity     Television     Both Fields

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

(I understand no salesman will call)

## RADIOCOM



### Citizens Band Transceiver

NEWEST DESIGN OF PROVEN UNIT  
DUAL NOISE LIMITER  
HIGHEST SENSITIVITY AND SELECTIVITY  
TRANSISTOR POWER SUPPLY  
MOST COMPACT—ONLY 3½" HIGH

**Yours with easy terms.**

**15.95 down — 12 months to pay**

Now you can own the finest transceiver on the market. The RADIOCOM has been designed, tested, and proven by the thousands in service over a two and half year period to be the ultimate in citizen band design. It is available to you for only 159.50, on easy payment terms of 15.95 down and 12 monthly payments of 12.95. Quantity discounts available for dealers.

Let us prove this is the one for you.

Send NOW for **FREE** color catalog

RADIOCOM, P. O. BOX 147, Garland 6, Texas

## Bookshelf

(Continued from page 24)


lems and review questions are given at the end of each chapter.

Published by John F. Rider Publisher, Inc., 116 W. 14th St., New York 11, N. Y. 104 pages. Soft cover. \$2.25.


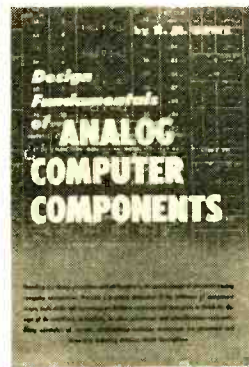
### DESIGN FUNDAMENTALS OF ANALOG COMPUTER COMPONENTS by R. M. Howe

The scientists and engineers who use analog computers and all those who



maintain analog computer installations will find this volume helpful in their work. Those familiar with general-purpose electronic analog computing techniques will gain the understanding they need of why analog-computer components are designed as they are

and how component errors affect the problems solved by the computer. There are many photographs and drawings illustrating existing commercial equipment, circuit details, and computer components.

Published by D. Van Nostrand Co., Inc., 120 Alexander St., Princeton, N. J. Hard cover. 268 pages. \$7.50.



### R/C PRIMER by Howard G. McEntee

Filling a long-felt need for a manual which would begin where the instruction booklets of commercial R/C equipment manufacturers leave off, this volume explains how to select, license, install, test, and maintain radio-control units. Emphasis is on model aircraft applications—a field which presents the most challenge to the R/C fan, and one chapter covers the special problems involved in

Always say you saw it in—POPULAR ELECTRONICS

# BUILD 20 RADIO

## CIRCUITS AT HOME

with the New  
**PROGRESSIVE RADIO "EDU-KIT"®**  
A Practical Home Radio Course

ONLY  
**\$26.95**

Reg. U. S.  
Pat. Off.



Training Electronics Technicians Since 1946

Now Includes

- ★ 12 RECEIVERS
- ★ 3 TRANSMITTERS
- ★ SQ. WAVE GENERATOR
- ★ SIGNAL TRACER
- ★ AMPLIFIER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR

- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools Needed
- ★ EXCELLENT BACKGROUND FOR TV
- ★ SCHOOL INQUIRIES INVITED
- ★ Sold In 79 Countries

**YOU DON'T HAVE TO SPEND  
HUNDREDS OF DOLLARS FOR A RADIO COURSE**

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our Kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn EVERY DETAIL, construction practice and servicing. THIS IS A COMPLETE RADIO COURSE, IN EVERY DETAIL. You will learn how to build radios, using regular schematics; how to wire and solder in a professional manner; how to service radios. You will work with the standard type of punched metal chassis as well as the latest development of Printed Circuit chassis.

You will learn the basic principles of radio. You will construct, study and work with RF and AF amplifiers and oscillators, detectors, rectifiers, test equipment. You will learn and practice code, using the Progressive Code Oscillator. You will learn and practice trouble-shooting, using the Progressive Signal Tracer, Progressive Signal Injector, Progressive Dynamic Radio & Electronics Tester, Square Wave Generator and the accompanying instruction material.

You will receive training for the Novice, Technician and General Classes of F.C.C. Radio Amateur Licenses. You will build 20 Receiver, Transmitter, Square Wave Generator, Code Oscillator, Signal Tracer and Signal Injector circuits, and learn how to operate them. You will receive an excellent background for television, Hi-Fi and Electronics.

Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with a basic education in Electronics and Radio, worth many times the complete price of \$26.95. The Signal Tracer alone is worth more than the price of the entire Kit.

### THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. Whether you are interested in Radio & Electronics because you want an interesting hobby, a well paying business or a job with a future, you will find the "Edu-Kit" a worth-while investment.

Many thousands of individuals of all

ages and backgrounds have successfully used the "Edu-Kit" in more than 79 countries of the world. The "Edu-Kit" has been carefully designed, step by step, so that you cannot make a mistake. The "Edu-Kit" allows you to teach yourself at your own rate. No instructor is necessary.

### PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore you construct, learn schematics, study theory, practice trouble shooting—all in a closely integrated program designed to provide an easily-learned, thorough and interesting background in radio.

You begin by examining the various radio parts of the "Edu-Kit." You then learn the function, theory and use of these parts. Then you build a simple radio. With this first set you will enjoy listening to regular broadcast stations, learn theory, practice testing and trouble-shooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are twenty Receiver, Transmitter, Code Oscillator, Signal Tracer, Square Wave Generator and Signal Injector circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

### THE "EDU-KIT" IS COMPLETE

You will receive all parts and instruction necessary to build 20 different radio and electronic circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, hardware, tubing, punched metal chassis, Instruction Manuals, hook-up wire, solder, selenium rectifiers, volume controls and switches, etc.

In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools; a professional electric soldering iron, and a self-powered Dynamic Radio and Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator. In addition to F.C.C.-type Questions and Answers for Radio Amateur License training, You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide and a Quiz Book. You receive Membership in Radio-TV Club, Free Consultation Service, Certificate of Merit and Discount Privileges. You receive all parts, tools, instructions, etc. Everything is yours to keep.

### PRINTED CIRCUITRY

At no increase in price, the "Edu-Kit" now includes Printed Circuitry. You build a Printed Circuit Signal Injector, a unique servicing instrument that can detect many Radio and TV troubles. This revolutionary new technique of radio construction is now becoming popular in commercial radio and TV sets.

A Printed Circuit is a special insulated chassis on which has been deposited a conducting material which takes the place of wiring. The various parts are merely plugged in and soldered to terminals.

Printed Circuitry is the basis of modern Automation Electronics. A knowledge of this subject is a necessity today for anyone interested in Electronics.

### FREE EXTRAS

- SET OF TOOLS
- SOLDERING IRON
- ELECTRONICS TESTER
- PLIERS-CUTTERS
- ALIGNMENT TOOL
- WRENCH SET
- VALUABLE DISCOUNT CARD
- CERTIFICATE OF MERIT
- TESTER INSTRUCTION MANUAL
- HIGH FIDELITY GUIDE • QUIZZES
- TELEVISION BOOK • RADIO TROUBLE-SHOOTING BOOK
- MEMBERSHIP IN RADIO-TV CLUB: CONSULTATION SERVICE • FCC AMATEUR LICENSE TRAINING
- PRINTED CIRCUITRY

### SERVICING LESSONS

You will learn trouble-shooting and servicing in a progressive manner. You will practice repairs on the sets that you construct. You will learn symptoms and causes of trouble in home, portable and car radios. You will learn how to use the professional Signal Tracer, the unique Signal Injector and the dynamic Radio & Electronics Tester. While you are learning in this practical way, you will be able to do many a repair job for your friends and neighbors, and charge fees which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have.

### FROM OUR MAIL BAG

J. Statalitis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself. I was ready to spend \$240 for a Course, but I found your ad and sent for your Kit."

Ben Valerio, P. O. Box 21, Magna, Utah: "The Edu-Kits are wonderful. Here I am sending you the questions and also the answers for them. I have been in Radio for the last few years, but like to work with Radio Kits, and like to build Radio Testing Equipment. I enjoyed every minute I worked with the different kits; the Signal Tracer works fine. Also like to let you know that I feel proud of becoming a member of our Radio-TV Club."

Robert L. Shuff, 1534 Monroe Ave., Huntington, W. Va.: "Thought I would drop you a few lines to say that I received my Edu-Kit, and was really amazed that such a bargain can be had at such a low price. I have already started repairing radios and phonographs. My friends were really surprised to see me get into the swing of it so quickly. The Trouble-shooting Tester that comes with the Kit is really swell, and finds the trouble, if there is any to be found."

### UNCONDITIONAL MONEY-BACK GUARANTEE

**ORDER DIRECT FROM AD—RECEIVE FREE BONUS  
RESISTOR AND CONDENSER KITS WORTH \$7**

- Send "Edu-Kit" postpaid. I enclose full payment of \$26.95.
- Send "Edu-Kit" C.O.D. I will pay \$26.95 plus postage.
- Rush me FREE descriptive literature concerning "Edu-Kit."

Name .....  
Address .....

**PROGRESSIVE "EDU-KITS" INC.**  
1186 Broadway, Dept. 581-D, Hewlett, N. Y.

# CITIZENS BAND SALE!

Closing out our stock of CB kits. Nationally advertised at \$39.95 up. Complete with power supply, tubes, crystal, cabinet, cabinet, coils, etc., less mike. Kit sales final. Rush your order today!!

- 110 VOLT CB TRANSCEIVER KITS **\$19.95**
- 12 VOLT CB TRANSCEIVER KITS **\$22.95**
- 6 VOLT CB TRANSCEIVER KITS **\$22.95**

## GROVE BREAKS THE CB ANTENNA PRICE BARRIER!!!

Our tremendous clearance sale brings you the lowest prices in the country.

- GROUND PLANE ANTENNA** (Reg. \$15.95) **SALE PRICE \$ 8.99**
  - 3-ELEMENT HORIZONTAL BEAM ANTENNA** (Reg. \$29.95) **SALE PRICE \$11.99**
  - FIELD STRENGTH METER KIT** (fantastically priced!!) **SALE PRICE \$ 6.99**
  - 11-PC. MOBILE NOISE SUPPRESSION KIT** (includes tunable Generator Filter) **SALE PRICE \$ 3.99**
  - FAMOUS BRAND CERAMIC CB MIKE** (Reg. \$11.00) **SALE PRICE \$ 4.95**
  - FAMOUS MAKE CB XMTG CRYSTALS** (Reg. \$3.95) (EACH) **SALE PRICE \$ 1.99**
- Lots of 3—\$1.89 each; Lots of 6—\$1.79 each

Check items wanted. Return ad w/check or M.O. Include Postage. Excess returned. C.O.D. orders 25% down (Note: Antennas must be shipped railway express or freight)

### GROVE ELECTRONIC SUPPLY COMPANY

4103 W. Belmont Ave., Chicago 41, Ill.

- Rush items checked
- Send FREE catalog of giant CB Values

Name..... (please print)

Address.....

City..... Zone..... State.....

## Bookshelf

(Continued from page 26)

model boating. The techniques described, however, apply to almost every use of radio control, and all but the most experienced R/C enthusiasts will find much useful information in this book.

Published by Kalmbach Publishing Co., 1027 N. 7th St., Milwaukee 3, Wis. 64 pages. Soft cover. \$2.00.



### DIAL CORD STRINGING GUIDE—VOLUME 8 by the Howard W. Sams Engineering Staff

A perennial favorite with servicemen, the Sams "Dial Cord Stringing Guide" Series makes an easy task of the otherwise tough restringing job. Volume 8, which brings the coverage of radio and TV receivers up-to-date through 1960, includes 214 dial cord diagrams of 1959-1960 receivers. The book also contains a comprehensive index of Volumes 5 through 8.

Published by Howard W. Sams & Co., Inc., 1720 E. 38th St., Indianapolis 6, Ind. 80 pages. Soft cover. \$1.00.

## New Literature

The H. H. Scott "Guide to Custom Stereo" is designed to help you select the proper stereo system to suit your needs. This 14-page booklet explains stereo and high fidelity, then shows you how to choose components, use them, and place them in your home. Write to H. H. Scott, 111 Powdermill Rd., Maynard, Mass., for your free copy.

Sonotone's broad line of audio and electronic products is covered in a new eight-page 1961 catalog. The attractive-looking booklet features the latest ceramic and crystal cartridges, tone arms, magnetic (velocity) equalizers, mono and stereo tape heads, and ceramic microphones. Also displayed and discussed are rechargeable flashlight battery cartridges, loudspeakers, and electronic tubes. Write to the Electronic Applications Division, Sonotone Corporation, Elmsford, N. Y., for a copy. -50-

## KUHN

"LEADERS IN SPECIALIZED RECEIVING EQUIPMENT"

### MOBILE FIXED CONVERTERS

- POLICE
- FIRE
- COMMERCIAL
- CITIZEN'S BAND

**331B** Crystal controlled. Requires no high voltage supply. For transistor car radios. Can be connected in moments for emergency use.

2-54 MC  
Complete \$24.95  
Other models for 108-162 MC available.



**315A**

A practical converter for emergency use with home or auto sets. Easily installed. Tunable over 12 MC in 26-54 MC or 30 MC in 108-174 MC band.

COMPLETE \$13.95



**315AC** Crystal controlled up to 54 MC. COMPLETE \$18.95  
Crystal controlled up to 165 MC. COMPLETE \$22.95

**315AD** Crystal controlled. For use with transistor car radios. 2-54 MC. COMPLETE \$17.95

**316A VARIABLE CONVERTER.** Front panel tuning permits rapid change between separated signals over 1D MC range in 26-54 MC or 108-174 MC band. COMPLETE \$19.95

**CONVERTERS  
ALL EQUIPPED  
WITH SELF  
CONTAINED  
SWITCHING  
AND LEADS  
FOR RAPID  
CHANGE-OVER**

ORDER TODAY or  
SEND FOR FREE  
CATALOG... containing complete  
information on a  
full line of:  
CONVERTERS AND  
RECEIVERS FOR  
EVERY APPLICATION



**326B SUPER CONVERTER.** Crystal controlled. For transistor car radios. Ultra high gain. Self contained ANL. 2-54 MC.

Complete \$44.95



20 GLENWOOD  
CINCINNATI 17,  
OHIO

# NOW IN KIT FORM!

The RCA Senior VoltOhmyst®

WV-98B(K)

ONLY \$62.50\* With probe, cable, clips and instruction booklet.

Featuring Pre-assembled Etched-Circuit Board and Pre-Assembled DC/AC-CHMS Probe (WG-299D)

- Easy-to-read meter—6 1/2" wide
- 200-microampere meter movement with less than 1% tracking error
- Precision multiplier resistors accurate to ± 1%
- Meter electrically protected against burnout
- Separate color-coded peak-to-peak and rms-voltage scales
- Die-cast aluminum case with leather carrying handle

### MEASURES:

DC voltages, 0 to 1500 volts.  
AC voltages, 0 to 1500 volt rms or 0 to 4200 volts peak-to-peak.  
Resistances from 0.2 ohm to 1,000 megohms.

RCA WV-98B available factory-wired and calibrated: \$79.50\*

Real dollar-savings!

Assembly time is cut to the bone!

This extra-heavy etched-circuit board comes with all components completely mounted and soldered. The input probe and cable, likewise, comes to you already assembled and wired.


## OTHER OUTSTANDING RCA KIT VALUES...



RCA VOLTOHMYST® KIT  
WV-77E(K) Only \$29.95\*

Famous VoltOhmyst® quality and performance at a low price! Special test features include: separate 1.5-volt rms and 4-volt peak-to-peak scale for accurate low AC measurements; Measures AC and DC voltages to 1500 volts; resistances from 0.2 ohm to 1,000 megohms. Complete with ultra-slim probes, long flexible leads, special holder or handle to store leads.

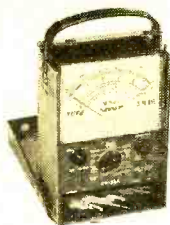
RCA WV-77E available factory-wired and calibrated: \$43.95\*



RCA WV-38A(K)  
VOLT-OHM-MILLIAMMETER KIT  
Only \$29.95\*

The V-O-M with the extras! • 0.25-volt and 1.0-volt DC ranges • Big easy-to-read 5 1/4" meter • Non-breakable sealed plastic case—no glass to crack or shatter • Jacks located below switches to keep leads out of the way • Spring clips on handle to hold leads • Attractive, scuff resistant, rugged carrying case, only \$4.95\* extra.

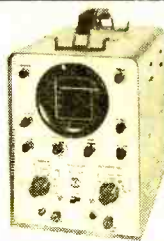RCA WV-38A available factory-wired and calibrated: \$43.95\*



RCA SUPER-PORTABLE  
OSCILLOSCOPE  
KIT WO-33A(K) Only \$79.95\*

Now in kit form. A "scope you can carry anywhere! Rugged and compact, yet weighs only 14 pounds. Just right for in-the-home and shop troubleshooting and servicing of black-and-white and color TV, radio, hi-fi components, tape recorders, etc. Ample gain and bandwidth for the toughest jobs. Scaled graph screen and internal calibrating voltage source for direct reading of peak-to-peak voltage.

RCA WO-33A available factory-wired and calibrated: \$129.95\*

See them all at  
your Authorized RCA  
Test Equipment Distributor



The Most Trusted Name in Electronics  
RADIO CORPORATION OF AMERICA

\*User Price Optional

**SPARTAN TEACHES**  
**ELECTRONIC**  
**TECHNICIANS**  
**THE EASY**  
**WAY**



Spartan teaches Electronic Technicians the easy way . . . by scientific methods and with ultra modern equipment. Write today for FREE brochure on methods and equipment. You learn by doing! If you really want to earn more money, get into the electronics field—NOW—where earnings are higher, jobs are plentiful. Ask about our Extended Payment Plan and Job Placement service. **YOUR FUTURE IS AT STAKE!**

Classes open to men and women . . . day and night courses available.

**SPARTAN SCHOOL OF ELECTRONICS**

Director of Admissions  
 Spartan School of Electronics  
 Dept. PE-61  
 Municipal Airport / Tulsa, Okla.

NAME.....

ADDRESS.....


CITY..... STATE.....

**NEW**  
**products**

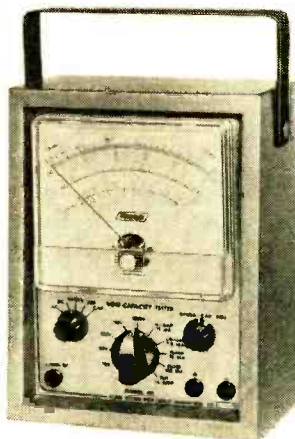**DUAL-PURPOSE TESTER**

A combination VOM and capacity tester has been announced by *Mercury Electronics Corp.*,

(77 Searing Ave., Mineola, N. Y.) Features of the Model 400 include a carrying handle which doubles as a support for the instrument, holding it in a tilted position; and a slope front projecting the 4½" meter forward for even



easier reading. The Model 400 has seven d.c. voltage ranges (0-15 to 0-7500 volts at 20,000 ohms per volt); six a.c. ranges (0-15 to 0-1500 at 5000 ohms per volt); five d.c. current ranges (0-15 ma. to 0-15 amperes). Capacity range is from .001 μf. to 80 μf.; resistance range is from 0.5 ohm to 10 megohms. The unit measures 5⅞" x 7¾" x 3½". Price, \$39.95.

**FIVE-BAND RECEIVER KIT**

The superheterodyne circuit in the Knight-Kit R-55 receiver covers the 530-kc. to 36-mc. range in four bands, and



also has a 47-54 mc. (6-meter amateur band) range. The dual 1650-kc. i.f.


POPULAR ELECTRONICS


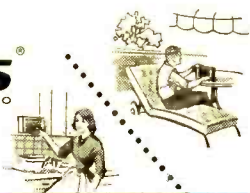
# NEW—simply great **knight-kits**<sup>®</sup>

A PRODUCT OF ALLIED RADIO

talk of the kit world... only at **ALLIED**



measures  
engine speed,  
0-8000 rpm



it's **WIRELESS**—  
just plug in  
and **TALK!**

## New Money-Saving Electronic Tachometer Kit

3% Accuracy Regardless of Temperature or Voltage Variations

Until Aug. 1 **\$19.95** Another KNIGHT-KIT first—a precision tachometer in money-saving, easy-to-build form. Helps you drive at your best engine speed efficiency, like the professionals. Transistor switching and Zener diode regulator contribute to exceptional 3%-of-full-scale accuracy, regardless of voltage or temperature changes. Operates with 4, 6 or 8 cylinder automotive engines; simple installation. Ideal also for outboard marine engines using battery or magneto ignition system from 2 cycle 2 cylinder and up. Big illuminated D'Arsonval meter; 0-8000 rpm scale; separate reference pointer may be preset to any desired speed. For 12-volt systems only. With cables, mounting hardware, wire and solder. Shpg. wt., 2 lbs.

83 Y 944. For negative ground systems (American cars).

83 Y 980. For positive ground systems (Foreign cars).

No Money Down. Introductory Price. EITHER TYPE..... \$19.95

## Deluxe Wireless Intercom System Kit at Lowest Cost

Works Anywhere Without Wires — No Installation!

This easy-to-assemble intercom operates without installation or wiring—just plug into any AC or DC wall outlet for step-saving communication! Change locations easily—anywhere. Ideal for home, office or store. In the home, you can communicate with nursery, garage, basement or patio. In office or shop, provides time-saving communication. Will operate between adjacent buildings that are on same electric-company line transformer. Perfect for baby sitting. Features power-line noise silencing circuit for absolutely quiet "standby"; premium quality throughout. Has Talk-Listen switch, with lock-on feature for constant listening. Handsome cream-toned plastic cabinet, 9 x 5½ x 5¼". Can be used in systems consisting of 2 or more units, as desired. Shpg. wt., 3½ lbs.

PAIR  
**\$37.90**

No Money Down

20 YX 272-2. Complete 2-Station System. NET ..... \$37.90

83 Y 941. Additional Station. NET EACH ..... \$18.95

SEE DOZENS OF GREAT

**knight-kit** BUYS IN

## Allied's Summer Sale Book!

Make your money-saving selections from page after page of great KNIGHT-KIT values and special offers! Save most on the best in build-your-own Stereo, hobby, instrument and Ham kits. Also see terrific closeouts on tape recorders, phonos, records and tape; specials in radios, cameras, TV accessories, Citizens Band radio, amateur gear, P.A., test instruments, tools and electronic parts. Send coupon today!



**free**

SAVE AS NEVER BEFORE on everything in Electronics—hundreds of special bargains—dozens of new products! Write for this big value-packed Sale Book today!

SEND  
FOR IT  
NOW!

ALLIED RADIO, Dept. 38-F1  
100 N. Western Ave., Chicago 80, Ill.

Send FREE Allied Sale Book No. 205

Ship me the following:

- 83 Y 944 Tachometer Kit.  20 YX 272-2 Intercom System  
 83 Y 980 Tachometer Kit.  83 Y 941 Intercom Station

\$ ..... enclosed

Name \_\_\_\_\_

PRINT

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

**ALLIED RADIO**

**FREE** **GIANT 1961 204 PAGE CATALOG**

**B-A 1961**  
ANNUAL CATALOG 611

Since 1927

A Complete Buying Guide for Everything in

**RADIO TV ELECTRONICS**

**BURSTEIN-APPLEBEE CO.**

Dept. PE, 1012 McGee St., Kansas City 6, Mo.

Send Free 1961 B-A Catalog No. 611

Name .....

Address .....

City ..... State .....

**SEND FOR IT TODAY**

SAVE UP TO 50% ON B-A SELECTED KITS

HI-FI AND STEREO SYSTEMS & COMPONENTS

TOP VALUES IN POWER AND HAND TOOLS

30 PAGES OF BARGAINS NOT IN ANY OTHER CATALOG

Guarantee

**NOW 30% OFF LIST**  
**ON VANGUARD ELECTRONIC ASSEMBLIES**

Available at your dealer or order direct.

All items are new, tested, guaranteed, and complete with tubes, transistors, and crystals, but less power supplies and cabinets. All transmitters meet FCC requirements.

- TRANSMITTER.** Code #253275, 5 watt, 27 mc crystal controlled, citizens band, reg. \$14.99 ea. now only \$10.49 ea.
- TRANSMITTER.** Code #253505, 5 watt, 50 to 54 mc., crystal controlled, amateur band, reg. \$14.99 ea. now only \$10.49 ea.
- TRANSMITTER.** Code #925327, 100 milliwatt, 27 mc., crystal controlled, citizens band, completely transistorized. Shirt pocket size, reg. \$18.99 ea. now only \$13.29 ea.
- RECEIVER.** Code #715271, frequency range 27 to 29 mc citizens band and 10 meter amateur band. Sensitivity better than 4 microvolts. Battery operated, reg. \$9.99 ea. now only \$6.99 ea.
- RECEIVER** Code #971527, similar to above but pocket size and completely transistorized. Operates on 4 pen light cells, reg. \$16.99 ea. now only \$11.89 ea.
- CONVERTER.** Code #260270, crystal controlled, adapts any broadcast radio to 27 mc citizens band. Tunes all 22 channels, reg. \$14.99 ea. now only \$10.49.
- CONVERTER.** Code #926027, similar to above except uses 3 high frequency transistors. Operates on 6 or 12 volts, reg. \$24.99 ea. now only \$17.49 ea.
- NOISE SILENCER.** Code #113300, for superb radio receivers. A superior circuit using 2 dual tubes which provides the most effective noise clipping and adjustable snitch without audio distortion or loss of gain, reg. \$14.99 ea. now only \$10.49 ea.
- SIGNAL BOOSTER.** Code #250270, improves reception of any superb citizens radio receiver by greatly increasing sensitivity and image rejection ratio with a high gain pentode amplifier, reg. \$10.99 ea. now only \$7.69 ea.
- I.F. AMPLIFIER AND DETECTOR.** Code #925455, a two stage subminiature 455 K.C.I.F. amplifier utilizing 3 transformers, 2 high frequency transistors, plus 1 diode. Very selective (3.5 K.C.), high gain and AVC, reg. \$16.99 ea. now only \$11.89 ea.

**FREE valuable gift if you order NOW from this adv.**  
**Immediate shipment if you include money order.**  
See your dealer or mail your order to our factory below.

**VANGUARD ELECTRONIC LABS, Dept. E-6**  
190-48 99 Ave., Hollis 23, N. Y.


**products**

(Continued from page 30)

stages provide high image-ratio and sensitivity, and a fused, transformer-type power supply with filter choke assures good voltage regulation. Priced at \$67.50, the kit is listed as Stock No. 83 YU 935. An optional crystal calibrator, which can be built right into the receiver chassis, sells for \$10.95. (Allied Radio Corp., 100 N. Western Ave., Chicago 80, Ill.)

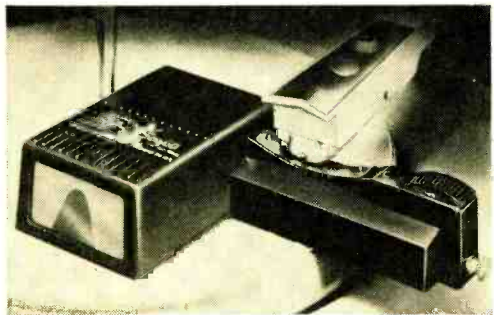**STYLUS CHECKER**

A new low-cost viewer helps record collectors guard against stylus wear. The Syl-A-Scope SG-33 magnifies the contours of a stylus and reflects the image



upon a large, illuminated, ground-glass screen. In most cases, it can be used without removing the stylus or cartridge from the tone arm. Listing at \$6.75, this compact unit operates on two pen-light batteries; a larger model, the SG-66 "Professional," operates on 117 volts a.c. and lists at \$19.95. (Robins Industries Corp., Flushing 54, N. Y.)

**SLIDE RULE KIT**

Special-purpose slide rules are easy to design and construct with a new kit placed on the market by Dyna-Slide. Ideal for those who must make recurring special calculations, the kit contains the parts for three 3" x 11" basic slide rule blanks (1-slide, 2-slide and 3-slide); a plastic scale-plotting ruler; a universal logarithmic chart; and a 25-page instruction booklet. Since the scales can be calibrated with the actual values they are to represent, it is not necessary to figure out decimal point placement. The



# NRI—Oldest and Largest Radio Television School Now Offers NEW HOME STUDY TRAINING IN INDUSTRIAL & MILITARY ELECTRONICS

## Special Training Equipment Included

No extra cost. In NRI Electronics training especially developed training equipment brings to life theory you learn in illustrated lessons. You get practical experience with thyratron tube circuits, multivibrators, capacitors, diodes, transistors, telemetry, computer circuits and other basic circuits and components.

**TRAINING AID 1** Get practical experience measuring voltage, current, building circuits.

**TRAINING AID 2** Build Vacuum Tube Voltmeter. Make tests on series and parallel circuits.

**TRAINING AID 3** Practice with resistors, capacitors, coils. Work with half-, full-wave, bridge, voltage doubler and pi-type filter circuits.

**TRAINING AID 4** Build circuits with pentode tubes, selenium rectifiers, transistors. Build oscillator, check signal phase shift with oscilloscope.

**TRAINING AID 5** Experiment with thyratron tube circuits, Lissajous patterns. Study basic amplitude detector circuits, modulation, demodulation.

**TRAINING AID 6** Get practical experience with magnetic amplifiers, learn to use modified Prony brake; determine motor torque. Use strobe disc to measure motor speed.

**TRAINING AID 7** Learn effects of feedback. You build and experiment with dc coupled (instrument) amplifier. Study broadband amplifiers; photocells.

**TRAINING AID 8** Experiment with multivibrators used as timing generators in binary counters, and as frequency dividers. Learn to use blocking oscillators, thermistors.

**TRAINING AID 9** Practical experience in telemetry circuits used in earth satellites, remote control devices. Work with basic circuits used in digital and analog computers.

**TRAINING AID 10** Assemble circuits in electrical and electro-mechanical systems, make valuable practical electronic circuits.

Growth creates need. Rapidly expanding use of Electronic equipment in industry, business, military is increasing the demand for Electronic Technicians. To help meet this demand, NRI now offers a complete course in ELECTRONICS—Principles, Practices, Maintenance in addition to NRI training in Radio-TV Servicing and Radio-TV Communications.



## Job Counselors Recommend

Job counselors will tell you that men with technical Electronic training are in demand—that future opportunities are great. And because the work is important—the pay is high. NRI catalog shows how you can join graduates now enjoying interesting careers in this age of Electronics.

## Learn More to Earn More

Waiting and wishing for a better job won't get you ahead. *You must act!* The ambitious man—with or without previous experience—can train at home the NRI "learn-by-practice" way. Keep your present job while training. NRI supplies training at low cost because it is the oldest, largest home-study school of its kind. Plan now to earn more. Send for FREE 64-page catalog.

**FOR MORE INFORMATION—TURN PAGE**

**Cut Out and Mail—No Stamp Needed**

**NRI** NATIONAL RADIO INSTITUTE  
WASHINGTON 16, D. C. Dept. 100-4

Send me your Electronic, Radio-TV catalog without cost or obligation. (No representative will call. Please PRINT.)

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

Send for  
64-Page  
CATALOG  
**FREE**



ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL

**ELECTRONICS NEEDS  
4 TO 7  
QUALIFIED TECHNICIANS**



**FOR EVERY  
GRADUATE ENGINEER**



**Choose from 3 Fields  
of Opportunity**

There's an NRI course for each of the three major branches of Electronics. The **FREE CATALOG** we send helps you select training of your choice.

- 1 INDUSTRIAL ELECTRONICS**  
Principles, Practices, Maintenance of computers, servomechanisms, telemetry, other Electronic equipment.
- 2 RADIO-TV SERVICING**  
Service and maintain Radios, TV sets, Hi-Fi, PA systems. A profitable field, full or spare-time.
- 3 COMMUNICATIONS**  
Training for men who wish to operate and maintain radio and TV stations, police, marine and mobile radio, etc.

**SEE OTHER SIDE**

FIRST CLASS  
PERMIT  
NO. 20-R  
(Sec. 34.9, P.L.&R.)  
Washington, D.C.

**BUSINESS REPLY MAIL**  
NO POSTAGE STAMP NECESSARY IF MAILED IN THE UNITED STATES

POSTAGE WILL BE PAID BY

**NRI** National Radio Institute  
3939 Wisconsin Avenue  
Washington 16, D.C.

**Join The Thousands  
Who Trained For  
Advancement With NRI**

Thousands of NRI graduates throughout the U. S. and Canada are proof that it is practical to train at home. NRI graduates are in every kind of Electronics work: inspectors, maintenance men, assistant engineers, testers, lab technicians, or holding essential Government posts. Read what these men have to say about NRI home-study "learn-by-practice" training:



**A GOOD CHANCE FOR ADVANCEMENT** exists for Roger E. Vallerand of Hartford, Conn., at Hamilton Standard, United Aircraft Corp. electronic division. "I can truthfully say that anyone contemplating taking the course will have no regrets. Many thanks to NRI."



**NOW FOREMAN FOR AN ELECTRONICS FIRM**, Thomas R. Favalaro started working even before finishing the NRI course. He is with Technical Appliance Corp., Shelburne, N. Y. In charge of all government and communications divisions. He says, "it is responsible for my whole future."



**"THE FINEST JOB I EVER HAD"** is what Thomas Bilak, Jr., Cayuga, N. Y., says of his position with the G. E. Advanced Electronic Center at Cornell University. He writes, "Thanks to NRI, I have a job which I enjoy and which also pays well."



**"I ACTUALLY ENJOY GOING TO WORK."** That's how Duane E. Bitner, Manchester, N. H., describes his position with Raytheon working on the Hawk Missile System. "I can truthfully say your course gave me my biggest boost."



**BUILDING ELECTRONIC CIRCUITS** on specially-designed plug-in type chassis, is the work of Robert H. Laurens, Hammonton, N. J. He is an Electronic Technician working on the "Univac" computer. "My NRI training helped me to pass the test to obtain this position."



**Oldest and Largest  
School of Its Kind**

Training men to succeed by home study has been the National Radio Institute's *only* business for over 45 years. NRI is America's oldest and largest Electronics home-study school. Don't delay. Cut out and mail **POSTAGE-FREE CARD**.

**MAIL POSTAGE-FREE CARD**

# products

(Continued from page 32)

complete kit is priced at \$8.50, and additional slide rule blanks are \$2.50 each. (Dyna-Slide Company, 600 S. Michigan Ave., Chicago 5, Ill.)


## RUST-PREVENTING TOOL WRAP

"Rust-Preventive Tool Wrap" eliminates the need for oiling or greasing to protect tools from rust. The chemically treated paper surrounds metal surfaces with a rust-preventing vapor which remains effective over long periods of time. Useful for sporting equipment, boat fixtures and motors, etc., as well as tools of all kinds, a 45-square-foot roll of the 18"-wide material sells for \$2.00. (Robbie's, 443 Encinitas Ave., San Diego 14, Calif.)
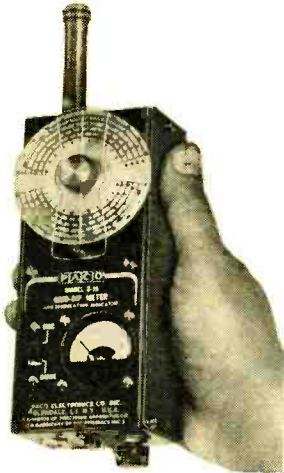
## GRID DIP METER KIT

A new addition to PACO's line of high-fidelity and test instrument kits is the Model G-15 grid dip meter. The unit functions either as a variable frequency oscillator or as an absorption wavemeter, completely covering the 400-kc. to 250-mc. range in eight bands. In addition, a modulation indicator gives both a visual and aural

check of "on the air" speech level. Price of the kit, complete with a set of eight plug-in coils, is \$31.95. The instrument is also available factory-wired for \$49.94. (PACO Electronics Co., Inc., 70-31 84th St., Glendale 27, Long Island, N. Y.)



## "PRIMER-SCOPE"

Weighing less than six pounds, the "Primer-Scope" Mark I telephone-directory-sized oscilloscope is intended primarily for beginners but is also handy for professionals who don't require an advanced unit. The sweep operates over a range

of 20 cps to 20 kc. with either internal or external synchronization, and a horizontal input is provided. Sensitivities are 250 millivolts per division for d.c.




signals, 6 millivolts per division for a.c. signals. Price, \$69.95, complete with easy-to-understand training manual. (Waterman Products Co., 2445 Emerald St., Philadelphia 25, Pa.)
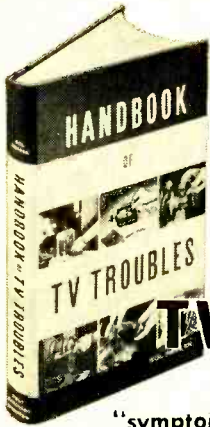
## "RADAR-LITE" LANTERNS

The redesigned 1961 line of Burgess "Radar-Lite" battery-operated lanterns incorporates many new features—including an over-size thumb switch, a gun-type lock to prevent accidental switching on or off, and an unbreakable polystyrene shield for the removable light-




head. Several different models are available, one of which is a 12-volt unit with twice the candlepower of the brightest 1961 automobile headlight. Prices range from \$8.95 to \$11.95. (Burgess Battery Co., Division of Servel, Inc., Freeport, Ill.)



**new**  
**Master Guide to**  
**TIME-**  
**SAVING**  
**TV SERVICE**

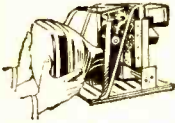**A modern manual for fast, "symptomatic trouble analysis" and servicing of TV receivers.**



**TAKES THE GUESSWORK OUT OF TV REPAIRS!**

*Covers all causes of practically every trouble you're ever likely to be called on to fix including:*

- BRIGHTNESS**
- CONTRAST TROUBLES**
- PICTURE DISTORTION**
- UNSATISFACTORY PICTURE DETAIL**
- LINE OR BARS IN PICTURE**
- SYNCHRONIZATION TROUBLES**
- MISSING PICTURE**
- SIZE AND CENTERING TROUBLES**
- SOUND TROUBLES**
- TELEVISION INTERFERENCE, ETC.**

This isn't a "study" book! From beginning to end, this big manual is designed for daily use at the bench as a complete easily understood guide to practically any TV receiver job.

Just turn to the Index. Look up the trouble symptoms exhibited by the TV you're working on. The **HANDBOOK OF TV TROUBLES** then tells you exactly what and where to check. Outlines time-saving short cuts. Explains puzzling details. Eliminates guesswork and useless testing. More than 150 test pattern, wave form and circuit illustrations help explain things so clearly you can hardly fail to understand.

**LOOK! LISTEN!**  
**Then Follow This Easy Guide!**

Almost regardless of set make or model, this remarkable new 302-page Handbook helps you track down TV troubles from the symptoms they produce in the set itself—screen intermittently dark; "blooming"; abnormal contrast in spots; "snow"; poor detail; sync troubles; sound troubles—and all the many others. Then it explains how to make needed adjustments or replacements.

Printed in large type. Has sturdy, varnished covers for "on the job" use. The **TV TROUBLE INDEX** helps you find what you want in a jiffy. Throughout, it's the ideal guide for beginners and experienced servicemen alike! Try it for 10 days **AT OUR RISK**. You be the judge!

**TRY IT 10 DAYS—See for yourself!**

623900

Dept. PE-61, HOLT, RINEHART and WINSTON, Inc.  
 Technical Div., 383 Madison Ave.  
 New York 17, N. Y.

Send new 302-page **HANDBOOK OF TV TROUBLES** (708-453) for 10-day **FREE** trial. If I decide to keep book, I will then send you \$7.50 in full payment. If not, I will return book postpaid and owe you nothing. **SAVE: Send \$7.50 with order and Rinehart pays postage.** Same 10-day return privilege with money promptly refunded.

Name .....

Address .....

City, Zone, State .....

**OUTSIDE U.S.A.—No free examination. Price \$8.00 cash only. 10-day return privilege with money refunded.**  
**Offer expires January 31, 1962**

**Tips**



**and**

**Techniques**


**PIN CONTACT IMPROVER**

Good electrical contact between a male pin plug and its socket is frequently lost as these parts wear. To regain it, you can coat the pin with silver or copper printed-circuit paint. For best results, renew the coating occasionally. This technique is particularly useful on coax connectors, where a small amount of contact resistance can mean an appreciable signal loss.

—John A. Comstock

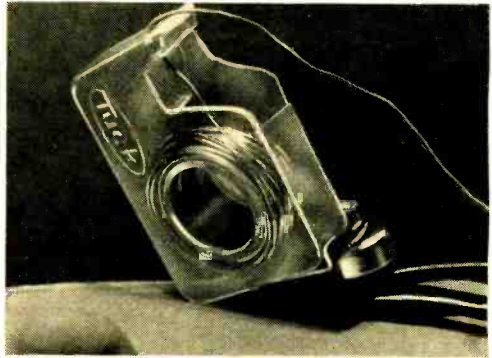**HANDY SOLDER DISPENSER**

If you're looking for a cheap but handy solder dispenser, try using an empty cellulose tape holder. Alter the holder by drilling a small hole for the solder below the holder's serrated cut-off flange as shown; wind the solder on the tape spool,



thread it through the hole, and the dispenser is ready for use. A small alnico magnet glued to the side of the dispenser will hold the dispenser to the metal sides of your workbench.

—Glen F. Stillwell

**EMERGENCY RECEIVING ANTENNA**

The "hot" side of the a.c. line makes an excellent emergency receiving antenna, and a receiver antenna circuit may be capacitively coupled to it through a piece of zip cord. Connect one lead of a 6' length of zip cord to one of the prongs of an a.c. plug; the other lead at that

Always say you saw it in—POPULAR ELECTRONICS

end of the cord is cut off just before it enters the plug. Separate the leads at the other end for a distance of about 6", forming two "stubs." The stub of the lead which is wired into the plug is cut off, and the exposed end taped. Strip the remaining stub in the usual way and connect it to the receiver's antenna post. Now insert the plug in an a.c. socket. If reception is poor, the wired prong of the plug may have been inserted into the ground side of the outlet; try reversing the plug.

—Charles Bautsch III

### MINIATURE TUBE STORAGE

A 10-dram transparent plastic vial, available at most drug stores, makes an excellent storage container for either a 7- or 9-pin miniature tube. The tube fits neatly into the vial, and its type marking can be read right through the transparent wall—eliminating the need for labeling. Wads of cotton batting placed at the top and bottom of the tube act as shock absorbers.

—Leonard I. Kindler

### INEXPENSIVE "SEAM RIPPER"

An inexpensive sewing tool known as a "seam ripper" is useful both for building and tearing down equipment. It makes an easy job of removing the sheath covering coax or multi-wire cable or stripping cable harnesses from surplus gear being "cannibalized" for parts.

—Darrel Foyst

### SAFER LINE CORD SPLICE

For a safer, neater line cord splice, you can stagger the joints in the two leads rather than making them side by side. There will be less chance of a short circuit, less tape is needed for a safe job, and the splice will be neater because the



tape is spread out more. To make such a stagger splice, just cut the cord so that the joints will not be directly opposite each other; twist, solder and tape each

joint; and finish the job with an overall tape wrapping.

—Carl Dunant

### EXTENDED PLAY FOR PORTABLES

If your portable radio uses flashlight cells, you can enjoy many more hours of playing time before replacement is necessary by installing photoflash units



instead. Photoflash cells are longer-lasting and are designed to give more dependable performance toward the end of their life. They are available in both size "D" and penlight sizes.

—James Clifford

### "TEAR-OFF" STORAGE CONTAINERS

"Tear-Off" polyethylene bags, available in rolls of various widths, make ideal storage containers for small pieces of test equipment, hardware removed from equipment being repaired, etc. These transparent bags effectively seal out dust and dirt, but allow a good view of their contents.

—H. Leeper

### BREADBOARDING POWER TRANSISTORS

Fahnestock clips and miniature tube socket contacts make excellent connectors for breadboarding diamond (T-30) cased power transistors. Bolt one or two Fahnestock clips to the transistor case for the collector connection. Then carefully remove two contacts from a 7- or 9-pin miniature tube socket, make the appropriate connections to them, and slip them over the transistor's base and emitter pins.

—Royland Petterson

from

# ELECTRONICS

BOOK SERVICE

books on radio  
& tv servicing  
...yours for a  
7-DAY FREE  
EXAMINATION!

Here is a comprehensive selection of books covering the field of radio and television servicing—for your use and profit! You'll find practical guides, reference books, background and advanced texts to give you step-by-step procedures for finding troubles and repairing radio receivers, television and FM sets, setting up your own servicing business, designing and building, and much more—each book filled with descriptive illustrations and diagrams.

And you can have one or more of these top notch best sellers—for 7 days FREE!

Simply write your choices on the coupon below and mail it today. Read and enjoy your books for seven full days. If, after that time, you do not agree that they are everything you want, return them and owe nothing. Otherwise, send along your payment of our bill plus a small charge for postage and handling.

Here is the perfect way for every serviceman to build the library he must have. Order now!



### 2404. FM RADIO SERVICING HANDBOOK, King

This is a practical guide to frequency-modulated V.H.F. radio receivers, their design, construction, alignment and repair. Includes chapters on adaptors,

aerials, and high-fidelity audio equipment. A good introduction to FM theory, kept as non-mathematical as possible. \$5.00

### 2410. TELEVISION AND RADIO REPAIRING, Markus

This book shows how to test, repair and replace each component of TV and radio receivers, power supplies, resistors and condensers, coils, tuning devices, and speakers. Shows what servicing involves, how to get information and tools necessary. The book includes the T.V. Detect-O-Scope. \$7.95

### 2422. HANDBOOK OF TV REPAIR, Hertzberg

The simple mechanical and electrical maladies which are the great majority of television set troubles—what you can do about them and what not to try. Covers tubes and testing, antennas, UGH converters, fringe-area reception, the set and the chassis. \$2.50

### 2506. FUNDAMENTALS OF RADIO AND ELECTRONICS, Everitt, et al

All you need to know on electronics and radios is found in this book—including transistors and vacuum tube principles and circuits. A product of close collaboration among five radio authorities, it is perfect for self-study. 832 pp. \$11.35

### 2402. PRACTICAL RADIO SERVICING, Marcus and Levy

Dealing with the common types of radios in use, a-c-d-c receivers, photograph players, and batter and three way portables. This book not only describes circuit fundamentals and servicing instruments and methods, but also gives graded job sheets giving valuable practical experience. Includes the indispensable Radio Detect-O-Scope. Illustrated. \$8.95

### 2403. ELEMENTS OF RADIO SERVICING, Marcus and Levy

Gives practical, step-by-step procedures for finding troubles in radio receivers and making repairs. Readers with a background of simple radio theory can easily understand the book. Emphasizes over-all servicing procedures. \$7.25

### 2406. ESSENTIALS OF TELEVISION, Slurzberg, Osterheld and Voegtlin

Comprehensive study of basic TV circuits. The operation of a color set and three monochrome receivers is described in detail from the antenna to the picture tube and loudspeaker. Features the sound section, waveforms, the picture tube, etc. Complete with illustrations, examples, questions, problems. \$8.95

### 2409. TELEVISION FOR RADIOMEN, Noil

Here are the principles and essential mathematics of television. Detailed studies of cascade tuners, new video amplifier techniques, large screen picture tubes, modern deflection systems, latest antenna detail. Covers U.H.F., color TV, transistors, some topics not dealt with before. Construction, operation and servicing of television. \$10.00



### 2411. TELEVISION SERVICING, Levy and Frankel

Explains how to find the section in which the trouble occurs and then to find the defective component. From the circuits discussed,

which are employed in over 95% of TV receivers now in use, the reader gains an understanding of the principles involved. A knowledge of basic electronics is essential. \$7.75

### 2423. BE YOUR OWN TELEVISION REPAIRMAN, Guth

Seventy-five percent of the time the only trouble with your TV set is a faulty tube. With this complete book, covering all manufacturers' models, you can easily replace the tube yourself. One dollar saves big repair charges. \$1.00



### 2804. RADIO AND TELEVISION MATHEMATICS, Fischer

Whenever you need to look up the use of a formula or the correct substitution of numbers, you can

find it here—rapidly. More than 700 step-by-step solutions of the usual problems encountered in radio, television and industrial electronics, including all those needed for FCC exams. \$6.95

### 2419. BASIC TELEVISION, Grob

The basic book for training television servicemen and technicians. No mathematics other than simple arithmetic and algebra is needed. 660 pages with illustrations. \$9.25

### 2420. TELEVISION FUNDAMENTALS, Fowler and Lippert

A simple nonmathematical presentation of the basic principles the radiotechnician must know in order to install and service television receivers. Sound treatment of each element of the system—from the antenna to the picture tube. \$8.50

### 2424. TELEVISION SERVICING, 3rd Edition, Buchsbaum

Complete, most recent information on the design, construction, and servicing of both black-and-white and color sets. Shows how to locate and repair every conceivable trouble. \$7.15

### 2427. COLOR TELEVISION FUNDAMENTALS, Kiver

This book can teach anyone familiar with monochrome television how to install and service color TV sets. All circuit discussions employ highly successful step-by-step approach. \$7.25





## BEST BUYS IN STEREO AND MONO HI-FI

New Transistorized Stereo / Mono 4-Track Tape Deck RP100



Semikit (electronics in kit form) \$289.95 Wired \$395.00



New FM-AM Stereo Tuner ST96 Kit \$89.95 Wired \$129.95 Incl. FET

New 70-Watt Integrated Stereo Amplifier ST70 Kit \$94.95 Wired \$149.95



New 40-Watt Integrated Stereo Amplifier ST40 Kit \$79.95 Wired \$129.95



28W Integrated Stereo Amplifier HF81 Kit \$69.95 Wired \$109.95

FM Tuner HFT90 Kit \$39.95 Wired \$65.95 Incl. FET Metal Cover \$3.95



Stereo Preamplifier HF85 Kit \$39.95 Wired \$64.95

Stereo Power Amplifiers



	Kit	Wired
100W HF89:	\$99.50	\$139.50
70W HF87:	\$74.95	\$114.95
28W HF86:	\$43.95	\$74.95

AM Tuner HFT94 Incl. FET Kit \$39.95 Wired \$65.95



Booksshelf Speaker System HFS1 Kit \$39.95 Wired \$47.95

Stereo / Mono Changer / Player 1007 with stereo cartridge and dual sapphire styli \$49.75



## BEST BUYS IN CITIZENS TRANSCEIVERS, HAM GEAR, RADIOS

Citizens Band Transceivers from Kit

\$59.95  
Wired \$89.95



New 60W CW Transmitter #723 Kit \$49.95 Wired \$79.95



Transistor Portable Radio RA6 Kit \$29.95 Wired \$49.95 Incl. FET

## BEST BUYS IN TEST EQUIPMENT

New Metered Variable AC Bench Supplies Model 1073 (3 amps)

Kit \$35.95 Wired \$47.95  
Model 1078 (7½ amps)  
Kit \$42.95 Wired \$54.95



Peak-To-Peak VTVM #232 & Uni-Probe® Pat. #2,790,051 Kit \$29.95 Wired \$49.95



VTVM #221 Kit \$25.95 Wired \$39.95

DC-5 MC 5" Scope #460 Kit \$79.95 Wired \$129.50



5" Push-Pull Scope #425 Kit \$44.95 Wired \$79.95

Tube Tester #625

Kit \$34.95 Wired \$49.95



RF Signal Generator #324 Kit \$26.95 Wired \$39.95



1000 Ohms/Volt V-O-M #536 Kit \$12.90 Wired \$14.90



6- & 12V Battery Eliminator & Charger #1050 Kit \$29.95 Wired \$38.95



Extra-filtered for transistor equip. #1060 Kit \$38.95 Wired \$47.95

R-C Bridge & R-C-L Comparator #950B Kit \$19.95 Wired \$29.95



Multi-Signal Tracer #145A Kit \$19.95 Wired \$28.95



**EICO**  
EXCELLENCE  
IN  
CREATIVE  
ELECTRONICS

Over 2 MILLION EICO instruments in use throughout the world. Compare, take them home — right "off the shelf" — from 1500 neighborhood dealers, most of whom offer budget terms.



EICO, 3300 N. Blvd., L.I.C. 1, N.Y. PE-6  
 Send free Catalog describing over 80 top-quality products, free Stereo Hi-Fi Guide, free Short Course for Novice License, name of nearest EICO dealer.  Send new 36-page GUIDEBOOK TO HI-FI for which I enclose 25¢ for postage & handling.

Name.....  
 Address.....  
 City..... Zone... State.....  
 Add 5% in the West



Underwood and Underwood



By KEN GILMORE

# THEY'LL FLY SAFELY

*Tomorrow's jets will be safer than ever, thanks to a growing network of electronic air traffic control*


**O**NE DAY a few months ago, a four-engine airliner with two experienced pilots in the cockpit circled an airport just outside of Atlantic City, N. J. Soon, the plane entered the traffic pattern and began its descent. A few minutes later, just above the end of the runway, the plane "flared out" perfectly, "greased" its wheels onto the runway, and rolled to a stop.

Sound like a perfectly normal landing? It was—except for one highly significant detail. *At no time during the approach or landing did either pilot touch any of the plane's controls.*

But completely automatic landing is only one in a long series of breakthroughs in aviation electronics which are making many of today's systems as obsolete as crystal sets. Scientists at the Federal Aviation Agency's research and development center near Atlantic City—where the "no-hands" landing took place—are working out



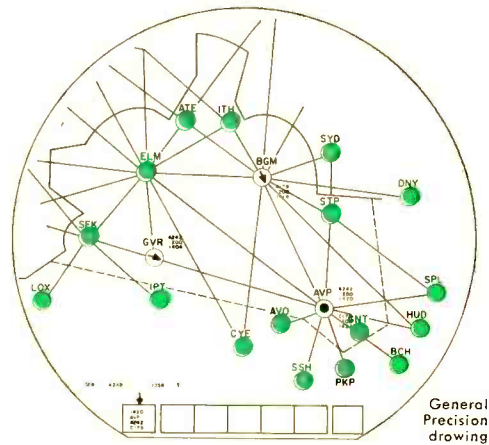Automatic flight course display developed by IT&T enables pilot to navigate by looking at map (left) showing his course and position. With IT&T display, pilot can easily guide his plane along any course he wishes.



A second map—this one for the ground controller—is part G of the electronic brain shown on page 45. Arrows at points BGM and GVR, above, indicate position of two planes; black dot at AVP identifies it as the point of their potential conflict.

final details on a number of day-after-tomorrow electronic developments. Among them:

- a proximity warning device which will automatically avoid mid-air collisions
- three-D radar to tell ground controllers each plane's altitude, as well as its range and bearing
- automatic flight course displays which will show pilots both the plane's progress and its current position instantly
- automatic plane-to-ground and ground-to-plane communications in which pilots and controllers will communicate in less than a hundredth of a second, simply by pushing buttons
- a giant, interconnected "electronic brain" complex which will keep track of thousands of planes all over the country, noting slight variations from predicted speeds and courses, and spotting potential conflicts long before planes get close to each other

**Traffic Control Plan.** An advanced air-traffic-control plan, being brought into

existence by devices such as those mentioned above, is rapidly becoming an absolute necessity. Although our present setup still does a good job—statistics show you're twice as safe today in an airliner as in your own car—it's swiftly going out of date.

The present system of air traffic control was designed in 1938, when fewer than 30,000 planes were in the air; most of them lumbered along at about 150 miles per hour. Today, we have 109,000 planes, each of which is in the air far more hours per day than were the old flying geese of a quarter century ago. In addition, many of today's craft zip along at speeds faster than that of sound.

Naturally, the basic 1938 system has been revised from time to time to keep up with the growing load. But essentially, today's operations stem from the same system that was in use before World War II, and which has just about reached its limit. Before 1975, when more than twice as many air miles will



Instrument landing systems in use at most major airports today employ three sets of transmitters on the ground, three receivers in each plane. One transmitter sends out a localizer beam, which tells the pilot that he is headed down the center of the runway. The second transmitter (at right) generates a glide-slope beam to signal the pilot that he is descending at the proper rate and in the proper path to make contact with the end of the runway. Other low-power transmitters (mushroom-shaped objects above) shoot signals straight up into the air to inform the pilot of his distance from the end of the runway. Although landings are instrument-controlled, present ILS systems require that pilots see the runways in order to land.



FAA photos

be flown each year, it will have broken down completely.

Obviously, we need a new system. To design one able to do a jet-age job, the FAA's research and development section was established three years ago. Now, it's spending 75 million dollars a year to attack the problem from every angle. Here's what your tax dollars are buying in the way of improved air safety.

**Height-Finding Radar.** In Atlantic City stands a sixteen-story-tall red and white tower that is the heart of the new ASHR-1 radar. With today's equipment, controllers can tell the direction and distance of planes in the area, but not the altitude. When two radar "blips" come together, controllers don't know if one plane is thousands of feet above the other, or whether the two planes are about to collide.

The ASHR-1, already proved successful in preliminary tests, will add this missing dimension. With height-finding radar in use, tragic mid-air collisions like

the one which claimed 138 lives over New York City last December will become much more unlikely.

**Proximity Detectors.** Since the beginning of aviation, planes have flown on a see-and-be-seen basis. At speeds up to several hundred miles an hour, this is good enough. But when two supersonic jets are approaching one another on a collision course, by the time the pilots see each other it's often too late for them to do anything about it.

To appreciate this fact, remember that jets five miles apart are actually *less than fifteen seconds away from disaster!* Yet a plane five miles off is just a tiny speck, easily overlooked. And, because of its speed and size, a fast-moving jet takes additional seconds to bite into the thin air and change its course. Obviously, in less than perfect weather and with even faster planes in the offing, men's eyes and reflexes simply aren't good enough for the job.

The answer lies in proximity warning

devices. Working on radar principles, they will detect approaching aircraft many miles away and either signal the pilot or automatically take evasive action. Three such systems are now under development.

**Automatic Course Display.** Today's airline pilot navigates by *VOR*, or very-high-frequency omnidirectional range equipment. This is a fine, accurate system, but it has one big limitation. The pilot must always fly directly toward (or directly away from) a *VOR* station. An indicator on the instrument panel tells him whether or not he is on course. In flying across country, he uses one *VOR* station after another along his course. Thus, many planes are flying from station to station on, for example, the crowded New York-to-Chicago route. Their *VOR* highway tends to hold them all on exactly the same course and actually increases the possibility of accidents.

Soon, there will be a gadget in the cockpit which will allow the pilot to fly any course he selects. He might, for example, elect to fly ten miles south of and parallel to the regular airways—a feat that would be very difficult under present conditions. Thus, an unlimited number of new airways would be opened up.

The heart of the new system will be a small computer which constantly takes bearings on *VOR* stations in the area and continuously plots the plane's position on a map. The pilot will see his course and present position drawn out before his eyes. If he wants to fly from Cleveland to Santa Fe, he can forget about *VOR* stations. He will simply guide the plane so that the course display equipment in front of him draws a line on the map between the two cities.

**Automatic Communications.** Under the present system, a pilot spends a lot of time reporting and talking to controllers, just as they do to him. Yet most of the messages are completely routine—the captain, for example, must report his position at regular intervals. When a device now under development is installed in planes, the pilot will simply push a button on his automatic communicator to transmit routine messages.

Using the same system, the controller will see the pilot's message appear on a panel in front of him. He will then

## AIR TRAFFIC



A



C

Here's how air traffic control works today. Let's say the pilot of flight 201 prepares to leave New York. He checks with ATC—air traffic control—in New York (A) to see if his route is open. When his flight is cleared, a copy of the flight plan for our fictitious flight 201 is given to each controller in the center through whose sector the plane will pass, and at the same time the flight plan is teletyped to scores of other air controllers in other centers across the country. Each controller involved writes out a flight strip for 201 and posts the strip in front of him (B) along with those of all other planes scheduled to enter his sector.

The pilot gets his clearance from the tower and takes off. At first, he is under control of the tower (C). A few minutes later ATC takes over as 201's radar echo is picked up and tracked. A New York controller puts a small block of plastic called a "shrimp boat" (D) over the radar blip and writes "201" on it. The shrimp boat is moved every few seconds to keep up with the plane's progress on the radar scope.

As 201 gets out of radar range, another controller in charge of the next sector keeps up

# CONTROL


## Today and Tomorrow

B



D

FAA photos

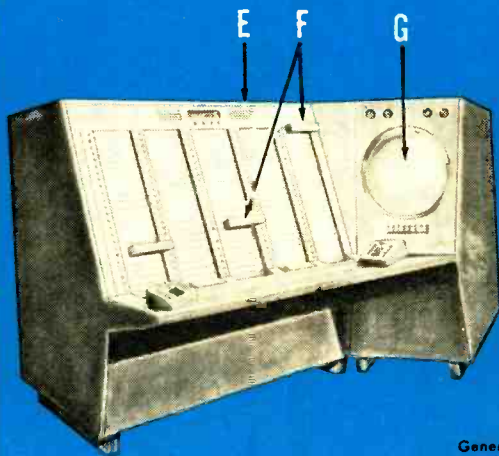

General  
Precision  
photo

with its progress by radio. He checks to see if 201 is on time. If corrections are necessary, he checks again for possible conflicts with other aircraft, and sends the corrected time on to other stations along the course.

With thousands of planes now in the air, this cumbersome system is on the verge of breaking down. Controllers must spend most of their time bookkeeping rather than controlling. But soon a new system—DPC (data processing central)—will be helping to do the job better, faster, and more reliably. Here's how it will work.


First, the flight plan is stored in DPC's electronic brain. The computer checks for conflicts, and if none exists, clears the flight. It then automatically passes the word to other computers across the country. Each computer automatically prints a flight strip for every controller who will handle the flight. Each radar blip is electronically identified so that a controller knows at a glance which echo belongs to which flight; no more "shrimp boats" to take time or cause confusion.

Updating of flight strips will be completely automatic. Let's say, for example, that flight 201 picks up a tailwind and arrives at a cer-


tain fix ahead of schedule. The computer notes it, refigures the entire course on the basis of this new information, and notifies every other computer along the flight course. Within seconds, on each flight controller's console (E) all across the country, automatic printing heads (F) run up lists of flight strips, stop at those for 201, cross out the old information, and print in the new.

If the new schedule creates a conflict, the computer in that district recognizes it automatically and flashes a red light to notify the controller. The controller in that sector presses a button and a map of the airways appears on the screen (G). On the map are shown the positions of flight 201 and the other plane in potential conflict. The controller suggests a possible solution to the computer. If this is all right, the computer okays it; if not, it indicates that there would be another conflict.

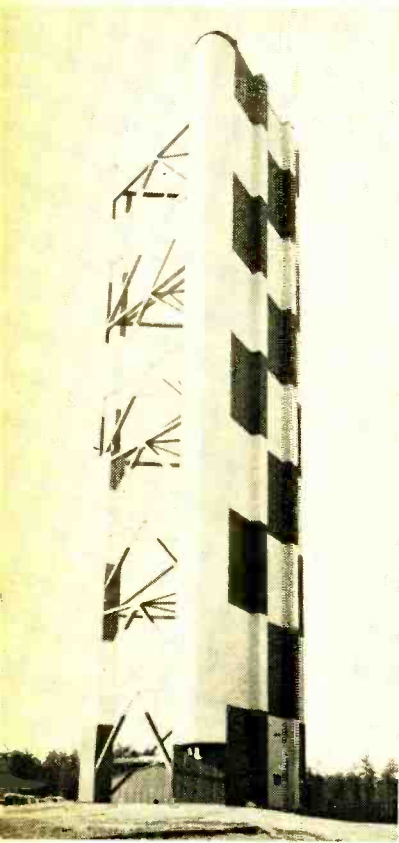When the controller has decided on and cleared a solution, he will not even have to talk to the plane in question to put it on a new course. He will simply press a button on his automatic communicator, and the trouble will be averted.



Height-finding radar transmitter housed in tower at left has hundreds of microwave receiving horns distributed along its front edge. Horns detect angle at which a radar echo approaches the tower and feed this information to a computing circuit. Computer in turn combines information with distance data from regular radar receiver to compute altitude of all aircraft in the area. Altitudes are displayed on standard position indicator (below) in special ring at outermost edge.

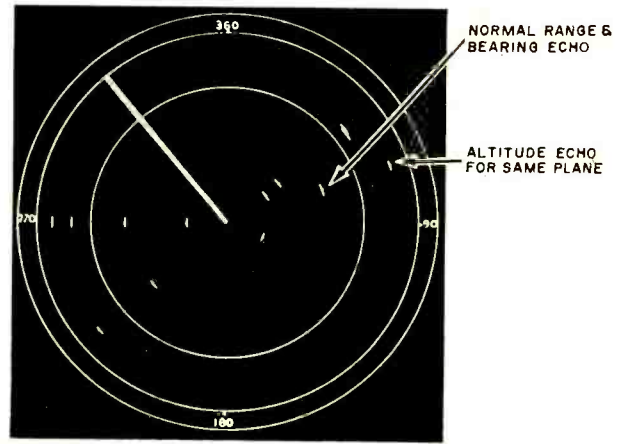

FAA photos



Push-button air-to-ground and ground-to-air communications will be standard procedure with devices now under development by Lear, Inc. Instrument above can display 64 separate words and phrases—more than enough for most routine communications.

push another button to answer, and his reply will appear on the pilot's instrument panel. The pilot will press an "acknowledge" button, flashing a light on the controller's panel and letting him know the message was received and noted. The entire operation will take only a few seconds, free crowded communications channels, and allow both pilot and controller to attend to other duties.

**Enter DPC.** Undoubtedly, the most important program under way for the improvement of our airways goes by the name of DPC—data processing central. This system, when complete, will be made up of dozens of giant computers in air traffic control centers all over the country. Each one will be interconnected with all others, so that they can chat electronically back and forth and keep each other up to date as planes pass from one area to another.


The new system will keep tabs on every controlled plane in the air, noting its progress and making sure that it keeps out of every other plane's way. (See pages 44 and 45 for a detailed explanation of how DPC will work.)

*(Continued on page 109)*



# LISTEN TO YOUR HEART

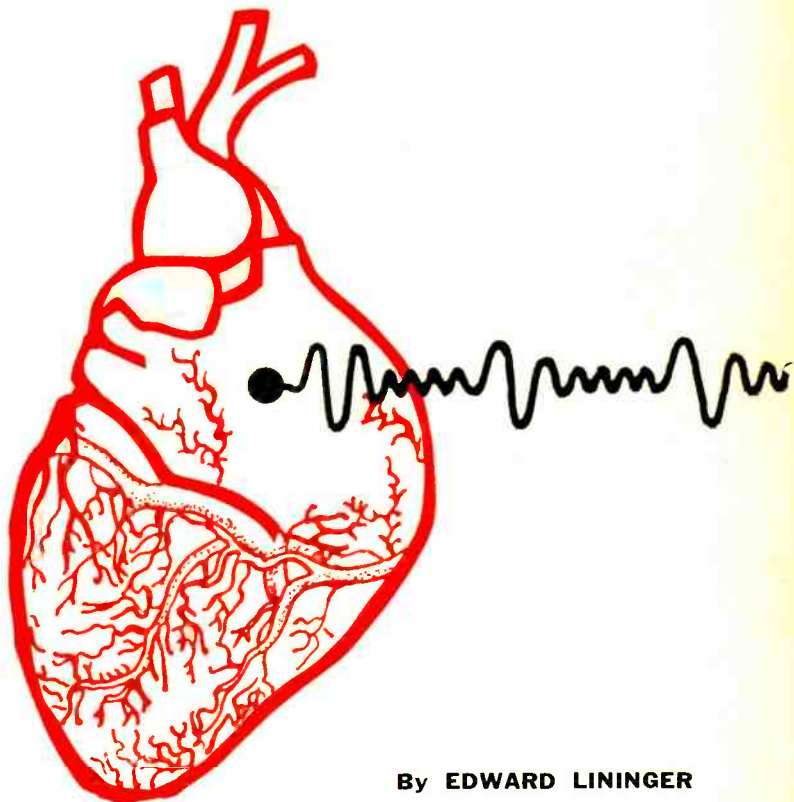**Electrical "signals" from the brain to the heart and other muscles are clearly audible on this easy-to-build four-transistor cardiac monitor**



By **EDWARD LININGER**

**E**VER THINK of the human heart as an electrically operated pump? It is—and you can prove it to yourself and your friends with this simple transistorized cardiac monitor.

Actually, not only the heart, but all muscles of the body are controlled by minute electrical signals sent by the brain to the "motor" nerves. A sample of the voltages governing the heart can be picked up from the skin with electrodes, amplified, then coupled to an indicating device such as a meter. The heart action will be displayed as peaks of voltage occurring as the heart muscles contract.

The cardiac monitor does just this. In addition, it provides audio reproduc-

tion of signals to the heart or signals to muscles of the body which are between the skin electrodes. Basically a four-transistor amplifier, the monitor is neither tricky to assemble nor does it need any alignment. It can be constructed by the average builder for \$19.00 to \$25.00.

**Construction.** Begin by laying out and drilling all holes required in both the chassis and the front panel—a 6" x 9½" section cut from an open-end aluminum chassis. Attach the front panel to the chassis by means of the nuts on gain control *R6* and jack *J1*, then install the four terminal strips and transformer *T1*.


Drill holes as necessary to mount the transistor sockets chosen: one type



Fun to use, the battery-powered heart monitor furnishes visual as well as audible heartbeat indications. It is completely safe to operate, even for children.

bands are available at medical supply houses in the types illustrated. Alternatively, electrodes can be fabricated from brass, copper, or stainless steel; suitable dimensions are about  $1\frac{1}{4}$ " x 2". Attach the electrodes to the input leads using solder or alligator clips.

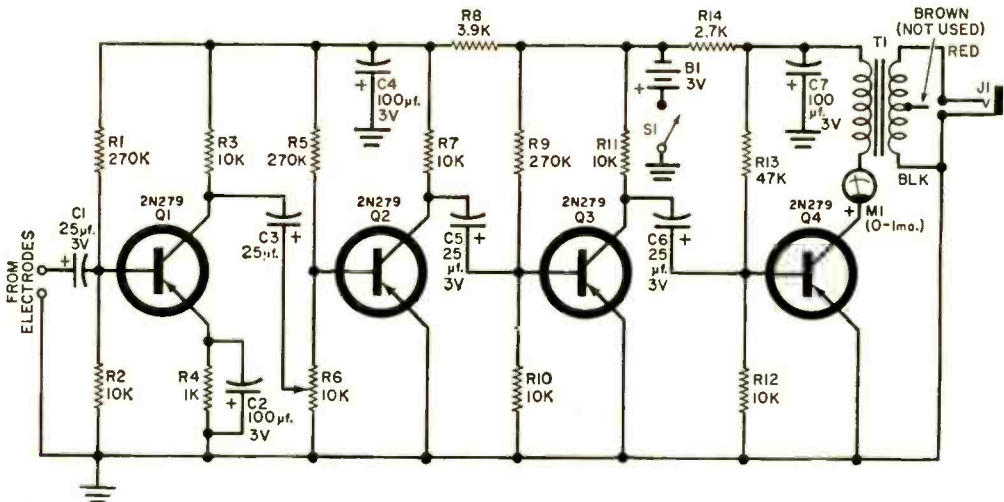After double-checking connections, trim the transistor leads and insert the transistors in their sockets, paying special attention to the red dot that identi-




Schematic diagram of cardiac monitor. Note that all four transistors are identical.

mounts in a round hole, another in a rectangular hole which can be made with a special punch or by filing a pair of pilot holes with a small file. In any case, the sockets should be installed so that the collector pins are nearest the back of the chassis.

Wire the monitor in any convenient fashion, working from the first through the fourth stages. Attach the input leads last, using No. 18 or No. 20 hookup wire made into a twisted pair about  $3\frac{1}{2}$  feet long. Standard electrodes with elastic

ties the collector in each case. With the switch off, install battery *B1*, which consists of two  $1\frac{1}{2}$ -volt flashlight cells in series. Then plug a pair of low-impedance headphones into jack *J1*. As an extra precaution, you may want to attach a metal bottom plate to the chassis to reduce interference from the a.c. line.

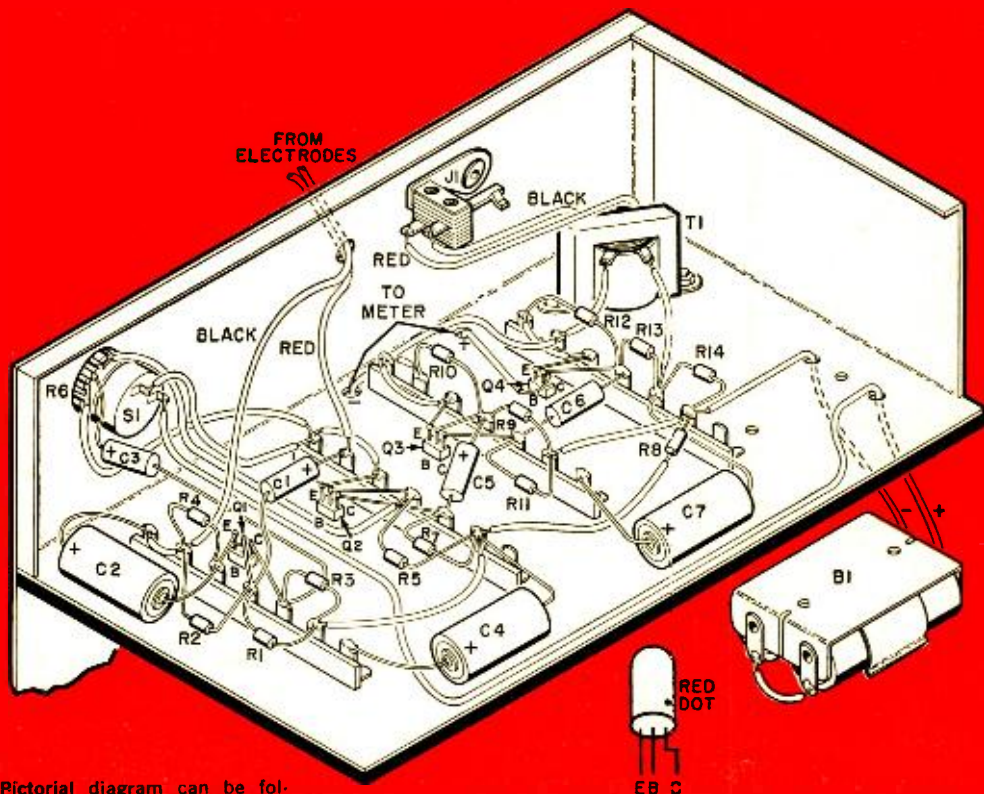**Operation.** Before the monitor can be put to use, it's necessary to prepare the "patient" for testing. The important thing is to reduce skin resistance by removing non-conductive material from



Pictorial diagram can be followed for ease in wiring. Be sure to observe polarities of battery, meter, and capacitors

## PARTS LIST

B1—3-volt battery—see text  
 C1, C2, C5, C6—25- $\mu$ f., 3-volt electrolytic capacitor  
 C3, C4, C7—100- $\mu$ f., 3-volt electrolytic capacitor  
 J1—Qp/n-circuit phone jack  
 M1—0.1 ma. d.c. meter  
 Q1, Q2, Q3, Q4—Audio frequency pnp transistor (Amperex 2N279 or equivalent)  
 R1—270,000 ohms  
 R2, R3, R7, R10, R11, R12—10,000 ohms  
 R4—1000 ohms  
 R5, R9—270,000 ohms  
 R6—10,000-ohm potentiometer with switch S1 (IRC Type Q13-116 and 76-1 switch or equivalent)  
 R8—100 ohms

R13—47,000 ohms  
 R14—2700 ohms  
 S1—S.p.s.t. switch (on R6)  
 T1—Line-to-voice coil transformer, primary, 500 ohms; secondary, 6-8 and 3.2 ohms (Stancor A-8101 or equivalent)  
 1—0 1/2" x 5" x 2" aluminum chassis (Bud AC-403 or equivalent)  
 1—6" x 9 1/2" aluminum panel—see text  
 1—Headphones, 4- to 8-ohm impedance (Lafayette M8-429 or equivalent)  
 4—Five-lug terminal strips  
 Misc.—Transistor sockets, battery holder, electrodes, wire, solder, etc.  
 All resistors 1/2 watt

## HOW IT WORKS

The amplifier of the cardiac monitor has four transistors and is powered by its own batteries. The incoming signal from the skin electrodes is capacity-coupled to the base of pnp transistor Q1. Resistor R3 provides the load for this stage; resistors R1 and R2 are bias divider. R3 is a fixed bias resistor to stabilize current against temperature variations. Capacitor C3 couples the signal into gain control R6.

Transistors Q2 and Q3 operate in a similar fashion but in Q4—the fourth stage—the collector current passes through meter M1. The meter responds to the low-frequency portion of the input signal waveform (inertia and damping of the meter needle confine its movement to the lower frequencies). The audio signal passed by output transformer T1 is fed into low-impedance headphones connected to jack J1.


its surface. This can be done by scrubbing the skin on the inside of each forearm with Ajax scouring powder or Lava soap and a solution of salt and water. (Doctors rub the skin with an electrode paste containing pumice and salts until it is slightly reddened.)

Next, wet the electrodes with salt water and attach them securely to the inner side of each forearm with elastic or adhesive tape. If a suction cup of the type illustrated is available, it should be used on the left side.

Turn on the switch and, after waiting a few seconds for voltages to stabilize, advance the gain control. To obtain proper indications, have your subject

crackling sound should be heard in the earphones accompanied by an erratic movement of the meter needle. Taking a deep breath should give the same result.

If you experience difficulty in obtaining a proper indication of the heartbeat on the meter, the trouble may be caused by 60-cycle interference from house wiring under the floor or in nearby appliances—especially fluorescent lamps. If hum is heard in the headphones, move the subject a few feet away and listen again. When a location giving a minimum hum level is found, try again for proper indication. For maximum signal from a muscle other than the heart,

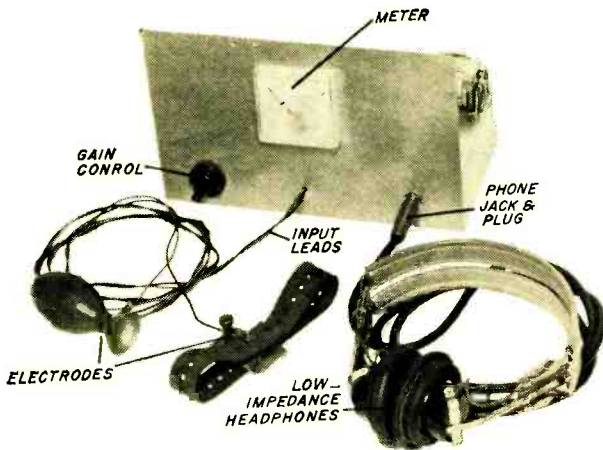

Completed monitor, shown with electrodes used by author. Suitable electrodes can be made by hand (see text), but you'll probably find it more convenient to purchase a pair from your local medical supply house.

seated and relaxed—you can be your own subject if you are careful to remain quiet after each adjustment. Observe the meter needle for a movement, advancing the gain control to full if necessary. Needle movements should follow a definite sequence—a slight rise, then an abrupt drop, a quick rise, a pause; then the same pattern all over again.

Although the a.c. signal sent by the brain to the muscles contains frequencies as high as 100 kc., naturally only the portion in the audio range can be heard in the headphones. Note that you do not hear the actual *sound* of the heartbeat—this would require a microphone. What you hear is the voltage sent to the heart muscles, greatly amplified.

To pick up signals to arm muscles, for example, try clenching your fist or pressing one arm tightly to your side. A sharp

place the electrodes so that the muscle lies between them.

**Applications.** Although the monitor opens an interesting field to experimenters by permitting study of electrical signals in the human or animal body, the basic design also has plenty of extremely practical applications. One very obvious use is in determining if heart action is present in victims of fires, drowning, electrical shock, and other accidents. In the hospital or home, an improved version could be used as a portable device to supplement the electrocardiograph by allowing continuous monitoring of a patient's heart action by medical personnel. More professional models based on this same design could be brought into the operating room to observe heart strength and frequency during an operation.



# HEADS...OR TAILS?

**Inexpensive**

**"no-cheat"**

**device**

**will**

**flip coins**

**electronically**

**By HAROLD P. STRAND**

**H**ERE'S an interesting device which could be a barrel of fun at your next party. A simple magnetic coin tosser, it can form the basis for an entertaining game of chance in which players bet on the way a coin will fall when it lands. As part of some other game, it can be used to decide which player starts off, or if a particular player should be allowed to continue his "turn" as long as "heads" keeps coming up for each play.

In fact, there is virtually no end to the "game" applications for this inexpensive gadget. And there's no chance to cheat with it, as there is when someone flips a coin and places it on the back of his own hand.

The device consists of an a.c. solenoid magnet which operates directly from the a.c. line, eliminating the need for batteries or a step-down transformer. The solenoid is fixed to the top of a utility box; a hole drilled in the top of the box allows a steel plunger to come through, the plunger being operated by the action of the solenoid.

A push-button switch of the momentary-contact type is mounted on top of





the box and serves to connect the a.c. line to the solenoid windings. When the circuit is closed by the switch, the steel rod plunger pulls up quickly with considerable force. If a quarter has been placed in the recess over the hole in the box, it will be thrown into the air for a distance of about two feet or more.



The coin is turned over many times in its flight upward due to the fact that the plunger does not strike it exactly in the center. The hole in the coin base is bored off center so that the plunger tends to flip the coin over rather than simply push it straight upward.

the inside top surface with 4-40 screws and two other holes to attach the small block of 1/4" birch plywood, which acts as the coin base, to the box with flat-head 4-40 screws and nuts. Finally, bore holes in one side of the box for the rubber line-cord grommet and the screw which holds the terminal strip.

The core for the solenoid is made from a 2" length of brass tubing; the two ends are cut from 1/8" plastic and, once on the tubing, form a spool (or bobbin) upon which the coil is wound. (See Detail 2.) In the author's case, the end pieces were cut out on a jig saw and dressed round and smooth on a sanding disc; however, they can be virtually any shape—even square, if you wish. A center hole is drilled in each piece just large enough to permit a tight "press fit" on the tubing.

After the end discs have been pressed completely over the ends of the tubing, lightly peen the tubing with a small hammer to make a burr at each end which will prevent the discs from being pushed off by the winding.

Next, drill and tap two 4-40 holes

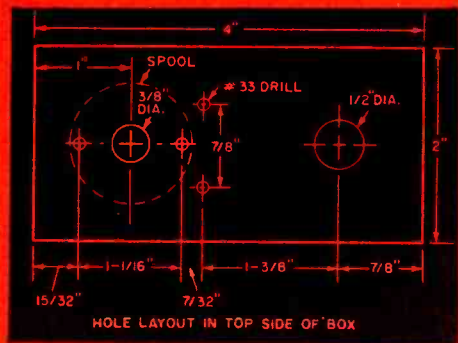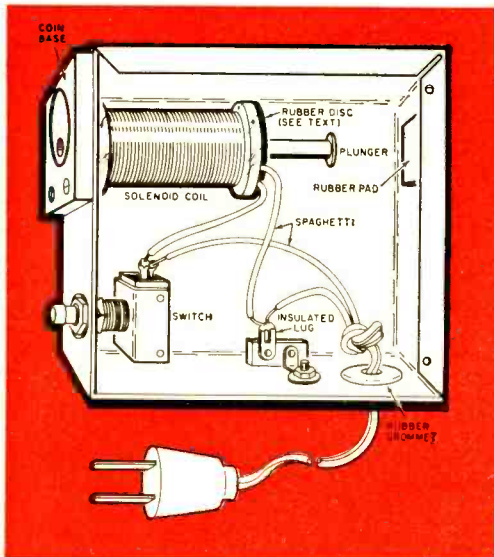

Detail 1.

**Preparing the Parts.** Begin construction by boring a 3/8" hole in the top of the utility box to clear the plunger and another 1/2" hole for the switch (see Detail 1 for size and location of holes). Drill two small holes for attaching the plastic end of the coil bobbin to

in one end of the spool to line up with those bored in the box for the screws that will hold the solenoid in place. Two holes are then drilled in the other spool end for the "start" and "finish" of the wire, as shown in Detail 2. Wrap a layer of paper masking tape around the

brass tubing for insulation, bringing the tape all the way to the ends. You are now ready to wind the coil.

**Winding the Coil.** The winding can be done best with a winding machine or lathe, but the coil can also be wound in a hand-winding jig. However, since there are a large number of turns required, hand-winding would be quite tedious.



Use No. 30 or No. 31 Formvar wire for the coil and slip a piece of spaghetti over the "start" end of the wire, forcing about  $\frac{1}{8}$ " of the spaghetti through the "start" hole in the plastic end. Wind the coil as uniformly and smoothly as possible; the total number of turns needed is about 3600—the exact number is not too important as long as you approximate this figure. Feed the "finish" end out the hole drilled near the edge of the disc, and use another piece of spaghetti on the wire, again bringing about  $\frac{1}{8}$ " of the spaghetti through the hole.

**Assembling the Tosser.** A disc of rubber, cut from an old inner tube, should be made up with a center hole and two slots to clear the leads. This is Pliobond-cemented to the lower end of the


## BILL OF MATERIALS

- 1—4" x 4" x 2" utility cabinet (Bud AU-1083 or equivalent)
- 1—S.p.s.t. momentary push-button switch, normally open (Hart and Hegeman 3391GL or equivalent)
- 1—2" length of brass tubing, 5/16" OD, 1/4" ID
- 1—2 1/2" length of soft iron or steel rod, 0.216" in diameter
- 1—Washer, 1/2" OD
- 1—1 1/4" x 2 1/2" x 1/8" piece of Lucite plastic (approx.)
- 1—2 1/8" x 1 1/2" x 1/4" piece of birch plywood or other hardwood stock
- 1—1-lb. spool = 30 Formvar magnet wire
- Misc.—Line cord with plug, one-lug terminal strip, scrap rubber from old inner tube, plastic spaghetti (about 1/16" OD), 1/16"-thick felt, paper masking tape, screws and nuts, etc.

Detail 3.

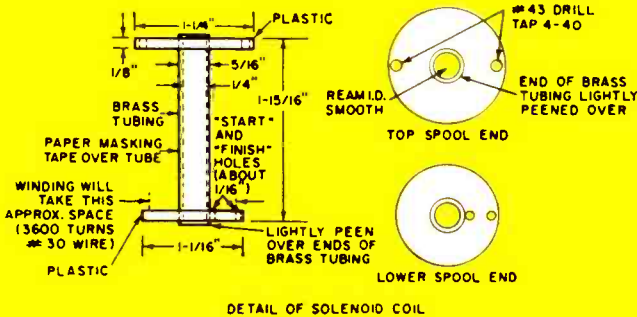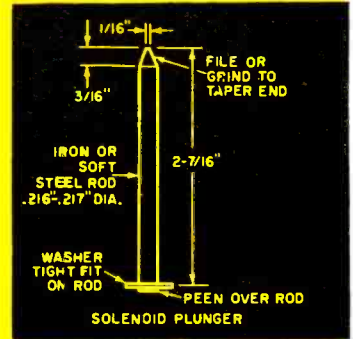

Detail 2.

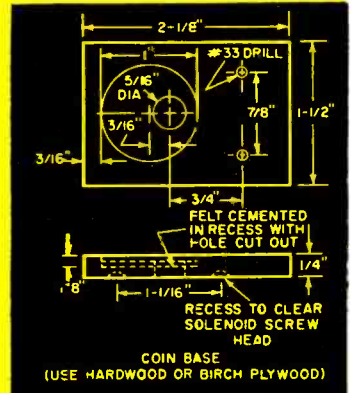

Detail 4.


spool to act as a bumper for the washer stop of the plunger.

The plunger consists of a piece of soft iron rod stock around 0.126" in diameter and 2 1/2" long. (See Detail 3.) A washer is reamed out to make a tight fit over  
(Continued on page 111)



# TRANSISTORIZED METRONOME

Portable timekeeper works while you play

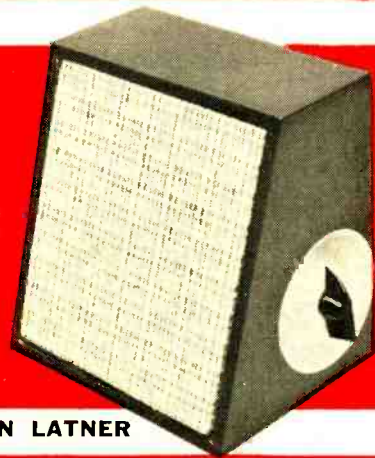

By NORMAN LATNER

ALMOST anyone who plays a musical instrument has at least an occasional need for a metronome. Commercial units are usually costly, but this reliable transistorized metronome is inexpensive enough to be practical for even the most casual user.

Completely portable, the instrument is powered by a small, but long-lasting, 9-volt battery. The tempo range (about 40-215 beats per minute) and sound are comparable to those of a commercial mechanical unit. Three low-cost transistors and a minimum of other components are used in the circuit.

**Construction.** The loudspeaker baffle serves a dual purpose—it also houses the electronic section of the unit. Mount the speaker in the baffle, then proceed with the wiring of the electronic section.


A 2-7/16" x 3 3/8" piece of perforated board is used for the chassis. The tempo control potentiometer (*R1*) is secured to the chassis by means of an "L" bracket made from a 1" x 2 1/2" piece of sheet metal. Make a 90° bend along the short dimension 1/2" from one end, then drill a 3/8" hole for the potentiometer shaft 5/8" from the other end. (See pictorial diagram.) Now bolt the bracket to the chassis and temporarily mount *R1*.

The transistor sockets are mounted by inserting their terminals through holes in the perforated board—bend the terminals slightly to hold the sockets in. Re-


sistors *R2*, *R3*, and *R4*, and capacitor *C1* are mounted in the same way; leave one lead from *R3* at the top of the board, since it will be soldered to the potentiometer. Use a strip of plastic tape or a commercially available clip to hold the battery in place.

Now you're ready to complete the wiring. The battery connections may be soldered, or you can use a set of commercially available snap terminals—but make sure you observe the proper polarity. A pair of leads should be provided which can be connected to the loudspeaker when you are ready to mount the chassis in the baffle.

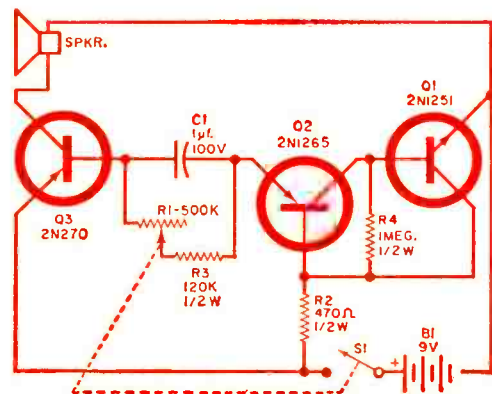Drill a hole in the baffle large enough for *R1*'s shaft. If the threaded portion of the shaft is too short to pass through the bracket and the baffle, you'll have to





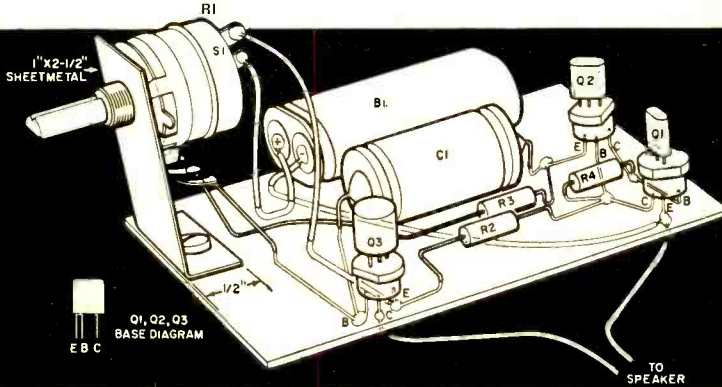

Lightweight lines in pictorial diagram indicate leads running under board. Mounting nut for potentiometer R1 also secures chassis to side of baffle.

countersink the hole. Make the countersunk area large enough in diameter to accommodate the potentiometer mounting nut and the tool which will be used to tighten it. Finally, the potentiometer-chassis assembly is mounted and the speaker connected.

**Calibration.** Make a paper dial for potentiometer R1's pointer knob and rubber-cement it in place. Then turn on the metronome and allow about 30 seconds for it to stabilize. A clock or watch with a second hand is used to determine the number of beats per minute at appropriate settings of R1, and the dial is marked accordingly.

After you've finished the calibration, add a final touch to the instrument by putting a protective coat of clear nail polish or Krylon spray on the dial. —30—


### HOW IT WORKS

Transistors Q1 and Q2, *npn* and *pnp* units respectively, are arranged to form a composite *pnp* transistor with a common base current gain greater than one. This composite transistor acts as a switch which closes when the voltage on C1 is high enough. Capacitor C1 charges through R1, R3 and the base resistance of Q3. The "charge-discharge" pattern is a sawtooth wave and is fed to Q3, which acts as a common emitter stage. The speaker serves as the load resistance.

Almost any *pnp* transistor with a common emitter current gain of over 20 and a collector voltage rating of over 10 volts will do for Q2. Any *npn* unit with a current gain of over 45 and a voltage rating of over 10 can be used for Q1. Transistor Q3 can be almost any *pnp* transistor, though some units will give lower sound output. If transistor substitution causes a change in the tempo range, the value of R3 should be raised or lowered to correct the condition; a change of the order of 10,000 or 20,000 ohms should be sufficient.
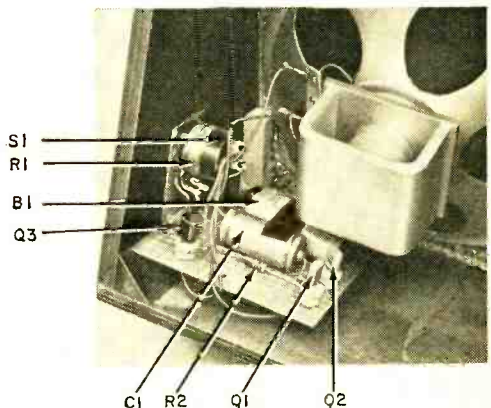
### PARTS LIST

- B1—9-volt battery (Eveready 216 or equivalent)
- C1—1- $\mu$ f., 100-volt paper capacitor (Elmenco 1DP-5-105 or equivalent)
- Q1—2N1251 transistor
- Q2—2N1265 transistor } see "How It Works"
- Q3—2N270 transistor
- R1—500,000-ohm potentiometer (with S1)
- R2—470-ohm, 1/2-watt resistor
- R3—120,000-ohm, 1/2-watt resistor
- R4—1-megohm, 1/2-watt resistor
- S1—S.p.s.t. switch
- Spkr.—6" PM loudspeaker (Lafayette SK27 or equivalent)
- 1—Speaker baffle
- 1—2 7/16" x 3 3/8" perforated board (Lafayette MS304 or equivalent)
- Misc.—Transistor sockets, knob, sheet metal, hardware, etc.



# TUNER KITS



Citation III



Model LT-10

*TOP: The Harman-Kardon Citation III FM tuner is more complex to assemble than the Scott kit, and more professional in appearance and performance. Since it costs \$229.95 factory-wired, you save \$80.00 by building your own.*

*BOTTOM: The H. H. Scott LT-10 FM tuner kit (\$89.95) is simple and fool-proof to assemble. Scott has manufactured FM tuners of fine quality for many years—the LT-10 is no exception.*

## COME OF AGE

**Of the eight FM tuner kits now on the market, the Harman-Kardon and Scott units represent new departures in both circuitry and packaging**

**TUNER KITS** for quality FM reception have been on the market for several years. Dynaco, EICO, Heath, Allied Radio (Knight), Lafayette and PACO are some of the manufacturers that produce such kits. But now, thanks to Harman-Kardon and H. H. Scott, there is a sudden, explosive rebirth of interest in building FM tuners.

This interest centers around two ingredients—true hi-fi performance and foolproof assembly. The Scott LT-10 tuner is a medium-priced kit that could

Under the Citation III chassis (at right, above) are the connections surrounding the Nuvistor r.f. stage; coil assembly is supplied partially pre-wired. The r.f. assembly of the LT-10 (right, center) is premounted and preassembled by the manufacturer; blank space on chassis is for a multiplex converter.




satisfy nine out of ten hi-fi enthusiasts. The Harman-Kardon "Citation III" is about the best your kit money can buy—it justifiably deserves the title "professional equipment."


**Citation III.** That the Citation III can be safely assembled from a kit represents an amazing piece of ingenuity on the part of the Harman-Kardon people. From a circuit viewpoint, the unit is as up-to-date as tomorrow's newspaper.

In the first r.f. stage, to maximize tuner sensitivity, is an RCA 6CW4 Nuvistor—the subminiature vacuum tube originally developed to improve weak-signal TV reception. This r.f. stage is followed by a second r.f. stage connected in a grounded-grid circuit. Between them, these r.f. stages make the Citation III one of the two or three most sensitive tuners ever developed.

After the r.f. stages come the converter stage and three stages of wideband i.f. Only one of the r.f. stages is wired by the constructor; the other five stages are all pre-assembled by the manufacturer—the constructor sim-

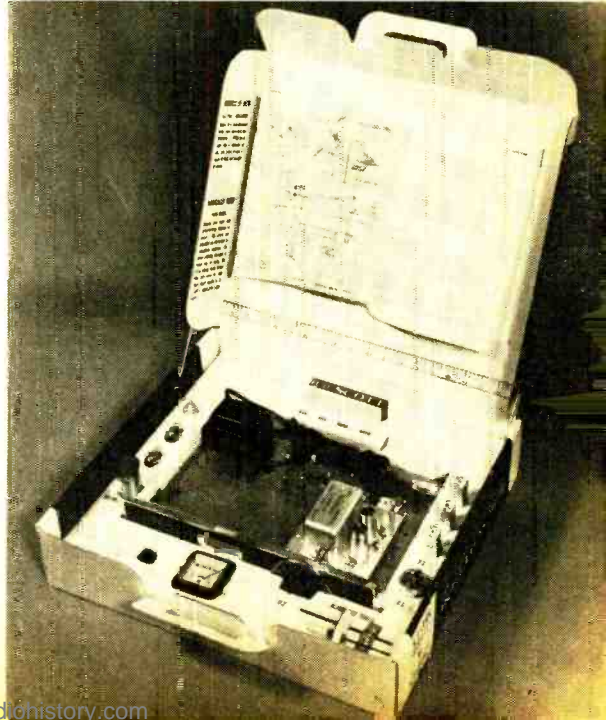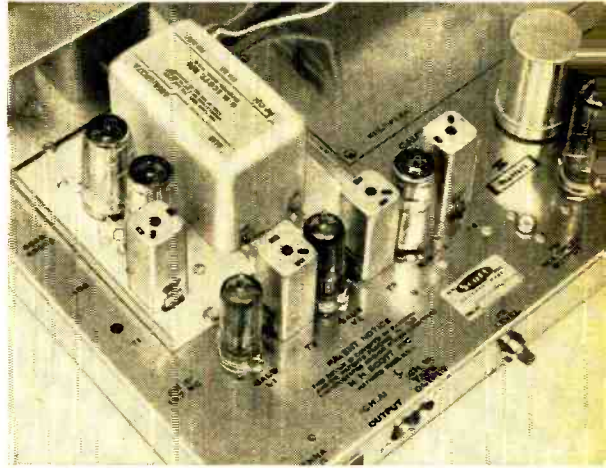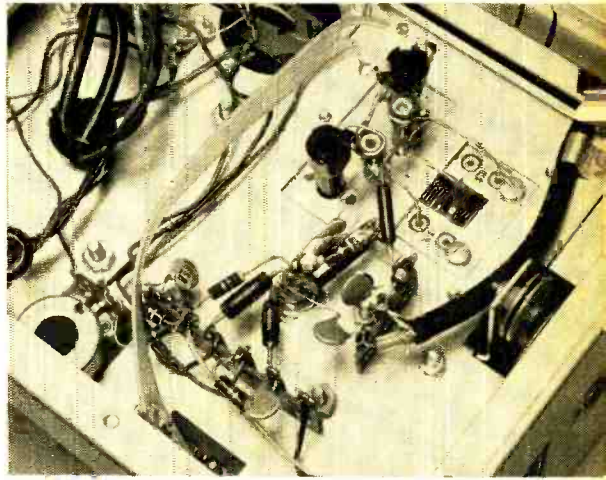Both tuner kits are marvels of packaging. Miscellaneous components for the Citation III are attached to a large card and bagged, while the Scott kit is boxed so that the carton itself can be used as a workbench.



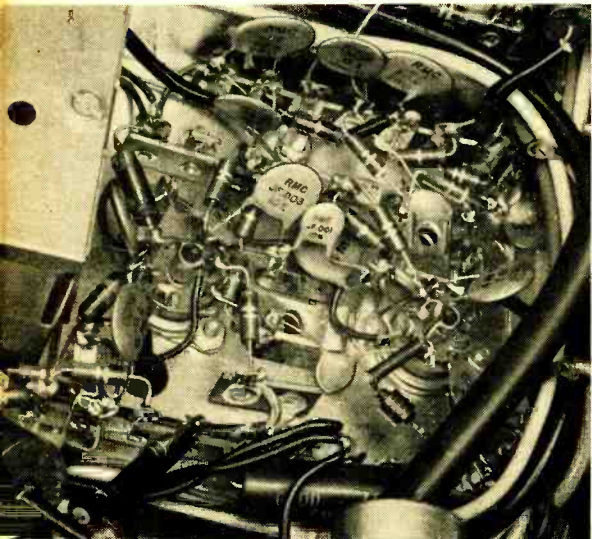

ply solders in the power connections and the input and output cables. Preassembly eliminates what could be a major headache in aligning as complex a tuner as the Citation III.

Two gated-beam tubes are fed the FM signal from the i.f. strip and are designed to act as cascade limiters. A conventional discriminator using crystal diodes follows the limiting stages. The tuner ends up with four triode stages (interchannel muting, a cathode follower after the discriminator, and dual-triode audio amplification).

If there are no wiring errors or omissions in the assembly of the Citation III, you can easily align this tuner in about five minutes—there are only *six steps!* The i.f. strip has been aligned by the manufacturer and is never touched. The Nuvistor r.f. stage is tuned up and the second limiter and detector are easily brought to balance using the two meters on the front panel.

**Scott LT-10.** When compared to the Citation III, the Scott LT-10 FM tuner kit is sheer, unadulterated simplicity. Circuit-wise, it is a superb example of how the hi-fi fan can readily obtain top-quality FM tuner performance with a minimum number of tubes. (There are only six tubes in the LT-10, including power rectifier; in the Citation III there are ten, not including rectifier.)

The LT-10 starts off with a cascade r.f. stage—a long-time favorite for sen-

Expect to spend nearly three hours wiring up the Citation III around the limiter and discriminator stages. Thirty-four resistors and capacitors are visible—go ahead, count 'em.

sitivity, low noise generation, and good weak-signal amplification. The converter stage is followed by two i.f. stages, a limiter and a ratio detector using crystal diodes. Audio output connections are made through a triode stage.

There are only three items on the front panel of the Scott LT-10—"on-off" switch, tuning meter, and tuning dial. On the top, or to the rear of the chassis, are controls for minimizing a.c. hum pickup, level or volume adjustment from the tuner, and a large blank space for a multiplex converter.

Unlike the procedure with the Citation III, the constructor aligns the i.f. stages in the LT-10. At first, the novice constructor might want to steer clear of this step and consider buying only a pre-aligned tuner. However, the wideband circuitry of the Scott, plus the amazingly easy tune-up process, makes it possible to get the alignment step down pat. You can spend more time reading the four pages of simplified instructions than it takes to do the complete alignment—which is not a bad idea, anyway. Once through the tune-up process is more than enough to get the tuner on the "nose."

**Summing Up.** You will need about eight hours to wire a Scott LT-10 and at least 12½ hours to wire a Harman-Kardon Citation III. For the price difference between the two kits, you buy more versatility (interstation muting, local-distant r.f. sensitivity, carrier centering meter, etc.) in the Citation. Both produce hi-fi sound with minimum distortion, and both are more than respectably sensitive—the Citation III a hair better in our opinion.

Each of these kits has many more features than can be described in the limited space of this article. We suggest that you get descriptive literature before making a choice (and don't forget the other tuner kit manufacturers—they may have something even more to your liking). But, no matter what you finally choose—FM tuner kits have "come of age."

—30—



# INTERPRETING TV TEST PATTERNS

***Knowing what to look for in test patterns  
will help you adjust your TV set for a better picture***

**By J. K. LOCKE**

**H**AVE your favorite TV stars appeared somewhat flat-headed lately? Do program titles run off one side of your TV screen so that you lose the first or last letter? Or perhaps your picture seems a little fuzzy, with less "snap" than it had when the set was new?

Whatever the difficulty, the TV test pattern transmitted by your local television station can help put you on the road to first-rate reception. If your set is simply out of adjustment, the pattern will help you readjust all front and back panel controls quickly, easily, and accurately. To be sure, you won't be able to clear up faulty interlacing, poor video frequency response, or some other technical defect with the controls. But still, the test pattern will tell you if troubles

of certain kinds are developing, and warn you when service is necessary.

## **MEET THE TEST PATTERN**

Before you can make any adjustments or even determine whether your set needs servicing, you must understand what each part of the TV test pattern means. Every component of the pattern—the various circles, rings, gray areas, wedges, and some tiny dots you may not have even noticed—can tell you something.

**Aspect ratio** is the ratio of the picture's width to its height. In television, the standard aspect ratio is 4 to 3. For example, a picture 20" wide should be 15" high.

The two large test pattern circles (see Fig. 1) help you set the aspect ratio

accurately. When the black circle just touches the top and bottom edges of the frame and the white circle just touches the sides, the aspect ratio has been set properly.

**Linearity** is simply the measure of whether the scanning circuits are properly adjusted in the set. By way of explanation, the electron beam which scampers back and forth "painting" pictures on the tube travels at one rate of speed from top to bottom and at another from side to side. Each of these scanning speeds should be "even."

If the scanning picks up or slows down as it goes from top to bottom, the picture "bunches" near the top of the screen and stretches out at the bottom, or vice versa. This results in poor *vertical* linearity.

Poor *horizontal* linearity shows up when the speed of the sweep changes as it goes from one side of the screen to the other. Let's say, for example, that the sweep starts across at very high speed, then begins to slow down as it approaches the right edge of the screen. In this case, everything on the left edge would appear to be stretched out, and all objects on the right would be bunched.

Both horizontal and vertical linearity can be checked by a quick look at the test pattern. If both the white and black circles appear round to your eye, then the linearity in both directions is good. If the circles look misshapen, on the other hand, linearity is poor. Both horizontal wedges should be the same length, and both vertical wedges should be the same length (see A and B in Fig. 2). If either the horizontal or vertical

wedges don't form a perfect pair, there's something wrong.

**Brightness and contrast** are easily judged by looking at the black dot in the center of the pattern (C in Fig. 2) and the four concentric circles around it (D). The dot should be a deep black and the outer circle a crisp white. The three circles in between should be evenly graduated shades of gray. Both brightness and contrast affect the overall balance, so both controls are used to get the black-and-white scale adjusted properly.

**Focus**—or lack of it—can be checked by looking at the narrow ends of the converging wedges. The lines should not blur, but you may not be able to get a focus so perfect that all of the lines are sharp all the way to the center. (This may be caused by poor resolution, which we'll talk about later.) You should, however, adjust the picture until the lines are as clear as you can get them. Don't be alarmed if the focus does not seem to be equally sharp over the entire picture. Television picture tubes, because of their construction, cannot be focused perfectly over their entire surfaces.

**Resolution** is a measure of the fineness of detail your set can reproduce. Let's say, for example, that a picture pattern of 300 horizontal lines is transmitted by your TV station. You can clearly see and—if you want to—actually count each one from the top to the bottom of your screen. Suppose, however, that the station increases the number and transmits a pattern of 325 lines. Now the lines become so fine on your set that they blur into a gray pattern, and you can no longer see the individual lines. Your



Fig. 1. Typical test pattern transmitted by television stations. Note parallel edges, square corners.

ASPECT RATIO CIRCLES

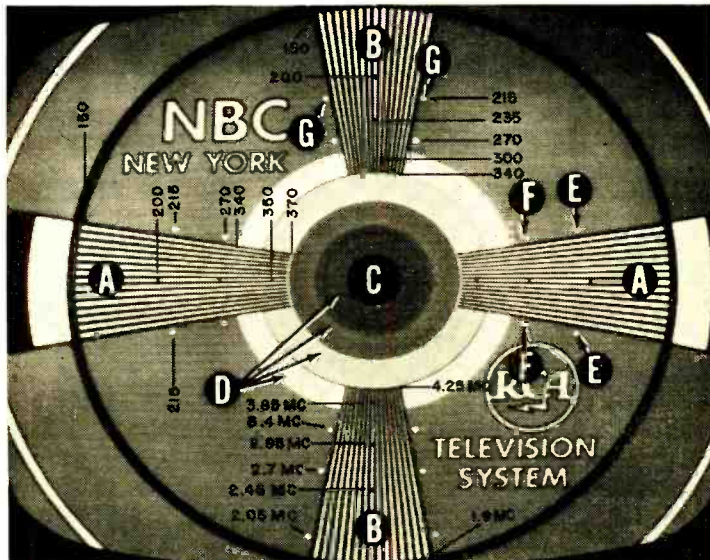


Fig. 2. This is how the test pattern should look on your set when it is properly adjusted. The corners are rounded, and part of the white circle is missing. See text for an explanation of letters and numbers.

set's maximum *vertical* resolution, then, is about 300 lines. *Horizontal* resolution works the same way; it is simply a measure of how many vertical lines you can count from one side of the screen to the other.

You can check the vertical resolution by looking closely at the horizontal wedges of the test pattern (A in Fig. 2). The tiny black and white dots serve as markers. If you can clearly see the individual white and black lines of the pattern at the outer edge, but the lines blur around the first set of white dots (E), then your set has a resolving power of only 215 lines. If, on the other hand, you can see separate lines all the way in to the next set of dots (F), your set is resolving 270 lines.

The horizontal resolution can be measured by looking at the vertical wedges (B in Fig. 2). Again, the dots are the guide—they represent not only resolving power but video frequency response as well. This is a useful measure, because horizontal resolving power is determined by the set's video frequency response. The first set of white dots nearest the outer circle on the top wedge (G in Fig. 2) represents a video frequency response flat to 2.7 mc. This is equivalent to 215-line resolution. (Incidentally, the test pattern used by TV stations for aligning their own equipment—see Fig. 3—shows frequency response to 7 mc., which rep-

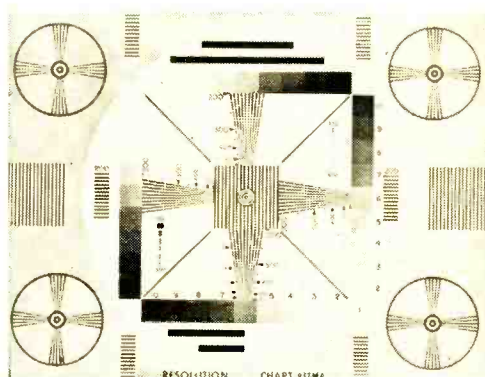


Fig. 3.

resents a resolving power of about 550 lines.)

The test pattern on the set we used for some of these pictures is shown in Fig. 8. As you can see, the vertical wedges blur pretty badly at about the 2.7-mc. dots. This means that the set has video circuits which pass a 2.7-mc. signal, but not much more. The vertical resolution is good down to about 370 lines, but since the wedge is beginning to blur at the center, it is obvious it would not resolve a much finer pattern.

The test pattern in Fig. 8 is typical of that found on many sets now on the market; in spite of its fairly limited response, it has a pretty good picture. Of course, the picture will not have the

crispness of that produced by a set with better resolution. The pattern of the set represented in Fig. 2 shows exceptionally fine resolution; note that all wedges are clear and sharp right to the very center, and contrast this with the pattern of Fig. 8.

It's a good idea to check and write down the vertical and horizontal resolution of your set. Then, from time to time, you can run another check to make sure they have not deteriorated. If they have, it might be a sign that your set needs a general overhaul, including realignment of its video circuits.

Incidentally, there is very little standardization of test patterns, so the dots on your screen may or may not represent the same resolution and frequency response shown here. If in doubt, ask your local station what figures the dots on their pattern represent.

### WHEN TO MAKE ADJUSTMENTS

Almost any set which hasn't been adjusted for some time can stand touching up for a number of reasons. Sometimes sets are accidentally thrown off course by cleaning. Sometimes, too, children may tamper with controls. But any set, regardless of its environment, needs occasional adjustment. Parts age, and aging causes changes in brightness, contrast, and even the size and shape of the picture. So for best televiewing, it's a good idea to check out the adjustments on your set periodically.

Since all sets don't have exactly the same controls, you may not be able to find one or more of those we mention. However, if your set lacks a particular control, it probably doesn't need it. New circuits in use in some sets make some of the older standard controls unnecessary.

Although all sets have most of the controls listed here, some have only a few within easy reach; you may have to take the back off to get at the others. One of the sets we used in preparing this article, for example, had the vertical size and linearity and horizontal size controls inside.

Here are some general rules and suggestions to follow in adjusting your set.

1. Most TV sets have a power interlock; when you remove the back, you automatically shut the set off. To make

adjustments with the back removed, you'll have to use a special cord, called a "cheater," which TV men have developed for service work. But remember, *the interlock is there to protect you against high voltages.*

2. Look at the test pattern carefully before you remove the back of the set—the controls inside may not need adjusting.

3. Unless you know exactly what you are doing, don't try to adjust any control you find inside the cabinet other than those described here.

4. Let the set warm up for 15 to 30 minutes before you begin your adjustments. It takes that long for all parts to heat up to operating temperature.

5. A large mirror is helpful if you have one. You can reach around most sets and adjust them while watching the screen directly, but it's a lot easier to stand behind the set and use a mirror to see the picture.

6. All of the troubles we'll talk about can be caused by circuit breakdowns of one kind or another. If the procedure described won't cure the trouble, your set may need repairing rather than adjusting. If this is the case, suspect tubes first. A quick check at the local hardware or drug store do-it-yourself tube tester may uncover the trouble, and you won't need to call in the serviceman. If you do replace a tube, the set may need readjusting as a result.

### HOW TO MAKE ADJUSTMENTS

Now, let's wrap it all up by going through the various adjustment steps one by one.

**Brightness.** Is your screen too bright, as in Fig. 4, or too dark (Fig. 5)? This is one of the simplest adjustments to make. You'll find the "brightness" control on the back panel of most sets. Adjust it until the picture is bright but the black areas are not washed out. The dot in the center and its four surrounding rings should shade evenly from black to white as shown in Fig. 6.

**Contrast.** The contrast control also helps to determine the general appearance of the picture. It is usually on the front of the set. Use this control in combination with the brightness control for best results, adjusting one, then the other, for the best picture. If the picture is





Fig. 4.

too contrasty, the darker shades of gray will merge into black. If there is not enough contrast, as in Fig. 7, the whole picture will appear in shades of muddy gray.

**Horizontal Size and Position.** If the picture doesn't go out to both edges of the screen, or if the reverse is true and you feel you're losing too much picture off the sides (as in Fig. 8) —we've lost the white circle completely here—the horizontal size control ("width" on some sets) will quickly remedy the situation. Turn the horizontal size control until you see blank screen on both sides of the picture. Adjust the horizontal position control until there is exactly the same amount of blank space on each side. Now slowly turn the horizontal size until the white circle just fills the screen from edge to edge. (See Fig. 1.)

**Vertical Size and Linearity.** The vertical size ("height" on some sets) and linearity controls are used together. They interact—when you adjust one, it affects the other (Figs. 9 and 10). So go back and forth between the two until the test

*(Continued on page 110)*

Fig. 8.

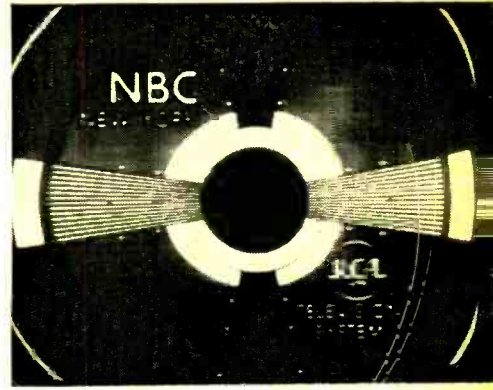


Fig. 5.




Fig. 6.



Fig. 7.



Fig. 9.

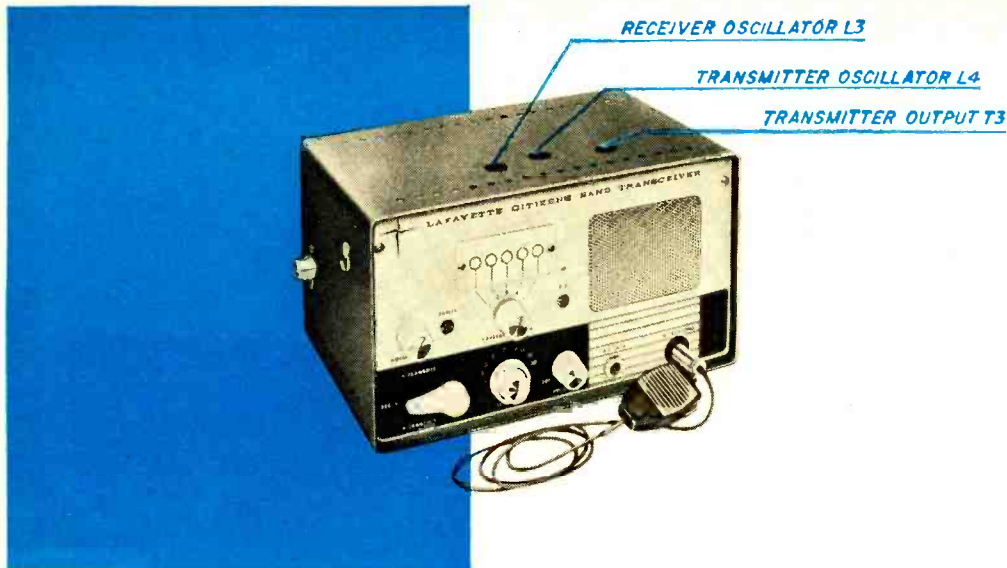

# CB RIG GOES "HAM"

**Hints on converting a CB transceiver  
for operation in the 10-meter amateur band**

By **EDWARD M. NOLL**, W3FOJ

**I**F YOU'RE one of the CB'ers who feels he's ready to step up to the more sophisticated world of the ham, you'll be happy to learn that there's no need to trade in your present CB transceiver. Assuming your transceiver is a typical moderately priced unit and incorporates a tunable receiver, it probably has all the essentials for 10-meter operation. The conversion described here involves a Lafayette HE-15A transceiver, but other rigs can be handled in a similar fashion.

Aside from retuning the final, you'll have to change only two circuits. One is the crystal oscillator in the transmitter; the other is the bandspread section of the local oscillator in the receiver. (See Fig. 1.) Incidentally, the changes outlined here are not irrevocable—should you ever develop nostalgic feelings for your old CB rig, you can simply reconvert the transceiver.


In most cases, the transmitter section

of the transceiver is easiest to change. Often, it is merely a matter of inserting a 10-meter crystal and retuning the oscillator and final. Depending on the circuit, it may also be necessary to change the value of a component slightly, or modify the crystal oscillator circuit to permit fast-starting with the available overtone crystals.

Modifying the receiver section will require peaking the resonant circuits of the r.f. amplifier and mixer, and setting the local oscillator to a higher frequency. This last step is important, since it is desirable that the receiver be capable of tuning over the entire 10-meter band, or at least a reasonably large segment of it.

**Transmitter Section.** It was found that most 10-meter crystals (third overtone type) started easily when the plate tank circuit of the crystal oscillator was retuned. If the oscillator is sluggish, however, some additional feedback should be incorporated. With the Lafayette HE-


Fig. 1. Two circuits in the transceiver must be changed to shift operation from the Citizens Band into 10-meter ham frequencies. Modifications to local oscillator in receiver (circuit shown in color at far right) appear in Fig. 3, those to crystal oscillator in transmitter (circuit in color, below, right) are shown in Fig. 2. Also, the transmitter final must be retuned and the CB whip antenna shortened (see Fig. 4) as explained in the text.

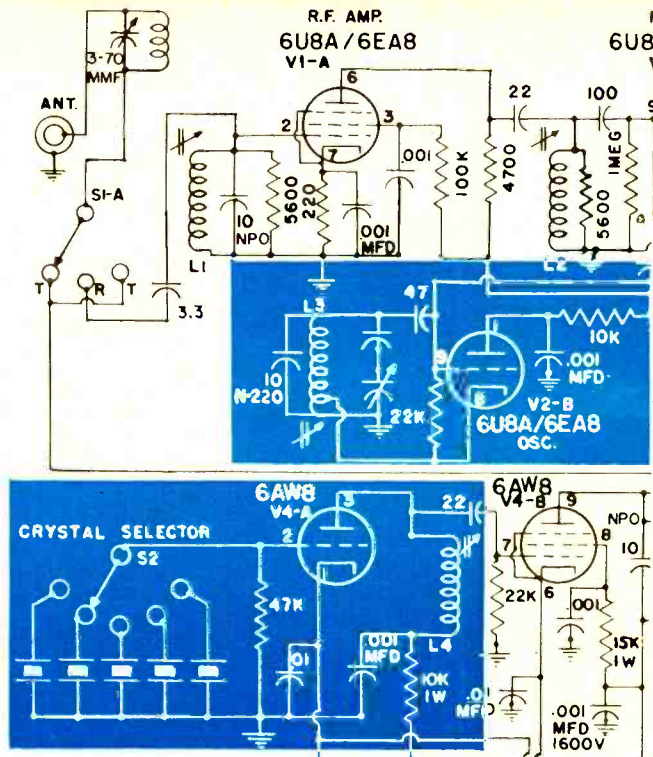

15A, this was accomplished by rewiring one of the positions of the crystal selector switch for use as a Jones-type overtone crystal oscillator (see Fig. 2).

Specifically, a 100- $\mu$ f. capacitor was inserted in series with the 0.001- $\mu$ f. capacitor which connects the bottom of tank coil  $L_4$  to ground. Then the common side of one of the crystal socket terminals was removed from ground and connected to the junction of the two capacitors. Sluggish crystals inserted into this section of the socket started without trouble in every case.


Fig. 2.

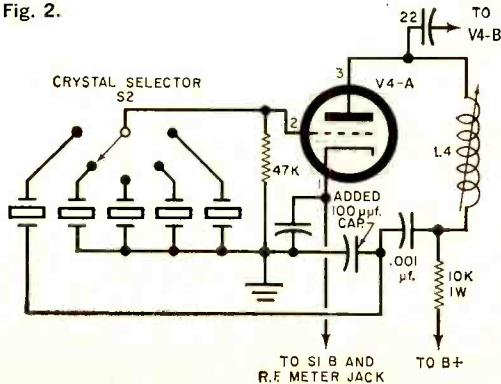

No circuit changes were made in the r.f. power amplifier. However, to facilitate retuning the two transmitter stages without removing the chassis, two holes were drilled in the top of the case; a third hole permits retuning local oscillator coil  $L_3$  in the receiver section (see photo). By simply inserting a long insulated screwdriver through the two holes, you can adjust for peak performance at any given frequency. If you would like greater tuning precision than that offered by the NE-2 neon bulb, plug a 0-50 ma. meter into the r.f. jack.

**Receiver Section.** Making the receiver section operate on the 10-meter band is fairly simple—retuning the local oscillator coil ( $L_3$ ) pulls the receiver into the 10-meter spectrum. However, the frequency range over which the local oscillator can be tuned is only a fractional part of a megacycle for any particular setting of the tuning slug in  $L_3$ . This may be acceptable if you anticipate working a limited section of the band, but circuit changes are in order if you want to utilize the full 10-meter spectrum.

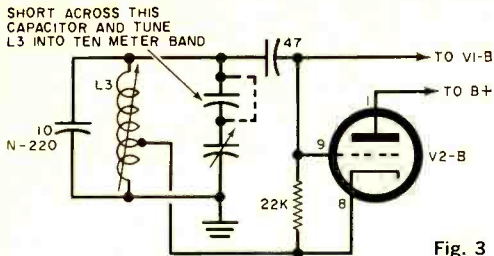The receiver section of the Lafayette transceiver was made to provide almost



ideal coverage of the 10-meter band by shorting out the small capacitor between the top of the tuning capacitor and the top of  $L3$  (see Fig. 3). There is no need to remove this capacitor and reconnect the leads—simply jumper across it. Then, if desired, CB operation can be restored by removing the jumper.

Maximum sensitivity can be obtained by slight retuning of the r.f. amplifier and mixer grid circuits (coils  $L1$  and  $L2$ , respectively). Note that  $L1$  must be tuned with the chassis removed because of its location.

**Antenna Shortening.** For top performance on the 10-meter band, your present CB antenna must be shortened. You can cut the antenna for either the specified frequency of operation or for the center of the 10-meter band to accommodate operation at various frequencies—use the following formula to determine the length of a quarter-wave antenna:


$$\frac{\lambda}{4} = \frac{2865}{f}$$

where  $\lambda$  (lambda) is the wavelength in inches and  $f$  is the frequency in megacycles.

If you're calculating the overall length of a quarter-wave whip antenna, be sure to measure between the point at which the transmission line is attached and the tip of the whip section, as shown in Fig. 4.

**Crystal Frequency.** Before selecting a crystal frequency, it's a good idea to monitor the 10-meter band in your vicinity—there are probably many fine local rag-chewers and radio clubs using this band. Many of these stations will have a dual location: one at home and another in a mobile unit operating at the same frequency.

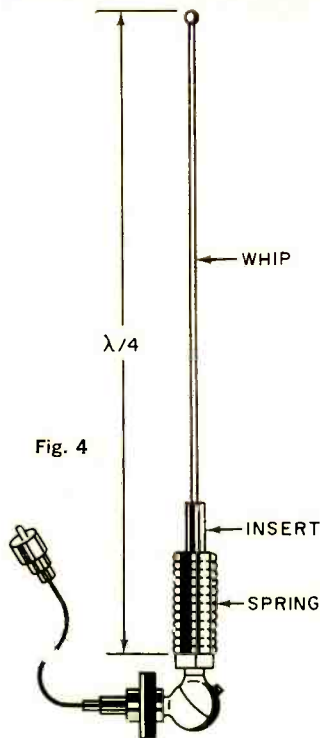If you use a crystal at a frequency that is isolated from most of the local transmissions, it may be difficult to establish contact with other low-power




rigs. For this reason, you'll be wise to select a crystal frequency that corresponds to the operating frequency of these local stations. In most areas, the high-frequency end of the band is used for local transmissions, the low-frequency end for long-distance or "DX."

Naturally, the distance that can be covered with such low-power transmitters is restricted. Since the input is unchanged, the range of reliable operation you can expect is approximately what you can obtain on the Citizens Band. When skip conditions are favorable, however, you may occasionally enjoy true DX communications. -30-
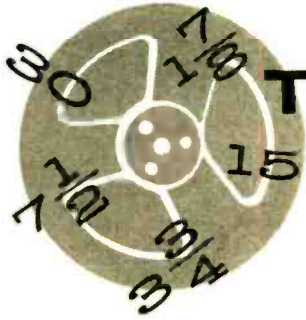
### IMPORTANT!

Operation on both the Citizens Band and the 10-meter amateur band is strictly controlled by FCC regulations. You can tune or operate a transmitter on the 10-meter band only if you hold a valid General Class or higher amateur license. To tune the transmitter of a licensed Citizens Band station, you must hold a first- or second-class commercial radio operator license.



# TAPE SPEEDS - Then and Now

By **RICHARD A. FLANAGAN**  
Associate Editor

**"STANDARDS"** have a way of becoming so firmly entrenched that we often forget how they all started. Take record and tape speeds—the common long-playing disc, for example, flips around 33 1/3 times every minute for no very good reason. As it happens, we measure time in a rather arbitrary interval we call minutes. We also count in ten's—because, anthropologists tell us, we have ten fingers and ten toes—and 33 1/3 happens to be the result of dividing ten times 10 by 3.

Tape speeds have an even more interesting history. Although the first magnetic recording device was invented by Denmark's Valdemar Poulsen shortly before the turn of the century, it was the Germans who first perfected a device using what we now call "tape." Known as the Magnetophone, the German instrument "captured" by the Allies at the end of World War II boasted a frequency response from 20 to 10,000 cycles. To achieve response to 10,000 cycles and beyond, the Germans moved their tape at a speed of 77 centimeters per second.

**At the Beginning.** How 77 centimeters happened to be chosen as the speed for the original Magnetophone is probably lost somewhere in history. But one thing is certain: when the Americans set about to duplicate the Magnetophone after the war, they didn't attempt to change speeds. If the Germans had produced better fidelity at 77 centimeters than was previously possible, then 77 centimeters would stand. Naturally, the Americans converted from the metric to the avoirdupois system of measurement. The result, roughly, was a speed of 30 inches per second.

As tape recording grew in acceptance and use, tapes were recorded at this very speed—30 inches per second. And while there are a number of economic factors on the negative side of the ledger for the old 30-ips speed, no one will deny that it offers exceptional fidelity.

**The Trend Downward.** For other than the most exacting requirements, however, 30 ips is no longer really necessary. As tape heads improved, so, too, did knowledge of the tape recording process—as well as the manufacture of magnetic tape itself.

Today, outstanding fidelity can be realized at 15 ips (which, incidentally, is a speed that was reached precisely as you might guess—by dividing 30 by 2). For semi-professional and home recording, half of the 15-ips speed delivers excellent sound and offers the attractive advantage of twice the playing time from a given reel of tape.

And while the 7 1/2-ips speed is often considered the slowest possible for hi-fi recording, very good results can be obtained at *half* this speed—the popular 3 3/4 ips.

Yet even this isn't "bottom"—the new CBS tape cartridge, not yet available commercially, moves at *half* the 3 3/4-ips speed—a phenomenal 1 7/8 ips! Only 3 1/2" square and 5/16" thick, it plays for over an hour and boasts a frequency response approaching that of some 7 1/2-ips equipment.



Unthinkable? To the designers of the original Magnetophone, perhaps. But to modern technicians, such performance is just another proof of the remarkable advances made in the art of magnetic tape recording during the decade or so of its existence.



# SPACE ELECTRONICS

By **OLIVER P. FERRELL**

Editor

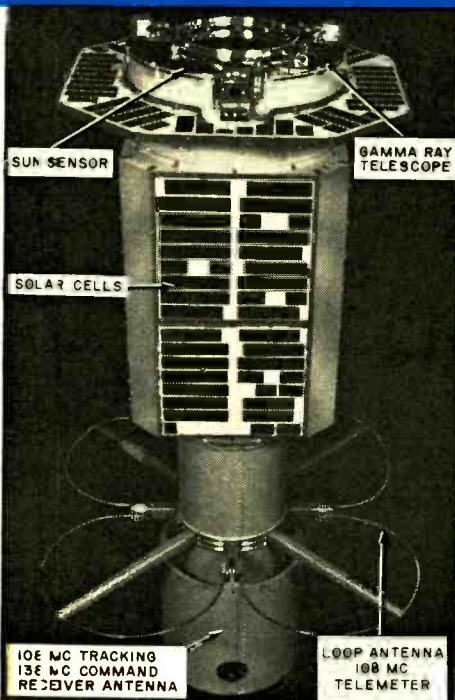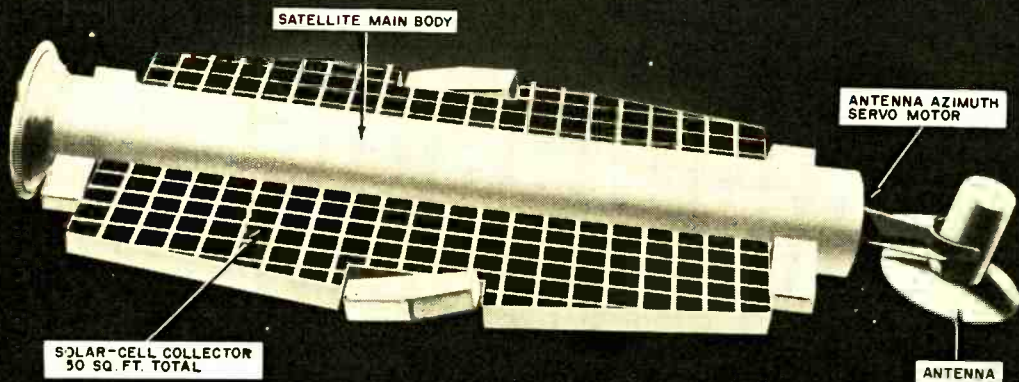



An all-purpose communications satellite has been proposed by RCA having the physical design shown above. Capable of relaying telephone, TV, telegraph or facsimile signals, it would orbit about 22,000 miles above the earth's surface, the antenna at far right automatically aiming itself at a particular point on the surface. Solar cells would recharge the receiver and transmitter batteries.

**A**ROUND the middle of March, 10,000-watt radar signals were bounced off the planet Venus and picked up by an 85-foot dish antenna in Goldstone, Calif. Using a frequency of 2388 mc. and a beam width of only 0.4 degree, the radar pulses took 6½ minutes to make the round trip.

Although weak radar echoes have been picked up before from Jupiter, Saturn,

Scheduled for launching this spring, NASA's S-15 satellite is expected to transmit data to earthbound receiving stations on 107.97 mc.

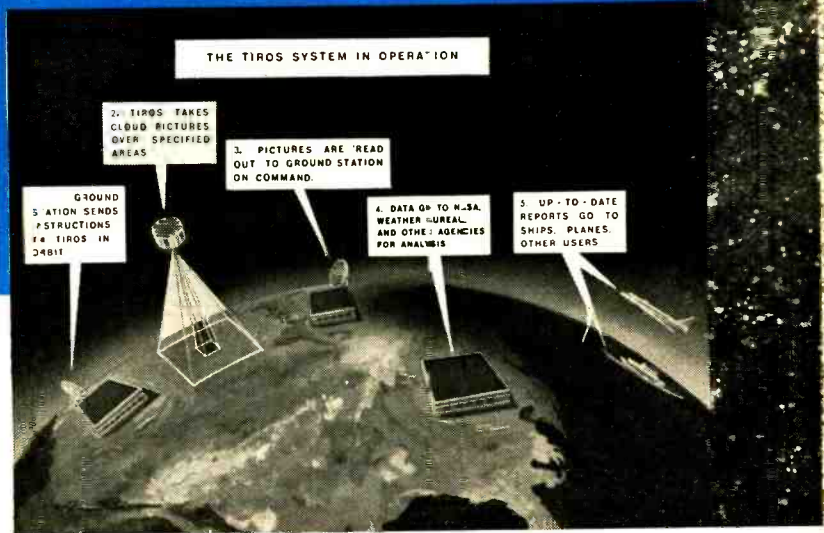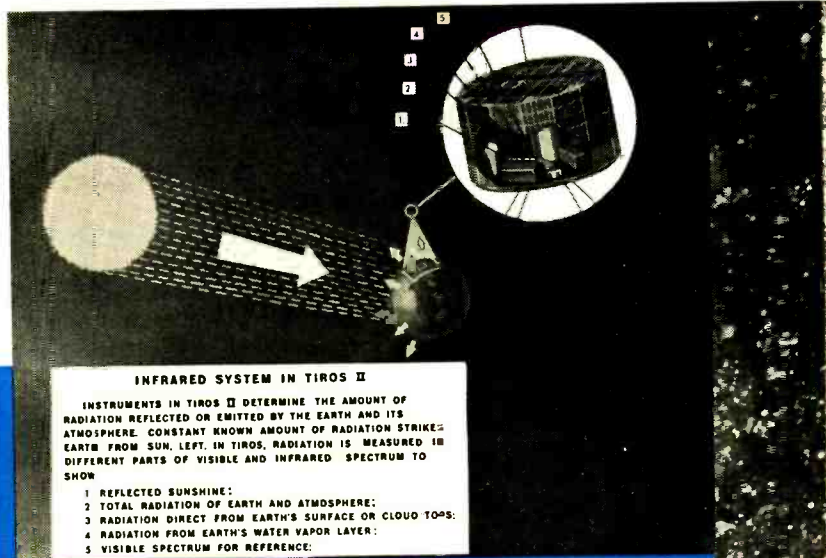The TIROS II is typical of several satellites to be launched by NASA for weather studies. Data collected from TIROS observations are made available to all cooperating foreign countries.



As TIROS satellite orbits the earth, ground command stations tell it when and where to take TV pictures. Although the TIROS transmitters are now off the air, similar satellites are to be launched later this year.

Venus and the sun, this is the first time that they have been strong enough to be immediately recognizable. Credit for this extra margin of sensitivity goes to the maser amplifier (see POP'tronics, April, 1960, page 41) used to reduce receiver noise to an extremely small quantity.

Radar observations of Venus will tell us if this cloud-covered planet is really revolving and how fast, and they will give us some idea of the density of the clouds. The experiments are being undertaken by the Jet Propulsion Laboratory and the National Aeronautics and Space Administration (NASA).

**New Signal on FM Band.** The NASA S-45 satellite (mentioned in the April column, page 65) failed to achieve an orbit. Had this satellite gone into orbit, it would have provided SWL's and experimenters in space science with at least one easily identifiable (20.0-mc.) radio signal.

NASA has now scheduled for launching (as this column is being written) its S-15 satellite. This 82-pound satellite is destined to detect and measure the intensity of gamma rays while swinging around the earth in a 98-minute orbit. (Gamma rays are known to be generated

by nuclear activity and are of such high energy levels that they are unaffected by magnetic fields—as radio waves are, for example.) The S-15 is really a “telescope,” and will spend part of its orbit life in scanning the sun.

Although not a “glamour” satellite—in terms of the publicity-conscious Soviet launchings—the S-15 will provide one or two readable signals that may be heard with the aid of an outdoor antenna and sensitive FM broadcast receiver. A weak signal for tracking—about 20 milliwatts—will be radiated on 108.06



A novel “sun-seeker” has been devised by Technology Instrument Corporation. Silicon cells at base of long arm are shaded by disc to cast shadow, and voltage developed by the cells is fed into a bridge circuit, driving small motors that track the sun. Such a device can be used with satellites which rotate at about 2 revolutions per minute.

mc. A considerably stronger signal (125 milliwatts) relaying gamma-ray data to earth will be on 107.97 mc., and should be heard throughout most of North America with minimum difficulty. The two transmitters will probably not be in continuous operation, but will be controlled by ground-level command signals. Solar batteries (probably silicon cells) will recharge 12 nickel cadmium batteries, giving the satellite a “life” of about one year.

If the S-15 goes into orbit, check the top end of your FM tuning dial—this is one that can be heard.

**Radio Signal Status.** Three satellite signals may be deleted from the listing of “Radio Signals from the Satellites”

which appeared on page 65 of our April column and was supplemented in May on page 76. The weak signal on 107.97 mc. from Echo I, the balloon reflector launched last August, is no longer heard; Samos II, a reconnaissance satellite, has ceased transmitting; and Discoverer XXI went off the air in late February. Frequencies used by the latter two satellites were never revealed by the Department of Defense.

Transit III-B and LOFTI, which never detached from their launch rocket, went into a wildly eccentric orbit. Radio signals were heard from both and proved to be of considerable value to American scientists. These two satellites re-entered the earth’s atmosphere on March 30 and burned up.

The Russian Venus probe was heard with a very weak signal on February 22nd, but has not been heard from since. Soviet Sputnik IX, launched on March 9th to test recovery mechanisms, did not transmit on any of the usual channels.

**Reading Matter.** Albert Parry’s new book entitled *Russia’s Rockets and Missiles* (Doubleday & Co., Garden City, N. Y., 382 pages, \$4.95) provides some thought-provoking reading on Soviet rocketry. Unlike many other communist claims of “prior invention,” a Russian by the name of Tsiolkovsky really did pioneer the field of rocketry—well before Germany’s Oberth and our own Robert H. Goddard. Parry analyzes what the Soviets have achieved (Sputniks, Luniks, etc.) through mid-1960, and presents some positive ideas on what the American research policy should be if we want to catch up. We recommend this book for its solid factual background and the digest of Soviet rocketry and satellite launchings.

A somewhat similar book, called *Soviet Space Technology* and written by Alfred J. Zaehring, has been released by Harper & Brothers (49 East 33rd St., New York 16, N. Y., 180 pages, \$3.95). While Dr. Parry is a regular writer on Soviet affairs (“Missiles & Rockets” magazine), Mr. Zaehring is president of the American Rocket Company and studies Soviet rocket activities as a hobby. His book is a faster-paced but less fact-filled account of what the Russians have done.

(Continued on page 108)



# Musical



# Telephone




# Holder



By HERBERT FRIEDMAN



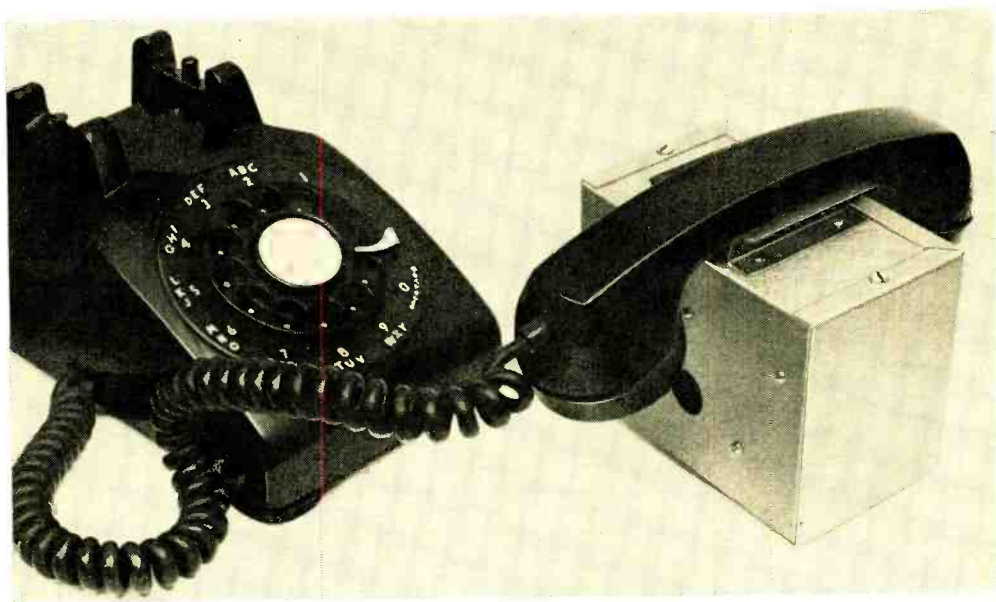**Electric music box "holds the phone" and entertains the caller**




Snap-action switch in box controls music box movement, keeps it playing till phone is removed.

**T**HE inexpensive electrically driven music box movements which have become available in recent years have made possible many interesting applications. These units never need to be wound, can be easily turned on and off by remote control, and will run for hours on a single 1½-volt flashlight cell.

One of these electric music box movements serves as the basis for the musical telephone holder described here. Designed to relieve the tedium of a caller who is "holding the phone," the tele-

phone holder provides a musical diversion while he waits. A snap-action switch in the cradle of the holder, actuated by the weight of the telephone handset, automatically starts the music—and stops it when the handset is removed.

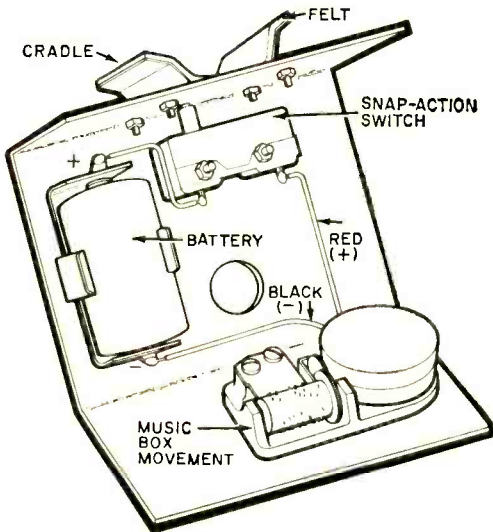**Construction.** The movement, flashlight cell, and switch fit neatly into a 3" x 4" x 5" aluminum box. Two pieces of scrap copper or aluminum are bent into "L" brackets and bolted to the outside of the box, forming a cradle for the telephone handset. Measure the width of your



The parts layout is simple and neat. Optional felt on cradle prevents gear noises from being picked up by receiver. Glue four rubber feet to bottom of box to protect furniture.



Music box movement, flashlight cell and switch fit in 3" x 4" x 5" aluminum box. Inexpensive movements can be found to suit almost any taste; available pieces range from "How Dry I Am" to "Moonlight Serenade."

handset before mounting the brackets; dimensions vary from model to model.

Center the switch plunger under the cradle—before mounting the switch, drill a hole in the top of the box to allow the plunger of the switch to pass through. Then finish the mechanical work by punching a  $\frac{3}{4}$ " hole in the side of the box, located so that the sound of the music box movement is directed to the telephone transmitter, and you're ready to wire up the unit.


The wiring couldn't be easier—the battery, switch, and movement motor are simply connected in series—but one precaution is necessary. Be sure to observe the proper polarity when hooking up the motor (its positive lead is usually red). If the motor is connected with reversed polarity, it will run backwards—and the movement may be damaged.

Electric music box movements are available from many mail order parts houses for less than two dollars (Lafayette Radio has a series priced at \$1.88). The author used a Unimax 2HBQ-1 snap-action switch, but any s.p.s.t., normally open, snap-action type will do. Use a Bud CU-2105-A Minibox or equivalent for the case. A commercial battery holder, such as the Keystone #175 makes it easy to mount the flashlight cell.

**Operation.** When it's necessary to ask a telephone caller to wait, place the handset on the cradle (with the transmitter facing the  $\frac{3}{4}$ " hole). The music box will start, and continue playing until you lift up the phone again.

If you find that the gears in the movement make noise which is picked up by the telephone, lubricate them with a small quantity of Vaseline or Lubriplate. You might also isolate the handset from the box by lining the cradle with felt.

-30-

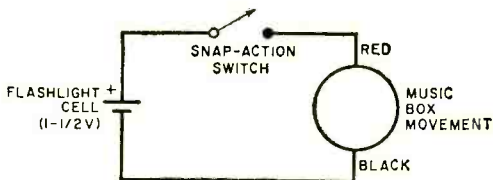

Flashlight cell, switch and movement motor are connected in series. Battery polarity must be observed in hooking up the motor.

# Your Connections Are Important

Careful grouping of hi-fi cables improves performance, reduces hum

By JIM KYLE, K5JKX/6

**T**OP PERFORMANCE from any audio system demands more than quality components. These components must be connected together properly to assure hi-fi without hum, noise, or distortion.

Naturally, each output must be connected to the appropriate input of another component; but there's more to proper cabling than that. The physical arrangement of the connecting cables plays an important role in determining the system's over-all performance.

In the interests of both good performance and a neat appearance, interconnecting cables should be grouped and laced. However, simply gathering all leads into a bundle and lacing them neatly is one of the quickest ways to assure poor performance. They must be separated by function.

Hi-fi cables can be classified into one of three groups: power and control leads, input lines, and speaker lines. Preamp output cables are grouped with the input lines.

A typical installation may include a turntable, a stereo tape deck, an AM-FM tuner, a stereo preamp, twin power amplifiers, and matched speakers. The cables involved with these units, by groups, include the following lines.

In the power lead group, you would find a tuner power line, one for the preamp, one to the tape deck, another for the turntable, and two more for the power amplifiers. This makes a total of six leads, all carrying 115-volt a.c.

In the input line group, there would be seven lines—two cables from the tone arm to the preamp, two from the tape deck, one from the tuner to the preamp, and two from the preamp to the two power amplifiers. All carry low-level audio.


Finally, in the speaker group, you would have two pairs of leads.

If all fifteen leads were grouped into a compact bundle, the low-level leads would certainly pick up hum and noise from the 117-volt lines, despite protective shielding. However, if you separate them into three appropriate groups, signal levels and content in each group will be equal, and no interaction will result.

Once separated into groups, the cables should be laced. The manner in which this is done will vary, depending primarily on whether your installation is cabinet-enclosed or is one of the "open" type in which cables will be exposed to public view.


*(Continued on page 107)*

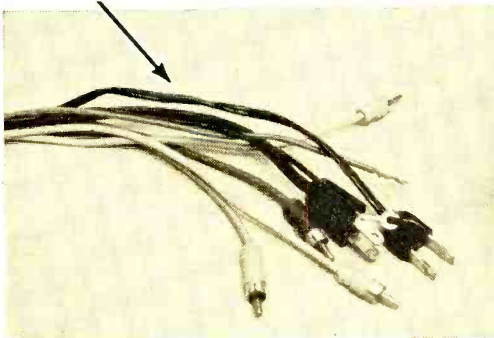LOW LEVEL AUDIO CABLES AND POWER LINES GROUPED TOGETHER



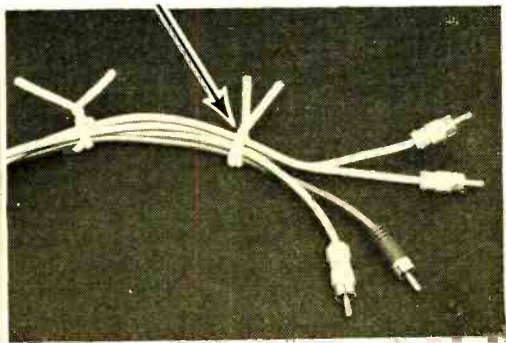**BAD**

LOW LEVEL AUDIO CABLES GROUPED TOGETHER AND LACED WITH PIPE CLEANERS



**GOOD**

POWER CABLES AND SPEAKER LEADS ARE LACED IN SEPARATE GROUPS AND SPACED APART

# ELECTRONIC FISH CALLER



## Unique one-transistor "beeper" lures fish with underwater sound

ANY sailor who has worked around sonar gear will testify to the fact that fish are attracted by certain man-made noises. The fish may believe that the sounds come from some source of food, such as another aquatic animal or a trapped insect, or their motivation may simply be curiosity. At any rate, the technique of calling fish with underwater sound really works, and has been successfully used by fishermen.


You can put together this neat little fish caller with a minimum of work and expense, and it should be well worth your while. The device produces a repeating, high-pitched "beep" which is attractive to many kinds of fish.

**The Circuit.** A single transistor ( $Q1$ ) is used in a Hartley oscillator circuit (feedback produced by tapped inductance). Although the author used a Sylvania 2N1265, most *pnp* audio transistors will work just as well. The tone and basic repetition rate are fixed by capacitor  $C1$  and resistor  $R1$ , and potentiometer

$R2$  varies the repetition rate over the small range required. The crystal earphone is simply connected in parallel with the inductance ( $L1$ ). Power is provided by battery  $B1$ , a penlight cell.

**Construction.** Begin by mounting the battery holder, earphone, transformer, transistor socket, and potentiometer on one side of a suitable perforated board. Fasten the earphone in place with cement, first removing the screw and back plate and passing the leads through two convenient holes in the board. You may not want to use a transistor socket, in which case transistor  $Q1$  can be mounted by simply pushing its leads through three holes in the board; these leads are later soldered directly into the circuit.

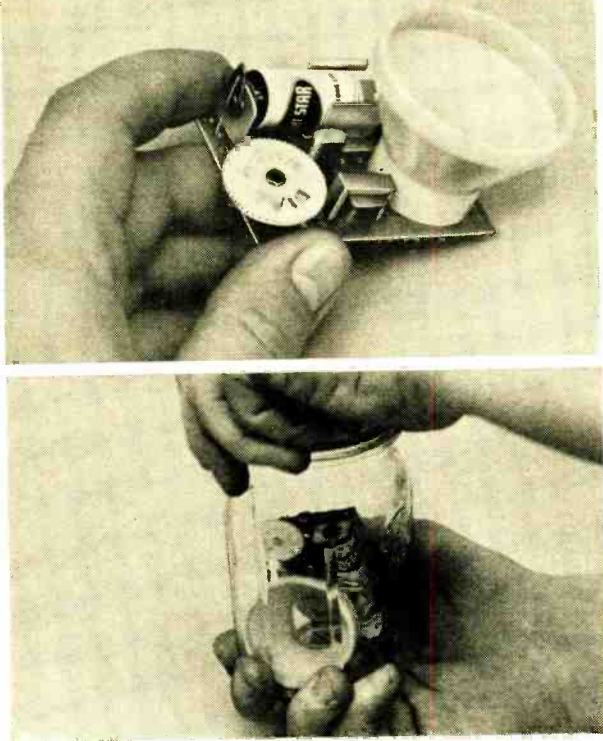Mount potentiometer  $R2$  by bolting it down through the holes in its switch terminals—it will be necessary to use spacers between these terminals and the board or to bend the terminals down and out, forming mounting brackets. Install soldering lugs between the



By **JAMES J. BUCHER**


mounting nuts and the bottom of the board for making connections to the switch (*S1*).

Only the three primary leads of the transformer are used, and the leads from the secondary may be cut off or taped up. The end of the battery holder nearest *R2* will be positive; mark it with a dab of red nail polish. When the battery is installed, its brass center terminal should be placed at the marked end; reversed polarity would damage the transistor.

The earphone specified in the Parts List comes with an interchangeable ear plug and mouthpiece (it may be used as a microphone in other applications). Discard the ear plug and finish the mounting job by cementing the mouthpiece (which will act as a speaker horn—amplifying the sound) in place.

The wiring is a simple job, but be sure to observe the proper polarity when hooking up the battery holder and electrolytic capacitor *C1*. If you install the

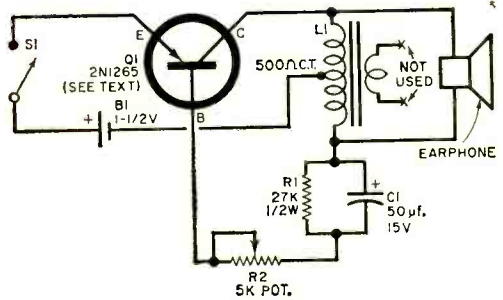Miniature components make completed unit extremely compact. Tiny potentiometer (*R2* in diagram) includes built-in on-off switch (*S1*).



#### PARTS LIST


- B1*—Penlight cell
- C1*—50- $\mu$ f., 15-volt subminiature electrolytic capacitor
- L1*—Subminiature output transformer; 500-ohm CT primary, secondary not used (Lafayette TR-99 or equivalent)
- Q1*—Audio-frequency npn transistor (Sylvania 2N1265 or equivalent)
- R1*—27,000-ohm,  $\frac{1}{2}$ -watt resistor
- R2*—5000-ohm miniature potentiometer with switch *S1* (Lafayette VC-62 or equivalent)
- S1*—S.p.s.t. switch (on *R2*)
- 1—Miniature high-impedance crystal earphone (Lafayette MS-439 or equivalent)
- 1— $1\frac{3}{4}$ " x  $2\frac{1}{8}$ " perforated board (half of Lafayette MS-30-1, or equivalent)
- Misc.—Battery holder, transistor socket (if used), hardware, etc.

transistor without a socket, be careful when soldering the leads; use a six-watt (or smaller) soldering iron—and use it sparingly.

Now install battery *B1*, flick on the switch, and your unit should operate. The author's model is adjustable from about 100 to 250 repetitions per minute, but an exact duplication of this range is not necessary.

**How to Use It.** To operate the fish caller, turn it on and seal it in a Mason jar or waterproof can, adding enough weight to make the assembly sink into the water. (A weighted plastic bag with the air squeezed out of it will also do.)

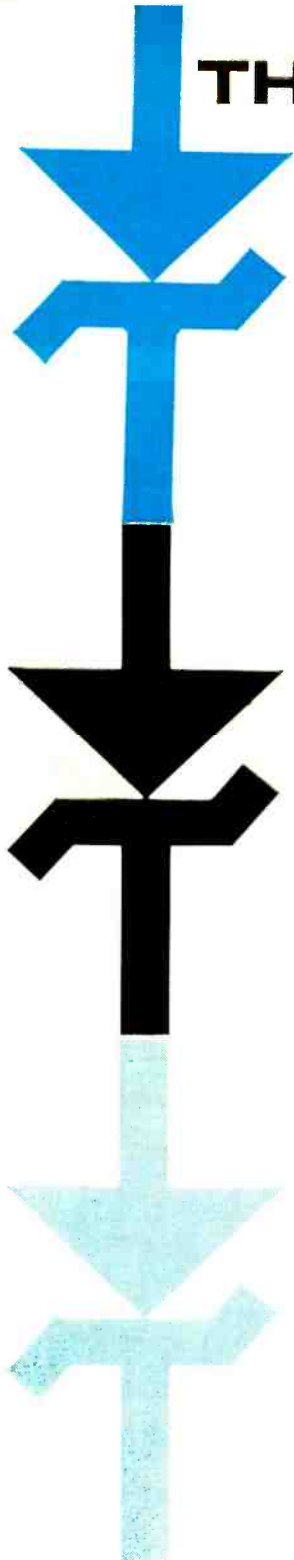Suspend the device at fishing depth from a float or a hand line, drop in your bait, and await results. If nothing happens, pull up the fish caller and try a different repetition rate. If you notice an unusual disturbance near your boat, be cautious—you might have dialed in a whale, or even the Loch Ness monster!



THE

# ZENER DIODE

By R. J. SHAUGHNESSY

NOW widely used as regulating elements in control and similar circuitry, zener diodes have yet to become part of the average hobbyist's or experimenter's stock in trade. However, by keeping a few simple facts in mind and becoming familiar with some of the zener's applications, you'll be designing your own special circuits in no time. In fact, you'll find that zener diodes can actually improve the performance of your older designs.

## WHAT ARE ZENER DIODES?

Zener diodes, or silicon regulators—as they are also called, are simply semiconductor versions of the familiar vacuum-tube voltage regulators—the 0A2, 0B2, etc. However, while vacuum-tube regulators can provide regulation only at certain specific voltages and over limited current ranges, silicon regulators can be made to work at almost any desired voltage and over a wide current range.

From the outside, these devices look exactly like ordinary semiconductor diodes. Inside, too, their con-

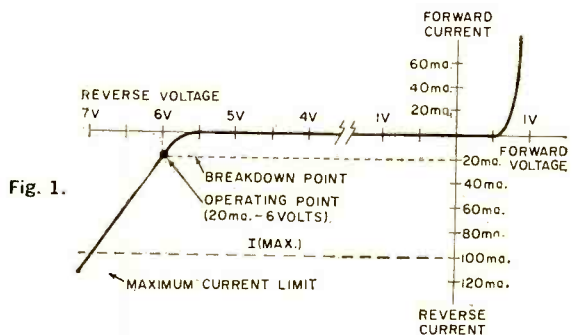


Fig. 1.

struction is much the same. In fact, you can even use them as rectifiers, provided the a.c. peak value does not exceed the characteristically low peak inverse voltage of the zener. The curve of Fig. 1 shows a typical 6-volt zener diode characteristic and will help make this point clear.

The forward side of the curve (anode positive) looks just like that of an ordinary diode; useful current flows as soon as the forward voltage reaches about 0.7 volt. In the reverse direction (anode negative), you can see that the zener would never make the grade as a really practical rectifier because of its low breakdown voltage. In this sense, it behaves as though it were a normal rectifier that had developed high leakage at this low voltage.

If this really were the case, however, the unit would very likely destroy itself through excessive current flow in a very short time. Not so the zener diode. The ability of this device to withstand high reverse currents and go on working while in a saturated state is actually its most important characteristic and makes it very useful in voltage-regulating applications, as we'll see shortly.

The curve also shows that breakdown occurs at about 6 volts, and that this voltage remains pretty constant even though the current varies from a few  $\mu$ a. to more than 100 ma.

## BREAKDOWN VOLTAGES


Ever wonder how the word "zener" came to be associated with these devices? The answer is simple: in the early days of semiconductor research, much of the information on breakdown mechanisms was derived from still earlier research on dielectric materials by Dr. Carl Zener. Later, when semiconductor researchers began to utilize breakdown effects in certain silicon devices, they called these devices "zener diodes" in recognition of Dr. Zener's pioneering efforts.

The point at which breakdown occurs can't be predicted exactly, although it can be controlled within certain limits. It is largely determined by the type of silicon used in the manufacturing process.

Breakdown of the crystal junction occurs in a natural distribution about the desired value. For example, a factory run of 6-volt units might have breakdowns in the range of 5.6 to 6.5 volts—a distribution span of about 15%. If closer tolerances are needed, the manufacturer must select special units from within this distribution. Naturally, because of the additional labor involved, these cost much more than regular units—especially if the desired tolerance is less than about 5%.

In practice zener diodes are readily available with

Motorola photos

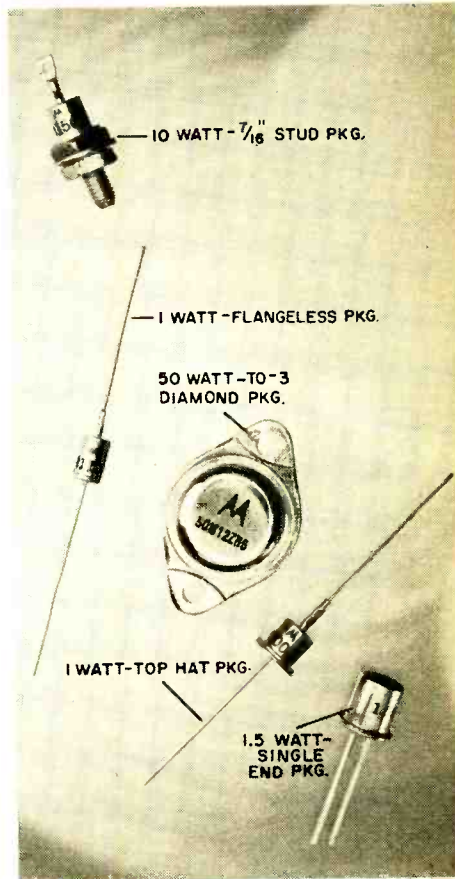

Like other semiconductor devices, zener diodes come in many shapes and sizes.

voltage accuracies of 20%, 10%, and 5%. Very close tolerances can be obtained by connecting lower voltage units in series in special packaged assemblies called reference elements.

## TEMPERATURE EFFECTS

As with all semiconductor devices, temperature plays an important role in the operation of zener diodes. A *temperature coefficient* is directly related to the saturation voltage, as shown in the curve of Fig. 2. The coefficient approaches 0.1% per degree centigrade at higher voltages, passes through zero in the region around 5 volts, and becomes negative at lower voltages. The importance of this effect can be appreciated

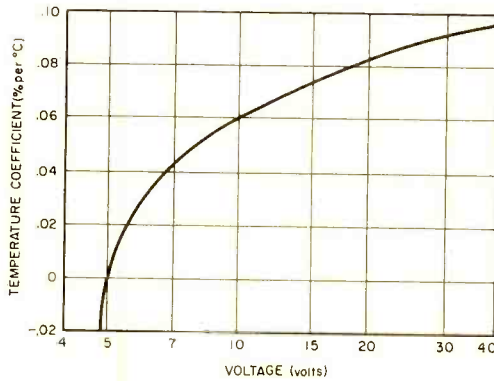


Fig. 2.

when we consider that a 10-volt unit at normal room temperatures ( $20^{\circ}\text{C}$ ) will measure 10.5 volts in an equipment cabinet where the temperature is  $75^{\circ}\text{C}$ .

This voltage change could be disastrous in certain applications. However, the danger can be avoided by selecting two lower voltage units with smaller coefficients. For example, if we had used two 5-volt units in series—each with a temperature coefficient of 0.002%—we would still have the desired 10 volts. But the change with temperature would be only a small fraction of a millivolt within the same range.

## DYNAMIC AND STATIC RESISTANCE

The basic factor in the regulating ability of a zener diode is its *dynamic resistance*. This is an expression for the change in saturation voltage with a small change in current. It can be measured by observing the a.c. voltage developed across the diode when a small a.c. current is superimposed on the operating



d.c. current. Because a.c. is used in these measurements, the term "a.c. resistance" might have more meaning than dynamic resistance, although both terms mean the same thing in this connection.

Values of dynamic or a.c. resistance vary from less than one ohm in high-current, low-voltage units to several hundred ohms in low-current, high-voltage units.

The d.c. or *static resistance* of a zener diode depends on its operating point and is simply the operating voltage divided by the operating current. In Fig. 1, this point has been set arbitrarily at 6 volts and 20 ma.; the static resistance is therefore  $6/.02$  or 300 ohms.

We can use the same curve again to obtain an approximate estimate of dynamic resistance. Select two values of saturation current that are spaced equal distances above and below the d.c. operating point; then draw vertical lines upwards from these points until the voltage axis is intersected. The dynamic resistance can now be found by dividing the peak-to-peak voltage by the peak-to-peak current. For the particular diode shown, this figures out to be about 10 ohms. In practical measuring equipment, the peak-to-peak current change is restricted to about 10% of the d.c. operating current.

## ZENER DIODES AS CIRCUIT ELEMENTS

In essence, a zener diode is a device which, when saturated in the reverse direction, will maintain an almost constant voltage across its terminals. The most popular application for a device of this type is, of course, voltage regulation.

Figure 3 shows a zener diode connected as a shunt-



Fig. 3.

regulating element across a load represented by resistor  $R_L$ . To analyze the circuit operation, let's assume that the input voltage,  $E_{in}$ , increases and see how this affects the output voltage. Note that the positive terminal of the input supply is connected to the cathode of the zener, and that the current flowing in the series resistor  $R_s$  is the sum of the diode and load currents. Let us assume also that the diode's characteristic is that shown in Fig. 1.

You'll remember we said that dynamic resistance



was associated with alternating or changing currents and voltages, and that it was the basic factor in the regulating ability of a zener diode. Now let's put these facts to work for us.

We have assumed that the diode in the circuit is the unit whose characteristic is shown in Fig. 1; its dynamic resistance therefore is about 10 ohms. Since we've set the operating point arbitrarily at 6 volts and 20 ma., the static resistance is 300 ohms.

Initially, conditions around the circuit are not changing and can be represented as shown in Fig. 4(A). We see the input voltage of 10 volts across two


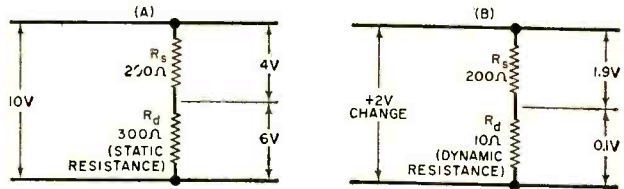


Fig. 4.

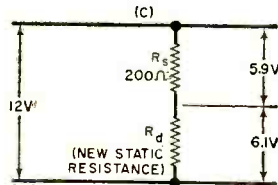

resistors—4 volts across  $R_s$  and 6 volts across  $R_D$ , which represents the parallel combination of the zener and the load resistor  $R_L$ . Now let's increase  $E_{IN}$  by 2 volts. Since the increase is a changing quantity and shifts the diode's operating point, we must analyze its effect on the circuit by means of the dynamic rather than the static resistance. Figure 4(B) shows how the 2-volt change will distribute itself around the circuit.


As soon as conditions settle down and become static again, the operating point will have shifted to a new position and the circuit voltages will now be the sum of the original voltages and those resulting from the 2-volt change. The new distribution will therefore be as shown in Fig. 4(C). Referring back to Fig. 4(B), it is obvious that lowering the dynamic resistance of the zener or increasing the value of  $R_s$  will improve the regulating action of the circuit. Increasing  $R_s$ , however, will mean a corresponding increase in input voltage to maintain the proper current levels.



# USING ZENER DIODES

The fact that a zener diode will maintain an essentially constant voltage drop independent of current suggests its use as a source of grid-bias voltage. The circuit conditions of Fig. 5 are such that the tube



Fig. 5.

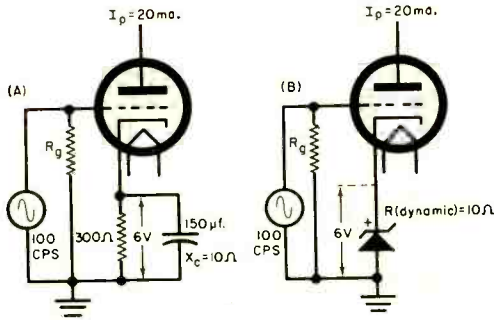

requires a bias of 6 volts at a cathode current of 20 ma. Figure 5(A) shows how this is obtained by conventional means with a cathode bias resistor of 300 ohms and a bypass capacitor of 150  $\mu$ f. Figure 5(B) shows how a zener diode can be substituted for both of these components.

The bias voltage is the zener voltage; because of its low dynamic resistance, the diode will hold the voltage constant even during wide swings of plate current. The bypass capacitor is not needed either, because the dynamic resistance is roughly equal to the capacitor's impedance even at low signal frequencies.

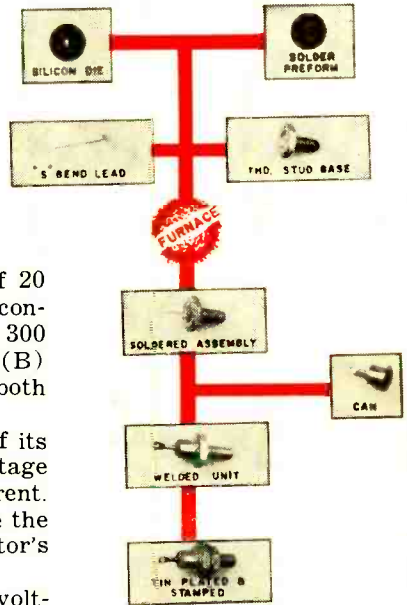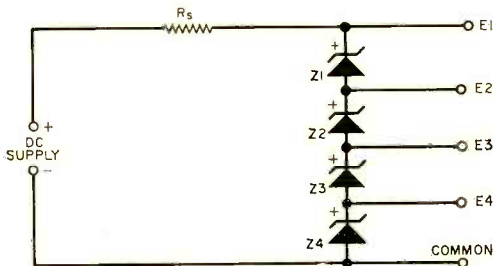Should you have need of a number of different voltages, you can build the voltage divider shown in Fig. 6 by connecting several zener diodes in series across a suitable d.c. supply. This divider would be useful



Major elements comprising zener diodes are fused in "furnace" before assembly.

Fig. 6.

around the workbench as an accurate voltage source for calibrating meters or as a stable d.c. bridge supply. In fact, it's applicable whenever a dependable, long-lived voltage source is required.

In certain critical, vacuum-tube circuits, every possible precaution must be taken to stabilize key voltage points against drift. The effects of plate voltage drift are particularly troublesome in high-gain d.c. amplifiers, and call for regulation not only of the B+ supply but of the tube's a.c. heater supply also.

Figure 7 shows how zener diodes can be used as effective a.c. voltage regulators. Two diodes must be


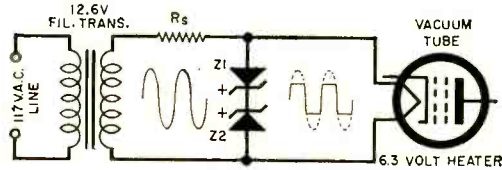


Fig. 7.

connected back-to-back in this application to prevent forward conduction in both at the same time as the a.c. waveform switches back and forth from plus to minus. With this arrangement, one of the diodes will always be biased in the reverse direction for either polarity of a.c. The diodes effectively clip the peaks of the waveform; as a result, the voltage at the heater is a flat-topped wave independent of line voltage changes.

As you might guess, special, double-anode units have been developed for this type of application. These units contain two zener diodes connected cathode-to-cathode inside a single package. This design simplifies mounting and can save considerable space in crowded chassis areas.

The application possibilities of zener's are far too numerous to be described individually here. But whatever the project being worked on, chances are that one or two of these devices, properly placed in the circuit, will improve its performance. Once you have used zener diodes and come to depend on their excellent performance and reliability, you'll wonder how you ever got along without them in the past. —30—

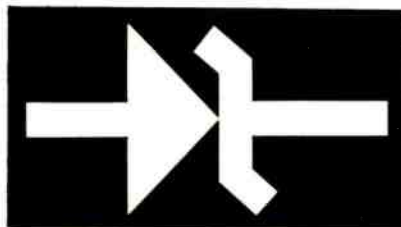



# Short-Wave Report

By **HANK BENNETT**  
W2PNA/WPE2FT

## FALSE REPORTING

**O**NE OF THE DUTIES of your Short-Wave Editor is to check out all incoming reports. For most items, we use the *World Radio Handbook* and the *Foreign Broadcast Information Service* as standard references—about 90% of all reports are confirmed in this manner. Stations listed in reports but not listed in the reference books are personally checked on the air whenever possible. In some instances, we write to one of several veteran DX'ers and ask for verification of certain stations or information.

Once in a while, all evidence will point to a report as being obviously incorrect. This can be due to a misinterpretation by the listener of what he heard, or thought he heard. Everyone is entitled to a few honest errors. One of our most reliable reporters, for example, recently reported hearing a station in Africa; after further investigation he found that the station was behind the Iron Curtain, far removed from Africa.

Then, again, there is always the chance that a report can be just plain phony. A guilty DX'er, when confronted by positive evidence of fraud, revealed that he only wanted to see his name in print. Deliberate false reporting is *not* the way to get your name listed—unless you are trying to have it listed in the blackball column.

Sometimes the wording of a report can determine whether we categorize it as honest or false. It is perfectly proper to copy schedules that are sent to you by the stations themselves so long as you indicate clearly that you are doing so. It is also okay to copy schedules from the *World Radio Handbook* or from club bulletins provided that you give your source of information—but the

chances of getting your name into print this way are small since we have the same sources of information here.

Every month we receive reports from readers who have the schedule of a rarely heard station in their possession. They list the schedule or a part of it, but rather than stating that the station is on the air at that time, they state that



Radio Nederland's new QSL card is a real beauty—Holland appears in bright yellow on an emerald green and blue background. This card replaces the green, blue and white combination we considered colorful enough to feature on our January cover.



Thomas F. Carten, WPE1APS/KN1FZU, of Stratford, Conn., has snagged 34 countries and 25 veries with his shack full of equipment. He uses a Hammarlund HQ-145 receiver, Heath DX-40 transmitter, home-made control board, Revere tape recorder, Hallicrafters S-20, and an AM standby receiver.

they "heard" the station. This is obviously false reporting. Do *not* list a station as having been heard unless you have actually heard it.

One report received here recently listed many stations of a certain country as having been "heard." These low-powered stations, serving local audiences, very likely were on the air. But the low power and low frequency, combined with the reported times, virtually assured us that the reporter in question did not actually

hear the stations; and a quick check in the *WRH* showed exactly the same listings. This reporter should have taken a few extra seconds of his time to indicate that he had copied the information from another source.

Deliberate false reporting is rare. True and correct reporting, happily, is evident in well over 90% of the reports coming in to us. But as a general reminder to all, we would like to emphasize the following three points:


- (1) Report what you heard;
- (2) If you copy information, be sure to indicate the source of your material;
- (3) Don't waste your time—or ours—with dishonest reports.

(Continued on page 118)

## Short-Wave Monitor Registration

If you haven't registered for your Short-Wave Monitor Certificate and call letters, fill out this form and mail it with ten cents in coin to: Monitor Registration, POPULAR ELECTRONICS, One Park Ave., New York 16, N. Y. Include *stamped, self-addressed* envelope so we can mail your certificate at once. If you live outside the United States, send two International Reply Coupons or equivalent value postage stamps. Canadians may send fifteen cents in coin.

(Please Print)		
Name .....		
Address .....		City .....
State .....		
Receiver	Make .....	Model .....
	Make .....	Model .....
Principal SW Bands Monitored .....	Number of QSL Cards Received .....	
Type of Antenna Used .....		
Signature .....		Date .....

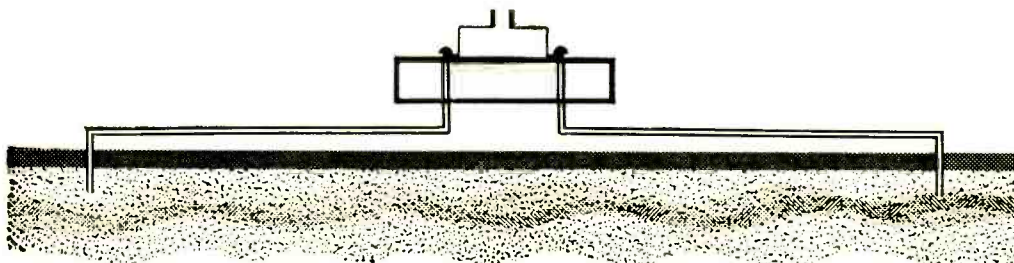

# Build a SOIL MOISTURE METER

By RONALD WILENSKY

**Simple ohmmeter circuit takes  
guesswork out of lawn watering**

**H**AVE you ever wondered whether you were watering your lawn or garden more than necessary—or not enough? This handy “moisture” meter will help you determine just how much water the soil needs at any time—it will take some of the guesswork (and the unnecessary work) out of the job.

Essentially a simple ohmmeter, the unit works on the principle that the wetter the soil gets, the lower its resistance becomes. A miniature 0-1 milliamperemeter (*M1*) is the heart of the device. Wired in series with a transistor battery (*B1*), calibrating potentiometer *R1*, resistor *R2*, and a special probe, the meter functions as an effective soil resistance indicator.

**Construction** couldn't be simpler. The ohmmeter circuit will fit in an aluminum Minibox with plenty of room to spare. Lead length and component placement are not critical. The simplest way to make the 1½"-diameter hole for the meter is to use a Greenlee chassis punch, but the light aluminum is easily cut, and a few minutes work with a ¼" drill and



a half-round file will yield the same results. The battery is mounted in a holder made of 1" sheet-metal stripping.

The probe is made from two lengths of coat hanger wire (paint removed) and a piece of scrap plastic or other insulating material. Construction details are shown in the pictorial diagram. A six-foot or longer length of zip cord, terminated in a phone plug, connects the probe to the meter box.




**To use** the soil moisture meter, you must first calibrate it. When your lawn or garden has been freshly watered, insert the prongs of the probe two inches into the ground; then adjust *R1* until

the meter reads eight-tenths of full scale (0.8 ma.). You may want to mark *R1*'s position with a pencil in case the shaft is accidentally moved.

When you think the ground should be watered again, insert the probe at several different points on your plot and take readings by depressing *S1*. If most of your readings are much less than 0.8 ma., the soil needs water. If they're over 0.8 ma., hold off the watering for a day or so. (Exact scale readings will vary for different types of soil.)

If you'd like to use the moisture meter on several kinds of soil, or in garden

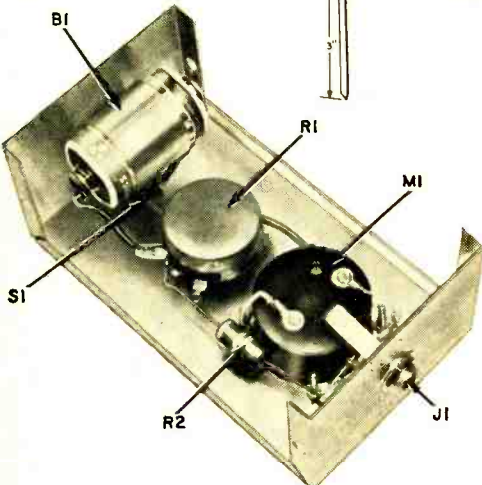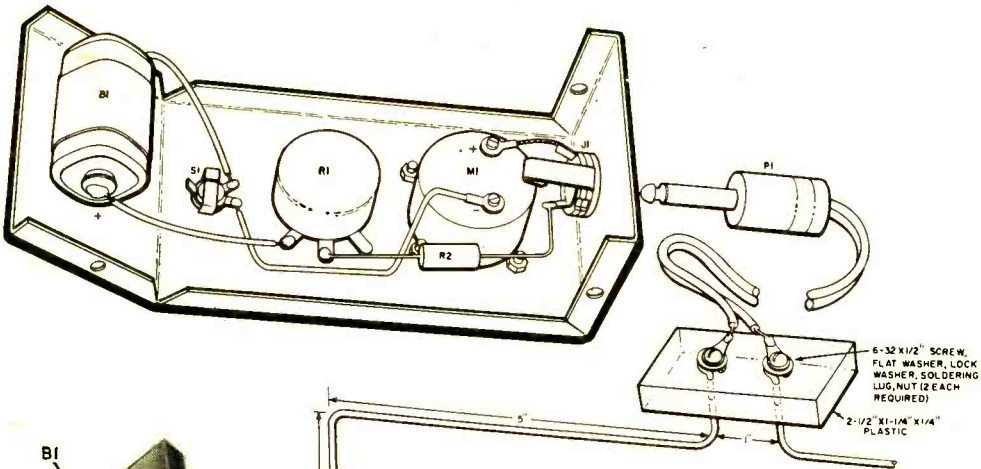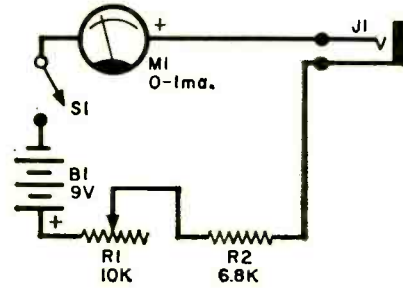Wiring the moisture meter is easy but be sure to observe proper polarities when connecting meter *M1* and battery *B1*.



All components fit nicely in a 5" x 3" x 2" aluminum box. The battery holder shown here is handmade, but a commercial unit may be used.

#### PARTS LIST

- B1*—9-volt transistor battery (Burgess P6 or equivalent)
- J1*—Open-circuit phone jack
- M1*—0-1 ma. miniature milliammeter (Lafayette TM-400 or equivalent)
- P1*—Phone plug
- R1*—10,000-ohm potentiometer, taper not important, slotted shaft (Mallory SU-20 or equivalent)
- R2*—6800-ohm, 1/2-watt resistor
- S1*—Miniature push-button switch (Lafayette MS-449 or equivalent)
- 1—5" x 3" x 2" aluminum box (Bud CU-3006A Minibox or equivalent)
- Misc.—Hardware, zip cord, 2 1/2" x 1 1/4" x 1/4" plastic block, coat hanger wire, etc.

areas requiring varying amounts of water, you'll probably need more than one calibration point. In this case, it might be handier to use a potentiometer with a pointer and scale rather than the screwdriver-adjusted type shown, and jot down the different calibration readings on the side of the box.



# On the Citizens Band

By TOM KNEITEL, 2W1965



**B**ET you didn't know that CB'ers share in a little piece of "space electronics." While digging through some "Proceedings of The I.R.E.," we came across a report by John D. Kraus of Ohio State University's Radio Observatory. The report, in Vol. 46 (pp 266-274, Jan., 1958), is called "Planetary and Solar Emission at 11 Meters Wavelength" and describes how we've received signals from the sun, Venus, and Jupiter on 11 meters. Jupiter came through with "clicks" and grinding noises, the Sun gave out with "solar" noise, and Venus produced a rumble.

The antennas used for this interplanetary DX included three right-handed helical beams 24 feet long by 11 feet in diameter. The helices had  $2\frac{1}{2}$  turns each and rotated on their axes. Another antenna used two colinear arrays, each consisting of two horizontal  $\frac{1}{2}$ -wave elements separated from each other by 180 feet.

Hey—wait a minute! Don't those guys on Venus, Jupiter or wherever know about the "no DX'ing" rule? Their FCC citations will be arriving on the next "Discoverer"!

**Wow! Whoopie! Zingo!** Those Raytheon people sure know how to keep your attention while they demonstrate a set. As you can see from the photo, their RAYCOM CB rig has beautiful coloring and is 5 ft. 3. . . . I mean, it has 5 watts input. I couldn't bring myself to concentrate much on the set, but I did learn that it has five channels, an ANL, an excellent modulation circuit, and will run on 12 or 32 volts d.c. and 117 volts a.c. Bless Raytheon for giving your tired old CB Editor something to live for—their new RAYCOM, of course!

An anonymous reader has sent us a clipping from the San Jose (Calif.) *News*. The item is headed "Radioman Panics, Sets Off a Search," and relates

how "a Woodside man sent police and amateur radio operators into a tizzy . . . by broadcasting for help." The CB'er kept pleading over the air that he was "being held by two men."

Two hours later, after he had aroused two sheriff's departments and several other CB'ers, his wife grabbed the mike. She said that she didn't know what the call letters were but there was no trouble and the station was going off the air. Then she pulled the switch.

When the sheriff's finally tracked down the station, they found that the "two men" were actually one landlady who was threatening the CB'er with eviction. The CB'er and his family lost the "battle" and spent the night in a motel. Since the FCC is always making such a fuss about mis-use of the 11-meter band, we wonder what action they took in this particular case.

There's a mistaken belief among some mobile CB'ers that they can step up the output from their voltage regulators and



pump a little extra juice into the rig to squeeze out that extra watt or two. The cost of replacing a whole set of French-fried tubes each week makes it hardly worth finding out if this will work. It won't. True, you may run more power into the set, but you'll also overheat the filaments and damage the cathodes. In the end, you won't get anything more out of the rig than the tubes.

**Speaking of mobile operation**, which is very popular this time of year, we'd like to mention that last summer there were a number of instances when mobile CB'ers were stopped by the law for an explanation of their two-way radio equipment.

In many areas it's illegal to keep radio equipment in your car if it can receive police frequencies. And even though a CB rig can't do this, rural "speed trap" sheriffs are always on the lookout for itinerant motorists sporting whip antennas on their buggies.

Before you venture forth, you'd better double-check to make sure that you have your "FCC Form 452-C, Revised"

UNITED STATES OF AMERICA	FCC Form 452-C
(Station call sign) FEDERAL COMMUNICATIONS COMMISSION	(Revised)
<b>TRANSMITTER IDENTIFICATION CARD</b>	
THIS CARD ATTESTS THAT AUTHORIZATION HAS BEEN RECEIVED FROM THE F. C. C. FOR INSTALLATION AND/OR OPERATION OF THE RADIO TRANSMITTER TO WHICH ATTACHED. (Fill in items 1 through 5)	
1. Name of permittee or licensee .....	.....
2. Name of permittee or licensee .....	.....
3. Location(s) of transmitter records .....	.....
4. Transmitter operating frequencies .....	.....
5. Signature .....	.....
(Permitter, licensee, or responsible official thereof)	

properly executed and attached to the rig. The "452's" are available from any FCC office.

One thing more—don't transmit while you're driving. This is also illegal in some places, but it's a dangerous habit no matter where you are. The rig you save may be your ohm! (Ouch!)

**Another popular place** for summertime CB activity is aboard small boats, and the Kaar Engineering Corp. (2995 Middlefield Rd., Box 1320, Palo Alto, Calif.) has designed a good-looking "monitoring poster" which they will supply at no charge to interested parties. The poster advises CB-equipped boats that Channel 13 is being monitored—see photo.

**We had a chance** to gaze into the CBCB (CB Crystal Ball) the other day at the Mahler Research Foundation's labora-

tories. Executive director Tracy Diers (2W4975/W2OQK/W2CXN) and engineer Herb Friedman (2W6045/W2ZLF) took us behind locked doors to give POP'tronics an exclusive scoop on a speech-scrambler they've perfected for CB.

It really works. You put one "scrambler" on a transmitter and one on a receiver, and nobody can understand what's going on except the stations in your system.

This appears to be the answer to the complaints of many "commercials" who don't want to be bothered by the gossipers on their channel. The gadget isn't ready for commercial distribution yet, but it is expected to be *very* inexpensive and easy to attach.

**If you'd like** some personalized "call letter" jewelry, license plates, decals, lapel pins, etc., drop a note to Chuck at K9TVA Enterprises, 6429 N. Glenwood Ave., Chicago 26, Ill., and ask for his catalog. There are a couple of dozen items in it worth looking over, and an order blank to boot.

**Many readers** have written to ask about the different call-sign prefix letters heard on 11 meters. Here's the story. Calls with "W's" were the original CB calls and were given out between September 1958 and December 1960. Some areas ran out of "W" calls, however, before the end of '60 and used "A" calls until the new "Q" system went into effect on January 1, 1961.

The "Q" calls will be assigned until the end of 1961, while "R" calls will be assigned for 1962, "S" for 1963, and so on, until "W" is reached again in 1967. Since CB licenses are valid for five years, no "Q" calls will be in use later than the

(Continued on page 112)



# AC DC

# ELECTRONIC LOAD

By HAROLD REED

**T**WO inexpensive semiconductors and a handful of other components make a useful electronic load that will take the place of a whole drawer full of test resistors. Having provision for both a.c. and d.c. inputs, it can be used for test-loading low-voltage power supplies, generators, batteries, audio amplifiers, etc.

The collector-emitter resistance of power transistor *Q1* provides the actual load. This resistance decreases as *Q1*'s base current increases, and vice-versa. The base current is supplied by battery *B1* and controlled by adjusting potentiometer *R3*; switch *S3*, the base current cutoff switch, is ganged with *R3*. Resistor *R2* limits the base current. The current drain of the electronic load is read by meter *M1*.


Silicon diode *D1* rectifies the a.c. input and capacitor *C1* smooths out the d.c. pulses. The resulting d.c. is then fed to transistor *Q2* through *S2* (the a.c.-d.c.

selector switch). Resistor *R1*, when switched across the a.c. input by *S1*, is used in checking calibration (see calibration procedure below).

**Hookup.** For d.c. testing, set *S1* to "Operate," *S2* to "D.C.," and *R3* to its maximum resistance. Connect the output of the device to be tested to the d.c. input terminals, being careful to observe the proper polarity. The setup for a.c. testing is the same, except that *S2* is set for "A.C.," and the a.c. input terminals are used.

Turn on the equipment under test and slowly reduce the value of *R3* (thereby reducing the load resistance of *Q1*). An appropriate voltmeter (d.c., a.c., or audio) connected to the input terminals in use, together with the internal ammeter, will show the output and/or regulation behavior of the unit being tested under increasing load.

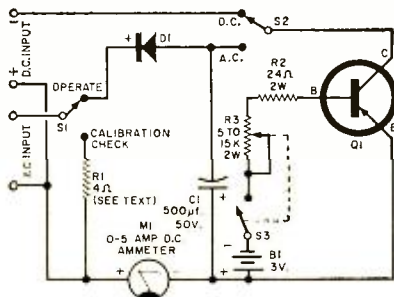
**Calibration.** To calibrate *R3* for specific amplifier load resistances, terminate the amplifier with a resistor of known



Parts are not critical, but *D1* and *Q1* depend on maximum voltages and currents needed. Resistor *R1* checks calibration.
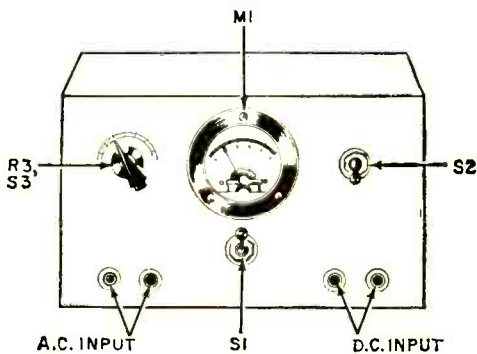
## PARTS LIST

- B1*—3-volt battery (two 1½-volt flashlight cells in series)
- C1*—500-µf., 50-volt electrolytic capacitor
- D1*—1N13-11 diode (see text)
- M1*—0-5 ampere d.c. ammeter
- Q1*—2N554 transistor (see text)
- R1*—4-ohm resistor (see text)
- R2*—24-ohm, 2-watt resistor
- R3*—5000 to 15000 ohm, 2-watt potentiometer (with switch *S3*)
- S1, S2*—S.p.d.t. toggle switch
- S3*—S.p.s.t. switch
- Misc. Binding posts, transistor mounting kit, hardware, etc.



Suggested front panel layout for a.c.-d.c. electronic load. Components may be housed in any convenient metal box.

value (say 4 ohms) and connect an audio voltmeter across this load. Feed a 1000-cycle signal into the amplifier and adjust the output to some convenient voltage (say 4 volts). The resistor's power rating should be much greater than the power it will dissipate ( $P = E^2/R$ ) to avoid undesirable heating.

Now disconnect the load resistor and connect the amplifier to the a.c. terminals of the electronic load, leaving the voltmeter in the circuit. Set the controls of the load for a.c. operation as described above, and adjust  $R3$  to obtain the same voltage—in this case, 4 volts. This position of  $R3$ 's pointer may now be marked

“4 ohms.” Repeat the procedure with other appropriate load resistances, such as 6, 8, and 16 ohms.


Resistor  $R1$  can be used to check the calibration at any time. A value of 4 ohms is shown for  $R1$  in the schematic, but any value at which  $R3$  is calibrated may be used. The calibration check is made using the same procedure as in the actual calibration, except that built-in-resistor  $R1$  is connected and disconnected by switch  $S1$ .

**Choosing Semiconductors.** The selection of diode  $D1$  and power transistor  $Q1$  depends on the voltage and current levels at which you will be working.

For  $Q1$ , a transistor such as the Motorola 2N554 (maximum voltage, 28 volts; maximum current, 3 amperes) is a good choice. In spite of the relatively high voltage and current maximums of the 2N554, the voltage-current product (power) should not exceed 10 watts on continuous duty; for instantaneous use, this figure can be increased to about 40 watts. Be sure to use the heat sink recommended by the manufacturer and to keep your tests as short as possible.

Diode  $D1$  should have voltage and current ratings consistent with those of the transistor. To match the 2N554, you'll find that the International Rectifier 1N1341 is a good bet. —30—

## TRANSISTOR SAVER

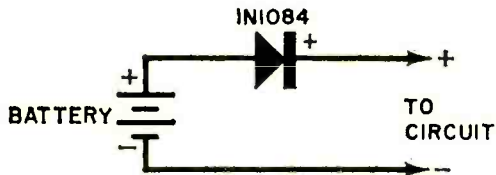

The “one-way” current-carrying property of a diode can be used to keep the transistors in an experimental circuit or in any transistorized piece of equipment from being ruined because of accidentally reversed battery polarity.

Simply place the diode in series with the battery's positive lead as shown in the diagram, and current will flow only in the direction indicated by the arrow in the diode's symbol. If it's

more convenient to wire the diode into the negative battery lead, install it so that its positive side connects to the negative terminal of the battery.


Though the diode presents a high resistance to current flow if the battery is connected in reverse, its resistance to current flowing in the correct direction is much lower. The voltage drop across a 1N1084 is only about ½ volt for a current of 30 ma., and it will be no more than 1 volt as the current is increased to 4 amperes.

The 1N1084 is not the only diode which can serve as a transistor saver, but check the one you plan to use for excessive voltage drop. A 1N60, 1N34A, 1N64, or 1N38B, for example, will develop a 4- or 5-volt drop with a current of 75 ma. —George E. Lang


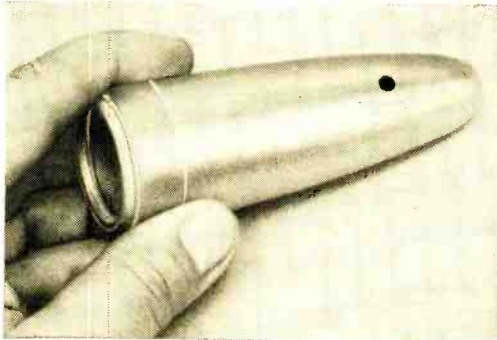
## FIRST MIKE KIT

**CBS Electronics offers ceramic microphone  
in easily assembled form**






Circular hole in case can be closed up with small screw.

IT is getting so that just about everything in electronics is available in kit form. This "adage" holds true even with microphones, since CBS Electronics has just introduced the "Mark III" ceramic microphone kit. Selling for \$7.50, the kit can be assembled in less than 20 minutes—there are only eight steps in the assembly process, including two solder connections. This kit is one of a variety of new items offered by CBS Electronics (Danvers, Mass.).

The "Mark III" is very sensitive and suitable for use with tape recorders, ham or CB transmitters, and dictation machines. Mounting of the ceramic element in the case is somewhat unconventional in that multiple vents

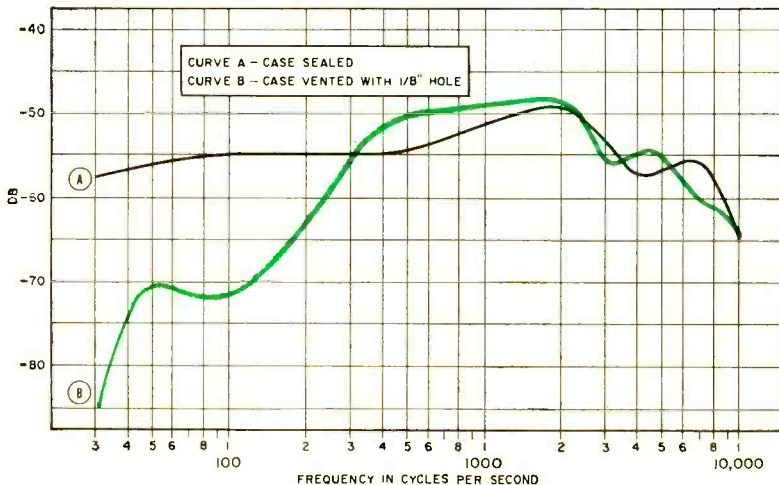Response of "Mark III" microphone may be altered by use of small vent in case (see photo, above left). When case is vented, bass response is greatly attenuated and voice frequencies between 300 and 2500 cycles are emphasized.



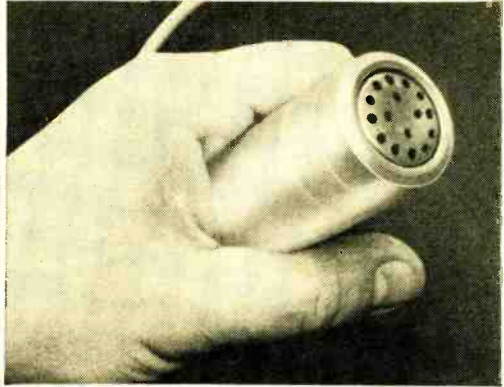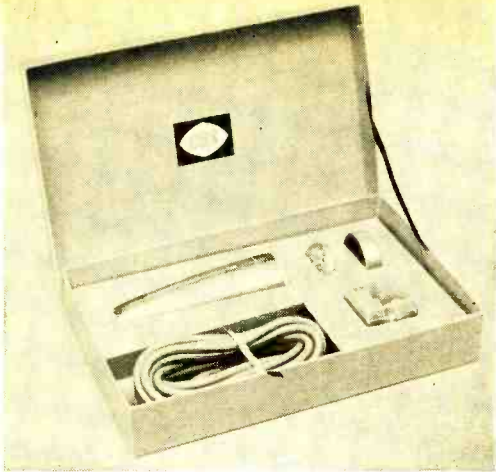

The eight pieces of the "Mark III" kit can be assembled in 20 minutes; assembled mike is semi-directional in position shown above, right, and omnidirectional when held vertically.

have been provided behind it to smooth out the response curve. Small bits of plastic foam are stuffed in the mike shell to eliminate a hollow sound.


In addition to these multiple vents, CBS recommends drilling a  $\frac{1}{8}$ " hole in the lower part of the microphone case, and tapping it to accept a small screw. This special vent relieves pressure behind the diaphragm attached to the ce-

ramic element. When the hole is open, bass response is reduced nearly 17 db at 100 cycles, making voices sound sharp and crisp. Closing the hole with the screw restores the bass response. The effect is similar to baffling and unbaffling a hi-fi speaker.

Assembling the "Mark III" takes much of the mystery out of microphones. We found it fun.

-30-

## STORAGE BATTERY TESTER

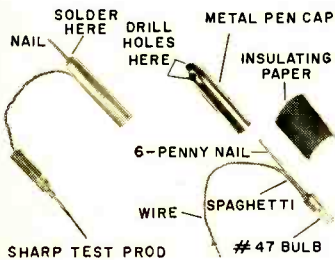

You can locate bad storage battery cells quickly with this simple tester made from a few junkbox parts. Just solder a 5" length of flexible wire to the base of a #47 (6-8 volt) bulb, and slide a 2" piece of spaghetti over the joint. Then sweat the head of a 6-penny finishing nail onto the bulb's center contact.

A metal pen cap houses the lamp assembly—make a hole in the tip large enough for the nail to pass through, and another one on the side, near the tip, for the wire. Now wrap the base of the bulb with insulating paper, and slide the cap over the assembly, maneuvering the wire through the side hole as you do so. With about 1" of the nail protruding through the tip of the cap, solder the nail to the cap. Finally, install a sharp test prod on the free end of the wire.

To test a cell, locate its two terminal posts by the bulges they make under the soft compound covering the top of the battery. Push the nail and the test prod through the compound so that each makes contact with a terminal, and note the brightness of the lamp. Check the other cells in the same way; if one of them shows a much dimmer glow than the others, it may be defective.

—I. C. Chapel



# Across the Ham Bands

By  
**HERB S. BRIER**  
W9EGQ

## HOW TO AVOID VIOLATING AMATEUR REGULATIONS

**E**VERY FEW MONTHS, the FCC issues a list of hams who have lost their licenses for various lengths of time because of serious violations of the amateur regulations. The one thing these hams have in common is that their violations are almost always deliberate—so you need not waste any tears over them. It might be wise, however, to review some of the ham regulations which are often innocently violated, so that you won't be among the approximately 6000 hams who will receive some sort of violation notice this year.

**Licenses and Photocopies.** Amateur regulation 12.25 states: "The original operator license of each operator shall be kept in the personal possession of the operator while operating an amateur station." Many hams never seem to have their licenses with them when they operate mobile or portable, or want to operate another ham's station. When I

pointed out this requirement to one such ham, he protested.

"I don't want to wear out or lose my ticket carrying it around with me," he said. "I'll get a photostat."

But 12.25 continues: "... No recognition shall be accorded to any photocopy of an operator license; however, nothing in this section shall be construed to prohibit the photocopying for other purposes of any radio operator license."

A photocopy of your license will come in handy if you want another ham to operate your station when you are absent and have your license with you. For example, you might want to go on a trip and arrange for another ham to use your rig so that you can work it from your mobile or portable transmitter—or from another ham's station. Before you go,

## .....Ham of the Month.....

On the air, Elmer E. Tafinger, W9GRN, is called "Mike"—short for "Michaelangelo"—because he is a well-known artist and art teacher. Mike's interest in short-wave radio began during World War II, when he monitored enemy broadcasts to get prisoner-of-war lists for a newspaper. He received his ham license in 1949.

Mike's ham station is located in a downtown Indianapolis studio. His states-worked total matches the number of stars on his flag—48, but he worked Alaska and Hawaii many times before they became states. A good place to find W9GRN is on the 75-meter phone band late at night, after his art classes are over.

W9GRN's experience as an artist, magazine illustrator, art director for the theatrical productions of the late David Belasco, foreign traveler, lecturer, and art instructor provides him with an endless range of subjects to talk about. Most hams, on learning that Mike is an artist, first ask what his girl models wear while posing; they are less interested in the fact that Mickey Hargity, husband of Jayne Mansfield, began his climb to fame from Mike's modeling stand.

Mike is always ready to help prospective hams get their licenses—more than one Indianapolis ham credits his call letters to Mike's tutoring.



Photo by Frank, W9EJW



Floyd, KN5CWS, has a record of over 800 contacts, 50 of them representing DX from 17 countries and 5 continents. He uses a Johnson Ranger transmitter and a Hallicrafters SX-28 receiver.

Chet, WA2LOC, made over 300 contacts in 2½ months as a Novice on 40 meters. Since he became a General, his Heath-kit DX-40 and Hallicrafters SX-99 have worked 22 countries on 20 meters.



post a photocopy of your license in a conspicuous place in your station (regulation 12.69). Also instruct the ham operating your station to have his own license with him, to use your call letters—not his own, and to keep up and sign your station log.

If you have difficulty getting a copy of your license made because the copying firm believes that making such a duplicate violates some federal law, show him this column or section 12.25 of the amateur regulations.

**Operating Other Stations.** There are two ways in which you can get into trouble operating someone else's station: (1) visiting a prospective ham who has a rig but no license and making a few contacts using your own call letters; and (2) visiting another ham and operating his station on an amateur band or mode of transmission not authorized by the other ham's *station* license or your own *operator* license.

The first situation is completely prohibited—no class of license authorizes anyone to operate an unlicensed station. In the second case, while any ham can operate another ham's station, you can do so only on bands and modes of transmission authorized by your own *operator* license or the other ham's *station* license—whichever has the most restrictions.

**Mobile and Portable Operation.** On c.w., you identify mobile or portable operation by following your station call letters with the fraction code symbol (DN) and the number of the call area in which you are operating. On phone, your call letters should be followed by an announcement of the geographical location in which the mobile or portable

operation is taking place. For example: ". . . This is W3DEF operating mobile 3 miles north of Bethesda, Md."


Special rules govern mobile operation aboard a vessel on the high seas or an aircraft on an international flight. They require that you send "/MM" or "/AM" after your call letters on c.w. or announce "Aeronautical Mobile" or "Maritime Mobile" at the end of each phone transmission. Also on either phone or c.w., the name or number of the vessel or aircraft and its approximate geographic location must be given immediately prior to the sign-off at the end of each contact.

These special rules apply only to operation outside the continental United States. Mobile operation from boats and aircraft within the United States is treated like mobile operation on land. This is important, because U.S. mobile operation is restricted to the 10- and 15-meter bands in many areas, and is never permitted below 7 mc. (See regulation 12.90, paragraph 2.) If you operate from your boat or a plane in the U.S. and sign "Maritime Mobile" or "Aeronautical Mobile" instead of plain "Mobile," you might find yourself telling the FCC why.
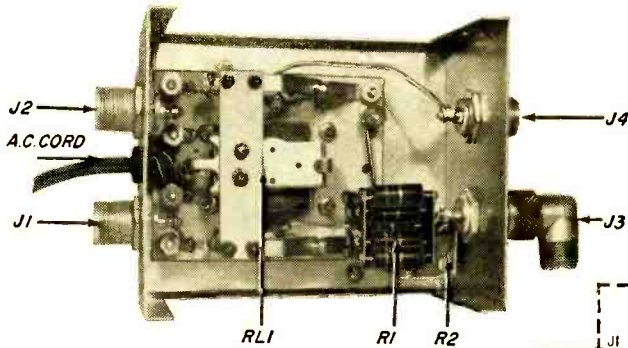
#### LOW-POWER/HIGH-POWER RELAY

This month's construction project, a low-power/high-power relay, was built






Relay circuit for automatically switching r.f. power amplifier in and out of transmitter. If attenuation is not required, substitute a short bus wire for R1 and omit R2.

by Jim Manning, K9RUH, to permit feeding his antenna directly from his exciter for local contacts or from his power amplifier for DX contacts. It's an easy-to-build unit which lets you comply with FCC regulations by using the minimum transmitter power necessary for satisfactory communications.

When the relay is not energized, the exciter feeds the antenna directly. In the energized position, the output of the exciter is transferred to the amplifier input circuit (either directly or through the optional power attenuator) and the antenna is switched to the amplifier output circuit. The relay is connected to the 117-volt primary circuit of the amplifier's power supply and the switching takes place automatically when the amplifier is turned on.

**Construction.** Mount the 117-volt, d.p.d.t., antenna changeover relay (RL1) on one-half of a two-piece 3" x 4" x 5" utility box, using 1/2" spacers to center it. Then mount two coaxial connectors on each end of the box, keeping each set of connectors at least two inches apart; in this way, the chance of r.f. feedback between the input and output connectors is minimized. A 3/8" hole lined with a rubber grommet accommodates the coil leads.

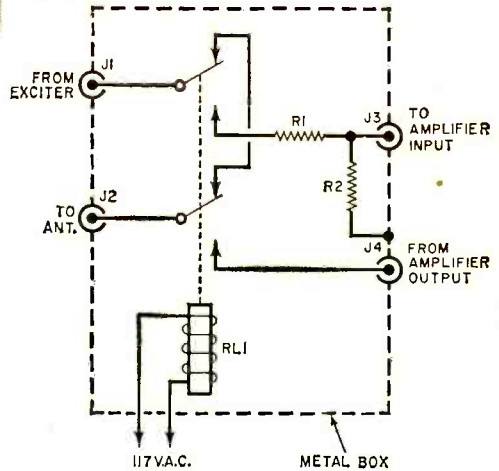Use No. 14 or No. 12 solid copper wire to connect the movable contacts of the relay to the connectors (J1, J2) on one end of the box. Join together the normally closed relay contacts, and connect the normally open contacts to the remaining coaxial connectors (J3, J4), keeping the leads short and well separated. These are the proper connections for driving practically any grounded-



#### PARTS LIST


- J1, J2, J3, J4—Chassis-type coaxial connectors (Dow-Key DKC-P or equivalent)
- \*R1—Ten 330-ohm, 2-watt, composition resistors connected in parallel
- \*R2—Five 150-ohm, 2-watt, composition resistors connected in parallel
- RL1—D.p.d.t., ceramic-insulated antenna changeover relay; approx. 2" spacing between poles; 117-volt a.c. coil (Ameco #51 or equivalent)
- 1—5" x 3" x 3" two-piece aluminum utility box (Bud CU-2105A or equivalent)
- \*4—Squares of "flashing" copper; two 1 1/2" and two 3/4"
- Misc.—3/8" grommet, 1/2" spacers (four), #14 or #12 solid copper wire

\*Parts used for optional attenuator

grid power amplifier with an exciter having an input power rating up to 200 watts.

**Attenuator.** To drive a grounded-cathode amplifier using tubes like 813's, 4-250A's, etc., with an exciter delivering much more than 10 watts output, you will need a power attenuator between the exciter and the amplifier to absorb some of the excess power.

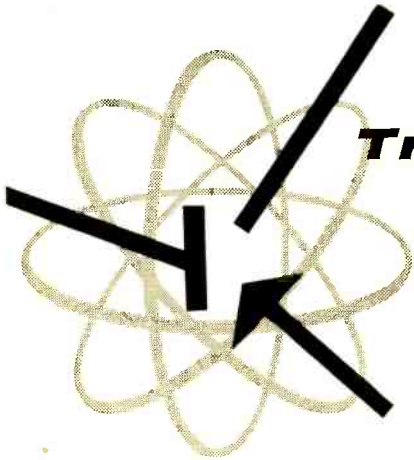To build the attenuator, place two 1 1/2" squares of "flashing" copper to  
(Continued on page 115)



# Transistor Topics

By LOU GARNER

**N**O MATTER how imposing they may appear, few—if any—digital electronic computers are inherently complicated. As discussed in an earlier column (October, 1960), their apparent complexity results from the multiple use of a few basic—and relatively simple—circuits. By way of comparison, a Citizens Band transceiver may use a greater *variety* of basic circuits than a typical computer. In the transceiver, each basic type of circuit is used only once or twice,

while in the computer the same circuit may be repeated dozens—or even hundreds—of times.

With only a few basic circuits needed, the customary procedure has been to preassemble these basic circuits on individual circuit boards as modular *elements* using printed-circuit techniques. Each board or element contains all the resistors, capacitors, transistors and diodes needed for a specific circuit function. Afterwards, the designer interconnects as many—or as few—of these digital elements as are needed to assemble a computer, test instrument, or automatic control circuit.

With military and industrial users of digital elements demanding high-speed operation, tight tolerances, and stable performance over wide temperature ranges, circuit-board manufacturers—in the past, at least—have been forced to use silicon transistors and other expen-

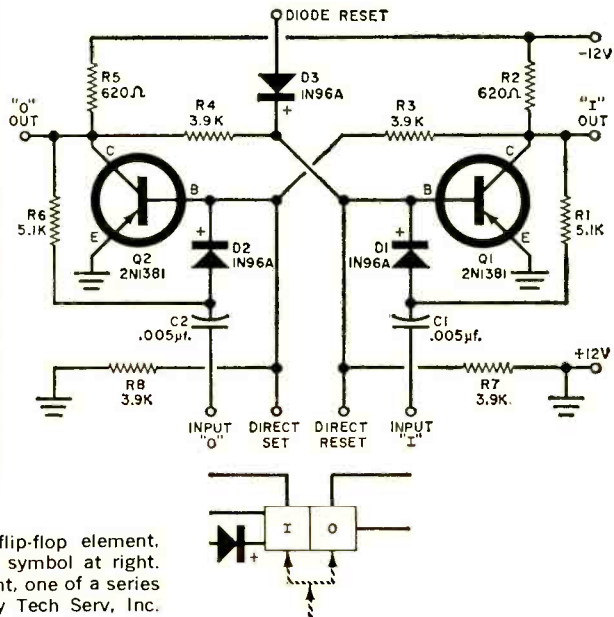
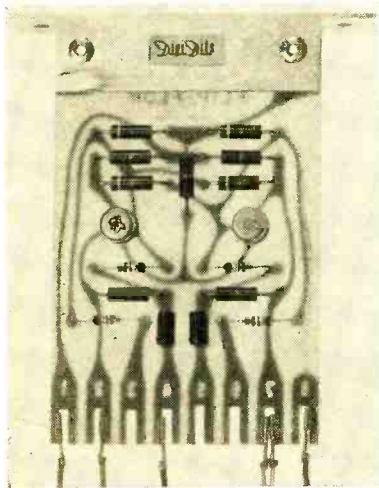


Fig. 1. Schematic diagram of DigiBit flip-flop element, shown with its functional block diagram symbol at right. Photo above shows typical flip-flop element, one of a series of low-cost digital elements produced by Tech Serv, Inc.

sive components in their products, with correspondingly high element prices. A single industrial-quality flip-flop, gate, or amplifier element, for example, might cost as much as forty or fifty dollars. With from two to as many as dozens of elements required for a single project, overall costs mount into the hundreds—or even thousands—of dollars.

Recognizing the increased interest in digital techniques on the part of hobbyists and educators, and realizing that the tight performance specifications demanded in military and industrial equipment needn't apply to elements designed

basic arrangements needed in digital circuit work, including flip-flops, "And" gates, "Or" gates, inverters, emitter followers, indicators, relay drivers, controls, and clocks (multivibrators).\*

Although each circuit package is completely assembled and attached to a mounting bracket, the element prices are not appreciably more than the cost of the individual components (transistors, diodes, resistors, etc.) would be if they were purchased separately at regular net prices. Typical DigiBit prices range from \$7.95 for a multivibrator or diode "Or" gate to \$9.95 for a flip-flop or three-section inverter amplifier, with an overall average of less than \$10.00 per element package.

The schematic diagram of a DigiBit flip-flop element is shown in Fig. 1, along with its functional block diagram symbol. The diode "And" gate element, shown schematically in Fig. 2, consists of both 2-leg and 3-leg gates mounted on a single circuit board and, if desired, can be used as a single 5-leg gate; the block diagram symbols appear below the schematic diagram.

Physically, the elements are quite easy to use. The mounting bracket serves as a ground connection for each circuit board, with individual connections made by means of solderless "Edg-on" jumper leads. Using these techniques, it's a simple matter to assemble a complete binary counter or test instrument in a matter of minutes. Operating power can be obtained from standard dry cells, except when a large number of elements are involved (here, the manufacturer recommends a storage battery or 12-volt regulated supply).

Although the DigiBit elements can be used for assembling complete digital computers, most individual experimenters probably will prefer to assemble simpler (and less costly) projects requiring, at the most, four or five elements . . . at least at the beginning. The range of possible projects is limited only by the imagination and skill of the individual hobbyist. Typical projects include electronic "games," simple counters, automatic controls for model railroads, and useful test instruments for the elec-

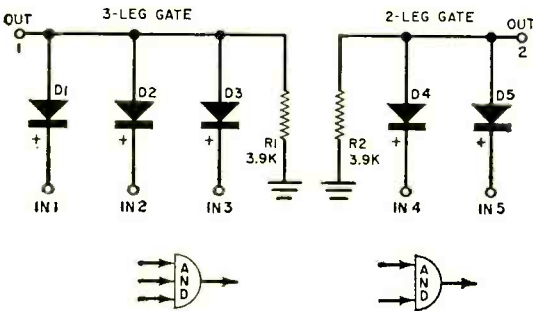


Fig. 2. Schematic diagram of DigiBit 3-leg and 2-leg diode "And" gates, with their corresponding block diagram symbols.


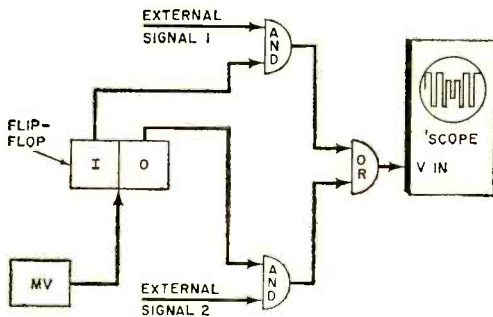
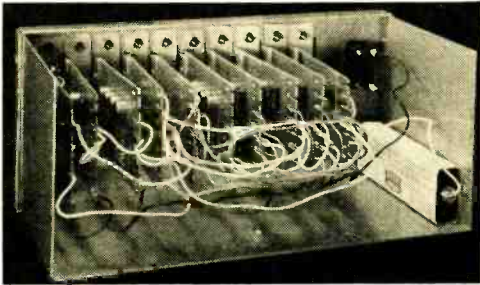


Fig. 3. Block diagram of a simple electronic switch made up of several DigiBit elements.

for hobbyist or school use, one manufacturer, Tech Serv, Inc. (4911 College Ave., College Park, Md.) has recently introduced a complete series of low-cost digital elements for the serious student and advanced experimenter. Dubbed *Digi-Bits*, these elements are offered in all the

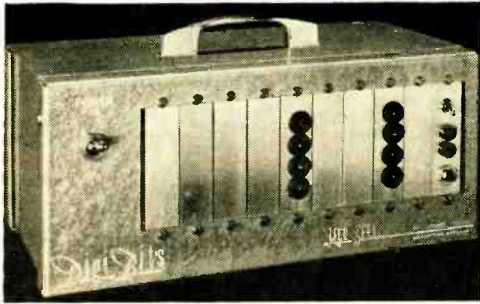\*DigiBits were mentioned briefly in our April column when they were first put on the market.



External and internal views of low-cost, portable binary counter assembled with DigiBit elements. Solderless clip-type connectors are used to interconnect individual circuit boards.

tronics workshop, such as electronic switches, oscilloscope calibrators, square-wave generators, pulse generators, and so on.

One typical project is shown in block diagram form in Fig. 3. Here, a clock (or multivibrator) element is combined with a flip-flop, a pair of "And" gates, and a single "Or" gate as an electronic switch for an oscilloscope, permitting two external signals to be displayed alternately on the CRT. In operation, the multivibrator (*MV*) triggers the flip-flop and this, in turn, "unlocks" first one "And" gate, and then the other, allowing the two external signals to pass alternately to the "Or" gate, where they are combined and applied to the 'scope's vertical input terminals. In many cases, the flip-flop may be eliminated, with the multivibrator driving the two "And" gates directly; thus, only three elements are needed for assembling the instrument.

The complete line of DigiBit elements and accessories is described in a six-page folder, available from the manufacturer at no charge. In addition, Tech Serv offers a 55-page "Instruction and Applications Manual," priced at \$1.00 per

copy, postpaid—it describes a number of practical projects that can be assembled with DigiBit elements.

**Reader's Circuit.** Circuits submitted by readers and featured in this column are derived, originally, from several different sources. Most are modifications or adaptations of circuits which readers have seen described in books or magazine articles. A lesser number are circuits discovered "by chance" while experimenting with various breadboard arrangements. A still smaller number are original designs developed by investing long hours in study and laboratory tests. On occasion, though, we'll receive a circuit "discovered" by a reader in a

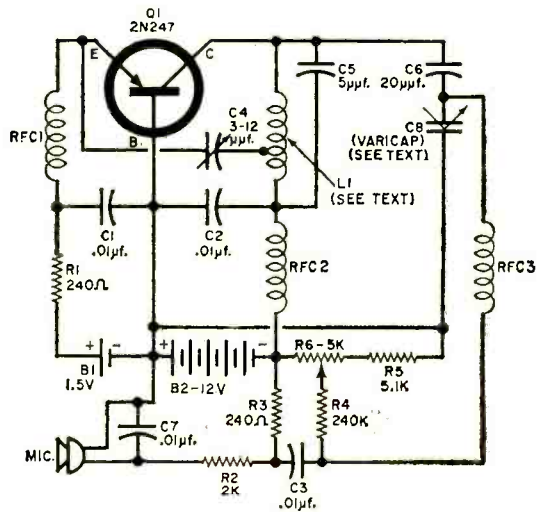


Fig. 4. Simple FM transmitter circuit sent in by reader/author E. G. Louis utilizes a power transistor and PSI Varicap capacitor.

manufacturer's technical bulletin or in a high-brow professional journal having limited circulation.

The simple FM transmitter shown in Fig. 4 was brought to our attention by reader/author E. G. Louis, who found it in a technical bulletin distributed by Pacific Semiconductors, Inc. (14520 Aviation Blvd., Lawndale, Calif.). This firm manufactures a number of interesting semiconductor devices, including a high-power r.f. transistor.

Transistor *Q1* is used in the common-base arrangement as a modified Hartley  
(Continued on page 113)



By  
**JOHN T. FRYE**  
W9EGV

## **Carl and Jerry**

### **First Case**

**I**T seemed odd. For years Carl and Jerry had dreamed of how "super" it was going to feel to be out of high school. Now, with graduation only a week behind them, they were bored and ill at ease in their new freedom. Playing with electronics and performing entertaining experiments, into which they had entered with such zest before, had suddenly become "kid stuff."

The boys felt that they should be earning money to help with their college education. But since they were going to the university in the fall, there was no point in trying to get a regular job—even if they could have found one. Business conditions were still slack in the community, and a week's search had convinced them that no part-time jobs were available.

So they decided to go into business for themselves. They spent a whole half-day carefully lettering a sign and neatly erecting it in Jerry's front yard:

#### **C & J Electronic Laboratories**

Let Us Solve Your  
Problem Electronically

(Please Use Basement Entrance)

On this bright June afternoon Carl and Jerry were sitting in their basement laboratory hopefully waiting for the world to beat a path to their door; but they were genuinely surprised when they heard light footsteps descending the outside stairs and a young slip of a girl—she could not have been more than twelve or thirteen—stood framed in the doorway. She was dressed in a white blouse and loud-checked tapered pants, and she leaned with studied casualness


against the door jamb. Peering in at them with a pair of blue eyes beneath a Veronica Lake mop of blonde hair, she said in a voice pitched surprisingly low for a child:

"Helooo, boys. I have a problem."

She waited expectantly. Jerry recovered first from his astonishment and invited, "Won't you come in and tell us about it?"

She minced over to the leather-covered couch in a walk that was a rather ludicrous imitation of the slinky gait of a 1930 movie vamp, then sat down and crossed her long thin legs.

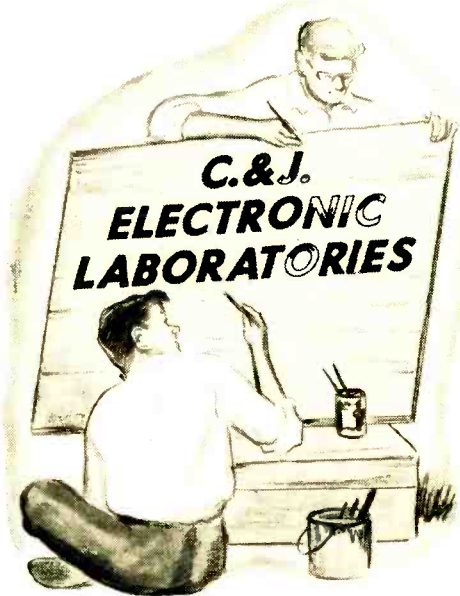
"Listen close, boys," she began in that strange, husky voice; "I'm expecting an important call and can't stay long. My name is Hall, Loree Hall, spelled



L-o-r-e-e; we moved into that big brown house across the street in March. Now I get a real blast out of detective programs on TV, but lately something has been clobbering my favorite program, 'The Private Eye Playboy,' on Channel 6 every Monday night. This interference occurs only when PEP—that's what I call 'Private Eye'—is on, and it completely blacks out the picture.

"At first I thought you two were causing the interference, since I'm told you noodle around with radio and stuff like that. But last Monday evening you were both out in front playing catch when it happened, so that gives you an air-tight alibi. What I want you to do is find out who or what is jamming my program and put a stop to it. No questions will be asked as to how you do it."

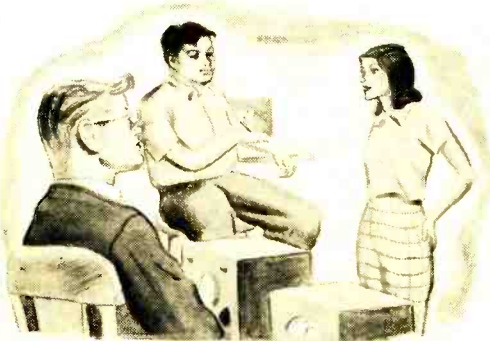Carl and Jerry exchanged glances, trying to conceal their amusement. The



girl tugged a little coin purse out of her pocket and extracted two limp dollar bills, holding them out to Carl. "I have a good income, and I'm willing to pay any reasonable amount," she said with great dignity. "Please consider this a retainer."

"Aw—we can't—I mean—professional ethics do not permit us to accept a retainer until we decide to take your case," Carl sputtered, backing away.

"Very well," the little girl said as she stood up. "Suppose you come over tonight a little before 7:30 and see for yourself. I'll be expecting you, gentlemen."

Just as she reached the door, the boys heard a woman's voice calling impatiently: "Laura, where are you? You come here right now and finish straightening up your room!"

"I'm coming, Mother," the girl answered, in a voice that suddenly rose to a normal childish treble. She forgot her siren-slink and took the steps two at a time.

"Man, what a performance!" Carl chuckled. "I'd say that there is a little girl who has been over-exposed to TV dramas. What do we do?"

"Help the maiden in distress," Jerry answered promptly. "After all, she's our first and only client; so we can't be choosy. Anyway, my curiosity is aroused. I'll meet you here about a quarter of seven. Bring along your portable TV."

**M**R. and Mrs. Hall, a pleasant-looking young couple, were sitting on their front-porch glider when Carl and Jerry walked across the street.

"You must be the young men Laura says are going to help her with her television problem," Mr. Hall said as he shook hands with them. "I certainly hope you can. Her imagination scares me sometimes, but she's a good child and gets a lot of pleasure from her TV programs. Laura," he called, "you have company!"

The little girl, wearing a sheath-like dress that looked a little old for her, ushered them up the stairs to her large, airy bedroom. As she snapped on her TV receiver, she turned to them and asked in the voice that had returned to its low-pitched huskiness: "Like a drink, fellows? Coke? Pepsi? Lemonade?"

"No, thanks," Jerry replied without cracking a smile. "We never drink when we're on a case."

Soon the station-break flurry of commercials was over, and "PEP" began with a long-shot of a pretty girl sunbathing on a lonely beach. At this instant the picture suddenly flashed and turned to a negative, the white and black tones reversing. The condition persisted long enough for Carl to turn on his portable receiver and find that the picture on it was about the same. When he moved over near the door, however, the interference was not quite so bad. He manipulated the fine-tuning control far to one side and heard a voice faintly giving some call letters; then both pictures snapped back to normal.

"Hey, that's Eddy!" Carl exclaimed

(Continued on page 104)

Now...assemble the finest:  
A Professional Quality  
CUSTOMIZED

# TV KIT

ON EASY  
"PAY AS YOU WIRE" TERMS \*

- ☆ Designed for the perfectionist seeking maximum performance.
- ☆ Easy to assemble; no technical knowledge required.
- ☆ An ideal "Learning" Kit with a complete Course of Study is available.


### Professional Quality Features

The Transvision "Professional" Model TV Kit (or Assembled Chassis) is designed to satisfy those video-and-audiophiles who seek the best possible performance of which the art is capable. Nevertheless, the kit builder can assemble this chassis for less than the cost of an ordinary receiver.

Note these unique features:

- Hi-Fi Audio (with 2 EL-84 output tubes, oversize audio output transformer, Woofer-Tweeter Speaker System with heavy magnets and cross-over; Extended Range Tone Control).
- Ultra-linear sweep circuits; D.C. restoration; Standard Coil Guided Grid Turret Tuner with provisions for UHF and special low noise tubes; 4 megacycle picture bandwidth; 10 microvolt sensitivity.
- Heavy-duty power supply (power transformer, two low voltage rectifier tubes — no silicon rectifiers).

The TRANSVISION  
"Professional"

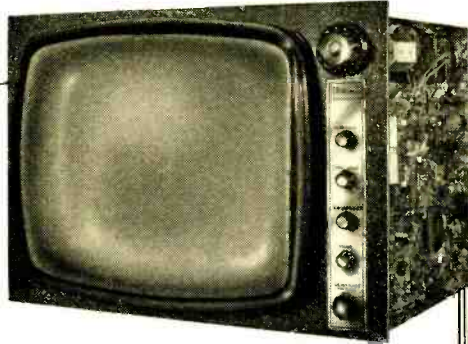

\* Only \$15 for the Starting Package!

**ALSO AVAILABLE AS AN  
ASSEMBLED CHASSIS**  
for custom installations

- Heavy-duty ruggedized construction, no printed circuits; built to give trouble-free performance for many years.
- Includes newest reflection-free 23" tube with bonded face, or the 24" or 27" CRT.
- Selected because of superior performance for use in Educational TV by over 3000 schools and colleges and U.S. Armed Services.

### Interested in Electronics?

Learn the basic principles of electronics from the Complete Course of Study which is available with the Kit.



As a preliminary, order the Assembly Instructions for only \$2.00; to be refunded if you purchase kit.

## TRANSVISION

Pioneers in Television Kits

NEW ROCHELLE, N. Y.

• NEW ROCHELLE 6-6000

----- START NOW — MAIL THIS COUPON -----

TRANSVISION, New Rochelle, N. Y.

Dept. P E

- Send Free 8-page Catalog       Enclosed is \$2. for Assembly Instructions so that I might see how easy it is to assemble the Transvision Kit. I understand that this will be refunded if I purchase a kit.
- Enclosed is \$15 for the Starting Package. I understand that I can buy packages one at a time as I wire. (Models range from \$119 to \$199.)

Name..... Address.....  
City..... Zone..... State.....

Only Heath offers  
Top Quality at the  
Lowest Price, and . . .



**NOW**—*we guarantee you*

**At your service . . .**

**THE NEW HEATHKIT AUTOMATIC GARAGE DOOR OPENER!**

Compare price, compare features, and you'll buy this latest Heathkit labor-saving wonder! Opens and closes all overhead track-type doors up to 8' high automatically! Garage light turns on when door is open, stays on for short period after door closes! Safety release device. Adjustable operating force! Tone-coded "hi-power" 6 or 12 v transmitter and special receiver prevents interference. Easy one-man assembly. All parts included. 65 lbs.


Kit GD-20 (mechanism, transmitter, receiver) . . .  
\$11 dn., \$10 mo. . . . . **\$109.95**  
Kit GDA-20-1 (extra transmitter) . . . \$2.50 dn., \$5 mo. . . . **\$24.95**



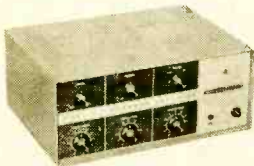**BIG-BUY PORTABLE 4-TRACK STEREO TAPE RECORDER**

All-in-one monophonic or 4-track stereo tape record and play-back! Two tape control levers; individual tone balance and level controls; monitoring switch for listening while recording; "pause" button for editing; two "eyes" to check recording levels. Also functions as "hi-fi stereo center" for record players, etc., or to feed tape music to separate hi-fi system. Parts for all amplifiers and speakers included; turquoise and white cabinet and 3 3/4"-7 1/2" speed tape deck are assembled. Less mic.

Kit AD-40 . . . 49 lbs. . . \$18 dn., \$16 mo. . . . . **\$179.95**  
Assembled ADW-40 . . . 49 lbs. . . \$30 dn., \$26 mo. . . . **\$299.95**




**NEW HIGH FIDELITY PA AMP.**

Heath exclusive; 20 watt *hi-fi* rated PA amp. Two inputs; equalization switches; electrical mixing; sealed "pads"; tape recorder, line, and voice coil output. Plug-in, low-Z mic. Xformers separate. 24lbs.  
Kit AA-31 . . .  
\$6 dn., \$6 mo. . . . . **\$59.95**  
Mic. Xformers. AN-11 **\$11.95**

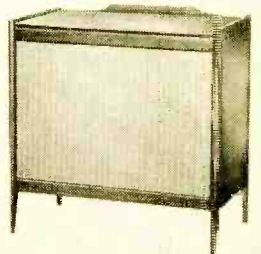**"LEGATO-COMPACT"**

All Altec Lansing speakers! 2-12" hi-compliance woofers; exponential horn and driver; range 30-22,000 cps; assembled. 800 cps network. 30 watts program; 16 ohm Z. Assembled, finished cabinets: 32" x 19" x 32 3/4" h 132 lbs.  
Kit AS-21U, unfin. **\$224.95**  
Kit AS-21W, wat. **\$229.95**  
Kit AS-21M, mahog **\$229.95**



**HEATH COMPANY** Benton Harbor, Michigan

a subsidiary of  
**DAYSTROM, INCORPORATED**





Introducing a new styling concept in two popular Heathkit Stereo Units



Here's a handsome matching pair for your new Heathkit stereo system! Both have new lowered wrap-arounds of luggage-tan vinyl-clad steel with contrasting charcoal-grey front panels framed with polished aluminum bezels... a regal new look to Heath's medium-price stereo line.

### HEATHKIT AJ-11 AM/FM TUNER

Successor to the popular AJ-10, this new version features fly-wheel tuning, two "magic-eye" tuning indicators, adjustable FM automatic frequency control. AM "fidelity" switch for max. selectivity or fidelity. dependable 12 tube circuit, built-in power supply. 21 lbs.

Kit AJ-11... \$7 dn., \$7 mo. **\$69.95**  
 Assembled AJW-11... \$13 dn., \$11 mo. **\$129.95**

### HEATHKIT AA-151 28-WATT STEREO AMPLIFIER

Here's the popular SA-2 model all dressed up in brand-new styling. Delivers 28 hi-fi rated watts (14 per channel) for plenty of power. Has clutched volume controls, ganged tone controls, 4 dual inputs. 28 lbs.

Kit AA-151... \$6 dn., \$6 mo. **\$59.95**  
 Assembled AAW-151... \$12dn., \$11mo. **\$119.95**

*can build any Heathkit!*



### IGNITION ANALYZER

Switch to primary, secondary, parade or superimposed patterns. See condition of plugs, points, wiring, coil & condenser. Plug-in ID-11 Timing Light available. 15 lbs.

Kit IO-20... \$9 dn. **\$89.95**  
 Assembled IOW-20. **\$169.95**



### NEW TELEPHONE AMPLIFIER!

Hands-free phone chats! Ideal for conferences, dictation, etc. Place handset on cradle, unit turns on, instantly ready! All-transistor; long-lasting battery power. Easy to build. Ivory color.

Kit GD-71... 4 lbs. **\$19.95**



### LOW COST DEPTH SOUNDER

Best value in marine electronics. Detects fish, submerged objects, and bottom depth. Big 4 3/4" dial calibrated from 0-100'. 6-transistor circuit, battery powered. Corrosion & splash-resistant aluminum cab. Transducer included. 9 lbs.

Kit MI-10 \$7 dn., \$7 mo. **\$69.95**



### LOW COST 3-BAND MARINE RDF

Deluxe features at minimum cost. Covers 200-400kc beacons, 550-1600 kc broadcast, 1700-3400 kc marine band. Loop and "sense" antennas eliminate double null. 9-transistor circuit, battery powered. Pre-assembled tuning unit.

Kit DF-3 12 lbs. \$10 dn. **\$99.95**

### You get guaranteed success with Heathkit!

Never before has a manufacturer of do-it-yourself kits guaranteed your success in completing a project. Heath does so and backs it up with an iron-clad, money-back guarantee! By making this guarantee, we hope to banish any doubt you may have about your ability to build a kit. How is such a guarantee possible? The careful planning that goes into the design of Heathkit equipment revolves around this paramount thought—anyone, regardless of background or experience, must be able to build any Heathkit. This same thought guides the writing of the detailed Heathkit assembly instructions with the world famous "check-by-step" system. These attributes plus the experience of a million customers attests to the fact that anyone can build a Heathkit. Order your favorite Heathkit today. Enjoy top quality equipment with savings of up to 50% and the satisfaction of doing it yourself. Get guaranteed success with Heathkit!

### MONEY BACK GUARANTEE

The Heath Company *unconditionally guarantees* that you can build any Heathkit product and that it will perform in accordance with our published specifications, by simply following and completing our check-by-step instructions, or your purchase price will be cheerfully refunded.

### FREE Catalog!



Contains complete descriptions and specifications on all of the above new models plus more than 200 other famous Heathkit items. Send for your free copy, use the coupon below; see how you can enjoy top quality equipment with savings of up to 50% with Heathkit!

Ordering Instructions: Fill out the order blank. Include charges for parcel post according to weights shown. Express orders shipped delivery charges collect. All prices F.O.B. Benton Harbor, Mich. A 20% deposit is required on all C.O.D. orders. Prices subject to change without notice. Dealer and export prices slightly higher.

Please send the following items:

Item	Model No.	Price

Order direct by mail or see your Heathkit dealer.

Ship  Parcel Post  Express  C.O.D.  Best Way



**HEATH COMPANY**  
 Benton Harbor 10, Michigan

PLEASE SEND MY FREE COPY OF THE 1961 HEATHKIT CATALOG

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

## Carl and Jerry

(Continued from page 100)

as he unplugged his portable TV. "He's a ham who lives right behind you, Loree. Let's go see him, Jer."

The boys started for the door; then Jerry stopped short and looked down at the little girl. "Want to go along, Loree?"

Her face lit up, and soon the three of them were sitting in Eddy's ham shack waiting for the teen-ager to finish his conversation with another ham in a neighboring town. When the QSO was over, they explained the reason for their visit.

"My older brother and I have a ten-meter ground-wave sked every Monday night at this time," Eddy said, "but I've never had a TVI complaint before. The transmitter is thoroughly shielded; all leads coming out of it are filtered; the feed-line standing-wave ratio is 1/1 on this frequency; I have a very efficient ground; and the transmitter feeds the beam antenna through a low-pass filter that attenuates harmonic frequencies around 80 db. There's no TVI on *my* receiver. How does it look on that portable, Carl?"

With the transmitter running full power, not even faint cross-hatching could be seen on Carl's receiver.


"Hm-m-m-m," Jerry mused; "Channel

6 interference is apparently coming from the third harmonic of your 28.7-megacycle transmitter frequency; yet no interference is picked up right here at your station. Something at Loree's house must be breaking some of your signal up into harmonics—all we have to do is find that 'something.' Carl, you go home and put your rig on 29.6-megacycle c.w. and start sending very long dashes in exactly ten minutes. Eddy, you start a continuous voice test on your present frequency at the same time. Both of you keep going until I call you on the 'phone. Loree, you come with me to pick up my transistor radio."

**L**AURA was obviously delighted to be included in these mysterious plans. She forgot her *femme fatale* role and skipped happily along beside Jerry to the lab, then back to her house.

Promptly at the appointed time, the picture on her TV blacked out. Jerry turned down the TV sound, tuned his little radio to 900 kc., and began moving around the room. As he came close to a small wire entering the window and running along the wall to a drawer of a bedside table, Eddy's voice came faintly from the transistor radio. "One, two, three, test for TVI," he droned and gave his call letters. Every few seconds the sound disappeared for an instant, then came back.

"Loree, where does this wire and that

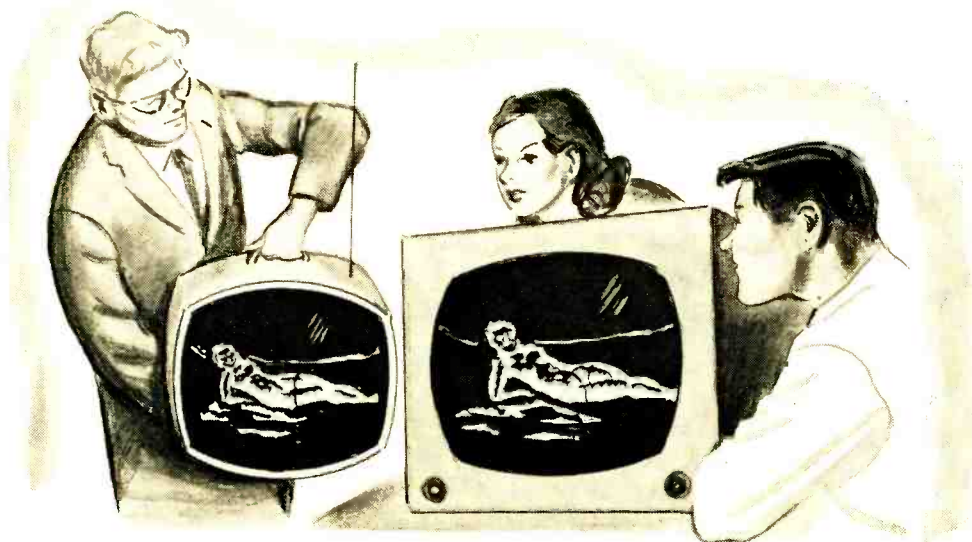



one coming from the cold air register go?" Jerry asked excitedly.

The child turned red as she pulled open the drawer and revealed a little crystal radio receiver and a pair of ear-phones.

"My folks won't let me listen to my clock radio after ten," she explained, "but that disc-jockey program on the local station at ten-thirty amuses me. You know—the one where silly girls request a number 'for Jack and Mary, who make a wonderful couple' and stupid stuff like that. Well, I listen to it on this little crystal set my uncle gave me for my birthday a month ago. The TV repairman fastened an aerial up on the TV antenna tower for me—that's it coming in the window. He called the wire going to the register a 'ground,' I think."

Without replying, Jerry unfastened the wire from the antenna post of the crystal set. Instantly the voice disappeared from the radio and the interference from the TV picture. Replacing the wire brought it back. Jerry picked up the telephone on the bedside table and told Carl and Eddy they could shut down their transmitters.

"Loree," he said, turning to the girl, "you saw for yourself that Eddy's transmitter was virtually free of TV-interfering signals, called harmonics. But often when a very strong signal near a transmitter encounters a device that passes current in only one direction—we call this a nonlinear system—two things can happen: first, the clean signal can be broken up into harmonics that will cause interference near the nonlinear system; and second, *two* strong

# RCA MARK VII RADIO-PHONE

**"TOP-OF-THE-LINE"  
CITIZENS' BAND  
2-WAY RADIO  
EQUIPMENT—  
GIVES YOU  
THE MOST!**



## **PROVEN PERFORMER FOR BUSINESS OR PLEASURE**

This quality equipment from the leader is a leader in performance . . . dependability. Operates from car, home, office, boat or truck. Terrific for business or pleasure two-way communications. Can be used at any location having 6 or 12 volt DC or standard 115 AC power source.

High reliability, stable reception, solid transmission. Provides four crystal controlled channels for both transmit and receive; also manual receiver tuning for all 23 channels. A tremendous value from the leader!

**See your RCA Radio-Phone dealer. Or mail coupon.**

**ONLY**  
**\$189<sup>95</sup>**

Manufacturer's  
Nationally Advertised Price



RADIO CORPORATION OF AMERICA  
Telecommunication Center  
Dept. W-420  
Meadow Lands, Pa.

Please send me FREE literature on the new RCA Mark VII Citizens' Band 2-Way Radio.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_ PHONE \_\_\_\_\_

CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_



The Most Trusted Name  
in Electronics

RADIO CORPORATION OF AMERICA

**FREE ALLIED**  
SPECIAL MONEY-SAVING  
**ELECTRONIC SALE BOOK**



**SAVE HUNDREDS OF BARGAINS!**

SAVE MOST on Allied Summer Specials! Terrific closeouts on quality Stereo hi-fi systems and components, tape recorders, phonos, records and tape. Top values in Allied's own KNIGHT® products and exciting build-your-own KNIGHT-KITS®. Hundreds of specials in radios, cameras, TV accessories, Citizens Band radio, amateur gear, P. A. systems, test instruments, tools and electronic parts. Dozens of new products. Write today!

ONLY \$2 DOWN on orders up to \$50; \$5 down up to \$200; \$10 downover \$200.

**FREE SEND FOR VALUE-PACKED SALE BOOK**


ALLIED RADIO, Dept. 54-F1  
100 N. Western Ave., Chicago 80, Ill.

Send FREE Allied Sale Book No. 205

Name \_\_\_\_\_  
PRINT  
Address \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

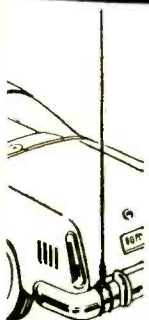**ALLIED RADIO**


**For BEST "CB" Reception**  
**MOST FOLKS USE**  
Antenna Specialists Co. Antennas



Model MB24

For your car—Model MB-24... all you need in one package: double chain bumper mount, spring, stainless steel whip, 20 feet of coaxial lead and whip-hold-down clip. No holes to drill. Fits virtually ALL cars.

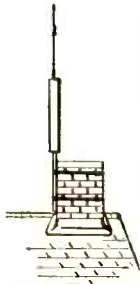Just two of over 200 models Antenna Specialists Co. offers. See your Electronic Parts Distributor or write us for free catalog. "We supply the antennas for set manufacturers, too!"



Model M-36

For your base station — Model M-36 Vertical coaxial antenna. Brings you solid signals over good distances. Extra sturdy. Neat and inconspicuous mounting.

Copyright 1960 by:

**the antenna specialists co.**  
12435 Euclid Avenue • Cleveland 6, Ohio  
Dept. P. E. 11

signals will be mixed in the system and produce two new frequencies representing the sum and difference of the frequencies of the strong signals."

"My, you're smart to know all that," Loree sighed as she fluttered her eyelashes admiringly at Jerry.

"Lots of things can constitute non-linear systems besides man-made rectifiers," Jerry went on. "All you need is a couple of pieces of metal with a little oxide, such as rust or corrosion, separating them. Poor connections in TV antennas, tower and mast joints, lightning arrestors, gutters and roof drains, electrical conduit, clothes-line, guy wires—these are only a few examples. A bad case of TVI was once caused by a clean-out poker hanging from a furnace pipe.

"The crystal detector in your little radio and that thirty-some-foot-long aerial wire were almost perfect for producing and radiating a ten-meter harmonic to black out Channel 6. When Carl and Eddy were both transmitting on frequencies 900 kc. apart, their signals were mixed in the detector and produced the difference frequency I picked up on my little broadcast receiver. That's how I hoped to find out what was causing the trouble, and it worked. I suggest you leave the aerial off your set when you're not listening to it."

"I will," Laura promised. "Now I know an amateur transmitter never causes TV interference unless there's a nasty old 'system' near the receiver."

"Unfortunately, that's not quite the case, Loree," Carl admitted as he came through the door. "Unless the ham transmitter is carefully shielded, filtered, and grounded, as Eddy's and mine are, it can send out harmonics directly from



the antenna; but there are cases, such as this one, where the ham transmitter might be blamed without reason."

"WELL," Laura said briskly, picking up her purse, "what do I owe you two? Your service has been most satisfactory."

"Oh—" Jerry began with a deprecating wave of his hand; but he stopped short as he saw Laura's father standing out in the hall shaking his head firmly from side to side. "Well, let's see, now: this case was very easily solved. We had no operating expense. Then there's our usual neighborhood discount. Our client was most charming and cooperative—I'd say two dollars would be fine."

Later, out on the porch, Mr. Hall explained: "Boys, the cruelest thing you can do to a little girl is to treat her as a child when she is feeling very grown up. Don't worry about the two dollars. You more than earned it, and I can do a little juggling with her allowance. But whether you want it or not, I'm sure you two have earned something else: the hero-worship of a little girl. That's quite a responsibility." -30-

### Connections Are Important


(Continued from page 73)

In an enclosed installation, simply dress the cables of each group close to each other and secure them by twisting a pipe cleaner or a short length of solid hookup wire around the group every six inches or so. Coil any slack neatly and secure the coil in the same manner. Keep each group separated from the other groups by several inches.

In an open installation, dress the cables as before. Instead of using pipe cleaners or hookup wire to lace the group, however, use telephone-cord spiral wrap, available in many stores for about 50 cents a yard. The wrap can be obtained in a number of colors, chosen to complement the decor of the listening room.

Speaker lines are almost always immune to hum pickup. The best way to connect speakers while avoiding unsightly cabling strung around the room is to use flat, 300-ohm, TV twin-lead, placed under the rug. -30-

# FREE CAREER BOOKLET

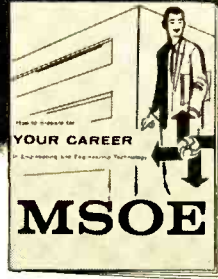

To guide you to a successful future in

## ELECTRONICS RADIO-TV COMPUTERS ELECTRICAL ENGINEERING

This interesting pictorial booklet tells you how you can prepare for a dynamic career as an Electrical Engineer or Engineering Technician in many exciting, growing fields:

**MISSILES • AVIONICS • AUTOMATION  
SALES • DEVELOPMENT  
ELECTRICAL POWER • ROCKETRY  
RADAR • RESEARCH**

Get all the facts about job opportunities, length of study, courses offered, degrees you can earn, scholarships, part-time work — as well as pictures of the Milwaukee School of Engineering's educational and recreational facilities. No obligation — it's yours free.

### MILWAUKEE SCHOOL OF ENGINEERING

#### MAIL COUPON TODAY!

**Milwaukee School of Engineering**  
Dept. PE-661, 1025 N. Milwaukee St., Milwaukee, Wis.  
Please send FREE "Your Career" booklet  
I'm interested in  
 Electronics     Radio-TV     Computers  
 Electrical Engineering     Mechanical Engineering

Name ..... Age .....

Address ..... PLEASE PRINT .....

City ..... Zone ..... State .....

I'm eligible for veterans education benefits.  
Discharge date .....

MS-117

## Space Electronics


(Continued from page 70)

**Satellite "Voices."** To my knowledge, there is only one informative LP recording of what satellite signals really sound like. This is a 10" disc titled "Voices of the Satellites," sold for \$3.95 through Taben Recordings, Box 224, Ardmore, Pa. The satellite radio signals were recorded by Professor T. A. Benham of Haverford (Pa.) College. Included are sounds of the signals from Explorer I, II and III, Vanguard I, plus Sputnik I and Sputnik II.

Professor Benham's narration on this disc tells much about the receiving conditions, the Doppler effects, sounds of telemetering, and—last but not least—the heartbeats of the Soviets' little dog Laika—a passenger on Sputnik II.

I use this recording to demonstrate the sound of signals from Vanguard I. This is the 10-milliwatt satellite still transmitting on 108.020 mc. whose solar batteries are likely to last another seven or eight years. Receiving this satellite is a good test of your FM receiver sensitivity—I have heard Vanguard I using the Scott and Harman-Kardon FM tuner kits.

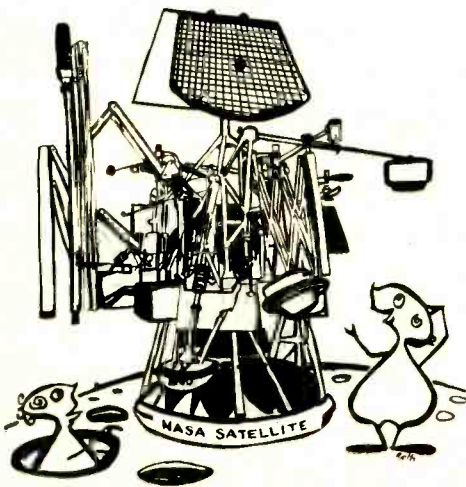"Voices of the Satellites" (although dealing with 1957-58 satellites) is a collector's item well worth the small investment it requires.



"That's funny, I thought earthmen would look a lot different."

**Space Q & A.** Here are the answers to some of the "space" questions you have been asking.

**Q:** Although the Soviets have frequently used telemetering signals near 20, 40 and 183 mc., haven't I seen newspaper reports of other frequencies being used?

**A:** During the first few days after the launching of Lunik I (Jan. 2, 1959), radio signals apparently associated with this satellite were heard on 70.2 and 212.0 mc. The recent Soviet Venus probe (announced as being on 922.8 mc.) may instead have been transmitting in the 120.0-mc. band. The Soviets have neither confirmed nor denied use of these frequencies.

**Q:** Is it true that we don't know the launching sites of the Soviet satellites?

**A:** Yes and no. Officially, the Soviets have not revealed this information, though it is more than likely that the launchings take place at large ICBM sites. Aralsk and Kapustin Yar are the most likely sites.

**Q:** A friend of mine has an SWL verification from Vanguard I. How did he get it?

**A:** George Jacobs, a good friend of the SWL's, took it on his own shoulders to supply veries through the facilities of the Voice of America; but he was forced to discontinue the practice due to the pressure of his other duties. No plans have been made to resume this service in the near future.

**At Minus-One.** Transatlantic television may not be far off now because of a new method of transmitting TV signals. Called "digital TV," the new system provides a better picture quality while using considerably less frequency space. Radio signals carrying digital modulation can easily be handled by present-day active satellite repeating equipment.

You had to be on your toes to hear the first Russian man-in-space aboard the Vostok satellite on April 12. Besides the beacon and TV transmitter on 143.62 mc., the Soviets used their old-favorite frequency (about 20.00 mc.) plus a brand-new frequency for c.w. transmission (9.019 mc.).

—30—

## They'll Fly Safely

(Continued from page 46)

**Automatic Landing.** As planes of the future approach their destination, pilots will take news on "knee-high ceiling, arm's-length visibility" as casually as they now hear that it's time for a coffee break. A pilot will simply fly into the proper position on instruments, flip on the automatic landing system and fold his arms. A few minutes later, he'll feel his plane "grease" onto the runway so smoothly that sleeping passengers won't even be awakened.

Today's pilot, of course, uses "ILS"—an instrument landing system—at all major airports in bad weather. But ILS is limited. The pilot must still be able to see the ground when he lands. If he doesn't break out of the "soup" at about 200 feet, he climbs again and heads for another airport. This costs money, upsets schedules, and, of course, lands passengers at a city where they didn't want to go. But it will be different with the new air traffic control systems.

**How Soon?** When will these advances be in operation? Some of them very soon. The first DPC will be installed in the Boston area in late 1962. Although this will be a somewhat limited version, a full-fledged system will be installed in New York about a year later. Others will follow as fast as they can be built, installed, and interconnected.


One system of automatic landing has performed hundreds of perfect landings in all kinds of weather at Atlantic City. Another kind, developed in England, is already guiding military planes and airliners into London airport. A third system is now being installed on aircraft carriers to bring in Navy planes under "zero-zero" conditions. Each of these systems has some disadvantage for regular civil use, but researchers in Atlantic City are trying to combine the best features to make one ideal system.

Thus, on the one hand, breath-taking advances in aviation present ever tougher problems of communications, navigation, and control. But the science of electronics is coming through just as fast with the hardware and systems to make air travel safer, faster, and more reliable for us all.

-30-

# Your Copies of **POPULAR ELECTRONICS**

**ARE  
VALUABLE**

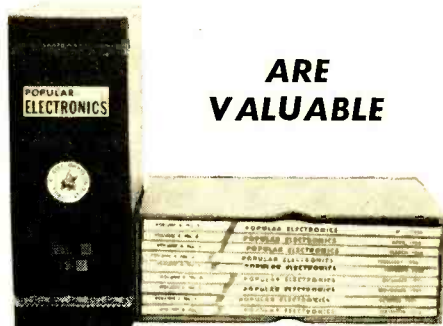

**KEEP THEM NEAT . . . CLEAN . . .  
READY FOR INSTANT REFERENCE!**

Now you can keep a year's copies of POPULAR ELECTRONICS in a rich-looking leatherette file that makes it easy to locate any issue for ready reference. Specially designed for POPULAR ELECTRONICS, this handy file—with its distinctive, washable Kivar cover and 16-carat gold leaf lettering—not only looks good but keeps every issue neat, clean and orderly. So don't risk tearing and soiling your copies of POPULAR ELECTRONICS—always a ready source of valuable information. Order several of these POPULAR ELECTRONICS volume files today. They are \$2.50 each, postpaid—3 for \$7.00, or 6 for \$13.00. Satisfaction guaranteed or your money back. Order direct from:

**JESSE JONES BOX CORP.** Dept. PE

(Established 1843)

Box 5120

Philadelphia 41, Pa.

## Interpreting TV Test Patterns

(Continued from page 63)

pattern forms a perfect circle. Then you may have to touch up the horizontal size setting again. Also, it is possible that either circle may go slightly beyond the edge of the screen when all controls are properly set. The pattern in Fig. 2 indicates a well-adjusted set; the white circle overlaps the edges just a little—a perfectly normal situation. Incidentally, when these adjustments have been correctly made, aspect ratio is automatically correct.

**Positioning Magnets.** If you can't get a perfect circle in exactly the right position—perhaps the top, bottom, or one side of the picture (Fig. 11) doesn't quite reach the edge of the tube—try adjusting the positioning magnets. These magnets shift the entire picture around the

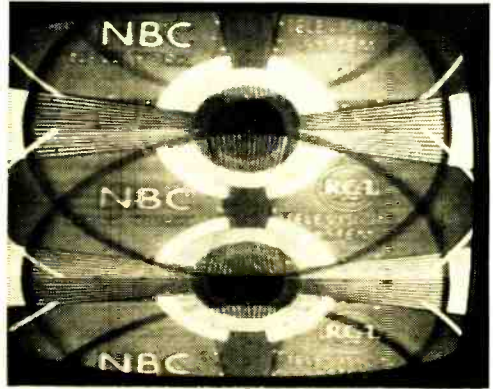


Fig. 12.



Fig. 13.

Fig. 10.

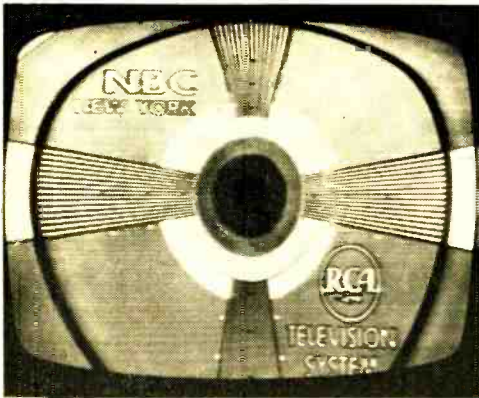


Fig. 11.



screen in any direction. By using both of them, you can get any combination of up-down and side-to-side movement you want.

**Vertical and Horizontal Hold.** After you've finished all other adjustments, it's a good idea to reset the horizontal and vertical hold adjustments. To set them most accurately, disconnect the antenna completely from your set and tune in a weak station. If it is weak enough, the picture may "roll over" (Fig. 12) or break up (Fig. 13), and there may be "snow." Readjust the vertical and horizontal controls for the steadiest picture possible under these conditions. The synchronization circuits are now in their most sensitive positions, and the picture is less likely to break or roll when signal strength fades momentarily or when a truck with noisy ignition passes your home.

Now, reconnect the antenna, check focus carefully, and sit back to enjoy really well adjusted television. —30—





**BUILD THE  
PROJECTS  
DESCRIBED  
IN THIS  
ISSUE OF**

**POPULAR  
ELECTRONICS**

**WITH THESE**



**PRODUCTS**

**ACROSS THE HAM BANDS**

Low-Power/High-Power Relay  
Uses Bud CU-2105A Utility Box.....\$1.20

**SOIL MOISTURE METER**

Uses Bud CU-3006A Chassis Box.....82c

**HEADS . . . OR TAILS**

Uses Bud AU-1083 Utility Box.....\$1.29

**MUSICAL TELEPHONE HOLDER**

Uses Bud CU-2105A Chassis Box.....\$1.20

**LISTEN TO YOUR HEART**

Uses Bud Aluminum Chassis AC-403.....\$1.24

All Bud products are available for immediate delivery from your Authorized Bud Distributor. They are the best for applications described in these projects.

WATCH FOR THESE LISTINGS EVERY MONTH

IN POPULAR ELECTRONICS

**BUD RADIO, INC.**

2118 East 55th Street Cleveland 3, Ohio  
Dept. P.E.

**The way to enjoy music outdoors!**



**with UNIVERSITY'S MUSIC/AIRE  
weatherproof high fidelity speaker systems**

No need to settle for the thin tone of a portable when you go outdoors. Instead, connect a Music/Aire speaker (or two for stereo) to the speaker terminals of your radio, phono, TV, or hi-fi amplifier, and thrill to wide-range, high fidelity sound. Each model is a genuine dual-range, with separate woofer and tweeter. Leave out in rain or shine — they're immune to everything but superb sound! For new illustrated brochure, write Desk A-6, University Loudspeakers, Inc., White Plains, N. Y.



MLC ideal for moderate-size areas. \$34.50



BLC with extended bass. \$53.70



**On the Citizens Band**

*(Continued from page 88)*

end of 1966, and they will be re-assigned when the "Q-to-W" cycle starts again in 1968.

In case you haven't heard, CB north of the border is going for real. Yep—Canada's good ol' DOT (Department of Transport to us uninitiated Yankees—their equivalent of the FCC) has set up a new "General Services Band" smack in the 27-mc. region. DOT's licensing policy probably won't be finalized until sometime during the summer, but it looks as though our Canadian cousins will be CB'ing it by October or November.

A nifty wallet-sized card (Form No. SD-104) is available from the Antenna Specialists Co., 12435 Euclid Ave., Cleveland 6, Ohio, which shows the frequencies of all the CB channels on one side

CLASS B CITIZENS BAND	CHANNELS TO MEGACYCLES CHART
Channels	Megacycles
1	26.965
2	26.975
3	26.985
4	27.005
5	27.015
6	27.035
7	27.035
8	27.055
9	27.065
10	27.075
11	27.085
12	27.105
13	27.115
14	27.135
15	27.135
16	27.155
17	27.165
18	27.175
19	27.185
20	27.205
21	27.215
22	27.225

the antenna specialists co.  
12435 Euclid Avenue Cleveland 6, Ohio  
— Communication Antennas —  
"The Finest Brand for The Citizens Band"

Trade Mark Stiles of Quality Form No. SD-104

and the states in each CB call area on the reverse. It's a handy thing to have, and it's free if you drop them a note and ask for one.

By the way, the same company also happens to make a darn nice line of CB antenna catalog—tell 'em we sent you.

All CB clubs are welcome to keep us posted on their activities by sending us their newspapers and press releases. Also, good-quality, sharp "glossy" photos of CB club activities will be appreciated—we'll be glad to use them in the column.

## Transistor Topics

(Continued from page 98)

oscillator. Emitter bias is furnished by battery *B1* through resistor *R1*, bypassed by capacitor *C1*, and through an r.f. choke, *RFC1*. Collector bias is furnished by *B2* through *RFC2*, bypassed by *C2* and through the tapped tank coil, *L1*. The feedback necessary to start and sustain oscillation is obtained from a tap on *L1* and coupled back through trimmer capacitor *C4* to *Q1*'s emitter. Battery *B2* also supplies a d.c. operating current to the carbon microphone cartridge (*MIC.*) through current limiting resistors *R2* and *R3*.

As we can see, the oscillator's operating frequency is determined by *L1*, shunted by *C5* and a network made up of fixed capacitor *C6* and a Varicap, *C8*. The Varicap's capacity varies with the voltage applied to it, providing a means of altering the instantaneous oscillator frequency and achieving frequency modulation. Voltage applied to *C8* has both d.c. and a.c. (audio) components. The

d.c. component is obtained from voltage divider *R5-R6* and is applied through isolating resistor *R4* and r.f. choke *RFC3*; *R6* is made variable to serve as a tuning control. The a.c. signal is obtained from the microphone circuit, with that portion of the audio signal appearing across *R3* applied through d.c. blocking capacitor *C3* and *RFC3* to *C8*.

In operation, then, *C8*'s capacity—and hence the frequency of oscillation—is first determined by the adjustment of *R6*. Then, when a signal is developed by the microphone, an a.c. signal is superimposed on the steady d.c. bias, changing *C8*'s instantaneous capacity and varying the oscillator's frequency accordingly.


The entire circuit can be assembled on a small chassis or printed-circuit board and housed in a small plastic case. Good high-frequency wiring procedures should be followed throughout, with all signal leads kept short and direct. All components except *C8* are standard and should be available from your local distributor. You may have to contact a larger (mail order) distributor to ob-

## DigiBit Application & Use
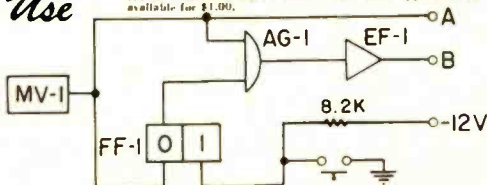
### Square Wave & Pulse Generator

This Multi-Frequency Square Wave and Single Pulse Generator can be readily assembled using DigiBits—transistorized digital packages. A continuous square wave is available at output "A" and a single pulse is generated at output "B" each time the push-button switch is closed. The MV Clock DigiBit is available with single, dual or a five frequency outputs and with clock rates of from 1 to 10,000 cps. Specify desired frequencies:

1, 10, 100, 500, 1,000, 5,000, 10,000 cps.



This Generator is only one of the many useful networks that can be built using the DigiBit building-block technique. A booklet describing digital elements and their application is available for \$1.00.

# TECH SERV

DEPT. D-3, 4911 COLLEGE AVE., COLLEGE PARK, MARYLAND

WRITE FOR FREE DIGIBIT CATALOG

DigiBits required to assemble Square Wave and Single Pulse Generators plus necessary accessories

- Single Frequency SW-1 \$37.95
- Dual-Frequency SW-2 \$43.75
- Five-Frequency SW-5 \$48.25

## Hear 'Em — Work 'Em Better with BROWNING CB Equipment

R-2700 CB RECEIVER  
\$149.00

S-NINE CB TRANSMITTER  
\$119.50



Make your CB base station a real communications center with this Browning team. Highly sensitive and selective R-2700 Receiver delivers sharp, noise-free reception on all CB channels. Overcomes even the most severe atmospheric and man-made interference. Browning S-NINE Transmitter allows full power transmission on all channels — introduces new features and advanced design never previously utilized in CB communications.

Also Available  
R-2700 Receiver PLUS  
T-2700 Transmitter  
SPECIAL PACKAGE PRICE  
Send for Free Literature



browning  
101 UNION AVE., LACONIA, N.H.

SATISFACTION GUARANTEED FOUR CONVENIENT PURCHASE PLANS

# MICRO

## ELECTRON TUBE CO.

P.O. Box 55, Park Station  
Paterson 3, New Jersey

# 37

¢  
ea.

# \$35

PER  
HUNDRED  
ASSTD

Select Stock of  
Used Tubes at a  
Fabulous Low Price

SEND FOR FREE COMPLETE LIST OF TUBES			
0A2	3Q4	6BC5	12A8
0A4		6B8	12A05
1A7GT	1BZ7	6BD6	12AT6
1B3GT	5A5B	6C4	12AT7
1H4G	5AT8	6C5	12AU6
1H5GT	5AV8	6C6	12AU7
1L4	5AW4	6CB6	12AV6
1L6	5BK7	6CD6G	12AX7
1N5GT	5J6		12AX7GT
1Q5GT	5T8		12AX7
	5U4G	7A1/XXL	
	5U8	7A5	
2A3		7A6	19BG6G
2AF4		7A7	19J6
3BC5	6A7	7A8	19T8
3BN6	6A8	7B4	21A
3BZ6	6AB4	7B5	23AV5
3CB6	6AC7	7B6	23BQ6
3CF6	6AF4	7B7	25DN6
3CS6	6B8	7B8	25L6GT
3LF4	6BA6	7C4	25W4GT
			25Z5
			25Z6
			26
			35A5
			35B5
			35C5
			35L6GT
			35W4
			35Y4
			35Z5GT
			37
			39/44
			42
			43
			45
			50A5
			78
			80
			84/6Z4
			117Z3

• All tubes lab-tested for mutual conductance, life test. • Guar. FREE 1 yr. replacement any tube failing under all operating cond. • Adv. tubes not necessarily new; may be elec. perf. fact. sections or used—clearly marked.

**POSTAGE PAID.** Send 25c handik. for orders under \$5. 25% dep. C.O.D.'s. Send approx. post. on Can. & foreign orders.

## twenty to one dividend...

from college education in engineering or business. Invest in yourself! BACHELOR OF SCIENCE DEGREE IN 27 MONTHS in Elect. (Electronics or Power major), Mech., Aero., Chem., Civil Engineering. IN 30 MONTHS in Business Administration (General Business, Acctg., Motor Transport Mgt. majors). Small classes. More professional class hours. Well-equipped labs. Campus. Dorms. Modest costs. Founded 1884. Enter Sept., Jan., Mar., June. Write J. D. McCarthy, Director of Admissions, for Catalog and "Your Career in Engineering and Commerce" Book.

### TRI-STATE COLLEGE

3661 College Avenue  
Angola, Indiana

## NEVER FAIL— ZONE YOUR MAIL

The Post Office has divided 106 cities into postal delivery zones to speed mail delivery. Be sure to include zone number when writing to these cities; be sure to include **your** zone number in **your** return address—after the city, before the state.

## GET INTO ELECTRONICS

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar, automation, basic & advanced courses in theory & laboratory. Assoc. degree in 29 mos. B. S. obtainable. ECPD accredited. G.I. approved. Graduates with major companies. Start Sept., Feb. Dorms, campus. H. S. graduates or equivalent. Catalog.

**VALPARAISO TECHNICAL INSTITUTE**  
Dept. PE VALPARAISO, INDIANA

tain C8, which is a PSI Type V27 Vari-cap.

Except for R6, a standard potentiometer, the resistors are all 1/2-watt composition units. Standard mica or ceramic capacitors (working voltage not critical) can be used for C1, C2, C3, C5, C6, and C7; C4 is a small 3-12 μf. ceramic trimmer capacitor. Ohmite Type Z-28 coils serve as the r.f. chokes (RFC1, RFC2, and RFC3), and B1 and B2 are standard penlight cells—with a single cell for B1 and eight in series for B2. Transistor Q1 is a 2N247 pnp r.f. transistor, and any standard carbon microphone cartridge may be used. Coil L1 is hand-wound, and consists of 10 turns of 20-gauge enameled copper wire on a 1/2"-diameter form, with a tap 3 1/2 turns from the bottom (ground end).

With the component values specified, the unit's operating frequency is approximately 45 mc. In most applications, the radiation obtained from coil L1 is adequate for short-range transmission and an external antenna is unnecessary. No data is available for modifying the transmitter for operation at other frequencies.

**Semiconductor Book.** A volume entitled "Semiconductor Devices," written by Rufus P. Turner, has been published recently by Holt, Rinehart and Winston, Inc. (383 Madison Ave., New York 17, N. Y.). Divided into ten major chapters, this excellent book covers the construction, operation, and application of all types of semiconductor devices.

Written for the individual with a basic knowledge of electronics, the book starts with a general discussion of the basic structure of semiconductor devices, then goes on to discuss individual types of devices and their practical circuit applications. Yours truly particularly liked Chapter 10, which covers test and measurement techniques.

We recommend this volume as a "must" for the technical library of technicians, practical engineers, and serious hobbyists. It sells for \$6.95.

**Product News.** According to the Bendix Radio Division (Baltimore 4, Md.), some 17 leading railroads are now using the new Bendix transistorized "2R" receivers in their radio systems, including the B & O, C & O, Rock Island, Santa Fe, New York Central, Great Northern,

Northern Pacific, L & N, and Erie-Lackawanna.

An all-transistor sound system has been developed by the Grass Valley Group, Inc., of California, for use in Cinerama theaters around the world. Capable of a total audio power of 450 watts, it has good response to 20 kc.

General Electric's Semiconductor Products Department (Syracuse, N. Y.) has announced a 41% price reduction on three industrial models of silicon Unijunction transistors, Types 2N1671, 2N1671A, and 2N1671B.

An extremely low dynamic-impedance temperature-compensated Zener diode has been introduced by Motorola Semiconductor Products, Inc. (5005 East McDowell Rd., Phoenix, Arizona). Type 1N821A is designed for ultra-stable reference applications in digital voltmeters, precision high-stability oscillators, analog-to-digital converters, and similar industrial and military circuits.

A new 9-volt, governor-regulated, battery-powered motor is now available from Jonard International, Inc. (624 Madison Ave., New York, N. Y.). This imported unit requires only 25 ma. under no-load conditions, and should be useful for powering transistorized record players, tape recorders, and similar electromechanical devices.

That's the picture for now. See you next month . . .

—Lou


## Across the Ham Bands

(Continued from page 95)

gether, and drill ten 1/16" holes spaced 3/8" apart. Parallel ten 330-ohm, 2-watt, composition resistors by sandwiching them between the two plates, pushing their leads through the holes, and soldering them. All but one of the leads protruding from each square should be trimmed off, and the remaining two leads used for connecting the resistors into the circuit. Then repeat the operation with two 3/4" copper squares and five 150-ohm, 2-watt composition resistors.

The 10-resistor unit (R1) should be connected from the relay to the center terminal of the coaxial connector (J3) feeding the grid circuit of the amplifier. Connect the 5-resistor unit (R2) from

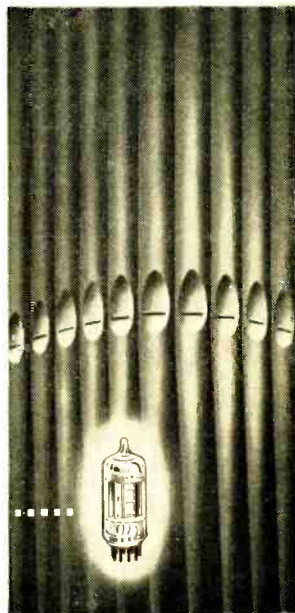*Schober*  
captures  
magnificent  
pipe organ  
tone  
in a tiny  
electronic  
tube.



Here is magnificent Pipe Organ tone; tremendous tonal color range; two 61-note pipe-organ keyboards; hand-rubbed cabinetry in the finish of your choice. Taken together they comprise a superlative electronic instrument comparable to organs selling for \$2,500 to \$6,000.

Yet, when you assemble the Schober of your choice, you save more than half the normal cost and create a superb instrument to bring the delightful gift of music to your family.

Work requiring knowledge and experience is eliminated. All that remains is the pride and pleasure of watching a fine musical instrument take shape under your own hands. The Schober organ you assemble will equal or surpass any factory-built organ for quality, reliability and circuitry.

The coupon brings you full details on how you can start building the Schober of your choice with an investment of as little as \$18.95. In addition, you may have an exciting 10" LP record demonstrating Schober's full range of tones and voices. The \$2 charge for the record is refunded when you order your starting kit. No salesman will call.

**THE SCHOBER ORGAN CORPORATION**  
Dept. PE-5, 43 West 61st St., N. Y. 23, N. Y.



The Schober Organ Corp.,  
Dept. PE-5,  
43 West 61 St., N. Y. 23, N. Y.

Please send me FREE full-color booklet and other literature on the Schober organ.

Please send me the Hi-Fi demonstration record. I enclose \$2 which is refundable when I order my first kit.


name \_\_\_\_\_

address \_\_\_\_\_

city \_\_\_\_\_ zone \_\_\_\_\_ state \_\_\_\_\_
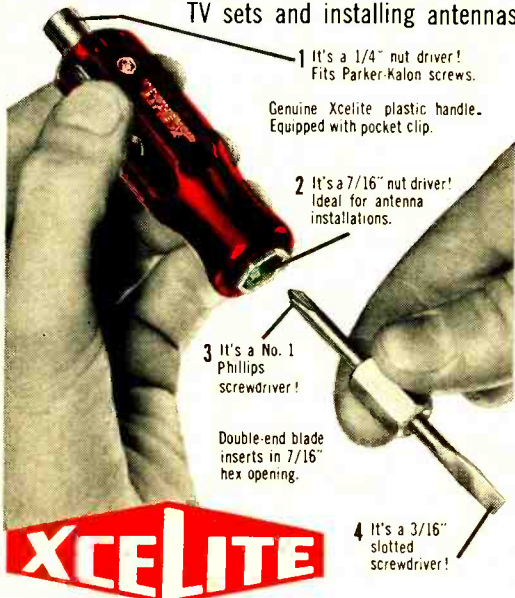
# NEW 4-WAY POCKET TOOL

a real "working partner" for removing backs of TV sets and installing antennas



1 It's a 1/4" nut driver!  
Fits Parker-Kalon screws.  
Genuine Xcelite plastic handle.  
Equipped with pocket clip.

2 It's a 7/16" nut driver!  
Ideal for antenna  
installations.

3 It's a No. 1  
Phillips  
screwdriver!


Double-end blade  
inserts in 7/16"  
hex opening.

4 It's a 3/16"  
slotted  
screwdriver!
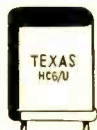
## XCELITE

XCELITE, INC. • ORCHARD PARK, N. Y.  
Canada: Charles W. Pointon, Ltd., Toronto, Ont.

See "No. 600" next  
time you pick up parts.



(add 5c per crystal  
for postage  
and handling)

## CITIZEN BAND CLASS "D" CRYSTALS

3rd Overtone—Hermetically Sealed  
.005% tolerance—Meet F C C require-  
ments, 1/2" pin spacing—.050 pin diameters.  
(.093 pins available, add 15c.)  
ALL 22 FREQUENCIES \$2.95 EACH  
IN STOCK!

The following Class "D" Citizen Band frequencies in stock (frequencies listed in megacycles): 26,965, 26,975, 26,985, 27,005, 27,015, 27,025, 27,035, 27,055, 27,065, 27,075, 27,085, 27,105, 27,115, 27,125, 27,135, 27,155, 27,165, 27,175, 27,185, 27,205, 27,215, 27,225.

Matched crystal sets for Globe, Gonsset, Cit-Fone and Hallcrafters Units . . . \$5.90 per set. Specify equipment make.

## RADIO CONTROL CRYSTALS in HC6/U HOLDERS—SIX FREQUENCIES

In stock for immediate delivery (frequencies listed in megacycles): tolerance .003%, 1/2" pin spacing—.050 pin diameter. (.093 pins available, add 15c per crystal.) Specify frequency.  
26,995, 27,045, 27,095, 27,145, \$2.95 EACH  
27,195, 27,255 . . . . . \$2.95 EACH  
(add 5c per crystal for postage and handling)

### ASK YOUR PARTS DEALER FOR TEXAS CRYSTALS

See big red display . . . if he doesn't stock them, send us his name and order direct from factory.

Send for FREE CRYSTAL CATALOG #860  
WITH OSCILLATOR CIRCUITS

Now! Engineering samples and small quantities for prototypes now made either at Chicago or at Ft. Myers plant. 24 hour service!  
CHICAGO PHONE GLadstone 3-3555

All orders Shipped 1st Class Mail. Rush order to:

**TEXAS CRYSTALS**  
Dept. P-61, 1000 Crystal Drive, Fort Myers, Fla.  
For fastest possible service, Phone WE 6-2100

the center terminal of *J3* to the metal box.

**Operation.** Mount the relay unit on or near the power amplifier, and connect it between the amplifier, exciter, and antenna, as shown on the diagram. Use coaxial cables for the connections.

Relay coil *RL1* is connected to the 117-volt circuit of the amplifier, so that the relay will be energized when the amplifier is turned on. Operation of the amplifier and the exciter should be completely normal with the relay unit installed.

### News and Views

**Norman Kurtin, WV6NON**, (12), 711 North Oakhurst Drive, Beverly Hills, Calif., has worked 28 states, with cards from 22 of them, in two months on the air. He excites a "long-wire" antenna that works only on 40 meters with a Heathkit DX-20 running 50 watts. Norm receives on a Hallicrafters S-38E. His two foreign countries worked are Macao, Asia, and Canada! . . . **Peter J. Crosby, WA2EYD**, 108 Waverly St., Cattaraugus, N. Y., got bit by the ham bug after reading our column for the first time in November, 1958. It took him six months to get his Novice license, but he is now a General, and has been for some time. Feeding a Globe Scout 65A into an "all-band" trap doublet and receiving with a Hammarlund HQ-110. Pete has 45 states worked, 44 confirmed. His country total is six, including Canada, Puerto Rico, Cuba, Panama Canal Zone, and Venezuela. He is especially proud of that last one, since he worked Venezuela on 75-meter phone with his 50 watts. A WRL 755A variable-frequency oscillator helps Pete find holes in the ham-band QRM, and a Globe linear amplifier will soon boost his power output.

**Don Fortner, K4SAO**, 9 Saco St., Brandon, Greenville, S. C., uses a Globe Scout 680-A transmitter running 65 watts on c.w. and 50 watts on phone, feeding a 40-meter dipole or a 1-element, 15-meter beam. He has 47 states worked and 46 confirmed. And on 15-meter phone, he has worked 12 foreign countries, the rarest of which is a VQ3. Don's dad is K4OIM, and they are having a contest to see who can work all states first. But his dad's score is as mysterious as what Don is using for a receiver—he didn't tell us. . . . **Thomas Brieady, WA2KLD**, 148 Ridgewood Drive, Syracuse 6, N. Y., has two transmitters: an EICO 720, which he uses on 40-meter c.w.; and a Globe Chief 90A, with an SM-90A screen modulator, which he uses on 40-meter phone. His antenna is a Mosley V-4-6 vertical. By the time you read this, Tom hopes to have retired his National NC-60 receiver in favor of a new NC-188. He divides his time about 50/50 on phone and c.w., and prefers a chat with a strong local to chasing DX.

**Floyd Chowning, KN5CWS**, P. O. Box 191, Clint, Texas, has worked 16 countries and 47 states in approximately 800 contacts during his eight months as a Novice. He feeds his

Viking Ranger into an 80-meter dipole, a 40-meter ground plane, or a 15-meter Cubical Quad antenna, and receives on a Hallicrafters SX-28A. Floyd needs Nevada, Rhode Island, and South Dakota, and will schedule anyone needing Texas on any 10-through-40-meter band. His Conditional Class license is on the way. . . . **Ted Levy, KN8WNY**, 28 W. 8th St., Manchester, Ohio, operated for a few weeks with a home-brew 35-watter but stopped operation when he found it generated harmonics like a crystal calibrator. Then, with a new Heathkit DX-40 feeding a 15' dipole, Ted worked nine states and Puerto Rico in four days. He receives on a Hallicrafters S-107, plus a Q-multiplier. . . . **Ed Hilsenhoff, WV6ODH**, 1310 Harding St., Long Beach 5, Calif., spends half of his time on 40 meters and half on 80 meters. He uses a 45' vertical antenna fed from a home-built 40-watt transmitter, and receives on a Hallicrafters S-38D helped along by a Q-multiplier. Ed had trouble with harmonic radiation from the transmitter, but cured it with the harmonic filters described in our May 1960 column.


Did you see **Lenore Conn, W6NAZ**, "Ham Of The Month" for November 1960, on NBC-TV's "This Is Your Life"? The telecast was on Sunday, Feb. 26, in most areas. Lenore was honored for her work in providing communications for men in isolated outposts and for the other reasons which prompted us to select her as our "Ham Of The Month." Congratulations, W6NAZ. . . . **Bob McGraw, K4TAX**, 401 Main St., Martin, Tenn., works for Radio

Station WCMT when he's not doing school work or hamming. Bob is a great believer in home-built equipment intermixed with kits. He uses a Knight T-50 transmitter to drive a pair of 6DQ5's in a home-built linear r.f. amplifier for AM and c.w. work, modulating the T-50 with a pair of 6L6's in a home-built circuit. For SSB, he has a home-built exciter, plus a Heathkit VOX system. A Knight VFO drives either "lash up," and he receives on a Knight R-100 receiver. A 135' inverted-'V' antenna feed with open-wire feeders and a home-built antenna coupler completes the setup.

**John Huetter, K8DZR**, 3438 W. 113 Rd., Cleveland 11, Ohio, got on 20-meter c.w. about the first of the year and is still surprised at how well his low power does on the DX there. He runs 65 watts to a Globe Scout transmitter feeding either a Hy-Gain 12-AVS vertical on 15 and 20 meters or a 40-meter dipole on 40 and 15 meters. John receives on a Hallicrafters SX-99. He has 48 states and eight countries worked.

As announced last month, we will present a free one-year subscription to POPULAR ELECTRONICS to whoever sends in the best Novice station picture each month—the first winning entry will appear in the next issue. Also, as always, I look forward to receiving your letters and suggestions for construction projects. Address all communications to: Herb S. Brier, W9EGQ, c/o POPULAR ELECTRONICS, One Park Ave., New York 16, N. Y. 73.

—Herb, W9EGQ

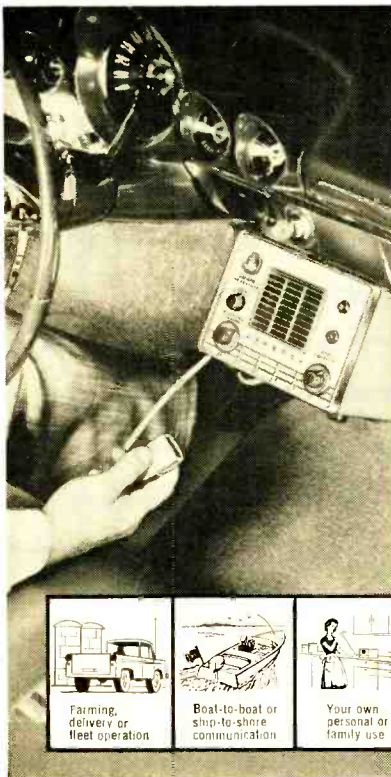

## "More than Citizens' Radio" ...

a complete, fully engineered "industrial-type" transceiver!

VIKING *Messenger*

Anyone can operate—license issued by the FCC on request

from **\$134<sup>95</sup>**

- Complete 23 channel Citizens' Band coverage—choose 1 of any 5 channels by the flip of a switch.
- Maximum legal power—excellent range—meets all FCC requirements.
- Excellent receiver sensitivity and selectivity—full fidelity voice reproduction.

"More than just 2-way Citizens' Radio equipment"—the Viking "Messenger" will deliver the finest performance of any equipment available in the field. Designed throughout for 10 watt power level—limited to 5 watts for Citizens' Radio. Easy to install anywhere in your home, business location, car, truck or boat . . . offers many unique features found only on more expensive communications systems. Built-in Squelch, Automatic Volume Control, and Automatic Noise Limiter. Compact, modern styling—only 5 3/8" high, 7" wide, and 11 3/8" deep. Complete with tubes, push-to-talk microphone, and crystals for one channel.



**FREE**  
Color Brochure



**E. F. JOHNSON COMPANY**

2410 Tenth Ave. S. W. • Waseca, Minnesota  
• Please rush me your full color brochure describing the Viking "Messenger" Citizens' Transceiver.


NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_

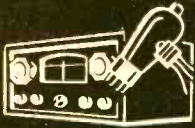**WRITE TODAY**

Manufacturers of the world's most widely used personal communications transmitters



**SELL YOUR USED  
EQUIPMENT Through  
POPULAR ELECTRONICS'  
Classified Columns!**

The 400,000  
purchasers of  
**POPULAR  
ELECTRONICS**  
are always interested in  
good used equipment  
or components.

So, if you have some-  
thing to sell, let PE  
readers know about it  
through our classified  
columns. It costs very  
little: just 60¢ a word,  
including name and ad-  
dress. Minimum mes-  
sage: 10 words.

For  
further  
information  
write:

Martin Lincoln  
**POPULAR ELECTRONICS**  
One Park Avenue  
New York 16, N. Y.

## Short-Wave Report

(Continued from page 84)

### Current Station Reports

This month's résumé of current reports features many frequency and schedule changes as well as a number of new stations. All times shown are Eastern Standard and the 24-hour system is used. At time of compilation all reports are as accurate as possible, but stations may change frequency and/or schedule with little or no advance notice.

**Angola**—Luanda has moved from 17,795 kc. to 17,705 kc. and is heard well at 1600-1730 in Portuguese, parallel to 4955 kc. (*WPE4FI*)

CR6RD, Nova Lisboa, has moved to 9665 kc. and is fair at 0115 with gong and ID for Nova Lisboa. This one fades before 0200. (*WPE3NF*)

**Bolivia**—CP39, *La Cruz del Sur*, La Paz, is now on 11,765 kc. with a new 10-kw. xmtr. It has been noted weak-to-fair at 0600-0700, but is covered by QRM evenings. (*WPE4FI*)

*R. Cochabamba*, Cochabamba, 5610 kc., a new station, has been heard from 1942 with L.A. music and ads; ID is at 1945 and 2007 as *Uds. estan a la escucha de Radio Cochabamba*. This all-Spanish outlet is listed for 5870 kc., and s/off time is 2009. (*PY1PE1D*)

Another rare station, *R. Cobija*, Cobija (Depart. de Pando), 4497 kc., has been heard at 1955 with a musical show, from 2000 with a request program. Classical music is broadcast at 2044. All announcements are in Spanish. (*PY1PE1D*)

**Brazil**—*R. Cultura de Sao Paulo*, Sao Paulo, now on 17,815 kc., was tuned from 1200 until covered by KCBR at 1700. ZYE21, *R. Marajuaba*, Belem, has moved to 15,251 kc. after a

#### SHORT-WAVE REPORTERS!

Your reports will be read and processed faster if you send them directly to:

Hank Bennett, Short-Wave Editor  
POPULAR ELECTRONICS  
P. O. Box 254  
Haddonfield, N. J.

Make sure you include your WPE call letters with your report.

short stay on 15,255 kc. and now operates at 0400-2100. (*WPE4FI*)

*R. Globo*, Rio de Janeiro, 11,805 kc., now operates regularly from 0900 to 1730, irregularly to 2100. (*WPE4FI*, *WPE6AGA*)

*R. Clube de Teresina*, Teresina, 3385 kc. (new?) is noted from 0345 (Sundays from 0405) in Portuguese with fading by about 0430. (*WPE4HJ*)

**Congo**—*R. Leopoldville* is now scheduled on 11,755 kc. as follows: to Europe at 1400-1830 with newscasts in German at 1445, Lingala-Kikongo at 1515, Portuguese at 1545, Swahili and Tshiluba at 1615, Eng. at 1645, French at 1715, Spanish at 1745, and Italian at

Always say you saw it in—POPULAR ELECTRONICS



1815; to N.A. at 1900-2130 with newscasts in Spanish at 1915, Eng. at 1945, French at 2015, and Portuguese at 2045. The mailbag is given on Sundays at 2045. Reports should be sent to *Radio Leopoldville*, Box 7699, Leopoldville, La Republique du Congo. (WPE1ADI, WPE1APS, WPE1BBB, WPE1ICE, WPE2LM, WPE3BCE, WPE3CCG, WPE4AJ, WPE4COK, WPE4FI, WPE6AA, WPE6BPO, WPE8BQH, WPE8HF/6, WPE8MS, WPE0AE)

**Dahomey**—R. *Dahomey*, Cotonou, 4870 kc., is tuned at 0050 with native music, French world news at 0115, more music from 0130. Dual to 7170 kc. (PY1PE1D)

**El Salvador**—YSU, San Salvador, 6187 kc., is heard well at 2300 in Eng. and is asking for reports. This station and YSS, 9552 kc., seem to be the only active YS stations. (WPE4FI)

**England**—Two 100-kw. xmtrs, manufactured by Marconi Wireless Telegraph Co., Ltd., have replaced two units at the Daventry station of the BBC that were installed in 1953. (WPE6EZ, WPE8OG)

**Finland**—Helsinki has been noted on 15,190 kc. with an Eng. mailbag at 1100-1130. (WPE9CD)

**Germany**—*Deutsche Welle*, Cologne, is now scheduled on 11,895 kc. at 1215-1515 to Africa (with the 100-kw. Dakar on the same channel!) and on 21,730 kc. to S. Asia at 0745-1045, replacing 21,700 kc. Other schedules: to Japan on 17,815 and 21,735 kc. at 0445-0745; to the Middle East on 21,730 and 17,875 kc. at 0745-

1045; to Eastern N.A. at 1900-2200 and to Western N.A. at 2200-0100 on 11,795 and 9640 kc.; to South America at 1730-2030 on 11,945 and 9735 kc.; and to Central America at 1615-1915 on 9735 and 5980 kc. and also at 2045-2345 on the same channels plus the unannounced 6140 kc. (WPE1CHS, WPE2AXS, WPE2VB, WPE4BC, WPE4FI, WPE8BZP, WPE8MS, VE7PE1R)

**Ghana**—Accra is now on 11,800 kc. and heard with fair strength at 1300-1630. (WPE1AGM, WPE3NF, WPE4AIX, WPE4FI, WPE4HJ, WPE8CKW)

**Greece**—The following Greek Forces stations have been heard: Jannina, 7079 kc., 2315-2335; Serrai, 7161 kc., 2354-0000; and Florina, 7284 kc., 2325-2330; all in Greek, mostly with talks. (WPE1HC)

**Guatemala**—TGJA, Guatemala City, has a harmonic on 11,980 kc. that is being heard irregularly at 1900-0000. (WPE4FI)

**Iran**—R. *Teheran*, now on 7030 kc., was tuned at 1545 with Eng. ID and news; also noted fair at 2130-0000. This is a move from 7285 kc. (WPE3NF, WPE4FI)

**Ivory Coast**—Abidjan has a new 100-kw. xmtr on 11,820 kc. and is heard well at 1245-1830; there is severe QRM from the BBC after 1330. Eng. news is heard at 1315. (WPE1AGM, WPE3NF, WPE4BC, WPE4FI)

**Japan**—New frequencies in use from Tokyo to N.A. at 1930 are 15,135, 17,725, and 21,520 kc. Being deleted from the schedule are 11,800 and 17,855 kc. (WPE2CKI, WPE4FI)

# 35¢

## TRU-VAC 1-YEAR GUARANTEED RADIO and TV TUBES

\$33

Per 100 TUBES

Factory Used or Factory Second Tubes! TRU-VAC will replace FREE any tube that becomes defective in use within 1 year from date of purchase! All tubes individually boxed, code dated & branded "TRU-VAC." Partial Listing Only - Thousands More Tubes in Stock!

SPECIAL!		65N7GT		306		6W4GT		304	
02A	4B5B	6AH6	6BC5	6CD6G	6E7	6W6GT	7F7	12AV7	12K7
1A7GT	4BZ7	6AK5	6C8	6CF6	6K6GT	6X4	7H7	12AX4GT	12L6
1B3GT	4CB6	6AL5	6BD6	6CG7	6K7	6X5GT	7H7	12AX7	12Q7
1H5GT	5AM8	6AM8	6BE6	6CGR	6N7	6X8	7N7	12AZ7	12R5
1R5	5AN8	6AN8	6C5	6CH6	6O7	6Y6	7O7	12B4	12SA7
1S5	5AT8	6AQ5	6BG6G	6CL6	6S4	7A4/XXL	757	12BA6	12SJ7
1T4	5AV8	6AQ6	6BH6	6CM6	6S8GT	7A5	7K6	12BA7	12SK7
1U5	5AZ4	6AQ7	6BJ6	6CN7	6S47	7A6	7K7	12B06	12SN7GT
1U5	5C6B	6AR5	6BK5	6CN7	6SD7GT	7A7	7Y4	12BE6	12SQ7
1V2	5R4	6A55	6BK7	6CQ8	6SF5	7B4	7Z4	12BF6	12V6GT
1X2	5T8	6AT6	6BL7GT	6CR6	6SG7	7B5	7B6	12AB5	12X4
2AF4	5U4	6AU4GT	6BN6	6C5	6SH7	7B6	7C4	12A05	12BR7
2BN4	5U8	6AUSGT	6BQ6GT	6CU5	6S7	7B7	7C5	12AT6	12B7
2CY5	5V4G	6AU6	6BQ7	6CU6	6SK7	7B8	7C6	12A07	12CA5
3AL5	5V6GT	6AUB	6BR8	6D6	6SL7	7C4	7C5	12A06	12CN5
3BC5	5X8	6AV5GT	6BS8	6DE6	6S07	7C5	7C6	12A07	12D4
3BN6	5Y3	6AV6	6BY5G	6DG6GT	6SR7	7C6	7C7	12A08	12F8
3BR4	6A34	6AW8	6B4	6D6	6T4	7C7	7C8	12AV6	12K5
3CB6	6AC7	6AX4GT	6BZ7	6F6	6T8	7E5	7E6		35W4
354	6AF4	6AX5GT	6C4	6H6	6U5	7E6	7E7		
3V4	6AG5	6BA	6CA8	6J6	6U8	7E7	7E8		
4BQ7A	6AGT	6BA6	6CB6	6J6	6V6GT	7F7			

BRAND NEW 1-YEAR GUARANTEED TV PICTURE TUBES

Below Listed prices do not include duty. Add Additional \$5.00 Deposit on tube sizes to 20", on 21" and 24" tubes—\$7.50. Deposit refunded immediately when tube is returned prepaid. Aluminized tubes—\$4.00 extra. Picture tubes shipped only to continental USA and Canada—All tubes F.O.B. Harrison, N. J.

10BP4	7.99	17CP4	16.99	21AMP4	17.99	21KP4	18.99
16GP4	16.09	17TP4	16.99	21AP4	18.79	21VP4	18.99
16RP4	11.99	20CP4	15.99	21WP4	17.49	21WP4	17.49
17AP4	15.29	20HP4	17.89	21EP4	17.29	21YP4	18.39
17BP4	13.49	21ALP4	18.79	21FP4	18.39	24CP4	27.79

ATTENTION QUANTITY USERS! Big Discounts Are Yours... Call or Write For Our 1000 Tube "Private Label" Special! Money cheerfully refunded within five (5) days, if not satisfied!

SHIPPING INSTRUCTIONS: TRU-VAC PAYS YOUR POST-AGE on orders of \$5 or more in USA and Territories. Send approximate postage on Canadian and foreign orders. Any order less than \$5 requires 25¢ handling charge. Send 25¢ on C.O.D.'s.

ANY TUBE NOT LISTED ALSO AVAILABLE AT 35¢ EACH!

Sensational Offer!

"Self Service"

TUBE CHECKERS

\$37.95

FOB Our Warehouse

Let our customers test their own tubes! These reliable, reconditioned 22-socket tube checkers will return your investment in one week or less with your part, no effort on tested console models. FIELD-PLATE WITH KEY FOR LIGHTED HEAD!

LOOK! 1000 USED TV'S

Costly, famous make console models with little or no tube replacement! Require only minor adjustments. Perfect for resale, or as your own second set! 16", 17" and 19" screens... none smaller! Sets shipped FOB, Harrison, N. J.


\$16.95

(As Is)

# TRU-VAC

Harrison Avenue • Box 107 • Harrison, N. J. Humboldt 4-9770

POPULAR ELECTRONICS

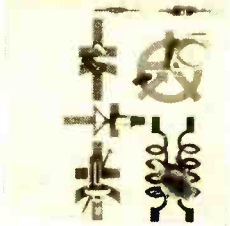

Send  
**POPULAR  
ELECTRONICS**  
Every Month

NAME.....

ADDRESS.....

CITY..... ZONE... STATE.....

3 years for \$10

Check one:  2 years for \$7

1 year for \$4

Payment Enclosed  Bill Me

In the U. S., its possessions and Canada.  
Foreign rates: Pan American Union countries, add .50 per year; all other foreign countries, add \$1 per year.

Mail to:

**POPULAR ELECTRONICS**

Dept. PE-661 H, 434 S. Wabash Ave.

CHICAGO 5, ILL.

**Kenya**—ZGW76, Mombasa, 4965 kc., was tuned with music and chanting from 2224 to 2300. at which time there was an Eng. ID. (PY1PE1D)

ZGW71, Nairobi, 4934 kc., has been noted from 2330 with Eng. ID and news; weak. (CB)

**Malaya**—The BBC Far Eastern Station, Singapore, 11,820 kc., is being tuned from

**FREE LEAFLET**

Your Short-Wave Editor has a new leaflet available on time and standard frequency stations. Ask for a copy of Leaflet L, addressing your request to Box 254, Haddonfield, N. J. Please include return postage.

1130 to 1150 s/off on Wednesdays with a pop music show, program preview, and close in English. (VE1PE1R)

**Monaco**—This is the latest schedule from *Trans-World Radio*, Monte Carlo: 9705 kc. at 0230-0330 in Eng. (0330-0800 Sundays); 7110 kc. at 1030-1055 in German; 11,765 kc. at 1100-1125 in Russian; 11,715 or 11,845 kc. at 1130-1145 in Arabic (Monday, Wednesday, and Friday only); 6140 kc. at 1155-1210 in Eng. and at 1210-1255 in German; 6115 kc. at 1400-1425 in German and at 1500-1600 in Eng.; and 9625, 9690, or 9705 kc. at 1300-1325 in Swedish and at 1330-1355 in Norwegian. (WPE2AXS, WPE2CKI, WPE3NF, WPE4FI, WPE6BOM)

**Mozambique**—Lourenco Marques, 15,148 kc., is heard at 1200-1300 in Portuguese, and at 1300-1400 on Tuesdays and Fridays in French. (WPE4FI)

CR7BV, Lourenco Marques, has moved up to 4843 kc. and was noted around 2325 with pop music and English. A tentative logging is Porto Amelia, 9598 kc., heard weakly from 1423 to 1430 s/off with Portuguese music and language. (WPE3NF)

**Netherlands**—Hilversum operates at 1615-1705 on 15,445 kc. (replacing 9590 kc.) and 11,730 kc. to N.A. and on 6020 kc. to Europe. The "Happy Station Program" is beamed to Australia, New Zealand, and Pacific areas on Sundays at 0100-0200 on 9715 and 11,800 kc. (WPE1CCC, WPE2BRH, WPE2CKI, WPE2EGU, WPE4CSZ, WPE6BAB, WPE8BAG, WPE8BZP, WPE9DS, WPE0ATE, VE4PE2U)

**New Zealand**—Wellington's current schedule reads: to Pacific Islands daily on ZL7, 6080 kc., and ZL2, 9540 kc., at 0100-0345; to Australia on the same channels daily at 0400-0645; to Antarctica on Sundays only at 0315-0345 on ZL3, 11,780 kc.; to Samoa in Samoan on Mondays at 1540-1555 and on Tuesdays at 0200-0215, and to the Cook Islands in Rarotongan on Wednesdays at 0210-0225 and Saturdays at 0300-0315 on ZL2, 9540 kc., and ZL7, 6080 kc. (WPE8AGY, WPE8CJA, WPE9NY, WPE0ARG, WPE0ATE, WPE0BFP)

**Nigeria**—The Western Nigerian Radio-vision Service, Ibadan, has moved from 6049 kc. to 6185 kc. where it has been noted with Eng. news at 0530-0535. (WPE3NF)

**Norway**—*R. Norway* now airs "Norway This Week" in Eng. on Sundays at 0700-0720 on 6130, 11,850, 15,175, 17,825, 21,730, and 25,900 kc.; at 0900-0920 and 1200-1220 on 6130, 9610, 17,825, 21,730, and 25,900 kc.; at 1900-1925 on 6130, 11,850, 15,175, and 17,825 kc.; and at 2100-2125 (and Mondays at 0000-0025) on 6130, 9610, 11,850, and 15,175 kc. The Norwegian Home Service is aired weekdays at 0100-0200 (Sundays at 0200-0520) on 6130, 11,850, 15,175, 17,825, 21,730, and 25,900 kc., and weekdays at 1215-1600 (Sundays at 1220-1700) on the same channels (except 11,850 kc.) plus 9610 kc. (*WPE1BDB, WPE1CE, WPE2DXB, WPE2ESP, WPE4FI, WPE5BGP, WPE8MS, JE, SCDX*)

**Pakistan**—Karachi has been tuned on 15,195 kc. with the Home Service Eng. news at 0955; on 9645 kc. with native music and Eng. news at 0015-0140; and on 11,672 kc. with Eng. to Turkey at 1315-1400. (*WPE2CKI, WPE3NF, WPE9BHZ*)

**Peru**—Two very rarely reported stations are *R. Pasco*, Cerro de Pasco, 6130 kc., noted in the clear after 0100 in Calif.; and *R. Cuzco*, Cuzco, 6240 kc., heard in Brazil around 1800 with commercials, L.A. music, all Spanish. (*WPE6BPN, PY1PE1D*)

**Pitcairn Island**—Several months ago *World Radio Handbook* listed VR6AC, 14,000 kc., as being on the air with a religious broadcast. This station was logged last December, tentatively, and a report sent. The veri is in; the station okayed the report. It was heard around 2130, very weakly, with what sounded like an anthem. (*WPE1KW*)

**Poland**—Warsaw has discontinued all Eng. service to N.A., and has no plans for resuming it. (*WPE9WR, WPE0VB*)

**Portugal**—Lisbon is again active at 0500-1230 on 21,495 kc., replacing 15,380 kc. (*WPE4FI*)

**Sarawak**—Kuching is heard in Eng. at 0800



The listening post of Peter Collins, WPE2BXD, in Elmira, N. Y., boasts a Hallicrafters SX-99 receiver, a Heath DX-20, and an ohmmeter. Peter has a total of 40 stations logged, 30 verified.

June, 1961

## CITIZENS' BAND 2-WAY RADIO!!



"Famous Name" Brand!

27 Mc. "Radio Phone"

Brand new & terrific!

Lowest Price Ever!

Only \$39.50!

Ideal for marine, mobile or fixed based 2-way communication: from ship to shore, home or club; vehicle to vehicle or home; house to car, garage or work. Hams, construction workers, sportsmen—this is for you—at a price you can afford!

- 5 W. transmitter crystal controlled for one channel.
- Built-in squelch control—stops useless noise.
- Range up to several miles.
- Compact, portable, weighs only 8 lbs!
- Dim.: 9 3/4" h. x 7 1/4" w. x 5" deep. Handy!
- Push-to-talk button on speaker-mike aids one-hand operation.
- Off-On Volume control.
- Eye-catching, aluminum weatherproof cabinet in 2-tone blue.
- The Radio-Phone is available in two models for operation from a 6-volt DC battery or standard 115-volt AC house current, or from a 12-volt DC battery or 115 volt AC house current. To operate, simply plug in.
- Limited quantity. Act NOW!

**\$39.50**

EA.:

**PAIR: \$75.00**

Send check with order. Include postage for 10 lbs. per unit (20 lbs. per pair) or we ship express collect.

### GLOBE ELECTRONICS

3103 W. Pico Blvd.

Santa Monica, Calif.

Phone: EX 3-7206

## PORT ARTHUR COLLEGE ELECTRONICS COMMUNICATIONS

AM FM Television Broadcast Engineering  
Industrial Electronics—Automation

CHECK THESE FEATURES: Tuition \$36 per mo., room & board \$52 per mo. in dorm on campus. College operates 5 KW broadcast station. Students get on-the-job training at studios on campus. FCC license training with all courses. Well equipped classrooms & lab., am fm transmitters, radar & marine eqmt., television camera chain, experiment lab test eqmt. & other training aids. Our graduates in demand at good salaries. Free placement service. Have trained men from all 50 states. Approved for GI. Write to Dept. P-661 for Free Booklet.

**PORT ARTHUR COLLEGE** Port Arthur  
Texas

Established in 1909

### Experimenters • Amateurs • Hobbyists

Extraordinary values await you in government surplus electronic components. Don't buy anything until you have our "Bargain Bulletin"; new material for mere dimes on the dollar. Remember, everything is brand new; here are typical values:

40 meter, 75 watt plug in RF coil, type OEL.....	12 oz.	\$0.95
Scope xfr, 115 v pri, 2500/3 and 2.5/1.75.....	3 lbs.	1.95
Selsyns, Husky type II-1, C56701, 115 v/60 cye.....	15 lbs.	7.95
Differential relay, one mil operates, 9000 ohm x 2.....	1 lb.	3.39
Pwr xfr for 1M freq meter, 510/25, 12.6/0.9 6.3/0.5.....	3 lbs.	2.19
Choke, 5 hy/105 mils, 100 ohm, double shell vert.....	3 lbs.	.95
Pwr xfr, 115/220/30 cye, 600 ct/350 & 12.6 ct/1.....	18 lbs.	4.29
Oil cond., 4 mfd/1650 dc. EV terminals.....	3 lbs.	2.29
6SN7 vacuum tubes, a dozen for.....	3 lbs.	5.95
Output xfr, 8000 to 15/125/250, 25 watts, compact.....	4 lbs.	1.95

WRITE TODAY FOR FREE GOVERNMENT SURPLUS BARGAIN BULLETIN

**JOE PALMER** P.O. Box 6188 CCC,  
Sacramento, California

# RADIO PARTS STORES & HI-FI SALONS!

Hundreds of dealers across the nation profit by selling POPULAR ELECTRONICS each month to their customers. Are you one of them? POPULAR ELECTRONICS helps build store traffic . . . keeps customers coming back month after month for the merchandise you sell—and, best of all, you earn a neat profit on each copy sold—NO RISK INVOLVED.

So get all the details on selling POPULAR ELECTRONICS, the world's largest selling electronics hobbyist magazine. Or, order your copies now. Just use the handy coupon below.

Direct Sales Department  
Popular Electronics  
One Park Avenue, New York 16, New York

At: Jerry Schneider

Send me ..... copies of POPULAR ELECTRONICS for resale in my store each month. No risk involved on my part.

Send me details on selling POPULAR ELECTRONICS in my store.

STORE NAME.....

ADDRESS.....

CITY..... ZONE..... STATE.....

SIGNATURE.....

PE-661

## SCIENCE ENGINEERING

B.S. Degree—36 mos. • B.E. degree—27 mos.  
Accelerated year-round program. Aero., Chemical, Civil, Elec., Mech., Metallurgical; Math., Chemistry, Physics. Modest rate. Earn board. New classes start June, July, Sept., Jan., March. Catalog, 2361 E. Washington Blvd., Fort Wayne 2, Indiana.

### INDIANA TECHNICAL COLLEGE



#### HEADS YOU WIN!

Yes, you'll be a winner every time by saving "heap plenty" on all of your high fidelity requirements. Write us and see! Ask too for audio discount catalog A-12.

#### KEY ELECTRONICS

120 Liberty St., N. Y. 6, N. Y.

## EARN Electronics Engineering DEGREE

You can earn an A.S.E.E. degree at home. College level HOME STUDY courses taught so you can understand them. Continue your education, earn more in the highly paid electronics industry. Missiles, computers, transistors, automation, complete electronics. Over 27,000 graduates now employed. Resident school available at our Chicago campus—Founded 1934. Send for free catalog.

AMERICAN INSTITUTE OF ENGINEERING & TECHNOLOGY  
1135 West Fullerton Parkway, Chicago 14, Ill.

with a BBC news relay and a variety music program at 0815. (WPEØVB)

South Africa—Paradys operates at 0600-1200 on 25,800 kc., replacing 21,495 kc., and at 0600-1100 on 15,235 kc., after which it moves to 15,300 kc. until 1500. (WPE4FI)

The 7185-kc. outlet has been noted in the

### SHORT-WAVE CONTRIBUTORS

Tommy Natkin (WPE1ADI), Stamford, Conn.  
Jim Silk (WPE1AGM), Madison, Conn.  
Thomas F. Carten (WPE1APS), Stratford, Conn.  
Richard T. White (WPE1BBB), Pawtucket, R. I.  
Robert Anderson (WPE1BDB), New Britain, Conn.  
Thomas Lizak (WPE1CCC), Fall River, Mass.  
David Gerns (WPE1CE), Concord, Mass.  
Thomas Cardullo (WPE1CHS), Somerville, Mass.  
Bud Barto (WPE1HC), Naugatuck, Conn.  
Johnny Chane (WPE1KW), Naugatuck, Mass.  
Robert Newhart (WPE1KNS), Merchantsville, N. J.  
Albert Mencher (WPE1BRH), Bayside, N. Y.  
Thomas Campanile (WPE1CKI), Brooklyn, N. Y.  
Jeffrey Fritz (WPE1CYE), Wantagh, N. Y.  
Bart Lee (WPE1DLT), Bergenfield, N. J.  
Ronnie Breiger (WPE1DTP), Englewood, N. J.  
Michael Russo (WPE1DXB), White Plains, N. Y.  
Michael Epstein (WPE1EGU), Brooklyn, N. Y.  
Frank Brandon (WPE1ESP), Schuylerville, N. Y.  
Elliot Feldman (WPE1ELM), New York, N. Y.  
Kay Barber (WPE1VB), Elmira, N. Y.  
Joseph Clawson, Jr. (WPE1BAR), Tarentum, Pa.  
Donald Campbell (WPE1BCE), Washington, D. C.  
Arthur White (WPE1CCG), Pittsburgh, Pa.  
George Cox (WPE1JNF), New Castle, Del.  
Gene Pearson (WPE1AIX), Birmingham, Ala.  
John Cobb, Jr. (WPE1AII), Cartersville, Ga.  
Grady Ferguson (WPE1ABC), Charlotte, N. C.  
Billy Piver (WPE1CKG), Washington, N. C.  
Donald Doyle (WPE1COK), St. Simons Island, Ga.  
Richard Snyder (WPE1CSZ), St. Petersburg, Fla.  
Roger Legge (WPE1FI), McLean, Va.  
Alan Knapp (WPE1HI), Roanoke, Va.  
William Bink (WPE1IG), New Orleans, La.  
Lee Prall (WPE1BGP), Tulsa, Okla.  
Stewart MacKenzie (WPE1A), Long Beach, Calif.  
Jerry Neves (WPE1AGI), Pacific Grove, Calif.  
John Hoogerheide (WPE1BIB), Medford, Oregon  
Jack Overcash (WPE1BOM), Fairfield, Calif.  
Shaler Panaseda (WPE1BPN), Pasadena, Calif.  
Bob Chamberlain (WPE1BPO), Los Angeles, Calif.  
J. Art Kussell (WPE1BEZ), San Diego, Calif.  
Ronald Luyster (WPE1AGI), Flushing, Ohio  
Lowell Shaffer (WPE1BAG), Dayton, Ohio  
James McDonald (WPE1BQH), Cincinnati, Ohio  
Bill Sweitzer (WPE1BZP), Cleveland, Ohio  
Dale Guthrie (WPE1CJA), Wheeling, W. Va.  
Joseph Bove (WPE1CKW), Norwood, Ohio  
Dan Wilt (WPE1HF/6), Ingewood, Calif.  
Mike Kander (WPE1MS), Dayton, Ohio  
Robin Fisher (WPE1OG), Beach City, Ohio  
Barry Norrgran (WPE1BHZ), Lansing, Ill.  
Charles Cowell (WPE1CD), Peoria, Ill.  
W. H. Foley (WPE1CKR), Depauw, Ill.  
Gene Staton (WPE1CNA), Kokomo, Ind.  
Jim Hall (WPE1DS), Loves Park, Ill.  
Mike Nielsen (WPE1NY), Park Ridge, Ill.  
Donald Sullivan (WPE1WR), Villa Park, Ill.  
John Beaver, Sr. (WPE1OE), Pueblo, Colo.  
Al Boettler (WPE1ARG), Ladue, Mo.  
Bill Holscher (WPE1BFP), Webster Groves, Mo.  
Tom Goetz (WPE1BFP), Ladue, Mo.  
George Buchanan (WPE1ØVB), Webster Groves, Mo.  
Bill Barclay (VE3PE1DZ), Scarborough, Ontario  
Jim Roik (VE4PE1U), Winnipeg, Manitoba  
David Bennett (VE7PE1R), Richmond, B. C.  
Giacomo Perolo (PY1PE1D), Bauru, Brazil  
Charles Boehnke (CB), Reno, Nevada  
John Eisentrager (JE), Fresno, Calif.  
Sweden Calling DXers Bulletin (SCDX)

Commercial Service in Eng. with world news at 2330-2335, music until 0000, then a weather report. (WPE9NY)

Spain—Malaga is being heard well on 6183 kc. (having moved from 6175 kc.) at 1600. (WPE3NF)

Always say you saw it in—POPULAR ELECTRONICS

Madrid is noted on 7105 kc. at 2245 in Spanish and at 2315 in Slovak to Europe, and from 0130 to 0212 in Spanish to Eastern Europe. Do not confuse this station with several other outlets which also use the same channel during these times. (WPE5AG, WPE0AE)

**Sweden**—Here is Stockholm's summer schedule: 0730-0845 on 15,420 and 17,845 kc. in Eng. and Swedish; 0900-0930 on 17,840 kc. in Eng.; 0945-1100 on 15,240 and 17,845 kc. in Eng. and Swedish; 1115-1230 on 11,705 and 15,240 kc. in Eng. and Swedish; 1245-1400 on

N.A.) and 2300-2345 on 11,805 kc. in Spanish. The Home Service Program I is relayed at 0000-0400 and 1200-1700 on 6065 kc., and at 0400-0715 on 11,880 kc. Motala, 7270 kc., also relays Program I, except Sundays at 0200-1700 and daily at 1200-1700 when it relays Program II. They are most anxious to receive reports for the 1200-1700 xmsn on 6065 kc. (WPE4CKG, WPE4FI, WPE9CKR, WPE9CNA, VE3PE1DZ, SCDX)

**Tanganyika**—Dar-es-Salaam is noted briefly at 2313 with Eng. news on 5050 kc. (WPE0VB)

**Togo**—Lome operates at 0100-0300 and at 1600-1700 (Saturdays to 1800). (WPE4FI)

**Turkey**—TAT, Ankara, 9515 kc., operates to N.A. in Eng. at 1815-1900; to Europe at 1645 on 7285 kc.; to S. E. Asia at 0845 on 17,820 kc. (WPE2CYE, WPE2DLT, WPE2DTO, WPE3BAR)

**United Arab Republic**—Damascus may use 6200 kc. rather than 5704 kc. around 2330 with an Arabic xmsn. (WPE3NF)

**Windward Islands**—The Windward Islands B/C Service, St. Georges, Grenada, is now operating on a new frequency of 11,955 kc. (replacing 11,715 kc.) at 1800-2115 for their evening xmsn to Jamaica. (WPE4FI, WPE8AGY)

**Unidentified**—WW2XAJ, 11,925 kc. has been noted at 1615-1800 as a steady 'whistle' behind *Deutsche Welle*. The tone is broken for four seconds every two minutes; the ID is given in low Morse code at 25 and 55 minutes past the hour. (Short-Wave Editor)

### SHORT-WAVE ABBREVIATIONS

anmt—Announcement	N.A.—North America
BBC—British B/C Corp.	ORM—Station interference
B/C—Broadcasting	R.—Radio
Eng.—English	s/off—Sign-off
ID—Identification	s/on—Sign-on
kc.—Kilocycles	veri—Verification
kw.—Kilowatts	xmsn—Transmission
L.A.—Latin America	xmtr—Transmitter

15,240 kc. in Eng. and Swedish; 1515-1515 on 11,705 kc. in German and Eng.; 1530-1600 on 7210 in Eng.; 1615-1745 on 11,705 kc. in Spanish and Portuguese; 1700-1730 on 6065 kc. in German; 1800-1930 on 11,705 and 15,240 kc. in Spanish and Portuguese; 2000-2045 on 11,705 and 11,805 kc. in Swedish; 2045-2115 on 11,805 kc. in Eng. (to N.A.); 2045-2215 on 11,705 kc. in Portuguese and Spanish; 2130-2245 on 11,805 kc. in Swedish and Eng. (to Western

34

¢

## ELECTRONIC MARKET

### 1 YEAR GUARANTEED

### RADIO-TV TUBES

**EACH**

**\$32**

Per 100 TUBES

**ELECTRONIC MARKET**

3750 E. 10th CT. MIAMI, FLORIDA

Phone: OXford 1-5331

ONE OF THE LARGEST INVENTORIES IN THE COUNTRY

All tubes not necessarily new but may be electronically perfect factory 2nds or used. Each clearly marked. ELECTRONIC MARKET will replace FREE any tube that becomes defective in use within 1 year from date of purchase. All tubes individually boxed and marked. Partial Listing Only—Thousands More Tubes in Stock.

024	354	513	6A9D	6BL7GT	6CW7	6D7	6U8	7B4	7E7	12A05	12BE6	12SA7
10B01	487A	5AR4	6AV5T	6BN6	6CB6	6CS7	6E5	6E6	7E5	12AT6	12BE6	12SB7
10V50	487B	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12AT7	12BE7	12SB7
185	487C	6AR5GT	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
114	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
104	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
105	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
106	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
107	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
108	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
109	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
110	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
111	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
112	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
113	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
114	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
115	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
116	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
117	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
118	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
119	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
120	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
121	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
122	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
123	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
124	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
125	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
126	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
127	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
128	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
129	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
130	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
131	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
132	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
133	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
134	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
135	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
136	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
137	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
138	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
139	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
140	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
141	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
142	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
143	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
144	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
145	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
146	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
147	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
148	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
149	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7
150	5A80	6AR5	6AV6	6BD7	6CB7	6CS7	6E6GT	7E5	7E6	12A05	12BE6	12SB7

**SHIPPING INSTRUCTIONS: ELECTRONIC MARKET**

**PAYS YOUR POSTAGE** on orders of \$5 or more in U.S.A. and Territories. Send approx. postage on Canadian and foreign orders. Any order less than \$5 requires 25c handling charge. Send 25¢ in C.O.D.

ANY TUBE NOT LISTED ALSO AVAILABLE AT 34¢ EACH

## new! 7-Band SWL/DX Dipole Kit

### for 11.13.16.19.25.31.49 meters

Here's a low cost 7-band receiving dipole antenna kit that will pick up those hard-to-get DX stations. Everything included . . . just attach the wires and you're on the air! Weatherproof traps enclosed in Poly-Chem for stable all-weather performance. Over-all length of antenna - 40 feet.

Complete with

- 8 Trap Assemblies
- Transmission Line Connector
- Insulators
- 45 ft. No. 16 Tinned Copper Wire
- 100 ft. of 75 ohm twin lead

WRITE FOR NAME OF NEAREST DISTRIBUTOR

## SWL-7 \$14.75

**Mosley Electronics, Inc.** 4610 N. Lindbergh • Bridgeton, Missouri

# INDEX

## TO VOLUME 14

### Jan.-June, 1961

#### AMATEUR RADIO AND SWL

Across the Ham Bands (Brier).....	
Zero-Beating and Stabilizing Transmitters.....	87 Jan.
SSB vs. AM Phone.....	87 Feb.
Trouble-Shooting Ham Equipment.....	67 Mar.
Selecting a Multimeter for your Shack.....	87 Apr.
Sending QSL and SWL Cards.....	85 May
How to Avoid Violations.....	93 June
Armed Forces Day Program.....	32 May
Booster, BC-Band DX (Swink).....	63 Feb.
Costra's Radio Voice (Stanbury).....	52 Mar.
CB Rig Goes "Hom" (Noll).....	64 June
Converter, Simple 6-Meter (Brier).....	89 Feb.
Converters, New Life for Obsolete (Smith).....	76 Apr.
DX'ing on the Bonus Band (Kneitel).....	55 Feb.
Edison Award, Amateur DX'ers Win.....	114 May
English-Language Voices from Europe (West).....	41 Jan.
Guying Tips for Ham Antenna Tower (Darr).....	52 Jan.
Ham's World, It's a (ARRL).....	79 Feb.
Modulator, Two-Tube Screen (Brier).....	68 Mar.
Nuvistor R.F. Amplifier (Brier).....	87 May
QSL, The ABC's of the (Bennett).....	78 Jan.
Radio Swan (Kneitel).....	52 Mar.
Relay, Low Power/High Power (Brier).....	95 June
Short-Wave Monitor Registration.....	
113 Feb., 109 Mar., 105 Apr., 123 May, 84 June	
Short-Wave Receiver, Selecting a.....	75 Jan.
Short-Wave Report (Bennett).....	
71 Jan., 90 Feb., 88 Mar., 91 Apr., 105 May, 83 June	
Between the Missions.....	90 Feb.
Standard Frequency and Time Stations.....	91 Apr.
Calibrating a Receiver.....	105 May
False Reporting.....	83 June
"Spotting" Switch (Brier).....	89 Jan.
Voltmeter, Kilowatt R.F. (Brier).....	89 Apr.

#### CITIZENS BAND RADIO

CB Heathkit (GW-10).....	90 Apr.
CB Rig Goes "Ham" (Noll).....	64 June
CB Under \$100 (Lafayette HE-20).....	67 Jan.
Channel Spatter (Stoner).....	90 Jan.
Converter, Low-Cost (Int'l. Crystal Mobilette 61).....	67 Apr.
FCC Report (Tall).....	
8 Jan., 12 Feb., 10 Mar., 10 Apr., 10 May	
Getting Peak CB Performance (Strippel).....	58 May
On the Citizens Band (Kneitel).....	
85 Jan., 55 Feb., 79 Mar., 93 Apr., 83 May, 87 June	
Q-Multiplier (Stoner).....	76 Mar.
Receiver, Radio-Control 11-Meter (Winter).....	81 Mar.

#### CONSTRUCTION PROJECTS

AC/DC Electronic Load (Reed).....	89 June
Amplifier, Direct-Coupled Hi-Fi (Keroes).....	46 Mar.
Amplifier, Nuvistor R.F. (Brier).....	87 May
Burglar Alarm, Infrared (Caringella).....	46 Feb.

Car Burglar Alarm System (Lewis).....	70 Mar.
CB Channel Spotter (Stoner).....	90 Jan.
CB Rig Goes "Ham" (Noll).....	64 June
Computer, Flip-Flop (Sienkiewicz).....	72 Apr.
Converter, Simple 6-Meter (Brier).....	89 Feb.
Converters, New Life for Obsolete (Smith).....	76 Apr.
Darkroom Meter (Friedman).....	50 Apr.
DX Booster, BC-Band (Swink).....	63 Feb.
Fire Alarm, Fast-Acting (Caringella).....	46 Apr.
Fish Caller, Electronic (Bucher).....	74 June
Flexiformer (Schmitt).....	62 Feb.
Flip-Flop Circuits (Sienkiewicz).....	59 Mar.
FM Listening, Private (Trauffer).....	62 Apr.
Heads . . . or Tails? (Strand).....	51 June
Heart, Listen to Your (Lininger).....	47 June
Intercom, 3-Way (Sienkiewicz).....	52 May
Metronome, Transistorized (Latner).....	54 June
Modulator, Two-Tube Screen (Brier).....	68 Mar.
Noise that Banishes Pain (Fowler).....	47 Jan.
Oscillator, Code Practice (Shmigelski).....	102 Jan.
Oscillator Experiment, Ferrarsonant (Patrick).....	102 Jan.
Personal Portables, Big Sound from (Pugh).....	69 Apr.
Pickups, Vibration (Garner).....	85 Apr.
Q-Multiplier, Citizens Band (Stoner).....	76 Mar.
Radiation Detector (Pugh).....	83 Jan.
Radio, Thinking Man's (Garner).....	68 Jan.
Receiver, Radio-Control 11-Meter (Winter).....	81 Mar.
Relay, Low-Power/High Power (Brier).....	95 June
R.F. Probe Peps up VTVM (Frantz).....	77 May
Soil Moisture Meter (Wilensky).....	85 June
Speaker, High-Compliance (Anderson).....	68 May
Spotting Switch (Brier).....	89 Jan.
Storage Battery Tester (Chapel).....	92 June
Sweet Sixteen (Kyle).....	55 Jan.
Sweet Sixteen, More About.....	58 Apr.
Telephone Holder, Musical (Friedman).....	71 June
Transidip (Aurick).....	70 May
Transistor Mounting Tips.....	80 May
Transistor Saver (Lang).....	90 June
Transistor Tester, In-Circuit (Henry).....	75 Feb.
Tweeter, Sweeter with a (Kyle).....	55 Apr.
Voltmeter, Kilowatt R.F. (Brier).....	89 Apr.

#### DEPARTMENTS

Across the Ham Bands (Brier).....	
87 Jan., 87 Feb., 67 Mar., 87 Apr., 85 May, 93 June	
Carl and Jerry (Frye).....	
103 Jan., 96 Feb., 89 Mar., 98 Apr., 107 May, 99 June	
FCC Report (Tall).....	
8 Jan., 12 Feb., 10 Mar., 10 Apr., 10 May	
Hi-Fi Showcase.....	
12 Jan., 28 Feb., 22 Mar., 14 Apr., 14 May, 18 June	
Letters from Our Readers.....	
18 Jan., 16 Feb., 14 Mar., 20 Apr., 35 May, 10 June	
New Products.....	
32 Jan., 22 Feb., 32 Mar., 32 Apr., 22 May, 30 June	
Notes from the Editor.....	6 Jan., 6 Feb., 6 Mar.
On the Citizens Band (Kneitel).....	
85 Jan., 73 Feb., 79 Mar., 93 Apr., 83 May, 87 June	
POP'tronics Bookshelf.....	
24 Jan., 24 Feb., 18 Mar., 22 Apr., 28 May, 24 June	
POP'tronics News Scope.....	
8 Feb., 8 Mar., 6 Apr., 6 May, 6 June	
Short-Wave Report (Bennett).....	
71 Jan., 90 Feb., 88 Mar., 91 Apr., 105 May, 83 June	
Space Electronics (Ferrell).....	64 Apr., 74 May, 68 June
Tips and Techniques.....	
111 Jan., 36 Feb., 26 Mar., 36 Apr., 38 May, 36 June	
Transistor Topics (Garner).....	
80 Jan., 84 Feb., 85 Mar., 82 Apr., 102 May, 96 June	

## FEATURE ARTICLES

Audible Ball for the Blind.....	82	May
Bone Mending, Electronics Checks (Busse).....	46	May
Carl and Jerry (Frye)		
103 Jan., 96 Feb., 89 Mar., 98 Apr., 107 May,	99	June
Castro's Radio Voice (Stanbury).....	52	Mar.
Connections are Important (Kyle).....	73	June
Curves (Harrison).....	63	Mar.
Dials and Nameplates, Make Your Own (Friedman)	59	Apr.
DX'ing on the Bonus Band (Kneitel).....	55	Feb.
Electron Chemistry (Ebel).....	72	Mar.
English-Language Voices from Europe (West).....	41	Jan.
Flip-Flop Circuits (Sienkiewicz).....	59	Mar.
Flip-Flop Computer (Sienkiewicz).....	72	Apr.
Fly Safely, They'll (Gilmore).....	41	June
Getting Peak CB Performance (Strippel).....	58	May
Ham Antenna Tower, Guying Tips for (Darr).....	52	Jan.
Ham's World, It's a (ARRL).....	79	Feb.
Hi-Fi Fan "Rolls His Own" (Corey).....	51	Jan.
Hi-Fi Speakers, Mounting.....	54	Feb.
Hi-Fi Testing (Parts 2 and 3) (Harrison)		
Intermodulation Distortion Analyzer.....	63	Jan.
Square-Wave Generator.....	68	Feb.
Infrared (Caringella).....	41	Feb.
Laser, Introducing the (Gilmore).....	50	Feb.
Lightning (Zuckerman).....	59	Jan.
Newark Airport Tower (Haas).....	72	Jan.
Noise that Banishes Pain (Fowler).....	47	Jan.
On the Grid (Sinclair).....	66	Feb.
Ping-Pong Stereo (Whyte).....	56	Mar.
QSL, The ABC's of the (Bennett).....	78	Jan.
Quiz, Vacuum Tube (Balin).....	59	Feb.
Radar Explores the Moon (Gilmore).....	41	May
Radar Waves, Danger of (Gilmore).....	41	Mar.
Radio Swan (Kneitel).....	52	Mar.
Robot Lawn Mower.....	110	Jan.
Roll-Away Nose Cone.....	73	May
Roundword Puzzle (Kindler).....	84	Jan.
Semiconductor Diode (Kyle).....	88	May
Space Electronics, Introducing (Ferrell).....	64	Apr.
Speed Mail, Electronic (Gilmore).....	41	Apr.
Tape Decks for Stereo (Flanagan).....	48	May
Tape Speeds—Then and Now (Flanagan).....	67	June
Tiros II, Tinting.....	60	Feb.
Toscanini in Stereo (Flanagan).....	62	May
Tuned Circuits, Explaining (Harris).....	64	May
TV Test Patterns, Interpreting (Locke).....	59	June
Zener Diode (Shaughnessy).....	76	June

## HI-FI, STEREO AND AUDIO

Amplifier, Direct-Coupled (Keroes).....	46	Mar.
Connections Are Important (Kyle).....	73	June
Curves (Harrison).....	63	Mar.
FM Listening, Private (Trauffer).....	62	Apr.
Hi-Fi Fan "Rolls His Own" (Corey).....	51	Jan.
Hi-Fi Showcase		
12 Jan., 28 Feb., 22 Mar., 14 Apr., 14 May,	18	June
Hi-Fi Testing (Parts 2 and 3) (Harrison)		
Intermodulation Distortion Analyzer.....	63	Jan.
Square-Wave Generator.....	68	Feb.
Ionovac, Introducing the.....	56	May
Mike Kit, First (CBS Electronics "Mark II").....	91	June
On the Grid (Sinclair).....	66	Feb.
Personal Portables, Big Sound from (Pugh).....	69	Apr.
Pickups, Vibration (Garner).....	85	Apr.
Ping-Pong Stereo (Whyte).....	56	Mar.
Speaker, High-Compliance (Anderson).....	68	May
Speakers for Stereo, Low-Cost.....	80	Apr.
Speakers, Mounting.....	54	Feb.
Sweet Sixteen (Kyle).....	55	Jan.

Sweet Sixteen, More About.....	58	Apr.
Tape Decks for Stereo (Flanagan).....	48	May
Tape Speeds—Then and Now (Flanagan).....	67	June
Toscanini in Stereo (Flanagan).....	62	May
Tuner, AM/FM Stereo (Heath).....	78	Feb.
Tuner Kits Come of Age.....	56	June
Tweeter, Sweeter with a (Kyle).....	55	Apr.

## PRODUCT REPORTS

CB Heathkit (GW-10).....	90	Apr.
CB Under \$100 (Lafayette HE-20).....	67	Jan.
Converter, Low-Cost CB (Int'l. Crystal Mobilette 61)	67	Apr.
Flexiformer (Superior Electric).....	62	Feb.
Ionovac, Introducing the (DuKane).....	56	May
Line Voltage, Vary that (EICO 1073).....	81	May
Mike Kit, First (CBS Electronics "Mark III").....	91	June
Short-Wave Receiver, Selecting a.....	75	Jan.
Speakers for Stereo, Low-Cost (Nordic, Realistic).....	80	Apr.
Tuner, AM/FM Stereo (Heath AJ-10).....	78	Feb.
Tuner Kits Come of Age (Scott, Harman-Kardon).....	56	June

## TEST EQUIPMENT


Hi-Fi Testing (Parts 2 and 3) (Harrison)		
Intermodulation Distortion Analyzer.....	63	Jan.
Square-Wave Generator.....	68	Feb.
R.F. Probe Peps up VTVM (Frantz).....	77	May
Transistor Tester, In-Circuit (Henry).....	75	Feb.
Vary that line Voltage (EICO 1073).....	81	May

## THEORY

Bone Mending, Electronics Checks (Busse).....	46	May
Curves (Harrison).....	63	Mar.
Flip-Flop Circuits (Sienkiewicz).....	59	Mar.
Flip-Flop Computer (Sienkiewicz).....	72	Apr.
Heart, Listen to Your (Lininger).....	47	June
Hi-Fi Testing (Parts 2 and 3) (Harrison)		
Intermodulation Distortion Analyzer.....	63	Jan.
Square-Wave Generator.....	68	Feb.
Infrared (Caringella).....	41	Feb.
Laser, Introducing the (Gilmore).....	50	Feb.
Noise that Banishes Pain (Fowler).....	47	Jan.
Radar Explores the Moon (Gilmore).....	41	May
Radar Waves, Danger of (Gilmore).....	41	Mar.
Semiconductor Diode, (Kyle).....	88	May
Tuned Circuits, Explaining (Harris).....	64	May
TV Test Patterns, Interpreting (Locke).....	59	June
Zener Diode (Shaughnessy).....	76	June

## TRANSISTORS

CB Channel Spotter (Stoner).....	90	Jan.
Computer, Flip-Flop (Sienkiewicz).....	72	Apr.
Fish Caller, Electronic (Bucher).....	74	June
Flip-Flop Circuits (Sienkiewicz).....	59	Mar.
Intercom, 3-Way (Sienkiewicz).....	52	May
Metronome, Transistorized (Latner).....	54	June
Mounting Tips.....	80	May
Oscillator, Code Practice (Shmigelski).....	102	Jan.
Personal Portables, Big Sound from (Pugh).....	69	Apr.
Radiation Detector (Pugh).....	83	Jan.
Receiver, Radio-Control 11-Meter (Winter).....	81	Mar.
Tester, In-Circuit (Henry).....	75	Feb.
Transidip (Aurick).....	70	May
Transistor Saver (Lang).....	90	June
Transistor Topics (Garner).....		
80 Jan., 84 Feb., 85 Mar., 82 Apr., 102 May,	96	June

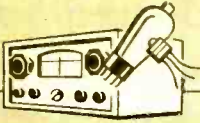

# ELECTRONICS MARKET PLACE

RATE: 60¢ per word. Minimum 10 words prepaid. August issue closes June 10th. Send order and remittance to Martin Lincoln, POPULAR ELECTRONICS, 1 Park Ave., New York 16, N. Y.

## FOR SALE

**UP To 80% Off—on Radio and TV Tubes—Largest Selection—Immediate Delivery.** Write for complete tube listing. Tube Mart Discount House, Dept. P6, Electronic Building, Paterson, N. J.

**AUTO Radio Distributor, Selling, Servicing, Becker Blaupunkt, FM-AM, other European, American Sets.** Save 30%+ Square Electronics, 150-60 Northern Blvd., Flushing, N. Y.

**CITIZENS' BAND!** Add a Hushpuppy noise suppressor to your Heathkit, Lafayette, Globe, etc. transceiver. Squeech Action! Completely Wired, Guaranteed, \$4.98. Western Mass. Electronics, Great Barrington 1, Mass.

**GOVERNMENT Sells Surplus: Electronics; Oscilloscopes; Transceivers; Test Equipment; Radar; Sonar; Walkie-Talkies; Boats; Jeeps; Aircrafts; Misc.—Send for "U.S. Depot Directory & Procedures"—\$1.00—Brody, Box 425(PE), Nanuet, New York.**

**SOMETHING for sale?** Place a classified ad in this section. Low-cost, fast results. It's easy.

**TV Tuners—Rebuilt or Exchanged \$9.95 complete—all types—fast, guaranteed service.** Send tuner with all parts to: L.A. Tuner Exchange, 4611 West Jefferson Blvd., Los Angeles 16, California.

**GOVERNMENT Surplus Receivers, Transmitters, Sniperscopes, Parabolic Reflectors, Picture Catalog 10¢.** Meshna, Malden 48, Mass.

**WPE-SWL-CB-QSL Cards — Samples 10¢ — "Brownie" W3CJ1, 3110A Lehigh, Allentown, Penna.**

**DIAGRAMS for repairing radios or television \$2.00.** Give make, model. Diagram Service, Box 672-PE, Hartford 1, Conn.

**BEFORE You Buy Receiving Tubes or Hi-Fi Components** send now for your giant Free Zalytron current catalog—featuring nationally known Zalytron First Quality TV-Radio Tubes, Hi-Fi Stereo Systems, Kits, Parts, etc. All priced to Save You Plenty—Why Pay More? Zalytron Tube Corp., 220 W. 42nd St., NYC.

**CITIZENS Band—Amateurs!** Add squelch action to your transceivers. OZCO "Snoozer" quiets beyond belief! Compact, completely wired, guaranteed. Easily installed! Only \$2.00 each, \$3.95 pair, postpaid, tax included. OZCO Sales, Canaan, Connecticut.

**NEW—16 Tested Transistor plans—25¢ with experiments, catalog.** Laboratories, 1131-L Valota, Redwood City, California.

**ELECTRONICS For The Home.** Music Systems, Radio Telephones, Telephone Dial Exchanges, Television Cameras, Radio Controlled Devices. Hundreds of Items. Equipment Catalog 50¢. Hometrronics, 8959 Wonderland Ave., Hollywood 46, Calif.

**SOUND Operated Relay—For dictating or private use—Actuate recorder only when sound is present—literature and price.** WJS Electronics, 1130 North Highland Ave., Hollywood 38, Calif.

**POLICE Radar Detector.** Stop before those radar speed traps. Fool proof, legal system. Complete diagrams and instructions \$2.75. C. Carrier Co., 5880 Hollywood Blvd., Hollywood 28, Calif.

**TELEPHONE Voice Switch (LS-500).** Actuates automatically and unattended any tape or wire recorder. Pictorial installation instructions included. \$23.75. Post paid US. WJS Electronics, 1130 N. Highland Ave., Los Angeles 38, Calif.

**BE A Spy.** Correspondence course on wire tapping, bugging, telescopic sound pickup, recording techniques, microphotography, and invisible photography. Lessons in surveillance, tailing, and use of equipment. Complete course \$22.50. C. Carrier Co., 5880 Hollywood Blvd., Hollywood 28, Calif.

**UNUSUAL Electrical Devices Wholesale.** Literature 25c. Wellico Products, Box 3055, North Hollywood, California.

**TV Camera.** Build for less than \$50. Construction Details \$4.75. DB Enterprises, 8959 Wonderland Ave., Hollywood 46, Calif.

**INVESTIGATORS!** Do your own sound word. Write for free brochure of latest electronic equipment. WJS Electronics, 1130 N. Highland Ave., Los Angeles 38, Calif.

**TELEPHONE Extension In Your Car.** Answer your home telephone by radio from your car. Complete diagrams and instructions \$2.00. C. Carrier Co., 5880 Hollywood Blvd., Hollywood 28, Calif.

**EAVESDROP** with a pack of cigarettes. Miniature transistorized FM Radio Transmitter. Complete diagrams and instructions \$2.00. C. Carrier Co., 5880 Hollywood Blvd., Hollywood 28, Calif.

**COLOR TV.** Convert your black and white TV to color. Completely Electronic. No mechanical gadgets. Costs about \$35. Complete construction details \$4.75. DB Enterprises, 8959 Wonderland Ave., Hollywood 46, Calif.

**JUNK Your Distributor and Voltage Regulator.** Improve automobile mileage and performance. Construction details for transistorized distributor and voltage regulator. \$4.75. No moving parts. DB Enterprises, 8959 Wonderland Ave., Hollywood 46, Calif.

**GOVERNMENT Surplus, Radios, Jeeps, Walkie-Talkies, Boats, Binoculars, Telescopes, Etc.—Send For "Depot Locations & Procedures"—25¢—Delta, Box 2262, Dallas 21, Texas.**

**EXTENSION Dial Telephone For Ham Shack, Den, Patio, Garage, Basement, Etc.; Simple to Hook Up Anywhere.** Instructions For Hookup included. \$14.95—Telephone Handset Only, \$5.95—Misc. Telephone Equipment, All Kinds, Price List 25¢—Delta Electronics, Box 2262, Dallas 21, Texas.

**TINY Radio. No Tubes—Batteries or Transistors.** Works forever. Send stamp for catalogue. Midway Radio, Dept. 6E, Kearney, Nebr.

**WORLDWIDE All-Wave Low-Cost Portable Radio.** Send stamp for catalogue. Western Radio, Dept. 6E, Kearney, Nebr.

**TALK from House to Car or to any Radio with Walkie Talkie.** Send stamp for catalogue. Western Radio, Dept. 6E, Kearney, Nebr.

**WORLD'S Tiniest Transistor Radio—Many others.** Send stamp for catalogue. Western Radio, Dept. 6E, Kearney, Nebr.

**TALK to others—Miles Away with Low-Cost Radiophone—No license.** Send stamp for circular. Western Radio, Dept. 6E, Kearney, Nebr.

**HEAR Russia—Europe—the Whole World! Short-Wave Adapter works on any radio—no hookups.** Send stamp for catalogue. Western Radio, Dept. 6E, Kearney, Nebr.

**AUTOMATIC Time Switch, extension cord and three-way outlet.** Beautiful cream finish. 6 foot cord, 0.4 hour time cycle. Rated 10 amps 125V A.C. Satisfaction guaranteed. \$5.25 post paid. F. W. McKinnon, Dept. A4, 200 North Perry Street, Hagerstown, Indiana.

**ELECTRONICS Research Surplus** from leading midwest manufacturer. 2 1/2 lbs.—\$3.00. Palan Associates, 851-17th St. S.W., Cedar Rapids, Ia.

**TUNNEL Diode Circuit Manual, 20 Practical tested circuits, theory, specifications, illustrations, test equipment \$1.00 ppd.** Steelman Electronics, 1040 S. Worth St., Indianapolis 41, Ind.

**CITIZENS' Band, Diagrams and Information.** Double transmitter efficiency and double your coverage with three stage RF lineup. Get rid of TVI headaches. Simplified method audio checking. Increase vibrator B+ supply 6 or 12 volt. Improve beam or ground antenna. Ignition noise problems. Mobile or home converter. Mobile field strength meter. Plus additional information. \$1.00 C.B. Improvement Co., 70 Hill St., Bloomfield, N. J.

**BARGAINS—Electronic Components—Books—Free list—ST Labs., 438 Third Ave., Newark 7, N. J.**

**CITIZEN-Banders!** Build your own 11 meter antenna at a fraction of the cost of many high priced antennas. Non-directional, easy to build. For complete instructions and diagrams send \$1.25 to Sherman Steel, 1468 Ducey Ave., Muskegon, Michigan.



**CANADIANS**—Tubes Wholesale—Write T.T.M., Box 91, Don Mills, Ont.

**CITIZENS' Band**—HE-15 & 15A owners, hear only the channel you tune. Dual conversion adapter available now in kit form. Complete parts, schematic and instructions, \$14.95, with tubes, \$16.95. \$5.00 deposit for C.O.D. Available soon for other sets. Free literature. Bainbridge Radio, 2649 Bainbridge Ave., New York 58, N. Y.

**SPECIAL WPE**—SWL—CB—QSL cards, 3 colors, \$2.50 per 100—Free samples—Garth, Jutland, New Jersey.

**CBERS'**—Special 5 minute sand type timers.  $\pm$  15 sec. accuracy. Full 3 1/2" high, red and white trim. 89¢ including postage. No C.O.D. or stamps please. F & S Electronic Service, 200 Maple Avenue, Graterford, Pa.

**FREE Confidential Bargain Sheets Of Electronic Components**—Lowest Prices in The Country—Knapp, 3174 8th Ave. S.W., Largo, Florida.

**CB**—WPE. Send Your Call and \$1.00 for Three giant 11"x7" Call Signs. New! Cbers Business Cards, Samples Free. P.O. Box 933Q, Aurora, Ill.

## WANTED

**QUICKSILVER**, Platinum, Silver, Gold, Ores Analyzed. Free Circular. Mercury Terminal, Norwood, Massachusetts.

**WANT** to buy good equipment and accessories? Place a low-cost classified ad in this space. For information, write: Martin Lincoln, Popular Electronics, One Park Avenue, New York 16, N. Y.

**WANTED** Circulated Indian Cents, Liberty V-Nickels and Buffalo Nickels Before 1936. 10¢ each in Large Quantities No Mutilated Coins Send To John J. Firpo, 2107 Van Ness, San Francisco 10, California.

**TRIGGER**—W91VJ. We Buy Shortwave Equipment For Cash. 7361 W. North, River Forest, Ill., Phone PR 1-8616. Chicago TU 9-6429.

## HIGH-FIDELITY



**DISGUSTED** with "Hi" Hi-Fi Prices? Unusual discounts on your High Fidelity Requirements. Write Key Electronics, 120 Liberty St., New York 6, N. Y. Cloverdale 8-4288.

**DON'T** Buy Hi-Fi Components. Kits. Tape, Tape Recorders until you get our low, low return mail quotes: "We Guarantee Not To Be Undersold." Wholesale Catalog Free. Hi-Fidelity Center, 220 PC-E.23 St., New York 10, N. Y.

**PRICES?** The Best! Factory-Sealed Hi-Fi Components? Yes! Send for free catalog. Audion, 25P Oxford Road, Massapequa, N. Y.

**RECORDERS**, Components. Free wholesale catalogue. Carston, 125-P East 88, N. Y. C. 28.

**PROMPT** Delivery, We Will Not Be Undersold. Amplifiers, Tape Recorders, Tuners, Etc. No Catalogs, Air Mail Quotes. Compare. L. M. Brown Sales Corp. Dept. P, 239 E. 24 St., N.Y. 10, N.Y.

**SOUNDTASTIC!** That's what our customers are saying upon receiving our prices on our latest High Fidelity Stereo and Monaural, Amplifiers, tuners, turntables, speakers, tape recorders, kits. All brand new with factory guarantee. Individual quotations only. No catalogues. Audio World, 2057 Coney Island Avenue, Brooklyn 23, New York. Dept. HR.

**OVER** 400,000 buyers and sellers will read your ad when placed in this space. It costs only 60¢ per word; minimum of 10 words including your name and address. Send order and remittance to: Martin Lincoln, Popular Electronics, One Park Avenue, New York 16, N. Y.

## TAPE & RECORDERS

**AMPEX**, Bozak, Citation, Concertone, Crown, Magnecord, Presto, Norelco, Tandberg, Sherwood, Thorans, Scott, Shure, others . . . Trades, Boynton Studio, Dept. PE, 10 Pennsylvania Ave., Tuckahoe, N. Y.

**Tape Recorders**, Hi-Fi, components, Sleep Learning Equipment, tapes, Unusual Values. Free Catalog, Dressner, 1523PE, Jericho Turnpike, New Hyde Park, N. Y.


**SOMETHING** for sale? Place a classified ad in this section. Low-cost, fast results. It's easy.

**RENT** Stereo Tapes—over 2,000 different—all major labels—free catalog. Stereo—Parti, 811-G Centinela Ave., Inglewood 3, California.

**WRITE** Martin Lincoln, Popular Electronics, One Park Avenue, New York 16, N. Y. for information on how to place a classified ad in this section.

**BUILD** This Stereo Hi-Fi Magnetic Tape Playback, Equivalent in Essentials to \$1000. Instrument. Complete Plans and Instructions Available. Send 10¢ For Description and Specifications. Merlyn Company (PE-7) Box 3053-A, Pasadena, Calif.

## INSTRUCTION

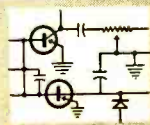

**SPECIAL** Home Study course; end unemployment worries; prepare for FCC exams. TV servicing. Citizens Radio; Increase your income; 60 lessons. \$5 down, \$5 month. Experimental Kits. Write for Free booklet and sample lesson. Florida Technical Schools, Box 8145A, Jacksonville 11, Fla.

**ENGINEERING** Education for the Space Age. Northrop Institute of Technology is a privately endowed, nonprofit college of engineering offering a complete Bachelor of Science Degree Program and Two-Year accredited technical institute curricula. Students from 50 states, many foreign countries. Outstandingly successful graduates employed in aeronautics, electronics, and space technology. Write today for catalog—no obligation. Northrop Institute of Technology, 1179 West Arbor Vitae Street, Inglewood 1, California.

**EXPERIMENT** with nature's electronics. Instructions—Stillwater, Box 337E, Morris Plains, New Jersey.

**PHOTOGRAPHY** For Pleasure or profit. Learn at home. Practical basic training. Long established school. Free booklet. American School of Photography, 835 Diversey Parkway, Dept. 253A, Chicago 14, Illinois.

**TECHNICAL** Writers earn \$6500 to \$18,000 annually. For job details and sample lesson, write DIAL, Box 245, North Syracuse, New York. Enclose \$2.00 and brief history of education and work experience. Free Job Counseling.

**EARN** \$150 Week as Electronics Draftsman. Send \$2 first lesson, or \$25 complete home study course. Prior, Inc., Dept. 12, 23-09 169 Street, Whitestone 57, New York.

## REPAIRS and SERVICING

**LET** us wire and test any kit for you. Naczas Kit Service, 18 Wolfe Street, Manchester, New Hampshire.

**WRITE** Martin Lincoln, Popular Electronics, One Park Avenue, New York 16, N. Y. for information on how to place a classified ad in this section.

**KITS** professionally wired. Write Easton, 521 Alden Road, Muncie, Indiana.

## INVENTIONS WANTED

**INVENTIONS** Wanted for immediate promotion! Patented, unpatented. Outright cash; royalties! Casco, Dept. BB, Mills Building, Washington 6, D.C.

**INVENTIONS** wanted. Patented; unpatented. Global Marketing Service, 2420-P 77th. Oakland 5, Calif.

**WRITE** Martin Lincoln, Popular Electronics, One Park Avenue, New York 16, N. Y. for information on how to place a classified ad in this section.

## BUSINESS OPPORTUNITIES

**I WANT A MAN** who wants a business of his own. I will train you, supply the equipment, help finance you, start you rolling. This is not a risky get-rich-quick scheme. It is a legitimate business, exclusive protected franchise, proved successful by hundreds throughout the country. Send name, address and phone number to Marion Wade, 2117 North Wayne, Dept. 47M, Chicago 14, Illinois.

**WRITE** Martin Lincoln, Popular Electronics, One Park Avenue, New York 16, N. Y. for information on how to place a classified ad in this section.



## SHOPPING GUIDE Classified

A HANDY REFERENCE TO PRODUCTS AND SERVICES NOT NECESSARILY ELECTRONIC, BUT OF WIDE GENERAL INTEREST

### PHOTOGRAPHY—FILM EQUIPMENT, SERVICES

**OPTICAL** Science-Math Bargains—Request Free Giant catalog "CJ"—144 pages—Astronomical Telescopes, Microscopes, Lenses, Binoculars, Kits, Parts, Amazing war surplus bargains. Edmund Scientific Co., Barrington, New Jersey.

**FREE!** New 1961 catalog of all photographic books available. For your copy, send postcard with name and address to Catalog Popular Photography Book Service, One Park Ave., New York 16, N. Y.

### STAMPS & COINS

**105** Different U.S. stamps 25¢. Approvals included. Shelron, Box 907-H, New York 8, N. Y.

**1960** United Nations commemorative stamps, all mint 4c and 8c commemorative sets only one dollar with request for approvals. Adults Only, Martin Stamp Co., Box 12-A, Gravesend Sta., Brooklyn 23, New York.

**SELLING** entire personal stamp collection. All foreign. Good condition. Assorted packets of 50—25¢ and self-addressed, stamped envelope. Popular Electronics, Box 107, One Park Avenue, New York 16, New York.

**WANTED** Circulated Indian Cents. Liberty V-Nickels And Buffalo Nickels Before 1936. 10¢ each in Large Quantities. No Mutilated Coins. Send To John J. Firpo, 2107 Van Ness, San Francisco 9, California.

## EDUCATIONAL OPPORTUNITIES

**DETECTIVE** Profession. Home Study. Badge, Certificate, Future 4563-AG York, Los Angeles 41, Calif.

**UNVEILED**—Mysteries of Electronics. Amaze your electronics associates by learning seldom understood electronics circuits and theory. Subjects easily mastered without complex math. For complete 40 page booklet mail \$1.00 to Comprehensive Electronics Publications, Box 203, Riverton, New Jersey.

## BOOKS

**BOOKS**—All 10¢. 2000 titles, all subjects, catalog free. Cosma, Clayton, Ga.

## SCHOOLS

**ELECTRONICS** By Sleep Teaching. \$12.00 per lesson. The thorough way to train. Tape recorder included at no extra cost. Catalog 25¢. Electro-Sleep, 8959 Wonderland Ave., Hollywood 46, Calif.

## LEATHERCRAFT

**FREE** "Do-It-Yourself" Leathercraft Catalog. Tandy Leather Company, Box 791-H-39, Fort Worth, Texas.

## PLASTICS

**NEW** Liquid Casting Plastic, clear, colors. Embed real flowers, butterflies, photos, coins. Send 25¢ for two handbooks "How to Cast Liquid Plastics" and "How to Make Extra Money at Home." Castolite, Dept. G-108, Woodstock, Illinois.

## EMPLOYMENT INFORMATION

**HIGH** Paying Jobs in Foreign Lands! Send \$2.00 for complete scoop! Foreign Opportunities, Box 172, Columbus 16, Ohio.

**EARN** Extra money selling advertising book matches. Free samples furnished. Matchcorp, Dept. MD 61, Chicago 32, Illinois.

## BUSINESS OPPORTUNITIES

**BUY** Direct from factories. Appliances, cameras, watches! Free details! Cam Co., 6810PE 20th Ave., Brooklyn 4, N. Y.

**VENDING** Machines—No Selling. Operate a route of coin machines and earn amazing profits. 32-page catalog free. Parkway Machine Corporation, Dept. 12, 715 Ensor St., Baltimore 2, Md.

**FREE** Book "990 Successful, Little-Known Businesses." Work home! Plymouth-455R, Brooklyn 4, New York.

**GROW** Mushrooms. Cellar, shed and outdoors. Spare, full time, year round. We pay \$4.50 lb. dried. We have 29,000 customers. Free Book. Mushrooms, Dept. 334, 2954 Admiral Way, Seattle, Wash.

**MAKE** \$25-\$50 Week, clipping newspaper items for publishers. Some clippings worth \$5.00 each. Particulars free. National, 81-DG, Knickerbocker Station, New York.

**SOMEONE** "borrowing" your personal copy of Popular Electronics each month? You ought to be taking advantage of Popular Electronics' convenient re-sale plan. Sell copies in your store . . . perform a good service for your customers . . . with no risk involved. For details, write: Direct Sales Department, Popular Electronics, One Park Avenue, New York 16, New York.

**FRANCHISE** Yourself with a reputable franchising firm, after surveying the full range of franchise offers published by N.F.R., the only recognized source. Write now for free "Franchise Profit Letter." National Franchise Reports, Dept. PE-528, 333 N. Michigan, Chicago 1, Ill.

**A Second Income From Oil Can End Your Toil!** Free Book And Oilfield Maps! National Petroleum, Panamerican Bank Bldg.—PE, Miami, Florida.

## MISCELLANEOUS

**WRITERS!** Request Free sample Pink Sheets listing markets USA. Literary Agent Mead, 915 Broadway, N. Y.

**"WINEMAKING," "Beer, Ale"** Strongest methods. Illustrated. \$2.20. Eaton Bookstore (Supplies), Box 1242-C, Santa Rosa, California.

**SENSATIONAL** Electric Wristwatch available under \$100. Other bargains. Catalog free. Long's, Box 7943, Portland 12, Oregon.

**TWO** Legal "Will" Forms, Instructions Booklet, \$1.00. National, Box 48313PE, Los Angeles 48, Calif.

**UNDERPAID?** Technical Writers Earn \$240.00 Up Week. Easy Condensed course. \$2.00 Tweco, P.O. Box 155, Indio, Calif.

## POPULAR ELECTRONICS

### Advertisers' Index

JUNE 1961

ADVERTISER	PAGE NO.	ADVERTISER	PAGE NO.
A.E.S. Inc.	21	Lafayette Radio	23
Airex Radio Corporation	24	Lektron	111
Allied Radio	31, 106	Micro Electron Tube Co.	114
American Institute Of Engineering & Technology	122	Milwaukee School of Engineering	107
Antenna Specialists Co.	106	Mosley Electronics, Inc.	123
Audio Devices, Inc.	17	Moss Electronic, Inc.	3rd, 4th COVER
Bailey Technical Schools	22	National Radio Institute	33, 34
Browning	113	National Technical Schools	9
Bud Radio, Inc.	112	North American Philips Co., Inc.	10
Burstein-Applebee Co.	32	Paco Electronics Company, Inc.	3
Cadre Industries Corp.	2nd COVER	Palmer, Joe	121
Capitol Radio Engineering Institute	25	Picture Tube Outlet	22
Cleveland Institute of Electronics	15	Port Arthur College	121
Coyne Electrical School	26	Progressive "Edu-Kits" Inc.	27
DeVry Technical Institute	5	RCA Institutes, Inc.	18, 19
EICO	40	Rad-Tel Tube Co.	130
Electronic Market	123	Radio Corporation of America	29, 105
Electronics Book Service	38, 39	Radio-Television Training School	11
General Electric Company	1	Radiocom	26
General Radiotelephone Company	14	Rider Publisher Inc., John F.	16
Globe Electronics	121	Schober Organ Corp., The	115
Grantham School of Electronics	7	Spartan School of Electronics	30
Grove Electronic Supply Company	28	Tech-Serv., Inc.	113
Heath Company	102, 103	Texas Crystals	116
Holt, Rinehart and Winston, Inc.	36	Transvision	101
Hy-gain Antenna Products	20	Tri-State College	114
Indiana Technical College	122	Tru-Vac	119
International Crystal Manufacturing Co., Inc.	12, 13	United Scientific Laboratories, Inc.	24
Johnson Company, E. F.	117	University Loudspeakers, Inc.	112
Key Electronics	122	Valparaiso Technical Institute	114
Kuhn Electronics, Inc.	28	Vanguard Electric Labs	32
		Xcelite, Inc.	116

# NOW! FAST ONE DAY SERVICE BRAND NEW RADIO & TV TUBES

## RAD-TEL'S FIRST QUALITY TUBES SAVE up to 75% ONE FULL YEAR GUARANTEE



### SERVICEMEN:

BUY DIRECT FROM RAD-TEL! YOU'LL SAVE PLENTY. YOUR ORDER SHIPPED WITHIN 24 HOURS AFTER RECEIVING AND PROCESSING. RAD-TEL SELLS ONLY BRAND NEW TUBES, NOT USED.

### 1st TIME OFFERED

NOW! RAD-TEL'S "SET TESTED" TRANSISTORS ... AT FABULOUS LOW PRICES

A Rad-Tel "general purpose transistor" for each class. Similar to 100's specified in many projects. All transistors are grouped into 4 general classes:

THE SIGN OF  
RAD-TEL'S  
RELIABILITY

LOW POWER AF TYPE  
DRIVER AND OUTPUT




39¢ ea.

LOW POWER RF  
MIXER AND IF



49¢ ea.

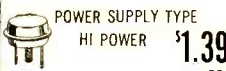HI POWER AF UNITS  
79¢ CAR RADIO TYPE  
POWER OUTPUT



\$1.39 ea.

SPECIAL PURPOSE

TETRODES, ETC.  
(Not available at this time)

YOU CAN SUBSTITUTE AND replace with Rad-Tel transistors when working with transistor projects. Transistor substitutions are based on "similar operating characteristics." All Rad-Tel transistors have expensive features, broad tolerances and are tested in AM radio, as radio frequency converter at 1.5 KC and 450 KC intermediate frequency, AF as audio frequency driver. You're safe building numerous projects when you use Rad-Tel's "set tested" transistors. Each Rad-Tel Transistor is fully tested and guaranteed to give sound operating performance without confusing you with COMPLICATED NUMBERS AND CHARACTERISTICS. Here are just a few suggested transistor projects:

Solar Powered Radio, Shirt Pocket Radio, Carrier Power Receiver, Sine, Square-Wave Generator, Transistor Preamplifier for VTVM, Regulated Power Supply, Meter Sensitivity Multiplier, Oscillator Audio & RF Electronic Counters.  
(Please note: Most projects, including diagrams, are appearing in current magazines. We don't have diagrams.)

59¢ ea.  
LOTS OF 5  
RAD-TEL'S  
SELECTED  
KITS  
UNBELIEVABLY  
LOW PRICED!  
WHILE THEY  
LAST!  
79¢ ea.

- 50 ASST'D TIE LUGS, NO. 1
- 10 ASST'D F.P. CONDENSERS, NO. 6
- 50 ASST'D RADIO KNORNS, NO. 8
- 15 ASST'D TV COILS, NO. 13
- 20 ASST'D MOLDING SOCKETS, NO. 5
- 50 ASST'D BRACKETS & HARDWARE, NO. 17
- 15 SETS ASST'D CONNECTORS, NO. 15
- 10 ASST'D T.V. SLUG TUNED COILS, NO. 25
- 10 ASST'D VOLUME CONTROLS, LG & SH SHAFT, NO. 2
- 8 ASST'D TV CONTROLS, SHORT SHAFT, NO. 21
- 8 ASST'D VOLUME CONTROLS, LONG SHAFT, NO. 22
- 10 ASST'D SWITCHES, DOUBLES, LONG & SHORT SHAFT, NO. 23
- 10 ASST'D T.V. PEAKING COILS, NO. 24
- 25 ASST'D TRIMMERS, NO. 7
- 10 ASST'D TUBE SHIELDS, NO. 26
- 1 LB. PROX. NUTS & BOLTS, NO. 20
- 4 ASST'D SOUND COILS, NO. 18
- 20 ASST'D HI-WATT RESISTORS, NO. 9
- 7 ASST'D HORIZONTAL COILS, NO. 19
- 15 ASST'D BINDING POST TERMINALS, NO. 16

RAD-TEL TUBE CO. NOT  
AFFILIATED WITH ANY  
OTHER MAIL ORDER  
TUBE COMPANY



SEND FOR FREE TROUBLE SHOOTER  
GUIDE AND NEW TUBE & PARTS CATALOG

# RAD-TEL TUBE CO.

DEPT. PE-661 55 CHAMBERS STREET, NEWARK 5, N. J.

TERMS: 25% deposit must accompany all orders, balance C.O.D. Orders under \$5: add \$1 handling charge plus postage. Orders over \$5: plus postage. Approx. 8 tubes per 1 lb. Subject to prior sale. Prices subject to change. No C.O.D.'s outside continental USA.

Qty.	Type	Price	Qty.	Type	Price	Qty.	Type	Price
	024M	.79		6AX7	.64		12AF6	.49
	1AX2	.62		6BA6	.50		12AJ6	.46
	1B3GT	.79		6BC5	.61		12AL5	.45
	1DN5	.55		6BC7	.94		12AL8	.95
	1G3	.79		6BC8	.97		12A05	.52
	1J3	.79		6BD6	.51		12AT6	.43
	1K3	.79		6BE6	.55		12AT7	.76
	1LN5	.59		6BF6	.44		12AU6	.50
	1R5	.62		6BG6	1.66		12A07	.61
	1S5	.51		6BH6	.65		12AV5	.97
	1T4	.58		6BH8	.67		12AV6	.41
	1U4	.57		6BJ6	.82		12AV7	.75
	1U5	.50		6BK7	.85		12AX4	.67
	1X2B	.82		6BL7	1.00		12AX7	.63
	2AF4	.96		6BN4	.54		12AZ7	.86
	3AL5	.42		6BN6	.74		12B4	.63
	3AU6	.51		6B05	.65		12BA6	.50
	3AV6	.41		6BQ6GT	1.05		12BD6	.50
	3BA6	.51		6B07	1.00		12BE6	.53
	3BC5	.54		6BR8	.78		12BF6	.44
	3BE6	.52		6B08	.70		12BH7	.77
	3BN6	.76		6BY6	.54		12BL6	.56
	3BU8	.78		6BZ6	.55		12BQ6	1.06
	3BY6	.55		6BZ7	1.01		12BY7	.77
	3BZ6	.55		6C4	.43		12BZ7	.75
	3CB6	.54		6CB6	.55		12C5	.56
	3CF6	.60		6CD6	1.42		12CN5	.56
	3CG6	.52		6CF6	.64		12CR6	.54
	3DK6	.60		6CG7	.61		12CUS	.58
	3DT6	.50		6CG8	.77		12CUB	1.06
	3Q5	.80		6CM7	.66		12CX6	.54
	3S4	.61		6CN7	.65		12DB5	.69
	3V4	.58		6CR6	.51		12DE8	.75
	4BC8	.96		6CS6	.57		12DL8	.85
<b>EACH TUBE INDIVIDUALLY &amp; ATTRACTIVELY BOXED</b>								
	4BN6	.75		6CU5	.58		12DM7	.67
	4B07	1.01		6CU6	1.08		12DQ6	1.04
	4BS8	.98		6CY7	.71		12DS7	.79
	4BU8	.71		6DA4	.68		12DZ6	.56
	4BZ6	.58		6DB5	.69		12EL6	.50
	4BZ7	.96		6DE6	.58		12EG6	.54
	4CS6	.61		6DG6	.59		12E26	.53
	4DE6	.62		6DQ6	1.10		12F8	.66
	4DK6	.60		6DT5	.76		12FM6	.45
	4DT6	.55		6DT6	.53		12K5	.65
	5AM8	.79		6EU8	.79		12SA7M	.92
	5AN8	.86		6EA8	.79		12SK7GT	.74
	5A05	.52		6HG6T	.58		12SN7	.67
	5AT8	.80		6IS6T	.51		12SQ7M	.78
	5BK7A	.82		6I6	.67		12U7	.62
	5B07	.97		6K6	.63		12V6GT	.53
	5BR8	.79		6S4	.51		12W6	.69
	5CG8	.76		6SA7GT	.76		12X4	.38
	5CL8	.76		6SK7	.74		17AX4	.67
	5EA8	.80		6SL7	.80		17BQ6	1.09
	5EU8	.80		6SN7	.65		17C5	.58
	5I6	.68		6SQ7	.73		17CA5	.62
	5T8	.81		6T4	.99		17D4	.69
	5U4	.60		6U8	.83		17DQ6	1.06
	5U8	.81		6V6GT	.54		17L6	.58
	5V6	.56		6W4	.60		17W6	.70
	5X8	.78		6W6	.71		19AU4	.83
	5Y3	.46		6X4	.39		19BQ6	1.39
	6AB4	.46		6X5GT	.53		19T8	.80
	6AC7	.96		6X8	.80		21EX6	1.49
	6AF3	.73		7AU7	.61		25BQ6	1.11
	6AF4	.97		7A8	.68		25C5	.53
	6AG5	.68		7B6	.69		25CA5	.59
	6AH6	.99		7Y4	.69		25CD6	1.44
	6AK5	.95		8AU8	.83		25CU6	1.11
	6AL5	.47		8AW8	.93		25DN6	1.42
	6AM8	.78		8BQ5	.60		25EH5	.55
	6AQ5	.53		8CG7	.62		25L6	.57
	6AR5	.55		8CM7	.68		25W4	.68
	6AS5	.60		8CN7	.97		25Z6	.66
	6AT6	.43		8CX8	.93		35C5	.51
	6AT8	.79		8EB8	.94		35L6	.57
	6AU4	.82		11CY7	.75		35W4	.42
	6AU6	.52		12A4	.60		35Z5GT	.60
	6AU7	.61		12AB5	.55		50B5	.60
	6AU8	.87		12AC6	.49		50C5	.53
	6AV6	.41		12AD6	.57		50DC4	.37
	6AW8	.90		12AE6	.43		50EH5	.55
	6AX4	.66		12AF3	.73		50L6	.61
							117Z3	.61

# SHIPPED ON APPROVAL NO MONEY WITH ORDER - NO C.O.D.

Superior's  
New Model  
TW-11

## STANDARD PROFESSIONAL TUBE TESTER



Model TW-11—Tube Tester  
Total Price \$47.50  
Terms: \$11.50 after 10 day trial, then \$6.00 monthly for 6 months if satisfactory. Otherwise return, no explanation necessary.

- Tests all tubes, including 4, 5, 6, 7, Octal, Lockin, Hearing Aid, Thyatron, Miniatures, Sub-miniatures, Novals, Subminars, Proximity Fuse Types, etc.
- Uses the new self-cleaning Lever Action Switches for individual element testing. All elements are numbered according to pin-number in the RMA base numbering system. Model TW-11 does not use combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket.
- Free-moving built-in roll chart provides complete data for all tubes. Printed in large easy-to-read type.

**NOISE TEST:** Phono-jack on front panel for plugging in either phones or external amplifier detects microphonic tubes or noise due to faulty elements and loose internal connections.

**EXTRAORDINARY FEATURE**  
**SEPARATE SCALE FOR LOW-CURRENT TUBES** Previously, an emission-type tube testers, it has been standard practice to use one scale for all tubes. As a result, the calibration for low-current types has been restricted to a small portion of the scale. The extra scale used here greatly simplifies testing of low-current types.  
Housed in handsome, Saddle-Stitched Texon case. Only **\$47.50**



Model 77—VACUUM TUBE VOLTMETER—Total Price \$42.50  
Terms: \$12.50 after 10 day trial, then \$6.00 monthly for 5 months if satisfactory. Otherwise return, no explanation necessary.

Superior's  
New  
Model 77

## VACUUM TUBE VOLTMETER WITH NEW 6" FULL-VIEW METER

Compare it to any peak-to-peak V. T. V. M. made by any other manufacturer at any price!

- Extra large meter scale enables us to print all calibrations in large easy-to-read type.
  - Employs a 12AU7 as D. C. amplifier and two 9006's as peak-to-peak voltage rectifiers to assure maximum stability. • Meter is virtually burn-out proof. The sensitive 400
- AS A DC VOLTMETER:** The Model 77 is indispensable in Hi-Fi Amplifier servicing and a must for Black and White and color TV Receiver servicing where circuit loading cannot be tolerated.
- AS AN ELECTRONIC OHMMETER:** Because of its wide range of measurement leaky capacitors show up glaringly. Because of its sensitivity and low loading, Intermittents are easily found, isolated and repaired.
- AS AN AC VOLTMETER:** Measures RMS values if sine wave, and peak-to-peak value if complex wave. Pedestal voltages that determine the "black" level in TV receivers are easily read.

micro-ampere meter is isolated from the measuring circuit by a balanced push-pull amplifier. • Uses selected 1% zero temperature coefficient resistors as multipliers. This assures unchanging accurate readings on all ranges.

### SPECIFICATIONS

- DC VOLTS—0 to 315/75/150/300/750/1,500 volts at 11 megohms input resistance.
- AC VOLTS (RMS)—0 to 315/75/150/300/750/1,500 volts. • AC VOLTS (Peak to Peak)—0 to 8/40/200/400/800/2,000 volts.
- ELECTRONIC OHMMETER—0 to 1,000 ohms/10,000 ohms/100,000 ohms/1 megohms/10 megohms/100 megohms/1,000 megohms.
- DECIBELS: -10 db to +18 db, -10 db to +38 db, -30 db to +58 db. All based on 0 db = 006 watts (6 mw) into a 500 ohm line (1.73v).
- ZERO CENTER METER—For discriminator alignment with full scale range of 0 to 1.5/7.5/37.5/75/150/375/750 volts at 11 megohms input resistance.

Comes complete with operating instructions, probe leads, and streamlined carrying case. Operates on 110-120 volt 60 cycle. Only **\$42.50**

We invite you to try before you buy any of the models described on this page and the following page. If after a 10 day trial you are completely satisfied and decide to keep the Tester, you need send us only the down payment and agree to pay the balance due at the monthly indicated rate.

### NO INTEREST OR FINANCE CHARGES ADDED!

If not completely satisfied, you are privileged to return the Tester to us, cancelling any further obligation.

## SEE OTHER SIDE

CUT OUT AND MAIL TODAY! ▶

MOSS ELECTRONIC, INC.  
Dept. D-881 3849 Tenth Ave., New York 34, N. Y.

Please send me the units checked on approval. If completely satisfied I will pay on the terms specified with no interest or finance charges added. Otherwise, I will return after a 10 day trial positively cancelling all further obligation.

Model 77 Total Price \$42.50  
\$12.50 within 10 days. Balance  
\$6.00 monthly for 5 months.

Model TV-50A Total Price \$47.50  
\$11.50 within 10 days. Balance  
\$6.00 monthly for 6 months.

Model TW-11 Total Price \$47.50  
\$11.50 within 10 days. Balance \$6.00  
monthly for 6 months.

Model 70... Total Price \$15.85  
\$3.85 within 10 days. Balance  
\$4.00 monthly for 3 months.

Name .....

Address .....

City ..... Zone ..... State .....

All prices net, F.O.B., N. Y. C.

# SHIPPED ON APPROVAL NO MONEY WITH ORDER — NO C.O.D.

Superior's New Model 70 UTILITY TESTER®

## FOR REPAIRING ALL ELECTRICAL APPLIANCES and AUTOMOBILE CIRCUITS



Model 70—UTILITY TESTER  
Total Price...\$15.85—

Terms: \$3.85 after 10 day trial, then \$4.00 monthly for 3 months, if satisfactory. Otherwise return, no explanation necessary.

### As an electrical trouble shooter the Model 70:

- Will test Toasters, Irons, Broilers, Heating Pads, Clocks, Fans, Vacuum Cleaners, Refrigerators, Lamps, Fluorescents, Switches, Thermostats, etc.
- Measures A.C. and D.C. Voltages, A.C. and D.C. Current, Resistances, Leakages, etc.
- Will measure current consumption while the appliance under test is in operation.
- Incorporates a sensitive direct-reading resistance range which will measure all resistances commonly used in electrical appliances, motors, etc.
- Leakage detecting circuit will indicate continually from zero ohms to 5 megohms (5,000,000 ohms).

### As an Automotive Tester the Model 70 will test:

- Both 6 Volt and 12 Volt Storage Batteries • Generators • Starters • Distributors • Ignition Coils • Regulators • Relays • Circuit Breakers • Cigarette Lighters • Stop Lights • Condensers • Directional Signal Systems • All Lamps and Bulbs • Fuses • Heating Systems • Horns • Also will locate poor grounds, breaks in wiring, poor connections, etc.



**INCLUDED FREE** This 64-page book—practically a condensed course in electricity. Learn by doing.

Just read the following partial list of contents: What is electricity? • Simplified version of Ohms Law • What is wattage? • Simplified wattage charts • How to measure voltage, current, resistance and leakage • How to test all electrical appliances and motors using a simplified trouble-shooting technique. • How to trace trouble in the electrical circuits and parts in automobiles and trucks.

Model 70 comes complete with 64 page book and test leads

**\$15<sup>85</sup>**  
Only

Superior's New Model TV-50A **GENOMETER**

## 7 Signal Generators in One!

- ✓ R.F. Signal Generator for A.M.
- ✓ R.F. Signal Generator for F.M.
- ✓ Audio Frequency Generator
- ✓ Marker Generator
- ✓ Bar Generator
- ✓ Color Dot Pattern Generator
- ✓ Cross Hatch Generator

This Versatile All-Inclusive GENERATOR Provides ALL the Outputs for Servicing:

- A.M. RADIO • F.M. RADIO • AMPLIFIERS • BLACK AND WHITE TV • COLOR TV

**R. F. SIGNAL GENERATOR:** 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 180 Megacycles on powerful harmonics.

**VARIABLE AUDIO FREQUENCY GENERATOR:** Provides a variable 300 cycle to 20,000 cycle peaked wave audio signal.

**MARKER GENERATOR:** The following markers are provided: 189 Kc., 262.5 Kc., 456 Kc., 600 Kc., 1000 Kc., 1400 Kc., 1600 Kc., 2000 Kc., 2500 Kc., 3579 Kc., 4.5 Mc., 5 Mc., 10.7 Mc., (3579 Kc. is the color burst frequency)

**BAR GENERATOR:** Pattern consists of 4 to 16 horizontal bars or 7 to 20 vertical bars.

**DOT PATTERN GENERATOR (FOR COLOR TV):** The Dot Pattern projected on any color TV Receiver tube by the Model TV-50A will enable you to adjust for proper color convergence.

**CROSS HATCH GENERATOR:** The pattern consists of non-shifting horizontal and vertical lines interlaced to provide a stable cross-hatch effect.

Complete with shielded leads **\$47<sup>50</sup>** Net



Model TV50-A—Genometer  
Total Price \$47.50

Terms: \$11.50 after 10 day trial, then \$6.00 monthly for 6 months if satisfactory. Otherwise return, no explanation necessary.

## TRY FOR 10 DAYS **BEFORE** you buy! **THEN** if satisfactory

pay in easy, interest free, monthly payments. See coupon inside.

We invite you to try before you buy any of the models described on this and the preceding page. If after a 10 day trial you are completely satisfied and decide to keep the Tester, you need send us only the down payment and agree to pay the balance due at the monthly indicated rate. (See other side for time payment schedule details.)

**NO INTEREST  
OR FINANCE  
CHARGES ADDED!**

If not completely satisfied, you are privileged to return the Tester to us, cancelling any further obligation.

**SEE OTHER  
SIDE**

CUT OUT AND MAIL TODAY!

FIRST CLASS

Permit No. 61430

New York, N. Y.

VIA AIR MAIL

BUSINESS REPLY CARD

No Postage Stamp Necessary if Mailed in the U. S.

POSTAGE WILL BE PAID BY —

MOSS ELECTRONIC, INC.

3849 TENTH AVENUE

NEW YORK 34, N. Y.