

BUILD NUCLEAR RADIATION RATEMETER

POPULAR ELECTRONICS

**NOVEMBER
1961**

**35
CENTS**

- ★ **All About Electroluminescence**
- ★ **Make Radio Double As Intercom**

Plans For:

- **Squelch For CB-1 Superregen**
- **Stereo Earphones**
- **AG-1 Slave Flash Gun**
- **Lab-Style Power Supply**



CB GOES ON TV

Roger Smith



EIGHTHOUSAND TWO HUNDRED
 FORTY TWO
 AM H. OELSCHLAGER JR
 COOKSTOWN & CLOVER
 BOX 1515 R R 1 RDS
 BETHLEHEM SMITHS N J

Jr.
 rip''

This is CADRE 2-Way Radio

developed by **CADRE INDUSTRIES CORP.**
for the 27 Mc **CITIZENS BAND OPERATION**

These CADRE units are built to the highest standards of the electronics industry, by a company that has been long established as a prime manufacturer of precision electronic research equipment and computer assemblies. CADRE transceivers are 100% transistorized — compact, lightweight . . . engineered for unparalleled performance and reliability.

The CADRE 5-Watt Transceiver, at \$199.95, for example, for offices, homes, cars, trucks, boats, aircraft, etc., measures a mere 11 x 5 x 3", weighs less than 6 pounds! Nevertheless, it offers 5 crystal-controlled transmit/receive channels (may be used on all 22), and a range of 10 miles on land, 20 over water!

The CADRE 100-MW Transceiver, \$124.95, fits into a shirt pocket! Weighs 20 ounces, yet receives and transmits on any of the 22 channels . . . efficiently, clearly . . . without annoying noise. A perfect "pocket telephone"!

For the time being, it is unlikely that there will be enough CADRE transceivers to meet all the demand. Obviously, our dealers cannot restrict their sale to the fields of medicine, agriculture, transportation, municipal services, etc. However, since these CADRE units were engineered for professional and serious commercial applications—and cost more than ordinary CB transceivers — we believe that as "water finds its own level," CADRE transceivers will, for the most part, find their way into the hands of those who really need them.

Write for complete information and detailed specifications.



CADRE INDUSTRIES CORP., Endicott, N. Y.

Prices appearing in this advertisement are suggested retail prices

www.americanradiohistory.com

ONLY AMERICAN BASIC SCIENCE CLUB GIVES YOU A **COMPLETE ELECTRONICS LAB** *plus*

a **Basic Radio Course**

Complete Lab and Course Comes
in **4 Kits**... One a Month.

ALL FOR ONLY
\$15⁸⁰



A COMPLETE ELECTRONICS COURSE

Developed with world famous SOUTHWEST RESEARCH INSTITUTE. The four instruction manuals are expertly written, clearly illustrated... making it easy for you to build 65 projects in electronics, step-by-step. You gain a valuable electronics background that will enrich your life and help shape your future! Basic enough for beginners... rewarding enough for experts. Nowhere else is a course of this scope available at this LOW PRICE!

ENTHUSIASTIC MEMBERS WRITE:

"basic principles unforgettably learned"...

It is only after having completed the experiments in your kits that I can say I have truly and unforgettably learned the basic principles of electronics. JOHN R. KANIA, 2 Berkeley Ave., Yonkers 5, N. Y.

"your kits are interesting and rewarding"...

I am an electronics student in the Air Force and find your kits interesting and rewarding. We have not covered anything in the school that you have not covered in the kits. JOHN G. DILL, Keesler Air Force Base, Biloxi, Miss.

"far ahead of friend taking another course"...

A friend of mine is taking a correspondence course in electronics, and I have learned more from your first two kits than he has in twenty lessons. RAY P. BILODEAU, 139 Exchange St., Leominster, Mass.

"the number of concepts presented is amazing"...

Your kits offer a range of experiments usually performed only in the better high school and college laboratories. The number of concepts presented, and the clarity and concreteness of their development is amazing. R. M. HELM, Professor of Physics, East Carolina College, Greenville, N. C.

KIT 1 — MAGNETISM AND ELECTRICITY

Subjects include:

- Magnetic Fields • Electron Theory
- Electric Charge • Direct Current
- Electro-Chemistry • Alternating Current
- Inductance • Transformer Principles

Builds 26 Projects including:

- Electroscope • Surprise Shock Box
- Electro Magnet • Galvanometer
- AC Buzzer • Demagnetizer • Relay
- Solenoid Coin Toss

KIT 2 — RESISTANCE, CAPACITANCE AND RECTIFICATION

Subjects include:

- Ohm's Law • Power Formulas • Rectification
- Resistance • Neon Glow Tubes • Capacitance • Filter Circuits

Builds 18 Projects including:

- Strobe Light • Thermocouple • Wheatstone Bridge • Voltmeter • AC Rectifier • DC Power Supply

KIT 3 — AMPLIFIERS AND OSCILLATORS

Subjects include:

- Vacuum Amplifier Tubes • Voltage Amplification • Oscillator Circuits
- Frequency and Wave Length Sound Waves, Pitch and Resonance

Builds 14 Projects including:

- Two Stage Amplifier • Capacitance Burglar Alarm • Proximity Detector
- High Speed Strobe Light • Ripple Tank Wave Generator • Code Practice Oscillator

KIT 4 — AUDIO AMPLIFICATION AND RADIO

Subjects include:

- Sound Amplification • Audio Amplifiers • Amplitude Modulation • Radio Theory • Regenerative Circuits • Tuning Circuits

Builds 7 Projects including:

- Microphone and Audio Amplifier
- Broadcast Radio • Short Wave Radio
- Signal Tracer • Transmitter

ALL THE EQUIPMENT FOR ALL THE ABOVE — Only **\$15⁸⁰**

SEND **\$2⁰⁰** WITH ONLY COUPON

PAY **\$3⁴⁵** ONLY

FOR EACH KIT YOU RECEIVE (ONE A MONTH FOR 4 MONTHS)



FREE

- AUXILIARY TEXTBOOKS
1. Simplified RADIO-TV SERVICING
 2. Steps to a HAM LICENSE

A VALUABLE ELECTRONICS LAB

Containing parts by RCA, MALLORY, PYRAMID, GE, CENTRALAB, STACKPOLE, TRIM and other reliable manufacturers. Retail value of parts alone is MORE THAN 25 DOLLARS!

Your Satisfaction or Your Money Back... AND You May Cancel at any time without obligation. These "No Risk" assurances because we know you will be

SURPRISED! AMAZED! DELIGHTED!

AMERICAN BASIC SCIENCE CLUB, Inc.
501 E. Crockett, San Antonio 6, Texas

Start sending me A.B.S.C.'s "Electronics Lab" in four kits, one each month. If not satisfied on inspection of first kit I may return it for immediate refund. (I choose the plan checked)

- () I enclose \$2.00 and will pay \$3.45 plus COD postage on arrival of each kit. I may cancel unshipped kits at any time.
- () I enclose \$15.80, full payment, POSTAGE PAID, for all four kits. I may cancel at any time and get full refund on unshipped kits.

NAME

ADDRESS

CITY and STATE

MAIL THIS MONEY-SAVING COUPON NOW!

POPULAR ELECTRONICS is published monthly by Ziff-Davis Publishing Company at 434 South Wabash Avenue, Chicago 5, Illinois. **Subscription Rates:** One year United States and possessions, \$4.00; Canada and Pan American Union Countries, \$4.50; all other foreign countries, \$5.00. Second Class postage paid at Chicago, Illinois, and at additional mailing offices. Authorized by Post Office Department, Ottawa, Canada, as Second-Class matter, November, 1961, Volume 15, Number 5.

POPULAR ELECTRONICS

VOLUME 15

NUMBER 5

NOVEMBER 1961



POPULAR ELECTRONICS is indexed
in the Readers' Guide
to Periodical Literature

Cover PHOTO courtesy Warner Bros.
Bert Six, Photographer

Special Feature

Electroluminescence..... James E. Pugh, Jr. 41

Electronic Construction Projects

Radiation Detector..... Jack Mandeville 45
Flea-Power Glow Light..... James E. Pugh, Jr. 49
Radio Doubles as Intercom..... Martin H. Patrick 62
Bi-Slave for AG-1's..... Jim Goss 67
Power A'Plenty..... E. H. Marriner, W6BLZ 71
Low-Pass Filter Reduces TVI..... Herb S. Brier, W9EGQ 80

Construction Techniques

4 Ways to Get Clipped..... John A. Comstock 54
Equipment Labeling—Simplified..... Charles Smith 60
Three-Hand Soldering..... John A. Comstock 85

Audio and High Fidelity

Hi-Fi Heat Wave..... Charles H. Welch 52
Fly Swatter Becomes Cartridge Tester..... Art Trauffer 64
Stereo Headset on a Budget..... 65
Stereo-itis..... James P. Cullen 78

Amateur, CB, and SWL

FCC Report..... Robert E. Tall 16
Add a Squelch to the CB-1..... R. L. Hawbaker, 1ØWØ975 55
On the Citizens Band..... Dick Strippel, 2W1452 75
How to Talk to Non-Hams..... Fred E. Ebel, W9PXA 76
Across the Ham Bands: DX'ing and the Sun..... Herb S. Brier, W9EGQ 79
Short-Wave Report: More Questions and Answers..... Hank Bennett, W2PNA 86
Short-Wave Monitor Certificate Application..... 117

Electronic Features and New Developments

CB Goes on TV..... 48
Electronic Analogy Quiz..... Robert P. Balin 59
Pediacometer..... Dennis J. Cipnic 66
Meet the Winners..... 70
Transistor Topics..... Lou Garner 82
Crossword Puzzle..... Thomas Windser 88
Carl and Jerry: Substitute Sandman..... John T. Frye, W9EGV 90

Departments


POP'tronics News Scope..... 6
Hi-Fi Showcase..... 10
Coming Next Month..... 22
Letters from Our Readers..... 24
POP'tronics Bookshelf..... 32
Tips and Techniques..... 99
New Products..... 106

Copyright © 1961 by ZIFF-DAVIS PUBLISHING COMPANY. All rights reserved.

POPULAR ELECTRONICS



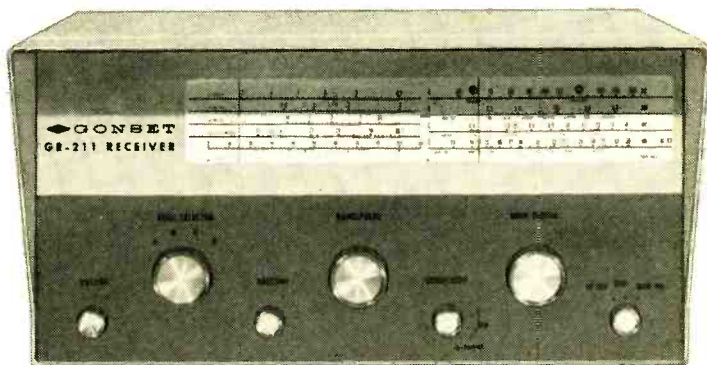From the world capitals where the news is made!
Get it DIRECT with



GONSET GR-211 ALL-BAND RECEIVER!

The GR-211 highly sensitive all-band receiver places the world at your finger tips. A turn of the knob and you're listening DIRECT to Berlin, Paris, Moscow, London, Tokyo. The GR-211 is designed for general coverage from standard broadcast through 34 mc band, including WWV, foreign and Voice of America.

Gonset GR-211 gives you all these deluxe features:

- Printed circuit techniques and advanced design for extra sensitivity, better, quieter reception, even on highest frequency bands.
- 5 tubes, 2 solid state rectifiers, transformer-powered (NOT AC/DC) for higher over-all gain, better signal-to-noise ratio.
- Circuit features leading to higher sensitivity include quality, high Q, permeability-tuned coils.
- Two full-vision, illuminated slide-rule type dials provide instant identification of broadcast and short-wave frequencies.
- Vernier tuning knob counter-weighted for smooth, non-critical short-wave tuning.

Amateur net price **\$6950**

For further information on the GR-211 and the name of your nearest Gonset distributor, fill out and mail this coupon!

COUPON: Please send me, without obligation, full information on the GR-211 all-band receiver.

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

GONSET Dept. PE-11, 801 So. Main Street, Burbank, Calif.

GONSET

DIVISION OF YOUNG SPRING & WIRE CORPORATION

POPULAR ELECTRONICS

World's Largest-Selling Electronics Magazine
Net Paid Circulation 387,690

Publisher **PHILLIP T. HEFFERNAN**

Editor **OLIVER P. FERRELL**

Managing Editor **JULIAN M. SIENKIEWICZ, WA2CQL**

Art Editor **JAMES A. ROTH**

Associate Editors **MARC E. FINKEL**

RICHARD A. FLANAGAN

MARGARET MAGNA

Draftsman **ANDRE DUZANT**

Editorial Assistant **MARY ANNE O'DEA**

Editorial Consultant **OLIVER READ, W4TWV**

Contributing Editors **H. BENNETT, W2PNA**

H. S. BRIER, W9EGQ

J. T. FRYE, W9EGV

L. E. GARNER, JR.

D. STRIPPEL, 2W1452

Advertising Manager **WILLIAM G. McROY, 2W4144**

Advertising Service Manager **ARDYS C. MORAN**

ZIFF-DAVIS PUBLISHING COMPANY

Editorial and Executive Office (ORegion 9-7200)
One Park Avenue, New York 16, New York

William B. Ziff, Chairman of the Board (1946-1953)

William Ziff, President

W. Bradford Briggs, Executive Vice President

Hershel B. Sarbin, Vice President and General Manager

M. T. Birmingham, Jr., Vice President and Treasurer

Robert P. Breeding, Circulation Director

Charles Housman, Financial Vice President

Midwestern and Circulation Office (WAbosh 2-4911)

434 South Wabash Avenue, Chicago 5, Illinois

Midwestern Advertising Manager **JAMES WEAKLEY**

Western Office (CRestview 4-0265)

9025 Wilshire Boulevard, Beverly Hills, California

Western Advertising Manager **WILLIAM J. RYAN**

Foreign Advertising Representative


D. A. Goodall Ltd., London, England



SUBSCRIPTION SERVICE: All subscription correspondence should be addressed to **POPULAR ELECTRONICS**, Circulation Department, 434 South Wabash Avenue, Chicago 5, Illinois. Please allow at least six weeks for change of address. Include your old address as well as new—enclosing if possible an address label from a recent issue.

EDITORIAL CONTRIBUTIONS must be accompanied by return postage and will be handled with reasonable care; however, publisher assumes no responsibility for return or safety of art work, photographs or manuscripts.

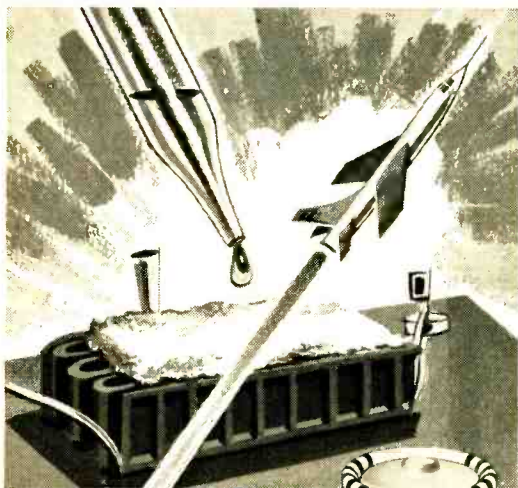Always say you saw it in—**POPULAR ELECTRONICS**



-100° F on two Amperes



Instant ice — and steam — from a battery powered device enables a leading aircraft maker to produce better planes. Better batteries? Buy **BURGESS** — famous for dependable, long-lasting power!

BURGESS BATTERY COMPANY

DIVISION OF SERVEL, INC.

FREEPORT, ILLINOIS NIAGARA FALLS, CAN.

We Really Mean It...When We Say

You **DON'T** Need

A High School Diploma

Previous Electronics Experience

to prepare **AT HOME** the DeVry way for a job that

Pays **REAL MONEY** in **Electronics!**

LET US TELL YOU WHY!

OUR INTEREST IN YOU... MAKES THE BIG DIFFERENCE!

In preparing you at home for a profitable job in the billion dollar opportunity field of electronics, DeVry Tech is more interested in your **DESIRE TO GET AHEAD** than we are in what you know about the field now. DeVry's training is thorough and practical. No previous electronic experience is required. We train you even if you don't know how to splice a lamp cord.

Our thorough training, with its many exclusive features such as home movies, has produced many graduates so well-trained, they have been employed by some of today's best-known firms and by scores of Radio and TV stations across the continent. DeVry Tech graduates are in demand. There are many job opportunities for them.

Becoming a DeVry Tech man in itself is a big lift. We have found during the past 29 years that by understanding a man's problems . . . by encouraging him in every way possible, we usually help him get the break he wants. It helps him do things he cannot do alone.

Another important benefit of becoming a DeVry Tech man is knowing you are part of an institution that not only trains you and helps you get started . . . but an organization that stands behind you on the job. It is such things as these that make DeVry Tech graduates **DIFFERENT** . . . it makes them **PREFERRED** men by so many employers.

Why don't you send the coupon below for 2 **FREE** booklets . . . Mailing that coupon could be a big step forward . . . toward greater heights . . . better pay!

Exclusive training movies help you learn **FASTER!**

We Have Residential Training for High School Graduates

MILITARY SERVICE We have valuable information for every man of draft age.	EARN WHILE YOU LEARN Practical training shows you how to earn good money in spare time.	RESIDENT TRAINING DeVry Tech has modern training centers in Chicago and Toronto.
---	---	--

WORK IN THESE EXCITING FIELDS WHEN TRAINED!

Radar • Guided Missile Control • Television • Radio
Micro-Waves • Communications • Industrial Electronics
Computers • Automation Electronics • Broadcasting
Remote Control Systems • Your Own Service Shop

DeVRY TECHNICAL INSTITUTE
CHICAGO • TORONTO

DeVry Sends You Actual Equipment You Need

At No Extra Cost!

DeVry Tech, in addition to its exclusive training movies, sends you the practical "Electro-Lab" system which includes 16 shipments of equipment to work more than 300 learn-by-doing projects in your own home. We know of nothing more effective than DeVry Tech's tool-in-hand training.

Send for these

2 FREE BOOKLETS



Accredited member of National Home Study Council

DeVRY TECHNICAL INSTITUTE
4141 Belmont Avenue • Chicago 41, Illinois • Dept. PE-11-R

Please give me your two free booklets, "Pocket Guide to Real Earnings" and "Electronics in Space Travel"; also include details on how to prepare for a career in Electronics. I am interested in the following opportunity fields (check one or more):

- | | |
|--|--|
| <input type="checkbox"/> Space & Missile Electronics | <input type="checkbox"/> Communications |
| <input type="checkbox"/> Television and Radio | <input type="checkbox"/> Computers |
| <input type="checkbox"/> Microwaves | <input type="checkbox"/> Broadcasting |
| <input type="checkbox"/> Radar | <input type="checkbox"/> Industrial Electronics |
| <input type="checkbox"/> Automation Electronics | <input type="checkbox"/> Special "Short Courses" |

Name _____ Age _____
PLEASE PRINT

Address _____ Apt. _____

City _____ Zone _____ State _____

Check here if you face military service.

Canadian residents: Write DeVry Tech of Canada, Ltd.

970 Lawrence Avenue West, Toronto 19, Ontario T078



POP'tronics


NEWS SCOPE



DEFECTIVE METAL DETECTIVE—Defects within ferrous metals are revealed by a portable “magnetic detector” which can be used to uncover cracked motor blocks in automobiles. Developed by the X-ray department of the Westinghouse Electric Corporation, the hand-held unit operates on auto batteries or may be plugged into any a.c. outlet. Checking for metal defects is simple. A special powder is sprayed onto the surface of the metal part to be inspected. Then the magnetic detector is held close by, and its magnetic field discloses any cracks or defects by forming tell-tale patterns in the powder. Used car dealers are reported to be unhappy.



“HOUSE-CLEANING” AIR is the job of a compact two-stage electronic air cleaner made by Minneapolis-Honeywell Regulator Company. The ionization stage sets up an electrical field between tungsten wires and grounded plates which ionizes the smallest dirt particles and vapors in the air stream. The collecting stage is a series of alternately charged negative and positive aluminum plates which attract and trap the ionized particles. This electronic air cleaning technique is designed to remove particles 100 times smaller than the usual filter in your air conditioner can. Pollen and other tiny airborne irritants that make life miserable for people with chronic allergies, plus unpleasant vapors, tobacco smoke and cooking fumes, “hit the dust” in the air cleaner—making your indoor air cleaner than the out-of-doors.

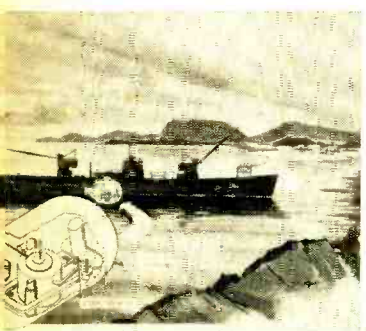

NUCLEAR BARGE POWER PLANT—The U.S. Army Corps of Engineers has just ordered into production the first floating nuclear power plant, to be built by The Martin Company for about \$17 million. The nuclear plant will be housed in a reconditioned and rebuilt Liberty ship, the “Walter F. Perry.” Packing enough power to supply the electrical needs of a civilian community of 20,000, the “atomic barge” will be towed from place to place as needed whenever normal supplies are cut off by peacetime disaster or wartime action. The reactor is a proven “pressurized water” system type. Water passing under pressure through the hot core of the reactor transfers the heat to water at lower pressure in a separate “secondary loop.” The steam thus produced turns the blades of a turbine, generating electricity.



TELEPHONE THIEVES? No, just a demonstration of what appear to be two standard telephones with “no strings attached.” Actually, the phones are experimental wireless transceivers developed by Automatic Electric Laboratories, Northlake, Ill. These wireless extension telephones could be used at restaurants, conventions, at pool sides or in the lobbies of hotels, and in other public settings. While practical working models have been developed, the wireless phone will not be available to telephone subscribers for a long time because of the lack of available radio frequencies.

(More on page 8)

F.C.C. COMMERCIAL OPERATOR LICENSE

Training... for Jobs in Electronics

F. C. C. LICENSE—THE KEY TO BETTER JOBS

An F. C. C. *commercial* (not amateur) license is your ticket to higher pay and more interesting employment. This license is Federal Government evidence of your qualifications in electronics. Employers are eager to hire *licensed* technicians.

WHICH LICENSE FOR WHICH JOB?

The **THIRD CLASS** radiotelephone license is of value primarily in that it qualifies you to take the second class examination. The scope of authority covered by this license is extremely limited.

The **SECOND CLASS** radiotelephone license qualifies you to install, maintain and operate certain radiotelephone equipment but not commercial broadcast station equipment.

The **FIRST CLASS** radiotelephone license qualifies you to install, maintain and operate every type of commercial radiotelephone equipment including all radio and television stations in the United States, its territories and possessions. This is the highest class of radiotelephone license available. Many companies which employ industrial electronics technicians require this license.

GRANTHAM TRAINING PREPARES YOU

The Grantham Communications Electronics Course prepares you for a **FIRST CLASS** F. C. C. license, and it does this by **TEACHING** you electronics. Each point is covered simply and in detail, with emphasis on making the subject easy to understand. The organization of the subject matter is such that you progress, step-by-step, to your specific objective—a first class F. C. C. license.

CORRESPONDENCE OR RESIDENCE CLASSES

Grantham training is available by correspondence or in resident classes. Either way, you are trained quickly and well. Write, or mail the coupon below, to any division of Grantham School of Electronics. Our free booklet will be sent to you immediately.

HERE'S PROOF . . .

that Grantham students prepare for F. C. C. examinations in a minimum of time. Here is a list of a few of our recent graduates, the class of license they got, and how long it took them:

	License	Weeks
Thomas Schutte, 736 Clinton, Hamilton, Ohio	1st	12
Gary Harrison, 29 Spencer Drive, N. Kingston, R. I.	1st	12
Louis W. Pavak, 838 Page St., Berkeley 10, Calif.	1st	16
William F. Bratton, Jr., 435 Etna Street, Russell, Ky.	1st	12
Darrell E. Cloce, 25 E. 32nd St., Kansas City, Mo.	1st	12
Thomas J. Hoof, 216 S. Franklin St., Allentown, Pa.	1st	22
P. B. Jernigan, Route 2, Benson, North Carolina	1st	12
Edward R. Barber, 907 S. Winnifred, Tacoma, Wash.	1st	20
Claude Franklin White, Jr., c/o Radio Sta. WJMA, Orange, Va.	1st	12
John M. Morgan, c/o KIRI-TV, 1530 Queen Anne Ave., Seattle, Wash.	1st	9½

FOUR SCHOOLS TO SERVE YOU

To better serve our many students throughout the entire country, Grantham School of Electronics maintains four Divisions—located in Hollywood, California; Kansas City, Mo.; Seattle, Wash.; and Washington, D.C. Grantham offers rapid courses in F. C. C. license preparation, either by home study or in resident classes.

Get your First Class Commercial F. C. C. License in 12 weeks by training at

Grantham School OF ELECTRONICS

HOLLYWOOD
CALIF.

1505 N. Western Ave.
Hollywood 27, Calif.
(Phone: HO 7-7727)

SEATTLE
WASH.

408 Marion Street
Seattle 4, Wash.
(Phone: MA 2-7227)

KANSAS CITY
MO.

3123 Gillham Road
Kansas City 9, Mo.
(Phone: JE 1-6320)

WASHINGTON
D. C.

821-19th Street, N. W.
Washington 6, D. C.
(Phone: ST 3-3614)

for **FREE** Booklet **CLIP COUPON** and mail
in envelope or paste on postal card.

MAIL COUPON NOW



TO: GRANTHAM SCHOOL OF ELECTRONICS

1505 N. Western • 408 Marion • 3123 Gillham Rd. • 821-19th, NW
Hollywood • Seattle • Kansas City • Washington

Please send me your free booklet telling how I can get my commercial F. C. C. license quickly. I understand there is no obligation and no salesman will call.

Name _____ Age _____

Address _____

City _____ State _____

I am interested in: Home Study, Resident Classes 13-S



NEWS SCOPE

Continued

AUTOMATIZED STAMP COLLECTING IS HERE! A handy gadget, tabbed the PDQ (for Patents Development Quorum, Inc.), dispenses supermarket stamps automatically and speeds up the checking out of purchases in the following manner: the clerk punches buttons on the PDQ corresponding to the total on the register, a motor is activated, and the PDQ spits forth the correct number of stamps—one for every 10 cents worth of merchandise. The dispenser has two circles of buttons, one for dollars and one for dimes; five small precision switches made by Micro Switch control the unit. A boon for philatelists? Hardly. But the housewife-collector should certainly appreciate it.



SKI SAFETY—A resourceful ski resort owner in Maine borrowed a cost-cutting communications idea from industry to give vacationers an extra measure of safety. Equipping the members of his Ski Patrol with Globe two-way "Pocket-phone" radios has saved up to ten valuable minutes in getting injured skiers down the slopes of Pleasant Mountain. The small 100-milliwatt units permit the ski patrolers to call for help while remaining at the victim's side.



PEEK-A-BOO TV—A costly and troublesome job in American industry is that of plant protection. Merck & Co., Inc., in Rahway, N. J., has solved the "gate-keeping" problem by having a guard keep one eye on the main plant entrance and another eye on a remote gate "around the corner" a half-mile away. This would be difficult for one man to handle if it were not for a Dage closed-circuit TV system. When an employee wants to pass through the remote gate, he simply presses a button. The guard at the main gate identifies the employee by looking into the TV monitor and, if all is well, automatically opens the gate and closes it behind him. The wide-angle view of the TV camera prevents unauthorized people from slipping in unnoticed.



CQ GRIZZLY BEARS! Naturalists with the Montana Cooperative Wildlife Research Unit are tagging grizzly bears in the Yellowstone National Park with tiny Philco transmitters. They plan to keep track of the grizzlies' roaming habits in the hope of discovering some hint as to the reasons for their high mortality rate—fewer than 1000 grizzlies survive south of Canada. The study is being sponsored by the National Geographic Society and the National Science Foundation.

POWER BRAIN—Out Philadelphia way, every time you flick a light switch on or off, an electronic digital computer measures the power need and gives orders to huge turbine generators of the Philadelphia Electric Company. The electronic "brain" is the heart of a complex control system—it automatically and continuously portions off the utility's total electrical load requirements to 34 generating units so that each can operate most economically. Almost as a bonus, the computer also performs billing calculations on the amount of power exchanged with interconnecting utilities.

POPULAR ELECTRONICS

NEWS! WEATHER! COMMUNICATIONS!



COMMAIRE PT-27...world's first long-range portable self-powered, two-way radio with AM receiver!

Totally new—and another first from Vocaline! Don't confuse the Commaire® PT-27 with ordinary-range, "line-of-sight" portable units. Here's an extraordinary, fully professional 4-channel long-range Citizens Band two-way radio, *plus* an outstanding built-in AM receiver. The entire unit is completely portable—and self-powered! There's never been a unit like it. Commaire PT-27 requires no costly installation. Goes anywhere. Works anywhere.

CHECK THESE EXCITING FEATURES:

Full-range two-way radio on the 11 meter Citizens Band that gives accurate, sensitive performance... up to 5 miles with portable antenna... still much greater range with full-size antenna.

Built-in AM receiver to keep you in touch with news, weather and entertainment.

Portable—and self-powered. Use anywhere on boats, in cars or business. No installation needed.

18 Transistors plus 2 tubes in transmitter section for greater stability.

Power output: ½ watt on transmit.

4 fixed channels—tunable receiver.

Receiver (double conversion superheterodyne) sensitivity is 0.1 microvolts; selectivity is 40 db down at ± 10 KC.

Built-in battery box, charger, antenna, microphone and crystal for one channel.

Measurements: Only 11" long x 4" wide x 9" high.

10 controls for convenient, simple operation.

Model PT-27—\$250.00 each, list.


Write for descriptive brochure.

COMPLETE COMMUNICATIONS SYSTEM

Also Model ED-27M, powerful base unit with 4 channels. Completes your perfect low-cost system. \$189.50. Base antenna extra.

VOCALINE

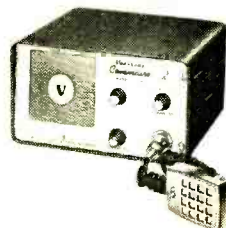COMPANY OF AMERICA, INC.
OLD SAYBROOK, CONNECTICUT



MUSIC BIG AS LIFE

Utah's High-Fidelity CONTINENTAL SPEAKERS



C12RD 12"
WOOFER
2 Lb. Alnico
V Magnet and
2" Voice Coil

YOU GET LIFE-SIZE SOUND in every range, from 20 to 20,000 CPS, with Utah's precision-engineered stereo/high-fidelity speakers. Tweeters and mid-range speakers feature a specially engineered horn formula to enhance "presence". Each speaker has color-coded 4-way terminals.



1124 Franklin St.
Huntington
Indiana

Please mail me prices, specifications and performance details of your Continental speaker line.

NAME _____

ADDRESS _____

CITY _____ STATE _____

Hi-Fi |



Showcase

*A quick look at
new products in the
stereo/hi-fi field**

DESIGNED to take advantage of the acoustic benefits of corner mounting, Argos Products' three new speaker baffles not only have a "clip-in" front to eliminate unsightly screws, but a slotted-back design makes them easy to hang as wall baffles. In addition, there are outside screw terminals which can be connected internally to the speaker voice coil, making it unnecessary to remove the front of the baffle once the speaker is installed. Produced in both straight and sloping-front models and for both 8" and 12" speakers, the baffles are priced from \$12.50 to \$18.90. An additional model, the SCB-208S, comes complete with an 8" Jensen "Profile" speaker and sells for \$22.75. . . . If you're in the market for a deluxe stereo preamplifier with just about every feature you've ever wanted in a "master control" center, you'll be interested in Heath's Model AA-11. For simplicity of operation, all switches and con-



Heathkit AA-11 stereo preamplifier

trols have been divided into two distinct groups: the basic or "primary" controls are located on the plastic front panel, while the "secondary" controls have been placed behind a hinged cover on the lower front panel. Among the primary controls: eight push-button switches for selection of five stereo inputs, three monophonic inputs; a push-button on/off switch; a volume/loudness control; and separate, Bax-andall-type bass and treble controls. Price, f.o.b. Benton Harbor, Mich., \$84.95.

A 4-track tape recorder from West Ger-

**Write to the manufacturers listed at the end of this column for more data on products mentioned*



"a CREI home study program helped me become an electronics engineer"

—Robert T. Blanks
 Engineer, Research & Study Division
 Vitro Laboratories, Silver Spring, Md.
 Division of Vitro Corporation of America



"THROUGH A CREI HOME STUDY PROGRAM I learned the practical theory and technology I needed to become a fully-qualified engineer—not a 'hardbook' engineer, either—and I did it while I was on the job," says Robert T. Blanks. Today thousands of advanced electronics personnel—engineering technicians, engineers, administrators, executives—attribute their present high salaries and positions to their home study of CREI Programs in Electronic Engineering Technology.

DEMAND FOR CREI-PREPARED MEN today far exceeds the supply—has exceeded the supply for many years. Specifically designed to prepare you for responsible positions in electronics, CREI Home Study Programs are the product of 34 years of experience, include the latest advancements in the field. CREI's curricula was among the first accredited by the Engineers' Council for Professional Development. Here Blanks discusses CREI with Director Wayne G. Shaffer of Vitro Labs.



WHEN YOU ENROLL IN A CREI Home Study Program, you join more than 20,500 students working in electronics in all 50 states and most countries of the free world. One CREI Program helped Robert Blanks become an Electronics Engineer. Another helped Robert I. Trunnell become an Electronics Technician. While John H. Scofield—a Mathematician—is enrolled in still a different CREI Program relating mathematics to electronics. All work at Vitro Laboratories.

YOUR LIVING IS BETTER when you prepare for—and get—desired promotions through CREI Home Study. CREI alumnus Blanks is understandably proud of his home in a comfortable neighborhood. The positions of CREI-prepared men in such companies as Pan American Airways, Federal Electric Corporation, The Martin Company, Northwest Telephone Company, Mackay Radio, Florida Power and Light and many others attest to the high calibre of CREI Programs.

YOUR WHOLE FAMILY BENEFITS. Engineer Blanks' growing family pitched in to provide free time for his CREI Home Study. Now they share his success. We invite you to check the thoroughness and completeness of CREI Home Study Programs in Electronic Engineering Technology in the catalog provided on request. For those who can attend day or evening classes in person, CREI maintains a Residence School in Washington, D.C. also offering ECPD Accredited Technical Institute Curricula.

INDUSTRY-RECOGNIZED CREI HOME STUDY PROGRAMS PREPARE YOU FOR INCREASED RESPONSIBILITIES, HIGHER-PAYING POSITIONS IN ELECTRONICS.

REQUIREMENTS FOR ENROLLMENT
 Pre-requisite is a high school education or equivalent plus basic electronics training and/or practical electronics experience. (Electronics experience and/or training not necessary for Residence School.) If you qualify, send for the latest CREI catalog at no cost. Veterans may apply under the G.I. Bill. If you're doubtful about your qualifications, let us check them for you. Mail coupon or send your qualifications to: The Capitol Radio Engineering Institute, Dept. 1211-H, 3224 Sixteenth St., N.W., Washington 10, D.C.

MAIL COUPON TODAY FOR FREE 58-PAGE BOOK

THE CAPITOL RADIO ENGINEERING INSTITUTE

ECPD Accredited Technical Institute Curricula — Founded 1927

Dept. 1211H, 3224 Sixteenth St., N. W., Washington 10, D. C.

Please send me details of CREI Home Study Programs and Free Book, "Your Future in Electronics and Nuclear Engineering Technology." My qualifications are noted to obtain immediate service.

- CHECK FIELD OF GREATEST INTEREST:**
- Servo and Computer Engineering
 - Automation and Industrial Electronic Engineering Technology
 - Electronic Engineering Technology
 - Nuclear Engineering Technology
 - Aero and Navigational Engineering Technology

Name Age

Address

City Zone State

Employed by

Type of present work

Education: Years High School Other

Electronics Experience


Check: Home Study, Residence School, G.I. Bill



SHERWOOD

only for those who want the ultimate in

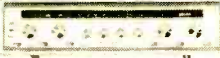FM Stereo Broadcast Reception and Stereo Record Reproduction



S-8000 FM/MX 64 Watt Stereo Receiver \$299.50
16 1/4" x 4" x 14" deep.



S-3000 IV FM/MX Stereo Tuner \$160.00
14" x 4" x 10 1/2" deep.



S-5000 II 80 Watt Stereo Amplifier \$199.50
14" x 4" x 12 1/2" deep.



Ravinia Model SR3 3-way
Speaker System \$139.50
26" x 15" x 13 1/4" deep.

Correlaire Walnut Hi Fi Furniture



With FM Stereo broadcasting (multiplex) an established reality, Sherwood proudly offers every component you need for superb stereo reception. Sherwood stereo amplifiers and tuners are pre-eminent in the field, and now—in the S-8000 Receiver—the ultimate in compact reception quality is achieved. The exciting new Ravinia Model SR3 3-speaker system features extremely low intermodulation distortion and unusually flat frequency response. Cabinet is hand-rubbed walnut. The perfect setting for hi fi components is Sherwood's Correlaire contemporary furniture modules—in hand-rubbed Walnut and Pecan. Sherwood Electronic Laboratories, Inc., 4300 N. California Ave., Chicago 18, Illinois.

For complete technical details,
write Dept. 112



Showcase

(Continued from page 10)

many—the *Korting 114*—features three separate heads for erase, record, and playback; is equipped with a preamplifier/equalizer for both recording and playback; and must be used with an external power amplifier. An ideal unit for incorporation into an existing stereo setup, the 114 is so designed that its internal preamplifier can be bypassed for mono recording or playback, and an external preamplifier used instead. Other features: a dubbing control which allows a previous recording on one track to be dubbed onto another track of the same tape, producing a perfect multiple-synchronized recording; a tape counter with zero adjustment; a pause button; and a recording level meter. Frequency response of the 114 is 40-15,000 cycles at 3 3/4 ips; 30-20,000 cycles at 7 1/2 ips; wow and flutter less than 0.2% at 7 1/2 ips. The 114 is priced at \$279.50.

If space is at a premium and decor important for your hi-fi setup, the "Verti-Sonic" speaker systems by *Lord's Electronics* may well be the answer. Consisting of one, two, or three speakers mounted on vertical "room divider" poles, the Verti-Sonic systems reproduce frequencies from 60 to over 13,000 cycles and can be pivoted a full 360 degrees. The systems use Jensen hi-fi speakers and prices start at \$129.95. . . . Flexible cabinet end panels constructed of stiff laminated materials and mounted on sponge rubber surrounds help extend the low-frequency response of an ultra-compact speaker system by *Rus-Lang*. Measuring 9 3/4" x 18" x 9 1/2", the system employs an 8" speaker and has a frequency range of 40-14,000 cycles. The unit is attractive, too: the enclosure is made of genuine oiled walnut, and the grille cloth is a contrasting white and gold. Price, \$34.95.

One of the first stereo receivers for the new FM multiplex stereocasts is *Sherwood's* S-8000. Incorporating two 32-watt



Sherwood S-8000 stereo multiplex receiver

amplifiers and a stereo preamp for phono, tape, and TV control, the S-8000 also contains a sensitive FM tuner complete with wired-in multiplex circuitry. Frequency re-

Always say you saw it in—POPULAR ELECTRONICS

want to
boost
your pay?

Move Ahead
in
ELECTRONICS

Get All
3 Free!



Get This Handy Pocket
Electronics Data Guide Folder
Free . . .

Puts all the commonly used conversion factors, formulas, tables, and color codes at your fingertips. Yours absolutely free if you mail the coupon today. No further obligation!



find out how . . .

1. You can get job security. Specialized education is the road to higher salary and important jobs in the growing field of electronics.
2. You can solve the problems that stump other technicians. Problems in electronics are becoming more complex. Your ability to solve problems will help you get ahead in your field.
3. You can handle new electronic devices. Every day, advances are being made in electronics. Only through education can you find out how to keep up with these developments and how to use the new devices.

Sorry—Not For Beginners!

Please inquire only if you really want to get ahead and to add to what you have already learned in school, in the service, or on the job. Some previous schooling or experience in electronics, electricity, or related fields is necessary for success in Cleveland Institute programs.

Cleveland Institute of Electronics

1776 E. 17th St. Desk PE-83 Cleveland 14, Ohio

**Your FCC License
Or Your Money Back!**

Completion of the Master Course (both Sections) will prepare you for a First Class Commercial Radio Telephone License with a Radar Endorsement. Should you fail to pass the FCC examination for this license after successfully completing the Master Course, you will receive a full refund of all tuition payments. This guarantee is valid for the entire period of your enrollment agreement.

Investigate Our NEW Training Program
in Computers, Servo Mechanisms
Magnetic Amplifiers, and others

Accredited by the National Home Study Council

MAIL COUPON TODAY



Cleveland Institute of Electronics

1776 E. 17th St., Desk PE83, Cleveland 14, Ohio

Please send Free Career Information prepared to help me get ahead in Electronics. I have had training or experience in Electronics as indicated below:

- | | |
|---|---|
| <input type="checkbox"/> Military | <input type="checkbox"/> Broadcasting |
| <input type="checkbox"/> Radio TV Servicing | <input type="checkbox"/> Home Experimenting |
| <input type="checkbox"/> Manufacturing | <input type="checkbox"/> Telephone Company |
| <input type="checkbox"/> Amateur Radio | <input type="checkbox"/> Other |

In what kind of work are you now engaged?

In what branch of Electronics are you interested?


Name Age

Address

City Zone State

PE83

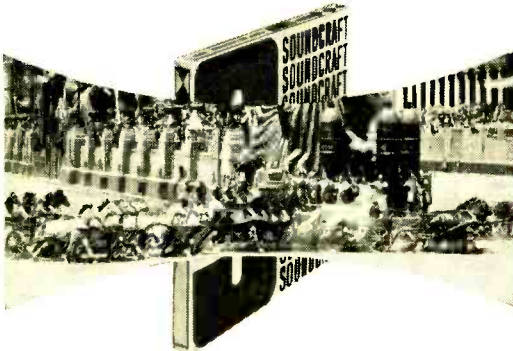IF YOU BELIEVE THAT ALL RECORDING TAPES ARE THE SAME... READ THESE FACTS ABOUT SOUNDCRAFT TAPES!



IT'S SOUNDCRAFT IN THE GREAT MOTION PICTURES

The course of a motion picture industry was revolutionized by the application of magnetic stripes on film... a Soundcraft achievement which has made possible the stereophonic sound tracks of the great MGM (Camera 65), Cinemascope and Todd-A O productions. For this contribution, Soundcraft received the coveted Academy Award "Oscar"—first and only tape manufacturer ever so honored. Soundcraft achievement never stops.

SOUNDCRAFT WAS FIRST TO OFFER YOU:

- Mylar* base tapes for longer life, longer play
- Plasticizer-free oxide to prevent chipping or flaking
- Micropolished tape surface to preserve the "highs" and minimize recorder head wear

■ FA-4 frequency adjusted formulation to capture the full dynamic range of sounds

BUY THE BEST — BUY SOUNDCRAFT TAPES



PHOTO FROM METRO-GOLDWYN-MAYER, WILLIAM WYLER'S PRESENTATION OF "BEN HUR," WINNER OF 11 ACADEMY AWARDS. *DU PONT T.M.

REEVES
SOUNDCRAFT
CORP.

Main Office: Great Pasture Road: Danbury, Connecticut


Showcase

(Continued from page 12)

sponse is within 1 db, 20 to 20,000 cycles, at 30 watts output, and the S-8000 needs only the addition of a pair of speakers to form a complete FM stereo setup. Equipped with 21 tubes and four silicon rectifiers, the S-8000 sells for \$299.50, less case. . . . Two ceramic phono cartridges by *Sonotone* are turnover types suitable for either stereo or monophonic records. With 22 db channel separation, the "16T" has a frequency response within 1 db from 20 to 10,000 cycles and precisely matches the RIAA characteristic. The "18T" offers somewhat higher output (0.7 vs. 0.5 volt), but less channel separation and heavier tracking force. Price: \$12.50 with sapphire styli; \$15.50 with diamond styli.

Stephens Trusonic has an 8" coaxial speaker with a "ring radiator" type tweeter.

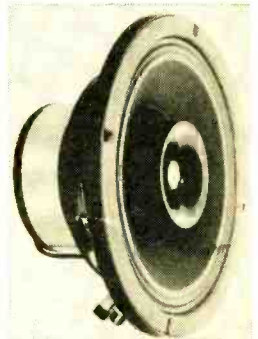The 80CX boasts a frequency response of 40-25,000 cycles and is equipped with a 5000-cycle cross-over network and attenuator control. Key to the speaker's remarkable performance is the RT-1 tweeter (also available separately) employing an edge-wound aluminum-ribbon voice coil which is attached to its form by



Stephens Trusonic 80CX

a special thermal-pressure method. The 80CX is priced at \$55.50; the RT-1 tweeter alone sells for \$26.50. . . . An adapter kit consisting of 11 frequently used audio adapters and one "universal" molded interconnecting cord is just the thing for interconnecting two pieces of equipment that do not have matching connectors. Manufactured by *Switchcraft, Inc.*, the kit (No. 331A) is supplied in a handy reusable plastic box and is intended for servicemen as well as audiophiles and experimenters. It's priced at \$15.00.

—30—





- Argos Products Co.*, Genoa, Ill.
- Heath Co.*, Benton Harbor, Mich.
- Kimberley Industries, Ltd.* (Korting), 346 W. 44th St., New York 36, N. Y.
- Lord's Electronics, Inc.*, 10 E. Kinzie St., Chicago, Ill.
- Rus-Lang Corp.*, 138 Hurd Ave., Bridgeport, Conn.
- Sherwood Electronic Laboratories, Inc.*, 4300 N. California Ave., Chicago 18, Ill.
- Sonotone Corp.*, Elmsford, N. Y.
- Stephens Trusonic, Inc.*, 8538 Warner Dr., Culver City, Calif.
- Switchcraft, Inc.*, 5555 N. Elston Ave., Chicago, Ill.

Always say you saw it in—POPULAR ELECTRONICS

**TWENTY-FIVE THOUSAND DOLLARS IN RESEARCH TIME
... NOTHING LIKE IT ON THE MARKET!**

Minivac[®] 601

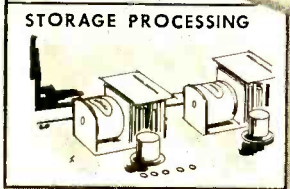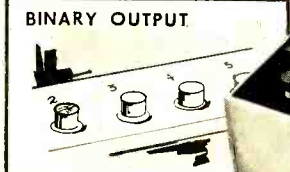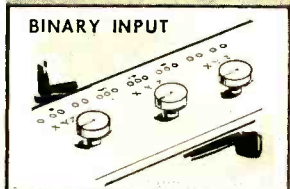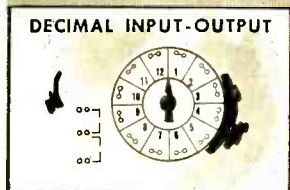**scientific exploration... education...
experimentation at the 24" console
of this amazing computer**



MINIVAC 601 is a unique digital computer — the small brother of huge electronic brains that are the newest tools of science and industry. MINIVAC has memory — it thinks . . . it can even play games. It prepares teenagers and adults for the world of tomorrow.

Created as a private project by Dr. Claude E. Shannon, now Donner Professor of Science, MIT, and developed by the SDC staff, MINIVAC 601 is built of professional components to professional standards.

It opens the way to exciting experimentation with circuits that solve problems and make decisions. It enables you to duplicate control systems like those used in advanced missiles. You may program it to demonstrate data processing techniques used in business. Hundreds of experiments are contained in the booklets. But this is only the beginning. The only limit to MINIVAC's accomplishments is the imagination of the machine's master.

\$8500

A complete set of 6 instruction manuals included. "Getting Acquainted with MINIVAC 601", "What is a Digital Computer?", "How Computers Make Logical Decisions", "How Computers Do Arithmetic", "How Computers Work for Man", and "MINIVAC Games".



SCIENTIFIC DEVELOPMENT CORPORATION

Department of Consumer Products

372 Main St., Watertown 72, Massachusetts

Scientific Development Corp.
Department of Consumer Products
372 Main Street, Watertown, Massachusetts

Gentlemen:

Please send free brochure giving complete information on Minivac 601... what it is... what it does... how it operates.

Name.....

Address.....

City..... Zone..... State.....



build your own PROFESSIONAL REK-O-KUT STEREOTABLE

ONLY \$59⁹⁵

Enjoy the performance of the world's finest turntable at remarkably low cost. In only a half hour's time, using just a screw-driver, you can assemble a Stereotable with the same unsurpassed performance as factory-assembled Stereotables! Features the Rek-O-Kut custom-built hysteresis synchronous motor and exclusive Rekothane belt—for lowest rumble ever achieved—plus the design and engineering qualities that make Rek-O-Kut the unchallenged leader in the field.

K-33H—33 $\frac{1}{3}$ rpm	\$59.95 net
K-34H—33 $\frac{1}{3}$ and 45 rpm	69.95 net
S-320 Stereo Tonearm	34.95 net
KB Walnut Base	14.95 net
APK-AUTO-POISE accessory (makes Stereotable and arm fully automatic)	49.95 net

Visit your high fidelity dealer now.
Literature on request.



REK-O-KUT STEREOTABLES

Rek-O-Kut Co., Inc., 38-19 108th St., Corona 68, N. Y.

P.K.32



FCC Report

☆☆☆☆☆ ☆☆☆☆☆☆☆☆☆☆☆☆☆☆☆☆☆☆☆☆☆

By **ROBERT E. TALL**
Washington Correspondent

BOMBARDED by requests from doctors, police and fire departments, civil defense officials, and many other "emergency" personnel for fast action on their CB applications, the FCC has, in effect, told these distinguished prospective CB'ers to get in line and sweat out the two-month-plus waiting period along with the rest of us. The standard FCC answer to "expedite" requests is that while the Commission would like to be helpful, only in "rare cases" where "there is an immediate need to use radio for the safety of life or property, or for a similarly compelling reason, have applications been considered ahead of their turns."

The Commission points out that the "sheer number" of CB applications which involve "possible emergency use" of the systems requested "makes it impossible to expedite all of them." Also, the agency "has found it necessary to restrict immediate action to those which deal with actual and existing emergencies." To put it more simply, there's not a ghost of a chance of getting a CB license in less than the normal time unless a disaster is either at hand or just around the corner. As of July 1, the CB license processing "delay time" was about 80 days.

Emergency Action. Examples cited of when CB "expedites" will be granted include applications from areas where a river above the town is at flood stage and preparations are being made to evacuate people from the danger area; where a forest fire is raging and is headed toward the applicant's area; where a risky job requiring radio communications is necessary to avoid disaster or to dispatch relief when disaster strikes; or when a sudden labor shortage endangers a seasonal industrial or agricultural activity and the use of radio would help the situation.


In a second type of example, quick licensing action can be had if it becomes necessary to move a station because of the unforeseen loss of a building when an owner cancels a lease, or if an original station is

(Continued on page 20)

RCA training at home can be the smartest investment you ever made


Look what you get in the Course in Radio and Electronic Fundamentals

40 Fascinating **THEORY LESSONS**

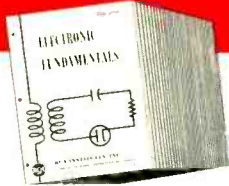


Containing all the basic principles of radio and electronics in easy-to-understand form.

40 EXPERIMENT LESSONS



Each containing absorbing, practical experiments bound together in 20 books.

40 SERVICE PRACTICES




Full of practical, time-saving and money-saving servicing tips, bound into 20 books.

PLUS ALL THIS AT NO EXTRA COST...

15 KITS

to build a Multimeter, AM Receiver and Signal Generator. Kits contain new parts for experiments, integrated so as to demonstrate what you learn in the lessons and to help you develop technical skills. Each kit is fun to put together!

MULTIMETER




A sensitive precision measuring instrument you *build* and *use* on the job. Big 4½" meter with 50 micro-amp meter movement. 20,000 ohms-per-volt sensitivity d-c. 6.667 a-c.

AM RECEIVER



Have the satisfaction of building your own radio receiver with this high-quality 6-tube superheterodyne set. Big 5" speaker, fine tone!

SIGNAL GENERATOR



A "must" for aligning and trouble-shooting receivers. Build it for your own use. 170 KC to 50 MC fundamental frequencies for all radio and TV work.

Practical work with the very first lesson! Pay-only-as-you-learn! No long-term contracts to sign! No monthly installment payments. Pay only for one study group at a time if and when you order it!

Stake out your future in electronics now!

SEND FOR OUR FREE HOME STUDY CATALOG TODAY!



Just fill out this card and drop it in the mail—no postage needed. ▶

RCA INSTITUTES, INC.

A Service of Radio Corporation of America • 350 W. 4th St., New York 14, N. Y. • 610 S. Main St., Los Angeles 14, Calif.

RCA INSTITUTES INC. Home Study School, Dept. PE-N1

A Service of Radio Corporation of America
350 West Fourth Street, New York 14, N. Y.

Without obligation, rush me the FREE 64-page illustrated book describing your electronic training program (check one). No salesman will call.

Home Study Los Angeles Resident School New York Resident School

Name (Please Print)

Address

City Zone State

Veterans: Enter discharge date.....

CANADIANS—Take advantage of these same RCA courses at no additional cost. No postage, no customs, no delay. Enclose this card in envelope and mail to: RCA Victor Company, Ltd., 5581 Royalmount Ave., Montreal 9, Quebec.



The Most Trusted Name in Electronics



RCA TRAINING CAN BE THE SMARTEST INVESTMENT YOU EVER MAKE

With RCA Institutes Home Study training you set your own pace in keeping with your own ability, finances and time. You get prime quality equipment as a regular part of the course . . . and you never have to take apart one piece to build another. Perhaps most important, RCA's liberal Pay-As-You-Learn Plan is the most economical home study method *because you pay only for lessons as you order them* . . . one study group at a time! If you drop out at *any* time, for *any* reason, you do not owe RCA one penny! No other obligations! No installment payments required! Licensed by New York State Education Department.

Choose **YOUR FUTURE** from this list of courses:

- Radio and Electronic Fundamentals (see reverse side)
- Television Servicing
- Color Television
- Electronics for Automation
- Transistors

START YOUR CAREER IN ELECTRONICS NOW AT RCA INSTITUTES in Los Angeles-New York City

CHOOSE FROM THIS LIST . . .

	Course	Qualifications	Length of Course
A	Advanced Electronic Technology (T-3)	High School grad. with Algebra, Physics or Science	Day 2 1/4 yrs. Eve. 6 3/4 yrs. (N.Y.) 4 1/2 yrs. (L.A.)
B	Television and General Electronics (V-7)	2 yrs. High School with Algebra, Physics or Science	Day 1 1/2 yrs. Eve. 4 1/2 yrs. (N.Y.) 3 yrs. (L.A.)
C	Radio and Television Servicing (V-3)	2 yrs. High School with Algebra, Physics or Science	Day 9 mos. Eve. 2 1/4 yrs. (N.Y.) 1 1/2 yrs. (L.A.)
D	Transistors	Radio background	Eve. 3 mos.
E	Electronic Drafting (V-11 v-12)	2 yrs. High School with Algebra, Physics or Science	Eve. Basic: 1 yr. Advanced: 2 yrs.
F	Color Television	Television background	Eve. 3 mos.
G	Radio Telegraph Operating (V-5)	2 yrs. High School with Algebra, Physics or Science	Day 9 mos. Eve. 2 1/4 yrs. (N.Y.) 1 1/2 yrs. (L.A.)
H	Computer Programming (C-1)	College Graduate or Industry sponsored	Eve. 24 weeks Sat. 30 weeks
I	Technical Writing (V-10)	High School Graduate	Day 9 mos. (L.A.) Eve. 2 1/4 yrs. (L.A.) 3 mos. (N.Y.)
J	Automation Electronics (V-14)	Background in Radio Receivers and Transistors	Eve. 9 mos. (N.Y.) Sat. 44 weeks (N.Y.)
K	Digital Computers	Electronics background	Eve. 3 mos. (L.A.)
L	Preparatory Math & Physics (P-O)	1 yr. High School	Day 3 mos. or 6 mos.
M	Preparatory Mathematics (P-OA)	1 yr. High School	Eve. 3 mos.

BUSINESS REPLY MAIL

No Postage Stamp Necessary if mailed in U. S.

Postage will be paid by —

RCA INSTITUTES, INC., Dept. PE-N1
350 West Fourth Street
New York 14, N. Y.

FIRST CLASS
PERMIT NO.
10662
NEW YORK, N. Y.



RCA Institutes is one of the largest technical institutes in the United States devoted exclusively to electronics. Co-educational Day and Evening classes. Free Placement Service. Applications now being accepted.

SEND FOR THIS FREE ILLUSTRATED BOOK TODAY

Fill in the other side of the postage-free card and check Resident School.










RCA INSTITUTES, INC.

A Service of Radio Corporation of America • 350 W. 4th St., New York 14, N. Y. • 610 S. Main St., Los Angeles 14, Calif.



The Most Trusted Name in Electronics


 <p>Model 650 GRID CIRCUIT ANALYZER TUBE TESTER</p> <p>Tests all standard tubes plus 10 pin miniatures, 12 pin Compactrons, 5 and 7 pin Nuvistors, Novar tubes and a wide variety of voltage regulator types, foreign and industrial tubes. Indicates gas current as low as 1 micro-ampere. Leakage sensitivity over 100 megohms. Net Price: \$69.95</p>	 <p>ADAPTER G-140 MULTI-SOCKET ADAPTER UNIT</p> <p>Modernizes any tube tester for the test of • 10 pin miniatures • 12 pin Compactrons • 5 and 7 pin Nuvistors and Novar tubes. Net Price: \$12.95</p>	 <p>Model ST-22 RF-AF SIGNAL TRACER</p> <p>High gain RF-AF Signal Tracer for AM, FM, TV and audio. Visual and audible signal indication from antenna to speaker. Noise test circuit, test amplifier and Wattmeter also included. Complete with shielded probe. Net Price: \$59.95</p>	
 <p>Model IC-60 IN-CIRCUIT CAPACITOR TESTER</p> <p>A great time saver! Reveals open or shorted capacitors without removing them from the circuit. Electrolytic dial indicates actual in-circuit electrolytic values from 2 mfd. to 400 mfd. Net Price: \$32.95</p>	 <p>Model ES-150 5 MC WIDE BAND OSCILLOSCOPE</p> <p>A deluxe, laboratory-type instrument in every sense, the ES-150 oscilloscope covers the entire range between DC and 5 megacycles with outstanding sensitivity and stability. Net Price: \$149.95</p>	 <p>Model E-75 RF SIGNAL GENERATOR</p> <p>A signal generator designed for AM-FM and TV. Frequency ranges from 160 kc. to 240 megs, direct reading in 8 bands. High RF output in excess of 100,000 microvolts. 400 cycle output approximately 15 volts. Net Price: \$49.95</p>	 <p>Model 48 VACUUM TUBE VOLTMETER</p> <p>All-purpose VTVM includes 7 DC (11 megohms input) and 7 AC ranges to 1,500 volts. Measures P-P to 4,000 volts. Resistance in 7 ranges to 1,000 megohms. Three-way probe for voltages and resistance included. Net Price: \$55.95</p>

NOW! A TOP-QUALITY LINE FROM **PRECISION** THAT EVERY SERVICEMAN CAN AFFORD!

In designing test equipment, Precision has always maintained a firm policy of quality first, price afterwards. Now, thanks to improved manufacturing techniques, we are able to offer a popular priced line which meets the same exacting standards of engineering that have made Precision a leader in the field of over a quarter of a century! This puts Precision Electronic

Test Equipment within the reach of virtually every radio technician, student and engineer. On this page, you'll find apparatus that meets your own specific requirements. And you'll find you can save time and do more jobs when Precision does the trouble-shooting. REMEMBER, ALL PRECISION TEST EQUIPMENT IS GUARANTEED FOR ONE FULL YEAR!

See these and PRECISION'S Industrial Test Instruments at your local electronics distributor.

<p>OTHER TOP ITEMS FROM THE NEW PRECISION LINE:</p> <p>Model CB-26 Resistance-Capacity-Ratio Bridge Net Price: \$79.95</p> <p>Model P-28 Battery Eliminator and Charger With Built-In Low-Ripple L/C Filter \$64.95</p> <p>Model RS-24 Regulated Power Supply \$99.95</p> <p>Model 1904 Decade Condenser \$29.95</p> <p>Model 1601 Decade Resistor/Divider \$29.95</p> <p>Model 1803 Condenser Substitution Box \$12.95</p> <p>Model 1702 Resistance Substitution Box \$15.95</p>	<p> Precision Apparatus Company, Inc., 70-31 84th Street, Glendale 27, N. Y.</p> <p>Please send me more information on the model numbers circled below:</p> <table border="0"> <tr> <td>650</td> <td>ES-150</td> <td>P-28</td> <td>1803</td> </tr> <tr> <td>G-140</td> <td>E-75</td> <td>RS-24</td> <td>1702</td> </tr> <tr> <td>ST-22</td> <td>48</td> <td>1904</td> <td></td> </tr> <tr> <td>IC-60</td> <td>CB-26</td> <td>1601</td> <td></td> </tr> </table> <p>Name _____</p> <p>Address _____</p> <p>City _____ Zone _____ State _____</p> <p>PE-11</p>	650	ES-150	P-28	1803	G-140	E-75	RS-24	1702	ST-22	48	1904		IC-60	CB-26	1601	
650	ES-150	P-28	1803														
G-140	E-75	RS-24	1702														
ST-22	48	1904															
IC-60	CB-26	1601															

FCC Report

(Continued from page 16)

destroyed by fire, earthquake, flood, or other natural disaster.

A third type of approved *expedite* has to involve "an immediate and urgent need to provide radio facilities in connection with national defense activities important to the country."

As stiff as these criteria are, however, the Commission does relent enough to issue quick, short-term, one-shot, non-recurring authorizations in connection with events of wide public interest, such as the search for and rescue of lost persons, boats, or airplanes, and for auto races, boat races, athletic events, parades, celebrations and political conventions. But the agency does *not* issue these authorizations for routine seasonal operations such as the installation and repair of air conditioners, the delivery of fuel oil, or the routine harvesting of farm products, where no emergency is involved.

What it all boils down to is this: don't ask for quick licensing action unless you are really *looking down the barrel*, because chances are you're not going to get it. Remember, in the time it takes the FCC to write you a letter to reject your rush-rush

request, about a dozen other applications could be processed.

If you do have a valid reason for an *expedite* of a pending application or for a special temporary authorization, you can make your request either by notarized letter or telegram. If you use a telegram, you have to follow it up with a notarized letter giving full details. In either case, you must state your reasons for thinking you should have preferred treatment. And be sure to give the Commission all essential details—such as eligibility and citizenship of the applicant, class of station involved, frequencies, number of transmitters, and other information called for on the CB application form.

Timber! Despite what you may have learned from your mother or Joyce Kilmer, the tree in your back yard is not a "natural formation"—in FCC parlance—and you can't hang your CB antenna on it more than 20 feet above ground, particularly when the limbs are bare and the Commission's field troops are about. This practice has apparently been bothering the FCC lately.

The latest word from the Commission on the subject (without regard to the back of your CB license) is that "no distinction can be made between a tree in its original location and one which has been reset as a *pole*



STEREO STEREO

NEW SONY TAPE DECK

Now, for less than the cost of a good record changer, you can add a versatile new dimension to your hi fi system.

■ The Sony 262-D tape deck has a 4 track stereo erase head and 4 track stereo record/playback head. Heads are wired to six output and input facilities for connection of external electronics to play and record four track stereo. This is the same quality mechanism used in the most expensive Sony Superscope tape recorders.

\$89⁵⁰

Other tape recorders in the remarkable Sony line include the dual track bantam at \$99.50, the Sterecorder 300, a complete portable stereo portable stereo system at only \$399.50, and the 262-SL parallel and sound-on-sound recorder at \$199.50. ■ For literature or nearest dealer, write: Superscope, Inc., Dept. F, Sun Valley, Calif.

SONY

SUPERSCOPE

The tapeway to Stereo


FREE!

LAFAYETTE

**340 PAGE
1962 Lafayette Radio Electronics
CATALOG # 620**

*"America's Hi-Fi &
Electronics Shopping Center"*

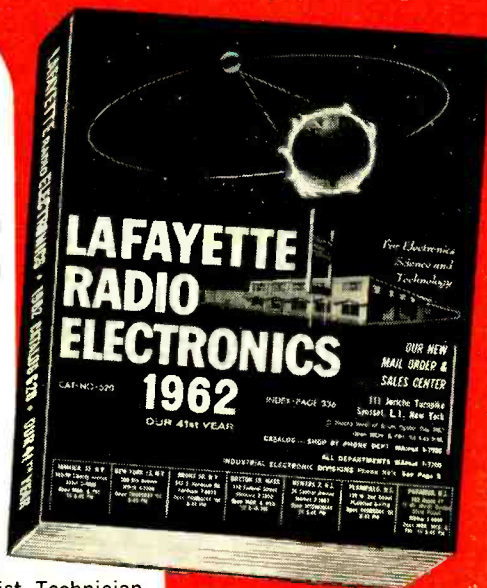Yours free for the asking — the biggest, best and most comprehensive catalog in the 41-year history of Lafayette Radio. Audiophile, Experimenter, Hobbyist, Technician, Engineer, Student, Serviceman, Dealer — you'll find what you want in this latest Lafayette catalog.



LARGEST STOCK SELECTION. Stereophonic Hi-Fi equipment, Citizens Band, Ham and Amateur equipment, Radio & TV parts, Optics, Industrial Supplies, and much more, including all the favorite name brands.

LAFAYETTE EXCLUSIVES. Featured are the famous Lafayette Kits . . . dollar for dollar the best value for your money today. You'll also see hundreds of Lafayette specials . . . available only from Lafayette. And, as always, **SATISFACTION GUARANTEED OR MONEY REFUNDED.**

LOWEST PRICES. You'll save money too with Lafayette's low, low prices. The lowest prices are always in the Lafayette catalog.

24-HOUR SERVICE. Quick, courteous service is your guarantee at Lafayette. Most orders are fully processed within 24 hours after receipt in the mail Order Division.

NEW EASY-PAY PLAN.
Now, **NO MONEY DOWN** . . .
up to 24 months to pay.



**COMPLETELY WIRED.
FULL SIZE TUBE TESTER
TE-15 \$19.95**



**SUPERHETERODYNE
COMMUNICATIONS RECEIVER
KY-200, Kit \$64.50
HE-10, Wired \$79.95**

**9-TRANSISTOR
CITIZENS BAND
"WALKIE TALKIE"
HE-29A each \$39.95
2-for \$78.88**



**10,000
OHMS-PER-VOLT
MULTITESTER
TE-10 \$9.95**



**TRANSISTORIZED
PORTABLE TAPE RECORDER
RK-125 \$29.95**



**FM STEREO
MULTIPLEX TUNER
LT-700 \$124.50**

**LAFAYETTE'S
NEW MAIL ORDER HEADQUARTERS
111 JERICHO TURNPIKE
(2 Blocks West of South Oyster Bay Rd.)
SYOSSET, LONG ISLAND, NEW YORK**



**Watch for Opening
Fall, 1961**

LAFAYETTE RADIO, Dept. IK1-1
P. O. Box 10 Syosset, N. Y.

Rush my FREE Lafayette 1962 Catalog 620

Please send me # _____, shipping charges collect.

I am enclosing \$ _____

Name _____

Address _____

City _____ Zone _____ State _____

news from hallicrafters



littlefone

CB-3 TRANSCEIVER

Only Hallicrafters offers 8-channel convenience and all these quality performance features.

The transmitter . . . output circuit matches 50 ohm antenna systems. Standardized CR23/U crystals (3rd overtone, series resonant) readily available. Output amplifier adjustable for max. legal input. 100% modulation on positive peaks. Series-tuned 2nd harmonic trap for excellent TV suppression.

The receiver . . . sensitivity less than 1.0 UV for 10 db. signal-to-noise ratio. Electronic squelch works on less than 6 db. signal strength change. 6 kc. selectivity. Image rej. 40 db. min. Audio output over 2 watts. Auto. noise limiter, series and shunt diodes. **\$149.50**

citizens band

Before you choose from the countless brands of CB equipment available, consider this fact: Nowhere in the field of communications is a manufacturer's experience, integrity and record of achievement more critical to performance and reliability than in citizen's band. Hallicrafters has built more precision communications equipment than *all other CB manufacturers.*

*the new ideas
in communications
are born at . . .*

h hallicrafters
Chicago 24, Illinois

Export Sales: International Div., Canada: Gould Sales Co.
Raytheon Mfg. Co., Waltham, Mass. Montreal, P.Q.

FCC Report

(Continued from page 20)


or *mast*" when it comes to your CB antenna.

The FCC notes that when it says "natural formation," it means "all permanent features of the natural terrane"—we lost a bet on the spelling of that one—"such as rocks, soil, etc. It does not include trees or any other form of vegetation which may be growing in or on such soil or rocks, nor does it include masonry or other additions such as dams and levees."

Amateur Reciprocity. Republican Senators Barry Goldwater (Arizona) and Andrew F. Schoepel (Kansas) have thrown a bill into the Congressional hopper providing for the reciprocity of amateur radio licensing.

Briefly, the measure would provide that the Commission "may, if it finds that the national security would not be endangered, issue licenses for the operation of an amateur station to certain aliens for any temporary period, not in excess of three years" provided that similar privileges are granted to U.S. citizens in the reciprocating countries. -30-

COMING NEXT MONTH

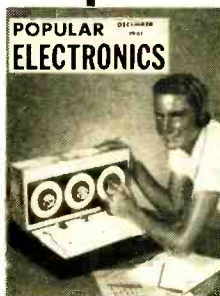

At Christmas time this year, parents will be buying educational electronic kits—not toys—for their budding young Edisons and Marconis. Our cover next month shows one of these new kits—G.E.'s analog computer, and an article explains some of the circuits and principles they are meant to teach.

(ON SALE NOVEMBER 28)

● SILENT SOUND

Does sound have any medical value? Can it clean dishes as well as help make better coffee? The answers are "Yes," and you'll learn why in next month's exciting feature story, "Successes of Silent Sound."

● THE WHIRLY-GIG

Here's a mystical motor that spins gaily on, day after day. Build one for yourself, then challenge your friends to explain "How It Works."

Earn Extra Money Soon

... while training at home for high-pay career or business of your own!

AMAZING PLAN FOR YOUR SUCCESS IN RADIO-TV-APPLIANCES and ELECTRONICS

Central will show you how to start making money soon . . . servicing AM-FM radios and television sets . . . repairing electrical appliances . . . building and installing electronic equipment in homes, factories, and business offices. Step-by-step, you'll learn how to get started in spare time at minimum cost; how to prepare for a bright future in servicing, audio, communications, broadcasting, or the gigantic electronic industry. Complete FCC license preparation included. High income, prestige, security, prosperity . . . all can be yours!

NO EXPERIENCE NEEDED!

You don't need high school diploma or previous knowledge of electronics to get started. Quick, low-cost home training for young and old. New illustrated lessons make learning easy. We supply equipment and *know how* you need to start making money soon. You learn by *doing*. You assemble useful, practical electronic projects—no incomplete "student" radios and testers—our kits meet commercial standards. Also recommended for citizen band and amateur radio operators, hi-fi and stereo enthusiasts, hobbyists, etc. Your personal pleasure and the savings you can make on home installations and repairs alone, make this course a profitable adventure. Keep your present job—set your own pace—add to your income—and find out how much fun Electronics can be!

New Frontiers Need You!



Cash in on growing demand for technicians in hundreds of exciting space-age fields: guided missiles, rocketry, outer space research and development, automation, nuclear power, computers, microwaves, radar, communications, oil field exploration, air traffic control, civil service, armed forces, etc. *Start now*. Get facts—mail coupon today for two FREE books!

NEW KITS!



You will build and keep this handy "transistorized" electronic and appliance tester that you'll use soon to start earning spare-time money. Many other practical and profitable electronic projects to choose from: 4 transistor portable radio—code oscillator—solar cell switch—RF signal generator—CB converter—oscilloscope—others! Fully described in our FREE 64-page catalog.



Central grad GLEN LEIRER, shown here, earned an attractive income from part-time Radio-TV Servicing. Now he's employed as a Computer Technician for RCA Service Co., Camden, N. J.

Over 50,000 Successful Graduates Since 1931!



"I averaged between \$60 and \$70 a month servicing radios and TV's part-time while taking my home study course. Plan to open my own shop soon." Student THEODOR SCHMIDT, Peshastin, Wash.



Central grads HOWARD EDMONDS & FLOYD CONKRIGHT are joint owners of EDCO FACTORY TV SERVICE CO., K. C., Mo., and RANCH MART TV & STEREO, Leawood, Kansas, have three service trucks, seven full-time employees.

Grad FRANK LEENKNECHT works in missile field for Convair Astronautics, San Diego, Calif., and as Transmitter Engineer for Station KDEO as a sideline.



RESIDENT TRAINING—Central also offers a full-time ECPD-Accredited Technical Institute program at its resident school in Kansas City, Mo., for qualified high school graduates. Details in FREE catalog.

FREE

FCC PREP BOOK

Profits from Electronics

We'll mail you FREE FCC License Prep Handbook that prepares you to pass the 3rd Class FCC Radiotelephone examination, and to qualify to operate radiotelephone transmitting stations used by airlines, police, railroads, emergency services, etc. You get FREE FCC Prep Book plus FREE 64-page catalog with facts about Central's practical electronics home study course.

NO OBLIGATION

TRADE THIS COUPON FOR 2 FREE BOOKS!

Central Technical Institute
1644 Wyandotte, Dept. PE-111A,
Kansas City 8, Mo.


(PLEASE PRINT)

NAME _____
ADDRESS _____
CITY _____
ZONE _____ STATE _____



Accredited Member
National Home Study Council

Central Technical Institute

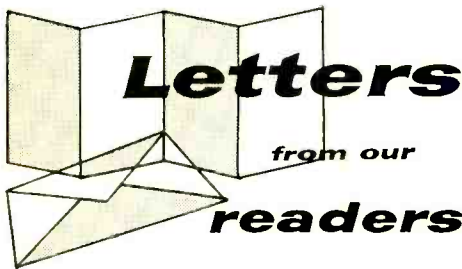

Letters

from our
readers

Codeless Technician Class?

■ We have just finished reading Mr. Sokol's suggestion in your August "Letters" column that the Technician code requirement be dropped. May we point out that perhaps 6Q048 and his friends without "auditory coordination" in reality lack the cerebral coordination to pass the simple Technician's code test. Without this test, any knucklehead who memorizes the small amount of required theory could operate on the already more than filled ham bands.

JIM KIRTLEY, K1SLK
DAVE EVANS, K1SLL
Ridgefield, Conn.

■ After reading Steve Sokol's letter, I am inclined to agree with him. Why not drop the code requirement for the people who, for some reason, can't learn code, while retaining the written test. The holder of this special license would be allowed to use phone—but not code. With this inducement,

many "rag-chewers" might be attracted away from the Citizens Band, leaving it free for those who would put it to the proper use.

KENNETH DONNELL, JR.
Kirkwood, Mo.

In a recent morning's mail, we received 12 letters disagreeing with Mr. Sokol's proposal that the code requirement for the Technician Class license be dropped—the message from readers Kirtley and Evans was one of the milder ones. Mr. Donnell, so far, stands alone in his support of the idea.

Help Wanted

■ I am a cardiac patient. Since I can only do light work, I must re-educate myself in a new field. I want to learn to repair appliances such as toasters, irons, mixers, electric roasters, stoves, etc., but I have no knowledge of the subject and must start from the very bottom. If you folks can recommend any suitable textbooks or other material, I would appreciate it.

RALPH BASLE
98 Old Bridge St.
West Springfield, Mass.

For a starter, you might contact the National Radio Institute, Appliance Division, Dept. D4J1, Washington 16, D.C.; they'll send you a free descriptive booklet on their correspondence course and a sample lesson. We hope, also, that some of our appliance-repairman readers will be able to help you out.

(Continued on page 28)



*How to buy
your first (or your last)
speaker system*

compare UNIVERSITY (in every price category) against all other brands.

UNIVERSITY
A Division of Line-Tempo-Foam, Inc.

Explore the totally different TMS-2—a remarkable all-in-one stereo speaker system. One cabinet! Only 30 inches wide! Thus, if you don't have room for two separate speaker systems, or if your decor doesn't permit same—the TMS-2 single cabinet stereo speaker system is the ideal problem solver.

How does the TMS-2 do it? Operating on the principle of the concert hall, where up to 90% of the sound you hear is reflected from the walls, the TMS-2 projects the sound to the sides . . . one side becomes Channel A, the other side, Channel B. Speaker spacing becomes unimportant . . . fully balanced stereo is had everywhere in the room . . . all with superb separation and uncanny depth. As a matter of fact, the TMS-2 is the only stereo speaker system which will work in a corner!

What's the secret? Well . . . there are five speakers operating as two complete 3-way systems. By utilizing the dual voice coil of the C12HC woofer, only one bass cabinet and woofer are required to handle the entire low frequency range of both stereo channels. The mid-range and highest frequencies of each channel are covered by an 8" cone speaker and a wide-angle horn-loaded tweeter . . . each with its own level control.

In two styles—Contemporary and Early American—the TMS-2 looks more like a fine piece of furniture than a speaker cabinet.

For complete information write:
Desk A-11, University Loudspeakers, Inc., White Plains, N.Y.



The Same School That Originated The RTS BUSINESS PLAN

...NOW
Proudly
Presents...

A SPECIAL COMPACT COURSE COVERING ALL THREE PHASES OF **ELECTRONICS**

The Entire Course Is Made
Up Of The Following:

- 35 LESSONS COVERING BASIC AND INTERMEDIATE ELECTRONICS
- 9 EQUIPMENT KITS COMPLETE WITH TUBES AND BATTERIES
- SOLDERING IRON
- 25 LESSONS COVERING THESE ADVANCED ELECTRONIC SUBJECTS:
 - Thyratron Tubes • Semiconductors • Electronic Symbols and Drawings • Voltage-Regulators • Electronic-Timers • Control Systems • X-Rays • Photoelectric Devices • Dielectric Heating • Geiger Counters • Pulse Circuitry • Clippers and Limiters • Multivibrators • Electronic Counters • Radar • Magnetic Amplifiers • Analog-Computers • DC Amplifiers • Digital Computers • Storage Systems • Input and Output Devices • Servomechanisms • Telemetering
- 60 EXAMINATIONS
- UNLIMITED CONSULTATION SERVICE
- KIT MANUALS
- DIPLOMA UPON GRADUATION

AND MUCH MORE...

BASIC • INTERMEDIATE • ADVANCED

DESIGNED FOR THE BUSY MAN OF TODAY

This is MODERN training for the MODERN man. You'll find no "horse and buggy" methods here. Every page of this streamlined course is devoted to important Electronics principles and practical projects. You'll be amazed how fast you grasp Electronics the RTS way. RTS has combined modern THEORY and PRACTICE to make this the finest training program of its kind available!

SATISFIES NOVICE, TECHNICIAN OR HOBBYIST

Whether you're new to Electronics or an old "pro," chances are you'll find this to be the ideal course for you. The novice will appreciate the completeness of the training. It starts with the most basic considerations, covering each important point thoroughly, yet concisely. The technician will enjoy the practical review of fundamentals and profit from the 25 advanced subjects covered.

RTS GIVES YOU "TOP MILEAGE" FOR YOUR TRAINING DOLLAR

The price quoted below buys EVERYTHING — there are no extras to pay for. RTS has gone "all out" to give you the best training value in America. Why pay hundreds of dollars for training such as we offer when it's available for this LOW PRICE? If you can find a better training bargain... BUY IT!

CAN BE COMPLETED IN MONTHS INSTEAD OF YEARS

Some students will complete this course with "Jet-Like" speed but we allow up to two years if your circumstances require it. You study at your own rate. You are ENCOURAGED but not pushed. You'll find the lessons professionally written but easy to understand. LET US SEND YOU ONE OF THESE LESSONS ALONG WITH YOUR CAREER BOOKLET SO YOU CAN SEE FOR YOURSELF. NO OBLIGATION!

COMPLETE
COST...
INCLUDES ALL KITS,
TUBES, BATTERIES, ETC.
\$125.00*

*TERMS ALSO AVAILABLE

AS LITTLE AS...

\$5.00 DOWN

\$5.00 PER MONTH

THE FIRST TRAINING KIT IS SENT
IMMEDIATELY UPON ENROLLMENT

DON'T LOSE OUT — FIND OUT!

RTS ELECTRONICS DIVISION Dept. PE111
815 E. ROSECRANS AVENUE LOS ANGELES 59, CALIFORNIA

Rush me full information by return mail. (Please Print)

Name _____ Age _____
Address _____
City _____ Zone _____ State _____

NO SALESMAN WILL CALL ON YOU!

RTS' Membership in
The Association of
Home Study Schools
is your assurance of
Reliability, Integrity and
Quality of Training.



RTS ELECTRONICS DIVISION
815 E. ROSECRANS AVENUE
LOS ANGELES 59, CALIFORNIA

Est. 1922



Rush
Coupon
for FREE
FACTS!

L 201A

BRING 'EM BACK ALIVE!



THE FIRST TRULY HIGH-QUALITY LOW-COST 3-WAY SPEAKER..ONLY \$29⁵⁰

It takes the most modern facilities in the industry to accomplish this:

The most spectacular loudspeaker value ever offered — a high-quality 3-way speaker at the cost of a coax!

And only Electro-Voice has these facilities, plus the production "know-how" . . . all under one roof! Every vital process from die-making to die-casting, from wire-flattening through automatic voice-coil winding, precision grinding, plating and polishing, to a completely automated belt assembly is under E-V's continuous personal control.

Introducing the new Wolverine LT12 — the latest addition to the famous Wolverine budget-priced line of quality speakers!

Imagine! A speaker that sounds better than speakers costing twice as much. With deep, rich bass and clean, clear treble from two cones, coupled by the famous E-V Radax principle. Plus smooth, peak-free highs that spread evenly throughout the room — without beaming — for outstanding stereo any-

where in the listening area . . . possible only with an E-V diffraction-horn compression-type tweeter.

The impressive list of LT12 "high-priced" features also includes a new ceramic magnet, plus edgewise-wound voice coil for highest efficiency . . . rugged die-cast frame to ensure perfect alignment of all moving parts . . . "deep-dish" bass cone design for higher power handling . . . long-throw suspension for minimum distortion . . . 3-position tonal balance switch that matches the LT12 to your acoustics . . . and a rich, jewel-like precision finish to all vital parts.


But, best of all, the LT12 is versatile: mounts in most high fidelity speaker enclosures, in the wall, ceiling, or even in a closet. And its wide dispersion makes placement far less critical than ordinary speakers — even for stereo!


See and hear the exciting new Wolverine LT12 at your nearby Electro-Voice/Wolverine high fidelity headquarters . . . today!

SPECIFICATIONS: Frequency response, 40 to 18,000 cps. Power handling capacity, 20 watts, program. Built-in crossover and 3-position balance switch. Impedance, 8 ohms. Size, 12 1/2 inches diameter, 6 inches deep. Shipping weight 15 pounds.


NOW, A COMPLETE LINE OF BUDGET-PRICED WOLVERINE SPEAKERS

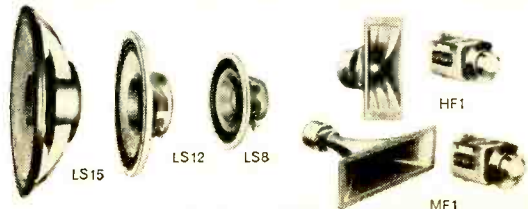- Model LS15 15" coax speaker, \$24.50
- Model LS12 12" coax speaker, \$19.50
- Model LS8 8" coax speaker, \$18.00
- Model HF1 Tweeter Step-Up Kit, \$20.00
- Model MF1 Mid-range Step-Up Kit, \$25.00



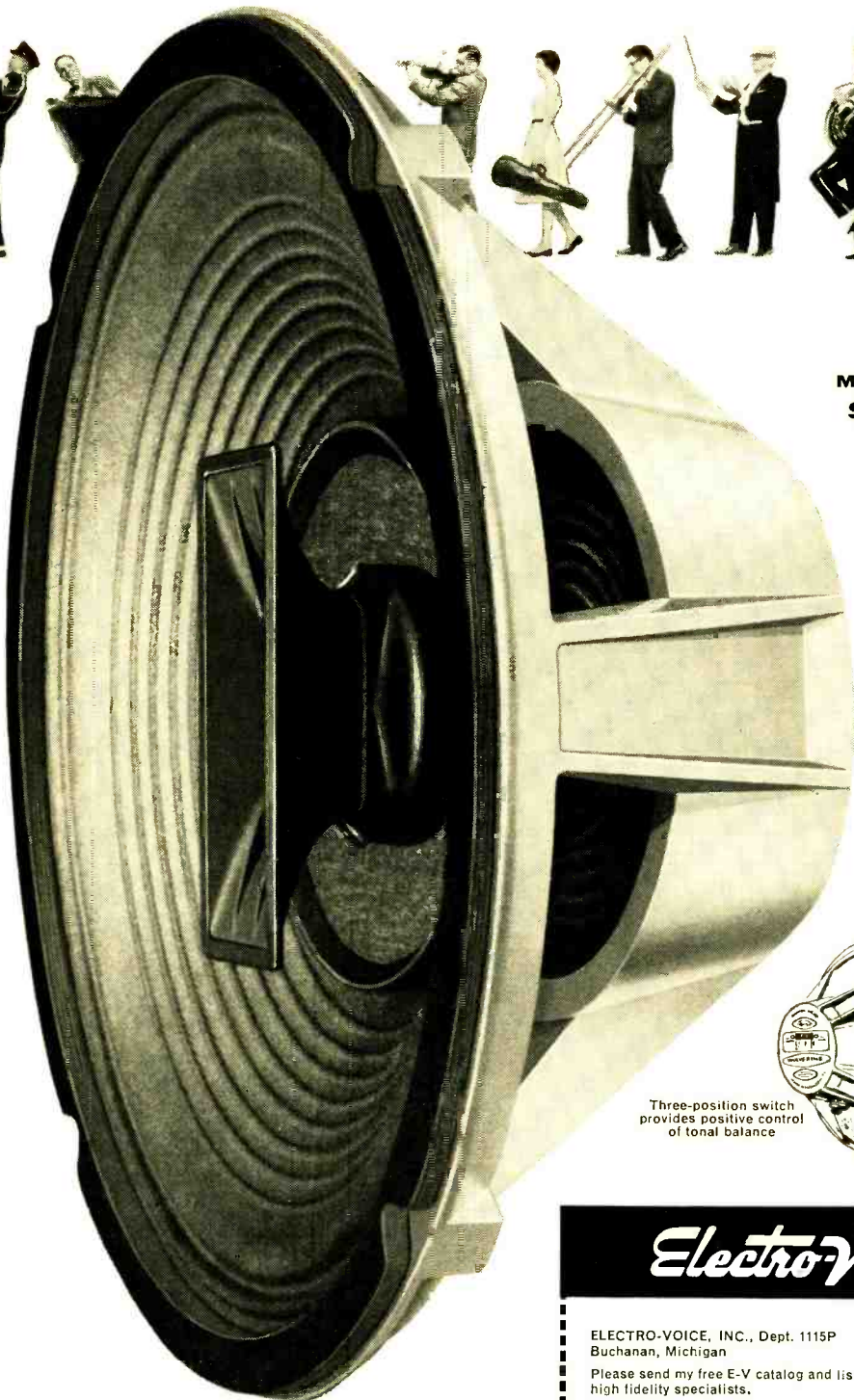

Model LT12
\$29.50

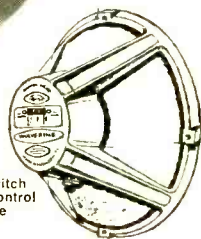

Three-position switch
provides positive control
of tonal balance

Electro-Voice[®]

ELECTRO-VOICE, INC., Dept. 1115P
Buchanan, Michigan

Please send my free E-V catalog and list of E-V/Wolverine
high fidelity specialists.

Name _____

Address _____

City _____ State _____

ELECTRO-VOICE, INC.

Consumer Products Division, Buchanan, Michigan

Letters

(Continued from page 24)

Metronome Calls Lobsters

■ I assembled Norman Latner's fine metronome circuit from the instructions in the June 1961 issue, and have been using it almost every day when practicing my guitar lessons. But recently I discovered another, quite different, use for the metronome—which might be of interest to some of your readers.

Taking a cue from the "Fish Caller" article in the same issue, I installed the metronome in a large (restaurant-size) mayonnaise jar—adding enough lead ballast so that it would barely float—



and took it along on a SCUBA diving trip. As I suspected, the metronome showed promise as a device for calling lobsters out of their holes.

Unfortunately, my experiments are temporarily

at a standstill because, at a depth of about 25 feet, the water pressure crushed the jar. This catastrophe had a somewhat dampening effect on the circuit oscillations.

JAMES R. WETHERBY
Long Beach 3, Calif.

This is a startling use, we must admit, for the transistorized metronome. Your idea may replace the lobster pot, Jim, but don't you think you'll have trouble practicing your guitar under water?

Solenoid for Coin Toss

■ Your magnetic coin tosser ("Heads . . . or Tails?" June, 1961) interested me very much, so I decided to build one for the family. Instead of winding my own solenoid, though, I managed to locate an excellent commercial substitute. It's a Guardian intermittent-duty model (Type 1A) and sells for only \$2.35, including plunger.

MICHAEL KAHANE
Brooklyn, N.Y.

It sounds as though you took the easy way out, Michael. Like to tell us how far your model tosses coins?

Radiation Detector Improvement

■ I'd like to suggest a minor improvement for my "Radiation Detector" (January 1961 issue of POPULAR ELECTRONICS). Placing a 1-megohm, 1/2-watt resistor in series with V1's positive lead will prevent the possibility of excessive pulse cur-

POLY-COMM "N"

WITH THE NUVISTOR RF STAGE




Steel encased
and completely weather-proofed

For matchless **CB RANGE**

Look inside the Poly-Comm "N". See why you get matchless performance! Nuvistor front end; Sensitivity—better than .1 microvolt for 6 db S/N, readable to .04 uv; dual conversion; 11 tubes and 7 diodes give you eighteen tube performance, unlike the usual 7 or 8 tubes found in other transceivers at the same price; sixteen tuned circuits for 60 db adjacent channel rejection; improved Noise Limiter; New steel encased ceramic mike and New audio system for sparkling modulation; better than 3 watts power output and 4 watts audio output.

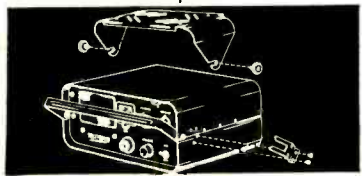Write for specifications **\$189⁵⁰** User Net



POLYTRONICS LAB inc.

Clifton, N.J. Phone: 772-1334



plink, plank, plink

Who can't play the piano? It's easy! Just pounding on the keyboard sounds like celestial music when you're small.

These simple joys fade fast. But, fortunately, life has its compensations. For the more discriminating ears of adults, there's Audiotape.

Make your next recording on Audiotape. Then listen. Audiotape has more clarity and range, less distortion and background noise than others. Make it your silent (but knowledgeable) partner in capturing everything from birthday party hi-jinks to the beauty of Brahms.

Remember: if it's worth recording it's worth Audiotape. There are eight types... one exactly suited to the next recording you make.



audiotape
TRADE MARK

"it speaks for itself"

AUDIO DEVICES INC., 444 Madison Ave., New York 22, N. Y.
Hollywood: 840 N. Fairfax Ave., Chicago: 7321 N. Hamlin Ave., Skokie, Ill.

Letters

(Continued from page 28)


rents at high count rates. The addition of this resistor makes no noticeable change in the sensitivity of the instrument.

J. E. PUGH, JR.
Menominee, Mich.

Pioneer Radio Broadcaster

■ One of the main contenders for the honor of having made the first public radio broadcasts on a regular daily schedule is Station KDKA at Pittsburgh, Pa. This station began its operation by broadcasting the Harding election returns in November, 1920. I believe, however, that I have a prior claim.

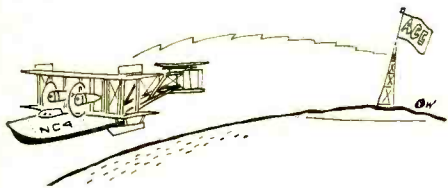In late 1918, I founded the Precision Engineering Association in Cincinnati, Ohio. We later in-



corporated as the Precision Equipment Company and began to manufacture and sell radio receivers and transmitters. Our trade name was "Ace," and we were licensed under the Armstrong regenerative patents.

With a c.w. transmitter which I built, the only one in the midwest at the time, I communicated with the NC-4 on her famous trip around the world. Copies of messages sent by Commander Read and another officer (I believe his name was Cirowich) are still in my possession.

It wasn't much of a step to adapt the c.w. rig to transmit voice and music, and this was soon done. In September, 1919, I got the call letters 8XB, erected an umbrella antenna on the roof, and went on the air.

In 1926 the Cincinnati Post appointed a Mr. Cooper and a Mr. Temple to check my claims against those of KDKA and some other stations. Their published findings gave the Precision station a lead of many months.

If this letter should be seen by Mr. Breck, who was my valuable assistant, I wish he would write to me. I'd also like to hear from any other old-timers who may still be around.

THOMAS E. NEW
651 Copeland Court
Santa Monica, Calif.

We can't resolve your disagreement with KDKA, Mr. New, but thanks for giving us such an interesting picture of your early radio activities. Our edition of the Encyclopaedia Britannica, incidentally, merely states that KDKA was "one of the earliest and most successful" commercial broadcasters.

Space-Saver Satisfactory

■ I'm in the process of putting together a component hi-fi system and, since my budget is limited, I

decided to try the "Space-Saver Speaker System" (July 1961 issue). A few evenings ago I hooked the system to my amplifier and was gratified by what I heard. Although some of the materials cost a little more than I anticipated, I'm quite happy with the outcome.

DICK SEDDON
Chariton, Iowa


Experienced Correspondent Wanted

■ I have just finished a course in electronics and plan to open a radio and TV service shop. As the experience of someone established in this business would be quite helpful to me, I'd like to correspond with an American serviceman. Advice on equipment, materials, and other problems would be very much appreciated.

INDUS MEMBER
Apdo. Postal 21
Tlalneapantla, Mex.
Mexico

Convertible Confusion

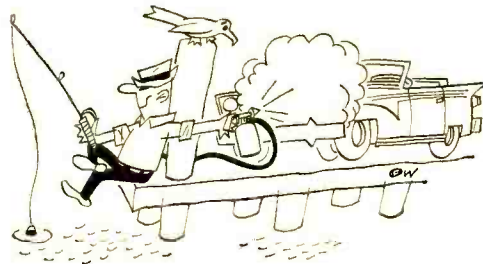■ Carl and Jerry were pretty quick to find the cause of the "floating fish" in the August issue of P.E., but they failed to explain the real mystery,



namely, how did J. P. Sellers' "brilliant red convertible" (p. 103) change into a "yellow convertible" (p. 108) overnight?

BOB DUPWE
Russellville, Ark.

We can't explain it either. Maybe Mr. Sellers (who is obviously rich enough to throw around his dough) has a stable of cars. Or, on the other hand, he may occupy himself by painting cars when he's not busy fishing.

-30-


HOW TO ORDER BACK ISSUES

Every month POPULAR ELECTRONICS receives many requests from readers who would like to know how to order back issues. Some readers want to obtain particular articles they have missed, while others want to complete their own back-issue files.

If you would like to order a specific issue of P.E., address your inquiry to:

Circulation Department
POPULAR ELECTRONICS
Ziff-Davis Publishing Co.
434 S. Wabash Ave.
Chicago 5, Ill.

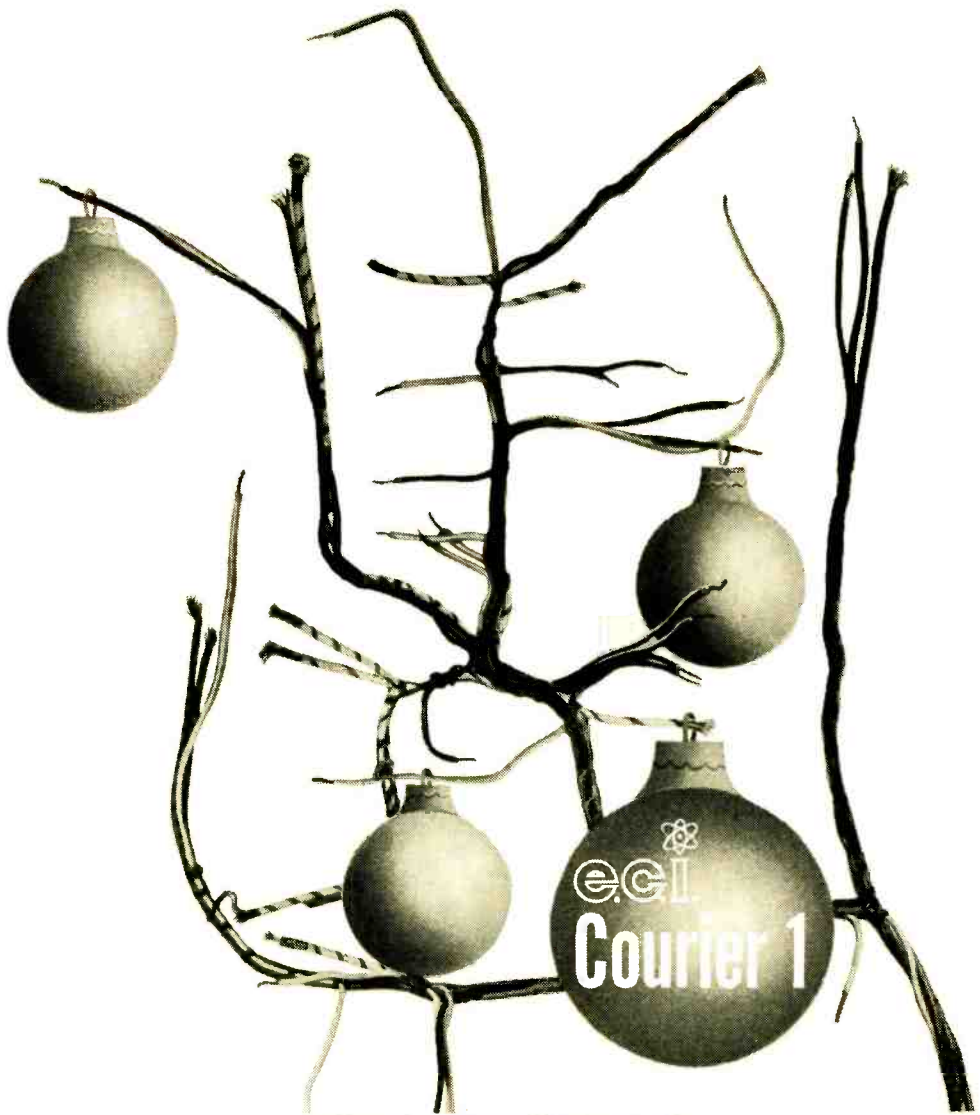Enclose 35 cents for each copy of issues less than six months old, 40 cents for each copy of older issues. Be sure to state the month and year of the issue(s) you want. In the event a requested issue is no longer in stock, your money will be returned.



CB TREE? It's actually the e.c.i. Courier 1 hand wired harness that ties together its five individual segments into a unitized chassis for simple installation, use and maintenance. And that's only part of the e.c.i. Courier 1 quality story. Think of every conceivable feature you need and want in a CB transceiver that will still get out more than 3 watts . . . e.c.i. Courier 1 has them. See for yourself.

write for free brochure

\$189.50

Slightly higher west of Rockies

- TRIPLE CONVERSION
- 12 CHANNEL TRANSMITTING
- FIXED & TUNABLE DRIFT-FREE RECEIVING
- BUILT-IN NOISE LIMITER & SQUELCH
- ELECTRONIC SWITCHING (no relays)
- FULLY MODULATED (100%)
- BUILT-IN "S" & "RF" METER
- LOWEST NOISE FRONT END
- MOBILE OR BASE (117 V. and 12 V.)
- ENTIRE UNIT SLIDES OUT ON TRACKS




electronics communications, inc. 325 no. macquesten pkwy. mt. vernon, n.y.

POPtronics Bookshelf

ESSENTIALS OF RADIO-ELECTRONICS, Second Edition by Morris Slurberg and William Osterheld

In a careful revision of the original edition, the authors use a minimum of mathematics to present an overall coverage of the principles of vacuum tube and transistor operation. Basic circuits are shown and their application to audio systems and radio receivers is discussed. Three chapters are devoted to transistors, and another one covers the principles and operation of FM receivers. An entirely new

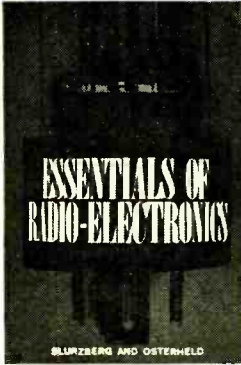


chapter is devoted to equipment and procedures used to check receiver circuits.

Published by the McGraw-Hill Book Co., Inc., 330 W. 42nd St., New York 36, N.Y. 716 pages. Hard cover. \$10.00.

INDUSTRIAL CONTROL ELECTRONICS by Matthew Mandl

This volume covers all of the fundamental principles and practices of modern electronics control circuitry. Following a summary and review of control signals, solid-state devices, amplifiers and oscillators, the author discusses thoroughly the more advanced materials used in industrial electronics, including reactors, generators, power supplies, transducers, motors, servo-mechanisms, and magnetic amplifiers;

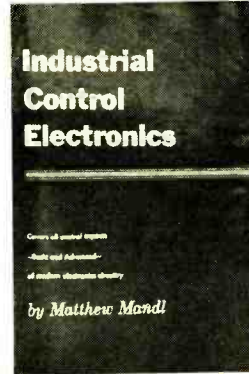

MAKE YOUR INTEREST IN ELECTRONICS PAY OFF

Get
Into . . .

The HIGH PAY - PRESTIGE Field of TECHNICAL WRITING

HERE'S WHAT YOU GET . . .

- 50 Meaty Lessons
- Over 110 pages on Electronics
- Covers ALL Military Specifications
- Real, practical writing projects
- Full consultation privileges
- Many manuals, charts and diagrams
- Low tuition terms
- Employment Assistance
- Close, personal supervision
- AND MUCH, MUCH MORE . . .

ELECTRONICS WRITERS NEEDED NOW—ATWS will train you at home at low cost for a profitable career in TECHNICAL WRITING. Thousands needed in all areas. Get in on the ground floor of this fascinating new field. ATWS offers training specifically designed for the needs of industry. Course includes everything you need to become a top-notch Tech Writer.

YOU ARE JUST A STEP AWAY FROM TOP PAY—Yes, with your present interest in Electronics, you're just a step from the BIG MONEY. Technical Writing is one of the highest paying fields NOT requiring college training. It's tailor-made for YOU—but you must ACT NOW.

THIS COUPON CAN BE YOUR PASSPORT TO SUCCESS
Fill in your name and address and rush coupon for full information. We will prove to you that we can train you without interfering with your present income or job.

CAREER BOOK AND SAMPLE LESSON

TRAINING AMBITIOUS



MEN FOR INDUSTRY

American Technical Writing Schools, Inc.
5504 Hollywood Blvd.
Hollywood 28, Calif.

American Technical Writing Schools, Inc. Dept. PE-11
5504 Hollywood Blvd., Hollywood 28, Calif.

Please RUSH full particulars,

Name _____ Age _____

Street _____

City _____ Zone _____ State _____

**BOTH
FREE**

NO SALESMAN WILL CALL ON YOU

BROWNING LABORATORIES ADDS MOBILE UNIT TO CB LINE

Browning Laboratories, Inc., Laconia, N.H., has introduced a new mobile transceiver to complete its line of Citizen's Band radio equipment.

The new Browning unit is known as the Mobilaire and utilizes the same advanced circuitry that has made the Browning S-NINE Transmitter one of the most popular base station units on the market. The receiver circuit has all the Browning features that insure sharp, interference-free reception, even from distant stations. Only high quality, U.S. made components are used in all Browning radio equipment.

Introduction of the Mobilaire unit was brought about principally by demand from present Browning base station equipment owners who asked for a mobile unit with the same basic specifications and features.

Priced at \$159.50, Mobilaire is available directly from Browning Laboratories on a "satisfaction guaranteed" basis. Four convenient purchase plans are available and a 5% discount is allowed for cash with order.

All requests for literature and information should be forwarded to Browning Laboratories, 101 Union Avenue, Laconia, N.H. — *Advt.*



Mobilaire
Transceiver

\$159.50

To complete the finest CB radio communications system available, Browning brings you Mobilaire, the mobile transceiver with the same quality components as Browning's base station equipment.

Now you can take Browning quality with you wherever you go . . . car, boat, other vehicles.

ORDER DIRECT FROM BROWNING AND SAVE!

Send for free
literature
and complete
specifications



browning

Browning Laboratories, Inc. 101 Union Ave. Laconia, N.H.



R-2700 Receiver
\$149.00

S-NINE
CB Transmitter
\$119.50

The Greatest Pair On The Air . . . Browning CB Radio Base Station Equipment

Here's the unbeatable combination of the airways you've heard so much about. The Browning R-2700 Citizen's Band base station receiver that builds up weak signals and lets you hear distant stations where other receivers fade out.

And, the revolutionary S-NINE CB transmitter that allows full power transmissions on all channels and introduces new features never previously utilized in CB communications.

Satisfaction Guaranteed. Four Convenient Purchase Plans


Write today for free literature and specifications. No obligation.

Browning Laboratories, Inc.
101 Union Ave. Laconia, N.H.



browning

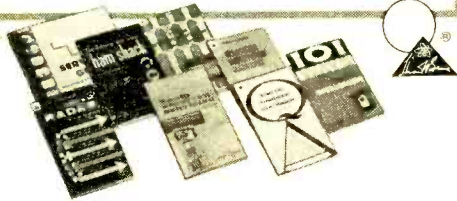LATEST SAMS BOOKS FOR EVERYONE IN ELECTRONICS



USE THIS HANDY ORDER FORM

- ABC's of Radar.** Comprehensive, easy-to-follow explanation of radar—principles, how it works, uses, types of radar systems, microwave, antenna systems, receivers, indicating systems, tuners and modulators, etc. 112 pages. Order **ABR-1, only**..... \$1.95
- Building Up Your Ham Shack.** Tells what you need to get a ham station on the air, and how you can upgrade your present station at minimum cost. Describes both factory-built and do-it-yourself gear. Covers transmitters, receivers, antenna systems, station arrangement, test and measuring equipment, etc. 128 pages. Order **NHP-1, only**..... \$2.50
- TV Servicing Guide.** Quick reference guide shows how to apply proper troubleshooting procedures based on analysis of symptoms, illustrated by picture tube photos. Includes troubleshooting and servicing hints for locating and eliminating troubles. 132 pages. Order **SGS-1, only**..... \$2.00
- Radio Receiver Servicing.** John T. Frye's down-to-earth book on how to really repair radios. Includes transistor sets and printed circuits. Has separate chapter on each type of trouble, and tells how to overcome it. 224 pages. Order **RS-2, only**... \$2.95
- Tube Substitution Handbook.** Latest edition—over 5,234 direct substitutions—2,759 for 1,687 receiving types; 224 industrial and 602 European substitutes for American receiving types; 513 American for European types; 465 picture tubes with 1,136 substitutions. Order **TUB-3, only**..... \$1.50
- Transistor Substitution Handbook.** Over 7500 direct substitutions; includes basing diagrams, polarity indications and manufacturers for over 3100 types; shows over 700 American replacements for Japanese transistors; plus semiconductor diode and rectifier directory. Order **SSH-2, only**..... \$1.50
- Second-Class Radiotelephone License Handbook.** Complete study course for elements I, II and III of the FCC exams. Helps you earn the license you need to repair (and in some cases to operate) communications equipment, including 2-way mobile radio. Order **QAN-1, only**..... \$3.95
- 101 Ways to Use Your Oscilloscope.** Shows you how to get the most from this versatile instrument, how to make required connections, how to test properly, how to evaluate results. 180 pages. Order **TEM-2, only**..... \$2.50



FREE! Ask for Free Sams Index to PHOTOFAC —the world's finest circuit data on more than 44,000 TV, radio, hi-fi, recorder models and related equipment. Send coupon below!

HOWARD W. SAMS & CO., INC.

Order from any Electronic Parts Distributor, or mail to Howard W. Sams & Co., Inc., Dept. L-91, 1720 E. 38th St., Indianapolis 6, Ind.

Send books checked above. \$_____ enclosed

Send Free Sams Index Send FREE Book List

Name _____

Address _____

City _____ Zone _____ State _____

IN CANADA: A. C. Simmonds & Sons, Ltd., Toronto 7 (outside U.S.A. priced slightly higher)

Bookshelf

(Continued from page 32)

commercial counting and indicating equipment is also analyzed. The mathematical treatment is kept to a minimum and review questions are provided at the end of each chapter.

Published by Prentice-Hall, Inc., Englewood Cliffs, N. J. 344 pages. Hard cover. \$10.65.



STEREOPHONIC SOUND, Second Edition

by Norman H. Crowhurst

Stereophonic Sound was originally written in the pioneering days of stereo, but this new edition contains the latest advances in the field. Comprehensive information has been included on the 45/45 disc (the now-accepted standard), and stereo tape and playback units are also thoroughly covered. An entirely new chapter helps the reader evaluate conflicting claims of component manufacturers when selecting a stereo system, and discusses the possibilities and pitfalls of converting existing monophonic systems to stereo.

Published by John F. Rider Publisher, Inc., 116 W. 14th St., New York, N. Y. Soft cover. 144 pages. \$2.90.



1961 REGISTRY OF BUSINESS AND MISCELLANEOUS RADIO SYSTEMS

edited by Ethel V. Sleeper

Compiled from the official license files at Washington, D.C., this revised edition contains data on radio transmitters operated by business, manufacturing, telephone maintenance, common carrier, and radio paging organizations. Part I lists the licensees by company name and gives addresses, call letters, number of mobile and fixed transmitters, operating frequencies, and make of equipment used. Part II, a listing by fre-

(Continued on page 38)

Always say you saw it in—POPULAR ELECTRONICS

NOW!
at a price
you can afford!


MAKE MORE MONEY in ELECTRONICS TELEVISION-RADIO

**BETTER...MORE COMPLETE...LOWER COST...
WITH NATIONAL SCHOOLS' SHOP-METHOD
HOME TRAINING!**

BETTER... Training that is proved and tested in Resident School shops and laboratories, by a School that is the **OLDEST** and **LARGEST** of its kind in the world.

MORE COMPLETE... You learn **ALL PHASES** of *Television-Radio-Electronics*.

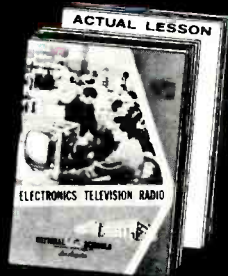LOWER COST... Other schools make several courses out of the material in our **ONE MASTER COURSE**... and you pay more for less training than you get in our course at **ONE LOW TUITION!**



These
two FREE books will
show you how!

TOP PAY...UNLIMITED OPPORTUNITIES LIFETIME SECURITY CAN BE YOURS!

You are needed in the Television, Radio, and Electronics industry! Trained technicians are in growing demand at excellent pay—in **ALL PHASES**, including Servicing, Manufacturing, Broadcasting and Communications, Automation, Radar, Government Missile Projects.

NATIONAL SCHOOLS SHOP-METHOD HOME TRAINING, with newly added lessons and equipment, trains you in your spare time at home, for these unlimited opportunities, including many technical jobs leading to supervisory positions.

YOU LEARN BY BUILDING EQUIPMENT WITH KITS AND PARTS WE SEND YOU. Your National Schools course includes thorough Practical training—**YOU LEARN BY DOING!** We send you complete standard equipment of professional quality for building various experimental and test units. You advance step by step, perform more than 100 experiments, and you build a complete TV set from the ground up that is yours to keep! A big, new TV picture tube is included at no extra charge.

EARN AS YOU LEARN. We'll show you how. Many students pay for their course—and more, while studying.

**GET THE BENEFIT OF OUR
OVER 50 YEARS EXPERIENCE**

APPROVED FOR
GI TRAINING



ACCREDITED
MEMBER



NATIONAL TECHNICAL SCHOOLS
World-Wide Training Since 1905

Write to Dept. R2G
4000 So. Figueroa Street
Los Angeles 37, California

YOU GET...

- 19 Big Kits—**YOURS TO KEEP!**
- Friendly Instruction and Guidance
- Job Placement Service
- Unlimited Consultation
- Diploma—Recognized by Industry
- **EVERYTHING YOU NEED FOR SUCCESS!**

**IMPORTANT
SEE OTHER SIDE**

You get all information by mail... You make your own decision... at home! **NO SALESMAN WILL CALL**

SEND FOR FREE FULLY-ILLUSTRATED BOOK AND ACTUAL LESSON TODAY. Your own copy of "Your Future In Electronics-Television-Radio" will be mailed to you at once. No salesman will call; there is no obligation. Cut out card along dotted lines, fill in and rush air-mail today!
NO POSTAGE NECESSARY.

CUT OUT AND MAIL THIS CARD TODAY

Yes, I want to make more money in Electronics-
TV-Radio. Send me your **FREE Fully-Illustrated
Opportunity Book and Actual Lesson** today.



RUSH AIR MAIL—NO POSTAGE NECESSARY

Name _____ Age _____


Address _____

City _____ Zone _____ State _____

Check here if interested only in Resident Training at Los Angeles. R2G
Veterans: Give date of discharge _____ A B

NO SALESMAN WILL CALL; NO OBLIGATION ON YOUR PART

DON'T BE HALF-TRAINED

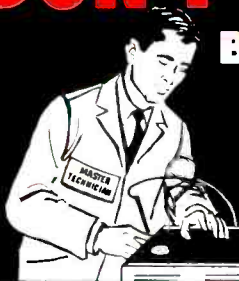

Be a MASTER TECHNICIAN in ELECTRONICS-TV-RADIO

Only N.T.S. offers you ALL 8 PHASES in
ONE MASTER COURSE

SUCCESS IS THEIRS; IT CAN BE YOURS TOO!



When I enrolled with N.T.S. last November, I was trained as a Seismograph

Observer. I was promoted to that job on May 1st of this year. With your school and my practical work in the field, my superiors recognized that I was capable of handling the job of Seismograph Recording. My superiors highly praise your school. The day I enrolled started me off to success.

Edgar Wesatzke

As field director of Berean Mission Inc., I have complete charge of our radio work.

With the expert advice and training I am receiving from you I can do my own repairs on our recorders and P.A. systems, besides keeping our radios going. My training from N.T.S. helps keep us on the air. I feel privileged to be a member of such a fine institution.

Rev. Enoch P. Sanford



Thanks to N.T.S. I have a business of my own right in my home. I am still in the

Air Force but I have paid for all my equipment with money earned servicing TV sets. Yes, N.T.S. gave me my start in television.

Louis A. Tabat

I have a TV-Radio shop in Yorkville, Illinois, about 4 miles from my home, and it

has been going real good. I started part-time but I got so much work that I am doing it full-time. Thanks to National Technical Schools.



Alvin Spera

ALL 8 PHASES IN ONE MASTER COURSE

**PHASE 1
TELEVISION**
INCLUDING COLOR TV
90% of homes have at least one set. Color TV is becoming more popular daily. TV Stations grow in number, need technicians. Maintenance and repair offer big opportunities.

**PHASE 5
FCC LICENSE
PREPARATION**
FCC License holders have a wide range of top jobs open to them. FCC License now a requirement for most Communication jobs.

**PHASE 2
RADIO—AM & FM**
Radios in homes, cars, schools, all need expert upkeep. Stations expand as FM becomes popular. Now transistors boom entire field.

**PHASE 6
RADAR AND
MICROWAVES**
These are the communications systems of the future, already used in tracking and contacting satellites.

**PHASE 3
ELECTRONICS**
Computers, Data-Processing machines, Electronic Controls, Guided Missile Systems are new fields where Electronics play a vital role.

**PHASE 7
AUTOMATION
& COMPUTERS**
Automation and Computer electronics are the new tools of industry and commerce. Skilled Technicians in these fields are in great demand at top pay.

**PHASE 4
SOUND SYSTEMS**
New popularity of Hi-Fi-Stereo, as well as industrial sound systems and business intercoms make this a highly specialized and important field.

**PHASE 8
BROADCASTING &
COMMUNICATIONS**
In the entertainment industry, or in commerce, communications and broadcasting have great importance. Installation and maintenance of equipment requires trained technician know-how.

SEE OTHER SIDE

BUSINESS REPLY MAIL
NO POSTAGE STAMP NECESSARY IF MAILED IN THE UNITED STATES

VIA AIR MAIL

FIRST CLASS

Permit No. 3087

Los Angeles, Calif.

— POSTAGE WILL BE PAID BY —

NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905

4000 So. Figueroa Street

Los Angeles 37, California

RESIDENT TRAINING
AT LOS ANGELES

If you wish to take your training in our famous Resident School in Los Angeles—the oldest and largest school of its kind in the world—check special box in coupon.



Approved for GI Training

NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905

Address correspondence to Dept. R2G

4000 So. Figueroa Street

Los Angeles 37, California

National Technical Schools also offers complete Home Study Training Programs in Auto Mechanics & Diesel, and Air Conditioning-Refrigeration-Electrical Appliances. For information and Free Book write the School, Department RDC, stating course desired.

Now you can build almost any kind of electronic device!



Here are the ABC's of 50 vacuum-tube circuits for electronics experimentation and project construction—all fully diagrammed, complete with parts list.

HOW many times have you wanted a diagram of a basic vacuum-tube circuit which you could use as a guide in building hi-fi components, receivers, transmitters, intercom systems, test equipment and other electronic gear? At last, in one book, you can find all the basic diagrams, schematics and other vital information on vacuum tubes and their circuits essential for such projects!

You'll Become An Expert On All Types of Vacuum Tubes

Beginning with the Edison effect (the birth of the diode), Julian M. Sienkiewicz, Managing Editor of Popular Electronics, leads you right up to the multi-element vacuum tubes used in everyday circuits. The first four chapters are devoted to the operation of diodes, triodes, tetrodes, and pentode and beam-power tubes. Chapter five covers construction practices, tools, and test equipment, along with workshop hints that will be a real boon to all who want to get the most out of their equipment. Chapter six contains a collection of fifty vacuum-tube circuits that gives you a basic library of useful circuits for quick and trouble-free reference.

One hundred vacuum-tube schematics, plate-characteristic curves, simplified diagrams, test circuits and other selected illustrations supplement the informative text to make this book one of the most useful and invaluable manuals for your electronic experiments and hobby projects.

192 pages, 100 illustrations \$4.95

SEE YOUR ELECTRONICS PARTS JOBBER OR BOOKSELLER OR USE COUPON BELOW!

PARTIAL CONTENTS:

DIODE VACUUM TUBES. Emission—Diode Operation—Rectification Power—Supply Filters—Detection (AM and FM). **TRIODE VACUUM TUBES.** Triode Operation—The Triode Test Circuit—Control—Triode Characteristics—Plate Characteristic Curves—Plate Resistance—Amplification Factor. **TRIODE AMPLIFIERS.** Load Lines—Operating Point—Cathode Bias—Cathode Load Lines—Signal Amplification—Signal Inversion—Voltage Gain—Computing Voltage Gain—Distortion. **MULTI-ELEMENT TUBES.** Miller Effect—Tetrodes—Pentodes—A.C. Plate Resistance—Transconductance—Amplification Factor—The Pentode Voltage Amplifier—Operating Point—Cathode Bias—Distortion—Beam-Power Vacuum Tubes—Audio Output Stage. **CIRCUIT CONSTRUCTION HINTS.** Checking Components—Fixed Resistors—Capacitors—Transformers and Coils—Vacuum Tubes—Where To Buy—Test Equipment—Vacuum Tube Voltmeter—Oscilloscope—Signal Generators—Tools—Soldering—Chassis Construction—**BASIC VACUUM TUBE CIRCUITS.**

ELECTRONICS BOOK SERVICE

One Park Avenue
New York 16, N. Y.



Please send me VACUUM-TUBE CIRCUITS FOR THE ELECTRONIC EXPERIMENTER for a free 7-day trial examination. I understand that if I am not completely satisfied, I may return the book and owe you nothing. Otherwise, I will remit \$4.95 plus small charge for postage, packing and handling. Same return privilege and prompt refund guaranteed!

NAME _____
(please print)

ADDRESS _____

CITY _____ ZONE _____ STATE _____

EF627

CASH FOR YOU-



Electric APPLIANCES

Learn at Home • \$3 to \$5 an Hour
Spare Time, Full Time • Be Your Own Boss

FREE BOOK tells about profitable business you can run — right at home. Repair Electric Appliances, using simple tools. Pays \$3-\$5 an hour!

CASH IN ON THIS BIG BOOM 400 MILLION Appliances are in American homes right now. People need them fixed. You make good money doing it. In your basement, garage, even your kitchen.

QUICK WAY TO GET STARTED
For less than 20¢ a day our

easy, pictured instruction — backed by 45 years of success in home-training — prepares you for top earnings. Earl Reid of Thompson, Ohio says: "Made \$510 in one month spare time." At no extra charge you get Appliance Tester, too. Finds trouble-spots, checks your work. Get your **FREE** Book and **FREE** Sample Lesson! Mail coupon below, letter or post-card, now.

NATIONAL RADIO INSTITUTE, Appliance Div.
Dept. D4M1, Washington 16, D. C.
Send **Free** Book, **Free** Appliance Repair Course Lesson. Am interested in:
 Spare Time Earnings My Own Business
 Better Job
Name.....
Address.....
City.....Zone.....State.....
Accredited Member National Home Study Council



Bookshelf

(Continued from page 34)

quencies, gives the locations of fixed transmitters, headquarters of the mobile units, class of service, and call letters.

Published by *Communication Engineering Book Co., Radio Hill, Monterey, Mass. 184 pages. Soft cover. \$5.00.*



MOST-OFTEN-NEEDED 1962 TELEVISION SERVICING INFORMATION

compiled by M. N. Beitman

A collection of factory-prepared data for all popular 1962 TV sets, this manual is designed to simplify servicing and adjustment. Double-page schematics, alignment data, and printed-board views are included, as well as recommended changes, waveforms, and voltage charts.

Published by *Supreme Publications, 1760 Balsam Rd., Highland Park, Ill. 192 pages. Soft cover. \$3.00.*

New Catalogs Available

You can keep informed of the latest equipment, parts, and prices with free 1962 catalogs now available from Lafayette Electronics, Allied Radio, and Radio Shack. For 340-page Catalog 620, write Lafayette Radio Electronics Corp., 165-08 Liberty Ave., Jamaica 33, N.Y. The Allied 444-page Catalog 210 is obtained from Allied Radio, Dept. 201-K1, 100 N. Western Ave., Chicago 80, Ill. "The Shack" will send along a copy of its 336-page "consumer" catalog if you drop a line to Radio Shack, 730 Commonwealth Ave., Boston 17, Mass.

Kit builders will want to have the latest Heathkit and EICO catalogs. Heathkit's comprehensive 100-page catalog lists over 250 different units—40 of them new ones; it's available for the asking from the Heath Co., Benton Harbor, Mich. The free 28-page EICO catalog includes over 80 items—write EICO Electronic Instrument Co., Inc., 33-00 Northern Blvd., L.I. City 1, N.Y.

Data on more than 400 industrial and special-purpose tubes are arranged in easy-to-read reference chart style in CBS Electronics' new 52-page catalog. Principal characteristics and ratings are shown, as well as base diagrams and physical dimensions. For catalog PA-400, send 50 cents to CBS Electronics, Danvers, Mass. —30—

KUHN

"LEADERS IN SPECIALIZED RECEIVING EQUIPMENT"

MOBILE FIXED CONVERTERS

- POLICE
- FIRE
- COMMERCIAL
- CITIZEN'S BAND

345A Complete \$29.95



A new high gain Crystal Controlled Converter. Excellent sensitivity. Rugged construction. Easy to install. Designed for standard transistor car radios. Requires no high voltage supply. 2-54 MC or 150-162 MC.

KUHN CONVERTERS . . . the most advanced line . . . designed for optimum performance.



348A Complete \$34.95

Transistorized, directly tunable Converter. Powered with self-contained mercury cell. Excellent sensitivity and stability. Designed for car, home or portable receivers. Two types available: Aircraft VHF 115-130 MC or 150-162 MC.



344A Complete \$23.95

A new low cost Crystal Controlled Converter designed for use with standard transistor car radios. Operates directly from 12V DC. Rugged construction. Good sensitivity. Range 2-54 MC.

ORDER TODAY or SEND FOR FREE CATALOG . . . containing complete information on a full line of CONVERTERS AND RECEIVERS FOR EVERY APPLICATION

315A




Complete \$14.95
A low cost Tunable Converter for any 10 MC area of: 26-54 MC. Aircraft VHF, or 150-160 MC. Easily installed. For use with home or auto sets. 315A Directly Tunable Converter. Available in four ranges: 26-30 MC, 30-50 MC, 115-130 MC, or 150-160 MC. Complete \$21.95



20 GLENWOOD CINCINNATI 17, OHIO

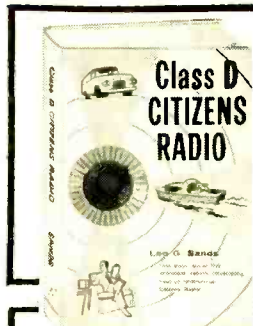We'd like to send you these important new books for a 7-DAY FREE TRIAL EXAMINATION



CLASS D CITIZENS RADIO

Leo G. Sands



Here is the first complete book on Citizens Radio Operation. Ever since the initial use of 2-way radiotelephone by police departments, this field has been growing in importance and application. Now, with more than a million vehicles equipped for its use, Citizens Radio is a major phase of the electronics field. This important new volume covers every aspect of the field—its history, rules, and everything about how it works—in seven big chapters with one hundred major sections. You'll learn exactly what Citizens Radio is, its applications, what equipment you need, the full story on receiver circuits and transmitters, antennas, installation, and maintenance, full FCC rulings, how to apply for licenses, etc. Many illustrations.

\$4.95

COMPUTERS AND HOW THEY WORK by James Fahnestock

Here is a fact-filled exciting guidebook to the wonderworld of electronic computers, with more than 120 illustrations and easy-to-follow tables in 10 big chapters. Step by step, you'll see and understand the workings of every type of computer ever used. This important new book illustrates the basic principles of computers in methods that require no knowledge of electronics. You'll learn all about computer memories, flip-flops and the binary counting system. You'll learn the mathematical language of computers where $1 + 1 = 10$. Other chapters show you how computers use tubes and transistors to make complex logical decisions in thousandths of a second. **COMPUTERS AND HOW THEY WORK** is must reading for career minded students and for electronics pros who want a more complete knowledge of this field.

\$4.95

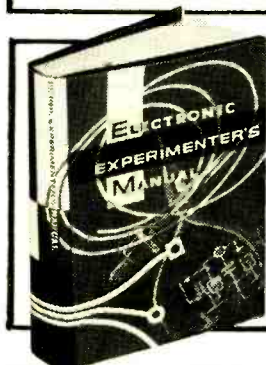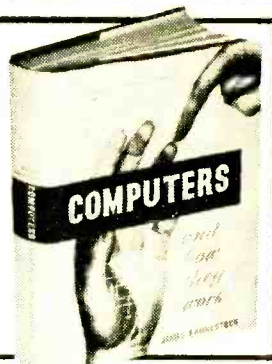

THE ELECTRONIC EXPERIMENTER'S MANUAL

by David A. Findlay

With a few dollars worth of basic tools, and this book to guide you, you can explore the magic of electronics experimentation more completely than ever before. In a few short hours, you'll start your first project. You'll learn about every component used in experimentation, every tool, its function and why it is used. There are 10 big sections, each covering a specific phase of construction. There's a giant section of projects you can build, test equipment you'll construct and use in your future work. **THE ELECTRONIC EXPERIMENTER'S MANUAL** will give you the professional know-how you must have no matter what phase of electronics is your specialty.

\$4.95

7 DAY FREE EXAMINATION

When your books arrive, read and enjoy their diversity of contents, the thoroughness of their coverage. Then after seven days examination, if you decide that they are not everything you want, send them back and receive a complete refund of the purchase price.

SEE YOUR ELECTRONICS PARTS JOBBER OR BOOKSELLER OR USE COUPON BELOW!

ELECTRONICS BOOK SERVICE •
One Park Avenue, New York 16, N. Y.



Please send me copies of **CLASS D CITIZENS RADIO** and bill me at only \$4.95 a copy plus postage and handling.

Please send me copies of **COMPUTERS AND HOW THEY WORK**, and bill me at only \$4.95 a copy plus postage and handling.

Please send me copies of **THE ELECTRONIC EXPERIMENTER'S MANUAL**, and bill me at only \$4.95 a copy plus postage and handling.

If I don't agree that this is one of the best electronics investments I've ever made, I may return the book(s) within seven days and get a full refund.
\$..... enclosed. (SAVE MONEY! Enclose payment with your order and we'll pay the postage.)

Name

Address

City Zone State EF 626

BEST BUYS IN STEREO AND MONO HI-FI

New Transistorized Stereo/Mono 4-Track Tape Deck RP100 Semikit (electronics in kit form) \$299.95 Wired \$399.95



New FM-AM Stereo Tuner ST96 Kit \$89.95 Wired \$129.95 Incl. FET

New 70-Watt Integrated Stereo Amplifier ST70 Kit \$94.95 Wired \$149.95



New 40-Watt Integrated Stereo Amplifier ST40 Kit \$79.95 Wired \$129.95



28W Integrated Stereo Amplifier HF81 Kit \$69.95 Wired \$109.95

FM Tuner HFT90 Kit \$39.95 Wired \$65.95 Incl. FET Metal Cover \$3.95



Stereo Preamplifier HF85 Kit \$39.95 Wired \$64.95

Stereo Power Amplifiers



	Kit	Wired
100W HF89:	\$99.50	\$139.50
70W HF87:	\$74.95	\$114.95
28W HF86:	\$43.95	\$ 74.95



AM Tuner HFT94 Incl. FET Kit \$39.95 Wired \$65.95

NEW FM-Multiplex Autodaptor MX99 Kit \$39.95 Wired \$64.95 (Patents Pending)



Bookshelf Speaker System HFS1 Kit \$39.95 Wired \$47.95

BEST BUYS IN CITIZENS TRANSCEIVERS, HAM GEAR, RADIOS

Citizens Band Transceivers from Kit

\$59.95
Wired \$89.95



New 60W CW Transmitter #723 Kit \$49.95 Wired \$79.95

NEW Walkie-Talkie Citizens Band Transceiver #740 Kit \$54.95 Wired \$79.95. Complete with rechargeable battery & charger.



BEST BUYS IN TEST EQUIPMENT

New Metered Variable Auto-Transformer AC Bench Supplies Model 1073 (3 amps)

Kit \$35.95 Wired \$47.95
Model 1078 (7½ amps)
Kit \$42.95 Wired \$54.95



Peak-To-Peak VTVM #232 & Uni-Probe® Pat. #2,790,051 Kit \$29.95 Wired \$49.95

VTVM #221 Kit \$25.95 Wired \$39.95



DC-5 MC 5" Scope #460 Kit \$79.95 Wired \$129.50

5" Push-Pull Scope #425 Kit \$44.95 Wired \$79.95



Tube Tester #625 Kit \$34.95 Wired \$49.95



RF Signal Generator #324 Kit \$26.95 Wired \$39.95



1000 Ohms/Volt V-O-M #536 Kit \$12.90 Wired \$16.90



6- & 12V Battery Eliminator & Charger #1050 Kit \$29.95 Wired \$38.95


Extra-filtered for transistor eqpt. #1060 Kit \$38.95 Wired \$47.95



NEW AC Volt-Watt Meter #260 Kit \$49.95 Wired \$79.95



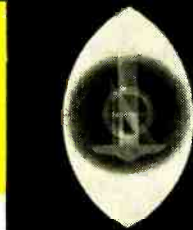Multi-Signal Tracer #145A Kit \$19.95 Wired \$28.95



EICO

EXCELLENCE IN CREATIVE ELECTRONICS

Over 2 MILLION EICO instruments in use throughout the world. Compare, take them home — right "off the shelf" — from 1500 neighborhood dealers, most of whom offer budget terms.



EICO, 3300 N. Blvd., L.I.C. 1, N.Y. PE-11
 Send free Catalog describing over 80 top-quality products, free Stereo Hi-Fi Guide, free Short Course for Novice License, name of nearest EICO dealer. Send new 36-page GUIDEBOOK TO HI-FI for which I enclose 25¢ for postage & handling.

Name _____
 Address _____
 City _____ Zone _____ State _____
 Add 5% in the West

electroluminescence electroluminescence

At one time only a dream of science, heatless illumination is now a reality. Electroluminescence is being put to work to make paper-thin panels which someday may light your home.


By JAMES E. PUGH, Jr.

IN EARLY TIMES, the glowing tree-trunk seen by a lone traveler in the woods or the strange "burning" of the sea noticed by a wide-eyed sailor seemed to portend evil and disaster. Today we know that both are caused by chemical reactions in the cells of tiny living things, and our superstition has changed to active interest. Scientists have been fascinated by the heatless light produced by certain organisms for decades but, until recently, they couldn't even come close to duplicating it on a practical scale.

The introduction of the fluorescent lamp (1938) was a step in the right direction. Here, less power was wasted in the production of use-less heat than with an incandescent bulb, though the loss was still substantial. In the late 1940's, however, the phenomenon of electroluminescence, a direct conversion of electricity to a "cold" light much like that found in nature, moved out of the laboratory. Today you can buy an electroluminescent lamp for a few cents in any hardware store.

But just what is electroluminescence? Well, Webster defines *luminescence* as "any emission of light not ascribable directly to incandescence, and therefore occurring at low temperatures." Generally speaking, luminescence is caused by excitation of the electrons in a chemical compound called a "phosphor." In the case of living things which luminesce, the excitation is brought about chemically and the phenomenon is usually referred to as chemiluminescence. Therefore, electroluminescence, as you might guess, is luminescence produced by a phosphor which has been excited electrically.

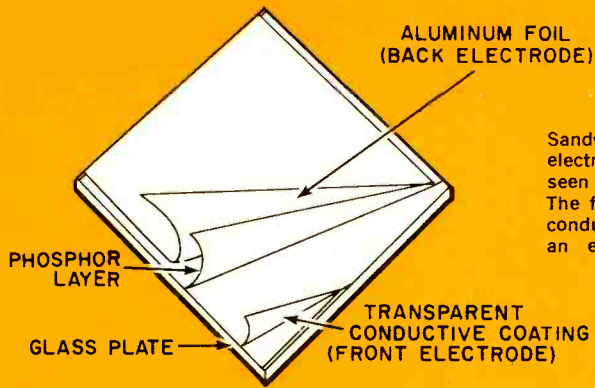Electrical "Sandwich." Though electroluminescent lamps are not yet efficient enough to provide general lighting (being most commonly used as night-lights), they have some unique physical and electrical char-



Sandwich-like construction of an electroluminescent lamp can be seen in this simplified drawing. The front plate has a transparent conductive coating which acts as an electrode, yet passes light.



acteristics which suggest many uses. The lamps are made by sandwiching a layer of phosphor (often zinc sulfide) between two plates of electrically conducting material. The front plate usually consists of glass having a special transparent coating which allows it to act as an electrode, and the complete unit is not much thicker than that plate.

When an alternating current is connected across the two plates, the electrons in the phosphor are excited to a higher energy level—causing it to emit a soft, glareless light with almost no accompanying heat. The color of the light depends on the selection of the phosphor

and the impurities which are deliberately introduced into it. Green, blue, orange, yellow, gold, red, and white phosphors are available, but at present green yields the most light.

Contrast the way in which light is produced by an electroluminescent lamp with the operation of standard fluorescent or incandescent units. Though a phosphor is also used in the fluorescent lamp, it is not excited directly by an electric current—but rather by ultra-violet rays. These rays are produced (along with wasted radiations at other frequencies) by an electrical discharge through mercury vapor gas. In the case

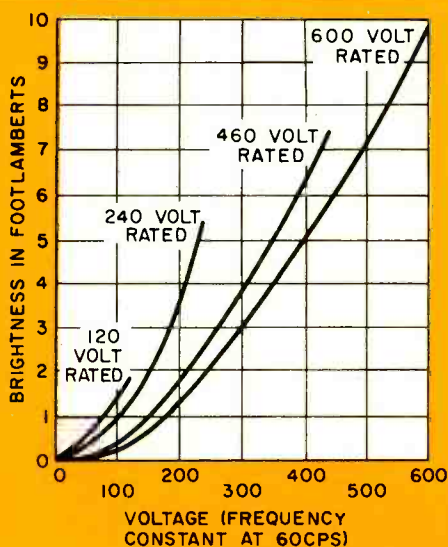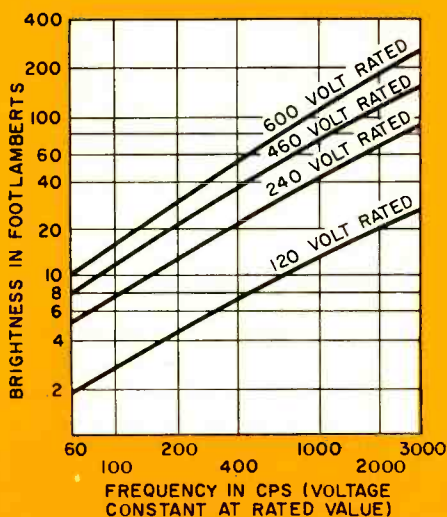Graphs show brightness versus frequency (left) and voltage (right) for lamps of different ratings.






Westinghouse

The manufacturing equipment, in theory, imposes the only limitation on the size of the lamps. Here, a phosphor layer is being baked in an infrared oven.


of the incandescent lamp, of course, the light is only a byproduct of the heat generated in a fine wire by the passage of an electric current.

Advantages and Drawbacks. The new light source is usually produced as a flat sheet, but it can be cut into almost any conceivable shape. And, since no vacuum is required for its operation, the only limits to its physical size are those imposed by the manufacturer's equipment. One unit recently made by Sylvania measures eight by two feet—a whole wall could be made to glow with a soft, pleas-

Sylvania

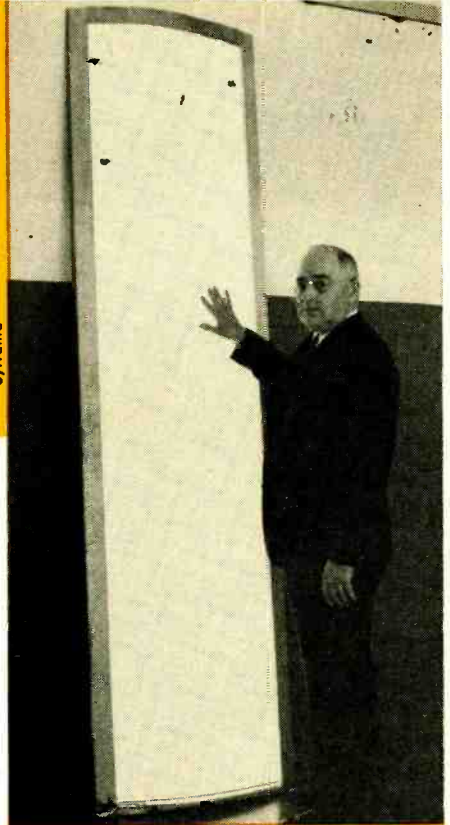

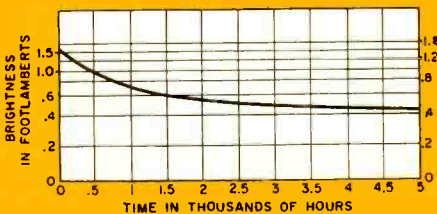What may be the world's largest electro-luminescent lamp measures eight by two feet. It has a brilliance of five foot-lamberts, an estimated life of five years.





Freedom from "burn out" is one feature of the new light source. Light output simply diminishes with time as illustrated in this graph of a typical lamp operating at 120 volts, 60 cycles. One manufacturer's conservative estimate of the maximum usable life of his product under these operating conditions is 5000 hours. Another maker claims up to 20,000 hours of useful operation.

TYPICAL CHARACTERISTICS OF ELECTROLUMINESCENT LAMPS


Operating Voltage	Available in standard voltages from 120 to 600 volts
Operating Frequency	Most useful range: 25-1000 cycles
Resistance (of a square foot)	24,000-55,000 ohms, depending on voltage rating
Capacitance	0.35-0.109 uf./sq. ft., depending on voltage rating
Operating Current (@ 120 v., 60 cps)	16-36 ma./sq. ft.
Light Output (@ 120 v., 60 cps)	0.5-1.9 footlam-berts
Life Expectancy (@ 120 v., 60 cps)	5000-20,000 hours



Sylvania photos

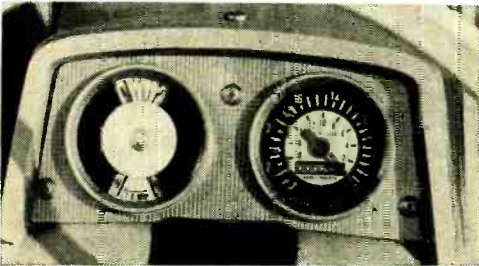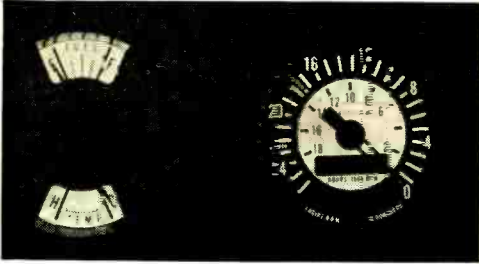

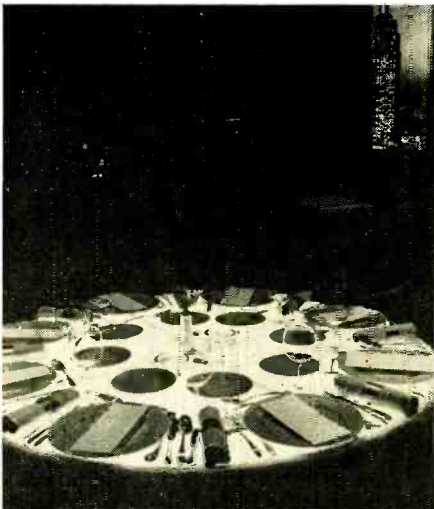Electroluminescent lamps are well suited for use as indicators of all kinds: above is a glowing street sign, plus night-and-day photos of a tractor dashboard incorporating the new light source. Interior decorators have also been finding applications for electroluminescent lighting—table top in photo below emits a soft “candlelight” glow flattering to diners.



Westinghouse

ant light by installing a number of these panels side by side.


The electroluminescent lamp's main drawback is its present inability to produce enough light for high-intensity applications. The light output of a given phosphor, however, can be increased by raising its supply voltage and/or frequency. Though 120-volt, 60-cycle operation is common, special oscillators have been used to provide higher frequencies (up to 20,000 cycles), and lamps rated at voltages up to 600 are readily available. An interesting idiosyncrasy of these lamps is that, with some phosphors, a color shift occurs as the frequency is raised. In the case of one green phosphor, the color changes to blue at frequencies over 400 cycles.

It will be a while before you can light your house with glowing ceiling or wall panels but, in the meantime, electroluminescent lighting will find plenty of applications. In addition to their other advantages, these “miracle” lights have a usable life expectancy of up to 20,000 hours. During this time a burn-out never occurs—the light intensity simply decreases slowly until it reaches a level so low that the unit must be replaced. Then, too, power consumption is quite low. A Westinghouse “Rayescent” lamp, for instance, draws only 0.6 watt per square foot when operating at 120 volts, 60 cycles.

Present and Future. Long life, freedom from “catastrophic” burn-out, and glareless light make these lamps particularly well suited for use as indicators of all kinds. Among the applications in this category which have been suggested or already developed are lighting for aircraft, auto, and boat instrument panels, highway signs, and “read-out” numbers.

Interior decorators, too, are excited by the possibilities of this flexible light source. Glowing walls and ceilings (primarily for decorative effect rather than illumination) are already a reality, and electroluminescent panels have been incorporated into many types of furniture. Perhaps in the not-too-distant future this revolutionary lighting material will be improved to the point where it can be used for general lighting as well as decoration—and you may have to look in an antique store to find one of today's “old-fashioned” light bulbs. —50—

Build a RADIATION DETECTOR

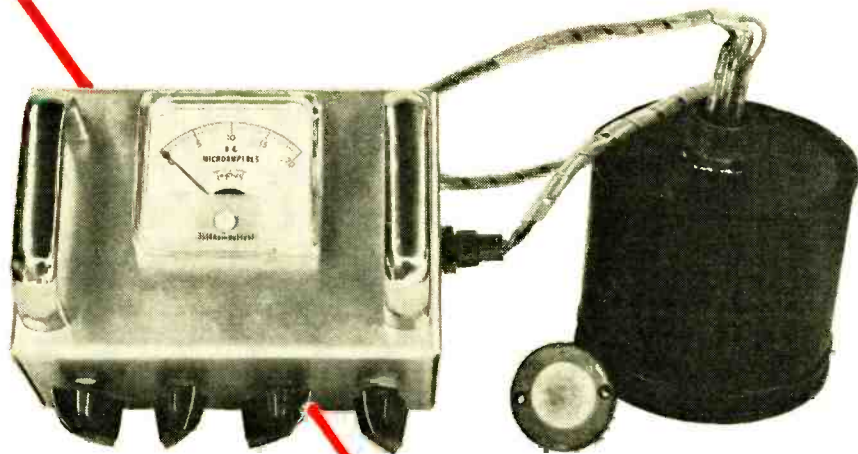

By JACK MANDEVILLE

CONSTRUCTION of an ionization-chamber type radiation detector is usually limited to a "laboratory" of sorts, since this is the only place where the special tools and machinery normally needed to fabricate and assemble such a detector will be found. But building the ionization chamber described here requires only hand tools and readily available, inexpensive materials.

This radiation detector is actually a rate meter which indicates radiation in terms of time (i.e., 10 milliroentgens per hour). The instrument gives a relative reading based upon the rate of radiation before and during exposure to the radiation source. With proper facilities, it could be calibrated to indicate the actual amount of radiation present.

Except for a tube and a meter, the necessary parts are frequently encountered in the spare parts box of any electronics experimenter. And even if you start out by purchasing all neces-

*Sensitive ionization chamber
detects ions produced by
nuclear radiation*



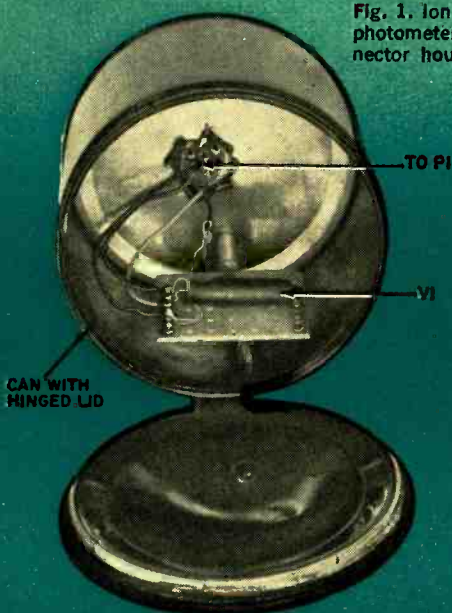


Fig. 1. Ionization chamber is made up of photometer tube (VI) and three-pin connector housed in empty shortening can.

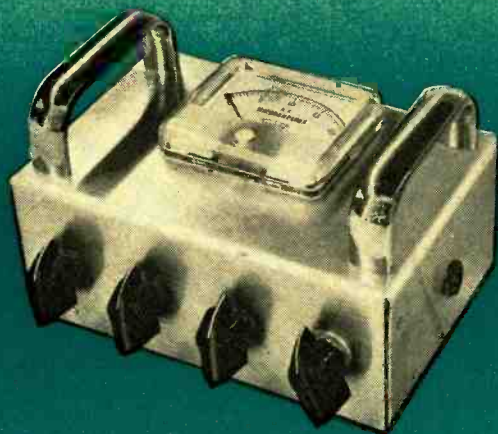


Fig. 2. Meter chassis contains simple d.c. amplifier and controls. Three-conductor cable (not shown) feeds output from ionization chamber into amplifier.

sary materials, you'll probably find that the total cost of the instrument won't exceed \$30.00 or so.

Construction. The ionization chamber consists of a medium-sized, thin-walled can with a lid. (A half-pound shortening can with a hinged lid is ideal.) Mounted in the chamber are a three-pin connector and a device (terminal board or clamp) to hold miniature electrometer tube *V1* (see Fig. 1).


The meter chassis (shown in Figs. 2 and 3) is connected to the ionization chamber by a plug and cable combination and contains a 0-50 μ a. meter, three potentiometers, a switch, batteries, and a transistor. Actually, meter *M1* can be almost any basic movement up to 0-250 μ a.—the more sensitive the meter, the more sensitive the instrument. (As a matter of fact, the author used a 20- μ a. Triplett unit he had on hand rather than the 50- μ a. meter specified.)

Take care during construction to avoid contaminating the electrometer tube by breathing on or holding its base. If the tube is thus contaminated (zero-signal plate current will exceed 150 μ a. in such cases), you can decontaminate it by washing it with alcohol and cleaning it with a brush.

Adjustment Procedure. To set up the unit for radiation measurements, perform the following steps in the order indicated here.

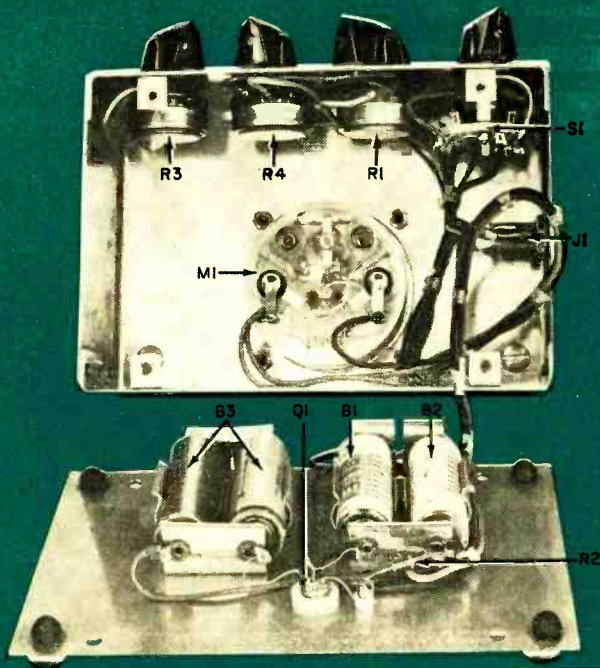- (1) Turn potentiometer *R1* to its full counterclockwise position.
- (2) Turn potentiometer *R3* to its full clockwise position.
- (3) Turn potentiometer *R4* to its full counterclockwise position.
- (4) Switch *S1* to "on."
- (5) Allow about a minute for conditions to stabilize.
- (6) If the meter reading is below mid-range, rotate *R4* clockwise until the meter indicates mid-range. If the meter reading is above mid-range, rotate *R3* counterclockwise until the meter indicates mid-range.
- (7) Adjust *R3* for zero (background radiation without source).
- (8) Place a radioactive source next to the chamber.
- (9) Adjust *R1* and *R4* for a full-scale meter reading.
- (10) Repeat steps 7, 8, and 9 until readings are constant.

Properly adjusted, this instrument is capable of detecting radiation from such weak sources as the dials of luminous wrist watches. But remember that the




PARTS LIST

- B1, B2—1.35-volt mercury cell (Mallory RM12R or equivalent)*
- B3—5.4-volt mercury cell (Mallory TR-134R or equivalent)*
- M1—0-50 μ a. d.c. meter (Beede Model 14 or equivalent)*
- Q1—2N35 transistor*
- R1, R4—25,000-ohm potentiometer, linear taper (Ohmite CU2531 or equivalent)*
- R2—680-ohm, 1/2-watt resistor*
- R3—500-ohm potentiometer, linear taper (Ohmite CU5011 or equivalent)*
- S1—3-position, 2-pole rotary switch (Centralab 140 or equivalent)*
- V1—CK5886 tube*
- I—2" x 7" x 5" chassis (Bud AC-402 or equivalent)*
- I—3" x 7" bottom plate for chassis (Bud BPA-1589 or equivalent)*
- I—Chn with hinged lid—see text*
- Misc.—hardware, wire, solder, connectors, handles, rubber feet, knobs, etc.*

Photos by Arthur Sula

Fig. 3. Controls and meter M1 are mounted on chassis (top), with batteries and transistor attached to bottom plate. Handles (see Fig. 2) and rubber feet (above) are both optional.

Fig. 4. Circuits for ionization chamber (box at left in diagram) and d.c. amplifier; J1 and P1 at top refer to connectors on cable between two units. Cable consists of three wires to connect points A, B, and C.

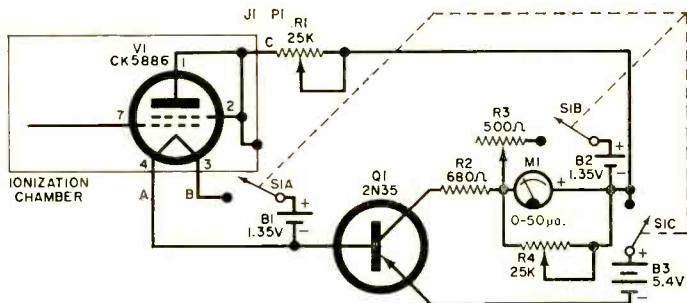

intensity of radiation varies inversely with the square of the distance, and large fluctuations in rate cannot be expected from weak sources at great distances.

About the Circuit. Radiation particles from the source to be detected will enter the chamber and ionize the atoms and/or molecules in the air. The resulting ions will have either a positive or a negative charge and will therefore be either repelled or attracted by the collector grid and the shell of the ion chamber.

The flow of these ions constitutes a flow of current in the grid-cathode-shell circuit. This flow of grid current in the

electrometer tube results in a corresponding increase or decrease in plate current.

The actual circuitry is shown in Fig. 4. The electrometer plate current (approximately 100 μ a.) is used for base bias and signal current for the transistor d.c. amplifier. Connected in series with the collector of transistor Q1, the meter effectively monitors the amplified d.c. signal.

Potentiometer R1 controls the basic sensitivity of the ion chamber and the base-emitter circuit of Q1. Resistor R2 is a current limiter for transistor protection, while potentiometers R3 and R4 control calibration of the meter. -30-

CB GOES ON TV



Private eye Roger Smith (center) awaits report via CB from colleague Efrem Zimbalist, Jr. (at left), as "Roscoe" hovers in the background. Zimbalist and Smith are the mainstays on ABC's "77 Sunset Strip."



EVERY Friday evening between the hours of 9 and 10, some 20 million-plus TV viewers watch "77 Sunset Strip." A Warner Bros. production broadcast over the ABC television network, "77 Sunset Strip" is the pioneer hour-long detective/adventure show.

Much credit for the continuing success of this show goes to the two leading men, Efrem Zimbalist, Jr., and Roger Smith. Ideally suited for the parts they portray, Zimbalist and Smith typify the American concept of a "private eye."

In the series of this show now being broadcast, observant POPULAR ELECTRONICS readers will be able to see these two detectives make use of CB equipment—employing the phony call-sign 11J5486. A CB transceiver has been made a part of the office furniture in this TV series, and hand-held transceivers will also appear from time to time.

We at POPULAR ELECTRONICS are proud to report that we assisted in this exposure of CB on network TV. Needless to say, we urge all of our readers to tune in the following three shows where CB equipment plays an important part: "The Bridal Trail Capers," "The Bel Air Hermit" and "The Unremembered." Your local TV program listings will tell you when these shows are on the air.

-30-

FLEA-POWER GLOW LIGHT




*A battery-operated power supply for portable operation
of a standard electroluminescent lamp*

By JAMES E. PUGH, JR.

THE electroluminescent night-lights now on the market are handy gadgets to have around. Drawing a minimum of current, they'll bathe a room in a soft, pleasant glow—yet can be left burning day and night at a cost of only a few pennies a year. Though designed to work on the a.c. line, the current demand of these units is so small that a battery-powered Hartley oscillator is more than adequate as a power supply.

With the oscillator described here, you can use your night-light on hunting trips; in trains, boats, and cars; or anywhere a soft, low-intensity lamp is needed. A line cord has been included for switching to a.c. when such operation is possible, and a convenient intensity control allows you to vary the brightness.

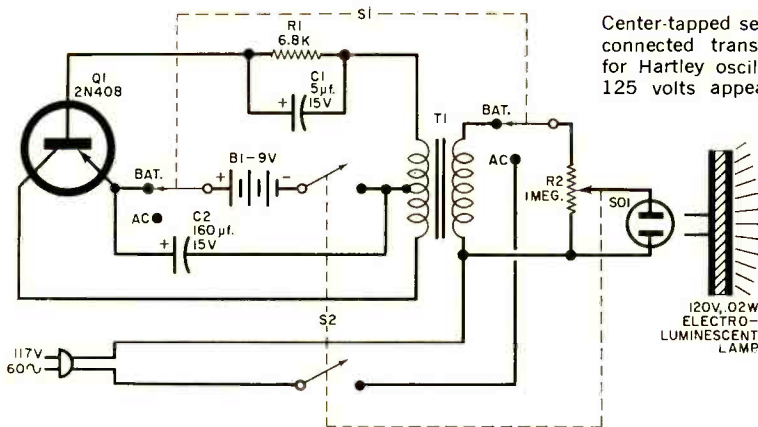
The Circuit. Transistor *Q1* is connected as a Hartley oscillator and powered by battery *B1*. The 6.3-volt secondary of transformer *T1* serves as a tapped oscillator coil. Resistor *R1* and capacitor



Center-tapped secondary of reverse-connected transformer T1 is coil for Hartley oscillator circuit. About 125 volts appear across primary.

PARTS LIST

- B1—9-volt battery (Burgess 2N6 or equivalent)
- C1—5-µf., 15-volt electrolytic capacitor
- C2—160-µf., 15-volt electrolytic capacitor
- Q1—2N408 transistor
- R1—6800-ohm, ½-watt resistor
- R2—1-megohm potentiometer (linear taper)
- S1—D.p.d.t. toggle switch
- S2—D.p.s.t. switch (on R2)
- SO1—Chassis-type a.c. receptacle (Amphenol 61-F or equivalent)
- T1—Filament transformer; primary, 117 volts; secondary, 6.3 volts @ 1.2 amp. CT (Stancor P6134)
- 1—4½" x 4⅜" x 4¼" sloping panel utility box (Premier ASPC-1200 or equivalent)
- 1—120-volt, 0.02-watt Sylvania "Panclescent" night light
- Misc.—Pointer knob for R2, 7-lug terminal strip, rubber feet, battery connector, cable clamp for line cord, hardware, etc.

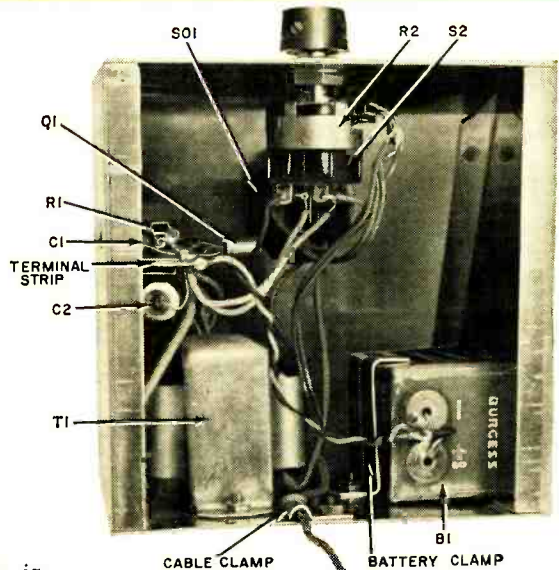


C1 determine the pulse rate, which is about 60 cycles with the values specified. When the oscillator is in operation, its output is stepped up by T1, and approximately 125 volts are available at the primary of this reverse-connected transformer. The primary of T1 is wired to the night-light socket (SO1) through intensity-control potentiometer R2.

In the schematic, switch S1 is shown set for battery operation as described above. When S1 is in the A.C. position, however, battery B1 is disconnected and potentiometer R2 and socket SO1 are switched from T1's primary to the a.c. line. Switch S2, which is ganged to po-

tentiometer R2, turns the unit on and off regardless of which type of operation S1 is set for.

Construction. For best appearance and ease of operation, the circuit is housed in a 4½" x 4⅜" x 4¼" sloping-panel utility box. To avoid damage to furniture, fasten three small rubber feet to the bottom of the box.

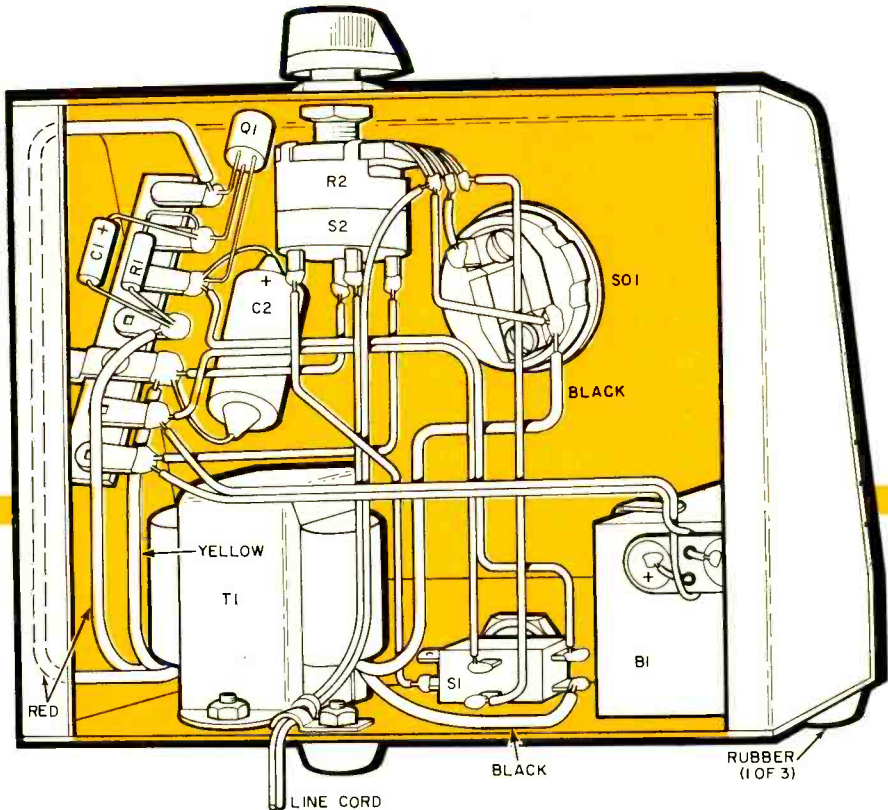Parts fit neatly in compact utility box. Note that most oscillator components mount on the terminal strip.



Pictorial diagram clearly shows parts layout and wiring details. Terminal strip at left is tilted forward for a better view of its connections, and color coding of T1's leads is shown.

Using the photograph as a rough guide, drill all the mounting holes. It's most convenient to make the opening for socket *SO1* with a $1\frac{5}{8}$ " punch or hole cutter, but it can be drilled out and filed to size. Now bend a $2\frac{1}{4}$ " x $\frac{1}{2}$ " strip of soft steel as shown to form a battery clamp.

With the above construction details carried out, you can proceed to the mounting and wiring of the components. Begin by mounting transformer *T1* and cutting its leads to the lengths needed. Next, solder all wires to switch *S1*, making sure to allow enough lead length to reach the various other components, and fasten the switch in place.

All of the connections to the terminal strip should now be made—take care to avoid heat damage when soldering in the transistor. Then mount the terminal strip, as well as socket *SO1* and poten-

tiometer *R2*/switch *S2*. Finally, install the line cord and battery and complete the wiring.


Using the Supply. For battery operation, set *S2* to the *Battery* position; to operate from the a.c. line, set the switch to *A.C.* In either case, *R2/S2* will turn the light on and off and control its intensity. The lamp glows green when operated from the line, but you'll notice that it's blue when the oscillator is being used as the power supply. The color change is caused by a high-frequency component in the oscillator's pulse.

If you'd like to experiment with different oscillator frequencies, you can change the values of *R1* and *C1*. Reduce either or both to increase the frequency, or increase them to decrease the frequency. For greater light output at very low frequencies, the pulse should be broadened by making *C1* much larger. -30-

HI-FI HEAT WAVE

Prolong the life of your equipment by giving it adequate ventilation

By CHARLES H. WELCH

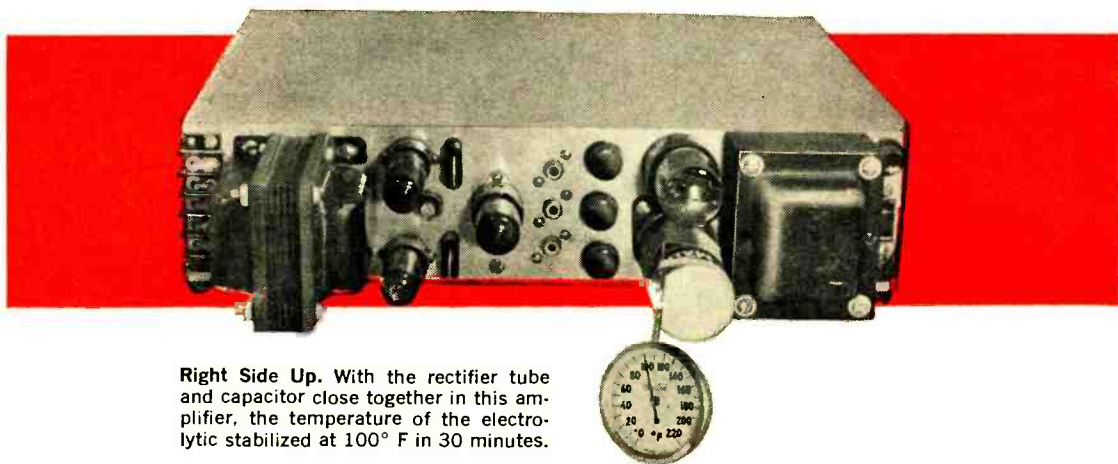

Right Side Up. With the rectifier tube and capacitor close together in this amplifier, the temperature of the electrolytic stabilized at 100° F in 30 minutes.

THE DAMAGING EFFECT of heat is one of the least understood and most neglected problems in operating electronic equipment. Hi-fi amplifiers and tuners have been particular casualties—they are often placed in poorly ventilated enclosures where excessive heat can make the most trouble.

To obtain a clear picture of what heat damage means to hi-fi owners, let's take a typical audio power amplifier tube, the 6AQ5, fit it with a standard tube shield, put the tube in an unventilated cabinet, and apply voltages equal to those found in the average amplifier. Within a few hours, the tube's glass bulb will reach a temperature of about 400°C, or 750°F. In other words, the tube is HOT.

What is the 6AQ5's response to this treatment? You may consider yourself lucky if the tube lasts for 1000-1500

hours. Since it is not uncommon for a 6AQ5 to last about 10,000 hours, excessive heat has lopped off possibly 90% of the useful tube life.

However, this isn't the only thing that has occurred—if the tube happens to be part of a hi-fi amplifier. The 6AQ5, together with other heat-dissipating components in the circuit, will have raised the temperature in the unventilated enclosure to about 125°C. This exceeds the rated operating temperatures for electrolytic capacitors, some resistors, and even a few transformers.

Our amplifier has started a frantic race to see which of its components will fail first. Let's look at what heat does to the various components.

Capacitors. Practically all capacitors used in hi-fi equipment will be temporarily or permanently damaged by ex-

cessive heat. The most sensitive is the electrolytic capacitor. When it is operated near its maximum voltage rating, and the temperature exceeds the manufacturer's rating, the leakage current goes up sharply. This causes additional heating, which again causes the leakage current to increase . . . making for a vicious spiral which ends abruptly in the explosive demise of the electrolytic.


Resistors. Not only can composition resistors be damaged by excessive heat, but in normal operation they may give off some heat of their own which adds to their problems—and those of surrounding components. One manufacturer of

emission, interelectrode leakage, and cathode emission loss.

When you purchase an amplifier, take a close look at how and where the tubes are mounted. They should be in a position where air can circulate freely.

Use of the common J-type tube shield generally raises the temperature of the tube envelope by 50°C. Some designers of hi-fi equipment now feel that too many tubes are often shielded in preamplifiers and amplifiers unnecessarily.

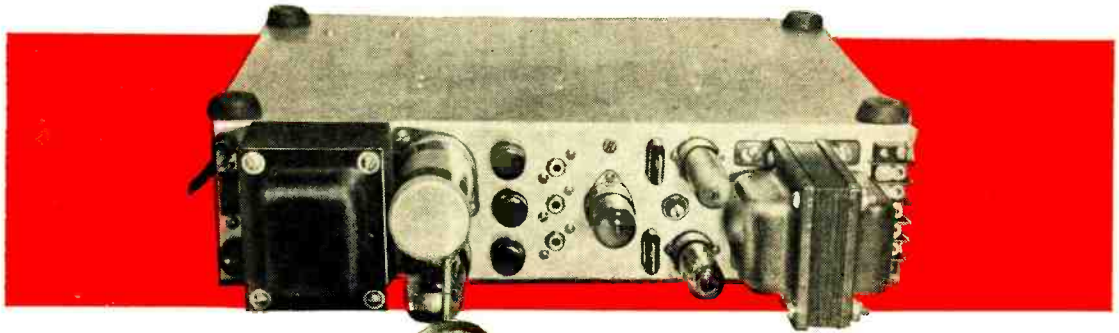Give your hi-fi a chance to breathe, and you'll find that it will work better and longer, with fewer—if any—breakdowns due to excessive heat. -30-




Wrong Side Up. Turning the amplifier over put the capacitor above the tube; its temperature rose to 136° F in 30 minutes and was still climbing.

quality composition-type resistors says that his product can be expected to increase in resistance by about 6% for each 1000 hours of operation at a temperature of 150°C. This means that the voltages and currents applied to the tubes in your hi-fi system can be expected to change, either throwing the system out of balance, or introducing distortion.

Semiconductors. Practically all selenium or silicon rectifiers and diodes are affected by heat. Generally speaking, the maximum forward current of a semiconductor must be lowered as the temperature goes up. In one typical unit, a forward current rating of 750 ma. at 40°C drops to 250 ma. at 125°C.

Tubes. Operating tubes above their rated temperatures often leads to the tubes becoming gassy. Other heat-induced reasons for tube failures are grid


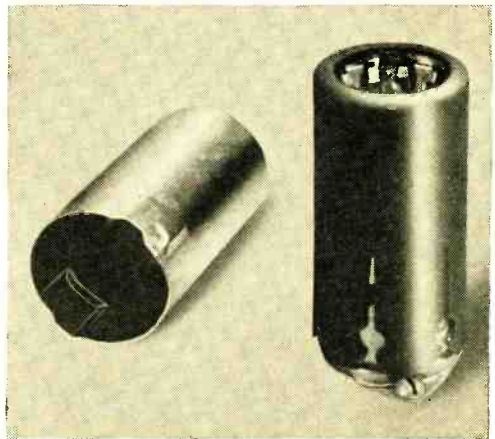
Improved Tube Shield. Five times as expensive as the J-type tube shield (left), the Type B shield from International Electronic Research (right) dissipates heat rapidly. In tests by the author, tubes fitted with this shield were 200° F cooler.



4 WAYS TO GET CLIPPED


Suggested by **JOHN A. COMSTOCK**

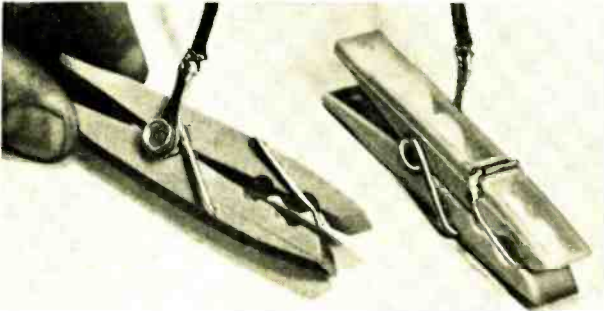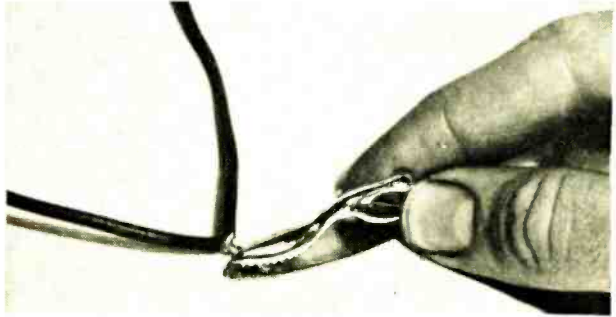TIE CLASP—TEMPORARY CLIP. Almost every male experimenter has a few old, battered tie clasps in his dresser. They can be put to use as heat sinks in transistor experiments, or as temporary connectors to hold several wires together which don't need to be soldered. A tie clasp will also serve as an alligator clip in the negative lead of a VOM or VTVM.



CLOTHESPIN TEST CLIPS. You can make a couple of jumbo-size test clips in a hurry from plastic spring-type clothespins. Solder lugs to the ends of your test leads and fasten them to each clip with self-tapping screws turned into the coil of the spring. Then cut a small U-shaped wire and solder it to the spring on either side of the clip; the other end of this wire is your electrical contact in the jaws of the plastic clip.

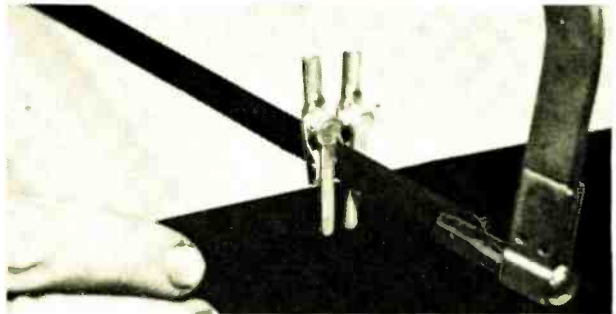ALLIGATOR CLIPS GUIDE SAW. A pair of alligator clips will help keep a hacksaw blade in place when you're starting a cut in thin sheet metal. On many occasions, you'll find that using these clips will be easier than filing a notch to start the new cut.



CURTAIN CLIP COILS CORD. If you're tired of tripping over dangling power leads, take up some of the slack with plastic curtain clips. These clips can be found in the housewares department of any five-and-dime store. If the cord is excessively long, use two curtain clips—one near the plug, the other near the appliance.

ADD A SQUELCH TO THE CB-1

Simple diode circuit eliminates superregenerative hiss



By R. L. HAWBAKER, 1ØWØ975

IF YOU OWN one of the popular Heathkit CB-1 Citizens Band transceivers, here's a neat way to add an efficient squelch circuit to the receiver section. The squelch will block almost all of the "between - stations" superregenerative hiss and man-made noise—yet, if set properly, it will pass the weakest r.f. carrier. Installation involves adding only a few components and making some simple wiring changes.

About the Circuit. The changes to be made center around the plate circuit of detector *V1b*. This circuit, before and after modification, is shown in Figs. 1 and 2 respectively. In both diagrams, all original components are marked with their Heath part numbers. In Fig. 2,

all new components are designated by numbers beginning with "50" (i.e., *V501*, *R502*, etc.). Portions of the circuit which are left unchanged have been drawn with dotted lines.

Tube *V501* is a 6AL5 dual diode, only half of which is used. Its plate voltage is taken from dropping resistor *R501* and filtered by a network consisting of *R503* and *R504* and capacitors *C502* and *C503*. The cathode is biased through resistor *R502* and potentiometer *R106*; it receives the audio output of tube *V1b* through capacitor *C501*. Capacitor *C504* couples *V501*'s audio output (by way of volume control *R108*) to the grid of the first audio amplifier (*V2b*).

Potentiometer *R106*, formerly the re-

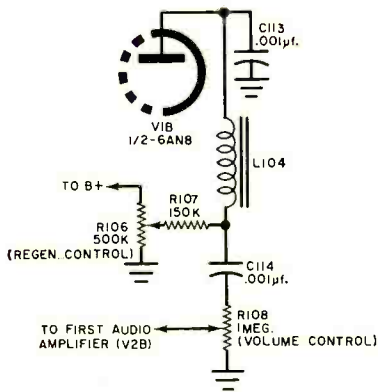


Fig. 1. Plate circuit of Heathkit CB-1's detector before modifications are made. Regeneration control R106 will become the squelch control.

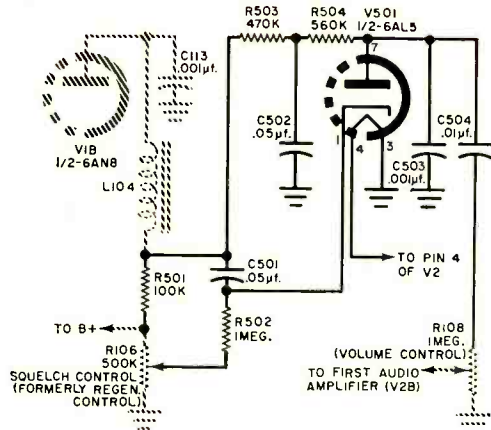


Fig. 2. The circuit in Fig. 1 after it is modified. Dotted portions of the schematic represent sections which have been left unchanged.

generation control. serves to control the squelch. Resistor *R501* sets the regeneration at a fixed value, and the author found that this causes no inconvenience—the model shown has operated over the entire Citizens Band with no noticeable loss in sensitivity.

Squelch control *R106* is normally set so that the cathode of diode *V501* is slightly more positive than the plate. In this condition, the tube will not conduct and no signal will pass through to *V2b*. When a carrier is received by detector *V1b*, however, the diode's plate voltage will rise until the plate becomes more positive than the cathode. The tube then conducts and the signal passes through.

With *R106* set so that *V501* is just on the threshold of conducting, a rise in plate voltage of only one volt will "break" the squelch. The average readable signal causes a rise of 3 to 5 volts, but superregenerative hiss and/or most man-made noise will not increase the voltage to the value necessary for conduction.

Remember, though, that this device is not a noise limiter. It serves mainly to squelch the hiss which is characteristic of a superregenerative receiver when no signal is being picked up. Man-made noise is also suppressed when no signal is present, but once a carrier causes the tube to conduct, any noise will ride through as well.


Installation. The only mechanical changes which must be made in the

CB-1 are the addition of a socket (*SO1*) for *V501* and an extra terminal strip (*TS1*). The pictorial diagram (Fig. 3), which shows the corner of the chassis (wiring eliminated) where these parts are located, will help you with the placement. The original parts are marked with their Heath designations.

The author installed a 5-terminal (one grounded) terminal strip, even though a 3-terminal unit would have worked, to get good spacing of the parts. Only the terminals marked 1, 2, and 3 are used. Notice also that, to conserve space and avoid drilling an extra hole, one side of the new socket is held in place by one of the mounting nuts for *V2*'s socket. Place a solder lug under the mounting nut for the other side of the socket.

Wiring Steps. Once *SO1* and *TS1* are in place, you're ready to go ahead with the wiring. The steps are itemized below—carry them out in order and check off each one as you have completed it. An asterisk appearing after a terminal means that the last connection has been made to it and it's okay to solder.

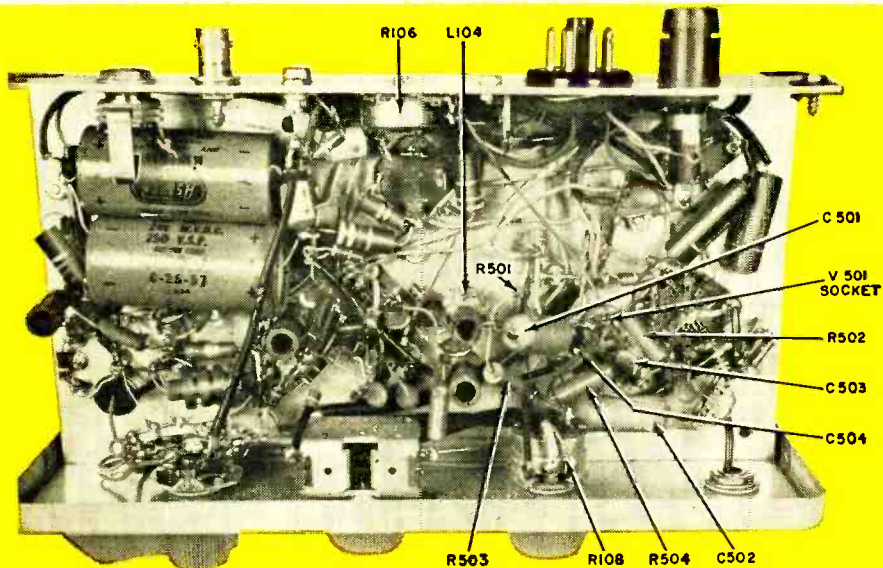All of the terminal numbers mentioned in the following instructions refer to Fig. 3, and the photo of the underside of the chassis will give you an idea of the relative positions of the components. When wiring, be sure to route all component leads so that they are as short and direct as possible. In this way, undesirable effects, such as hum pickup or




PARTS LIST


C501, C502—0.05- μ f. 400-volt capacitor
 C503—0.001- μ f. ceramic disc capacitor
 C504—0.01- μ f. ceramic disc capacitor
 R501—100,000 ohms
 R502—1 megohm
 R503—470,000 ohms
 R504—560,000 ohms
 SO1—7-pin miniature tube socket
 TS1—5-lug terminal strip (center lug grounded)
 V501—6AL5 tube
 Misc.—Tube shield for V2, solder lug, hardware, etc.

Bottom view of CB-1 chassis shows some of the components to be added. Extra terminal strip (not visible) makes for a professional-looking installation.

Fig. 3. Components in area of chassis where changes are made. Part and terminal numbers are keyed to installation and wiring instructions in text.

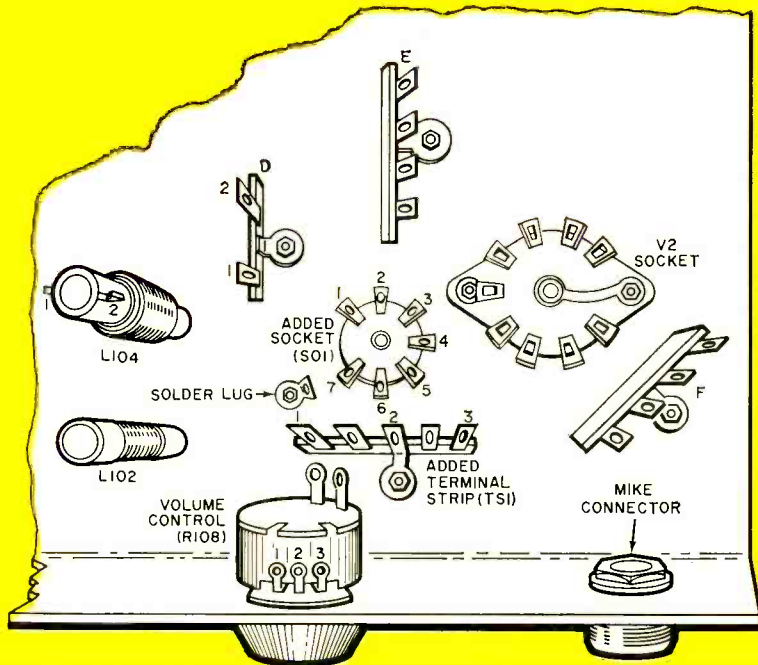

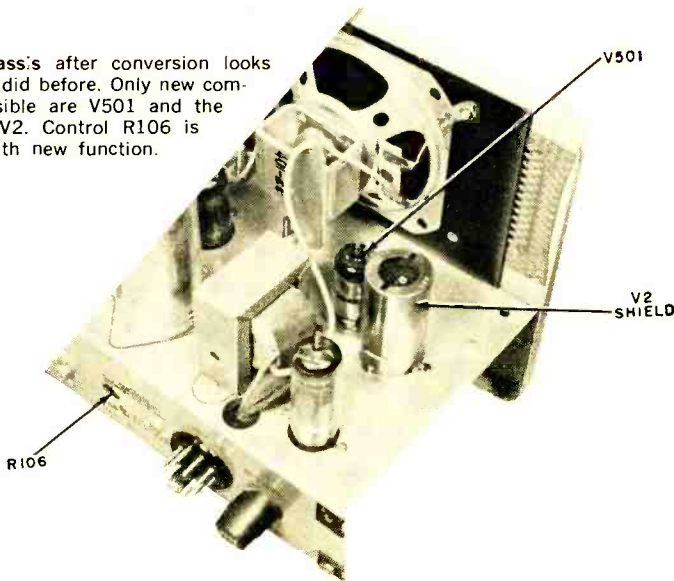Top of chassis after conversion looks much as it did before. Only new components visible are V501 and the shield for V2. Control R106 is old part with new function.



the introduction of feedback will be avoided. In addition, you'll have a neater-looking job.

(1) Remove the 150,000-ohm resistor (*R107*) connected between terminal 2 of choke *L104* and terminal 1 of terminal strip "D."

(2) Remove and save the 0.001- μ f. capacitor (*C114*) connected between terminal 2 of *L104* and terminal 1 of volume control *R108*.

(3) Connect a 100,000-ohm resistor (*R501*) between terminal 2 of *L104* and terminal 1^{*} of terminal strip "D."

(4) Disconnect the lead from the center terminal of regeneration control *R106* (not shown in Fig. 3) and move it to the ungrounded end terminal.*

(5) Connect the center terminal^{*} of *R106* to terminal 3 of terminal strip *TS1*.

(6) Connect pin 3^{*} of socket *SO1* to *SO1*'s center shield terminal.

(7) Connect *SO1*'s center shield terminal^{*} to the solder lug^{*} installed under *SO1*'s mounting nut.

(8) Connect pin 4^{*} of *SO1* to pin 4^{*} of *V2*'s socket.

(9) Connect *R502* (1,000,000 ohms) from terminal 3^{*} of *TS1* to terminal 1 of *SO1*.

(10) Connect *C501* (0.05 μ f.) from terminal 2 of *L104* to terminal 1^{*} of *SO1*.

(11) Connect *R503* (470,000 ohms)

from terminal 2^{*} of *L104* to terminal 1 of *TS1*.

(12) Connect *C502* (0.05 μ f.) from terminal 1 of *TS1* to terminal 2 (ground) of *TS1*.

(13) Connect *R504* (560,000 ohms) from terminal 1^{*} of *TS1* to terminal 7 of *SO1*.

(14) Connect *C503* (0.001 μ f.—formerly *C114*) from terminal 7 of *SO1* to terminal 2^{*} of *TS1*.

(15) Connect *C504* (0.01 μ f.) from terminal 7^{*} of *SO1* to terminal 1^{*} of volume control *R108*.

With the wiring completed, the only work remaining is to install a shield on *V2*. Tube *V2*'s socket could be changed to the type having a fitting for a shield, but the author found it more convenient simply to slip the shield over *V2* and solder it to one of the socket mounting screws.
















Using the Squelch. After all of the wiring has been double-checked, turn on the receiver and let it warm up. Start with *R106* at its maximum resistance position, rotating it until the super-regenerative hiss just stops. The control is now set for proper operation and need not be readjusted until the set has been shut off and turned on once more. After you've used your new squelch circuit for a while, you'll wonder how you ever got along without it.

-30-

ELECTRONIC ANALOGY QUIZ

By ROBERT P. BALIN

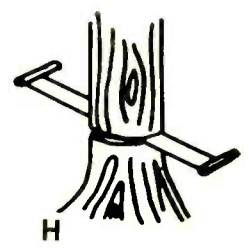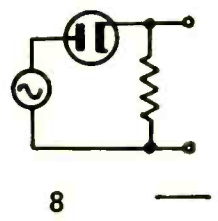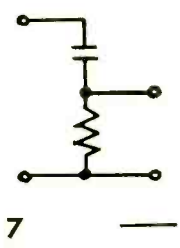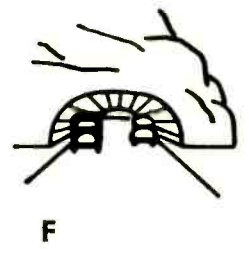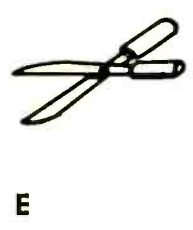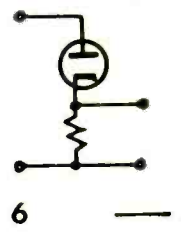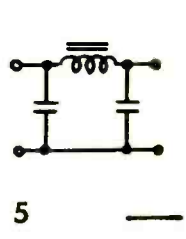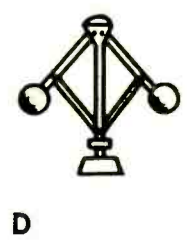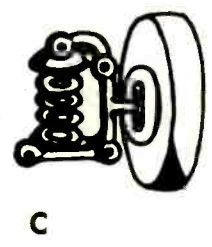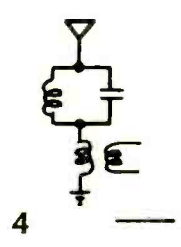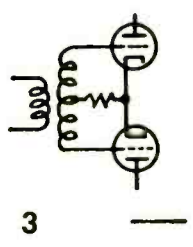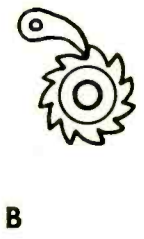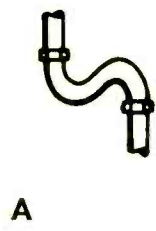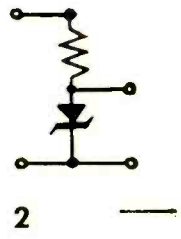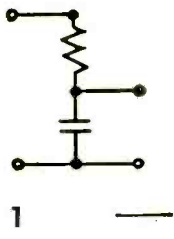Electronic circuits perform functions similar to many mechanical devices and natural phenomena, and finding an analogy between them often leads to a better understanding of both. See if you can match the numbered electronic circuits on the left with the lettered sketches on the right. Answers appear on page 124.





EQUIPMENT



Does it strike you that some home-built equipment should go back where it came from—the junk box? You can make good-looking labels from Cello-Pat, A-type or Prestype, available from your local art supplier.

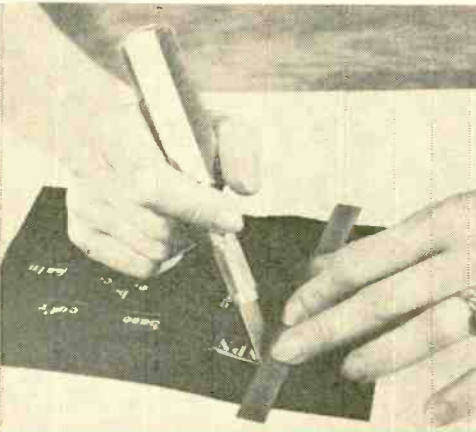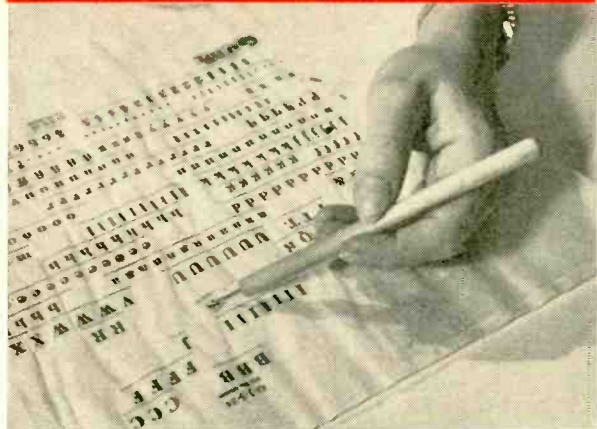Letters are printed on cellophane sheets having a weak adhesive backing. Cut them out with a needle-sharp stylus and transfer them to a sheet of transparent acetate. White paper will do if you plan to use photostat labels.



With a straight edge and sharp knife, carefully cut the individual labels from the photo negative (white lettering on black background) or photostat. Make the cuts evenly to insure that the labels will all be rectangular.



Carefully glue each label into its proper position on the instrument's panel. You can use any one of the numerous glues and adhesives that will bond dissimilar substances. Do NOT use rubber cement—the labels will peel off.


LABELING--SIMPLIFIED

By CHARLES SMITH

Align the horizontal lines printed below each letter. Watch your letter-to-letter spacing. Using a bone burnisher or the bowl end of a tablespoon, press the letters down on the acetate so that the adhesive holds them in place.



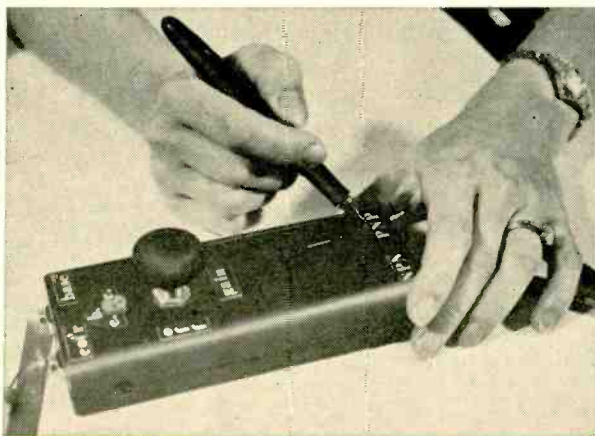
The acetate with the pressed-on letters can be used as a negative to make a contact print. Ask a photographer friend to let you use his enlarger to increase or decrease type size. Photostat copies are good but cost a bit more.



After gluing a label in place, you may find the white edge of the photo paper distracting. Paint the edge with thinned-out black nail polish or with India ink. Use a very fine brush and take care that the ink doesn't run.



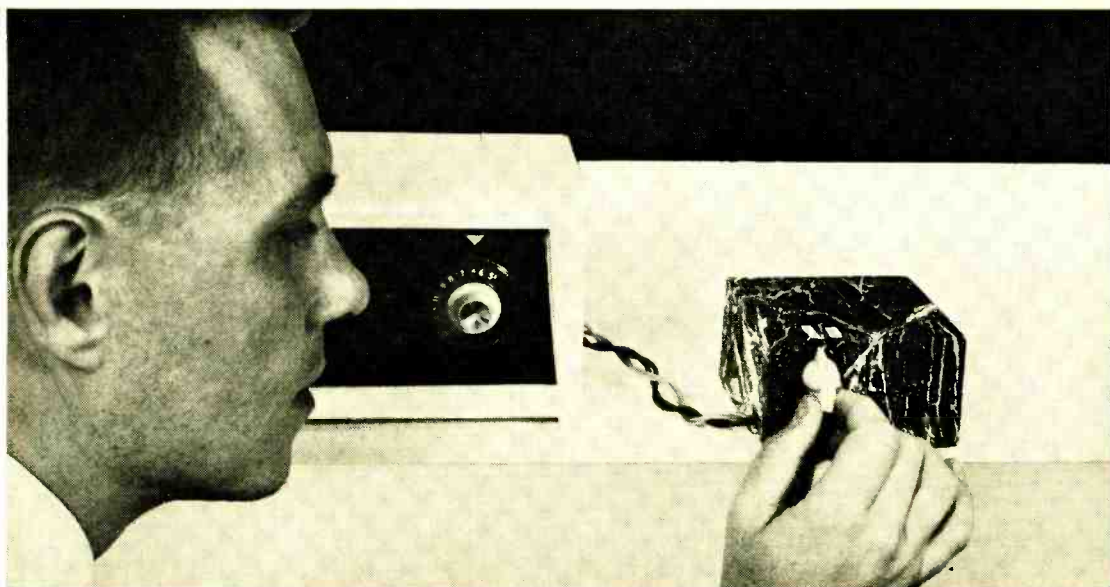A world of difference! This looks like a professional piece of equipment—one that you can proudly show to your friends and acquaintances.



RADIO DOUBLES AS INTERCOM

Hartley oscillator circuit transmits intercom signal through home receiver

By MARTIN H. PATRICK

ALMOST any home radio receiver will perform as an efficient intercom with the addition of this simple circuit. Because the intercom signal is actually "broadcast" into the receiver, it's not necessary to make extensive modifications to the radio's audio system. When it isn't in use for communication, the set can be operated normally—or even played through the remote intercom speaker. Handy to have around the house, the sensitive intercom can be used as a "baby sitter," door announcer, or paging system.



The Circuit. Transistor *Q1* is connected in a simple Hartley oscillator circuit which is tuned to the broadcast band. A PM loudspeaker, connected in series with the tap of coil *L1* and used as a microphone, supplies the modulation. The oscillator is powered by *B1*, a single penlight cell.

The receiver's loudspeaker is discon-

nected from the output transformer, and the speaker and transformer leads are connected to "Talk-Listen" switch *S2*. Also connected to *S2* is a second, remote speaker (*SPKR 1*).

Switch *S2* is so wired that, in its "Listen" position, remote speaker *SPKR 1* modulates the oscillator and the receiver speaker is connected to the output transformer. Anything spoken into *SPKR 1* is transmitted to the receiver by the oscillator and heard in the receiver speaker. In the "Talk" position, the connections are reversed—the receiver speaker does the modulating and the receiver's audio output is connected to the remote speaker.

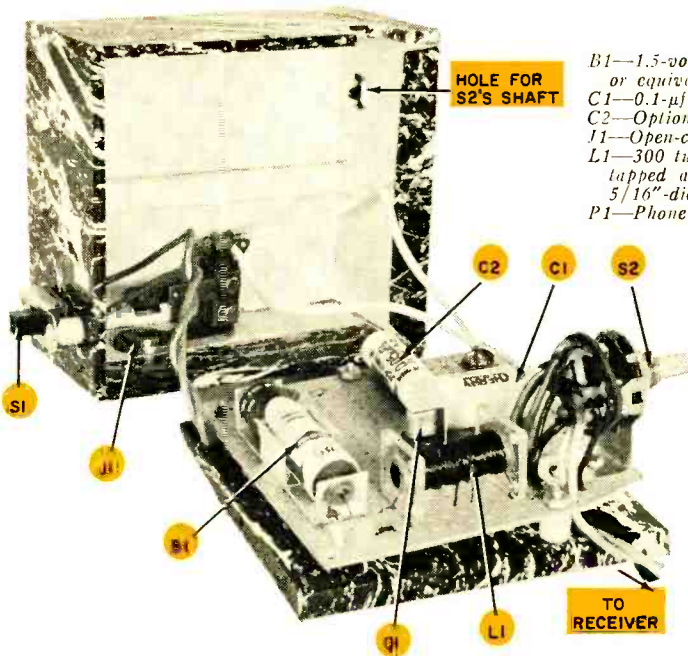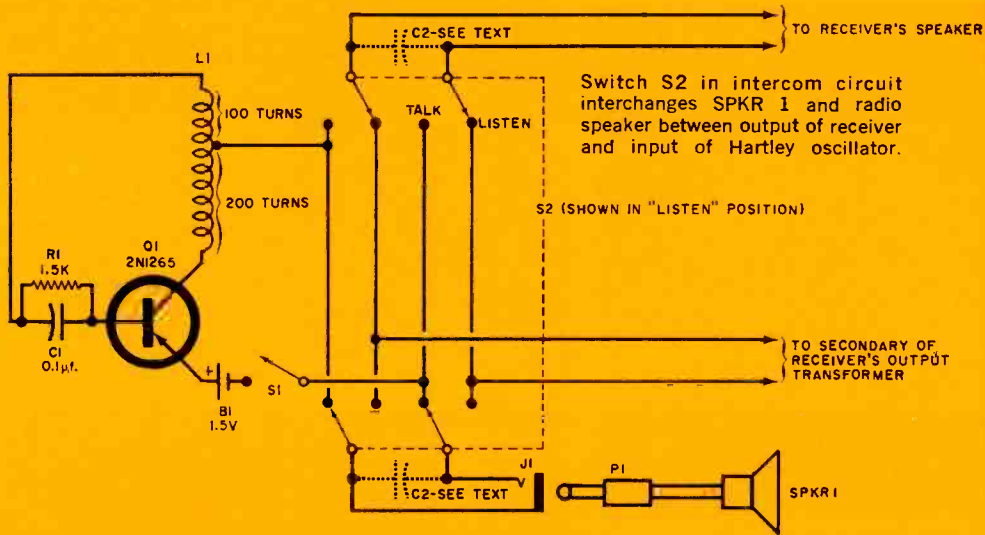Construction. First check to see that the receiver you're planning to use has a PM (permanent magnet) loudspeaker. Most of the newer sets do, but older ones are often equipped with dynamic speakers (you can recognize these units by



PARTS LIST

- B1—1.5-volt penlight cell (Burgess Type "Z" or equivalent)
- C1—0.1-µf., 200-volt paper capacitor
- C2—Optional—see text
- J1—Open-circuit phone jack
- L1—300 turns of #29 or #30 enameled wire, tapped at 100 turns, scramble-wound on a 5/16"-diameter, 1"-long form—see text
- P1—Phone plug
- Q1—2N1265 transistor
- R1—1500-ohm, ½-watt resistor
- S1—S.p.s.t. switch
- S2—4-pole, 2-position rotary switch (Mallory 3242J or equivalent)
- SPKR 1—PM speaker to match unit in radio—see text
- Misc.—3½" x 3½" perforated board, wood or plastic box, transistor socket, battery holder, enclosure and cable for remote speaker, etc.

Major components are mounted on perforated-board chassis housed in wooden box, but plastic case could be used instead.

the fact that they have four leads rather than two). Receivers with dynamic speakers are not suitable for use with this intercom circuit.

When you've got your set picked out, remove it from its cabinet and disconnect the loudspeaker from the output transformer secondary. Next, attach new sets of leads (each about three feet long) to the speaker and transformer secondary. The receiver can now be re-

installed in the cabinet with the new leads running through a convenient opening in the rear. The free ends of these leads will be connected to S2.

With the receiver modifications completed, proceed to the construction of the oscillator/control unit. The author mounted all of the parts, with the exception of switch S1 and jack J1, on a 3½" x 3½" piece of perforated board.

The board was housed in a homemade

wooden box to which *S1* and *J1* were fastened. Switch *S2*'s shaft extends outside the box through a $\frac{5}{16}$ "-diameter hole.

You can vary the construction details to suit yourself, but don't use a metal box. Coil *L2* is also the oscillator's "antenna," and to shield it in a metal enclosure would prevent the signal from reaching the receiver. A small plastic instrument case or utility box should make a good substitute.

Wiring the unit is a simple job, but be sure to keep the leads as short and direct as possible. Capacitor *C2* should not be installed at this point, since it may not be necessary (see "Operation" section).

Coil *L1* consists of 300 turns of No. 29 or No. 30 enameled wire "scramble-wound" on a $\frac{5}{16}$ "-diameter, 1"-long form. At the 100th turn, make a tap about 4" long by twisting together a loop of the wire. Bring the tap out to the end of the coil and wind the remaining 200 turns over it. The form can be cut from a piece of $\frac{5}{16}$ "-diameter polystyrene rod or tubing. A $\frac{3}{4}$ " x $\frac{3}{4}$ " plastic square glued to each end of the form retains the wire and makes a handy mounting base.

To finish up, select a remote loudspeaker (*SPKR 1*) that matches the one in the receiver as closely as possible and house it in an appropriate enclosure.

Install phone plug *P1* on the end of *SPKR 1*'s cord, plug it into *J1* on the oscillator/control unit, and you're ready to try out the intercom.

Operation. Place the oscillator/control unit so that coil *L1* is parallel to the receiver's loop antenna and as close to it as possible. Then move remote speaker *SPKR 1* into the next room (to avoid feedback) and snap on power switch *S1*. Turn on the receiver and tune in the oscillator's signal; it should be strong enough to "drown out" any broadcast station which happens to be on the same frequency.



With a friend stationed at *SPKR 1*, turn *S2* to "Talk" and speak into the receiver's speaker—your voice should come from the remote speaker. To receive an answer, turn *S2* to "Listen" and have your friend talk into the remote unit—you should be able to hear his voice through the receiver speaker.


If *SPKR 1* and the receiver speaker are well-matched, the remote and local volumes should be about the same. If they are not, you should be able to equalize them by connecting a paper capacitor, size determined by experimentation, across one speaker or the other (see *C2* in the schematic). In the author's model, a 0.05- μ f. unit was installed at *SPKR 1*. -30-

FLY SWATTER BECOMES CARTRIDGE TESTER

An inexpensive plastic fly swatter is the basis for this simple, but handy, gadget for testing phono cartridges. Cut off 10" of the swatter's handle and discard the "business end." Then tape a 30" length of standard phono pickup arm cable to the handle as shown in the photo below, installing a pair of miniature alligator clips on the short end and a phono plug on the long end. In use, the cartridge is taped to the end of the

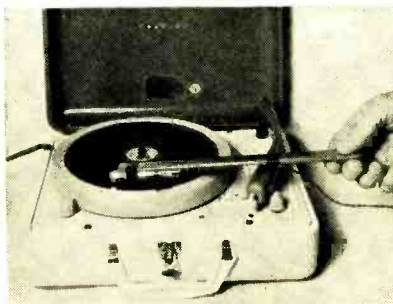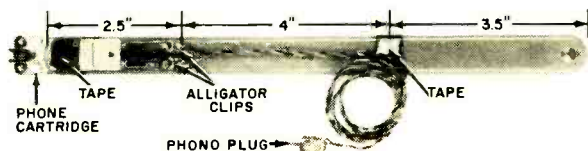handle and connected to the cable via the alligator clips. Plug the free end of the cable into an amplifier and support the cartridge over a record revolving on any turntable. —Art Trauffer



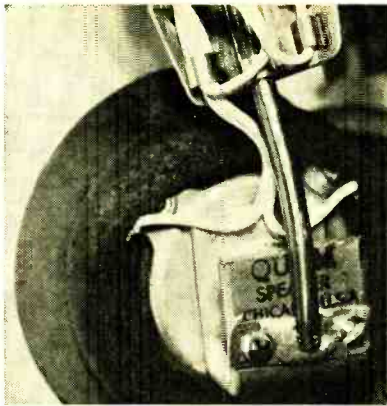

Headband bracket matches tapped holes.



Use separate leads for each speaker, and phase for best bass.

STEREO HEADSET on a BUDGET

By R. F. DRISCOLL

YOU CAN ASSEMBLE your own stereo headset for about half the price of a factory-made product. Pick up a pair of Quam 25A07N replacement speakers (they come with holes tapped in the back plate), a pair of headset cushions, and a Trimm headband. Cut the four flanges off the speakers, and fit the speakers into the headset cushions (be careful of the speaker cones) after attaching some flexible wire leads to the voice coil terminals. Attach the Trimm headband by sweat-soldering a bracket with holes to match the spacing of those already in the speakers. Connect each pair of leads to plugs, reversing the leads to one plug for best bass, then sit back and listen. -30-

Total cost of the five items you will need to make the stereo headset should be approximately \$4.60.



Speaker mounting flanges should be clipped off as shown. Enlarge holes in cushions for best response.





PEDIACOU METER

Electronic jack-in-the-box aids hearing tests of small fry

TESTING the hearing of children too young to understand the usual methods is a difficult problem. To solve it, Dr. C. Olaf Haug of the University of Texas medical school has developed an electronic jack-in-the-box.

Called a "Pediaccoumeter," the machine is equipped with seven dolls—each representing a different audio tone. The child is told (see photo sequence starting at top left) that if he hears a doll cry out and presses the button, the doll will be released.

Each ear is tested for the seven tone signals. A hidden operator controls the test via a selector switch and a master switch to prevent accidental or premature release of a doll head. Then the operator increases the strength of the tone signal until the child reacts.

With 3- and 4-year olds, the Pediacoumeter has been providing complete audiograms in 80% of the cases tested. Dr. Haug reports that evaluation of hearing deficiencies at a time when they are most easily cured can prevent permanent psychological damage to a child.

—Dennis J. Cipnic





for photographers

Bi-Slave for AG-1's

The flash bulb on your camera triggers the slave into action—providing an extra “sync-in” flash

By **JIM GOSS**

PHOTOFLASH FANS, both amateurs and pros, are always interested in adding at least one photoelectric slave unit to their lighting equipment. But the Bi-Slave is unique since it has no competitors on the market which can fire the mighty but tiny AG-1 flash bulb. (The “Bi” in the unit’s name is derived from two photoelectric cells which pick up the triggering light from the camera’s flash bulb.)


Costing less than \$16.00 to build, the Bi-Slave can be assembled in an evening.

In fact, building two or three at once adds only about one hour to the construction time because you save valuable workshop “tooling-up” time. If you make two Bi-Slaves and like to tote around a case of AG-1 bulbs (144), you’ll find that the total weight is only two pounds.

To use the Bi-Slave, you simply snap in an AG-1 flash bulb, set a switch (S1) to “on,” aim the reflector at the subject, then let the flash bulb on your camera do the rest. The Bi-Slave will



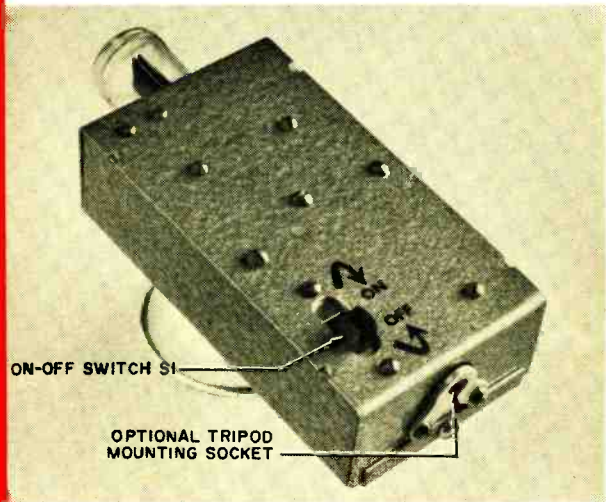Compact design keeps slave's weight down to six ounces; reflector adaptor can be removed when slave is not used. "Open Flash" switch (S2) does not fire bulb unless S1 is set at "on."



synchronize up to 1/30th of a second on X and F and up to 1/125th of a second on M sync.

The brighter the room, the shorter the distance the unit must be from the triggering flash bulb. Tests made using the AG-1 as the triggering light determined that, in normal room illumination, the slave could be 12 feet away. In semi-dark rooms, it's possible to position the slave up to 20 feet away. But this distance can be increased by using #5 or larger type flash bulbs. (Electronic flash units will not trigger the Bi-Slave because the flash duration is normally too short to activate the photoelectric-relay circuit.)

Since the two photoelectric cells face out, the AG-1 Bi-Slave can be placed on either side of the camera. An added push-button switch (S2) permits the user to trigger the slave by hand whenever open flash shots are taken.

The circuit is simplicity itself. When the series-connected photoelectric cells (PC1 and PC2) sense a burst of light, their voltage output climbs suddenly, providing a positive pulse through C1 to the base of Q1. This causes Q1 to conduct heavily and energize the relay, K1.


As the contacts on K1 close, the charge stored in C2 is discharged through the flash bulb in socket S01.

When the bulb fires, it opens C1's discharge path and B1 begins to recharge the capacitor. By the time the spent bulb is removed and a new unit installed, C1 is fully charged and set to fire again when the next pulse energizes the relay.


Mounting the parts is easy provided that you spend enough time positioning them and marking hole centers. Follow the parts layout the author used and you should have no trouble.

Punch a 3/4" hole for the reflector adaptor in the chassis box cover, centering it exactly over the location of bayonet socket S01. An off-centered hole will prevent you from mounting the reflector adaptor properly.

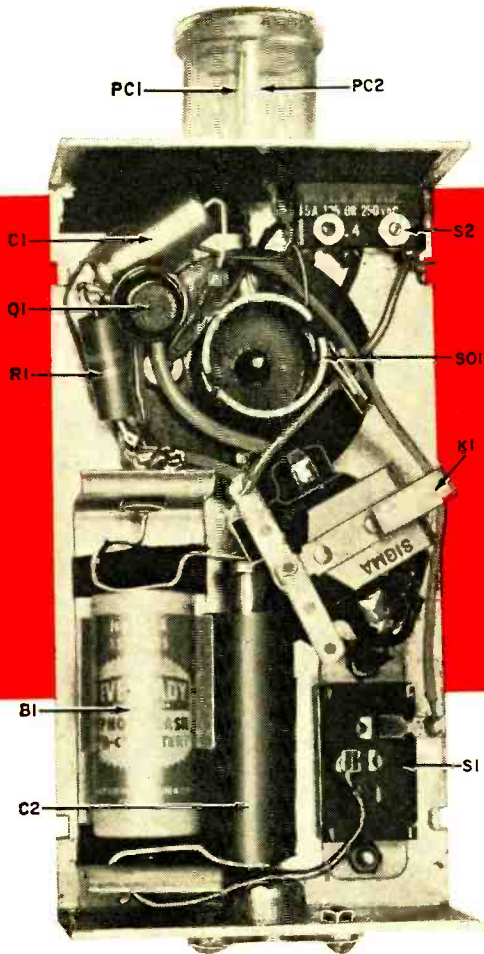Mount the two B2M photoelectric cells on top of the unit, making sure that you face the glossy-coated surfaces on the cells out to the sides. A clear plastic tube, of the type that many drugstore items come in, is cemented over the cells to protect them from accidental knocks. An optional plate tapped for a 1/4-20 thread secured to the bottom of the unit serves as a tripod socket.



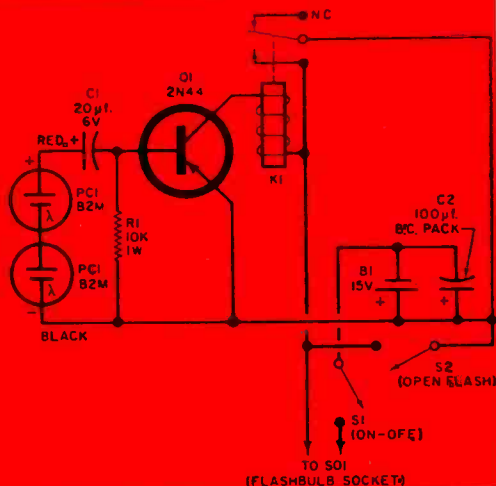Battery B1 snaps into holder springs of B.C. pack (C2) which, in turn, is mounted in the penlight cell holder. Metal shell connected to negative terminal of C2 must be taped to prevent shorts.



PARTS LIST

- B1—15-volt battery (Eveready #504 or equivalent)
- C1—20- μ f, 6-volt electrolytic capacitor
- C2—Kodak Midget B.C. pack (100- μ f.)*
- K1—S.p.s.t. relay, 1000-ohm d.c. coil, 7-ma. pull-in (Sigma 11F-1000-G/S1L)
- PC1, PC2—Solar cell (International Rectifier B-2M Sun Battery)
- Q1—2N44 transistor
- R1—10,000-ohm, 1-watt resistor
- S1—S.p.s.t. slide switch
- S2—S.p.s.t. switch, normally-open push-button type (Switchcraft Tini-Switch 951 or equivalent)
- SO1—Single-contact bayonet candelabra socket (Allied Radio 52E857 or equivalent)
- 1—Walz AG-1 reflector adaptor*
- 1—Penlight dry-cell holder (mounts B1 and C2)
- 1— $4\frac{1}{4} \times 2\frac{1}{4} \times 1\frac{1}{4}$ chassis box (LMB 101 or equivalent)
- Misc.—Wire, solder, hardware, etc.

*Available from most photographic supply stores.

Wiring up the unit introduces no problems except at the transistor leads—grip each lead with a pair of long-nose pliers between the transistor and the solder joint to prevent the heat of the soldering iron from damaging the transistor. When the wiring is finished, be sure to tape the metal shell on the B.C. pack capacitor, C2, to prevent shorting. Also, a careful check should be made for other accidental shorts and wiring errors.

To test the unit, insert the battery and secure the cover on the chassis box. Snap the Walz AG-1 reflector adaptor into the bayonet socket and plug in an AG-1 flash bulb. Then set off a flash bulb about 10 feet from the Bi-Slave, and POP!—the flash bulb in the slave should ignite. Use a new bulb and test the *Open Flash* button—it should fire the flash bulb only when S1 is "on."

Your photographic supply dealer has nondestructive test lamps that you can use in place of the AG-1 flash bulbs during these tests if you wish.

Now you are all set to take some pictures. Incidentally, if you forget to turn the unit off, don't worry about it. The battery circuit will be disconnected until you remove the burned-out bulb and put a new flash bulb in the socket.

MEET THE WINNERS!

If you read POPULAR ELECTRONICS for December, 1960, carefully, you'll remember the "Bonus for Authors" awards we outlined at that time. Checks totaling \$625.00 are now in the hands of six authors whose articles were published during the first half of 1961. As promised, "bonus payments" equal to the original purchase price of their stories were made to three of these authors. In addition, consolation checks of \$50.00 each went to the three "runners-up."



BEST "ELECTRONIC NEWS" FEATURE ARTICLE

The winner of the bonus for the most outstanding "electronic news" article in any issue of POPULAR ELECTRONICS published between January and June, 1961, is Charles Fowler. His article, "The Noise That Banishes Pain" (January, page 47), told the story of audio analgesia, including results of tests and equipment designs that he had perfected. Hundreds of readers asked for more information—especially as to where the "white noise" phonograph records could be purchased. Mr. Fowler, now a freelance writer, is probably best remembered for his long tenure as the editor of High Fidelity magazine.


A close second in this category was Ken Gilmore's story "The Truth About the Danger of Radar Waves." Although not of as great immediate personal interest as Mr. Fowler's article, the radar story was recognized as a prime example of factual reporting. Appearing in the March issue (page 41), it has since been reprinted for the U.S. Air Force safety training program.



BEST HI-FI ARTICLE

There was never any serious competition for Jim Kyle's "Sweet Sixteen" story in the January issue (page 55). This story described the construction of a speaker system using 16 five-inch speakers wired in series-parallel. For months the author was deluged with mail, while manufacturers happily sold over 12,000 speakers for use in "Sweet Sixteen's." Jim's follow-up article in the April issue (page 55) elaborating on the design of this system augmented the downpour—whetting more appetites and further deluging the author with hundreds of postcards and letters.

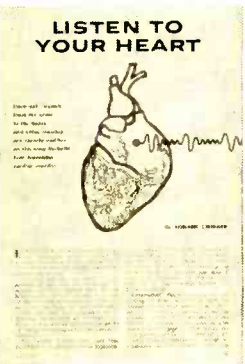Runner-up in this category was "Sinclair" for his humorous article called "On The Grid." This surprise-ending story, which appeared in our February issue (page 66), received much favorable comment.




BEST ELECTRONIC CONSTRUCTION ARTICLE

Selecting the best article in this category was not an easy job. However, reader interest definitely favored the four-transistor cardiac monitor described and built by Edward Lininger ("Listen to Your Heart," June, page 47). This device picks up the minute voltages generated by muscular action and converts them to audible sounds. Scores of readers could not resist duplicating it for friends working in the field of medicine, and it has also turned out to be a great Science Fair project.

CB'ers cast their votes for Don Stoner's "Citizens Band Q-Multiplier" (March, page 76) in such great numbers that Don is the runner-up in this category. His device sharpens the selectivity of many CB transceivers.

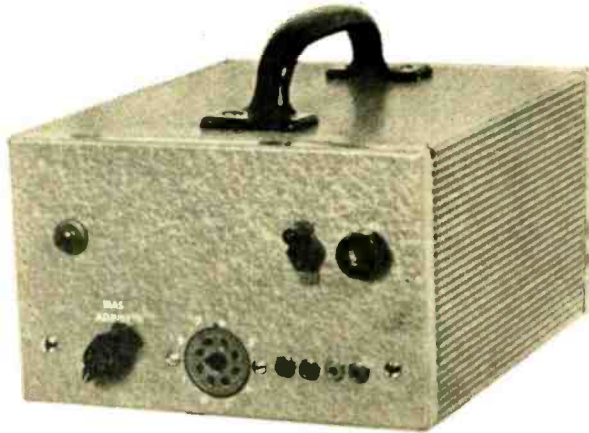Congratulations to all the winners—and thanks to all of our readers who told us about the stories they liked best



POWER A' PLENTY

Pick up your plate, screen, bias, and heater voltages from one compact supply

By **E. H. MARRINER**, W6BLZ


THIS VERSATILE bench supply is ideal for test-powering receivers, amplifiers, small transmitters, and a variety of other types of electronic gear. Designed around the now-familiar silicon diode rectifiers, it dispenses with the usual rectifier tubes and their associated filament transformers. The four d.c. outputs deliver 560 volts at 100 ma., 250 volts at 100 ma., 150 volts (regulated) at 15 ma., and 0-130 volts (negative) at 15 ma. An additional output provides 6.3 volts a.c. at 8.5 amperes.

About the Circuit. The high-voltage secondary of transformer *T1* is connected to a bridge rectifier circuit employing diodes *D1* - *D8*. Two 400-PIV diodes in series are used in each leg of the bridge, each diode pair being the equivalent of a single 800-PIV unit. Choke *L1* and capacitors *C1* and *C2* form a filter which smooths the pulsating d.c. from the rectifier circuit. The output of the filter is about 560 volts under a full load of


100 ma. Bleeder resistors *R1* and *R2* also act as a voltage-dividing network, insuring that the same voltage appears across each of the two filter capacitors.


Transformer *T1*, incidentally, has a rating of 200 ma. But this assumes the use of a standard full-wave rectifier, which delivers only about half of the transformer secondary voltage (270 volts). With the bridge circuit actually used, almost the full 540-volt secondary r.m.s. voltage is available. The power capabilities of the transformer remain the same, however, so its current load must be cut in half.

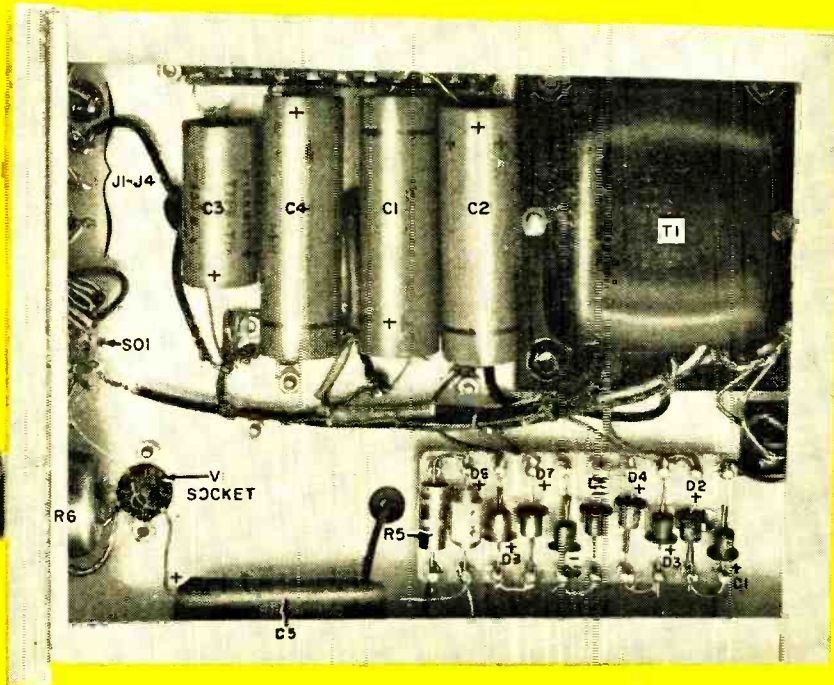The center-tap of transformer *T1* would not be used if the full secondary voltage were all that was desired. Available at the center-tap, though, is half of the bridge rectifier's output. Feeding this output through another filter system (capacitors *C3* and *C4*, choke *L2*) gives us a 250-volt, 100-ma. source. Part of this voltage is dropped, through resistor



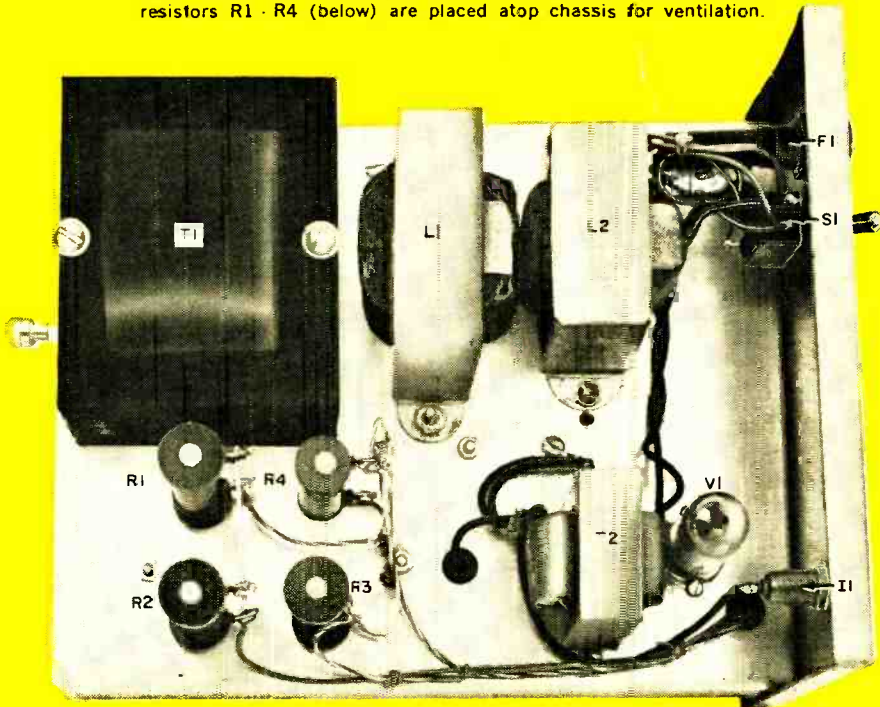Photographs of bottom and top of the power supply chassis clearly show parts layout and most wiring details. Capacitors C1 - C4 (above) are mounted on terminal strips. Wiring of diodes D1 - D9 and resistor R5 is simplified by use of a terminal board. Power resistors R1 - R4 (below) are placed atop chassis for ventilation.



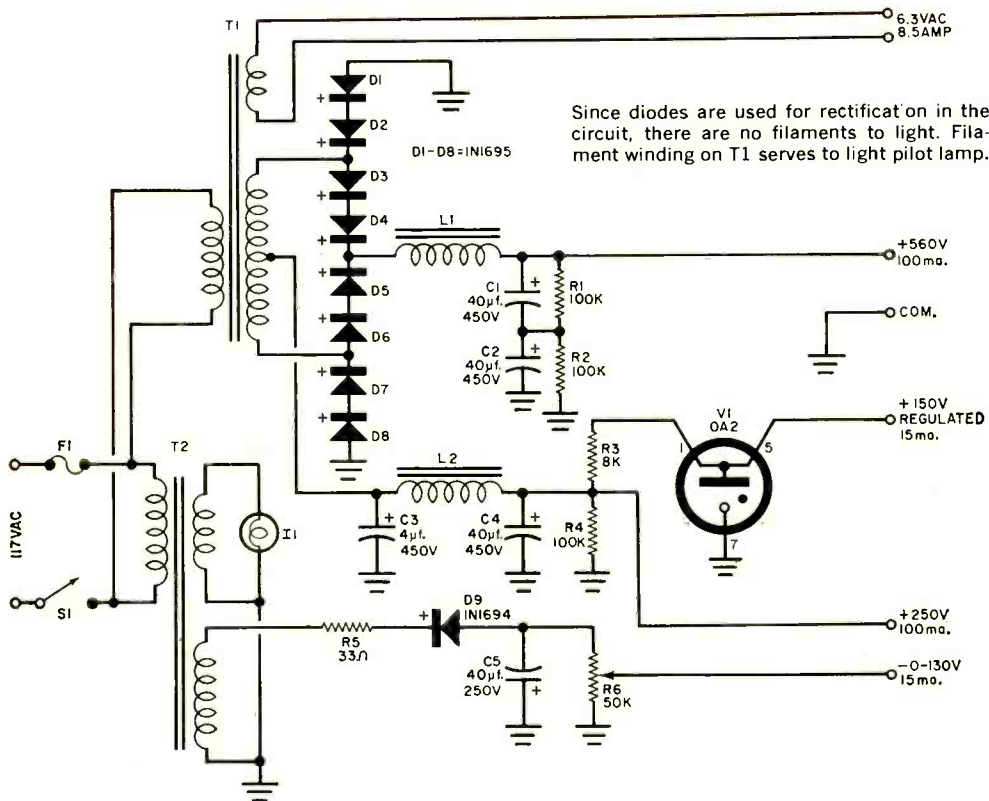

Since diodes are used for rectification in the circuit, there are no filaments to light. Filament winding on T1 serves to light pilot lamp.

PARTS LIST


- C1, C2, C4—40-µf., 450-volt electrolytic capacitor
- C3—4-µf., 450-volt electrolytic capacitor
- C5—40-µf., 250-volt electrolytic capacitor
- D1 - D8—1N1695 diode or equivalent
- D9—1N1694 diode or equivalent
- F1—3-ampere, 3AG fuse
- I1—6-volt pilot lamp (G.E. Type 47 or equivalent)
- J1, J2, J3, J4—Insulated tip jack
- L1—2.3-henry, 150-ma. filter choke (Stancor C2304 or equivalent)
- L2—8-henry, 100-ma. filter choke (Thordarson 20C53 or equivalent)
- R1, R2, R4—100,000-ohm, 20-watt, wire-wound resistor
- R3—8000-ohm, 5-watt, wire-wound resistor
- R5—33-ohm, 2-watt resistor
- R6—50,000-ohm, 1-watt potentiometer
- S1—S.p.s.t. toggle switch
- SO1—Octal socket
- T1—Television replacement power transformer; primary, 117 volts; secondaries, 540 volts CT @ 200 ma., 5 volts @ 3 amperes (not used), 6.3 volts @ 8.5 amperes (Stancor P-8172 or equivalent—see text)
- T2—Power transformer; primary, 117 volts; secondaries, 125 volts @ 15 ma., 6.3 volts @ 0.6 amperes (Stancor PS-8415 or equivalent)
- V1—0A2 tube
- 1—Chassis-cabinet combination (California Chassis LTC-463 or equivalent—see text)
- Misc.—Binding post, fuse holder, pilot light assembly, terminal strips, terminal board, grommets, solder lugs, line cord and plug, insulating washers for R1 - R4, etc.

R3, across an 0A2 regulator tube (V1), providing a 150-volt, 15-ma., regulated output. Resistor R4, of course, is a bleeder for the filter system.


It should be kept in mind that the 560-volt, 250-volt, and 150-volt outputs are all drawn from the same power transformer (T1). To avoid overloading T1, the combined loads on these outputs should not exceed about 100 ma.

A separate transformer (T2) is the basis of an independent bias supply delivering 0-130 volts (negative) at 15 ma. Diode D9 (protected by current-limiting resistor R5) and capacitor C5 do the rectifying and filtering. Potentiometer R6 controls the voltage. The 6.3-volt winding on transformer T2 powers pilot light I1, and is not used for anything else.

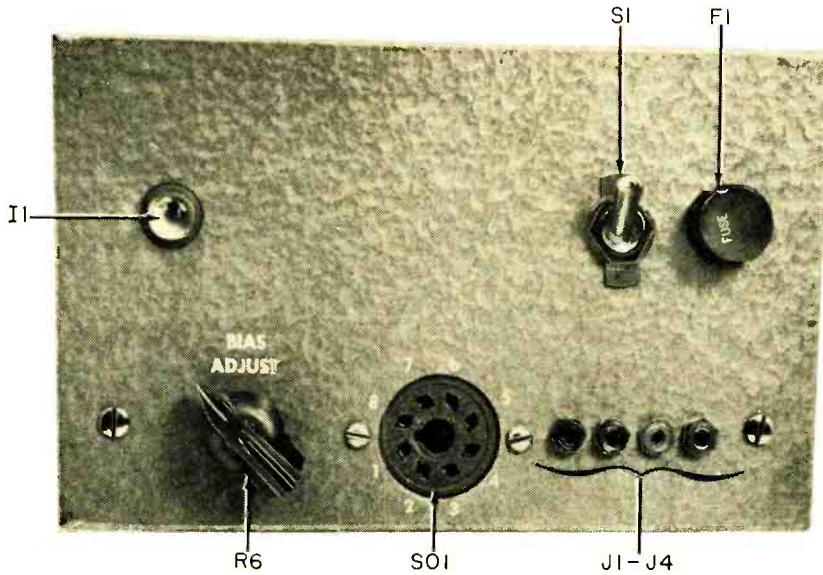All of the outputs from both transformers are brought to an octal socket (SO1) located on the front panel. In addition, the four d.c. outputs are connected to monitoring jacks (J1 - J4), so that voltages may be measured while a load is plugged into SO1. A grounded



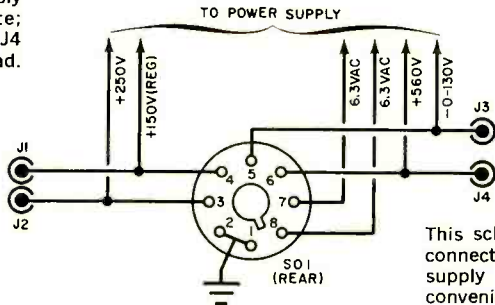Front panel of power supply is simple, yet complete; SO1 is output socket, J1-J4 allow metering under load.



This schematic shows how author connected SO1 and J1-J4 to power supply outputs, but any other convenient arrangement will do.

binding post for use with the monitoring jacks is on the rear lip of the chassis.

Construction. The author housed the power supply in a chassis-cabinet combination (Model LTC-463) available from the California Chassis Co., 5445 E. Century Blvd., Lynwood, Calif. The chassis measures $1\frac{1}{2}'' \times 6\frac{1}{16}'' \times 8\frac{1}{16}''$ and the $4\frac{1}{2}'' \times 7\frac{3}{16}'' \times 9\frac{3}{16}''$ perforated cabinet is fitted with a $4\frac{1}{2}'' \times 7\frac{1}{4}''$ front panel. (Any similar unit may be used.)

Switch *S1*, the fuse holder, and pilot light *I1* occupy the upper half of the front panel. Potentiometer *R6*, socket *SO1*, and jacks *J1-J4* are mounted through matching holes in the chassis front and lower front panel.

On top of the chassis are transformers *T1* and *T2*, chokes *L1* and *L2*, tube *V1* and resistors *R1-R4*. (Transformer *T1* in the author's model is a Philco 32-8673 TV replacement unit which was purchased at a surplus sale; an exact Stan-

cor equivalent is indicated in the Parts List.) It may be necessary to remove *T1*'s top cover to provide clearance for the chassis to slide into the cabinet. Resistors *R1-R4* are held down with long machine screws passed through their centers—insulating washers on the ends of the resistors prevent shorts to the screw heads and the chassis.

The rest of the components are mounted beneath the chassis. Diodes *D1-D9* and resistor *R5* are wired to an insulated terminal strip. Capacitors *C1-C4* are fastened to a system of terminal strips and solder lugs bolted to the chassis.

To make a neater looking job, the author cabled most of his wiring. This is not necessary, however, and the leads may be routed in the most convenient manner. Be sure, though, to use rubber grommets to protect all leads passing through the chassis.

On the Citizens Band



By **DICK STRIPPEL**, 2W1452

ALONG ABOUT the end of this year, Citizens Band licensees should pass the quarter-million mark: applications have been pouring into the FCC at the rate of better than 10,000 per month. And with all this activity on the band, many users have been giving serious thought to possible ways of reducing or eliminating interference.

Back in June, 1961, mention was made in this column of an inexpensive "scrambler" that was being developed for CB use. Since then, we have heard of another such device being readied for the market.

It's possible that enterprising CB'ers with the required electronics knowledge will be building adapters for their sets that will trip a squelch control when a certain coded signal is received. The use of tone signals to establish voice communication is permitted by the FCC, so perhaps we could borrow a page from the radio control boys and come up with something of this sort.

Here are two other "blue sky" ideas for gadgets which might stimulate some thinking among our readers who have construction experience:

- an adapter which would not only "open" the receiver when a certain signal was received, but would also indicate, perhaps by a flashing light, when the channel was in use by other parties.

- a device, possibly using a telephone dial, which could single out one of a group of mobile units, or permit a call from one mobile station to the base station without other mobiles hearing it.


If foolproof units of this nature could be developed, which the average electronics hobbyist could build from readily obtainable parts, your CB Editor would like to be one of the first to know.

Tech Notes. From Almon Hyrum Clegg of Provo, Utah, comes this idea for a base-loaded mobile antenna. He says that it cost him about \$2.00 and

has given excellent results through snow, rain and hot sun.

The loading coil is wound on a 5" length of broom handle or dowel stock with .209" galvanized wire, and has 24 turns; leave 3 1/2" leads on the coil. Drill a 1/8" hole to a depth of 1 1/2" in one end of the coil form and insert a 38" length of spring steel wire. Then wrap the coil end around the wire whip and solder securely.

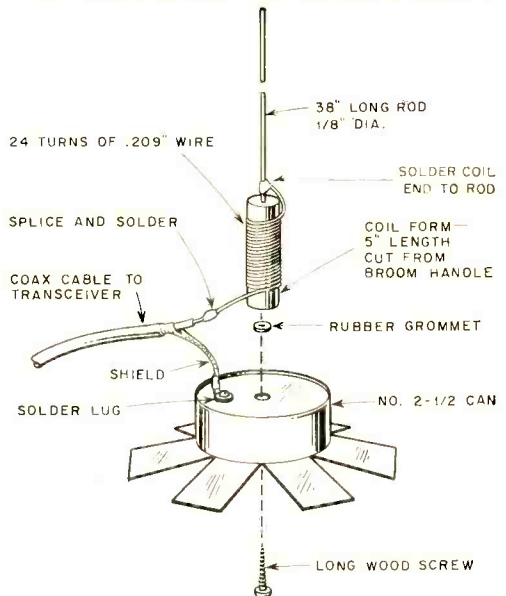Mount the coil and whip on the end of a No. 2 1/2 can (soup can), using a long wood screw, and insert a rubber



grommet between the top of the can and the bottom of the coil for a shock absorber. With tin snips, cut the sides of the can to within one inch of the top and "flange out" the strips thus formed. Attach the center conductor of a length of coaxial cable to the free lead from the loading coil, and connect the coax braid—with a solder lug—to the can.

Now mount the antenna on the auto-
(Continued on page 112)

How to talk to Non-Hams

By FRED E. EBEL, W9PXA

IT HAPPENED during one of those awkward conversational vacuums abhorred by party hosts. My host, an up-and-coming insurance man, suddenly turned to me and said, "I understand you're a radio ham."

I produced one of those it's-really-nothing type of smiles. But secretly I was flattered. All eyes were on me, including those of three beautiful young ladies. And then came the question that must come to all hams at one time or another.

"What do hams talk about?"

My interrogator was a platinum blonde. When our eyes met, it was like an a.f.c. locking circuit. We resonated.

"Well," I began, "take that QSO—that means talk—I had with a ham in India the other day. He—"

"I know, I know!" broke in a bearded chap who had just recited some weird poetry while tapping a bongo rhythm on his knees. "This fellow had just been bitten by a king cobra. Your message made it possible to fly in antitoxin in the nick of time."

"No, this ham lives in the Himalayan country—"

The blonde squealed. "The home of the

man-eating tiger. The tiger had attacked a native and was roaming the village for its next victim. The ham wanted you to send in professional hunters."

I winced. "No, no, no! This ham was just an ordinary postal clerk. He gave me an S9 report and said my modulation was tremendous."


I had delivered this information with considerable heat. But all I saw were blank expressions. Perhaps they didn't understand. I cleared my throat. "You see, this ham was on the other side of the world, yet he gave me that wonderful S9 report. It meant I was really barrel-ing in."

Another of those vacuums resulted. My host smiled through clenched teeth. His words would have made good battery acid. "How *very* interesting. Please tell us more."

"Yes," a pretty redhead said, "tell us, what do hams *really* talk about?"

I searched my brain for a typical example. I had it. A very interesting QSO during which my DX contact had successfully made two transmissions, though his antenna had fallen to the deck of the ship.

I managed a smile, then: "I once

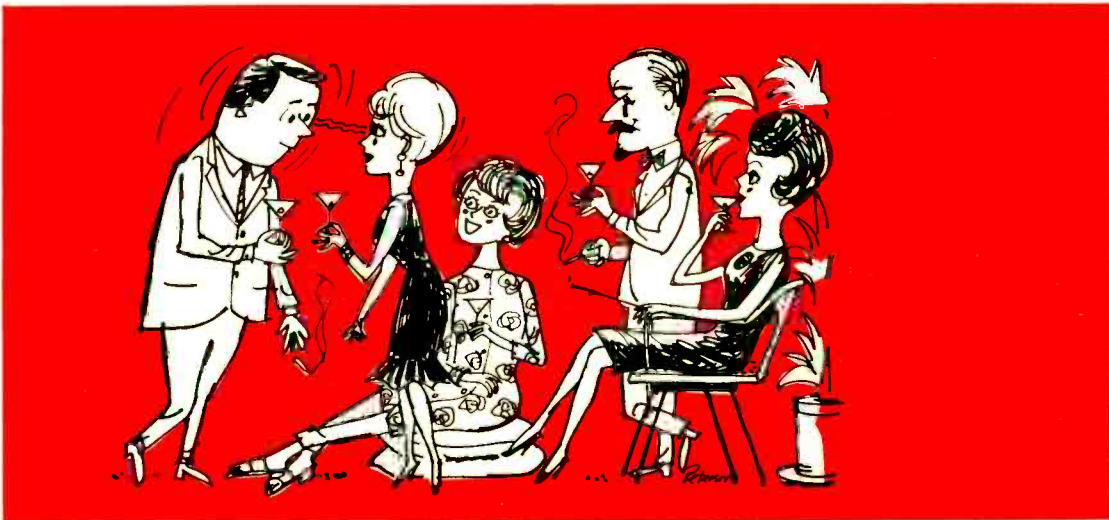

talked to a ham who was the radio operator on a tramp schooner that was crossing the South China Sea, and here's the interesting part—"

"The ship was caught in a typhoon, sinking fast. But thanks to your quick action, port authorities were notified and a rescue ship got there just in time," said the redhead, beaming like a quiz kid.

I wiped my brow, counted down from x minus nine to zero before I answered. "No, the interesting part was that the antenna wasn't in the air. It was lying on—" But I got no further.

"I know," blurted a shiny-eyed guest. "Mutiny had broken out on the ship. The captain already was bound to the mast and the crew of cutthroats was trying to get to the radio operator!"

The circuits in my brain shorted out. I jumped to my feet and ran out as I screamed: "Yes, that was it. Mutiny! The crew had gone berserk. The typhoon had ripped open the cages of the wild-animal cargo. Three gorillas, two tigers, an elephant, and five cobras were loose. The boiler had just exploded, and—and—" But the rest of my words were lost in the wind as I raced home, hat-and coat-less.

HOW LONG I stood behind the closed door of my apartment having visions of two men in white coats coming to get me, I don't know. But finally, letting out a huge sigh of relief, I sank into an easy

chair, after automatically switching on the TV set. It was time to review the past events with analytic calm. What had happened? What had caused me to blow my top?

Breaking into my thoughts came an excited voice . . . "CQ emergency! CQ emergency."

I looked up. There on the television screen, parka-clad and kneeling next to a dog sled, was a man speaking into the microphone of an emergency transceiver.

Then a cut to the radio shack of a young operator. "Read you loud and clear, old man. What is your message?"

Cut back to the frozen north. "Dogs broke loose, partner broke legs in crevasse fall, wolves closing in. Need immediate help! Our position is—"

I switched off the TV, smiled. Of course, that was it. The public is conditioned to make-believe hams who have exciting adventures. For them, no talk about weather or technical stuff. These fictional hams are men of action, their conversation laced with "Medical help on the way" . . . "Stand by for instructions on emergency appendix operation. . ."

An idea played around in the back of my head. Why not give my friends a show? They wanted drama. I would give them drama. Hama-drama!

I immediately wrote a dramatic sketch of exciting, imaginative ham adventures and put it on tape. Being a mimic, I had


(Continued on page 122)



STEREO-itis

STEREO


as it affects *Cullen*

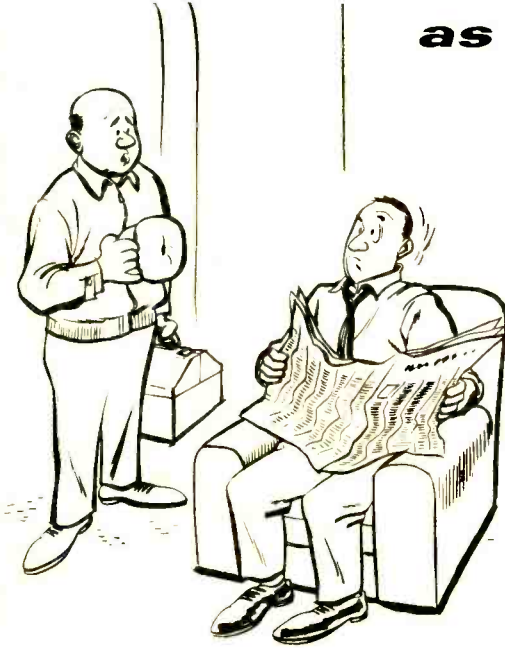

"I'm sorry to report that your living stereo . . . has died."



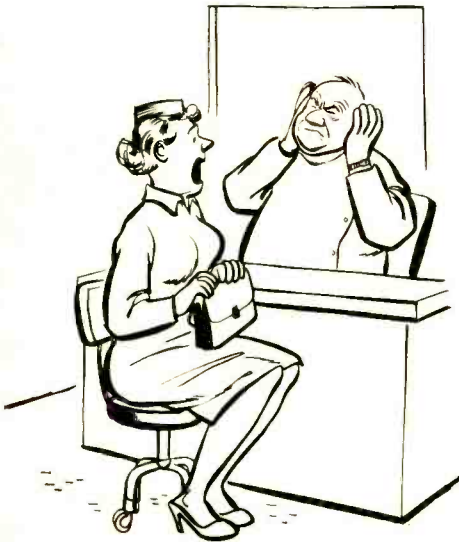"I'd like to try that anesthesia by stereo, but all I have are Desi Arnaz records."



"It's about my husband and that damn stereo, Doctor."



"With three women in the house, I don't think I could stand stereo."



Across the Ham Bands

By
HERB S. BRIER
W9EGQ

DX'ING AND THE SUN

THE MOST EXCITING PART of ham radio for many old-timers and newcomers alike is working distant places (DX'ing). But, according to some of the stories heard on the ham bands lately (quoting or misquoting various authorities), the days of good DX conditions are gone for the next 5 to 50 years. These reports are based upon the decline of the present 11-year sunspot cycle and predictions that solar activity in the next few cycles will be low.

Actually, such pessimism is not justified. While the 10- and 15-meter ham bands are gradually becoming less reliable for regular long-distance work (say 700 to 12,000 miles), they will improve again in a few years. More important, DX conditions on the 40-, 80-, and 160-meter ham bands are good right now, and are getting better.

As we enter the 1961-62 DX season, 15 meters is livelier during the day than it was a few weeks ago, and even 10 meters occasionally shows some signs of life. In general, though, 20 meters remains the best daytime DX band. As day turns into night, however, these bands usually go dead, leaving only 40, 80, and 160 meters useful for regular DX work. Fortunately, static is now low on these bands, and nighttime signals from remote points are plentiful.

Ionization Effects. High-frequency radio waves, like light waves, travel in straight lines. Therefore, the curvature of the earth would limit our communications range to line-of-sight distances if these waves could not be 'bent' in some manner. Obviously, they can be . . . and this is where the sun comes in.

As the sun's rays beat down towards the earth, they ionize the atoms in the "ionosphere," a region located between about 45 and 300 miles above the earth.

These ionized particles gather together in layers, called the D, E, F1, and F2 layers, located at average heights of 45, 70, 140, and 200 miles, respectively, above the earth. At night, the D and E layers usually disappear completely, and the two F layers combine in a single layer approximately 175 miles high.

If the ionization is intense enough and the frequency is not too high, radio signals striking these layers are gradually bent, or refracted, back towards the earth. The D and E layers, being the

Novice Station of the Month

Danny Weatherman, KN9ZGQ, Waveland, Indiana, submitted the winning photo in this month's contest. Danny has worked 22 states so far with his Johnson "Adventurer" transmitter and Hallicrafters SX-43 receiver. His paper route and neighborhood odd jobs pay for his ham equipment, and he's saving now for a new transmitter to go with his General Class license—which is on the way.

Danny will receive a 1-year free subscrip-



tion to P.E. for his photo. If you'd like to try for a similar award, send us a picture of your station—preferably with you at the controls, and include some information about yourself, your equipment, and your activities. Maybe you'll be one of the lucky winners. Entries should be sent to Herb S. Brier, c/o POPULAR ELECTRONICS, P.O. Box 678, Gary, Indiana.

farthest from the sun, are the least highly ionized. Frequencies above 7 mc. usually blast right through them. On good days, however, frequencies up to about 30 mc. are "fielded" by the F2 layer and reflected back to earth.

"Skip" Conditions. The distance between the transmitter and the point where the signal returns to the earth is called the "skip distance." Depending upon the height of the reflecting layer and the angle at which the signal strikes it, the skip distance varies from as little as zero miles on 80 meters in the daytime to over 500 miles at night. On 40 meters, daytime "skip" is currently over 500 miles, increasing to over 1000 miles at night;

during periods of intense sunspot activity. Since the sun is actually closer to the earth in winter, daytime m.u.f.'s are higher in winter than in summer. Winter days are short, however, and the m.u.f. starts decreasing as the sun sets—therefore, winter night m.u.f.'s are low.

Other Effects. Unpredictable solar explosions and magnetic storms (the latter often accompanied by visible *aurora borealis* displays) may blank out all DX signals for days at a time. On the other side of the ledger, intensely ionized patches often suddenly appear, near the height of the E layer, at any hour of the day or night, summer or winter. They will reflect signals, over distances up to

"Ike" Kisilevich, PJ2CR, P.O. Box 533, Curaçao, Dutch West Indies, spends most of his time on 15 meters. He's trying to work all states with his screen-modulated Globe Chief De luxe—he QSL's 100%. More details on PJ2CR appeared in last month's "News and Views."



and on 20 and 15 meters, minimum "skip" is currently around 1000 and 1500 miles, respectively.

The maximum distance that can be covered in a single hop is approximately 2500 miles, representing a signal transmitted on a tangent to the earth and reflected by the F2 layer. Actual "one-hop" distances are usually less than this ideal figure, but the signal is not restricted to a single hop. It may bounce between the earth and the ionosphere several times, vastly increasing the transmitting range.

The highest frequency that can be used for "skip" communication between two specified areas is called the maximum usable frequency (m.u.f.). The m.u.f., depending as it does on the degree of ionization in the ionosphere, is highest

1400 miles, on frequencies up to 70 mc. Scientists call this phenomenon "sporadic-E propagation." Hams call it "short skip."

The sun also agitates the molecules in the "D region," the lowest of the ionized layers. The only effect of the D region seems to be to absorb low-frequency radio signals. Fortunately, it dissipates rapidly with the setting sun, which is why 80 meters improves so rapidly as dusk arrives.


LOW-PASS FILTER REDUCES TVI

If your transmitter is reasonably well shielded, yet still radiates v.h.f. harmonics which interfere with your own or your neighbor's TV receiver, a low-pass filter may be the answer to your problems. The 50-ohm unit described here

works on all ham bands up to and including 10 meters. It also covers the 11-meter Citizens Band.

A model of this filter was connected to a 150-watt transmitter which had been seriously interfering with a TV set located five feet away. It reduced the TVI to a negligible amount—and a \$17.00 commercial low-pass filter, connected to the same rig, did no better. The unit is easy to put together and, if built according to instructions, requires no adjustment after completion.

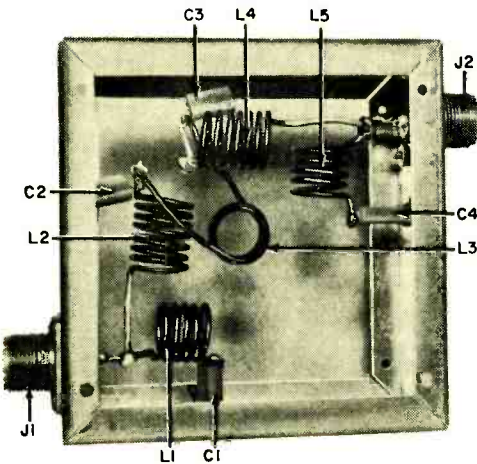Construction. The low-pass filter shown here is built in a 4" x 4" x 2" aluminum utility cabinet. The input and output connectors (*J1* and *J2*) are mounted on




diagonally opposite sides of the box, approximately $\frac{3}{4}$ " in from the corners. Next, four holes are drilled, one on each 2" side of the box, to accommodate 6-32 screws for fastening the solder lugs to which the silver mica capacitors (*C1*, *C2*, *C3* and *C4*) are grounded. The lugs for grounding *C1* and *C4* are positioned approximately $1\frac{1}{2}$ " away from *J1* and *J2* respectively; those for grounding *C2* and *C3* are positioned approximately $2\frac{1}{2}$ " away (see photo).

After winding the five coils (see data in Parts List), carefully scrape and tin their leads. Also scrape the capacitor leads clean. These preparations permit rapid soldering of the connections, so the values of the capacitors will not be changed by excessive heat. Position the coils as shown in the photo to minimize

coupling between them, and cut the capacitor leads as short as possible.

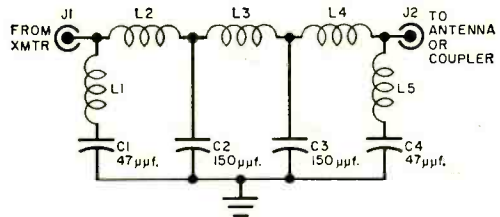Installation. Screw the covers on the box and, for best results, bolt the unit directly to the transmitter case. Use the minimum practical length of coaxial cable between the output connector of the transmitter and the input connector of the filter. You may be able to get



Low-pass filter circuit is quite simple, but parts placement and lead length are critical. If you use the layout shown and follow the instructions carefully, the filter should require no adjustment after it has been completed.


PARTS LIST

- C1, C4*—47- μ f., 5% silver mica capacitor (Cornell-Dubilier Series 22R or equivalent)
- C2, C3*—150- μ f., 5% silver mica capacitor (Cornell-Dubilier Series 22R or equivalent)
- J1, J2*—Chassis-type coaxial receptacle (Amphenol 83-1R or equivalent)
- L1, L5*—5 turns } wound from #14 enameled
- L2, L4*—7 turns } wire, $\frac{1}{2}$ " inside diam-
- L3*—8 turns } ter, 8 turns per inch
- I*—4" x 4" x 2" aluminum utility cabinet (Bud AU-1083 or equivalent)
- Misc.*—Solder lugs, screws, nuts, etc.

away without any cable at all by using an appropriate combination of coax fittings. Connect the coaxial line from the antenna or antenna coupler to the output connector of the filter.

The filter is designed to work with 52-ohm coaxial cable such as RG-8/U or RG-58/U. If the SWR on the line is low (under 2:1), the unit will safely handle 50 watts on 10 meters, over 100 watts on 15 meters, and over 200 watts on 20 meters or lower. Although tests were made at 150 watts input on 10 meters for short periods of time, regular operation at this power level would probably have resulted in blown capacitors.

(Continued on page 115)

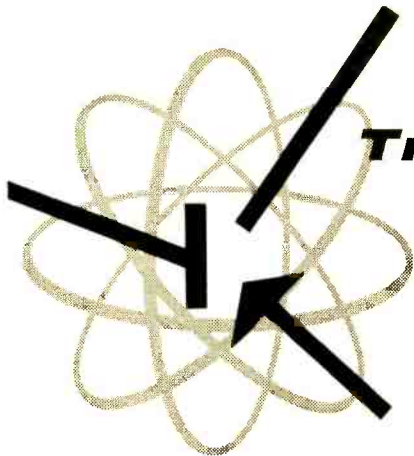


Transistor Topics

By LOU GARNER

NEW photoelectric semiconductor devices have been announced by two manufacturers: Philco (Lansdale, Pa.) and Solid State Products (1 Pingree St., Salem, Mass.). The Philco GAU-401 is a gallium arsenide photovoltaic detector with greater sensitivity than related devices such as photomultiplier tubes and silicon photodiodes, while the Solid State Products' "Photran" is basically a *pnpn* semiconductor switch that can be triggered by light energy instead of (or in addition to) an electrical signal.

Philco's GAU-401, shown in Fig. 1, provides high sensitivity for both visible and near-infrared radiation and, unlike conventional photodiodes, does not suffer a loss of sensitivity when exposed to daylight. In addition, it can be used at operating temperatures up to 120°C with no loss of sensitivity. The detector crystal itself is mounted in a standard

Fig. 1. Philco's GAU-401 photovoltaic detector uses standard TO-18 case modified to pass light.

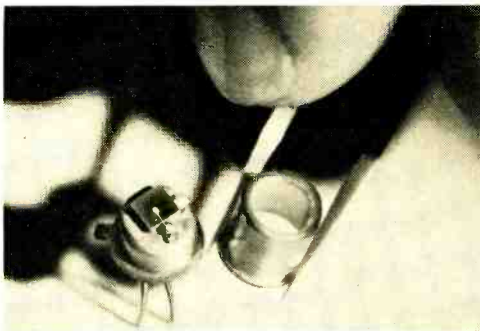

TO-18 transistor case, modified by the addition of a small glass window.

Not yet in full production, the GAU-401 carries a price tag of \$100.00 (each) in small quantities. As with other semiconductor devices, this price will probably drop considerably when mass production is started.

In contrast to the GAU-401, which is essentially a photovoltaic cell, the "Photran" is roughly analogous to a light-controlled thyatron. Before light strikes its sensitive area, it is in a high-impedance (over 10 megohms) "off" state. When a light impulse is applied, it switches rapidly to a low-impedance (under 10 ohms) "on" condition and will remain "on" indefinitely until turned off electrically. The light signal used to trigger the Photran need only be a momentary pulse. In some respects, the operation of the Photran is similar to that of the "Dynaquad" discussed in the September column, except that light rather than a base current impulse provides the initial triggering signal.


Typical Photran circuit arrangements are given in Fig. 2. Component values are not shown, since they will vary with the type of Photran, the supply voltage, the sensitivity desired, and the nature of the load. In Fig. 2(A), a d.c. power source is used, and the Photran acts as a light-actuated latching relay. When light strikes the device, power is applied to the load. Since the Photran continues to conduct even when the light is removed, an s.p.s.t. "reset" switch is provided to turn load power "off."

On the other hand, if an a.c. power source is used, as shown in Fig. 2(B), the Photran will provide half-wave rectified d.c. to the load when light is applied and no power when the light is removed. The Photran itself will not conduct during negative half-cycles whether or not light is applied; this means that it is

turned "off" automatically on alternate half-cycles, eliminating the need for a special "reset" switch.

A variation of the a.c. control circuit is shown in Fig. 2(C); here, power is applied to the load *only* when there is *no*

Fig. 2. Three typical circuits incorporating Solid State Products' "Photran." See text for details.

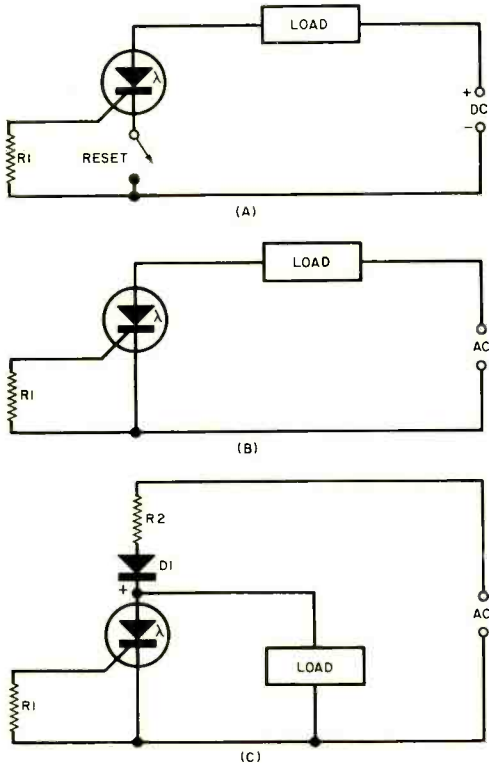

light on the Photran, and is removed when light strikes the unit.

As of this writing, prices range from \$14.00 for a 15-volt Type 3P15 Photran to \$46.00 for a 200-volt Type 3P200. In all types, the maximum continuous forward current (d.c.) is 300 ma., but 8-millisecond pulses of up to 5 amperes can be handled.

Both the GAU-401 and the Photran have potential applications in light sensing and measuring instruments, in automatic controls, in burglar alarms, and in some types of computers. As far as the hobbyist is concerned, these new units might be used in such items as automatic door openers, annunciators, automatic

light dimmers for automobiles, automatic light switches for the home, special types of light meters for photography, and . . . whatever an active mind can devise.

Reader's Circuit. The majority of low- to medium-priced commercial transistor testers are designed to make *static* tests, i.e., checks of the transistor's basic *d.c. characteristics*. In general, leakage is checked by applying a d.c. voltage to one pair of electrodes and noting current, while gain (or *beta*) is determined by applying a fixed d.c. base bias and comparing it to the corresponding collector current. A *dynamic* tester, on the other hand, checks the transistor's *a.c. characteristics*, i.e., its ability to amplify a small a.c. signal. Most dynamic testers are relatively expensive and are designed primarily for precision laboratory tests.

Seeking a simple technique for performing dynamic tests in his own workshop, reader E. S. Millman, W3WNE (5700 Ogontz Ave., Philadelphia 41, Pa.), has devised an interesting dual-purpose instrument: an easy-to-build and inexpensive transistor checker that can "double in brass" as a code practice oscillator. The circuit he used is shown in Fig. 3.

Assuming that a transistor is connected to the base (*B*), emitter (*E*), and collector (*C*) leads, we see that the unit is basically a modified Colpitts-type audio oscillator. Base bias is provided by voltage divider R_1 - R_2 , while R_3 serves to

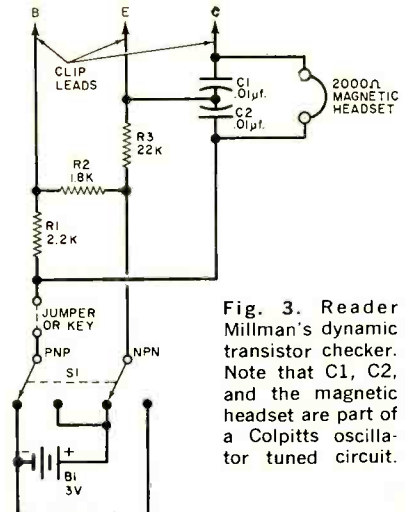


Fig. 3. Reader Millman's dynamic transistor checker. Note that C_1 , C_2 , and the magnetic headset are part of a Colpitts oscillator tuned circuit.

isolate the emitter electrode and to stabilize operation. The feedback necessary to start and maintain oscillation is furnished by a "tapped" capacitor made up of two units, $C1$ and $C2$, in series; $C1$ and $C2$ form a resonant circuit with the inductance of the magnetic headphones used as a collector load. Operating power


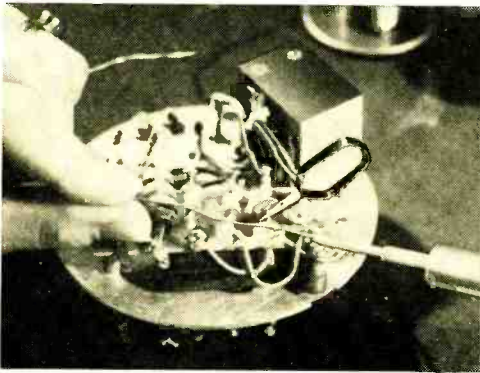


Fig. 4. Hunter Tools' miniature clip-on heat sink.

Fig. 5. MacDonald & Company's "Little Joe" units.

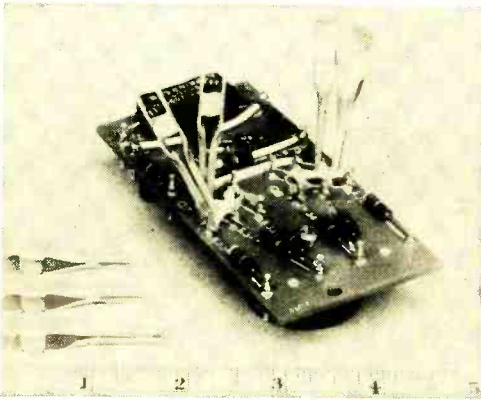

is furnished by a 3-volt battery, $B1$, through a polarity reversing switch, $S1$, to permit checks of both *pnp* and *npn* types.

A duplicate instrument can be assembled in a single evening without trouble. All components are readily available and neither layout nor lead dress should be critical. Resistors $R1$, $R2$ and $R3$ are half-watt units; capacitors $C1$ and $C2$ are small paper or ceramic types, working voltage non-critical; and switch $S1$ is a d.p.d.t. toggle, slide or rotary switch. The power supply is made up of

two penlight or flashlight cells connected in series ($B1$). Short, flexible leads terminated with miniature alligator clips are provided as transistor connectors, but a socket may be employed if you prefer. Standard 2000-ohm magnetic headphones are used.

In operation, the jumper is installed and $S1$ is preset for the basic type of transistor to be checked. The test leads are connected to the transistor. If the transistor is "good," the circuit will oscillate and a tone can be heard in the earphones. If the transistor is excessively leaky or has low gain (or both) . . . or is shorted or open . . . the circuit will not oscillate. The instrument can be used as a CPO by installing a "good" transistor and replacing the jumper with a standard handkey.

Although W3WNE's dynamic tester is fairly reliable, it is not completely fool-proof. For best results, both static and dynamic tests should be made.

Product News. Recognizing that excessive heat while soldering can play havoc with semiconductors, two firms have recently introduced low-cost clip-on heat sinks. Hunter Tools (9851 Alburto Ave., Santa Fe Springs, Calif.) is producing miniature units made of BERYLCO 10 alloy and equipped with plastic-covered handles; illustrated in Fig. 4, these units carry stock number 51G. And Macdonald & Company (Glendale 6, Calif.) is offering a series of "Little Joe" aluminum units in three different sizes—see Fig. 5.

Radio Corporation of America (Semiconductor Division, Somerville, N. J.) has announced a new line of high-voltage silicon rectifiers having peak inverse voltage ratings from 1200 to 10,000 volts and average current ratings from 550 to 825 ma. at 60°C. These rectifiers are made up of a series of hermetically sealed diffused-junction rectifier cells shunted by RC voltage equalizing networks, and molded into a rugged case of insulating material.

Most of the large mail order supply houses have issued their 1962 catalogs, and the number of transistor items offered is amazing. Glancing through the new catalog put out by Radio Shack (730 Commonwealth Ave., Boston 17, Mass.), yours truly spotted such items


(Continued on page 110)

Three-Hand Soldering


Suggested by **JOHN A. COMSTOCK**
(who has only two hands)



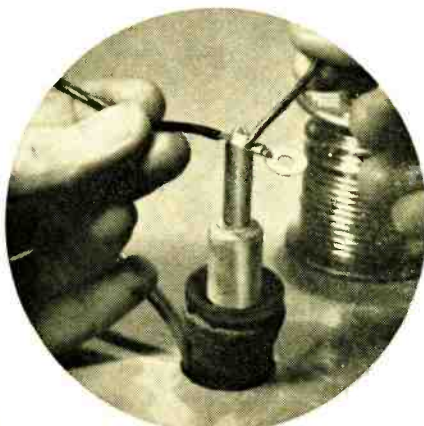
SOLDERING TABLE CLIP. Take two large tin can lids and bend one to a U-shape. Solder the ends of the U to the other lid. Now glue a piece of asbestos to the flattened-out bottom of the U, and use it as a soldering bed or table—you can hold small parts in place with an alligator clip.



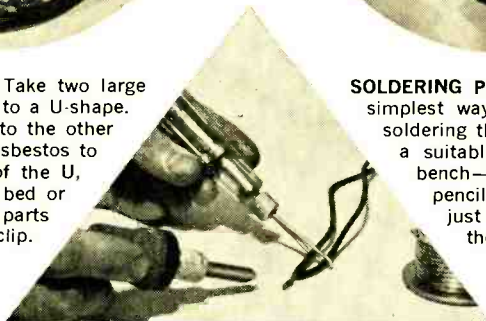
SOLDERING PENCIL WEDGE. One of the simplest ways to get a third hand for soldering those difficult jobs is to drill a suitable-sized hole in your workbench—then wedge the soldering pencil into the hole. Make the hole just big enough to squeeze in the cork barrel and line cord.



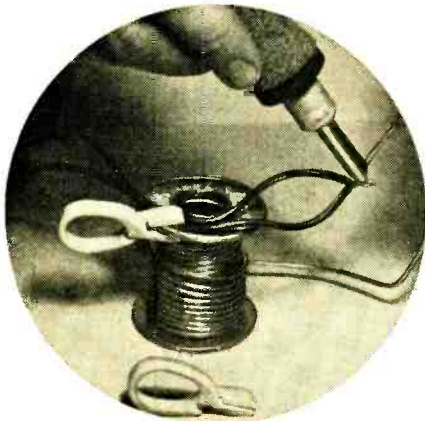
SCREWDRIVER THIRD HAND. To convert the handle of one of those interchangeable screwdriver sets into a soldering tool, cut off a 5" length of solder, loop it, and chuck it in the handle. Slip the loop over wires to hold them in place.



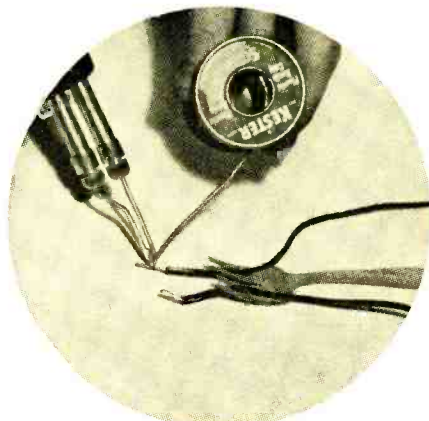PLASTIC CLIP CLAMP. Keep a couple of those plastic curtain or drapery clips on your workbench, and the next time a three-hand soldering job is called for—clamp the work to your roll of solder.



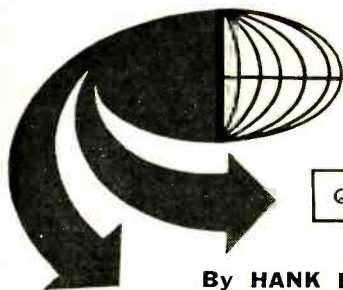SECOND-HAND FORK IS THIRD HAND. When your wife isn't looking, raid the kitchen and grab one of her old stainless steel forks for your workshop. You can use the tines to steady wires for tinning.



Short-Wave Report

By **HANK BENNETT**
W2PNA/WPE2FT

MORE QUESTIONS AND ANSWERS

IN JULY of this year, your Short-Wave Editor answered in print several questions that were being asked most frequently by the readers of this column. Judging from the mail since then, this question-and-answer format was well received, and many readers have asked that we do it again. As before, the questions listed below are typical ones.

Q: You have mentioned IRC's from time to time in connection with sending reports. What is an IRC? Where can they be obtained, how much do they cost, and what is their purpose?

A: International Reply Coupons (IRC's) are obtainable at post offices for 15 cents each. They are used when it is necessary to send postage to a foreign country. Needless to say, stations in foreign countries cannot use U.S. postage stamps on verifications sent into this country. However, if you furnish an IRC with your report, a foreign-country station can redeem it at the local post office for the postage needed to send you a reply by surface mail. If you would like to have an airmail

reply, you should include several IRC's with your report. Check with *your* local post office for airmail rates into the U.S.A. from other areas.

Q: Where can I obtain a general listing of amateur stations?

A: While this question is not really in the s.w. broadcast category, it is frequently asked. You can purchase the *Radio Amateur Callbook* (two volumes; one covering the U.S.A., the other listing foreign stations) from Callbook Magazine, 4844 West Fullerton Ave., Chicago 39, Ill., or from many of the wholesale radio parts shops. The American Edition, which costs \$5.00, is published in March, June, September and December, while the Foreign Edition (\$3.00) comes out in March and September.

Q: What can you tell me about radio clubs I might join?

A: We have a free leaflet available which lists several clubs: "Leaflet H—Clubs and Publications," and you can obtain
(Continued on page 88)

Clarence C. Huff, WPE6BL, Los Angeles, Calif., has been DX'ing on the medium waves since the 1920's. Four years ago he turned to short-wave DX'ing, with a Hallicrafters SX-100 receiver (shown) and a S-20R Sky Champion (not shown) as a standby.





NOW! A FULL LINE OF FAMOUS **REALISTIC** ELECTRONIC KITS AT RADIO SHACK

- Easy to assemble—enjoy the pride of craftsmanship with very little effort.
- Save up to 42%! Put your savings into quality.
- Look like professionally assembled equipment and last as long.
- Widest assortment of designs to choose from

Radio Shack's whole new family of audio and test equipment kits employs the most advanced designs and engineering concepts known today! They meet the most exacting requirements in performance and appearance. They're easy and fun to build! Critical areas are pre-wired, factory-aligned. Even a novice can follow the simplified assembly manuals. And they're easy to own on No Money Down credit terms. Every kit backed by a money-back guarantee. We show here six kits newly introduced in our exciting 1962 Catalog.


Plug 'n Talk Intercom Kit—Beautifully styled by Realistic! New completely wireless 2-station Intercom System—easy to build yourself. Operates over 1 mile! 3-position switch: talk, listen, permanent. "B" speaker for good voice reception. Rear panel squelch control. Front panel volume. Use it in kitchen, bedroom, sickroom—ideal as a baby-sitter. 117-V power line circuit operates anywhere. 90LX844—\$29.50

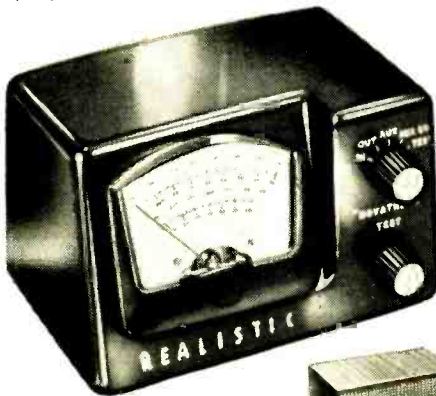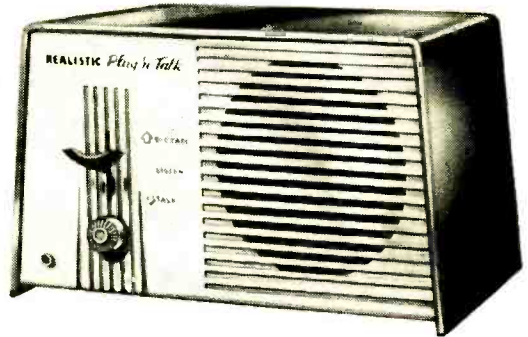

Realistic "Novatherm" Kit—the one and only professional-type electronic thermometer for the home! Compact, supremely accurate! Use in refrigerator, freezer, fish aquarium, lab. At flip of switch reads 2 temperatures in 2 different locations. Instantaneous readings from -20°F . to 120°F . Portable, uses 13c battery. Has "accessory probe"—use in freezer, liquid, even acid. Thermister type. Meter— $0-200\mu\text{a}$ D'Arsonval movement. All 1% resistors. 94LX095—\$19.95

Radio Shack's 1962 Line of Kits Includes All These:

- Stereophonic Preamplifier Kit
- Stereo 140W Basic Amplifier Kit
- 40 Watt Stereo Amplifier Kit
- Complete Stereo System Kits
- Universal Multiplex Adapter Kit
- Hi-Fi 12 Watt Amplifier Kit
- FM Adapter Kit
- Stereo Balance Meter Kit
- Wireless Intercom Kits
- Deluxe Signal Generator Kit
- Deluxe VTVM Kit
- Standard VTVM Kit
- Ultra-Modern Tube Tester Kit
- 500W Variable AC Supply Kit
- VOM Kit with $4\frac{1}{2}''$ Meter
- Signal Generator Kit
- AC VTVM Preamplifier Kit
- Electronic Photo Relay Kit
- "Novatherm" Thermometer Kit
- 5-Tube Teakwood Radio Kit
- 2-Transistor Home Radio Kit
- 6-Transistor Portable Radio Kit
- Transistor Experimental Lab Kit

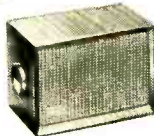

Teak AM Radio Kit. 5 tube superhet circuit. Handsome teakwood case. 90LX637—\$12.95



6-Transistor Radio Kit. Major parts pre-mounted. Easy to do and save! 90L636—\$16.95



30-in-1 Transistor Experimenter Kit. Build 30 different circuits! 98LX375—\$18.95



Stereo Balance Indicator Kit. Top quality! Gold anodized case. Easy to build. 91L547—\$5.95



Send today for **FREE** 1962 Catalog

Gentlemen:

Please send me your giant new 340-page Electronics Catalog of over 100,000 items and every exciting supplement for one full year—all FREE and POST-PAID.

Your Name 61L7D

Your Address

City and Zone

State

For a Friend 61L7D1

Address

City and Zone

State

Mail coupon to

RADIO SHACK Corp.
730 Commonwealth Ave.
Boston 17, Massachusetts

See complete specifications of these fine kits in Free Catalog

a copy of it for return postage. In the near future, your Short-Wave Editor plans to run a complete listing of clubs in this column, and all of the presently operating clubs are invited to write in. We would like to know the club name, dues and membership requirements, type and frequency of publication (if any), how long the club has been in existence, total number of members, type of organization (one man or full board), and future plans. Any awards program that might be in effect would also be of interest. Although we need all of this information, we will be glad to withhold certain items if requested (such as the total number of members, for instance).

Q: Why is it that I am unable to tune in many (or any!) of those so-called rare stations that you list? Others seem to hear them.

A: If we could all hear those rare stations, my friend, we wouldn't be able to refer to them as "rare," would we? To log the real rough ones, you must have (1) an infinite quantity of patience and (2) good ears. A "hot" receiver with a good antenna/ground system will also help. Some of the rare stations are only heard by the experts at infrequent intervals—one a month, perhaps—but those fellows will park on one frequency night after night and continually tune and listen.

(Continued on page 125)

CROSSWORD PUZZLE


By Thomas Windser

ACROSS

- 1 Rotating part found in analog computers.
- 4 Part of a circuit having one function.
- 9 Street: German abbrev.
- 12 _____ Khan.
- 13 Planet path.
- 14 It disappears when you stand up.
- 15 Type of lever switch.
- 17 Element used in the coating of vacuum-tube cathodes.
- 19 Standing waves have them.
- 21 Boy.
- 22 Length times width.
- 24 Single-cotton-covered: abbrev.
- 26 One of equal rank.
- 29 Units of electrical power.
- 31 Unit of work.
- 33 Electronics corporation: abbrev.
- 34 Preposition.
- 35 Distress call.
- 37 Rowing implement.
- 39 High frequency: abbrev.
- 40 Rhode Island Academy: abbrev.
- 42 _____ generator used on color TV sets.
- 44 Common use for No. 47 bulb.
- 46 Ages.
- 48 _____ cell uses liquid electrolyte.
- 50 Girl.
- 51 Eight: combining form.
- 53 Titled.
- 55 Lead coming from the side of a component.
- 58 Small capacitor in series with main tuning capacitor.
- 61 Suffix used in chemistry.
- 62 Loudspeaker diaphragms.
- 64 Ohm's law: abbrev.
- 65 Found inside thyratrons.
- 66 Potentiometer networks used in audio distributing circuits.
- 67 Notes in music.

DOWN

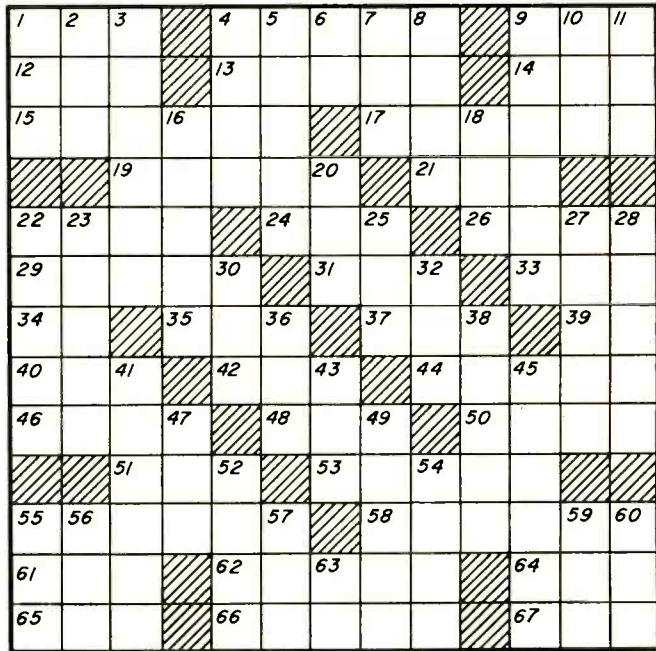- 1 _____ whisker.
- 2 In the past.
- 3 Used to attract iron.
- 4 Made a sale.
- 5 Sometimes suitable for supporting an antenna.
- 6 Type of battery pack used in portables.



- 7 A plate machined to hold other parts in place.
- 8 Latin phrase meaning "and others."
- 9 Moving part in potentiometer.
- 10 Greek letter.
- 11 Dial calibration used in tachometers.
- 16 Some believe they eat tin cans.
- 18 Light blow.
- 20 Single-cotton-enameled: abbrev.
- 22 Conscious of.
- 23 Type of FM detector circuit.
- 25 Cathode-ray oscilloscope: abbrev.
- 27 Seen on radar screens.
- 28 Floating platforms.
- 30 Soil.
- 32 Spark-_____ transmitter.
- 36 Plant seeds.
- 38 Vexed.
- 41 Diodes have them.
- 43 _____ calls used by CB'ers.
- 45 Adjustable attenuator network.
- 47 Science: abbrev.
- 49 Sounds are _____ at recording studios.
- 52 Diplomacy.
- 54 Matter has _____.
- 55 Slang for station equipment.
- 56 Collection of information.
- 57 Cut off.
- 59 Electronic industry association: abbrev.
- 60 Railroads: abbrev.
- 63 Continent: abbrev.

(Answers on page 114)

BUILD YOUR OWN RADIO

Reg. U. S.
Pat. Off.

CIRCUITS AT HOME
with the New

ONLY
\$26.95

PROGRESSIVE RADIO "EDU-KIT"®
A Practical Home Radio Course



Training Electronics Technicians Since 1946

Now Includes

- ★ 12 RECEIVERS
- ★ 3 TRANSMITTERS
- ★ SQ. WAVE GENERATOR
- ★ SIGNAL TRACER
- ★ AMPLIFIER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR

- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools Needed
- ★ EXCELLENT BACKGROUND FOR TV
- ★ **SCHOOL INQUIRIES INVITED**
- ★ Sold In 79 Countries

**YOU DON'T HAVE TO SPEND
HUNDREDS OF DOLLARS FOR A RADIO COURSE**

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our Kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction practice and servicing. THIS IS A COMPLETE RADIO COURSE IN EVERY DETAIL. You will learn how to build radios, using regular schematics; how to wire and solder in a professional manner; how to service radios. You will work with the standard type of punched metal chassis as well as the latest development in printed circuit chassis. You will learn the basic principles of radio. You will construct, study and work with RF and AF amplifiers and oscillators, detectors, rectifiers, test equipment. You will learn and practice code, using the Progressive Code Oscillator. You will practice practice trouble-shooting, using the Progressive Signal Tracer, Progressive Signal Injector, Progressive Dynamic Radio & Electronics Tester, Square Wave Generator and the accompanying instructional material. You will receive training for the Novice, Technician and General Classes of F.C.C. Radio Amateur Licenses. You will build 20 Receiver, Transmitter, Square Wave Generator, Code Oscillator, Signal Tracer and Signal Injector circuits, and create them. You will receive an excellent background for television, Hi-Fi and Electronics. Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with a broad education in Electronics and Radio, worth many times the complete price of \$26.95. The Signal Tracer alone is worth more than the price of the entire KIT.

THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. Whether you are interested in Radio & Electronics because you want an interesting hobby, a well paying business or a job with a future, you will find the "Edu-Kit" a worth-while investment. Many thousands of individuals of all

ages and backgrounds have successfully used the "Edu-Kit" in more than 79 countries of the world. The "Edu-Kit" has been carefully designed, step by step so that you cannot make a mistake. The "Edu-Kit" allows you to teach yourself at your own rate. No instructor is necessary.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore you construct, learn schematics, study theory, practice trouble shooting—all in a closely integrated program designed to provide an easily learned, thorough and interesting background in radio. You begin by examining the various radio parts of the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set you will enjoy listening to regular broadcast stations, learn theory, practice testing and trouble-shooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician. Included in the "Edu-Kit" course are twenty Receiver, Transmitter, Code Oscillator, Signal Tracer, Square Wave Generator and Signal Injector circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instruction necessary to build 20 different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, hardware, tubing, punched metal chassis, Instruction Manuals, hook-up wire, solder, selenium rectifiers, volume controls and switches, etc. In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electric Signal Injector, a self-powered Dynamic Radio and Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator. In addition to F.C.C.-type Questions and Answers for Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector a High Fidelity Guide and a Quiz Book. You receive Membership in Radio-TV Club, Free Consultation Service, Certificate of Merit and Discount Privileges. You receive all parts, tools, instructions, etc. Everything is yours to keep.

FREE EXTRAS

• SET OF TOOLS

- SOLDERING IRON
- ELECTRONICS TESTER
- PLIERS-CUTTERS
- ALIGNMENT TOOL
- WRENCH SET
- HIGH FIDELITY DISCOUNT CARD
- CERTIFICATE OF MERIT
- TESTER INSTRUCTION MANUAL
- HIGH FIDELITY GUIDE & QUIZZES
- TELEVISION BOOK & RADIO TROUBLE-SHOOTING BOOK
- MEMBERSHIP IN RADIO-TV CLUB: CONSULTATION SERVICE & FCC AMATEUR LICENSE TRAINING
- PRINTED CIRCUITRY

SERVICING LESSONS

You will learn trouble-shooting and servicing in a progressive manner. You will practice repair on the sets that you construct. You will learn symptoms and causes of trouble in home, portable and car radios. You will learn how to use the professional Signal Tracer, the unique Signal Injector and the dynamic Radio & Electronics Tester. While you are learning in this practical way, you will be able to do many a repair job for your friends and neighbors, and charge fees which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have.

FROM OUR MAIL BAG

J. Statitis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself. I was ready to spend \$240 for a course, but I found your ad and sent for your Kit."

Ben Valerio, P. O. Box 21, Magna, Utah: "The Edu-Kits are wonderful. Here I am sending you the questions and also the answers for them. I have been in Radio for the last seven years, but like to work with Radio Kits, and like to build Radio Testing Equipment. I enjoyed every minute I worked with the different kits; the Signal Tracer works fine. Also like to let you know that I feel proud of becoming a member of your Radio-TV Club."

Robert L. Shuff, 1534 Monroe Ave., Huntington, W. Va.: "Thought I would drop you a few lines to say that I received my Edu-Kit, and was really amazed that such a bargain can be had at such a low price. I have already started repairing radios and phonographs. My friends were really surprised to see me get into the swing of it so quickly. The trouble-shooting Tester that comes with the Kit is really swell, and finds the trouble, if there is any to be found."

PRINTED CIRCUITRY

At no increase in price, the "Edu-Kit" now includes Printed Circuitry. You build a Printed Circuit Signal Injector, a unique servicing instrument that can detect many Radio and TV troubles. This revolutionary new technique of radio construction is now becoming popular in commercial radio and TV sets.

A Printed Circuit is a special insulated chassis on which has been deposited conducting material which takes the place of wiring. The various parts are merely plugged in and soldered to terminals.

Printed Circuitry is the basis of modern Automation Electronics. A knowledge of this subject is a necessity today for anyone interested in Electronics.

UNCONDITIONAL MONEY-BACK GUARANTEE

**ORDER DIRECT FROM AD—RECEIVE FREE BONUS
RESISTOR AND CONDENSER KITS WORTH \$7**

- Send "Edu-Kit" postpaid. I enclose full payment of \$26.95.
- Send "Edu-Kit" C.O.D. I will pay \$26.95 plus postage.
- Rush me FREE descriptive literature concerning "Edu-Kit."


Name

Address

PROGRESSIVE "EDU-KITS" INC.

1186 Broadway, Dept. 586-D, Hewlett, N. Y.

CREATIVE ELECTRONICS KITS from CONAR

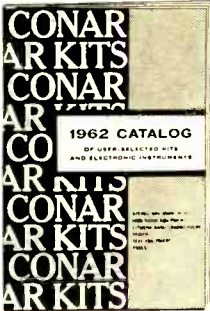

Mail Coupon for
FREE
1962 CATALOG

TEST INSTRUMENTS • STEREO
& MONO HI-FI • HAM RADIO
EQUIPMENT • CITIZEN'S BAND
TRANSCIVERS • TOOLS

CONAR products are low in cost, high in quality and kit-engineered for easy construction. All American-made parts. Performance-tested, approved and GUARANTEED by NRI... the first name in Electronics training for half a century. Monthly payment plans.

MAIL TODAY FOR FREE CATALOG
CONAR INSTRUMENTS
3939 Wisconsin Ave., Washington 16, D. C. MA

Print Name _____

Address _____

City _____ Zone _____ State _____

A DIVISION OF NATIONAL RADIO INSTITUTE

PURCHASING A HI-FI SYSTEM?

TIME PAYMENTS AVAILABLE
Up to 2 Years to Pay!

Send Us
Your List of
Components
For A Package
Quotation

YOU CAN BUY WITH
CONFIDENCE AT AIREX

All merchandise is brand new,
factory fresh and guaranteed.

Free Hi-Fi Catalog

AIREX
RADIO
CORPORATION

85-PE Cortlandt St., N. Y. 7

WO 4-1820

Jim Lansing*
Altec Lansing
Electrovoice
Jensen • Hartley*
University • Viking
Acoustic Research
Janszen • Superscope
Wharfedale
USL Citizen Band
Gonset • Hallicrafter
Texas Crystals
International Crystals
Concertone
Bell • G.E.
Weathers
Horman-Kardon
Eico • Pilot • Fisher
ESL • Roberts
Bogen • RCA • TEC
DynaKit • H. H. Scott
Thorens* • Sherwood*
Dual Changer
DeWald
Sony • Challenger
Wollensack • National
Garrard • Frazier
Miracord • Pickering
Glaser-Steers
Polytronics
Rek-O-Kut • Tandberg*
Audio Tape • Conrac
Norelco • Magnecord*
Fairchild • Sonar
Rockford Cabinets
*Fair Traded



Carl and Jerry

By
JOHN T. FRYE
W9EGV

SUBSTITUTE SANDMAN

SELDOM were Carl and Jerry separated for long, but this weekend Jerry had gone home from the university to attend the wedding of a cousin while Carl remained at school to do some studying. It was now Sunday evening, and Carl drifted into his and Jerry's room for the umpteenth time to see if his pal had returned. Bruce, a fat boy from across the hall, tagged along.

Carl pushed open the door to discover Jerry speakingly slowly and distinctly into the microphone of a tape recorder sitting on the desk before him:

"The derivative of a quotient of two functions is the denominator times the derivative of the numerator minus the numerator times the derivative of the denominator, all divided by the square of the denominator. . . . the derivative of the product of two functions is—, oh, hi there, Carl; hi, Bruce."

"Hah! You finally flipped and started talking to yourself!" Bruce exclaimed with a loud laugh. "I knew that math would get you."

"Not quite yet," Jerry answered with a good-natured grin, stopping the moving tape. "I just decided to do a little experimenting with 'sleep learning.'"

"You mean you put material you want to memorize on tape and play it back to yourself while you're asleep? I've heard of that. It's a lot of hogwash," Bruce sneered as he flung himself on his back on Carl's bed.

A frown crossed Carl's face, but he turned to his friend and said quietly, "Tell me about it, Jerry."

"I've wanted to try it for a long time. My curiosity was aroused when I saw a *You Asked For It* program on which a

student, under test conditions, learned conversational French while asleep in seven days time, and then demonstrated his ability to a French language authority in front of the camera. After that I saw an Art Linkletter program on



which Art talked to some sort of Chinese government official, speaking to him in Mandarin Chinese, one of the world's most difficult languages. Art learned his Mandarin in ten nights of sleep learn-

ing, and the Chinese gentleman said Art could travel in China and make himself understood by anyone who spoke the Mandarin dialect.

"Candidly, I don't know if the method works or not; but the military forces used it during the war to speed up the learning of code and languages. Many medical authorities, however, scoff at the idea that the brain can learn anything while it is asleep and resting. Others, on the other hand, maintain that the brain never really rests; and they prove it with electroencephalograph waves."

"I didn't think anyone believed what they saw on TV any more," Bruce scoffed.

"Oh, I don't know," Carl retorted, getting a little red in the face. "Ignorance comes in several flavors. It's just as stupid to deny a truth as it is to believe a lie. Our English teacher says education is the process by which a person moves from cocksure ignorance to thoughtful uncertainty. Some folks are hard to move."

(Continued on page 94)

FOR SHARPEST, CLEAREST VOICE TRANSMISSION WITH ANY CITIZENS BAND TRANSCEIVERS, SPECIFY THE TURNER 350C

Even the best citizens band equipment is no better than the microphone it uses. That's why more Turner 350C microphones are used as original equipment in CB than any other. That's why it will pay you to specify the Turner 350C when you buy CB equipment or replace your microphone.

■ The 350C is furnished with an 11" retracted (five foot extended) coiled cord. Hanger button and standard dash bracket are included for mobile rig mounting. Response: 80 to 7000 cps. Output: -54 db. Net price: \$10.08. ■ See Turner microphones at your electronic parts distributor or send coupon for complete information and the name of your nearest Turner distributor.



TURNER 254C FOR BASE STATION

Desk type ceramic mike operates by a touch bar on-off switch and lever lock on-off switch. Response: 80-7000 cps. Output: -54 db. Net price: \$14.10.

THE  MICROPHONE COMPANY

946 17th Street NE,
Cedar Rapids, Iowa

Gentlemen: send me further information on the 350C and 254C CB microphones and the name of my nearest Turner distributor.

NAME _____

ADDRESS _____

CITY _____

STATE _____

*Do your
Christmas shopping
the easy, economical
satisfying way
with the
1962 HEATHKIT®
Catalog*


World's biggest kit catalog—offers over 250 kit selections. The big, new 100-page Heathkit catalog is the world's shopping center for kit builders. It offers over 40 completely new kits and a variety of products priced from \$7.95 up. Heathgift certificates are available in any dollar amount you wish.

New easy terms; order now—pay later!

Heathkit's new relaxed terms are the easiest ever. Now, no down payment is necessary . . . and take as long as 18 months to pay. See the order blank in the 1962 Heathkit catalog or write for application forms today.

Heathkits give a world of pleasure—at half the price!

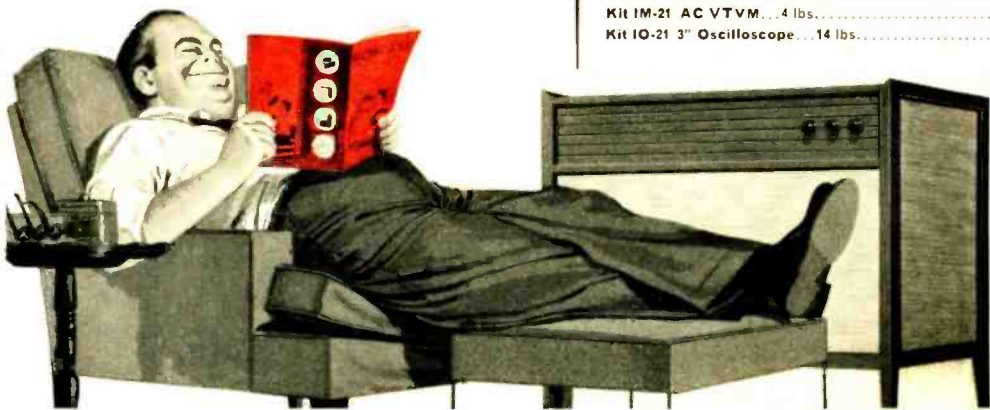With Heathgifts you provide more than just a remembrance. You open an exciting, challenging, satisfying new world of pleasure—that lasts a lifetime. What's more, you give the highest quality electronic equipment, but pay up to 50% less than the cost of ready-made units.



**New "value-packed"
FM Tuner in charcoal gray and ivory**

Performs in the true Heathkit quality tradition. Loaded with such features as flywheel tuning and slide rule dial. AFC control, assembled prealigned front end for easy kit completion. 9 tube function. $\pm 20,000$ cps. A honey for looks! Features multiplex jack for use with the Heathkit AC-11 Multiplex Converter to provide FM stereo.

Kit AJ-31 FM Tuner (shown) . . . 8 lbs. **\$39.95**
Kit AC-11 Multiplex Converter . . . 4 lbs. **\$32.50**

New HEATHGIFTS



**New Test Instruments
for the technician or serious amateur**

The IM-21 AC VTVM has clean design. Extended freq. response 1 db 10 cps to 500 kc. 10 megohm input imp.; 10 voltage ranges; -50 to +50 calibrated db scale.


Versatile IO-21 "general purpose" 3" oscilloscope perfect for industrial, medical and general use. Push-pull vert. and horiz. amplifiers; 20 to 100,000 cps sweep; automatic sync.

Kit IM-21 AC VTVM . . . 4 lbs. **\$33.95**
Kit IO-21 3" Oscilloscope . . . 14 lbs. **\$49.95**

**Deluxe
9 transistor
Walkie-Talkie
keeps you in touch
anytime, anywhere**



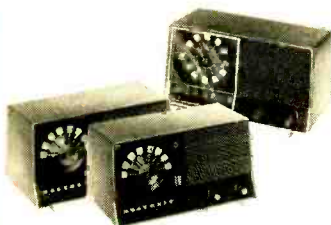Units at twice the price can't compare! Operating range of 1 to 3 miles; meets FCC regulations. Crystal controlled superhet receiver; squelch noise limiter circuit; push-to-talk switch; rugged, 2-tone alum. case. Use for private reception, as wireless mike or for paging. 75 hours on 9 volt battery. Collapsible 35" whip antenna.
Kit GW-21... 3 lbs. \$44.95



**A Handsome Radio for every
room in the house**

Choose from 3 spanking new ivory and beige radios. Low cost AM set provides hours of pleasure. Economical FM table radio is noise-free; has preassembled tuner. AM Clock-Radio has Telechron unit, sleep switch, radio alarm, pillow speaker jack.
Kit GR-121 AM Clock-Radio, 8 lbs. \$29.95
Kit GR-11 FM Table Radio, 7 lbs. \$27.50
Kit GR-10 AM Table Radio, 7 lbs. \$19.95



**Learn as you build—an
Educational Kit on Transistors**

Teaches basic fundamentals of transistors while performing interesting experiments! Text is written in simple easy-to-understand language. Final product is highly useful two-station intercom. Textbook provides a storehouse of valuable reference material. Designed for youngsters and adults alike. All components and materials furnished.
Kit EK-3 Basic Transistors... 4 lbs. \$16.95

make it a merrier Christmas for anyone!



**New
Accessories
to make a "Ham" happy**

Ham accessories that sing performance, price, features! Spectacular, compact tunnel diode "dip" meter does everything a "grid dip" can do. New rugged VFO covers 80 thru 2 meters. New "Q" multiplier has 2 peak I. F. positions. Exceptional values!
Kit HG-10 VFO... 12 lbs. \$34.95
Kit HM-10 "Tunnel Dipper".... 3 lbs. \$34.95
Kit HD-11 "Q" Multiplier... 2 lbs. \$14.95

**Safe
cruising**

for the Boating Enthusiast



Compare for price, for quality! See why the 3-band "Mariner" gives you so much. Includes consolan, beacon, broadcast and marine phone bands. 10 transistor, 1 diode circuit. Functionally styled with "sense" antenna, waterproofed 4" x 6" speaker. Preassembled tuner. Bearing accuracy of $\pm 3^\circ$.
Kit MR-11 3-band "Mariner".... 12 lbs. \$109.95



**Short Wave Radios put the
world at your fingertips**


Hours of fascinating broadcast, amateur radio, and short wave pleasure await you in the GR-91. Covers 500 kc to 30 mc in 4-bands. Illuminated 7" slide-rule dial & meter. Versatile controls for top reception. "Velvet touch" tuning. Easy circuit board assembly. Beige & Aqua color.
Kit GR-91 SWL Radio... 9 lbs. \$39.95



**New Wireless Intercom
saves time, saves steps**

No home, office or factory should be without this transistorized all-master intercom system. Imagine, only 3c a month to operate. No wires between units, just plug in. Any station calls other stations. Easy to build. In beautiful two-tone beige.
Kit GD-51 Intercom... 4 lbs. \$22.95
Kit GD-51-2 (pair)... 8 lbs. \$45.90

HEATH COMPANY
Benton Harbor 10, Michigan

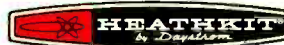

Yes, send me my free 1962 Heathkit catalog

NAME _____
 ADDRESS _____
 CITY _____ ZONE _____ STATE _____

Order direct by mail or see your Heathkit dealer.
 Ship Parcel Post Express C.O.D. Best Way

Ordering Instructions: Fill out the order blank. Include charges for parcel post according to weights shown. Express orders shipped delivery charges collect. All prices F. O. B. Benton Harbor, Mich. A 20% deposit is required on all C.O.D. orders. Prices subject to change without notice. Dealer and export prices slightly higher.

ITEM	MODEL NO.	PRICE

Free Catalog!



Send in today for your free 100-page catalog. Over 250 kits (more than 40 are new) in this most complete catalog of kits. Every piece is top quality... save up to 50%. Get a catalog now and receive 1962 Heathkit supplements.

This Christmas Give a Heathgift... from the World's Shopping Center for Electronic Kits

Jerry hastily broke in. "The output of the recorder is fed into this under-the-pillow speaker so I can hear the material I want to memorize without the sound disturbing anyone else in the room—namely you, Carl. The tape recorder is controlled by this clock-timer salvaged from a clock-radio. The 'sleep switch' will keep the recorder running for better than an hour after I go to bed, and the turn-on mechanism will start the recorder again about an hour before I expect to awaken. These two periods, at the beginning and end of a night's rest, are supposed to be the best for implanting material in the memory. The recording, of course, is on an endless loop of tape so that it will repeat over and over."

"This doesn't look like an endless loop of tape to me. It looks more like a tape cartridge of some sort," Carl observed as he looked closely at the small roll of tape nesting inside the round, clear plastic case.

"It's a Cousino 'Audio Vendor,'" Jerry explained. "It was originally designed to repeat an advertising message over

and over; hence, the name. Here's how it works.

"Inside the case is a 225-foot roll of special, friction-free tape. The inside end of the roll is brought out at a small angle through this slit in the top of the case and is fed past the record and play-back heads into the tape-pulling mechanism. As the end comes out from between the capstan and pinch-roller, it's spliced to the outside end of the roll of tape. The roll turns freely on a spool inside the case, so that the tape which is pulled from the inside of the roll is constantly fed back on the outside. Since no tension is put on the tape, it doesn't wind tightly; and the whole thing works very smoothly. The cartridge is placed on the supply roll spindle simply for support at the proper level. Turning of the supply or take-up spindles has nothing to do with the operation."

"How long does it play?" Carl asked.

"At 3 3/4 ips, it runs for about twelve minutes; but I've put a Möbius loop in the tape to make it run twice that long."

"Hold it!" Carl interrupted. "Don't give me that Möbius loop jazz. A Mö-

A GRANCO FIRST!

Only Granco brings the magnificent new sound of stereophonic FM radio into your home—today! Fine Granco FM/AM radio with AFC... and matching speaker-amplifier for total listening pleasure never before possible. Hear Granco stereophonic FM radio now—at fine dealers.

STEREO FM RADIO



MODEL 704 STEREO FM/AM RADIO with Automatic Frequency Control \$49.95* Also available as Model 604 FM Radio \$39.95*



MODEL SC-4 GRANCO FM STEREO COMPANION \$29.95* for use with Models 704 and 604

Write for free booklet "THE WONDERFUL WORLD OF STEREO FM"

GRANCO A Product of **Emerson Radio**
Dept. PE 680 FIFTH AVENUE, NEW YORK 19, N. Y.

*Suggested list. Prices slightly higher in some areas.

34¢

ELECTRONIC MARKET

1 YEAR GUARANTEED
RADIO-TV TUBES

EACH

\$32

Per 100 TUBES

ELECTRONIC MARKET

3750 E. 10th CT. HIALEAH, FLORIDA
Phone: OXford 1-5331

ONE OF THE LARGEST INVENTORIES IN THE COUNTRY

All tubes not necessarily new but may be electronically defect-free 2nds or used. Each clearly marked. ELECTRONIC MARKET will replace FREE any tube that becomes defective in use within 1 year from date of purchase. All tubes individually boxed and marked. Partial listing only—thousands more tubes in stock.

01A	354	513	641E	680	681	682	999	1000
-----	-----	-----	------	-----	-----	-----	-----	------

ORDER SHIPPED SAME DAY RECEIVED
SHIPPING INSTRUCTIONS: ELECTRONIC MARKET PAYS YOUR POSTAGE on orders of \$10 or more in U.S.A. and Territories. Send approx. postage on Canadian and foreign orders. Any order less than \$10 requires 25¢ handling charge. Send 25¢ on C.O.D.'s.
ANY RECEIVER TUBE NOT LISTED ALSO AVAILABLE AT 34¢ EACH!

bius loop is formed by cutting a loop of tape, twisting one end through 180 degrees, and splicing the ends back together, right?"

"Right," Jerry answered with an amused smile.

"So, okay! One time around, the coated side is pressed against the heads and you get a normal recording; the next revolution, the plastic backing is against the heads and you have a very weak and unnatural recording, even with 1/2-mil Mylar which places the minimum space between the magnetic coating and the heads. A Möbius loop is fine to insert a space between repeats of the message recorded on the coated side, but it's strictly blah as far as doubling the playing time is concerned."

"That's true with ordinary tape," Jerry commented; "but remember I said this tape was special. It's coated on *both* sides. One side is red and the other black, but you can see under a microscope that both sides are covered with magnetic particles. Naturally a Möbius loop of this stuff gives you a continuous recording for two complete revolutions of the loop."

"Why fool around with that?" Bruce asked as he heaved himself to a sitting position. "Let me hypnotize you into remembering the derivative formulas. Carl will tell you that I can put you under."


Carl answered Jerry's questioning look. "He can hypnotize a person, all right. Just before you got back a bunch of us were watching him hypnotize Mike Garrick down the hall. He had Mike doing all sorts of kookie things. Bruce claims he learned to hypnotize out of a book."

"Guess I'll skip the offer and stick to my sleep learning," Jerry said firmly. "I don't know much about hypnotism, but I never thought it was a toy to be played with. No one is going to hypnotize me unless he has respect for his powers."

Bruce's small blue eyes glinted with anger. He suddenly got to his feet, lumbered over to the tape recorder, started the tape moving, and chanted:

*D of x, g of x, dielectric K,
Latera recta, operator j;
Secant, asymptote, coordinate pair,
Old Jerry is a root-mean-square!*

FREE CAREER BOOKLET

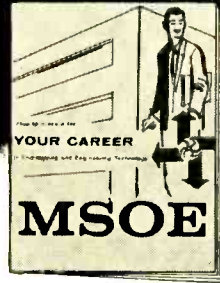

To guide you to a
successful future in

ELECTRONICS RADIO-TV COMPUTERS ELECTRICAL ENGINEERING

This interesting pictorial booklet tells you how you can prepare for a dynamic career as an Electrical Engineer or Engineering Technician in many exciting, growing fields:

**MISSILES • AVIONICS • AUTOMATION
SALES • DEVELOPMENT
ELECTRICAL POWER • ROCKETRY
RADAR • RESEARCH**

Get all the facts about job opportunities, length of study, courses offered, degrees you can earn, scholarships, part-time work — as well as pictures of the Milwaukee School of Engineering's educational and recreational facilities. No obligation — it's yours free.

MILWAUKEE SCHOOL OF ENGINEERING

MAIL COUPON TODAY!

Milwaukee School of Engineering
Dept. PE-1161, 1025 N. Milwaukee St., Milwaukee, Wis.

Please send FREE "Your Career" booklet

I'm interested in

Electronics Radio-TV Computers
 Electrical Engineering Mechanical Engineering

Name..... Age.....

PLEASE PRINT

Address.....

City..... Zone..... State.....

I'm eligible for veterans education benefits.

Discharge date..... MS-117

GROVE CB SALE!!

Closing out our stock of CB kits. Nationally advertised at \$39.95 up. Complete with power supply, tubes, crystal, cabinet, coils, etc., less mike. Kit sales final. Rush your order today!!

- 110 VOLT CB TRANSCEIVER KITS \$19.95
- 12 VOLT CB TRANSCEIVER KITS \$22.95
- 6 VOLT CB TRANSCEIVER KITS \$22.95

GET THE GROVE PRICE ON ANTENNAS!

- 3-ELEMENT BEAM ANTENNA (Reg. \$29.95) \$11.99
(Mounts horizontally or vertically)
- GROUND PLANE ANTENNA (Reg. \$15.95) \$9.99
(Heavy duty—solid aluminum rods)
- 11-PC. MOBILE NOISE SUPPRESSION KIT \$3.99
(Includes tunable Generator Filter)
- BODY MOUNT + 102" WHIP + SPRING \$6.99
- BUMPER MOUNT + 102" WHIP + SPRING .. \$8.99
- 100 ft.—RG 58U COAX CABLE \$2.99
- 100 ft.—RG 8U COAX CABLE \$7.99
- JK RECEIVING CB CRYSTALS (.002% Tol.—Specify make, model & channel) \$2.49
- JK CB XMTG CRYSTALS (.002%) (27MC Series—Specify make, model & channel) \$1.99

Lots of 3 or more, \$1.89 ea.—6 or more, \$1.79 ea.

Check items wanted. Return ad w/check or M.O. Include Postage. Excess returned. C.O.D. orders 50% down (Note: Beam and Ground Plane Antennas must be shipped railway express)

GROVE ELECTRONIC SUPPLY COMPANY

4103 W. Belmont Ave., Chicago 41, Ill.

- Rush items checked
- Send FREE catalog of giant CB Values

Name (please print)
Address
City Zone State

RADIOCOM



Citizens Band Transceiver

NEWEST DESIGN OF PROVEN UNIT
DUAL NOISE LIMITER
HIGHEST SENSITIVITY AND SELECTIVITY
TRANSISTOR POWER SUPPLY
MOST COMPACT—ONLY 3 1/2" HIGH

Yours with easy terms.

15.95 down — 12 months to pay

Now you can own the finest transceiver on the market. The RADIOCOM has been designed, tested, and proven by the thousands in service over a two and half year period to be the ultimate in citizen band design. It is available to you for only 159.50, on easy payment terms of 15.95 down and 12 monthly payments of 12.95. Quantity discounts available for dealers.

Let us prove this is the one for you.

Send NOW for FREE color catalog

RADIOCOM, P. O. BOX 147, Garland 11, Texas

"Knock it off, Bruce," Carl said sharply.

Bruce laughed mockingly, but he swaggered out the door Carl suggestively held open for him.

"What a character!" Jerry mused as he backed up the tape and erased the doggerel. "As soon as I dictate a few more formulas I'll take you over to the Co-Rec Gym and give you a couple of lessons in badminton."

IT WAS a couple of hours later when the boys returned to their room and got ready for bed. Jerry set his timer clock and reached over to turn on the recorder. "Hm-m-m, that's funny," he muttered. "The recorder is still warm. It must have gotten pretty hot when I was recording."

The lights went out, and Carl could hear the faint whirring of the recorder. Before long, Jerry's rhythmic breathing indicated he was asleep, and Carl was not far behind. When Carl awoke the next morning, the sleep-learner was already up and had switched off the tape recorder.

"Well," Carl asked as he picked up a towel and headed for the shower, "do you feel any smarter?"

"No, I can't say I do," Jerry admitted; "but at least the playing of the tape didn't keep me awake. I don't remember hearing more than the first five minutes of it."

The boys had no time to discuss the matter further. Their busy schedule kept them on the hop until finally Bruce, Carl, and Jerry met in math, the final class of the day. The period was about half over when Mr. Carney, the instructor, mentioned the word "derivative." As soon as he heard this, Jerry jumped to his feet and began to recite in a loud sing-song:

*D of x, g of x, dielectric K,
Latera recta, operator j;
Secant, asymptote, coordinate pair,
Old Jerry is a root-mean-square!*

The shocked silence that followed was finally broken by Mr. Carney. "You may sit down, Mr. Bishop," he remarked acidly; "and may I suggest that there might be a better time and place for you to rehearse your football cheers, or whatever they are?"

Jerry, red to the tips of his ears,

slumped down in his seat while his classmates, including Carl, stared at him in wonder. Across the room. Bruce grinned broadly at Jerry's obvious discomfiture.

Nothing else happened until the very end of the class, when Mr. Carney was giving the assignment and again used the word "derivative." Instantly Jerry was on his feet repeating the ridiculous poem. He broke off in the middle of it and bolted from the room with Carl right behind him.

"What's the matter with you?" Carl demanded of his white-faced chum as

they walked through the gathering dusk toward the residence hall.


"I don't know; I simply don't know!" Jerry admitted miserably. "All at once I had an uncontrollable urge to stand up and say that stupid verse. I wanted to stop but I couldn't. It was like a nightmare."

"The word 'derivative' seemed to touch you off," Carl mused. "Do you suppose messing around with this sleep-learning thing may have unhinged you just a little?"

"Naw, it's not that—I don't think. What beats me is how I had that verse down so pat after only hearing it once. Ordinarily I'm not too good at memorizing, but I didn't hesitate a bit when I was reciting the thing."

"Come on," Carl said as he broke into a trot. "You've given me an idea. Perhaps you heard that verse more than once. I want to listen to that sleep-tape of yours."

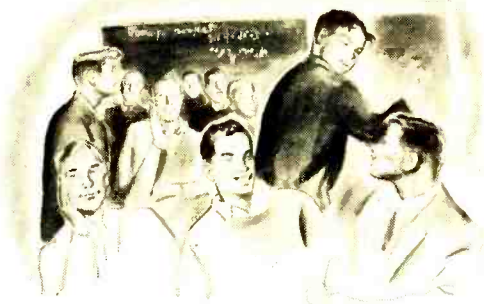A FEW MINUTES LATER the boys were in their room playing the tape. The whole first half of it had obviously



TV-RADIO Servicemen or Beginners...

Send for *Coyne's*
7-Volume Job-Training Set
on 7-Day **FREE TRIAL!**



The First
Practical
TV-RADIO-
ELECTRONICS
Shop
Library!

**Answers ALL Servicing Problems QUICKLY...
Makes You Worth More On The Job!**

Put money-making, time-saving TV-RADIO-ELECTRONICS know-how at your fingertips—examine Coyne's all-new 7-Volume TV-RADIO-ELECTRONICS Reference Set for 7 days at our expense! Shows you the way to easy TV-Radio repair—time saving, practical working knowledge that helps you get the BIG money. How to install, service and align ALL radio and TV sets, even color-TV, UHF, FM and transistorized equipment. New photo-instruction shows you what makes equipment "tick." No complicated math or theory—just practical facts you can put to use immediately right in the shop, or for ready reference at home. Over 3000 pages; 1200 diagrams; 10,000 facts!

SEND NO MONEY! Just mail coupon for 7-Volume TV-Radio Set on 7 Day FREE TRIAL! We'll include the FREE BOOK below. If you keep the set, pay only \$3 in 7 days and \$3 per month until \$27.25 plus postage is paid. Cash price only \$24.95. Or return set at our expense in 7 days and owe nothing! Either way, the FREE BOOK is yours to keep. Offer limited, so act NOW!

**"LEARNED MORE FROM THEM
THAN FROM 5 YEARS WORK!"**

"Learned more from your first two volumes than from 5 years work."
—Guy Bliss, New York

"Swell set for either the serviceman or the beginner. Every service bench should have one."—Melvin Masbruch, Iowa.

FREE DIAGRAM BOOK!

We'll send you this big book, "150 Radio-Television Picture Patterns and Diagrams Explained" ABSOLUTELY FREE just for examining Coyne's 7-Volume Shop Library on 7-Day FREE TRIAL! Shows how to cut servicing time by reading picture-patterns, plus schematic diagrams for many TV and radio sets. Yours FREE whether you keep the 7-Volume Set or not! Mail coupon TODAY.



Like Having An Electronics Expert Right At Your Side!

VOL. 1—EVERYTHING ON TV-RADIO PRINCIPLES! 300 pages of practical explanations; hundreds of illustrations.

VOL. 2—EVERYTHING ON TV-RADIO FM RECEIVERS! 403 pages; fully illustrated.

VOL. 3—EVERYTHING ON TV-RADIO CIRCUITS! 336 pages; hundreds of illustrations, circuit diagrams.

VOL. 4—EVERYTHING ON SERVICING INSTRUMENTS! How they work, how to use them. 368 pages; illustrated.

VOL. 5—EVERYTHING ON TV TROUBLESHOOTING! Covers all types of sets. 437 pages; illustrations, diagrams.

VOL. 6—TV CYCLOPEDIA! Quick and concise answers to TV problems in alphabetical order, including UHF, Color TV and Transistors; 868 pages.

VOL. 7—TRANSISTOR CIRCUIT HANDBOOK! Practical Reference covering Transistor Applications; over 200 Circuit Diagrams; 410 pages.

BOOKS HAVE BRIGHT, VINYL CLOTH WASHABLE COVERS

FREE BOOK—FREE TRIAL COUPON!

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL
1455 W. Congress Parkway, Dept. B1-PE, Chicago 7, Ill.
Yes! Send me COYNE'S 7-Volume Applied Practical TV-RADIO-ELECTRONICS Set for 7-Days FREE TRIAL per offer. Include "Patterns & Diagrams" book FREE!

Name Age

Address

City State Zip

Check here if you want Set sent C.O.D. Coyne pays postage on C.O.D. and cash orders. 7-Day Money-Back Guarantee.

Coyne

Educational Book Publishing Division
ELECTRICAL SCHOOL
1455 W. Congress Parkway Dept. B1-PE, Chicago 7, Illinois

been prepared at home, for it was given over to a background of organ music against which Jerry spoke slowly and soothingly of the vanishing cares of the day, of muscles relaxing, of nerves quieting, of the body sinking down, down, down into sweet and restful slumber, and of the mind being prepared to accept effortlessly but to hold firmly the material soon to be offered it.

Carl started yawning just listening to it, but he snapped wide awake as the voice suddenly changed. It was unmistakably Bruce's voice now coming from the recorder:

"You will not awaken, Jerry. Instead you will sink deeper and deeper into sleep. Now you are *really* asleep. You cannot awaken until I tell you to. You are asleep; yet you can hear everything I say. You will do what I tell you to do. Tomorrow, in math class, whenever you hear the word 'derivative,' you will stand up immediately and recite this beautiful poem:

*D of x, g of x, dielectric K,
Lutera recta, operator j;*

*Secant, asymptote, coordinate pair,
Old Jerry is a root-mean-square!*

All who hear you will admire you for being able to memorize and recite so well. When you wake up in the morning, you will feel rested and refreshed. You will remember nothing of this, but you *will* recite the poem when you hear the word 'derivative.'

"Just as I suspected," Carl said as he switched off the recorder. "That hood sneaked in here while we were over at the gym last night and recorded that post-hypnotic suggestion over the top of your derivative formulas. No wonder you remembered the poem after having it drilled into your subconscious for about two hours! You said he wasn't going to hypnotize you; he was determined to show you he could—hey, where you going?"

Jerry, a grim look on his face, was headed for the door. "I'm thinking that our playful friend, Bruce, ought to add phrenology to his study of the occult sciences," he grated. "I'm going to give him some bumps to practice on!" -30-

LOWER THAN WHOLESALE

ARGUS CAMERA C3 Match-Matic #184 COMPLETE.....	48.95
TURNER 350-C Microphone	8.39
MAGNUM-27 M-81 Antenna	27.87
7.5W 7 Watt Fuse Resistors	10 for 1.39
6' U/L Chenter Cords	10 for 1.89
DeLuxe Brighteners SERIES OR PARALLEL	5 for 3.99
ASTATIC #20 Univ. Xtal with needle	1.29

Prices effective to Nov. 30, 1961. COMPLETE STOCKS OF EICO-PACO

Get put onto our confidential mailing list. We specialize in STANDARD NAME BRANDS at LOWER THAN WHOLESALE. Write today.

Terms:

25% cash with order, balance C.O.D.

BANNER

ELECTRONICS, INC.

2304 Chamberlayne Pkwy., Richmond 22, Va.

CITIZENS BAND EQUIPMENT LIGHTNING PROTECTION

- "BLITZ-BUG" →
 - For any standard coaxial cable
 - Will not effect performance
- See your Local Distributor



CUSHCRAFT

621 HAYWARD ST.
MANCHESTER, N. H.



Save 30% 4 track
Stereo music on tape

EMPTY 3 in. plastic reels 7¢ ea.

Bargain Prices! Send for our Recorder/blank/pre-recorded tape catalog E-1 and see why!

SAXITONE TAPE SALES

(Div. of Commissioned Electronics, Inc.)
1776 Columbia Road, Washington, D.C.

with 1 pair of crystals, microphone and power cables

\$179.50

NOW... Tomorrow and for years to come!

Sonar CITIZENS BAND RADIO

- 8 Channels, crystal controlled transmitter and receiver
- Tunable receiver for 22 channels
- Transmitter 100% Class B modulated
- Adjustable squelch
- Automatic noise limiter
- R. F. Power indicator
- 1 Year guarantee
- Easy to install. Ideal for home, boat, car or business. Weighs only 9 lbs. ... 4 3/4 x 9 1/2 x 11 1/4
- FCC Type accepted (*in preference to only certification).

SONAR RADIO CORPORATION, 3050 W. 21 St. • B'klyn 24, N.Y.
Please send me complete information on Model "E" CB Radio.

NAME _____
ADDRESS _____
CITY _____ STATE _____

Tips and Techniques

NEON NIGHT-LIGHT

The relatively new high-current neon lamps now on the market are bright enough to serve as useful night-lights. The unit pictured here incorporates an NE-51H, the high-current counterpart of the NE-51. To construct it, solder one lead of a 25,000-ohm, 1/4-watt resistor to one lamp contact and a short piece of wire to the other—then slip the whole assembly into the neck of a rubber plug. Finish the job by wiring the free ends of the resistor and wire to the prongs of the plug. A careful check for shorts should be made before you finally attempt to plug in the night-light.

—R. L. Winklepfeck

HOLDER FOR WRENCH SOCKETS

Keep your loose wrench sockets from rattling around in the tool box or becoming separated and lost by storing them on a long bolt. The sockets are simply slipped onto the bolt and held in place by a nut. If




the bolt is cut to the exact length of the stacked-up sockets, you'll be able to tell immediately if one is missing.

—Homer L. Davidson


USES FOR INK CARTRIDGES

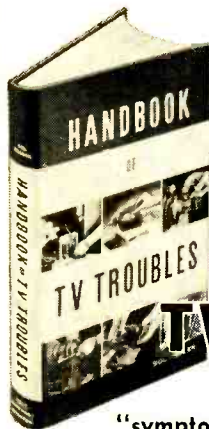Empty plastic ink cartridges, such as those from a Sheaffer "Skripsert" pen, can be put to many uses by the electronics hobbyist. To make a waterproof splice, for instance, slide a cartridge over the joint and melt the ends closed with a soldering gun. Need a small coil form? Use another cartridge,



new Master Guide to TIME-SAVING TV SERVICE

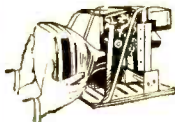A modern manual for fast, "symptomatic trouble analysis" and servicing of TV receivers.



TAKES THE GUESSWORK OUT OF TV REPAIRS!

Covers all causes of practically every trouble you're ever likely to be called on to fix including:

- BRIGHTNESS
- CONTRAST TROUBLES
- PICTURE DISTORTION
- UNSATISFACTORY PICTURE DETAIL
- LINE OR BARS IN PICTURE
- SYNCHRONIZATION TROUBLES
- MISSING PICTURE
- SIZE AND CENTERING TROUBLES
- SOUND TROUBLES
- TELEVISION INTERFERENCE, ETC.

LOOK! LISTEN! Then Follow This Easy Guide!

Almost regardless of set make or model, this remarkable new 302-page Handbook helps you track down TV troubles from the symptoms they produce in the set itself—screen intermittently dark; "blooming"; abnormal contrast in spots; "snow"; poor detail; sync troubles; sound troubles—and all the many others. Then it explains how to make needed adjustments or replacements.

Written by Sol Heller, TV instructor at Vorhees Technical Institute; former editor of Technician magazine and owner of a TV-Radio repair shop. From beginning to end, it is a down-to-earth, intensely practical book based on ACTUAL SHOP EXPERIENCE and not mere theory or guesswork!

Printed in large type. Has sturdy, varnished covers for "on the job" use. The TV TROUBLE INDEX helps you find what you want in a jiffy.

TRY IT 10 DAYS—See for yourself!

Dept. PE-111, HOLT, RINEHART and WINSTON, Inc. 623900
 Technical Div., 383 Madison Ave.
 New York 17, N. Y.

Send new 302-page HANDBOOK OF TV TROUBLES (708453) for 10-day FREE trial. If I decide to keep book, I will then send you \$7.50 in full payment. If not, I will return book postpaid and owe you nothing. **SAVE: Send \$7.50 with order and we pay postage. Same 10-day return privilege with money promptly refunded.**

Name

Address

City, Zone, State

OUTSIDE U.S.A.—No free examination. Price \$9.00 cash only. 10-day return privilege with money refunded.

Offer expires July 15, 1962

DEWALD



MFD. BY . . .



LEADS AGAIN WITH CITIZENS BAND "RADIO-PHONE" TR-910 TRANSCIVER



Amazing at only

99.95

LIST

- Push-to-talk Mike with dropout relay
- Full Squeech control
- Built-in 500-ohm and plate current meter
- 5 channel Transmit
- 22 channel Vernier controlled receive
- Automatic noise limiter

Furnished with Ceramic Microphone and one Transmitting Crystal
Write for Brochure and Name of Your Nearest Dealer

Made by . . . **UNITED SCIENTIFIC LABORATORIES, INC.**
35-09 37th AVE., LONG ISLAND CITY 1, N. Y.
Also Mfr's of DeWald HI-FI Stereo Components and FM Radio

SENDING A BILL?

It'll get there quicker if you give your postal delivery zone number with your address.

The Post Office has divided 106 cities into postal delivery zones to speed mail delivery. Be sure to include zone number when writing to these cities; be sure to include **your** zone number in **your** return address—after the city, before the state.

NEW!

First Miniaturized

TWO-WAY RADIO!

\$24.95

each postpaid
with batteries
Two for \$49.90

Just 5" HIGH



SPACEPHONE—FITS IN SHIRT POCKET! Two-way walkie-talkie sending and receiving set in the smallest case at the lowest price! Absolutely self-contained: microphone—loud-speaker, 9-volt transistor radio battery, transistorized transmitting and receiving sets with the latest miniaturized printed circuitry. U.S. designed and made. Volume control and tuning. Range 1/2 mile up.

Citizen's band—NO LICENSE, NO EXAMINATION—NO AGE LIMIT. For hunting, boating, fishing, hiking, all sporting uses, farms and ranches. Will operate between vehicles.

Electrosolids Corp. products are now in use on such projects as the Explorer VI Satellite. Spacephone replaces and does the same job as equipment costing from \$114 to \$300 per pair.

TO ORDER: Enclose check, cash or M.O. for postpaid shipment, \$5 deposit per unit for C.O.D. 10-day unconditional money-back guar. Dealers inquire. Calif. res. add 4% state tax. Electrosolids Corp., 13745 Saticoy Street, Panorama City 68, Calif.

Tips

(Continued from page 99)

mounting it by cutting off the closed end and enlarging the hole in the other end to take a small screw. These cartridges can also be used for insulated spacers, stand-offs, or shaft extensions.

—David Keller

WRENCH FOR WING NUTS


Antenna installers and other electronics workers know that tightening wing nuts is apt to be tough on the fingers. Pliers aren't really fitted for the job either—it's hard to get a good grip and the nut is often marred or bent. A wrench made from a 5" length of broom handle is the answer. Just saw a 1"-deep slot in one end, making it wide enough to fit over the largest nut apt to be encountered.

—John A. Comstock



CLEANING CORRODED TUBE PINS

When a radio is noisy, erratic, or intermittent, sometimes the only trouble is that corrosion has spoiled the connection between tube pins and their contacts. This condition is usually found in sets that have been operated for years without a change of tubes. To check for it, rock each tube in its socket with a circular motion. If you find a noisy connection, grasp the guilty tube firmly and move it straight up and down in

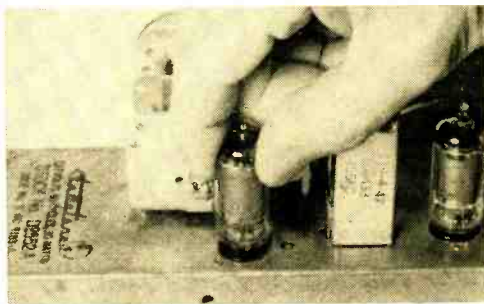

its socket several times—the friction should clean both pins and contacts. If the corrosion is especially bad, try scraping the pins and using a commercial contact cleaner.

—Carl Dunant

(Continued on page 103)



Special Training EQUIPMENT INCLUDED

Pick the field of your choice—and train at home with the leader—NRI. In addition to Industrial Electronics and FCC License training explained at the right, NRI offers comprehensive courses in Radio-TV Servicing and Radio-TV Communications. Except for the FCC course, all NRI courses include—at no extra cost—special training equipment for actual practice at home building circuits and working experiments. Make theory you learn come to life in an interesting, easy-to-grasp manner.

Multiplexing, FM Stereo Broadcasting Included

NRI training keeps up with the times. New, additional profit opportunities exist for the Technician who understands the latest technical advances. Course material now covers FM Stereo Broadcasting, tells you about Multiplexing equipment, other recent developments.

Learn More to Earn More

Act now. The catalog NRI sends you gives more facts about the field of your choice, shows equipment you get and keep. No obligation. Cost of NRI training is low. Monthly payments. 60-Day Trial Plan. Mail postage-free card today. NATIONAL RADIO INSTITUTE, Washington 16, D.C.

NRI—Oldest and Largest Radio Television School Now Offers NEW HOME STUDY TRAINING IN INDUSTRIAL ELECTRONICS & MILITARY ELECTRONICS

This is the age of Electronics. Rapidly expanding uses for Electronic Equipment in industry, business, the military demand more trained men. Prepare now for a career as an Electronic Technician. NRI now offers a complete course in **ELECTRONICS**



—Principles, Practices, Maintenance. Computers, telemetry, automation, avionics are changing our world, yet all employ the same basic principles . . . and that is what this NRI course stresses with illustrated lessons, special training equipment. Mail card below.

NEW HOME STUDY TRAINING FOR YOUR FCC LICENSE



An FCC Commercial License combined with NRI time-tested training can be the keys to a better future for you with higher pay, interesting work, more rapid advancement. Prepare at home *quickly* for your FCC examinations through NRI's new, low-cost, special training. Like other NRI-trained men, you can be monitoring TV shows, radio broadcasts, operating shipboard and aviation radio, or holding down other important jobs. Get full details—mail the card below.

**TURN
PAGE**

Cut Out and Mail—No Stamp Needed



**NATIONAL RADIO INSTITUTE
WASHINGTON 16, D. C.**

Send me your Electronic, Radio-TV catalog without cost or obligation. I am interested in the course checked below: (No representative will call. Please PRINT.)

- | | |
|---|---|
| <input type="checkbox"/> Industrial Electronics | <input type="checkbox"/> Communications |
| <input type="checkbox"/> FCC License | <input type="checkbox"/> Servicing |

9

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

**Send for
64-Page
CATALOG
FREE**


**The Amazing
Field of
Electronics**



ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL

www.americanradiohistory.com

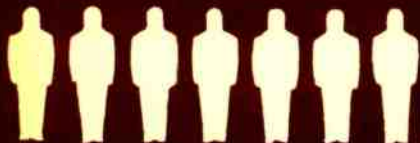**ELECTRONICS NEEDS
4 TO 7
QUALIFIED TECHNICIANS**



FOR EVERY ENGINEER



Choose from 4 Courses

- 1. INDUSTRIAL ELECTRONICS**
Learn about Electronic equipment used today by business, industry, the military. Covers computers, servos, telemetry, multiplexing, other subjects.
- 2. FCC LICENSE**
Communications stations must have FCC-licensed operators. New NRI course prepares you for your First Class FCC exams. Train at home in spare time.
- 3. COMMUNICATIONS**
Operation and maintenance of radio and TV stations; police, marine, aviation, mobile radio, etc. Includes FM Stereo broadcasting. Course also prepares you for your FCC license exam.
- 4. SERVICING**
Service and maintain AM-FM Radios, TV sets, Stereo Hi-Fi, PA systems, etc. A profitable, interesting spare or full-time business of your own.

SEE OTHER SIDE

**Join The Thousands
Who Trained For
Advancement With NRI**

Thousands of NRI graduates throughout the U. S. and Canada are proof that it is practical to train at home. NRI graduates are in every kind of Electronics work: inspectors, maintenance men, lab technicians, testers, broadcasting and mobile communications operators, Radio-TV service technicians, or in essential military and government posts. Catalog tells more about what NRI graduates do and earn. Mail postage free card.



"THE FINEST JOB I EVER HAD" is what Thomas Bilak, Jr., Cayuga, N. Y., says of his position with the G. E. Advanced Electronic Center at Cornell University. He writes, "Thanks to NRI, I have a job which I enjoy and which also pays well."



BUILDING ELECTRONIC CIRCUITS on specially-designed plug-in type chassis, is the work of Robert H. Laurens, Hammonton, N. J. He is an Electronic Technician working on the "Univac" computer. Laurens says, "My NRI training helped me to pass the test to obtain this position."



"I OWE MY SUCCESS TO NRI" says Cecil E. Wallace, Dallas, Texas. He holds a First Class FCC Radio-telephone License and works as a Recording Engineer with KRLD-TV.



MARINE RADIO OPERATOR is the job of E. P. Searcy, Jr., of New Orleans, La. He works for Alcoa Steamship Company, has also worked as a TV transmitter engineer. He says, "I can recommend NRI training very highly."



FROM FACTORY LABORER TO HIS OWN BUSINESS that rang up sales of \$158,000 in one year. That's the success William F. Kline of Cincinnati, Ohio, has had since taking NRI training. "The course got me started on the road," he says.

FIRST CLASS
PERMIT
NO. 20-R
(Sec. 34.9, P.L.&R.)
Washington, D.C.

BUSINESS REPLY MAIL

NO POSTAGE STAMP NECESSARY IF MAILED IN THE UNITED STATES

POSTAGE WILL BE PAID BY



National Radio Institute

**3939 Wisconsin Avenue
Washington 16, D.C.**



**Oldest and Largest
School of Its Kind**

Training men to succeed by home study has been the National Radio Institute's *only* business for over 45 years. NRI is America's oldest and largest Electronics home-study school. Don't delay. Cut out and mail POSTAGE-FREE CARD.

MAIL POSTAGE-FREE CARD

Tips

(Continued from page 100)

BULB AND CELL TESTER

A simple device for checking flashlight batteries or bulbs can be made from a 6" length of No. 12 or No. 14 wire and an alligator clip. Form the wire as shown in the photo, sharpen one end, and solder the other




end to the alligator clip. The jaws of the clip are bent slightly for a better grip on bulb bases. To use the tester, just slip a bulb into the alligator clip and bridge it across the ends of the cell. If you use a No. 112 bulb (1.2 volts) and let it burn for a while, you'll be able to judge the condition of the cell; doubtful cells might be strong at first, then die down.

—Art Trauffer

SPOOL PROPS MULTIMETER

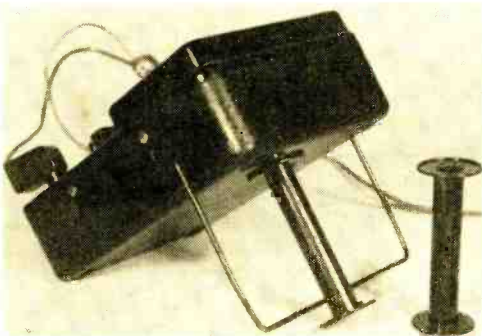If your multimeter has a wire handle, you can easily make a prop to hold the instrument in a convenient viewing position. Sim-



ply saw a slot in one end of a film spool and fit it over the handle as shown. Get a plastic spool if possible—you'll find that it's easier to saw than a metal one.

—Jerome Cunningham

**ANNUAL
DOUBLE
BONUS**

FREE!

B
O
N
U
S
=1

\$50⁰⁰

WORTH OF
RADIO-TV
PARTS
(over 300 pcs.)

Add 25c
for
Handling

B
O
N
U
S
=2

PLUS \$7 POLY PAK®
ANY OF YOUR CHOICE
LISTED BELOW

NOW BOTH FREE with every \$15.00 order

- 40 TUBE SOCKETS \$1
- 4 to 12 prongs, Worth \$8
- 30 Allen Bradley Resistors World's finest 5% 100, 1/2's, 1's, 2Ws. \$1
- 10 RCA PLUG-N-JACK Sets for amps, tuners, re-corders, etc. Worth \$2
- 60 Insulated Resistors IRC, 1/2, 1W to 1 meg. 5% 100, Worth \$15
- 100 1/2-Watt Resistors \$1
- 70 1-Watt Resistors \$1
- 40 2-Watt Resistors \$1
- 4 Output Transformers 50LB, etc. Open frame types. Worth \$8
- 35 POWER RESISTORS Ass't. to 10 W to 10,000 ohms. Worth \$12
- CRYSTAL PHONE \$1 Sensitive, cool & plug.
- 60 COILS & CHOKES HP, ant. osc. slug-tuned. 1-P, Worth \$16
- 10 "POLY" BOXES Snap-top covers; sizes to 4". Worth \$3
- 70 TERMINAL STRIPS 1 to 10 tie ohms. Worth \$5
- \$25 SURPRISE PAK Wide variety of usable radio-TV-hobby parts.
- 65 Condenser Special Incl: discs, ceramics, molded, mica. Worth \$12
- 60 Tubular Condensers Papers, molded, oil, etc. Worth \$16
- 300-FT. HOOKUP WIRE Ass't. colors, insulation. \$1
- 10 Transistor Sockets Fit all types of transistors and mini tubes. 100.
- 50 Disc Condensers Ass't. .001 to .01 to 1000V. Worth \$10
- CRYSTAL MIKE mini 1 1/2" \$4, 100-7000 cps.
- 1 1/2 LBS. HARDWARE Nuts, bolts, etc. Wide variety. Handy shop asst.
- 15 AC-DC LINE CORDS 2-cond. rubber, molded plugs, short lengths.
- 2000 OHM PHONE With cord & plug, ear loop. Worth \$3
- 15 ROTARY SWITCHES Ass't. gauges, contacts; for circuit changing. Worth \$17
- 10 Electrolytic C'nd'n'rs Incl: can & paper types. Dual top. Worth \$12
- 35 SILVER MICAS 1 & 5% asst. values. Finest mica. Worth \$8
- 60 MICCA CONDENSERS Incl: silvers top, .0025 to .01 to 400V. Worth \$20
- 60 Plugs & Receptacles Incl: power, audio, battery, etc. Worth \$8
- 6 NPN TRANSISTORS Worth 100's of uses.
- 100 Ceramic Condensers Incl: discs top! Worth \$10
- 60 RADIO 'N' TV KNOBS Ass't: colors, sizes, shapes. Some worth \$1 ea.
- 10 PANEL SWITCHES Micros, power, rotary types. Exc. variety. Worth \$10
- 10 VOLUME CONTROLS Ass't. to 1 meg. Some with switch. Worth \$15
- 10 GERMANIUM DIODES Glass-encd. like 1N34. \$1
- 2 SUN BATTERIES Lite sensitive, etc. \$1
- 65 RESISTOR SPECIAL Carbons, precision, W.W., 10 50W, 1/2 to 100. Worth \$10
- 10 115V AC SWITCHES Toggle type, SPST, DPDT, etc. A shon must. 115V AC.
- 30 PRINTED CIRCUITS Resistor & component net. works.
- 50 HI-Q CONDENSERS Resistor & component net. \$1
- 6 PNP TRANSISTORS Ass't. Finest made. Force. \$1
- 3 POWER TRANSISTORS For all types of audio use \$1
- 4 SILICON RECTIFIERS 500 mils. top hat type. \$1
- 5 Selenium Rectifiers 115V AC, 65 mil rect. 1/2" wave.
- 25 PILOT LITES Buy & screw types; 1-3 \$1 to GV.
- 5 Micro Switches \$1 Rated 115V AC, SPST cont.
- \$25 Relay Surprise \$1 Guaranteed satisfaction.
- 50 Precision Resistors WW & carbon film. Val: 5% ohms to 1 meg. 1/2, 1, 2W, 1% tol.
- RCA INVERTER 110 VAC to 110AC. Comes less tubes.
- 3 Sylvania Transistors Popular makes. Worth \$3 ea.
- HEAVY DUTY Line cords, all rubber, 18-ft. lengths. \$1
- TWO 9V BATTERIES Same as Burgess 20G. 100% fresh stock.
- 4 BRAND NEW 1U4s Tubes by Sylvania. Orig. boxes.
- 30 Transistor "Thins" Disc condensers, 0.05mfd. \$1 30 to 100 PPM.
- 40 "Tiniest" Resistors Body only 4/16" long, 5% values 1/8W.


**CUT
OUT
AND
MAIL**

LEKTRON

245 EVERETT AVE.
CHELSEA 50, MASS.
Write for Free Catalog

HOW TO ORDER: Avg. wt. per pak 1 lb. Return ad with check or M.O. including postage; excess returned. C.O.D. orders, 25% down; rated, net 30 days. Include Postal Zone in address.

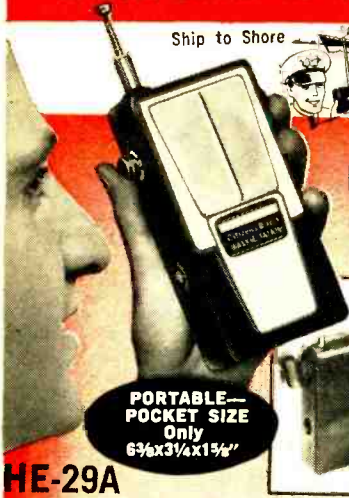LAFAYETTE is America's Citizens Band Headquarters



Ship to Shore



On the Farm



Construction Work




**NO LICENSES,
TESTS OR
AGE LIMITS**

**9 LAFAYETTE
TRANSISTOR
CITIZENS BAND
"WALKIE TALKIE"**

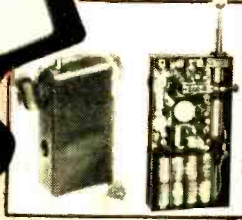39.95
2 for 78.88
NO MONEY DOWN

**PORTABLE—
POCKET SIZE**
Only
6 3/4" x 3 3/4" x 1 3/4"



- Completely Wired—Ready to Operate • Fully Transistorized—9 Transistors plus 1 Diode • Uses Inexpensive Penlight Batteries
- No License, Tests or Age Limits • Comes with Leather Carrying Case, Earphone, Antenna, Batteries and Crystals

As simple and easy to use as the telephone—and twice as handy. Receives and transmits up to 1.5 miles under average conditions. Weighs only 18-oz. and slips into your pocket. Push-to-talk button operates built-in speaker as sensitive microphone.


HE-29A

LAFAYETTE HE-20A

Citizens Band TRANSCEIVER

- Pi-Network for Greater Power Output • Calibrated "S" Meter • Series Gate Noise Limiter • Tuneable Superhet Receiver over all 23 Channels • 4 Crystal-Controlled Transmit Positions • 4 Crystal-Controlled Receive Positions • Dependable Push-To-Talk Ceramic Microphone & Relay • Illuminated Dial • Built-in 12-Volt Power Supply • Complete with Matched Crystals for Channel 9

109.50
NO MONEY DOWN

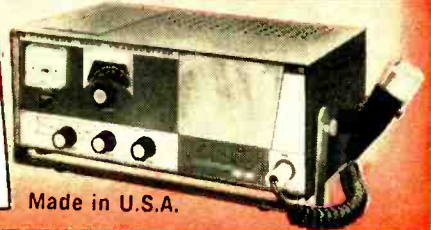

Made in U.S.A.

LAFAYETTE HE-15A Citizens Band TRANSCEIVER

SUPERHET

- Completely Wired—Not A Kit • 5 Crystal-Controlled Transmitting Positions • Tuneable Receiver Over Full 23 Channels • High Output Ceramic Microphone • Complete with Transmitting Crystal for Channel 9

A compact, precision transmitter and receiver covering up to a 20 mile or more radius, depending upon conditions. The HE-15A features an effective full-wave variable noise limiter, planetary vernier tuning. RF and microphone jack on front panel, 12 tube performance from 4 dual-function tubes, 2 single-function tubes, 2 rectifiers.

**ONLY
59.50**
NO MONEY DOWN



Made in U.S.A.

- HE-19 Telescoping Whip Antenna Net 3.95
- HE-16 Power Supply for 12 Volts Net 10.95
- HE-18 Power Supply for 6 Volts Net 10.95

LAFAYETTE ALL-IN-ONE CITIZENS BAND MOBILE ANTENNA

*The Scoop Buy for
Citizens Band Mobiles*

6.95

HE-800WX

- Chrome Swivel Base • Stainless Steel Spring
- 102 1/2" Stainless Steel Whip for Optimum 11-Meter Performance

Chrome swivel ball mount base designed for mounting on any surface. Stainless steel spring holds rod in properly adjusted position and prevents rod damage from shocks and blows. Stainless steel whip for maximum resiliency and strength.



NEW! LAFAYETTE RADIO FIELD INDICATOR

TM-14

6.95

- Continuously Indicates Transmitter Output • Rugged 200 ua Meter Movement • Requires No Electricity, Batteries or Transmitter Connection
- Check the performance of marine, mobile or fixed transmitter. Features 3 200 ua meter movement with variable sensitivity control. Earphones can be plugged in for an aural check of output. Antenna extends from 3 1/4" to 10 3/4". Magnet on bottom plate allows easy mounting on car dash or metal surfaces. Size, less antenna, 3 1/8"W, 2 1/4"H, 2"D.



LAFAYETTE RADIO

SEND MAIL ORDER TO LAFAYETTE RADIO
111 JERICHO TURNPIKE, SYOSSETT, L. I., NEW YORK

OTHER LOCATIONS
JAMAICA, N. Y.
165-08
Liberty Avenue

PLEASE INCLUDE SHIPPING CHARGES WITH ORDER

NEW YORK, N. Y. 100 6th Avenue	BOSTON, MASS. 110 Federal Street	PARAMUS, N. J. 182 Route 17
BRONX, N. Y. 542 E. Fordham Rd.	NEWARK, N. J. 24 Central Avenue	PLAINFIELD, N. J. 139 W. 2nd Street

LAFAYETTE

Engineered To Professional Standards . . . Designed For
The Home . . . Dedicated To Music

STEREO HIGH-FIDELITY COMPONENTS



Made in U.S.A.

FACTORY WIRED & TESTED **124.50**

NEW! LAFAYETTE LT-700 **Criterion**™

FM STEREO MULTIPLEX TUNER

Ready for Stereo and no Adapter Needed . . . opening a new era in stereo, the new Lafayette Criterion FM Stereo Multiplex Tuner is entirely self contained with its own built-in multiplex facilities. Capable of achieving the highest Laboratory Standards, its exceptional selectivity and sensitivity together with drift-free AFC performance insures effective reception of even the weakest multiplex or monaural FM signals.



Made in U.S.A.

KT-250A 50-WATT INTEGRATED STEREO AMPLIFIER

KT-250A **74.50** in Kit Form LA-250A **99.50** Completely Wired

- Separate Bass & Treble Controls • 3rd Channel Output
- Response: 15-40,000 cps \pm .5db (at normal listening level)
- 50-Watts Monophonically—25 Watts Each Stereo Channel


Pacesetter quality, performance and design. Features include: unique "Blend" control for continuously variable channel separation—from full monaural to full stereo, 4-position Selector, Mode, Loudness and Phase switches. Individual bias and balance controls. Harmonic distortion, less than 0.25%. IM distortion, less than .5%. Hum and noise 77db below full output.

KT-550

Criterion™

100-WATT BASIC STEREO AMPLIFIER

Made in U.S.A.

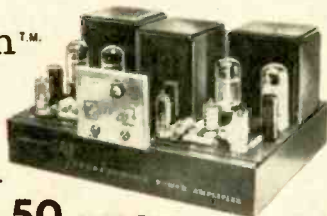


KT-550 **134.50** in Kit Form

LA-550 **184.50** Completely Wired

- Rated at 50-Watts per Channel
- Response from 2-100,000 cps; 0-1 db at 1-watt
- Massive Grain Oriented Silicon Steel Transformer
- Multiple Feedback Loop Design (over 50 db)
- Metered Calibration Control Panel
- Absolutely Stable Under Any Conditions of Load

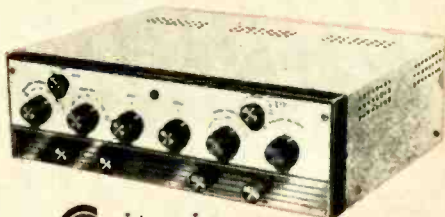A new "Laboratory Standard" dual 50-watt amplifier guaranteed to outperform any basic stereo amplifier on the market. Advanced engineering techniques plus the finest components ensure flawless performance. Distortion levels so low they are unmeasurable. Hum and noise better than 90 db below 50-watts. Complete with metal enclosure.



KT-600A **Criterion**™ Made in U.S.A.

PROFESSIONAL STEREO CONTROL CENTER

KT-600A **79.50** in Kit Form LA-600A **134.50** Completely Wired

- "Null" Balancing System • Response 5-40,000 cps \pm 1 db
- Bridge Control Provides Variable 3rd Channel Output
- Tape Head Playback Equalization for 4-Track Stereo
- Variable Cross Channel Signal Feed Eliminates Hole-In-The-Middle Effects

Sensitivity 2.2 mv for 1 volt out. Dual low impedance "plate follower" outputs 1500 ohms. Less than .03% IM distortion; less than .1% harmonic distortion. Hum and noise 80 db below 2 volts.



LT-200 MULTIPLEX ADAPTER **47.50** FACTORY WIRED & TESTED

Now enjoy stereo with all the fidelity and convenience that only FM can provide, by adding this brilliant new multiplex adapter to your tuner. Performs beautifully with virtually any late model wide band tuner equipped with a multiplex output.

Made in U.S.A.

Front panel selector switch provides for On-Off, Mono-FM and Stereo FM, while pilot lights indicate when power is on and when adapter is operating stereophonically. Complete with enclosure and all necessary audio cables.

Lafayette's NEW Easy-Pay-Plan **NO MONEY DOWN**



FREE!
YOURS FOR THE ASKING

LAFAYETTE RADIO, DEPT. 1K 2-1
P.O. BOX 10, SYOSSET, L. I., N. Y.

Send FREE 1962 Catalog featuring the complete line of Lafayette Stereo Components.

\$ Enclosed for Stock No.

Name _____

Address _____

City _____ Zone _____ State _____

find new
adventure in
amateur
radio...

with
Viking
1st choice of
amateurs the
world over!

loaded with features... kit or wired!



ADVENTURER —50 watts CW input 80 through 10 meters. 240-181-1... Kit Am. Net \$54.95	RANGER —75 watts CW input; 65 watts phone—160 through 10 meters. 240-161-2... Kit Am. Net \$229.50	VALIANT —275 watts CW and 55B; 200 watts AM—160 through 10 meters. 240-104-2... Kit Am. Net \$349.50
	240 161-1... Wired Am. Net \$329.50	240-104-2... Wired Am. Net \$439.50

FREE CATALOG



Complete specifications and schematics on all Johnson transmitters, amplifiers, station accessories, keys and practice sets!



E. F. JOHNSON CO.

2433 10th Ave. S.W. • Waseca, Minn.

NAME _____
ADDRESS _____
CITY _____ STATE _____

NEW products

POWER-LINE MONITOR

A power-line monitor manufactured by the Radio Corporation of America, 30 Rockefeller Plaza, New York 20, N.Y., alerts technicians to voltage problems before they can cause trouble. The Model WV-120A has an expanded scale from 100 to 140 volts (r.m.s.) and an accuracy of $\pm 2\%$ at 120 volts, $\pm 3\%$ at 100 and 140 volts. Fluctuations and "bounces" in the line voltage are revealed by the fast, moving-vane action, and the large scale can be read clearly from a distance of 10 feet or more. Price, \$14.95.



Model WV-120A has an expanded scale from 100 to 140 volts (r.m.s.) and an accuracy of $\pm 2\%$ at 120 volts, $\pm 3\%$ at 100 and 140 volts. Fluctuations and "bounces" in the line voltage are revealed by the fast, moving-vane action, and the large scale can be read clearly from a distance of 10 feet or more. Price, \$14.95.

TUBE TESTER MODERNIZING PANEL

Sencore's Model TM116 tube tester modernizing panel adapts any tube tester (except the "cardomatic" types) for handling RCA Nuvistors and Novars, G.E. Compactrons, and Sylvania 10-pin tubes. Plugging into an octal socket on the existing tester, the TM116 enables the instrument to make all



checks on the new tubes that it would normally carry out on standard types. Price, \$24.95. (Sencore, Inc., 426 S. Westgate Drive, Addison, Ill.)

LIGHTWEIGHT SOLDERING IRON

The lightweight "Penline-120" soldering iron introduced by the General Electric Co., Schenectady 5, N.Y., is intended primarily for production line operations, but it's also well-suited for maintenance, repair, laboratory, and "do-it-yourself" use. The plastic

BUILD THE
PROJECTS
DESCRIBED
IN THIS
ISSUE OF

WITH THESE



PRODUCTS

POPULAR
ELECTRONICS

LOW-PASS FILTER

Uses BUD AU-1083, 4"x4"x2" aluminum box \$1.29

BI-SLAVES FOR AG-1

Uses BUD CU-3002A, 4"x2 1/8"x1 1/8" aluminum chassis box 64¢

FLEA POWER GLOW LIGHT

Uses BUD AC-1610, 4"x4 1/2"x4" aluminum sloping panel box \$1.68

BUILD A RADIATION DETECTOR

Uses 2"x7"x5" zinc-steel chassis BUD CB-629 \$1.30

BUD BOTTOM PLATE

BP-706 69¢


All Bud products are available for immediate delivery from your authorized Bud Distributor. They are the best for applications described in these projects.

WATCH FOR THESE LISTINGS EVERY MONTH
IN POPULAR ELECTRONICS

BUD RADIO, INC.

2118 East 55th Street Cleveland 3, Ohio
Dept. P.E.

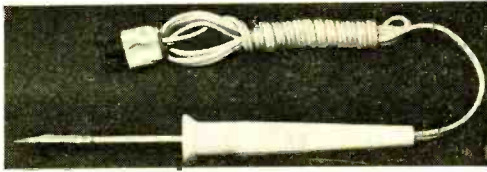
handle, designed for coolness and comfort. can be fitted with either 30- or 50-watt tip-and-heater assemblies in a variety of tip



styles. Price of the iron, complete with handle, cordset, and tip assembly, is about \$8.00.

SWEEP GENERATOR AND MARKER ADDER

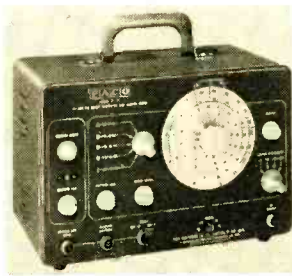Covering frequencies from 3 - 220 mc. in five fundamental ranges, the Paco G-32 sweep generator and marker adder is designed for easy operation.




An electronic voltage regulator keeps the amplitude constant as the r.f. output is swept in frequency, and dual attenuators permit

close control of output voltage. Sweep width is continuously variable (from 0 to over 20 mc. on high-frequency ranges). Internal blanking eliminates the return trace and provides a zero voltage reference line. The marker pips indicate spot frequencies on the displayed waveform without distorting its shape. Selling price of the G-32 in kit form is \$85.95, \$119.95 completely wired and tested. (Paco Electronics Co., Inc., 70-31 84th St., Glendale 27, N.Y.)

CRT REJUVENATOR/TESTER

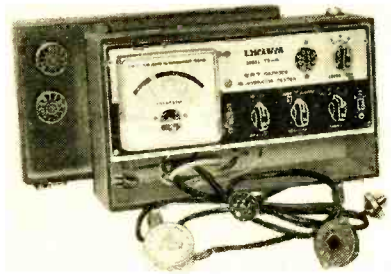Specifically designed for TV service technicians, the Model TE-19 CRT rejuvenator/



tester checks and repairs both black-and-white and color TV picture tubes without


BUILD THE FINEST

Professional Quality
CUSTOMIZED

TV KIT

On Easy "Pay As You Wire" Terms. Only \$15 for the Starting Package!

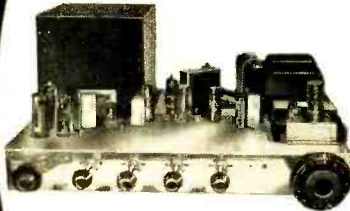The "PROFESSIONAL" Series—designed for the perfectionist seeking the finest in TV performance. Easy to assemble. No technical knowledge required. An ideal "Learning" Kit with a Complete Course of Study is available.



Also available:
WIRED CHASSIS
for custom installations with a choice



of vertical or horizontal controls and the newest 23", 24" or 27" CRT.

A few of the **Professional Quality Features:**

Choice of push-pull 10-watt audio or output to your Hi-Fi system... D.C. restoration... Ultra-linear sweep circuits... Standard Coil Guided Grid Turret Tuner... Super-sensitivity for fringe areas... Complete line of Accessories for Custom Installations.

Choice of 23", 24" or 27" CRT. Prices range from \$119 to \$199.

U.S. Armed Services and over 4000 schools and colleges have selected Transvision Receivers for educational television.

Interested in Electronics?

Learn the basic principles of electronics from the Course available with the Kit.



TRANSVISION New Rochelle, N.Y.
NE 6-6000



Beautiful Cabinets designed to enhance sound quality and blend with modern decor. For TV or combination TV and Hi-Fi.

ASSEMBLY MANUAL - \$2

See how easy it is to assemble the Transvision Kit. Cost of Manual refunded on purchase of Kit.

----- **START NOW - MAIL THIS COUPON** ----- Dept. PE
TRANSVISION Electronics, Inc., New Rochelle, N.Y.

- Send Free 8-page Catalog Enclosed is \$2. for Assembly Instructions so that I might see how easy it is to assemble the Transvision Kit. I understand that this will be refunded if I purchase a kit.
- Enclosed is \$15 for the Starting Package. I understand that I can buy packages one at a time as I wire. (Models range from \$119 to \$199.)

Name..... Address.....
City..... Zone..... State.....



FREE
TO YOU
and your friends

**RADIO SHACK'S
1962 ELECTRONICS
CATALOGS**

Plus
Every New Supplement
For Next 12 Months!

Our bigger, better catalogs offer the widest line of electronic parts and equipment in the world! Stereo, Hi-Fi, Ham Radio, Test Equipment, Pre-Recorded Tapes, Tape Recorders, Records, Parts—plus 30 pages of Kits! 340 pages—over 100,000 items! No Money Down credit terms. Money back guarantee of satisfaction.

MAIL THIS COUPON TODAY

RADIO SHACK Corp.
730 Commonwealth Ave., Boston 17, Mass.

Send Radio Shack's famous electronics catalogs for one year—FREE and POSTPAID.

Your Name _____

Your Address _____ 61L7A

City and Zone _____ State _____

For a Friend _____

Address _____ 61L7A1

City and Zone _____ State _____

Wiley BOOKS

Want to get ready for
COMPUTERS?

Start here! Read
**UNDERSTANDING
DIGITAL COMPUTERS**

By PAUL SIEGEL, *International Electric Corp.*

Here's the firm grounding you need, for what makes computers and data processors tick. Study this book: it gives bed-rock principles rather than the gadgets that go so quickly out of date. Study this, and you'll soon be able to talk the computer language. Most of the book goes from theory to basic building blocks, then on to showing how these blocks combine into computers. Capstone of the book: the description of the making of a specimen computer. 1961. 403 pages. \$8.50.

At your bookstore, or

JOHN WILEY & SONS, Inc.

440 Park Avenue South, New York 16, N.Y.

products

(Continued from page 107)

removal from the set. The TE-19 checks for emission, shorts and leakage; repairs inter-element shorts and open circuits. Each gun of a color tube is checked and corrected separately. The unit, including tube socket adapters to accommodate 110° tubes, is priced at \$32.50. (*Lafayette Radio Electronics Corp.*, 165-08 Liberty Ave., Jamaica 33, N.Y.)


ALL-PURPOSE VTVM

A versatile and rugged all-purpose VTVM for radio, TV, and experimental work is offered by the *Precision Apparatus Co., Inc.*, Glendale 27, L.I. The Model 48 employs a balanced vacuum-tube bridge circuit for all voltage and resistance measurements. It provides 7 d.c. voltmeter ranges (7 1/3 megohms/volt sensitivity on the 1.5-volt range), 7 a.c. voltmeter ranges (peak to peak and r.m.s.), 7 decibel ranges, and 7 ohmmeter ranges. A 3-way probe permits rapid, accurate testing. Price, \$55.95.



ULTRAVIOLET KIT

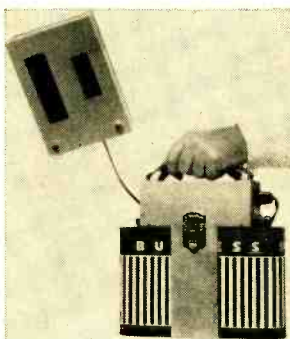The hobbyist or young scientist needs only a screwdriver to assemble the "Mineralight Gemini" ultraviolet kit.




Equipped with both long- and short-wave lamps, it can be used for fluorescent analysis, mineral exploration, and gem identification. The lamps operate from a wall plug or, with the aid of the "Mineralight

Power Pack" adapter, from a 6-volt battery (illustrated). The kit costs \$19.95, the adapter, \$14.95. (*Ultra-Violet Products, Inc.*, 5114 Walnut Grove Ave., San Gabriel, Calif.)

SUBMINIATURE UTILITY LAMP

Small in size but high in intensity, the Tensor Model 5979 subminiature all-purpose utility lamp can easily be carried in an overnight bag. The lamp, which measures only 3" x 2" x 7" when folded, gives more than adequate light for hobby work, reading or shaving. Available in a variety of colors, the Model 5979 is priced at \$14.95. (Tensor Electric Development Co., Inc., 1873 Eastern Parkway, Brooklyn 33, N. Y.)

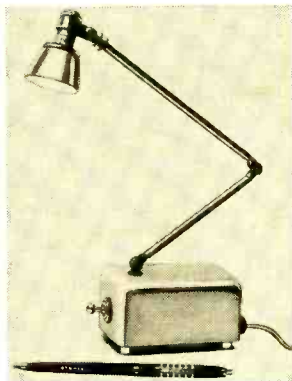

velopment Co., Inc., 1873 Eastern Parkway, Brooklyn 33, N. Y.)

BATTERY ELIMINATOR/CHARGER

The EICO Model 1064 extra-low ripple battery eliminator and charger provides the undistorted d.c. necessary for servicing transistorized equipment or for any other application where ripple must be held to a minimum. Its two ranges (0-8 volts @ 10 amperes, continuous, and 0-16 volts @ 6 amperes, continuous) are controlled by a variable transformer and monitored by a voltmeter and dual-range ammeter. More than enough current is available for battery charging, and all parts are operated well below their stated voltage and current ratings. The Model 1064 sells for \$43.95 in kit form, \$52.95 wired. (EICO Electronic Instrument Co., Inc., 33-00 Northern Blvd., L.I. City 1, N.Y.)




RADIO CONTROL RECEIVER

A new ruggedized, single-channel receiver has been released by Gyro Electronics Co., 36 Walker St., New York 13, N. Y. Said to be the best available for proportional control, the "Tone King" has a tuning range of 26.995 to 27.255 mc. and is actuated by a 400-800 cycle tone. Use of a vacuum-tube detector and 2-stage transistor amplifier in-

dures maximum sensitivity and temperature stability. The relay is a standard 5K Gem. Power requirements: 1½ volts "A" and 22½ volts "B"; weight, 2.2 oz.; size, 1" x 1⅝" x 2". The unit is priced at \$24.95.

VERSATILE TUBE TESTER

Claimed to be obsolescence-proof, the Model 700 dynamic mutual conductance tube tester checks both old and new TV and radio tubes, including Nuvisors, 10-pin tubes, and 12-pin Compactrons. European hi-fi tubes, voltage regulators, and most industrial types are also accommodated. A multiple-socket section provides a quick check for most standard tubes, and other types are tested in a simplified switch section. The tester, which automatically compensates for line voltage variations, sells for \$169.95. (B&K Manufacturing Co., 1801 W. Belle Plaine Ave., Chicago 13, Ill.)

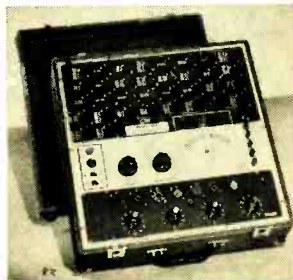

HAM COMMUNICATIONS RECEIVER

Lafayette Radio's Model HE-30, a 0.55-30 mc. communications receiver, is just the thing for today's crowded ham bands. Its illuminated slide-rule dial has markings every 5 kc. on 80 and 40 meters, every 20 kc. on 20 and 15 meters, and every 50 kc. on 10 meters. The receiver's sensitivity is 1.0 microvolt with a 10-db signal-to-noise ratio, and there is a built-in Q-multiplier for better selectivity. Among the HE-30's other features are an automatic noise limiter, an adjustable BFO, and a transformer-



powered full-wave rectifier circuit. Price, \$99.95; an additional \$7.95 will buy you a matching Model HE-11 external speaker. (Lafayette Radio, 165-08 Liberty Ave., Jamaica 33, N.Y.)

Transistor Topics

(Continued from page 84)


as: a 50-watt stereo amplifier; a transistorized thermometer; a 10-transistor portable radio; a 5-band portable receiver; a number of hearing aids, including eyeglass styles; miniature tape recorders, power megaphones, intercoms; transistorized CB equipment; and a variety of kit and component bargains, including high-frequency transistors for \$1.65 and "packs" of four *pnp* or *npn* transistors for 98 cents.

Specs Got You Down? The interpretation of semiconductor data sheets can be a real chore. Even experienced design engineers run into trouble on occasion. One reason for the difficulty is the many different ways in which a basic characteristic can be specified, depending on individual manufacturer preferences. High-frequency characteristics, for example, may be specified as *alpha* cutoff, *beta* cutoff, figure of merit, gain-bandwidth product, or, in the case of switching units, as switching speed in microseconds. Another reason is that "maximum" ratings must be correlated with circuit conditions.

Motorola has taken a giant step toward eliminating the mystery of data sheets with the publication of a useful little booklet entitled "How To Get More Value Out of a Transistor Data Sheet." For your free copy, write to Motorola Semiconductor Products, Inc., 5005 East McDowell Road, Phoenix 8, Arizona, and request Bulletin No. PX-104.

That does it for now. We'll have more info and news in December.

—Lou

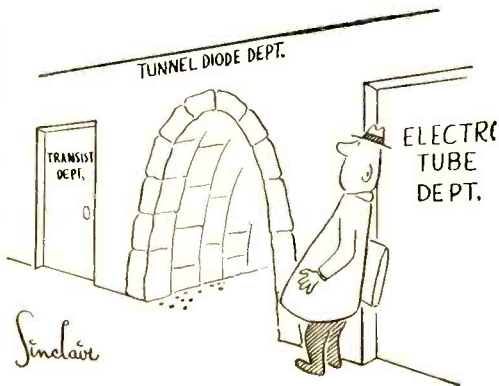

Always say you saw it in—POPULAR ELECTRONICS



FREE
TO YOU
and your friends

**RADIO SHACK'S
1962 ELECTRONICS
CATALOGS**

Plus
Every New Supplement
For Next 12 Months!

Our bigger, better catalogs offer the widest line of electronic parts and equipment in the world! Stereo, Hi-Fi, Ham Radio, Test Equipment, Pre-Recorded Tapes, Tape Recorders, Records, Parts—plus 30 pages of Kits! 340 pages—over 100,000 items! No Money Down credit terms. Money back guarantee of satisfaction.

MAIL THIS COUPON TODAY

RADIO SHACK Corp.
730 Commonwealth Ave., Boston 17, Mass.

Send Radio Shack's famous electronics catalogs for one year—FREE and POSTPAID.

Your Name _____
Your Address _____ 61L7B
City and Zone _____ State _____
For a Friend _____
Address _____ 61L7B1
City and Zone _____ State _____



**SELL YOUR USED
EQUIPMENT Through
POPULAR ELECTRONICS'
Classified Columns!**

The 400,000 purchasers of **POPULAR ELECTRONICS** are always interested in good used equipment or components. So, if you have something to sell, let PE readers know about it through our classified columns. It costs very little: **just 60¢ a word**, including name and address. Minimum message: 10 words.

For
further
information
write:

Martin Lincoln
POPULAR ELECTRONICS
One Park Avenue
New York 16, N. Y.

now, for the first time,

Cabinart

SPEAKER SYSTEMS

yours
for
only

\$15.

... and \$22.50

test and compare

in your own home... the reputation for quality which we have built since 1948 is in your hands... for 13 years Cabinart has been a leader in the high fidelity field. This introduction of quality speaker systems at low cost is completely in line with our progressive development program... prove to yourself that CABINART MAKES THE AUDIBLE DIFFERENCE!

cabinart guarantees

- you must be satisfied that this unit is the best performing you have ever heard — at any comparable price or in many systems costing dollars more,
- you must be satisfied that this unit is the greatest advance in Cabinart's 13-year experience,

YOU MUST BE SATISFIED WITH CABINART SPEAKER SYSTEMS FOR 10 FULL DAYS OR YOUR MONEY BACK

All Cabinart Systems Guaranteed In Writing For One Full Year!


cabinart cabinets

are made of an extremely dense wood product 3/4 inch thick throughout, solidly glued. Sanded, ready to finish. Extra heavy construction achieves maximum possible speaker response. Cabinart's unique principle creates acoustical resistive loading of the loudspeaker cone effectively improving low end efficiency to make it comparable to mid and high range response.

cabinart acoustical eng. corp.

Haledon, New Jersey

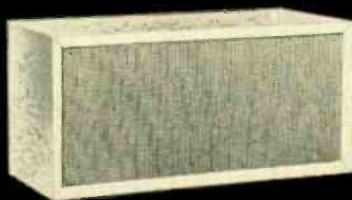Cabinart Is One Of America's Largest Manufacturers of Speaker Systems and Enclosures




mark I 8" model

11" high x 9 1/2" deep x 23" long
Shipping Weight: 27 lbs.

\$15.00 FOB Factory

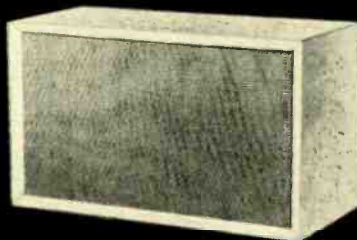Extended range domestic speaker with new hi-efficiency magnetic circuit. Ideal for medium and low level monaural or stereo reproduction. 1" voice coil with 8 ohms impedance. Speaker response 45 to 13,000 cps. 3.16 oz. new type magnet.



mark II 12" model

14" high x 11 1/2" deep x 23 3/4" long
Shipping Weight: 37 lbs.

\$22.50 FOB Factory

12" coaxial 6.3 oz. Alnico V magnet with 1" voice coil, heavy one-piece cone and specially designed 3" Alnico V PM tweeter. Power rating, 12 watts; impedance, 8 ohms. Speaker response 40 to 15,000 cps. Built-in high pass filter.

These units also available in Lafayette Radio Stores or through Lafayette's mail order division.

Cabinart Acoustical Eng. Corp.
36 Geyer St., Haledon, N. J.

Please ship the following to be used in my home for 10 full days. I understand unit (s) may be returned and my money refunded within that time unless fully satisfied.

_____ Mark I \$15.00 each _____ Mark II \$22.50 each

(Please make check or money order payable to Cabinart Acoustical.)

Name _____

Address _____

City _____ State _____



If you've recently changed your address, or plan to in the near future, be sure to notify us at once. We'll make the necessary changes on your mailing plate, and see to it that your subscription continues without interruption. Right now—print the information requested in the spaces below and mail it to: POPULAR ELECTRONICS, 434 So. Wabash Ave. Chicago 5, Illinois.

Name *Please PRINT!*

*Account No.

Old Address

City State

New Address

City Zone State

Mail copies to new address starting with issue.

*(Your Account Number appears directly above your name on the mailing label.)

NEW **FIRST MINIATURIZED TWO-WAY RADIO!**
WALK-A-PHONE TWO-WAY WALKIE-TALKIE **\$29.50** EACH

Crystal Control American Made—sending and receiving set in the smallest metal case at the lowest price!

Crystal microphone loud speaker 9-volt transistor radio battery, transistorized transmitting and receiving sets with the latest miniaturized printed circuitry. **CITIZENS BAND—NO LICENSE. NO EXAMINATION. NO AGE LIMIT.**

A ruggedly constructed hand held unit for hunting, fishing, construction workers, surveyors, stockyards, warehouses, firemen, police, etc. Will operate between vehicles.

EXCLUSIVE! WORLD'S SMALLEST 5-TRANSISTOR TRANSCIEVER CITIZEN'S BAND
Made in U.S.A. Fully Guaranteed.

TO ORDER: Enclose check, cash or money order for postpaid shipment, or \$5.00 deposit per unit for C.O.D.—ten days unconditional money back guarantee. California residents add 4% Sales Tax. Dealers inquire.

WORLD WIDE COMPANY
 1212 TOWNE WAY DRIVE EL MONTE, CALIFORNIA



On the Citizens Band

(Continued from page 75)

mobile roof with plastic tape applied in long strips. (Tape placed on the car's sharp edges will protect your car's finish.) Then run the coax to your transceiver through a window. Note that no holes need be drilled and the antenna can be removed with no after-effects.

Cut Thermal Drift. With the cold weather coming upon us in many parts of the nation, CB'ers using tunable receivers in their cars might notice what they consider to be excessive warm-up drift. Temperature compensation is a difficult thing to accomplish to perfection when you consider that the range of temperature in a mobile unit might be from below zero (if the car is parked outside overnight) to above 100 degrees when the set warms up.

If you do park your car out-of-doors during the winter, don't turn your transceiver on until your car heater is going strong. You'll cut thermal drift in the receiver and lessen the chance of cracking the glass on a tube or two when the tubes warm up.

New CB Products. In line with the idea of selective calling and communications, the Martin Development Company has announced the availability of a CB-



BEEPER. A transistorized 1000-cycle tone generator designed for use with any transceiver, the BEEPER measures only 2" x 3" x 4" and is finished in attractive antique black and gray hammertone.

Always say you saw it in—POPULAR ELECTRONICS

Two models are available, a de luxe self-powered unit, and a unit which takes its power either from the transceiver or a separate source. The manufacturer states that transceiver connections are easily made. For further details, write to P. O. Box 82, San Antonio, Texas.

An interesting adaptation of an antenna technique used on jets and guided missiles is represented by the new General Electromagnetics Corp. "Omni-Slot Boundary Antenna." The manufacturer of this broadband vehicular antenna



claims that the device has the same gain as a full $\frac{1}{4}$ -wave vertical antenna, yet its circular design places it only two inches above the car roof. Three models are being made, one maintaining full efficiency over CB frequencies plus the amateur 10- and 6-meter bands. Fading and blind spots are said to be eliminated, and full gain at high vehicular speeds is claimed. Contact this company at 11719 East Washington Blvd., Whittier, Calif., for further information.

"CB News and Views." That's the name of an outstanding publication in "Chicagoland," and the official voice of the Citizens Radio League (Box 28, Northlake, Ill.). Each month's issue spotlights a club member as "Personality of the Month," and other items tell of the various activities of the club and its members. Although this is only a two-sheet publication, it's printed by offset and runs some excellent-quality photographs.

Two items in a recent issue of "CB News and Views" especially caught our eye, since they are subjects which probably concern CB'ers everywhere. The first item, headed "No Exclusive Channels," dealt with the problem of who has the prior right to the use of a particular channel—a Civil Defense Net or a private individual. The club paper

FREE

to you and your friends RADIO SHACK'S 1962 ELECTRONICS CATALOG

Plus

**EVERY NEW
SUPPLEMENT
FOR NEXT
12 MONTHS**



Send coupon below for your FREE personal copy of Radio Shack's 1962 giant catalog ... a 340-page book—largest in our history!

It simply brims with over 100,000 items for everyone who enjoys the fascination of electronics. See the world's largest line of Stereo, Hi-Fi, Ham Radio, Test Equipment, Pre-Recorded Tapes, Tape Recorders, Records, Test Equipment . . .

Plus a brand new line of build-it-yourself kits—finest for the money.

Every item is easy to own on our new No Money Down Credit terms. Your satisfaction guaranteed or money back.

When you send coupon, you get our giant catalog plus all other books for 1 year. Fill in a friend's name, too.

RADIO SHACK Corp.
Boston, Massachusetts

MAIL COUPON TODAY

RADIO SHACK Corp.
730 Commonwealth Ave., Boston 17, Mass.

Send Radio Shack's famous electronics catalogs for one year—FREE and POSTPAID.

Your Name _____ 61L7


Your Address _____

City and Zone _____ State _____

For a Friend _____ 61L7I

Address _____

City and Zone _____ State _____

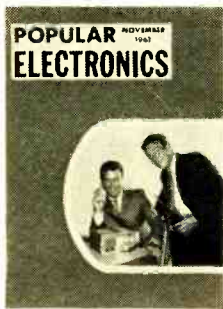

Send
POPULAR
ELECTRONICS
Every
Month

NAME.....
ADDRESS.....
CITY..... ZONE..... STATE.....

- 3 years for \$10
- Check one: 2 years for \$7
- 1 year for \$4
- Payment Enclosed Bill Me

In the U. S., its possessions and Canada. Foreign rates: Pan American Union countries, add .50 per year; all other foreign countries, add \$1 per year.

Mail to: POPULAR ELECTRONICS

Dept. PE-1161H, 434 S. Wabash Ave., Chicago 5, Ill.

LEARN WHILE YOU SLEEP!



Experiment in this fascinating, educational new field. Use your phono, recorder or amazing new "Electronic Educator" endless tape recorder. Free catalog lists over 200 unusual tapes, records, equipment for sleep-learning & hypnosis experimenters. Sleep-Learning Research Ass'n., Box 24-PE, Olympia, Wash.

POLICE, CITIZENS BAND, AIRCRAFT



Monitor these and other signals, from any auto radio using the inexpensive and dependable Model 107 transistorized converter. Any SINGLE frequency between 25-50 and 108-175 mcs. Fully miniaturized, it can be installed in seconds. Designed to give years of dependable, trouble free service. Order now, or send for free information. State frequency. Guaranteed for one full year.

Model 107 \$14.95

ROBIN RADIO CO. Box 217 Greenville, Texas

pointed out that regulations provide for the shared use of all CB channels. In the event that a private party wants to use a channel on which a CB drill is being held, he can request the CD net to stand by. The only possible exception would be if the net were actually handling emergency traffic, but in this situation all other civilian communications would probably be closed down anyway.

The second item concerned a cross-country "Mayday." A CB'er aboard his boat was in distress on Lake Superior. Two operators, one in Chicago and another in Duluth, Minn., heard his call and telephoned the Coast Guard. Meanwhile, skip signals from Texas were booming in. But when the Texas operators were informed of the emergency, they stood by.

The channel on which this little drama took place? Of all the ones to choose, Channel 11! While we do offer a hearty "well done" to all those stations who participated, even if it was only by *not* transmitting, the implications behind this incident should be clear. In every call area, Channel 11 is over-crowded, while many others, including Channel 13, are empty.

We'd like to make a strong plea for the organized monitoring of Channel 13 in areas where boating is popular, and for a continuous "watch" by motels, restaurants, etc., of Channel 15, the semi-official "national travel channel." -50-

Solution to Crossword Puzzle

(Puzzle appears on page 88)

C	A	M		S	T	A	G	E		S	T	R
A	G	A		O	R	B	I	T		L	A	P
T	O	G	G	L	E		B	A	R	I	U	M
		N	O	D	E	S		L	A	D		
A	R	E	A		S	C	C		P	E	E	R
W	A	T	T	S		E	R	G		R	C	A
A	T		S	O	S		O	A	R		H	F
R	I	A		D	O	T		P	I	L	O	T
E	O	N	S		W	E	T		L	A	S	S
		O	C	T		N	A	M	E	D		
R	A	D	I	A	L		P	A	D	D	E	R
I	N	E		C	O	N	E	S		E	I	R
G	A	S		T	P	A	D	S		R	A	S

Across the Ham Bands

(Continued from page 81)

News and Views

Gary Yantis, KØBHM, 10809 Johnson Dr., Shawnee, Kansas, whose Novice station photo was the July contest winner, brings us up to date on his activities. Gary now has his General Class ticket, and has become a DX and contest man. "If there is a big 'pile up' after a rare DX station, look for me at the bottom of the pile," he reports. Gary has earned the following certificates so far: WAC, WAS, WAK, WWC, CP-20, and RCC. He is also very close to DXCC. WAC is "Worked All Continents," WAS is "Worked All States," CP-20 stands for "Code Proficiency 20 WPM," RCC is "Rag Chewers' Club," and DXCC is "DX Century Club," but I have no idea what the other two are. . . . **"Ken," KN3OEO**, 909 Blunston St., Columbia, Pa., offers to help you obtain your Novice license. He operates on 40 meters with a Knight T-50 transmitter and a Knight R-100 receiver. . . . **Ron Pavlucik, KN1REN**, 87 Clover St., Stratford, Conn., worked 10 states in two months on 80 meters with his Heathkit DX-60 feeding a 65' end-fed antenna. Then he tried 15 meters and worked three new states in two days. Ron receives on a National NC-54.

Tim Wright, KNØBFR, Hamburg, Iowa, has worked 33 states, Canada, and Puerto Rico

in seven months on the air, operating on 40 and 15 meters. He also earned a 15-wpm code-proficiency certificate. . . . **Art Kobres, K4FWJ**, 3904 San Juan St., Tampa, Fla., worked 20 states the first two days after getting his Novice ticket. It took another five months to work the other 30 states. Art also worked all continents as a Novice. He used a Knight T-50 transmitter feeding a great variety of antennas from "long wires" to Cubical Quads, and a Hallicrafters S-53A aided by a Q-multiplier in running up this record. As a General, Art is now using a Heathkit DX-100B transmitter and a Hammarlund HQ-110C receiver.

Bob Hough, WN4AJF, 3824 Cambria St., Lynchburg, Va., receives on a National HRO-7, which he says was original equipment on Noah's Ark. With it and his EICO 720 transmitter feeding a dipole and a couple of long-wire antennas—not all at once—he worked 21 states his first month on the air. He spends most of his time on 80 and 40 meters, dipping into 15 meters for an occasional contact. . . .

Cary Africk, WV2SYD, 3739 Neptune Ave., Brooklyn 24, N. Y., only has room for a 15-meter dipole, which is just 10' high; but in five days on the air, he made 22 contacts in four states. An EICO 720 transmitter generates his r.f., and an old Hallicrafters S-20R, plus a Heathkit Q-Multiplier, draws in the signals.

Ira Reed Moore reports that his boss and "pardner," **W4TRQ**, Orlando, Fla., who also operates "portable-7" in Salt Lake City, Utah, at 1281 Hyland Lake Drive, is **Karl von Mueller**, the writer, treasure hunter, and ad-

Up in the air over your next project? Make it . . .

hallicrafters great new "SKY BUDDY" short wave ^{PLUS} _{AM} receiver kit!

You're "airborne" fast with this outstanding new HALLI-KIT, precision-engineered in the most respected communications laboratories in the world—Hallicrafters.


- AM plus 2 short wave bands (2-5.5 mc. and 5.7-16.4 mc.) covering aircraft, ships, foreign stations, amateurs, etc.
- Transformer-type power supply. Superheterodyne circuit with superb sensitivity and planetary drive for sharp, selective tuning.
- Built-in speaker and headphone jack, with function switch. Separate switch for voice or code reception.



S-119K "Sky Buddy" Kit
ONLY \$39.95

P.S. For another \$10.00, you can buy it factory wired and tested.

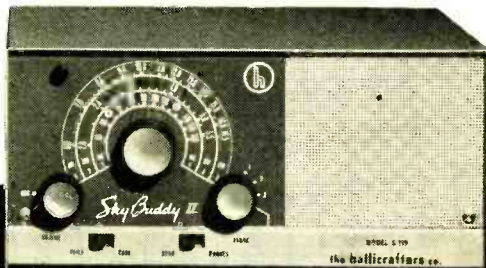Sold only through authorized
Hallicrafters distributors and dealers.




Send for Hallicrafters'
"GUIDE TO
SHORT WAVE LISTENING"



We've just published a new miniature book that tells you the entire story of Short Wave—64 pages of facts on how it works, what you can hear, where and when to listen, antennas, tuning information, etc. Send 35¢ to Hallicrafters, Dept. 21, Chicago 11, Ill.

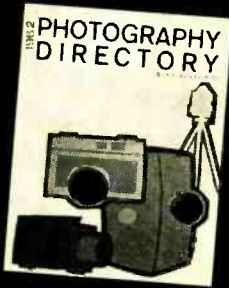THE WHOLE
WORLD OF
PHOTOGRAPHIC
EQUIPMENT
IS YOURS IN



Your guide to what to buy...
how to buy... where to buy!

Featuring over 176 pages of vital information on all the products on the photo market—cameras, projectors, flash attachments, lighting and sound equipment, darkroom supplies, accessories, and film. Makes selecting your new equipment as easy as

1 COMPARE

performance data on still and movie cameras, movie projectors, and electronic flash equipment with easy-to-read charts.

2 CHECK

the detailed specifications on each and every product. Get prices, manufacturers, and distributors.

3 SEE

clear, accurate pictures of everything from gadget bags to underwater apparatus.

It's all yours in the 1962 Photography Directory and Buying Guide—now on sale at your favorite newsstand. Or order your copy with this handy coupon. **ONLY 1.00**

Popular Photography Book Service
One Park Avenue, New York 16, N. Y.

Please send me a copy of the 1962 PHOTOGRAPHY DIRECTORY AND BUYING GUIDE. I enclose \$1.00, the cost of the DIRECTORY, plus 10¢ to cover mailing and handling charges. (Canada and Foreign \$1.25 plus 10¢ postage)

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

EF2039



J. E. Brazee, KNØCWW, Sumner, Nebr., worked 26 states in his first 5 months on the air—not bad for a 34-year-old “beginner.” His transmitter is an EICO 720, his receiver a Hammarlund HQ-145.

venturer. If you make a solid contact with Karl and follow it up with a QSL card, you will get a return QSL with a \$500.00 bill attached. Of course, the bill is Confederate money. Look for W4TRQ, fixed, portable, or mobile, on 20 and 40 meters. He uses a Multi-Elmac AF-68 transmitter and a PMR-8 receiver. When not in the car, the antenna is a vertical. In the car, it is a Mosley MA-3 “Mobileer.” . . . Lyle “Shortie” Murphy, KN5KJY, 8174 Crestview Drive, Houston 28, Texas, has been on the air for about 10 weeks. Working 40 meters almost exclusively, he has worked over 100 stations in 16 states. A Johnson Adventurer running 50 watts generates the r.f. that his ½-wave dipole antenna bounces off the ionosphere. A Hallicrafters SX-101 and an S-38E do the receiving. . . .

Mark Alan Rowland, W4UCZ, checked with the FCC about what type of calls the WN4's now on the air would receive when they get their Generals. The answer was “WA4,” not “W4.” The FCC did not issue WV4 calls in the southern states, since “WV4” was already reserved for Novices in the Virgin Islands.

Larry Aldrich, KN8ZZW/K8ZZW, Maple Rapids, Mich., likes 80 and 15 meters. He has a dipole for 80 and a “1-element beam” for 15. An EICO 720 does the transmitting, and a Hammarlund HQ-110C does the receiving. In two months on the air, he has made 110 contacts, 69 of them confirmed. Alaska is his best DX. Larry's General license is on the way, so his Novice career is going to be a short one. . . . Dave Edger, KN5JBW, 4006 N. Elgin Ave., Tulsa 6, Okla., would like to work Alaska and Hawaii, but he does not think he is the only Novice with that wish. If you want to work Oklahoma, Dave is your boy. He's on 40 and 15 meters, with 40 being his best band. His Globe Chief De luxe transmitter excites a Mosley V-4-6 vertical antenna, and his receiver is a Hammarlund HQ-129X. Thirty-four states, 30 confirmed, and 250 contacts make up his record. Dave does his best to paper the walls of other ham shacks by QSL'ing 100%.

Send all your material for “Across the Ham Bands” to: Herb S. Brier, W9EGQ, POPULAR ELECTRONICS, P.O. Box 678, Gary, Indiana. Until next month, 73,
Herb, W9EGQ

Herb, W9EGQ

Herb, W9EGQ

Always say you saw it in—POPULAR ELECTRONICS

SHORT-WAVE MONITOR CERTIFICATE APPLICATION

To become a Short-Wave Monitor registered with POPULAR ELECTRONICS, just follow these simple directions:

- 1 Fill out the form below. (You must be a short-wave listener presently active in the hobby to be eligible for a Short-Wave Certificate.)
- 2 Send us 10 cents in coin to cover the cost of the certificate as well as the handling and registration

costs. If you live outside the United States and cannot obtain U. S. coins, send either 15 cents in Canadian currency or two International Reply Coupons (IRC's).

- 3 Insert the application form, coins (or IRC's) and a stamped, self-addressed envelope in another envelope and mail it to:

Monitor Registration, POPULAR ELECTRONICS
One Park Avenue, New York 16, N. Y.

(Please Print)		Ham Call-Area Prefix	
Name		State	
Address		City	Zone
Receivers	Make	Model	
	Make	Model	
Principal SW Bands Monitored		Number of QSL Cards Received	
Type of Antenna Used			
Signature		Date	



PERSONAL Messenger

- No license required—may be used at once!
- Meets FCC requirements for use with licensed Citizens' Band stations, too!

This is the new "Personal Messenger"—a superbly engineered 2-way crystal-controlled transceiver so compact it fits in your hand—so flexible it can be used in thousands of applications! 11 transistors and 4 diodes—superheterodyne receiver with exclusive tuned R.F. amplifier gives you twice the sensitivity and more than 40% more range than units with conventional circuitry! Powerful two-stage transmitter delivers more power output than similar units with the same rated input! Unmatched audio intelligibility and razor-sharp voice reproduction—automatic noise limiter—automatic volume control—positive squelch control—elastic hand strap—operates on penlight or rechargeable nickel-cadmium batteries. **\$109.50**

ILLUSTRATED AT LEFT—The Viking "Messenger"—maximum legal power Citizens' Band crystal-controlled transceiver. Excellent receiver sensitivity and selectivity—highly efficient transmitter punches your signal home! Built-in squelch—AVC—ANL. With tubes, push-to-talk microphone and crystals for 1 channel. **FROM \$134.95**



FREE
Color Brochure

WRITE TODAY



E. F. JOHNSON COMPANY

2411 Tenth Avenue S. W. • Waseca, Minnesota

• Please rush me your full color brochure.

NAME _____

ADDRESS _____

CITY _____ STATE _____

Manufacturers of the world's most widely used personal communications transmitters

Free

ALLIED

444-PAGE ELECTRONICS CATALOG

WORLD'S BIGGEST • MOST COMPLETE

*best buys
for 1962*

**EVERYTHING IN
ELECTRONICS
including exclusive
products & special
values available
only from
*ALLIED***

**Send
for it
today!**

including the
complete 1962
knight-kit
CATALOG
pages
585-640

ALLIED
ELECTRONICS
for everyone

1962
OUR 41st YEAR
CATALOG 210
INDEX: PAGE 201

ALLIED RADIO
100 W. WESTERN AVENUE • CHICAGO 24, ILLINOIS • HAYMARKET 1-6000



**SAVE
MOST
ON EVERYTHING IN ELECTRONICS**

- New Stereo Hi-Fi Systems—Everything in Hi-Fi Components
- New Multiplex Stereo FM • All-Transistor Stereo Hi-Fi
- Money-Saving Build-Your-Own KNIGHT-KITS® for Every Need
- Best Buys in Tape Recorders, Tape, and Supplies
- Citizens Band 2-Way Radios • Short-Wave Receivers
- Amateur Receivers, Transmitters, and Station Gear
- Latest Public Address Systems, Paging and Intercom Equipment
- TV Tubes, Antennas, Accessories • Batteries, Wire and Cable
- Test and Laboratory Instruments • Tools, Hardware
- Huge Listings of Parts, Tubes, Transistors, Technical Books

**NEW Multiplex Stereo FM
All-Transistor Stereo Hi-Fi**

exclusive money-saving KNIGHT® products

SAVE MOST on famous KNIGHT Stereo Hi-Fi—comparable to the best in quality, styling and performance, yet priced far lower. Select super-value KNIGHT components or complete systems (including latest Multiplex Stereo and All-Transistor hi-fi) and save most. KNIGHT products are acclaimed by all those who recognize integrity in design and manufacture and who appreciate value.

new

NO MONEY DOWN

on Allied's new Credit Fund Plan
Now—enjoy 50% more buying power—up to 24 months to pay—see our 1962 Catalog for simple details.

SEND FOR 444-PAGE CATALOG TODAY!

Satisfaction Guaranteed or Your Money Back

ALLIED

BIG PLUS!
in your 1962
ALLIED
CATALOG

includes complete catalog featuring over 90 exciting

knight-kits 
A PRODUCT OF ALLIED RADIO

NEW for '62 and simply great!

available only from **ALLIED**

new
HI-FI KITS



All-In-One FM-AM Tuner-Amplifier Kit with latest built-in MULTIPLEX Stereo FM, less case \$129.95



MULTIPLEX Self-Powered Adapter Kit, for Stereo FM reception..... \$19.95



Deluxe Stereo FM-AM Tuner Kit with latest built-in MULTIPLEX Stereo FM.....\$99.95



ALL-TRANSISTOR 50-Watt Stereo Amplifier Kit, less case.....\$79.95

new
HOBBYIST KITS



ALL-TRANSISTOR Wireless Intercom System Kit (2 units).....\$45.90



TRANSISTORIZED Electronic Tachometer Kit. \$24.95



Amazing 100-In-1 Electronic Science Lab Kit..... \$29.95



ALL-TRANSISTOR 2-Band AM-Shortwave DX'er Radio Receiver Kit..... \$19.95

building a Knight-Kit is the most satisfying do-it-yourself experience in the world!

5 BIG REASONS WHY:

- **Convenience Designed**—makes you a kit-building expert—even the very first time!
- **Wonderful to Build**—you'll marvel at the sheer ease of assembly with the exclusive "show-how" manual guiding you like a good instructor.
- **You Own the Best**—you'll enjoy with pride a true custom-built product, professional in its engineering and performance.
- **You Save So Much**—because you buy direct from Allied at our money-saving volume prices—and because you do the easy assembly yourself.
- **Easiest to Buy**—NO MONEY DOWN on Allied's new Credit Fund Plan—easiest terms ever!

MONEY BACK GUARANTEE: Buy any Knight-Kit. Build it! Use it! You must be satisfied or you get your money back!

see more than 90 KNIGHT-KITS

- 21 HIGH-FIDELITY KITS
- 25 HOBBYIST KITS
- 31 INSTRUMENT KITS
- 14 AMATEUR & CITIZENS BAND KITS

KNIGHT-KITS are also available in Canada


new



Phone and CW 60-Watt Ham Transmitter Kit.....\$49.95



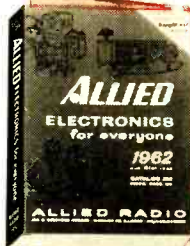Mutual Conductance Tube Tester Kit..... \$99.50



- World's Largest Stocks • Lowest Money-Saving Prices
 - Fastest Shipment • Expert Help • Easiest-Pay Terms
 - Satisfaction Guaranteed or Your Money Back
- send for the world's biggest electronics catalog!

Free

ALLIED RADIO, Dept. 201-L1
100 N. Western Ave., Chicago 80, Ill.

Send FREE 1962 ALLIED 444-page Catalog

Name _____
PLEASE PRINT

Address _____

City _____ Zone _____ State _____

Send for it today!

RADIO  World's Largest Electronic Supply House

DOUBLE POWER WITH 20 DB GAIN

IN SIGNAL TO NOISE RATIO

Hy-gain Colinear Ground Plane FOR CITIZENS BAND

3.4 DB OMNIDIRECTIONAL GAIN IN FIELD STRENGTH INTENSITY AS MEASURED BY THE NATIONAL BUREAU OF STANDARDS APPROVED METHOD.

The Hy-Gain colinear 3-way length colinear ground plane—unlike multielement beam antennas which concentrate energy in one or more directions at a sacrifice in power in other directions, achieves gain through colinear action which concentrates more power at lower angles to the horizon. The Colinear Ground Plane performs equally well receiving or transmitting, greatly increasing the range of Citizens Band communications. An exclusive Hy-Gain design—precision tuned and matched for 52 ohm coaxial cable, either RG-58 U or RG-58 U. Conforms to legal limitations—overall height only 20 feet. Built to heavy duty commercial specifications, radiator is 1/2" O.D. to 1/2" O.D. heavy wall heat-treated aluminum tubing. Radiator is 9 feet long 1/2" O.D. heavy wall heat-treated aluminum tubing. Cycloac plastic base insulator and steel bracket assembly accepts all masts up to 1 1/2" diameter. Complete with matching stub and complete instructions for quick and easy assembly.



PROVEN PERFORMANCE!

SEE YOUR HY-GAIN
DISTRIBUTOR
OR WRITE

Hy-gain
antenna products
1135 NO. 27ND • LINCOLN NEBRASKA

WALKIE TALKIE RADIO SENDING SET

YOUR OWN POCKET SIZE RADIO STATION
Talk to any house or car radio without wires or hookups of any kind! Built-in antenna. Self-contained flashlight batteries—Power transistor! Talk to radios in the same building and to cars or between cars up to a mile or more away—depending on local conditions. No license or permit needed! **SEND ONLY \$3.00**—(cash, c.k. mail and pay postpaid only \$9.95 plus C&D postage or send \$12.99 for hosted delivery. Shipped complete ready to operate. Order yours now—Today! Available only from: **WESTERN RADIO, Dept. TEL-11, Kearney, Nebr.**

SAY YOU SAW IT IN POPULAR ELECTRONICS

EXPERIMENTERS • AMATEURS • HOBBYISTS

Want to save real money on your radio parts? Write today for free 32 page BARGAIN BULLETIN illustrating and describing hundreds of values, many priced 50% below list. All are new unless otherwise indicated. No obligation to purchase. Here is a typical value from the current BARGAIN BULLETIN.

BASIC COMPONENTS KIT



Here are all the major components for the construction of a power supply suitable for the operation of receivers to eight tubes, low to medium powered audio amplifiers etc. All components are new. Big RICA power transformer is rated 500 volts center-tapped at 150 ma, 5 volts at 2 amps and 6.3 volts at 3 amps, 115 volts, 50 cycle input of course. Filter choke is rated 12 henry at 150 ma. Two filter condensers are 10 mfd each rated at 50 volts DC. Complete with bleeder resistor, octal rectifier socket and quality hookup wire, you supply the line cord, solder, chassis etc. All material is top quality government surplus representing a real value—well in excess of \$20.00. Shipping weight 1.6 pounds.

JOE PALMER
ELECTRONICS

\$5.95 SEND FOR CATALOG TODAY
P.O. BOX 6188 CCC
SACRAMENTO, CALIFORNIA

How to Talk to Non-Hams

(Continued from page 77)

no trouble taking off three different voices, representative of hams from three different parts of the world. I even inserted sound effects, teletype and fast code—who ever heard a re-broadcast of a short-wave transmission without those dah-dit-dahs?

The big job in taping the playlet was synchronizing the voices so that my live voice would track with what my characters said. I arranged to have a relay in the transmitter actuate the recorder hidden in a closet, and I used my regular receiver speaker to heighten believability.

How does it work? Wonderfully! My public relations are the very best. Guests in the ham shack no longer suppress yawns—they're on tenterhooks waiting for the next thrilling installment.

CONSIDER the demonstration I gave last Sunday to a new neighbor and his family—including two kids. After seating my guests comfortably, I put on the show—with a warm-up period first.

The warm-up feature is actually an audio-visual aid as I fuss over ancient ham gear—a spiral-wound oscillation transformer, rotary spark gap, huge capacitors, and loose couplers. It's junk, but the effect is terrific. My modern transmitter and receiver don't even get a glance—how could anything so small, compact and silent be effective?

With my audience properly primed, I started the main event by giving the globe a twirl, stroking my chin, and then muttering: "Hmmm, suppose we contact this part of the earth."

My neighbor gulped. "You can talk—anywhere?"

My smile was indulgent, as I nodded in the affirmative, my finger stopping the globe at the Arctic Zone. "I haven't talked to the top of the world for some time. I wonder what Professor Schloggenfloober's doing. He's the scientist, you know, who's heading that project to determine what lies at the bottom of the ice cap."

Open-mouthed heads nodded as I grabbed the dead mike to intone: "CQ, CQ, CQ Schloggenfloober expedition!"

After an appropriate time, I switched

on the tape recorder, and from the speaker came what I like to think of as a pretty good imitation of a German scientist. . . "Dis iss Professor Schloggenfloober shpeaking from de Nort Pole. Ve are haffing a heat vave here—sixty degrees below zero."

"Thanks for coming back, Professor. What's new in Santa Claus land?"

This was for the benefit of the children, who leaned forward to catch every word.

Chuckling came through static—I didn't forget to throw in some static on the sound track. "Tell the sshildren that ve got a pet walrus. Ve call him Blubber Boy unt ride him every day. Oh, unt annuder ding, ve found a mastodon at the two-hundred foot level in a vunderful state of preservation. Dose mastodon steaks go good vit canned mushrooms."

"Boy, a pet walrus. Wish I had one," said Junior.

I signed off with the professor, then purposely yawned as if I were bored.

"I'll try to raise something more interesting," I said, noticing through the corner of an eye the amazement on the faces of my guests. "Suppose we point the beam in the direction of the South Pacific Ocean."

Again, after a suitable pause, we heard a voice (mine, of course), this time the voice of an excited British radio operator of a steamship. . . "This is the S. S. *Glugkloop* (I had put my hand in front of my mouth) . . . Can you take a message? Very urgent! Very urgent!"

My neighbor poked his wife in the ribs. "Did you hear that—*very urgent!*"

"Go ahead," I said, reaching for a pencil and pad of paper.

"Here's the message." The voice was almost a scream, as though some awful thing were impending. "Just sighted strange sea animal with huge serpent-like head. Body length estimated one hundred feet with ten loops breaking water. Crossed bow some fifty feet ahead, creating wave estimated six feet high. Position—mid-Pacific near Ogre Island. Relay message to the Society for the Investigation of Unusual Sea Life. The address is . . ." Here the voice rises to a blood-curdling scream, and a sound effect as of wood splintering is heard.

Naturally I make a valiant effort to learn what has happened. But only static



* **FREE**

* **FREE**

* **FREE**

* **FREE**

* **FREE**



Fill in coupon for a FREE One Year Subscription to OLSON'S Fantastic Bargain Packed Catalog — Unheard of LOW, LOW, WHOLESALE PRICES on Brand Name Speakers, Changers, Tubes, Tools, Hi-Fi's, Stereo Amps, Tuners and other Bargains.

10 OLSON STORES
Plus
MAIL ORDER
Visit your local
Olson Stores at . . .

AKRON, OHIO
69 W. State Street

BUFFALO, N.Y.
711 Main Street

CHICAGO, ILL.
4101 N. Milwaukee Ave.

CHICAGO, ILL.
123 N. Western Ave.

CLEVELAND, OHIO
2020 Euclid Ave.

CLEVELAND, OHIO
6813 Pearl Road

COLUMBUS, OHIO
142 N. High Street

INGLEWOOD, CALIF.
4642 W. Century Blvd.

MILWAUKEE, WISC.
423 W. Michigan

PITTSBURGH, PENN.
5918 Penn. Ave.

MAIL TO: ■ ■ ■ ■ ■



OLSON ELECTRONICS
826 S. Forge Street
Akron 8, Ohio

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____



* A thirty-second note...and when talking about musical notes one's thoughts should automatically revolve around this new concept in a stereo record changer! The LESA CD2/21 is compatible with any cartridge, amplifier and speaker. **\$44.50** SLIGHTLY HIGHER WESS

Imported by LESA of America



For FREE brochure and nearest dealers, write: ELECTROPHONO & PARTS CORP., DEPT. E.C., 530 CANAL ST., N.Y., N.Y.

TV PICTURE TUBES	All Aluminized Glass Types	BUY DIRECT AND SAVE
• 12LP4 . . . \$8.95 • 21AL/ATP4 . . . \$16.75		
• 17BP4 . . . \$9.95 • 24DP4 . . . \$24.50 • 27EP4 . . . \$39.95		
ALL TYPES AVAILABLE		FREE... Write for complete Picture Tube list
These tubes are made from reprocessed glass. All materials including electron gun are brand new.		
All Prices with old tube F.O.B. Chicago		
PICTURE TUBE OUTLET • 2922 MILWAUKEE, Chicago 18		

Say You Saw It
In
POPULAR ELECTRONICS

double your income with degree

A college education is a good investment! More rapid advancement, too. *Important firms like Tri-State College graduates* return regularly to interview seniors on campus. Become an Electronics Engineer. Qualify faster here Bachelor of Science Degree in 27 Months in Electrical (Electronics or Power major), Mechanical, Chemical, Aeronautical, Civil Engineering. IN 36 MONTHS B.S. in Business Administration (General Business, Accounting, Motor Transport Management majors). For earnest, capable, mature students. Small classes. More professional class hours. Beautiful campus. Well-equipped labs, modernized buildings, new dorms. Year-round operation. Enter Jan., Mar., June, Sept. Founded 1884. Write J. D. McCarthy, Director Admissions, for Catalog and "Your Career in Engineering and Commerce" Book.

TRI-STATE COLLEGE

36111 College Avenue
Angola, Indiana

comes through. I turn to my white-faced guests, say: "I—I wonder what happened?"

But I know that, in their mind's eye, they know what happened. They see the huge head of a sea serpent landing on the ship's cabin, spike-like fangs ripping the wood asunder. . . .

LATER THAT EVENING, I turned on the last installment, which is a harrowing account of an explorer in a Burma jungle making an urgent request for penicillin.

How do I feel about these hama-dramas? Like a kindly Santa Claus who wouldn't tell the kids for all the money in the world that the beard isn't real. My guests get quite a kick out of these mythical adventures.

So do I. So much so that a strange and somewhat frightening thing is happening. Instead of going on the air and having real QSO's with real hams, I find myself writing and recording new adventures and talking to myself. Maybe those two men in the white coats will get me yet!

-30-

Electronic Analogy Quiz Answers

(Quiz appears on page 59)

CIRCUIT ANALOGY

- Low-pass filter** **F. Tunnel**
A low-pass filter "clips off" signals above a certain frequency; a tunnel "clips off" objects above a certain height.
- Zener diode regulator** **D. Centrifugal governor**
A zener diode "resists" changes in voltage; a governor resists changes in speed.
- Push-pull circuit** **H. Two-man saw**
A signal is alternately "pushed" and "pulled" in a push-pull circuit; a two-man saw is alternately "pushed" and "pulled" by its operators.
- Wave trap** **A. Drain trap**
A wave trap removes unwanted signals; a drain trap "removes" unwanted odors.
- Smoothing filter** **C. Coil spring suspension**
A filter "absorbs" signal "peaks" before they reach the associated circuits; a spring "absorbs" vibration "peaks" before they reach the associated chassis.
- Diode clipper** **E. Hedge clipper**
A diode clipper "clips" off "peaks" in a signal; a hedge clipper "clips" off "peaks" in a hedge.
- High-pass filter** **G. Mountains**
A high-pass filter obstructs the passage of signals below a certain frequency; a mountain obstructs the passage of objects below a certain height.
- A.C. rectifier** **B. Ratchet-and-pawl**
An a.c. rectifier allows current to flow in one direction; a ratchet-and-pawl allows a shaft to turn in one direction.

Short-Wave Report

(Continued from page 88)

There are all sorts of interference that can add to the problem but, by golly, those rare stations WILL and DO come through just when you might least expect them to do so.

- Q:** I hear numerous stations that seem to do nothing but continually announce as being "... for circuit adjustment purposes. ..." What kind of stations are they?
- A:** The large majority of such stations belong to telephone companies in foreign countries. When not engaged in actual overseas telephone conversations, these stations broadcast a form of "running marker" which gives their general location and, at times, the name of the telephone company operating the station. There are a great many of these stations on the air, but although they are on shortwave frequencies, they are not included in the broadcast category. Even at rare



Edward S. Light, WPE2FBT, New York, N. Y., does his DX'ing with a Hallicrafters S-120 receiver aided by a Heath HD-20 100-kc. crystal calibrator.

times when they are used for broadcast relaying, they cannot be declared to be broadcasters in the sense of the word as we know it. Many of them will verify, however.

- Q:** I would like to have my photograph published in your column. How should I go about it?
- A:** Photographs for reproduction in this column should in general be at least 5" x 7" although, at times, good

TRU-VAC

1-yr. guaranteed Radio & TV Tubes

35¢

\$33 PER 100 EA TUBES ANY TUBE NOT LISTED \$1.50 AT \$35 EACH

FREE

UP TO 100
1-YR. GUARANTEED TRU-VAC TUBES

TO QUANTITY BUYERS!

Now quantity buyers get a FREE assortment of individually-boxed, regular stock TRU-VAC tubes with each order.

PLACE YOUR ORDER TODAY! GET UP TO 100 TUBES FREE!

Here's how this FREE offer works!

15 FREE TUBES	With Order of	\$25
25 FREE TUBES	With Order of	\$50
50 FREE TUBES	With Order of	\$100
100 FREE TUBES	With Order of	\$500

Factory Used or Factory Second Tubes! TRU-VAC will replace FREE any tube that becomes defective in use within 1 year from date of purchase! All tubes individually boxed, code dated & branded "TRU-VAC." Partial Listing Only—Thousands More Tubes In Stock!

SPECIAL	48Z7	6SN7GT	30¢	6W4GT	30¢		
0Z4	48Z7	6AL5	6BC5	6CA8	6HG	6SR7	7C4
1A7GT	4CB6	6AM8	6BC8	6C48	6J5	6T4	7C5
1B3GT	5AM8	6AN8	6BD6	6CF6	6J6	6T8	7C6
1H5GT	5AN8	6AQ5	6BE6	6CG7	6J7	6U5	7C7
1R5	5AT8	6AQ6	6BF5	6C88	6K5GT	6U8	7E5
155	5AV8	6AQ7	6BG6G	6CMB	6M7	6V6GT	7E6
1T4	5AZ4	6AR5	6BH6	6CL6	6N7	6W6GT	7E7
1U4	5C68	6AS5	6BJ6	6CM6	6O7	6X4	7F7
1U5	5R4	6AT6	6BK5	6CM7	6S4	6X5GT	7F8
1V2	5T8	6AU4GT	6BK6	6CN7	6S7	6Y8	7G7
1X2	5U4	6AUSGT	6BL7GT	6CQ8	6SA7	6Y8	7G7
2AF4	5U8	6AU6	6BN6	6CR6	6SC7	7A4	XXL7N7
2BNA	5V4C	6AUS	6BQ6GT	6CU5	6SD7GT	7A5	7Q7
2CV5	5V6GT	6AV5GT	6BQ7	6CU5	6S55	7A6	7X6
3AL5	5X8	6AV6	6BR8	6CU6	6S67	7A7	7X6
3BC5	5Y3	6AW8	6BS8	6C6	6S7	7B5	7Y4
3BN6	6B4	6AX4GT	6BY5C	6DE6	6S7	7B5	7Y4
3BZ6	6AC7	6AX5GT	6BZ6	6DGGT	6SK7	7B6	7Z4
3SB6	6AF4	6B8	6BZ7	6DQ6	6SL7	7B7	12A8
354	6AC5	6RA6	6C4	6F6	6SQ7	7B8	12A8
3V4	6AH4GT						12B5
4BTA	6AG6						12B6
4BS8	6AK5						12B6

12A06 12BE6 12S37
12AF6 12BF6 12SN7GT
12A05 12BM7 12SQ7
12AT6 12BQ6 12V6GT
12AT7 12BR7 12W6GT
12AU6 12BY7 12X4
12AU7 12CA5 17AX4
12AV6 12CN5 17D4
12A7 12D4 19AU4GT
12AK4GT 12F6 19BG6
12A7 12K5 19T8
12A27 12K7 25Z6GT
12B4 12L6 35A5
12A6 12Q7 35B5
12B7 12R5 35C5
12B6 12S7 35W4

BRAND NEW 1-YEAR GUARANTEED TV PICTURE TUBES

Below Listed prices do not include shipping. Add Additional \$5.00 Deposit on tube sizes to 20"; on 21" and 21" tubes—\$7.50. Deposit refunded immediately when tube is returned prepaid. Aluminized tubes—\$4.00 extra. Picture tubes shipped only to continental USA and Canada. All tubes F.O.B. Harrison, N. J.

10BP4	7.99	17CP4	16.99	21AMP4	17.99	21KP4	18.39
16BP4	16.08	17P4	15.99	21AVP4	18.79	21VP4	18.39
16P4	11.99	20CP4	15.99	21WP4	17.49	21WP4	17.48
17AVP4	15.48	20HP4	17.89	21EP4	17.29	21YP4	18.39
17BP4	13.49	21ALP4	16.79	21FP4	18.39	24CP4	27.79

ATTENTION QUANTITY USERS: Big Discounts Are Yours . . . Call or Write For Our 1000 Tube "Private Label" Special!

Money cheerfully refunded within five (5) days, if not satisfied!

SHIPPING INSTRUCTIONS: TRU-VAC PAYS YOUR POSTAGE on orders of \$5 or more in USA and territories. Send approximate postage on Canadian and foreign orders. Any order less than \$5 requires 25¢ handling charge. Send 25¢ on C.O.D.'s.

TRU-VAC

Harrison Avenue • Box 107 • Harrison, N. J. HUmboldt 4-9770

VOCATIONAL STUDENTS

It Took Us 2 Years To Design
This TV Kit Especially For You

Videola by Tech-Master

Every Part Custom-Engineered
Exclusively For This Chassis



With this kit you build more than a chassis . . . You build a career in electronics. Tech-Master's VIDEOLA guarantees you the ultimate in training and development. For this is the most up-to-date professional kit available. Every possible improvement in tubes and circuitry is included. Each and every component is absolutely related . . . engineered precisely for this kit . . . designed for flawless assembly and maximum performance. There are no printed circuits. You build everything yourself. Step-by-step instructions with pictorial and schematic diagrams are easy to follow.

FEATURES:

Advanced and improved, super-selective, 12 channel tuner—Full power transformer for safe cold chassis operation—Operates new low-voltage electrostatic focus kinescope (17" to 27" . . . including 19" and 23" sizes) . . . 110 to 114 degree deflection—18 to 20 KV anode voltage—High efficiency circuit—sensitivity of 9uv at 20V peak-to-peak—High power audio output—Three-stage stagger-tuned IF using high-gain bi-filar coils—Keyed automatic gain control—Adjustable noise cancellation circuit—Bright spot eliminator circuit—Ceramic core horizontal output transformer with beam power amplifier—Chassis constructed so that tuning and related controls are on separate panels. Can be placed away from chassis proper to accommodate custom requirements—Sockets, terminal strips and connectors riveted on chassis. 6 x 17 x 1 3/4 chassis size—Weight 21 lbs. MODEL 1561 PRICE \$99.95

COMPLETE CONSTRUCTION MANUAL \$3.75
Cost Of Manual Refunded With Kit Purchase

VIDEOLA by Tech-Master, 75 Front St., Brooklyn 1, N. Y.

ELECTRONICS

Train in the
new shop-labs of
the world famous



COYNE

ELECTRICAL SCHOOL
on a quarter of a million dollars worth
of equipment or learn at home in your
spare time with Coyne's modern tele-
vision training.

Use this coupon to get our FREE BOOK
"GUIDE TO CAREERS"

COYNE ELECTRICAL SCHOOL training training
1501 W. Congress Pkwy. at Coyne at home
Dept. of Electronics 31-W, Chicago 7, Ill.

NAME _____

ADDRESS _____

CITY _____ STATE _____

Unlike most other schools, we do not employ salesmen.

photos of a smaller size will reproduce well. The photo may have either a glossy or a dull finish, but it *must* have good black-and-white contrast. Color photos and transparencies, as



Victor Penan, WPE1CKZ, Fitchburg, Mass., uses a Lafayette HE-10 and a 40-meter dipole antenna. To date, he has 38 countries logged, 11 veries.

well as color negatives, do not reproduce well. Some types of Polaroid shots do not seem to reproduce well either. Make sure that the photo of you and your station is good and sharp, back it up so that it will not bend, and send it to P. O. Box 254, Haddonfield, N. J., together with a list of all the equipment which appears in the photo. We'll do the rest.

Monitor Certificates

Applications for Monitor Certificates have been piling up again, but as a rule they are processed within two weeks of receipt. Julian Sienkiewicz, WPE2FY, reports that most of the delay in handling is due to the fact that correspondence is often tucked in with the applications. If you want to receive your certificate without delay, simply follow the instructions on page 117. And be sure to enclose a stamped, self-addressed envelope with your application. A business-size envelope (about 9 1/2" x 4") is the best type to use—smaller ones require many folds in the certificate.

Short-wave monitors, both newcomers and old-timers alike, are commenting fa-

Always say you saw it in—POPULAR ELECTRONICS



vorably on the new two-color certificates which are now being issued. Old-timers who would like to obtain a new certificate, but also want to keep the old station identification sign, may do so—just print your present call right after your name on the application form, fill in the rest of the data, and send in the form along with a dime.

Incidentally, many Canadians have been enclosing two IRC's with their applications (as is required of all other non-U. S. residents). However, it is permissible (and less costly) to send 15 cents in Canadian coins.

Current Station Reports

Here is a resume of the current station reports. All times shown are Eastern Standard and the 24-hour system is used. At time of compilation all reports are as accurate as possible, but stations may change frequency and/or schedule with little or no advance notice. Please send your reports to P. O. Box 254, Haddonfield, N. J., in time to reach your Short-Wave Editor by the eighth of each month.

Afghanistan—A verification from M. N. Ghayan states that the 1400 Eng. program has been discontinued. (WPE1BM)

Albania—R. Tirana has been noted on 7090 kc. at 1735-1759 with Eng. to Europe; talks, commentaries, very little music. The power is 25 kw. This station is also heard on 9700 kc. daily at 1930-2000 and in Eng. daily at 1730-1800 on 6950 kc. (WPE3CEF, WPE0VB)

Andorra—R. Andorra International, a new station, is said to be operating on 6195 kc. in Spanish, French, Eng., and German. Reports go to Post Box 1, Principality of Andorra. The exact schedule is not known as yet and, to date, no broadcasts have actually been heard. (GM2PE1L)

Angola—A rarely heard station is CR6RK, R. Clube Do Sul Angola, Lobita, on 3603 kc. The schedule is 0500-0700 and 1130-1600 daily, in Portuguese, and the IS is four guitar notes of the tune "Maria de Fonte." (VE7PE2M)

Belgium—Brussels is currently scheduled in Eng. at 1515-1550 daily on 17,840, 15,335, and 15,435 kc. to Africa; at 1900-2000 daily except

Build your own superb Scott STEREO COMPONENTS!



HAVE
FUN...
SAVE
MONEY

Have fun... save money... build the best! Now you can get world-famous Scott stereo components in kit form. Think of it... you can build the fabulous new LT-110 FM Multiplex Stereo Tuner... your choice of two complete stereo amplifiers, or a preamp and separate power amp... all from H. H. Scott!

Write today. Find out about these exciting Scottkits.

Choice of 3 Booklets
FREE



H. H. Scott, Inc. 111 Powdermill Road, Maynard, Mass. Dept. 520-11
Send me the booklets checked below:
 20-page "Guide to Custom Stereo" Complete technical information on kits 16-page booklet explaining FM Stereo
Name _____
Address _____
City _____ Zone _____ State _____
Export: Morhan Exporting Corp., 458 Broadway, N.Y.C.

CB Owners: IT'S WHAT GOES OUT ON THE AIR THAT COUNTS!

Get maximum amplifier output and outstanding performance from your 5-watter by using famous PR CRYSTALS. These high-active crystals get greater distance than ordinary sluggish crystals. Clearer reception too. Put PR Crystals in your set today, and get the STRONGEST SIGNALS POSSIBLE WITHIN POWER LIMITS.

SWITCH TO A BETTER CHANNEL



Be smart... have several sets of PR Crystals... two or three sets at least. Then you can switch channels at will, to avoid jamming. PR CRYSTALS ARE AVAILABLE IN ALL 23 CITIZENS BAND CHANNELS.

Type Z-9R, Calibrated .005%, \$2.95 each. EVERY PR CRYSTAL IS UNCONDITIONALLY GUARANTEED.



Get PR's Now From Your Jobber.

PETERSEN RADIO CO., INC.

2800 West Broadway
Council Bluffs, Iowa

MICRO

ELECTRON TUBE CO.

P. O. Box 55, Park Station
Paterson 3, New Jersey

37

¢
CO.

\$35

PER
HUNDRED
ASSTD

Fabulous Low Prices!
Large Select Stocks!
Dependable, Fast Service!

SEND FOR FREE COMPLETE LIST OF TUBES

0A2	3Q4	6BC5	12A8	25Z5
0Z4		6BC8	12A05	25Z6
1A7GT	4BZ7	6BD6	12A26	26
1B3GT	5AS8	6C4	12A77	35A5
1H4G	5AT8	6C5	12A0U	35B5
1H5GT	5AV8	6C6	12A07	35C5
1L4	5AW4	6CB6	12AV6	35L6GT
1L6	5BK7	6CD6G	12AV7	35W4
1N5GT	5J6		12AX4GT	35Y4
1Q5GT	5T8		12AX7	35Z5GT
	5U4G	7A4/XXL		37
	5U8	7A6	19B6G	39/44
2A3		7A7	19I6	42
2AF4		7A8	19T8	43
3BC5	6A7	7B6	24A	45
3BN6	6A8	7B5	25AV5	50A5
3BZ6	6AB4	7B7	25BQ6	78
3CB6	6AC7	7B8	25DN5	80
3CF6	6AF4	7B9	25L6GT	84/6Z4
3CS6	6B8	7C4	25W4GT	11Z3
3LF4	6BA6			

• All tubes 100%-tested for mutual conductance, life test. • Guar. FREE 1 yr. replacement any tube falling under all operating cond. • Adv. tubes not necessarily new; may be elec. perf. fact. seconds or used—clearly marked.

POSTAGE PAID. Send 25¢ handl. for orders under \$5, 25¢ dep. C.O.D.'s. Send approx. post. on Can. & foreign orders.

Mondays and Fridays on 9705 and 11,850 kc. to Africa and on 11,805 kc. to N.A.; at 1945-2000 (news) on Mondays and Fridays to Africa and N.A. on the same channels. (WPE2FNV, WPE4DKG, WPE8CXT, WPE9AGB)

Bolivia—A recently opened station is *R. Indoamerica*, Potosi, 6202 kc. Commercials are noted around 2100; a time check at 2105; non-stop music to 2125; then local news. Broadcasts are all-Spanish, and the signal may be very weak. (PY2PEIC)

Bulgaria—Sofia has Eng. to N.A. daily at 2000-2030 and 2300-2330 on 9700 kc., and a daily concert at 1835-1900 on 9700 and 11,850 kc. There is a DX program every Friday and a mailbag every Thursday and Sunday. (WPE1DAD, WPE2CYY, WPE2DVO, WPE2FSI, WPE8DIA)

Burma—Rangoon is testing on 17,870 kc. at 1030-1115 with announcements in Eng. and French. (WPE8CTN, GM2PEIL)

Canary Islands—A verification (which took 11 months to arrive) gives a new QTH as *R. Clube Tenerife*, Apartado de Correos 560, Santa Cruz. The listed schedule is 1200-1300 and 1630-1700 (it may run to 1800) daily on 7295 kc. (WPE1BM)

Chile—CE970, *R. La Cooperativa Vitalicia*, Santiago, 9700 kc., was tuned at 2125-2130 with L.A. music; ID and IS at 2130 (IS is "Music and Circumstance"); talks to 2140; classical music until 2155 fade-out. Power is rated at 10 kw. (WPE9CIS)

Cuba—*R. Havana's* schedule as given over the air is 2200-2300 to North, Central and South America on 11,770 kc., 2300-2340 on 11,875 kc. to the same areas. English is followed by French from 2340. Programs

SHORT-WAVE ABBREVIATIONS	
Eng.—English	N.A.—North America
ID—Identification	QSL—Verification
IRC—International	QTH—Address
Reply Coupon	R.—Radio
IS—Interval signal	s/off—Sign-off
kc.—Kilocycles	s/on—Sign-on
kw.—Kilowatts	xmsn—Transmission
L.A.—Latin America	xmtr—Transmitter

consist mostly of news but there is some music. A new channel, dual to 11,700 kc., is 15,305 kc. (it varies from 15,300 to 15,310 kc.) noted at 1330-1415 and 1530-1615 in Spanish; Eng. at 1245-1319; then French to 1330. A European xmsn in Eng., Spanish and French is given daily at 1200-1400 on 21,630 kc. Reports on all channels should go to P. O. Box 7026, Havana, Cuba. (WPE1APS, WPE1BDE, WPE2DVO, WPE2FRM, WPE2FUJ, WPE3EX, WPE3PV, WPE4BC, WPE4BQU, WPE4DED, WPE4DLT, WPE6BLV, WPE6BPN, WPE7KY, WPE8CES, WPE8FV, WPE9AGB, WPE9CXW, WPE0AE, WPE0BOQ, VE1PE2U, DG, DH, JM, and many others).

Dominican Republic—A clandestine station believed to be located in this country has been noted on 13,998 kc. at 1900-1945 and 2200-2245 with the ID *La Voz De La Libertad*, and all-Spanish talks, little music. This station may not operate regularly, for it has been noted

Always say you saw it in—POPULAR ELECTRONICS

NEW! Mark II SUPER BEACON

with "STATIC SHEATH"

THE ULTIMATE IN CITIZEN BAND BASE STATION ANTENNAS

Improves signal/noise up to 20 DB by eliminating precipitation static

The new MARK II Super Beacon with exclusive "Static Sheath"* is the most efficient, most rugged 27 mc. base station antenna made! 19 feet overall, MARK II places the radiated signal directly on the horizon for maximum contact with mobile units. The "Static Sheath"* is a protective, highly attractive gray plastic covering that virtually eliminates noisy precipitation static... increases receiver sensitivity up to 20 DB! Furnished with launcher-matcher cable and coax connector; eliminates ground radials or skirts. 50 ohm impedance. Easily installed with clamp mounting.

*U.S. Process Patent 2,938,210

Your Electronic Parts Distributor has the MARK II in Stock for Immediate Delivery.

MARK MOBILE, Inc.

Dept. PE-11, 5441 West Fargo Ave.
Skokie, Illinois

MMI

as being off the air for several days at a time. (WPE6BPN, KP4PE1G)

Ecuador—HCXZ, *Radiodifusora Nacional del Ecuador*, Apartado Postal 1316, Quito, operates on 4940 kc. with 10 kw. at 0630-0000 (Sundays at 0830-2330) with music, news, feature programs, dramas, and transcriptions from numerous other stations and organizations, all in Spanish. There is an Eng. lesson at 1645 on Mondays, Wednesdays and Saturdays, and French lessons at the same time on Tuesdays and Thursdays. This station is usually heard well. (WPE0ATE)

Falkland Islands—Port Stanley verified by letter in nine months after two reports, a follow-up letter, and some IRC's. The latest schedule reads: 1745-2015 (Saturdays at 1630-2100, Sundays at 1500-2030) on 3958 kc. (PY2PE1C)

Finland—English is broadcast from Pori to Europe on 15,190, 11,805, and 9555 kc. on Mondays and Fridays at 1100-1130 (also at 1600-1630 on Fridays on 6120 kc.). "Around The World" is heard on the first and third Friday of the month, "Musical Mailbag" on alternate Fridays. A repeat program for Europe on 11,805 and 9555 kc., and for N.A. on 15,190 kc. is given at 1530-1600 Mondays and Fridays (May 7 to Sept. 6) and at 0630-0700 Tuesdays and Saturdays (Sept. 7 to May 6). (WPE9DAG)

Germany—R. *Bremen* is tuned on 6190 kc. in German from 0005 to 0020 fade-out. They have a new QSL card. (WPE0JJ)

Ghana—The latest schedule from Accra reads: National Service at 0030-0300 and 1130-1715 (Saturdays to 1800) on 3366 kc., at 0030-0300 and 0700-1715 (Saturdays to 1800) on 4915 kc., at 0700-1715 (Saturdays to 1800) on 7295 kc., and at 0700-1100 on 9640 kc.; Special Service to Ghanaian Forces in the Congo at 0700-1315 on 17,865 and at 1345-1715 (Saturdays to 1800) on 15,210 kc.; External Service at 1000-1500 on 9545 kc., at 1330-1500 on 15,285 kc., and at 1000-1030 on 17,740 kc. The former schedule for 15,285 kc. was 0700-1100 and 1430-1715. (WPE1BM, WPE2FGX, WPE4ADS, WPE4BNA, WPE4CKH, WPE5AG, WPE8AQZ, WPE8CTN, WPE9AGB)

Goa—A recent letter from Director Cap. Jose de Carvalho Figueira at *Emissora de Goa* states that the African beam at 1130-1330 has returned to 17,835 kc. Broadcasts are planned for Europe, Middle and Far East areas. Reports are welcomed. (WPE1BM, WPE2CRX)

Grand Cayman Island—This small Caribbean island has no broadcast outlet but you might try for it via the airline channels. It has been noted working Miami on 6567 kc. between 1923 and 1940 in connection with a regular Friday night flight. (AD)

Indonesia—Two rarely heard stations are YDU, Singaradja, 4840 kc. (300 watts), and YDT, Sao Siu, West Irian Province, 3960 kc. Station YDU is scheduled at 2237-0200 in a home service relay, YDT at 2027-0130 in Indonesian. (VE7PE2M)

Ireland—There are conflicting reports on the Irish Signal Corps xmsns to the Forces in the Congo. Some reports say 1100-1115, 1145-1200, and 1230-1245 on 17,845 kc.; others give

COORDINATE "voice-to-voice" via RCA's New Low-Cost INTERCOM



A complete line of quality Intercoms, wired or wireless—designed for office, factory, or home use, at lowest prices. Suitable for many applications, from simple wireless 2-way talk-listen systems to flexible, multi-unit systems with a variety of talk-listen-monitor options.



Low-Cost 2-WAY RADIO, too!... In your hand

Rugged, dependable, fully transistorized 27-mega cycle 2-way radio, designed for business and personal uses. Small and light, weighs less than one pound. Operates from long-life mercury battery or economical rechargeable battery. Factory installed plug-in modules available to increase transmission range.

in your vehicle



Low-cost dependable means of communication from vehicle-to-vehicle, vehicle-to-office. Can be used at any point having 6 or 12 volt DC or standard 115 volt AC power source. Compact, lightweight. Tuneable receiver permits reception of all 23 channels in 27 MC band.

Write for complete information on any or all of these items.
RCA, Special Products, Dept. B-420, Meadow Lands, Pa.



The Most Trusted Name
in Electronics

RADIO CORPORATION OF AMERICA

the frequency as 17,800 kc. One listener in Norway has heard this station at 1200 on 17,544 kc. with news, sports, and taped greetings. Reports go to Irish Defense, Dublin, Ireland. (WPE1BUF, WPE2FSY, WPE4DJK, LA1PE1R)

Japan—Here is the schedule for *R. Japan* (abbreviations for languages used are *A* for Arabic, *E* for English, *F* for French, *G* for German, *I* for Italian, *J* for Japanese, *R* for Russian, *S_p* for Spanish, *S_w* for Swedish): to N.A. at 1930-2030 on 17,725, 15,135, and 21,520 kc. (*E, J*); to North and Latin America at 2200-0000 on 11,800, 15,135, 17,725, and 21,520 kc. (*E, S_p, J*); to Hawaii at 0030-0200 on 17,725 and 15,235 kc. (*E, J*); to Europe (I) at 0230-0330 on 17,725, 15,135, and 21,610 kc. (*E, J*); to Europe (II) at 1400-1600 on 11,800, 15,135 and 9675 kc. (*R, G, F, E, I, S_w, J*); to Middle East and Northern Africa at 1145-1345 on 11,800, 15,135, and 9525 kc. (*A, E, F, J*); African Service at 1430-1530 on 11,705 and 9525 kc. (*E, F, J*) to Australia, at 0430-0530 on 11,875 and 15,235 kc. to New Zealand (*E*). The General Service (*E, J*) is given at 1000-1030 on 11,815 kc. (and/or 11,780, 15,235 kc.); at 1930-2030, 2100-2130, 2200-2230, 2300-2330, 0000-0030 on 15,115 kc. (and/or 17,795, 21,610 kc.); at 0100-0200, 0300-0330, and 0400-0430 on 11,815 kc. (and/or 15,105, 17,755 kc.); at 0500-0530 on 11,815 kc. (and/or 17,755 kc.); and at 0600-0630, 0700-0730, and 0800-0900 on 11,815 kc. (and/or 11,780, 15,235 kc.). (WPE2EPC, WPE4CMJ, *R. Japan*)

Liberia—ELWA, Monrovia, operates on Tuesdays to N.A., opening at 2000 with drums.

The announced frequency is 11,825 kc., but they are actually on 11,973 kc. The Mid-East service runs to 1430 in Eng. on 15,155 kc., then reopens to North Africa at 1430 on 15,133 kc. Both channels are good. (WPE1BM, WPE2EPC)

Navassa Island—A new anti-Castro station is reported being planned by an American organization. Two xmtrs will be utilized, one 50-kw. unit, the other 20 kw.; frequencies were not given. This island is near Cuba in the Caribbean. (*R. Sweden*)

Peru—OAX5U, *R. Huancavelica*, Casilla No. 86, Huancavelica, is a new station on 4995 kc. (although they announce as being on 4815 kc.) with 2000 watts. On Mondays and Fridays they have music from 2205 to 2258. S/off time varies from 0005 to 0105. All-Spanish programs. (PY2PEIC)

Portugal—The Eng. Service from Lisbon is aired at 0815-0900 on 21,495 kc. (to S.E. Asia); and at 1315-1430 on 17,895 kc. (W. Africa), 15,380 kc. (S. and S.E. Asia), and 6025 kc. (Europe). These XMSNs replace the previously scheduled broadcasts at 1315-1430 on 15,380 kc. to S. and S.E. Asia and on 15,125 kc. to Europe and W. Africa. (WPE1COV, WPE1PJ, WPE2EFF, WPE2FIY, WPE4BUJ, WPE8CIO, WPE8MS, WPE9DN, RC)

Sierra Leone—Freetown has been heard recently on 3316 kc. from 0100 s/on with a religious program. News in Eng. is given at 0155 (local) and at 0200 (London relay). (WPE8MS)

Singapore—*R. Singapore* is presently scheduled as follows: Eng. on 7250 kc. Mon-

GET INTO ELECTRONICS

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar, automation. Basic & advanced courses in theory & laboratory. Assoc. degree in 20 mos. B. S. obtainable. ECPD accredited. G.I. approved. Graduates with major companies. Start Feb., Sept. Dorms, campus. H. S. graduates or equivalent. Catalog.

VALPARAISO TECHNICAL INSTITUTE
Dept. PE VALPARAISO, INDIANA

WALKIE-TALKIE RADIOPHONES

Made in U.S.A.

From \$24.98 for electronic chassis



Send for FREE literature on the new SPRINGFIELD TR-28 kit, or the VAN-GUARD Mark-1 factory assembled kit. (No phone. Fully transistorized, portable. High quality industrial types. C B or amateur bands. 3 year service guarantee.)

VANGUARD ELECTRONIC LABS.
190-48 99th Ave., Hollis 23, N. Y.

Dept. E-11

MOVING?

Make sure you notify our subscription department about any change of address. Be sure to include your postal zone number as well as both old and new addresses. Please allow four weeks' time for processing.

POPULAR ELECTRONICS 434 South Wabash Avenue, Chicago 5, Ill.

GETTING STARTED

THERE'S NO BETTER BEGINNING THAN INSTALLING A MOSLEY BASE STATION ANTENNA! FOR EFFECTIVE PERFORMANCE - FOR RUGGED DURABILITY - CHOOSE MOSLEY... LIKE THE EXPERTS DO!

NEW! A low-cost omnidirectional ground plane with features usually found in much more expensive types. This unity gain base station antenna will provide years of dependable, effective and maintenance-free performance!



Model V-11-UGP
Net Price, \$21.95

IN CITIZENS RADIO ?

FEATURES:

- 100% Rust Proof!
- Heavy-Wall, Heat Treated 6061-T6 Aluminum Elements!
- Entire Antenna Grounded for Positive Lightning Protection and Improved Signal to Noise Ratio!
- "Cyclac" Base Supports Vertical Without Guys in Winds Up To 75 mph!
- Low Angle of Radiation for Greater Range!
- 360 degree Radiation Pattern!

Mosley Electronics, Inc.

4610 NORTH LINDBERGH BOULEVARD - BRIDGETON, MISSOURI

day to Friday, at 1730-2030, 2230-0230, and 0430-1030, Saturdays at 1730-2030 and 2230-1130, Sundays at 1730-1130; Indian Service on 6175 kc. at 1730-1845, 0045-0230, 0400-0630 (Sundays at 1730-1845, 2030-2230, 0400-0630); Malayan Service on 6175 kc. Monday to Thursday at 1845-2030, 2330-0045, and 0700-1130. Fridays at 1845-2030, 0030-0045, 0230-0400, and 0700-1130, Saturdays at 1845-2030, 2130-0045, 0230-0400, and 0700-1130, Sundays at 1845-2030, 2130-0045, 0230-0330, and 0700-1130;

SHORT-WAVE REPORTERS!

Your reports will be read and processed faster if you send them directly to:

Hank Bennett, Short-Wave Editor
POPULAR ELECTRONICS
 P. O. Box 254
 Haddonfield, N. J.

Make sure you include your WPE call letters with your report.

Chinese on 4820 kc. daily at 1730-2030 (Sundays at 1730-1130), 2230-0230 (Saturdays at 2230-1130), and 0330-1100. (WPE8FV)

Spanish Guinea—R. Santa Isabel, 6231 kc., s/on 0129 with a march number and ID in Spanish at 0130. Non-stop music runs to 0155. This station was heard on Monday and Wednesday, not on Thursday. The only ID given was at the beginning of each broadcast. (PY2PE1C)

Switzerland—Recent changes in Berne's schedule include the deletion of 15,315 kc. with Eng. to the Middle East at 1145-1330. French, German, and Italian programs beamed to Africa are now carried on 15,305 kc. at 0045-0145 weekdays (0115-0200 on Sundays) and at 1230-1645 daily. (WPE1AXH, WPE5AWM, VP5PE1D, RR, R. Switzerland)

Thailand—A letter from R. Thailand gives this schedule: to N.A. at 2315-0015 in Eng.; to Thai Forces in Korea, Vietnam, and Cambodia at 0430-0520 in Thai, Cambodian, and Vietnamese; General Overseas Service at 0525-0657 in Eng. (mostly), Malay, and Chinese; and the Home Service relay in Thai at 0800-0900. All broadcasts are on 11,910 kc. All correct reports will be verified and return postage is not required. (WPE2DTO, WPE8CUS)

Turkey—Agricultural Land Produce Radio, Ankara, now operates on 7651 kc. with Turkish and western music and talks. S/off is at 1430. (R. Sweden)

United Arab Republic—Cairo has been observed with two xmsns on 17,835 kc. as follows: at 1100-1332 with Eng. at 1245-1330 and the ID *This is the Voice of Africa from Cairo*, and at 1342-1545 with French at 1345-1445 (news at 1400) and the French ID *Ici la Voix d'Afrique*. (WPE1KO, WPE4BC, WPE5BFU, WPE8CXT, WPE8MS, WPE9DN, WPE0VB, VE2PE3W)

Venezuela—YVQA, *Ondas Portenas*, Puerto la Cruz, 4790 kc., has an Eng. newscast at 2225-2230. (WPE1BM)

Yugoslavia—The latest scheduled broadcasts in English are at 1030-1100 on 15,240,



FREE

TO YOU

and your friends

RADIO SHACK'S

1962 ELECTRONICS

CATALOGS

Plus

Every New Supplement
For Next 12 Months!

Our bigger, better catalogs offer the widest line of electronic parts and equipment in the world! Stereo, Hi-Fi, Ham Radio, Test Equipment, Pre-Recorded Tapes, Tape Recorders, Records, Parts —plus 30 pages of Kits! 340 pages—over 100,000 items! No Money Down credit terms. Money back guarantee of satisfaction.

MAIL THIS COUPON TODAY

RADIO SHACK Corp.
730 Commonwealth Ave., Boston 17, Mass.

Send Radio Shack's famous electronics catalogs for one year—FREE and POSTPAID.

Your Name _____

Your Address _____ 61L7C

City and Zone _____ State _____

For a Friend _____

Address _____ 61L7C1

City and Zone _____ State _____



YOU NEED THIS

FREE GIANT B-A CATALOG



1962

RADIO-TV-ELECTRONICS

BA

SINCE 1937

35th Anniversary

SAVE UP TO 50% ON B-A SELECTED KITS

HI-FI AND STEREO SYSTEMS & COMPONENTS

TOP VALUES IN POWER AND HAND TOOLS

30 PAGES OF BARGAINS NOT IN ANY OTHER CATALOG

BURSTEIN-APPLEBEE CO.

Dept. PE, 1012 McGee St., Kansas City 6, Mo.

Rush me New 1962 B-A Catalog No. 621

Name _____

Address _____

City _____ State _____

SEND FOR IT TODAY

YOU SAVE MONEY!

RUSH US YOUR LIST
OF HI-FI COMPONENTS
FOR A VERY SPECIAL
GROUP QUOTATION

WRITE FOR FREE AUDIO
DISCOUNT CATALOG A-15

New low prices on tape re-
corders, amplifiers, tuners,
loudspeakers, cartridges, etc.

KEY ELECTRONICS COMPANY
120 LIBERTY STREET
NEW YORK 6, N. Y.

NEVER FAIL— ZONE YOUR MAIL

The Post Office has divided 106 cities into postal delivery zones to speed mail delivery. Be sure to include zone number when writing to these cities; be sure to include **your** zone number in **your** return address—after the city, before the state.

B. S. DEGREE IN 36 MOS.

INDUSTRY AND GOVERNMENT NEED 50,000 NEW ENGINEERS EACH YEAR!

Accelerated year-round program puts you in the job-market a whole year early! Also B.S. degree in 27 mos. Aeronautical, Chemical, Civil, Electrical, Mechanical, Electronics, Math, Chemistry, Physics. Quality instruction; widely recognized. Graduates employed from coast to coast. Self-help program. Modest rate. Start Jan., Mar., June, July, Sept. Catalog: 2611 E. Washington Blvd., Fort Wayne 2, Ind.


INDIANA TECHNICAL COLLEGE

11,735, and 9505 kc., at 1330-1400 on 7200 and 6100 kc., and at 1700-1715 on 9505, 7200, and 6100 kc. Reports go to Box 880, Beograd. (WPE1BM, WPE2FGX)

Unidentified—A station has been noted in Azerbaijan at 2240-2330 on 11,695 kc., mostly with talks but with some patches of music. (WPE6BPN) -30-

SHORT-WAVE CONTRIBUTORS

Tom Carten (WPE1APS), Stratford, Conn.
Frank Futchiero (WPE1AXH), Niantic, Conn.
Roger Demers (WPE1BDE), Springfield, Vt.
Jerry Berg (WPE1BM), W. Hartford, Conn.
William Lyons (WPE1BUF), Fitchburg, Mass.
Albert Shumilla (WPE1COV), Dorchester, Mass.
Joseph Cagnina (WPE1DAD), Woburn, Mass.
Edward Bowker (WPE1KO), Keene, N. H.
Dennis Bourassa (WPE1PJ), Bridgeport, Conn.
Joseph Russo (WPE2CRX), Toms River, N. J.
Don Gross (WPE2CYY), Brooklyn, N. Y.
Ronnie Brieger (WPE2DIO), Englewood, N. J.
Dan Predpali, Jr. (WPE2DVO), Merrick, N. Y.
Richard Dubriške (WPE2EFF), Mt. Vernon, N. Y.
Michael Biel (WPE2EPC), Teaneck, N. J.
Dave Listort (WPE2FGX), Elmont, N. Y.
Richard Russoman (WPE2FI), Newark, N. J.
George Bremner (WPE2FNV), Niagara Falls, N. Y.
Jim Yayer (WPE2FRM), Buffalo, N. Y.
Larry La Duc (WPE2FSI), Ticonderoga, N. Y.
Arnold Skemer (WPE2FSY), Flushing, N. Y.
Thomas Dietrich (WPE2FU), West Long Branch, N. J.
Larry Heckman (WPE3CEF), Nazareth, Pa.
Kene Reixach (WPE3EX), Washington, D. C.
Barry Bergman (WPE3PV), Philadelphia, Pa.
Gene Casey (WPE4ADS), Birmingham, Ala.
Grady Ferguson (WPE4BC), Charlotte, N. C.
Leich Lerner (WPE4BNJ), Atlanta, Ga.
Charles Felmlee (WPE4BOU), Lynchburg, Va.
Charles Douglas (WPE4BU), Alma, Ga.
Dwight Fisk (WPE4CKII), Birmingham, Ala.
Ken Burger (WPE4CMJ), Manchester, Tenn.
Steve Colquett (WPE4DED), Opp, Ala.
Donald Smith, Jr. (WPE4DK), Springfield, Va.
Chuck Amory (WPE4DRG), Williamsburg, Va.
Richard Derrickson (WPE4DLT), Alexandria, Va.
William Bing (WPE5AG), New Orleans, La.
W. A. Hutson (WPE5AW), San Antonio, Texas
Ray Bacon (WPE5BFU), U. S. Air Force, England
M. Hinderaker (WPE6BLV), Culver City, Calif.
Shaler Hanisch (WPE6BPV), Pasadena, Calif.
Dick Stewart (WPE7KT), Portland, Oregon
John Rowe (WPE8AQZ), Massillon, Ohio
Pete Mondron (WPE8CLES), Mt. Vernon, Ohio
Fred Cunningham, Jr. (WPE8CIO), Cleveland, Ohio
Richard McNeely (WPE8CTV), Dayton, Ohio
Tim Daum (WPE8CUS), Portsmouth, Ohio
Leroy Gruber (WPE8CVT), Deer Park, Ohio
David L. Kushman (WPE8DIA), Cleveland, Ohio
Richard England (WPE8FV), Columbus, Ohio
Mike Kander (WPE8MS), Dayton, Ohio
Earl Kimmonth (WPE9IGF), Joliet, Ill.
Tom Jepsen (WPE9CIS), Rockford, Ill.
K. Cullet (WPE9CIV), Chicago, Ill.
Bruno Davilas (WPE9DAG), Broadview, Ill.
John Arendt (WPE9DY), Aurora, Ill.
John Beaver, Sr. (WPE9LE), Pueblo, Colo.
Bill Holscher (WPE9ATE), Webster Groves, Mo.
Greg Palfe (WPE9BOO), St. Paul, Minn.
Gerry Dexter (WPE9JI), Waverly, Iowa
George Buchanan (WPE9JB), Webster Groves, Mo.
Gerald Traynor (GM2PEL), Johnstone, Scotland
Hector Davila (KP4PETG), Bayamon, Puerto Rico
Ellmann Ellingsen (LA1PEIK), Hamar, Norway
Giacom Perolo (PT2PEIC), Bauru, Brazil
M. G. Feenry (VEF2U), Halifax, N. S.
Barton Lutz (VEF3IV), Howick, Que.
Richard Laviolette (VE7PEIM), Richmond, B. C.
David Ufitone (VPSPEID), Kingston, Jamaica
Rahib Colaianno (RC), Tampa, Fla.
Arthur Delibert (AD), Lynbrook, N. Y.
David Geeska (DG), Oklahoma City, Okla.
Douglas Herda (DH), Hales Corners, Wis.
Joe Miklas (JM), Pensacola, Fla.
Richard Reynolds (RR), Livingston, N. J.
R. Japan, Tokyo, Japan
R. Naeden, Stockholm, Sweden
R. Switzerland, Berne, Switzerland

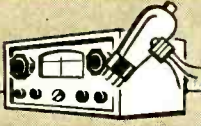

ELECTRONICS MARKET PLACE

RATE: 60¢ per word. Minimum 10 words prepaid. January issue closes November 6th. Send order and remittance to Martin Lincoln, POPULAR ELECTRONICS, 1 Park Ave., New York 16, N. Y.

FOR SALE

GOVERNMENT Sells Surplus: Electronics; Oscilloscopes; Transceivers; Test Equipment; Radar; Sonar; Walkie-Talkies; Boats; Jeeps; Aircrafts; Misc.—Send for "U.S. Depot Directory & Procedures"—\$1.00—Brody, Box 425(PE), Nanuet, New York.

TV Tuners—Rebuilt or Exchanged \$9.95 complete—all types—fast, guaranteed service. Send tuner with all parts to: L.A. Tuner Exchange, 4611 West Jefferson Blvd., Los Angeles 16, California.

GOVERNMENT Surplus Receivers, Transmitters, Snooper-scopes, Parabolic Reflectors, Picture Catalog 10¢. Meshna, Malden 48, Mass.

WPE-SWL-CB-QSL Cards — Samples 10¢ — "Brownie" W3CJ1, 3110A Lehigh, Allentown, Penna.

DIAGRAMS for repairing radios or Television \$2.00. Give make, model. Diagram Service, Box 672-PE, Hartford 1, Conn.

BEFORE You Buy Receiving Tubes or Hi-Fi Components send now for your giant Free Zalytron current catalog—featuring nationally known Zalytron First Quality TV-Radio Tubes, Hi-Fi Stereo Systems, Kits, Parts, etc. All priced to Save You Plenty—Why Pay More? Zalytron Tube Corp., 220 W. 42nd St., NYC.

INFRA-RED!! Snooper-scopes, Optics, Lamps, Parts. World's largest stock Infra-red components. Write for Free Infra-red Catalog. McNeal Electric & Equipment, Dept. EW-9, 4736 Olive, St. Louis 8, Mo.

FREE Confidential Bargain Sheets of Electronic Components—Lowest Prices Anywhere. Knapp-3174-P 8th Ave., S.W., Largo, Florida.

WALKIE-Talkie radiophones from \$24.98. Free literature. Vanguard Labs, 190-48 99 Ave., Hollis 23, N. Y.

GARAGE Door Operators \$59.95. Rugged chain drive automatic units. Highest quality. Free literature. DemSCO, Inc., Sebring 27, Ohio.

16 Tested Transistor plans—25¢, including "Experimenters' Electronics" magazine; 12 issues \$2.50. Laboratories, 1131-L Valota, Redwood City, California.

RADAR King, all frequency police radar detector. Plans (refundable) \$1. Kits \$19.95. Wired units \$29.95. Extra antennas \$4.50 each. S, K, or simultaneous band operation. For kits and wired units, state antenna desired. Wardell Smith, 65 Glenwood Road, Upper Montclair, New Jersey.

PORTABLE Transistor Tape Recorder Complete with Case, Microphone, Tape, Speaker. Guaranteed \$19.60 Postpaid. Eight Transistor Radio, Slide Tuning, PM Speaker, Battery, Leather Case, Earphone. Guaranteed. \$19.60 Postpaid. Eastmann, Box 7, Cedarhurst, N. Y.

CITIZENS Band HE-15 & 15-A, TR800 & 910, RA-395 & 449, Etc. Owners. Disgusted? Relax! Hear only the channel you tune. Dual conversion adapter increases selectivity & sensitivity beyond belief. In easy-to kit form, all parts, schematic, pictorial, complete \$14.95, with tubes \$16.95, or \$5.00 deposit + C.O.D. Order Now! Bainbridge Radio, 2649 Bainbridge Ave., New York 58, New York.

TRANSISTORIZED Test Equipment. New Products. Popular Price Range. PEL-Electronics, Box 555A, Ridgewood, N. J.

CITIZENS Band—Maximum quieting with OZCO "Snoozer." Largest selling add-on squelch still only \$2.00 each, \$3.95 pair postpaid! Guaranteed. OZCO, Canaan, Connecticut.

CBERS—Improve sensitivity of your transceiver. Our RF Preamp fits Heathkit GW-10. Kit \$8.99, wired \$11.99. Holstrom Associates, Box 8640-PE, Sacramento 22, California.

"HOMEBREW Guide" Complete Illustrated Instruction Manual, \$2.00. Supply Catalog Included. Hydrometers \$2.95. CalBrew Supplies, Box 1005-Y, Seaside, California.

RECORDS—Out-of-print hillbilly phonography records. Four catalogues \$1.00. Box 121, Fort Worth, Texas.

CONVERT any car radio to home use. Instructions \$1.00. Custom Design, PO Box 63, Roslyn, Pa.

SPECTACULAR Dancing Lights from your HI-FI or radio. Costs about \$15.00. Up to 50 lamps may be used. Patented design. Easy plans \$4.50. J. Strang, 1478 No. Kings Rd., Los Angeles 69, Calif.

INVESTIGATORS! Do your own sound work. Write for free brochure of latest electronic equipment. WJS Electronics, 1130 N. Highland Ave., Los Angeles 38, Calif.

TELEPHONE Extension in your car. Answer your home telephone by radio from your car. Complete diagrams and instructions \$2.00. C. Carrier Co., 5880 Hollywood Blvd., Hollywood 28, Calif.

EAVESDROP with a pack of cigarettes. Miniature transistorized FM Radio Transmitter. Complete diagrams and instructions \$2.00. C. Carrier Co., 5880 Hollywood Blvd., Hollywood 28, Calif.

BE A Spy. Correspondence course on wire tapping, bugging, telescopic sound pickup, recording techniques, microphotography, and invisible photography. Lessons in surveillance, tailing, and use of equipment. Complete course \$22.50. C. Carrier Co., 5880 Hollywood Blvd., Hollywood 28, Calif.

TV Tape Recorder. Build your own Video Recorder. Complete correspondence course and construction details \$22.50. C. Carrier Co., 5880 Hollywood Blvd., Hollywood 28, Calif.

JUNK Your Distributor and Voltage Regulator. Improve automobile mileage and performance. Construction details for transistorized distributor and voltage regulator \$4.75. No moving parts. DB Enterprises, 8959 Wonderland Ave., Hollywood 46, Calif.

TV Camera. Build for less than \$50. Construction Details \$4.75. DB Enterprises, 8959 Wonderland Ave., Hollywood 46, Calif.

TELEPHONE Voice Switch (LS-500). Actuates automatically and unattended any tape or wire recorder. Pictorial installation instructions included. \$23.75. Post Paid US. WJS Electronics, 1130 N. Highland Ave., Los Angeles 38, Calif.

POLICE Radar Detector. Stop before those radar speed traps. Fool proof, legal system. Complete diagrams and instructions \$2.75. C. Carrier Co., 5880 Hollywood Blvd., Hollywood 28, Calif.

MORSE Code By Sleep Teaching. Guaranteed. 4 taped lessons to 18 WPM: \$12.95 each. Electrosleep, 8959 Wonderland Ave., Hollywood 46, Calif.

INVESTIGATORS, Write for Free Brochure on Latest Subminiature Electronic Listening Devices. Dept. 2A Ace Electronics, 11500 NW 7th Ave., Miami 50, Fla.

FOR Sale: TV Cameras, Teletype, Panadapters, Transmitting Tubes, Transistors, SSB gear. Spera Electronics, 37-10 33 Street, L.I.C., N. Y. Stillwell 6-2199.

CB'S—Want to transmit further? Add #5686 final RF tube to get maximum efficiency 75%. Plus diagrams information on many other ideas. \$1.00 C.B. Improvement Co. 70 Hill St. Bloomfield, N.J.

CB—QSL—SWL cards. Samples 10c. Include your personal picture on cards. No extra Cost. Signal, Adams County, Manchester, Ohio.

"SPECIAL! WPE-SWL-CB-QSL cards, 3 colors, \$2.50 per 100—Free Samples, Garth, Jutland, New Jersey."

FAST Computer. Tells time anywhere. Instructions included. \$1.25P. P. Loeber, 224-T2 Wyatt, Lincoln, Ill.

EXPERIMENTERS! Electronic components and goods at bargain prices. Send for Free list. 10-8 Electronics P.O. Box 61, Batavia, Illinois.

POLICE Radar Detector Plans \$1.00; Kits and Hardware also available from Radet, P.O. Box 7432, Cleveland 30, Ohio.

WANTED

TRIGGER—W9IVJ. We Buy Shortwave Equipment For Cash. 7361 W. North, River Forest, Ill., Phone PR 1-8616. Chicago TU 9-6429.

QUICKSILVER, Platinum, Silver, Gold. Ores Analyzed. Free Circular. Mercury Terminal, Norwood, Massachusetts.

HIGH-FIDELITY



DISGUSTED with "Hi" Hi-Fi Prices? Unusual discounts on your High Fidelity Requirements. Write Key Electronics, 120 Liberty St., New York 6, N. Y. Cloverdale 8-4288.

DON'T Buy Hi-Fi Components, Kits, Tape, Tape Recorders until you get our low, low return mail quotes: "We Guarantee Not To Be Undersold." Wholesale Catalog Free. Easy time payment plan, 10% down—up to 24 mos. to pay. Hi-Fidelity Center, 220 PC-E.23 St., New York 10, N. Y.

PRICES? The Best! Factory-Sealed Hi-Fi Components? Yes! Send for free catalog. Audion, 25P Oxford Road, Massapequa, N. Y.

RECORDERS, Components. Free wholesale catalogue. Carston, 125-P East 88, N. Y. C. 28.

PROMPT Delivery, We Will Not Be Undersold. Amplifiers, Tape Recorders, Tuners, Etc. No Catalogs, Air Mail Quotes. Compare. L. M. Brown Sales Corp. Dept. P, 239 E. 24 St., N.Y. 10, N.Y.

Hi Fi Tuners, Amplifiers, Speakers, Walkie Talkies, Radios, Telescopes, Microscopes, Cameras, Top Quality Imports, Low Prices. Free Catalog, GM Photoelectronics, 623 Gay, Knoxville, Tennessee.

TAPE & RECORDERS

TAPE Recorders, Hi-Fi, components, Sleep Learning Equipment, tapes. Unusual Values. Free Catalog. Dressner, 1523PE, Jericho Turnpike, New Hyde Park, N. Y.

RENT Stereo Tapes—over 2,000 different—all major labels—free catalog. Stereo—Parti, 811-G Centinela Ave., Inglewood 3, California.

AMPEX, Bozak, Citation, Concertone, Crown, Magnecord, Presto, Norelco, Tandberg, Sherwood, Thorans, Scott, Shure, others . . . Trades. Boynton Studio, Dept. PE, 10 Pennsylvania Ave., Tuckahoe, N. Y.

WRITE for stereo component prices, no catalogues. We ship anywhere in the U.S. (We say: If you can beat our prices, You're lying!.) Masterpiece, 1801 Kings Highway, Brooklyn. In business 16 years—Custom made Cabinets for TV, Stereo, Bars, & HiFi.

SELF-Hypnosis may help you many ways. New tape or LP-record teaches you quickly, easily! Free literature. McKinley Company, Box 3038, San Bernardino, California.

REPAIRS and SERVICING

ELECTRONIC Sheet Metal Work. Professional Quality. Send Drawing for Estimate. Spencer, 256 West 15th St., New York 11, N. Y.

ELECTRONIC kits wired and tested. Write for free estimate. Naczas Kit Service, 18 Wolfe Street, Manchester, New Hampshire.

PATENTS


PATENT Searches, \$6.00. For free Information Record, and "Information Inventor's Need, write: Miss Heyward, 1029 Vermont Avenue NW, Washington 5, D. C.

INVENTIONS WANTED

INVENTIONS wanted. Patented; unpatented, Global Marketing Service, 2420-P 77th, Oakland 5, Calif.

INVENTIONS Wanted for immediate promotion! Patented, unpatented. Outright cash; royalties! Casco, Dept. BB, Mills Building, Washington 6, D.C.

INSTRUCTION

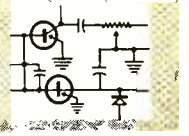

EXPERIMENT with natures electronics. Instructions—Stillwater, Box 337E, Morris Plains, New Jersey.

EARN \$150 Week Mechanical, Electronics Drafting. Send \$2 First Lesson, \$25 Complete Home Study Course. Prior, Inc., Dept. 122, 23-09 169th Street, Whitestone 57, New York.

BEGINNERS. Radio Electronics Explained Simply. Clear. Basic. Plans. 24 Pages. Send \$1. Transspace Laboratory, Box 111, Princeton Junction, New Jersey.

GOVERNMENT SURPLUS

JEEPS \$278, Airplanes \$159, Boats \$7.88, generators \$2.68, typewriters \$8.79, are typical government surplus sale prices. Buy 10,001 items wholesale, direct. Full details, 627 locations, procedure only \$1.00. Surplus, Box 789-C9Z, York, Penna.

GOVERNMENT Surplus, Radios, Jeeps, Walkie Talkies, Boats, Binoculars, Etc. Buy Direct. Send for "Depot Locations & Procedures"—50¢—Delta, Box 2262, Dallas 21, Texas.

STAMPS & COINS

NEW Approval Service—300 world-wide stamps only 25¢ to serious collectors with request for approvals. Special selections for beginners. Martin Stamp Co., Box 12, Gravesend Station, Brooklyn 23, New York.

TERRIFIC Stamp Bargain! Israel—Iceland—San Marino—plus triangle set—Plus Antigua—Borneo—Virgin—Scouts—Congo—Russia—Plus large stamp book—all four offers free—Send 10¢ for mailing cost. Empire Stamp Corporation, Dept. Z2, Toronto, Canada.

200 Different U.S. Stamps \$1.00 Approvals included. Shelron, Box 907-H, New York 8, N. Y.

500 Terrific Beauties \$1.00. Starbright, P. O. Box 999, Chicago 90, Ill.

FREE! 100 different worldwide stamp collection with our colorful inexpensive approvals. Martin, Box 218, Tustin 6, California.

BOOKS

BOOKS—All 15¢, 2000 titles, all subjects, catalog free. Cosma, Clayton, Ga.

PLASTICS

NEW Liquid Casting Plastic, clear, colors. Embed real flowers, butterflies, photos, coins. Send 25¢ for two handbooks "How to Cast Liquid Plastics" and "How to Make Extra Money at Home." Castolite, Dept. L-108, Woodstock, Illinois.

LEATHERCRAFT

FREE "Do-It-Yourself" Leathercraft Catalog. Tandy Leather Company, Box 791-W-41, Fort Worth, Texas.

PHOTOGRAPHY—FILM EQUIPMENT, SERVICES

SCIENCE Bargains—Request Free Giant Catalog "CJ"—144 pages—Astronomical Telescopes, Microscopes, Lenses, Binoculars, Kits, Parts, War surplus bargains. Edmund Scientific Co., Barrington, New Jersey.

EDUCATIONAL OPPORTUNITIES

DETECTIVE Profession. Home Study. Badge, Certificate, Future 4563-AG York. Los Angeles 41. Calif.

ENGINEERING Education for the Space Age. Northrop Institute of Technology is a privately endowed, nonprofit college of engineering offering a complete Bachelor of Science Degree Program and Two-Year accredited technical institute curricula. Students from 50 states, many foreign countries. Outstandingly successful graduates employed in aeronautics, electronics, and space technology. Write today for catalog—no obligation. Northrop Institute of Technology, 1179 West Arbor Vitae Street, Inglewood 1, California.

COMPLETE Your High School at home in spare time with 64-year-old school. Texts furnished. No classes. Diploma. Information booklet free. American School, Dept. X836, Drexel at 58th, Chicago 37, Illinois.

HIGHLY Effective Home-Study review for FCC Commercial Phone Exams. Free Literature. Wallace Cook, Box 10634, Jackson 9, Miss.

BUSINESS OPPORTUNITIES

BUY Direct from factories. Appliances, cameras, watches! Free details! Cam Co., 436 PE Bloomfield Ave., Verona, N. J.

VENDING Machines—No Selling. Operate a route of coin machines and earn amazing profits. 32-page catalog free. Parkway Machine Corporation, Dept. 12, 715 Ensor St., Baltimore 2, Md.

ELECTROPLATING equipment and supplies. All types for home work shops. Free Catalog. HBS Equipment Division, 1624 East First Street, Los Angeles 33, California.

BECOME a telephoneman, experience unnecessary. details free. Occupations Unlimited, 1100 Reeve, Santa Clara, Calif.

MAKE \$25-\$50 Week, clipping newspaper items for publishers. Some clippings worth \$5.00 each. Particulars free. National, 81-DG, Knickerbocker Station, New York.

RAISE Rabbits and Fishworms on \$500 month plan. Free details. White's Rabbitry, Mt. Vernon 50, Ohio.

FREE Book "990 Successful, Little-Known Businesses." Work home! Plymouth—455R, Brooklyn 4, New York.

\$3.00 HOUR—home, sparetime, assembling pump lamps. Easy. Write. OUGOR, 67 E. Caldwell, Arkansas.

\$50.00 in your mailbox every day. Sensational home mailorder business. Cameras \$2.35; watches \$2.60; radios \$1.93. Hundreds of fabulous items. 500% profits. What, where, how to buy and sell. Thousands now doing it. 128 pages loaded with complete information sent immediately. Satisfaction absolutely guaranteed. Send \$2.00 to: Impex-R, 714 Howard Avenue, New Orleans 12, Louisiana.

SECOND Income From Oil Can End Your Toil! Free Book And Oilfield Maps! National Petroleum, Panamerican Bldg.—PE, Miami 32, Florida.

OIL "Many Fortunes Began With an Oil Lease." How to get into the Oil Business. Send for free details. Petroleum Investors Management Corp., P. O. Box #7344, Dallas 9, Texas.

EMPLOYMENT INFORMATION

HIGH Paying Jobs in Foreign Lands! Send \$2.00 for complete scoop! Foreign Opportunities, Box 172, Columbus 16, Ohio.

EARN Extra money selling advertising book matches. Free samples furnished. Matchcorp, Dept. MD 111, Chicago 32, Illinois.

SPACE Lab—Proposed in Houston, Classified's \$1.25. R. Parks, Box 493, Stafford, Texas.

MISCELLANEOUS

WRITERS!—Free Sample copy of Pink Sheets listing top-notch USA markets for short stories, articles, books and plays available to you upon request. Write today! Literary Agent Mead, 915 Broadway, New York 10, N. Y.

FREE Catalog and Samples, quality line of printing. Low prices. Bennetts, Strong, Ark.

POPULAR ELECTRONICS

Advertisers' Index November 1961

ADVERTISER	PAGE
Airex Radio Corporation	90
Allied Radio	118, 119, 120, 121
American Basic Science Club, Inc.	1
American Technical Writing Schools, Inc.	32
Audio Devices Inc.	29
Banner Electronics, Inc.	98
Browning Laboratories, Inc.	33
Bud Radio, Inc.	106
Burgess Battery Company	4
Burstein-Applebee Co.	131
Cabinart Acoustical Eng. Corp.	111
Cadre Industries Corp.	2nd COVER
Capitol Radio Engineering Institute, The	11
Central Technical Institute	23
Cleveland Institute of Electronics	13
Commissioned Electronics, Inc.	98
Conar Instruments	90
Coyne Electrical School	97, 126
Cushcraft	98
DeVry Technical Institute	5
E.C.I. Electronics Communications, Inc.	31
EICO	40
Electro-Voice, Inc.	26, 27
Electronic Market	94
Electronics Book Service	37, 39
Electrophono & Parts Corp.	124
Electrosolids Corp.	100
Gonset	3
Granco	94
Grantham School of Electronics	7
Grove Electronic Supply Company	96
Hallicrafters	22, 115
Heath Company	92, 93
Holt, Rinehart & Winston, Inc.	99
Hy-Gain Antenna Products	122
Indiana Technical College	132
Johnson Company, E. F.	106, 117
Key Electronics Company	132
Kuhn Electronics, Inc.	38
Lafayette Radio	21, 104, 105

Lektron	103
Mark Mobile, Inc.	128
Micro Electron Tube Co.	128
Milwaukee School of Engineering	95
Mosley Electronics, Inc.	130
Moss Electronic, Inc.	3rd, 4th COVER
National Radio Institute	38, 101, 102
National Technical Schools	35, 36
Olson Electronics	123
Palmer Electronics, Joe	122
Petersen Radio Co., Inc.	127
Picture Tube Outlet	124
Polytronics Lab	28
Precision Apparatus Company, Inc.	19
Progressive "Edu-Kits" Inc.	89
RCA Institutes, Inc.	17, 18
RTS Electronics Division	25
Rad-Tel Tube Co.	136
Radio Corporation of America	129
Radio Shack Corp.	87, 108, 110, 113, 131
Radiocom	96
Reeves Soundcraft Corp.	14
Rek-O-Kut Co., Inc.	16
Robin Radio Co.	114
Sams Co., Inc., Howard W.	34
Saxitone Tape Sales	98
Scientific Development Corp.	15
Scott, Inc., H. H.	127
Sherwood Electronic Laboratories, Inc.	112
Sleep-Learning Research Ass'n	14
Sonar Radio Corporation	98
Superscope, Inc.	20
Tech-Master	126
Transvision Electronics, Inc.	107
Tri-State College	124
Tru-Vac	125
Turner Microphone Company, The	91
United Scientific Laboratories, Inc.	100
University Loudspeakers, Inc.	24
Utah Electronics Corp.	10
Valparaiso Technical Institute	130
Vanguard Electronics Labs	130
Vocaline Company of America, Inc.	9
Western Radio	122
Wiley & Sons, Inc., John	108
World Wide Co.	112

RAD-TEL Tube Values Defy Comparison!

RAD-TEL'S
Quality
BRAND NEW
TUBES!

1 YEAR GUARANTEE

UP TO
75% OFF



Mr. Serviceman: Do yourself a favor! The COMPARESON tells the story of RAD-TEL'S "MONEY-SAVING" SALE OF VALUES. Dependable ONE-DAY SERVICE. RAD-TEL SELLS ONLY NEW TUBES.

EACH TUBE INDIVIDUALLY & ATTRACTIVELY BOXED

Qty.	Type	Price	Qty.	Type	Price	Qty.	Type	Price
—	6AU7	.61	—	6I6	.67	—	12D04	.69
—	6AU8	.87	—	6I7	.62	—	12D05	.59
—	6AV6	.41	—	6K6	.63	—	12D08	.75
—	6AW8	.90	—	6L6	1.06	—	12D18	.85
—	6AX4	.66	—	6N7	.98	—	12D07	.67
—	6AX5	.74	—	6S4	.51	—	12D06	1.04
—	6AX7	.64	—	6S8	.76	—	12D57	.79
—	6AX8	.92	—	6SA7GT	.76	—	12D15	.76
—	6BA6	.50	—	6SG7GT	.41	—	12D17	.79
—	6BA7	.84	—	6SH7GT	.49	—	12D18	.79
—	6BA8	.88	—	6S17	.88	—	12D08	.89
—	6BC5	.61	—	6SK7GT	.74	—	12D26	.56
—	6BC7	.94	—	6SL7GT	.80	—	12E66	.54
—	6BC8	.97	—	6SN7GT	.65	—	12E66	.56
—	6BD5	1.25	—	6S87	.73	—	12E16	.50
—	6BD6	.57	—	6T4	.99	—	12EM6	.79
—	6BE6	.55	—	6T8	.85	—	12EN6	.78

—	6BF5	.90	—	6U8	.83	—	12EZ6	.53
—	6BF6	.44	—	6V6GT	.54	—	12F8	.66
—	6BG6	1.66	—	6V8	.86	—	12FA6	.79
—	6BH6	.65	—	6W4	.60	—	12FM6	.43
—	6BH8	.87	—	6WG	.71	—	12FR8	.91
—	6BJ6	.62	—	6X4	.39	—	12FX8	.85
—	6BJ7	.79	—	6X5GT	.53	—	12G6C	1.06
—	6BK7	.85	—	6X8	.80	—	12I8	.84
—	6BL7	1.00	—	6Y6	.65	—	12I6	.65
—	6BN4	.57	—	7A8	.68	—	12L6	.58
—	6BN6	.74	—	7AU7	.61	—	12S8	.62
—	6BQ5	.65	—	7B6	.69	—	12SA7	.92
—	6BQ6	1.05	—	7EY6	.73	—	12SF5	.50
—	6BQ7	1.00	—	7F8	.90	—	12SF7	.69
—	6BR8	.78	—	7Y4	.69	—	12SH7	.49
—	6BS8	.90	—	8A4	.83	—	12SJ7	.67
—	6BU8	.70	—	8AW8	.93	—	12SK7	.74

—	6BX7	1.02	—	8B8	.90	—	12SL7	.80
—	6BY5	1.15	—	8B8B	.75	—	12SN7	.87
—	6BY6	.54	—	8B05	.60	—	12SQ7	.78
—	6BY8	.66	—	8C67	.62	—	12T17	.62
—	6BZ6	.55	—	8CM7	.68	—	12V6	.53
—	6BZ7	1.01	—	8CN7	.97	—	12W6	.69
—	6BZ8	1.09	—	8C57	.74	—	12X4	.38
—	6C4	.43	—	8CX8	.93	—	17AX4	.67
—	6C8	.90	—	8E88	.94	—	17B06	1.09
—	6CB6	.55	—	8S7	.66	—	17D4	.69
—	6CD6	1.42	—	9C18	.79	—	17D06	1.06
—	6CE5	.57	—	11CV7	.75	—	17L6	.58
—	6CF6	.64	—	12A4	.60	—	17W6	.70
—	6CG7	.61	—	12AB5	.55	—	18FW6	.49
—	6CG8	.77	—	12AC6	.49	—	18FX6	.53
—	6CK4	.70	—	12AD6	.57	—	18FY6	.50
—	6CL8	.79	—	12AE6	.43	—	19AU4	.83

—	6CM6	.64	—	12AE7	.94	—	198G6	1.39
—	6CM7	.66	—	12AF3	.73	—	19T8	.80
—	6CN8	.90	—	12AF6	.49	—	19V8	.79
—	6CN7	.65	—	12A16	.46	—	21E6	1.49
—	6CR8	.84	—	12A15	.45	—	25AV5	.83
—	6CQ6	.51	—	12A18	.95	—	25AX4	.70
—	6CS6	.57	—	12A05	.60	—	25BK5	.91
—	6CS7	.69	—	12A76	.43	—	25B06	1.11
—	6CU5	.58	—	12A77	.76	—	25C5	.53
—	6CU6	1.08	—	12A06	.51	—	25CA5	.59
—	6CY5	.70	—	12A70	.60	—	25CD6	1.44
—	6CY7	.71	—	12A67	.41	—	25CU6	1.11
—	6DA4	.68	—	12A77	.75	—	25DN6	1.42
—	6DB5	.69	—	12AK4	.67	—	25EH5	.55
—	6DB6	.51	—	12AK7	.63	—	25L6	.57
—	6DE5	.58	—	12A17	1.44	—	25W4	.68
—	6DC6	.59	—	12A27	.86	—	25Z6	.66
—	6DK6	.59	—	12B4	.63	—	32E75	.55

—	6DN6	1.55	—	12BA6	.50	—	32L7	.90
—	6DQ6	1.10	—	12BA7	.84	—	35B5	.60
—	6DT6	.53	—	12BD6	.50	—	35C5	.51
—	6D78	.79	—	12BE5	.53	—	35L6	.57
—	6EA8	.79	—	12BF6	.44	—	35W4	.42
—	6EB5	.72	—	12BH7	.77	—	35Z5	.60
—	6EB8	.94	—	12B85	1.00	—	36AM3	.36
—	6EM5	.76	—	12BL6	.56	—	50B5	.60
—	6EM7	.82	—	12BQ6	1.06	—	50C5	.53
—	6EU8	.79	—	12B77	.77	—	50EH5	.55
—	6EW6	.57	—	12BZ7	.75	—	50L6	.61
—	6EY6	.75	—	12C5	.56	—	57E3	1.00
—	6F5GT	.39	—	12CN5	.56	—	70L7	.97
—	6F6	.69	—	12CR6	.54	—	70Z5	.69
—	6GK6	.79	—	12C05	.58	—	84/624	.46
—	6GN8	.94	—	12C06	1.06	—	80T	.70
—	6H6	.58	—	12CX6	.54	—	117Z3	.61
—	6J5GT	.51	—			—		

• NOT AFFILIATED WITH ANY OTHER MAIL ORDER TUBE COMPANY •



SEND FOR FREE TROUBLE SHOOTER
GUIDE AND NEW TUBE & PARTS CATALOG

RAD-TEL TUBE CO.

DEPT. PE-1161 55 CHAMBERS STREET, NEWARK 5, N. J.

TERMS: 25% deposit must accompany all orders, balance COD. Orders under \$5: add \$1 handling charge plus postage. Orders over \$5: plus postage. Approx. 8 tubes per 1 lb. Subject to prior sale. Prices subject to change. No CDO's outside continental USA.

SHIPPED ON APPROVAL NO MONEY WITH ORDER — NO C. O. D.



Model TW-11—Tube Tester
Total Price \$47.50
Terms: \$11.50 after 10 day trial, then \$6.00 monthly for 6 months if satisfactory. Otherwise return, no explanation necessary.

Superior's
New Model
TW-11

STANDARD PROFESSIONAL TUBE TESTER

• Tests all tubes, including 4, 5, 6, 7, Octal, Lockin, Hearing Aid, Thyatron, Miniatures, Sub-miniatures, Novals, Subminars, Proximity Fuse Types, etc.

• Uses the new self-cleaning Lever Action Switches for individual element testing. All elements are numbered according to pin-number in the RMA base numbering system. Model TW-11 does not use combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket.

• Free-moving built-in roll chart provides complete data for all tubes. Printed in large easy-to-read type.

NOISE TEST: Phono-jack on front panel for plugging in either phones or external amplifier detects microphonic tubes or noise due to faulty elements and loose internal connections.

EXTRAORDINARY FEATURE
SEPARATE SCALE FOR LOW-CURRENT TUBES Previously, on emission-type tube testers, it has been standard practice to use one scale for all tubes. As a result, the calibration for low-current types has been restricted to a small portion of the scale. The extra scale used here greatly simplifies testing of low-current types.

Housed in handsome, Saddle-Stitched Texon case. Only **\$47.50**



Model 77—VACUUM TUBE VOLT-METER. Total Price. . . \$42.50
Terms: \$12.50 after 10 day trial, then \$6.00 monthly for 5 months if satisfactory. Otherwise return, no explanation necessary.

Superior's
New
Model 77

VACUUM TUBE VOLTMETER WITH NEW 6" FULL-VIEW METER

Compare it to any peak-to-peak V. T. V. M. made by any other manufacturer at any price!

• Extra large meter scale enables us to print all calibrations in large easy-to-read type.
• Employs a 12AU7 as D. C. amplifier and two 9006's as peak-to-peak voltage rectifiers to assure maximum stability. • Meter is virtually burn-out proof. The sensitive 400

AS A DC VOLTMETER: The Model 77 is indispensable in Hi-Fi Amplifier servicing and a must for Black and White and color TV Receiver servicing where circuit loading cannot be tolerated.

AS AN ELECTRONIC OHMMETER: Because of its wide range of measurement leaky capacitors show up glaringly. Because of its sensitivity and low loading. Intermittents are easily found, isolated and repaired.

AS AN AC VOLTMETER: Measures RMS values if sine wave, and peak-to-peak value if complex wave. Pedestal voltages that determine the "black" level in TV receivers are easily read.

micro-ampere meter is isolated from the measuring circuit by a balanced push-pull amplifier. • Uses selected 1% zero temperature coefficient resistors as multipliers. This assures unchanging accurate readings on all ranges.

SPECIFICATIONS

• **DC VOLTS**—0 to 3/15/75/150/300/750/1,500 volts at 11 megohms input resistance.
• **AC VOLTS (RMS)**—0 to 3/15/75/150/300/750/1,500 volts. • **AC VOLTS (Peak to Peak)**—0 to 8/40/200/400/800/2,000 volts.
• **ELECTRONIC OHMMETER**—0 to 1,000 ohms/10,000 ohms/100,000 ohms/1 megohm/10 megohms/100 megohms/1,000 megohms. • **DECIBELS:** -10 db to +18 db, +10 db to +38 db, +30 db to +58 db. All based on 0 db = 0.06 watts (6 mw) into a 500 ohm line (1.73v). • **ZERO CENTER METER**—For discriminator alignment with full scale range of 0 to 1.5/7.5/37.5/150/375/750 volts at 11 megohms input resistance.

Comes complete with operating instructions, probe leads, and streamlined carrying case. Operates on 110-120 volt 60 cycle. Only **\$42.50**

We invite you to try before you buy any of the models described on this page and the following page. If after a 10 day trial you are completely satisfied and decide to keep the Tester, you need send us only the down payment and agree to pay the balance due at the monthly indicated rate.

NO INTEREST OR FINANCE CHARGES ADDED!

If not completely satisfied, you are privileged to return the Tester to us, cancelling any further obligation.

SEE OTHER SIDE

CUT OUT AND MAIL TODAY! ▶

MOSS ELECTRONIC, INC.
Dept. D-907 3849 Tenth Ave., New York 34, N. Y.

Please send me the units checked on approval. If completely satisfied I will pay on the terms specified with no interest or finance charges added. Otherwise, I will return after a 10 day trial positively cancelling all further obligation.

Model 77 Total Price \$42.50
\$12.50 within 10 days. Balance
\$6.00 monthly for 5 months.

Model TV-50A... Total Price \$47.50
\$11.50 within 10 days. Balance
\$6.00 monthly for 6 months.

Model TW-11... Total Price \$47.50
\$11.50 within 10 days. Balance \$6.00
monthly for 6 months.

Model 70... Total Price \$15.85
\$3.85 within 10 days. Balance
\$4.00 monthly for 3 months.

Name

Address


City Zone.....State.....

All prices net. F.O.B. N. Y. C.

SHIPPED ON APPROVAL NO MONEY WITH ORDER — NO C. O. D.

Superior's New Model 70 UTILITY TESTER®

FOR REPAIRING ALL ELECTRICAL APPLIANCES and AUTOMOBILE CIRCUITS

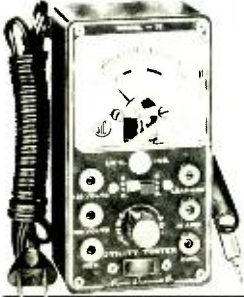

Model 70—UTILITY TESTER
Total Price... \$15.85—
Terms: \$3.85 after 10 day trial,
then \$4.00 monthly for 3 months,
if satisfactory. Otherwise return, no
explanation necessary.

As an electrical trouble shooter the Model 70:

- Will test Toasters, Irons, Broilers, Heating Pads, Clocks, Fans, Vacuum Cleaners, Refrigerators, Lamps, Fluorescents, Switches, Thermostats, etc.
- Measures A.C. and D.C. Voltages, A.C. and D.C. Current, Resistances, Leakages, etc.
- Will measure current consumption while the appliance under test is in operation.
- Incorporates a sensitive direct-reading resistance range which will measure all resistances commonly used in electrical appliances, motors, etc.
- Leakage detecting circuit will indicate continuity from zero ohms to 5 megohms (5,000,000 ohms).

As an Automotive Tester the Model 70 will test:

- Both 6 Volt and 12 Volt Storage Batteries • Generators • Starters • Distributors • Ignition Coils • Regulators • Relays • Circuit Breakers • Cigarette Lighters • Stop Lights • Condensers
- Directional Signal Systems • All Lamps and Bulbs • Fuses • Heating Systems • Horns • Also will locate poor grounds, breaks in wiring, poor connections, etc.

INCLUDED FREE This 64-page book—practically a condensed course in electricity. Learn by doing.



Just read the following partial list of contents: What is electricity? • Simplified version of Ohms Law • What is wattage? • Simplified wattage charts • How to measure voltage, current, resistance and leakage • How to test all electrical appliances and motors using a simplified trouble-shooting technique. • How to trace trouble in the electrical circuits and parts in automobiles and trucks.

Model 70 comes complete with 64 page book and test leads

\$15.85
Only

Superior's New Model TV-50A **GENOMETER**

7 Signal Generators in One!

- ✓ R.F. Signal Generator for A.M.
- ✓ R.F. Signal Generator for F.M.
- ✓ Audio Frequency Generator
- ✓ Marker Generator
- ✓ Bar Generator
- ✓ Color Dot Pattern Generator
- ✓ Cross Hatch Generator

This Versatile All-Inclusive GENERATOR Provides ALL the Outputs for Servicing:

- A.M. RADIO • F.M. RADIO • AMPLIFIERS • BLACK AND WHITE TV • COLOR TV

R. F. SIGNAL GENERATOR: 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 180 Megacycles on powerful harmonics.

VARIABLE AUDIO FREQUENCY GENERATOR: Provides a variable 300 cycle to 20,000 cycle peaked wave audio signal.

MARKER GENERATOR: The following markers are provided: 189 Kc., 262.5 Kc., 456 Kc., 600 Kc., 1000 Kc., 1400 Kc., 1600 Kc., 2000 Kc., 2500 Kc., 3579 Kc., 4.5 Mc., 5 Mc., 10.7 Mc., (3579 Kc. is the color burst frequency)

BAR GENERATOR: Pattern consists of 4 to 16 horizontal bars or 7 to 20 vertical bars.

DOT PATTERN GENERATOR (FOR COLOR TV): The Dot Pattern projected on any color TV Receiver tube by the Model TV-50A will enable you to adjust for proper color convergence.

CROSS HATCH GENERATOR: The pattern consists of non-shifting horizontal and vertical lines interlaced to provide a stable cross-hatch effect.

Complete with shielded leads **\$47.50** Net



Model TV50-A—Genometer
Total Price \$47.50
Terms: \$11.50 after 10 day trial,
then \$6.00 monthly for 6 months
if satisfactory. Otherwise return,
no explanation necessary.

TRY FOR 10 DAYS BEFORE you buy! THEN if satisfactory

pay in easy, interest free, monthly payments. See coupon inside.

We invite you to try before you buy any of the models described on this and the preceding page. If after a 10 day trial you are completely satisfied and decide to keep the Tester, you need send us only the down payment and agree to pay the balance due at the monthly indicated rate. (See other side for time payment schedule details.)

NO INTEREST OR FINANCE CHARGES ADDED!

If not completely satisfied, you are privileged to return the Tester to us, cancelling any further obligation.

SEE OTHER SIDE

CUT OUT AND MAIL TODAY!

FIRST CLASS

Permit No. 61430

New York, N. Y.

BUSINESS REPLY CARD

No Postage Stamp Necessary if Mailed in the U. S.

VIA AIR MAIL

POSTAGE WILL BE PAID BY —

MOSS ELECTRONIC, INC.

3849 TENTH AVENUE

NEW YORK 34, N. Y.