

FINDING A JOB IN ELECTRONICS

POPULAR ELECTRONICS

OCTOBER
1966

50
CENTS

How To Use
Integrated Circuits

Build Intercom
Burglar Alarm

Impossible Circuit
Fools Everyone

Build Strain-Gauge
Hi-Fi System

Those Darn Things
Called Decibels

Build \$6.00
IC Amplifier

THE TIME IS
14 HOURS
26 MINUTES
Beep!



WV - CHU


TIME - SIGNAL RECEIVER

E0368 642676J0H2982PG0BK
G JOHNSON
2982 POPLAR ST
ERIE PA 16908

BUILD
TIME-SIGNAL-ONLY
POCKET RECEIVER

AVAILABLE UNDER NEW GI BILL

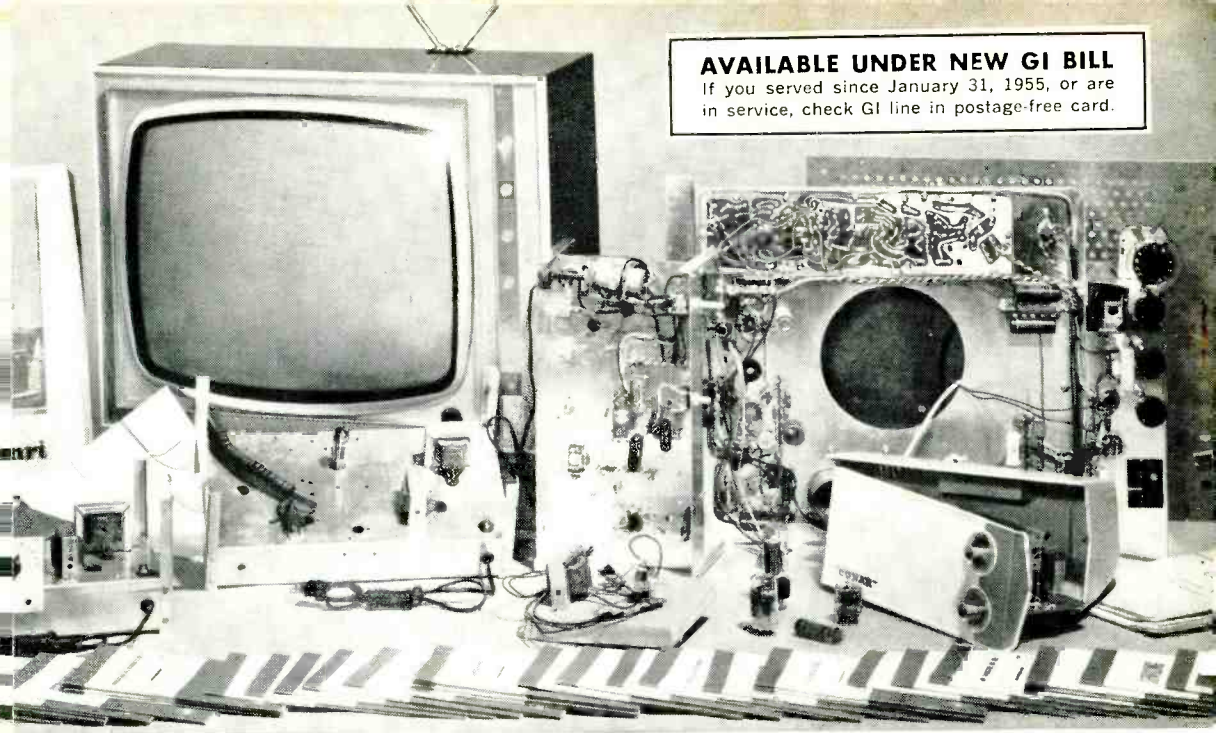If you served since January 31, 1955, or are in service, check GI line in postage-free card.



COMPARE. You'll find—as have tens of thousands of NRI graduates—that NRI training gives you more value. From the delivery of your first lessons in the remarkable NRI Achievement Kit we send you on enrolling, to “bite size” easily-read texts carefully programmed with custom-designed training kits . . . NRI can't be beat. Text for text, kit for kit, dollar for dollar —your best home-study buy is unquestionably NRI. (And NRI training costs you less than one semester's tuition at most colleges.)

Get a Faster Start with NRI's New, Exciting Achievement Kit

The day we receive your enrollment application we mail out your new NRI Achievement Kit. This attractive starter kit is an outstanding, logical way to help you get an easier, faster start in the training of your choice. It is the first of a number of special training aids developed in the NRI laboratories to make your adventure into Electronics exciting, meaningful. What's

in it? Your first group of lesson texts; a rich, vinyl desk folder to hold your material; the industry's most complete Radio-TV Electronics Dictionary; valuable reference texts; lesson answer sheets; envelopes; pencils; pen; engineer's ruler; even postage. No other school has anything like it.

Learning Becomes an Absorbing Adventure with NRI Training Kits

Electronics comes alive with NRI training kits. What better way to learn than by *doing*? NRI pioneered and perfected the “home lab” technique of training at home in spare time. You get your hands on actual parts to build, experiment, explore, discover. NRI invites comparison with training equipment offered by any other school. Begin *now* this exciting program of practical learning. Whatever your need . . . what ever your education . . . there's an NRI instruction plan for you, at low tuition rates. Get all the facts. Fill in and mail the postage-free card today. NATIONAL RADIO INSTITUTE, Electronics Division, Washington, D. C. 20016

Join the thousands who gained success with NRI



“I average \$150.-\$170. a month in spare time fixing radio and TV sets, and plan to start my own full-time business. I wish it were possible to tell every man of the wonderful opportunities.” WILLIAM L. KING, Yoakum, Texas.



“I am a Frequency Coordinator for the 11th Naval District. The course I completed was priceless in my work. I was a blue collar worker, now I am a white collar worker.” JOHN J. JENKINS, San Diego, Calif.

“Many thanks to NRI for the Electronics training I received. I hold a First Class FCC License and am employed as a studio and master control engineer/technician with KXJB-TV.” RONALD L. WOOD, Fargo, N. D.



“I am a Senior Engineering Aid at Litton Systems, in charge of checkout of magnetic recording devices for our computers. Without the help of NRI I would still be working in a factory.” DAVID F. CONRAD, Reseda, Calif.



Pick your field of ELECTRONICS

Now NRI offers you 12 ways to train at home in spare time

Any training—if it is to be worth your time and money—must give you the knowledge and the skills you seek, the knowledge and the skills employers want. That's why NRI puts emphasis on providing a *choice* of carefully developed training plans in Electronics. NRI now offers you 12 ways to train at home . . . 12 ways to meet the challenge of today's job market by training with NRI for a career in Electronics, for part-time

earnings, or simply for developing a new, fascinating hobby. The proof of the quality of NRI training plans is in its record of tens of thousands of successful graduates and the reputation NRI holds throughout the Electronics industry. Move ahead now in this exciting, growing field. Select the training plans of most interest to you and mail the postage-free card. NATIONAL RADIO INSTITUTE, Electronics Division, Washington, D. C. 20016.



TELEVISION-RADIO SERVICING

Training from fundamentals to home entertainment equipment. Learn to fix radios, hi-fi and stereo sets, black-and-white and color TV, etc. A profitable field full or part-time.



INDUSTRIAL-MILITARY ELECTRONICS

From basic principles to computers. Comprehensive training teaches fundamentals, then takes you into such modern-day miracles as servos, telemetry, multi-plexing, phase circuitry, others.



COMPLETE COMMUNICATIONS*

Teaches and provides actual practice in operation, service, maintenance of AM, FM, and TV broadcasting stations. Also covers marine, aviation, mobile radio, facsimile, microwave, radar.



FCC LICENSE*

Prepares you for First Class FCC Radiotelephone License exams. You begin with fundamentals, advance to required subjects covering equipment, procedures.



MATH FOR ELECTRONICS

A brief course for engineers and technicians who need a quick review of essential math used in industry, communications, government. Basic arithmetic review, short-cut formulas, modern digital number systems, much more.



BASIC ELECTRONICS

A concise course in Electronic terminology and components. A wealth of useful information to help you better understand the field. For anyone who wants a basic understanding of Radio-TV Electronics.



ELECTRONICS FOR AUTOMATION

Not for beginners, but for men with some knowledge of Electronics who want an understanding of process control, ultrasonics, telemetering and remote control, electromechanical measurements, other subjects.



AVIATION COMMUNICATIONS*

Prepares you to install, maintain, service direction finders, ranges, markers, Loran, Shoran, Radar, landing systems. Earn your FCC License with Radar Endorsement.



MARINE COMMUNICATIONS*

Covers transmitters, direction finders, depth indicators. Radar, Sonar, other equipment on commercial ships, pleasure boats. Prepares for FCC License with Radar Endorsement.



MOBILE COMMUNICATIONS*

Learn to install and maintain mobile transmitters and receivers used by police and fire departments, public utilities, construction firms, taxis, etc. Prepares for FCC License.



ELECTRICAL APPLIANCE REPAIR

Prepares you quickly to repair all types of appliances, including air conditioning, refrigeration, small gasoline engines. An easy, practical course leading to profitable part-time or full-time business of your own.



ELECTRONICS FOR PRINTERS

Designed to teach operation and maintenance of Electronic equipment which controls the latest devices developed for the graphic arts industry. From basic principles to computer circuits. Approved by major manufacturers.

* NOTE: You must pass your FCC License exam (any Communications course) or NRI refunds in full the tuition you have paid.

Over 50 Years of Leadership in Electronics Training



POPULAR ELECTRONICS

WORLD'S LARGEST-SELLING ELECTRONICS MAGAZINE

VOLUME 25

OCTOBER, 1966

NUMBER 4

SPECIAL CONSTRUCTION FEATURE

- CHARLES CARINGELLA, W6NJV **41** **TIME-SIGNAL-ONLY RECEIVER**
Pocket-size unit is permanently tuned to either CHU or WWV

FEATURE ARTICLES


- KEN GILMORE **47** **CAREERS IN ELECTRONICS**
Results of POPULAR ELECTRONICS' survey of the job market
- DON LANCASTER **52** **INTEGRATED CIRCUITS—WHAT ARE THEY?**
Circuits so small you need tweezers to pick them up
- DON LANCASTER **57** **INTEGRATED CIRCUIT AMPLIFIER YOU CAN BUILD FOR UNDER \$6**
Work with IC's today and be ready for tomorrow
- ROBERT P. BALIN **64** **VOLTAGE DIVIDER QUIZ**
- ART TRAUFFER **65** **BUILD HI-FI AMPLIFIER FOR SOLID-STATE PHONO CARTRIDGE**
Stereo hi-fi with two transistors
- THEODORE M. HANNAH, K3CUI **68** **FROM OUT OF THE PAST**
- 70** **ZERO-BEATING THE NEWS**
- LUIS VICENS **72** **THE IMPOSSIBLE CIRCUIT**
- LOU DEZETTEL, W9SFW **73** **BUILD AN 80/40 METER BANDSWITCHING VERTICAL**
- MARSHALL LINCOLN **75** **WHAT ARE THESE THINGS CALLED DECIBELS?**
What they are, and without math, too
- 79** **THE IMPOSSIBLE CIRCUIT MADE POSSIBLE**
- CARL KOHLER **80** **UNPOPULAR ELECTRONICS**
- 82** **REFLEXOMETER REFLECTIONS**
- LOU GARNER **84** **SOLID STATE**
- RYDER WILSON **90** **BUILD A STICK-SHIFT ELECTRIC SHAVER**
- HERB S. BRIER, W9EQG **91** **AMATEUR RADIO**
Thumbnail review of "Dua-Bander 84" SSB transceiver
- MATT P. SPINELLO, KHC2060 **93** **ON THE CITIZENS BAND**
The CB image
- BILL LEGGE & BOB HILL, W2ARR 3 **94** **BROADCASTS FROM AFRICA AND MIDDLE EAST**
- HANK BENNETT, W2PNA **95** **SHORT-WAVE LISTENING**
IRC's not valid in some countries
- ROBERT LEGGE **96** **ENGLISH-LANGUAGE BROADCASTS TO NORTH AMERICA**
- CHARLES VIAHOS & BYRON G. WELS **97** **BUILD A HIP SQUAWK BOX**
- 130** **DX PROVINCES AWARDS PRESENTED**

DEPARTMENTS



Electronics hobby has dwinus types, too **80**

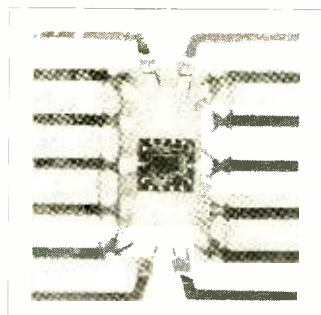- 6** **LETTERS FROM OUR READERS**
- 14** **TIPS & TECHNIQUES**
- 15** **READER SERVICE PAGE**
- 22** **NEW PRODUCTS**
- 27** **ELECTRONICS LIBRARY**
- 28** **NEW LITERATURE**
- 30** **OPERATION ASSIST**



Can this spider-like IC do YOUR job? **52**

POPULAR ELECTRONICS is indexed
in the Readers' Guide
to Periodical Literature

Copyright © 1966 by ZIFF-DAVIS PUBLISHING COMPANY. All rights reserved.

POPULAR ELECTRONICS, October 1966, Volume 25, Number 4, Published monthly at 307 North Michigan Avenue, Chicago, Illinois 60611. One year subscription rate for U.S., P.S. Possessions and Canada, \$5.00; all other countries, \$6.00. Second class postage paid at Chicago, Illinois and other mailing offices. Subscription Service: Portland Place, Boulder, Colorado 80501.

This month's cover photo by
Bruce Pendleton

DEVRY TECH NOT ONLY TRAINS
YOU... BUT HELPS YOU GET
STARTED AT NO EXTRA COST IN
THE **BIG-MONEY FIELD** OF

ELECTRONICS!



HOME LABORATORY EQUIPMENT
— YOURS TO KEEP!

✓ PREPARE AT HOME

Whether you want to prepare for a good-paying new job or for advancement in Electronics with your present employer, DeVry Tech offers specialized educational programs designed to meet your needs. You set up your own HOME LABORATORY and work over 300 construction and test procedures to develop on-the-job type skills. You build a quality Transistorized Meter, a 5-inch Oscilloscope and a special Design Console. DeVry also includes modern "programmed" texts, instructive motion pictures, Consultation Service. Effective? Yes!



EXPERIENCED
INSTRUCTORS!

✓ RESIDENT SCHOOL

If you prefer you may get all of your training in DeVry's U.S. or Canadian resident schools under the close guidance of friendly, experienced instructors. You work with a wide variety of commercial equipment similar to that actually used in industry as you prepare in our laboratories for a technician's job in Communications, Microwaves, Radio-Television, Automation, Radar, Computers, or other branch of Electronics. DeVry even provides part-time job placement service to those who wish to earn extra money while attending day or evening classes.



✓ PLACEMENT SERVICE

Meet W. E. Bartz, who has helped thousands of DeVry men toward exciting, profitable careers in Electronics. When YOU complete your program, he will help you too. As Placement Manager in touch with business and industry across the nation, Bartz knows the employer demand for DeVry-trained men. He has cooperated in placing our graduates with thousands of firms!
Men 18-45, start preparing NOW for this vast opportunity field. Soon you should be ready for DeVry's valuable employment help!

MAIL COUPON TODAY!

No Advanced
Education or
Previous Technical
Experience Needed
to Get Started

Your ambition and desire to succeed are more important! DeVry guides you every step of the way toward success.

Free

Send coupon
for these two
factual book-
lets NOW!



DeVry TECHNICAL INSTITUTE
4141 Belmont Avenue, Chicago, Ill., 60641 Dept. PE-10-W
Please give me your two free booklets, "Pocket Guide to Real Earnings," and "Electronics in Space Travel"; also include details on how to prepare for a career in Electronics. I am interested in the following opportunity fields (check one or more):

- | | |
|--|---|
| <input type="checkbox"/> Space & Missile Electronics | <input type="checkbox"/> Communications |
| <input type="checkbox"/> Television and Radio | <input type="checkbox"/> Computers |
| <input type="checkbox"/> Microwaves | <input type="checkbox"/> Broadcasting |
| <input type="checkbox"/> Radar | <input type="checkbox"/> Industrial Electronics |
| <input type="checkbox"/> Automation Electronics | <input type="checkbox"/> Electronic Control |

Name _____ Age _____

Address _____ Apt. _____

City _____ State _____ Zip _____
Code _____

Check here if you are under 16 years of age.

HOME STUDY AND RESIDENT SCHOOL TRAINING
AVAILABLE IN CANADA

2103

DeVry TECHNICAL INSTITUTE

4141 Belmont Avenue • Chicago, Illinois 60641

Accredited Member of National Home Study Council


LET THE BUYER BEWARE!

CAVEAT EMPTOR

The Roman phrase "Caveat Emptor" cautions the purchaser to examine the article he is buying, and act on his own judgment, and at his own risk! We print it here as a reminder to you, hopefully a happy owner of a Shure Stereo Dynetic® cartridge, that the superior performance of all Shure cartridges depends upon the Shure Stereo Dynetic Stylus assembly—and alas, there are indeed imitations.

May we caution you that an inferior replacement stylus can audibly detract from and significantly reduce the cartridge's performance, and increase record wear. Obviously, if an imitation Stereo Dynetic stylus is used, we cannot guarantee that the cartridge will perform to published specifications. Accept no substitute.

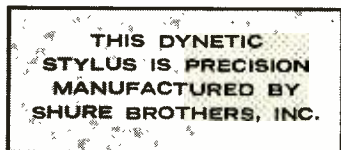LOOK FOR THIS WORDING ON THE BACK OF PACKAGE



It is your assurance that the stylus you buy will enable your cartridge to perform up to Shure standards . . . incomparable Shure standards, that is.

INSIST ON



REPLACEMENT STYLUS

SHURE BROTHERS, INC.

222 Hartrey Ave., Evanston, Illinois 60204

Manufactured Under One or More of the Following U. S. Patents and Other Patents Pending, 2,983,516, 3,055,988, 3,077,521, 3,077,522, D 183,366, D 185,168, D 187,229, D 187,230, D 189,144, D 193,006, D 193,007, D 193,854, D 193,934.

CIRCLE NO. 44 ON READER SERVICE PAGE

POPULAR ELECTRONICS

PHILLIP T. HEFFERNAN
Publisher

OLIVER P. FERRELL
Editor

ROBERT CORNELL. WA2HDQ
Managing Editor

JOHN D. DRUMMOND
Technical Editor

WILLIAM GALBREATH
Art Director

MARGARET MAGNA
Associate Editor

ALEXANDER W. BURAWA
Assistant Editor

ANDRE DUZANT
Technical Illustrator

NINA KALAWSKY
Editorial Assistant

PATTI MORGAN
Artorial Assistant

H. BENNETT, W2PNA
H. S. BRIER, W9EGQ

L. E. GARNER, JR.

M. P. SPINELLO, KHC2060
Contributing Editors

LAWRENCE SPORN
Advertising Sales Manager

ARDYS C. MORAN
Advertising Service Manager

ZIFF-DAVIS PUBLISHING COMPANY

Editorial and Executive Offices
One Park Avenue, New York, New York 10016
212 679-7200

Eastern Advertising Manager, RICHARD J. HALPERN

Midwestern Office
307 North Michigan Avenue, Chicago, Illinois 60601
312 726-0892

Midwestern Advertising Manager, JAMES WEAKLEY

Western Office
9025 Wilshire Boulevard, Beverly Hills, California 90211
213 CRestview 4-0265; BRadshaw 2-1161
Western Advertising Manager, BUD DEAN

Japan: James Yagi
c/o Sekihara
1, Sakamachi, Shinjuku-ku
Tokyo, Japan

Circulation Office
Portland Place
Boulder, Colorado 80302

William B. Ziff, Chairman of the Board (1946-1953)
William Ziff, President
W. Bradford Briggs, Executive Vice President
Hershel B. Sorbin, Vice President and General Manager
Phillip Sine, Financial Vice President
Walter S. Mills, Jr., Vice President, Circulation
Stanley R. Greenfield, Vice President, Marketing
Phillip T. Heffernan, Vice President
Frank Pamerantz, Vice President, Creative Services
Arthur W. Butzow, Vice President, Production
Edward D. Muhlfeld, Vice President

Ziff-Davis also publishes *Skating, Flying, Business & Commercial Aviation, Boating, Car and Driver, Cycle, Popular Photography, HiFi/Stereo Review, Electronics World, Modern Bride, Skating Trade News, and Skating Area News.*

All subscription correspondence should be addressed to POPULAR ELECTRONICS, Circulation Department, Portland Place, Boulder, Colorado 80302. Please allow at least six weeks for change of address. Include your old address, as well as new one (losing it possible an address label from a recent issue).

EDITORIAL CONTRIBUTIONS must be accompanied by return postage and will be handled with reasonable care; however, publisher assumes no responsibility for return or safety of art work, photographs or manuscripts.



Member Audit Bureau of Circulations

POPULAR ELECTRONICS



Where the action is you'll find the hot new . . .
Hallicrafters CB-20 "Reactor"—\$99.95!

Yours today—the ruggedest, cleanest, most powerful basic CB transceiver that ever rode the range!

You get Hallicrafters' field-proven, solid-state design—compact, fool-proof. You get high-order modulation, superb sensitivity and built-in noise suppression. You get five-channel convenience.

In short—you get performance equal to that of equipment more than double the price.

*Get the full story from your
Hallicrafters authorized
CB outlet today!*



Quality through craftsmanship is the whole idea at *hallicrafters*

Export: International Division,
Canada: Available through Gould Sales Co.

5th & Kostner Aves., Chicago, Ill. 60624

CIRCLE NO. 21 ON READER SERVICE PAGE

Grooveless record demonstrates anti-skating on the

Garrard[®] LAB 80



Due to the offset angle of any cartridge and the rotation of the record, all tone arms tend to skate towards the center as you see in this blank disc. The grooves on ordinary records generally keep the tone arm in place, but a side pressure is constantly present, causing poor tracking, right channel distortion, and uneven record wear.



The Lab 80 Automatic Transcription Turntable has a patented simple anti-skating control which equalizes the pressure. Here you see that even on the same blank record, the Lab 80 tone arm tracks perfectly, as if there were grooves!



LAB 80—\$97.50 less base and cartridge

For copy of 32-page Comparator Guide describing all features, write Garrard, Dept. GP-356, Westbury, New York 1159C.

NAME _____
 ADDRESS _____
 CITY _____ STATE _____ ZIP _____

CIRCLE NO. 19 ON READER SERVICE PAGE

LETTERS

FROM OUR READERS

Address correspondence for this department to:
 Letters Editor, POPULAR ELECTRONICS
 One Park Avenue, New York, N. Y. 10016

HAM RADIO EQUIPMENT JAMBOREE

Looking for the amateur radio column in the August, 1966, issue, I found in its place "Amateur Equipment Jamboree: 1966" which informed me how "professional" my amateur station could be in performance and appearance if I used factory-built equipment, or built my station from commercial kits. This sort of article has become typical in the current electronics and amateur radio publications. At one time the radio amateur was a distinguished individual who was envied because of his competence and ingenuity in constructing and operating his own wireless station. But today's amateur simply writes a check, buys a load of factory-built machinery,



strings up an antenna (often factory-built, too), plugs it all in, twists the knobs and pushes the buttons according to the instruction book. He knows, of course, that if anything burns up, the rig can be sent back to the factory for repairs; in fact, a service guarantee usually comes with it. Hamming has become a fun-communicating type of operation with few individuals building their own equipment, or even taking an interest in the technical side of radio. Perhaps it is out of monetary interest that the magazines are pushing this commercialism, but the trend has got to be reversed if we are to keep our hobby colorful and interesting.

DONALD CHESTER, K4KYV
 Woodlawn, Tenn.

I would like to point out an error made in the "Amateur Equipment Jamboree" concerning the Heathkit SB-300 receiver. It is listed as a Heathkit SB-301.

DON WILLIAMSON, KPM3960
 Florence, Ky.

There's a mistake in the "Radio Amateur Equipment Sampler" on page 73. It says that the Hallicrafters HT-10 is designed to operate on 80-10 meters. It also operates on 6 meters.

JOHN BOHN
 Minot, N.D.

Donald, if our children are forced to do everything our parents did, we would still be

WE GUARANTEE THE claricon® "RANGEMASTER" CB TRANSCEIVER TO OUTPERFORM ALL OTHERS IN ITS CLASS!

The Claricon "RANGEMASTER" by TOKAI is a professional transceiver with every feature necessary to insure dependable long range communication. Dynamic microphone cartridge delivers 100% modulation. Interchangeable plug in crystals permit use of all 23 CB channels. Housed in a rugged drawn metal case. Jacks for earphone and AC adaptor.

1. ADDITIONAL RF AMPLIFIER STAGE FOR CRISP, LONG RANGE RECEPTION
2. SEPARATE MICROPHONE AND SPEAKER FOR TELEPHONE LIKE-OPERATION
3. EXTRA SENSITIVE SUPERHETERODYNE RECEIVER
4. SWITCH CONTROLLED SQUELCH
5. AC BASE STATION AVAILABLE \$19.95 each.
6. NO LICENSE REQUIRED

SPECIFICATIONS: 11 Transistors and 1 Diode; Input to final Amp. 100MW; Audio 130MW; IF Frequency, 455 KC; 30db Signal to Noise Ratio; 18db selectivity. Uses 6 Penlites. 8" x 2½" x 3"; Weight 1½ lbs.

RANGE: MAXIMUM 10 MILES AVERAGE 2-5 MILES

\$39⁹⁵
each

COMES COMPLETE WITH
EARPHONE, BATTERIES
AND LEATHER CARRYING CASE.

Money Back Guarantee

The Claricon "Rangemaster" will outperform any Class "D" CB Transceiver in range and clarity. Claricon has authorized its dealers to refund your money within 10 days from the purchase date if you can show that the "Rangemaster" does not perform better than any other 100MW unit.



ORDER FROM YOUR AUTHORIZED Claricon Dealer! PE-10

If no local dealer order from:
CLARICON, 663 DOWD AVE., ELIZABETH, N.J.

- Please send me Claricon "Rangemaster" Transceivers @ \$39.95 each.
(Prices may vary in your local area)
- Please send me AC Base Station @ \$19.95 each.
- Please send information on the "Rangemaster" Transceiver

Name.....

Address

City & State.....

**FULLY EQUIPPED FOR
IMMEDIATE OPERATION
ON ALL 23 CHANNELS**

reach
way out
with

the NEW
Cobra CAM-88



**23-CHANNEL CB
mobile and base station
AM TRANSCEIVER**

GREATER RANGE POWER with the exclusive new **DYNA-BOOST** circuit that intensifies speech signals and extends the signal range.

The new Cobra CAM-88 is rugged, handsome and field proven. Compare it, feature for feature, with other CB equipment and you'll be convinced that the Cobra CAM-88 is by far the best.

Outstanding Features

- Fully-Equipped for Immediate 23-channel Transmit and Receive
- Double Conversion Superheterodyne Receiver
- Transistorized 117V AC 12V DC Power Supply
- Speech Compression with Switch
- Delta-Tune Fine Tuning
- Squelch Control and Standby Switch
- Illuminated Dual-Purpose Meter
- Power-in (Receive)-Power-out (Transmit)
- Modulation Indicator
- Detachable Press-to-talk Microphone
- Convertible to a Public Address Amplifier

Carefully engineered design makes the Cobra completely reliable and easy to operate. Completely self-contained. *No additional crystals needed.* \$21495



DIVISION OF **DYNASCAN CORPORATION**
1801 W. BELLE PLAINE AVE. • CHICAGO, ILL. 60613

Export: Empire Exporters, 123 Grand St., New York 13, U.S.A. Also available in Canada
CIRCLE NO. 6 ON READER SERVICE PAGE


LETTERS

(Continued from page 6)

listening to Atwater Kents. You can build a station from scratch and strain to get on the air, and there's nothing wrong with that, if that is what you want to do, or you can get on the air as expeditiously as possible, and devote time and energy to things new, different, and better. There's no doubt that a home-brew rig demands of the builder a good deal more aptitude and practical know-how, but is he getting the most out of his energies by punching holes in chassis to make a conventional transmitter or receiver instead of, say, building a moon-bounce capability? Besides, there's nothing to prevent the kit builder or owner of a "store-bought" unit from knowing all about his equipment, and the purpose of each resistor and capacitor. Don, the Heathkit SB-301 is a new model. John, you are right about the Hallicrafters HT-40; it does go up to 6 meters. That's pretty fine and fancy reading of the fine print—and we appreciate it, because this sort of thing helps keep editors on their toes.

HAVANA PROPAGANDA

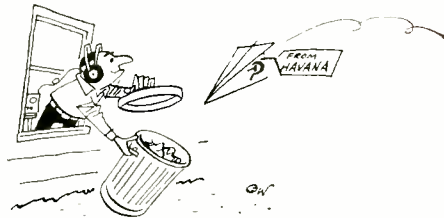I truly agree with the letter entitled "Damaging QSL" (July, 1966). Every hobby has its bad points, and being on a propaganda list is not very enjoyable. I, too, have been receiving propaganda from *Radio Havana*. How about printing a list of the countries that send



propaganda to listeners when all the listeners want is a verification of report of reception? In this way, we would know which countries not to write to.

MITCHELL HERBACH
Brooklyn, N.Y.

Please tell your readers to stay away from *Radio Havana*, Cuba. I have not SWL'ed now for two years, but the communist propaganda rubbish keeps coming. Help!

BILL BRADFORD
Murray, Utah

Okay, Mitch, we'll publish the info as we get it. Bill, wonder what the *Radio Havana* people would do if you wrote to them and asked them, in a nice way, to take your name off their mailing list.

SWIMMING POOL SPLASH ALARM

I put together the "Swimming Pool Splash Alarm" (July, 1966) and followed the diagram



SPECIAL OFFER from the famous Gernsback Electronics Book Club, an affiliate of RADIO-ELECTRONICS Magazine. For 10 years the Club has helped men in electronics get ahead and stay ahead in this fast-changing field. See how it can help you . . .

Gernsback Library Inc., Electronics Book Club
 Dept. PE10, 154 West 14th Street, New York, N.Y. 10011
 Enroll me in the Electronics Book Club and send me the TWO-HANDBOOK SET: How to Fix Transistor Radios and Printed Circuits. Bill me only 99¢ plus shipping. If not pleased, I may return both books in 10 days and forget the matter.
 As a member, I need accept as few as 4 additional books a year—and may resign any time after purchasing them. All books will be described to me in advance, every other month, in the Club Bulletin, and a convenient form will always be provided for my use if I do not wish to receive a forthcoming book. You will bill me the special Club price for each book I take. This will often be as much as 30% off retail prices, plus a few cents postage.

Name.....
 (please print)

Address.....

City..... State..... Zip Code.....


SAVE POSTAGE COSTS—enclose 99¢ now and we will pay postage. Same return privilege.

THIS VALUABLE COUPON BRINGS YOU the \$9.90 ELECTRONICS GUIDE below for only 99¢ with trial membership in the famous Gernsback Electronics Book Club!

You are invited to accept—at a mere fraction of the original price—an electronics guide that answers every question you've ever had on fixing transistor radios and printed circuits. We make this extraordinary offer to demonstrate just one of the many advantages you will enjoy as a member of the famous Gernsback Electronics Book Club.

Here is a complete, self-training course by expert Leonard C. Lane. It tells you all you want to know, including specific servicing methods and techniques. You get practical, down-to-earth guidance you can use at once to spot trouble in the audio section, pinpoint speaker and earphone circuit defects, check distortion in the audio amplifier, locate front-end troubles, eliminate printed-circuit board pitfalls, and work more effectively with the signal generator vtvm, scope and isolation probe.

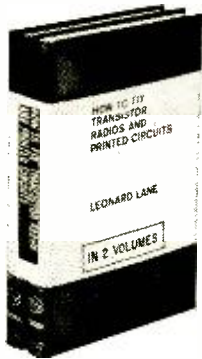NOTHING IS LEFT OUT. This giant 2-volume guide treats every area—much of it original, unavailable anywhere else in book form. Hundreds of illustrations and schematics practically turn equipment inside out for you to examine. You get practical tips to save shop time, to lessen servicing trial and error, to find and fix any trouble with professional know-how.



SEND NO MONEY NOW mail coupon for free trial

You risk nothing, now or ever, by mailing the coupon above. You will receive these 2 skill-building handbooks for free examination. If not pleased, return books in 10 days and forget the matter. Otherwise, start your membership and discover how the Club will help you build your know-how, boost your income, and get more fun out of electronics!

Gernsback Library, Electronics Book Club
 Dept. PE-10, 154 West 14th Street
 New York, N.Y. 10011

Learn more, earn more!

Every other month the Club's News Bulletin will tell you about a significant new self-teaching book on color TV or radio servicing, test instruments, transistors, hobby projects, stereo, tape recording, industrial electronics, appliance repair, communications, or on some other area of vital interest to you. Each is a working tool designed to help you learn the subject quickly and easily.

Big cash savings!

As a member, you alone decide whether you want a particular book or not. You get 2 books now for 99¢ and need take only 4 more within a year. And the Club saves you up to 30% off retail prices on the books you take!

FREE reference service!

What's more, our staff agrees to answer for you personally, any specific electronics questions of your choice. You're entitled to 3 questions for every book purchased—an extraordinary membership benefit!

Mail coupon and enjoy these benefits at once!

- * Get two books immediately for 99¢.
- * Free 10-day examination privilege.
- * Continuous cash savings.
- * Free reference service.
- * Free charts given with many books.
- * You alone decide which books you want. Books are always returnable.
- * Club books are practical tools.
- * Choose only 4 more books in a year.



**TECHNICAL TRAINING
INTERNATIONAL, Inc.**
Chicago, Illinois 60617

**TRAIN AT HOME FOR
A HIGH-PAY JOB**

LEARN Electronics Engineering AT HOME

Today, **ELECTRONICS** is the fastest growing field, and has the greatest growth potential. You only have to look around you to see this - Radio, Television, Computers, Telemetry, - there are literally thousands of facets to this giant and growing industry.

Training is the key to success in this highly technical field - to meet the demands of today and the exciting future of tomorrow. Training is the one big important step between "Wanting To Get Into Electronics" and "Being In Electronics".

To accomplish this, there are two well-known guidelines that you must follow:

"Choose a field that is rapidly expanding with a good future growth potential."

"Prepare yourself for a job in that field by learning everything you can about it."

Free

**NEW INFORMATIVE
BROCHURE** ▶



TECHNICAL TRAINING INTERNATIONAL, Inc.
10447 South Torrence Avenue
Chicago, Illinois 60617

Yes, I'm interested in the Electronics Field. Please send me your **FREE BROCHURE**. I understand there is no obligation.

Occupation Age

(please print)

Name

Address

City State Zip



"Over a Quarter of a Century of World Wide Professional Experience in Training Men"

CUT OUT & MAIL TODAY. PE-10-001

LETTERS

(Continued from page 8)


and text very closely. The alarm worked on the first two trials and cut out on the third. Transistors Q1 and Q3 were found to be defective and were replaced, but on subsequent tests the same thing happened. Is it possible that the diagram is at fault?

GENE H. ALBRIGHT
New Stanton, Pa.

The "Swimming Pool Splash Alarm" can also be used as a burglar alarm. All you have to do is connect a normally-open microswitch across the probes and place the switch in contact with a door or window.

JIM VARRONE
N. Miami Beach, Fla.

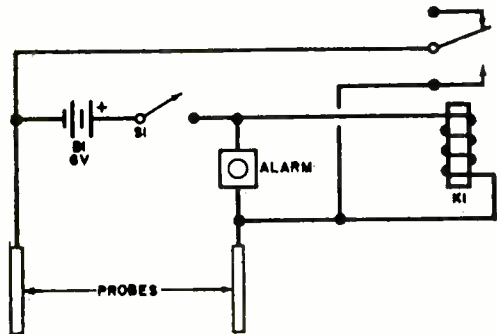I have found an easier way to make this alarm. By eliminating most of the compo-



nents and the separate battery, but retaining all of the features and the relay in the original circuit, cost, time, and space can be saved.

WILLIAM A. RUSSO
N. Merrick, N.Y.

Gene, the diagram is correct; diode D1 is supposed to protect the transistors from reverse current surges. Try adding a resistor in series with the relay winding to reduce the amount of current flow. The larger the ohmic value of the resistor, the less current will flow; but don't use a value large enough to interfere with proper relay action. The Potter and Brumfield RS5D relay is available with different coil ratings. Did you get the one specified? Jim, your suggestion is a good one—actually, there are a great many variations of and applications for this circuit. Bill, your circuit could work if the conductivity of the water allows enough current flow to energize the relay. Don't sell the transistors short; they do increase circuit sensitivity significantly.

BEWARE OF SILVER SOLDER

We have received a report from the New Mexico Department of Health on a case of cadmium poisoning involving a television station repairman who had been using silver solder with a high cadmium content. Also, two deaths have occurred, one in California,

Reach out
into Hy-Gain
DUO-BEAM
territory.

Biggest "Talk Power" in Citizens Band!

With a powerful Hy-Gain Duo-Beam, your signal reaches out loud and clear into territories miles beyond the range of other antennas. At the same time, in areas you've been working, your signals are stronger and clearer...on both transmit and receive. And, because Duo-Beams are rotatable, you can direct your extra power with pinpoint accuracy in any of the 360 degrees surrounding your station!

3 Models to choose from—pick your "Talk Power!"

120 watts "Talk Power" DUO-BEAM 10

Hy-Gain's twin-driven 10-element Duo Beam that's guaranteed to out-perform any other legal antenna for Citizens Band. Heavy gauge aluminum construction...survives 80 MPH winds. Installs on 1½" mast. Model 1110DB \$99.95 Net

93 watts "Talk Power" DUO-BEAM 6

Hy-Gain's twin-driven 6-element Duo-Beam that's guaranteed to out-perform any legal antenna for Citizens Band other than the Duo-Beam 10. Rugged construction survives 80 MPH winds. Installs on 1½" mast. Model 116DB \$69.95 Net

42 watts "Talk Power" DUO-BEAM 4

Hy-Gain's twin-driven 4-element Duo-Beam. Guaranteed to out-perform any legal antenna for Citizens Band other than the Duo-Beam 10 or the Duo-Beam 6. Rugged aluminum construction survives 80 MPH winds. Installs on 1¼" to 1½" mast. Model 1140B \$39.95 Net

Available now from your Hy-Gain Distributor or Dealer

Send for complete descriptive literature—Form No. 13

hy-gain ELECTRONICS CORPORATION

8501 N.E. Highway 6 • Lincoln, Nebraska 68501

www.americanradiohistory.com

2 Complete Tube Testers In 1 Instrument

1. RECEIVING TUBE TESTER
plus:
2. TV PICTURE TUBE TESTER

SAVE MORE THAN \$50!

(compared to buying two separate testers)



\$9295 Net

Precise's New 'GREEN LINE' Model 115

1. RECEIVING TUBE TESTING

Eliminates Obsolescence Problem! A unique 10-circuit switching design allows testing of all the new type tubes that have elements with multiple pin connections—the Model 115 is the first and only obsolete-proof receiving tube tester in the speed-type class. ■ Grid emission test provides a sensitive grid emission and gas check by the use of built-in balanced VTVM circuitry. This all-important feature provides a revealing and significant tube condition test. ■ Basic dynamic cathode emission test is supplemented by a hot cathode shorts and leakage check. ■ Includes all latest type sockets, plus pin straighteners.

2. TV PICTURE TUBE TESTING & REJUVENATION (B&W and COLOR)

The basic picture tube test (for each gun of color picture tubes, and the single gun of B&W tubes) is picture-producing beam current (not total cathode emission which is rarely indicative of picture brightness). The beam current test checks all picture tubes for proportionate screen brightness. The critical central area of the picture tube cathode is checked in addition to the controlling action of the first grid. ■ Rejuvenation of picture tubes is accomplished by a unique capacitor discharge circuit which welds most intermittent elements, and redistributes cathode oxide over the beam-producing central cathode area. Meter directly indicates increase in brightness after each "shot".

GENERAL DATA

Wide visibility, 2% accuracy meter includes separate scales for quality test, grid emission, and picture tube beam current. ■ Complete up-to-date data book supplied. New data constantly available. ■ Size 16" x 9" x 4 3/4". Weight 8 pounds. ■ ACCESSORIES AVAILABLE: Model CTA Color Tube Socket Adapter, \$6.50 Net.

See the complete "GREEN LINE"—power supplies, scopes, VTVMs, signal generators, tube testers, decade boxes, probes—at your local distributor, or write direct for full information and specs.

PRECISE ELECTRONICS

Division of Designatronics Incorporated
76 East Second Street, Minneapolis, L. I., New York

ENGINEERED EXCELLENCE IN TEST EQUIPMENT

CIRCLE NO. 37 ON READER SERVICE PAGE

LETTERS (Continued from page 10)

and one in Utah. Not all silver solder contains cadmium. However, the following precautions should be followed: warning labels, which should be on all packages, should be carefully read and followed; the working area should be properly ventilated; and workers should tell their physicians what their jobs are and what types of materials they handle. Occupationally-caused illnesses and diseases can be easily overlooked if physicians do not have this vital information.

U.S. Department of
Health, Education, and Welfare
Public Health Service
Washington, D.C. 20201

ELECTRIC DICE GAME—NO DICE

I think it a misnomer to call the device designed by Ken Greenberg (July, 1966) an electronic dice game. The device can perform the function of one twelve-sided die but not of two conventional six-sided dice, for a number of reasons. First, one cannot obtain the number 1 when two dice are tossed in a game. Second, even if you were willing to discard the number 1, the numbers 2 to 12 that the electric gadget offers the player are equiprobable, which is contrary to the probabilities associated with these numbers on a tossed pair of dice. It is well known, for example, that a 7 has a far greater probability ($1/6$) than a 12 ($1/36$). I think this should be brought to the attention of your readers.

SOLOMON ROSENSTARK
Department of Electrical Engineering
New York University
University Heights, N.Y. 10453


Like the Solomon of old, your words of wisdom are well spoken; but authors and editors, being what they are, do take poetic license from time to time. At least the electronic "dice" weren't loaded. We agree that equiprobable situations are atypical of dice.

SO WHY NOT HERTZ?

I made a list of the "Measurement Units" in the article entitled "Test Measurements Profile" in the April 1966 issue (the same issue in which you announced the change from cycles to hertz), together with the names of some of the devices mentioned. I observed that every one of them is named for some early experimenter in electronics: *ampere* (Andre Marie Ampere, French physicist); *farad* (Michael Faraday, English chemist and physicist); *gauss* (Karl Friedrich Gauss, German mathematician); *henry* (Joseph Henry, American physicist); *Maxwell bridge* (James Clerk Maxwell, Scottish physicist); *ohm* (George Simon Ohm, German physicist); *volt* (Count Alessandro Volta, Italian physicist); *watt* (James Watt, Scottish inventor); *Wheatstone bridge* (Sir Charles Wheatstone, English physicist);

(Continued on page 103)

POPULAR ELECTRONICS

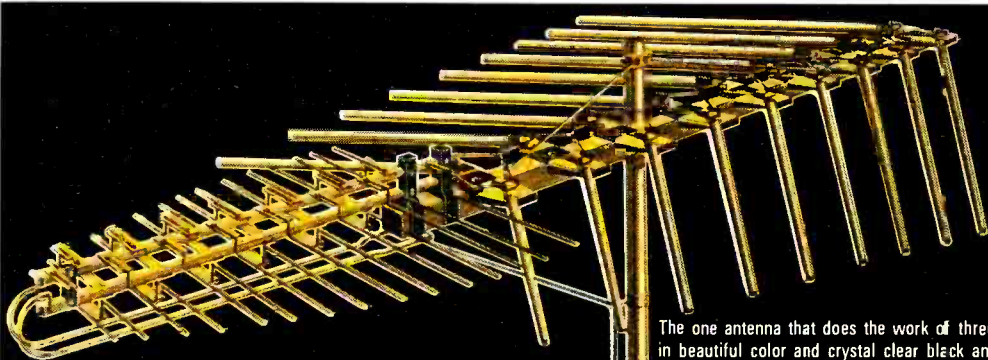

FINCO ALL-BAND UHF-VHF-FM ANTENNA
75 OHM Model CX-UVF-24 \$72.10 List

FINCO ALL-BAND UHF-VHF-FM ANTENNA
300 OHM Model UVF-24 \$59.95 List

The one antenna that does the work of three! Pulls in beautiful color and crystal clear black and white pictures on both UHF and VHF channels... plus the finest stereophonic and monophonic FM sound reproduction.

300-ohm models for normal reception areas from \$18.50 to \$59.95

75-ohm models for poor reception areas from \$42.65 to \$72.10


FINCO

introduces / 75-ohm COLOR VE-LOG ANTENNAS
FOR UHF-VHF-FM RECEPTION

Finco's Sweep-Element Antenna challenges all competition. Its unique design assures the finest color and black and white TV reception—plus superb FM and FM Stereo tone quality.

300-ohm models for normal reception areas from \$16.95 to \$54.50

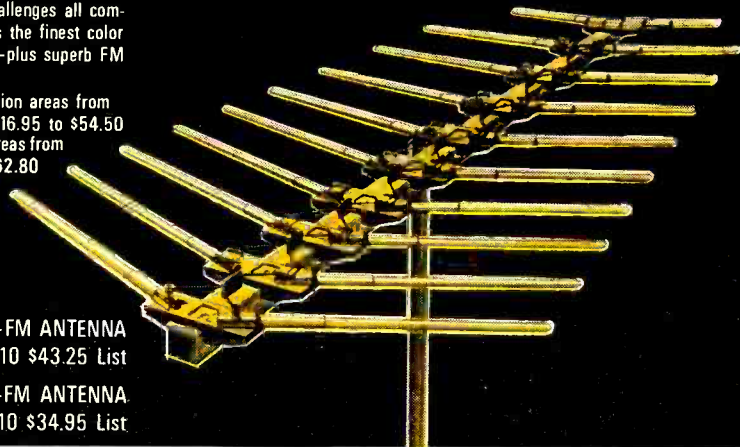75-ohm models for poor reception areas from \$18.55 to \$62.80



FINCO SWEEP-ELEMENT VHF-FM ANTENNA
75 OHM Model CXVL-10 \$43.25 List

FINCO SWEEP-ELEMENT VHF-FM ANTENNA
300 OHM Model VL-10 \$34.95 List

FREE! ALL FINCO CX-VL, CX-UVF AND UVF ANTENNAS COME WITH A FREE INDOOR SET-MOUNTED TRANSFORMER, VHF-UHF TRANSFORMER SPLITTER OR VHF-UHF SPLITTER.



THE FINNEY COMPANY


34 WEST INTERSTATE STREET, DEPT. PE, BEDFORD, OHIO

PARTS
METHODS
IDEAS
GADGETS
DEVICES


TIPS & TECHNIQUES

VERNIER DIAL PROVIDES MECHANICAL BANDSPREAD

If you own one of those inexpensive communications receivers with stations crowded on the dial, you can improve station separation dramatically with a modest investment of about 89 cents, and a few spare moments of your time. All you do is replace your existing fine tuning or bandspread knob with a vernier dial that you can get at most electronic supply houses. If you cannot mount the dial directly on the panel over the control shaft, first mount the dial on a small support panel

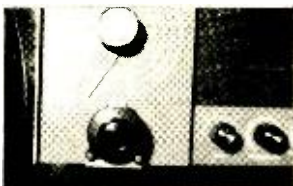

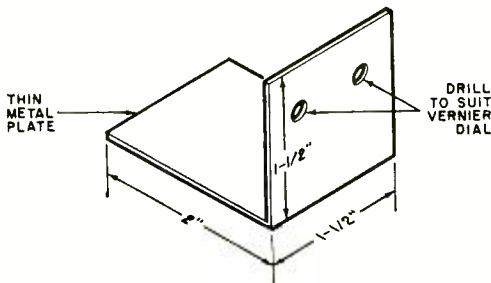fabricated from light-gauge aluminum or sheet metal as shown in the drawing. Then secure the panel, with the installed dial, to the bottom of the chassis or cabinet after



slipping the vernier dial over the bandspread or fine tuning shaft. You'll be pleasantly surprised by the change in tuning ease.

—Bruce Carlin

TRUNK ROLLER MAKES DIAL CORD BRACKET

Hobbyists and experimenters who design or assemble their own receivers are usually faced with the problem of running the dial cord from the tuning dial through holes to the underside of the chassis and back up again. Keeping the dial cord from rubbing against the sides of the holes usually presents a challenge to the builder. A pulley bracket

(Continued on page 20)


ADC 606

Features and Specifications. Power: 90 watts (IHF) @ 4 ohms; 70 watts (IHF) @ 8 ohms
 Total Harmonic Distortion @ rated output: .5%; 2 db below rated output: .2%
 Usable Sensitivity: 1.6 uv (IHF)
 Stereo Separation: 35 db @ 400 Hz; 20 db @ 8,000 Hz
 First, true compact size: 17" wide, 5" high, 9" deep
 Side panels eliminate

need for separate cabinet
 Large, readable dial
 Complete playback and monitoring facilities
 Musical instrument input
 Automatic Frequency Control (switchable)
 Full independent control for 2 sets of speakers
 Headphone jack
 Each channel separately fused, plus main power fuse
 Automatic stereo switching
 2-year warranty

Heard about the new \$279 receiver with \$400 specifications?

This is about the size of it

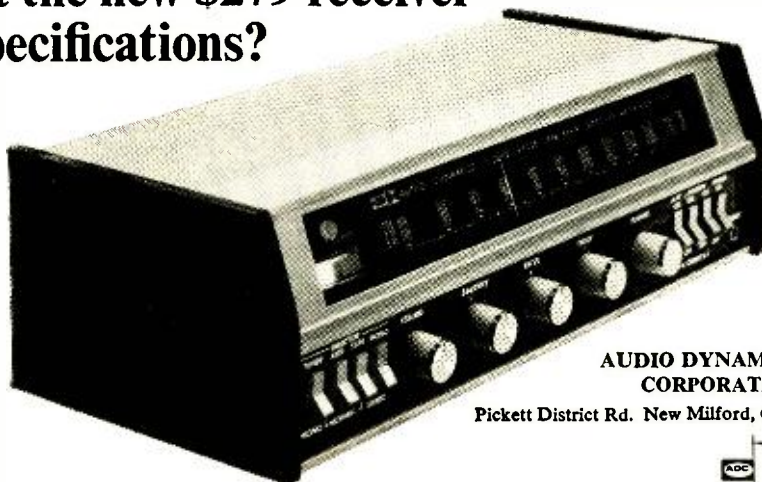

AUDIO DYNAMICS CORPORATION

Pickett District Rd. New Milford, Conn.



CIRCLE NO. 5 ON READER SERVICE PAGE

POPULAR ELECTRONICS

POPULAR ELECTRONICS

READER SERVICE PAGE

**You can get
additional information promptly
concerning
products advertised or mentioned
editorially
in this issue**

1

Circle the number on the coupon below which corresponds to the key number at the bottom of the advertisement or is incorporated in the editorial mention that interests you.

2

Mail the coupon to the address indicated below.

3

Please use this address only for Product Service requests.

**POPULAR ELECTRONICS
P. O. BOX 8391
PHILADELPHIA, PA. 19101**

Please send me additional information about the products whose code numbers I have circled

1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24 25
26 27 28 29 30 31 32 33 34 35 36 37 38 39 40 41 42 43 44 45 46 47 48 49 50
51 52 53 54 55 56 57 58 59 60 61 62 63 64 65 66 67 68 69 70 71 72 73 74 75
76 77 78 79 80 81 82 83 84 85 86 87 88 89 90 91 92 93 94 95 96 97 98 99 100

NAME (Print clearly) _____

ADDRESS _____

CITY _____ **STATE** _____ **ZIP CODE** _____

VOID AFTER NOVEMBER 30, 1966

10

Choose Your Tailor-Made Course in N.T.S. "PROJECT METHOD" ELECTRONICS

Now! N.T.S. — one of America's oldest leading home-study and resident technical schools—offers you **GREATER CAREER OPPORTUNITIES IN ELECTRONICS.**



You can install and maintain electronic circuitry in missiles and rockets . . . specialize in microwaves, radar, and sonar.



You can succeed in TV-Radio Communications . . . prepare for F.C.C. License, service advanced satellites for industry and defense.



You can service and repair the electronic "brains" of industry — computers, data processing and other automation equipment.



You can become a highly-paid TV-Radio Technician, an electronics field engineer, or succeed in your own sales and service business.

CHOOSE YOUR FIELD—INSURE YOUR FUTURE!

1 ELECTRONICS-TV-RADIO SERVICING AND COMMUNICATIONS

A basic course thoroughly covering fundamentals of electronics, radio, TV servicing and communications.

2 MASTER COURSE IN ELECTRONICS-TV-RADIO, ADVANCED TV AND INDUSTRIAL ELECTRONICS

Qualifies you as a Master Electronics Technician — the Man in Demand.

3 FCC LICENSE COURSE

Preparation for this government license essential for many interesting jobs in radar, radio, television, communications, guided missiles, many others. Upon completion of this course, if you do not pass the FCC exam, your tuition will be refunded in full.

4 RADIO SERVICING (AM-FM-TRANSISTORS)

Train for radio sales and service with dealer or distributor.

5 TELEVISION SERVICING (INCLUDING COLOR)

Covers installation, adjustment, repair and servicing of black and white and color television . . . prepares you for your own sales and service business.

6 STEREO, HI-FI AND SOUND SYSTEMS

A growing field. Prepares you to build, install and service modern sound equipment for home or industry.

7 BASIC ELECTRONICS

Gives you the fundamentals you must know to build on for a future Electronics career. Also offers an excellent background for Salesmen, Purchasing Agents, and others in Electronics.


8 ELECTRONICS MATH

Simple, easy-to-follow instructions in the specialized math you need in many electronics jobs.

INDUSTRY WELCOMES N.T.S. STUDENTS AND GRADUATES

N.T.S. HOME TRAINING: QUICK, PRACTICAL WAY TO HIGHER PAY, LIFELONG BENEFITS

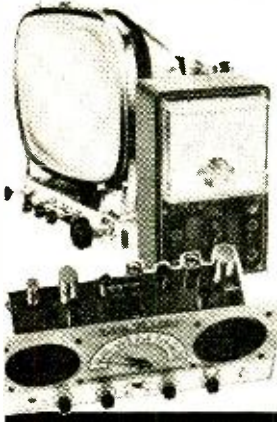N.T.S. "Project Method" Courses can help you get a new and better job — or move up to higher pay in your present one.



N.T.S. "Project Method" home training lessons are shop-tested in the Resident School in Los Angeles. You work on practical job projects, learn to use shop manuals and schematics. Your N.T.S. training is individual. You proceed at your own pace. The Schools' practical methods plus more than 60 years of experience have helped thousands of students all over the world to successful careers.



Most courses include Equipment Kits. There are no Kit Deposits. Everything included in your low tuition.

HIGH SCHOOL AT HOME

Learn easily. New modern method. National also offers accredited high school programs for men and women. Take only subjects you need. Study at your own pace. Latest approved textbooks — yours to keep — everything included at one low tuition. Check High School box in coupon for information.



BENEFIT NOW AND ALL YOUR LIFE WITH N.T.S. HOME TRAINING

The personal guidance you receive during your training can be very helpful to your progress. Many N.T.S. students are able to earn more money within a few months. You can pick and choose your career. Work in industry or go into business for yourself.

Your services will always be in demand wherever you go — and you can pick your spot!

N.T.S. Graduate Advisory Service can help you answer technical questions in establishing your own business and in countless other ways after you've completed your training.

MAIL REPLY CARD

OR COUPON FOR
FREE BOOK AND
SAMPLE LESSON

In Field of Your Choice

You Enroll by Mail — and Save Money.
No Salesmen: This means lower tuition for you.
Accredited Member N.H.S.C.

Sample Lesson



CLASSROOM TRAINING AT LOS ANGELES

If you wish to take your Electronics-TV-Radio training in our famous Resident School in Los Angeles — the oldest and largest School of its kind in the world — write for special Resident School catalog and information, or check coupon.



NATIONAL TECHNICAL SCHOOLS
WORLD-WIDE TRAINING SINCE 1905
4000 S. Figueroa St., Los Angeles, Calif 90037

NATIONAL TECHNICAL SCHOOLS

4000 S. Figueroa St., Los Angeles, California 90037

Please Rush FREE ELECTRONICS "OPPORTUNITY BOOK" and SAMPLE LESSON on Course Checked Below:

- ELECTRONICS-TV-RADIO Servicing & Communications
- Master Course in ELECTRONICS-TV-RADIO Color TV & Industrial Electronics
- FCC LICENSE
- RADIO SERVICING (AM-FM-Transistors)
- TELEVISION SERVICING (Including Color)
- STEREO, HI-FI and SOUND SYSTEMS
- BASIC ELECTRONICS ELECTRONICS MATH
- HIGH SCHOOL Department

Dept.
205-106

Name _____ Age _____

Address _____

City _____ State _____ Zip _____


- Check for Veteran Training under new G.I. BILL.
- Check here if interested ONLY in Classroom Training at Los Angeles.



TIPS

(Continued from page 14)

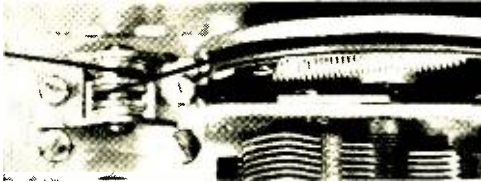fabricated from a small trunk roller and dial cord pulley can be used to simplify the project. Just remove the roller and use the bear-




ing portion of the assembly to support one or more pulleys as shown. The support housing can be mounted on the chassis with machine screws.

—Ronald L. Ives

INDIAN BEADS KEEP 'EM STRAIGHT AS AN ARROW

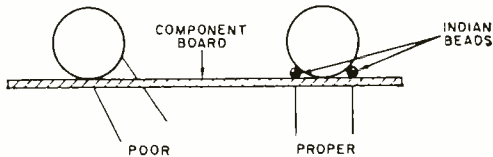If you've had the occasion to mount a ceramic disc capacitor on a circuit board, you might



have wound up soldering the capacitor in an ungainly position, giving your project a "biased" appearance. To insure correct posture of the component, and an overall improvement in the project, slip a small-sized Indian bead onto each lead of the capacitor before soldering it.

—Jan Rosenbaum

FROM PILL BOTTLE CAP TO POSITION INDICATOR

Those seemingly useless pill container caps with a pointer to remind you when it's time



to take your next pill can also be used as shaft position indicators on your electronic projects. To make such an indicator, remove the pointer disc from the lid and drill a 3/8"-diameter hole in the center of the cap. Then slice off the dial portion of the cap, using a

sharp knife or razor blade. Slip the dial onto the potentiometer shaft and secure it in place with a nut. Now replace the indicator knob on the dial.

—Art Trauffer

(Continued on page 100)

SCOTT



Scott's new one-afternoon tuner kit delivers amazing FET Performance

Now you can get factory-wired performance from a kit that takes only one afternoon to build! Scott's new LT-112B is the only kit with Field Effect Transistor circuitry*, enabling you to enjoy more stations more clearly. Interstation Muting Control effects complete quiet between FM stations . . . oscilloscope output allows laboratory-precise correction for multipath distortion.

"Scott's LT-112 . . . is one of the finest FM stereo tuners we have tested and it is easily the best kit-built tuner we have checked . . . Because of its simple construction and trouble-free nature, it is a logical choice for anyone who wants the finest in FM reception at a most remarkable price." HiFi/Stereo Review.

LT-112B specifications: Usable sensitivity, 1.8 μ V; Cross modulation, 90 dB; Stereo separation, 40 dB; Capture ratio, 2.5 dB; Price, \$189.95.

*Patents pending

For your free copy of Scott's 16-page full-color illustrated Guide to Custom Stereo, (circle Reader Service Number 43.)



Write to: H. H. Scott, Inc., Dept. No. 527-10, 111 Powdermill Road, Maynard, Mass. Export: Scott International, Maynard, Massachusetts.

Scott . . . where innovation is a tradition

Prices slightly higher west of Rockies. Subject to change without notice. We reserve the right to make changes and improvements without notice.


CIRCLE NO. 43 ON READER SERVICE PAGE

Be the man who's always
first to say: "I've got
the answer right here!"



START USING THIS REMARKABLE

ELECTRONICS SLIDE RULE

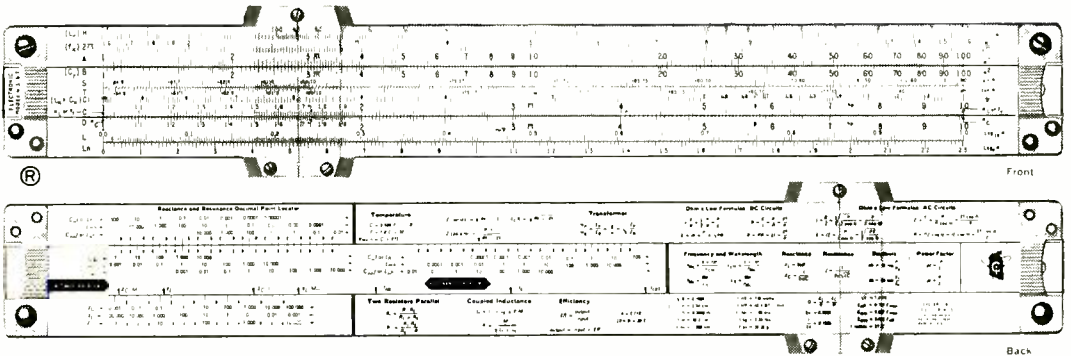

SOME DAY EVERYONE in electronics may have a slide rule like this. Till then, the man who uses one will seem like a wizard as he solves reactance and resonance problems in 12 to 20 seconds—without pencil and paper.

This is a professional slide rule in every detail, a full 10" long, made exclusively for Cleveland Institute of Electronics, to our rigid specifications, by Pickett, Inc. It can be used for conventional computation as well as special electronics calculations. All-metal construction assures smooth operation regardless of climate.

Handsome top-grain leather carrying case has heavy-duty plastic liner to protect slide rule; removable belt loop for convenient carrying. "Quick-flip" cover makes it easy to get rule in and out of case.

You also get four full-length **AUTO-PROGRAMMED™** Lessons, which teach you how to use the special electronics scales on the slide rule. These lessons have been carefully designed to meet the same high educational standards as the electronics career courses for which our school is famous. Even if you've never used a slide rule before, you'll soon whiz through the toughest problems with this CIE rule.

Deliberately underpriced. Many men in electronics have told us that this unique slide rule, leather case, and 4-lesson course easily add up to a \$50 value. But we have deliberately underpriced it at less than \$25. Why? Our reason is simple: we are looking for men in electronics who are ambitious to improve their skills...who know that this will require more training. If we can attract you with the low price of our slide rule and course—and impress you with its quality—you are more

likely to consider CIE when you decide you could use more electronics training.

Send for free booklet. See for yourself why this amazing slide rule and course have made such a big hit with busy electronics men everywhere. No obligation, of course—just an opportunity to get in on the best offer ever made to people in electronics. Just mail coupon, or write Cleveland Institute of Electronics, Dept. PE-125, 1776 East 17th St., Cleveland, Ohio 44114.

CIE Cleveland Institute of Electronics
1776 East 17th Street, Cleveland, Ohio 44114

MAIL THIS COUPON FOR **FREE BOOKLET**

Cleveland Institute of Electronics
1776 East 17th Street Cleveland, Ohio 44114
Please send me without charge or obligation your booklet describing CIE Electronics Slide Rule and Instruction Course, **ALSO FREE** if I act at once: a handy pocket-size Electronics Data Guide.



Name _____ (please print)

Address _____

City _____ State _____ Zip _____



Accredited Member National Home Study Council
A Leader in Electronics Training...Since 1934

PE-125

CIRCLE NO. 13 ON READER SERVICE PAGE



NEW PRODUCTS

Additional information on products covered in this section is available from the manufacturers. Each new product is identified by a code number. To obtain further details on any of them, simply fill in and mail the coupon on page 15.

ELECTRONIC IGNITION SYSTEM

Attention: motorcycle owners. The Judson "Cycle-Tron" is a completely integrated electronic ignition system designed specifically for motorcycles. The output of the Cycle-Tron, unlike that of the standard coil ignition system, does not fall off as the speed of the engine increases. Providing positive ignition under all conditions at any speed, the Cycle-Tron enables improved performance, a smoother running engine, and quicker starting. Because there is less wear or erosion on ignition components, fewer tune-ups are required. Installation is simple and can be made on the average motorcycle in less than 30 minutes. The unit carries a 3-year warranty.



Circle No. 75 on Reader Service Page 15

STEREO TAPE RECORDER KIT

Considerable savings can be realized by a builder of the kit version of the professional Magnecord 1020 four-track stereo tape recorder being offered by the Heath Company. Total assembly time is about 25 hours; assembly



involves two circuit boards and mechanical mounting of the transport components. Included in the Model AD-16 kit are precut, prestripped, and marked connecting wires and shielded cables. Walnut cabinet is optional. With the AD-16, you can play back and record "live" from microphone or from auxiliary sources in four-track stereo or mono at either $7\frac{1}{2}$ or $3\frac{3}{4}$ in/s. It also has sound-on-sound, sound-with-sound (mixing), and echo capabilities.

Circle No. 76 on Reader Service Page 15

INSTANT-LOADING CARTRIDGE RECORDER

This three-pound, battery-powered cartridge recorder by Concord Electronics, Model F-100, plays or records for a full hour on one snap-in cartridge, then shuts off automatically. The C-60 cartridge, interchangeable with those of most better quality cartridge recorders now on the market, snaps into place instantly. Tape speed is 17½ in/s; frequency response, 60-10,000 hertz. The F-100's compact size (3" x 5" x 8"), light weight, and rugged construction make it useful for travelers—in automobiles, aircraft, or other moving vehicles. Accessories include a remote control microphone, microphone stand and pouch, two patch cords, and a carrying strap.



Circle No. 77 on Reader Service Page 15

5" WIDE-BAND OSCILLOSCOPE

The Model 315A high-sensitivity 5-MHz 5" oscilloscope announced by Precise Electronics is intended for audio and industrial testing as well as for TV servicing (both black-and-white and color). The "Green Line" panel-controls layout makes for increased efficiency and ease of operation on the part of the user. Some of the 315A's features: vertical response to 5 MHz with 10 mV r.m.s./cm. sensitivity; three-step frequency-compensated vertical attenuator with separate stepless control; two-stage push-pull vertical amplifier plus cathode-follower input; panel-mounted astigmatism control; drift-free positioning control; and fully automatic sync.



Circle No. 78 on Reader Service Page 15

COMMUNICATIONS RECEIVER

Hallicrafters' Model S-210 six-band receiver includes the AM and FM broadcast bands plus the 49-, 31-, 25- and 19-meter short-wave bands. "Spread" tuning (the spreading apart of distant stations electronically) permits the listener to zero in on short-wave stations with local-station ease and precision. On the front panel are band selector/a.f.c., tuning, on-off volume, and tone controls. The metal cabinet is covered in walnut-colored vinyl with wood grain inlay trim.

Circle No. 79 on Reader Service Page 15

CARBON MICROPHONE

Available both in kit form and as a completed unit, the Dart M-100 carbon mike put out by



Introducing EICO's New "Cortina Series"!

Today's electro-technology makes possible near-perfect stereo at moderate manufacturing cost: that's the design concept behind the new EICO "Cortina" all solid-state stereo components. All are 100% professional, conveniently compact (3 1/8"H, 12"W, 8"D), in an esthetically striking "low silhouette." Yes, you can pay more for high quality stereo. But now there's no need to. The refinements will be marginal and probably inaudible. Each is **\$89.95 kit, \$119.95 wired.**

Model 3070 All-Silicon Solid-State 70-Watt Stereo

Amplifier: Distortionless, natural sound with unrestricted bass and perfect transient response (no inter-stage or output transformers); complete input, filter and control facilities; failure-proof rugged all-silicon transistor circuitry.

Model 3200 Solid-State FM/MPX Automatic Stereo Tuner: Driftless, noiseless performance; 2.4µV for 30db quieting; RF, IF, MX are pre-wired and pre-tuned on printed circuit boards — you wire only non-critical power supply.

7 New Ways to make Electronics more Fun!

Save up to 50% with EICO Kits and Wired Equipment.



You hear all the top-ranked models of the world with the **NEW EICO 711 "Space Ranger" 4-Band Short Wave Communications Receiver** plus ham operators, ship-to-shore, aircraft, Coast Guard, and the full AM band, 550KC to 30MC in four bands; Selective, sensitive superhet, modern printed circuit board construction. Easy, fast pinpoint tuning; illuminated slide-rule dials, logging scale; "S" meter, electrical bandspread tuning, variable BFO for CW and SSB reception, automatic noise limiter, 4" speaker, Headphone jack. **Kit \$49.95. Wired \$69.95.**



More fun for your dollar than ever — with the one and only SSB/AM/CW 3-Band Transceiver kit, new **Model 753** — "the best ham transceiver buy for 1966" — Radio TV Experimenter Magazine. 200 watts PEP on 80, 40 and 20 meters. Receiver offset tuning, built-in VOX, high level dynamic ALC, silicon solid-state VFO. Unequaled performance, features and appearance. Sensationally priced at **\$189.95 kit, \$299.95 wired.**




NEW EICO 888 Solid-State Engine Analyzer

Now you can tune-up, trouble-shoot and test your own car or boat.

Keep your car or boat engine in tip-top shape with this completely portable, self-contained, self-powered universal engine analyzer. Completely tests your total ignition/electrical system. The first time you use it — just to tune for peak performance — it'll have paid for itself. (No tune-up charges, better gas consumption, longer wear) 7 instruments in one, the EICO 888 does all these for 6V and 12V systems; 4, 6 & 8 cylinder engines.

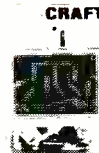The EICO 888 comes complete with a comprehensive Tune-up and Trouble-shooting Manual including RPM and Dwell angle for over 40 models of American and Foreign cars. The **Model 888** is an outstanding value at **\$44.95 kit, \$59.95 wired.**



New EICOCRAFT easy-to-build solid state electronic TruKits — great for beginners and sophisticates alike. As professional as the standard EICO line — only the complexity is reduced to make kit-building faster, easier, lower cost. Features: pre-drilled, copper-plated etched printed circuit boards; finest parts; step-by-step instructions; no technical experience needed — just soldering iron and pliers. Choose from: Fire Alarm; Intercom; Burglar Alarm; Light Flasher; "Mystifier"; Siren; Code Oscillator; Metronome; Tremolo; Audio Power Amplifier; AC Power Supply. **From \$2.50 per kit.**

circuit boards; finest parts; step-by-step instructions; no technical experience needed — just soldering iron and pliers. Choose from: Fire Alarm; Intercom; Burglar Alarm; Light Flasher; "Mystifier"; Siren; Code Oscillator; Metronome; Tremolo; Audio Power Amplifier; AC Power Supply. **From \$2.50 per kit.**



There's more PUNCH in the new EICO "Sentinel-Pro" 23-channel Dual Conversion 5-watt CB Transceiver. New advanced Big-Reach "Range Plus" circuitry lengthens "talk-power" reach. Automatic noise limiter super-sensitizes for weak signals. "Finger Tip" antenna loading and transmitter tuning controls. 23 crystal-controlled transmit and receive channels — all crystals supplied. Rear-illuminated S/R/F meter. Transistorized 12VDC and 117VAC dual power supply. **Wired only, \$169.95. Positive-Negative Ground/Mobile Marine Modification kit (optional \$5.95).**



Model 460 Wideband Direct-Coupled 5" Oscilloscope. DC-4.5mc for color and B&W TV service and lab use. Push-pull DC vertical amp., bal. or unbal. input. Automatic sync limiter and amp. **\$99.95 kit, \$139.50 wired.**

FREE 1967 CATALOG

PE-10

EICO Electronic Instrument Co., Inc.
131-01 39th Ave., Flushing, N. Y. 11352

Send me **FREE** catalog describing the full EICO line of 200 best buys, and name of nearest dealer. I'm interested in:

- test equipment
- stereo/hi-fi
- automotive electronics
- ham radio
- Citizens Band radio

Name _____
Address _____
City _____
State _____ Zip _____



Model 232 Peak-to-Peak VTVM. A must for color or B&W TV and industrial use. 7 non-skip ranges on all 4 functions. With exclusive Uni-Probe. **\$29.95 kit, \$49.95 wired.**

CIRCLE NO. 16 ON READER SERVICE PAGE

PRODUCTS (Continued from page 22)

Semitronics Corp. is suitable for CB, ship-to-shore communications, intercoms, mobile radio, or for any other amateur or professional use. Each do-it-yourself kit comes complete with a schematic plus diagrams for using the mike. The Dart M-100 has an output impedance of 100 ohms, a sensitivity of -43 db = 3 db, and a frequency response from 300 to 3000 hertz. The exciting voltage is 6 volts at 50 mA.

Circle No. 80 on Reader Service Page 15

SIGNAL MONITOR

Said to perform with virtually any receiver on the market today, the *Heathkit SE-610* signal monitor visually displays both transmitted and received signal waveforms. It displays the actual signal envelopes or trapezoid patterns from ham radio transmitters and can be used with any transmitter from 160 to 6

meters. The comprehensive assembly manual includes procedures for displaying signals from 5-watt CB equipment, and also provides the ham or CB'er with characteristic waveforms for signal analysis—including SSB and RTTY.

meters. The comprehensive assembly manual includes procedures for displaying signals from 5-watt CB equipment, and also provides the ham or CB'er with characteristic waveforms for signal analysis—including SSB and RTTY.

Circle No. 81 on Reader Service Page 15

ADJUSTABLE WRENCH

A wrench that grips like a pair of pliers has been announced by *Neff Enterprises, Inc.* Called "GEAR-GRIP," it's available with three different jaw configurations; smooth "V" jaws, straight jaws, and "V" jaws with pipe teeth. The "V" jaw models have a capacity from 5/16" to 1" and the

straight jaw model from 0" to 15/16". Plier-like ratchet action is obtained—without removing the tool from the work—by simply relaxing your grip and allowing the jaws to slip around the work quickly to get a new grip.

straight jaw model from 0" to 15/16". Plier-like ratchet action is obtained—without removing the tool from the work—by simply relaxing your grip and allowing the jaws to slip around the work quickly to get a new grip.

Circle No. 82 on Reader Service Page 15

SOLID-STATE CB TRANSCEIVER

Crystal socket accessibility and solid-state switching are featured in the "Slimline 675" 10-channel, 5-watt CB transceiver introduced by the *Amphenol Corporation*. To add trans-

mitter and receiver crystals, you just remove three knobs and two shaft nuts from the front panel controls; the panel is then lifted away, exposing the backs of the crystal sockets and the channel indicator dial. Use of solid-state switching provides protection against accidental "no-load" and "front-end" burnout—there are no contacts to stick, short out, or corrode due to arcing. The receiver is a dual-conversion superhet, equipped with squelch control. Frequency stability is at least $\pm 0.005\%$ from -20°C to $+85^{\circ}\text{C}$. Average power output: 3.5 watts. Measuring only $2\frac{1}{2}'' \times 6\frac{1}{2}'' \times 9''$, the "Slimline 675" also boasts a built-in public address system.

Circle No. 83 on Reader Service Page 15

TWO-IN-ONE TUBE TESTER

Designed to perform professional-quality tests on receiving tubes and the latest type color and black-and-white TV picture tubes, the Model 115 tube tester being marketed by *Precise Electronics* offers many features previously found only in much higher priced instruments. It includes VTVM circuitry for grid circuit emission and gas tests on receiving tubes, and a unique 10-circuit switching design permits testing of all the new tube types that have elements with multiple pin connections. For TV picture tubes, the Model 115 has facilities for beam-current tests (rather than total cathode emission) and rejuvenation without danger of burnout. Weighing only 8 pounds, the "Green Line" tester is packaged in a rugged portable carrying case.




Circle No. 84 on Reader Service Page 15

STEREO TAPE RECORDER

Lafayette Radio Electronics has introduced the Model RK-815 four-track, three-speed, solid-state portable tape recorder which incorporates a heavy-duty, 5-position selector control (rewind, stop, run, pause, and fast forward). Other features include: four-track stereo/mono record/playback, 5-watt audio output, sound-with-sound, sound-on-sound, separate tone and volume controls for each channel, a stereo record/playback vu meter, and a 3-digit tape counter with

preset button. Frequency response is ± 3 db, 40-15,000 hertz at $7\frac{1}{2}$ in/s; -3 db, 40-10,000 hertz at 3" in/s. The RK-815 is mounted in a textured solid vinyl case.

Circle No. 85 on Reader Service Page 15

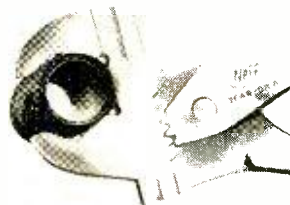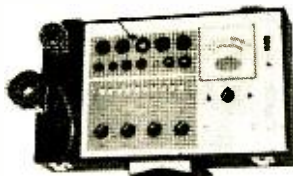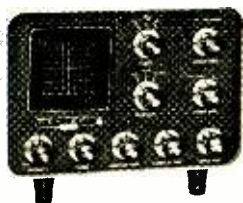

Build this famous *knight-kit*[®] Star Roamer[®] 5-Band Shortwave Receiver Kit



and have the whole wide world at your fingertips!

Think of it!—even if you know nothing at all about electronics—in a few fun-filled evenings you can assemble the Knight-Kit Star Roamer that lets you listen to the four corners of the world!

You visit the famous cities of Europe, Asia, Africa . . . get continuous 24-hour-a-day aviation weathercasts . . . zero-in on Coast Guard LORAN signals . . . get the exact time from station WWV in Washington, D. C. . . listen in on the interesting conversations of Hams, Citizens Banders and Radio Telephoners—AND listen to your favorite programs on the standard AM band, too.

Thousands of folks of all ages have assembled the Star Roamer and have been amazed at how easy it is. All you do is follow crystal-clear, non-technical instructions and extra-large illustrations that show where every part fits . . . and almost

before you know it you're listening to exciting broadcasts from all over the world!

The Star Roamer covers 200 to 400 kc and 550 kc to 30 mc in 5 bandswitched ranges, and features a reliable superhet circuit . . . plus Automatic Volume Control to prevent fading and blasting, illuminated "S" meter for fine tuning, and many other features found only in shortwave receivers that cost many times more.

Complete with all parts, handsome 5½ x 12¼ x 8" charcoal gray and aluminum case, and easy-to-follow assembly instructions for only

\$39⁹⁵

Read the unique money-back guarantee . . . exclusive in the industry . . . then rush coupon for full details and Special Introductory Offer.

KNIGHT-KIT GUARANTEE

Build a Knight-Kit in accordance with our easy-to-follow instructions. When you have completely assembled the kit, you must be satisfied or we will return your money, less transportation charges, under the Allied guarantee of satisfaction.

ALLIED RADIO

ALLIED RADIO, Knight-Kit., Dept. 3KK
P. O. Box 4398, Chicago, Ill. 60680

Please rush full details and Special Introductory Offer on the Knight-Kit Star Roamer 5-Band Shortwave Receiver.

Name _____ PLEASE PRINT
Address _____
City _____ State _____ Zip _____



When a crack electronics expert is needed fast, you're the guy they call.

Sometimes you feel like a country doctor with sixteen cases of measles in town.

But working on emergencies is nothing new to you.

You're the expert and emergencies are your job.

You're the one guy in the company that can practically field strip a computer and put

it back together again. Circuits are so pressed into your brain you can almost hear a short one. They make the TV's you repaired back in high school look like crystal sets.

If it wasn't for the electronic training you got in the Army, you'd still be a tube tester. But the Army opportunity came along and you took it.

A full-dress, eight-hours-a-day, five-days-a-week school that taught you a skill you'll build a career on.

A solid career that can mean sound security all your life.

There's nothing like being an expert. That's what you can be in today's action

Army

ELECTRONICS LIBRARY

CREATIVE ELECTRONICS FABRICATION

by Owen G. Patrick

How much pride do you take in projects built from plans in POPULAR ELECTRONICS? When you have a project working to your satisfaction, do you show it off? Or is it operative but ugly? Psychologists tell us that a handsome project always "works" better. Using some simple and some not-so-simple construction techniques, Owen G. Patrick designs and "builds" a signal tracer in this book; and when the unit is finished, it's a beauty. *Creative Electronics Fabrication* tells you how to work with metal chassis, boxes, and cabinets for best results. The information is practical and well presented.

Published by Holt, Rinehart and Winston, Inc., 383 Madison Ave., New York, N.Y. 10017. Hard cover. 258 pages. \$6.50.

SERVICING TRANSISTOR TV

by Robert G. Middleton

Transistorized television receivers are being marketed in an ever-increasing volume, and heretofore little practical servicing information on transistor TV circuits has been available. Bob Middleton has organized this service guide so that it will be useful for quick reference to a particular section when a particular set of trouble symptoms is encountered. The book is divided into the various receiver sections and subdivided according to symptoms. Most of the possible causes for each symptom are listed, and those troubles frequently encountered are analyzed.

Published by Howard W. Sams & Co., Inc., 4300 W. 62 St., Indianapolis, Ind. 46206. Soft cover. 223 pages. \$3.95.

TRANSISTOR CIRCUIT ANALYSIS AND DESIGN, Second Edition

by Franklin C. Fitchen

Intended as an electronics course for electrical engineering students, this book will also prove useful to the practicing engineer—who will find the analysis and design examples helpful as background for the solution of specific problems. Vast changes in the characteristics of available devices sparked the revision of this text. Also, this edition is larger than its predecessor. Several advanced design techniques are described, and ties between semiconductor physics and device characteristics have been made stronger.

Published by D. Van Nostrand Company, Inc., 120 Alexander St., Princeton, N.J. Hard cover. 412 pages. \$8.50.

—30—



How you can become an expert in today's action Army.

Your first step should be towards your Army Recruiting Sergeant. He has all the facts on more than 300 courses open to you. You'll get the course you select guaranteed in writing *before* you enlist. And there's no obligation until you enlist.

Call him today. He's in the phone book listed under U.S. Government.

Meantime, get a colorful, exciting 40-page booklet about Army life and Army opportunities. Simply fill out and mail this coupon. There's no obligation.

Army

FE 10-66

OPPORTUNITIES
Box 1041
Mt. Pleasant, Iowa 52641

Please rush me your 40-page booklet,
"The Secret of Getting Ahead."

NAME _____

ADDRESS _____

CITY _____

STATE _____

ZIP CODE _____

PHONE _____

EDUCATION _____ AGE _____

CIRCLE NO. 50 ON READER SERVICE PAGE

Weller® SOLDERING GUN KITS



for the
homecrafter who's aiming
at **PERFECTION**

Get fast professional results on hobbies and home-repair jobs with the guns preferred by electronics manufacturers. Just squeeze the trigger and you get instant high or extra-high heat plus prefocused spotlight. Get the one you want from your hardware dealer:

Weller Heavy-Duty Dual-Heat Soldering Gun Kit Features Weller heavy-duty 240/325 watt dual-heat gun with twin spotlights plus extra cutting and smoothing tips (for thermoplastics, tile, etc.) tip-changing wrench, 60/40 rosin core solder and "Soldering Tips" manual—all contained in rugged plastic case. (Gun **\$12.95** alone is \$8.95.) Kit Model D-550 PK only: **list**

Weller Dual-Heat Soldering Gun Kit Includes 100/140 dual-heat gun with single spotlight, three copper soldering tips, wrench, flux brush, soldering aid tool, 60/40 rosin core solder and "Soldering Tips" manual in plastic case. **\$8.95** (Gun alone is \$6.95.) Kit Model 8200PK **list**

WELLER ELECTRIC CORP., Easton, Pa.
WORLD LEADER IN SOLDERING TECHNOLOGY
CIRCLE NO. 53 ON READER SERVICE PAGE

NEW LITERATURE

To obtain a copy of any of the catalogs or leaflets described below, simply fill in and mail the coupon on page 15.

Everything in electronics for home, industry, and laboratory is claimed for the contents of *Lafayette Radio's* 1967 catalog, No. 670. Consisting of 512 pages, it covers stereo hi-fi, CB, and ham gear, test equipment, radios, TV's and accessories, auto accessories, etc. As usual, all major manufacturers are represented, plus Lafayette's own components.

Circle No. 86 on Reader Service Page 15

Regency Electronics has produced a 16-page booklet that explains how the Regency solid-state "Tone Program System" enables firemen to turn out within five seconds after receiving an emergency call. The booklet, which tells how tone alerting works for small, medium, and large emergency units, is offered free to fire chiefs, civil defense directors, fire equipment distributors, and municipal officials.

Circle No. 87 on Reader Service Page 15

"Barry's Green Sheet," a new catalog released by *Barry Electronics Corp.*, covers tubes, semiconductors, transformers, chokes, meters, wire, and test equipment, together with other components and equipment. The catalog is said to be unusual in that it contains many hard-to-find and unique items available at tremendous savings.

Circle No. 88 on Reader Service Page 15

A 12-page, two-color catalog on "G," "M" and other series panel meters—including a 1½" edgewise meter for use where panel space is at a premium—is being offered by the *Triplet Electrical Instrument Company*. The "G" Series meters, which come in a variety of sizes and shapes, feature flexibility and interchangeability and are equipped with the Triplet BAR-RING magnet and one-piece die-cast frame.

Circle No. 89 on Reader Service Page 15


All U.S. Signal Corps technical manuals that are available from *Quaker Electronics* are listed in an 8-page booklet. The manuals are either new or like-new. Also available, and included in the listing, are instruction books and other material pertaining to Signal Corps equipment.

Circle No. 90 on Reader Service Page 15


POPULAR ELECTRONICS

The ideal base/mobile combination for CB radio

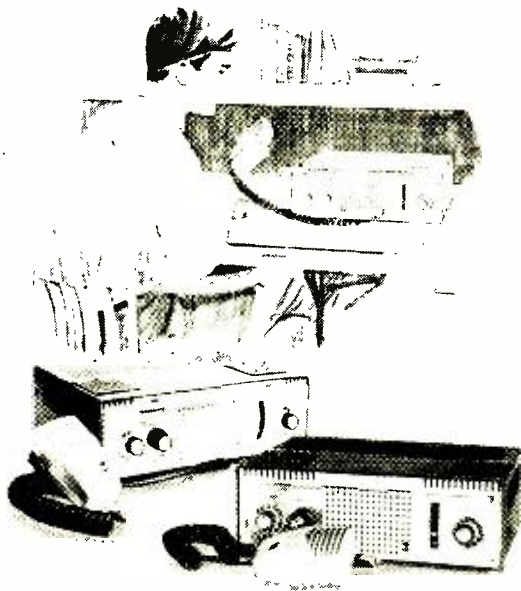FOR BASE STATIONS where
117 V 60 cycle AC current is available...



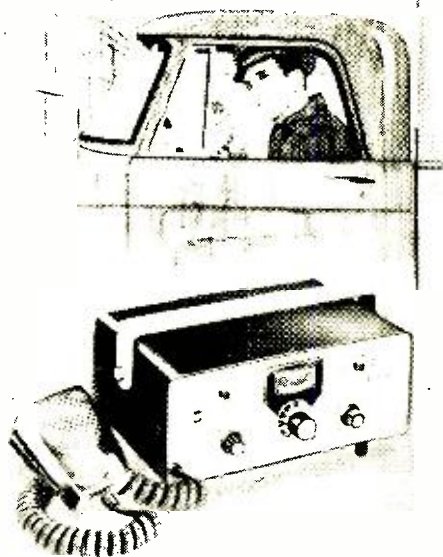FOR MOBILE UNITS where low
power consumption is important...



The Low-Cost RCA Mark VIII and Mark NINE

- 9 crystal-controlled transmit and receive channels.
- Tunable receiver for reception of 23 C-B channels; dial marked in both channel numbers and frequency.
- Exceptionally good voice reproduction.
- Highly selective superheterodyne receiver with one RF and two IF amplifier stages.
- Electronic switching—no relay noise or chatter.
- Illuminated "working channel" feature.
- Light and compact—only 3 3/4 inches high, weighs only 9 pounds with mike.
- Improved Automatic Noise Limiter.

Plus these EXTRA features in the Mark NINE

- Combination "S" Meter and relative RF Output Meter indicates the relative strength of incoming signal and Relative RF Output Meter indicates relative strength of signal being transmitted.
- Spotting Switch. Permits precise manual tuning of receiver without use of receiver crystals.
- External Speaker Jack. Lets you connect an external speaker to set, so that incoming calls can be heard in remote locations.

Mark VIII: \$99.95*

Mark NINE: \$114.50*

The all-solid-state MARK 10

- All silicon transistors assure low power consumption, dependable communications at temperatures from -23° to +130° F.
- Compact, lightweight. Fits easily under dash of any car or truck. Only 3 3/4" high, 5 3/4" deep, 8 1/2" wide. Weighs less than 4 1/2 pounds.
- 12 crystal-controlled transmit and receive channels with illuminated channel selector.
- Combination "S" Meter and relative RF Output Meter.
- Operates from 12-volts DC power source (positive or negative ground).
- Crystal-controlled double conversion, superheterodyne receiver provides frequency accuracies greater than 0.004%.
- Separate AGC amplifier eliminates blasting and overloading, minimizes fading.
- Six-stage IF bandpass filter for maximum selectivity without ringing.
- Low-distortion, series-type noise limiter with automatic threshold adjustment.
- Receiver power regulated for maximum stability.
- Acoustically designed cabinet with audio characteristics shaped for maximum intelligibility.
- External speaker jack (de-activates internal speaker).

Mark 10: \$189.95*

*Optional distributor resale price.

See them at your Authorized
RCA CB Radio Distributor.
Look for stores
displaying this symbol.



RCA ELECTRONIC COMPONENTS AND DEVICES, HARRISON, N. J.

The Most Trusted Name in Electronics

© CIRCLE NO. 38 ON READER SERVICE PAGE

www.americanradiohistory.com

Incomparable Excellence



The Super-Sharp TRAM TITAN CITIZENS BAND BASE STATION

*Multi-function meter reads: "S" units, SWR, and absolute power in watts into built-in dummy load. Measures power through the antenna.

*Super-sharp selectivity with Collins mechanical filter—adjacent channel rejection is 90 db or better. *First class sensitivity. *All 23 transmit channels.

*Transmitter delivers 3.5 watts minimum output; separate indicators for carrier on and modulation. *RF gain control.


*Tone control. *Built-in low pass filter for minimum T.V.I. \$434.

For full details write:

Tram Electronics, Inc.
Dept. No. E-10, Lower Bay Road P.O. Box 187
Winnisquam, N. H. Phone 603-524-0622

All use must conform with Part 95 F.C.C. regulations. Hobby type communications or aimless small talk prohibited.

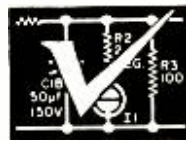For information write directly to advertiser



OPERATION ASSIST

Through this column we try to make it possible for readers needing information on outdated, obscure, and unusual radio-electronics gear to get help from other P.E. readers. Here's how it works: Check the list below. If you can help anyone with a schematic or other information, write him directly—he'll appreciate it. If you need help, send a postcard to Operation Assist, POPULAR ELECTRONICS, One Park Avenue, New York, N.Y. 10016. Give maker's name, model number, year of manufacture, bands covered, tubes used, etc. State specifically what you want, i.e., schematic, source for parts, etc. Be sure to print or type everything legibly, including your name and address. Because we get so many inquiries, none of them can be acknowledged. POPULAR ELECTRONICS reserves the right to publish only those items not available from normal sources.

Pierson KE-93 receiver with "Vipak" unit; tunes BC; has 12 tubes. Schematic and operating manual needed. (Carl Grahn, 14801 Sunset Ave., Oak Forest, Ill. 60152)

Philco Model 37-650 receiver; tunes BC and s.w. on 3 bands; has 8 tubes. Schematic needed. (Dale Carlow, W. Pembroke P.O., Charlotte, Me.)

Stewart-Warner TRF receiver, ser. 14761, circa 1928; tunes BC; has 5 01A's. Schematic and source for tubes needed. (James Royer, R. R. 3, Colliwater, Mich.)

Weston Model 661 capacity meter. Operating manual needed. (Edward J. Lamanski, 75 Palisade Ave., Bogota, N.J. 07603)

RCA Model K 80 receiver; tunes BC and 2 s.w. bands; has 7 tubes. Dial face needed. (W. Paul Chamberlain, 2417 Kenwood Rd., Bakerfield, Calif. 93306)

American Bosch Model 610 receiver; tunes 550 to 16,000 kHz on 3 bands; has 6 tubes. Schematic needed. (Benny Bigasol, 859 Commercial Ave., Apt. 1, S. San Francisco, Calif. 94080)

Motorola TV receiver, ser. 242037, circa 1948; has 23 tubes and 12" picture tube. **Hallicrafters** Model S-20R receiver, circa 1942; tunes s.w. on 4 bands; has 9 tubes. Schematics and parts lists needed. **American** receiver, ser. 25-112265, circa 1938; tunes 550 kHz to 90.5 MHz on 2 bands; has 5 tubes. Schematic, parts list, filter choke, and source for L-49-C tube needed. (Dennie Egan, 210 Highland Oaks Dr., Los Gatos, Calif. 95030)

R.M.E. Model 4350 receiver, circa 1957. Schematic and operating manual needed. (Mike Czuhajewski, RFD 3, Paw Paw, Mich. 49079)

Capehart 17M3 radio/phonograph, ser. 65778. Schematic needed. (Robert L. Tumpkin, 8036 Brush, Detroit, Mich.)

E. H. Scott SLR-H receiver, ser. 3705; tunes 0.53 to 15.6 MHz on 2 bands; has 11 tubes. (Raymond L. Stone, 2172 Marshall Ave., Napa, Calif. 94558)

Hallicrafters S-106 receiver. Schematic needed. **Garod** crystal calibrator and monitor, surplus, CGQ-60133, circa 1945. Parts list needed. (Kenneth J. Romm, 6520 W. 82 St., Los Angeles, Calif. 90045)

L. W. Electronic Lab. LW-51 transmitter; 6 meters. Schematic, parts list, and tune-up procedure wanted. (William M. McDonald, 19 Sargent St., Lawrence, Mass. 01841)

Silvertone receiver, circa 1914; tunes 550 kHz to 18 MHz on 3 bands; has 8 tubes. Schematic needed. (J. E. Christian, 2623 Shelby, Apt. 136, Dallas, Tex. 75219)

(Continued on page 32)

If You Service Citizens Radio Transceivers ...

you should have

AN INTERNATIONAL

C-12B

FREQUENCY METER

Four Instruments In One

The C-12B is more than a frequency standard — it measures power output, measures AM modulation, and is a signal generator . . . all self contained in one convenient unit.

check these features!

- **Frequency Measurement** — Range 26.965 mc to 27.255 mc. Frequency stability $\pm .0025\%$ 32°F to 125 F; $\pm .0015\%$ 50°F to 100°F.
- **Power Measurement** — 0 to 5 watts, accuracy $\pm \frac{1}{4}$ watt.
- **Counter Circuit** — Frequency range 0 to 3 kc. Residual error 100 CPS @ zero beat.
- **AM Modulation Measurement** — Range 0 to 100%. Accuracy 3% @ 400 CPS @ 80% modulation.
- **Signal Generator** — Frequency range 26.965 mc to 27.255 mc. Low output 1 microvolt through special pick-off box furnished with meter. High output 100 microvolts through output jack.


- **Panel Controls** — Channel selector, 24 positions • "Hi-Lo" frequency adjust • RF level control • Modulation set • Power • Meter calibration adjust • Function selector, 7 positions • Modulation • RF • Deviation • Calibration • Battery Test "A" • Battery Test "B" • Battery Test "C".

- **Battery Power Required** — 1½ vdc @ 60 ma, 67½ vdc @ 5 ma, 9 vdc.

The C-12B is capable of holding 24 crystals and comes with 23 crystals installed. Everything you need including connecting cable, PK box, dummy load, and batteries.

Cat. No. 620-101 \$300.00

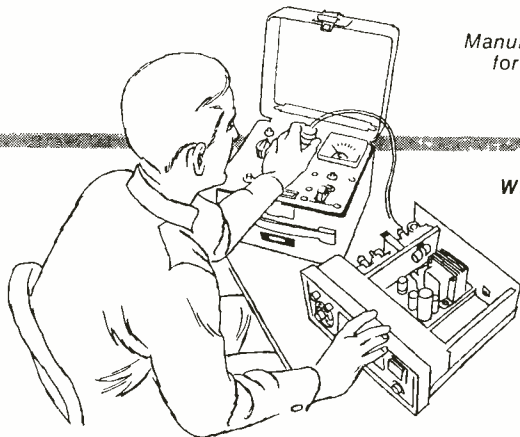Manufacturers of precision electronic products for home, industry and aerospace needs.



WRITE FOR COMPLETE CATALOG



CRYSTAL MFG. CO., INC.
18 NO LEE OKLA CITY, OKLA 73102

\$169.

Courier's 23-channel solid-state CB rig. Guaranteed for 10 years!



Look for everything you've ever wanted in a CB rig in Courier's TR-23S. Silicon-transistors throughout bring the size down to 5 $\frac{3}{4}$ " W x 6 $\frac{1}{4}$ " D x 1 $\frac{7}{8}$ " H. Crystals supplied for all 23 channels. Complete with microphone. Illuminated S meter. Illuminated channel selector. PA system. Auxiliary speaker jack. Single-knob tuning. Modulation indicator. DC cord. Exclusive Courier "Safety-Circuit" to protect against mismatched antenna, incorrect polarity, and overload. Plus the biggest guarantee in the business—10 full years!



COURIER COMMUNICATIONS, INC.

A Subsidiary of

e.c.i. electronics communications inc.

56 Hamilton Avenue, White Plains, N. Y.

Yes! I'd like to know all about the \$169
Courier TR-23S with the 10-year guarantee.

Name _____

Address _____

City _____ County _____ State _____

CIRCLE NO. 15 ON READER SERVICE PAGE

PE-610

ASSIST (Continued from page 30)

Atwater-Kent 55C receiver, ser. 4001709. Cabinet and source for parts needed. (Lorne E. Baker, Box 128, Mt. Pearl, Newfoundland, Canada)

Webcor 2030-1A tape recorder, circa 1953; has 5 tubes. Schematic and operating manual needed. (George Downes, Jr., Rt. 1, Magnolia, Ohio 41643)

TS-239/UP oscilloscope, surplus. Schematic needed. (S. P. Christian, 23653 Hazen, Southfield, Mich. 48075)

Garrard R.C. 98/4 record player. Record spindle needed. (Jeffrey Blumenfeld, Belmont Dr., Colonial Pk., Monticello, N.Y. 12701)

Rex UC-1 UHF/TV converter, circa 1953. Schematic and tube complement needed. (Russell Cox, Jr., 7195 E. Towntline Rd., Rt. 1, Bridgeport, Mich. 48722)

Western Electric D-153964 receiver, ser. 809, lot 3; has 8 tubes. Schematic needed. (C. Fred Mullins, 3258 Robert Pike, Springfield, Ohio)

VCR97 cathode-ray tube base connections needed. (Jerry Proc, 76 Barnesdale Ave. N., Hamilton, Ontario, Canada)

RBB-2 or **RBC-2** receiver, made by RCA, circa 1941; tunes 4 to 27 MHz on 4 bands. Schematic for receiver and power supply (RBA-1 or RBB-1 or RBC-1) needed. (Dick Atkinson, 1679 W. 15 St., Erie, Pa. 16505)

Triumph Model 335 VOM. Navy Dept. Model OCR-1, 1CTU 60143. Schematic needed. (Frank Keegan, 189-10 46 Ave., Flushing, N.Y. 11358)

CRV-46152 DZ-2 aircraft direction finder, ser. 365, made by RCA, 6/30/39. Loop assembly, loop assembly drive, and drawings needed. (Charles Lane, 5201 Roland Ave., Baltimore, Md. 21210)

Solar CE capacitor analyzer, type 1.60. **Sonar** Model CFC VFO. Operating manuals needed. (Dennis Dufour, 148 Clayton Dr., Norco, La. 70079)

Eicor Model 15 tape recorder. Schematic and source for parts needed. (W. F. Goepel, 265 Carol Rd., Stratford, Conn. 06497)

Eldico SSB-500 linear amplifier, circa 1956; 80 through 10 meters. Operating manual and schematic needed. (John Vanloon, Rt. 3, Lemont, Ill. 60439)

TCS-9 receiver, type COL-46159, made by Collins, ser. 250. Schematic and information on operation of "Osc. Selector" needed. (Ronnie Schmidt, 2611 Stratford Ct., San Antonio, Tex. 78223)

Harmon-Kardon Model A 250 "Epic" stereo amplifier; 25 watts; has 8 tubes, 3 transformers. Schematic and operating manual needed. (Steven Terry, 147 Columbia Heights, Brooklyn, N.Y. 11201)

Atwater Kent Models 9, 10, 12, 19, 20. Schematics needed. (Gerald Grulkey, 2801 Greenwood Dr., Richmond, Calif. 94806)

National NC-57 receiver, circa 1950; tunes 560 kHz to 31 MHz on 5 bands; has 9 tubes. First and second i.f. transformers and detector input transformer needed.

RCA Model 96T2 receiver; tunes BC and s.w. from 550 kHz to 18 MHz; 7 tubes. Schematic and speaker needed. (Robert M. Miller, 107 N. Long Dr., Rockingham, N.C. 28379)

Sears "Meteor" Model 6146 TV set, circa 1957; has 12 tubes and 21A1P4A picture tube. All available information wanted. (Philip Hodge, 5628 S. Harper, Chicago, Ill. 60637)

Montgomery Ward 62-451 receiver, series A2, circa 1936; has 11 tubes; tunes 528 kHz to 22.0 MHz on 4 bands. Schematic, parts list, and operating manual needed. (R. J. Gehring, 501 $\frac{1}{2}$ Humboldt Ave., Wausau, Wis. 54401)

Supreme Model 567 receiver, ser. 201. Wiring diagram needed. (Robert Sauve, Mont Sacré-Coeur, Granby, Quebec, Canada)

Knight C-27 CB transceiver. Construction manual needed. (E. C. Galland, William H. Carr Jr. H. S., 157 St. & 17 Ave., Whitestone, N.Y. 11357)

Polytronics PC-6 ("Polycomm 6") transceiver, ser. 82A120. Schematic and instruction manual needed. (Howard H. Halperin, 9712 S. Merrion Ave., Chicago, Ill. 60617)

Radio City Products 662-663 electronic multitester, circa 1948. Schematic and operating manual needed. (J. Flavin, 8809 W. 81 Terr., Overland Park, Kan.)

(Continued on page 38)

POPULAR ELECTRONICS

Technicians:

Keep learning while you earn.

IBM Customer Engineers learn every day. If you are qualified, you'll receive a training program with full pay. You'll be taught how to install and service IBM data processing equipment.

After that you will be given your own territory to handle. But you'll still keep learning. You will attend classes to keep you up-to-date on the latest in your field. IBM Customer Engineers spend more than a month each year in education programs.

It's a great way to learn a specialty. And you'll be preparing yourself for positions of greater responsibility in the fast-growing field of information handling and control.

If you have 2 years of technical school education (or equivalent experience), are handy with tools and know electronics, we'd like to see you. IBM is an Equal Opportunity Employer.

Please write, outlining your qualifications and interests, to Dept. 783X at any of the locations listed below:

W. S. Bedford, IBM Field Engineering
400 Wyman Street
Waltham, Mass. 02154

D. L. Potts, IBM Field Engineering
425 Park Avenue
New York, New York 10022

C. E. Farnham, IBM Field Engineering
66 Glen Avenue
Glen Rock, New Jersey 07452

D. H. O'Neil, IBM Field Engineering
Seven Penn Center
Philadelphia, Pa. 19103

R. M. Baker, IBM Field Engineering
3833 North Fairfax Drive
Arlington, Virginia 22203

O. J. Agee, IBM Field Engineering
Room 240, 1371 Peachtree St., N.E.,
Atlanta, Georgia 30309

F. W. Garvin, IBM Field Engineering
20700 Greenfield Road
Oak Park, Michigan 48237

R. O. Berger, IBM Field Engineering
29 North Wacker Drive
Chicago, Illinois 60690

T. W. Dickey, IBM Field Engineering
6811 West 63rd Street
Shawnee Mission, Kan. 66201

R. L. Norton, IBM Field Engineering
2929 Cedar Springs Road
Dallas, Texas 75219

L. A. McWilliams, IBM Field Engineering
9045 Lincoln Boulevard
Los Angeles, Calif. 90045

C. G. Kruse, IBM Field Engineering
340 Market Street
San Francisco, Calif. 94119

IBM®

The background of the advertisement is a collage of various job advertisements for technicians. Visible text includes 'TECHNICIANS', 'APPLICANTS', 'MAINTENANCE TECHNICIANS', 'ELECTRONIC EQUIPMENT', 'APPLICANTS', 'RESEARCH TECHNICIANS', 'ELECTRONIC TECHNICIAN', 'TECHNICIAN PARTSMEN', and 'LOCAL TECHNICIANS'.

We're looking for the men who want these well paid jobs!

And RCA Home Training can help you qualify
Just mail card today for details

Thousands of well paid jobs for men skilled in electronics are unfilled now

RCA INSTITUTES CAN TRAIN YOU —AT HOME—AND HELP YOU QUALIFY FOR JOBS LIKE THESE!

Every Sunday—and most week days—you will find *The New York Times*, *The Houston Chronicle*, *The Los Angeles Times* and many, many other newspapers cram-full of ads like these. Actively seeking qualified men for jobs in electronics and related fields.

Many of the men who *could* qualify for these jobs—well paid jobs—that is, men with the aptitude and native interest to enjoy a career in electronics—are handicapped because for one reason or another they have not had the opportunity to train themselves for jobs like these.

NOW—THANKS TO RCA INSTITUTES HOME STUDY—YOU CAN TRAIN FOR A CAREER IN ELECTRONICS

Realizing that thousands of technical jobs—well paid jobs—in electronics are or will be available, RCA Institutes has done something positive about the problem. To help sincerely interested men to get started toward a well-paid electronics job, RCA offers an ideal home training program!

HOME STUDY CAN PROVIDE CAREER OPPORTUNITIES!

To help meet the need for qualified men in the electronics field, RCA Institutes has created a wide variety of Home Training Courses, all geared to a profitable, exciting electronics career in the shortest possible time. Included are exclusive "Career Programs" designed to train you quickly for the job you want! Your study program is supervised by RCA Institutes experts who work with you, help

guide you over any "rough spots" that may develop along the way.

OFF TO A FLYING START WITH AMAZING RCA "AUTOTEXT" METHOD

Each "Career Program" starts with the amazing "AUTOTEXT" Programmed Instruction Method—the new, faster way that's almost automatic! "AUTOTEXT" helps even those who have had trouble with conventional learning methods in the past. It is truly the "Space Age" way to learn everything you need to know with the least amount of time and effort.

RCA INSTITUTES ENGINEERED KITS SPEED YOUR PROGRESS

To speed you on your way to a successful electronics career, your "Career Program" will include a variety of RCA Institutes engineered kits at no extra cost—each complete in itself. As a bonus, you will also receive and build a valuable Oscilloscope. You'll get the new Programmed Electronics Breadboard for limitless experiments, including building a working signal generator and a fully transistorized superheterodyne AM receiver and Multimeter.

CHOOSE YOUR CAREER PROGRAM NOW

To get started today on the electronics career of your choice, look over this list of RCA Institutes "Career Programs", pick the one that appeals most to you, and check it off on the attached card:

- Television Servicing
- Telecommunications
- FCC License Preparation
- Automation Electronics
- Automatic Controls
- Digital Techniques
- Industrial Electronics
- Nuclear Instrumentation
- Solid State Electronics
- Electronics Drafting

To meet other specific needs, RCA Institutes also offers a wide variety of separate courses which may be taken separately from the "Career Programs". Those range from Electronics Fundamentals to Computer Programming. They are described in the material you receive.

ADVANCED TRAINING TOO

If you are already working in electronics or have some experience but want to move on up, you may start RCA Institutes training at an advanced level. No tedious repetition of work you already know!

UNIQUE TUITION PLAN

With RCA Institutes, you learn *at your own pace*, and you pay only as you learn. There are no long term contracts to sign . . . no staggering down-payments to lose if you decide to stop . . . no badgering bills. You pay for lessons only as you order them, and should you decide to interrupt your training at any point, you may do so and not owe one cent.

CLASSROOM TRAINING AVAILABLE

RCA Institutes Resident School is one of the largest schools of its kind in New York City with classroom and laboratory training available in day or evening sessions. Coeducational classes start four times a year. Just check "Classroom Training" on the attached card for more details.

FREE PLACEMENT SERVICE, TOO!

In recent years, 9 out of 10 Resident School students who used the Free Placement Service have been placed before or shortly after graduation. This service is now available to Home Study students.

SEND ATTACHED POSTAGE PAID CARD TODAY FOR COMPLETE INFORMATION. NO OBLIGATION FOR FREE BOOK AND DETAILS. NO SALESMAN WILL CALL.

RCA INSTITUTES, Inc., Dept. ZPE-06
350 West 4th Street,
New York, N. Y. 10014



The Most Trusted Name in Electronics

POPULAR SAMS BOOKS



ASSIST

(Continued from page 32)

USE THIS HANDY ORDER FORM

RECENTLY PUBLISHED! TIMELY!

- Building Your Amateur Radio Novice Station.** Exceptionally clear and complete construction details for building an inexpensive transmitter and receiver, plus accessory items. Will efficiently serve the General-Class ham as well. Order **ASP-1**, only **\$3.50**
- Computers Self-Taught Through Experiments.** Explains and demonstrates principles of computer operation through 28 simple, low-cost construction projects. Transistor use and individual computer operations are covered in detail. Full instructions given for each project. Order **CEB-1**, only **\$4.25**
- ABC's of Citizens Band Radio.** NEWLY REVISED & UPDATED. All you need to know about planning and setting up a CB 2-way radio system. Explains functions, principles, setup and operation, latest rules and regulations. Order **ACR-2**, **\$2.25**
- ABC's of Transistors.** NEWLY REVISED and FULLY UPDATED. Helps anyone understand the structure and function of the transistor. Explains not only what transistors are but how they operate. Describes basic transistor circuits and testing procedures. Order **TRA-2**, only **\$1.95**
- How To Read Schematic Diagrams.** Not only shows you how to read and interpret diagrams, but analyzes each component, its construction, and its circuit purpose and use. Order **RSD-1**, only **\$ 2.25**
- TV Servicing Guide.** Tells you how to apply proper trouble shooting procedures based on analysis of symptoms, illustrated by picture tube photos. Packed with troubleshooting and servicing hints. Order **SGS-1**, only **\$2.00**
- Color-TV Servicing Made Easy.** Full explanation of color principles, circuitry, setup adjustments, and servicing of all color-TV sets. Takes the mystery out of servicing color-TV. Order **CSL-1**, only **\$3.25**
- 101 Ways to Use Your VOM & VTVM.** Shows you how to get the most from these popular instruments, how to make required connections, how to test properly, how to evaluate results. Order **TEM-3**, only **\$2.00**
- Transistor Ignition Systems Handbook.** **IGS-2** **\$2.95**
- TV Tube Symptoms & Troubles.** **TVT-2** **1.95**
- Citizens Band Radio Handbook.** **CBH-2** **3.50**
- 2nd-Class Radiotelephone License Handbook.** **QAN-2** **4.75**
- Modern Dictionary of Electronics.** **DIC-2** **7.95**
- Handbook of Electronic Tables & Formulas.** **HTF-2** **3.95**
- Troubleshooting With the Oscilloscope.** **TOS-1** **2.50**
- Color TV Trouble Clues.** **COL-1** **1.95**
- Tube Substitution Handbook.** **TUB-9** **1.50**
- Solving TV Tough-Dogs.** **TDM-2** **3.25**

FAMOUS ABC'S BOOKS

- Short Wave Listening. **SWL-1**... \$1.95
- Lasers & Masers. **LAL-2**... 2.25
- Electronic Test Probs. **APG-1**... 2.25
- Computer Programming. **CPL-1**... 1.95
- Modern Radio. **ARS-2**... \$1.95
- Electronic Organs. **ECO-1**... 1.95
- Hi-Fi & Stereo. **HSF-1**... 1.95
- Tape Recording. **TAP-2**... 1.50

— HOWARD W. SAMS & CO., INC. —

Order from any Electronic Parts Distributor, or mail to Howard W. Sams & Co., Inc., Dept. PE-10 4300 W. 62nd St., Indianapolis, Ind. 46206

Send books checked above, \$ _____ enclosed.

Send FREE Sams Book Catalog.

Name _____

PLEASE PRINT

Address _____

City _____ State _____ Zip _____

CIRCLE NO. 41 ON READER SERVICE PAGE

Crosley Model 51 receiver. circa 1924. Schematic and source for tubes needed. (Ray Carino, 7855 S.W. 17 St., Miami, Fla. 33155)

BC624A receiver. surplus, part of 8CR 522 package. Schematic and operating manual needed. **Reiner Electronic Co.** Model OBL-2 oscillograph, surplus, ser. 375. Schematic, operating manual, information on probes, and conversion data needed. (Herman W. Frisch, 14602 S. Avis Ave., Lawndale, Calif. 90260)

Stromberg Carlson Model 410-M receiver. circa 1941; covers 3 bands; has 8 tubes. **Sparks-Withington** (Sparton) Model 36-6-SX, circa 1915; covers 6 bands; has 6 tubes. Schematics and source for parts needed. (Mark L. Miner, 610 Dellwood Ave., St. Simons Is., Ga. 31522)

Crosley Model 58 XA receiver: tunes 550 kHz to 22 MHz on 3 bands. Schematic and alignment data needed. (Harold Shuff, Jr., Box 774, Plevna, Kan. 67568)

RCA Model 1T receiver: tunes from 510 to 1720 kHz; has 4 tubes. Schematic, parts list, and specs for antenna needed. (L. M. Palladino, 318 W. Emerson St., Melrose, Mass.)

E. H. Scott "Philharmonic XXX" receiver. circa 1939; covers 6 bands; has 30 tubes. Schematic of power supply needed and service notes. (John Morrison, 30 Walnut Ave. E., Farmingdale, N. Y.)

E. H. Scott receiver, ser. M-257. circa 1934; tunes AM and s.w. on 4 bands; has 15 tubes. Wiring diagram and coil alignment procedure needed. (Pat Morgan, Box 1-16, Athens College, Athens, Ala.)

Hammarlund Model HQ-110X receiver: tunes from 540 kHz to 31 MHz. Operating manual needed. (Michael Jaworek, 28 Mapes Ave., Nutley, N.J. 07110)

Hallicrafters Model S-20-R receiver, ser. HA-29668: tunes 550 kHz to 22 MHz on 4 bands; has 9 tubes. **Fada Radio Corp.** Model 1007 audio signal generator, ser. 53; has 5 tubes. Schematics and alignment procedures needed. (Wilfredo L. Galimba, Pangasinan School of Arts and Trades, Lingayen, Philippines)

Crosley Model 173 receiver, ser. AGC A526956; has 6 tubes. Schematic needed. (Sam Casella, 2938 S. Juniper St., Philadelphia, Pa. 19118)

Knight-Kit Model T-50 transmitter; tunes from 80 through 10 meters. Schematic and operating manual needed. (John E. Evans, 12414 Rt. 4, Mechanicsburg, Ohio 13041)

Heath Model AR-3 receiver. circa 1956; tunes 550 kHz to 30 MHz on 4 bands; has 5 tubes. Source for parts and construction manual needed. (Ben H. Lane, Jr., 5012B Ave. C., Malmstrom AFB, Mont. 59401)

Triplett Model 1252 VTVM. Schematic, operating manual, and parts list needed. (Robert Macfarlane, Thayer Rd., Higganum, Conn. 06441)

Stewart-Warner Model 9001-G radio-phonograph combination; tunes BC and s.w. and from 9 through 12 meters; has 7 tubes. Schematic needed. (M. Hoffman, 7G Research Rd., Greenbelt, Md.)

Philips Model S143U receiver. circa 1947; tunes 150 kHz to 22 MHz on 3 bands; has 3 tubes. Schematic and service information needed. (A. Mandelkern, Katamonet, Block 21, Jerusalem, Israel)

Microtone mine detecting set (C), contract #DA-30-075-ENG-3036, surplus, circa 1954; has 8 tubes. Operating manual and transmit-receive head needed. (Neil Horowitz, 144-55 68 Dr., Flushing 67, N.Y.)

Hammarlund "Super-Pro 200" receiver. circa 1943; tunes 100 kHz to 20 MHz. Schematic and operating manual needed. (Aristotle Bouras, 1753 Cottage Grove Ave., San Mateo, Calif. 94401)

Heathkit Model GC-1 receiver. circa 1959; tunes 550 kHz to 32 MHz on 5 bands. Assembly manual needed. (Buford B. Banes, 3524-A Nevada St., Bell, Calif. 90201)

Supreme Model 570 signal generator, ser. 570 316. Schematic or operating manual needed. (Paul Wewe, 2215 New Tampa Hwy. #5, Lakeland, Fla. 33801)

Ampro Model 731 tape recorder. circa 1950; has 4 tubes. Schematic, operating manual, and source for replacement heads needed. (Scott Marovich, 2407 S. Rose St., Kalamazoo, Mich. 49001)

Radio Craft, any 1917 and 1948 copies wanted. (Jack Messenger, Glenwood, Minn.)

—30—

Amphenol's new 675 goes to pieces in twenty seconds



Amphenol Quality for only

\$179.95

No, the new Amphenol 675 doesn't fall apart. It's just that we've designed a set that makes crystal changing a snap.

Actually it's three pulls, two spins and a snap. Just pull off the three control knobs on 675's faceplate, spin off two lock washers under the knobs, and snap off the faceplate. Insert crystals in easily accessible front sockets. Reverse faceplate removal steps and you're back on the air.

See it soon at your local Amphenol Distributor. Or write to Amphenol, Box 134, Broadview, Illinois 60153

Other Amphenol 675 Features:

- ***Completely Solid State—Even T & R Switching***
- ***Build-In Double TVI Traps***
- ***P.A. and External Speaker Provisions***
- ***Illuminated Numbered Channel Indicator***
- ***Compact Size 2½ x 6½ x 9***



AMPHENOL

CIRCLE NO. 3 ON READER SERVICE PAGE

**A complete line of CB accessories for
all around operating convenience and
improved station performance from...**



JOHNSON



ANTENNA METER and CB MATCHBOX


Measure and correct high SWR from antenna-transmitter mismatch with two of the most important CB accessories ever offered. The Johnson Antenna Meter reads SWR up to 10:1. Inserts temporarily in feedline with two SO 239 coaxial connectors. The CB Matchbox corrects SWR up to 5:1 to proper match of 1:1 or less.

- Cat. No. 250-849 Antenna Meter \$14.95 NET
- Cat. No. 250-49 CB Matchbox \$15.95 NET

TONE ALERT SELECTIVE CALLING UNIT

Silence skip, noise and other distractions with the Johnson Tone Alert selective calling unit. Tone Alert silences your receiver until another tone alert station calls you. Red light and tone indicate when you are called. Simple, one-switch operation. For any Messenger (except "350") and most other tube-type CB units.

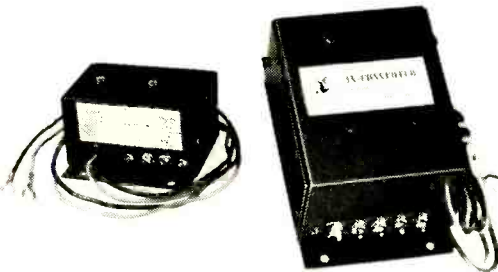- Cat. No. 250-810
Tone Alert for 6V filaments \$59.95 NET
- Cat. No. 250-811
Tone Alert for 12V filaments \$59.95 NET
- Cat. No. 250-819-1
Tone Alert Kit for Messenger I \$ 9.95 NET
- Cat. No. 250-819-2 Tone Alert Kit
for other manufacturers CB units \$ 7.75 NET
- Cat. No. 250-827 Tone Alert for
Messenger III and Messenger 100 \$69.95 NET



VOLTAGE REGULATOR and IN-CONVERTER

The Voltage Regulator and In-Converter are two of the handiest accessories to be made available to CB operators. Now you can convert any DC power source from 6 volts to 32 volts, regardless of polarity into a usable voltage for transistorized CB radios or other electronic equipment requiring 14 watts or less. The In-Converter converts 6 Volts DC to 12 or 18 . . . 12 Volts DC to 24 . . . and inverts polarity from positive to negative or negative to positive. The Voltage regulator converts any DC voltage in the range of 24-32 volts to 13 Volts DC. Compact size—installs anywhere.

- Cat. No. 239-120-1 In-Converter \$22.95 NET
- Cat. No. 239-119-1
Voltage Regulator (Pos. Grd.) \$14.95 NET
- Cat. No. 239-119-2
Voltage Regulator (Neg. Grd.) \$17.95 NET

**POWER
PACK**



Convert any transistorized Johnson Messenger into a full power hand-carried portable unit with the Power Pack. Uses rechargeable nickel-cadmium batteries for long life. Attaches to rear of Messenger. Adds only 2 lbs. to weight and 3" to length. Operates 8 hours or more between charges.

- Cat. No. 250-845-1
Power Pack Messenger III \$69.95 NET
- Cat. No. 250-854-1
Power Pack Messenger 100 \$69.95 NET
- Cat. No. 250-855-1
Power Pack Messenger 350 \$69.95 NET
- Cat. No. 250-846-1
Battery Charger for Power Pack \$17.50 NET

WRITE TODAY! for complete literature or see your **JOHNSON Distributor.**



The most reliable name in communications

E. F. JOHNSON COMPANY

2446 10th Ave. S W • Waseca, Minn 56093


CIRCLE NO. 26 ON READER SERVICE PAGE

BUILD Time-Signal-ONLY Receiver

EASILY DUPLICATED
TRANSISTORIZED RECEIVER
IS CRYSTAL-CONTROLLED
ON CHU OR WWV

By **CHARLES CARINGELLA**, W6NJV

COVER STORY

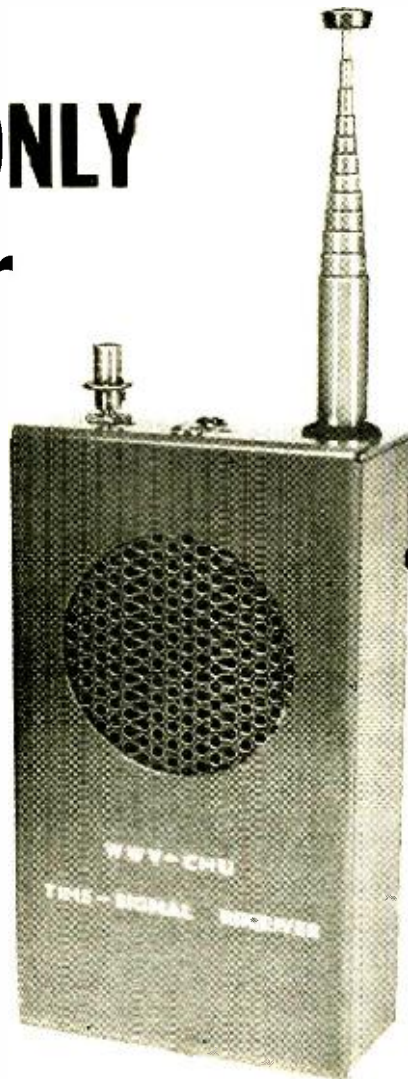

BUILD a portable time-signal receiver and you can tune in on standard time broadcasts from your living room, picnic table, boat, car, or even from a private plane. This miniature receiver is a complete superhet circuit with crystal-controlled local oscillator, prepackaged pretuned i.f. module, and *transformerless* audio amplifier. A printed circuit board makes it easy to build and only a screwdriver (no test equipment) is needed for alignment!

Standard time signals can be heard in almost every country in the world. In the United States, radio stations of the

National Bureau of Standards (all having the call-sign WWV) continuously transmit time signals on a number of frequencies. Besides accurate time-signal information, the transmissions also provide: standard radio frequencies, standard audio frequencies, standard musical pitch, standard time intervals, radio propagation forecasts, and geophysical alerts. This receiver can be used to monitor WWV on a frequency of 10 MHz or 15 MHz.

You can also use the time-signal receiver to tune in CHU, Ottawa, Canada, on a frequency of 7335 kHz, or on 14.670

MHz. The CHU time-signal broadcasts are very popular because of their voice-time announcements each *minute*. A short tone or "beep" is broadcast each second.

The model of the WWV-CHU receiver shown on the cover (a portable, crystal-controlled, 8-transistor receiver) can be built for a little less than thirty dollars. It has an r.f. amplifier, a mixer, a pre-aligned J. W. Miller i.f. amplifier, and a push-pull Class B audio output. Powered by an ordinary transistor radio battery, the receiver has a low power consumption and battery life is quite good.

The WWV-CHU receiver is portable and can be used anywhere. A telescoping, built-in whip antenna can be extended to 52 inches for increased signal pickup. The audio stage drives a built-in speaker. In a noisy environment, or for private listening, an earphone can be plugged into the jack provided for that purpose. Since the receiver is crystal-controlled, there is no need to tune for the station.


Sensitivity is excellent, being better than one microvolt for a S/N ratio of 10 dB, which compares favorably with the large multi-tube communications receivers. Although the circuit is fairly complex, the receiver is *easy* to build. There are *no* coils to be wound since pre-wound, molded r.f. chokes are used. The receiver is even *easier* to align. The only

piece of "equipment" needed for alignment is a screwdriver.


How It Works. The r.f. front end uses several new, low-cost, encapsulated, *npn* silicon transistors. Transistor *Q1* is the r.f. amplifier, and transistor *Q2* is the mixer. Coils *L1* and *L2* are prewound iron-core r.f. chokes and are specified as being either 10 μ H or 5.6 μ H. If 10- μ H chokes are used, then CHU on 7335 kHz or WWV on 10 MHz can be tuned. The 5.6- μ H chokes will enable the receiver to be tuned to three time-signal stations: WWV on 10 MHz, CHU on 14.670 MHz, or WWV on 15 MHz. Midget trimmer capacitors *C2* and *C6* tune or resonate the chokes to the respective frequencies. Transistor *Q3* is the local oscillator, which is crystal-controlled and "untuned." Fundamental crystals are used in this circuit.

The miniature i.f. module eliminates the need to build a separate i.f. amplifier. Within the module are two transistors, three i.f. 455-kHz transformers, a crystal diode detector stage, and miscellaneous decoupling capacitors.

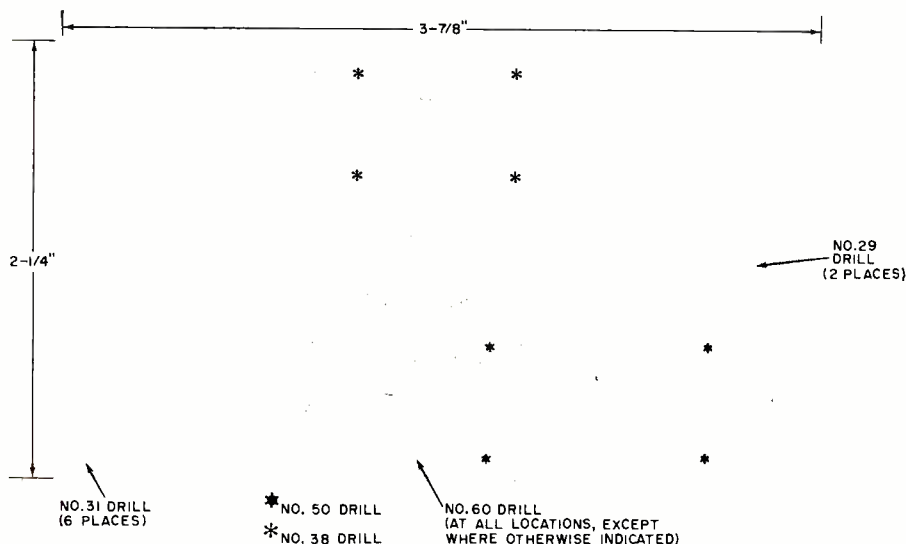The volume control is potentiometer *R12*. There are *no* transformers in the audio amplifier section so that cost and receiver weight are kept down. The audio preamplifier is *Q4*, a *pnp* germanium transistor. Transistors *Q5* and *Q6* operate push-pull Class B in a complementary-



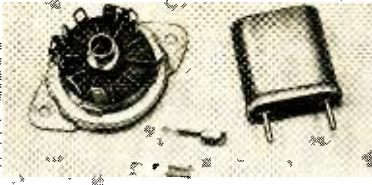Copper foil side of homemade printed circuit board should have the outline shown in the 1:1 drawing above. Holes to pass wire leads are drilled with a #60 drill. All other holes are drilled to the sizes indicated.



The edge-view drawing of the printed circuit board shows special preparation of the C2 and C6 soldering tabs. Shown in photo at left is method employed to obtain socket clips to hold the crystal. Use an expendable 9-pin socket.

MOUNTING PINS FOR THE XTAL ARE SALVAGED FROM 7 OR 9 PIN MINIATURE TUBE SOCKET. MAIN BODY OF PINS SHOULD PROTRUDE THRU CIRCUIT BOARD. BEND SOLDER TABS 90° AND SOLDER BACK SIDE OF CIRCUIT BOARD

BEFORE MOUNTING TRIMMER CAPACITORS, CUT AWAY SHADED PORTION OF SOLDER TAB




MOUNT ALL CAPACITORS FLUSH TO CIRCUIT BOARD

MOUNT RESISTORS AND RF COILS VERTICALLY

TRANSISTOR


BACK COVER

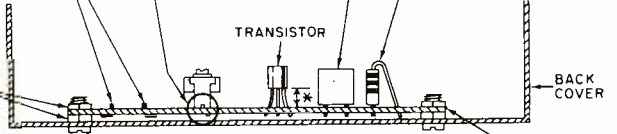



4-40 HEX NUTS (8 REQUIRED TO MOUNT CIRCUIT BOARD)

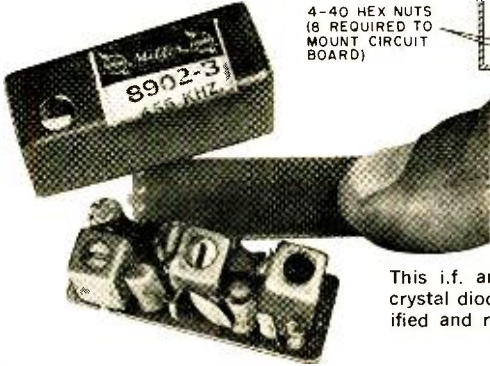4-40 X 3/8" SCREW (4 REQUIRED TO MOUNT CIRCUIT BOARD)

* MOUNT TRANSISTORS FROM 3/16" TO 1/4" AWAY FROM CIRCUIT BOARD




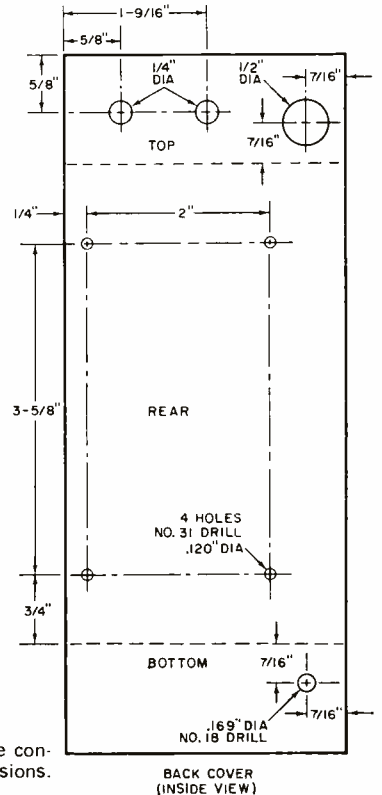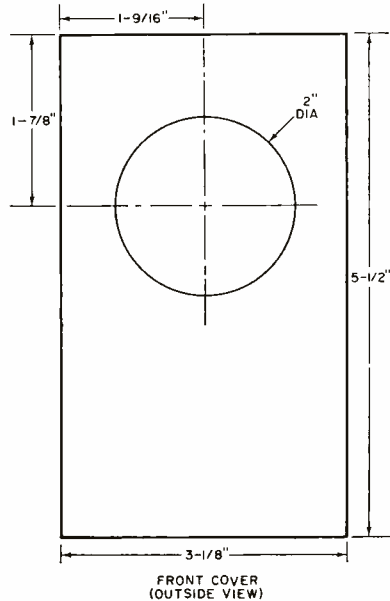This i.f. amplifier contains two transistors, three i.f. transformers, and crystal diode detector. Be sure to get the J. W. Miller Model 8902-B specified and not the older-style Model 8902 with outboard i.f. transformer.




If you purchase an LMB aluminum box No. 139, you can duplicate construction of the receiver shown on the cover using these dimensions.

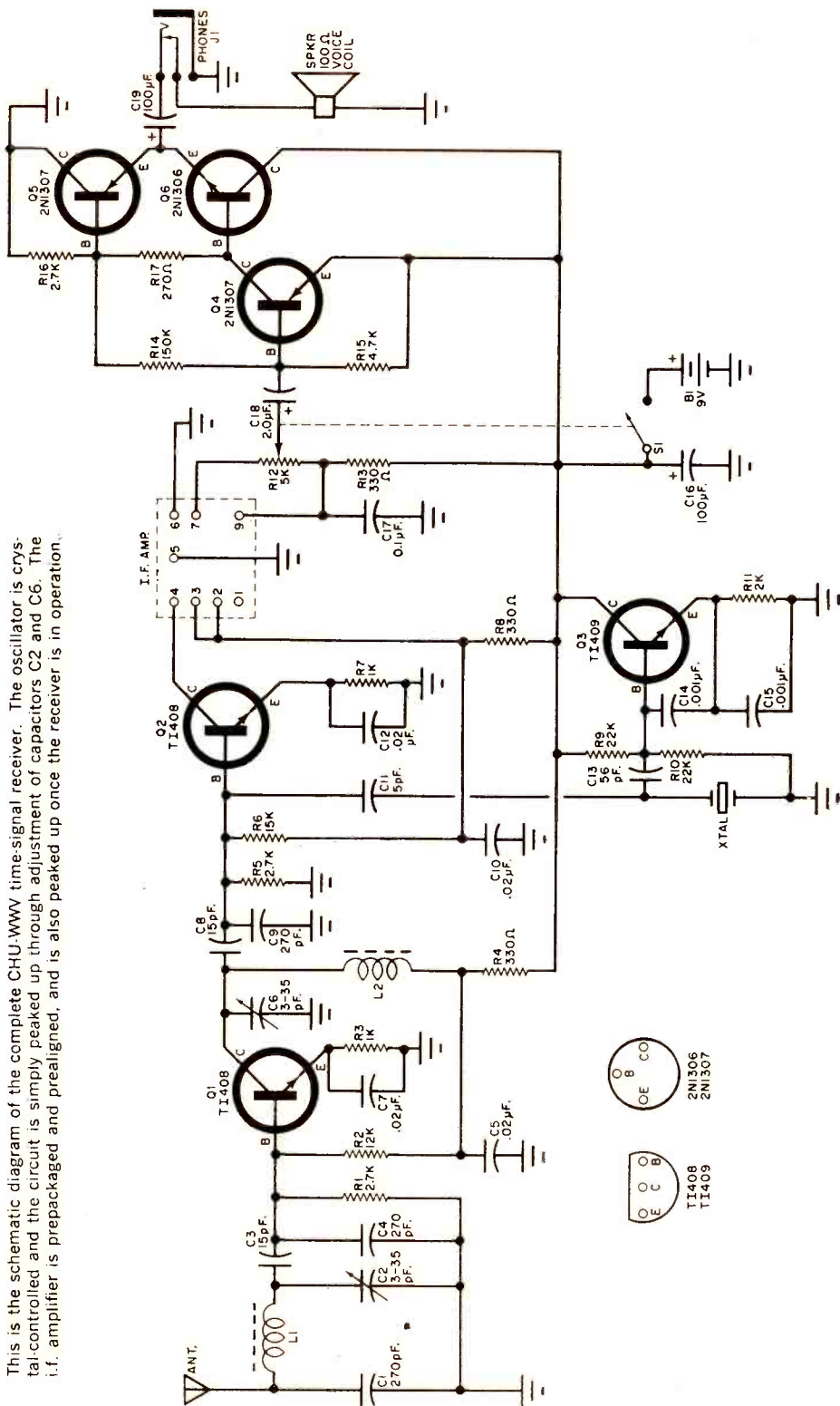This is the schematic diagram of the complete CHU-WWW time-signal receiver. The oscillator is crystal-controlled and the circuit is simply peaked up through adjustment of capacitors C2 and C6. The i.f. amplifier is prepackaged and prealigned, and is also peaked up once the receiver is in operation.



Use the layout of the top side of the printed circuit board shown below to spot the positions for the components in the wiring diagram above. Holes for the loud-speaker apply only if a Quam 2 1/4" PM speaker is installed in the space provided.

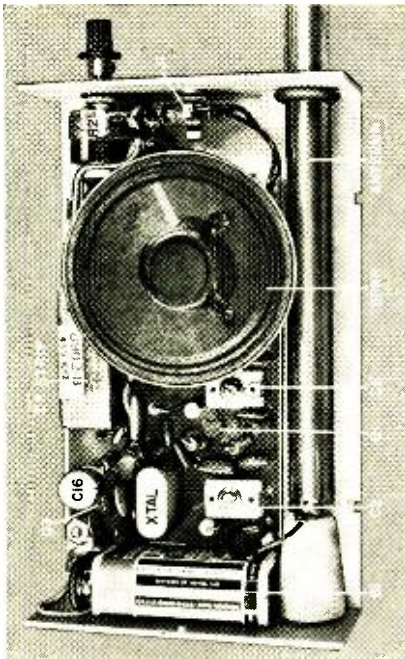Compare photo below with board layout at left. Speaker is now fastened to printed circuit board and the chassis cover with speaker cutout slips over U-shaped back cover seen in this photo.



symmetry configuration. A 100-ohm speaker is fed from the audio output stage through closed-circuit phone jack *J1*. When headphones are plugged into the phone jack, the speaker is automatically disabled. Any impedance headphone can be used. The audio output stage delivers over 50 milliwatts of power.

Construction. The entire time-signal receiver circuit is constructed on a printed circuit board measuring only 3 $\frac{3}{4}$ " x 2 $\frac{1}{4}$ " in size. A glass epoxy circuit board, etched and drilled, is available from the author (see Parts List).


Component mounting should follow that shown in the photo at left. All resistors are mounted vertically and all capacitors mounted as close to the printed circuit board as possible. Prior to mounting the miniature trimmer capacitors, *C2* and *C6*, cut the soldering tabs as shown on page 43.

Space limitations will not permit the use of a crystal socket on the printed circuit board. Instead, two socket pins salvaged from a 7- or 9-pin tube socket are soldered directly to the board. Once these have been soldered in place, also as shown on page 43, they serve as the "socket" for the crystal.

All of the transistors should be mounted approximately $\frac{1}{4}$ " away from the circuit board. Carefully observe correct placement of the "flat" side of transistors *Q1*, *Q2* and *Q3*. As usual in soldering transistors, keep the heat applied to the leads to a minimum, but consistent with a good connection.

The connecting leads to the circuit board (from *B1*, *J1*, *R12* and *S1*) should be approximately 2" long. These will be cut to the proper length once the circuit board has been installed in the chassis box. The speaker mounts directly on the printed circuit board where the holes are provided—it is installed last. Two 4-40 screws secure the speaker to the printed circuit board.

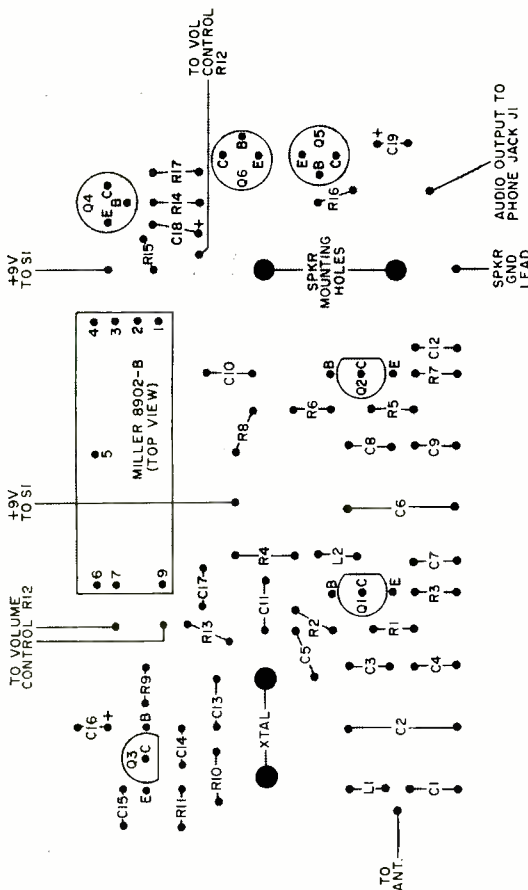Prepare the metal box by drilling the holes in the back cover and making the 2" cutout in the front cover (see drawing on p. 43). Cement a 2 $\frac{1}{2}$ " x 2 $\frac{1}{2}$ " piece of perforated sheet aluminum in back of the 2" cutout. Use epoxy cement for this step. If you wish, you can paint the perforated sheet before cementing it in place.



PARTS LIST

- B1—9-volt battery
 C1, C4, C9—270-pF, 500-volt, dipped silver mica capacitor
 C2, C6—3-35 pF, miniature trimmer capacitor (similar to Arco 403)
 C3, C8—15-pF, 500-volt, dipped silver mica capacitor
 C5, C7, C10, C12—0.02- μ F, 75-volt miniature ceramic capacitor (similar to Lafayette 33 R 6906)
 C11—5-pF, 500-volt, dipped silver mica capacitor
 C13—56-pF, 500-volt, dipped silver mica capacitor
 C14, C15—0.001- μ F, 75-volt, miniature ceramic capacitor (similar to Lafayette 33 R 6902)
 C16, C19—100- μ F, 12-volt, miniature printed circuit electrolytic capacitor (similar to Lafayette 99 R 6086)
 C17—0.1- μ F, 75-volt, miniature ceramic capacitor (similar to Lafayette 33 R 6908)
 C18—2.0- μ F, 6-volt, miniature printed circuit electrolytic capacitor (similar to Lafayette 99 R 6070)
 J1—Miniature closed-circuit phone jack
 L1, L2—10.0- μ H miniature iron core r.f. choke (similar to J.W. Miller 9310-36) or 5.6- μ H miniature iron core r.f. choke (similar to J.W. Miller 9310-30); to tune 7-10 MHz, use the 10.0- μ H chokes, and to tune 13-16 MHz, use the 5.6- μ H r.f. chokes*
 Q1, Q2—Npn low-cost silicon r.f. transistor (similar to Texas Instruments TI408, Semitronics T-33, etc.)
 Q3—Npn low-cost silicon r.f. transistor (similar to Texas Instruments TI409, Semitronics T-33, etc.)
 Q4, Q5—2N1307 germanium pnp transistor
 Q6—2N1306 germanium npn transistor
 R1, R5, R16—2700-ohm, $\frac{1}{2}$ -watt resistor
 R2—12,000-ohm, $\frac{1}{2}$ -watt resistor
 R3, R7—1000-ohm, $\frac{1}{2}$ -watt resistor
 R4, R8, R13—330-ohm, $\frac{1}{2}$ -watt resistor
 R6—15,000-ohm, $\frac{1}{2}$ -watt resistor
 R9, R10—22,000-ohm, $\frac{1}{2}$ -watt resistor
 R11—2000-ohm, $\frac{1}{2}$ -watt resistor
 R12—5000-ohm potentiometer with s.p.s.t. switch, $\frac{3}{4}$ "-diameter (similar to Lafayette 32 R 7363)
 R14—150,000-ohm, $\frac{1}{2}$ -watt resistor
 R15—4700-ohm, $\frac{1}{2}$ -watt resistor
 R17—270-ohm, $\frac{1}{2}$ -watt resistor
 S1—S.p.s.t. switch (on R12)
 SPKR—2 $\frac{1}{2}$ "-diameter P.M. speaker (similar to Quam 22A06Z100 for exact mounting on printed circuit board)
 XTAL—Fundamental frequency crystal, 0.01% tolerance, with HC/6U holder (similar to International Crystal Type FA-5); use 7790.0 kHz to receive CHU on 7335 kHz (\$3.30); use 9545.0 kHz to receive WWV on 10.0 MHz (\$3.30); use 14,215 kHz to receive CHU on 14,670 kHz (\$4.40); use 14,545 kHz to receive WWV on 15,000 kHz (\$4.40); any crystal available from International Crystal, 18 N. Lee, Oklahoma City, Okla. 73102 plus postage*
 I.F. AMP.—Subminiature, 2-transistor i.f. package (must be J.W. Miller 8902-B)*
 1—Printed circuit board (available from author with mounting hardware for \$2.50, postpaid)*
 1—5 $\frac{1}{2}$ " x 3" 1 $\frac{1}{4}$ " aluminum box (similar to LMB 139)
 1—Telescoping antenna; 52" fully extended, 5 $\frac{7}{8}$ " retracted; 8-32 stud at bottom (similar to Lafayette 99 R 3008)
 1—Steatite cone insulator (similar to E.F. Johnson 135-501)
 Misc.— $\frac{1}{2}$ " rubber grommet, battery clip, plastic knob for R12, wire, solder, etc.

*To assist in building the WWV-CHU receiver, the author has available a kit of parts containing the printed circuit board, i.f. strip, one crystal (your choice of frequency), and a set of matching r.f. chokes for \$13.50, postpaid. Write to Caringella, P.O. Box 327, Upland, Calif. 91786. California residents should add 4% sales tax.

Mount the telescoping whip antenna through a $\frac{1}{2}$ " rubber grommet in the hole in the top of the back cover. The bottom of the whip is held by a steatite insulator. The solder lug, provided with the antenna, should be installed between the bottom of the antenna and the top of the insulator. Next, install the volume control, R12, and the phone jack, J1.

The completed circuit board, with speaker installed, is mounted last. If you follow the layout provided in the drawings, the speaker will automatically line up directly behind the 2 $\frac{1}{2}$ " opening when the front cover is installed.

Place a solder lug under the 4-40 nut in the lower left-hand corner of the circuit board. The solder lug will thus serve as the ground point for the negative lead of the battery. Run the battery's positive lead along the underside of the circuit board and solder the end to switch S1.

Alignment and Operation. The completed receiver can be aligned with an "on the air" signal from WWV or CHU. Since the receiver's local oscillator is crystal-controlled, there is no need to "hunt" for the station.

Assuming propagation conditions will permit reception of the desired station at the time you select (see box entitled "Time Signal Broadcasts"), simply tune C2 and C6 for maximum station volume or background noise. Also, a slight "tweaking" of the input transformer in the i.f. strip might be necessary. A hole in the top of the i.f. module enclosure allows access to the input transformer tuning slug.

In most cases, the built-in antenna is all that is needed. However, it is possible to improve reception with a "long wire" antenna. An external antenna can be clipped to the top of the whip. The

(Continued on page 116)

Help

Help Wanted—Male

Cont'd From Preceding Page
ELECTRO-TECHNICAL

Not just a job...
A CAREER
is waiting for you

Engin.
Scien

an
Skilled
Immediat

Do you have good mechanical ability?
New York State's largest private employer has technical jobs available in radio, TV, transmitters and maintenance of equipment.

CAREERS IN ELECTRONICS

POPULAR ELECTRONICS ANALYZES THE JOB OPPORTUNITIES FOR ELECTRONICS TECHNICIANS

By KEN GILMORE

ELECTRONIC
Salary \$12,000
Preferably with 2 years experience using design and drafting equipment exp will be considered. Management for electronic in UPSTATE N.Y. area.
Aero-Base Technology
201-662-9147

ELECTRONIC TECH
Training prog for I-3 states mil. exp. to \$17,500
X-L AGENCY

TECHNICIAN
FIELD
EAST N. ELECTRON
SPERRY
Division of Great Lakes
An Equal Opportunity Employer

ENGINEER
Rochester, N. Y. 14620
An Equal Opportunity Employer

ELECTRONICS
An invitation to
ELECTRONICS TECHNICIANS

...with AAS degrees or equivalent (or 1-year of military electronics training) to attend...

NEW YORK INTERVIEWS

Wed. & Thurs., July 27-28
Phone 10 AM to 9 PM
Rochester, N. Y. 14620
LO 8-6886

ELECTRONICS
The key to a
challenging
future is in
"INTEGRATED
CIRCUITS"
Integrated Career
Opportunities
San Francisco
Bay Area
See our ad
in the
Business Pages

INTE
An ENGINEER degree...
try. Must...
position...
paper int...
electronic...
progressive...
You will...
ment res...
ty to top...
salary cc...
Send res...
The Fir...
Flint, M...
in strict...
ington...
ENGINE...
We're...
are...
to

FEW PEOPLE study electronics just to satisfy their curiosity. They do it to get jobs, establish a career, and fulfill a desire to improve their position in the community.

In the two previous parts of this series of articles^{1,2}, the discussion centered around the training of electronics technicians. The advantages and disadvantages of home study and resident schools were highlighted with particular emphasis placed on the time involved, tuition costs, types of study courses, etc.

But how about the payoff? What kind of job can you get once you've nailed your diploma to the wall? What do the companies who hire electronics technicians think of home-study and resident school graduates? What do they look for in a prospective employee? In other words, what's the best way to prepare yourself for a career in electronics?

To find out, POPULAR ELECTRONICS queried more than 150 manufacturers and service organizations—large and small—about their electronics technician hiring policies. Some 30 percent agreed to answer our questions in detail. And

¹ Resident Schools, September, 1965
² Correspondence Schools, February, 1966

HOME STUDY HAS A GREAT ADVANTAGE IN PREPARING YOU FOR A JOB IN RADIO/TV REPAIR WORK

from these answers, we have a good picture of how technician jobs are being filled.

Jobs for electronics technicians, we found, generally fall into three categories. Broadly speaking, they are: (1) the radio/TV service technician; (2) the broadcast-communications technician; and (3) the industrial engineering technician.

The Radio/TV Service Technician

A lot of guys make a good living these days repairing radios, television sets, hi-fi equipment, public address systems, and other electronic gear. The possibilities here for employment are wide open. Almost every school—home-study or residence—can give you bushels of case histories of graduates who have gone into radio/TV repair work, started their own shops, and are now running modestly prosperous businesses.

Scores of electronics schools can prepare you for such a career. Home-study schools offering this kind of training generally supply you with test equipment that you build from kits as part of your training, then use in your business when you complete the course. Some schools also supply lots of helpful advice about starting your own business.

Home study has a great advantage in preparing you for a job in radio/TV repair work: you can keep your regular job while learning to be a service technician at night. Of course, you can also attend a local residence school that offers night courses. Obviously, the home-study approach allows more flexibility: you move at your own pace. And interruptions—vacations or illness—won't in-

terfere with your study as they would if you were attending regularly scheduled classes.

As for getting a job in a radio/TV shop, it's equally easy for the resident school and home-study graduate. If you're a good man with a soldering iron, voltmeter, and scope, you won't have any trouble getting started. "We hire both home-study and resident school graduates," stated the employment manager of a very large service organization. "Some men go right to work on a direct-hire basis; others go into a training program that we conduct. We take men with varying amounts of education and start them off at whatever level their training qualifies them for."

Radio and TV servicing and repair technicians, like other craftsmen, are in short supply. "When we opened up service outlets some time ago," says the district service manager of a nationally advertised brand of electronic appliances, "it took us months to find enough men to staff them. It's always a struggle to get enough really good men."

Says the owner of a large repair service in Chicago, "I could use two or three good men right now if I could find them. But it's useless to advertise. All the answers are from *would-be* technicians. I need men with training—men who can walk up to the bench and go to work."

The color TV and CATV explosion has accentuated the demand for radio/TV servicing technicians. Color TV receivers need converging, and the majority of the receivers need good outdoor antennas. Both the home-study and resident schools have tooled up to offer good study courses in color TV.

Broadcast-Communications Technician

The first requirement for getting a job in this field is an FCC license—*First Class Radiotelephone* for AM, FM, or TV broadcast work; *Second Class Radiotelephone* for communications equipment servicing. You can get either license after either home-study or residence

DID YOU MISS THE PREVIOUS STORIES?

Readers who missed the earlier stories by Ken Gilmore on electronics training in resident schools and through home-study courses will be able to read them in the Fall Edition of the ELECTRONIC EXPERIMENTER'S HANDBOOK. This Handbook is now on sale at many newsstands—look for it.

"WE'VE ALWAYS GOT VACANCIES . . . WE CAN NEVER FIND ENOUGH QUALIFIED MEN"

school training. Many schools, in fact, guarantee that you will get a license if you stay with it. If you fail your FCC exam the first time, they'll give you additional instruction—and keep on giving it—until you have the price of admission to a good job: your FCC ticket.

If you choose the home-study route, you can always keep your present job while you study for your ticket. But whichever type of training you elect to undertake, you'll be qualified to apply for a job with a radio or television station or go to work in communications equipment installation and maintenance. "We get so many requests from radio and TV stations," says an executive of one home-study school, "that we can't list them in our monthly newsletter. When a graduate asks what jobs are open, we simply send him a list of those jobs available in his area, or whatever part of the country he wants to work in."

There's plenty of room for communications technicians these days: gas and electric companies, taxi fleets, forestry services, and many other organizations now have cars and trucks outfitted with two-way radio. Some communications technicians are specializing in the repair or maintenance of Citizens Radio Service transceivers—a paying field that didn't even exist eight years ago! And, of course, all airplanes are now radio-equipped and laden with plenty of sophisticated gear.

"We need people for computer repair and installation of communications gear," said one employment manager who regularly hires technicians from all over the country. "We don't expect a new man to know our particular equipment, but if that man has a good background in electronics, we'll hire him and train him to handle our gear." And, added this manager, his company routinely hires both home-study and residence school graduates.


Several large companies that hire technicians to work in communications told POPULAR ELECTRONICS that they hire strictly on the basis of electronics know-

how and couldn't care less *where* the applicants got their training. One Midwest employment manager indicated that he saw very few applications from home-study graduates! And he couldn't figure out why.

Industrial-Engineering Technician

Practically every phase of industry needs electronics technicians desperately. Every big electronics company seeks technicians to work with design engineers, to build and test prototypes of new equipment, to help figure out production-line techniques, to test, calibrate, and troubleshoot equipment, to work as service engineers and keep customers happy with their equipment.

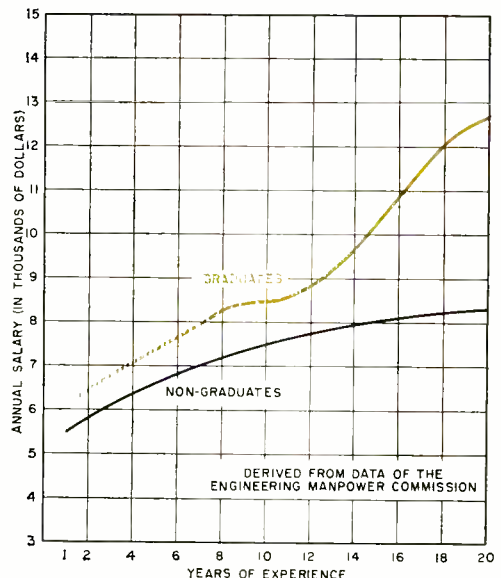"We've always got vacancies," said one employment manager. "We can never find enough qualified men." Adds an-



Comparative earnings of non-graduate technicians vs. technical institute graduates have been analyzed by the Engineering Manpower Commission of the Engineers Joint Council, Inc. The above graph was prepared from advance information released by the EMC prior to publication of its detailed study on the careers of nearly 35,000 technicians. Not only are starting salaries higher for the graduates, but earning power increases with on-the-job experience.

"I'LL HIRE ANY GRADUATE IF HIS KNOWLEDGE AND PRACTICAL ABILITY EQUALS THAT OF OTHER TRAINEES ..."

other employment manager who hires 100 electronics technicians a year: "We always need more skilled technicians, especially those who know something about digital computers and telemetry." "We have trouble finding people to work on microwave equipment," says a third one.

If you want one of these jobs as an industrial or engineering technician, you'll need more training than for either of the above careers. Furthermore, you'll find that when it comes to landing that job, you'll be on the inside track if you have some electronics job experience or if you got some training at a residence school. This employment attitude is slowly softening and more and more companies are looking at a man's ability rather than his method of training.

One employment manager who hires up to 25 school graduates a year as assembly, test, and calibration technicians put it this way: "I'll hire any graduate if his knowledge and practical ability equals that of other trainees we hire."

On-the-Job Experience

"We take all training with a grain of salt," says the personnel manager of an eastern electronics company, "whether it be a technical institute, college, home-study school, or service school. Our real interest is in a man's experience and in his desire to learn. Frankly," he adds, "our needs are for specialists in three areas: microwave, radar, and digital techniques. Generally we find that graduates of most schools—residence or home-study—don't know enough about any of these subjects for our purposes, usually having had only a course or two in each. So we hire them as trainees and offer them the opportunity to pick up enough knowledge on the job to become an associate engineer. For this reason, we look at each technician candidate individually; if a fellow projects a deep interest in electronics and a strong desire to learn, we feel that we can use him in our R&D atmosphere."

Another employer says he hires home-study graduates as trainees, but admits

that some have weaknesses. "They may have theoretical knowledge," he says, "but lab experience is becoming increasingly important. And that, they generally don't have." Consequently, this man adds, the home-study graduate does not generally begin at as high a salary level as the man who had the chance to handle laboratory-type equipment in a residence school.

One West Coast employment manager, doubtful about home-study graduates, gave this reason: "They consistently fail our *very tough* entrance examinations." Another employer, who said he rarely hired recent home-study graduates, added that he does hire them as soon as they have had on-the-job experience. "They lack experience in laboratory techniques," he remarked, "so we seldom hire them right out of school. But if they get some practical experience, then we find them satisfactory."

Our survey turned up several important points that home-study graduates should consider when looking for a job. The most critical is to try to get your first job with a big company. Practically every major organization hiring between 10 and 100 new electronics technicians per year have special "in-plant" training courses designed to take the graduate with a broad electronics background and make him into a specialist. The smaller companies that hire three to five technicians per year rarely have indoctrination courses. If a small company needs a technician, its officials expect to hire a man capable of going right to work the following morning. The moral is obvious: Don't let that biggest of the big companies scare you—it's the best place for a school graduate to start a career.

Need for Highly Trained Technicians

The strange attitude of a few companies toward most home-study graduates. POPULAR ELECTRONICS believes, grows out of three things. First, the emphasis these days is on the very highly trained electronics technician—the man who has

A BASIC ELECTRONICS COURSE WAS NEVER DESIGNED TO TRAIN A MAN TO BE A COMPUTER TECHNICIAN

had essentially the same technical education as a graduate electrical engineer! Such a man is also expected to have had practical experience with computers, servo systems, microwave technology, high-powered transmitters, and other complex, expensive equipment. This is what some graduates get in such outstanding technical schools as RCA Institutes, DeVry Technical Institute, Central Technical Institute, Milwaukee School of Engineering, Capitol Institute of Technology, and others.

A graduate of the best home-study courses offered by Cleveland Institute of Electronics, Capitol Radio Institute, National Radio Institute, National Technical Schools, and others may have covered essentially the same ground in theory. But, obviously, the home-study school cannot ship each student a transmitter, a computer, or any massive equipment to play with.

Second, 10-15 years ago home-study schools concentrated primarily on basic electronics and radio-TV repair. That situation has changed rapidly in the past decade, and the better home-study schools have gone far beyond this old concept. A few manufacturers, nevertheless, still think of "TV Repair" training when they hear the term, "home study." Fortunately, more and more manufacturers are astonished to find that home-study graduates are well versed in many other things besides radio/TV repair.

Third, some home-study students themselves may have the wrong objectives. A man, for example, can sign up for a course in basic electronics. As soon as it is completed, he applies for a job as an engineering technician with a computer manufacturer. He flunks the employment examination. The student is then dissatisfied with the school, which he believes let him down. And the computer company has a nagging feeling that home study is no good. Neither is true; the fact is simply that a basic electronics course was never designed to train a man to be a computer technician.

It Takes Time and Effort

Graduates of two- or three-year residence courses in top-rated schools attend classes for an average of some six hours a day, then spend two to three hours doing homework, with perhaps another session with the books over the weekend. Such students, in other words, spend virtually their entire time for two or three years studying electronics. Altogether, they may devote some 3000 to 4000 hours to becoming highly trained technical experts. By the time they've finished the better schools, they know calculus, Boolean algebra, and solid-state theory. They are thoroughly familiar

(Continued on page 109)

WHAT ARE THE STARTING SALARIES?

Those with the most training get the fattest pay checks. Graduates of three-year courses at top-rated technical institutes or junior colleges, and of the advanced home-study courses, make more money than those with less training. One manufacturer, for example, told us that the general run-of-the-mill graduate technician who qualifies for employment at his plant gets \$93-\$115 a week as a starting salary. Graduates of the high-level courses generally start at \$120-\$150 a week. These are graduates with no "on-the-job" experience. Geographical location has a strong influence on pay checks. Electronics concerns in large cities and in the heavily industrialized regions such as those on the East and West Coasts and in some parts of the Midwest tend to pay more than those in smaller towns and cities. Any talk about specific figures must be general, since variations are wide. Normally, however, technicians working for industrial firms whose payrolls tend toward the low end of the salary scale might get only \$80 to \$95 a week as beginning pay. Those at the high end of the scale tend to cluster in the \$100-\$120 range, though some go higher. In communities where pay scales are lowest, of course, living costs also tend to be low.

In general, the same principles apply for radio/TV service technicians. Starting salaries for technicians who have completed a residence or home-study course may range from \$75 to \$115 a week, depending on the course and where they work. Men who plan to work in communications will normally earn salaries in between those of service technicians and industrial technicians.

INTEGRATED




By **DON LANCASTER**

Testing integrated circuits is one of the costlier operations of the industry. Powerful semiautomatic optical instruments, such as the one shown at left, are used to inspect components a few thousandths of an inch thick. (Photo courtesy of Motorola)

IC's at all? Aren't they so expensive now that only the military can afford them, and so specialized that only computer specialists can use them? Not at all! Integrated circuits have become so cheap, reliable, and easy to use that most engineers consider it unwise to design new "ordinary" circuits with separate parts in applications where IC's can be used.

An Old Concept. Remember the 6SN7 radio tube? There must have been millions of them in use at one time or another. This tube is the octal-based dual triode that helped start the computer industry, served as a tone generator in electronic organs, and starred in the horizontal circuits of countless TV sets. The 6SN7's big advantage over its older counterparts was its two-for-the-price-of-one feature. Now two tubes occupied the space of one, and only one socket was needed. You saved two filament wires, four stripping operations, two solder joints, and lots of space. No longer did you talk of a single tube function, since *a system of devices and interconnections in a single compact package was now available.* And this is precisely what an integrated circuit is.

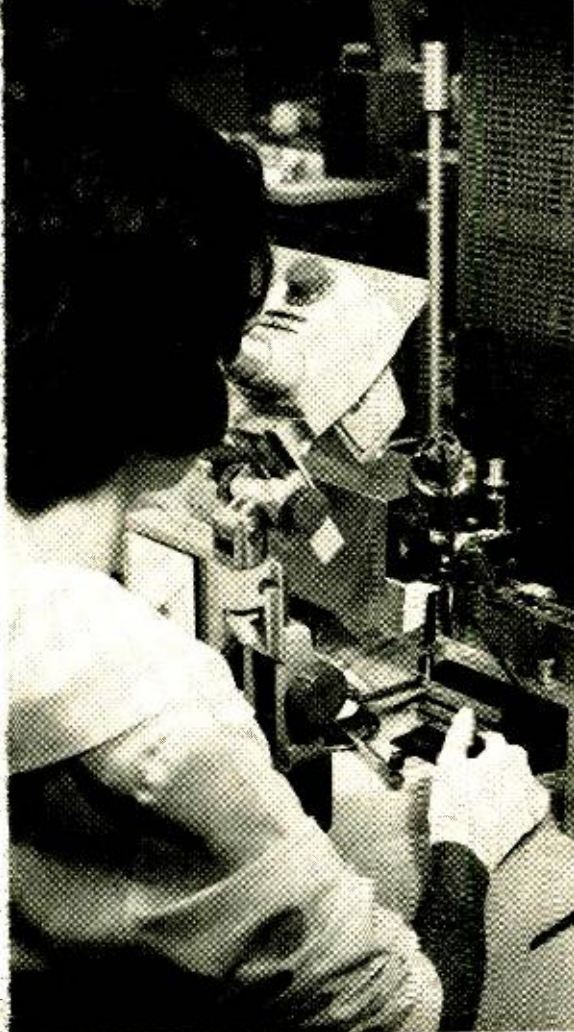The 6SN7 was followed by the smaller 12AU7 and 12BH7, after which came the semiconductor devices with a new set of problems. The devices (transistors and diodes) got smaller and smaller while




THE MAGIC wand of microminiaturization has cast a spell on the electronics industry—a spell that will lead in the next few years to unheard-of new electronic devices and applications. Picture-on-the-wall TV, vehicular anticollision radars, home computer centers, portable electronic calculators smaller than a slide rule, precision controls for home appliances, person-to-person viewers—these are but a few samples of the vast cornucopia of low-cost, high-reliability, and extremely small size electronic miracles that are to be ours in the very near future.

The components produced by this technology are called integrated circuits—or simply IC's. But just what is an integrated circuit? And why talk about

CIRCUITS

THERE IS A BRIGHT FUTURE FOR A NEW TECHNOLOGY IN MOLECULAR ELECTRONICS THAT COULD MAKE POSSIBLE A NEW GENERATION OF PRODUCTS FOR INDUSTRY AND HOME

WHAT ARE THEY?

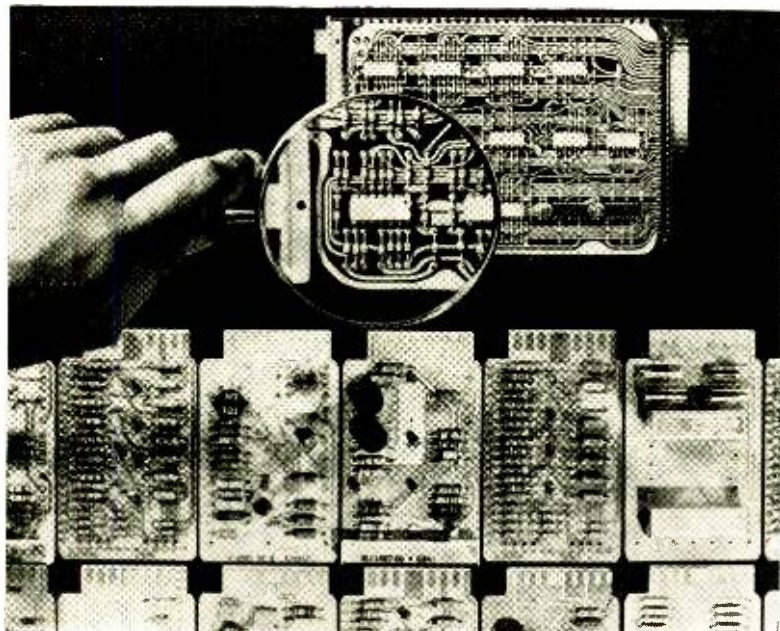

Monolithic integrated circuits, such as the one shown magnified above, are used in Sperry Rand's new UNIVAC 9000 series data processing systems. They perform the same functions as the large conventional printed circuit boards. One chip is the equivalent of 14 conventional printed circuit boards like the ones shown in the lower area of the photo.


external circuit wiring remained essentially as bulky as ever. However, since the transistor and diode generate little or no heat, the normal requirement for air ventilation was no longer critical. This being the case, the only remaining obstacles to miniaturization were the other circuit components.

The next step in the stride toward miniaturization was the putting together of two transistors in a single six-legged can to form what seemed like a "2N-6SN7" unit. Not only did this procedure simplify the wiring and basing requirements, but it also brought along other

definite advantages. Since the two transistors were made side by side on a single slab of silicon perhaps no bigger than 25 mils square, they maintained the same temperature—which provided perfect tracking in critical, wide-temperature-range circuits. Identical geometry made the pair perfectly balanced, and for the first time it was possible to get a truly complementary *pnp-npn* pair.

Because transistors were able to operate at extremely low power levels, and the power dissipated in load and bias resistors was negligible, substantially


Typically, the manufacturing sequence for a monolithic IC is as follows: (1) Processing starts with a chip of lapped and polished P-type silicon wafer (P-substrate) about 0.010 of an inch thick. (2) An N-type epitaxial layer is grown over the wafer; this is followed by a thin layer of silicon dioxide that is formed by heating in an oxidizing atmosphere. (3) Grooves are etched around the areas to be isolated using normal photoengraving process. (4) A highly doped P-type impurity is diffused into the grooves down through the epitaxial layer to the substrate. This impurity is covered by a second layer of silicon dioxide formed by heating again. (5) A photo-resist pattern masks those areas that must be etched to form the transistor base area and resistor patterns. (6) A P-type impurity is diffused into the etched areas to (continued on next page)

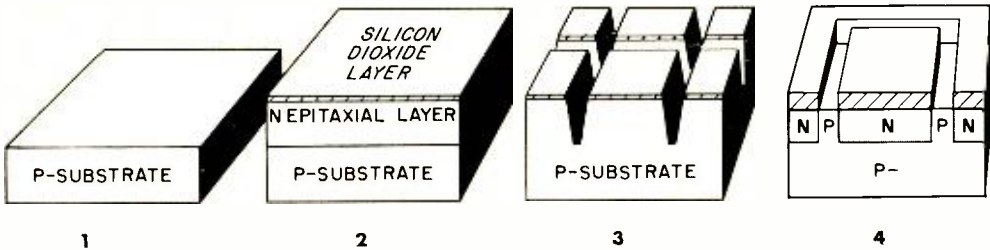

smaller components could be used. Having gotten this far in the size reduction scheme, the next step could be easily anticipated: how to put resistors, capacitors, and inductors in the same can with the transistors. After all, since there are many identical circuits that are used over and over again with only slight changes, a few standard circuits would allow a wide variety of applications. Therefore, if the designer used lots of transistors and resistors, and built entire systems in small cans, he could eliminate countless interconnections.

Ways To Make IC's. The resistors were easy to put on a silicon slab. Nichrome or nickel can be evaporated in place through a mask to build up the approximate resistance and trimmed to an exact value by abrasion or electron beam cutting. Other possibilities include the use of resistive inks, which can be directly silk-screened or offset-printed into place. Or, as is more popular today, silicon substrate (semiconductor material) itself can be made into resistors. By controlling the doping level, it is possible to obtain a given resistivity from which a desired resistance value can be derived. A reverse bias technique is used to isolate the various resistors, which are made from *n*-type material.

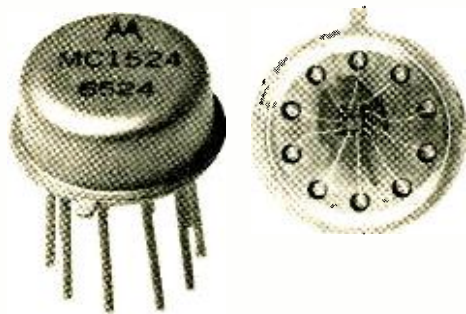If all resistors are connected to a positive supply, the *pn* junctions formed will be reverse-biased, neatly isolating the resistors from the substrate and




The standard package for most integrated circuits is the multi-lead TO-5 case. Shown above is a 10-lead version of the common transistor case. Wires 0.001" in diameter link each contact pad on the circuit with a pin on the base as shown at right.


from each other, since the junctions cannot conduct current under reverse bias conditions. Newer techniques add a thin layer of glass between the substrate and the resistors to minimize the effects of nonlinear stray capacitance in high-frequency IC's.

Newer transistors like the metal-oxide semiconductor (MOS) variety, and the insulated gate field-effect transistor (IGFET), can be made to exhibit the property of resistance or conductance, depending on the biasing employed. Furthermore, since these transistors do not require any special manufacturing process, they can be formed together with resistors, resulting in higher yields at lower costs.

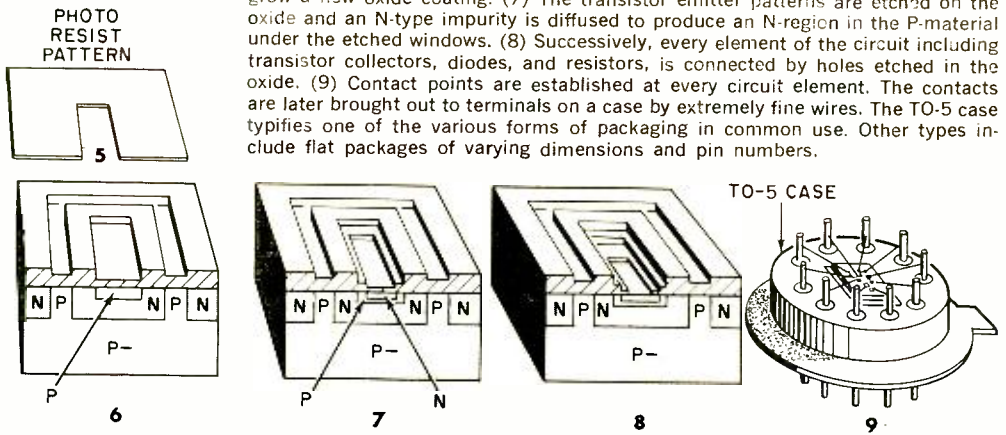But the forming of capacitors was a much more difficult task, and IC induc-



grow a new oxide coating. (7) The transistor emitter patterns are etched on the oxide and an N-type impurity is diffused to produce an N-region in the P-material under the etched windows. (8) Successively, every element of the circuit including transistor collectors, diodes, and resistors, is connected by holes etched in the oxide. (9) Contact points are established at every circuit element. The contacts are later brought out to terminals on a case by extremely fine wires. The TO-5 case typifies one of the various forms of packaging in common use. Other types include flat packages of varying dimensions and pin numbers.

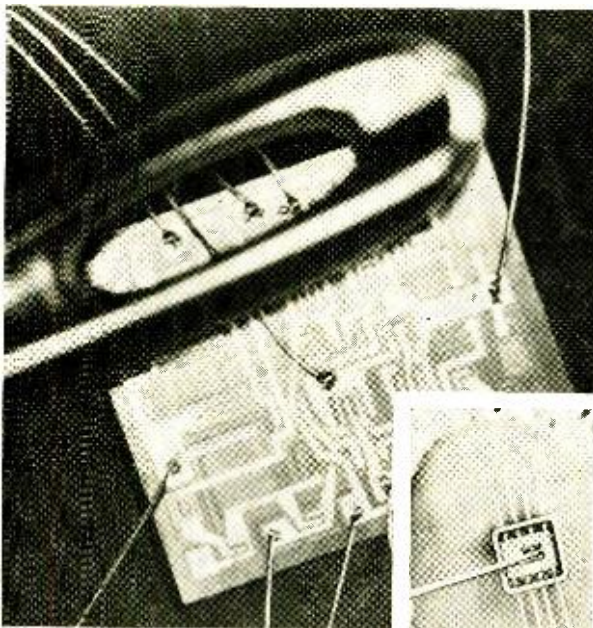

Magnified view through eye of needle emphasizes minuteness of tiny welded connections that attach spider-web thin aluminum wire to elements of micro-electronic circuit. (Photo courtesy Cutler-Hammer)


a bit and decided instead to redesign their circuits to fit the IC's. This meant the elimination of all inductance, and as much capacitance as possible, from the circuit. For r.f. applications, where tuning or filtering is a must, separate LC units were placed in separate miniature cans and used like r.f. transformers. Wherever possible, all circuits are d.c.-coupled to eliminate practically all capacitors. And although this requires the use of more transistors, there is no extra cost. Adding more transistors in an integrated circuit requires only the making of a few more holes in the series of masks used during manufacture. It costs just as much to make one transistor as it does to make a dozen. And a dozen often occupy less space than the single capacitor they replace in a d.c. circuit. The use of numerous transistors is usually less expensive, anyway, since the capacitor manufacturing steps are eliminated.

This is why integrated circuit schematics always seem so complicated. Extra transistors are used to eliminate any component that would be expensive or hard to include in a tiny space.

tors were essentially impossible to make. Capacitors had to be built up by metalization of silicon or glass, in repeated layers. But even then they were somewhat leaky, and large values of capacitances required large areas of the integrated substrate. As for inductors, it simply wasn't possible to achieve large "L" values or high Q's.

So the circuit designers backed away

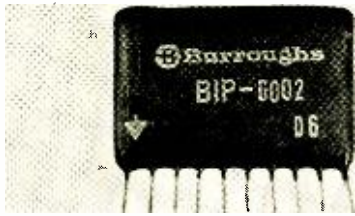Common Types of IC's. Every manufacturer has his own way of putting the many tiny components or circuit functions and interconnections into a single IC. However, since production techniques change so fast, it really isn't important for the IC user to know just what manufacturing steps are in use. But there are several basic IC types that



Similar in appearance to a packaged electronic circuit, this Burroughs' IC package features rugged dependability, making its use in electronic equipment subject to shock and vibration most desirable.

are likely to be around for a while. You should learn to recognize these types. Here are some of them:

Monolithic IC's have all their individual components etched out on a solid silicon chip. Their construction is very rugged, and the manufacturing cost relatively low.

Hybrid IC's consist of a number of interconnected monolithic IC's, discrete transistors, capacitors, and possibly power resistors. The hybrids lend themselves to high power outputs and custom-designed circuitry where the inter-

connections can be altered to suit a particular requirement. They are usually low-frequency devices and generally quite expensive.

Thin-Film IC's employ an IC technique through which layers consisting of a few atoms of a semiconductor material are evaporated onto a ceramic substrate (the newest designs use sapphire) through a series of masks. This technique permits exceptionally high frequency response and extremely small size. Some low-priced models operate with power in the nanowatt range.

Thick-Film IC's employ an old and cheap method similar to the printed circuit couplates. Resistors are silk-screened or offset printed in place; capacitors are made by overlapping layers of ceramic and metallic material. Ordinary transistors without cases are cemented or ultrasonically welded in place. This type of IC is recognized by its postage-stamp size and shape, and its external protective epoxy dip.

What's Available Now? Today there are thousands of different IC's available.
(Continued on page 106)

LOW-COST INTEGRATED AMPLIFIERS FOR THE EXPERIMENTER

CIRCUIT	TYPE	NUMBER	MANUFACTURER	PRICE (Approx.)
OPERATIONAL AMPLIFIER	Linear	uA702	Fairchild Semiconductor	\$14.40
R.F. OR I.F. AMPLIFIER	Linear	uA703	313 Fairchild Drive	4.50
COMPARATOR	Linear	uA710	Mountain View, Calif.	7.50
BUFFER	Digital	uL900		1.63
DUAL TWO-INPUT GATE	Digital	uL914		1.63
COUNTING FLIP-FLOP	Digital	uL923		3.95
LATCHING FLIP-FLOP	Digital	MC352	Motorola Semiconductor	4.55
DUAL TWO-INPUT GATE	Digital	MC359	Box 955	3.70
DUAL-COUNTING FLIP-FLOP	Digital	MC790	Phoenix, Ariz.	5.30
OPERATIONAL AMPLIFIER	Linear	MC1430		18.00
1-WATT AUDIO AMPLIFIER	Linear	MC1519		70.00
D.C. AMPLIFIER	Linear	CA3000	RCA Electronic Components	6.80
VIDEO AMPLIFIER	Linear	CA3001	Harrison, N. J.	6.40
I.F. AMPLIFIER	Linear	CA3002		4.40
R.F. AMPLIFIER	Linear	CA3004		4.40
AUDIO DRIVER	Linear	CA3007		6.80
OPERATIONAL AMPLIFIER	Linear	CA3010		12.00
COMPLETE FM I.F. STRIP	Linear	CA3013		2.65
HEARING-AID AMPLIFIER	Linear	SN1220	Texas Instruments Box 5012 Dallas, Texas	16.20
HIGH-GAIN AUDIO AMPLIFIER	Linear	WC183	Westinghouse Electronics	10.00
R.F. AMPLIFIER	Linear	WC1146	Box 7737 Elkridge, Md.	10.00

AT LAST...



By DON LANCASTER

AN INTEGRATED CIRCUIT AMPLIFIER

you can build for under \$6!

SIMPLE PROJECT OPENS DOOR TO NEW MICROCIRCUITS

HERE'S the "bargain basement" integrated circuit (IC) amplifier that hobbyists and experimenters have been waiting for. Ideally suited for use as a phonograph or dynamic microphone pre-amplifier, as a boost amplifier in a receiver i.f. or r.f. stage, as well as in practically all applications employing low-level signals, the complete IC amplifier can be built for under \$6.00. The IC, packaged in a TO-5 case, contains the equivalent of six 2N918 transistors and seven resistors, and provides a voltage gain of 40, a current gain of 120, and a power gain of nearly 5000.

Frequency response is essentially flat from 20 Hz to 30 MHz, and distortion is negligible at outputs of up to 0.7 volt peak-to-peak. Clipping occurs at output levels of 1 volt peak-to-peak and over. When assembled with the external components itemized in the Parts List, the IC amplifier has an input impedance of 3300 ohms, and an output impedance of approximately 25 ohms.

How It Works. The integrated circuit amplifier (Fig. 1) consists of two separate transistor differential amplifiers (they respond to the difference between

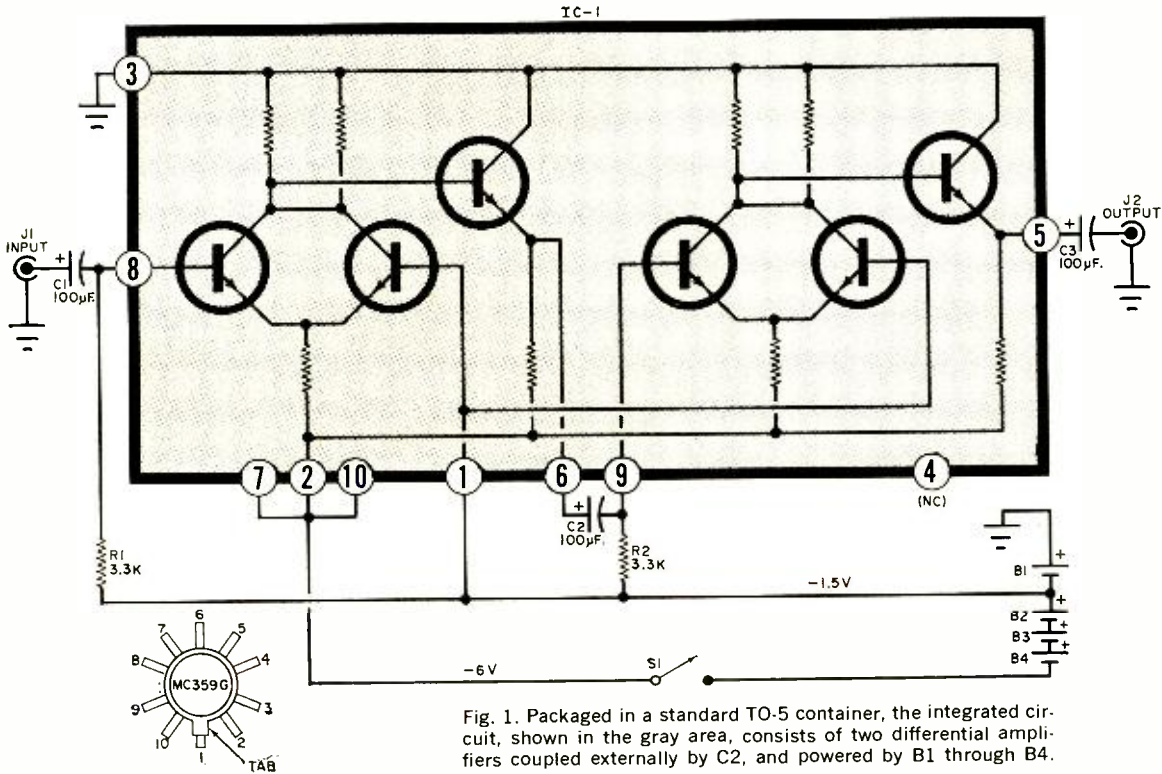


Fig. 1. Packaged in a standard TO-5 container, the integrated circuit, shown in the gray area, consists of two differential amplifiers coupled externally by C_2 , and powered by B_1 through B_4 .

two voltages or currents), each coupled to an emitter follower stage. The output of the first emitter follower is applied to the base of the second differential amplifier input transistor through coupling capacitor C_2 .

Capacitor C_1 couples the input from J_1 to the base of the first amplifier which is biased through R_1 . Resistor R_2 applies bias to the base of the second differential amplifier input transistor. The IC amplifier output is applied to J_2 through C_3 .

Base bias for the second transistor of each amplifier pair is applied directly from a $1\frac{1}{2}$ -volt tap on the 6-volt supply battery. The full supply voltage is applied to the circuit through S_1 .

Important: The values of capacitors C_1 , C_2 , and C_3 determine the frequency response of the circuit. For low-frequency response (about 20 hertz) only, 100- μ F capacitors are used; for frequencies above 100 kHz, 0.02- μ F disc capacitors are used *instead* of the 100- μ F units. For a full frequency coverage (20 hertz to 30 MHz), parallel the two capacitor values.

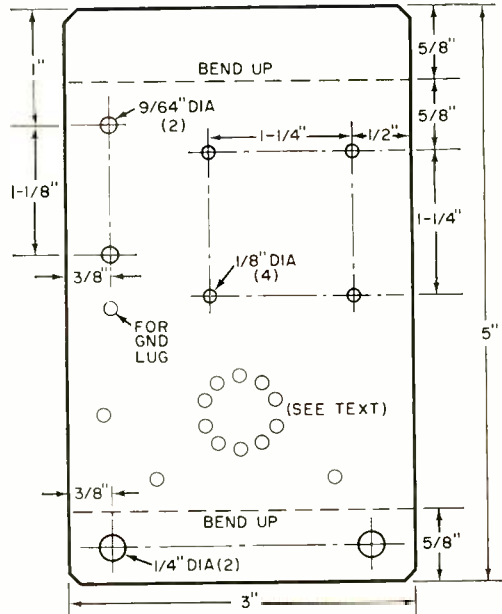


Fig. 2. The complete IC, including the battery supply, can be mounted on a small (3" x 5") aluminum plate, drilled and bent to form a chassis support.

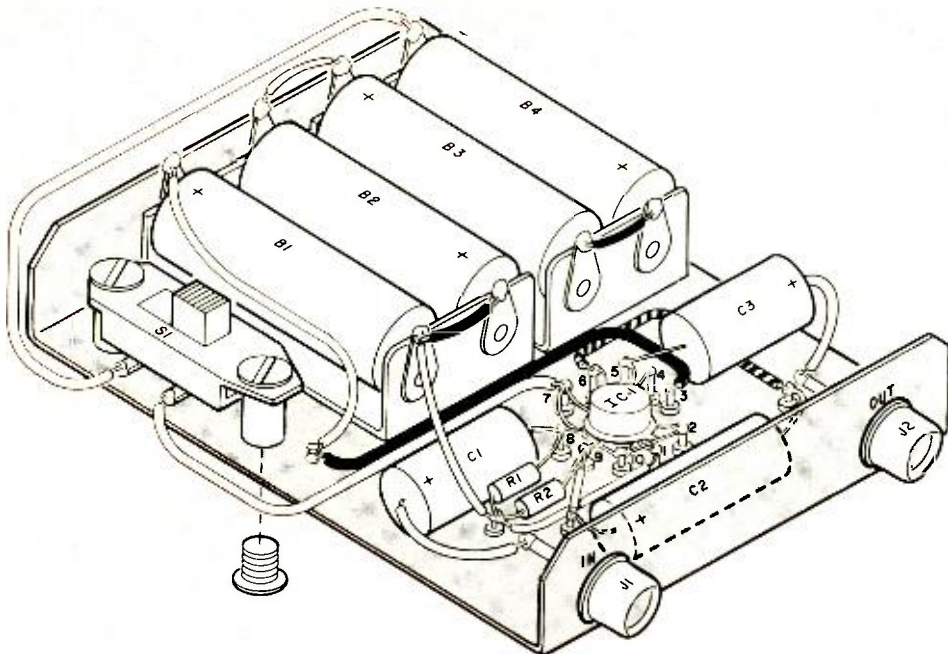


Fig. 3. Pictorial of fully assembled integrated circuit shows simplicity of layout and wiring details. The 10 teflon terminals that mount the TO-5 case can be replaced with one Sealectro IC socket.

Construction. The circuit is easily assembled on an improvised aluminum plate laid out and drilled as shown in Fig. 2. The IC socket used by the author is made up of 10 teflon press-fit standoff terminals inserted into appropriately-sized holes drilled in the plate. Then the leads from the IC case are fanned out and each soldered to a standoff.

However, it is suggested that the builder follow a much easier and efficient procedure. A single Sealectro press-fit socket (see Parts List) can be press-fitted in a $\frac{1}{2}$ " hole drilled in the plate instead of bothering with the 10 small holes.

The four $\frac{1}{8}$ "-diameter holes in the upper portion of the plate mount the two penlight battery holders that are either riveted or screwed to the plate. Slide switch *S1* is mounted on $\frac{1}{2}$ "-long spacers threaded at both ends for ≈ 6 screws, through the two $\frac{3}{16}$ "-diameter holes. The three unidentified holes in the vicinity of the IC socket accommodate press-fit standoffs that serve as tie points for

PARTS LIST


B1, B2, B3, B4—1.5-volt penlight cell
C1, C2, C3—100- μ F, 6-volt electrolytic capacitor for 20 Hz to 1.5 MHz; 0.02- μ F ceramic capacitor (10 volts or more) for 100 kHz to 30 MHz; both values in parallel for full range
IC1—Motorola dual two-input gate MECL circuit (Allied Radio MC350G, \$3.70)
J1, J2—Chassis-mounting phono jack
R1, R2—3300-ohm, $\frac{1}{4}$ -watt resistor
S1—S.p.s.t. slide switch
1—Sealectro IC 10-pin socket, Part No. RTC-1010 SL (available from Joseph Kurzan, Inc., or Arrow Electronics, Inc., both in New York City)
1—3" x 5" sheet of 1/32"-or 1/16"-thick aluminum
Misc.—Battery holders for four penlight cells (2), teflon press-fit terminals (3), ground terminal, $\frac{1}{2}$ "-long threaded spacers (2) with ≈ 6 $\frac{1}{4}$ "-long screws (4), rivets or screws for battery holder, solder, hookup wire

component leads. The input and output jacks are mounted on the raised front panel as shown in Fig. 3.

All circuit components should be mounted and wired in place before installing the IC package; but do not
(Continued on page 108)

**“Get more
education
or
*get out of
electronics***

...that's my advice.”

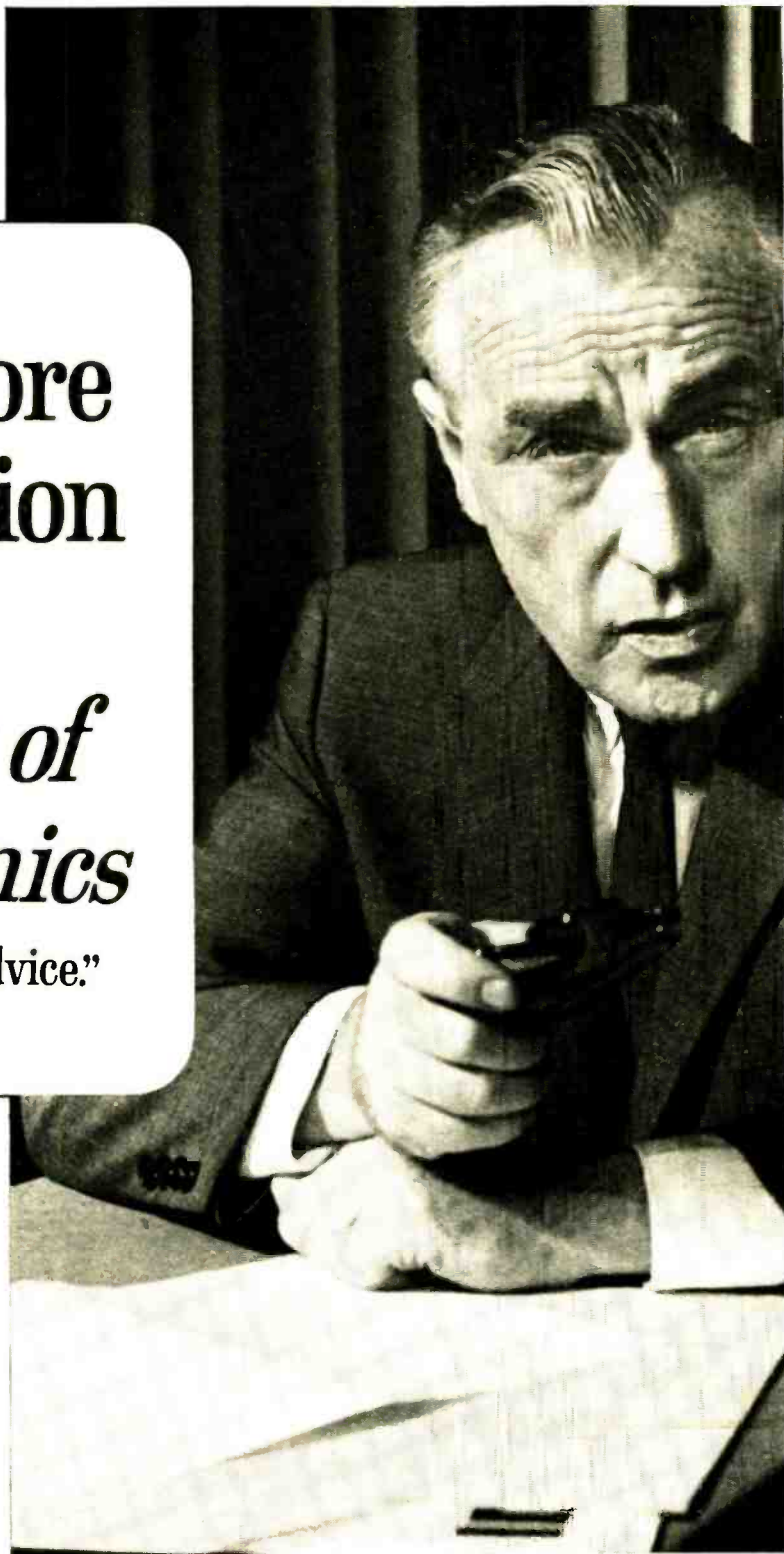



NOW! 2 NEW PROGRAMS!
 ● Industrial Electronics for Automation
 ● Computer Systems Technology

Ask any man who really knows the electronics industry. Opportunities are few for men without advanced technical education. If you stay on that level, you'll never make much money. And you'll be among the first to go in a layoff.

But, if you supplement your experience with more education in electronics, you can become a specialist. You'll enjoy good income and excellent security. You won't have to worry about automation or advances in technology putting you out of a job.

How can you get the additional education you must have to protect your future—and the future of those who depend on you? Going back to school isn't easy for a man with a job and family obligations.

CREI Home Study Programs offer you a practical way to get more education without going back to school. You study at home, at your own pace, on your own schedule. And you study with the assurance that what you learn can be applied on the job immediately to make you worth more money to your employer.

You're eligible for a CREI Program if you work in electronics and have a high school education. Our **FREE** book gives complete information. Airmail postpaid card for your copy. If card is detached, use coupon below or write: CREI, Dept. 1220-D, 3224 Sixteenth Street, N.W., Washington, D.C. 20010.



The Capitol Radio Engineering Institute
 Dept. 1220-D, 3224 Sixteenth Street, N.W., Washington, D.C. 20010

Please send me **FREE** book describing CREI Programs. I am employed in electronics and have a high school education.

NAME _____ AGE _____

ADDRESS _____

CITY _____ STATE _____ ZIP CODE _____

EMPLOYED BY _____

TYPE OF PRESENT WORK _____ GI BILL


I am interested in Electronic Engineering Technology
 Space Electronics Nuclear Engineering Technology
 NEW! Industrial Electronics for Automation
 NEW! Computer Systems Technology

VOLTAGE DIVIDER QUIZ

By ROBERT P. BALIN

To bat 1000 with this quiz, all you need to know is Ohm's law. Can you determine between which set of terminals (A-H) on the schematic diagram a voltmeter must be connected to read the individual voltages listed below? Some of these voltages can be obtained at more than one set of terminals. Extra space is allotted for your answer where multiple combinations exist. HINT: Start out by letting terminal A or B serve as your reference point.

(Answers appear on page 111)

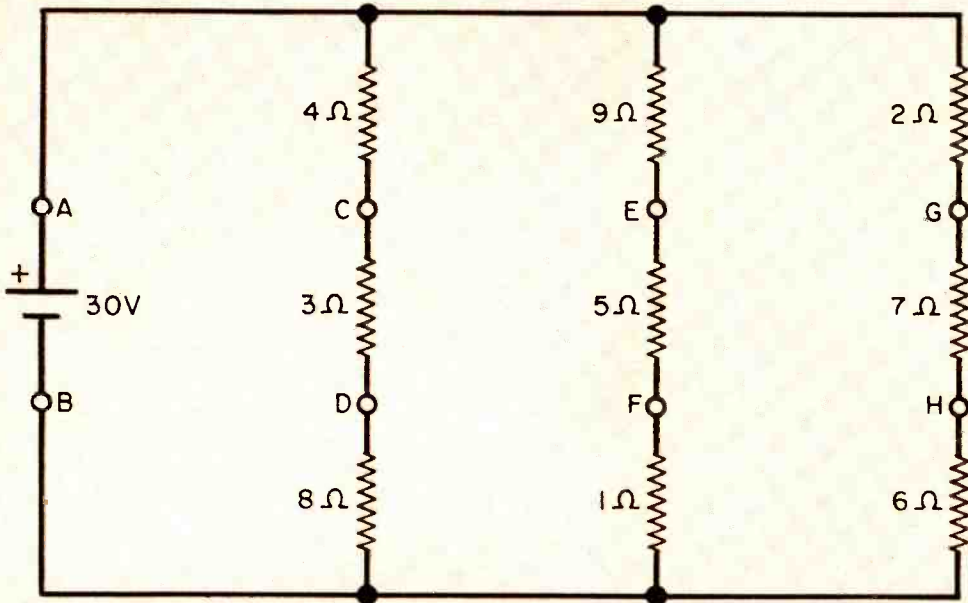

VOLTS

TERMINALS

VOLTS

TERMINALS

0

2

4

6

8

10

12

14

16

18

20

22

24

26

28


30

BUILD HI-FI AMPLIFIER FOR SOLID-STATE PHONO CARTRIDGE

NEW STRAIN-GAUGE STEREO
PHONO CARTRIDGE STREAMLINES
AMPLIFIER REQUIREMENTS AND
PROVIDES BROAD FREQUENCY RESPONSE

By ART TRAUFFER

THE NEW PIEZORESISTIVE semiconductor strain-gauge phono cartridges open up a whole new field of endeavor for hi-fi enthusiasts, experimenters, hobbyists, and record player manufacturers. These cartridges work like variable resistors. Unlike ceramic and magnetic cartridges, they do not generate any voltage. They *do* utilize a varying resistance characteristic to modulate an external d.c. voltage in step with stylus motion. The small voltage needed can be obtained directly from an amplifier

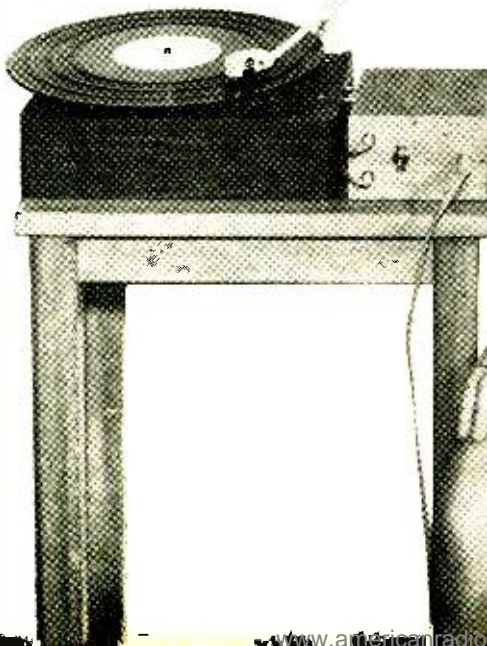

power supply, or from a separate battery.

Interest in these piezoresistive phono cartridges is running high at the present time because of their compatibility with transistor applications. They have several good inherent characteristics: they closely match the inputs of transistorized audio amplifiers; they effectively deliver more power to the amplifier and reduce the number of stages of amplification; frequency response is from d.c. to more than 30,000 hertz; and there are no coils to pick up a.c. hum.

A two-transistor amplifier especially designed for use with one of these cartridges is shown in Fig. 1 and discussed in the following paragraphs.

How Amplifier Works. A stereo cartridge, equipped with a double sapphire flip-over stylus, is coupled to a pair of stereo headphones through a basic stereo amplifier.

The two-channel amplifier is beautiful in its simplicity. It has only four resistors, two capacitors, and two transistors, as shown in Fig. 1. Resistors *R3* and *R4* set up bias for *Q1* and *Q2*, respectively. Capacitors *C1* and *C2* serve as signal couplers and d.c. blockers. A 1½-volt flashlight battery (D cell) is used to operate the transistors.

Voltage from a lantern-type battery (6 volts) is divided equally and oppositely across each element in the stereo cartridge. Any d.c. voltage source on

the order of 6 to 18 volts can be used for this purpose. The higher the voltage, the greater the volume. However, comfortable listening levels are obtained with a 6-volt source.

Resistors *R1* and *R2* form voltage dividers with their respective cartridge elements and are hooked up in such a way as to have a negative-going voltage in one channel and a positive-going voltage in the other channel when both cartridge elements are moved in the same direction. Vertical stylus motion (up or down) causes both elements to move in the same direction. Lateral motion moves one element up and the other element down.

This phase-inverting technique is used to obtain an out-of-phase signal for vertical stylus motion and an in-phase signal for lateral motion, to conform to

PARTS LIST

- C1, C2*—20- μ F, 25-volt electrolytic capacitor
- J1, J2*—Phono jack (RCA type, single-hole mounting)
- J3*—Three-circuit phone jack (should match headset plug)
- Q1, Q2*—2N217 transistor
- R1, R2, R3, R4*—2200-ohm, ½-watt resistor
- S1*—D.p.s.t. toggle switch
- I*—Solid-state stereo cartridge (similar to Sonotone 43T)
- I*—Stereo headphone set (similar to Jensen HS-2)
- Misc.—1½-volt "D" cell battery and holder, 6-volt lantern battery, 5-lug terminal strip, 3/8" wood stock for cabinet (see text), 1/8" Formica or composition board, 10,000-ohm miniature potentiometer (optional), hardware, etc.

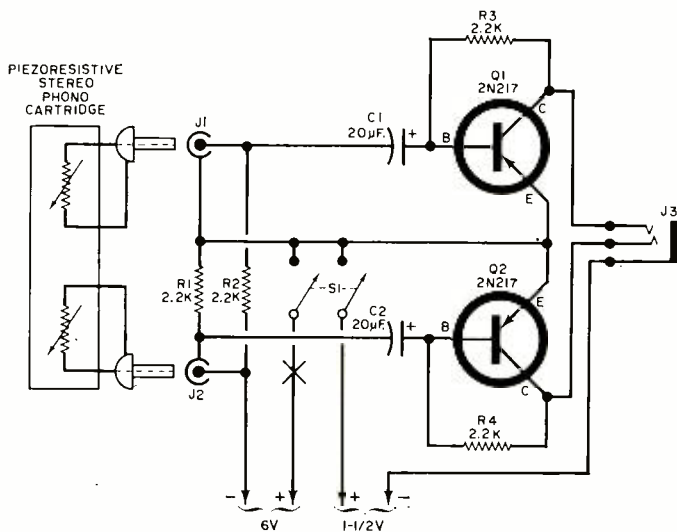


Fig. 1. Strain gauge cartridge acts like a variable resistance and modulates 6-volt d.c. source to drive simple stereo amplifier in step with stylus motion. Text explains stereo phase manipulation.

Fig. 2. Mount all parts except the batteries on the back of the front piece of the cabinet. There is enough room to permit installation of an optional volume control. Observe polarity of capacitors.


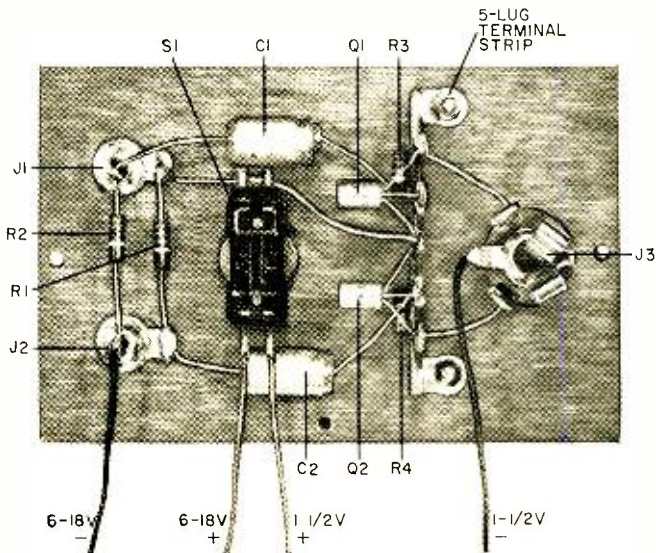


Fig. 3. A wood screw (under the "D" cell) is used to hold down the "D"-cell holder and one end of the metal strap. Countersink the other end of the strap and fasten it to the back of the cabinet.

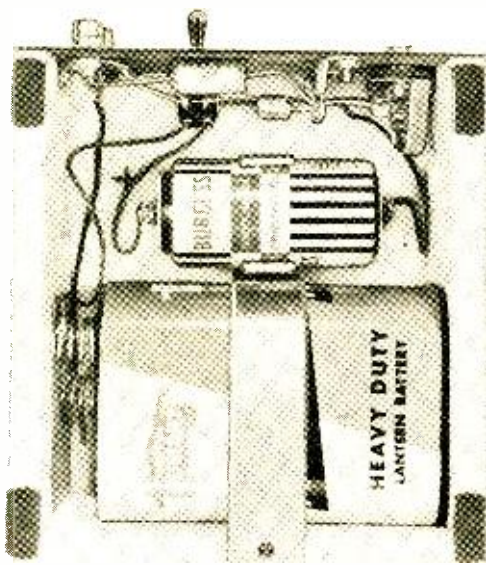

stereo disc recording standards. It is easier to reverse the phase of the modulating voltage than to flip the wiring of one of the headphones. You cannot reverse the phase of one element in the cartridge by simply reversing the connections to the element, because the elements are resistive.

A 10,000-ohm potentiometer can be wired in at point "X" to serve as a volume control. Use a pair of low-impedance dynamic-type headphones similar to the Jensen HS-2.


Construction. The same simplicity apparent in the electronic circuitry is passed on to the construction, as shown in Fig. 2. Parts placement is not critical, and if it is desired to install the optional volume control, use a miniature unit and mount it on the panel between J3 and S1. Dress the other components away from the control to prevent short circuits.

A 5" x 3³/₁₆" x 1/4" Formica or composition board panel can be used. Resistors R3 and R4, and transistor Q1 and Q2 are mounted on a five-lug terminal strip. You can heat-sink the transistor leads with a pair of long-nose pliers to prevent damage to the transistors while soldering. Observe polarity when installing C1 and C2.

The optimum value of R3 and R4 may vary a little from transistor to transistor, but normally is satisfactory as shown. If you wish to obtain maximum fidelity, you can try to vary the bias a bit by changing the value of these resistors.


Figure 3 shows how the batteries are mounted inside the 5¹/₂" x 5" x 3³/₁₆" wood cabinet. Cabinet type and material used for construction is not critical, but size depends upon the size of the batteries you use. The lantern battery is held in place by a sheet metal strap, and the D cell fits into a regular holder. Non-skid rubber or felt pads can be cemented to bottom of cabinet.

FROM

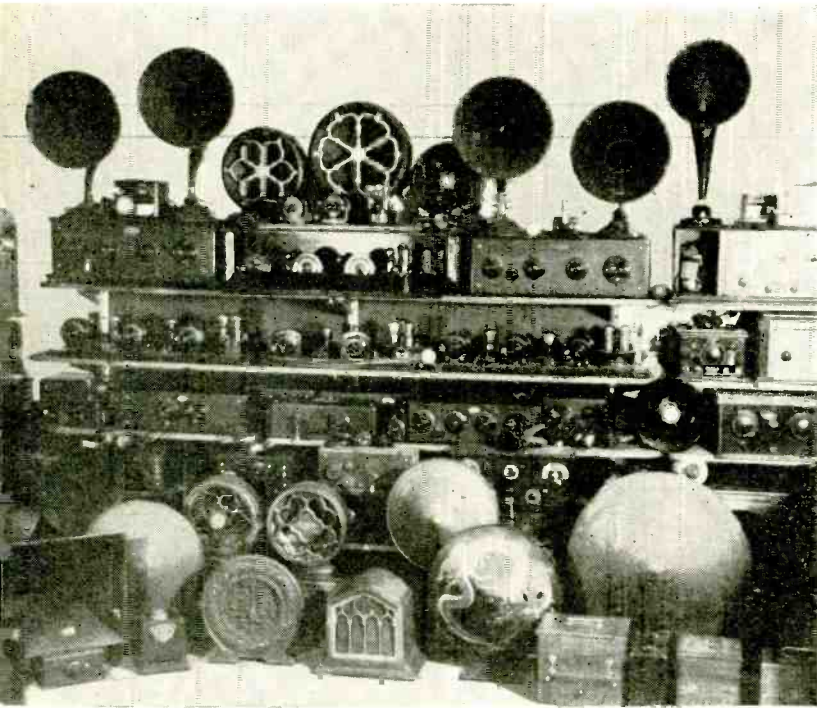

This view shows only a small part of the broadcast receiver collection assembled by Ralph Barnett, W9UIA, 3434 E. Oakwood, Decatur, Ill. 62521. Among these early receivers and loudspeakers are 21 different Atwater Kent models. Altogether, the collection consists of about 150 sets made before 1926.

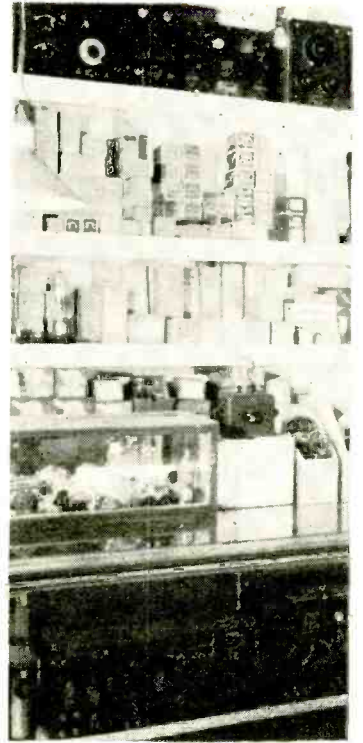The Antique Wireless Association's Historical Museum in Holcomb, N.Y., even contains a "store." Displayed at right are products found in radio stores 40 years ago. Many of the items are new and in original cartons.




One of the finest wireless museums in North America has been built by Jack Gray, W8JDV, 500 W. Church St., Mason, Ohio 45040. This section of the museum, being viewed by Bruce Kelley, W2ICE, and Linc Cundall, W2QY, shows part of a Crosley receiver collection

OUT OF THE PAST


WIRELESS MUSEUMS
PRESERVE THE EARLY DAYS
OF RADIO

By THEODORE M. HANNAH, K3CUI

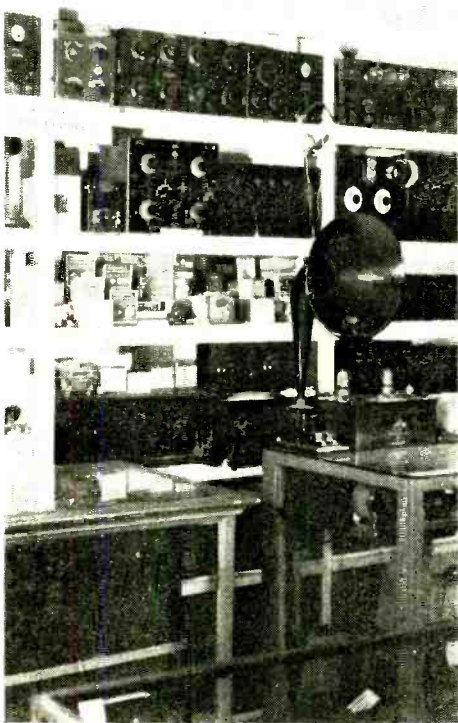

Authentic to the last detail is the working restoration (above) of a Western Union telegraph office as seen 80 years ago. It is part of the unique National Telegraph Office assembled by E. Stuart Davis, W2ZH, 1149 Weber St., Union, N.J. 07083.

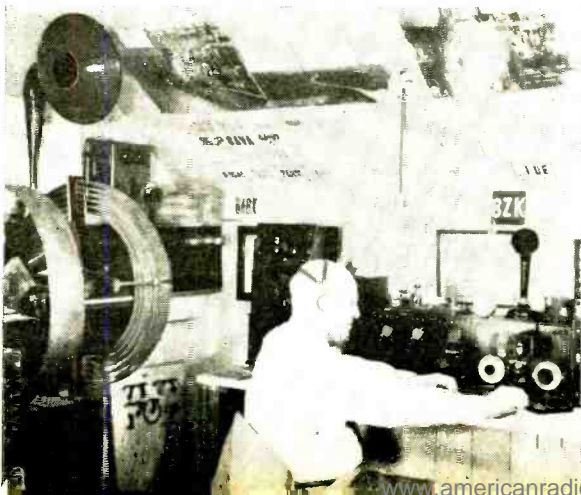
In 1922, this was the last word in high-powered ham stations. In 1966, it is one of the stations owned by the Antique Wireless Association, several of which operate under the call W2AN. Shown here is George Batterson, W2GB.




PRESERVING the spirit and the substance of early wire and wireless communications history is the hobby of a growing number of collector-historians. Some 400 of them are members of the Antique Wireless Association, an ARRL affiliate formed in 1953. (If you would like more information on the AWA, write to Bruce Kelley, W2ICE, Main Street, Holcomb, N.Y. 14469.)

The museums shown here are all privately owned, and in most cases they are in the owners' homes. Although most collectors welcome visitors, courtesy requires that you call or write for an appointment. Entering a wireless museum is truly taking a step into the past, into the rich history of the wonderful world of communications.

-30-

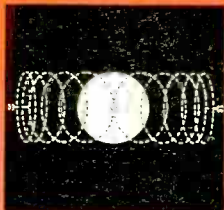



ZERO-BEATING THE NEWS

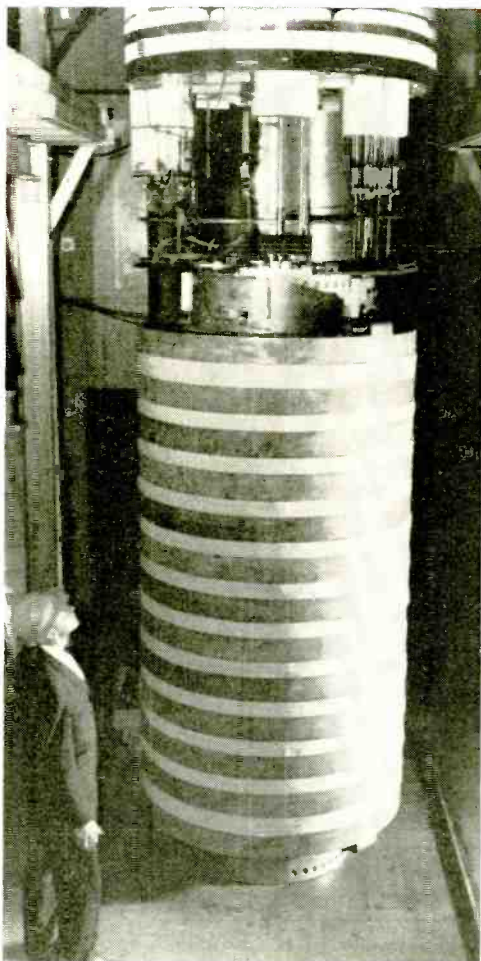

GIANT MAGNET—What is believed to be the world's largest superconducting magnet, shown on display at Avco Everett Research Laboratory, produces 40,000 gauss over a 5' x 12" field region. Weighing 15,675 pounds, the giant magnet stands 10' high, and stores 5,000,000 joules of energy. Designed for use in a magnetohydrodynamic (MHD) power generator, the saddle-shaped magnet was made possible by a recently developed (by Avco) "stabilized" composite superconductor.

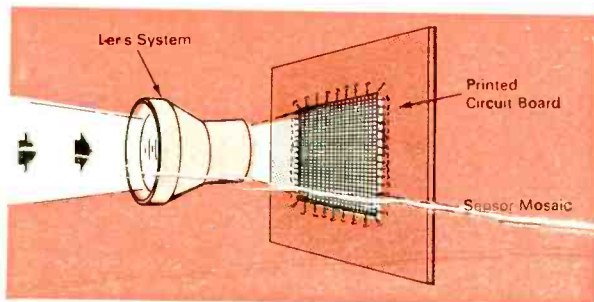
FASE WON'T PHASE COMPUTER—To prevent computer confusion about the relationship of words in a sentence, a new form of English has been devised by Dr. Lee E. McMahon (below) of Bell Telephone Laboratories. Called FASE (for Fundamentally Analyzable Simplified English), it is indistinguishable from ordinary English by a reader, but can be uniquely resolved into parts of speech by a computer.



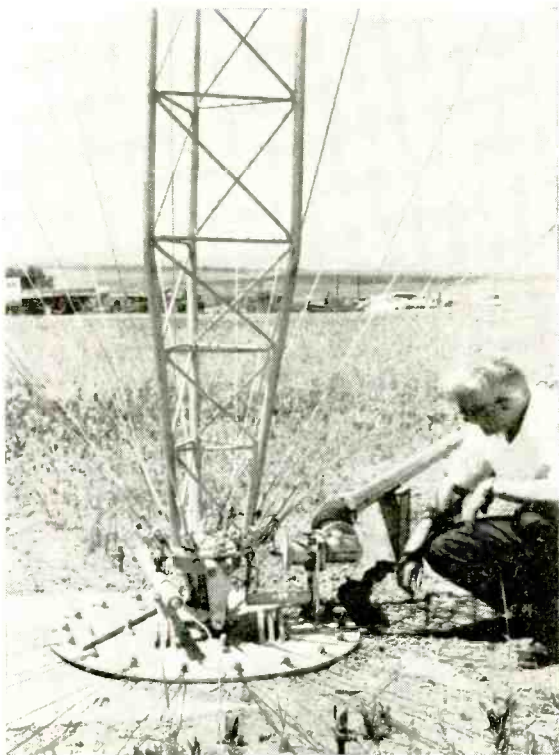


WWV RELOCATES—Construction is nearly completed on the new WWV transmitter building and control center at Fort Collins, Colo., from which the NBS standards broadcast station is scheduled to transmit beginning in December. Photo shows standby antenna fed by $3\frac{1}{8}$ " coax line.


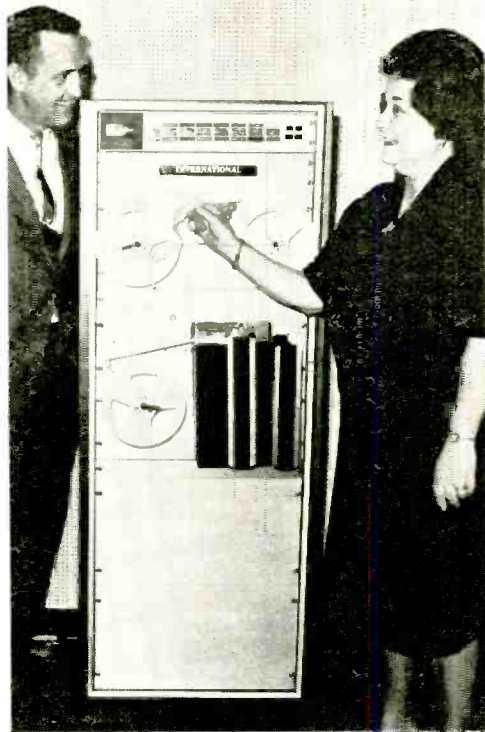
DATEX DATA—A data communications system that transmits 1200 words a minute is now operating between GT&E International's New York headquarters and its Swiss subsidiary in Geneva. Called "Datex," it replaced a "telex" system which had a maximum speed of only 66 wpm.



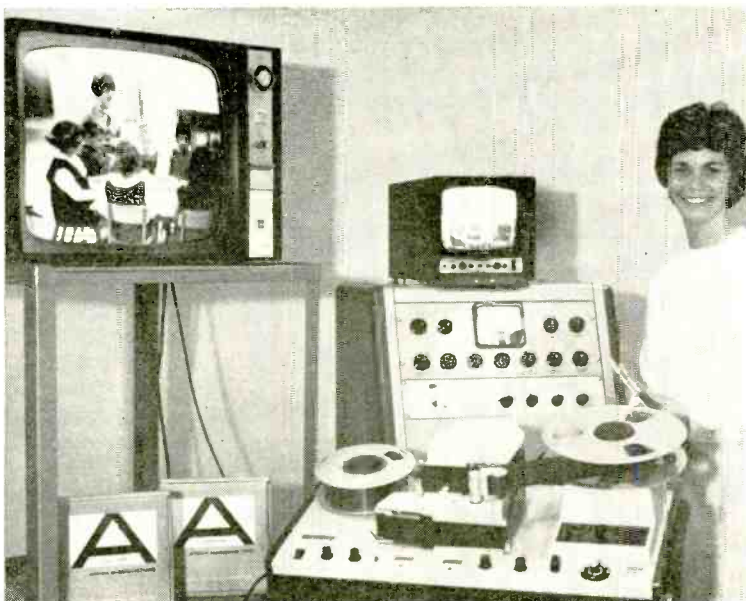CUTTING RED TAPE—Knox College (Ill.) senior Ingrid Bletzer (right) views Ampex video tape recording of her teaching some 40 first grade pupils during a student teaching assignment. Video tape was then sent to prospective employer—and Miss Bletzer got the job.



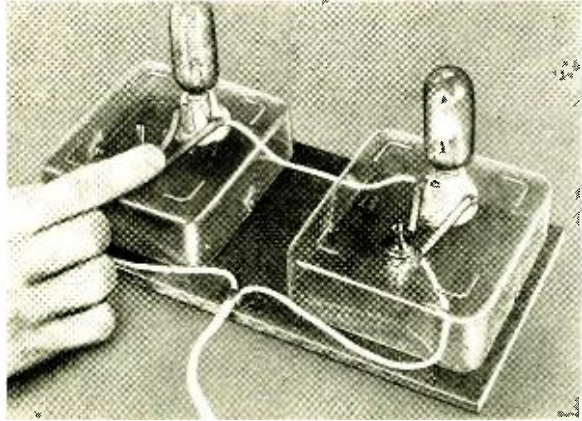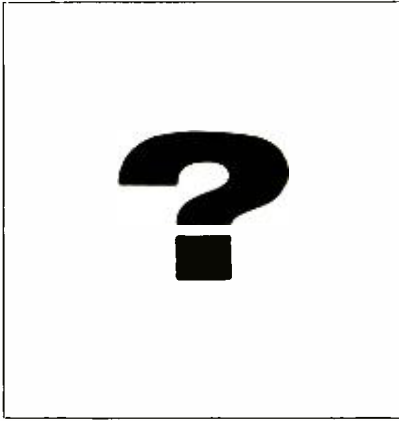TINY TV CAMERA—The vidicon tube has been eliminated in a $6" \times 4" \times 3\frac{1}{2}"$ TV camera designed for NASA by Westinghouse for use in the U.S. space program. Requiring 4 watts of power, the camera uses a solid-state device in the form of a phototransistor mosaic sensor (left) for light-sensing and image conversion.



THE “IMPOSSIBLE” CIRCUIT

BAFFLE THE BOSS ...
CONFUSE YOUR CHUMS ...
JOLT THE NEXTDOOR GENIUS ...
TEASE YOUR TEACHER ...
NAG THE NEIGHBORS ...

By **LUIS VICENS**


YOU CAN do all of these things—and more—just by challenging your technically inclined friends to solve *The Case of the Impossible Circuit*. Pictured below, the circuit is really a very simple affair. It consists of two boxes, *A* and *B*, each of which contains a lamp and a switch. There is a single power line lead to each box and a single connecting lead

between the two boxes. Whenever a.c. power is applied and switch *A* is thrown *ON*, lamp *B* lights. When switch *B* is thrown *ON*, lamp *A* lights. When both switches are *ON*, both lamps light—and when both switches are *OFF*, both lamps are dark.

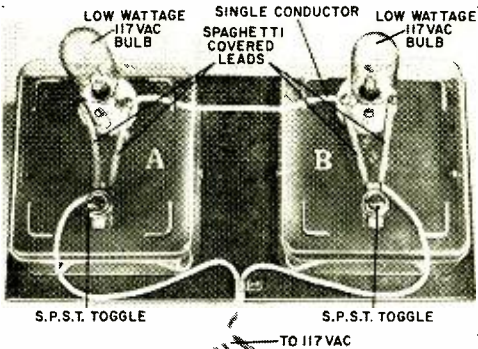Question: *What is the circuitry in each box?*

Clues: Neither box contains amplifiers, transformers, oscillators, nor relays. The circuits are essentially identical in both boxes. The lamps are standard, identical, ordinary household incandescent bulbs. The power source is a standard 117 volts a.c. But, most important—the circuit is a practical one which can be easily duplicated at home, either for demonstration purposes or as part of a science fair project.

If you can't figure it out—or you think you have a solution and want to check it—turn to page 79.




—30—

BUILD AN 80/40 Meter BANDSWITCHING VERTICAL

OR . . . HOW I DECIDED TO
CHANGE BANDS FROM INSIDE THE SHACK

By **LOU DEZETTEL**, W9SFW

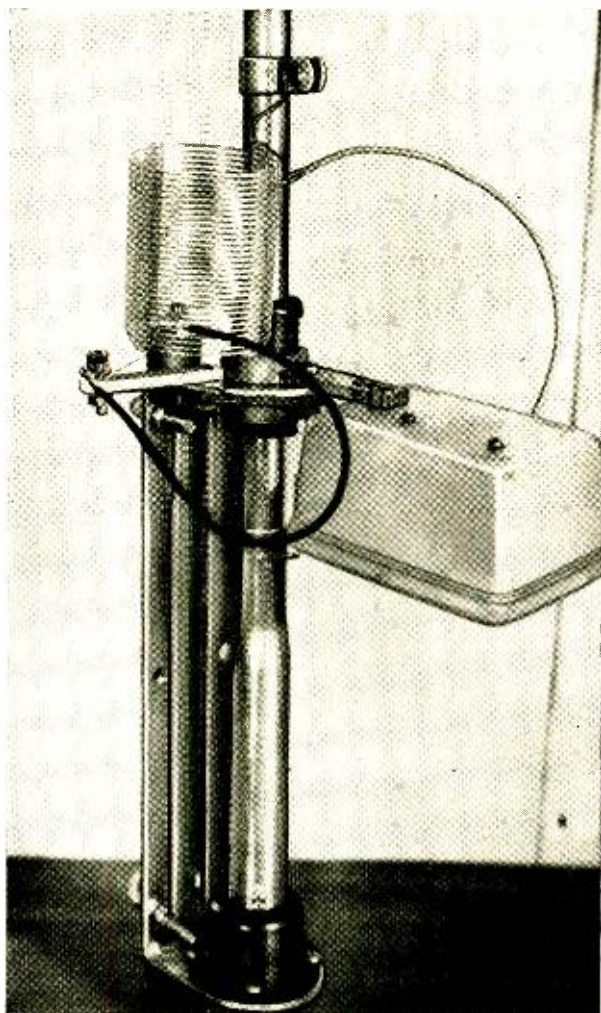



IF CB has nothing else to its credit, it has stimulated the manufacture of vertical antennas. Although many hams preferred vertical antennas in the pre-CB days, it has only been within the past six or seven years that a variety of modestly priced ham-band vertical antennas have been marketed.

Some vertical antennas are designed for switchless operation on 80 or 40, and the higher bands, while others are short verticals (18') with a loading coil at the base. The latter are much cheaper, but necessitate manual band changing—a gruesome task in the cold, wet, or heat.

Use the Feed Line. The problem of band changing can be resolved by placing a s.p.s.t. relay adjacent to the loading coil and controlling the relay action from the ham shack. When the relay contact is open, the loading coil tap for 80-meter operation is in use. When the contact closes, additional turns on the coil are shorted out and the antenna resonates in the 40-meter band.

The beauty of this arrangement is that it is possible to control the relay using

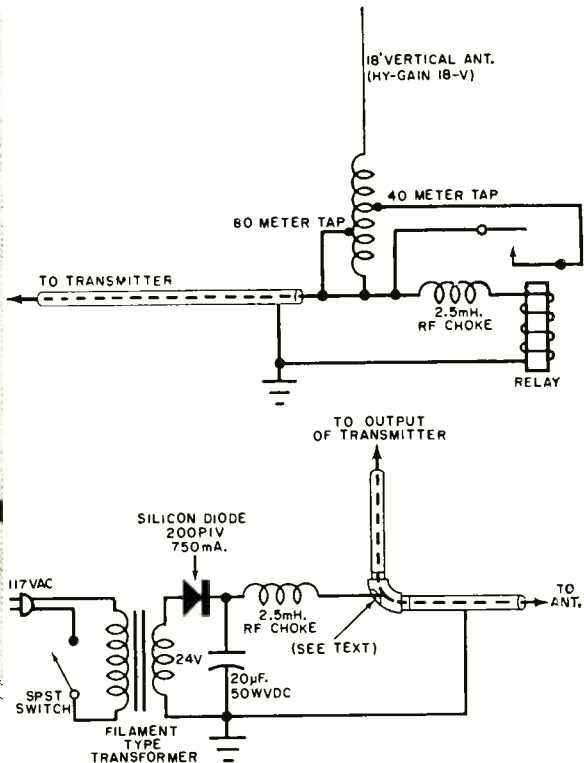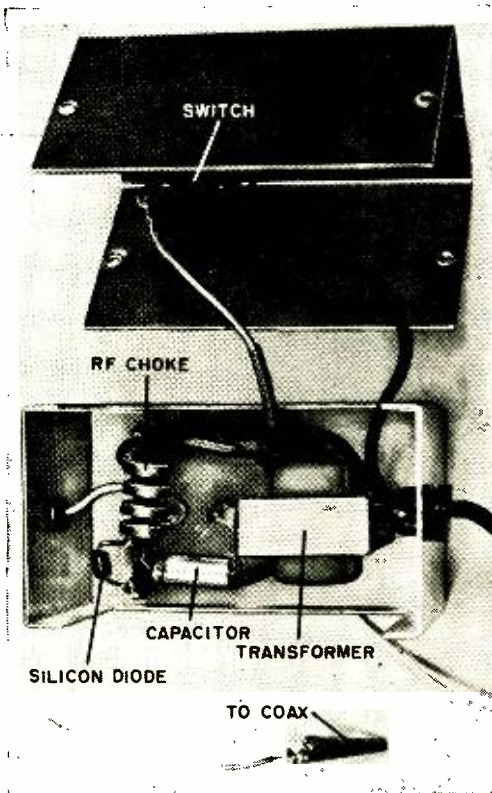The author used an inverted plastic refrigerator dish to "weatherproof" the relay. The heavy black lead is the 80-meter tap and the other lead is the 40-meter tap. Relay shorts out coil when it closes.



All parts needed to operate the antenna relay from the ham shack are mounted in a small metal box. Note in the diagram how the small chokes keep the r.f. out of the relay circuit. See text for elbow details.

the coaxial feed line—there are no extra wires or cables to be installed. The coax can be made to carry low-voltage d.c. from the shack to the relay while the r.f. is isolated by r.f. chokes. The wiring diagram is shown above.


You may find it advantageous to adapt parts from your junk box for this circuit. The author found a 1500-ohm plate circuit relay and used a small audio transformer (wired backwards) for dropping 117 volts a.c. down to 40 volts. The current drain is about 14 mA and the voltage drop about 20 volts. This jury-built arrangement works, but parts that can be purchased are spelled out in the diagram.

There's nothing difficult about building the power supply, but some care must be exercised in attaching the d.c. to the coax. The preferred method is to use a coax "L" connector. Mount the connector firmly in a vise and cut a 45° slice out of the right-angle bend. Solder a short stub of #12 wire to the exposed inner con-

ductor and clip the power supply output to the stub as shown in the photo.

Getting Good Results. If your experience with a vertical antenna is minimal, bear in mind that results will only be as good as the ground under the antenna—not the physical ground, but the electrical ground. A shortened vertical antenna cut for a quarter-wave is really a half-wave antenna turned on end. One-quarter wavelength extends above ground and the other quarter is in the ground itself.

If the antenna coupling network in your transmitter has an r.f. choke or other direct connection to ground, the setup shown here should not be used—to prevent shorting out the d.c. voltage to the relay. You can run a length of bell wire or other single conductor to the relay and use the shield on the coaxial transmission line as a return. Of course, you can simply run a length of two-conductor line cord to the relay and eliminate the tricky wiring. —30—

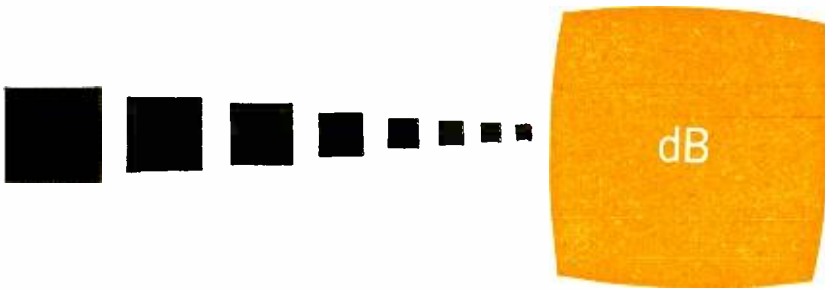

HERE'S HOW TO USE THEM
WITHOUT
RESORTING TO MATHEMATICS

By **MARSHALL LINCOLN**

DID YOU EVER wonder about the strange language you must learn before you can understand these things called decibels? Some of the electronics measurements given in decibels sure look peculiar, don't they?


For instance, how about the spec sheet on a mike that says it has an output of -55 dB? Now, what kind of output is that? If it's minus, it must be less than no output at all! Yet you could connect the mike up to a 10-watt amplifier and rattle the windows with it.

So just what are decibels, anyhow? What use are they to the experimenter, hobbyist or engineer? Can they be measured like volts, amperes, and watts?

The answer to the latter question is a simple *yes*. Volts (and amperes) are specific units of measurements, but they often represent different things and convey different meanings; the significance of 1 volt of d.c. is not the same as the significance of 1 volt of a.c. Neither is 1 volt of a.c. peak the same as 1 volt of a.c. average, or 1 volt of a.c. r.m.s. Beginning to sound complicated? It isn't really, especially if you have worked with these figures, even for only a little while. Actually, working with dB's is not much more complicated than working with volts and amperes; decibels do have their own body of meanings, but they are essentially dimensionless units.



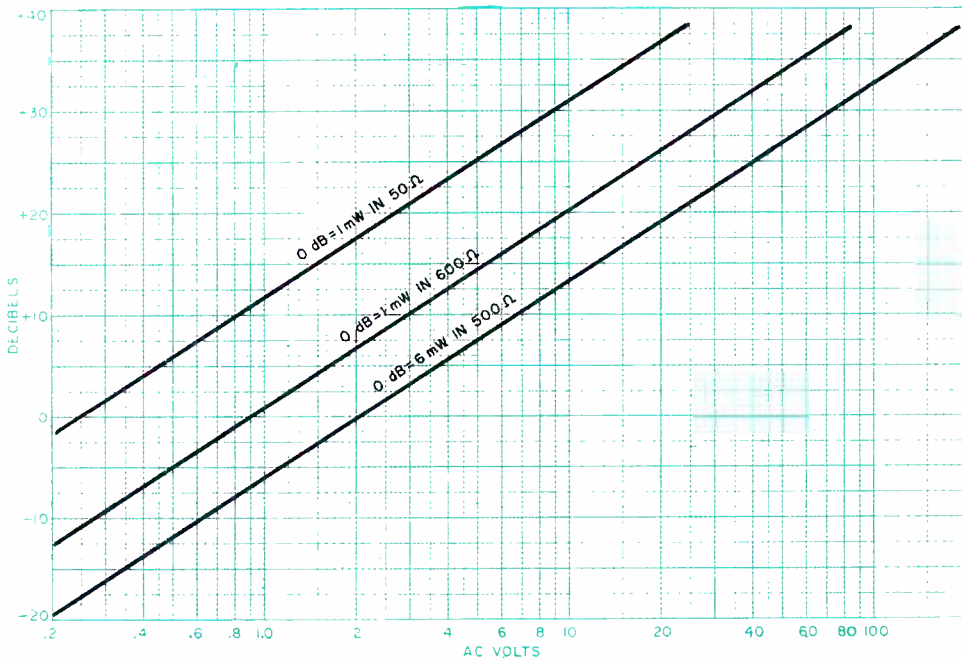**WHAT
ARE
THESE
THINGS
CALLED
DECIBELS?**




AC VOLTS TO DB GRAPH

To convert an a.c. voltage reading on a VOM or VTVM to dB, find the vertical line that coincides with the reading, follow it up to the point where it touches the diagonal line representing the appropriate zero reference level, and read across to the number of dB's. For example, if you are measuring across a 600-ohm impedance and your reading is 20 volts, the chart shows it to be about 28 dB.

Log Scale Confusion. In an effort to figure out why so many people have trouble understanding the significance of decibels (as units of power measurement), the one thing that stands out is that the progression of one decibel after another follows a log scale while most units of measurements follow a linear scale. Even watts (as units of power which are a function of the square law) have a linear characteristic—the power level of 12 watts is twice as large as 6 watts and four times as large as 3 watts. This is easy for most people to understand. But when 12 dB is twice as large as 9 dB, four times as large as 6 dB, eight times as large as 3 dB, 16 times as large as 0 dB, 32 times as large as -3 dB (following a log scale), that's when the trouble begins.

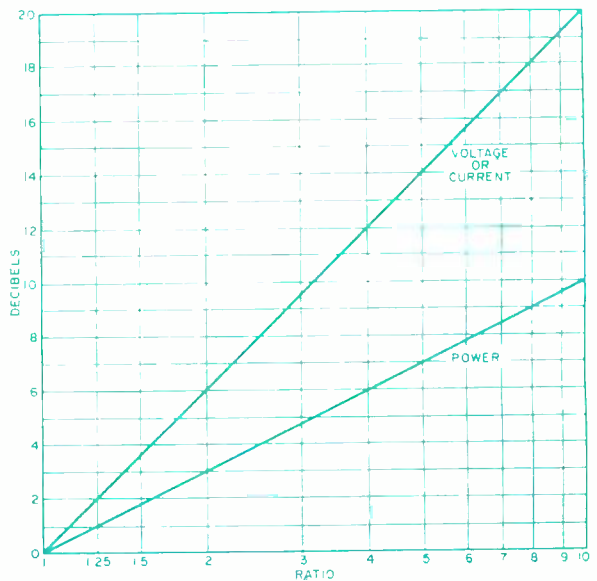It doesn't take much to see that for every 3 dB increase, there is a doubling of the power level, and for every 3 dB



RATIO TO DB GRAPH

To convert output-to-input-signal-ratio to dB, find the ratio on the bottom line, read up to the appropriate diagonal, and then across to find the value in dB. For ratios greater than 10 to 1, multiply the bottom line by 10 and add 10 dB for power (add 20 dB for voltage or current). For ratios of less than 1 to 1, divide the bottom line by 10, and subtract 10 dB for power (subtract 20 dB for voltage or current). For example: the difference in output levels in dB between a 200-watt and a 100-watt amplifier is 3 dB; the gain of an amplifier having a 1-volt input and a 20-volt output is 26 dB.

decrease, there is a halving of the power level. From this you could conclude that the decibel system follows some kind of geometric progression; and if your analytical thinking cap is really sharp, you will see that in the above example each 3 dB represents a *ratio* of one power level to another, on the order of 2 to 1.

Don't go away; that's only part of the story. You now know that 12 dB is twice as large as 9 dB, but how large is 9 dB? You really don't know, at least not yet. What you have so far is a *relative* measurement, not a *specific* one.

Specific Measurements. When decibel measurements are made with respect to a specific standard or reference point, they do have specific meanings, and they can be used just like an absolute measurement to enable you to compare equipment, and to solve audio, r.f., and other electronic problems.

For example, when the gain of an audio amplifier is specified in decibels, the number of dB indicates that the output power is a certain number of times greater (or less) than the input power, or it could mean that the output power is a certain specific amount relative to a *standard reference* level of power. The minus sign (-55 dB) in the microphone specification, for instance, means that this level is *below* that of the standard measurement unit which is used as a reference. This specification doesn't mean the mike is defective, but it does represent a definitive level and is in the form of an absolute measurement which the experimenter, technician, or engineer can understand.

Decibels Vs. Watts. A basic understanding of decibels is a mighty handy measuring stick. With it you can compare audio power levels in speaker systems, gain of audio or r.f. amplifiers, performance of antennas, strength of radio signals, and the loss in audio and r.f. transmission lines—just to name a few applications.

Wait a minute, you might say, what's wrong with using watts as a measure of power and as a basis for comparison of signals and equipment? Nothing really—it can be done, but not without a lot of meaningless confusion.

FOR MATHEMATICIANS ONLY

If you like to work with formulas, and if logarithms are no mystery to you, here are the formulas that were used to develop the tables and graphs and to trigger some of the comments in this article:

$$\text{dB} = 10 \log \frac{P_2}{P_1}$$

where dB = decibels, P_2 = power output in watts, and P_1 = power input in watts.

$$\text{dB} = 20 \log \frac{E_2}{E_1}$$

where E_2 = signal voltage output, and E_1 signal voltage input. The use of 20 times the log instead of 10 times the log when working with voltage and current is due to the fact that power is equal to E^2/Z , or I^2Z , which makes the "long form" of the formula for power ratio look like:

FOR VOLTAGE

$$\text{dB} = 10 \log \frac{(E_2)^2}{(E_1)^2} + 10 \log \frac{Z_1}{Z_2}$$

FOR CURRENT

$$\text{dB} = 10 \log \frac{(I_2)^2}{(I_1)^2} + 10 \log \frac{Z_2}{Z_1}$$

where Z_2 = output impedance, Z_1 = input impedance, I_2 = current output, and I_1 = current input.

Since the log of a squared number is double the log of the same number not squared, it is sufficient to show the formula as $20 \log E_2/E_1$ or $20 \log I_2/I_1$, if the input and output impedance is the same. The $+10 \log$ of Z_1/Z_2 is simply the correction factor that must be added if voltage measurements are made across different impedances. When Z_1 and Z_2 are equal, their ratio is 1; the log of 1 is 0; 10 times 0 is 0; therefore, no correction is needed for measurements across equal impedances. (Notice that for current measurements Z_1 and Z_2 are reversed.)

The above formulas for voltage and current are valid only if output and input measurements are made across the same impedance, unless a correction factor is used.

If you are using a meter calibrated to 0 dB = 1 mW in 600 ohms and measuring power levels across different impedances, you can find the correction factor in dB and add it to your readings by using the following formula:

$$\text{dB} = 10 \log \frac{600}{Z}$$

For a meter calibrated to 0 dB = 6 mW in 500 ohms, use:

$$\text{dB} = 10 \log \frac{500}{Z}$$

For example, consider a change in a certain amplifier's output from 1 watt to 2 watts, and a change in another amplifier's output from 10 watts to 11 watts. In both amplifiers the change was only 1 watt, yet in the first case the change represented a doubling of power, and in the latter case an increase of only 10%. So you can see that even with watts you must relate your measurements, know their significance, and be able to develop a ratio, or a percentile, or what have you.

VOLTMETER SCALE FACTORS			
0 dB = 1 mW in 600 ohms		0 dB = 6 mW in 500 ohms	
Scale (volts)	Add (dB)	Scale (volts)	Add (dB)
5	10	2.5	0
50	30	10	12
150	40	50	26
500	50	250	40
1500	60	1000	52

Table 1. For meters equipped with a dB calibrated dial, simply add the number of dB to your reading, according to the a.c.-volt scale you are using and the zero reference level of the calibrations.

When decibels are used, they have a unique way of representing a ratio or relationship of one power level to another. When it is said that every 3 dB increase represents a doubling of power, just that is meant, whether you are going from 3 dB to 6 dB, or from 100 dB to 103 dB.

Decibels Minus Math. The basic unit for measuring power ratio is the *bel* (B), named for Alexander Graham Bell, inventor of the telephone and a pioneer in audio research. The bel is too large for most electronic measurements, so the decibel (dB), which is equal to 1/10 bel, is generally used. Decibels can be derived by comparing different quantities of power, or voltage, or current.

Decibel calculations with formulas require the use of logarithms, which are an obstacle to many people, and while it's a small hurdle which can be easily overcome, there is an easier way to work with decibels—without formulas. You can use a graphic method and you can work with meters, oscilloscopes, etc.

Essentially, the meters function as a.c. voltmeters and many of them are calibrated in dB to enable you to make measurements directly, and to eliminate the paper and pencil work.

These absolute types of measurements are made possible through the establishment of certain standards for measuring power levels. These standards set forth a "reference level" (zero dB level), and if you work within the framework of the standards you will have done much to eliminate confusion and double-talk. The standards make it possible to express a single dB figure above or below the reference level, and have it make sense. This is what is done in the case of microphones, speakers, S-meters, tape recorders, etc.

The most common "zero dB reference level" used today, particularly in audio work is 1 milliwatt dissipated in a 600-ohm load at 1000 Hz. Remember, this zero dB level is not a zero output level. Any power level above this zero dB level is designated in positive dB, and any power below it is referred to in negative dB.

Another reference level sometimes encountered is 6 milliwatts in a 500-ohm load, and occasionally other standards are used.

Standards come and go, and zero dB reference levels have been changing accordingly. The dBm is now in vogue and is the most commonly used reference level. It's another way of saying 1 mW in 600 ohms.


The volume unit (vu), a favorite of the audio and telephone industries, is also based on the same reference level as the dBm, except that vu's are used to represent complex waveforms as encountered in voice and music, while dBm's are used in making measurements of simple sine waves. Since vu's represent average levels in a waveform, it is taboo to work with dBm when you should be working with vu and vice versa.

Meter Calibration and dB Readings. The way to tell for sure how your meter is calibrated is to notice what point on the a.c. voltage scale corresponds to zero on the dB scale. If it's 0.775 volt, the meter is calibrated using 1 mW in 600 ohms. If the zero dB point on the

(Continued on page 117)

THE "IMPOSSIBLE" CIRCUIT

MADE POSSIBLE

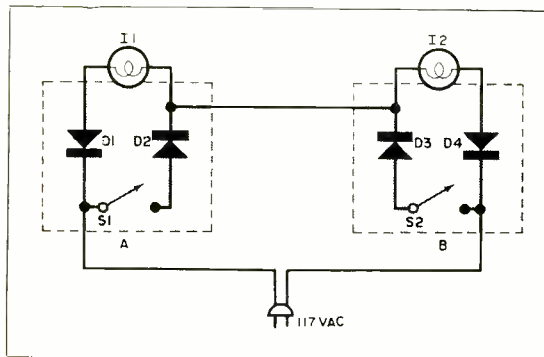

ARE YOU STUMPED by the "Impossible" Circuit on page 72? If so, don't be despondent—this seemingly innocent circuit has stumped even the best electronics engineers.

The "trick" in solving the circuit is to *think simple*. Obviously it is not a complicated design using multiple switches, tuned circuits, tunnel diodes, crossbar networks, filters, interlocked gate circuits, or similar techniques.

How "Impossible" Circuit Works. The circuit uses four standard diodes in addition to the lamps and switches. Circuit operation is possible because (A) diodes are unidirectional devices, permitting current flow only in one direction, and (B) an a.c. power source is used.

If both switches are open, the only current path is through diode *D1*, lamp *I1*, lamp *I2* and diode *D4*. But diodes *D1* and *D4* are connected "back to back" and each blocks current flow on alternate half-cycles. As a result, when the switches are both *OFF*, little current flows and the two lamps remain dark.

Suppose that switch *S1* on box *A* is closed. Diodes *D2* and *D4* are now connected in a series-aiding configuration on either side of *I2*. On alternate half-cycles current can flow through *S1*, *D2*, *I2*, and *D4*, and the lamp lights. Lamp *I1* remains dark because current flow through it is still blocked by *D1*.

Similarly, if switch *S1* is open and switch *S2* is closed, diodes *D1* and *D3* are in series, and current can flow through *D1*, *I1*, *D3* and *S2* on alternate

half-cycles. Lamp *I1* lights, and lamp *I2* remains dark, for current flow through it is blocked by *D4*.

When both switches are closed, both lamps light, but each only on *alternate* half-cycles of the applied a.c. voltage. However, the thermal lag of the incandescent filaments and persistence of vision combine to produce what appears to be a steady glow, so both lamps seem to be on simultaneously.

Assembling the Circuit. A demonstration model of the "Impossible" circuit can be assembled in a single evening. Neither layout nor lead dress is critical, nor—for that matter—are the component parts. Either standard (Edison) base or candelabra lamp bulbs can be used. The lamps are familiar 117-volt incandescent types, rated at from 7 to 60 watts—take your pick! The switches can be toggle, slide, push-button or rotary s.p.s.t. switches, while the diodes (*D1* through *D4*) may be anything with a 200-PIV (or higher) voltage rating and a 1-ampere (or more) current rating.

The boxes should be of transparent plastic and mounted on a sturdy base, with the external wiring clearly visible. Use an insulating material for the base, such as wood, Masonite, or clear plastic, to avoid the suspicion of a "ground return." The subminiature diodes (International Rectifier Type 804) can be concealed in short lengths of tight-fitting spaghetti tubing.

With *all* wiring apparently visible, the circuit becomes—as the King of Siam would say—a real *puzzlement!* —50—

UNPOPULAR ELECTRONIKS

A SALUTE TO THE
FAILURES IN
EXPERIMENTAL ELECTRONICS

By **CARL KOHLER**

It's a proven theory that into every pastime a little bane must crawl—and the fine old field of electronics is no exception. Populated for the most part by brilliant, inventive people, the electronics hobby has also known its dismal share of dubious types. The otherwise respectable history of electronics is spotted by militantly neurotic individuals whose various obsessions have added nothing to ham radio, SWL'ing, CB'ing, etc. Shown here is a small handful of nuts whose collective quasi-creativity certainly classifies them as "Electroniks." This clumsily minted term aptly describes these bohemians who have vainly wielded screwdriver and soldering gun with a breathtaking lack of success.



SEAN GONNN intrepidly ignored the Reciprocity Theory and succeeded in developing his distinctive "Gonnn Boomerang Signal" which—upon being transmitted—instantaneously returned and thoroughly deactivated its own R/C transceiver.




HYRAM VON KRUUNK labored over his concept of an automatic turntable featuring a specially designed tone arm. The design permitted the stylus to move from corner to corner as Hynam played his vast collection of square Wayne King, square Guy Lombardo, and square Lawrence Welk platters.




LOTHAR SYMTH-SYMTH shrewdly framed his copper-clad laminated etched circuit boards and profitably sold them as electronics abstractions—mainly because all of the circuits were inoperative. No one told Lothar that the copper background is etched off, not the connecting strips.



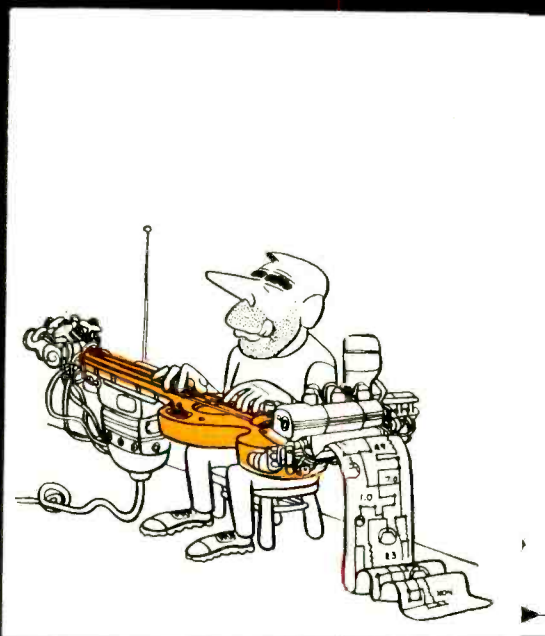MARIO SILVERGOLD tackled the formidable task of composing a rather stirring essay on Plasmonics and Hydronics without once mentioning water. This was not a trivial accomplishment since the entire manuscript was in layman's Sanskrit.



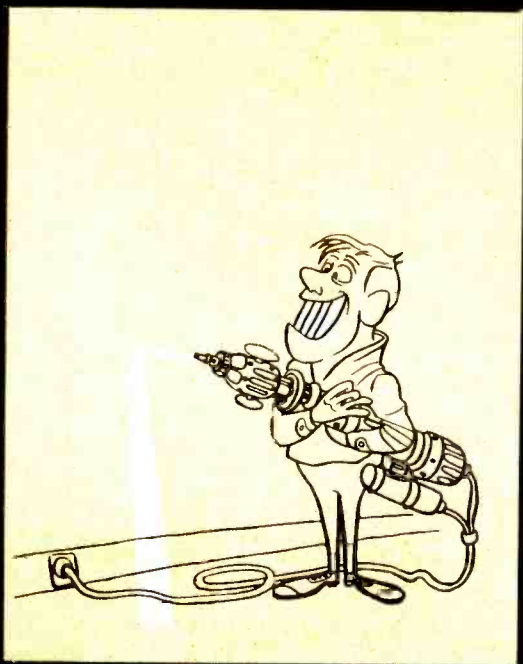NOAH TERWILLIGER ingeniously designed and constructed an electronically controlled instrument that produced graphic sketches of wiring schematics from tonal patterns. However, all of the sketches morbidly tended to induce disastrous feedback.



EUSTACE ROUNK diligently studied Laser Beam theory for many years for the sole purpose of perpetrating a practical joke. His energyless "Roonk Lazier Beam" always fell short of the mark.



MORDECAI GHEE, a CB malcontent, sat patiently for more than 33 hours waiting to "break" channel 9. When the opportunity arose, this unfrocked eavesdropper had forgotten what he wanted to say.

REFLEXOMETER REFLECTIONS

READERS MODIFY GAME CIRCUIT TO EARN CASH AWARDS


THERE MAY BE more ways to skin a cat, but there are almost as many ways to build a "Reflexometer." In the March, 1966, POPULAR ELECTRONICS, on page 47, there is a pretty young lady testing her skill at the game of "Reflex." The idea is to avoid "flinching" while trying to respond to a situation faster than the competition. Whether it's the reaction to the roll of a pair of dice or the winner of a slot-car race, the Reflexometer tells who or what responded first; second best, no matter how tricky, sneaky, or cheaty, just doesn't get paid off.

The original gadget was equipped with four-pole, double-throw relays. Since it was published, many readers have sent in versions of their own to let us know how they can do it better, easier, and much cheaper; how to add bells and buzzers; and even how to eliminate the relays altogether. Most of the ideas received looked like they would work satisfactorily; some circuits were more complex and some were quite simple.


In the "Letters from Our Readers"

column, June, 1966, we agreed to present in a future issue the best or most unusual modifications, for which cash prizes would be offered. Well, here are the best three entries. Seven cash awards were sent out because five readers sent in the same suggestion.

Simpler Relays. The identical modification was submitted by Rex R. Rickly of Columbus, Ohio; Carl Stanislawski of Adelphi, Md.; John Pobanz of Athens, Ohio; Donald O. Wurst of Wright Patterson Air Force Base, Ohio; and F. I. Shoaf of Clemmons, N.C. Their circuit contains d.p.d.t. relays in place of the 4-p.d.t. relays in the original circuit. The first person who presses the button causes his relay to energize. This throws the relay contacts into their alternate position. The upper pair of contacts disarms all other opponents' switches, and the lower contacts hold the relay closed since the holding circuit is completed to ground. The circuit is reset for another round with S5. (See diagram below).

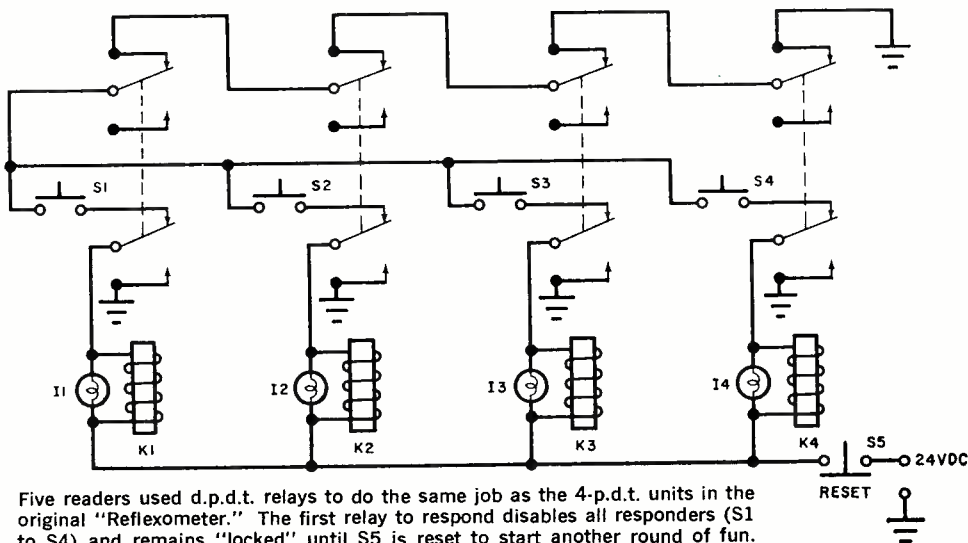

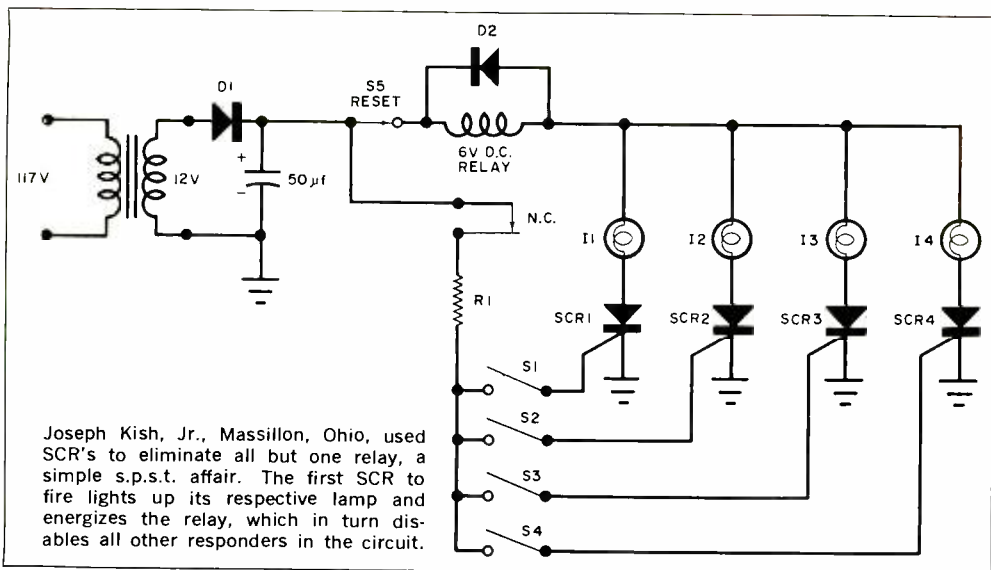
Five readers used d.p.d.t. relays to do the same job as the 4-p.d.t. units in the original "Reflexometer." The first relay to respond disables all responders (S1 to S4) and remains "locked" until S5 is reset to start another round of fun.



Silicon Controlled Rectifiers. Joseph Kish, Jr., of Massillon, Ohio, used silicon controlled rectifiers (SCR's) to replace the relays. The player who closes his switch first sends a pulse to the related SCR, triggers it into conduction, and causes the lamp to light. When this happens, the single relay energizes, and "disarms" the other players' switches.

No Relays. John T. Hunt, of Pittsburgh, Pa., was honest enough to tell us that the circuit he submitted came from

"Signalite Application News," a monthly publication put out by Signalite, Inc. The ability of this circuit to tell who is first, second, third, and fourth, as well as its simplicity, is responsible for its being a winner. The first player to respond causes all three of his lights to go on. The second, third, and fourth responders cause two, one, and no lights to fire, respectively. The switches are of the regular on/off type since they must remain *ON* to register. To play another round, switches are reset to *OFF*. 50-

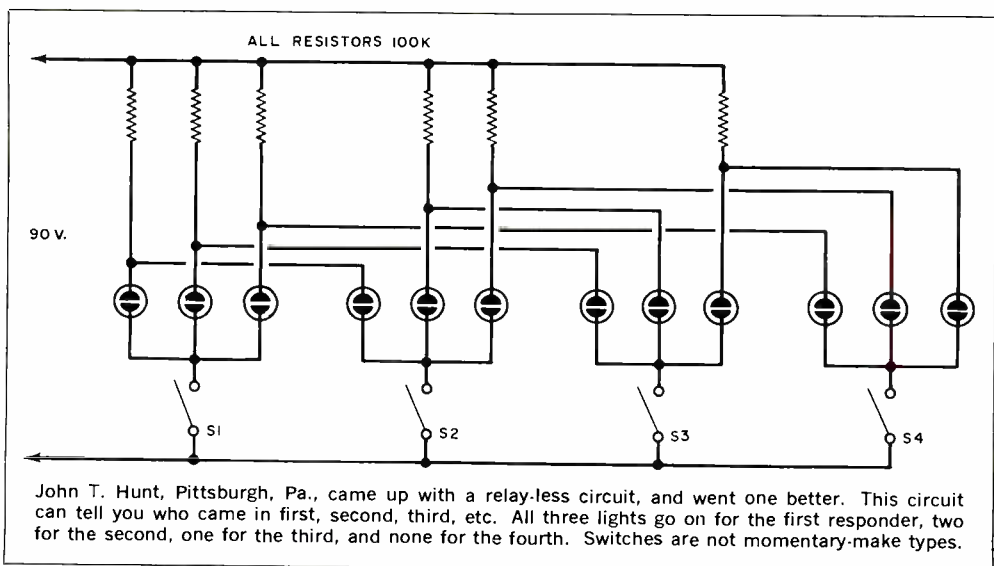



SOLID STATE

By LOU GARNER, Semiconductor Editor

EVERY solid-state circuit, no matter how efficient, requires a power supply of some kind. Without question, the most popular power source is the dry battery, since it furnishes a fixed d.c. which can be divided down with dropping resistors or raised to any desired level by adding more batteries in series. Alternating current can also be used to provide the necessary d.c. operating power, once it is stepped down with a transformer, then rectified and filtered. The only drawback here is that such an arrangement is not truly portable. Of course, portability could be achieved if we used an a.c. battery as the primary source instead of the a.c. power line. What? . . . you never heard of an a.c. battery?

The truth is that such a battery has been little more than a dream. In fact, back in the good old days, apprentice electronic technicians were often sent on fools' errands to the supply room to pick up a.c. batteries, much in the same spirit that apprentice machinists were sent to the tool crib for left-handed monkey wrenches. While left-handed monkey wrenches are still as rare as hens' teeth, a.c. batteries may be commercially available within a couple of years!

Engineers of the U.S. Army Electronics Command (Fort Monmouth, N.J.) have developed a battery that is the closest thing yet to an "a.c. battery." About the size of two standard flashlight cells, the unit delivers a pulsating current with its own characteristic waveform and frequency. Prototypes having a peak voltage of 0.8 volt and peak currents of nearly 400 mA have been produced.

Although these units generate power at only 15 Hz, Army engineers hope to develop future models with frequencies of up to 50 Hz. According to a report released by the U.S. Department of Commerce, the batteries use platinum anodes and lead-lead dioxide cathodes, with the electrolyte consisting of formaldehyde dissolved in sulphuric acid.

Another interesting development in the battery field has been announced by the Olin Mathieson Chemical Corp. (460 Park Ave., New York, N.Y. 10022) . . . a battery with a self-contained detector that indicates its condition. Carrying the Winchester

brand, it consists of a 1½-volt D-size cell equipped with a built-in "Sight-Test" top. The detector is a litmus indicator with a clear plastic overlay. As long as the indicator remains blue, the cell is in good condition. The blueness gradually fades as the cell becomes weak, eventually changing to pink when the cell becomes unserviceable.

Reader's Circuit. Would you believe that a complete audio power amplifier could be made up of only three transistors and no other components? How about an amplifier with three transistors, one resistor and one capacitor? You're not buying that either? Then look at the circuit illustrated in Fig. 1. Switch *S1*, input jack *J1*, and gain control *R1*, are optional; and the loudspeaker (*SPKR*) and power supply *B1* are accessories . . . hence the amplifier proper consists only of *C1*, *R2* and the three transistors—*Q1*, *Q2* and *Q3*.

This simple, but interesting, circuit was submitted by reader Scott Marovich (2407 S. Rose St., Kalamazoo, Mich.), who writes that he has assembled several successful versions using an almost random selection of components, supply voltages, and speaker impedances. He writes, further, that he has achieved multi-watt operation with reason-

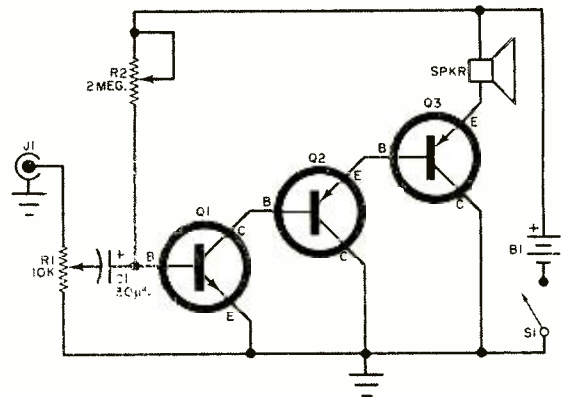


Fig. 1. Audio amplifier featuring input transistor *Q1* direct-coupled to Darlington pair *Q2-Q3*. Overall gain is product of the betas of the transistors.

able fidelity and acceptable bass response. (Wonder if he means milliwatts?)

Surprisingly enough, Scott's circuit is a familiar one to design engineers. It is seldom used in commercial equipment, however, because of its relatively low efficiency (which it shares with all Class A amplifiers), critical bias adjustment, and sensitivity to temperature changes. But, for general use in the home and experimental applications in the lab, this amplifier is hard to beat so far as economy, versatility, and simplicity are concerned.

An input signal at *J1* appears across *R1*, the gain control. Part of this signal, depending on *R1*'s setting, is applied to *Q1*'s base-emitter circuit through capacitor *C1*. Transistor *Q1* is direct-coupled to *Q2* and *Q3*, driving the loudspeaker's voice coil which acts as a low-impedance load. Circuit power is furnished by *B1* through switch *S1*.

Performance can vary considerably from one such amplifier to another, depending on the characteristics of the transistors used. With direct coupling employed throughout, *Q1*'s base bias, established by series resistor *R2*, determines the operating conditions for the entire amplifier. Thus, the adjustment of *R2* can be quite critical. Furthermore, any variation in *Q1*'s base current, such as that produced by temperature changes, can affect overall circuit operation.

Transistor *Q1* is a general-purpose *npn* type similar to the 2N170. Transistor *Q2* is a low-signal *pnp* type such as a CK722 or 2N109. The output transistor, *Q3*, is a medium-to-high power *pnp* type equivalent to the 2N256, 2N301, or 2N441. Jack *J1* is a conventional phono type, and *S1* is any old s.p.s.t. toggle or slide switch. Potentiometers *R1* and *R2* are standard units.

The speaker is a PM type; use any size from 4" to 10", and any impedance from 4 to 16 ohms. The power supply, too, is not critical, and the rating of *B1* can vary from as little as 3 volts to as much as 18 volts . . . but it should be capable of supplying several hundred milliamperes. Finally, the coupling capacitor, *C1*, may be any value from 20 to 50 μF , with any voltage rating from 15 to 25 volts.

The only transistor that requires a heat sink is *Q3*. This can be the metal chassis (if one is used), or a fair-sized commercial heat sink if the unit is assembled on a perforated phenolic board or printed circuit board. Be sure to keep input leads short and direct, and allow a wide separation between input and output circuits.

Once the wiring is completed and checked, the speaker and battery can be connected. With an audio signal applied to *J1*, turn on the amplifier and adjust gain control *R1* to its mid-position. Then adjust *R2* for the best compromise between maximum gain

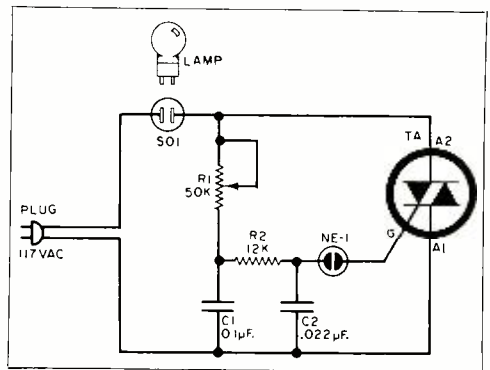


Fig. 2. Lamp-dimming circuit capable of handling up to 2.5 amperes on a continuous basis employs Triac switch (TA) to control current through lamp.

and low distortion. Depending on the signal source, *R1* may require readjustment to prevent overload. If high-gain transistors are used in the circuit, it may be necessary to connect a 1- or 2-megohm resistor in series with *R2* (or to replace this unit with a 5-megohm control) to obtain a satisfactory bias setting.

Manufacturer's Circuit. Featuring RCA's new low-cost, sensitive-gate "Triac," the circuit illustrated in Fig. 2 permits the easy control of lamps and a.c. household appliances. Unlike the familiar SCR, which is a unidirectional device and, therefore, conducts only on alternate half-cycles, the Triac is a bi-directional switch and thus permits the full-range control of circuit current. The lamp dimming circuit shown can handle currents of up to 2.5 amperes, r.m.s., and peak surges as high as 18 amperes.

Average current through the lamp is controlled by the conduction period of the Triac (TA). In operation, the Triac is switched from a nonconducting high-resistance state to a conducting state by the application of a trigger signal to its gate (G) electrode. This switching signal is obtained from a phase-shift network, *R1-C1*, and coupled through an RC integrator *R2-C2*, and a neon bulb (NE-1), to TA's gate. The Triac's average conduction period, then, depends on the phase relationship between the line voltage and its gate signal.

The dimmer can be easily duplicated, since the circuit uses standard parts. Potentiometer *R1* is a standard radio pot. *R2* a half-watt resistor. Capacitor *C1* is a 200-volt tubular paper type and *C2* can be either a ceramic or paper capacitor. The neon bulb is a type NE-83. Triac TA currently carries RCA type number TA2893, but this designation may be changed at a later date to a standard EIA number.

(Continued on page 119)

In today's electronics boom, the demand for men with technical education is far greater than the supply of graduate engineers. Thousands of real engineering jobs are being filled by men without engineering degrees—provided they are thoroughly trained in basic electronic theory and modern application. The pay is good, the future is bright...and the training can now be acquired at home—on your own time.

How to become a “Non-Degree Engineer”



The electronics boom has created a new breed of professional man—the non-degree engineer. Depending on the branch of electronics he's in, he may "ride herd" over a flock of computers, run a powerful TV transmitter, supervise a service or maintenance department, or work side by side with distinguished scientists on a new discovery.

But you do need to know more than soldering connections, testing circuits and replacing components. You need to really know the fundamentals of electronics.

How can you pick up this necessary knowledge? Many of today's non-degree engineers learned their electronics at home. In fact, some authorities feel that a home study course is the *best* way. *Popular Electronics* said:

"By its very nature, home study develops your ability to analyze and extract information as well as to strengthen your sense of responsibility and initiative."

Cleveland Method Makes It Easy

If you decide to advance your career through home study, it's best to pick a school that *specializes* in the home study method. Electronics is complicated enough without trying to learn it from texts and lessons that were designed for the classroom instead of the home.

The Cleveland Institute concentrates on home study exclusively. Over the last 30 years it has devel-

oped techniques that make learning at home easy, even if you once had trouble studying. Your instructor gives the lessons and questions you send in his undivided personal attention—it's like being the only student in his "class." He not only grades your work, he analyzes it. And he mails back his corrections and comments the same day he gets your lessons, so you read his notations while everything is still fresh in your mind.

Students who have taken other courses often comment on how much more they learn from CIE. Says Mark E. Newland of Santa Maria, Calif.:

"Of 11 different correspondence courses I've taken, CIE's was the best prepared, most interesting, and easiest to understand. I passed my 1st Class FCC exam after completing my course, and have increased my earnings by \$120 a month."

Always Up-to-Date

Because of rapid developments in electronics, CIE courses are constantly being revised. This year's courses include up-to-the-minute lessons in Microminiaturization, Laser Theory and Application, Suppressed Carrier Modulation, Single Sideband Techniques, Logical Troubleshooting, Boolean Algebra, Pulse Theory, Timebase Generators...and many more.

CIE Assures You an FCC License

The Cleveland method of training is so successful that better than 9 out

of 10 CIE men who take the FCC exam pass it—and on their first try. This is despite the fact that, among non-CIE men, 2 out of every 3 who take the exam fail! That's why CIE can promise in writing to refund your tuition in full if you complete one of its FCC courses and fail to pass the licensing exam.

This Book Can Help You

Thousands who are advancing their electronics careers started by reading our famous book, "How To Succeed in Electronics." It tells of many non-degree engineering jobs and other electronics careers open to men with the proper training. And it tells which courses of study best prepare you for the work you want.

If you would like to cash in on the electronics boom, let us send you this 40-page book free.

Just fill out and mail the attached card. Or, if the card is missing, write to:

CIE Cleveland Institute of Electronics

1776 E. 17th St., Dept. PE-45
Cleveland, Ohio 44114

Accredited Member National Home Study Council

VETERANS

If you had active duty in any branch of the Armed Forces after January 31, 1955, you may be entitled to Government-paid tuition for any CIE course.





BUILD A STICK-SHIFT ELECTRIC SHAVER



ADAPTER FOR
BRISK
WHISKER WHISKING

IN ORDER TO make electric shavers "universal" and capable of operating on both a.c. and d.c., there has to be a design compromise in the motor. Most electric shavers will cut faster and smoother if operated from d.c., or even pulsating d.c. But occasionally you may want to slow the electric razor down, and this gadget was built so that "High" and "Regular" speed control could be provided.


Mounting and wiring of the components is obvious from the photographs. A d.p.d.t. slide switch was used so that the extra terminals could be employed as tie points to support some of the wiring. Diode *D1* can be any silicon rectifier diode with a rating of 400 volts PIV and 750 mA. Don't ground any of the wires intentionally or accidentally to the metal box.

To use the shaving aid, simply plug it into a convenient outlet, set the slide switch to "High" or "Regular" speed, plug in your shaver, and you're in business. For maximum convenience—if your shaver is only used in the bathroom—replace plug *P1* with a short length of zip cord and a suitable a.c. cap. and mount the box on the wall.

—Ryder Wilson

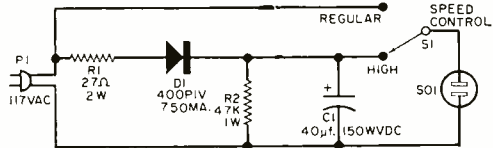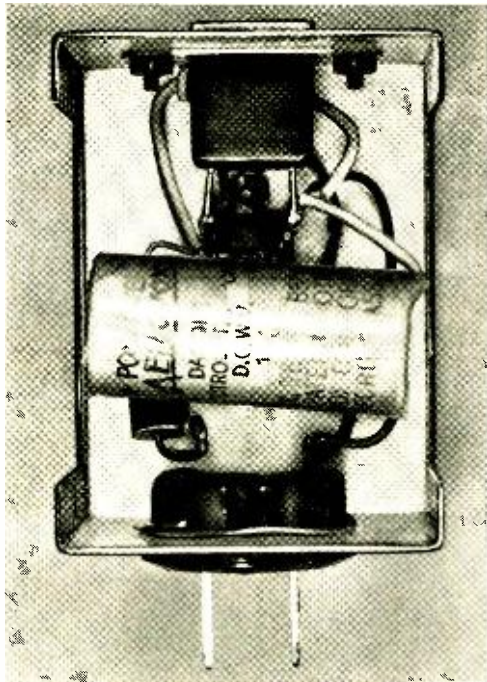

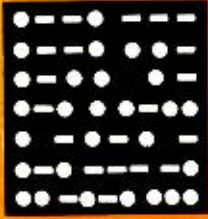You can house this handy electric shaver adapter in a small metal box using an Amphenol 61-M-1 a.c. plug at *P1* and a chassis receptacle at socket *S01*. Float all of the wiring, and make certain that none of the components accidentally shorts to the box.



AMATEUR RADIO

By **HERB S. BRIER**, W9EGQ
Amateur Radio Editor

THUMBNAIL REVIEW OF "DUO-BANDER 84" SSB TRANSCEIVER

CONSIDERING the number of amateurs who operate exclusively on the 75- and 40-meter phone bands, it was inevitable that some manufacturer would eventually come up with an SSB transceiver for these bands. The one who did it first is World Radio Laboratories, Inc. (3415 West Broadway, Council Bluffs, Iowa), and the transceiver is the WRL "Duo-Bander 84."

The announced intention of WRL in designing the new unit was to give 75- and 40-meter operators the most mileage for the least money in a ready-to-operate SSB transceiver. To achieve this aim, the 9-tube, 7-transistor, 4-diode circuit has been divested of all unnecessary frills; but, after observing the Duo-Bander in operation at two separate locations, your Amateur Radio Editor can report that nothing essential to good performance has been omitted.

The balanced modulator and crystal-lattice filter produce a clean lower sideband signal with excellent suppression of carrier and unwanted sidebands. Both the transmit and receive modes are VFO-controlled. When the "Duo-Bander 84" is used with either its companion 117-volt a.c. power supply or 12-volt d.c. supply, power input is 300 watts, PEP, on both 75 and 40



meters. (A light-duty, 260-watt a.c. power supply is also available.)

Selectivity on receiving is 2.7 kHz, and sensitivity—rated at 1 μ V—is more than sufficient to give full output from the built-in loudspeaker for any signal above the noise level on either band. And the unit's a.g.c. system works equally well on transmit and receive modes.

At its price of \$159.95, plus \$79.95 for the deluxe a.c. power supply or \$49.95 for the economy power supply, and \$89.95 for the 12-volt mobile power supply, this transceiver should satisfy the amateur on a limited budget who wants a good, basic, 75- and 40-meter SSB transceiver either for fixed-station or mobile work.

Walter Stein, WA5IYK, trustee for station W5TAC located at the Dallas Home and Hospital for Jewish Aged in Texas, is shown demonstrating the station to four residents of the home. The equipment consists of a Galaxy V, 300-watt, CW/SSB transceiver, remote VFO, and deluxe control console. We are sending WA5IYK a one-year subscription (for the pleasure of the residents) for submitting the winner for October in our Amateur Station of the Month photo contest. To enter the contest, send us a clear photo of your station with you at the controls, and some details on your ham career and the equipment you use. Entries go to: Amateur Radio Contest, c/o Herb S. Brier, Box 678, Gary, Indiana 46401.

AMATEUR STATION OF THE MONTH



UPDATED "SECOND OP" AVAILABLE

If you're looking for a handy guide to foreign postal rates, DX country prefixes, great circle bearings, time differentials, etc., you can't afford to be without the new W9IOP "Second Op." This is the fourth revision of the popular rotary slide rule. Also listed on the "Second Op" are the QSL bureaus around the world, WAZ zone designations, continent location, and spaces for maintaining a country QSO and QSL record. Sold by many radio parts jobbers, the updated "Second Op" can also be ordered directly from W9IOP, Electro-Voice, Inc., Buchanan, Mich. Price: \$1.00.

Amateur Radio Hall of Fame. An International Amateur Hall of Fame is being organized to provide permanent recognition of individual contributions made by hams around the world to the advancement of amateur radio. Each year five amateurs will be honored by having their names and call letters inscribed on a plaque to be displayed on the premises of the International Amateur Radio Club in Geneva, Switzerland. Each will receive a replica of the plaque.


The five amateurs will be selected by a board of judges internationally known to the amateur fraternity from nominations made by fellow amateurs from all parts of the world. Nominations are called for in the following fields of activity: advancements in electronic techniques and equipment; traffic and DX activity; achievements in exotic phases of amateur radio

(moon-bounce, space probes, etc.); emergency and disaster communications; and the development of amateur radio. A nominee may be any man or woman holding a radio amateur's license issued by a recognized authority in a member country of the International Telecommunications Union.

Is there anyone that you would like to nominate? Amateurs everywhere are invited to join in honoring those hams who have made significant contributions to the art in their respective fields by submitting their names and call letters, and a brief outline of their accomplishments to Dorothy Strauber, K2MGE, Secretary, International Amateur Radio Hall of Fame, 12 Elm St., Lynbrook, N.Y. 11563, by December 31, 1966. The Hallicrafters Company will provide the plaques and donate advertising space for the International Amateur Hall of Fame as a public service.

Third-Party Messages. In one of the club papers we saw recently, the editor was bemoaning the fact that club members were unwilling to make phone patches for some missionaries in central Africa. The trouble with his concern was that third-party messages via amateur radio are illegal between the United States and the country involved.

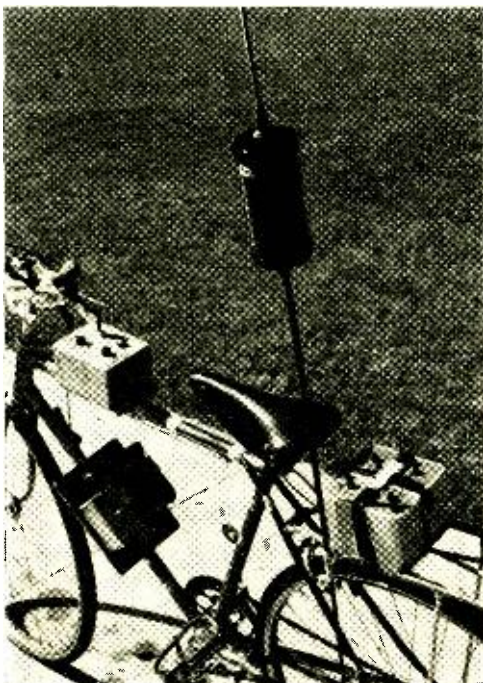The latest FCC list of countries with which U.S. amateurs may exchange unimportant third-party traffic includes: Bolivia (CP); Brazil (PY); Canada (VE, VO); Chile (CE); Colombia (HK); Costa Rica
(Continued on page 122)



"Ty" Conboy, WN7DOX, St. Helens, Oregon (above), will probably be signing WA7DOX by the time this is in print. If you need an Oregon contact, try Ty—preferably on Sunday. At left is the transistORIZED bicycle mobile of Brad Good, WB6LUC, Long Beach, Calif. Brad made several contacts while in motion before the "station" was demolished in an accident; he does NOT recommend that anyone duplicate his experiment. You'll find more information on both of these hams in "News and Views" on page 123.



ON THE CITIZENS BAND

By MATT P. SPINELLO, KHC2060, CB Editor

A NATIONAL wire service has presented a lopsided view of the CB service. Newspapers across the nation have erroneously informed readers that the current state of the CB service can be compared to a city of 800,000 population with only 23 party lines for all of its telephone calls! This is certainly not the type of information to encourage the potential CB'er to put Citizens Band Radio to work for his communication needs. It is unfortunate that the originator of the story was not aware that there is no comparison between 800,000 telephone calls on 23 party lines in *one* city and 800,000 CB calls on 23 channels *spread* across more than 3000 miles of the United States.

Does a bad press establish the CB image? Do the statistical actions of the rule-breakers constitute the image for all licensees? Or are we all a little responsible through lack of interest in the areas that can help or hurt us the most? The CB club newspapers should stand as *the* vehicles to promote the proper use of the CB service, as well as to *inform* all readers of the commend-

THE CB IMAGE

Your CB Editor is shown here in a shot taken from a TV screen during one of a series of six telecasts in which he has appeared to inform the public about the worthwhile public service aspects of CB radio.



able actions taken by individuals or groups of CB'ers in local activities, for public service or in emergencies. Many club news bulletins do an excellent job in these areas: most do not!

Who's responsible for the CB image? All 800,000 licensees are! News media will pick up the negative side of a CB story if it's large enough. That sells newspapers. And there's no denying that we have an over-abundance of problems on the Citizens Band. If, however, CB clubs, rescue teams, and individuals are quick to report worthwhile CB radio activities on a local basis, time might paint a brighter picture for the uninformed reader of local and national news sheets.

Area newspapers, radio and TV studios are not as apt to pick up a story on your latest coffee "clutch" or board meeting as they are to cover an item pertaining to flagrant misuse of the band, overcrowded conditions during evening hours, or the issuance of a fine from the FCC to a local CB user. The news media might, however, be interested in knowing that a local CB group is working with civil defense, police, and other
(Continued on page 124)

BROADCASTS FROM AFRICA AND MIDDLE EAST

Prepared by **BILL LEGGE** and **BOB HILL, W1ARR/3**

Many countries throughout the world do not transmit broadcasts specifically intended for reception in North America. However, these countries can often be heard in North America if a listener knows on what frequency and at what time to listen. Although some of the broadcasts come through surprisingly well, they are in general more difficult to hear and identify than broadcasts beamed to North America. The following listing gives some of the best times and frequencies for listeners to tune in countries in Africa and the Middle East that do not have special broadcasts to this area.

AFRICA				
COUNTRY	CITY	TIME—GMT	FREQUENCIES (MHz)	LANGUAGES
ALGERIA	Algiers	2200-2230	6.175	English
ANGOLA	Dundo	1800-1930	11.687	Portuguese
ASCENSION ISLAND	(BBC Relay)	1700-2000	15.350	English
CAMEROON	Yaounde	0430-0600	4.972	French
CANARY ISLANDS	Tenerife	2300-0400	11.800	Spanish
CONGO REP. (DEM.)	Kinshasa	0400-0600	4.880	French
CONGO REP.	Brazzaville	1900-2000	15.190	English
DAHOMEY	Cotonou	0500-0645	4.870	French
ETHIOPIA	Addis Ababa (ETLF)	1330-1345 1830-1930	15.410 11.875	English English
GABON	Libreville	0500-0630	4.777	French
GHANA	Accra	2045-2215	9.545	English
GUINEA	Conakry	2100-2300	9.650	French
IVORY COAST	Abidjan	2100-2400	6.015	French
LIBERIA	Monrovia (ELWA)	2115-2145	15.155	English
MALAGASY REPUBLIC	Tananarive	1600-1700	15.265	Fr. & Eng.
MALI	Bamako	0600-0700	4.835	French
MAURITANIA	Nouakchott	0630-0730	3.222	French
MAURITIUS	Forest Side	0400-0415	9.710	English
MOROCCO	Rabat	2000-2230	11.735	Arabic
MOZAMBIQUE	Lourenco Marques	0400-0600	4.833 11.780	English
NIGERIA	Lagos	0430-0600	4.990	English
PORT. GUINEA	Bissau	2200-2400	5.042	Portuguese
RWANDA	Kigali (DW)	2000-2300	15.380	German
SENEGAL	Dakar	0600-0700	4.890	French
SIERRA LEONE	Freetown	0600-0730	3.316	English
SOMALI REP.	Mogadiscio	0315-0330	6.095	English
SPANISH GUINEA	Sta. Isabel	2100-2300	6.250	Spanish
SUDAN	Omdurman	0400-0500	4.992	Arabic
TANZANIA	Dar-es-Salaam	0315-0400	5.050	Kiswahili
TOGO	Lome	2100-2115	5.047	English
TUNISIA	Tunis	0500-0600	6.195	Arabic
MIDDLE EAST				
COUNTRY	CITY	TIME—GMT	FREQUENCIES (MHz)	LANGUAGES
IRAN	Teheran	0130-0300	7.065	Persian
IRAQ	Baghdad	2100-2140	6.095	English
ISRAEL	Tel Aviv	2015-2045	9.009	English
JORDAN	Amman	2000-2200	9.530	Arabic
KUWAIT	Kuwait	0225-0330	4.967	Arabic
SAUDI ARABIA	Riyadh	2000-2200	9.720 11.950	Arabic
TURKEY	Ankara	2200-2300	15.160	English



SHORT-WAVE LISTENING

By HANK BENNETT, W2PNA/WPE2FT
Short-Wave Editor

IRC'S NOT VALID IN SOME COUNTRIES

USE OF International Reply Coupons (IRC's) is generally considered to be the easiest method of sending return postage to a foreign country when writing for a verification. In the U.S., you can purchase IRC's at most post offices for 15 cents each (be sure to have them postmarked in the left-hand circle), simply attach one to your report, and send it on its merry way. The station in the foreign country can then cash the IRC in at its post office for sufficient postage to cover a reply to you by surface mail and for the minimum weight limit. (If you want a reply by airmail, you'd better enclose two, three, or more IRC's, especially to the most distant countries.)

Not all countries, however, will accept IRC's. An item in an overseas publication listed Peru as being one such country, and a subsequent reference to the U.S. Postal Manual has revealed that IRC's will not be accepted in any of the following areas: Bulgaria, Congo (formerly Leopoldville—now Kinshasa), Peru, Pitcairn Island, Saudi Arabia, Somali, Sweden, Soviet Union, Yemen, and Yugoslavia.

Some of the countries listed above will

verify your reports without return postage; others will not. In lieu of IRC's, we suggest that you consider the use of mint stamps of the foreign countries involved. For the face value of the stamps, plus a small fee for the service, you can obtain mint (unused) stamps for virtually all of these countries. They can be purchased from any of the many dealers who specialize in this service. Most Sunday newspapers that carry a stamp column also have listings of stamp dealers.

News Items. *Radio DX'ing Worldwide* (Station WNYW) reports that the American transmitting station, WBOU, Bound Brook, N.J., has been dropped from the *Voice of America* broadcast lists. The station was last used for regular VOA service in March, and has since been used for special United Nations transmissions. Now these duties have been assumed by other VOA transmitters in Bethany, Ohio, and Greenville, N.C.

Another news item from WNYW states that feminine voices are now being featured over the New York City area's FM air—
(Continued on page 126)

COME ON, BROADCASTERS—LET'S GET WITH IT!

There's no great secret to international short-wave broadcasting. You put a signal on the air on the right frequency at the right time of day and a foreign audience is supposed to hear it. But some international broadcasters seemingly ignore the listening habits of the people they're trying to reach.

When Radio Ghana completed installation of its 250-kW transmitters last year, transmissions to North America were scheduled for 2000-2100 GMT on 9760 kHz, and for 0330-0430 GMT on 6110 kHz. The 2000 GMT broadcast reaches eastern North America at 3 p.m., a time when most people interested in short-wave broadcasts are away from home during the week, and likely to be otherwise occupied on weekend afternoons. The night broadcast is from 10:30 to 11:30 p.m., EST, too late for most East Coast listeners, although suitable for the West Coast.

Another example of poor scheduling is Radio Sweden's morning broadcast at 1400 GMT, or 9

a.m. EST, another time when most listeners are not at home. Radio Sweden advises that a new transmission schedule is being worked out, so it is hoped that this month the broadcasts will be moved to 1230 GMT (7:30 a.m., EST), preferably on 15,195 kHz.

Argentina transmits in English to eastern North America from 0300 to 0400 GMT, to western North America from 0600 to 0700 GMT, and to Great Britain from 2300 to 2400 GMT. These late-hour broadcasts stem from the fact that the station has only one high-power transmitter and broadcasts a solid hour of programming to each area. Why not transmit for 30 minutes to permit scheduling of the broadcasts at more convenient or listenable times?

What's the purpose of beating the ether to death with powerful broadcast signals if chances are that the greatest part of your audience is either in bed or at work? Come on, broadcasters—let's get with it!
—ROGER LEGGE

ENGLISH-LANGUAGE BROADCASTS TO NORTH AMERICA

FOR THE MONTH OF OCTOBER

Prepared by **ROBERT LEGGE**

TO EASTERN AND CENTRAL NORTH AMERICA				
COUNTRY	CITY	TIME-EST	TIME-GMT	FREQUENCIES (MHz)
MORNING BROADCASTS				
AUSTRALIA	Melbourne	7:15-8:15 a.m.	1215-1315	9.58
CANADA	Montreal	7:15-8:15 a.m.	1215-1315	5.97, 15.32
DENMARK	Copenhagen	7:30-8 a.m.	1230-1300	15.165
FINLAND	Helsinki	7:15-7:45 a.m.	1215-1245	15.185 (Tues., Sat.)
GREAT BRITAIN	London	9:30-11:30 a.m.	1430-1630	15.35, 17.81
SWEDEN	Stockholm	9:9:30 a.m.	1400-1430	15.195
EVENING BROADCASTS				
ALBANIA	Tirana	7-7:30 p.m.	0000-0030	7.265
BULGARIA	Sofia	7-8 p.m.	0000-0100	9.70
CHINA	Peking	8-10 p.m.	0100-0300	11.945, 15.06, 17.68
CUBA	Havana	8-11 p.m.	0100-0400	9.525
CZECHOSLOVAKIA	Prague	8-9 p.m.	0100-0200	5.93, 7.115, 7.345
ECUADOR	Quito (HCJB)	9-11:30 p.m.	0200-0430	9.745, 11.915
EGYPT	Cairo	8:30-10 p.m.	0130-0300	9.585
GERMANY	Berlin	8-9 p.m.	0100-0200	6.16, 9.73
	Cologne	8:30-9:50 p.m.	0130-0250	6.075, 9.64
GREAT BRITAIN	London	4:15-10:30 p.m.	2115-0330	7.13, 9.51, 11.78
HUNGARY	Budapest	8:30-9:30 p.m.	0130-0230	6.235, 9.883
ITALY	Rome	8-8:20 p.m.	0100-0120	5.96, 9.63
JAPAN	Tokyo	6:45-7:45 p.m.	2345-0045	15.135, 17.825
LEBANON	Beirut	9:30-10 p.m.	0230-0300	9.575
NETHERLANDS	Hilversum	8:30-9:30 p.m.	0130-0230	9.59 (Bonaire relay)
PORTUGAL	Lisbon	9-9:45 p.m.	0200-0245	6.025, 6.185
ROMANIA	Bucharest	8:30-9:30 p.m.	0130-0230	6.15, 11.94
SOUTH AFRICA	Johannesburg	7:30-8:30 p.m.	0030-0130	9.525, 11.90
SPAIN	Madrid	8-9:30 p.m.	0100-0230	6.13, 9.76
SWEDEN	Stockholm	8:15-9:45 p.m.	0115-0245	9.705
SWITZERLAND	Berne	8:15-9:15 p.m.	0115-0215	6.12, 9.535
U.S.S.R.	Kiev	7:30-8 p.m. (Mon., Thurs., Fri.)	0030-0100 (Tues., Fri., Sat.)	7.31, 9.665, 9.685
	Moscow	5-5:30 p.m. and hourly to 12-1 a.m.	2200-2230 and hourly to 0500-0600	7.15, 9.665, 9.685 " "
VATICAN	Vatican	7:50-8:10 p.m.	0050-0110	5.985, 7.25, 9.645

TO WESTERN NORTH AMERICA				
COUNTRY	CITY	TIME-PST	TIME-GMT	FREQUENCIES (MHz)
ARGENTINA	Buenos Aires	10-11 p.m. (Mon.-Fri.)	0600-0700 (Tues.-Sat.)	9.69
AUSTRALIA	Melbourne	5-7 p.m.	0100-0300	15.22, 17.84
BULGARIA	Sofia	8-8:30 p.m.	0400-0430	9.70
CHINA	Peking	7-9 p.m.	0300-0500	9.457, 11.82, 15.095
	Taipei	6:50-7:50 p.m.	0250-0350	11.86, 15.345
CZECHOSLOVAKIA	Prague	7:30-8:30 p.m.	0330-0430	5.93, 7.115, 7.345
GERMANY	Berlin	7:45-8:15 p.m.	0345-0415	6.16, 9.73
	Cologne	9-9:40 p.m.	0500-0540	6.145, 9.735
HUNGARY	Budapest	7-8 p.m.	0300-0400	6.235, 9.833
JAPAN	Tokyo	6-7 p.m.	0200-0300	15.135, 17.825
KOREA	Seoul	7-7:30 p.m.	0300-0330	15.125
PORTUGAL	Lisbon	8-8:45 p.m.	0400-0445	6.025, 6.185
SOUTH AFRICA	Johannesburg	6:30-7:30 p.m.	0230-0330	9.525, 11.90
SWEDEN	Stockholm	7:15-7:45 p.m.	0315-0345	9.705
SWITZERLAND	Berne	8:15-9:15 p.m.	0415-0515	6.12, 9.535
U.S.S.R.	Moscow	7-10:30 p.m.	0300-0730	9.735, 11.755, 11.85



AN INTERCOM that just sits there doing nothing for 90 percent of the time is like a night watchman on the alert for a burglar or a fire but who fails to notice a water leak in the basement that can cause thousands of dollars' worth of damage. Unlike the watchman, however, an intercom can be modified to sound an alert in the event of almost any type of emergency, and it never sleeps.

Because most modern intercoms, especially the transistor types, draw so little current, they cost practically nothing to operate and can be left on all the time; and, since most of them contain suitable electronic circuits, it is possible and desirable to have them perform other duties. As a matter of fact, some commercially available intercoms come equipped with built-in alarm functions.

Burglar, fire, and moisture alarm functions can be incorporated into most intercoms with very little effort. All you need do is install a capacitor to set up a feedback loop and a phone jack to accommodate a simple alarm-type switch. The switch, when activated, will set up a loud howl in your intercom.

How It Works. Fortunately, in intercoms, as in all good audio amplifiers, great pains are taken to suppress or eliminate all extraneous noises, especially those resulting from feedback. The trick is to obtain a feedback howl in an emergency, yet prevent any undesirable noise while the intercom is functioning as an intercom.

BUILD A **HIP SQUAWK BOX**

INTERCOM DOUBLES AS A BURGLAR
AND FIRE ALARM

By **CHARLES VLAMIS AND BYRON G. WELS**

As shown in the schematic, which is that of the Heathkit GD-51A transistor intercom, a regenerative feedback loop is set up when a portion of the signal from the collector of transistor X4 is fed back to the base of transistor X3 through a closed alarm switch plugged into the jack. When the alarm switch is open, or the plug is not in the jack, the intercom functions in a normal manner.


In order for the intercom to function as an alarm, the talk-listen switch must be in the *listen* position. Only the master unit in which the feedback loop is installed will act as the alarm, and nothing else in the intercom system is disturbed.

Almost any intercom can be modified in like manner, including the tube types. Also, you can try various sizes of capacitors to obtain more or less feedback as needed.

The Alarm Switch. Any simple device that will act as a short when it is activated and an open when it is in its passive state will serve as the alarm switch. A microswitch mounted on the sash a few inches above the lower casement of a window makes an effective burglar alarm switch. The window can be lifted to allow ventilation; open it further, and the intercom lets out a loud howl.

Klixon fire alarm buttons can be placed near stoves, heaters, or any appliance which could cause a fire. A rise in temperature will close the thermostatic switch in the alarm button, and sound an alarm. (Note: There are different types of fire alarm buttons avail-

(Continued on page 109)

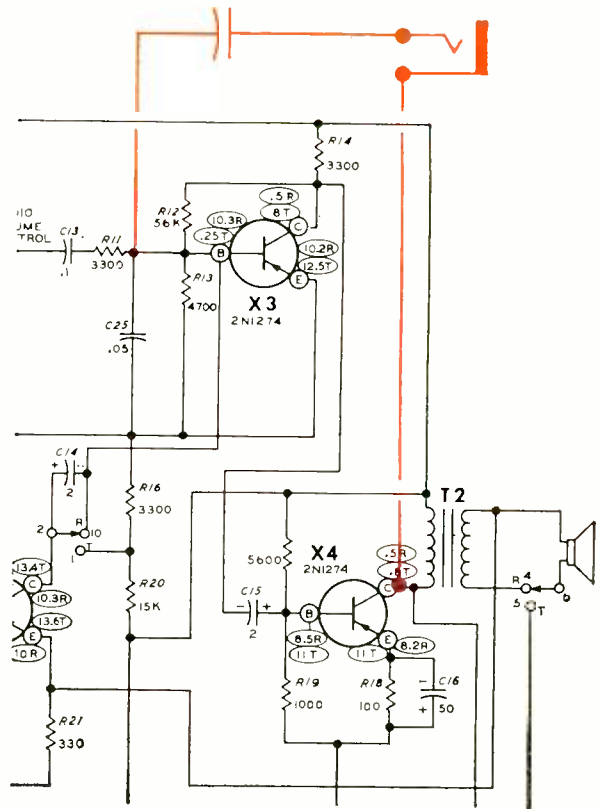


Lines in color on this partial schematic of the GD-51A Heathkit transistor intercom show simple feedback loop. Capacitance value is not critical. Try 0.01 to 0.1 μ F units to obtain maximum howl. Almost any intercom can be modified using this technique.

Several normally-open type fire alarm buttons can be wired in parallel and installed strategically around the house (left, below). Aspirin tablet and antenna clothespin-type connector (center) can be made to serve as moisture detector. A normally-open microswitch mounted on window (right) or door acts to sound an alarm if burglar tries to get in.



Get this \$65 RCA color TV course FREE

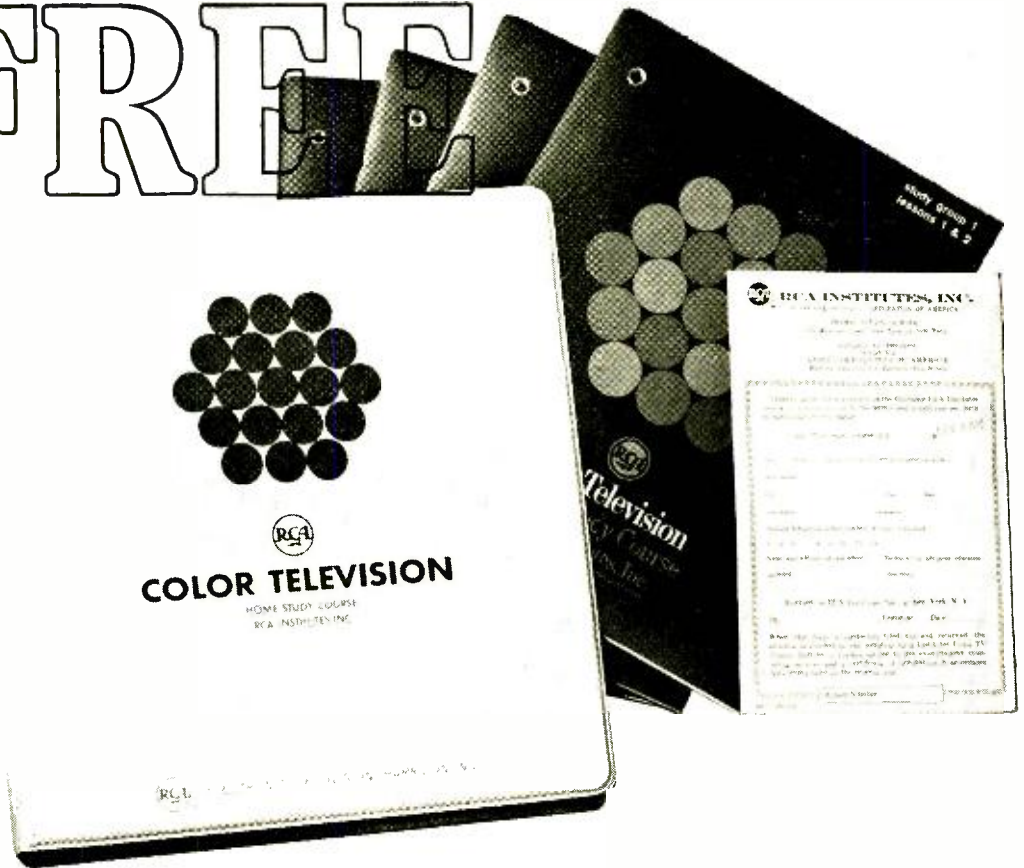

when
you buy
this



WR-64B RCA Color
Bar/Dot/Crosshatch Generator

or this




WR-69A RCA TV-FM
Sweep Generator

or this



WR-99A RCA Marker Generator

or this

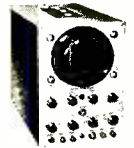

WO-91B RCA 5" Scope

That's right! RCA Institutes famous Home Study Color TV Servicing Course FREE, when you buy ANY ONE of the instruments shown here. Buy all four...get four courses. Enroll all your technicians while you equip your shop with the instruments you'll need for color TV servicing anyway.

Here's how it works: Simply buy one, or all, of the four instruments shown, the WR-64B, WR-69A, WR-99A, or WO-91B—ALL essential color TV test instruments—from your Authorized RCA Test Equipment Distributor between now and November 15, 1966. Fill out your warranty registration card and attach the white identification label on the carton. Send them to RCA, Test Equipment Headquarters, Bldg. 17-2, Harrison, New Jersey. We will send you the enrollment form and a binder

containing the first two lessons. When you complete the lessons and forward them to RCA Institutes for grading, the next lessons will be supplied to you directly from RCA Institutes, all without charge to you.

But do it now. This offer is good only for equipment purchased between September 1, and November 15, 1966. To allow for postal delay, we will honor cards received up until December 1, 1966. Here's your chance to equip your shop for color servicing while we train your people for FREE!

Electronic Components and Devices, Harrison, N.J.



The Most Trusted Name in Electronics

CIRCLE NO. 39 ON READER SERVICE PAGE

www.americanradiohistory.com

ASSEMBLE YOUR OWN ALL-TRANSISTOR *Schober* ELECTRONIC ORGAN



3 NEW MODELS
 Recital \$7500
 Console II \$850
 Spinet \$550

This is the new, all-transistor Schober Console II... the most luxurious "home-size" organ available today. Full 61-note manuals, 17 pedals, 22 stops and coupler, 3 pitch registers, and authentic theatre voicing leave little to be desired. Comparable to ready-built organs selling from \$1800 to \$2500.

The pride and satisfaction of building one of these most pipe-like of electronic organs can now be yours... starting for as low as \$550. The Schober Spinet, only 38 inches wide, fits into the smallest living room. The all-new, all-transistor Schober Recital Model actually sounds like a fine pipe organ; its 32 voices, 6 couplers, 5 pitch registers delight professional musicians... making learning easy for beginners.

AND YOU SAVE 50% OR MORE BECAUSE YOU'RE BUYING DIRECTLY FROM THE MANUFACTURER AND PAYING ONLY FOR THE PARTS, NOT COSTLY LABOR.

It's easy to assemble a Schober Organ. No special skills or experience needed. No technical or musical knowledge either. Everything you need is furnished, including the know-how. You supply only simple hand tools and the time.

You can buy the organ section by section... so you needn't spend the whole amount at once.

You can begin playing in an hour, even if you've never played before—with the ingenious Pointer System, available from Schober.

Thousands of men and women—teen-agers, too—have already assembled Schober Organs. We're proud to say that many who could afford to buy any organ have chosen Schober because they preferred it musically.

Send for our free 1966 Schober Catalog, describing in detail the exciting Schober Organs and optional accessories; it includes a free 7-inch "sampler" record so you can hear before you buy.

THE *Schober Organ* CORPORATION

43 West 61st Street, New York, N. Y. 10023

Also available in Canada, Australia, Hong Kong, Mexico, Puerto Rico, and the United Kingdom

THE SCHOBER ORGAN CORP., DEPT. PE-21

43 West 61st Street, New York, N. Y. 10023

Please send me FREE 1966 Schober Catalog and FREE 7-inch "sampler" record.

Enclosed find \$2.00 for 10-inch quality LP record of Schober Organ music. (\$2.00 refunded with purchase of first kit.)

Name _____

Address _____

City _____ State _____ Zip No. _____

CIRCLE NO. 42 ON READER SERVICE PAGE

TIPS

(Continued from page 20)

MAGNETIC "FISHING" ROD RETRIEVES SMALL OBJECTS

Screws, washers, nuts, and other small objects that accidentally fall into your wired chassis or along the inner walls of an electronic equipment cabinet can easily be retrieved with a simple "fishing" rod made by gluing a small bar magnet to one end of a steel measuring tape. If the object is nonmagnetizable, wrap a bit of



masking tape—sticky side out—around the magnet. The flexibility and slimness of the steel tape enables the magnet to be positioned in extremely close quarters to pick up the fallen object. —Glen F. Stillwell

EYE SCREWS SUPPORT BREADBOARD COMPONENTS

When breadboarding, use an assortment of ordinary eye screws of the type available in 5 & 10 and hardware stores to mount your potentiometers, switches, phone jacks, binding posts, etc., as shown in the accompanying photo. Determine, by trial, the right size eye screw for the component being mounted. If necessary, open up the screw eye a bit with a pair of pliers. Then, after planning your layout, insert the screw far enough into the breadboard to support the component that is being mounted.

—Art Trauffer

TAPE RECORDER
(Liquidation Stock)
\$899




Liquidation of our special purchase of tape recorders complete with remote 2 1/4" speaker-microphone, on-off switch with play and record positions and remote battery case, plus tape, ready to play. Takes 2 ordinary "C" flashlight batteries. Beautifully made for long-life high quality audio-visual displays. Comes with standard 1/4" magnetic tape. A \$20 value. Use for messages, rig with invisible thread as detection device, hides anywhere. Conceal in toy animal and let it make outrageous remarks to your guests. 1000 fun and practical uses. To order: Send check, cash or M.O. for post-paid shipment. \$1.00 deposit for C.O.D. 10-day money back guarantee.



MISSION LIQUIDATORS
 Dept. A, P.O. Box 4187 San Fernando, Calif. 91342

NEW! LAFAYETTE HB-525 Solid State 2-Way Radio

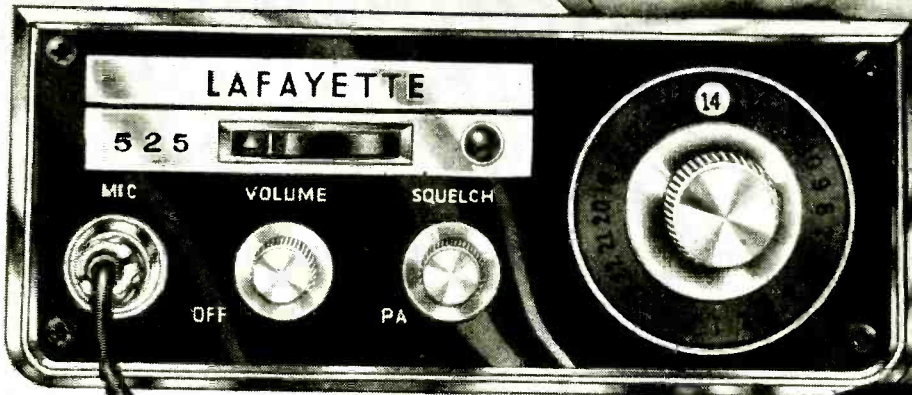**OBSOLETES ALL 23 CHANNEL
CB TRANSCEIVERS!**



• Size: 2 3/8" by 6 1/4"

99-3076WX*

All **25** Channels
Crystal Controlled

149⁹⁵

- 25 Channel Crystal Control
- 19 Transistors, 7 Diodes, Thermistor
- Dual Conversion Receiver for Extra Selectivity and Sensitivity
- Full 5-Watt Input
- Range Boost™ Circuitry for Added Power
- 3-Position Delta Tune—Provides Accurate Fine Tuning

- Mechanical 455KC Filter for Superior Selectivity
- Variable Squelch plus Series Gate Automatic Noise Limiting
- Public Address System (with external speaker)
- 12-Volt DC Operation (pos. or neg. ground) 6-Volt DC (with optional DC Power Supply)
- Pi-Network for Optimum RF Output

*Imported

FREE
Over 500 Pages



1967 CATALOG NO. 670

Featuring Everything in Electronics for

• HOME • INDUSTRY • LABORATORY

from the "World's Hi-Fi & Electronics Center"


LAFAYETTE Radio ELECTRONICS
Dept. 1J-6, P.O. Box 10
Syosset, L. I., N. Y. 11791

Send me the FREE 1967 LAFAYETTE Catalog 670 1J-6

Name -----

Address -----

City ----- State ----- Zip -----

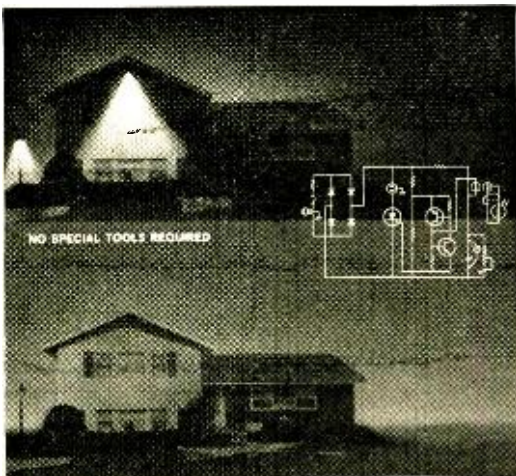

BUILD YOUR OWN LIGHT-OPERATED SWITCH

**In and Around the House
For Dozens of Applications**

Light up the night with RCA SCR Experimenter's Kits. These kits, containing a full complement of active components, rectifiers, transistors, a silicon controlled-rectifier, and a photocell, plus other readily available passive components and hardware enable you to build a light-operated switch for garage, yard or path, or even a sign that can be activated by auto lights. RCA Experimenter's Kits offer considerable flexibility in the number and kind of control circuits you as a hobbyist can build. With just three RCA kits, you can build any of 14 different circuits with hundreds of applications. Easy-to-follow directions for all 14 circuits are given in RCA Experimenter's Manual, KM-70.



Your RCA Semiconductor Distributor has Basic and Add-On Kits as well as the RCA Experimenter's Manual on display. See him about the solid-state circuit you have in mind. Do it today!

AVAILABLE FROM YOUR RCA SEMICONDUCTOR DISTRIBUTOR

RCA Electronic Components and Devices, Harrison, N. J.



The Most Trusted Name in Electronics

CIRCLE NO. 40 ON READER SERVICE PAGE

Back Issues Available

Use this coupon to order back issues of POPULAR ELECTRONICS

We have a limited supply of back issues that can be ordered on a first-come, first-served basis. Just fill in the coupon below, enclose your remittance in the amount of 50¢ each and mail.

ZIFF-DAVIS SERVICE DIVISION

Dept. BCPE, 589 Broadway
New York 12, New York

Please send the following back issues of POPULAR ELECTRONICS.

I am enclosing..... to cover cost of the magazine, shipping and handling.

Month Year

Month Year

Month Year

Name

Address

City Zone State

No charge or C.O.D. orders please.

PE

Get Your First Class Commercial F.C.C. LICENSE and your A.S.E.E. DEGREE

Move up. Take advantage of the good pay and security now offered by an electronics career. Grantham can train you quickly, in resident classes or by correspondence.

We offer the following courses—all of which are approved under the new G.I. Bill. Select the course you are interested in, and write or phone for free details.

- Electronics Engineering Technology* (resident course, which leads to the A.S.E.E. degree)
- Basic Electronics Engineering Technology* (correspondence course, which covers the first 1/2 of the EET course listed above, and credit for which can be applied toward the A.S.E.E. degree.
- Communications Electronics* (resident course which leads to the FCC first class license and trains you to be a communications technician)
- F.C.C. License Course* (correspondence course, which leads to the FCC first class license)
- Radio & Television Servicing* (resident course, which trains you to be a service technician)

For complete information without obligation, write or telephone the School at any of the addresses listed below, and indicate the course you are interested in.

Dept. 63-P

Grantham School of Electronics

1505 N. Western Ave., Hollywood, Cal. 90027

Phone: (213) 469-7878

408 Marion Street, Seattle, Wash. 98104

Phone: (206) 622-7227

818-18th St., NW, Washington, D.C. 20006

Phone: (202) 298-7460

CIRCLE NO. 59 ON READER SERVICE PAGE

POPULAR ELECTRONICS

LETTERS (Continued from page 12)

and *Wien bridge* (Wilhelm Wien, German physicist). So why not: *hertz* (Heinrich Rudolph Hertz, German physicist)?

WILLIAM G. O'BARR
South Laguna, Calif.

William, we have been giving some thought to volts and watts and such, too, and we recently made the decision to change our abbreviation style to A for ampere, F for farad, H for henry, V for volt, and W for watt.

"PANIC BUTTON" STILL CREATES PANIC

My friend and I built the "Don't Panic . . . Push the Button" alarm (January, 1966), and on the last day of school we set it down on the floor between two of the tables in the lunchroom and plugged it in. (We also installed a dummy plug as described in one of your reader's letters.) Then, telling the students at the tables not to touch the button, we went to get our food. Sure enough, just as I was putting ketchup on my hamburger, I heard the wail



of the siren rising over the din of the lunchroom. Minutes later, our assistant principal rushed in, and, not knowing what the thing was, carried it out of the lunchroom. Later we found it in the trash can, but unfortunately, in many pieces. All the wires had been torn off the siren module with such devastating vigor that we have been unable to get the thing working again.

DAVE BLOCH
Detroit, Mich.

I built the "Panic Button" and it worked very well on most people, but a few turned over the box and discovered the hidden switch. I believe I have solved that problem. I just installed the parts from the "Tickle Stick" (February, 1966). I did it by covering a wooden box with thin metal, leaving a thin uncovered strip down the middle. Then I hooked up the works to the 60-second delay switch and watched the fun.

DAVE CLARK
Livingston, N.J.

CONNUBIAL COMPUTER

I have been a subscriber to POPULAR ELECTRONICS almost from the beginning of publication, and I do not remember seeing in the magazine any article of lower quality than "The Connubially-Oriented Computer" (July, 1966). The editorial staff must be completely bankrupt! I hope its inclusion was a

October, 1966



From a Range Gain II Base

to a Ranger Mobile—

You've Never Had It so Good in CB Coverage

Regency offers you Range Gain II on base (or mobile). It gives you 23 channels of big sound range, quality and value. Double Side Band, Reduced Carrier provides up to 4 times more coverage. And . . . the Regency Ranger Solid State 11-channel transceiver has a dial system with numbers instead of letters. The speaker is up front, so you hear the source instead of driving it into the floor board. You get CAP external speaker, and F.A. capability, too. So if you want CB elegance—shop for Regency. You'll like the results.

Regency ELECTRONICS, INC.


The name that gives you
1 full year warranty

Department 106
7900 PENDLETON PIKE
INDIANAPOLIS, INDIANA 46226

CIRCLE NO. 55 ON READER SERVICE PAGE 103

CONAR KITS

AND OTHER ASSEMBLED PRODUCTS

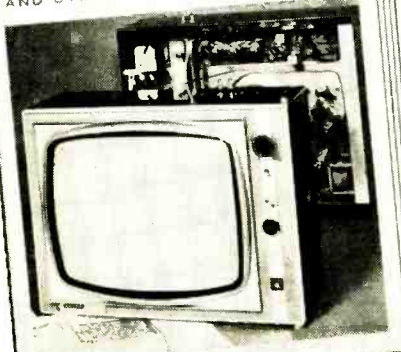

Your copy is waiting The do-it-yourselfer's newest catalog

Here's your new catalog of quality electronic kits and assembled equipment . . . your shopping guide for TV set kits, transistor radios, voltmeters, scopes, tube testers, ham gear, PA systems, and a host of other carefully engineered products. Every item in the Conar catalog is backed by a no-loopholes, money-back guarantee. It's not the biggest catalog, but once you shop its pages you'll agree it's among the best. For years of pleasurable performance, for fun and pride in assembly, mail the coupon. Discover why Conar, a division of National Radio Institute, is just about the fastest growing name in the kit and equipment business.

CONAR

MAIL NOW!

CONAR

KAGC

3939 Wisconsin Avenue, Washington, D.C. 20016

Please send me your new catalog.

Name _____

Address _____

City _____

State _____

Zip

Code _____

LETTERS (Continued from page 103)

case of careless judgment, rather than an indication of degenerating taste on the part of the editors. If the latter proves true, I will probably cancel my subscription.

RICHARD W. PRICE
Barker, N.Y.


Can you please explain to me how the "luscious and outrageously constructed Red-head" on page 54 turned into a "Brunette Doll" on page 97? Inconsistencies like this can ruin a romance. I know!

ARNOLD GERSHON
New York, N.Y.

I just read the story of Otto Tronix, and I think it was very cleverly done, using electronics as the backbone. I found it extremely entertaining, especially the well-twisted ending. Let's have more of these stories.

BRIAN LO
Vancouver 16, B.C.
Canada

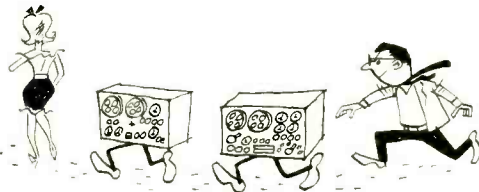Richard, the last we heard, the two computers were chasing after the Redhead, and we aren't likely to see them again, so don't



cancel your subscription. Arnold, your letter sounds as if you had a bad experience; well, that's what happens when you can't get the story straight—there are TWO "dolls" in this article. Brian, maybe you can catch up with the computers.

NIGHTTIME TV MYSTERY

Soon after my television set is turned on at night, some form of interference completely blanks out both picture and sound. It cannot be the TV set as I have had the same problem with as many as four other sets. Neither is it the antenna, as I have tried a variety of antennas. It is quite maddening to watch U.N.C.L.E. Headquarters under siege and then come under siege myself just at the most interesting part of the story. Is there anything that could possibly be done about this? Do you have a filter that could be attached to eliminate this unwelcome T.H.R.U.S.H. agent?

KEVIN FITZGERALD
Dorchester, Mass.

Sorry, we don't have any T.H.R.U.S.H. filters. Kevin, but you can try a line-voltage regulator. Trouble at night, and not in the daytime, is usually an indication of low-line voltage.

-30-

YOUR
POSTMASTER
SUGGESTS:
ALWAYS
INCLUDE YOUR
(ZIP CODE)
NUMBER
IN YOUR
RETURN ADDRESS

POPULAR ELECTRONICS SUBSCRIBER SERVICE

Please include an address label when writing about your subscription to help us serve you promptly. Write to: Portland Place, Boulder, Colo. 80302

Change of Address:

Please let us know you are moving at least 4 weeks in advance. Affix magazine address label in space to the right and print new address below. If you have a question about your subscription, attach address label to your letter.

To Subscribe:

Check boxes below.

- New Renewal
 5 years \$20
 3 years \$13
 1 year \$5

Specify

- Payment enclosed
 — You get 1 extra issue per year FREE!
 Bill me later.

← AFFIX LABEL →

If you have no label handy, print OLD address here.

name please print

address

city

state zip-code

name _____ please print _____ 0182

address _____

city _____

state _____ zip-code _____

There's GOOD NEWS Today!

PRICES REDUCED

on the famous

MARK TEN SCR IGNITION SYSTEM

Factory
Assembled



ONLY **\$44⁹⁵** ppd.

OR IN
EASY-TO-ASSEMBLE
DELTAKIT

ONLY **\$29⁹⁵** ppd.

Here's why DELTA offers you these unparalleled savings!

You read it in the June 1965 issue of this magazine: "First SCR Ignition System in mass production." Now Delta—the ORIGINAL manufacturer and the largest—offers this price reduction due to high production levels. Thousands have purchased and installed our remarkable automotive system. We at Delta can now pass along our lowered manufacturing costs to you—with extra savings in addition to the Excise Tax reduction effective January 1st! Save on gas. Increase the life of your points and plugs. Dramatically improve your car's acceleration and general performance. Buy the ORIGINAL, and for less! ORDER TODAY!



DELTA PRODUCTS, INC.

P.O. Box 1147PE • Grand Junction, Colo. 81501

Enclosed is \$ _____ Ship prepaid. Ship C.O.D.
 Please send: Mark Tens (Assembled) @ \$44.95
 Mark Tens (Delta Kit) @ \$29.95
 SPECIFY — Positive Ground Negative Ground 6 or 12 Volt
 Car Year _____ Make _____
 Name _____
 Address _____
 City, State _____ Zip _____

DP 6-1

CIRCLE NO. 57 ON READER SERVICE PAGE

INTEGRATED CIRCUITS

(Continued from page 56)

Some are experimenter units that are priced at less than a dollar each when purchased in large quantities. Others are of the expensive variety, limited to a few critical applications.

The table on page 56 lists some of the lower-priced integrated circuits that can be purchased from distributors as off-the-shelf items; data sheets are available from the manufacturers represented. Digital IC's are of the flip-flop switching variety used in computer or counting circuits, while linear IC's are used as r.f. and a.f. amplifiers.

None of the IC's listed is as expensive as the corresponding parts would be if purchased separately, not counting the extra assembly time and reduced reliability that discrete parts provide. Furthermore, with discrete parts it is impossible to obtain the temperature tracking inherent in integrated circuits.

In The Cards For Tomorrow. The trend is plain to see—more, smaller, and better integrated circuits at lower costs. The experts call for a 10:1 price cut in IC's in the next fifteen years. So the time to obtain a working familiarity with these circuits is—now!


Even more exciting is today's development of IC's using some astounding new electronic techniques that will become important factors in the manufacture of tomorrow's distributor components. The MOS-type transistors have essentially infinite input impedance and

zero switching time, but are built with half the steps necessary for a conventional transistor and in a tiny fraction of its size.

The *Gunn* effect and the *Read* effect are new techniques through which the avalanching semiconductors directly generate substantial microwave power. Microwave IC's are already in the works, as are switching mode amplifiers—produced through the use of a “why didn't they think of it before?” technique by which a 40-watt amplifier is put in a TO5 case with no heat sink required, and no heat problems either.

There is also a totally molecular approach by which entire functional blocks are built up on a molecular scale. Then there's a resonant gate transistor—a spanking-new device with a built-in tuning fork that gives you high-*Q*, stable resonant circuits—from audio to microwave—in extremely cramped quarters. And the list goes on.

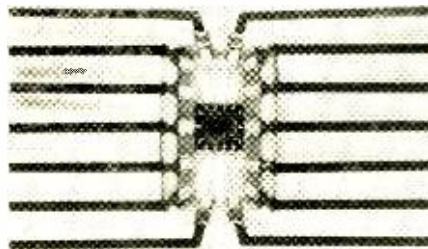Today's laboratories are turning out tomorrow's IC's. Will you be ready for them when they arrive? -30-



Ceramic flat pack is used when maximum miniaturization is required. It occupies less than half the space of a TO-5 transistor package. This configuration sometimes replaces as many as 50 components.

The famous **Mercury** Model 1101 TUBE TESTER

NOW in a wire-it-yourself KIT!

Illustrated step-by-step instructions make the Model 1101 extremely easy-to-build. Tests more tubes for dynamic cathode emission, shorts, grid leakage and gas than many testers costing hundreds of dollars... tests new Decals, Magnavols, 7-pin Nuvistors, Novars Compactrons, 10-pin type, battery type, auto radio hybrid tubes, foreign and hi-fi tubes and industrial types. Employs brilliant 2-point test principle—greatest safeguard against obsolescence. Modern airplane luggage design case.

• Also tests all popular picture tubes


Write for complete catalog of kits and wired instruments—and name of nearest distributor

MERCURY ELECTRONICS CORP. 315 Roslyn Road
Mineola, N. Y. 11501


Model 1101K
Kit... Net

\$39.95


Model 1101... wired
Net \$69.95

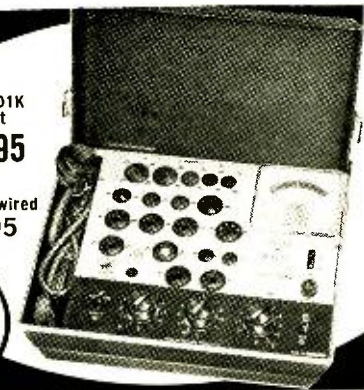

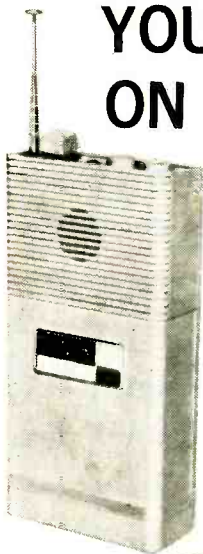YOU CAN STAKE YOUR LIFE ON **POLYTRONICS** PERFORMANCE



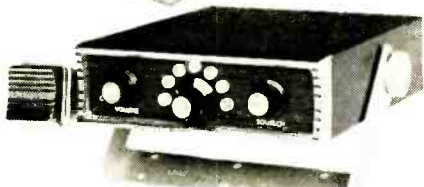DUO-COMM 120—Citizens Band
(120B—AM Business Band)
FG-125—Govt./Military
All Solid State Walkie-Talkies



The New POLY-PUP
Smallest 7 channel CB
Transceiver available —
all transistor.



POLY-COMM "B" & "H"
FM Business Band

THE ONLY 2-WAY RADIO TO CLIMB MOUNT EVEREST AND SURVIVE

And you can find a Polytronics engineered transceiver to fit **your** needs and budget... equipment you can stake your life on as Willie Unsoeld did when he scaled the peak of Mt. Everest on May 22, 1963.

In addition to the sets pictured, there is the POLY-COMPACT, the world's smallest **eleven**-channel all solid state CB Transceiver; the POLY-COMM 23 offering 23-channel "Spectramatic tuning" for instant operation on any citizens band channel; the amazing POLY-COMM 30 with 23 CB channels and 7 extra "in between" part 15 channels (100mw).

Before you buy, make sure that you have seen the best... send in the coupon below for descriptive literature and dealer information.

SEE...

POLYTRONICS

BEFORE YOU BUY!

CITIZENS RADIO
BUSINESS/INDUSTRIAL RADIO
(AM & FM)
ACCESSORIES

POLYTRONICS LABORATORIES, INC.

A Subsidiary of Vitro Corporation of America
900 Burlington Ave., Silver Spring, Md.

Please send me full details on:

CITIZENS RADIO EQUIPMENT BUSINESS/INDUSTRIAL RADIO EQUIPMENT
and information about the nearest POLYTRONICS dealer.

Name.....

Address.....

City..... State..... Zip.....

Dealer Inquiries Invited

Air

Even your Hi Fi Components need it to survive.

You can minimize thermal drift and lengthen the life of Hi Fi sets, FM stereo receivers, communications and other equipment with this low noise fan. The Hi Fi Boxer was designed by engineers who have produced airmover designs for computers, broadcasting equipment, and the Minute-man Missile.

For more detailed information write the address listed below.

To obtain the Hi Fi Boxer see your local dealer or send a check* or money order for \$14.85 to:

*Hi Fi Boxer, New Hampshire Division,
IMC Magnetics Corp., Route 16B
Rochester, New Hampshire*

*Allow 10 days for personal checks to clear.

CIRCLE NO. 24 ON READER SERVICE PAGE

New sound column



High Fidelity Speaker System

Looks beautiful, sounds excitingly different! Sound column design uses scientific focusing principle to add extra projection to high tones, re-create music with startling fidelity. Ideal for stereo. 33 1/4" h. x 10 1/2" w. x 4" d. 4 Jensen speakers — 2 specially-designed high compliance woofers, 2 direct radiator tweeters. 50 to 17,000 cps. Cabinet of genuine walnut with oiled finish . . . designed to hang on the wall like a picture.

The Astra

SAVE
Stereo pair only
\$89⁹⁵

\$49⁹⁵ each
audiophile
net


Argos
PRODUCTS COMPANY

Write for free catalog showing Argos systems for every purpose

Dept. C 600 S. Sycamore St., Genoa, Ill. 60135
CIRCLE NO. 4 ON READER SERVICE PAGE

INTEGRATED CIRCUIT AMPLIFIER

(Continued from page 59)

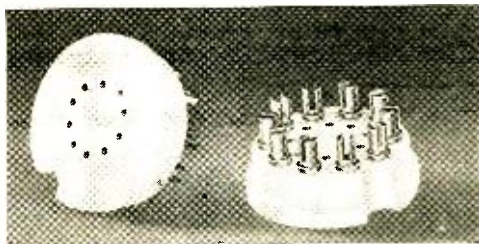

This type of press-fit socket, put out by Sealectro, can be used to simplify your project. With it you simply plug in your IC as you would a transistor.

solder the leads to the IC socket until the case is in place. When wiring this unit in the circuit, observe that the locating tab on the IC is directly over pin 1. Viewed from the top of the case, the pins are numbered counterclockwise. Also, observe that pins 2, 7, and 10 are tied together and returned to a terminal on S1.

Operating Hints. Distortion will result if too large a signal is applied to the amplifier input. For applications not requiring a wide bandpass, a step-up transformer can be used to couple the output of the first differential amplifier to the input of the second amplifier, replacing capacitor C2. However, some amount of experimentation is required to select the right transformer, since poor matching of the stages can transform your amplifier into a blocking oscillator due to the sensitivity of emitter followers to inductive loads.

For additional gain, two or more IC packages can be cascaded together. But care must be taken to keep the signal at a level low enough so that clipping will not take place.

The values of R1 and R2 have been chosen for best overall performance and circuit stability. But where it is desirable to change the amplifier input and output impedances, the value of these resistors can be raised to as high as 22,000 ohms with only a slight loss in gain and stability. One advantage of this change is that smaller values are required for C1 through C3 for any given frequency response.

-30-

POPULAR ELECTRONICS

HIP SQUAWK BOX

(Continued from page 98)

able; those that are open when they are cold, and those that are open when they are hot. Some have different temperature ratings.)

One way to eliminate a wet headache is to place an aspirin tablet between a couple of thumb tacks mounted on a spring-action clothespin, and hang the contraption outside your window. In case of rain, the aspirin tablet will dissolve, the clothespin will close, and the alarm will sound. One tack is fastened to each jaw of the clothespin, and a length of wire is attached to each tack. A clothespin-type antenna connector is ideal for this purpose, but you will have to bend the metal ends towards the center until they touch each other when the pin is closed.

Greater area coverage can be obtained by connecting several alarm switches in parallel. Also, it is possible to create a more sophisticated alarm system by having several alarm stations, each switching in different values of capacitance to obtain a unique sound for a specific location or type of emergency. But you would have to have a good musical ear to identify the different sounds. -30-

CAREERS IN ELECTRONICS

(Continued from page 51)

with what goes on in a computer, have a speaking acquaintance with PPM, micro-electronics, radar pulse and Doppler techniques, SSB, etc.

The man who takes a 250-hour course at home may have had excellent training—as far as it goes. But it simply can't cover the same ground as a resident course that takes ten times as much time and effort. And the fellow who thinks he can spend a few spare-time hours for a year or so and come out as a high-level technician is due for an unhappy awakening.

The home-study schools aren't trying to fool any one. Look over the catalogs and you can tell quickly which courses

October, 1966

FREE!

BIGGER... BETTER THAN EVER!



40th ANNIVERSARY 1967 CATALOG



YOUR BUYING GUIDE FOR:

- Stereo & Hi-Fi Systems & Components.
- Tape Recorders.
- Electronics Parts, Tubes, Tools
- Phonos & Records
- Ham Gear.
- Test Instruments & Kits
- Cameras & Film.
- P.A.
- Citizens Band.
- Radio & TV Sets.
- Musical Instruments.

**SEND FOR
YOURS TODAY!**

BURSTEIN-APPLEBEE CO.

Dept. 1012 McGee, Kansas City, Mo. 64106
 Rush me the FREE 1967 B-A Catalog.

Name.....
Address.....
City..... State..... Zip Code.....

CIRCLE NO. 11 ON READER SERVICE PAGE

STEP UP YOUR INCOME

Learn at Home to Fix ELECTRICAL APPLIANCES

If you have a business or job in Radio-TV Servicing or other home service, you'll find Electrical Appliance Repair a natural, profitable addition. NRI trains you quickly in spare time, shows you how to add to your income long before you finish training. NRI gives you parts to build your own Appliance Tester. Learn how to repair small and large appliances plus air conditioning, refrigeration, small gasoline engines, equipment used on farms and commercially. Cash in on this money-making sideline. Mail coupon for catalog. No obligation. NATIONAL RADIO INSTITUTE, Appliance Div., Washington, D.C. 20016

Training Available Under New GI Bill

FREE
CATALOG
MAIL COUPON



NATIONAL RADIO INSTITUTE
Washington, D.C. 20016

501-106

Please send me your Electrical Appliance Repair catalog. No salesman will call.

Name..... Age.....
Address.....
City..... State..... Zip.....

Check for facts on new GI Bill

ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL

they've designed to train men to be industrial technicians. The home-study schools offer high-powered courses that will prepare a man to work as a test or calibration technician, or as a junior technician who can look forward to a bright future and to continuing advancement as he becomes ever more expert. (Incidentally, he's likely to find the home-study schools the best place to constantly upgrade his training, once he's on the job.)

One of the easiest ways to pick the courses that will be most valuable is simply to see how long the school estimates it will take you to complete the course. Capitol Radio Engineering Institute's programs in Electronic Engineering Technology, for example, are certainly among the most advanced offered through the mails. These courses will take the average student studying some three hours a day about three years to complete. That means he'll spend upwards of 2000 hours on the course. *And CREI's courses aren't meant for rank beginners.* The school requires that students must already be working in electronics, with

some basic knowledge in the field and the opportunity to apply their new knowledge working on actual equipment as they advance. In other words, the amount of time a student spends on such a course begins to approach the amount of time he'd put in if he attended one of the regular engineering technology institutes. Obviously, when a man finishes such a course, he'll have something valuable to offer an employer.

How Much Education Do You Want?

If you want to be an industrial electronics technician and plan to get your training at home, here are a few hints: Compare the school catalogs—not for fancy presentation, but for hard facts about subject matter and course objectives—a communications technician is not an industrial technician. See how long the course lasts—how many hours you'll be putting in. Be realistic and don't expect things of a study course that it was never designed to produce. A good course in basic electronics or radio/TV repair may be worth every cent it costs and more, but it is not in-

GET THE HOT ONES



...the Turner +2
with volume control



... and a **FREE**
Florentine Lighter

To introduce you to the +2 (the first microphone with a fingertip volume control), Turner is offering a FREE bonus — a beautiful Florentine lighter with each +2 sold! The lighter is the windproof type, decorated by the intricate carvings made famous by ancient Florentine silversmiths; and the microphone is the one-of-a-kind unit that is drawing acclaim all over the country.

The +2 is a transistorized base station microphone with a tailored frequency re-

sponse of 300-3,500 cps; it features touch-to-talk or lock on off switching, and works with all transistor or tube sets. And more important, the +2 lets your present transmitter perform like it was NEW again — provides up to 50 times the output level you now have, with just the turn of a dial! List price, \$49.50.

See your CB dealer or parts jobber soon. Get your new +2 and ask about the free Florentine lighter.

In Canada: Tri-Tel Associates, Ltd.
Export: Ad Auriema, Inc., 85 Broad Street,
New York, N.Y. 10004

THE TURNER MICROPHONE COMPANY
933 17th Street N.E.
Cedar Rapids, Iowa

CIRCLE NO. 49 ON READER SERVICE PAGE

tended to train engineering technicians.

To put it another way, if you want to work in industry, think in terms of how *much* education you're going to get—whether you hope to get it at home or in a residence school. Then, with a sound education, no matter where you get it, you'll qualify when you apply for a job with a firm that has up-to-date attitudes.


As one employment manager for a computer firm put it, "We don't expect a student to learn everything he'll need at school. But we do look for students who have a sound background, and who have growth potential far beyond their present capabilities. When we find a man like that, we hire him. And we don't care where he went to school." —30—

QUIZ ANSWERS

(Quiz appears on page 64)

Since the total circuit resistance is 5 ohms, by Ohm's law the total current is 6 amperes ($I = E/R = 30/5 = 6$). Thus, the current through each branch is 2 ohms, and the drop across each resistor is as shown in the schematic diagram. The voltage readings, and the test points across which they are taken are listed below.

VOLTS	TERMINALS
0	EH
2	FB
4	AG, DE, HD, GC
6	CD
8	AC
10	CE, CH, EF, GD, HF
12	EB, HB
14	AD, DF, GE, GH
16	DB
18	AE, AH
20	CF
22	CB
24	GF
26	GB
28	AF
30	AB

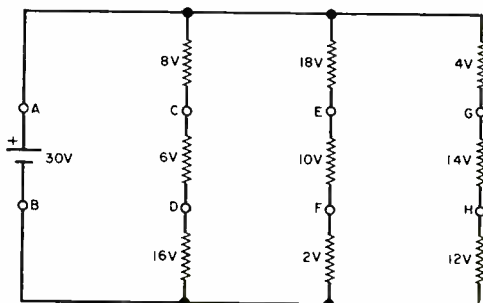

October, 1966

GET MORE ACTION WITH

MULTI-ELMAC
PRECISION MADE,
POPULAR PRICED
CB UNITS!

*** CITI-FONE SS \$16950**

**FULL
23 CHANNEL**

AC-DC Operation
Illuminated Meter
& Channel Selection
Triple Tuned RF
"Noise Immune"
Squelch, Double
Tuned H's, Ready to Operate



*** CITI-FONE 99 \$9950**

**FULL
8 CHANNEL**

AC-DC Operation
Delayed AVC
Electronic Switching
2 Stage Pre-Amp
Illuminated "5"
Meter, Complete
with Crystal for 1 Channel



*** CITI-FONE II \$4995**

SOLID STATE

Transmitter Converter
Compact 5 1/4 x
4 1/2 x 11 1/2 9
Transistor, 2
Diodes, 5 Watt
Input (FCC Max.)
100% Modulation, 12 VDC
Operation, Complete with Crystal for
1 Channel



Please send further information on Citi-Fone SS , 99 , II

MULTI-ELMAC CO.

21470 Coolidge • Oak Park, Michigan 48237

NAME _____

ADDRESS _____


CITY _____

STATE _____ ZONE _____

CIRCLE NO. 33 ON READER SERVICE PAGE

What's New With Heath These Days?

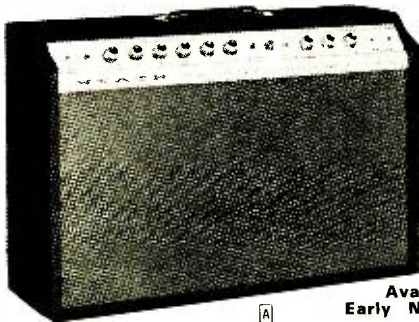Harmony-by-Heathkit Electric Guitars & Heathkit Guitar Amplifier



Kit TA-16
\$129⁹⁵

A

Available
Early November

B
Kit TG-46
\$219⁹⁵
(save \$109.55)

C
Kit TG-26
\$99⁹⁵
(save \$45)

D
Kit TG-36
\$119⁹⁵
(save \$38.55)



A NEW Heathkit Transistor Guitar Amplifier

60 watts peak power; two channels — one for accompaniment, accordion, organ, or mike, — the other for special effects . . . with both variable reverb and tremolo; 2 inputs each channel; two foot switches for reverb & tremolo; two 12" heavy-duty speakers; line bypass reversing switch for hum reduction; one easy-to-build circuit board with 13 transistors, 6 diodes; 28" W. x 9" D. x 19" H. leather-textured black vinyl cabinet of 3/4" stock; 120 v. or 240 v. AC operation; extruded aluminum front panel. 44 lbs.

American Made Harmony-By-Heathkit Guitars

All guitars include instruction book, tuning record, pick, connecting cord, deluxe red leather cushioned neck strap and chipboard carrying case. All wood parts assembled and factory finished — you just mount metal parts, pickups & controls in pre-drilled holes and install strings.

B Deluxe Guitar . . . 3 Pickups . . . Hollow Body

Double-cutaway for easy fingering of 16 frets; ultra-slim fingerboard — 24 1/2" scale; ultra-slim "uniform feel" neck with adjustable Torque-Lok

reinforcing rod; 3 pickups with individually adjustable pole-pieces under each string for emphasis and balance; 3 silent switches select 7 pickup combinations; 6 controls for pickup tone and volume; professional Bigsby vibrato tail-piece; curly maple arched body — 2" rim — shaded cherry red. 17 lbs.

C Silhouette Solid-Body Guitar . . . 2 Pickups

Modified double cutaway leaves 15 frets clear of body; ultra-slim fingerboard — 24 1/2" scale; ultra-slim neck for "uniform feel"; Torque-Lok adjustable reinforcing rod; 2 pickups with individually adjustable pole-pieces under each string; 4 controls for tone and volume; Harmony type "W" vibrato tail-piece; hardwood solid body, 1 1/2" rim, shaded cherry red. 13 lbs.


D "Rocket" Guitar . . . 2 Pickups . . . Hollow Body

Single cutaway style; ultra-slim fingerboard; ultra-slim neck, steel rod reinforced; 2 pickups with individually adjustable pole-pieces for each string; silent switch selects 3 combinations of pickups; 4 controls for tone and volume; Harmony type "W" vibrato tailpiece; laminated maple arched body, 2" rim; shaded cherry red. 17 lbs.

NEW 12" Transistor Portable TV — First Kit With Integrated Circuit


Unusually sensitive performance. Plays anywhere . . . runs on household 117 v. AC, any 12 v. battery, or optional rechargeable battery pack (\$39.95); receives all channels; new integrated sound circuit replaces 39 components; preassembled, prealigned tuners; high gain IF strip; Gated AGC for steady, jitter-free pictures; front-panel mounted speaker; assembles in only 10 hours. Rugged high impact plastic cabinet measures a compact 11 1/2" H x 15 3/4" W x 9 3/8" D. 23 lbs.

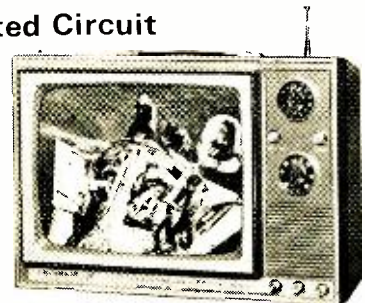Kit GR-104
\$119⁹⁵
AVAILABLE
LATE OCTOBER



9 New Kits You Can Build

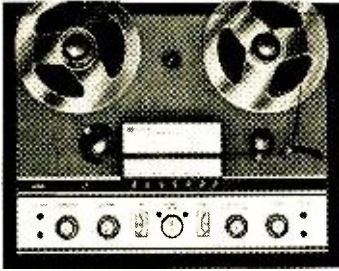NEW Heathkit® /Magnecord® 1020 4-Track Stereo Recorder Kit



Kit AD-16
\$399⁵⁰
 (less cabinet)

Save \$170 by doing the easy assembly yourself. Features solid-state circuitry; 4-track stereo or mono playback and record at 7½ & 3¼ ips; sound-on-sound, sound-with-sound and echo capabilities; 3 separate motors; solenoid operation; die-cast top-plate, flywheel and capstan shaft housing; all push-button controls; automatic shut-off; plus a host of other professional features. 45 lbs. Optional walnut base \$19.95, adapter ring \$4.75

NEW Deluxe SB-301 Amateur Band Receiver Kit



Kit SB-301
\$260⁰⁰
 (less speaker)

Complete coverage of 80 thru 10 meters with all crystals furnished, plus 15 to 15.5 MHz coverage for WWV; full RTTY reception capability; built-in switch-selected ANL; front-panel switching for control of 6 and 2 meter plug-in converters; crystal-controlled front-end for same rate tuning on all bands; 1 kHz dial calibrations — 100 kHz per dial revolution; plus the same styling and features of the famous Heathkit SB-300 Receiver. 23 lbs.

2-Watt Walkie-Talkie



Assembled
 GRS-65A
\$99⁹⁵

New . . . Factory Assembled. Up to 6 mile range; rechargeable battery; 9 silicon transistors, 2 diodes; superhet receiver; squelch; ANL; aluminum case. 3 lbs. 117 v. AC battery charger & cigarette lighter charging cord \$9.95. Crystals \$1.99 ea.

NEW Portable Phonograph Kit

Kit GD-16
\$39⁹⁵

All Transistor. Assembles in 1 to 2 hours. Preassembled 4-speed automatic mono changer; 4" x 6" speaker; dual Sapphire styli; 45 rpm adaptor; olive & beige preassembled cabinet; 117 v. AC. 23 lbs.



FREE

World's Largest
 Electronic Kit
 Catalog!

108 pages ... many in full color ... describe these and over 250 easy-to-build Heathkits for color TV, stereo/hi-fi, CB, ham, marine, shortwave, test, educational, home and hobby items. Mail coupon for your free copy.

HEATH COMPANY, Dept. 10-10
 Benton Harbor, Michigan 49022

Enclosed is \$ _____, plus shipping.

Please send model (s) _____

Please send FREE 1967 Heathkit Catalog.

Name _____

Address _____



City _____

State _____

Zip _____

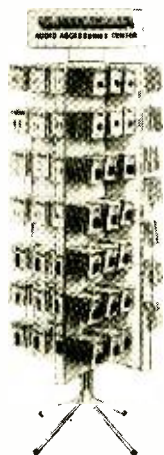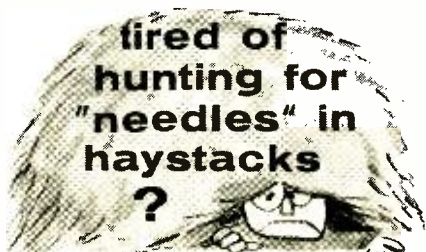Prices & specifications subject to change without notice. CL-258





SWITCHCRAFT®

AUDIO ACCESSORY SELF-SERVICE CENTER

At last! All the confusion and "wait" gone. Fail-Safe quality. Packages factory sealed, precisely labeled by name, type, mating part, price. Guaranteed.

Send for Complete Catalog:

SWITCHCRAFT, INCORPORATED

5563 No. Elston Ave., Chicago, Illinois 60630

CIRCLE NO. 56 ON READER SERVICE PAGE

**FIND THE
PRECISE
AUDIO
ACCESSORY
YOU NEED
FAST!**

- Jacks
- Plugs
- Adaptors
- Couplers
- Extension Jacks
- Speaker Controls
- "Mini-Mix"—mixers, etc.

look for the

GET INTO ELECTRONICS

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar, automation. Basic & advanced courses. Electronic Engineering Technology and Electronic Technology curricula both available. Associate degree in 29 months. B.S. obtainable. G.I. approved. Start February, September, Dornas, campus. High School graduate or equivalent. Catalog

VALPARAISO TECHNICAL INSTITUTE

DEPARTMENT PE, VALPARAISO, INDIANA



LEARN Electronics Engineering AT HOME

Fix TV, design automation systems, learn transistors, complete electronics. College level Home Study courses taught so you can understand them. Earn more in the highly paid electronics industry. Computers, Missiles, theory and practical. Kits furnished. Over 30,000 graduates now employed. Resident classes at our Chicago campus if desired. Founded 1931. Catalog: "Yes" write for information about G.I. Bill Training.

AMERICAN INSTITUTE OF ENGINEERING & TECHNOLOGY
1137 West Fullerton Parkway, Chicago, Illinois 60614

TIME-SIGNAL RECEIVER

(Continued from page 46)

author found that indoor reception could be improved by placing the receiver's antenna close to a telephone or an electrical fixture.

If you find it hard to decide which "band" of frequencies is best suited to your location, you can monitor each frequency for a period of time with a communications receiver. The optimum frequencies and listening time can be determined quickly in this manner.

To change frequencies in the receiver, simply plug in the appropriate crystal, and tune *C2* and *C6*. Remember, you can cover *two* time-signal stations with the 10- μ H coils, and *three* stations with the 5.6- μ H coils. -30-

TIME SIGNAL BROADCASTS

CHU Reception of CHU on 7.335 MHz is possible along most of the eastern seaboard (north of South Carolina) at any time between 0400-1100 and 1400-0100 EST. On the frequency of 14.670 MHz, CHU is heard throughout the remainder of the eastern seaboard and as far west as Denver, Colo., from 0800 to 2100 CST. CHU on 14.670 MHz is also audible along the West Coast in the early evenings.

WWV Pending the move of WWV from Maryland to Colorado, it is difficult to accurately predict reception on either 10.0 or 15.0 MHz. However, it is believed that the 10.0-MHz broadcast will be audible with good signal strength throughout most of North America from 0800 to 2200 EST. At the present time, West Coast users should tune to 10.0 MHz or 15.0 MHz for the transmission of WWVH, Maui, Hawaii.

It will be necessary to choose the "listening" frequency best suited to your needs and to your geographical location. Reception 100% of the time, day and night, is not possible on one frequency only (unless, of course, you live close to the transmitters). Some frequencies are better at night, others during the day.

Complete information on the technical services provided by the NBS standard time stations can be found in "Standard Frequency and Time Services of the National Bureau of Standards, Miscellaneous Publication 236," which is available from the Superintendent of Documents, U.S. Government Printing Office, Washington, D.C. 20402, for 15 cents. Complete technical information on CHU is contained in a leaflet entitled "Time Service Bulletin B-16," available from the Department of Mines and Technical Surveys, Dominion Observatory, Ottawa, Canada, at no charge.

DECIBELS

(Continued from page 78)

scale is opposite 1.732 volts on the a.c. scale, then the meter is calibrated using 6 mW in 500 ohms as the reference level.

Just as different a.c. voltmeter ranges require different scale markings or multipliers, so do the different ranges affect the dB readings. However, for dB readings you simply add a fixed number of dB to the direct readings, depending upon which range you are using. For example, if the signal is strong enough to throw the meter off scale, you should switch to a higher a.c.-volts range, and add the number of dB to the dB scale reading as shown in Table 1, which appears on page 78.

Suppose your meter reads +4.5 dB and the range switch is set to the 150-volt range (where 0 dB = 1 mW in 600 ohms). The true dB reading would be +4.5 plus 40, or +44.5 dB, if measured across a 600-ohm impedance.

If the indicated reading is below 0 dB, remember that this is a negative quantity and must be added *algebraically* to get the true reading. For example: if the indicated reading is -3.5 dB, and the function switch is set to the 500-volt range, the true reading is $-3.5 + 50$ or +46.5 dB.

Making dB Measurements. Even if your VOM does not have a dB scale, you still can obtain dB measurements. Just make a.c. voltage measurements across a 600-ohm impedance, or 500-ohm impedance, depending upon which reference you want to use, and use the "Volts to Decibels" graph to find the dB value.

But, what if you can't measure across a 600-ohm or 500-ohm impedance in the circuit you want to measure? For instance, can you measure dB across an 8-ohm load, such as a speaker? Yes, you can. First measure the a.c. voltage across the impedance you are dealing with, and apply it to the same graph to obtain an "unadjusted" dB value. If your meter has a dB scale, you can read the meter instead of the chart to obtain this unadjusted dB value.

To save you the fuss of using a for-

The most experienced all-channel amplifiers keep getting better and better

Blonder-Tongue pioneered and developed the industry's first all-channel, all-transistor TV signal amplifier. That was more than two years ago. During that period this top-rated original design has brought superior all-channel and color reception to homes located in all reception areas.

Now, we are employing the better performing silicon transistor in these amplifiers. The result: 40% more gain in the lowband, 100% more in the highband, greater ability to handle strong signals without overloading and better signal to noise ratio. Color or black-and-white TV reception on any and all channels from 2 to 83 is better than ever.


Only Blonder-Tongue gives you a choice of all-channel, color-approved amplifiers:

U/Vamp-2 — mast-mounted, deluxe 2-transistor UHF/VHF amplifier. Weatherproof housing. Remote power supply. AC operated. Separate UHF and VHF 300-ohm inputs and outputs. Ideal for separate UHF and VHF antennas.

Coloramp-U/V—same as the U/Vamp-2 except it has a single UHF/VHF input. Matches the new all-channel antennas.

V/U-AII-2 — deluxe 2-transistor indoor UHF/VHF amplifier. Can drive up to 4 TV sets. Has built-in 2-way splitter with excellent impedance match and isolation for interference and ghost-free reception.

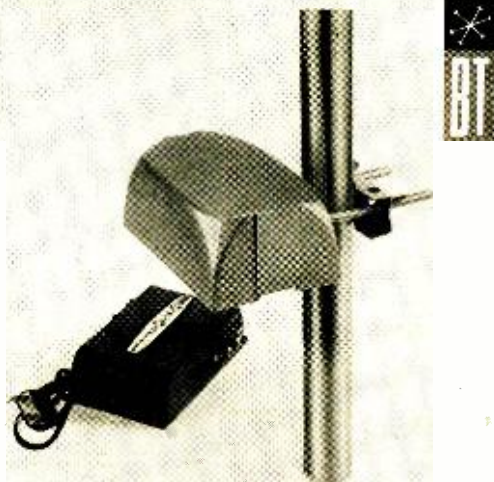These UHF/VHF amplifiers are just one more reason to go all-channel from antenna to TV with color-approved Blonder-Tongue TV products. Of course, we also have a full line of top quality VHF, VHF/FM and UHF-only amplifiers. Write for free catalog #74. Blonder-Tongue Laboratories, Inc., 9 Alling St. Newark, N.J.



CIRCLE NO. 7 ON READER SERVICE PAGE

PACE


the
NEW
 leader
 in
 all
 solid
 state
 design
 presents
 the
 most
 complete
 line of
 high
 quality
 all silicon
 transistor
Citizen
Band
2-way
 radios
 ((P))
PACE




2 watt hand held
 PACE MATE — \$119



6-Channel mobile
 PACE I — \$129

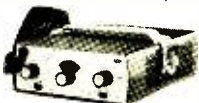

12-Channel mobile
 PACE II — \$169

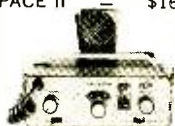

12-Channel mobile
 with S-meter
 PACE II-S — \$179



23-Channel complete
 PLUS-23 — \$199



Prestige
 base or mobile
 PACE 5000 — \$250



Prestige portable
 PACE VPH — \$384

Write for literature and
 the name of your
 nearest Pace dealer.

COMMUNICATIONS CORP.

24049 FRAMPTON AVE., HARBOR CITY, CALIF. 90710
 PHONE: (213) 325-8444

CIRCLE NO. 35 ON READER SERVICE PAGE

mula to find the correction factor to adjust your reading, just add the number of dB as shown in Table 2. If, for example, you measure the signal across an 8-ohm speaker voice coil, you must add 18.8 dB to the "unadjusted" dB reading (if your meter is calibrated to 0 dB = 1 mW in 600 ohms) to obtain a true reading.

When making dB measurements, be sure you are measuring the signal only—don't allow your meter to be influenced by other voltages, such as bias and B+ voltage. Most VOM's with dB scales have a separate test-lead jack or function-switch position which puts a capacitor in series with one of the test leads to block d.c. voltage. If your meter doesn't have a capacitor connected in this manner, you should insert one between one test lead and the measuring point. A 0.1- μ F tubular, 600-WVDC capacitor is ample for most conditions.

When measuring low-level high impedance circuits, such as the input grid of a tube, even a high-resistance VOM can impose enough of a load on the circuit to produce "false" readings. In such cases, a VTVM should be used. Its high-input resistance is not likely to appreciably load most circuits.

Many VTVM's have a dB scale which is used in the same way as the dB scale on a VOM. If your VTVM does not have a dB scale, use the a.c. volt scale, refer to the graphs, and forget about the formulas. -30-

IMPEDANCE CORRECTION FACTORS

0 dB = 1 mW in 600 ohms		0 dB = 6 mW in 500 ohms	
Impedance (ohms)	Correction (dB)	Impedance (ohms)	Correction (dB)
600	0	600	-0.8
500	+0.8	500	0
300	+3.0	300	+2
250	+3.8	250	+3
150	+6.0	150	+4.8
50	+10.8	50	+10
8	+18.8	8	+18
3.2	+22.7	3.2	+21.9

Table 2. If for some reason you cannot make dB measurements across a reference impedance, you can still use your meter. Simply add the appropriate correction factor. You can drop the fractional part of a dB and work to the nearest whole number.

SOLID STATE

(Continued from page 85)

The Triac comes in a TO-5 case, and the other components are small enough to fit on a 1" x 2" circuit board which can then be placed in a standard electrical box beneath the outlet. With care, the complete circuit could be assembled in a lamp base or even in a lamp socket.

New Developments. Several new items can be reported this month:

- Industry's first plastic-encapsulated power transistor for audio applications has been announced by Texas Instruments, Inc. (Dallas, Tex.). Designated as Type TIP24, the new transistor is an epitaxial planar silicon device designed for Class B operation with up to 20 watts r.m.s. power. The TIP24's collector is in electrical contact with a special mounting tab, as shown in Fig. 3. This permits the unit to be mounted on a heat sink or chassis by means of a single hole, and with one sheet-metal screw.
- Motorola Semiconductor Products (Phoenix, Ariz.) has introduced a line of four digital-type integrated circuits as part of its expanding HEP line. To guide experimenters in the use of these new devices, Motorola has also published an interesting 100-page "Integrated Circuit Projects" manual. Selling for one dollar, the book describes a number of IC projects, including a binary computer, square-wave generator, and an electronic organ.
- Meanwhile, back at the research labs, IBM has discovered a negative-resistance effect in metal-oxide-semiconductor (MOS) junctions which may lead to a simple, in-

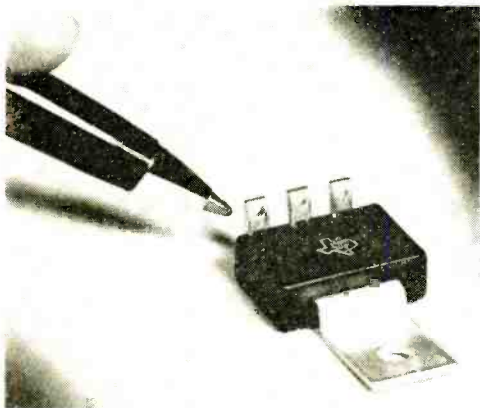


Fig. 3. Produced by Texas Instruments, Inc., this plastic encapsulated power transistor can handle up to 20 watts r.m.s. of audio frequency power.

October, 1966

Don't blame the TV set for poor color reception...


Good TV reception starts on the roof. If the signal delivered to the TV set isn't good to begin with, there's nothing any TV set can do about it. The moral: start at the top with the best. That's Color Ranger UHF/VHF/FM log periodic antennas by Blonder-Tongue.

There's a Color Ranger for any location from deep fringe to prime signal area, and they all offer flat response for top reception on *all* channels; a broad, flat bandpass for top color reception; exceptional front-to-back ratio to eliminate ghosting, and precise impedance match to insure maximum signal transfer to the set to prevent reflected signals in the cable.

Color Rangers have construction features found on no other antenna: double-boom construction; extra thick elements reinforced with 6" tubing; spring-loaded knife-edge contact points which maintain permanent electrical contact; strain-relief lugs for 300-ohm twinlead connections with a choice of 75-ohm coax or 300-ohm twinlead connection.

For UHF there's the 11-element log periodic U-Ranger. Slips quickly and easily on any VHF Color Ranger, makes your VHF Color Ranger an all-channel antenna... and with only a single download! No additional couplers to buy!

If you go for FM-Stereo, get acquainted with the Stereo Rangers for unbelievably brilliant high-fidelity FM-Stereo reception. Color Ranger and Stereo Ranger antennas are just two more reasons for you to go all-channel from antenna to TV set with color-approved and certified-for-stereo Blonder-Tongue TV/FM products. Write for free catalogs #52 and #88. Blonder-Tongue Laboratories, Inc., 9 Alling Street, Newark, N.J.

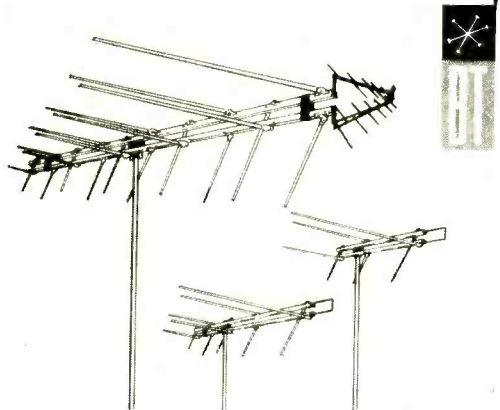


CIRCLE NO. 8 ON READER SERVICE PAGE

119

Plan and build your speaker system of tomorrow today!

The P.S.E. Way

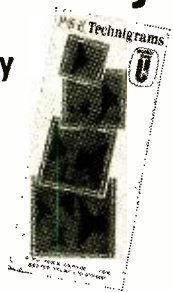University's PSE — Planned Speaker Expansion is a master blueprint for better stereo speaker systems. See your University Dealer today, or write for your FREE PSE Technigrams.



UNIVERSITY SOUND
A DIVISION OF LTV LING ALTEC, INC.

Dept. K64 P.O. Box 1056, Oklahoma City, Okla.

Name _____

Address _____

City _____

State _____ Zip _____

CIRCLE NO. 52 ON READER SERVICE PAGE

AM/FM VHF RECEIVERS POLICE • FIRE • AIRCRAFT AMATEUR • GENERAL COVERAGE

The new 364B is a completely self contained highly sensitive receiver offering the user continuous AM/FM coverage from 26 to 54 and 88 to 174 MC in eight bands. Features: superhet circuitry, full vision calibrated dial with vernier drive, speaker, power transformer, ready to use for 110/120 V AC.



364B
\$49.95

348A Transistorized tuneable converter for use with car, home or portable radio. Ranges: 30-50, 115-130, 150-162 MC. Bat. incl. Same but crystal controlled for 12 V car use. (345A) \$29.95. Economy tuneable model (315T) same ranges \$18.95



348A
\$34.95



361C AUDIO EQUALIZER
\$44.95

Variable equalizer necessary for professional quality recording or playback. Ideal for use between mixer and tape recorder or tape to tape, etc. Write for details or send \$2.00 for LP demonstration record. Covers tape and disc recording techniques. Refunded with purchase.

Order direct or write for information

KUHN ELECTRONICS
20 GLENWOOD CINCINNATI 17, OHIO

CIRCLE NO. 29 ON READER SERVICE PAGE

expensive process for manufacturing tunnel diodes. In another area, IBM has developed a device which might be used for tuning monolithic integrated circuits . . . a sort of "tuning fork" consisting of a cantilevered silicon chip that vibrates at its given resonant frequency.

Transitips. In the last paragraph of his letter containing this month's featured circuit, reader Scott Marovich asked for tips on determining the amount of feedback needed by an oscillator circuit. Here are a few:

Theoretically, the feedback needed in a given circuit can be determined mathematically by taking into account the Q of the tuned circuits used, transistor gain, estimated circuit losses, coupling coefficients (if inductive feedback is used), and similar factors. In general, the feedback needed approximates the transistor's output signal level divided by stage gain.

In practice, however, the actual technique used by most engineers is a combination of intuition, measurement, calculations, testing, and empirical values. In other words, it is an "educated guess" followed by experiments and readjustments.

The feedback signal level is important if optimum circuit operation is to be achieved. If too little feedback is used, the circuit will not oscillate at all. If a critical amount is employed, the circuit may be unstable, either shifting frequency or dropping in and out of oscillation. If too much feedback is used, the circuit may again be unstable or may deliver a distorted output signal containing unwanted harmonics. Finally, if the feedback is excessively high, the oscillator may "block" at a rate determined by the circuit's RC time constant. With optimum feedback, the oscillator will be fairly stable, and deliver a clean, harmonic-free signal.

Three standard oscillator circuit configurations are illustrated in Fig. 4. They are (A) tickler feedback, (B) Hartley, and (C) Colpitts, using *pnp* transistors in common-emitter configurations. Tuning capacitors have been omitted to simplify the explanations, except where they are essential to circuit operation. However, *nnp* transistors can be used in any of the circuits if battery polarities are reversed. Also, modified forms of the circuits can be used in common-base and emitter-follower configurations if desired. With suitable component values, all three circuits can be used at frequencies ranging from audio through UHF, and at input power levels in the microwatt or multi-watt range.

Looking at the tickler feedback circuit in Fig 4(A), coil $L1$ serves as $Q1$'s collector load. In practice, this coil is generally

POPULAR ELECTRONICS

tuned by a shunt capacitor. Coil L_2 , inductively coupled to L_1 , provides an in-phase feedback signal to $Q1$'s base through capacitor $C1$. Base bias is furnished through $R1$.

The level of the feedback signal is determined primarily by the turns ratio of L_1 and L_2 , as well as by the degree of coupling. In practice, the turns ratio used is proportional to $Q1$'s gain, its base input impedance vs. collector output impedance, and circuit losses. The L_1 - L_2 turns ratio used with average transistors varies from 10:1 to 20:1. In heavily loaded power oscillator circuits, or in circuits where low-gain transistors are used, the turns ratio can be as low as 2:1. In high-gain, low-loss, lightly loaded circuits, on the other hand, ratios as high as 50:1 or 100:1 can be employed.

The Hartley oscillator in Fig. 4(B) is generally similar to the tickler feedback circuit, except that feedback is provided by an autotransformer or tapped coil (L_1) rather than by a two-winding transformer. As before, the feedback signal is coupled to $Q1$'s base through capacitor $C1$, while base bias is supplied through $R1$. Here, the point at which the ground (or emitter) tap is made is based on the same factors which determined the L_1 - L_2 ratio in the previous circuit. In typical oscillators of this type, the tap can be from 5% to 10% of the total number of turns, counting from the base end of the coil. In special cases, the tap can range from 50% of the turns to 1%.

In contrast to the Hartley circuit, which features a tapped inductor, the Colpitts os-


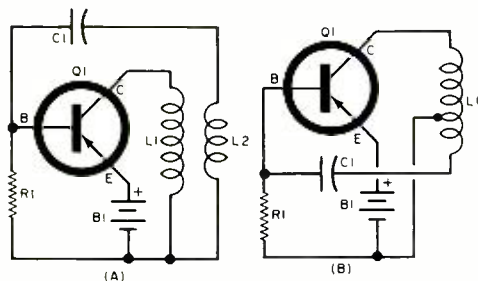


Fig. 4. Employing pnp transistors in common emitter configuration, the oscillator circuits shown here are: (A) tickler feedback, (B) the familiar Hartley, and (C) Colpitts. With suitable component values, all of these circuits can be used at UHF frequencies, in addition to low-frequency audio. Stable operation is achieved with controlled feedback.

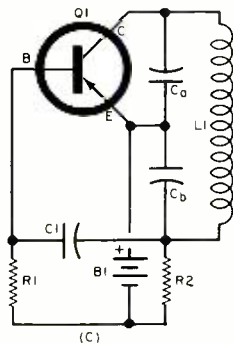

How "saving" 50¢ can ruin a \$700 color TV system!

The coupler is the least expensive item in a home TV system. Yet the wrong coupler can send the investment in a quality distribution system and TV set right down the drain.

At Blonder-Tongue, the same engineering skill and meticulous quality control goes into couplers that goes into professional MATV products. The result: high isolation between sets, extremely low insertion loss and sharp pictures (they're backmatched).

Blonder-Tongue gives you variety, too... the widest variety of color-approved, all-channel coupler models in the industry:

A-102U/V—deluxe 300-ohm 2-set model. Connects two sets to a single download.

A-104U/V—similar to A-102U/V-4-set model.

MDC-2VU—connects two coax (75-ohm) cables from TV sets to a single coax download.

TV-2—economy indoor model connects two sets to a single 300-ohm twinlead. Not recommended for weak signal areas.

Quality combiners and splitters are also essential to a good all-channel Color TV system. When you specify Blonder-Tongue, you get high quality, low loss and high isolation.

UVF-1—deluxe 300-ohm weatherproof model. Provides separate UHF, VHF and FM outlets from download carrying all three signals or feeds a single download from separate UHF, VHF and FM antennas.

UVF-C/S—a lower priced version of the UVF-1.

A-107—deluxe, weatherproof unit combines UHF and VHF antennas to a single 300-ohm download or provides separate UHF and VHF output at the TV set.

UV-C/S—indoor unit provides separate UHF and VHF outputs from a single 300-ohm cable carrying both signals, for connection to converter or TV set with separate UHF and VHF inputs.

Write for free catalog #74. Blonder-Tongue Laboratories, Inc., 9 Alling Street, Newark, N.J.



CIRCLE NO. 9 ON READER SERVICE PAGE

Olson



*** FREE**

Fill in coupon for a **FREE** One Year Subscription to **OLSON ELECTRONICS'** Fantastic Value Packed Catalog—Unheard of **LOW, LOW PRICES** on Brand Name Speakers, Changers, Tubes, Tools, Stereo Amps, Tuners, CB, and other Values. Credit plan available.

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

If you have a friend interested in electronics send his name and address for a **FREE** subscription also.

OLSON ELECTRONICS
INCORPORATED

525 S. Forge Street Akron, Ohio 44308

CIRCLE NO. 34 ON READER SERVICE PAGE

radio —

USEFUL TOOL, ABSORBING HOBBY

RADIO is not only a useful tool for business and personal use, but can also be an enjoyable leisure time activity. Licensed radio amateurs partake in the full range of radio's fascinations with the encouragement of the Federal Communications Commission — Emergency and CD work, message relaying, building, designing, experimenting, modifying, DX chasing, contests and even ragchewing.

THE mysteries of radio theory melt away, the erratic rhythms of Morse code begin to make sense when you base your study for an amateur license on the GATEWAY TO AMATEUR RADIO, a series of four booklets published by the hams' own society.

AMERICAN RADIO RELAY LEAGUE, Inc.
Newington, Connecticut 06111

The Radio Amateur's License Manual P10
Operating an Amateur Radio Station
\$2.00 Learning the Radiotelegraph Code
How to Become a Radio Amateur

Name.....

Street.....

City..... State..... Zip.....

cillator uses a tapped capacitor to furnish feedback. In Fig. 4(C), feedback is provided by series capacitors C_a to C_b , with $L1$'s tuning determined by their combined value (always less than the smallest capacitor in the series circuit). The actual ratios used for C_a and C_b range from 1:10 to 1:20 in practical circuits, but may drop to as low as 1:1 or go as high as 1:100 in critical designs. In a typical circuit, for example, C_a may have a value of 500 pF and C_b about 10,000 pF (or 0.01 μ F).

As a general rule, tickler feedback and Hartley-type oscillators are preferred where the circuit must cover a band of frequencies, as in receivers and signal generators, while the Colpitts circuit is used in fixed tuned applications, as in code practice oscillators, transmitters and signal calibrators.

That concludes our *Solid State* story for this month, fellows . . . until next month, may your transistors all have high *beta*'s and low leakage!

—Lou

AMATEUR RADIO

(Continued from page 92)

(TI); Cuba (CM, CO); Dominican Republic (HI); Ecuador (HC); El Salvador (YS); Greenland (stations whose call letters begin with XP); Haiti (HH); Honduras (HR); Israel (4X); Liberia (EL); Mexico (XE); Nicaragua (YN); Panama (HP); Paraguay (ZP); Peru (OA); Venezuela (YV); and all U.S. territories—without restriction.

Running patches or handling messages with countries *not* on this list is no way to score points for our side, but doing so with countries on the list is excellent public relations work.

NEWS AND VIEWS

Frederico "Fred" Po, DU1FP, 77 Mayon St., Quezon City, Philippines, built the "High Performance Transmitter" described in our January, 1962, column with the hope that he could work locals with it. The "locals" turned out to be all over the Philippines, Australia, India, Japan, Korea, Malaysia, Okinawa, and the 5th, 6th, and 7th U.S. call areas—not too bad for a 6L6 running 20 watts feeding a 40-meter dipole on 40 meters! Fred works into the United States best between 0800 and 1400 GMT . . . **Ron Azark, WN9RHU**, 8153 S. Hermitage St., Chicago, Ill., works the three low-frequency Novice bands with a Knight-Kit T-60 transmitter and two receivers. One receiver is a Lafayette HE-40, and the other is a "home-brew" unit which covers 10 through 160 meters. When not hamming, Ron is usually SWL'ing; he thinks that Generals are missing a good bet by not using 160 meters more for local contacts. If all goes according to plan, Ron will be a General when you read this and may be practicing what he preaches . . . **Patrick Devlin, WA5BPS**, president of the Tulsa

POPULAR ELECTRONICS

Repeater Organization, reports that they operate an "open" 2-meter repeater station on top of a 30-story building in the center of Tulsa. Talk-in frequency is 146.94 MHz; talk-out frequency is 146.34 MHz. The primary receiver is located on a water tower eight miles from the transmitter, and secondary receivers are being installed 20 and 35 miles away. Transmitter power is 330 watts, and all functions of the repeater are controlled via leased telephone lines and a 448-MHz radio link. Reputed to be the most sophisticated amateur repeater station in the United States, WA5LVT covers northeastern Oklahoma, southeastern Kansas, and adjacent parts of Arkansas and Missouri. It has also been heard with a "full-quieting signal" in Baltimore.

Ever since he earned his General Class license at the age of 12 back in 1961, **John Yurek, K3PGP**, Trafford Harrison City Rd., R.D. #6, Irwin, Pa., has been setting higher goals in amateur radio for himself—and reaching them. His latest achievement was to win first place in a Pennsylvania Junior Academy contest for an oral presentation of his success in bouncing his 432-MHz signals off the moon and back to the earth. John's next goal is to span the half-million mile round-trip journey to the moon on 2300 MHz. On the lower frequencies, K3PGP's Heathkit DX-100 transmitter and SB-10 SSB adapter, and Hallcrafters SX-100 receiver, have worked all states and many countries in all continents. An RCC certificate indicates that John likes to rag-chew, too—probably about his coin collection . . . **Brad Good, WB6LUC**, 4420 Charlemagne, Long Beach, Calif., installed the "Camper's Special" transmitter described in the August, 1965, issue on his bicycle and worked several stations, including a W7, on 3718 kHz CW. Then, Brad connected a carbon microphone in series with the battery lead to the output transistor and almost got himself killed. He was talking to W6KCX when he had an accident which demolished the bicycle and his receiver and left him bleeding from a deep gash in the chin and with a broken finger. Although he could not hear replies, Brad sent out a call for help, to which W6KCX and WB6OFD responded. After this experience, Brad feels that "bicycle mobile" is entirely too dangerous to be recommended . . . **Dave T. Motooka, WH6GBC**, 3812 Paki Ave., Honolulu, Hawaii, runs 70 watts to a home-brew transmitter feeding a Hy-Gain 14-AVQ vertical antenna on 40 meters; he receives on a venerable Hammarlund HQ-129A. Dave has worked Japan and American Samoa and has cards from 12 of the 13 states he has worked. With 2000 miles to go to the nearest one, Dave feels he may have a slight handicap in working all states, but he already has managed to work Georgia, North Carolina, and other states east of the Mississippi River.

Gary Thomas, WN1FJJ, 1973 East St., Pittsfield, Mass., keeps his home-built 25-watt transmitter and converted ARC-5 war-surplus receiver on 80 meters (the only amateur band the latter will tune, incidentally). He has QSL cards from nine of the 13 states he has worked, but he didn't mention whether any of the Canadians he has worked have come through with cards . . . **Phil Flick WA9NVY**, 1851 Church St., Wauwatosa, Wis., works AM and CW on all bands between 80 and 10 meters, and AM on two meters. A Johnson "Ranger" transmitter handles the lower bands and a Gonset G-63 does the receiving. A Heathkit "Twoer" and a converter ahead of the G-63 take care of 2 meters. Phil likes to collect certificates and just rag-chew—preferably on CW . . . **Terry "Ty" Conboy, WN7DOX**, 1670 Tualatin St., St. Helens, Oregon, has managed to get an 80-meter inverted-V antenna, a 15-meter "long wire," and a 15-meter vertical on a 100' x 65' lot. Supplementing the antennas with an EICO 723 transmitter and a Hammarlund HQ-170A receiver, Ty had Japan and 40 states worked when he passed his General examination. Ty will sked you—preferably on

Why professional MATV installers are fussy about matching transformers

The purpose of a matching transformer is to match 300- to 75-ohm or 75- to 300-ohm impedance . . . and match it precisely! Otherwise you get all the problems of mismatch—poor color, smear, ghosting, snow. And installers of coax systems know that Blonder-Tongue is famous for its honest-to-goodness UHF/VHF/FM matching transformers that offer really precise match at all frequencies.


Next time try one of these all-channel, color-approved matching transformers:

MT-283—Deluxe indoor or outdoor UHF/VHF/FM network. Great for matching all-band antennas to coaxial downlead, or 300-ohm set impedance to 75-ohm coax downlead. Mast-mounting hardware and mating male coax connector supplied.

Cablematch U/V—Indoor model. The same unit used in all-channel MATV systems. Features spade lugs for easy connection to 300-ohm TV set terminals. Mating Autoplug for coax supplied.

In addition to these all-channel models, B-T offers a wide choice of VHF/FM matching transformers to meet any need.

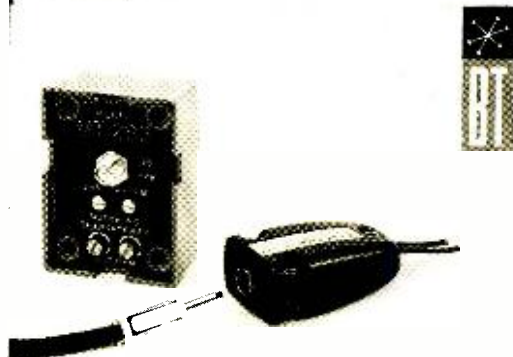Quality matching transformers like these are just one more reason why you should go Blonder-Tongue from antenna to TV set terminals. Write for free catalog #74. Blonder-Tongue Laboratories, Inc., 9 Alling Street, Newark, N.J.



CIRCLE NO. 10 ON READER SERVICE PAGE

NEW

"tray biens"

most versatile of all nutdriver sets

Handy "Tray Bien" sets lie flat or sit up on a bench, hang securely on a wall, pack neatly in a tool caddy.


Lightweight, durable, molded plastic trays feature fold-away stands, wall mounting holes, and a snap lock arrangement that holds tools firmly, yet permits easy removal.

Professional quality Xcelite nutdrivers have color coded, shockproof, breakproof, plastic (UL) handles; precision fit, case-hardened sockets.


Hangs up



Stands up

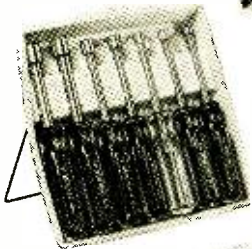

Holds tools securely

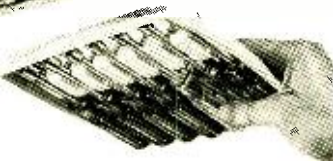

No. 127TB "Tray Bien" set — 7 solid shaft nutdrivers (3/16" thru 3/8" hex openings)

No. 137TB "Tray Bien" set — 5 solid shaft nutdrivers (3/16" thru 3/8" hex openings) and 2 hollow shaft nutdrivers (1/2" and 5/8" hex openings)

No. 147TB "Tray Bien" set — 7 hollow shaft nutdrivers (1/4" thru 1/2" hex openings)



XCELITE INC. • 20 BANK ST., ORCHARD PARK, N. Y. 14127
Send Bulletin N666 on "Tray Bien" Nutdriver Sets.

name _____
address _____
city _____ state & zone _____

CIRCLE NO. 54 ON READER SERVICE PAGE

Sunday—if you need Oregon or a Rag Chewer's Club certificate.

Let's see your "News and Views" in next month's column. Pictures and club bulletins are welcome. Send them to: Herb S. Briar, W9EGQ, Amateur Radio Editor, POPULAR ELECTRONICS, P.O. Box 678, Gary, Ind. 46401.

73. Herb, W9EGQ

ON THE CITIZENS BAND

(Continued from page 93)

authorities to help when and where needed with communications, first aid, and other types of assistance. There's an even better chance that they would do a story involving an emergency where CB radio lent a helping hand, regardless of whether the assist involved a lone CB'er in his car, or an entire network involving the city, county, or state.

Follow these guidelines the next time your group has an item you feel would be of interest to area and national readers and viewers:

(1) Carefully, with necessary detail, type the story on one side of as many pages as needed, double-spaced. Be factual, but not wordy. Be sure to identify the source of the material, the writer, and where he may be contacted for further information. (If the story originates from a club that publishes its own newspaper, the same printing process can be used for the story.) Be sure to identify the item as a "Press Release" or "News Release."

(2) Send copies of the story to all radio stations within reception range of your area. Send copies, with a good, clear glossy



"Us CB operators would rather fight than switch channels."



The latest in CB gear was displayed by local dealers during the Rock River Valley CB Club's second annual jamboree in the Rockford, Ill., Armory.

photograph pertaining to the story, if possible, to all newspapers in your city or town; an 8" x 10" print is usually preferred, but a 4" x 5" size is acceptable in some instances. And send copies to all TV stations covering the vicinity. Television stations can also use polaroid prints (in addition to 8" x 10" photos) by shooting them on "live" TV cameras. Most TV stations are also equipped with 35-mm. projection equipment to show black and white or color transparencies.

(3) If the story is of the utmost urgency, (in the case of an emergency assist), telephone the local news media as soon as possible. They will take your story by landline and then rewrite prior to air or press time.

(4) Finally, take the same story in its original form, or in the form of a reprint from the newspaper, plus photo if possible, and forward it to Matt P. Spinello, CB Edi-

tor, POPULAR ELECTRONICS, One Park Avenue, New York, N. Y. 10016. Newspapers and TV studios will usually cooperate by supplying you with a print and permission to reprint. We'll spread the same story to our half-million readers to help promote the CBI (Citizens Band Image) to those who should know that "there are two sides to every story."

Successful Jamboree. The Rock River Valley CB Club, of Rockford, Ill., advises that attendance at its second annual hoopla last summer was nearly double that in 1965. An estimated 9000 to 10,000 passed through Rockford Armory doors during the one-day event. The jam featured a long list of entertainment, nearly a hundred prizes, and excellent displays by local and area dealers. Club membership is currently 220.

1966 OTCB CLUB ROSTER

The following are recently organized CB clubs or groups reporting to "On the Citizens Band" for the first time:

Lake Charles, Louisiana—*Pelican CB Club*. Attached to REACT, this club assists in all community emergencies. Membership: 18. Officers: Alvin O. Chambers, KMR5245, president; David Sweet, KMR6814, vice president; Mrs. Bettie Chambers, secretary; J. B. Clark, KMR1952, treasurer; Edmond Vital, KKR3902, secretary/treasurer; Essie May Vital, business manager; and Wilfred Mathew, KKR3877, assistant business manager.

Bronx, New York—*North East Bronx REACT*. Club monitors REACT official calling channel 9, plus channel 21. Six mobiles have been appointed to various parts of the city to serve the Bronx, Manhattan, and Westchester. Current membership: 12. Club coordinators: Tom Gregor, KMD4148; and Dave Nager, KOD0761.

Port Townsend, Washington—*Jefferson County CB Club*. Also registered with REACT, this group monitors channel 9 on a 24-hour basis, and keeps in contact with police and sheriff departments, both monitoring CB radio. They are also associated with CD activities and search and rescue. Membership: 42. Current officers: Cres Raines, KLD0066, president; Willie Stratton, KLD2246, vice president; Maxine Doubek, KLD2389, secretary; and John Doubek, KLD2589, treasurer.

I'll CB'ing you!

—Matt, KHC2060

BE ON THE ALERT! with SONAR FM MONITOR RECEIVER



Perfect for

- Police • Fire
- Tow Trucks
- Civil Defense
- Weather
- Ship to Shore



\$89⁹⁵

Monitor the calls and know the facts as it happens.

NOW!—8 Super Deluxe FM communication receivers to meet your particular needs for home, office or car. Powerful and dependable. Engineered for rugged service under all operating conditions. Featuring High frequency oscillator, temperature compensated for stability, RF amplifier for maximum sensitivity, illuminated dial, safety rated components and ALL Aluminum construction plus many other outstanding features. Operates on 110 VAC. Includes power cord, mounting bracket.

Model FR-101 — (25-50 mc) Model FR-102 — (15-17.5 mc)

Slightly higher prices for DC and XTAL controls

SONAR RADIO CORPORATION, 73 Wortman Ave., Bklyn. 7, N.Y.
Please send complete information FR101/102 Monitor Receiver Dept. 502

Name _____
Address _____
City _____ State _____

CIRCLE NO. 46 ON READER SERVICE PAGE



(ACTUAL SIZE)


HOW GOOD IS A TEENY WEENY CARTRIDGE THAT CAN'T EVEN HUM?

Great! Full stereo separation even at 15,000 cps./4 poles, 4 coils & 3 magnets for better balance & phenomenal frequency response/ Fully shielded/ Lowest 1M distortion (elasto-shear suspension)/ Highest output (8 Mv. per channel)/ Lowest tracking for longer record wear/ Empire 888 living cartridge series from \$14.95




EMPIRE SCIENTIFIC CORP., 845 STEWART AVENUE, GARDEN CITY, NEW YORK
CIRCLE NO. 17 ON READER SERVICE PAGE

The Heart of your

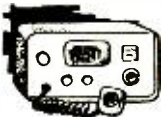

Radio is Its

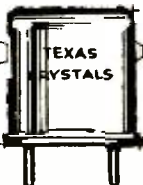

INSIST ON

CQC*

* Controlled Quality Crystals available only from Texas Crystals dealers. Extensive precision testing throughout manufacture enables Texas Crystals to unconditionally guarantee their frequency control crystals. Use of Texas Crystals in space program and by other governmental agencies is evidence of the quality you can count on.

If your dealer can't supply your needs, send his name with your request for catalog to our plant nearest you.



TEXAS CRYSTALS

Division of Whitehall Electronics Corp.

1000 Crystal Drive
Fort Myers, Fla. 33901
Phone: 813-936-2109

4117 W. Jefferson Blvd.
Los Angeles, Calif. 90016
Phone: 213-731-2258

CIRCLE NO. 48 ON READER SERVICE PAGE

SHORT-WAVE LISTENING

(Continued from page 95)

ways—thought to be a first for this area. According to this item, WNEW-FM has five girl broadcasters who are on the air, live, 14 hours daily, seven days a week.

The North American Short-Wave Association has decided to restrict club activities to the short-wave broadcasting band. Heretofore, the NASWA had considered reporting on BCB, utility stations, TV & FM, plus short-wave DX. Don Jensen and Ron Luyster will share the duties of collecting DX information. You can get more details on the NASWA by writing to William Eddings, 1503 Fifth Ave., Apartment A2, Altoona, Pa. 16602.

A new pirate station has been noted by West Coast listeners. Operating on about 5675 kHz, or "55 meters" as stated by the station, it has been heard around 0500-0530 with American rock-and-roll records. The identification is *The Voice of the Purple Pumpkin*, and the station urges its listeners to "protect your country from the Communist conspiracy, support the Vietnam Day Committee and the John Birch Society." As is generally the case with American bootleg stations, its broadcasters will probably continue to have their fun and believe that they cannot be located. Then the FCC will knock at the door!

CURRENT STATION REPORTS

The following is a resume of current reports. At time of compilation all reports are as accurate as possible, but stations may change frequency and/or schedule with little or no advance notice. All times shown are Greenwich Mean Time (GMT) and the 24-hour system is used. Reports should be sent to SHORT-WAVE LISTENING, P.O. Box 333, Cherry Hill, N.J. 08034, in time to reach your Short-Wave Editor by the fifth of each month; be sure to include your WPE Monitor Registration and the make and model number of your receiver. We regret that we are unable to use all of the reports received each month, due to space limitations, but we are grateful to all contributors.

Andorra—*R. des Valles*, La Vieja, is definitely operating; it was noted erratically on 6305 kHz. A recent QSL gave no schedule or other program information.

Ascension Island—*R. Sweden* reports that the BBC relay installation here is expected to be in operation and that monitors should check 15.350 kHz after 1800. An item received at deadline time indicates that the station may already be on the air; it was noted at 1645 in Somali to W. Africa although no positive ID was given.

Austria—*Osterreichischer Rundfunk*, Vienna, was logged on 17.875 kHz at 0558-0630 with German music and ID's in German, English, and French to the Middle East and India.

POPULAR ELECTRONICS

Bechuanaland—The BBC relay, Francistown, is now scheduled weekdays at 0400-0800 and 0945-2045 and on Sundays at 0400-2045 on 602 and 926 kHz, with 50 kW power; daily at 0400-0515 and 1700-2045 on 4845 kHz; weekdays at 0530-0800 and 0945-1645 and on Sundays at 0530-1645 on 7295 kHz. A station was noted on 7295 kHz at 0505 with an ID for the BBC World Service but the signal is far too strong for listening in non-target areas.

Bolivia—A new station, tentatively identified as *R. Trigal*, Trinidad, has been found on 4958 kHz until 0200/close; there is a world news bulletin in Spanish at 0045. *R. Union*, unlisted and possibly new, has been heard on 6305 kHz at 0139-0200 with Latin American programs, no advertising.

Brazil—Seldom-heard *R. Nacional*, Brasilia, was found on 15,445 kHz at 2324 with native music. *R. Rio*, also listed for this channel, apparently is inactive. *R. Jornal do Comercio*, Recife, has moved up from 11,825 to 11,838 kHz, dual to 9565 kHz, and was heard around 2128-2135. Also look for *R. Sao Carlos* on 2420 kHz evenings (local time) with music, including some Eng. selections.

Brunei—*R. Brunei*, 4865 kHz, is noted at 1023-1045 with Eng. pop tunes and anmts in an Oriental language, possibly Chinese. Time pips and anmts are given at 1045.

Congo—What is possibly *R. Bakwanga* is being heard around 0430 with native African music and a soft African dialect. Listed for 7295 kHz, it was logged on 7298 kHz.

Dominican Republic—Though listed as inactive, HIBE, *R. Mil*, Santo Domingo, is being noted from 0115 to 0400 in Spanish with Latin American vocals and some U.S. records. S/off is reported to be 0500. Tune for it on 4940 kHz.

Ecuador—Station HCJB, Quito, has been found on 15,325 kHz at 2000 s/on in German and at 0357 s/off on 6040 kHz. Station HCGB4, Esmeraldas, was noted from 0337 with Latin American vocals

SHORT-WAVE ABBREVIATIONS

anmt—Announcement	QRM—Station interference
BBC—British Broadcasting Corporation	QSL—Verification
B/C—Broadcast	R.—Radio
Eng.—English	s/off—Sign-off
ID—Identification	s/on—Sign-on
IS—Interval signal	WRTH— <i>World Radio Television Handbook</i>
kHz—Kilohertz	xmsn—Transmission
kW—Kilowatts	xmt—Transmitter
N.A.—North America	

and some "teen" music to 0401/close on 2495 kHz; different sources list it as *La Estacion de la Alegria* and *R. Nacional Espejo*. Station HCOB5, *R. Ondas Azules*, Cuenca, listed for 5025 kHz, is currently on 5023 kHz, which represents a move from the former 5105-kHz spot; the best time to hear it is 0230 and later.

Egypt—A new frequency for Cairo is 9580 kHz; the station can be heard in Eng. at 0130, but there are others on the channel, so you may have to dig for it.

Ethiopia—Station ETLF, Addis Ababa, has been caught on 15,400 kHz at 1625 s/off, following a program in native language but with closing anmts in English.

Ghana—This is the latest program schedule from Accra: to N.A. and the Caribbean on 6110 kHz at 0330-0430 and 11,800 kHz, dual to 9760 kHz at 1930-2130; to Ethiopia, Sudan, Somalia, India, Pakistan, China, Japan and the Far East on 6103 kHz at 0230-0330, 9545 kHz at 0430-0530, 15,280 kHz at 1830-1900, and 17,910 kHz at 1330-1430; to S. Africa, Central Africa, and Australasia on 9760 kHz at 0430-0530, 0600-0630, and 1430-1530; to W. Africa on 3240 kHz at 0530-0730 and 2000-2230, and on 6130 kHz at 1400-1945; to Europe on 9545 kHz

PEARCE-SIMPSON

CB IN ACTION AROUND THE WORLD



SENTRY • \$99.90
6 Channel Transistorized CB
• Hybrid circuitry



\$279.90
COMPANION II
5 Channel CB
• AC/DC power Supply



COMPANION III • \$139.90
All Solid State 6 Channel CB
• Exclusive "Touch-lap" Tuning



ALL SOLID STATE CB'S
Escort II • 11 Channel CB **\$219.90**
Director • 23 Channel CB **\$269.90**



GUARDIAN 23
23 Channel CB • **\$269.90**
• AC/DC power supply

PEARCE-SIMPSON, INC. PE1066

P.O. Box 800 • Biscayne Annex • Miami, Fla. 33152

Please send full information and model specifications.

Name

Address

City State

CIRCLE NO. 36 ON READER SERVICE PAGE


Silence IS Golden

(In Mobile Installations)

Only the Squires-Sanders Noise Silencer eliminates noise caused by ignition, power lines, etc. Only two transceivers have this exclusive feature—the Squires-Sanders "23'er" with full 23-channel capability (all crystals supplied) at \$235 and the "SSS" 5-channel model at \$185. Other features include an ultra-sensitive receiver and a powerful, long-range transmitter (special high efficiency RF output amplifier clipped and filtered audio, 100% modulation), 12 VDC power supply. Squires-Sanders Inc., Millington, N. J. 07946.



Squires Sanders

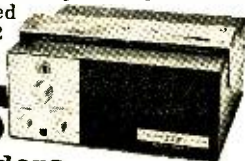

CIRCLE NO. 47 ON READER SERVICE PAGE



**WE DON'T
CEASE OUR
ELECTRONIC
IGNITION
SYSTEM
IS BEST...**

**OUR
CUSTOMERS DO!**

WRITE TODAY FOR FREE LITERATURE

JUDSON

RESEARCH AND MFG. CO.
CONSHOHOCKEN, PA. U.S.A.



CIRCLE NO. 27 ON READER SERVICE PAGE

at 0630-0730 and 2030-2230; to E. Africa on 6070 kHz at 0230-0330, on 15,285 kHz at 1630-1730, and on 21,720 kHz at 1430-1530.

Greece—Here's a list of active local Greek stations which differs from the latest *WRTH* listing: Larissa, 5954 kHz; Tripoli, 6003 kHz; Mytilini, 6240 kHz; Kurpenission, 6500 kHz; Chios, 6590 kHz; Sidirokastron, 7000 kHz; Serrai, 7028 kHz; Janina, 7099 kHz; and Kozani, 7948 kHz.

Guam—DX'ers have a good opportunity to verify this country via KUK25, an RCA utility station. On 15,475 kHz, it operates Saturdays, Sundays, and some weekdays from 1800 to as late as 0400, relaying telephone calls from servicemen. Listen for its beeper tone, sent out at 3-second intervals. This station verifies willingly, and no return postage is required. Reports go to 66 Broad Street, New York, N. Y., c/o RCA Communications, Inc.; mark them to the attention of C. N. Macpherson, Plant Opns., Eng.

Honduras—Station HRN, *La Voz de Honduras*, Tegucigalpa, is still on 5875 kHz and readable after 0000 in Spanish. Station HRHR, *La Voz de Occidente*, Santa Rosa de Copan, has been tuned at 0030 with commercials in Spanish and Latin American pop tunes on 5960 kHz.

Hungary—*R. Budapest* suffers intense BBC QRM on 9766 kHz at 0430 when news is presented in English.

India—*All Indian Radio*, Delhi, now has four General Overseas Service Eng. xmsms. Frequencies listed on the new schedule were given in meter bands only: at 2245-0115 to E., S.E., N.E. Asia, including Japan on 25, 31, 41, 49, and 75 meters; at 1000-1100 to China, Korea, Japan, Australia, and New Zealand on 16, 19, and 25 meters; at 1330-1500 to S. E. Asia on 19 and 25 meters; and at 1745-2230 to the United Kingdom and W. Europe (and to E. Africa to 1945, N. & W. Africa from 1945 to 2045, and Australia and New Zealand from 2045) on the 25-, 31-, and 41-meter bands.

Netherlands—The tentative schedule for *R. Nederland* for the period from November 6, 1966, to March 5, 1967, to N. A. is as follows: 0130-0400 on 9590 kHz (via Bonaire); 1600-1630 on 11,730 and 15,425 kHz; 1845-2030 on 15,115 kHz; 1930-2100 on 11,730 kHz; 2000-2200 on 6085 and 9590 kHz; and 2030-2100 on 9715 kHz.

Religious services for Dutch ships on the North Sea are broadcast from the Dutch hospital/church ship "De Hoop" on 2316 kHz, 500 watts, on Sundays at 0930-1030 and 1745-1830, Wednesdays at 1800-1900. Reports go to Damrak 95, Amsterdam.

Pakistan—Karachi was noted on 17,741 kHz, but weak, at 0355 in Urdu or a similar language; the ID, which was given in the same language at 0400, began a rapid fade. The dual outlet on 11,885 kHz was not readable.



Forty countries logged, 30 verified, is the record of Stephen Toder, WPE2NYR, of Kingston, N.Y. Steve's receiver is a Knight-Kit "Star Roamer."

POPULAR ELECTRONICS

SHORT-WAVE CONTRIBUTORS

Roger Camire (WPE1GEK), Manchester, N. H.
 William Graham (WPE2LMU), Binghamton, N. Y.
 Kenneth Coyne (WPE2LSI), Long Beach, N. Y.
 C. N. Coombe (WPE2MOB), Trenton, N. J.
 Bill Hafner (WPE2OJJ), West Islip, N. Y.
 Glenn Maler (WPE2OYO), Wildwood Crest, N. J.
 Don Jewler (WPE3GGH), Takoma Park, Md.
 Dan Henderson (WPE4GW), Laurel, Md.
 David Jones (WPE4HID), Albany, Ga.
 Mike Pearce (WPE4IVE), Abooskie, N. C.
 Danny Jamison (WPE4JEK), Richmond, Va.
 Walter Fair, Jr. (WPE5ECJ), Houston, Texas
 Eric Sands (WPE5ENH), New Orleans, La.
 Mac Wood (WPE6EOO), Piedmont, Calif.
 Trev Clegg (WPE6FAF), Fresno, Calif.
 Robert Eddy (WPE6EOW), Newport, Ohio
 Robert French (WPE6FGH), Bellaire, Ohio
 William Carlile (WPE6ISO), Columbus, Ohio
 Herbert Mickle, Jr. (WPE6IBU), Columbus, Ohio
 Mark Stein (WPE6IDD), Detroit, Mich.
 A. R. Niblack (WPE6KAM), Vincennes, Ind.
 John Beaver, Sr. (WPE6QAE), Pueblo, Colo.
 John Orven (WPE6QAT), Beatrice, Neb.
 Dave Carlson (WPE6QEOB), St. Louis, Mo.
 Jack Perolo (WPE6PEIC), Milwaukee, Wis.
 Dave Alpert, Morton Grove, Ill.
 Roger Dooley, Buffalo, N. Y.
 Bob Hill, Washington, D. C.
 Roy Langlands, Jr., Cranbrook, B. C., Canada
 Bernie Lansing, Rochester, N. Y.
 Edward Ramras, Queens Village, N. Y.
 Robert Smith, Jr., U. S. Embassy, Saigon, Vietnam
 George Stradtman, Jr., Bloomsburg, Pa.
DX'ing Worldwide, New York, N. Y.
Sweden Calling DX'ers, Stockholm, Sweden

Peru—Station OAX61, *R. Universidad de Arequipa*, is now on 6245 kHz and can be noted at times with lengthy classical music; peak listening time is around 0130 and later.

Philippines—The Far East Broadcasting Corp., Manila, has been monitored on a new frequency of 11,890 kHz, dual to DZH8, 11,855 kHz, in Russian to the Soviet Union with religious talks and music.

Portuguese Guinea—Bissau is thought to be the station noted leaving the air at 2359 with a Portuguese speaker after "A Portuguesa"; if so, this is a move back to 5042.5 kHz from the previously used 5017 kHz.

South Africa—*R. South Africa* is operating on a new and unlisted frequency, 5980 kHz, as logged at 0510/close, with an Eng. newscast being given just before that time. A new DX program has been introduced for Europe on Fridays in Eng. at 2245 on 9525 and 7270 kHz.

Sudan—*R. Omdurman* was noted twice with a move in frequency to 4950 kHz, and with s/on at 0400.


Switzerland—*R. Switzerland*, Berne, has Spanish to Central America on 9695 kHz from 0300 s/on, and Arabic to the Middle East on 17,830 kHz, from 1645 to 1715 with news, talks, and music.

USSR—*R. Moscow* was observed using 11,570 kHz for the Home Service in Russian at 2238, but the station switched to the N. A. Service at 2300. A station announcing as *R. Kier* has been noted on 11,850 kHz on Fridays at 0455 with a mailbag program.

Vatican City—*Vatican Radio* was noted on 15,285 kHz from 2300 in Portuguese and on 15,135 kHz to 1752/close with Eng. to Africa.

Vietnam (South)—We have received the following schedule for *R. Vietnam* through the courtesy of the U. S. Embassy in that country. Channel A, 9620, 6165, and 4877 kHz, is beamed north in Vietnamese (this schedule is printed in Vietnamese, and our best translation shows that Channel A operates 24 hours daily—Ed.). Channel B, 7245 kHz, beamed north-south, operates at 2200-0200, 0330-0700, and 0900-1600 (with Eng. dictation-speed news daily except at 1530-1600). Channel C, 9755 kHz, is beamed to Cambodia, at 2158-0000, 0400-0500, and 1015-1300 (Eng. lessons at 2230-2300, 2330-

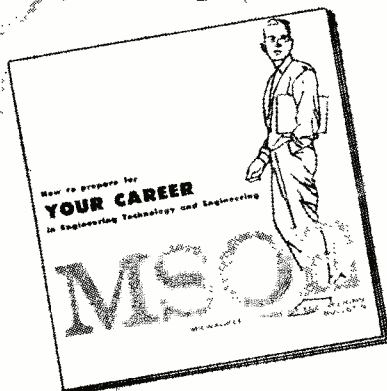Thinking of college and a space age career?



Send for this booklet on ENGINEERING TECHNOLOGY AND ENGINEERING

Learn how you can prepare for a dynamic career as an electrical or mechanical engineering technician or engineer in such exciting, growing fields as avionics, missiles, reliability control, fluid mechanics, data processing, metallurgy, microelectronics, and advanced aerospace research.

MSOE offers residence study programs leading to these degrees in engineering technology and engineering:

- 2 years — Associate in Applied Science
- 4 years — Bachelor of Science

Also get facts about scholarships and financial aids, job placement and other student services, plus photographs of MSOE technical laboratories and student activities. Courses approved for veteran training. For your copy, just mail the coupon — no obligation.

MSOE

Milwaukee, Wisconsin 53201

Milwaukee School of Engineering
 Dept. PE-1066, 1025 N. Milwaukee Street
 Milwaukee, Wisconsin 53201

Please send the "Your Career" booklet.
 I'm interested in

- Electrical fields Mechanical fields

Name.....Age.....

Address.....

City.....State.....ZIP.....

0000. and 1415-1430: Eng. dictation-speed news at 1200-1230; Eng. program listed for 1230-1300. Xmitr power is listed as 10 kW on 9755 kHz, 50 kW on 9620 kHz, 20 kW on other channels.

Zambia—The Zambia B/C Service General Service is scheduled weekdays at 0400-0445 and 1800-2105 on 2455 and 3275 kHz, at 0445-0630 and 1430-1800 on 3275 kHz and at 0630-1430 on 4911 kHz. The same schedule applies to Sundays except that opening is at 0500 and closing at 2010. The 2455-kHz outlet made a surprise appearance in East

Coast areas at 0405 with Eng. news and at 0413 with the weather; the dual 3346-kHz channel (not listed in the latest schedule—Ed.) was barely audible.

Clandestine—R. *Euzkadi* was noted varying in frequency between 15,030 and 15,080 kHz, with best reception from 2030 to 2205 s/off (it may run as late as 2305 at times); close-down includes an anthem and IS. The only Eng. heard seems to consist of ID's at 2030 and 2130. *The Voice of the Basque Underground*. —30—

DX PROVINCES AWARDS PRESENTED

To be eligible for one of the DX Provinces Awards designed for WPE Monitor Certificate holders, you must have verified stations (any frequency or service) in 6, 8, 10, or 12 Canadian provinces. (For these awards, the Yukon Territory and the Northwest Territories are considered as provinces.) The following Drivers have qualified for and received awards in the categories indicated.

TWELVE PROVINCES VERIFIED

Frank Diehl (WPE2GUJ), Buffalo, N. Y.

TEN PROVINCES VERIFIED

Ziba Knapp (WPE6EOG), South San Gabriel, Calif.
 Conrad Durocher (WPE1ASP), Framingham, Mass.
 Thomas Lachajczyk (WPE9HJO), Chicago, Ill.
 William Chapman (WPE1DRZ), Middletown, Conn.
 John Reasoner (WPE0CLU), Bowling Green, Ky.
 James Eudaily, Jr. (WPE4GLQ), Millers Creek, N. C.
 James Neff (WPE2RS), Springville, N. Y.
 Ron Kusmack (VE4PE4U), Winnipeg, Manitoba, Canada
 Jack Winther (WPE6BJD), Moraga, Calif.
 Edward Fellows (WPE7BLN), Seattle, Wash.
 Jack Lane (WPE9EVU), Lafayette, Ind.

EIGHT PROVINCES VERIFIED

Pete Sils (WPE0EAX), Cedar Falls, Iowa
 William Gardiner (WPE2DLX), Perry, Fla.
 Jan Stetson (WPE2NSQ), Albion, N. Y.
 John Schnaidt (WPE6CDU), Shafter, Calif.
 Paul Kilroy (WPE3FOB), Washington, D. C.
 Jerry McMahan (WPE0SS), Cedar Rapids, Iowa
 David Kaplan (WPE1FIJ), Hartford, Conn.
 Charles Dobbins, Jr. (WPE8BEV), Detroit, Mich.
 Peter Bartlett (WPE1FSX), Marshfield Hills, Mass.
 David Johnson (WPE0ELO), Denver, Colo.
 Robert Crowell (WPE4HKO), Fort Walton Beach, Fla.
 Le Roy Ackerman (WPE7BXS), Phoenix, Ariz.
 Kenneth Coyne (WPE2LSI), Long Beach, N. Y.
 Arthur Peterson (WPE6FMV), San Pablo, Calif.
 Tim Kerfoot (VE3PE1TH), Toronto, Ont., Canada
 William Rodgers (WPE0EX), Florissant, Mo.
 George Hemingway (WPE1DYC), Taftville, Conn.
 Edward Smith (WPE7AVQ), Corvallis, Oreg.
 James McFadden (WPE2OKV), Pleasantville, N. J.
 Jack Forbing (WPE9AMH), Fort Wayne, Ind.
 Roger Camire, Jr. (WPE1GK), Manchester, N. H.
 Stephen Schmidt (WPE2IXG), Webster, N. Y.
 Charles Matterer (WPE6DGA), San Leandro, Calif.
 Michael Fletcher (WPE4DPS), Marietta, Ga.
 Ernest Wesolowski (WPE0AHV), Omaha, Nebr.

SIX PROVINCES VERIFIED

Thomas Blossom (WPE9FHQ), Fort Wayne, Ind.
 Frank Halpin (WPE2GRC), Queens Village, N. Y.
 Daryl Salmon (VE7PE1BC), Burnaby, British Columbia, Canada
 Pat Laird (VE5PE5F), Swift Current, Saskatchewan, Canada
 Dwain Davis (WPE1GJO), Cranston, R. I.
 James Mason (VE3PE2FB), Kingston, Ont., Canada
 Mike Doherty (VE3PE2FJ), Willowdale, Ont., Canada

Tom Layde (WPE9HWS), Milwaukee, Wis.
 Walter Pratt (WPE1FHE), Shrewsbury, Mass.
 James Smedley (WPE3BBS), Sykesville, Md.
 Richard Lauhead (WPE0DTX), Elwood, Nebr.
 Lothar Koenig (WPE2NTB), Brooklyn, N. Y.
 Paul Petosky (WPE8ASF), Pickford, Mich.
 Victor Lipinski (WPE4HTV), Alexandria, Va.
 John Martorana (WPE3FSP), Bridgeville, Pa.
 Ray Salvo (WPE6DEM), Hayward, Calif.
 Clarence Hagerman (WPE2NRU), Delaware, N. J.
 John Creamer (WPE2OCT), Syracuse, N. Y.
 Jack Page, Jr. (WPE5DXH), Pontotoc, Miss.
 Bruce Reynolds (WPE0EKU), Warrensburg, Mo.
 Allan Jones (VE3PE2AM), Islington, Ont., Canada
 Lawrence Bennett (WPE2NEU), Forest Hills, N. Y.
 Tom Kelly (WPE2MRB), Norristown, Pa.
 Neil Hauser (WPE2LQQ), Lake Success, N. Y.
 H. Zimberg (VE4PE6Q), Winnipeg, Man., Canada
 Roger Burket (WPE3EKS), Altoona, Pa.
 Leo Baca (WPE5CLR), Bernard, Texas
 David Miller (WPE2MNS), Medina, N. Y.
 Aldridge Salisbury (WPE4HLD), Falls Church, Va.
 Bob Du Buisson (WPE1GGL), Longmeadow, Mass.
 Ronald Whiffen (WPE2NFX), Richmond Hill, N. Y.
 Michael Pihcik (WPE2JDF), Woodside, N. Y.
 Irwin Tatelman (WPE9HIF), Chicago, Ill.
 John Draut (WPE2JVI), Bronx, N. Y.
 Michael Hayden (WPE7CGZ), Winslow, Wash.
 Stuart Miller (WPE1GMT), Marblehead, Mass.
 Alvan Fisher (WPE1GHE), Newton, Mass.
 Elliott Straus (WPE2NOO), West Orange, N. J.
 Edward Bassett (WPE9EHF), Toledo, Ill.
 Harold Allen (VE2PE1JM), Arvida, Que., Canada
 Robert Chrysler (VE6PE6K), Edmonton, Alta., Canada
 James Myers (VE3PE2EJ), Val Caron, Ont., Canada
 John Zaharek (WPE1GUM), Torrington, Conn.
 Robin Martin (WPE2GEH), Glen Head, N. Y.
 Don Hollingsworth (VE6PE7B), Edmonton, Alta., Canada
 Lyle Lunsford (WPE3GGK), Baltimore, Md.
 Ralph Vatalaro, Jr. (WPE1GQP), Somerville, Mass.
 Mike Jeffrey (WPE7CLK), Wenatchee, Wash.
 Salvatore Trapasso (WPE1EQI), South Peabody, Mass.
 Paul Slater (WPE1FRT), Medford, Mass.
 Ron Hopkins (VE7PE7P), Trail, B. C., Canada
 Drew Kalman (WPE8ILL), Dearborn, Mich.
 William Via (WPE3FHB), Baltimore, Md.
 Robert Wilson (VE3PE2GA), Ottawa, Ont., Canada
 Donald Lee (WPE3EVB), Lebanon, Pa.
 Richard Cooper (WPE1GHI), Wayland, Mass.
 Robert Braunwart III (WPE7CJO), Moses Lake, Wash.
 Viktor Decyk (WPE1FCD), Colrain, Mass.
 Park Barton (WPE4INA), Troy, Ala.
 Robert Johnston (VE3PE1SX), Oshawa, Ont., Canada

ELECTRONICS MARKET PLACE

COMMERCIAL RATE: For firms or individuals offering commercial products or services. \$1.00 per word (including name and address). Minimum order \$10.00. Payment must accompany copy except when ads are placed by accredited advertising agencies. Frequency discount: 5% for 6 months; 10% for 12 months paid in advance.

READER RATE: For individuals with a personal item to buy or sell. 60c per word (including name and address). No Minimum! Payment must accompany copy.

GENERAL INFORMATION: First word in all ads set in bold caps at no extra charge. Additional words may be set in bold caps at 10¢ extra per word. All copy subject to publisher's approval. Closing Date: 1st of the 2nd preceding month (for example, March issue closes January 1st). Send order and remittance to: Hal Cymes, POPULAR ELECTRONICS, One Park Avenue, New York, New York 10016.

FOR SALE

FREE! Giant bargain catalog on transistors, diodes, rectifiers, SCR's, zeners, parts. Poly Paks, P.O. Box 942, Lynnfield, Mass.

MESHNA'S TRANSISTORIZED CONVERTER KIT \$5.00. Two models converts car radio to receive 30-50 mc or 100-200 mc (one mc tuning). Meshna, North Reading, Mass. 01864.

GOVERNMENT Surplus Receivers, Transmitters, Snooper-scopes, Radios, Parts, Picture Catalog 25¢. Meshna, Nahant, Mass. 09108.

"SPECIAL! WPE-SWL-CB-QSL cards, 3 colors, \$2.50 per 100—Free Samples, Garth, Jutland, New Jersey."

CANADIANS—GIANT Surplus Bargain Packed Catalogs. Electronics, Hi-Fi, Shortwave, Amateur, Citizens Radio. Rush \$1.00 (Refunded). ETCO, Dept. Z., Box 741, Montreal, CANADA.

WEBBER LAB'S Police—Fire Transistorized Converter kit 30-50mc. & 100-200mc. (1 mc. spread) \$5.00 each. 26-200mc. on broadcast band using any type radio, crystal controlled \$23.00 wired pp. tunable—crystal controlled \$11.00 kit. 72 Cottage Street, Lynn, Mass.

JAPAN & Hong Kong Electronics Directory. Products, components, supplies. 50 firms—just \$1.00. Ippano Kaisha Ltd., Box 6266, Spokane, Washington 99207.

CANADIANS, TRANSISTORS AND PARTS. Free catalogue contains reference data on 300 transistors. J. & J. Electronics, Dept. PE, Box 1437, Winnipeg, Manitoba.

TRANSISTORS—Miniature Electronic Parts. Send for free Catalog. Electronic Control Design Company, P. O. Box 1432K, Plainfield, N.J.

INVESTIGATORS, FREE BROCHURE, LATEST SUBMINIATURE ELECTRONIC SURVEILLANCE EQUIPMENT, ACE ELECTRONICS, 11500-L NW 7TH AVE., MIAMI, FLA. 33168.

TELEPHONE VOICE SWITCH: (LS-500). ACTUATES AUTOMATICALLY AND UNATTENDED ANY TAPE OR WIRE RECORDER. PICTORIAL INSTALLATION INSTRUCTIONS INCLUDED. \$23.75. POST PAID USA, WJS ELECTRONICS, 737 NORTH SEWARD, HOLLYWOOD, CALIF. 90038.

INVESTIGATORS: KEEP IN STEP WITH ADVANCEMENTS IN THE ART OF ELECTRONICS FOR THE PROFESSIONAL. SEND \$1.00 FOR EQUIPMENT BROCHURE. WJS ELECTRONICS, 737 NORTH SEWARD, HOLLYWOOD, CALIF. 90038.

WE SELL CONSTRUCTION PLANS. Telephone Equipment: \$40 Answering Machine, \$15 Bell System Type Speaker Phone, \$10 Legal Telephone Connector, Telephone Extension in your car, \$25 Automatic Dialer, Central Dial System, Phonevision. Television Equipment: \$50 Camera, \$30 3DTV Converter, \$35 All Electronic Color Converter, Video Recorder. Hobbyist: \$50 Ultrasonic Dishwasher, Transistorized Teletype and Morse Code Copier, \$75 Electron Microscope, Electronic Tranquilizer, Private Eye Tail Transmitter, Police Radar Detector plus Legal Jammer. Plans \$4.95 each. Telephone Engineering Course \$39.50. **SUPER HURRY CATALOG 25¢.** Don Britton Enterprises, 7906 Santa Monica Blvd., Hollywood, Calif. 90046.

BUG DETECTOR: WILL DETECT AND LOCATE SURREPTITIOUS TRANSMITTING DEVICES IN CONFERENCE ROOMS, HOME AND OFFICES, ETC. WRITE FOR DETAILS. WJS ELECTRONICS, 737 NORTH SEWARD, HOLLYWOOD, CALIF. 90038.

CB-WPE-QSL CARDS. Same High Quality, Beautiful, Glossy multi-color cards. New **LOW PRICES. 26 SAMPLES, 25¢.** Dick, W8VXK, 19QA0625, Gladwin, Mich. 48624.

DIAGRAMS—SENT AIRMAIL—TELEVISION \$3.00. RADIO 1919-1965 \$2.00. GIVE MODEL DIAGRAMS, BOX 55, WILLIAMSPORT, PA. 17704.

ELECTRONIC "CRACKAJACKS," relays, transistors, photocells, etc. Guaranteed prizes. \$1.00 ppd. **DART ELECTRONICS, Box 214, Jericho, N.Y.**

R.F. CONVERTERS. World's largest selection. Also CCTV cameras, transmitters, etc. Lowest factory prices. Catalog 10¢. Vanguard 196-23 Jamaica Ave., Hollis, N.Y. 11423.

INVESTIGATORS—DETECTIVES—INDUSTRIAL SECURITY OFFICERS: New 1966 line of Electronic Surveillance Devices. Incorporating most advanced subminiature design. Greater range; lower battery drain; unique sophisticated circuitry; extremely durable. **HIGH QUALITY PROFESSIONAL EQUIPMENT AT ROCK BOTTOM PRICES.** Fool-proof wireless units are extremely **SIMPLE TO USE!** You **DO NOT** have to be an engineer to get **PROFESSIONAL** results with **THIS** equipment. **TROL 1966** models ready **NOW!** Take advantage of Special Introductory Offer. Don't delay! For **FREE** details write **TROL ELECTRONICS-PE, 31 West 8th Street, New York, N.Y.**

RECTIFIERS, transistors, other components. Catalog free. Electronic Components Co., Box 2902C, Baton Rouge, La.

TRANSISTORIZED Products Importers catalog. \$1.00. Intercontinental, CPO 1717, Tokyo, Japan.

RADIO — T.V. Tubes—33¢ each. Send for free catalog. Cornell, 4213 University, San Diego, Calif. 92105.

ORIENTAL Electronics Directory, 200 Japanese—Hong Kong Manufacturing Exporters. All products. \$2. Dee, Box 211, Beverly Hills, Calif. 90213.

CIRCUIT Boards, Parts for "Poptronics" projects. Free catalog. **DEMCO, Box 16297, San Antonio, Texas 78216.**

GIANT TESLA COIL—FORTY-INCH SPARKS! Complete plans \$5.00. Details, color photo 50¢. Huntington Electronics, Inc., Dept. A, Box 9 Huntington Station, Shelton, Conn. 06484.

SOLID STATE CONVERTERS. 50-54 mc input, 14-18 mc output. Crystal controlled, 2.5 db noise figure. Wired and tested, \$25 ppd. **SYNTELEX, 39 Lucille, Dumont, N.J. 07628.**

WELL EXPERIMENTERS! Am retiring—have 50 year accumulation, give me a hand. Send stamped envelope for list. **ELCO, Box 35, Donora, Pa. 15033.**

SEE YOURSELF ON TV! Closed-circuit TV CAMERA KITS for experimenters, industry, schools. Wide selection of tube and transistor models. \$18.95 up. **EASY-TO-FOLLOW PLANS** included **FREE** with each kit or available separately (\$3 to \$5)—refundable with later order. **CHECK OUR UNBELIEVABLE PRICES.** Informative catalog 10¢. **ATV RESEARCH, Box 396P, So. Sioux City, Neb. 68776.**

HOBBYISTS, EXPERIMENTERS, AMATEUR SCIENTISTS, STUDENTS . . . CONSTRUCTION PLANS—All complete including drawings, schematics, parts lists, prices, parts sources . . . **LASER**—Build your own coherent-light optical laser. Operates in the pulsed mode, in the visible light range—\$6.00 . . . **DIODE LASER**—Invisible light (infrared) can be continuously modulated—\$3.00 . . . **REVERBERATOR (ECHO) UNIT**—Build your own. Use with your automobile radio, home radio or hifi, electric guitar, etc.—\$3.00 . . . **RADAR**—Build your own ultrasonic doppler radar. Detect motion of people, automobiles, even falling rain drops. Transistorized, uses standard small 9-volt battery—\$4.00 . . . **TV CAMERA**—Build your own. The real thing—no rotating disc. Uses 5 tubes plus videon tube. Output: 72 frames or receive on any TV set channel 2-6. Excellent circuit—good picture—\$6.00 . . . **STROBOSCOPE**—Flash rate variable from about 10 to 1,000 flashes per second. Stop effect will allow you to view rotating or oscillating objects while in motion—\$3.00 . . . **STEREO AMPLIFIER**—Uses two 6T9 compactrons—for stereo phono, tuner, etc.—\$3.00 . . . **TWO-WAY TALK OVER FLASHLIGHT BEAMS**—Hand-held microphone, loudspeaker volume. Use in daylight or darkness—\$3.00 . . . **VIBRATO UNIT**—Use with electric guitar and other musical instrument amplifiers. Uses two transistors and two 9V batteries—\$3.00 . . . **VOLUME COMPRESSOR/EXPANDER**—Use with your HiFi—\$4.00 . . . **LONG-RANGE "SOUND TELESCOPE"**—This amazing device can enable you to hear conversations, birds and animals, other sounds hundreds of feet away. Very directional. Transistorized. Uses 9V battery—\$3.00 . . . **CIGAR BOX ELECTRIC ORGAN**—Portable, self-contained battery. Eight notes, one octave. Two transistors, 9V battery—\$3.00 . . . **ANALOG COMPUTER**—Multiply, divide, add, subtract, square and find square roots. Uses two flashlight batteries—\$3.00 . . . **BINARY READOUT**—Program in decimal numbers and readout binary—\$3.00 . . . **SOLID STATE BINARY COUNTER (COMPUTER-ADDER)**—Uses transistor flip-flop stages. Lightbulb readout. Punch in pulses, read binary count. Five stage. Includes easy to understand discussion of decimal to binary arithmetic conversion. Excellent start in digital computer technology—\$6.00 . . . **TECHNICAL WRITERS GROUP, Box 5501, STATE COLLEGE STATION, RALEIGH, N.C. 27607.**

ROCKETS: Ideal for miniature transmitter tests. New illustrated catalog, 25¢. Single and multistage kits, cones, engines, launchers, trackers, rocket aerial cameras, technical information. Fast service. Estes Industries, Penrose 18, Colorado.

ELECTRONIC Ignition Kits, Components, Free Diagrams. Anderson Engineering, Epsum, New Hampshire 03239. **"GREAT BUYS"** Catalog 10¢ Multimeter 20,000 Ω/v \$9.95. 1001 Bargains. Fertik's, 5249 "D" St., Phila., Pa. 19120.

COMPONENTS? Kits? Hardware? For catalogue write Trans-Vu-Pacs, Box 267, Chelsea, Mass. 02150.

110VAC 60cy from car generator. Powers lights, refrigerator, transmitter, receiver, etc. Simple, easy to convert. Plans, \$2.00. Tedco, P.O. Box 12098, Houston, Texas 77017.

LOWEST Prices Electronic Parts. Confidential Catalog Free. KNAPP, 3174 8th Ave. S.W., Largo, Fla.

SURVEILLANCE EQUIPMENT—NEW HIGH PERFORMANCE SUBMINIATURE MODELS. ELECTRONIC COUNTERMEASURE DEVICES TO PROTECT PRIVACY. FREE DATA: SECURITY ELECTRONICS-PE, 15 EAST 43RD STREET, NEW YORK, N.Y. 10017.

SAFEGUARD your privacy. Learn the facts, procedures and techniques in the art of de-bugging your home, office, boardroom or auto. \$7.95. Tron-X, Post Office Box 38155, Hollywood, Calif. 90038.

DIAGRAMS for repairing Radios \$1.00. Television \$2.50. Give make model. Diagram Service, Box 1151 PE, Manchester, Connecticut 06042.

DETECTIVES! Free Brochures! Electronic Surveillance Devices. SILMAR ELECTRONICS, 3476 N.W. 7th Street. Miami, Fla. 33125.

FREE ELECTRONICS (new and surplus) parts catalog. We repair multimeters. Bigelow Electronics, Bluffton, Ohio 45817.

WHOLESALE: microphones 89¢, speakers 49¢, amplifiers \$4.39. Hundreds of items. Catalog 25¢. Royal, 8632 La Mesa Blvd., La Mesa, Calif.

SAFEGUARD PRIVACY! New instrument detects electronic 'bugs,' wire-tapping and snooping devices. Free information. Dee Equipment, Box 7263-E7, Houston 8, Texas.

CLASSIFIED ADVERTISING ORDER FORM

Please refer to heading on first page of this section for complete data concerning terms, frequency discounts, closing dates, etc.

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

_____ Words { @ 60¢ (Reader Rate) } = \$ _____
 { @ \$1.00 (Commercial Rate) }

Insert _____ time(s) Total Enclosed \$ _____

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

Signature _____

WORD COUNT: Include name and address. Name of city (Des Moines) or of state (New York) counts as one word each. Zone or Zip Code numbers not counted. (Publisher reserves right to omit Zip Code if space does not permit.) Count each abbreviation, initial, single figure or group of figures or letters as a word. Symbols such as 35mm, COD, PO, AC, etc., count as one word. Hyphenated words count as two words. PE-1066

SURPRISE electronics equipment \$5.00, \$10.00 package. Tang, Box 162, Framingham Center, Mass. 01701.

CB-QSL CARDS, New Designs, Record Books, Blabbermouth Awards, Gag Signs, Warning Decals, Novelties. Free Brochure. **WOODY**, 8474 Watson, St. Louis, Mo. 63119.

CRYSTALS... largest selection in United States at lowest prices. 48 hr. delivery. Thousands of frequencies in stock. Types include HC6/U, HC18/U, FT-241, FT-243, FT-171, etc. Send 10¢ for catalog with oscillator circuits. Re-fused on first order. Jan Crystals, 2400F Crystal Dr., Fort Myers, Fla. 33901.

DIAGRAMS, service information, Radio \$1.00, Television \$2.00. **BEITMAN**, 1760 Balsam, Highland Park, Ill. 60035.

TELEPHONE RECORDER-ACTUATOR (TWL-007) SOLID STATE MODULE AUTOMATICALLY TURNS TAPE RECORDER OR AMPLIFIER ON WHEN TELEPHONE IN USE. CONNECTED ANYWHERE ON LINE. SIMPLE INSTALLATION INSTRUCTIONS INCLUDED. PREPAID \$18.65. TWILIGHT ELECTRONICS, BOX 11595, ST. LOUIS, MO. 63105.

10 DISTANCE Crystal set plans—25¢; 20 different—50¢. Includes Transistor experiments, catalog. Laboratories, 12041-L Sheridan, Garden Grove, Calif. 92640.

CHANGE B/W TV to novel color, \$2.98. State size screen. Delecto Electronics, 4725 45th NE, Seattle, Wash. 98105.

HIFI speaker system. Small, walnut. Magnificent. \$29.95. **TANG**, Box 162A, Framingham Ctr., Mass. 01701.

COMPUTER MODULES FOR HOME EXPERIMENTERS. M-C MODULES, 43-17 54th STREET, WOODSIDE, NEW YORK 11377.

NEW supersensitive transistor instrument detects buried gold, silver, coins. Kits, assembled models. \$19.95 up. Free catalog. **Relco-A33**, Box 10563, Houston 18, Texas.

CONVERT any television to sensitive, big-screen oscilloscope. Only minor changes required. No electronic experience necessary. Illustrated plans, \$2.00. **Relco-A33**, Box 10563, Houston 18, Texas.

INVESTIGATORS, ELECTRONIC SURVEILLANCE DEVICES. SEND \$1.00 FOR BROCHURE. BUGTRONICS, POST OFFICE BOX 2056, MONTCLAIR, CALIFORNIA 91763.

DIAGRAMS with voltages, layouts, troubleshooting information. **RADIO** \$1.00. **TELEVISION**, etc. \$2.50. Add 50¢ for **AIR MAIL**. Send make, model: Healy Enterprises, 2436 Delafield, Houston, Texas 77023.

McGEE RADIO COMPANY. Big 1966-1967 catalog sent free. America's best values. HiFi Amplifiers—speakers—electronic parts. Send name, address and zip code number to McGee Radio Company, 1901 McGee Street, Dept. EG, Kansas City, Missouri 64108.

ELECTRONIC SURVEILLANCE DEVICES, detectives, hobbyists. **SNOOPER FM** wireless microphone \$44.50. **TAIL-ABEEP**, bumper beeper \$99.50. **TELEGAB** phone transmitter \$49.50. Other guaranteed high quality items in our catalog. **Fudalla Associates**, 1134 Avenue Road, Toronto 12, Ontario, Canada.

EXPERIMENTERS Transistorized Projects Catalog 10¢. Hazelton Scientific, Box 163, Hazel Park, Mich. 48030.

SHORTWAVE LISTENING

SWL GUIDE, English programs listed by the hour. **REVISED EDITION**, \$2.00. **SWL Guide**, 218 Gifford, Syracuse 2, N. Y.

HAM EQUIPMENT

CBers, HAMS, SWL'S! 3-30 MC Preselector kit, \$18.98. **CB booster Kits**. Novice transceiver kit, \$29.95. Free catalog. **HOLSTROM**, Box 8640-E, Sacramento, Calif.

BARGAINS! Transmitters, Receivers offered, wanted in "Ham Trader". Interesting copy 10¢. Brand, Sycamore, Ill.

HIGH FIDELITY

"**LOW**, Low quotes: all components and recorders. HiFi, Roslyn 9, Penna."

HI-FI Components, Tape Recorders, at guaranteed "We Will Not Be Undersold" prices. 15-day money-back guarantee. Two-year warranty. No Catalog. Quotations Free. **Hi-Fidelity Center**, 239 (P) East 149th Street, New York 10451.

FREE! Send for money saving stereo catalog #P10E and lowest quotations on your individual component, tape recorder, or system requirements. **Electronic Values, Inc.**, 200 W. 20th St., New York, N.Y. 10011.

WANTED

CASH Paid! Unused tubes, electronic equipment. **Barry**, 512 Broadway, N.Y.C. 10012.

QUICKSILVER, Platinum, Silver, Gold. Ores Analyzed. Free Circular. **Mercury Terminal**, Norwood, Mass.


PLANS AND KITS

BUILD A CODETYPER. Transistorized electronic computer-typewriter for Morse teaching or keying your rig with fb fist. For schematic, parts list and technical dope send \$2 to **Computronics Engineering**, Box 6606 Metropolitan Station, Los Angeles 90058.

BUILD your own Custom professional stereo tape transport. Up to 8 tracks 3" to 14" reels easy, fun, rewarding, ideal school project. Literature 25¢. Detailed plans \$7.50. **Curtronics**, 4006 Thornton, Annandale, Virginia 22003.

ALLWAVE RADIO KIT. Tube, transistor included \$5.00. Headset \$2.50. **Ekeradio**, Box 131, Temple City, Calif.

BEGINNER KITS, Crystal Radio \$1.95, Solar Powered Radio \$4.95, Wireless Transmitter \$3.95. **Lectronix**, Box 42 (PE), Madison Heights, Michigan 48071.



SPECIAL INTRODUCTORY OFFER

15 EPOXY RECTIFIERS WITH EVERY \$5.00 PURCHASE. MANY OVER 600 PIV. NO SHORTS OR OPENS. FET'S "N" CHANNEL TYPE SIMILAR TO C-610 USED AS AMP, SWITCH, CHOPPER—VERY HIGH INPUT Z \$1.25 EACH

SILICON POWER RECTIFIERS			5A INSUL BASE		TOP HAT EPOXIS 750 MA		
PRV	3A	20A	PRV	50	PRV	50	
.30	.05	.20	.50	.10	100	.05	
100	.10	.40	100	.20	200	.07	
200	.20	.60	200	.40	400	.09	
400	.25	.80	400	.60	600	.12	
600	.35	1.20	600	1.00	800	.20	
800	.45	1.50	800	1.25	1000	.25	
1000	.65				1200	.50	
					1400	.65	
					1600	.85	
					1800	1.00	
					2000	1.15	
						2000	1.35

A) Sim to 2N1640 Bidirectional Transistors, collector and emitter are interchangeable. \$4.00 each

B) Sim. to 2N728. A high frequency TO-18 (NPN) unit extending to the UHF range. \$5/\$1.00

C) Sim. to 2N2885 (npn) and TMT 8035 (pnp) microtransistors 75 mW power at high fre. Both units. \$1.00

D) Sim. to 2N1648 non high voltage 20 watt silicon unit, used in power output stages & power transistor drivers. 2/\$1.00

E) Glass diodes color coded \$1 20/\$1.00 6E 30/\$1.00

SEND FOR FREE CATALOG (to be available soon)

CIRCLE NO. 45 ON READER SERVICE PAGE

TUBES

BEFORE You Buy Receiving Tubes, Transistors, Diodes, Electronic Components and Accessories . . . send for Giant Free Zalytron Current Catalog, featuring Standard Brand Tubes; RCA, GE, etc.—all Brand new Premium Quality Individually Boxed, One Year Guarantee—all at Biggest Discounts in America! We serve professional servicemen, hobbyists, experimenters, engineers, technicians. Why Pay More? Zalytron Tube Corp., 469-E Jericho Turnpike, Mineola, N. Y. 11502.

TUBE Headquarters of World! Send 10¢ for Catalog (tubes, electronic equipment) Barry, 512 Broadway, N.Y.C. 10012.

TUBES "Oldies", latest. Lists free. Steinmetz, 7519 Maplewood, Hammond, Indiana 46324.

FREE Catalog. Electronic parts, tubes. Wholesale. Thousands of items. Unbeatable prices. Arcturus Electronics ZD, 502-22 St., Union City, N.J. 07087.

RADIO & T.V. Tubes—33¢ each. Send for free list. Cornell, 4213 University, San Diego, Calif. 92105.

TUBES, FREE LIST. Gamma, 140 West 26th, Hamilton, Ont.

SEND FOR wholesale radio tube catalog. Lowest prices, many more bargain items. CeCo, 120 West 18th Street, New York, N. Y. 10011.

EQUIPMENT

FREE electronics catalog. Tremendous bargains. Send postcard. Electrolabs, Department C-670D, Hewlett, New York 11557.

MOVIE FILMS

ORDER NOW—'66 INDY 500; 8mm COLOR . . . Most Incredible in 50 years of Speedway History, \$12.95 ppd (Super 8mm \$13.95). Other **INSTRUCTIONAL/COLOR ACTION SPORTS FILMS**—8/16mm. Catalog Available. Write: **SPORTLITE FILMS-PE**, 20 North Wacker Drive, Chicago, Illinois 60606.

TAPE AND RECORDERS

BEFORE Renting Stereo Tapes try us. Postpaid both ways—no deposit—immediate delivery. Quality—Dependability—Service—Satisfaction—prevail here. If you've been dissatisfied in the past, your initial order will prove this is no idle boast. Free Catalog. Gold Coast Tape Library, Box 2262, Palm Village Station, Hialeah, Fla. 33012.

RENT 4-TRACK STEREO TAPES—Dependable service our keynote—**ALL MAJOR LABELS—FREE CATALOG** (48 States)—**TRIMOR** Company, P.O. Box 748, Flushing, N.Y. 11352.

STEREO TAPES. Save up to 60% (no membership fees, postpaid anywhere U.S.A.). Free 60 page catalog. We discount batteries, recorders, tape accessories. Beware of slogans "not undersold." as the discount information you supply our competitor is usually reported to the factory. **SAXITONE**, 1776 Columbia Road, Washington, D.C.

AUTOMATIC telephone connection for Concord and other transistORIZED recorders. **SURVEILLANCE** and Privacy Protection Devices. Free Data: Security Electronics-PER, 15 East 43rd Street, New York, N.Y. 10017.

TAPE transport. NAB recording studio quality. Build yourself for amazingly low cost. Detailed plans \$5.00. Free particulars. Pepke Laboratories, 309-B West 19 Street, New York, N.Y. 10011.

TAPE-MATES now offers **ALL TAPES—ALL LABELS** at **TRE-MENDOUS SAVINGS** plus **FREE** Tape-Mates membership. For **FREE** brochure write **TAPE-MATES**, 5280-PE W. Pico Blvd., Los Angeles 90019.

TAPES, TAPE RECORDERS—sold, exchanged. Free catalog. Tower, Lafayette Hill, Pa. 19444.

TAPE RECORDER SALE. Brand new, latest models, \$10.00 above cost. Arkay Sales, 1028-C Commonwealth Ave., Boston, Mass. 02215.

RENT Stereo Tapes—over 2,500 different—all major labels—free brochure. Stereo—Parti, 1616-PE Terrace Way, Santa Rosa, California.

TAPE RECORDERS, Hi-Fi, components, Sleep Learning Equipment, tapes. Unusual Values Free Catalog. Dressner, 1523PE, Jericho Turnpike, New Hyde Park 11, N. Y.

REPAIRS AND SERVICES

TV Tuners rebuilt and aligned per manufacturers specification. Only \$9.50. Any make UHF or VHF. We ship COD. Ninety day written guarantee. Ship complete with tubes or write for free mailing kit and dealer brochure. JW Electronics, Box 51C, Bloomington, Indiana.

INSTRUCTION

LEARN ELECTRONIC ORGAN SERVICING at home all makes including transistors. Experimental kit—trouble-shooting. Accredited NHSC. Free Booklet. **NILES BRYANT SCHOOL**, 3631 Stockton, Dept. A, Sacramento 20, Calif.

LEARN While Asleep, hypnotize with your recorder, phonograph. Astonishing details, sensational catalog free! Sleep-Learning Association, Box 24-ZD, Olympia, Wash.

FCC License in 6 weeks. First Class Radio telephone. Results Guaranteed. Elkins Radio School, 2603B Inwood, Dallas, Texas.

REI First Class Radio Telephone License in (5) weeks Guaranteed. Tuition \$295.00. Job placement free. Radio Engineering Institute, 1336 Main Street, Sarasota, Fla.

BEGINNERS code. 5wpm at 33 $\frac{1}{3}$. Guided sending. Three 12" records, \$6.85. Page Electronics Institute, 1158 W. 54 St., Los Angeles 90037.

F.C.C. LICENSE (first class) in seven weeks. Resident classes or correspondence. Grantham, 1505 N. Western, Hollywood, California 90027.

HIGHLY—effective home study review for FCC commercial phone exams. Free literature! Cook's School of Electronics, P.O. Box 10634, Jackson, Miss. 39209.

BOOKLETS: Chinese writing manuals for beginners. Kern, 9932 Mason Ave., Chatsworth, Calif 91311.

"HOW TO MAKE MONEY WITH SIMPLE CARTOONS"—Everyone who likes to draw should have this book; **FREE.** Send name, zip code. Cartoonists' Exchange, 21310 Pleasant Hill, Ohio 45359.

BUILD YOUR OWN TEST EQUIPMENT AND A STEREO AM-FM RADIO. Practical Home Study Courses in Electronics in Theory, Practice and Servicing with Complete kits and tools included in price. Write for free booklet with no obligation to: **INESCO, INTERCONTINENTAL ELECTRONICS SCHOOL, DEPT. 16A**, 9100 St. Lawrence Blvd., Montreal 11, Quebec, Canada.

FCC LICENSE THROUGH TAPE RECORDED INSTRUCTION. Bob Johnson Audio-Visual Training, 1060D Duncan, Manhattan Beach, Calif. 90266.

DRAFTING (Electronic, Mechanical, Architectural, Art). Home Courses \$25.00. Send \$2.00 first lesson. Prior, Inc. 23-09 169 Street, Whitestone 57, N.Y.

IF YOU CAN READ "YOU CAN LEARN ELECTRONICS ON YOUR OWN." Simplest TV home study course. No previous knowledge needed. Money back guarantee. Write for descriptive literature. N. Siegel, 328 Surrey Drive, New Rochelle, New York 10804.

COINS

BARGAIN LISTS—coins and supplies, 25¢. Bill Comby, Conover, N.C. 28613.

INVENTIONS WANTED

INVENTIONS wanted. Patented; unpatented. Global Marketing Service, 2420-P 77th. Oakland 5, Calif.

INVENTIONS—IDEAS developed: **CASH/ROYALTY SALES.** Member: United States Chamber of Commerce. Raymond Lee. 130-G West 42nd, New York City 10036.

INVENTORS! Sell your invention for cash or royalties! Our client manufacturers eagerly seek new items. Patented. Unpatented. Financial assistance if needed. 25 years proven performance. For free information, write Dept. 20, Gilbert Adams, Invention Broker, 80 Wall St., New York 5, N.Y.

INVENTORS! Don't sell your invention, patented or unpatented, until you receive our offer. Eagle Development Company, Dept. P, 79 Wall Street, N.Y. 5, N.Y.

PATENT Searches including Maximum speed. full airmail report and closest patent copies, \$6.00. Quality searches expertly administered. Complete secrecy guaranteed. Free Invention Protection forms and "Patent Information." Write Dept. 9, Washington Patent Office Search Bureau, 711 14th Street, N.W., Washington 5, D.C.

INVENTORS. We will develop, help sell your idea or invention, patented or unpatented. Our national manufacturer clients are urgently seeking new items for outright cash sale or royalties. Financial assistance available. 10 years proven performance. For free information, write Dept. 41, Wall Street Invention Brokerage, 79 Wall Street, New York 5, N.Y.

INVENTORS! Outright cash sale or royalties for your inventions. Patented. Unpatented. Active demand from our client manufacturers. Financial assistance available. Write Dept. 35, United States Invention Brokerage, 78 Wall Street, New York 5, N.Y.

INVENTIONS WANTED; Patented, unpatented. Extensive manufacturers' lists. Free details. Pioneer Invention Service, Dept. 79; 150 Broadway, New York, N.Y. 10038.

GOVERNMENT SURPLUS

"GOVERNMENT SELLS".—Surplus Electronics; Oscilloscopes; Transceivers; Test Equipment; Radar; Walkie-Talkies; Boats; Jeeps; Aircraft; Misc.—Send For—"U.S. Depot Directory-Procedure"—\$1.00—Service, Box 425 (ZE), Nanuet, N.Y.

GOVERNMENT Surplus. Complete Sales Directory \$1.00. Surplus Publications, Box 45781E, Los Angeles 45, Calif.

JEEPS Typically From \$53.90 . . . Trucks From \$78.40 . . . Boats, Typewriters, Airplanes, Electronics Equipment, Photographic Equipment, used. 100,000 Bargains Direct From Government. Complete Sales Directory and Surplus Catalog \$1.00 (Deductible First \$10.00 Order). Surplus Service, Box 820-J, Holland, Mich. 49424.

BOOKS

FREE Book. Prophet Elijah Coming Before Christ. Wonderful Bible Evidence. PE Megiddo Mission, Rochester, New York 14619.

FREE Catalog Aviation/Electronics/Space books. Aero Publishers, 329PE Aviation Road, Fallbrook, Calif. 92028.

AUTHORS' SERVICES

AUTHORS! Learn how to have your book published, promoted, distributed. **FREE** booklet "ZD." Vantage, 120 West 31 St., New York 1.

WANTED WRITERS! Short stories, articles, books, plays, poetry. Will help place, sell your work. Write today, free particulars! Literary Agent Mead, Dept. C-45, 915 Broadway, New York 10, N.Y.

SONGWRITERS WANTED. Send songs for recording—royalty contract. Tin Pan Alley, 1650-H Broadway, New York 10019.

DON'T BUY TUBES!!

RADIO or T.V.-XMITTING

or **SPECIAL-PURPOSE TYPES**
UNTIL YOU GET OUR PRICE LIST
GUARANTEED TO BE THE
LOWEST PRICES IN THE U.S.A.
OVER 5000 TYPES—ALL 100 %
GUARANTEED BRAND NEW

"WE'RE NEVER UNDERSOLD"

SEND POST CARD FOR T.V. OR
SPECIAL PURPOSE PRICE LIST

ESTABLISHED 1920

UNITED RADIO CO.

56 FERRY ST., P.O. BOX 1000
NEWARK, N.J. 07101

CIRCLE NO. 51 ON READER SERVICE PAGE

MUSIC

POEMS wanted for new songs. Nashville Music Institute, Box 532-E, Nashville, Tennessee.

POEMS wanted for songs. Send poems. Crown Music 49-EL West 32nd, New York 1.

SONGS, POEMS WANTED! For publishing, recording at our expense! Ted Rosen, 17-PE Longwood Road, Quincy, Mass.

MUSICAL INSTRUMENTS

ACCORDIONS, GUITARS, BAND INSTRUMENTS! Save to 50%. Terms. Trades. Free trial. Free catalog. Mention instrument. Music Mart, 5535-PE, Belmont, Chicago 60641.

REAL ESTATE

FREE Fall-Holidays CATALOG! Big 180 pages! Selected Best thruout the U.S. Thousands of properties described pictured—Land, Farms, Homes, Businesses—Waterfront, Recreation, Retirement. 66 Years' service, 490 Offices 36 states Coast to Coast. Mailed **FREE** from the World's Largest! **STROUT REALTY**, 50-ZD, East 42nd St., N.Y., N.Y. 10017.

FREE!!! 168-page **FALL-WINTER** catalog! Over 2,100 **PICTURES!** Farms, Ranches, Homes, Businesses, Vacation and Retirement properties in 29 states coast to coast! **UNITED FARM AGENCY**, 612-EP West 47th St. Kansas City, Mo. 64112.

CANADIAN VACATION LANDS: Full price \$385.00. 40 acres, \$10 month. Suitable cottage sites, hunting, fishing, investment. Free information. Land Corporation, 3768-P, Bathurst, Downsview, Ontario, Canada.

HELP WANTED

CHRISTMAS CARDS—Business and Personal. Customer's name imprinted. Earn unusually high commissions from this medium—and high-priced line. Free Sample Album. Process Corp. (our 45th Year). 3470D S. 54th Ave., Chicago, Ill. 60650.

RUBBER STAMPS

RUBBER ADDRESS STAMP \$1.00. Signature \$2.88. Free catalog. Jackson Products, 1433 Winnemac, Chicago, Ill. 60640.

PHOTOGRAPHY—FILM, EQUIPMENT, SERVICES

MEDICAL Film—Adults Only—"Childbirth"—1 reel 8mm \$7.50—16mm \$14.95. International-E, Greenvale, L.I., New York.

SCIENCE Bargains—Request Free Giant Catalog "CJ"—148 pages—Astronomical Telescopes, Microscopes, Lenses, Binoculars, Kits, Parts. War surplus bargains. Edmund Scientific Co., Barrington, New Jersey.

EDUCATIONAL OPPORTUNITIES

LEARN While Asleep. Remarkable, Scientific, 92% Effective. Details Free. ASR Foundation, Box 7021, Dept. e.g., Lexington, Kentucky.

PROFESSIONAL Engineering, Electronics. Free Prospectus. CIST, Suite 695, 263 Adelaide Street, West, Toronto, Canada.

DO-IT-YOURSELF

SAVE! Build Transistorized Treasure Finder. Details Free. Del Research, Box 436A, Centerville, Georgia 31093.

PERSONALS

INVESTIGATORS, FREE BROCHURE, LATEST SUBMINIATURE ELECTRONIC SURVEILLANCE EQUIPMENT. ACE ELECTRONICS, 11500-K NW 7th AVE., MIAMI, FLA. 33168.

BILL PROBLEMS? Poor credit no trouble. Not a loan company. Send for free application. Automatic Acceptance, 307PE, Pocasset Ave., Providence, R.I.

BUSINESS OPPORTUNITIES

INVESTIGATE Accidents—Earn \$750 to \$1,400 monthly. Men urgently needed. Car furnished. Business expenses paid. No selling. No college education necessary. Pick own job location. Investigate full time. Or earn \$6.44 hour spare time. Write for Free literature. No obligation. Universal, CZ-10 6801 Hillcrest, Dallas, Texas 75205.

VENDING Machines—No Selling. Operate a route of coin machines and earn amazing profits. 32-page catalog free. Parkway Machine Corporation, 715PE Ensor Street, Baltimore 2, Md.

ELECTROPLATING Equipment and supplies. All types for home workshops and industrial. Send \$1.00 (refundable) for equipment guide formulas, operating data, catalog. HBS Equipment Division 90, 3543 East 16th, Los Angeles, California. 90023.

I MADE \$40,000.00 Year by Mailorder! Helped others make money! Start with \$10.00—Free Proof. Torrey, Box 63566-N, Oklahoma City, Oklahoma 73106.

FREE Book "990 Successful, little-known Businesses." Work home. Plymouth-945M, Brooklyn, N.Y. 11218.

PIANO Tuning learned quickly at home. Tremendous field! Musical knowledge unnecessary. Information free. Empire School of Piano Tuning. Dept. PE, Box 327, Shendoah Station, Miami, Florida 33145. (Founded 1935.)

CITIZENS BAND Radio Dealerships Available. Sell Full or Part Time. Knox Electronics, Dept. 274, Galesburg, Ill. 61401.

IT'S FUN to sell by Mailorder! Free catalogue. Methods, 1406-FD, Lafayette Hill, Pa. 19444.

FREE \$125 MACHINE HELPS EARN AS YOU learn locksmithing! Professional's key machine sent you as part of course. Earn 90% on keys for cars, homes and offices while learning this needed, high-pay craft. All tools and supplies sent you with working lessons. Write for **FREE BOOK**—no obligation. **BELSAW INSTITUTE**, 2179 Field Bldg., Kansas City, Mo. 64111.

RAISE RABBITS for us on \$500 month plan. Free details. White's Rabbitry, Mt. Vernon 52, Ohio.

EARN \$240.00 a Month at home, spare time, doing only two \$5.00 Invisible Mending jobs a day. Big money paid for service that makes cuts, tears disappear from fabrics. Steady demand. Details free. Fabricon, 1572 Howard, Chicago 26, Ill.

FREE CATALOGS. Repair air conditioning, refrigeration. Tools, supplies, full instructions. Doolco, 2016 Canton, Dallas, Texas 75201.

EMPLOYMENT INFORMATION

CAPE KENNEDY area and overseas. Sample resumes. Application forms. Information \$2.00. Interocean, Dept. E10, Box 1883, Cocoa, Florida 32922.

CIVIL Service jobs. Free details. Alena, 1513 64th Street, Brooklyn, New York 11219.

EMPLOYMENT Resumes. Get a better job & earn more! Send only \$2.00 for expert, complete Resume Writing Instructions. J. Ross, 80-34 Kent St., Jamaica 32, N.Y., Dept. PE.

FOREIGN and **USA** job opportunities available now. Construction, all trades. Earnings to \$2,000.00 monthly. Paid overtime, travel, bonuses. Write: Universal Employment, Woodbridge, Connecticut 06525.

STAMPS

FREE! 110 **BRITISH** Empire Stamps (worth over \$2.50 at standard catalog prices) when you send only 10¢ for mailing costs! Get this big, valuable collection—from Antarctica, to Zambia! Spectacular issues picturing Conquest of Ice Continent, Papuan Cannibal, Flying Dragon of Wales; plus many others from Tanganyika, Sharjah, Dubai, South Georgia, Christmas Island, etc. A Sensational offer to introduce you to World's Most Rewarding Hobby. 110 genuine, all-different stamps plus Special **FREE Bonus**—a Complete Set of England's 42 Kings and Queens. Also, selections of attractive and unusual stamps from our Stamps-on-Approval Service for Free Examination. You may return selections without buying and can cancel service any time. Plus **FREE** "How to Recognize Rare Stamps" booklet, and Big Illustrated Collectors' Catalog! Send 10¢ to: Kenmore, Milford QR-58, New Hamp. 03055.

EMPLOYMENT OPPORTUNITIES

ELECTRONIC INSTRUCTOR—For advanced, high level technical program must have E. E. or related degree plus work experience in field of electronics, teaching background desirable but not absolutely essential. Forward resume. L. K. Jonas, Texas A&M University, Box 236 F. E., College Station, Texas.



PERMANENT PROTECTION!

POPULAR ELECTRONICS

Deluxe Magazine Files that hold a full year's copies!

Designed to keep your periodicals orderly and easy to refer to. These durable files guard against soiling, tearing, wear or misplacement of issues. They look, feel like leather and are washable! 23kt. gold lettering and exquisite 2-color binding make them highly-decorative additions to your bookshelves.

Shipped POSTPAID! FULLY GUARANTEED!
Only \$3.50 each—3 for \$10, 6 for \$19!

Jesse Jones Box Corp., Box 5120, Dept. PE
 Philadelphia 41, Pa.

Enclosed is \$_____ Please send me _____ Popular
 Electronics Magazine Files in the colors checked below:

Black backing/maroon sides
 Maroon backing/black sides

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP CODE _____

Orders outside U.S.A. please add \$1 additional for each file ordered.

(Payment must accompany order)

HYPNOTISM

HYPNOTIZE UNNOTICED! PATENTED new hand device makes you a Hypnotist first day or refund! Hypnotist's Handbook included! \$2.00 Hypnosis Foundation, Box 487, La Mesa 9, California.

FREE Hypnotism, Self-Hypnosis, Sleep Learning Catalog! Drawer H400, Ruidoso, New Mexico 88345.

"FEMALE HYPNOTISM" Exposed, explained! "Secret Method"—they never know! \$2, rushed. Guaranteed! Isabella Hall, Silver Springs, Florida.

HYPNOTIZE INSTANTLY! Secret Methods! Nerves! Females! Magnetic Healing! Self-Hypnosis, Illustrated Course, \$2.20. Brugenheimer Publishers, Box 158-E30, Lexington, Mass.

FREE TRIAL!! Sensational self-hypnosis record kit. Forum, 333-AA10 Michigan, Chicago 60601.

HYPNOTIZE FEMALES!—Unnoticed! Instantly! Nerves! Send \$2.25. Research Enterprises, 29-SN21 Samoset, Woburn, Mass.

MISCELLANEOUS

WINEMAKERS: Free illustrated catalog of yeasts, equipment. Semplex, Box 7208, Minneapolis, Minn. 55412.

BEERS, PEACH BRANDY, WINES—Strongest Formulas, \$2.25. (complete brew supplies hydrometers catalog 10¢) —Research Enterprises, 29-D Samoset, Woburn, Mass.

BEER, ALE, WINES! Powerful Methods! Secrets! Illustrated Booklet, \$2.25. (supplies catalog 10¢). Interstate Products, Box 1-VF3, Pelham, New Hampshire.

STAMMER—Stutter—No More. (Dr. Young.) Write: Gaucho, Box 9309-E8, Chicago 90.

POPULAR ELECTRONICS

OCTOBER 1966

ADVERTISERS INDEX



READER SERVICE NO.	ADVERTISER	PAGE NO.
1	Allied Radio 138, 139, 140	THIRD COVER
	American Institute of Engineering & Technology	116
	American Radio Relay League, Inc	122
3	Amphenol	39
4	Argos Products Company	108
5	Audio Dynamics Corporation	14
6	B & K	8
7	Blonder Tongue	117
8	Blonder Tongue	119
9	Blonder Tongue	121
10	Blonder Tongue	123
11	Burstein-Applebee Co	109
	Capitol Radio Engineering Institute, The	60, 61, 62, 63
12	Claricon	7
13	Cleveland Institute of Electronics	21
	Cleveland Institute of Electronics	86, 87, 88, 89
	Conar	104
57	Delta Products, Inc	105
	DeVry Technical Institute	3
15	E.C.I. Electronics Communications Inc	32
16	EICO Electronic Instrument Co., Inc	23
14	Electro-Voice, Inc	FOURTH COVER
17	Empire Scientific Co	126
18	Finney Company, The	13
19	Garrard	6
	Gernsback Library Inc	9
59	Grantham School of Electronics	102
21	Hallcrafters	5
22	Heath Company	112, 113, 114, 115
23	Hy-Gain Electronics Corporation	11
	IBM Corporation	33
24	IMC Magnetics Corp	108
25	International Crystal Mfg. Co., Inc	31
26	Johnson Company, E.F.	40
27	Judson Research and Mfg. Co	128
28	Knight-Kit Div., Allied Radio	25
29	Kuhn Electronics	120
30	Lafayette Radio Electronics	101
31	Mercury Electronics	106
32	Milwaukee School of Engineering	129
	Mission Liquidators	100
33	Multi-Elmac Company	111
	National Radio Institute	SECOND COVER, 1, 109
	National Technical Schools	16, 17, 18, 19
34	Olson Electronics Incorporated	122
35	Pace Communications Inc	118
36	Pearce-Simpson, Inc	127
60	Polytronics Laboratories, Inc	107
37	Precise Electronics	12
38	RCA Electronic Components and Devices	29
39	RCA Electronic Components and Devices	99
40	RCA Electronic Components and Devices	102
	RCA Institutes, Inc	34, 35, 36, 37
55	Regency Electronics, Inc	103
41	Sams & Co., Inc., Howard W	38
42	Schober Organ Corporation, The	100
43	Scott Inc., H.H.	20
44	Shure Brothers, Inc	4
45	Solid State Sales	133
46	Sonar Radio Corporation	125
47	Squires-Sanders, Inc	128
56	Switchcraft, Inc	116
	Technical Training International	10
48	Texas Crystals	126
	Tram Electronics, Inc	30
49	Turner Microphone Company, The	110
50	U.S. Army	26, 27
51	United Radio Co	135
52	University Sound	120
	Valparaiso Technical Institute	116
53	Weller Electric Corp	28
54	Xcelite, Inc	124

CLASSIFIED ADVERTISING 131, 132, 133, 134, 135, 136, 137

NEW 1967 ALLIED CATALOG

See everything new in electronics . . featured first at Allied, the world's largest electronics headquarters!



<p>New! for the audiophile . .</p>  <p>Knight-Kit® Deluxe Stereo FM-AM Tuner. Easy-to-build solid-state design.</p>	<p>New! for the ham operator...</p>  <p>Knight-Kit® 6-Meter Amateur Transceiver with universal solid-state power supply.</p>	<p>New! for the serviceman . . .</p>  <p>Knight-Kit® Portable Solid-State Color/Bar Pattern Generator. A top value!</p>
<p>New! for the CB user . . .</p>  <p>KNIGHT® 2-Way Radio. Compact solid-state design at amazingly low cost!</p>	<p>New! for everyone . . .</p>  <p>Ampex 6200HVR Home Video-tape Recorder. Make video-tapes at home!</p>	<p>New! for the TV and FM owner . . .</p>  <p>Antenna and Rotor Systems for color and black-and-white TV . . . FM, too!</p>

FREE!

Send for new 1967 ALLIED Catalog

ALLIED RADIO, Dept. 3K
P.O. Box 4398, Chicago, Ill. 60680

Send FREE 1967 Allied Catalog

Name _____

PLEASE PRINT

Address _____

City _____ State _____ Zip _____

Printed in U.S.A.

Plus hundreds more new and exclusive items, and scores of special Allied values!


NO MONEY DOWN! 24 MONTHS TO PAY!

Enjoy the things you want now, while you take 24 months to pay for them on the convenient, easy-on-the-budget Allied Credit Fund Plan.

ALLIED RADIO

P.O. Box 4398, Dept. 3K
Chicago, Illinois 60680

FREE! RUSH
CARD
TODAY

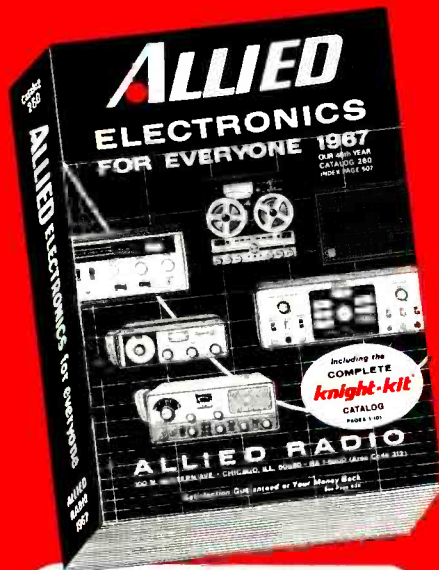

NEW 514-PAGE
ALLIED
1967 CATALOG

NAME—PLEASE PRINT

ADDRESS


CITY

STATE

3K

ZIP

FREE
ALLIED
1967
CATALOG

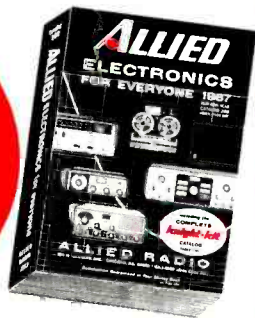

CHOOSE FROM THE WORLD'S LARGEST
SELECTION IN ELECTRONICS... AND SAVE!

Buy from the world's largest electronics supplier.
Use the Allied Credit Fund Plan to enjoy what you
want NOW—no money down, 24 months to pay.

RUSH THIS CARD NOW!




TO:
ALLIED RADIO
P. O. BOX 4398
CHICAGO, ILLINOIS 60680

PLACE
STAMP
HERE

FREE!


Send today for your
money-saving 514-page

ALLIED
1967 CATALOG

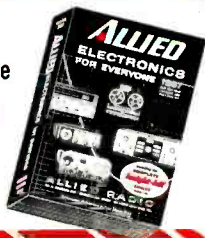

Save Most On:

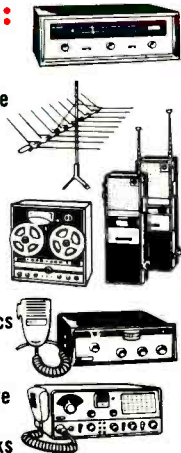- Stereo Hi-Fi
- Famous Knight-Kits
- Tape Recorders & Tape
- CB 2-way Gear
- Walkie-talkies
- FM-AM & AM Radios
- Short Wave Radios
- Portable TV
- Phonographs
- Amateur Gear
- Intercoms & P.A.
- Automotive Electronics
- Test Instruments
- TV Antennas & Tubes
- Power Tools, Hardware
- Tubes, Transistors
- Parts, Batteries, Books




**RUSH CARD TODAY
FOR FREE CATALOG!**

MAIL
CARD
NOW!

FREE

NEW 1967 ALLIED CATALOG

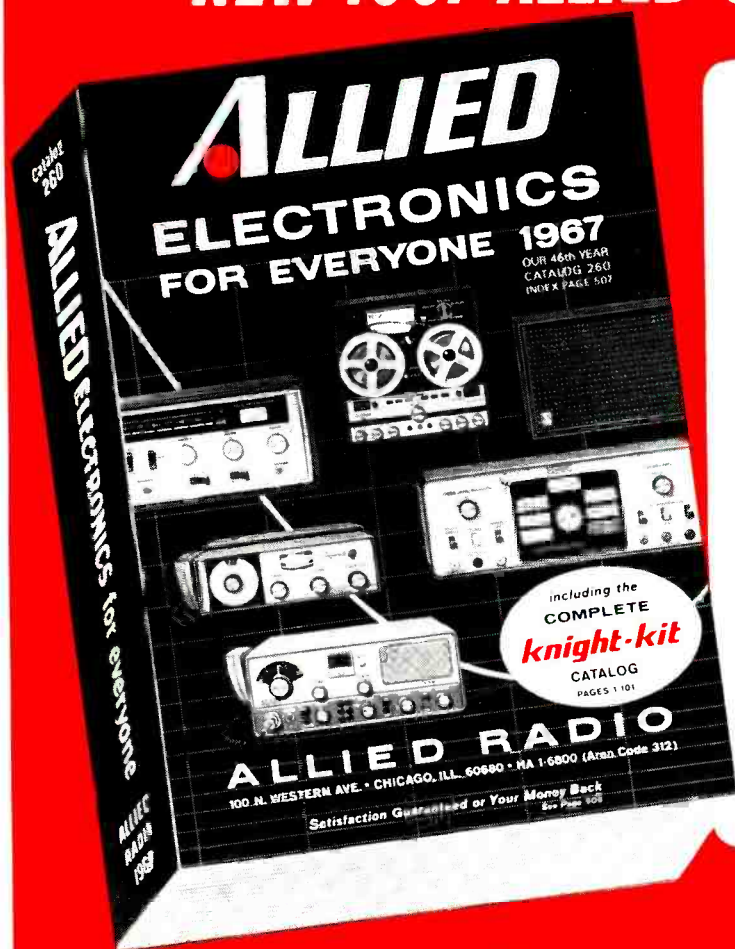

514 Pages
of top savings
on the best
in electronics
for everyone . . .

- Famous Knight-Kits
- Tape Recorders & Tape
- CB 2-Way Gear
- Walkie-talkies
- FM-AM & AM Radios
- Short-Wave Radios
- Portable TV
- Phonographs
- Amateur Gear
- Intercoms & P.A.
- Automotive Electronics
- Test Instruments
- TV Antennas & Tubes
- Power Tools, Hardware
- Tubes, Transistors
- Parts, Batteries, Books

ALLIED RADIO

WORLD'S LARGEST ELECTRONICS HEADQUARTERS

CIRCLE NO. 1 ON READER SERVICE PAGE

E-V The E-V SEVEN was born in the eerie silence of an anechoic chamber — the world's largest devoted to high fidelity design. This vast sound absorbing room let E-V engineers get right down to basic engineering. Nothing disturbed their silence — or their concentration on the subtle differences that distinguish a great speaker.

After months of experimentation, the E-V SEVEN met every design objective. Then expert listeners were invited to judge the sound — again and again — until engineers and critics were fully satisfied with E-V SEVEN performance.

But superb sound, once established, can easily slip away in the routine of mass production. We don't let it. A completely equipped anechoic chamber — right on the production line — measures every speaker against perfection. And it's ruthless. All this may seem rather elaborate for a \$66.50 compact system...and it is. You can hear the difference!

Any fine component amplifier can display the E-V SEVEN at its best, but the new

E-V 1144 stereo amplifier is uniquely suited to the purpose. Like the E-V SEVEN, the E-V 1144 is compact, handsome, and modest in cost (just \$124.50).

We threw tradition to the winds when we built the E-V 1144. Tossed out "old-hat" ideas about size and weight. Put 50 watts of stereo power in an attractive walnut-paneled cabinet no taller than a coffee cup. It's easier when you can start from scratch — yet have years of experience in miniature solid-state electronics behind you. The young tigers in the E-V lab took in on as a personal challenge — and solved it beautifully.

So plug in any stereo phono, tape recorder, or matching E-V stereo tuner. Connect a pair of E-V SEVENS. Then turn up the volume of your E-V 1144. Natural sound? Absolutely. And that's what high fidelity is all about!

Window-shop through our complete high fidelity catalog for the answer to your high fidelity needs. It's free.

**Big sound.
A natural for these
compact E-V SEVENS.
All you need is a
very good amplifier...**



**like this one.
The new E-V 1144.**



Electro-Voice

high fidelity systems and speakers • tuners, amplifiers, recorders • guitars, basses, headphones, loudspeakers
• microphones • phonograph needles and cartridges • organs, pianos • defense electronics

Electro-Voice, Inc., Dept. 1064P, 630 Cecil Street, Buchanan, Michigan 49107.

CIRCLE NO. 14 ON READER SERVICE PAGE

www.americanradiohistory.com