

STARTING THIS ISSUE! "EXPERIMENTER'S" COLUMN

# Popular Electronics

WORLD'S LARGEST-SELLING ELECTRONICS MAGAZINE

OCTOBER 1975 / 75¢

8

## HOW TO DESIGN SOLID-STATE OSCILLATORS

**Experimenting with Phase-Lock-Loop IC's**

**Build an Electronic Wheel of Fortune**

**Rhombic Antenna Plans for TV**

**How to Interface Mechanical Switches to Digital Logic**

**What's New For HI-FI in 1976**

## HIRSCH-HOUCK TESTS

**Sony's New V-FET Power Amplifier & Koss' Quadraphonic Headphones**

**PLUS REPORTS ON B&K's Transistor Tester & SBE's Digital Mobile CB Transceiver**




**BUILD THE**

# "Senior Scientist" Calculator

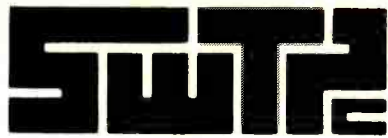**10 LEVELS OF ADDRESSABLE MEMORY**

The calculator features a numeric keypad (0-9), a decimal point, and various function keys including STO, SIN, COS, TAN, and memory keys (RCL, CLR, etc.). A small display window is visible at the top of the calculator's face.



# CD-4 DEMOMULATOR



**TRUE FOUR CHANNEL SOUND**  
Southwest Technical Products is proud to offer the most advanced CD-4 demodulator available. Our new CD-4 has characteristics superior to anything previously available thanks to the QSI-5022 integrated circuit used in the unit. This IC and the balance of the circuit was designed by Quadracast Systems Inc. under the direction of Mr. Lou Dorren. The QSI-5022 contains all the sub-system functions needed to demodulate a CD-4 disc, from the phono cartridge input to the output drive for the four power amplifiers. It may be used with either an RIAA equalized magnetic cartridge, or a semiconductor cartridge with flat equalization.

**INEXPENSIVE**  
Now anyone can afford to add discrete true 4 channel sound to their system. You no longer need be satisfied with matrix techniques that produce acoustrical enhancement, but not true 4 channel sound. The Southwest Technical Products CD-4 demodulator when added to your system will produce four channel sound from a CD-4 encoded disc that will equal, or surpass anything you can buy—no matter what the price.

**EASY INSTALLATION**  
The SWTPC demodulator connects

between the cartridge and the volume-tone control portion of your system. If you did not want tone controls, actually all that would be needed in addition to our CD-4 demodulator would be volume controls for the front and rear amplifiers. The demodulator is self powered from any 115 Volt 60 Cycle line. When normal stereo discs are played on your system a muting system automatically turns off the rear channels. A manual override 2 or 4 channel selector switch is provided on the rear panel.

**SIMPLE CONSTRUCTION**  
As shown in the photograph, the vast majority of the parts mount on the epoxy-fibreglass circuit board. Part numbers and package outlines printed on the top of the board make proper assembly quite simple. Anyone with a minimum of electronic experience should be able to assemble this project without any problems. A copy of the article describing the CD-4 demodulator and assembly instructions are supplied in the kit.

**CD-4 Demodulator Kit..... \$50.00 ppd**

**CD-4 CARTRIDGE**  
For those who do not already own a CD-4 cartridge, we are offering the "Technics" EPC-451C semiconductor

strain-gauge cartridge at a special low price when purchased with our new CD-4 demodulator kit. This cartridge features a Shibata-type stylus and excellent response out to 50 kHz. This eliminates any chance of "carrier drop-out", or "carrier crosstalk" which result in abnormal noise or distorted sound. The EPC-451C produces a high output (about 30 times that of an average magnetic cartridge) and does not pick up hum from magnetic, or electrostatic fields. Easily replaced stylus.

**EPC-451C CD-4 Cartridge.....\$25.00 ppd**

**TEST RECORD**  
Lou Dorren has recorded a special test record for Southwest Technical Products Corp. that will allow you to properly adjust your CD-4 demodulator for the best possible sound. This special test and demonstration record is yours for only \$5.00 when purchased with the CD-4 demodulator kit.

**CD-4 Test Record..... \$5.00 ppd**

**WANT MORE INFORMATION?**  
Send the coupon below and \$0.50 and we will send you by return mail a copy of the article describing our new CD-4 kit along with our catalog of other kit projects.



CD-4 DEMODULATOR


### MAIL THIS COUPON TODAY

- Enclosed is \$ \_\_\_\_\_ or BAC # \_\_\_\_\_
- or Master Charge # \_\_\_\_\_ Bank # \_\_\_\_\_ Expire Date \_\_\_\_\_
- CD-4 Demodulator Kit     Cartridge     Test Record

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

\$0.50 Enclosed for catalog & CD-4 Data  
Southwest Technical Products Corp., Box 32040, San Antonio, Texas 78284

# Digital Watch Breakthrough!

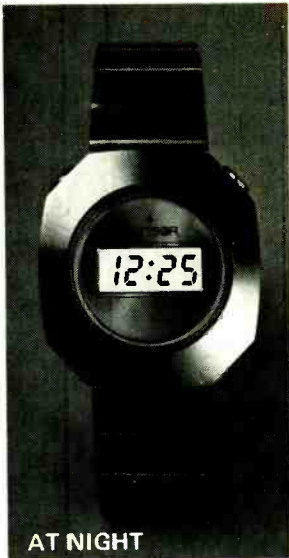

AT NIGHT



IN SUNLIGHT



The new CDR display dramatically increases legibility and battery life and opens a new era of watch technology.

Would you do this with your solid-state watch? Of course not. Practically all solid-state watches require care and pampering. Not the Sensor 770. You can dunk it, drop it and abuse it without fear during its unprecedented five year parts and labor warranty.

At night or during the day, the Sensor's large, constantly "alive" CDR display is clear and easy to read.

A glance at your solid-state watch won't give you the time. Sound incredible? If it's an LED (light-emitting diode) watch, you've got to press the button first. If it's an LCD (liquid crystal display) watch, you must have plenty of light at just the right angle.

Now there's a new solid-state display technology called CDR (crystal diffusion reflection) incorporating the best features of the LED and the LCD displays. You can easily and constantly read your watch under any light conditions without strain or inconvenience.

The new CDR display takes the properties of the field-effect liquid crystal display, puts a strong reflective substance behind two closely-aligned polarization lenses, and the resulting large digits can be read clearly from practically any angle. When engaged, an integrated light source illuminates the display at night. The Sensor's constantly "alive" high-contrast display makes legibility outstanding under all light conditions.



Press the button on the Sensor 770 and the date and seconds appear in large black numerals—easy to read in any light.

## A WORRY-FREE WATCH

Solid-state watches pose their own problems. They're fragile, they must be pampered, and they require frequent service. Not Sensor! Here are just five common solid-state watch problems you can forget about with this advanced space-age timepiece:

**1. Forget about batteries** Sensor is powered by a single EverReady battery that will actually last years without replacement. In fact, if your battery fails during the first five years, we will replace it free of charge. A low-power indicator tells you when to change the battery one month in advance and you simply open the hatch at the back of your watch and replace the battery yourself.

**2. Forget about water** Take a shower or go swimming. The Sensor is so water-resistant that it withstands depths of up to 100 feet.

**3. Forget about shocks** A three foot drop onto a solid hardwood floor or a sudden jar. Sensor's solid case construction, dual strata

crystal, and cushioned quartz timing circuit make it the most rugged solid-state quartz watch ever produced.

**4. Forget about service** The Sensor 770 has an unprecedented five-year parts and labor unconditional warranty. Each watch goes through weeks of aging, testing and quality control before assembly and final inspection. Service should never be required, but if it should anytime during the five year warranty period, we will pick up your Sensor at your door and send you a loaner watch while yours is repaired—all at our expense.


**5. Forget about changing technology** The Sensor is literally years ahead of every other watch in durability and technology. But should Sensor's technology improve anytime during the next five years, you may trade in your watch for Sensor's newer model under JS&A's liberal trade-in policy.

## COMPARED TO EVERY OTHER

The \$275 Pulsar uses the LED technology which requires pressing a button each time you want to review the time. Even the \$500 solar-powered Synchronar watch, in our opinion, can't compare with the Sensor and its 5-year warranty. And no solid-state watch can compare to Sensor's quality, accuracy, ruggedness and exceptional value.
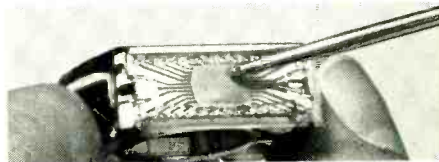
## PLENTY OF ADVANCED FUNCTIONS

Sensor's five functions give you everything you really need in a solid-state watch. Your watch displays the hours and minutes constantly. Depress a button and your watch displays the seconds and date constantly. There's also an AM/PM indicator. To adjust the time, insert a ball-point pen into the four-channel time-control switch. Each channel independently controls one time function. In short, you can change the hours without affecting the date, and the minutes without affecting the hours.



A pin points to the new decoder/driver integrated circuit which takes the input from the oscillator countdown integrated circuit and computes the time while driving the display. This single space-age device replaces thousands of solid-state circuits and provides the utmost reliability—all unique to Sensor.

Sensor's accuracy is unparalleled. All solid-state digitals incorporate a quartz crystal. So does the Sensor. But crystals change frequency from aging and shock. And to reset them, the watch case must be opened and an air-tight seal broken which may affect the performance. In the Sensor, the crystal is first aged before it is installed, and secondly, it is actually cushioned in the case to absorb tremendous shock. The quartz crystal can also be adjusted through the battery compartment without opening the case. In short, your watch should be accurate to within 5 seconds per month and maintain that accuracy for years without adjustment and without ever opening the watch case.

## STANDING BEHIND A PRODUCT

JS&A is America's largest single source of electronic calculators, digital watches and other space-age products. We have selected the Sensor as the most advanced American-made, solid-state timepiece ever produced. And we put our company and its full resources behind that selection. JS&A will unconditionally guarantee the Sensor—even the battery—for five years. We'll even send you a loaner watch to use while your watch is being repaired should it ever require repair. And our liberal trade-in policy guarantees that new watch technology will never leave you behind.

Wear the Sensor for one full month. If you are not convinced that the Sensor is the most rugged, precise, dependable and the finest quality solid-state watch in the world, return it for a prompt and courteous refund.

To order your Sensor, credit card buyers may simply call our toll-free number below or mail us a check in the amount indicated below plus \$2.50 for postage, insurance and handling. (Illinois residents add 5% sales tax) We urge you, however, to act promptly and reserve your Sensor 770 today.

Stainless steel w/leather strap . . . . . \$99.95  
Stainless steel w/metal band . . . . . \$109.95  
Gold plated w/leather strap . . . . . \$119.95  
Gold plated w/metal band . . . . . \$129.95

**JS&A** NATIONAL SALES GROUP

DEPT. PE 4200 DUNDEE ROAD  
NORTHBROOK, ILLINOIS 60062  
CALL TOLL-FREE. . . . (800) 323-6400  
In Illinois call . . . . . (312) 498-6900

© JS&A Group, Inc., 1975

# Cobra 19, the mini 23 that talks like Big Brother

If you've ever heard a Cobra 21, you know it's hard to believe all that talkpower is legal. Cobra found the way to make their radios really talk—and still obey the rules.

Now you can talk just as loud and far with a smaller package.

Cobra 19 is thin and narrow enough to mount conveniently in any car—even the latest subcompacts—Cobra 19 has other features you'd expect like plug-in mike and external speaker jack.

And has it got ears! Cobra 19 has the same receiver sensitivity, selectivity, and interference rejection as its big brother, Cobra 21. It has an efficient automatic noise limiter too; you'll hear clearly in the heart of heavy traffic.

Like every Cobra radio, it's backed by warranty service stations in all fifty states even though Cobra quality assures you of minimum need for service. See Cobra 19 at your dealer. It's small on the counter and pocketbook and big on the air.



 **Cobra 19**

PRODUCT OF DYNASCAN CORPORATION • 1801 W. Belle Plaine • Chicago, Ill. 60613

OCTOBER 1975 VOLUME 8, NUMBER 4

# Popular Electronics®

WORLD'S LARGEST SELLING ELECTRONICS MAGAZINE

## FEATURE ARTICLES

- HOW TO "DEBOUNCE" MECHANICAL SWITCHES FOR DIGITAL LOGIC USE ..... E. W. Gray 51  
*Interface circuitry eliminates false pulses.*
- HOW TO DESIGN SOLID-STATE OSCILLATORS ..... Jim Huffman 61  
*Easy-to-follow approach to basic principles.*

## CONSTRUCTION ARTICLES

- BUILD THE "SENIOR SCIENTIST" CALCULATOR ..... Martin Meyer 33  
*Has combinational, statistical and probability functions.*
- EXPERIMENTING WITH PHASE-LOCKED LOOPS ..... Herb Cohen 47  
*Four useful, easy-to-build projects to increase your understanding.*
- BUILD A HIGH-GAIN RHOMBIC TV ANTENNA ..... George L. Monser 58  
*Inexpensive TV antenna on your roof.*
- ELECTRONIC WHEEL OF FORTUNE SIMULATES MECHANICAL GAME ..... Robert D. Pascoe 69  
*Solid-state game uses LED's as spinning ball.*
- BUILD AN AUDIO SWEEP MARKER GENERATOR ..... Jon Paul 71  
*Identify frequencies on audio swept waveform display.*

## COLUMNS

- STEREO SCENE ..... Ralph Hodges 22  
*What's New for Hi-Fi in 1976.*
- SOLID STATE ..... Lou Garner 62  
*The Goodflasher—Part II.*
- CB SCENE ..... Len Buckwalter 91  
*Harmonic TV Interference.*
- AMATEUR RADIO ..... Herbert S. Brier 93  
*More on Restructuring Licensing.*
- TEST EQUIPMENT SCENE ..... Leslie Solomon 100  
*Using Diodes in Power Supplies.*
- EXPERIMENTER'S CORNER ..... Forrest M. Mims 102  
*A Programmable Timer/Counter.*

## PRODUCT TEST REPORTS

- SONY MODEL TA-4650 V-FET STEREO AMPLIFIER ..... 74
- KOSS PHASE/2 + 2 QUADRAFONE 4-CHANNEL HEADPHONES ..... 76
- AUDIOANALYST MODEL A-200X SPEAKER SYSTEM ..... 78
- SBE "FORMULA D" TYPE 26 CB TRANSCEIVER ..... 79
- B&K MODEL 520 TRANSISTOR TESTER ..... 80

## DEPARTMENTS

- EDITORIAL ..... Art Salsberg 4  
*The New Product Warranty Law.*
- LETTERS ..... 6
- NEW PRODUCTS ..... 12
- NEW LITERATURE ..... 16
- ELECTRONICS LIBRARY ..... 108
- ADVERTISERS INDEX ..... 123

POPULAR ELECTRONICS, October 1975, Volume 8, Number 4. Published monthly at One Park Avenue, New York, NY 10016. One year subscription rate for U.S., \$6.98. U.S. Possessions and Canada, \$7.98; all other countries, \$8.98. Second Class postage paid at New York, NY and at additional mailing offices. Authorized as second class mail by the Post Office Department, Ottawa, Canada and for payment of postage in cash. Subscription service and Forms 3579, P.O. Box 2774, Boulder, CO 80302. POPULAR ELECTRONICS including ELECTRONICS WORLD. Trade Mark Registered. Indexed in the Reader's Guide to Periodical Literature. COPYRIGHT © 1975 BY ZIFF-DAVIS PUBLISHING COMPANY. ALL RIGHTS RESERVED.

Ziff-Davis also publishes Boating, Car and Driver, Cycle, Flying, Modern Bride, Popular Photography, Skiing and Stereo Review.  
**Editorial correspondence:** POPULAR ELECTRONICS, 1 Park Ave., New York, NY 10016. Editorial contributions must be accompanied by return postage and will be handled with reasonable care, however, publisher assumes no responsibility for return or safety of manuscripts, art work, or models.  
**Forms 3579 and all subscription correspondence:** POPULAR ELECTRONICS, Circulation Dept., P.O. Box 2774, Boulder, CO 80302. Please allow at least eight weeks for change of address. Include your old address, enclosing, if possible, an address label from a recent issue.

**EDGAR W. HOPPER**  
Publisher

**ARTHUR P. SALSBERG**  
Editorial Director

**LESLIE SOLOMON**  
Technical Editor

**JOHN R. RIGGS**  
Managing Editor

**ALEXANDER W. BURAWA**  
Associate Editor

**EDWARD I. BUXBAUM**  
Art Director

**JOHN McVEIGH**  
Assistant Editor

**ANDRE DUZANT**  
Technical Illustrator

**HERBERT S. BRIER**  
**LEN BUCKWALTER**  
**LOU GARNER**  
**GLENN HAUSER**  
**JULIAN D. HIRSCH**  
**RALPH HODGES**  
**ART MARGOLIS**  
**JERRY OGDIN**  
**WILFRED M. SCHERER**  
Contributing Editors

**JOSEPH E. HALLORAN**  
Advertising Director

**JOHN J. CORTON**  
Advertising Sales

**LINDA BLUM**  
Advertising Service Manager

**PEGI McENEANEY**  
Executive Assistant

**STANLEY NEUFELD**  
Associate Publisher

**FURMAN HEBB**  
Group VP, Electronics & Photo

ZIFF-DAVIS PUBLISHING COMPANY  
Popular Electronics  
Editorial and Executive Offices  
One Park Avenue New York, New York 10016  
212-725-3500

Hershel B. Sarbin, President  
Furman Hebb, Executive Vice President  
Vincent Perry, Financial Vice President and Treasurer  
Phillip T. Hefernan, Senior Vice President, Marketing  
Edward D. Muhlfeld, Senior Vice President, Sports Division  
Philip Sine, Senior Vice President  
Frank Pomerantz, Vice President, Creative Services  
Arthur W. Butzow, Vice President, Production  
Lawrence Sporn, Vice President, Circulation  
George Morrissey, Vice President  
Sydney H. Rogers, Vice President  
Sidney Holtz, Vice President  
Charles B. Seton, Secretary  
Edgar W. Hopper, Vice President, Electronics Div.

William Ziff, Chairman  
W. Bradford Briggs, Vice Chairman

Midwestern Office  
The Patis Group, 4761 West Touhy Ave.,  
Lincolnwood, Illinois 60644, 312 679-1100  
GERALD E. WOLFE, THOMAS HOCKNEY  
Western Office  
9025 Wilshire Boulevard, Beverly Hills, CA 90211  
213 273-8050 BRadshaw 2-1161  
Western Advertising Manager, BUD DEAN

Japan: James Yagi  
Oji Palace Aoyama, 6-25, Minami Aoyama  
6 Chome, Minato-Ku, Tokyo 407-1930/6821,  
582-2851



The publisher has no knowledge of any proprietary rights which will be violated by the making or using of any items disclosed in this issue.



## Editorial

### THE NEW PRODUCT WARRANTY LAW

Hallelujah! Did you know that we have a wonderful (?) new product warranty law to protect buyers from those terrible ogres, the manufacturers? With this law, unleashed by the Federal Trade Commission and effective for products made after July 4, 1975, the buyer will probably enjoy warranties that offer less protection than ever before. He will also probably pay more and watch our Federal bureaucracy (and hence his taxes) grow even larger.

In a giant step backward, the consumer will now have a choice of buying products carrying one of two types of warranties: "Limited" or "Full," depending on which one the manufacturer wishes to declare. Some gutsy manufacturers will doubtlessly choose the Full one, hoping to gain a competitive advantage. But they'll also run the risk of having to abide by very vague Federal standards—which could be interpreted differently at a later time and expose them to legal damages. (By vague we mean such things as the FTC's partiality for the word "reasonable," as in "repair within a reasonable time," "full refund after a reasonable number of repair attempts," etc.)

Though the law is now in effect, the FTC has not yet clearly defined the rules (and may not for years to come), leaving manufacturers in a quandary. How do they interpret "reasonable"? Who is responsible for sending a defective product to the company? What about house service calls for portable TV receivers? The auto tire maker wants to know if he can still deduct depreciation when a refund is in order. As a result of all this confusion, many manufacturers will take the conservative route rather than risk a financial bath. The loser, I think, will be the consumer. For example, *Business Week* reports that Wright & McGill Co. will drop the "lifetime guarantee" from all of its "Eagle Claw" line of fishing rods and reels. This decision has been reached, it seems, because a Full warranty under the new law is fraught with legal uncertainties, and the company doesn't want to fall back on a Limited warranty.

Certainly, product warranties have been a source of anguish to some consumers over the years. More often than not, however, this has not been due to the wording of the warranty. In most instances, dissatisfaction was caused by the actual intent and action of the manufacturer, dealer or authorized service company. The new Warranty/FTC Improvement Law won't change this! As in the past, the dealer or manufacturer who treats a buyer fairly will retain him or her as a customer—and as a good-will ambassador to attract other buyers. The manufacturer who doesn't pursue this policy soon loses out in the marketplace.

The new warranty law is only the tip of the iceberg, as one might expect. There are proposed rules requiring pre-sale availability of retailers' complete written warranties, with products carrying a printed message inviting consumers to ask to see a copy of the warranty.

Interestingly, the FTC's Director of the Bureau of Consumer Protection admits that the FTC could only police this at enormous cost. One member of the FTC warned that the rule could cost consumers millions of dollars a year. While acknowledging that he supports the principle that people who make and sell products ought to stand behind them, he added, "There are some things the citizen must learn to do for himself. . . ." Amen!

*Art Salsberg*

POPULAR ELECTRONICS

# New Mallory Ni-Cad Batteries. Rechargeable 1000 times.



Economical recharging —  
Mallory BC-1 Charger draws only two watts.

Team these long-life nickel-cadmium cells with an automatic Mallory Charger, and you can recharge them 1000 times, or more.

You'll be sure of having fresh D, C, and AA batteries, while saving money, time and trouble. Mallory Rechargeable Nickel-Cadmium Batteries keep on coming back for more in electronic calculators, tape recorders, radios, cameras, toys, other battery-powered products.

Keep a spare set of Mallory Ni-Cads on hand,

and you'll never run out of battery power again. They recharge to full strength, two or four at a time. And unlike ordinary dry cells that lose voltage during discharge, Mallory Ni-Cads with a full charge maintain operating voltage during the entire work cycle. You get maximum power, continuously, for top product performance.

For the long run, Mallory Rechargeable Ni-Cads . . . the 1000-time batteries. Get them now at your Mallory Distributor.

## MALLORY

**MALLORY DISTRIBUTOR PRODUCTS COMPANY**

a division of P. R. MALLORY & CO. INC.

Box 1284, Indianapolis, Indiana 46208; Telephone: 317-856-3731

Batteries • Capacitors • Controls • Security Products • DURATAPE® • Resistors • Semiconductors • SONALERT® • Switches • Fastening Devices

DURATAPE® and SONALERT® are registered trademarks of P. R. Mallory & Co. Inc.

CIRCLE NO. 37 ON FREE INFORMATION CARD

## Sound reasons 6 thru 10 why an SAE gives you what you pay for.

You are an audio connoisseur. You know exactly what you are looking for in audio components. The right features. The right functions. The right power. But you can't find one at the right price. And you won't. What you're looking for costs plenty to produce. Some build additional price right into their units. We build additional unit into our price. Here are some reasons why an SAE gives you what you pay for.



Our Mark VIII FM Digital Stereo Tuner sets new industry standards for moderately priced tuners—\$650. Wide-open stereo separation, crystal clear reception, and precise smooth operation have been accomplished by the newest linear and digital technology. Linear-phase filters and phase-locked-loop stereo multiplex circuitry are permanently aligned to provide minimum distortion and maximum interference-rejection. A dual metering system, combined with our LED digital readout, assures precise station logging, maximum signal strength and center-of-channel tuning.

A "basic" for all SAE tuners is the eight permanently aligned linear-phase monolithic IF filters. These filters provide 120dB alternate-channel selectivity while achieving minimum harmonic and inter-modulation distortion.

There are many important but expensive standards that we employ in our tuner production. Included are seven-stage differential-amplifier IC limiters that achieve 100dB AM and high-impulse noise rejection. Five-gang variable capacitors and three MOS-FET (metal oxide silicon-field-effect transistor) RF front ends result in a spurious response rejection of over 100dB and an IHF sensitivity of 1.6  $\mu$ V.

Then there is care. At SAE we're emphatic about it. We start by procuring the finest parts available from all over the world. Then we screen the parts to insure that each one meets our rigid requirements. We also perform all of our own manufacturing operations in our modern facility, such as wave soldering, metal work, transformer coil winding and fabrication. Processes that others subcontract. But we want control to insure that each step is performed correctly.

The testing (quality assurance) process is an integral part of our manufacturing philosophy. After testing the parts, we test subassemblies, and then completed units (even on a shaker table). After a unit is complete, it gets a 48 hour burn-in (as compared with 3 hours and less for some manufacturers). In fact, 25% of the time devoted to production of a unit is in quality control. This of course means that it will cost a little more, but you'll get what you pay for.



There are many other reasons. Send us the attached coupon and we'll send you an additional 25, plus literature, and the location of a dealer who'll be able to supply even more.

### Components for the Connoisseur



Scientific Audio Electronics, Inc. PE10/75  
P.O. Box 60271 Terminal Annex,  
Los Angeles, California 90060  
I want more reasons, thank you.  
Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

CIRCLE NO. 49 ON FREE INFORMATION CARD

# Letters

## VARIABLE AUDIO FILTER

In the article "Active Filter Sharpens CW Reception" (June 1975), the author alludes to difficulty in tuning in CW signals when the 100-Hz filter is switched into the circuit. Autek Research (Box 1494, Canoga Park, CA 91304) markets an audio filter which is continuously variable from 30 Hz to approximately 2 kHz, with a center frequency of 800 kHz. The "Q-Box" is priced at \$17.95 plus \$1 for shipping. I have been using one for over a year and find it a great help in digging through the clutter of the Novice bands.—*Thomas R. Sundstrom, Willingboro, NJ*

## ORDERING STETHOSCOPE KITS

Due to a slip-up at the Post Office, the first few orders for the stethoscope kit ("Listen to Your Heart with Doppler Ultrasound," August 1975, p 60) were unfortunately returned to the senders. I apologize for the mix-up. The situation has now been corrected and readers who wish to return their orders to the same address will receive the kit.—*Joseph Jaffe*

## WANTS SHORTWAVE UV LIGHT

"Build a Blacklight Lantern" (April 1975) was a project I have been waiting to see in print for some time. However, I was disappointed that the Parts List did not include a source for a shortwave fluorescent tube and its associated cobalt glass filter. Working in the underground zinc mine here in the Fluorescent Mineral Capital of the World and being a rock collector for years, I know that most minerals that fluoresce at all will be more appealing under shortwave UV light. As long as one uses a shortwave UV light with a reasonable amount of caution and does not look directly into the light source, he need not be concerned with "sun-burned" eyes.—*Joseph Williams, Franklin, N.J.*

We wanted to keep the project as safe as possible for even an uninformed user, which precluded the inclusion of eye-damaging (if improperly used) shortwave UV light. However, if you really want a shortwave UV light, you might try looking through the latest Edmund Scientific Co. (300 Edscorp Bldg., Barrington, NJ 08007) catalog for ready-to-use shortwave UV lights starting at about \$40.

## CHECK YOUR CMOS

I have had several letters telling of problems involving the CMOS oscillator in my article "Build a Versatile Digital LED Thermometer" (November 1974). I have double-checked the schematic to determine that it is correct. One thing to remember is that a TTL NAND will not work in the place of the CMOS NAND because the resistances used are too high for TTL. Also, CMOS circuits are notoriously tricky if rejets are used. I would advise trying several prime CMOS units before rejecting the circuit.—*Thomas R. Fox*

## EQUIPMENT FOR AM BCB DX'ING

In "How to Listen to Out-of-State AM Broadcasts" (April 1975), the author failed to mention the type of equipment needed to get started in this hobby. I am a sports fan and would like to receive broadcasts of sporting events outside of the Connecticut area. Just what type of equipment would I need to get started in AM broadcast band DX'ing?—*Daniel Protas, Stamford, Conn.*

First of all, you need a sensitive AM broadcast band receiver or tuner. Then, you need a good antenna system that will pull in those weak signals originating out of state. One such antenna is the McKay Dymek Model DA-3.

## IC FOR THE VR12 VOLTAGE REGULATOR

General Electric has discontinued the manufacture of the PA230 IC which was originally used for the Beco VR12 voltage regulator. The VR12 has been redesigned around the UA741 (full temperature range) IC.—*C. R. Ball, Jr., Beco Inc., Salem, VA.*

## ELECTRONICS UNLIMITED ORDERS






On March 14, I ordered the LED kit from Electronics Unlimited, Inc., as described in Lou Garner's March "Solid State" column. So far, I have not received the kit. After getting my cancelled check from the bank, I wrote E.U.I. I have still heard nothing from them. This is the first time I have had any difficulty ordering from your advertisers.

—*P.A. Shackelford, Paducah, Ky.*

This is one of many letters we have received concerning nondelivery of paid-for parts from E.U.I. First, E.U.I. is not an advertiser. Lou Garner simply gave the company a free plug for what he thought was an unusual \$8.95 kit that readers would welcome. He had been assured by E.U.I. (before mentioning it in the column) that they would be happy to fill orders on the kit. A number of phone calls from Lou to E.U.I. elicited a host of reasons for shipment delay, including waiting two weeks for checks to clear and back-ordered perf boards. If any reader experiences difficulty in reaching the company through its P.O. Box number, please let us know (enclosing a stamped, self-addressed envelope) and we will send you a more complete address.



# INSIDE the Altair® Computer

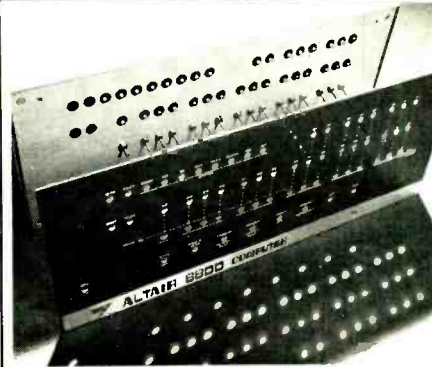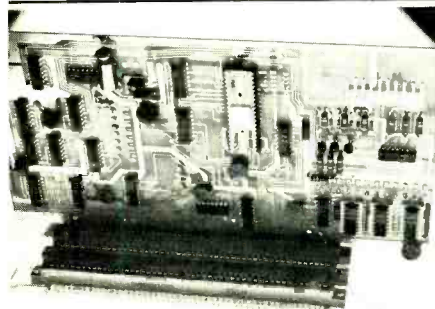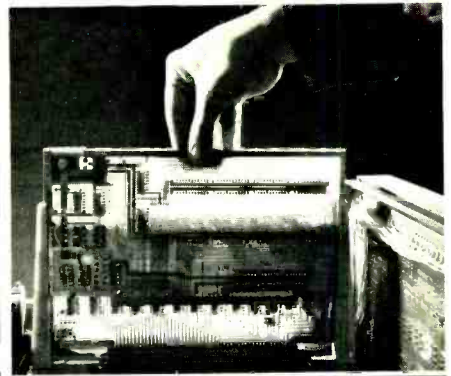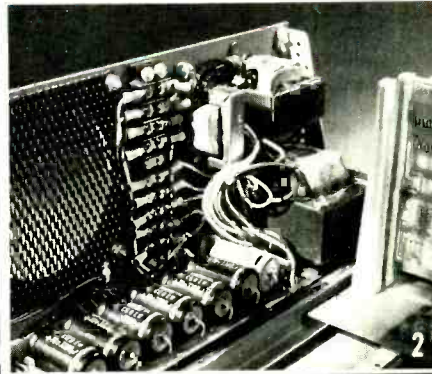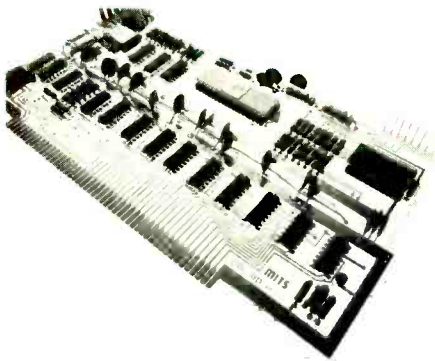

## 1. Central Processing Unit (CPU) Board.

This double-sided board is the heart of the Altair 8800. It was designed around a powerful, byte oriented, variable word length processor—a complete central processing unit on a single LSI chip using n-channel, silicon gate MOS technology. The CPU board also contains the Altair System Clock—a standard TTL oscillator with a 2.000 MHz crystal as the feedback element.

## 2. Power Supply.

The Altair Power Supply provides two +8, a +16 and a -16 volts. These voltages are unregulated until they reach the individual boards (CPU, Front Panel, Memory, I/O, etc.). Each board has all the necessary regulation for its own operation.

The Altair Power Supply allows you to expand your computer by adding up to 16 boards inside the main case. Provisions for the addition of a cooling fan are part of the Altair design.

## 3. Expandability and custom designing.

The Altair has been designed to be easily expanded and easily adapted to thousands of applications. The basic Altair comes with one expander board capable of holding four vertical boards. Three additional expander boards can be added inside the main case.

## 4. Altair Options.

Memory boards now available include a 1024 word memory board, a 2048 word memory board, and a 4096 word memory board. Interface boards include a parallel board and 3 serial boards (RS232, TTL and Teletype). Note: Interface boards allow you to connect the Altair Computer to computer terminals, teletypewriters, line printers, plotters and other devices.

Other Altair Options include additional expander boards, computer terminals, audio-cassette interface board, line printers, ASCII keyboards, floppy disc system, alpha-numeric display and more.

## 5. All aluminum case and dress panel.

The Altair Computer has been designed both for the hobbyist and for industrial use. It comes in an all aluminum case complete with sub-panel and dress panel.

## 6. It all adds up to one fantastic computer.

The Altair is comparable to mini-computers costing 10-20 thousand dollars. It can be connected to 256 input/output devices and can directly address up to 65,000 words of memory. It has over 200 machine instructions and a cycle time of 2 microseconds.

You can order the Altair Computer by simply filling out the coupon in this ad or by calling us at 505/265-7553. Or you can ask for free technical consultation or for one of our free Altair System Catalogues.

## PRICES:

Altair Computer kit with complete assembly instructions	\$439.00
Assembled and tested Altair Computer	\$621.00
1,024 word memory board	\$97.00 kit and \$139.00 assembled
2,048 word memory board	\$145.00 kit and \$195.00 assembled
4,096 word memory board	\$264.00 kit and \$338.00 assembled.
Full Parallel Interface board and \$114.00 assembled.	\$92.00 kit
Serial Interface board (RS232)	\$119.00 kit and \$138.00 assembled.
Serial Interface board (TTL or teletype)	\$124.00 kit and \$146.00 assembled
Audio Cassette Record Interface	\$128.00 kit and \$174.00 assembled
Expander Board (adds 4 slots to 8800)	\$16.00 kit and \$31.00 assembled

**NOTE:** Altair Computers come with complete documentation and operating instructions. Altair customers receive software and general computer information through free membership to the Altair User's Club. Software now available includes a resident assembler, system monitor, text editor and BASIC language.

MITS/6328 Linn NE, Albuquerque, NM, 87108 505/265-7553

# MITS

"Creative Electronics"

Prices and specifications subject to change without notice. Warranty: 90 days on parts for kits and 90 days on parts and labor for assembled units.

## MAIL THIS COUPON TODAY!


- Enclosed is check for \$ \_\_\_\_\_
- BankAmericard # \_\_\_\_\_
- or Master Charge # \_\_\_\_\_
- Credit Card Expiration Date \_\_\_\_\_
- Altair Computer     kit     Assembled
- Options (list on separate sheet)
- Include \$8.00 for postage and handling.
- PLEASE SEND FREE ALTAIR SYSTEM CATALOGUE

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE & ZIP \_\_\_\_\_

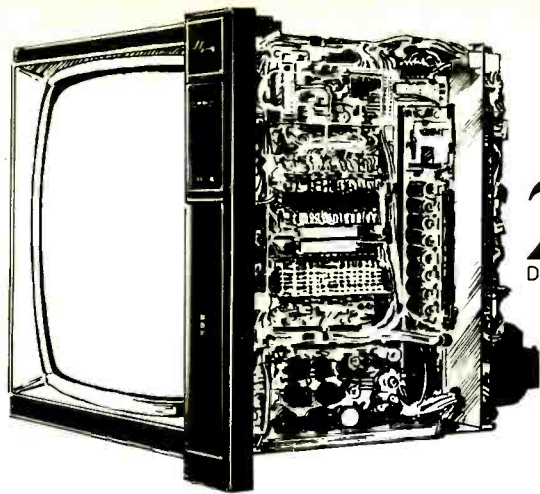MITS/6328 Linn NE, Albuquerque, NM, 87108  
505/265-7553



**You get the same  
25" hobby-kit color  
TV from three  
different schools.**

DIAGONAL



**You get  
this designed-  
for-learning  
25" color TV only  
with NRI training.**

DIAGONAL

No other home-study school gives you a TV like the one you build with NRI's Master Course in Color TV/Audio servicing. Some schools give you three or four plug-in sub-assemblies off the production line to put together a commercial set. Others give you a hobby-kit bought from outside sources. And because neither type was originally designed to train people for TV servicing, lessons and experiments must be "retro-fitted" to the set as it comes.

That's why we went to the trouble to engineer our own, exclusive solid-state TV. It's the only way a student can (1) get the feel of typical commercial circuitry, (2) learn bench techniques while building a complete set from the "ground" up, (3) perform over 25 "in-set" experiments during construction, and (4) end up with a 25" diagonal solid-state color TV with console cabinet and all the modern features you'll find on sets you'll service. Nobody else can give you this combination of advantages because nobody else invested the time and money to design a set with learning in mind.



## More know-how per dollar

That's what it all boils down to, the quality of training you get for the money you spend. In our 60-year history, more than a million students have come to NRI and we're fully approved for career study under the G.I. Bill. We must be teaching something right.

Some of those "right" things are bite-size lessons to ease understanding and speed learning . . . personal grading of all tests, with comments or explanations where needed . . . a full-time staff of engineer/instructors to help if you need it . . . plenty of "real-life" kits and experiments to give you hands-on training . . . and fully professional programs oriented to full- or part-time career needs.

## NRI passes the savings on to you

You don't pay a big premium to get this unique TV as part of your training, because NRI engineering eliminates the cost of buying from an outside source. And we pay no salesman's commission. We enroll students by mail only. We pass the savings along to you in the form of low tuition fees, extras like a cabinet for the TV, a solid-state radio you learn on as you build, and actual instrument kits for servicing TVs . . . triggered sweep oscilloscope, integrated circuit TV pattern generator, and 3½ digit digital multimeter. You can pay hundreds of dollars more for a similar course and not get a nickel's worth more in training and equipment.

## Widest choice of career opportunities


NRI offers not one, but five excellent TV/Audio servicing courses so you can tailor your training to your budget. Or, you can study other opportunity fields like Computer Electronics, Communications, Aircraft or Marine Electronics, Mobile Radio, and more. Free catalog describes them all, showing lesson plans, equipment and kits, and career opportunities. There's no obligation and no salesman will ever call, so send for your copy today. See for yourself why NRI experience, selection, and exclusives give you something no other school can.

If card is missing, write to:



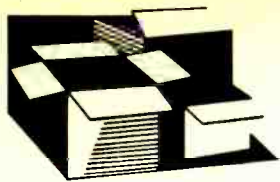**NRI SCHOOLS**

McGraw-Hill Continuing Education Center  
3939 Wisconsin Avenue,  
Washington, D.C. 20016




# New Products

Additional information on new products covered in this section is available from the manufacturers. Either circle the item's code number on the Free Information Card or write to the manufacturer at the address given.
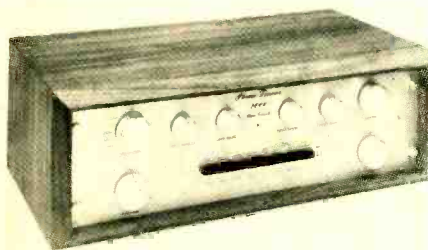
## PHASE LINEAR STEREO PREAMP

Phase Linear's new stereo preamplifier, Model 2000, features low-noise IC designs, individual detented bass and treble controls for each channel, and a choice of four



tone turnover points. Two tape monitors and a low-frequency active equalizer are included. "Variable Ambience Injection" is said to enhance the dimensions of stereo reproduction. THD is rated at less than 0.1%, and phono S/N at 74 dB below 10 mV. \$299.

CIRCLE NO. 70 ON FREE INFORMATION CARD

## BEARCAT WEATHER-PROOF SPEAKER

The Bearcat speaker by the Electra Company is weather-proof (made of white heavy-duty plastic), making it well suited for patio, garden, or marine installation. It can handle 5 watts rms (12 watts peak), and its response is 500 to 5000 Hz. Shipping weight is 1.4 lb. \$16.95.

CIRCLE NO. 71 ON FREE INFORMATION CARD


## EICO DIGITAL LOGIC PROBE

The Model DLP-6 Digital Logic Memory Probe can be used with DTL and TTL systems, and provides detection capabilities for pulse durations as short as 50 nanoseconds. The indicator system consists of three LED's. The bottom LED lights green for logic 1, the center LED lights red for logic 0, and the top LED lights yellow to indicate a positive- or negative-going transition. Each LED remains in the "on" stage for 200 nanoseconds regardless of pulse duration. A memory switch causes the LED to remain on permanently after a positive or negative pulse occurs. Available in either kit (\$19.95) or factory-assembled (\$29.95) form.

CIRCLE NO. 72 ON FREE INFORMATION CARD
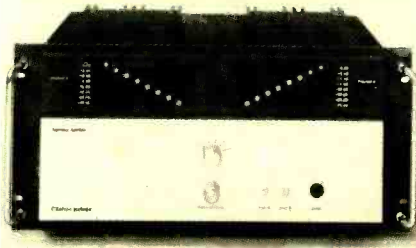
## HARMAN/KARDON STEREO POWER AMPLIFIER

The Citation 16 is a new stereo amp from Harman/Kardon with a power rating (as per FTC rules) of 150 W/channel, and twin power level indicators using a series of



LED's whose sensitivity is switchable for 4- and 8-ohm loads. It is said that the amplifier offers a wide power bandwidth, and incorporates a design which deals effectively with transient intermodulation distortion (TID). Also included is a test switch for checking the readouts. The Citation 16 can be operated in a "bridged" one-channel mode with higher output capacity. \$795.

CIRCLE NO. 73 ON FREE INFORMATION CARD


## HEATHKIT ELECTRONIC WORKSHOP

Budding scientists can build up to 35 different experiments while learning electronics basics with the new Heathkit Jr. JK-18A Electronic Workshop. Connections are solderless spring terminals and power is supplied by four "D" cells. Each experiment is accompanied by a simple schematic to help teach circuit and component identification. Circuits which can be built with the kit include code flasher, continuity tester, battery and diode testers, rain alarm, timing relay, and intercoms. \$34.95 (mail order, less batteries)

CIRCLE NO. 5 ON FREE INFORMATION CARD
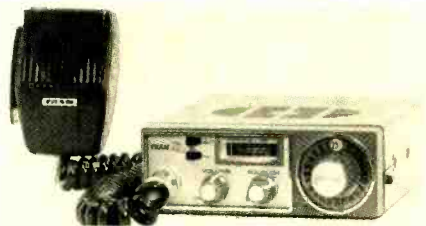
## TRAM/DIAMOND MINI-MOBILE CB RIG

The Tram XL, a new mini-mobile unit from Tram/Diamond, features PA/CB operation, switchable ANL, illuminated S/r-f meter,



scquelch, 23-channel operation, 13.8-volt (positive or negative ground) supply voltage, front-panel plug-in mike, and mounting bracket with tamper-proof bolts (wrench included). Rated frequency tolerance is  $-0.005\%$ , sensitivity  $0.6 \mu\text{V}$  for 10 dB S+N/N (1-kHz sine wave, 30% modulation), and selectivity at 6 dB at 4 kHz, 60 dB at 20 kHz. Included are spare fuses, instruction manual, and FCC license application. Measures 6.3"D x 5.5"W x 1.97"H (16 cm x 14 cm x 5 cm) and weighs 2.5 lb. (1.1 kg). \$159.95.

CIRCLE NO. 74 ON FREE INFORMATION CARD

## RF/AF ANALYST

The Nikoltronix RF/AF Analyst is a solid-state, battery-powered servicing test instrument that combines a crystal-controlled r-f generator, a 400-Hz sine-wave generator (which can modulate the r-f unit), and an r-f and a-f signal tracer. The r-f generator contains a crystal tester with LED readout, covering the 3.5- to 90-MHz range. The r-f module is also available with built-in crystals providing up to 12 fixed frequencies spanning the same frequency range. The signal tracer section has a high-input-impedance probe and can trace signals riding on dc levels up to 500 V, according to Nikoltronix. \$129.45.

CIRCLE NO. 75 ON FREE INFORMATION CARD

## BURWEN LOW-NOISE PREAMPLIFIER

The Model SP5200 Low-Noise Stereo Preamplifier by Burwen Laboratories has a claimed dynamic range of 115 dB at 0 dB gain, a small-signal frequency response of



20 to 20,000 Hz  $\pm 0.1$  dB, and a THD of 0.05% max. from 20 to 10,000 Hz. Output is dc coupled, delivering 2.5 V (rated), 8 V max. Burwen states that the use of FET input circuitry and selectable feedback loop provides quiet (90 dB below 10-mV input) performance in the open 47k phono input mode. A monitor is provided, as well as a turn-on/turn-off silencer and short-circuit protection. A total of 33 input and output jacks are available, including a center channel output. One unswitched and four switched ac outlets are built-in, which can handle a total of 1000 W. Matched slide pots form the volume control.

CIRCLE NO. 76 ON FREE INFORMATION CARD

## PANA VISE "THIRD HAND"

Builders of projects involving pc boards and other small, fragile components will find PanaVise's Model 396 the equivalent of a "third hand" at their workbenches. Offered with various bases and heads, all interchangeable, the basic unit tilts, turns, and rotates to any position while holding delicate parts gently yet firmly.

CIRCLE NO. 77 ON FREE INFORMATION CARD

## PIONEER "PRO" TURNTABLE

A professional direct-drive turntable featuring an automatic tonearm return and an S-shaped low-mass tonearm with low-capacity cable has been introduced by Pioneer as its Model PL-55X. The platter is driven by a brushless dc servo-controlled motor and operates at 33 $\frac{1}{3}$  and 45 rpm (changed electronically). Speed can be adjusted to  $\pm 2\%$ . Wow and flutter are 0.05%

POPULAR ELECTRONICS

Wrms and S/N ratio exceeds 58 dB, according to the manufacturer. It accommodates cartridges weighing 4 grams (min.) to 14 grams (max.). In addition, the turntable includes an anti-skating device, lateral balancer, plug-in headshell, and stylus-pressure direct-readout counterweight. Wood base measures 18 29/32" W x 16 5/32" D x 7 9/32" H (48 x 41 x 18 cm). \$249.95

CIRCLE NO. 78 ON FREE INFORMATION CARD

### HARTLEY STEREO SPEAKER SENTRY

The latest version of the Hartley Stereo Speaker Sentry is an electronic control that



limits power applied to a speaker at a pre-set level between 5 and 200 W rms. If the power limit is exceeded, the input signal to the amplifier is automatically reduced to bring the output to the desired level. According to Hartley, it is self-powered, expends milliwatts of the amplifier output, and acts faster than a common fuse, responding to an overload in a fraction of a millisecond. \$35.00.

CIRCLE NO. 79 ON FREE INFORMATION CARD

### UNGAR SOLDERING STATION

A portable, rechargeable soldering station (No. 194), made by Ungar, incorporates a rechargeable nickel-cadmium battery. The lightweight pencil iron features an indicator light, operating trigger control with interlock "off" switch, and built-in lamp. It accepts two interchangeable tips. The high-impact plastic charging holder has a tip-cleaning sponge receptacle and is rated at 120-V ac input: 3.2-V ac at 120 mA output.

CIRCLE NO. 80 ON FREE INFORMATION CARD

### TEAC MULTICHANNEL MIXER

Teac's new multichannel (6-in, 4-out) mixer, Model 2, has low- and high-cut fil-



## NOW there's a quick, easy way for you



### to learn . . . review . . . improve your understanding of Electronics fundamentals.

That's right. A new "audio visual" learning experience in basic Electronics and Electricity. Quick. Easy. And it's fun, too.

Four pre-recorded cassette tapes take you right into a classroom in Electronics. Eleven class sessions in all . . . it's just like you are there! You'll listen to a CIE instructor and his students explore AC/DC, transistors, circuits, cells, batteries, IC's, electronic symbols and other meaningful subjects.

As you listen, you'll follow along through six instruction manuals that contain over 150 easy-to-understand illustrations, photos, and diagrams. Sit back, relax, and learn.

Nearly 3 hours of recorded, programmed instruction . . . designed and developed to help you grasp the all-important basic theories and applications of Electronics and Electricity.

Order your exciting Audio Visual "Class in Electronics" TODAY and qualify for this special Bonus Offer.

### BONUS OFFER

Order now and receive a one-year FREE subscription to the bi-monthly *CIE Electron* newspaper. Packed with timely, thought-provoking electronics articles — new developments — service tips — job opportunities. Free with each order.

**You must be completely satisfied or return the material within 10 days for a complete — no questions asked — refund.**

**RUSH** me your no-risk Audio Visual program that combines sight and sound in a new, exciting learning experience and put me down for a FREE one-year subscription to the *CIE Electron*.

Check One, please

- #01-122. Set includes instruction manuals, 4 recorded cassette tapes, binder/file. \$24.95 (Ohio Res. add 4½% Sales Tax)
- #01-124. Set includes Cassette Tape Recorder, 4 recorded cassettes, remote-control mike and stand, earphone, AC adapter, power cord, batteries, 6 instruction manuals, binder/file. \$49.95 (Ohio Res. add 4½% Sales Tax)

Enclosed is my . . .

Check  Money Order BC-13-75

Print Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_ Apt. \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_


## CIE Bookstore

1776 E. 17th Street • Cleveland, Ohio 44114  
Educational/Entertainment values by mail  
Subsidiary of Cleveland Institute of Electronics, Inc.


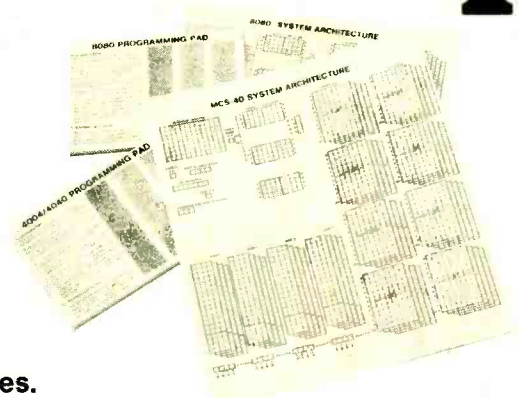
# design is a snap.

have made this six-volume collection the most valuable and meaningful series ever published on microcomputer design. The books combine the most effective methods of programmed instruction with the entire gamut of essential information vital to the designer of a micro-based system. You begin with the ABC's of microcomputers and go through a virtual post-doctoral course... **and the unique, self-testing programmed learning lasis course enables you to understand and absorb every bit of the information every step of the way through the six volumes.**




The lasis course gives you more than 700 pages of detailed, illustrated microcomputer information—including more than 1,700 self-tests you use to evaluate your progress—plus programming and design aids that make the design of practical systems very, very easy for you.

Specific details are provided on four of the industry's most versatile microcomputers—the 4004, 4040, 8008 and 8080 from Intel Corporation—but the basic design information will apply to any and all microprocessors. The six volumes you receive with the course are: 1) BINARY ARITHMETIC; 2) MICROCOMPUTER ARCHITECTURE; 3) THE 4-BIT MICROCOMPUTER; 4) THE 8-BIT MICROCOMPUTER; 5) ASSEMBLERS AND PROTOTYPING SYSTEMS; and 6) 8-BIT ASSEMBLERS AND COMPILERS. Plus, this detailed course provides you with two programming pads and two simplified design aids so you may quickly and easily develop both 4-bit and 8-bit microcomputer systems. Use the coupon below to order your course from lasis, Inc., 110 First St., Suite PE Los Altos, California 94022

course are: 1) BINARY ARITHMETIC; 2) MICROCOMPUTER ARCHITECTURE; 3) THE 4-BIT MICROCOMPUTER; 4) THE 8-BIT MICROCOMPUTER; 5) ASSEMBLERS AND PROTOTYPING SYSTEMS; and 6) 8-BIT ASSEMBLERS AND COMPILERS.

Plus, this detailed course provides you with two programming pads and two simplified design aids so you may quickly and easily develop both 4-bit and 8-bit microcomputer systems. Use the coupon below to order your course from lasis, Inc., 110 First St., Suite PE Los Altos, California 94022

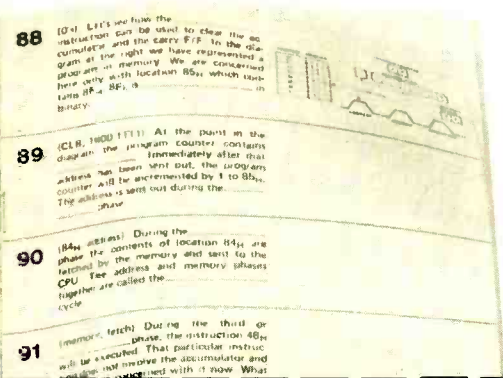Special introductory price on this remarkable new course is just \$99.50... and if it isn't everything we say it is or even more, return it within 15 days for a full refund!



**Order before Nov. 30, and you'll save a full \$25 on the Programmed Learning Course on Microcomputers! In addition, all introductory orders will include a bonus seventh volume, the Microcomputer Applications Handbook!**

(After Nov. 30, 1975 price for the complete lasis course will be \$124.50, plus \$2.50 for postage and handling.)

Here's my check or money order (no cash, please). **RUSH** my 6-volume Programmed Learning Course on Microcomputers, including the bonus Applications Handbook and programming aids, to the address below. **HURRY!**

- Send one complete course for \$99.50 in U. S. funds. My payment is attached. (California residents, please add \$5.97 State sales tax.)
- Send me information by return mail on quantity discounts.

ALLOW 15 DAYS FOR DELIVERY IN THE U. S. AND 6 WEEKS FOR DELIVERY OUTSIDE THE UNITED STATES.



Mail today to: lasis,  
110 First St. Suite PE  
Los Altos, California 94022

**You can use your BankAmericard or Master Charge, too!**

CHARGE MY ORDER TO THE CREDIT CARD NO. BELOW:

BankAmericard No. \_\_\_\_\_

Master Charge No. \_\_\_\_\_

For Master Charge, add 4-digit number immediately above your name on the card. It is \_\_\_\_\_

HERE'S MY SIGNATURE \_\_\_\_\_

(Sign here if credit card charge)

Credit card expiration date \_\_\_\_\_

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

ORGANIZATION \_\_\_\_\_ MAIL STOP \_\_\_\_\_

CITY/STATE/ZIP \_\_\_\_\_

# now **9** midget driver sets BY Xcelite®



## FOR DOUBLE DUTY ON DOZENS OF POPULAR SCREWS AND NUTS



Three new assortments have joined Xcelite's family of "Compact Convertibles." Each an Xcelite "original." No-where will you find such a variety of sizes and types in a midget set, for driving slotted, Phillips, Allen, Scrulox®, hex, and clutch head screws. And hex nuts.

All of professional quality, precision made of finest materials. All doing "double duty" with torque amplifier handle that slips over color-coded midget tools for longer reach, greater driving power. Each easily identifiable on the bench or in the service kit thru Xcelite's exclusive, optically clear, plastic "show case" that closes securely with positive snap-lock.



### NEW!

**PS130** — 3 slot tip, 2 Phillips screwdrivers, 5 nutdrivers

**PS140** — 4 slot tip, 3 Phillips screwdrivers, 3 nutdrivers

**PS6** — 3 slot tip, 3 Phillips screwdrivers

**PLUS** — PS88, PS120, PS7, PS89, PS44, and PS-TR-1 with varying selections of screwdrivers and nutdrivers.



Ask your local distributor or write . . .

## Weller-Xcelite Electronics Division



The Cooper Group

P. O. BOX 728,  
APEX, NORTH CAROLINA 27502


CIRCLE NO. 63 ON FREE INFORMATION CARD

ters plus panning on each input, as well as cue out, bus in, and accessory send/receive patch points. Push/push channel assignment buttons are color-coded to correspond to the output buses. A signal from any input channel can be assigned to any or all output channels. When more than one channel is assigned, Pan is engaged, giving the recordist the ability to shift around the acoustic image. The Model 2 features a straight line fader as the level controls for the input channels, while a master fader controls the output levels. The MIC IN accepts a 1/4-inch phone plug, and LINE IN accepts a standard phono plug. LINE OUT serves as the program bus out, and AUX OUT acts as an additional line output in parallel with the main line output. \$299.50.

CIRCLE NO. 81 ON FREE INFORMATION CARD
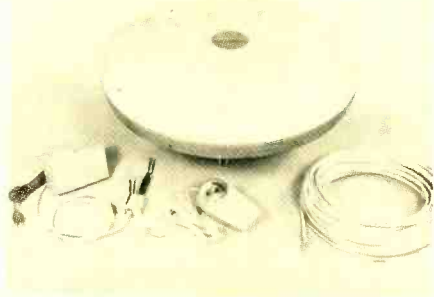
### RCA MINI-STATE TV ANTENNA

RCA's new Mini-State TV Antenna System includes a 60-ft. length of 75-ohm coaxial cable and three rotor wires within a single outer jacket. The system's built-in rotor




and amplifier enable it to pick up signals from stations up to 35 miles away, according to RCA. A hand-held remote control with lighted direction indicator lets the viewer adjust the antenna's directivity for best reception. The Mini-State is housed in a compact plastic case measuring 21" (53.3 cm) in diameter and 6" (15.2 cm) thick. The antenna system can be mounted outdoors or indoors. \$79.95.

CIRCLE NO. 82 ON FREE INFORMATION CARD
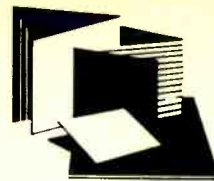
### WIK-IT DESOLDERING WICK

"Wik-It," developed by the Wik-It Electronics Corp., is a chemically treated wire braid, which draws up molten solder through capillary action. After the solder has been removed from the connection, the user snips off the saturated piece of Wik-It, and draws out another length from its spool. Wik-It comes in various diameters to suit small IC and pc-board work, as well as tube and chassis applications. The wick is packaged in lengths from 5 to 100 feet. Price of a 5-foot roll of Wik-It varies from \$1.59 to \$1.79 according to braid diameter. Address: Wik-It Electronics Corp., 140 Commercial St., Sunnyvale, CA 94086



## New Literature

### LAFAYETTE 1976 CATALOG

"The Electronics Shopping Center" is the title of Lafayette's catalog for 1976, and it does contain listings of just about every electronic item imaginable. Included are hi-fi components and accessories, CB and other communication equipment, antennas, tools, musical instruments, calculators, watches, vacuum tubes, solid-state devices, etc. Also, the Lafayette and Criterion brands of their own products. Address: Lafayette Radio Electronics, 111 Jericho Turnpike, Syosset, NY 11791.

### JENSEN LOUDSPEAKER SYSTEM CATALOGS

A new series of catalogs is available from Jensen Sound Laboratories. The catalog for Models 1 through 6 contains specifications, illustrations, and features of the Jensen high-fidelity line. A separate full-color catalog describes the Jensen Serenata™ sound system. Various catalog sheets describe the Dynamount™ mobile high-fidelity unit, the full mobile speaker line, and the professional sound line. Address: Jensen Sound Laboratories, 4310 Trans World Road, Schiller Park, IL 60176.

### MOBILE COMMUNICATIONS BROCHURE

A new 16-page, full-line brochure from Motorola Communications describes mobile communications equipment. "Vehicular Communications" covers the latest Motorola offerings in the mobile two-way field, including car telephones, data communications equipment, and mobile radios. Among the equipment highlighted are MICOR/Systems 90 group which provides selective signalling, multi-channel monitoring, and voice scrambling; the MCR-100 motorcycle radio; and the PULSAR mobile telephone. Address: Motorola Communications and Electronics, Inc., 1301 E. Algonquin Road, Room 4420, Schaumburg, IL 60172.

### TAB BOOKS CATALOG

More than 340 current and forthcoming technical books are listed in Tab Books' new 1975 catalog. Among the areas covered are amateur radio, audio, broadcasting CB and mobile radio, FCC license study guides, equipment servicing, electronic devices, and hobby and experimentation. Address: Tab Books, Blue Ridge Summit, PA 17214.


POPULAR ELECTRONICS



Now—solve your workbench problems faster with the help of this comprehensive, fully illustrated
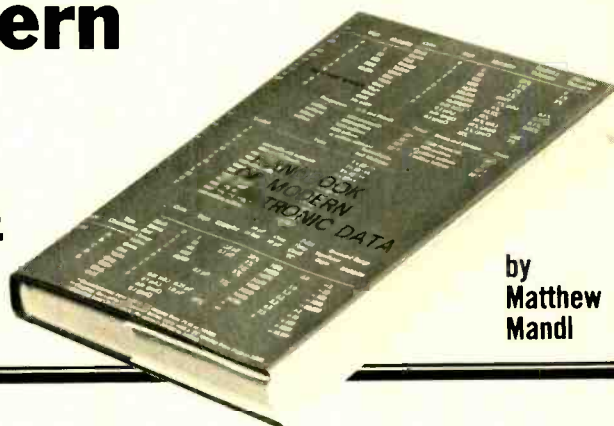
# Handbook of Modern Electronic Data

This \$14.95 volume is yours for just **\$1.98** when you enroll in an obligation-free trial membership in the Electronics Book Service. And there's no obligation to ever buy a minimum number of books!



by  
Matthew  
Mandl

This book—truly a volume no electronics workbench should be without—is typical of the practical selections offered to members of the *Electronics Book Service*. Although it is selling actively at its list price of \$14.95, we have arranged for you to receive a copy for just \$1.98, together with an obligation-free, trial membership in this unusual book club.

“Obligation-free” means what it says, and that’s why the *Electronics Book Service* is unusual. There are *NO* minimum purchase requirements. Once you have paid \$1.98 for your copy of the *HANDBOOK OF MODERN ELECTRONIC DATA*, you are under no obligation whatsoever to purchase any further selections offered to you.

With this book on your workbench, you’ll save hours by letting it serve as your main reference. All the information you need is there. Just look in the index, flip to the subject you want, and you’re guaranteed of finding the techniques you need for faster, easier design and analysis of circuits, switches, relays and many other electronic units.

Here are 274 pages of accurate, up-to-date data that the practicing technician/engineer uses constantly—BASIC EQUATION, EXPLANATIONS OF CIRCUITRY, TABLES, GRAPHS, SOLID-STATE THEORY, and many other informational items—including data on LASERS, HOLOGRAMS, ANTENNAS, COLOR CODES, SYMBOLS, VECTORS, PHASE FACTORS, UNIT SYSTEMS and the INTERNATIONAL SYSTEM OF UNITS.

And it’s all indexed and cross-indexed so that you can find what you’re looking for *in seconds!*

To make this vital information *easy for you to find*, the author has grouped the topics in related categories. For example, in the first chapter Matthew Mandl groups descriptions of fundamental units, terms and their appropriate mathematics.

Here, you’ll quickly find what you need to know about capacitance, prefix values, hertz, units of current and voltage, wavelength, the coulomb, Ohm’s Law, magnetic properties, inductance, rectangular notation, resonance, dynes, and Basic SI Units and Symbols—to name but a few of this chapter’s items.

And Chapter Two brings together various series-parallel circuit combinations—and their mathematics.

In each of these two chapters, you’ll find over 80 electronic and electric equations. These equations aptly illustrate the applied mathematics required in electronics and circuitry.

In the third chapter, Mandl takes up the fundamentals of transistors and tubes—including parameters for both junction transistors and field-effect transistors. Chapter Four covers transmission line and antennas.

The next two chapters put at your fingertips such essential information as common logarithms, trigonometric ratios, international atomic weights, exponential functions, Bessel functions, conversion and comparison tables, UHF television station allocations, television signal data, antenna gain and Z factors, thermal units, binary math—and even important data on lasers, masers, holograms and cryogenics.

And Chapter Seven gives you a wealth of ready-reference information on *basic circuitry*—including functional aspects, typical configurations and applications.

## Here is the practical efficient way in which the ELECTRONICS BOOK SERVICE operates—

1. When you enroll as a member, you receive—for only \$1.98 (plus postage and handling with tax where applicable)—your copy of *HANDBOOK OF MODERN ELECTRONIC DATA*. This is the *only* obligation you are committed to make.
2. You are under *no* obligation to accept any minimum number of selections within any time limit. You can make as many or as few as you wish. And, you may resign at any time with no obligation once you have paid for your copy of *HANDBOOK OF MODERN ELECTRONIC DATA*.
3. On selections you do accept, your membership entitles you to a discount from the publisher’s list price. This discount is available to members only and provides you with substantial savings.
4. Every four weeks we’ll send you a free bulletin describing the current selection. If you want the selection, no action is required; you will receive it automatically. If you don’t want it, just return the card enclosed with the bulletin.
5. You have at least 10 days to decide whether you want the selection or not. Return the card so we receive it no later than the date specified. If you don’t have 10 days to answer and receive an unwanted selection, return it *at our expense*.
6. Each bulletin also describes a number of alternate or additional selections, also available to you at the special discount price for members.

The meter ranges, color codes and symbols frequently used by technicians and engineers make up the contents of Chapter Eight. The last chapter discusses and illustrates vectors and three-phase fundamentals in full detail.

Yes, in this one comprehensive, fully illustrated handbook are the answers to practically every question you might have about the circuitry and applications, ratings and characteristics of transistors, semiconductors, IC’s, antennas, amplifiers and just about any other piece of equipment.

And, remember, the *Electronic Book Service* has *NO* minimum purchase requirements as do many book clubs. Once you have paid \$1.98 for your copy of the *HANDBOOK OF MODERN ELECTRONIC DATA*, you need purchase no further selections.

So why delay? Mail the coupon below to get your copy of the handbook of *MODERN ELECTRONIC DATA* for only \$1.98—and to receive all the benefits of membership in the *Electronics Book Service* on a RISK-FREE trial basis. Fill out and mail your coupon right now.

### ELECTRONICS BOOK SERVICE

Dept. 6651-M1(8)  
Englewood Cliffs, New Jersey 07632

Please enroll me in Electronics Book Service on a risk-free trial basis. I am to receive all announcements, free of charge, and will be entitled to full privileges as a Member without obligation to buy any specific number of club selections. As my first selection under this trial membership, send me the *HANDBOOK OF MODERN ELECTRONIC DATA* for only \$1.98.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

# Build this set...



# And build your career in electronics at the same time.

You build and keep a *future* when you learn electronics the ETI way.

“Building” is a key word through all the 16 ETI electronics courses and programs. Whether your goal is to get into TV repair and service, get your FCC license, move into computers,



advance in your present job through learning solid-state

technology, or become an electronics draftsman... you build your tomorrow. You build a lot more than TV sets. You build a solid future in the field where—despite all recent changes in the economy—the action has to come.

You build that future on a foundation of learning that is useful... practical... step-by-step... hands-on.


You build it from the beginning by a special, simplified, building-block teaching system called *Autotext*, exclusive with Electronics Technical Institute, that makes learning fun. You keep building, combining hands-mind-equipment in the most practical way, so you can “talk shop” or present an idea *effectively*, but you can also *do the job*. You’ve learned by doing, and you gain all the confidence that comes with it.

You build with the concerned personal help of a licensed instructor who knows the subject and wants to know *you*. You build with the reputation of the school that began as the Marconi Institute back in 1909.

In many phases of building your technical know-how, you use specially developed Project Kits that move in a logical sequence, hands-on, from the first step through completion of basic units. There is no surer way to build solid electronics knowledge *and* your own confidence in what you can do.

And it’s simple to check it all out right now, with no obligation—and no salesman will call. All it takes to get the colorful new 44-page ETI Career Book is a card or coupon. If you like electronics, you’ll enjoy reading about it. You owe it to yourself to get the facts.

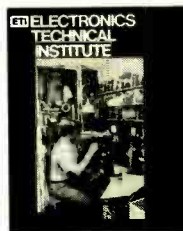The Career Book itself may be worth real money to you, as you make plans for your future and consider the many opportunities open to you through 16 different courses and programs in electronics.



To build a future in electronics, the first step is to send for your free ETI Career Book today!

## Electronics Technical Institute

Division of Technical Home Study Schools

Electronics Technical Institute, Dept. 2-473-105  
Little Falls, New Jersey 07424


Send me the Electronics Technical Institute Career Book.

Tell me how I can get ahead in Electronics through ETI. I've checked the fields of special interest to me.

- |   |   |                                    |   |
|---|---|------------------------------------|---|
| <input type="checkbox"/> TV/Audio Servicing | <input type="checkbox"/> Communications | <input type="checkbox"/> Computers | <input type="checkbox"/> Business and Engineering |
| Black and White                             | FCC License                             | Digital Electronics                | Electronics Fundamentals                          |
| Color                                       | Aircraft                                | Computer Technology                | Electronics Drafting                              |
| Solid-State                                 | Marine                                  | Computer Programming               | Industrial Electronics                            |
| CATV  | Mobile Two-Way                          |                                    | Advanced Electronics                              |
| Closed Circuit                              | Microwave                               |                                    | Industrial Instrumentation                        |
| Video Recorders                             |   |                                    | Electronics Technology                            |
| Radio                                       |   |                                    | Medical Electronics                               |
| Hi-Fi Stereo                                |   |                                    |   |

Check here for Veterans information.

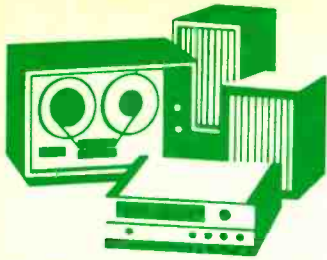Name \_\_\_\_\_ (please print)  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_



# Stereo Scene

By Ralph Hodges

## WHAT'S NEW FOR HI-FI IN 1976

**N**OW THAT the summer Consumer Electronics Show (CES) has come and gone, I've had a leisurely month or so to reflect on the new audio products seen there. In retrospect, I'm surprised at the emergence of a few trends I was scarcely conscious of noting as I toured the show.

**Integrated Amplifiers.** It's been years since anyone asked me for a recommendation on integrated stereo amplifiers, and I had made up my mind that this type of component was pretty much eclipsed by the ever-popular receiver (except for high-power aficionados, who would, of course, choose separate preamp

and power amp). What, then, were all those new integrated amplifiers doing at the CES? The answer to this question comes in several parts, gleaned from several sources. First, a few West Coast manufacturers, notably Marantz and SAE, are said to have discovered lively regional markets for integrated amps.

Second, for various good reasons the integrated amplifier enjoys much greater acceptance abroad; and, with few exceptions, almost all the major new units are of overseas origin.

Third, by design, the integrated amplifier seems to be eking out a new image for itself as a poor man's Phase Linear 700 or Marantz 500. Since the real beginning of the tran-

sistor era, an integrated amp was simply the control and power-output sections of the corresponding model in the manufacturer's receiver line, abstracted from the larger unit for the convenience of buyers with special needs or budgetary considerations. Today, more and more, integrated amplifier's are being marketed as the direct offspring of heftier preamp/power-amp ensembles, which they tend to resemble closely in features, construction, and styling. For example, Pioneer's SA-9900 integrated unit (110 watts per channel) actually preceded the introduction of the company's SPEC 1 preamplifier and SPEC 2 power amplifier (250 watts per channel) at the CES, although the three products obviously share a common design philosophy. Now Pioneer has three smaller integrated amps descended from the larger model.

Sansui's new amplifier line sprang up fully grown at the show. It comprises, in descending order, the BA 5000 power amplifier (300 watts per channel), the somewhat less powerful BA 3000, the CA 3000 preamplifier, and then the integrated amplifiers: the AU-20000 (170 watts per), AU-11000 (110 watts), and AU-9900 (80 watts). All these follow a common styling scheme that is distinct from the manufacturer's receivers and other product lines. Likewise, JVC, with a new 180-watt-per-channel power amplifier (the JM-S1000) and four-channel preamplifier (the JP-V1000), has combined the essential characteristics of the two into the JA-S20 integrated amplifier (120 watts per channel). Also, Fisher now has a large power amplifier, the BA-4500 at 150 watts per channel, a new preamplifier (the CA 4500), and three new integrated amplifiers to bask in their reflected glory.

The Rotel line lacks separate power amplifiers and preamplifiers, but it now includes an integrated amp, the 110-watt RA-1412, that looks like it logically might have evolved from larger units. On the other hand, the Luxman line, currently being reintroduced to the U.S., includes no receivers, but has four power amplifiers (300 down to 75 watts per channel), two preamplifiers, and three integrated amplifiers ranging from 110 to 75 watts per channel, as well as several separate tuners.

A little apart from this trend are the Pilot 225, a 25-watt-per-channel inte-



# AUTO-MAGIC® GLIDE-PATH® QUATRAVOX®



Model Shown: STA-225

**399<sup>95</sup>**

The Same Price it Was in July, '74

## How Come Only Realistic® Has These Features?

**Super Value!  
Save on this Complete  
STA-225 System**

A demonstration of these Realistic STA-225 features at any Radio Shack store will make you wonder when — if ever — the other "famous" brands will catch up. Maybe we just love audio-philos a little better? Auto-Magic gives you precision FM fine-tuning — automatically. Glide-Path slide controls let you see and feel volume and balance settings. And Quatravox lets you enjoy the added realism of synthesized 4-channel sound simply by adding a 2nd speaker pair. Power output is 50 watts per channel, minimum RMS at 8 ohms from 20-20,000 Hz, with no more than 0.5% total harmonic distortion. U.L. listed. #31-2058. There's only one place you can find it . . . Radio Shack!



**Save  
60<sup>80</sup>**

Reg. 659.80  
Only  
**\$599**

Realistic STA-225 Receiver • Two Optimus-1B Walnut Veneer Speakers • LAB-34 Changer, Base, and \$17.95-Value Cartridge



Use your credit card at participating stores

## Radio Shack®

A TANDY CORPORATION COMPANY  
OVER 3500 STORES • 50 STATES • 7 COUNTRIES



### FREE! 1976 CATALOG 568

See What's Really New in Electronics!  
164 Pages • Beautiful Color • Over 2000 Items

Mail to Radio Shack, P.O. Box 1052, Ft. Worth, TX 76101  
(Please print)

Name \_\_\_\_\_ Apt. # \_\_\_\_\_  
Street \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip

Retail prices may vary at individual stores and dealers.

grated model with no super-power brethren, the modest but handsome Harman/Kardon A-401 (20 watts), and the 85-watt Sherwood SEL-400, which was reportedly conceived as a companion to the SEL-300 digital-readout tuner. As for the rest of the new integrated amps, they look like an attempt to provide caviar on a salmon-roe budget, and as such they should be welcome to those with moderate power requirements who have felt technologically disenfranchised by the super-power stir.

**Moving-Coil Cartridges.** Do you remember how happy everyone was when moving-coil phono cartridges virtually disappeared more than ten years ago? Well, they're back, and with most of the same old practical problems. Stylus replacement still necessitates a factory return, and output voltages are still discouragingly low (although not quite so low as before), requiring the use of step-up transformers or special gain stages ahead of the preamplifier and causing no end of worry about hum and other forms of noise.

All the current crop of moving-coil pickups is made abroad; and when this new wave materialized a few years ago, it was easy to believe that it merely reflected the foreign manufacturers' difficulties in selling moving-magnet (or moving-iron or whatever) cartridges in the U.S., where Shure, Pickering, Stanton, Empire, and ADC hold strong basic patents on the design. However, Ortofon, which offers both types of pickup, has kept the faith over the years, continuing to offer moving-coil models for what are said to be good sonic reasons (in fact, a CD-4 moving-coil cartridge from Ortofon is working its way past the prototype stage). Best-known of the newer moving-coil manufacturers are Supex, Fidelity Research, and Denon, all of which are Japanese companies, with their products handled by only a few small distributors in this country.

Considering the short supply of these cartridges, their inconveniences, and their substantial prices, they seemed destined to remain exclusively esoteric products for the most passionately involved audiophiles. And that may still be the greatest notoriety they'll achieve, but be it noted that such comparative heavyweights as Yamaha, Sony and Great American Sound have acknowledged the existence of

these cartridges by providing amplifier gain to boost their outputs to usable levels. In particular, the CES brought the debuts of the Thaedra preamplifier from G.A.S. and Yamaha's new C-1 all-FET preamplifier, both with what are becoming called "head amps"—highly sensitive phono preamplifiers such as were heretofore only available as separate "pre-preamplifiers" from such small outfits as Mark Levinson Audio and one or two others. ("Head" is a name for a phono cartridge that is somewhat archaic in the U.S., but is still seen occasionally in British publications.) The Yamaha C-1, incidentally, is one of the most elaborate stereo preamplifiers now offered—a fitting companion to the B-1 FET power amplifier introduced earlier this year. Also, kit versions of Dynaco's new PAT-5 preamplifier can be wired to give an additional 6 dB of gain to the phono preamp—enough, it is said, to be usable with the higher-output moving coil pickups.

**Sub-Woofer.** You may recall sub-woofers from the last time they were in vogue, when hobbyists were busily converting spare garage and basement space into monster speaker enclosures with openings onto one wall (often occupying the entire wall) of the listening room. The latest sub-woofers are nowhere near as large. The offering from Dahlquist, in fact, is little larger than a bookshelf speaker system.

The sub-woofer concept is simple. It is a speaker system for low frequencies only, with high power-handling and output capability. It is intended to be simply a supplement to an existing, complete sound system and to augment the reproduction of frequencies below about 50 Hz, where the low-frequency resonance of many fine speaker systems occurs. Connection into the system is by means of a passive crossover network or an electronic crossover (requiring additional amplification facilities for the sub-woofer). The point is to thoroughly maul the listener with a deep, loud bass that his otherwise preferred loudspeakers (especially electrostatics or other dipole film-diaphragm types) might not be capable of generating without severe distortion. A convenience feature is also involved. Because low bass is non-directional (one way of saying that it's difficult to localize the source of low-

frequency energy), the main speakers can be small and placed according to the requirements of good stereo imaging. Then the sub-woofer can be located anywhere in the room (compatible with good acoustic practice) and still "join up" satisfactorily with the stereo image.


Besides Dahlquist, Hegeman offers a sub-woofer, and so does a new company called Bottom End. Others are becoming available on special order from several manufacturers. Note that two such units are not necessarily required. Low frequencies can be electronically "summed" and directed to one sub-woofer, which should be adequate for smaller rooms.

**Automatic Turntables.** Automatic turntables a new trend? Yes, considering that manual turntables have been the going thing for the past two years. Actually, automatic turntables with manual features are the big news, the important features being a belt-driven (offered by B.I.C. last year) or direct-drive platter (as in Technics' Model 1350). Technics still has the only direct-drive automatic, but Garrard has come up with two units that are belt-driven through an intermediate idler pulley. One of these units, the Z2000B, has the Zero Tracking Error tone arm. Also, there are two belt-driven automatics from BSR, and the striking Model 1249 of Dual.

**Three-Head Cassette Decks.** The surprising thing about three-head cassette decks is that there haven't been more of them since the successful introduction of the Nakamichi 1000 and 700 some time ago. So now welcome the Akai GXC-760D, with three motors as well as three heads, and a dual-capstan drive system to create a closed tape loop around the head nest. Akai will also offer several less expensive models, as will Fisher, which claims to have a three-head machine selling for less than \$250.

The one new three-head machine I've had a chance to examine in some detail is the Hitachi D-3500, which may be a genuine winner. A tricky problem with three-headers has been alignment between record and playback heads, which are generally spaced (because of the limited number of openings in the cassette housing) so that the tape is free to twist and skew between them enough to upset any hope of accurate

# The Monster

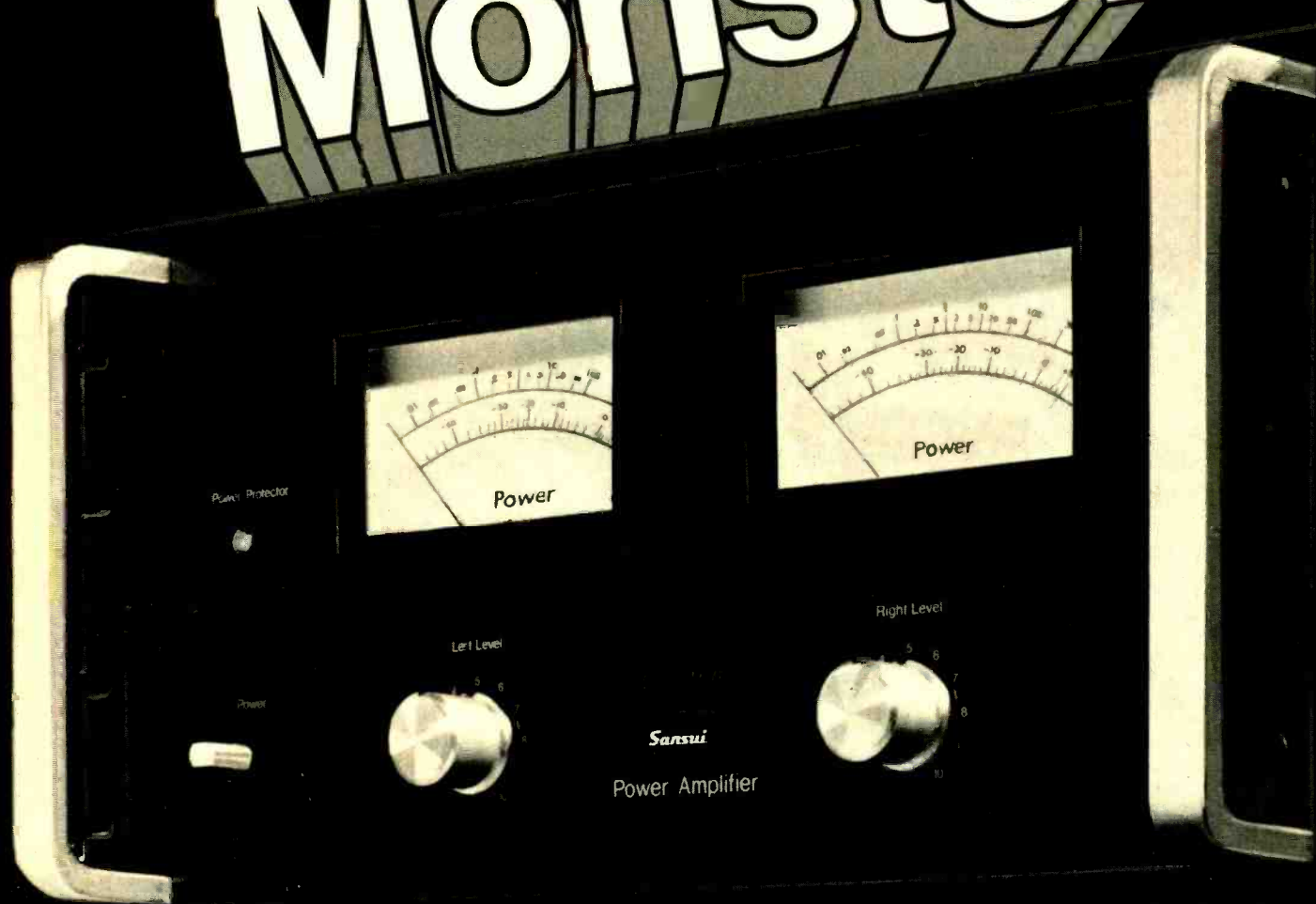

## The new BA 5000 Power Amplifier from Sansui

The most dramatic component in Sansui's new "DEFINITION" Series, the BA 5000 solid-state power amplifier is capable of 300 watts rms per channel into 8 ohms, both channels driven, from 20 to 20,000 Hz with no more than 0.1% harmonic distortion in the stereo mode. What's more, the BA 5000 can be strapped for mono operation to deliver 600 watts rms under the same conditions.

A true monster amplifier.

But that's not all. Unlike other solid-state amplifiers, the BA 5000 has a huge, laboratory-quality output transformer, enabling it to deliver rated power into 2, 4 or 8 ohms plus 25 volt line

output in stereo and 4, 8 or 16 ohms plus 70 volt line output in mono. A rating of 600 watts into a 16 ohm mono load with no more than 0.1% harmonic distortion, 20 to 20,000 Hz, is simply unprecedented in transistor equipment.

The "DEFINITION" series also includes the BA 3000, our Junior Monster, and the CA 3000, a very high quality, low distortion preamplifier.

For professionals, sophisticated audiophiles and monster lovers everywhere. See it and touch it if you wish at your nearest Sansui franchised dealer or write for complete literature.


**SANSUI ELECTRONICS CORP.**  
Woodside, New York 11377 • Gardena, California 90247  
SANSUI ELECTRIC CO. LTD. Tokyo, Japan • SANSUI AUDIO EUROPE S.A. Antwerp, Belgium  
ELECTRONIC DISTRIBUTORS (Canada) E.C.

*Sansui*

CIRCLE NO. 50 ON FREE INFORMATION CARD
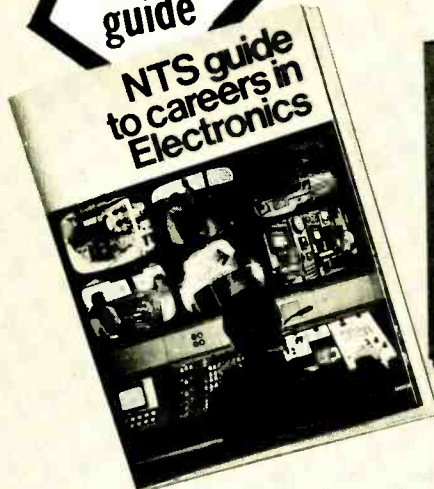
# The better the training the better you'll

Send for  
**FREE**  
illustrated  
career  
guide





NTS guide  
to careers in  
Electronics


IN-CIRCUIT TRANSISTOR TESTER

COMPU-TRAINER


TROUBLESHOOTER  
VOM

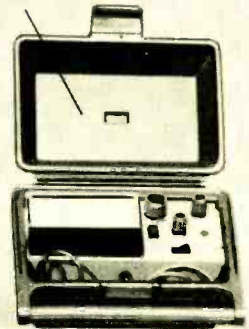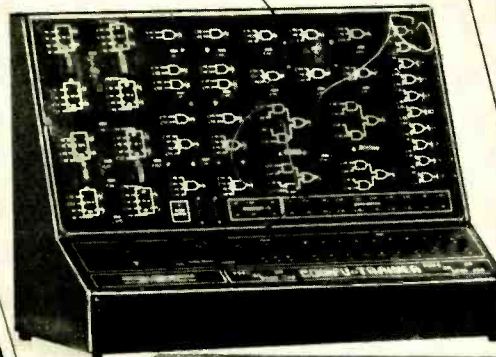

SOLID-STATE  
OSCILLOSCOPE

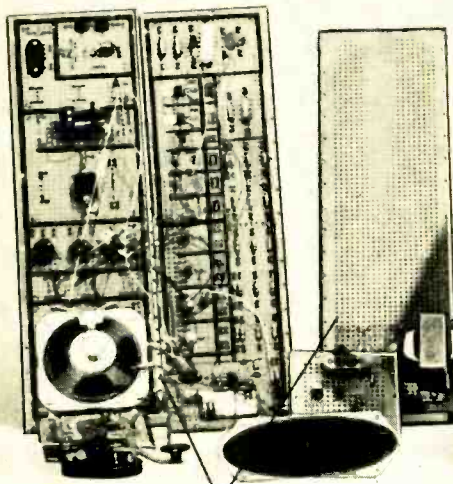

ELECTRO-LAB

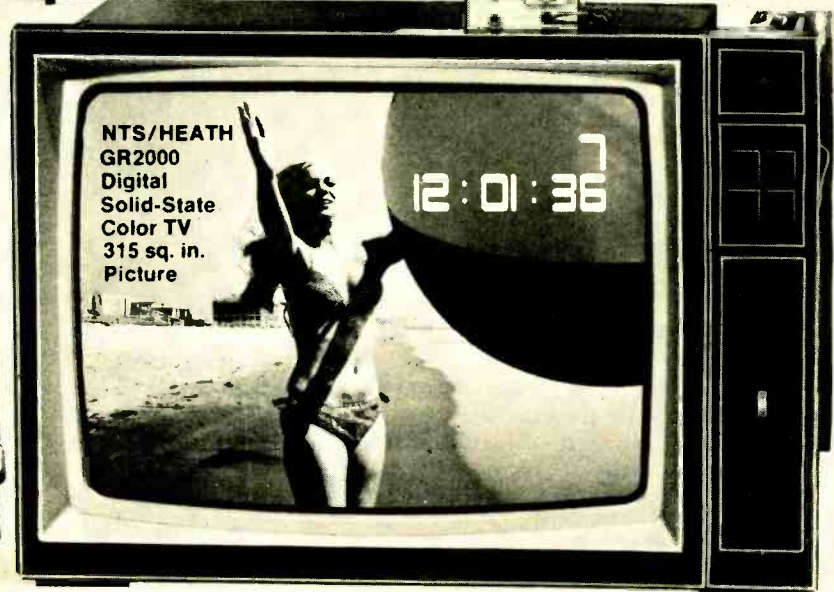

(Simulated TV Reception)

As an NTS student you'll acquire the know-how that comes with first-hand training on NTS professional equipment. **Equipment you'll build and keep.** Our courses include equipment like the **NTS/Heath Digital GR-2000 Solid State color TV** with first-ever features like silent varactor diode tuning; digital channel selection, (with optional digital clock), and big 315 sq. in. ultra-rectangular screen.

Also pictured above are other units — 5" solid state oscilloscope, vector monitor scope, solid-state stereo AM-FM receiver with twin speakers, digital multi-meter, and more. It's the kind of better equipment that gets you better equipped for the electronics industry.

This electronic gear is not only designed for training; it's field-type — like you'll meet on the job or when you're making service calls. And with NTS easy-to-read, profusely illustrated lessons you learn the theory behind these tools of the trade.


**Choose from 12 NTS courses** covering a wide range of fields in electronics, each complete with equipment, lessons, and manuals to make your training more practical and interesting.

**Compare our training; compare our lower tuition.** We employ no salesmen, pay no commissions. You receive all home-study information by mail only. All Kits, lessons, and experiments are described in full color. Most liberal refund policy and cancella-


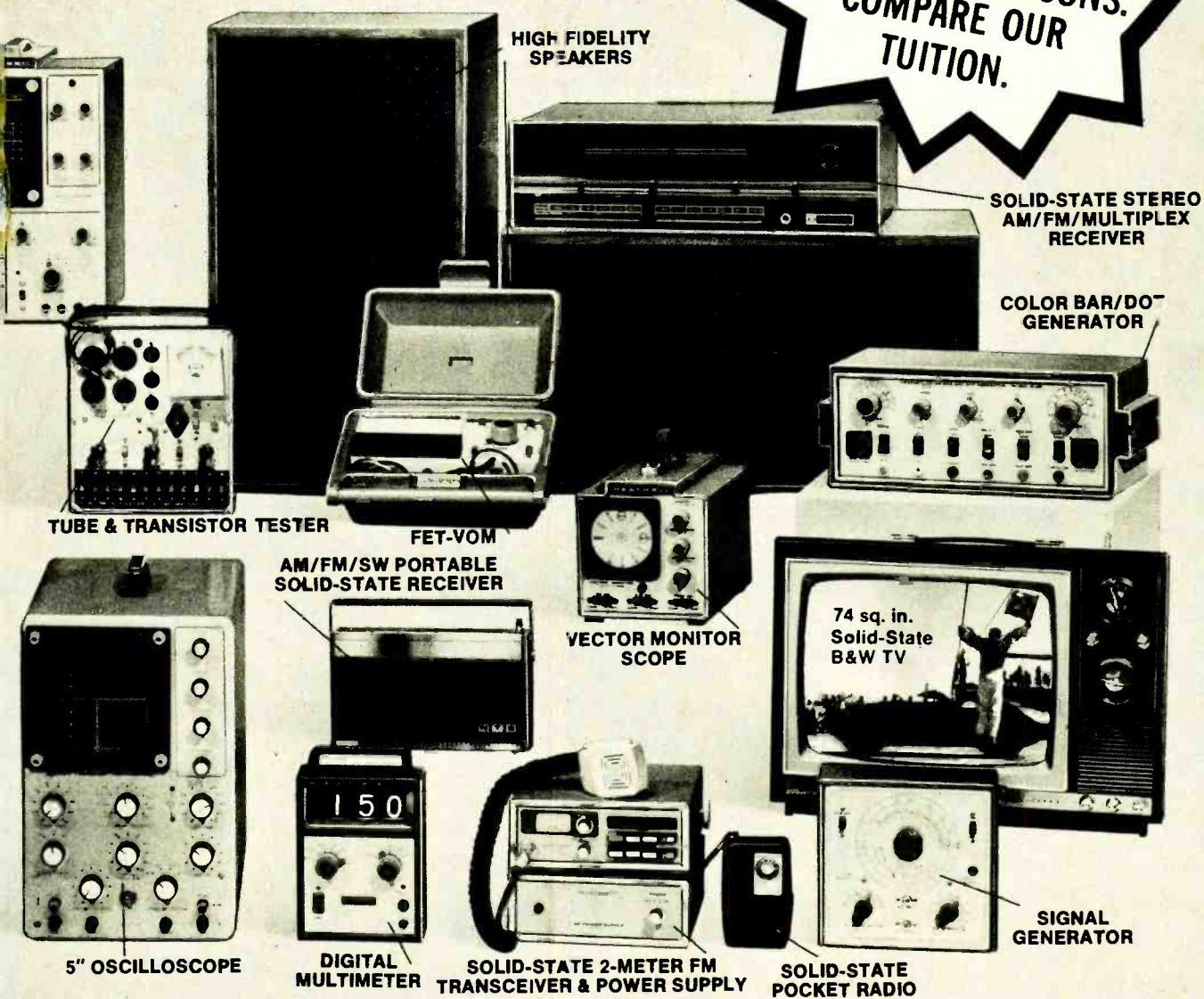
# and the equipment be equipped.

COMPARE OUR  
KITS AND LESSONS.  
COMPARE OUR  
TUITION.



tion privileges spelled out. Make your own comparisons, your own decision. Mail card today, or clip coupon if card is missing.

**NO OBLIGATION. NO SALESMAN WILL CALL**

APPROVED FOR VETERAN TRAINING  
Get facts on new 2-year extension

**NATIONAL TECHNICAL SCHOOLS**  
TECHNICAL-TRADE TRAINING SINCE 1905  
Resident and Home-Study Schools  
4000 So. Figueroa St., Los Angeles, Calif. 90037

**NATIONAL TECHNICAL SCHOOLS** Dept. 205-105  
4000 South Figueroa St., Los Angeles, Calif. 90037  
Please send FREE Color Catalog and Sample Lesson.  
NO OBLIGATION. NO SALESMAN WILL CALL.

Color TV Servicing  
 B & W TV and Radio Servicing  
 Electronic Communications  
 FCC License Course

Electronics Technology  
 Computer Electronics  
 Basic Electronics  
 Audio Electronics Servicing

NAME \_\_\_\_\_ AGE \_\_\_\_\_

ADDRESS \_\_\_\_\_ APT # \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_

Please fill in Zip Code for fast service \_\_\_\_\_

Check if interested in G.I. Bill information.  
 Check if interested ONLY in classroom training in Los Angeles.

# You can't experience today's high fidelity with yesterday's record changer.

Most high fidelity manufacturers watch each other to find out what's new. At Pioneer, we keep our eye on the audio enthusiast to find out what he wants. That's what keeps us ahead of all the others who are watching all of the others.

If you look at the sale of record playing devices — and we have — you'll see that sales of manual turntables are increasing four times faster than the sale of record changers. The reasons are clear: Record changers were designed a generation ago — for another generation. Designed for hours of uninterrupted background music at cocktail parties.

Today, your needs are probably different. When you listen to music, you listen to music. You're involved with the sound — and with your equipment. And only a manual turntable can offer you this level of involvement.

It's part of Pioneer's responsibility to understand and anticipate your changing needs. As a result, we now offer you the most complete line of professional manual turntables available. Each one of them delivers the highest level of performance, the most sophisticated features and the greatest value in its price category. And all of them have the precision engineering and quality that are part

of the Pioneer legend.

When you buy your next record player, shop smart. Consider what you want — and what you need. If you need performance, precision and quality — and want the involvement that only a professional turntable can provide — you'll get a Pioneer.

It's as simple as that.

U.S. Pioneer Electronics Corp.,  
75 Oxford Drive, Moonachie,  
New Jersey 07074.  
West: 15300 S. Estrella, Los Angeles  
90248 / Midwest: 1500 Greenleaf,  
Elk Grove Village, Ill. 60007 /  
Canada: S. H. Parker Co.

 **PIONEER**<sup>®</sup>  
when you want something better




PL-71 Direct-Drive Turntable

CIRCLE NO. 61 ON FREE INFORMATION CARD



*This new-generation scientific calculator features combinatorial, statistical, and probability functions, plus ten levels of addressable memory.*
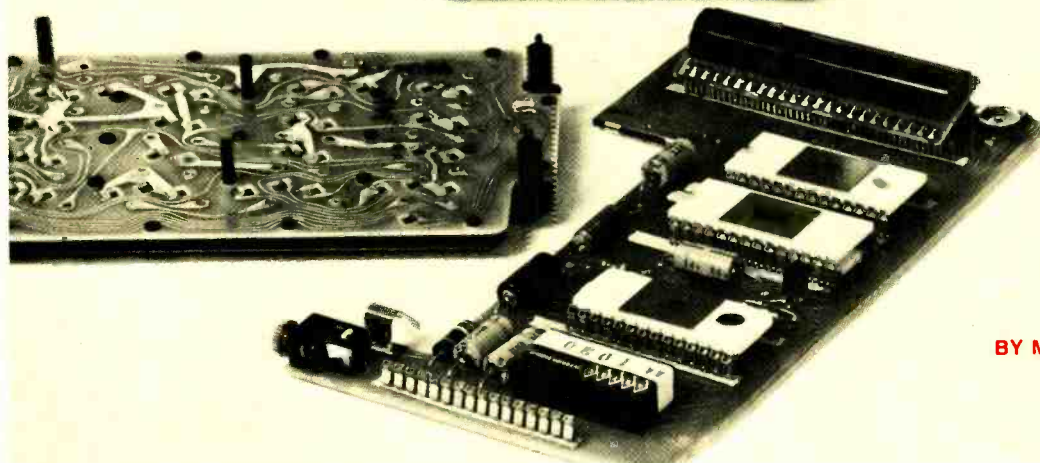
# NOW... BUILD THE 'SENIOR SCIENTIST' CALCULATOR



BY MARTIN MEYER

**T**HE simple four-banger electronic calculator can do little more than add, subtract, multiply, and divide. Since it was first introduced, however, we have welcomed at least two other "generations" of calculators—each with added capabilities. Now, we've taken another quantum jump in calculator capability with the "Senior Scientist." In addition to the functions that most scientific calculators can perform, (roots, powers, trigonometrics, summations, factorials, various conversions, nested parentheses, etc.) the Senior Scientist makes available combinatorial, statistical, and probability functions. Furthermore, it has 10 levels of storage memory that can be addressed independently in any order desirable. And it's a snap to build this

advanced hand calculator, whose kit price is just \$115.


**The Specifics.** There are 40 keys on the Senior Scientist's keyboard, divided into two groups of 20 keys each. The lower 20 keys are assigned the numbers 0 through 9, decimal point, arithmetic functions (+, -, ×, ÷, =), π, exponentiation ( $x^y$ ), and two-level parentheses functions. These are all single-function keys. Of the remaining 20 keys, 19 are assigned double-function status, while the remaining key (labelled F) serves the single function of shifting the dual-function keys to their alternate functions.

The calculator's LED display consists of a 12-place arrangement. The left-most place is reserved for indicating mantissa sign, calculation error,

degrees/radians status (degrees implied, bar segment on for radians), and low-battery condition. Ten digits of the display are for the mantissa, while two are for the exponent. The sign for the exponent is located between the mantissa and exponent displays. (Only the - sign is displayed for both mantissa and exponent; + is implied.) The calculator has a built-in battery saver feature that blanks the display after a preset (adjustable) time when no operations are being performed; this is indicated by the - sign for the exponent coming on. For easy identification, the exponent displays are half the size of the displays used for the mantissa and are shown as superscripts at the right.

The ability to solve complex and  
(Continued on page 35)

DIGIT DRIVERS

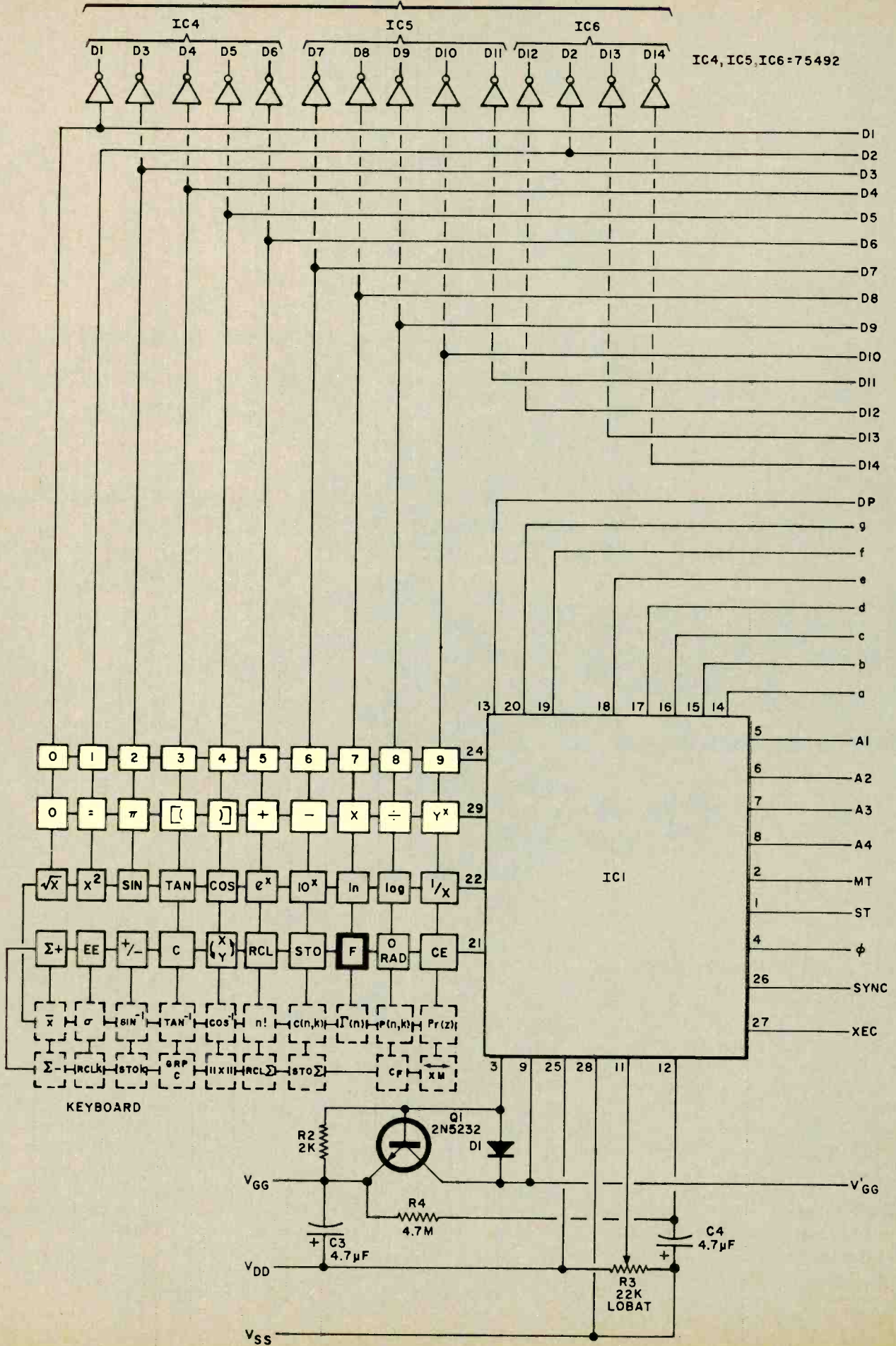

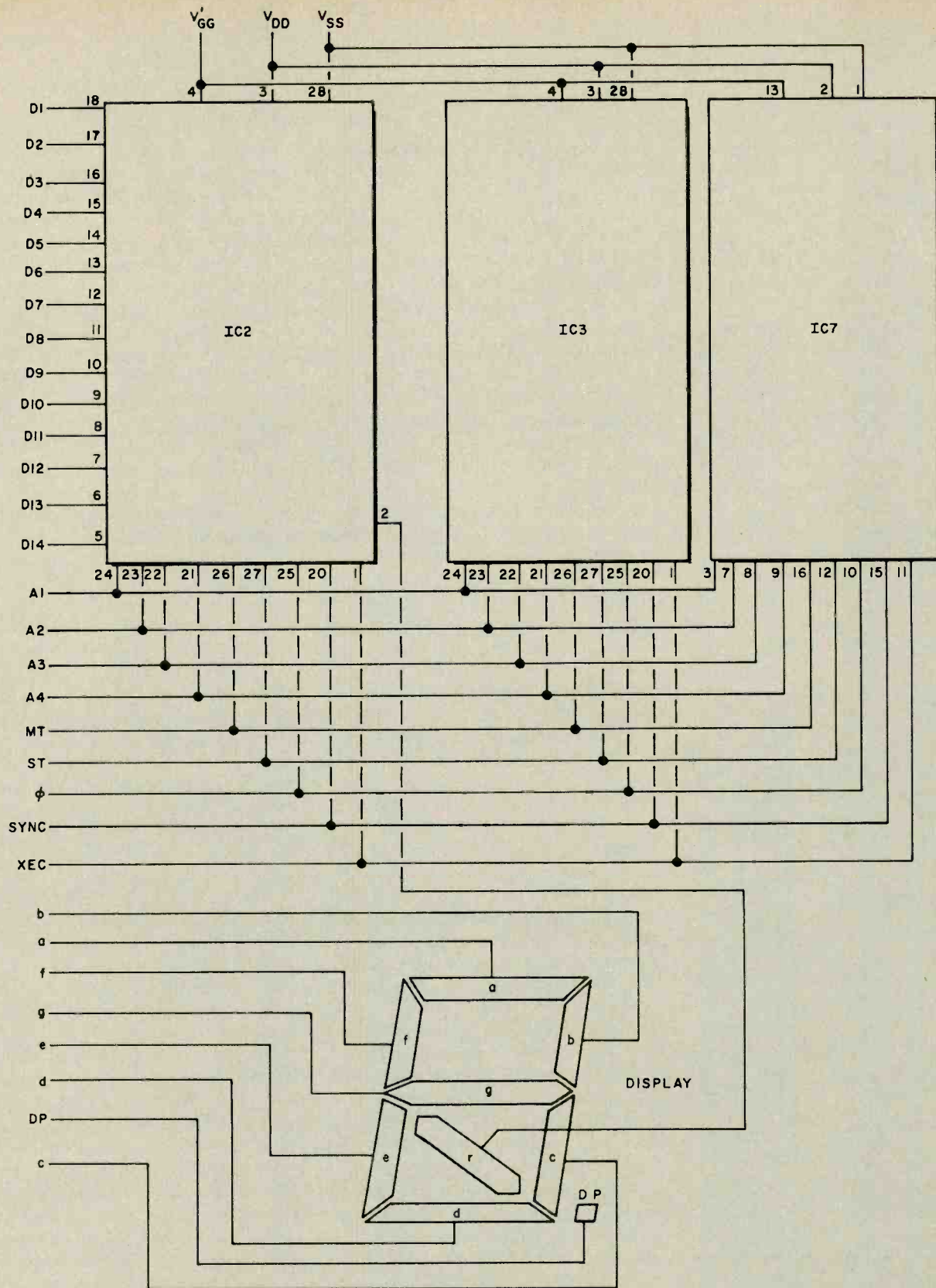


Fig. 1. Schematic of calculator is shown above and opposite. Unshaded keys are primary functions. Others are dual-function keys. Arrangement here is electrical—actual layout shown in photograph.

time-consuming mathematical problems is greatly enhanced by the calculator's two-level parenthetical capability. In stating an equation, in-

formation contained within the parentheses defines a specific variable. The solution of this variable is computed and retained. This allows a

problem to be entered as it is written or stated.

The 10 levels of memory greatly enhance the calculator's power, giving

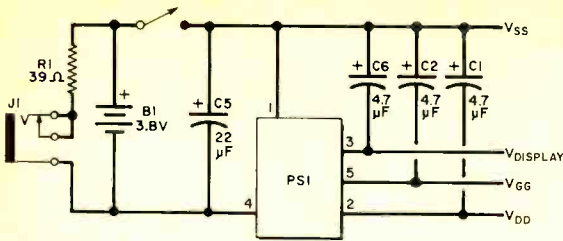


Fig. 2. Power supply uses a dc/dc converter to step up voltage.

a simple programming capability. Without the 10-level memory, the calculator has three memory levels (sum, sum-of-the-squares, index). The 10-level memory is a single IC that can be added at any time. It "plugs" into the holes provided for it on the pc board: no board changes are required. Entry into the 10 levels is accomplished by pressing STO and then the numeral (0 to 9) key that corresponds to the memory location desired. To recall a number from memory, simply press RCL and then the appropriate numeral key.

The Senior Scientist operates up to five hours on its built-in nickel-cadmium battery. The battery can be fully recharged in about nine hours, using the ac adapter/recharger supplied with the kit.

## PARTS LIST

- B1—3.8-volt rechargeable nickel-cadmium battery
- C1, C2, C3, C6—4.7- $\mu$ F, 20-volt electrolytic capacitor
- C4—56- $\mu$ F, 6-volt electrolytic capacitor
- C5—22- $\mu$ F, 10-volt electrolytic capacitor
- D1—1N914 silicon diode
- IC1, IC2, IC3—Mathematical integrated circuit set
- IC4, IC5, IC6—75492 hex inverter integrated circuit
- IC7—10-level memory integrated circuit
- J1—Miniature phone jack
- PS1—Dc/dc converter assembly
- Q1—2N5232 npn transistor
- R1—39-ohm, 1/8-watt resistor
- R2—2000-ohm, 1/8-watt resistor
- R3—20,000-ohm, linear-taper miniature pc potentiometer

Misc.—Keyboard; 14-digit LED display assembly; printed circuit board; case; ac adapter/recharger; Molex Soldercons (124); masking tape; solder; etc.

Note: The following items are available from Netronics Research & Development Ltd., 27 Eagle St., Spring Valley, NY 10977: complete kit of parts, including assembly/instruction manual; battery; ac adapter/recharger, soft carrying case, and 10-level memory IC (N2000MX) for \$114.95; same kit minus memory IC (N2000X) for \$99.95; keyboard (N201) for \$12; double-sided pc board with plated-through holes (N202) for \$5.50; 47A026 memory IC (IC8) for \$15; 75492 IC's for \$1.50 each; dc/dc converter assembly (N203) for \$5.80; mathematics IC set (IC1, IC2, IC3) (N204) for \$65 per set; 14-digit LED display assembly (N205) for \$19.50. New York state residents please add sales tax.

**Special Functions.** The standard arithmetic and scientific functions incorporated into the Senior Scientist need not be detailed here. Anyone who has used a second-generation calculator will be familiar with their use. However, the special advanced math functions in this calculator require a few words of explanation. These functions include the gamma [ $\Gamma(n)$ ]; combinatorial ( $n!$ ); permutation [ $P(n,k)$ ] and combinations and binomial coefficient [ $C(n,k)$ ]; normal probability [ $Pr(z)$ ]; statistical group operation (such as the summations  $\Sigma+$  and  $\Sigma-$ ), arithmetic mean ( $\bar{x}$ ), standard deviation ( $\sigma$ ), square-root-of-the-sum-of-the-squares ( $\| \times \|$ ); and factor reversal (transposing  $x$  and  $y$  terms) functions, and such group operations as STO  $k$ , RCL  $k$ , RCL  $\Sigma$ , and group (GRP) clear.

Combinatorial analysis is a powerful tool for obtaining the probabilities of complex events, binomial coefficients, combinations, and permutations. With the Senior Scientist, a few simple keystrokes let you evaluate the number of combinations of  $n$  different objects taken  $k$  at a time where the order of the resulting subsets does not distinguish one subset from another. The number of possible combinations of size  $k$  from group  $n$  is given by  $C(n,k) = n/[k!(n-k)!]$ , where  $k$  is the number stored in the group index and  $n$  is the number in the display.

The function  $C(n,k)$  also gives the binomial coefficients for the binomial expansion  $(a + b)^n = \sum_{k=1}^n C(n,k)a^{n-k}b^k$  and allows the binomial distribution functions where  $P$  is the probability that an event will occur in a single trial and  $q$  is the probability that the event will not occur in a single trial ( $q = 1 - P$ ). The probability that the event will occur exactly  $k$  times in  $n$  repeated trials is given as  $C(n,k)P^kq^{n-k}$ . This is known as the binomial probability function, since its terms for  $k = 0, 1, 2, 3 \dots n$  correspond to the successive terms for the binomial expansion.

The Senior Scientist also evaluates the number of permutations of  $n$  different objects taken  $k$  at a time where, from a group of  $n$  items,  $k$  items are

selected under conditions where the order of the resulting subgroups does distinguish one subgroup from another.

As one example of using combinatorial functions, evaluate the condition  $C(n,k)$ , where  $n$  is 7 and  $k$  is 4. Six keystrokes on the calculator give the solution as 35. Another example: how many different five-man teams can be formed from a pool of 16 people? Again, six keystrokes provide an answer of 4368. If you were to perform these problems with pencil and paper, even with the aid of a less advanced calculator, it would take you considerable time to reach the solutions. With the Senior Scientist, you can have the answer within seconds of stating the problem. (Note: We are not going into the details of the keystroke sequence to use here, as the instruction manual that comes with the IC's and calculator kit fully covers this subject.)

Normal probability functions are a thing unto themselves. Besides permitting you to determine the area of a Gaussian distribution curve, the probability functions in the calculator let you do some mundane things. For example, if you have an installation containing 4000 light bulbs, each of which has an average life of 1000 hours and a standard deviation of 200 hours, you can quickly calculate how many lamps can be expected to fail in the first 700 hours.

The Senior Scientist is capable of evaluating the arithmetic mean, standard deviation, and square root of the sum of the squares of any data. The data need be entered only once; thereafter, only single keystrokes are required to complete the calculations. Besides providing the arithmetic mean, the calculator can solve geometric mean, which is the type of average that is applied in situations that approximate a geometric progression, geometric growth, or exponential law (for example, population growth).

Solution of the harmonic mean is also simple. This mean is the measure of the central tendency to employ when dealing with rates or prices, such as mph, dollars/gallon, etc. An example of this type of problem is the old school math question that requires the student to determine the average speed of an airplane flying a square course that is 100 miles long on each side and where the speed is

(Continued on page 38)


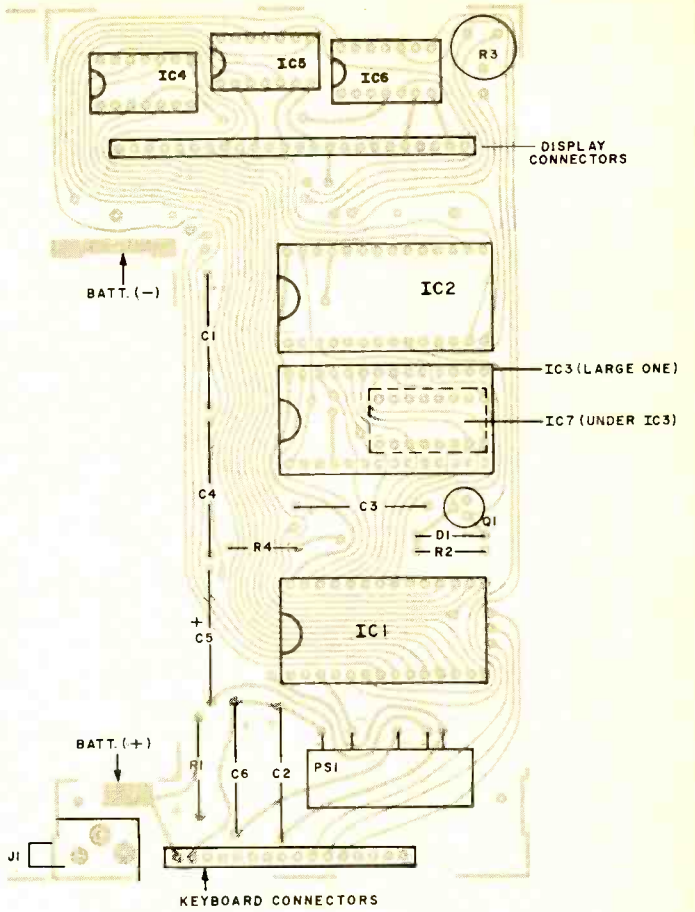
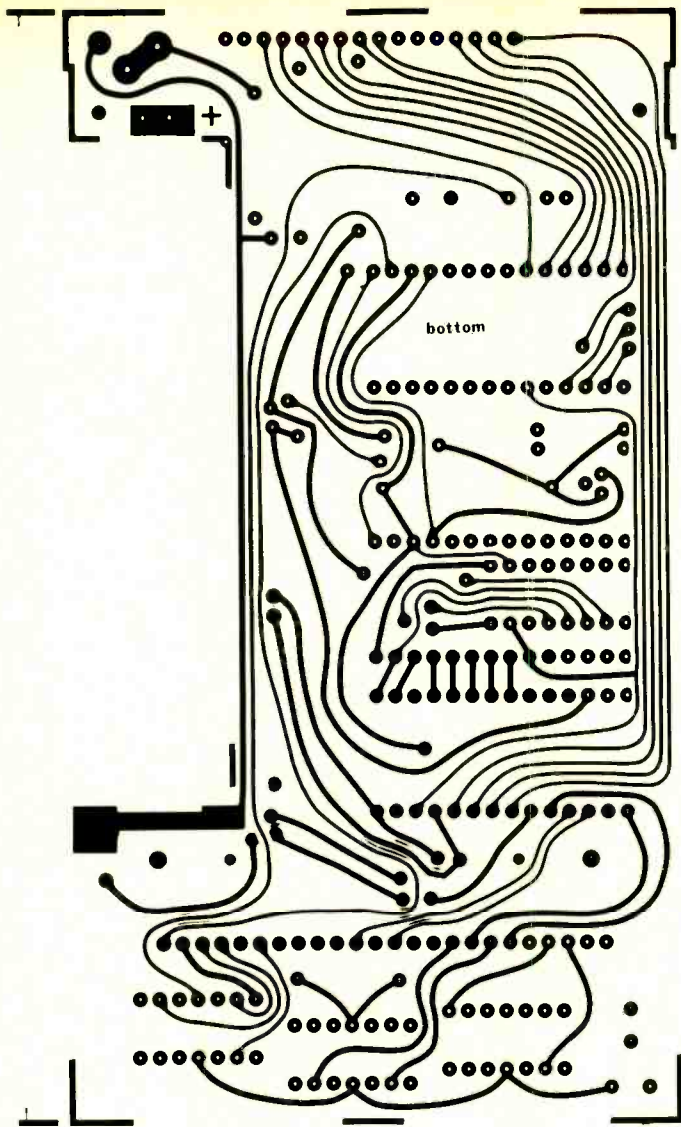


Fig. 3. Etching and drilling guides for the two sides of the printed circuit board are shown at left and below. Component placement is made as shown above on the top side of the board (below). Be sure to observe polarities and placement of IC's.

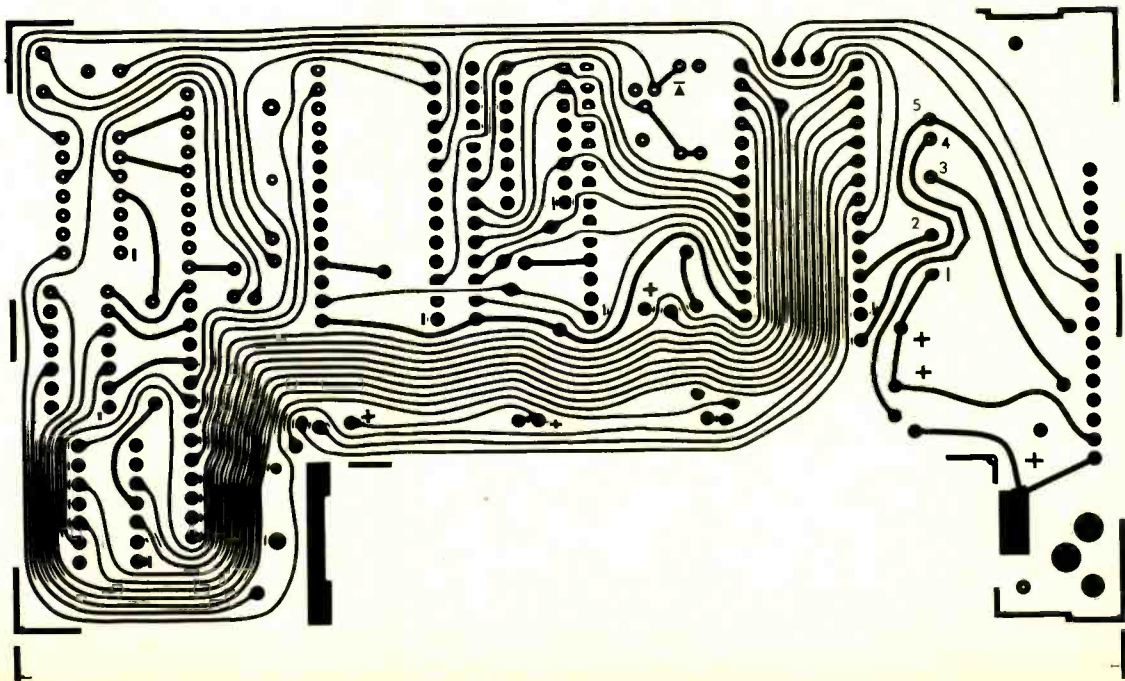

100 mph on the first leg, 200 mph on the second, 300 mph on the third, and 400 mph on the fourth. With a few simple keystrokes, the Senior Scientist provides an answer of 192 mph.

Last but not least, the calculator can evaluate the gamma function of all positive values of  $n$  where  $n \leq 2$ . The gamma function can be considered as a type of interpolation of the factorial function of nonintegral values of  $n$ .

With the features and functions incorporated into the Senior Scientist, it is not difficult to see that this is a calculator that will be highly useful for any science, technology, and mathematics major right on through college and beyond.

**About the Circuit.** The schematic diagram of the Senior Scientist's basic circuit is shown in Fig. 1. It would be pointless to attempt a stage-by-stage analysis of this circuit, especially since what goes on inside of mathematical integrated circuits *IC1* through *IC3* would require a manual to explain. Consequently, only the highlights are presented here.

The schematic shows a 40-key matrix for the keyboard. The unshaded boxes in the upper two rows are the single-function keys. The shaded boxes in the second two rows are the dual-function keys and are labelled with their primary functions. The secondary functions of these keys are illustrated by the phantom boxes in the last two rows. The F key, shown with a heavy outline box is responsible for shifting the two-function keys to their secondary functions.

Integrated circuits *IC1*, *IC2* and *IC3* form the special mathematics system that is responsible for all of the arithmetic and mathematics functions in the calculator. Integrated circuits *IC4*, *IC5*, and *IC6* isolate the display system from the low-power math IC's and provide the necessary drive current for the display. Last but not least, *IC7* is the 10-level memory system.

The power supply circuit for the calculator is shown in Fig. 2. This circuit employs an ingenious dc-to-dc converter that boosts the voltage available from battery *B1* to the level required by the calculator circuit. By employing this scheme, physical battery requirements are minimized and the calculator is kept to hand-held size.

**Construction.** There is no practical way to assemble the calculator without using a printed circuit board. The

board requires conductors on both sides. You can make your own board by using the actual-size etching guide shown in Fig. 3, but you will not be able to plate-through the holes as required. So, don't forget to solder component leads to both sides of the board.

Start assembly by soldering the battery clips (see Fig. 3 for component placement) to both sides of the board. Next, install *IC4*, *IC5*, and *IC6*. Solder their pins directly to the pads on the board. Do *not* use sockets. (The pin-1 pads for all IC's are indicated by short bars on the top of the board near the respective pads.) Install the capacitors, dc/dc converter, diode, power jack, potentiometer, and resistors.

Cut six 1½" (3.8-cm) lengths of ⅛" (3.2-cm) wide masking tape and press them onto the top of the board over the lead holes for *IC1*, *IC2*, and *IC3*. Press a 2½" (6.4-cm) length of the tape over the display board connector holes and a 2" (5.1-cm) length over the keyboard connector holes.

Break off a strip of 23 Soldercons and force their pointed ends through the tape and into the display connector holes. (Note: The hole at the far right is not used.) Solder the Soldercons to the pads on the board and carefully break away the connecting strip. Similarly, install 16 Soldercons at the bottom of the board for the keyboard and six sets of 14 Soldercons in the *IC1*, *IC2*, and *IC3* holes.

Before you remove the remaining IC's from their protective carrier, you must familiarize yourself with the following procedures to avoid damaging them by static electricity:

- Wear only anti-static clothing, such as cotton, when working with MOS devices. (Synthetics readily build up static charges.)

- Ground your work surface.

- Ground yourself; wrap a length of wire mesh around your wrist and terminate it at a cold water pipe or the grounding screw of an electrical outlet.

- Ground your soldering tip in a similar manner, but use heavy solid wire—not mesh—around the tip.

- Always install a MOS device immediately into its circuit after removal from its protective carrier and replace it in the carrier immediately after removal from the circuit.

- NEVER install a MOS device in, or remove it from, a circuit to which power is applied.

- Always install MOS devices last.

Once you have familiarized yourself with the proper procedures to use, remove *IC7* from its carrier and install it into place on the board, without using Soldercons. This done, install the remaining IC's.

Plug the display and keyboard assemblies (they come ready to use), into their respective connectors. When the keyboard is properly seated, two plastic posts on it drop into small holes in the pc board. The foam plastic on the back of the display board should be compressed against *IC4*, *IC5*, and *IC6*.

At this point, you can check out the calculator. Slip the battery into its connectors and turn over the calculator. Turn on the power; a 0, followed by a decimal point should come on. If not, the battery needs to be charged. Charge it, with the battery charger, for about an hour. (Note: If you operate the calculator at any time, *the battery must be installed.*)

Press C, 9, STO, 1, C, 5, STO, 5. The number 9 should now be stored in the second level of memory (0 is the first level) and 5 in the sixth level of memory. Now, press C, RCL, 1 (9 displayed), +, RCL, 5 (5 displayed), =; the display should now read 14.

Finally, press C, 8, Σ+, 5, Σ+, 3, Σ+, F, RCL; the answer displayed should be 16, which is the sum of 8 + 5 + 3. Set the power switch to OFF.


Potentiometer *R3* sets the point in the battery's charge condition at which the battery-low indicator (L) is displayed in the left-most digit. Set the pot to the center of its rotation initially. Then if you find that the L comes on too soon or doesn't come on soon enough, you can readjust the pot's setting.

To complete assembly, insert the bottom of the calculator assembly into the top half of the case and swing the assembly into place. It is properly positioned when the keyboard fits snugly into the case surround and a pair of plastic posts protrude through the bottom of the pc board. Thread a pair of small nuts onto the plastic posts to hold the assembly firmly in place. (It may be necessary to pre-thread the posts.) Insert the two lugs on the bottom of the back half of the case into the slots in the top half and snap the halves together.

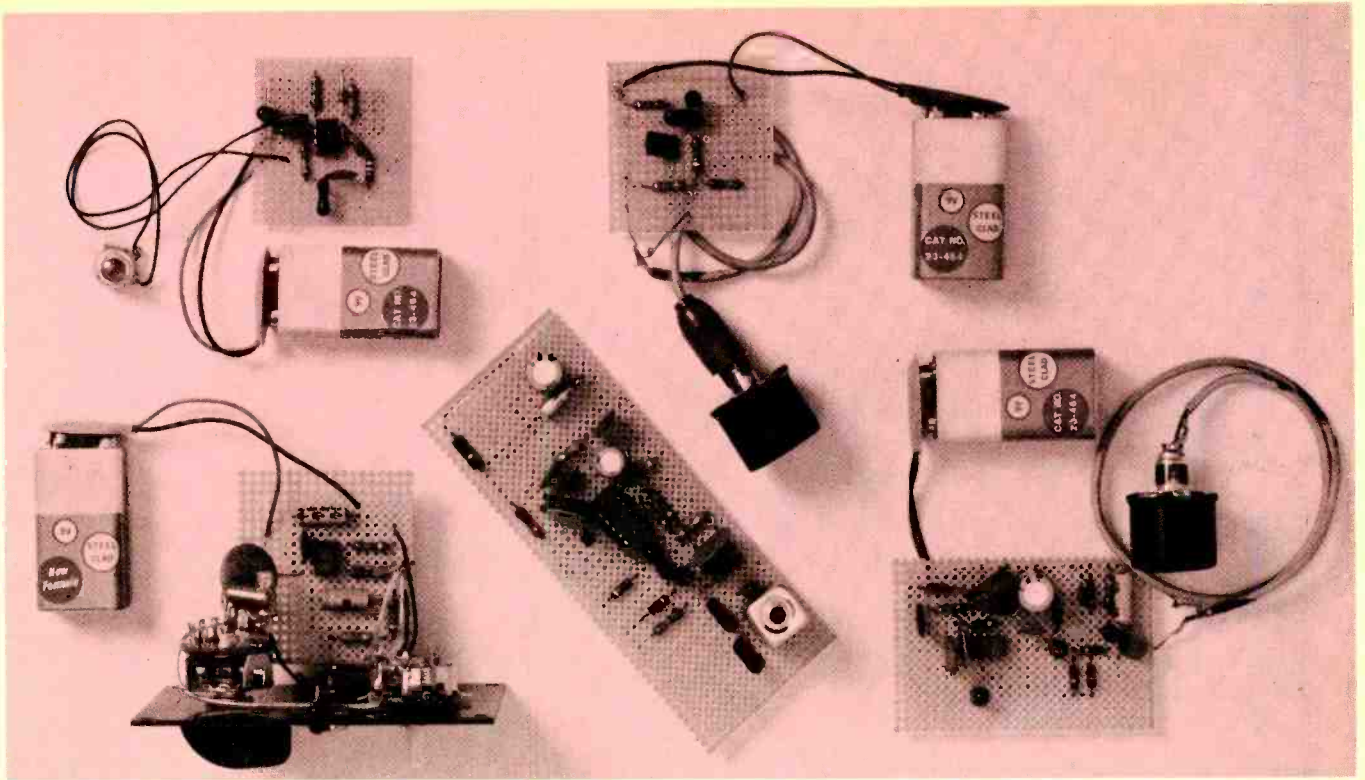Plug the adapter/charger into the jack on the side of the Senior Scientist and the plug into a wall outlet and let the battery charge for at least nine hours.







# EXPERIMENTING WITH PHASE-LOCKED LOOPS

*Four simple but useful circuits that will increase your understanding of these versatile 565 and 567 IC's.*

BY HERB COHEN

**W**HEN phase-locked-loop (PLL) integrated circuits began to appear on the hobby market, the experimenter was faced with the same problem always encountered with new devices: what to do with it. If he tried to understand the theory—usually available in abundance—he was clouted with terms like rads/second, capture ratio, lock range, and lag networks. Needless to say, there was an urge to slam shut the book and treat the IC as a “black box”—not really such a bad idea.

Although there have been a number of articles published in various magazines explaining the basics of PLL theory (see “How Phase-Locked Loops Work,” February 1975), a “hands-on” session with these IC’s will tell you more about them than all the reading you’re likely to do. As an example, the 565 and 567 PLL’s are so simple to work with and require so few external components that you don’t

need a stage-by-stage understanding of what goes on inside them to put them to use.

In this article, we describe four simple projects you can build around a pair of commonly available PLL’s to give a “feel” for how they perform. Each project illustrates a different aspect of phase-locked-loop technology, and each is a practical circuit you can put to immediate use. Before proceeding to the projects themselves, however, let us first discuss the specific PLL’s used in our projects.


**Two PLL’s.** Of the many phase-locked-loop IC’s available, the 567 is the only one that is designed primarily for switching applications. When this PLL goes into lock, its output transistor, driven from a quadrature detector, is capable of passing 100 mA of current. This makes the 567 ideal as an SCR or relay driver.

Another unique feature of the 567

PLL is its ability to be driven from a low-voltage (4.5 to 10 volts) power supply at a nominal 10-mA drain. This means that the IC can be powered by a 9-volt transistor battery with good life expectancy. So, although it doesn’t have the bandwidth or sensitivity of other PLL’s, the 567 is ideal for hundreds of tone-decoder applications in the range from 1 Hz to 100 kHz.

The 565 is a general-purpose PLL IC and is by far the most popular now being used. It exhibits a very wide  $\pm 60\%$  locking range and a 1-mV input sensitivity. This PLL is ideal for use as an SCA decoder, which will let you receive the hidden subchannels on FM.

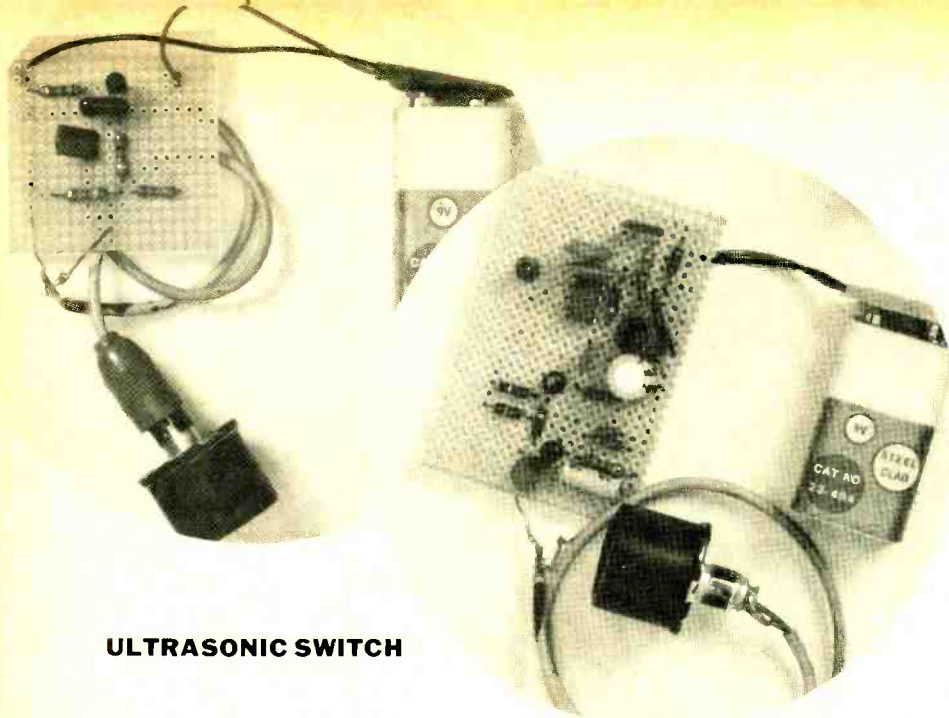The following four projects are examples of the simplicity and versatility of the PLL IC. The first three are built around the 567, while the fourth—an SCA decoder—employs the 565 PLL. The circuits can be assembled easily on perforated boards or pc boards.



## ULTRASONIC SWITCH

**Ultrasonic Switch.** The simple transmit/receive system shown in Fig. 1 can receive a signal from distances of up to 40' (12 m) and more in hallways and enclosed areas where the acoustical properties are good. The transmitter is shown in B, while the receiver is shown in A.

Transducers *TR1* and *TR2* in the receiver and transmitter are 40-kHz barium-titanate ultrasonic transducers. Transducer *TR1* in the receiver picks up the sound waves from transmitter transducer *TR2* and passes them to the amplifier consisting of

transistors *Q1* and *Q2*. The PLL (*IC1*) then accepts the amplified signal and rejects any spurious responses and out-of-band noise pulses.

Light-emitting diode *LED1* and limiting resistor *R9* are installed in the circuit only temporarily to assist in tuning the system. Once the system has been properly tuned, these components are removed and replaced with the load to be driven (relay, lamp, etc.).

The transmitter shown in B is a Colpitts oscillator configuration that uses transducer *TR2* in the resonance cir-


cuit. This circuit puts out a minimum of 2 volts rms across *TR2*, which develops more than enough sound power for the system.

To tune the receiver, place the transmitter about 5' (1.5 m) away from the receiver with both transducers facing each other. Adjust potentiometer *R10* until *LED1* comes on. Turn off the power to the transmitter; *LED1* should immediately extinguish. (Note *LED1* may light up when *R10* tunes the system to a submultiple or harmonic of the transducer frequency, so make sure you're tuned to the fundamental frequency.)

Once the receiver has been properly tuned, the range you can obtain with this system is dependent mainly on room acoustics. However, you should be able to obtain a minimum of 20' (6.1 m) of range.

The ultrasonic relay system can be used as an intruder alarm, garage door opener, or remote relay. It can even be made to operate as a simple motion detector. To do this, place the transmitter and receiver about 10' (3 m) apart and with their transducers facing the same wall in a room. The LED in the receiver should come on; if it doesn't, move the transmitter closer to the receiver until it does. Then, move it away until the LED just extinguishes. Now, walk along the side of the room that the transmitter and receiver are facing. As you move, the LED will blink on and off.

Fig. 1. A simple transmit/receive ultrasonic relay.

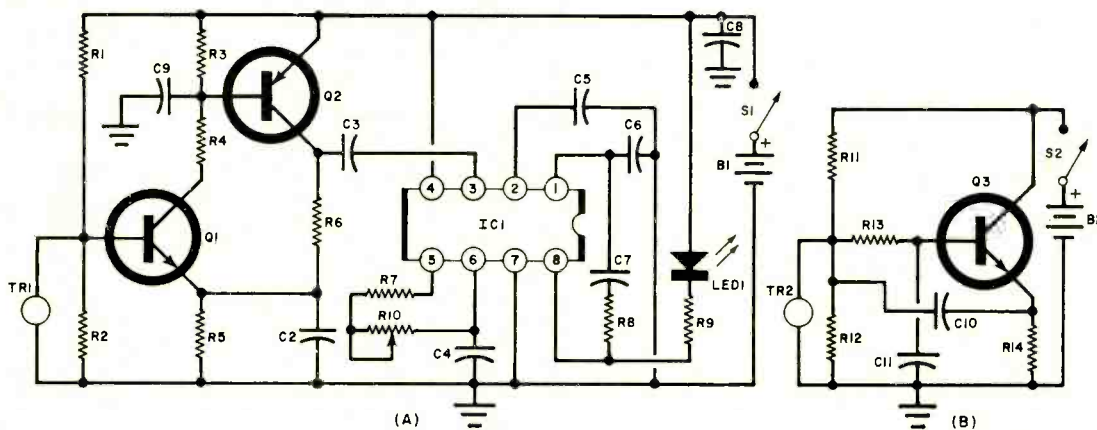


### PARTS LIST

B1, B2—9-volt battery  
 C1, C6—0.04- $\mu$ F disc capacitor  
 C2—5- $\mu$ F, 10-volt electrolytic capacitor  
 C3, C4—0.0047- $\mu$ F disc capacitor  
 C5—0.1- $\mu$ F disc capacitor  
 C7, C10—0.02- $\mu$ F disc capacitor  
 C8—100- $\mu$ F, 10-volt electrolytic capacitor  
 C9—0.001- $\mu$ F disc capacitor  
 C11—330-pF disc capacitor  
 IC1—567 PLL IC

LED1—Light-emitting diode  
 TR1, TR2—Ultrasonic transducer (Detector No. HC1)  
 Q1—2N4946 pnp transistor  
 Q2—2N4917 npn transistor  
 Q3—HEP S0007 npn transistor  
 The following are 1/4-watt, 10% resistors:  
 R1—180,000 ohms  
 R2—43,000 ohms  
 R3, R4—2200 ohms

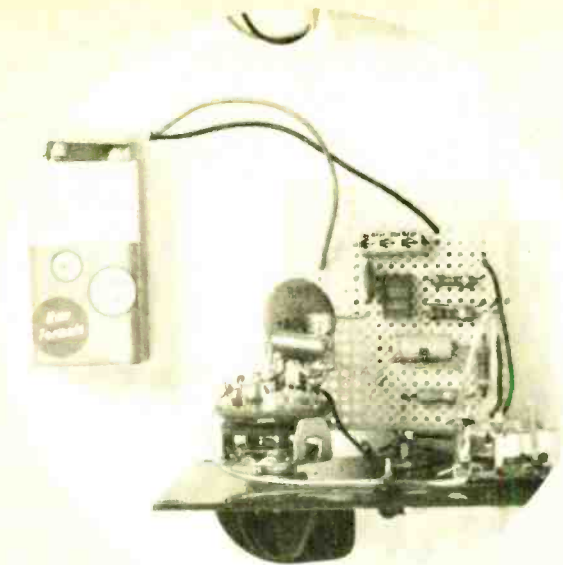R5, R13, R14—1000 ohms  
 R8, R7—2700 ohms  
 R9—330 ohms  
 R11—22,000 ohms  
 R12—47,000 ohms  
 R10—10,000-ohm miniature potentiometer  
 S1, S2—Spst switch  
 Misc.—Battery clips; hookup wire; solder; etc.




**TUNABLE FILTER**

**Tunable Filter.** The circuit shown in Fig. 2 illustrates the use of the 567 PLL as a wideband (10-to-100-kHz) tunable filter. Potentiometer *R4* is the fine-tuning control. If its dial is accurately calibrated, the knob pointer can indicate to better than 5% accuracy, the frequency of any incoming signal within the filter's range. This circuit can be used for stereo tuning and tape bias oscillator adjustments. As a tone decoder, it would be hard to beat.


The circuit has several interesting features. First, the bandpass of the filter is proportional to the input voltage, from 1% to about 14% of the bandwidth. Second, when the PLL starts to lock onto the incoming signal, the

*Fig. 2. Tunable filter circuit can be used as a tone decoder.*

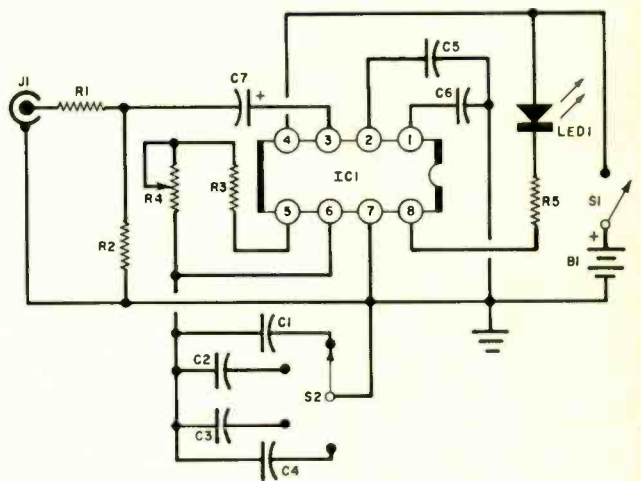


**PARTS LIST**

- |   |   |
|---|---|
| B1—9-volt battery                                 | LED1—Light-emitting diode                     |
| C1—0.01- $\mu$ F disc capacitor                   | R1—4700-ohm, 1/4-watt resistor                |
| C2—0.1- $\mu$ F disc capacitor                    | R2—2200-ohm, 1/4-watt resistor                |
| C3—1- $\mu$ F, 15-volt electrolytic capacitor     | R3—1000-ohm, 1/4-watt resistor                |
| C4—10- $\mu$ F, 10-volt electrolytic capacitor    | R4—10,000-ohm, linear-taper potentiometer     |
| C5—0.05- $\mu$ F disc capacitor                   | R5—330-ohm, 1/4-watt resistor                 |
| C6, C7—5- $\mu$ F, 15-volt electrolytic capacitor | S1—Spst switch                                |
| C8—100- $\mu$ F, 15-volt electrolytic capacitor   | S2—4-position non-shorting rotary switch      |
| IC1—567K PLL IC                                   | Misc.—Battery clip; hookup wire; solder; etc. |
| J1—Phono jack                                     |   |

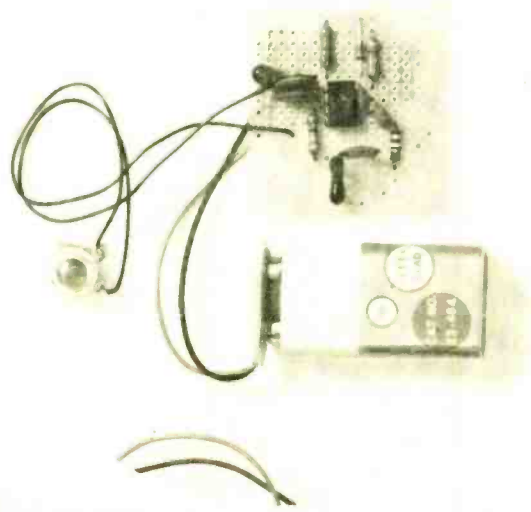

**TOUCH SWITCH**

*Fig. 3. Touch switch can be made to latch in by adding the jumper.*

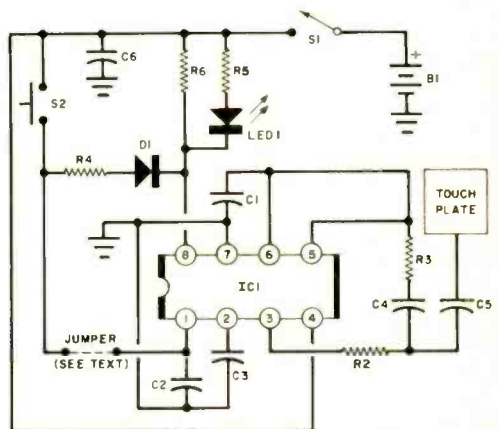

**PARTS LIST**

- |   |   |
|---|---|
| B1—9-volt battery                       | C6—30- $\mu$ F, 10-volt electrolytic capacitor                            |
| C1—0.005- $\mu$ F disc capacitor        | D1—1N914 diode  |
| C2, C3, C4—0.04- $\mu$ F disc capacitor | IC1—567 PLL IC  |
| C5—33-pF disc capacitor                 | S1—Spst normally open, momentary-action switch                            |
|   | Misc.—3" x 3" solderable metal for touch plate; hookup wire; solder; etc. |

**Touch Switch.** As a convenience feature in a home, the touch switch,

shown in Fig. 3, is hard to beat. Just by touching the plate, body capacitance unbalances the circuit and pulls IC1 into lock. An external signal is normally fed into the PLL (IC1) via pin 3 and C1 and R1 are used to tune the voltage-controlled oscillator to the input frequency. When lock occurs,


the vco adjusts itself to be 90° out-of-phase with the input signal.

With the input signal at pin 3 coming from the output of the vco (pin 5 of IC1) through C4, R2, and R3, the two signals are in-phase with each other and the circuit cannot lock. However, when the touch plate is approached,

enough capacitive phase shift is introduced to allow the circuit to lock.

Wiring the jumper into the circuit as shown allows the system to latch in the on position even after your hand is removed from the touch plate. To reset the system to off requires S1 to be closed momentarily.

## SCA DECODER

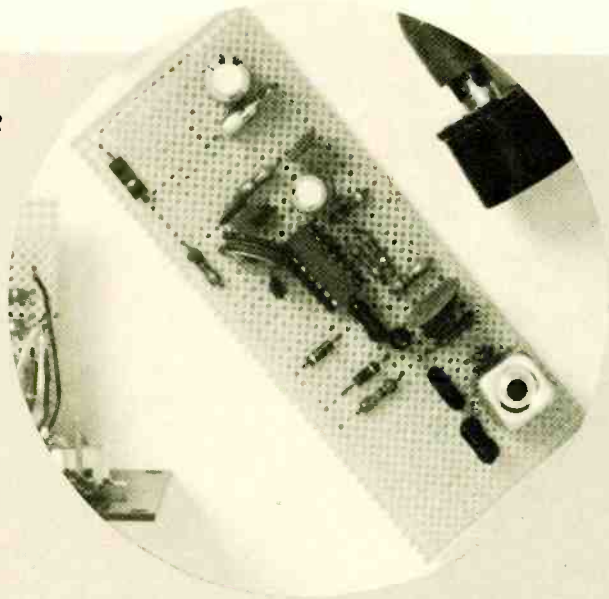

**SCA Decoder.** Our final PLL project is an SCA decoder built around the 565 phase-locked-loop IC. This is es-

entially a 67-kHz FM detector. However, a PLL is a better detector for FM than any of the traditional detector de-

signs because it has the ability to dive 6 dB below the noise level and still lock onto a signal.

In the case of an SCA subchannel where the information is only 10% of the total program power (most of that lost in the audio filtering), the 565 IC's ability to reject noise is an important factor in building a simple and effective SCA decoder.

Capacitors C1, C2, and C3 and coil L1 (Fig. 4) form a bandpass filter that peaks at 67 kHz and rejects all low-frequency components of the audio signal in an FM tuner. Transistor Q1 amplifies this signal and passes it to IC1. The PLL IC is tuned by C7, R6, and R10. Since the tuning frequency is also a function of the supply voltage, the IC should be zener-diode regulated.

The demodulated audio signal comes out of the decoder at a 50-mV level. It has a 7,000-Hz audio bandwidth that can hardly be considered hi-fi. This bandwidth, however, is more than sufficient for background music.

The tuning procedure is simple. Connect the output of your FM tuner to the input of the SCA decoder and the output of the decoder to your audio amplifier. Set R10 to the center of rotation. Scan the FM dial; all you should be able to hear at this point is noise and no stations. An SCA subchannel will appear as a sharp drop in the noise level, accompanied by a distorted music program. Now, adjust R10 for the best signal-to-noise (S/N) ratio and highest fidelity.

Tune to the weakest SCA subchannel you can find. Adjust L1 for the lowest possible noise level. The SCA decoder is now ready to use.

**Closing Comment.** The preceding four projects illustrate only a small portion of the possible applications to which the versatile phase-locked-loop IC can be put. A couple of the projects should be able to suggest other projects of your own.

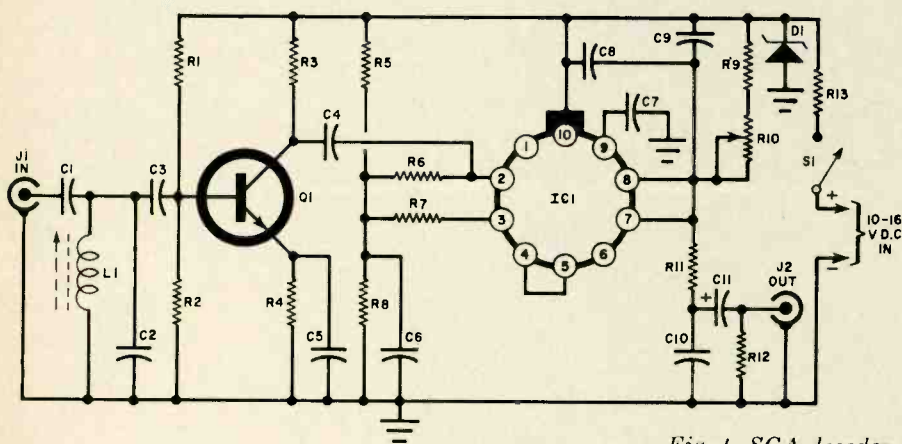


Fig. 4. SCA decoder.

### PARTS LIST

C1—220-pF disc capacitor  
 C2—0.002- $\mu$ F disc capacitor  
 C3—330-pF disc capacitor  
 C4—560-pF disc capacitor  
 C5, C9, C10—0.04- $\mu$ F disc capacitor  
 C6—0.1- $\mu$ F disc capacitor  
 C7—0.001- $\mu$ F disc capacitor  
 C8—0.001- $\mu$ F disc capacitor  
 C11—30- $\mu$ F, 15-volt electrolytic capacitor  
 D1—12-volt zener diode  
 IC1—565 PLL IC  
 J1, J2—Phono jack  
 L1—10-mH slug-tuned inductor (Miller No. 9060)  
 Q1—2N2926 npn transistor

The following are 1/4-watt, 10% resistors:  
 R1—100,000 ohms  
 R2—22,000 ohms  
 R3—8200 ohms  
 R4—1500 ohms  
 R5—15,000 ohms  
 R6, R7, R11—4700 ohms  
 R8—6800 ohms  
 R9—1000 ohms  
 R12—47,000 ohms  
 R10—10,000-ohm, linear-taper potentiometer  
 R13—47,000-ohm, 1/2-watt, 10% resistor  
 S1—Spst switch  
 Misc.—Battery clip; hookup wire; solder; etc.

# How to "DEBOUNCE" Mechanical Switches for Digital Logic Use

Interface circuitry eliminates false pulses.

BY E. W. GRAY

**M**ANY projects involving digital logic require the use of one or more mechanical switches. These can take the form of toggle switches, relays, pushbuttons, or keyboards. Two characteristics of these devices, switching noise and timing, require special consideration when connecting them to a digital logic system.

All mechanical switches, regardless of type, normally generate some electrical noise when the contacts transfer from one position to the other. This is due to bouncing of the contacts for several milliseconds after actuation. They actually make, break, and remake several times before finally coming to rest in the new position. This bounce period is called settling time. Digital logic elements, being much

faster in their operation than mechanical switches, respond to each transition during the bounce period if the logic is connected directly to the switch. Thus false signals are produced. For this reason, "debouncing" circuits are used between the mechanical switch and the driven logic.

**Contact Bounce in Spdt Switches.** A single-pole, double-throw (form-C) switch and an idealized timing diagram of its action during transfer from normally closed to normally open are shown in Fig. 1. Initially, the movable arm (operating strap) is in contact with the normally closed contact. As transfer begins, the arm moves away from the normally closed side, opening the contact. The

slightly springy, normally closed contact attempts to follow the arm and bounce occurs. This is called "break bounce;" the multiple openings and closings of the normally closed contact and the arm as the switch transfer is initiated.

As transfer continues, break bounce ceases. At this time the arm is not in contact with either side of the switch, but is "in transit" to the opposite side. Both normally closed and normally open contacts are now open. (Note: "Make-before-break," or shorting, switches are available; similar bounce conditions can occur, however.)

When the arm reaches the normally open contact, the two collide, and "make bounce" begins. The arm and the normally open contact close, open, and close again until the mechanical movement ceases. The switch transfer is then complete. In most switches, make bounce is much more severe than break bounce.

When the form-C switch is released from the transferred position, the reverse of the above actions occur. Break bounce takes place at the normally open contact and make bounce occurs at the normally closed contact.

**Debouncing Spdt Switches.** To use the form-C switch successfully in digital logic, the debounce circuit must mask both break and make

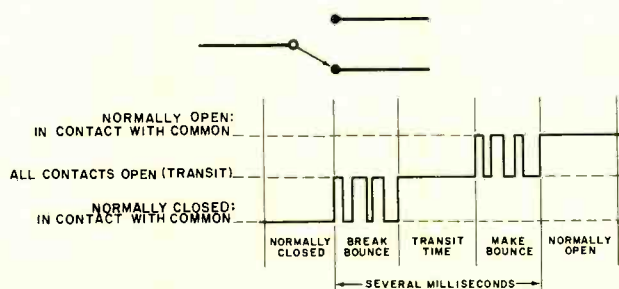


Fig. 1. During the few milliseconds it takes a switch to operate, erroneous pulses can confuse digital logic.


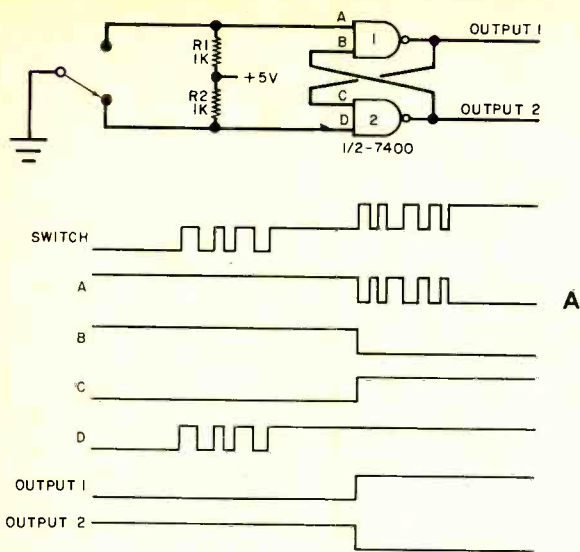
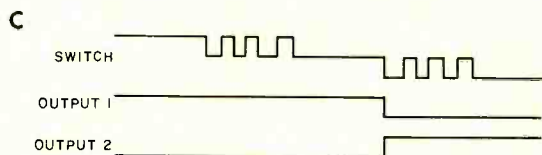
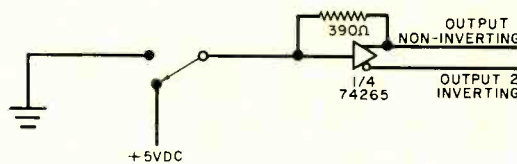
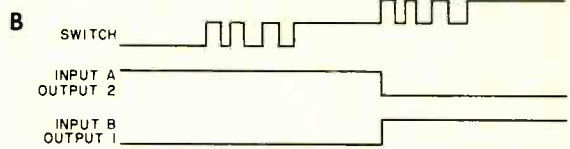


Fig. 2. Debouncing circuits: (A) simple NAND gate; (B) inverter configuration; (C) circuit used in a recently announced complementary device.

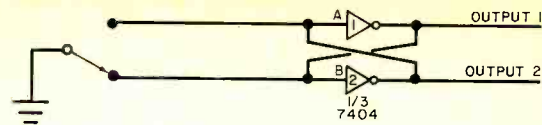

bounce and produce a single, noise-free transition at its output each time the switch is operated or released.

Three circuits to accomplish this are shown in Fig. 2. TTL devices and positive logic are used. (High voltage equals logic one; low voltage equals logic zero.)

In the circuit of Fig. 2A, two cross-coupled NAND gates are used to form a latching circuit. With the switch not operated, the ground (logic zero) applied to input D, gate 2, holds output 2 at logic one. Output 2 is applied to input B, gate 1. This high voltage level, and the high voltage level on input A, gate 1 (through R1 to +5 volts) cause output 1 to be logic zero.

When the switch is operated, input D, gate 2, changes in step with the break bounce. However, outputs 1 and 2 do not change state since the movable arm has not yet grounded input A, gate 1, and the logic zero on output 1 (fed back to input C, gate 2) main-

tains output 2 at logic one. Thus break bounce is ignored at the outputs.

As mechanical action continues, break bounce ceases and the arm makes its first contact with the normally open side. This applies ground (logic zero) to input A. With input A low, output 1 and input C switch to logic one. Inputs C and D are now both at logic one and output 2 goes to logic zero. Fed back to input B, output 2 now latches output 1 high and the circuit is stable.

This switching action between outputs 1 and 2 requires very little time: a maximum of 52 nanoseconds if 7400 NAND gates are used. Thus, the switching is complete long before the first bounce during make occurs. Input A will continue to follow the make bounce transitions but no output changes will occur. When the switch is released, the action is reversed, with output 2 reverting to logic one and output 1 to logic zero.

A somewhat simpler circuit is shown in Fig. 2B. The 7400 NAND gates are replaced by 7404 inverters. Pullup resistors are not required for this circuit. The switching operation is similar to that of Fig. 2A, except that one gate output will be short-circuited for about 37 nanoseconds each time the switch is activated. Device operation is not affected by the short-circuited output; the manufacturer's specification allows a single output in the logic one state to be grounded temporarily.

Note that switch bounce can be observed with an oscilloscope at inputs A and D of Fig. 2A. It cannot be observed at the inputs of the circuit of Fig. 2B due to the direct coupling of input and output.

Both of the above circuits provide complementary outputs, and both require two input lines from the switch. If both ground and +5 volts are available at the switch, debouncing can be ac-


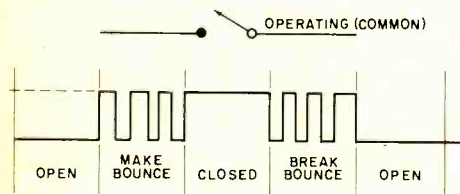


Fig. 3. Bounce pattern of a single-pole-single-throw switch.

Fig. 4. Simple Schmitt trigger can be used to debounce a spst switch.

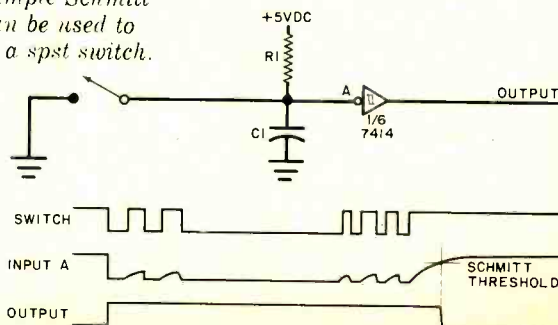

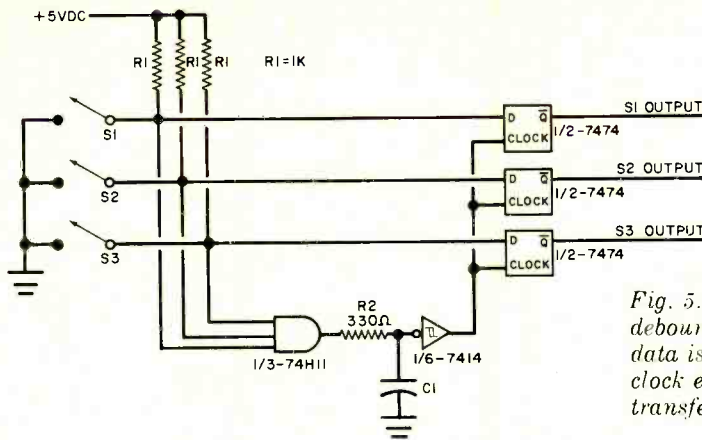


Fig. 5. In keyboard debouncing, switch data is stored until clock enable transfers the data.

completed with only a single input line as illustrated in Fig. 2C. The integrated circuit used is the 74265, a recently announced complementary output device. Here, the noninverting output is fed back to the input, providing stabilizing action much like the 7404 latch of Fig. 2B.

**Contact Bounce in Spst Switches.** A single-pole, single-throw (form-A) switch and its idealized timing diagram are shown in Fig. 3. This switch is equivalent to a single side of the form-C switch. When a spst switch is operated, break bounce occurs between the movable arm and the normally closed contact. No further action occurs until the switch is released. Following release, the operating strap remakes with the normally closed contact, bounces, and make bounce occurs. As in the form-C switch, make bounce is usually more severe than break bounce. The time required for make bounce to subside is an important factor in debouncing the form-A contact.

**Debouncing Spst Switches.** Since only a single output is available from the form-A switch, the latching method of debouncing previously described cannot be used. Instead, a delay circuit is normally used to mask the contact bounce. The debounce circuit must: (1) detect the switch transition; (2) delay response for a sufficient amount of time to allow all bounce to cease, and (3) produce an output defining the new switch position. A simple circuit to accomplish this is shown in Fig. 4.

The gate used is a Schmitt trigger device such as 7413 or 7414. With the switch contacts open as shown, input A will be approximately 5 volts, and the

output will be logic zero. When the switch is operated, input A goes low and the output switches from low to high. Each time the switch bounces open, point A starts to return to the 5-volt level at a rate determined by the time constant of  $R1$  and  $C1$ . As long as input A does not reach its positive-going threshold voltage of about 1.7 volts, the output will remain at logic one. Therefore, the time constant of  $R1$  and  $C1$  should be sufficiently long to allow all bounce to subside before this threshold is reached. Usually about 5 to 10 milliseconds is satisfactory.

**Keyboard Debouncing.** Keyboards, having many switches, pose a special problem when debouncing is considered. Building a debounce circuit for each switch is impractical. Many keyboards include a strobe, or gating, contact which is activated whenever any key is operated. In such keyboards, this common switch should be debounced and its output used to test the state of the remaining switches. Where a common switch is not available, the individual switches can be logically "OR'ed" and the resultant output used as input to the debounce circuit. A typical circuit is shown in Fig. 5. Note that this is an application of the circuit of Fig. 4. Each time a switch is operated, the output of the debounce circuit clocks a flip-flop register which stores the switch information until another switch is operated.

Note that only Schmitt trigger gates should be used with RC networks as shown, since such networks on the input of an ordinary gate can cause oscillation at the gate's output. Series resistance such as  $R2$  in Fig. 5 should not exceed 330 ohms. ♦



## A very quiet announcement from Phase Linear:

Just between you and us, the new Phase Linear 2000 preamplifier is one of the quietest preamps ever made... so quiet it can match the performance of preamplifiers selling at twice the price.

The latest generation of integrated circuits reduces total harmonic distortion to 0.1%, typically .03%, and gives you a signal-to-noise ratio of 74dB below 10mV. That's quiet!


A highly advanced integrated circuit phono preamplifier creates the sonic excellence you have come to expect from Phase Linear.

A variable ambience injection circuit gives you more of the music - allows for the recovery of music lost with most preamplifiers.
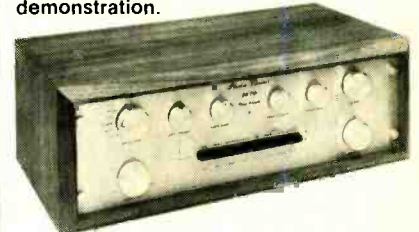
### Other features:

*Individual detented bass and treble controls* with a professional feel in each channel. Turnover points at 50Hz, 150Hz, 2kHz, and 5kHz, where up to 12dB of boost or cut may be applied... *a switchable low frequency active equalizer* for up to 6dB boost below 50Hz for a flatter bass response... *two complete tape circuits* for easy control and tape-to-tape dubbing... *a comfortable size* that complements other Phase Linear products: 5½" x 19" x 6"... and an *outstanding value at \$299.00.*

Visit your dealer and quietly ask for a demonstration.



# Phase Linear 2000

THE POWERFUL DIFFERENCE  
CIRCLE NO. 44 ON FREE INFORMATION CARD

# When you're exploring technology... books





# a fascinating new alone are not enough.

If you're like most men, deep down inside there's still a bit of the boy who loved to go exploring... and who'd love to go again. Well, now you can.

Only this time you'll explore the expanding world of electronics... a world more fascinating than any you ever dreamed of as a boy.

**Learn by exploring... Bell & Howell Schools offers an exciting way for you to gain new occupational skills in electronics.**

Everybody enjoys learning something new, but why learn it the old way? Classes to go to. Lectures to sit through. And only a bunch of books to keep you interested.

Bell & Howell Schools' adventure in learning is a far cry from all that.

You can probe into electronics and learn exciting new occupational skills right in your own home, in your spare time. On whatever days and whatever hours you choose. So there's no need to give up your present job and paycheck just because you want to learn something new.

What's more, when you're exploring a field as fascinating as electronics, reading about it is just not enough. That's why throughout this program you'll get lots of "hands on" experience with some of today's latest electronic training tools.

**You'll be stimulated for hours on end as you build, experiment and learn while using the latest ideas and techniques in this fascinating field.**

As part of the program you'll actually learn to build and work with your own electronics laboratory. Using it to put many of today's most dynamic electronic discoveries to the test... including electronic miniaturization.

Among the things you'll discover is how the development of tiny integrated circuits has made possible an electronic calculator small enough to fit into a shirt pocket! And a wristwatch that flashes the time with the push of a button.

You'll investigate the concept of "logic circuits." An idea that has been with us for centuries but only in recent years put to use as the "brain" behind all the new digital consumer appliances we see today.

But more important than anything else is the new occupational skills you'll develop in electronics troubleshooting. While no assurance of income opportunities can be offered, you'll develop skills that could lead you in exciting new directions. Use your training:

1. To seek out a job in the electronics industry.
2. To upgrade your current job.
3. As a foundation for advanced programs in electronics.

**You build and perform many exciting experiments with Bell & Howell's Electro-Lab<sup>®</sup>, an exclusive electronics training system.**

Using our successful step-by-step method,

you'll build:

1. A design console, for setting up and examining circuits.
2. A digital multimeter for measuring voltage, resistance and current (it displays its findings in big, clear numbers like a digital clock).
3. A solid-state "triggered sweep" oscilloscope—similar in principle to the kind used in hospital operating rooms to monitor heartbeats. You'll use it to monitor the "heartbeats" of tiny integrated circuits. The "triggered sweep" feature locks in signals for easier observation.

**Step-by-step you'll build and experiment with Bell & Howell's new generation color TV—investigating digital features you've probably never seen before!**

This 25" diagonal color TV has digital features that are likely to appear on all TV's of the future. As you build it you'll probe into the technology behind all-electronic tuning. And into the digital circuitry of channel numbers that appear right on the screen! You'll also build in a remarkable on-the-screen digital clock, that flashes the time in hours, minutes and seconds. Your new skills will enable you to program a special automatic channel selector to skip over "dead" channels and go directly to the channels of your choice.

You'll also gain a better understanding of the exceptional color clarity of the Black Matrix picture tube, as well as a working knowledge of "state of the art" integrated circuitry and the 100% solid-state chassis.

After building and experimenting with this TV, you'll be equipped with the skills that could put you ahead of the field in electronics know-how.

**We try to give more personal attention than other learn-at-home programs.**

1. Toll-free phone-in assistance. Should you ever run into a rough spot during the program, we'll be there to help. While many schools make you mail in your questions, we have a toll-free line for questions that can't wait.
2. In-person "help sessions." These are held in 50 major cities at various times throughout the year where you can talk shop with your instructors and fellow students.

**No electronics background needed.**

What you really need is the thing you've never lost. A boy's love for exploring. Now you can go again, only this time learning new occupational skills all along the way.

**Mail the postage-paid card today for more details!**

Taken for vocational purposes, this program is approved by the state approval agency for Veterans' Benefits.

If card has been removed, write:

An Electronics Home Study School  
DEVRY INSTITUTE OF TECHNOLOGY

ONE OF THE  
**BELL & HOWELL SCHOOLS**  
4141 Belmont, Chicago, Illinois 60641

Simulated TV test pattern.

"Electro-Lab<sup>®</sup>" is a registered trademark of the Bell & Howell Company.



# BUILD A HIGH-GAIN RHOMBIC TV ANTENNA

*This easy-to-build antenna offers  
high gain, good directivity, wide bandwidth—and  
costs less than \$10 for parts.*

BY GEORGE L. MONSER


**T**HE rhombic is a nearly ideal TV antenna. It's easy to build and install, provides good reception, and costs less than \$10 in materials. If you live in a house with a nonmetallic roof and are located in a medium signal-strength area (with a rather clear "shot" to the transmitter), it can be installed without support masts. The rhombic can also be shaped to the roof contour so it will not detract from the house's appearance. High gain (up to 14 dB), broad bandwidth, and good directionality are characteristic of the rhombic's performance.

**About the Rhombic.** The rhombic is a long-wire antenna in the shape of a rhombus, with sides usually greater than three halves of a wavelength (Fig. 1). In this configuration, it is a non-resonant antenna with a resistive termination. The presence of the resistor converts the rhombic into a unidirectional antenna with the favored direction looking toward the termination. (Unterminated rhombics are bidirectional). This is desirable in most situations since many viewers want to receive signals which are all transmitted from the same high antenna site. The legs of the antenna are formed from

foam-filled 300-ohm twinlead, because the use of multiple conductors increases the gain and bandwidth of the antenna.

Both the leg length  $l$  and the "tilt angle"  $\theta$  are variables, and the rhombic's overall gain depends on this combination and the angle at

which the signal approaches the antenna. The dimensions ( $l$  and  $\theta$ ) can be chosen either to give maximum gain and directivity or to fit certain physical constraints (like the shape and size of your roof!). In general, maximum gain is found as  $\theta$  increases. The gain of a diamond-shaped rhombic ( $\theta = 65^\circ$ ) is

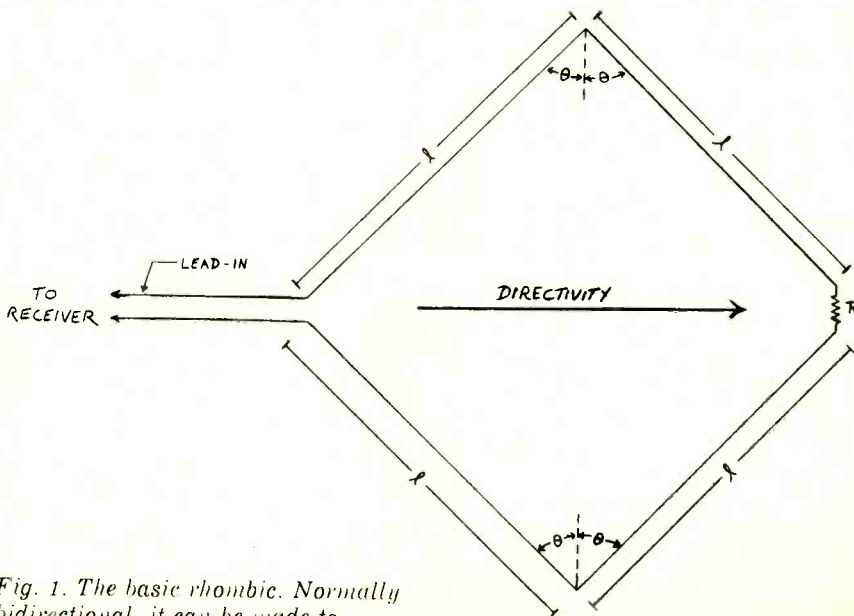

*Fig. 1. The basic rhombic. Normally bidirectional, it can be made to focus in one direction by adding the resistive termination.*

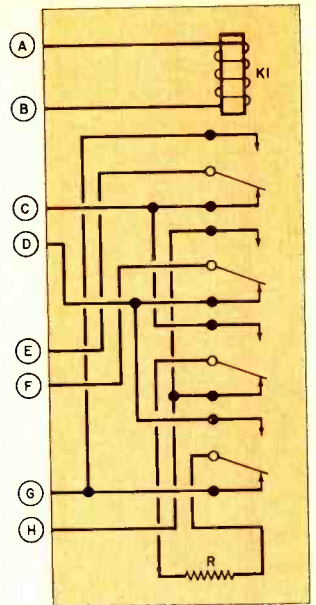
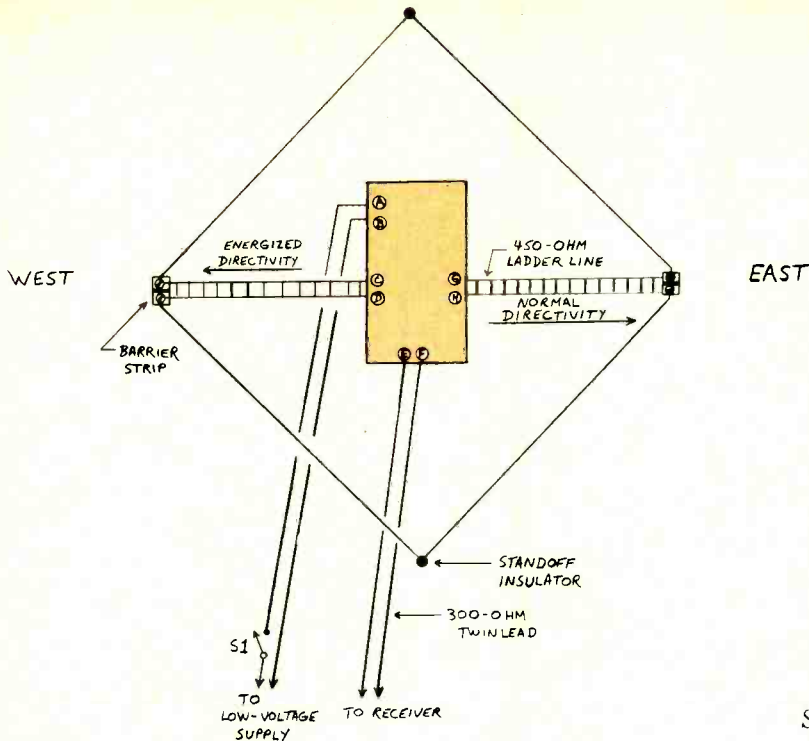


Fig. 2. At left is switchable rhombic antenna. Shaded area is relay switching circuit above. Switching feed and termination changes direction.

about twice that of a square antenna ( $\theta = 45^\circ$ ).

Feedpoint impedance poses an important question—what type of transmission line should be used with the rhombic? The antenna's impedance is not a constant value over variations in frequency, and the physical dimensions have some effect. A square antenna has an impedance of 600 to 800 ohms, while smaller values of  $\theta$  mean it will generally lie between 450 and 600 ohms.

Most TV receivers, on the other hand, have an input impedance of 300 ohms, and most TV transmission line is of the 300-ohm twinlead variety. This means that, if 300-ohm line is used to bring the signals down to the receiver, an SWR will develop on the line. Some signal loss will exist because of the reflections induced by the impedance mismatch. It's not all that bad, since the greatest SWR you're likely to encounter is 2.7:1. This corresponds to a signal loss of about 25%, or 1.25 dB—which will not really be noticed.

**Multidirectional Rhombics.** If you want to receive stations from more than one direction, you will either have to put up a few unidirectional rhombics or resort to a switching scheme such as that shown in Fig. 2. In this case, we want to receive signals coming along one axis of the rhombic (see arrows). Most of the time, we listen to

station X, whose broadcasts come in from the east. So, we leave S1 open and relay K1 de-energized. The antenna favors signals facing east, since that's where the termination (R) is with respect to the feedpoint.

Now, let's say that there's a good program on station Y's channel, whose signals come in from the west. Closing S1 will energize the relay coil, reversing the feed and termination points. The antenna thus "looks" west. Although only two directions are realized in this design, it's possible to use a more complex switching system to include the other two corners of the rhombic. This would allow selection of each of the four cardinal directions

(with respect to the antenna). If you want to use this relay switching technique, it's advisable to have a low-capacitance relay mounted in a weather-sealed box to avoid excessive signal loss. Also, for safety's sake, use a low-voltage ac or dc relay coil and good outdoor wire between the coil and voltage source.

**Antenna Design.** The first step in designing the rhombic is to decide what channels you want to receive, the relative location of their transmitting antennas with respect to your home, and the physical layout of the installation site. (In this article, we assume the antenna is mounted horizontally on

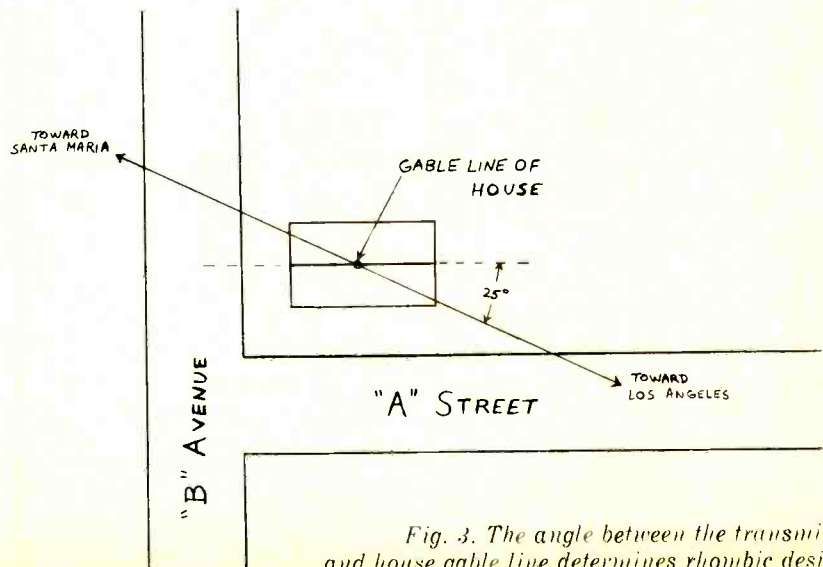


Fig. 3. The angle between the transmitter and house gable line determines rhombic design.

the pitched roof of a wood-frame house.)

For optimum results, three basic designs are described, covering the vhf LO, vhf HI, and uhf bands. The vhf LO antenna measures 25 feet (7.6 m) on a side, and covers channels 2 through 6 and the FM broadcast band. The vhf HI design, spanning channels 7 through 13, has legs one-third the length of those for vhf LO. For the uhf channels (14 through 83), a rhombic that is 55 inches (139.7 cm) on each side is recommended. One rhombic can be installed within another with a different cant to receive higher channels from another direction.

Once you have chosen which size(s) you want to use, locate your reception site and the transmitting antenna on a state or city map. Determine the alignment of your house with respect to the station locations as shown in Fig. 3. In our example, we want to receive stations in Los Angeles and Santa Maria. These roughly lie along the same line, at a 25-degree angle from the gable line of the house. If the angle to the station exceeds 30°, it's best to use the square rhombic ( $\theta = 45^\circ$ ). But we are within the limit for a diamond-shaped antenna, and we'll take advantage of its higher gain to get the distant (100 miles) signals. A vhf LO band antenna will be set up.

**Construction.** First, we cut a 100-ft. (30.5-m) length of foam-filled 300-ohm TV twinlead in half. A few inches of the insulation are removed at each end of the twinlead segments, and the bared

wires are twisted together and soldered. Then, install 3½-inch (not critical, larger units can be used) standoff insulators at the four corners of the rhombic design. Slip the twinlead segments through standoffs 1 and 3 until they are halfway through. The free ends of the twinlead are now connected to individual terminals on two barrier terminal strips, which are secured with nylon rope to standoffs 2 and 4. Install relay K1 and the terminating resistor in a small weatherproof box near the center of the antenna. Weatherproof all connections with epoxy or a commercial preparation made for this purpose. The terminating resistor should be either 470- or 680-ohm, half-watt carbon types. Experiment with the two values and choose the one that gives best reception.

The geometry and physical installation of the rhombic may have to be tailored to your location. Use Figs. 4 and 5 as guides—but by all means ex-

periment. Try to keep all leads to the relay short, and have the 300-ohm line take off at right angles to the gable line.

**Performance.** How well the rhombic performs is pretty much a function of the leg length and the tilt angle. For the antenna described, about 6 dB of gain is realized on channel 2, rising to about 14 dB on channel 6 and the FM broadcast band. If the vhf HI-band rhombic is built along the same lines, the gain would be 6 dB on channel 7 and increase to 11 dB on channel 13. The uhf model would deliver about 7 dB gain on channel 14, rising to 12 dB on channel 83. (These figures are referenced to a dipole, and are approximate.) With the rhombic aimed toward the channel(s) of interest, the antenna should yield better results than a 5-element yagi beam mounted at the same height. While reception won't be quite as good as that experienced with the multi-element, long-boom commercial antennas, the rhombic will deliver amazing results—considering that it was built for less than \$10!

#### Other Uses for the Rhombic.

Though we have described a rhombic for the TV bands, there's no reason why it can't be adapted for SWL, CB, amateur and vhf monitor use. The only major modifications would be in size. At lower frequencies, a larger antenna (and mounting area) would be needed. Remember though, that hf rhombics (14 MHz and below) can be unwieldy. A matching network would also be required to step down the high impedance of the rhombic feedpoint to the low-impedance, unbalanced inputs and outputs of communications receivers, transceivers, and transmitters. For more design information on this high-performance antenna, see "The ARRL Antenna Handbook" or other reference works on antennas.

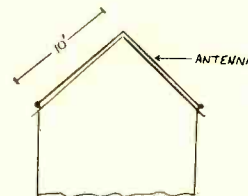
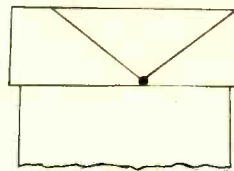
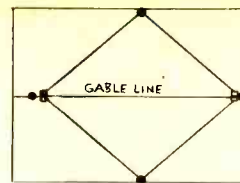


Fig. 5. Top, side, and edge views show how to install antenna on a pitched roof.

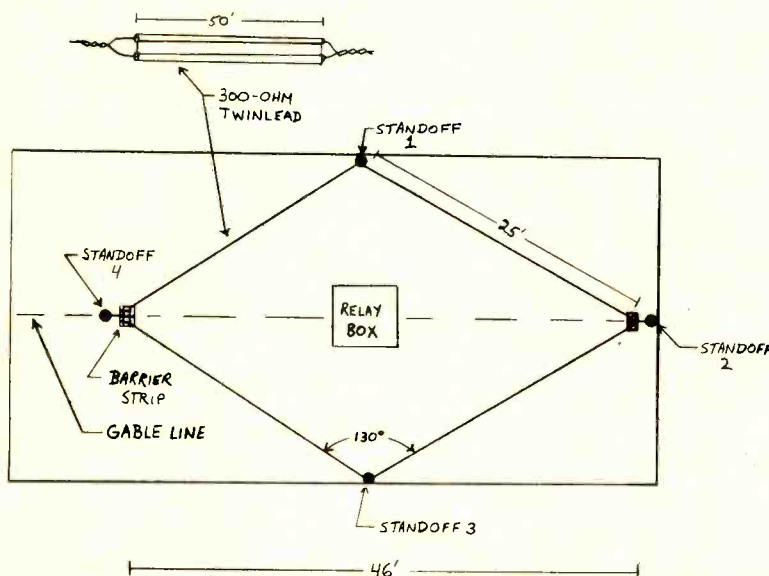


Fig. 4. Installation on a pitched wooden roof. TV insulators support the rhombic about 3" off the roof.

# HOW TO DESIGN SOLID-STATE OSCILLATORS

*An easy-to-follow approach to basic design of this important part of electronic systems.*

BY JIM HUFFMAN

**T**HE oscillator is one of the major building blocks of electronic systems. As differentiated from an amplifier, which merely applies gain to any signal fed to its input, the oscillator converts dc applied to its input to an ac signal at its output. Many people who know how to design an amplifier are stymied when it comes to designing oscillators.

There are many types of oscillators. They can be all-electrical or electromechanical. In this article, our concern is with the former, which includes the negative-resistance, Hartley, Colpitts, RC, Armstrong, avalanche, etc., oscillators commonly found in everyday electronic equipment. We will limit our discussion to oscillators that are most practical for the experimenter to use.


**Preliminary Information.** The configuration of the basic feedback-type oscillator is shown in Fig. 1. It is simply an amplifier to which has been added a feedback network. This type of oscillator goes by various names (Hartley, Colpitts, Armstrong, etc.), but the op-

eration is the same no matter what the name given to it.


If the output of the feedback network is in phase with the input of the amplifier and the output signal of the network is of sufficient level, the amplified output will return to the input and be reamplified. This signal, made even greater in amplitude through double amplification, goes back around to the input of the amplifier continuously, causing the output of the amplifier to alternate in such a manner that the dc power supply voltage to the amplifier is changed to an ac signal at the output of the amplifier. If the feedback network is frequency sensitive, as well as being phase-shifted, the frequency of the oscilla-

tor's output signal can be accurately predicted.

The obvious problem to the foregoing is that if the feedback energy keeps building each time it is amplified, the ac signal's amplitude will attempt to exceed the dc supply voltage, which is an impossibility. Instead, clipping results and the waveform becomes distorted. In some cases, the distortion is acceptable, but if the oscillator is used in an application such as the vfo (variable-frequency oscillator) in a transmitter, it will cause unacceptable spurious outputs. So, the feedback network must be prevented from feeding too high a signal amplitude to the input of the amplifier. Alternatively, you can reduce amplifier gain. In fact, maximum stability and cleanest waveform occurs when overall gain (including losses in the feedback network) is just slightly greater than unity. If gain is too low, however, there will not be enough feedback to initiate oscillation in the first place and you will end up with an amplifier with frequency-selective positive feedback.

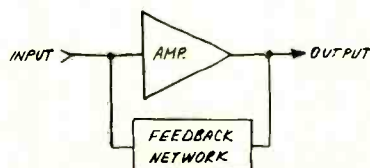

*Fig. 1. Basic oscillator is amplifier with feedback.*

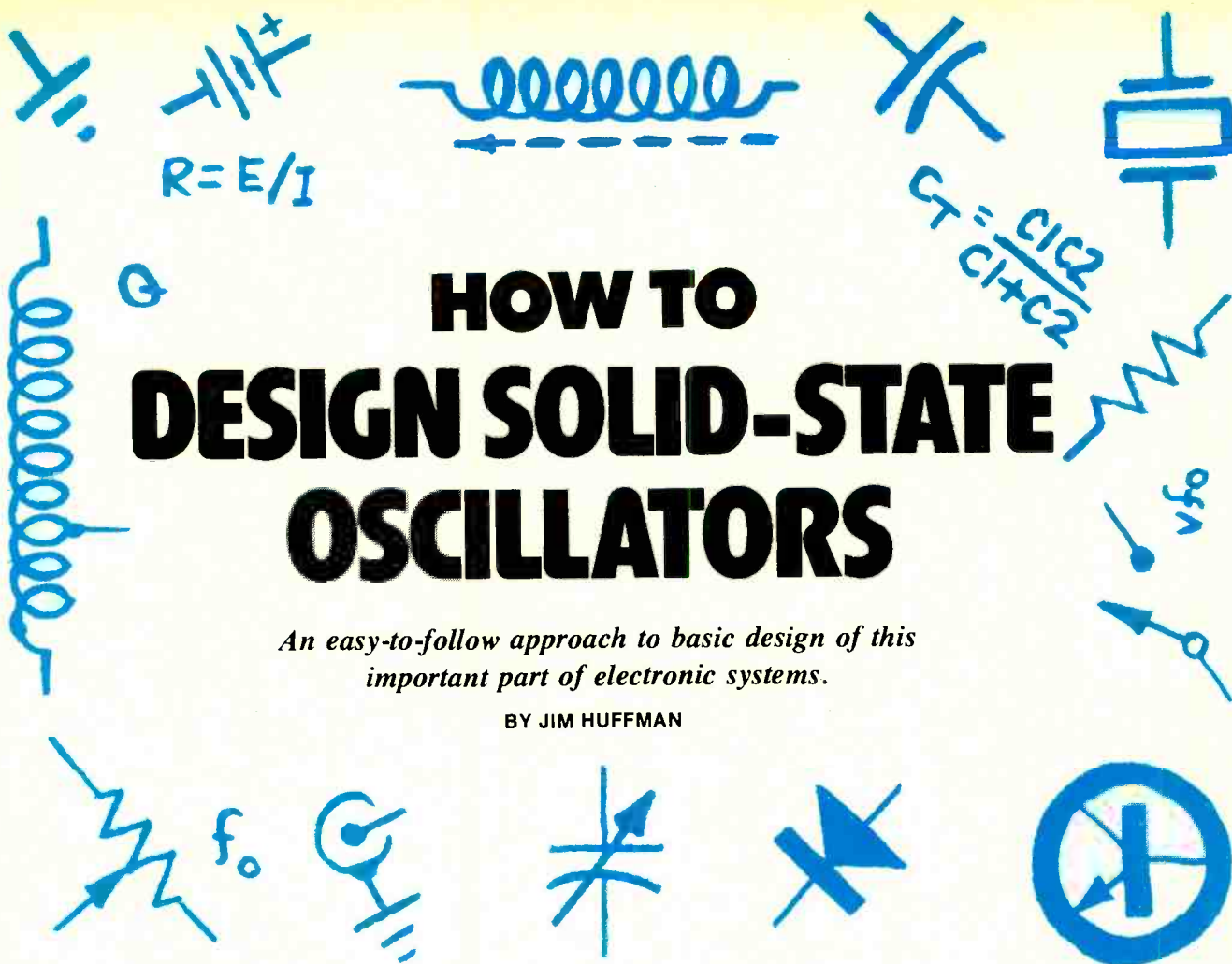

Five basic feedback oscillators are shown in Fig. 2. Each feedback network (tuned circuit) provides the proper phase shift to make the network output in phase with the amplifier's input. In the case of the RC (resistive-capacitive) oscillator, the phase shift in each RC network adds to those of the other networks to produce the total phase shift in the amplifier. Since the proper amount of phase shift occurs at only one frequency, the output frequency of the oscillator is predictable.

The real design problems come in deciding, for example, where to tap the Hartley oscillator's coil, determining the ratios of the capacitors in the Colpitts oscillator, and making sure that the losses in the RC oscillator do not exceed the amplifier's gain so that oscillation can occur.

In the following, we will deal mainly with the Colpitts oscillator, since it is representative of the others and is commonly used in vfo's and other exacting applications where stability must be very good. Another reason for focusing on the Colpitts oscillator is that it is capable of some rather high power levels and it makes a good crystal oscillator simply by replacing the coil with a crystal.

In approaching the design phase, we have three options. First, we can design for maximum stability and little output power. Or, we can forget about stability and go for a lot of power. Finally, we can compromise and design for as much as possible of both stability and output power. Our option will be dictated by the application in which the oscillator is to be used. Whichever option is decided upon, we will use the common-emitter circuit configuration because it yields good power and voltage gain.

**Designing the Oscillator.** Let us assume we want an oscillator for the vfo in a transmitter. This means that stability must be excellent and the waveform must be clean. Furthermore, the oscillator should be capable of delivering a clean 30-mW signal, which should hardly prove difficult, while maintaining a high degree of stability.

Figure a power supply potential of 9 volts, which can be obtained from an ordinary battery or a zener-diode or IC regulator. Plan on operating the oscillator class A for best stability with an output frequency in the 80-meter (3.5-to-4-MHz) band.

Begin your design by drawing a rough schematic of the oscillator circuit as shown in Fig. 3. Now, determine some of the basic parameters. Start with the load resistance, which is equal to the supply voltage squared divided by two times the output power ( $R_L = V_{cc}^2/2P_o$ ). In your calculations, let  $V_{cc}$  be 7 volts to allow some margin of safety. Then, using 7 volts,  $R_L$  comes out to 817 ohms, which you can round off to 800 ohms. Pencil in these figures in the appropriate places on your schematic.

The next step is to determine the value of inductance needed. For this, you will have to refresh your memory on Q—the figure of merit for a coil—which is a ratio between the dc resistance of the winding and the winding's reactance at some specific frequency. Most coils have a reasonable enough Q as long as the wire in the winding is not so thin that it inherently exhibits a high dc resistance. Note that our concern here is with the Q that is imposed on the coil by paralleling it with the 800-ohm load. This "loaded Q," or  $Q_L$ , is the ratio of the coil's reactance to the load resistance.

If your oscillator used a coil with 800 ohms of reactance and then powered up to 30 mW with an 800-ohm  $R_L$ , the ratio would be 800:800 (1:1), which would yield a 3.5-MHz bandwidth (output frequency/Q=3.5 MHz/1=3.5 MHz). Remember that bandwidth has a direct bearing on the Q; so, the narrower the bandwidth, the better the Q. (Of course, too high a Q would be detrimental.) A Q of 10 to 20 would be acceptable in our oscillator circuit.

Since the oscillator is to be used as the vfo in a transmitter, where we want the cleanest and most stable signal possible, we will settle for a Q of 20. Now, we must design our coil to have a reactance of 40 ohms.

Choosing a capacitor is a relatively simple task. Rearranging the capacitive-reactance formula  $X_C = 1/(2\pi fC)$ , we obtain  $C = 1/(2\pi fX_C) = 1/(6.28 \times 3.5 \times 10^6 \times 40) = 1.12 \text{ nF}$ . Round this off to 0.001  $\mu\text{F}$  (1000 pF). This would be the total capacitance in the circuit, which means that each of the two capacitors across the coil would have a value of approximately 0.002  $\mu\text{F}$  penciled in on your schematic. Total capacitance  $C_T = C1C2/(C1+C2) = 0.002^2/(0.002 + 0.002) = 0.001 \mu\text{F}$ .

**Feedback Selection.** So far, we have done only the easy work. Now we have to start the design of the oscillator itself. First, find a transistor that will give satisfactory performance at 3.5 MHz. A quick look through the manuals reveals that the Motorola HEP-50 transistor has plenty of gain at 3.5 MHz. But let's go a step further to insure that we obtain a stable vfo design.

It is time to identify the components in your schematic, and this time don't forget to draw in tuning capacitor C5. You should end up with a circuit like that shown in Fig. 4. Note that single battery biasing would be used for maximum stability.

It would seem that all you have to do is plug in 0.002- $\mu\text{F}$  capacitors for C1 and C2 to obtain the required 0.001- $\mu\text{F}$

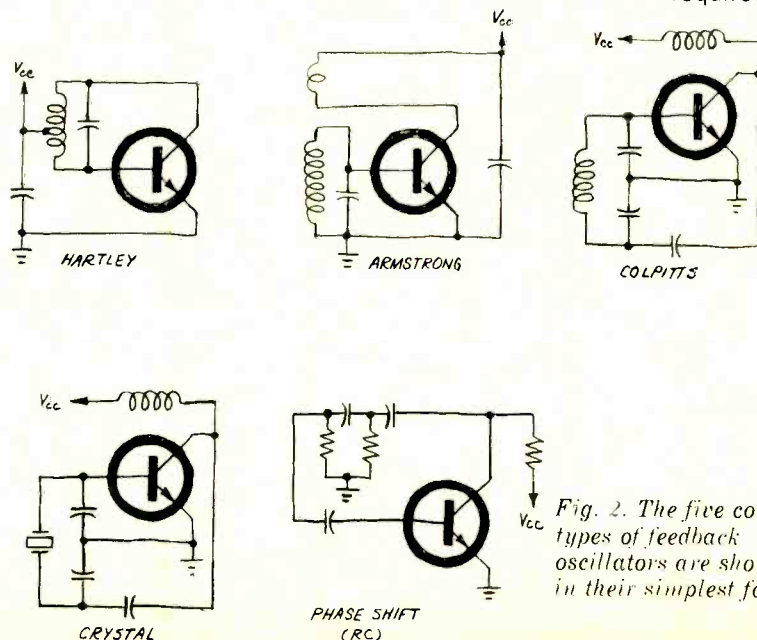


Fig. 2. The five common types of feedback oscillators are shown in their simplest forms.

figure. Make tuning capacitor  $C_5$  small in value—say, a few picofarads—and tweak the slug in coil  $L_1$  a little to lower the inductance to make up for the extra capacitance in the circuit. Then put in the correct biasing resistors.

We mentioned earlier the danger of having the feedback network deliver too much energy to the input of the amplifier. One way to keep the energy down is to add the resistor shown in phantom to reduce stage gain. In many cases, this would be valid. But if you go a step further, your approach will work in all cases.

You can find detailed information on how to design basic amplifier circuits in "Solid-State Circuits for the

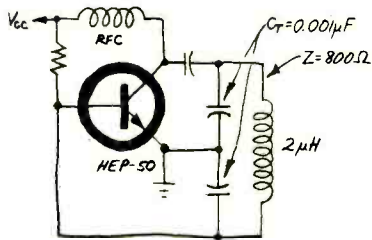


Fig. 3. Start with this basic Colpitts oscillator circuit.

Experimenter" (September 1972 POPULAR ELECTRONICS or 1975 Winter ELECTRONIC EXPERIMENTER'S HANDBOOK). If you can obtain a copy of either, refer to the box to help you fill in the values for the components in Fig. 4.

Use the information given in the box to determine the gain of the amplifier. We know that  $R_1$  is 800 ohms. From the information listed on the back of the transistor's box, we know that its  $\beta$  is 85. If you bias the transistor for class A operation, it will be in the middle of its operating range. From Ohm's Law, the maximum current the stage will draw will be:  $I = E/R = 9 \text{ volts}/800 \text{ ohms} = 11 \text{ mA}$ . If the stage is in the middle of its operating range, bias it for 5 mA with no signal. From the box, you can see that input impedance  $Z_{in}$  is about 400 ohms and stage gain is 160. Divide the gain by 4, which yields a gain of 40. (This is a handy rule of thumb for oscillators.) In designing a Hartley oscillator, you would now select a coil tap that would transform at a 40:1 ratio, and your design would be complete.

We now have a gain of 40. Using the two 0.002- $\mu\text{F}$  capacitors in series would divide the gain by 2 to yield an effective gain of 20. For maximum stability of the oscillator, however, we

want the gain to be roughly unity. It would seem logical to allow  $C_1/C_2$  equal 20 as in the Hartley oscillator design. However, we want power as well as stability from our oscillator. So, let us pursue another optimum approach to design: impedance matching. This means to obtain maximum power transfer within the oscillator and then adjust the amplifier's gain to obtain a clean output signal. We can assume that matching the impedances is the best approach when power is required from the oscillator.

The capacitive divider provides the impedance match. Impedance ratios in tuned circuits vary as the square of the turns ratio (in this case, the capacitive divider). Now, the object is to find two capacitors whose series capacitance equals about 900 pF, which allows 100 pF for the tuning capacitor ( $C_5$ ). Gain in the amplifier is reduced as necessary by the unbypassed phantom resistor.

Getting back to the design again, we must sift through a few simple algebra equations. First, the formula for total series capacitance ( $C_T$ ) is:  $C_T = C_1 C_2 / (C_1 + C_2)$ . The value of  $C_T$  in our example is 900 pF. Next, the ratio of  $R_{in}$  to  $R_{out}$  is  $R_{in}/R_{out} = (n_{in}/n_{out})^2 = [C_1/(C_1 + C_2)]^2$ , which translates to the simple formula for determining the value of  $C_2$ :  $C_2 = C_T \sqrt{R_{out}/R_{in}}$ . In our case,  $C_T = 900 \text{ pF}$ ,  $R_{out} = 800 \text{ ohms}$ , and  $R_{in} = 400 \text{ ohms}$ . So,  $C_2 = 900 \sqrt{800/400} = 1270 \text{ pF}$ . The value of  $C_1$  can be determined from the formula:  $C_1 = C_T / [1 - (C_T/C_2)] = 3100 \text{ pF}$ . Rounding out the two values, we obtain:  $C_1 = 1200 \text{ pF}$  (0.0012  $\mu\text{F}$ ) and  $C_2 = 0.003 \mu\text{F}$ .

With the oscillator set for maximum power gain, you must now add some negative feedback to obtain the cleanest output signal. The phantom resistor's value is easy to determine. When it comes time to assemble the circuit, temporarily connect a 500-ohm potentiometer between the transistor's emitter and ground. Adjust the pot, while observing the oscillator's output on an oscilloscope, for the cleanest possible waveform. Then, without touching the setting, remove the pot from the circuit and measure its resistance. Use a fixed resistor of the same or approximately the same value as that measured across the pot in the circuit.

From this point on, it is just finishing touches. The reactance of  $C_3$  should be roughly  $R_1/10 = 800/10 = 80 \text{ ohms}$ . Using the formula  $C = 1/(2\pi f X_C)$ ,


obtain a figure of roughly 570 pF, which can be rounded out to a more common 0.001- $\mu\text{F}$  value. The reactance of  $C_4$  should be at least  $R_{in}/5\beta$  or about 1 ohm in this case. (This value can be adjusted to prevent quenching.) The formula used for  $C_3$ , when applied to  $C_4$ , yields a value of about 0.05  $\mu\text{F}$ . To prevent the r-f choke's (RFC's) dc resistance from limiting the output of the oscillator, it should be considerably less than the 800-ohm value of  $R_1$ . A 2.5-mH choke would look like 55,000 ohms at 3.5 MHz, which should be very effective in comparison to the 800 ohms for  $R_1$ .

All that is left now is to assemble the circuit, using the calculated component values, and measure the parameters to determine if all is well with the design.

**Design Checkout.** The next step is to breadboard your design, preferably with perforated phenolic board and
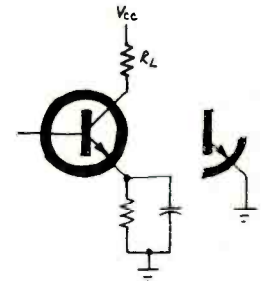
#### QUICK AMPLIFIER STAGE DESIGN

Shown below are some rules-of-thumb formulas you can use to design your own common-emitter amplifier stages. Combining this information with the design details given in the text, you can design a complete oscillator stage.



$$V_G \text{ (VOLTAGE GAIN)} \approx \beta (R_L / Z_{in})$$

$$Z_{in} \text{ (INPUT IMPEDANCE)} \approx \beta (R_1 / I_E)$$

\*  $I_E$  IS IN mA

$$I_G \text{ (CURRENT GAIN)} \approx 0.9 \beta$$

$$Z_{out} \text{ (OUTPUT IMPEDANCE)} \approx R_L$$



$$I_C \text{ (COLLECTOR CURRENT)} \approx I_E$$

$$I_E \text{ (EMITTER CURRENT)} \approx V_G / R_E$$

$$V_E \text{ (EMITTER VOLTAGE)} \approx V_G [R_2 / (R_1 + R_2)]$$

$$R_1 = [(R_2 V_{cc}) / V_E] - R_2$$

$$R_2 = 5 R_E$$

$$V_E = \text{VOLTAGE DROP ACROSS } R_E$$

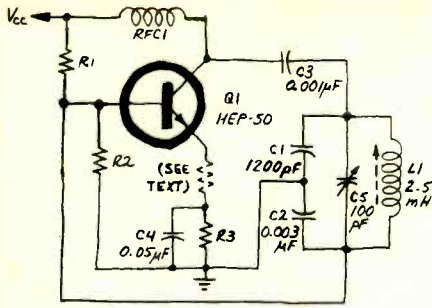


Fig. 4. Here we have added some values and a tuning capacitor.

solderless clips. This will permit you to adjust component values as needed before proceeding to final assembly. Test equipment that will be handy to have during checkout includes a variable power supply, a frequency counter for checking that the oscillator is on-frequency, an oscilloscope to view the output waveform, and a good general-coverage communication receiver to listen for signal purity and check for harmonics.

None of the above test equipment is essential. For example, you could use an ordinary 9-volt battery in lieu of a variable power supply. However, you will need at least a VOM (set to ac volts) or, better yet, an oscilloscope to check for the presence of oscillation.

You can check for instability, in the form of drift, by beating the oscillator's output signal against a known reference signal of good stability, such as from a crystal oscillator. Some of the sources of drift and instability are the input and output capacitances of the transistor itself, which can vary with bias, temperature, supply voltage, etc. There are also coil dimension changes that occur with changes in temperature and instabilities caused by capacitance changes with heating and cooling. All of these can be minimized or limited in some or all of the following ways.

Since transistor parameters vary with changes in bias, single-battery (or regulated-dc) bias systems should be used when stability is a critical factor. To keep the transistor's parameters from changing with variations in the supply voltage, regulate the  $V_{cc}$  line with a zener diode or IC regulator. Also, to keep capacitance changes in the transistor junctions at a minimum, use a high-Q, high-LC-ratio tuned circuit. (The major advantage of the Colpitts design is that  $C1$  and  $C2$ , whose values we took so much pains to calculate, tend to swamp out the varia-

tions in input and output capacitances.) The high LC ratios demand a coil of fewer number of turns, and the wire should be firmly wound on the coil form and held in place with coil dope to minimize dimension changes due to temperature changes.

High-quality capacitors, such as the silver-mica variety, will not be as susceptible to thermal drift as are other types of capacitors. The oscillator should be well ventilated, component leads should be kept short, and all components should be firmly mounted in place to minimize vibrational effects.

**Final Touches.** Under final touches, we rid our oscillator of spurious oscillations that are common in transistor designs. We will cover only a few of the problems likely to be encountered and their solutions. Most of the problems can be avoided at the time the circuit is still on paper.


One problem is "quenching" or "squegging." This is a lower-frequency oscillation often caused by too

minimized by bypassing both r-f and audio frequencies. Higher-frequency parasitics can be minimized by adding r-f chokes that act as high impedances at the parasitic and short circuits at the operating frequency. One such choke can be fabricated by slipping ferrite beads over component leads. You can make your own by winding a turn or two of enameled wire on a toroid core made from a tuning slug of a tunable coil. The hole runs lengthwise along the slug so that a few turns of No. 28 enameled wire wound through the hole makes an excellent parasitic choke.

The schematic diagram shown in Fig. 5 illustrates all design techniques that can be employed in an oscillator. It is doubtful, however, that all of these techniques will be needed in any given oscillator.

Once you've debugged your oscillator design, you can proceed to final assembly. The preferable medium would be printed-circuit board construction, but perforated board and solder clips will serve equally well.

Fig. 5. A completed oscillator circuit which may contain more refinements than you need.

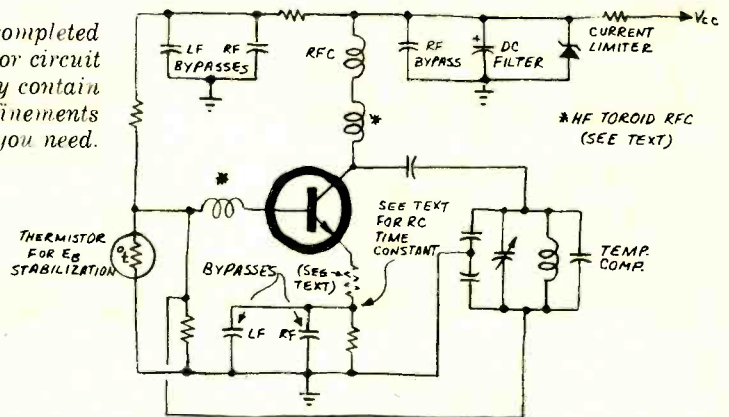

high a time constant in the emitter circuit bypass. It allows the emitter bypass capacitor to charge up to a voltage that eventually cuts off the transistor. This occurs repeatedly at some lower frequency and superimposes itself on the oscillator's output signal. The output signal is then loaded with spurious outputs that may occur every few kilohertz on the radio dial. When quenching occurs, reduce the time constant by making the values of  $R3$  and  $C4$  as low as possible and readjusting the bias circuits to compensate for the lower resistance.

Another problem is that of an additional high-frequency oscillation in the circuit. There can also be low-frequency oscillations caused by such things as the inductance of the r-f chokes. The lower frequencies can be

**In Conclusion.** We've covered one basic type of oscillator here. Obviously, there are many more. The oscillator and approaches used in its design in these pages are very simple and extremely dependable. Using the guidelines, you can design your own oscillator circuits. Special requirements, such as working at temperature extremes, super-high stability, etc., can all be achieved by starting with our modest approach.

You can design crystal oscillators that operate in the series mode by replacing the coil with a crystal in the Colpitts design. You can use pre-tapped coils in Hartley circuits and still design system gain for optimum oscillator performance by adding negative feedback. We can go on and on *ad infinitum*, but you get the idea. ♦






*Solid-state version  
uses LED's as  
the spinning ball.*

BY ROBERT D. PASCOE

# ELECTRONIC WHEEL OF FORTUNE

## SIMULATES MECHANICAL GAME

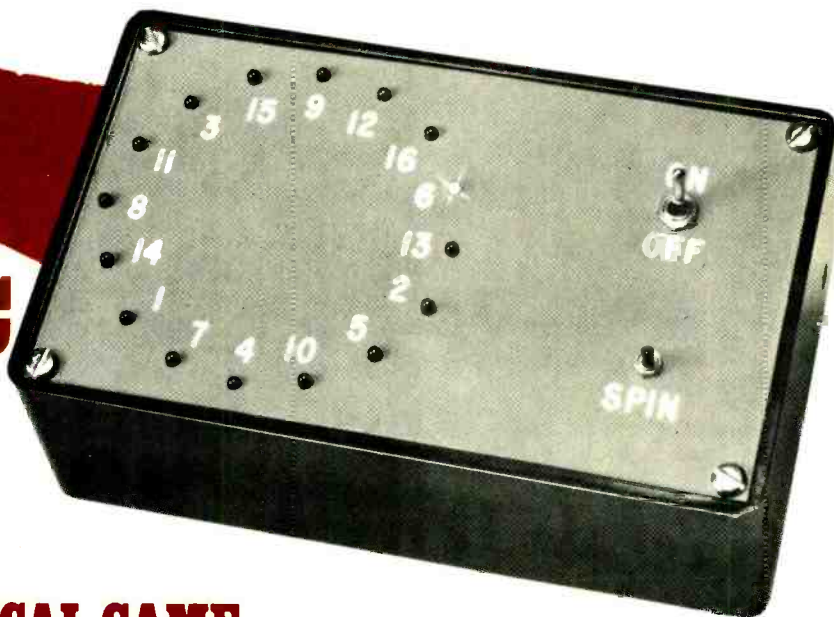

**T**HE WHEEL of fortune has always been one of the favorite games of chance. Perhaps it is because of the fascination of watching the wheel go around and around and not knowing where it will stop. You can build an electronic roulette which has little red lights going around and around, stopping eventually at a completely randomly selected number between 1 and

16. Players can select their number for each spin of the wheel, watch the lights, and collect their winnings if the light stops on their number. Like a mechanical wheel, the lights go fast at first and then slow down gradually before stopping at the winning number.

**Circuit Operation.** As shown in Fig. 1, a clock oscillator (*IC1*) operates at

about 100 Hz when the SPIN pushbutton is depressed. When the switch is released, a time constant in the circuit causes the oscillator to slow down to a stop in about 10 seconds. The output of the clock is conditioned for the TTL logic by transistor *Q1*.

To understand how the 16 LED's are operated, note that the combinations of numbers 1 and 9, 2 and 10, through 8 and 16 are driven by the output of the first flip-flop and the 8-bit shift register. However, the selection of which of the eight combinations is in the circuit at one time is made by the state of the second flip-flop. As the clock delivers pulses to the first flip-flop, the digital one level is propagated from 1 through 8 on the LED's.

At the eighth clock pulse, the output of *IC3* operates a one-shot (*IC2*). This causes the output flip-flop to change states, so that the second eight LED's are selected. Simultaneously, the first flip-flop and the shift register are

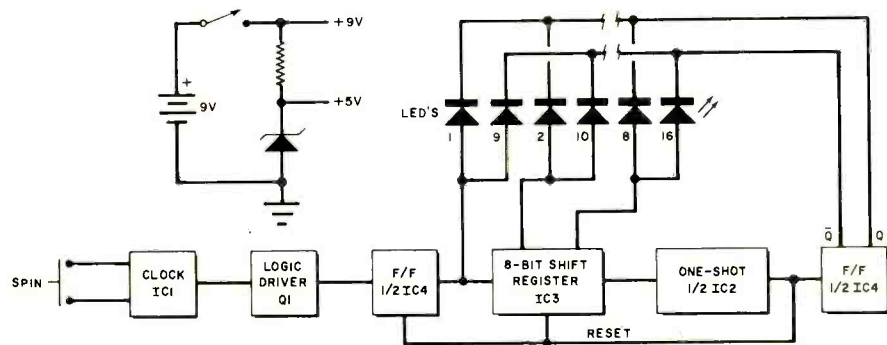


Fig. 1. Pressing the SPIN button starts the clock oscillator.

← CIRCLE NO. 33 ON FREE INFORMATION CARD

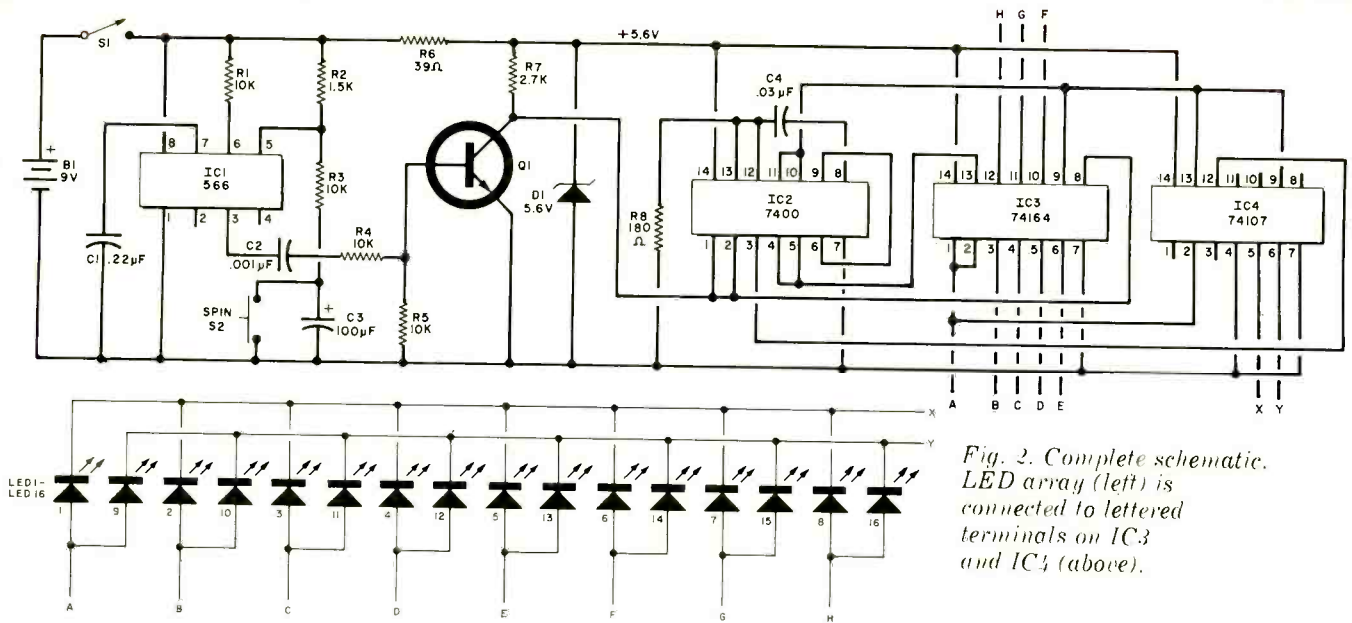


Fig. 2. Complete schematic. LED array (left) is connected to lettered terminals on IC3 and IC4 (above).

### PARTS LIST

- B1—9-volt battery (6 C cells)
  - C1—0.22- $\mu$ F capacitor
  - C2—0.001- $\mu$ F capacitor
  - C3—100- $\mu$ F, 15-V electrolytic capacitor
  - C4—0.03- $\mu$ F capacitor
  - D1—5.6-V zener diode
  - IC1—Function generator (566)
  - IC2—Quad 2-input NAND gate (7400)
  - IC3—8-bit shift register (74164)
  - IC4—Dual JK flip-flop (74107)
  - LED1 to LED16—Light emitting diode
  - Q1—Silicon npn transistor
  - R1, R3-R5—10,000-ohm, 1/4-W resistor
  - R2—1500-ohm, 1/4-W resistor
  - R6—39-ohm, 1/4-W resistor
  - R7—2700-ohm, 1/4-W resistor
  - R8—180-ohm, 1/4-W resistor
  - S1—Spst switch
  - S2—Normally open spst pushbutton switch
  - Misc.—Suitable enclosure, press-on type, C-cell holders, insulated wire, mounting hardware, etc.
- Note—The following are available from Hoffelt Electronics, 224 Opal Blvd., Steubenville, OH 43952: etched and drilled printed circuit board at \$5.00; case and engraved front panel at \$5.00; complete kit of parts at \$24.95.

reset. In this way, the same logic is used for all 16 LED's. The complete schematic is shown in Fig. 2.

**Construction.** The circuit can be assembled on perforated board or on a pc board such as that shown in Fig. 3. Be sure to observe the polarities and coding on all components and use a low-power soldering iron. Note that there are three jumpers on the board.

The prototype was housed in a plastic enclosure 6 1/2" x 3 3/4" x 2". As shown in the photo, the cover of the box was drilled for the 16 LED's arranged in a

circle. The holes should be just large enough to fit the tops of the LED's. The lights can be identified at random using press-on type. The two switches can be mounted on the cover as shown.

Since the project has a current drain of about 100 mA, six C cells, in holders mounted on the bottom of the enclosure, can be used. This allows about 10 mA for the LED's. Any color can be used for the LED's, but it is advisable to have a few extras so that they can be selected to have all 16 glow with about the same brilliance. ♦

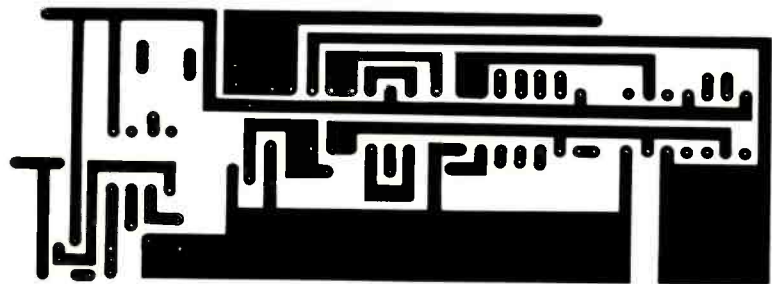


Fig. 3. Etching and drilling guide above; component layout below.


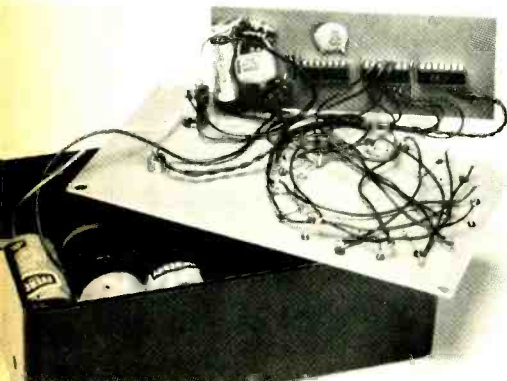
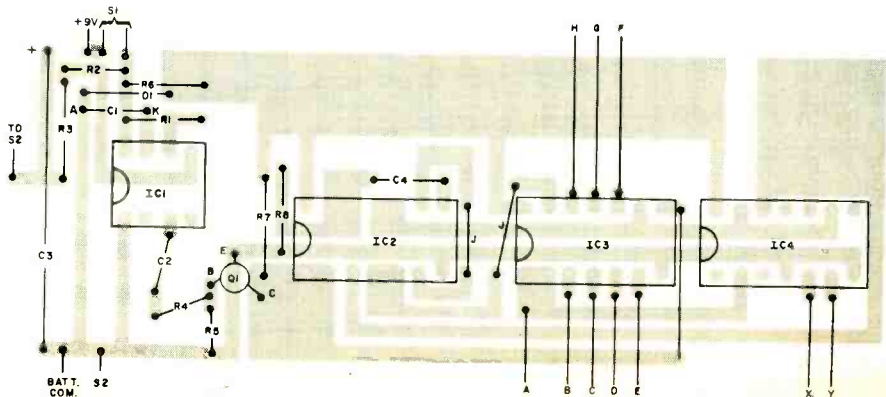


Photo shows how LED's were arranged on top of the enclosure.

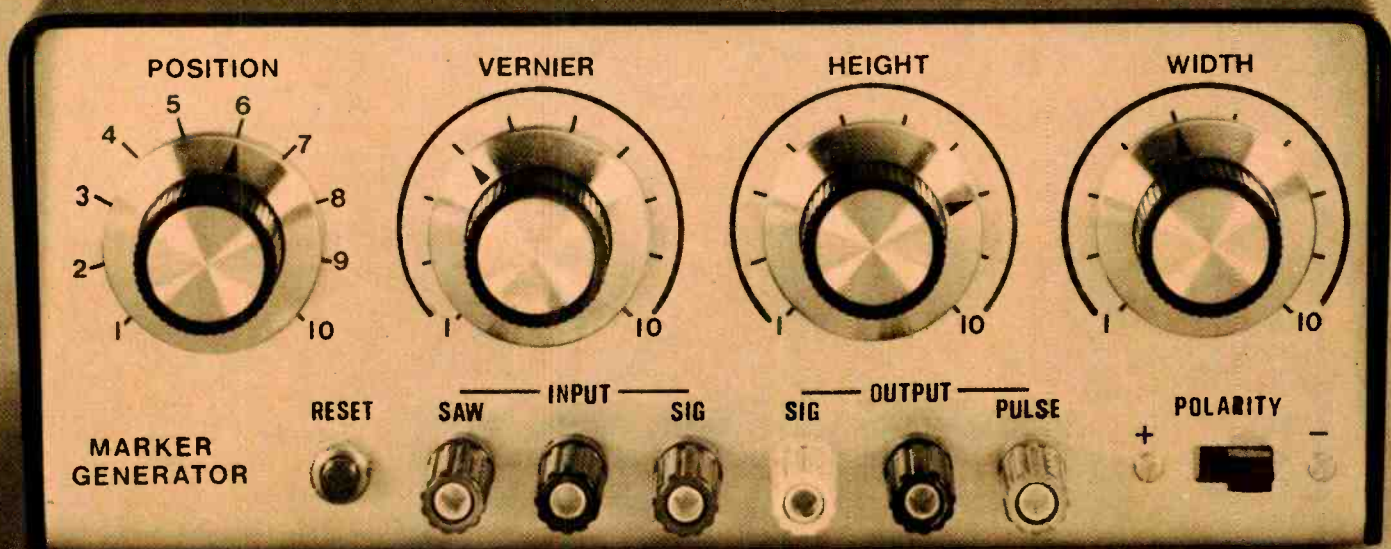

## BUILD AN **AUDIO SWEEP MARKER GENERATOR**

*Now you can easily identify any frequency on an audio swept waveform display.*

BY JON PAUL

**T**HE USE of a sweep generator is practically a necessity in any serious testing of audio equipment. Some sweep generators are not sufficiently calibrated however (especially for a logarithmic sweep) to provide an easy identification of an unusual response at a particular frequency. This can be easily remedied by mixing the output of a marker generator with the sweeper's output. Then, when the signal is displayed on a scope, a particular frequency can be identified.

The audio sweep marker generator described here provides two approaches to marker display. One is a sharp vertical pulse as shown in Fig. 1, which can be positioned on the scope at the frequency of interest. Or the pulse can be fed through the scope's intensity axis to generate a bright spot on the display. The marker automatically covers the same range as the sweeper being used, and the only condition required is that the sweeper's main sawtooth be available.


**How It Works.** The sawtooth output from the audio sweeper (the waveform within the sweeper that is performing the actual frequency sweep—not a

sawtooth audio output) is coupled to the marker generator through *BP1* as shown in Fig. 2. This signal is buffered in *IC1* and fed to *IC2* and *IC3*, which form a peak detector.

As the input rises in voltage, *IC2* places a charge on *C2* through *D1*. When a peak value is reached and the signal drops to zero, the output of *IC2* goes negative and *D1* is reverse biased. However, *C2* remains charged at the peak value of the sawtooth ( $V_{peak}$ ). When **RESET** pushbutton *S1* is depressed, *C2* discharges through *R3* so that, on the next sweep, a new value of  $V_{peak}$  is detected. Integrated circuit *IC3* is a unity gain buffer that prevents succeeding circuitry from loading *C2*. The output of *IC3* goes to *IC2* to supply the feedback necessary for the peak detection process. It is also applied to two adjustable voltage dividers—*R4*, which is used as a **VERNIER** control, and the resistor network associated with *S2*.

The voltages selected by *S2* and *R4* are mixed in *R14* and *R15* so that the input to *IC4* can be selected to be between 0 and 90% of  $V_{peak}$  in 10% steps with the vernier providing smooth adjustment between steps.

The output of *IC4* is applied to two comparators—*IC5* and *IC6*. Transistor *Q1* develops a constant current (*I*) in *R21* to produce an offset at the input to *IC5*. Thus one input to *IC4* is  $V_{ref}$  (from *IC4*) + ( $R21 \times I$ ). The other input is  $V_{sweep}$  from *IC1*. The output of *IC6* switches when  $V_{sweep}$  equals  $V_{ref}$  and the output of *IC5* switches slightly later due to the offset provided by *R21*.

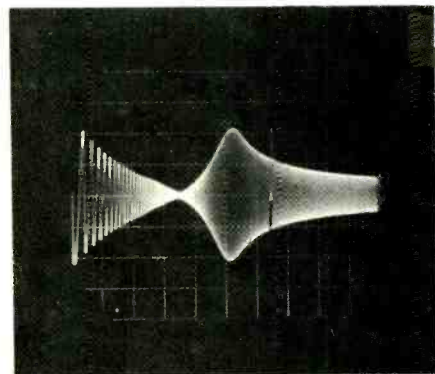

*Fig. 1 Photo of marker "pip" on a typical scope display.*

Diodes *D5* and *D6* and resistor *R27* form an AND gate whose output is negative only when *IC5* and *IC6* have negative outputs. This generates a

## PARTS LIST

- BP1 to BP6—Five-way binding post  
 C1, C6—0.001- $\mu$ F ceramic capacitor  
 C2—47- $\mu$ F, 20-volt tantalum capacitor  
 C3, C5—33-pF ceramic capacitor  
 C4—3.3-pF ceramic capacitor  
 C7, C8—150-pF ceramic capacitor  
 D1 to D9—1N914 diode  
 IC1—741 op amp  
 IC2 to IC6—301A op amp  
 Q1—2N4250 transistor  
 Q2—2N3642 transistor  
 Following resistors are  $\frac{1}{4}$ W, 10% unless otherwise noted  
 R1, R30—4700 ohms  
 R2, R18—8200 ohms  
 R3—10,000 ohms  
 R4—10,000-ohm linear potentiometer  
 R5 to R13—1000-ohm, 1% carbon-film  
 R14—2-megohm, 1% carbon-film  
 R15—221,000-ohm, 1% carbon-film  
 R16—200,000 ohms  
 R17, R27—2200 ohms  
 R19—2-megohm linear potentiometer  
 R20—160,000 ohms  
 R21 to R24, R34—22,000 ohms  
 R25, R26—10 megohms  
 R28, R29—27,000 ohms  
 R31—6800 ohms  
 R32—20,000-ohm linear potentiometer  
 R33—100,000 ohms  
 S1—Spst normally open pushbutton  
 S2—10-position, single-pole rotary switch  
 S3—Spdt switch  
 Misc.—Suitable enclosure, knob (4), dry transfer lettering, mounting hardware, etc.  
 Note—The following is available from MITS Inc., 6328 Linn. N.E., Albuquerque, NM 87108: complete kit including prepunched board and cabinet (MG-1K) at \$98; complete kit without cabinet and hardware (MG-1P) at \$71; pc board alone (MG-PC) at \$8; assembled unit, with 90-day warrantee (MG-1A) at \$138. Add \$5 for postage and handling on all items except for pc board alone.

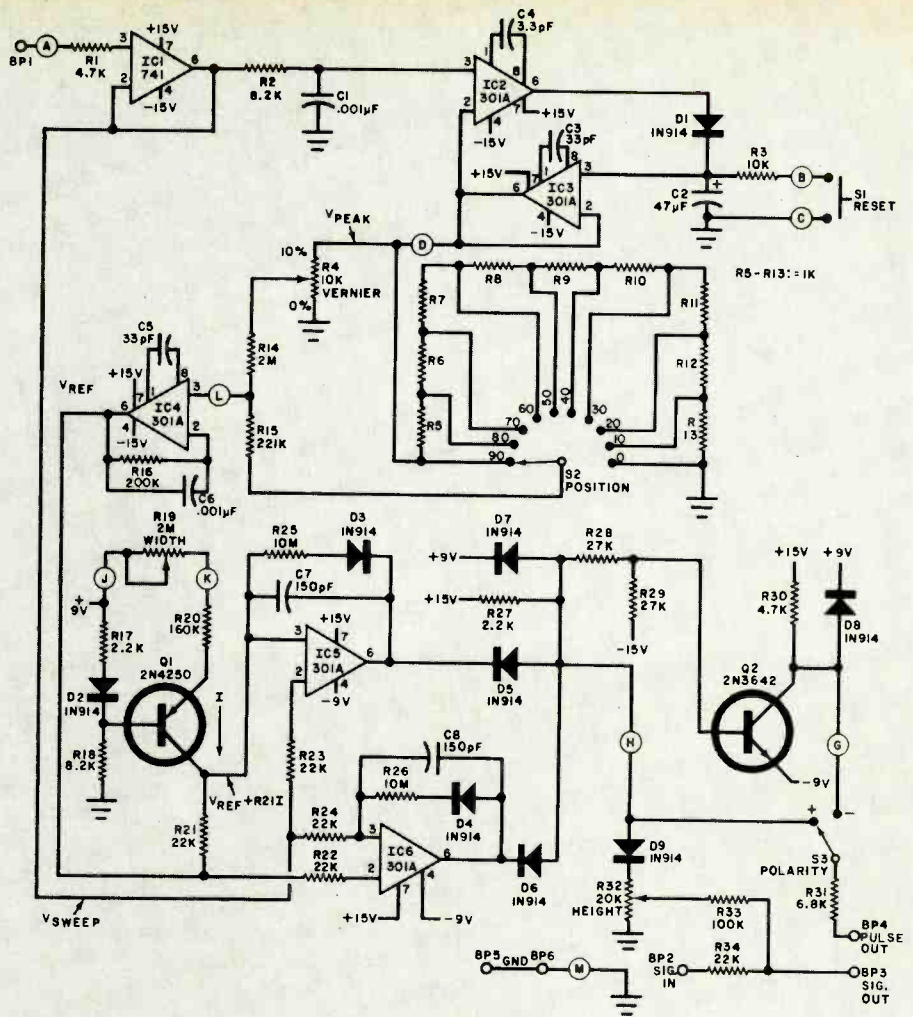


Fig. 2. Position of marker pulse is determined by S2 and R4, while width and height are controlled by R19 and R32.

pulse which is negative only when  $V_{\text{sweep}}$  is greater than  $V_{\text{ref}}$  but less than  $V_{\text{ref}}$  plus the offset. The width of the pulse is proportional to  $I$ . Since the current is determined by the setting of R19, the setting controls the width of the pulse. The various waveforms involved are shown in Fig. 3.

The pulse from the AND gate is applied to the base of Q2, which is an inverter. POLARITY switch S3 can then select either a positive or an inverted pulse. The mixed marker is formed by adding a variable-amplitude pulse from R32 to the swept audio signal connected to BP2.

**Construction.** The circuit can be built on a pc board such as that shown in Fig. 4. Be sure to obtain proper orientation of the diodes, the IC's and C2.

The marker generator requires four power sources:  $\pm 9$  and  $\pm 15$  volts. These may be available in the sweep generator (as they are in the unit described in the October 1973 issue of POPULAR ELECTRONICS). Or small sepa-

rate supplies can be constructed. The two 15-V sources can be unregulated and any value between 13 and 17 V. The 9-V sources should be regulated (using zener diodes) and can be derived from the 15-V supply.

The front panel of the chassis should be large enough to accommodate the POSITION switch (S2), the VERNIER potentiometer (R4), the HEIGHT control (R32), the WIDTH control (R19), the RESET switch (S1), the POLARITY switch (S3), and six input and output connectors.

The vernier potentiometer should be calibrated for 1% increments by measuring its resistance in 10% steps. The switches and connectors should also be marked as shown in the photograph.

**Operation and Use.** No calibration of the circuit is necessary since the peak detector works automatically.

Connect the sweep and marker generators to the unit being tested and the scope as shown in Fig. 5. The marker's POLARITY switch determines the type of intensity modulation (bright or dark marker), while the HEIGHT control varies the marker am-

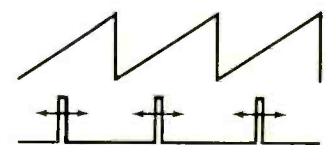
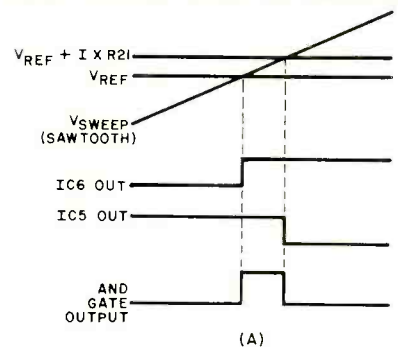


Fig. 3. Pulse is generated as shown at (A). Position can be varied as shown at (B).

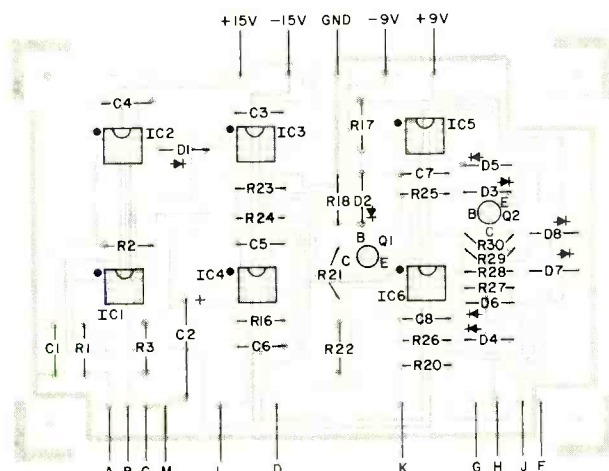
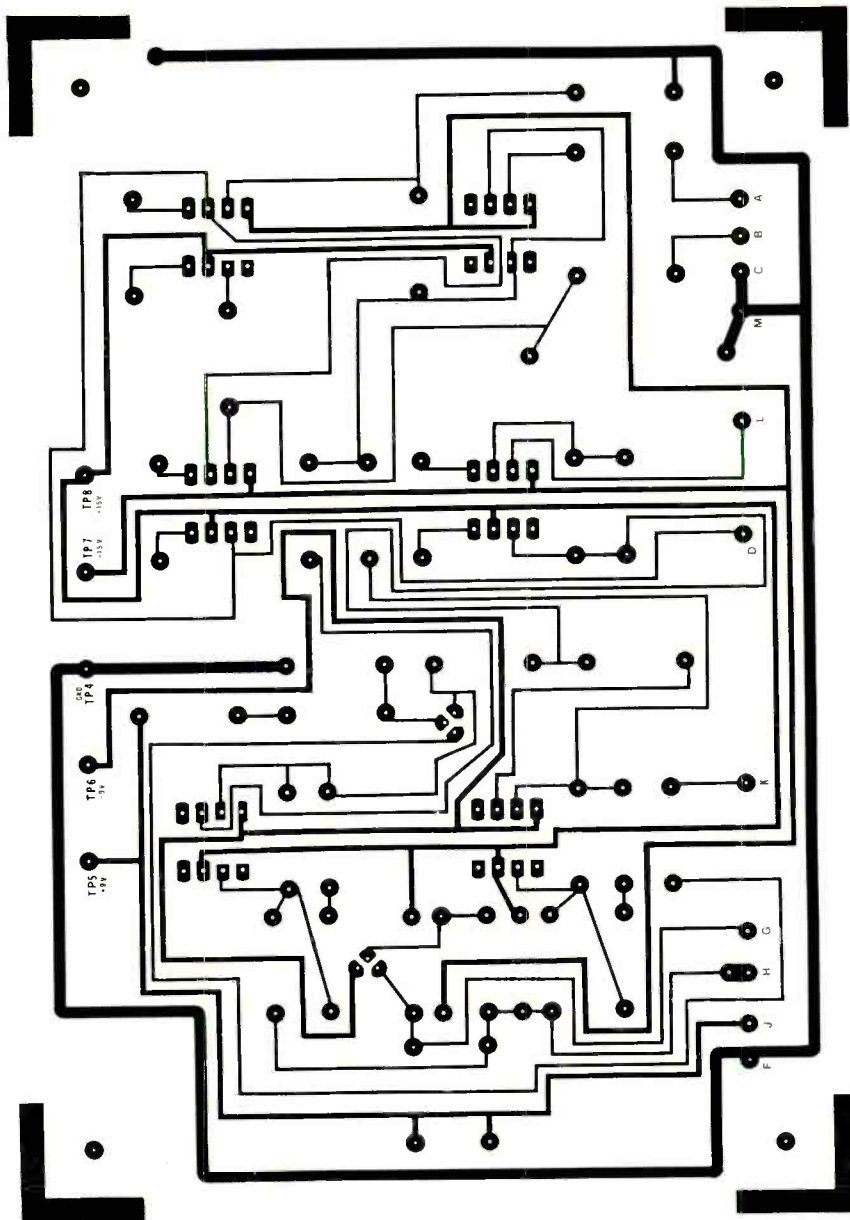


Fig. 4. Actual-size foil pattern is at top; component layout below. Lettered pads correspond to those on schematic and are used for interconnections.

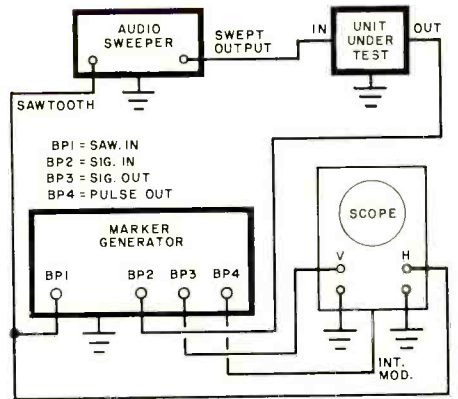


Fig. 5. Interconnections for setting up a test.

plitude. Three types of display are shown in Fig. 6.

The accuracy of the marker generator is determined by the matching of  $R5$  through  $R13$  (all 1% resistors). The sweep linearity of the scope, however, will rarely be better than 2%.

RESET pushbutton  $S1$  is rarely used. If the marker suddenly shifts position on the display, or if high-value markers cannot be displayed, a noise pulse

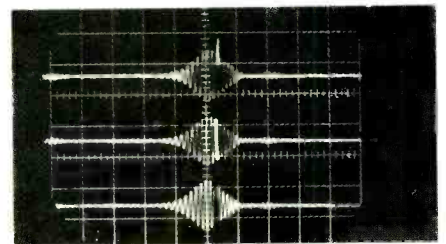


Fig. 6. Pip marker is at top. Bright and dark intensity markers in display at center and bottom.

has probably disturbed the peak detector. In this case, depress  $S1$  so that the circuit will automatically recalibrate itself on the next peak.

Assuming that the sweep generator is set to operate in the linear mode between 0 and 10,000 Hz and you want to determine the frequency of a "glitch" near the center of the display, proceed as follows. Set the marker generator for the type and amplitude of marker desired and adjust the POSITION switch until the marker is just below the frequency of interest. Then adjust the VERNIER to refine the position. If the POSITION switch is at 5 and the VERNIER at 7, the marker frequency is 57% of the swept frequency, or 5700 Hz.

Note that there are no "frequency" dials on the marker generator—only percentages of swept frequency. ♦



# Product Test Reports

## ABOUT THIS MONTH'S HI-FI REPORTS

The truly novel aspects of Sony's new Model TA-4650 integrated stereo amplifier, reviewed here, are not readily obvious. This is one of the first consumer audio products to use the recently developed "Vertical FET," or V-FET, in its power output stages. The V-FET has been heralded for its electrical characteristics (similar to those of a triode vacuum tube) and its exceptional power-dissipation capability and ruggedness.


Since Koss is one of the leaders in the development of stereo headphones, we would expect it to come up with something out of the ordinary in 4-channel phones. On testing the company's new Phase/2 + 2 phones, we have not been disappointed. They offer some surprises—such as "rear" drivers located in front of the "front" drivers—and one of the most unusual features is an integral "Programmer" control box that lets the listener adjust sound quality to his personal taste, making available 127 different combinations. Even if you do not yet own a 4-channel system, the Phase/2 + 2 phones can simulate an excellent "surround-sound" effect from ordinary stereo programs, and they are almost as much fun to experiment with as to listen to seriously.

Audioanalyst's new Model A-200X speaker system, with five drivers, is priced to compete with some very fine systems. Judging by its many attributes—unusually high accuracy, moderately high efficiency, and excellent listenability—it should be a formidable competitor.

—Julian D. Hirsch
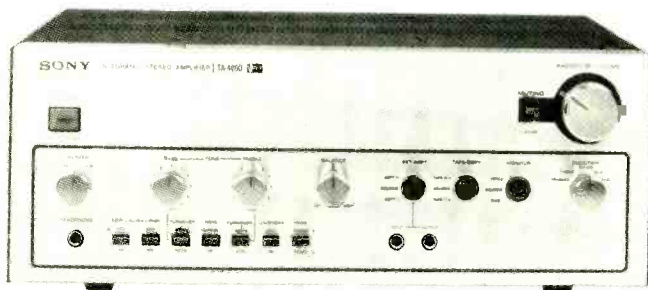
## SONY MODEL TA-4650 V-FET STEREO AMPLIFIER

Versatile control amplifier features no crossover distortion.



Several Japanese manufacturers have recently begun to market audio amplifiers using the vertical field-effect transistor. The V-FET has characteristics that closely match those of an ideal triode vacuum tube. It is inherently immune to thermal runaway which can destroy a bipolar transistor, has the high input impedance of low-power FET's, and is capable of dissipating very large amounts of power.

The Sony Model TA-4650 is the first V-FET amplifier we have had an opportunity to test. It is an integrated stereo amplifier, rated at 30 watts/channel into 8-ohm loads with less than 0.1% distortion over a frequency range of 20 to 20,000 Hz. In addition to its technical circuit innovations, this is a highly versatile control amplifier.

The amplifier measures 16 7/8"W × 12 3/4"D × 6 5/8"H (43 × 32 × 17 cm) and weighs about 25.5 pounds (11.5 kg). Its retail price is \$400.



**General Description.** The styling of this amplifier differs from that of previous Sony hi-fi products, but it matches that of the company's new Model ST-4950 tuner. The lower portion of the satin gold panel has most of the operating controls, including the bass and treble, balance, and speaker selector controls, as well as the source selector switch. The amplifier can handle two pairs of speaker systems and has two magnetic phono-cartridge and three high-level inputs. There is also a stereo headphone jack on the front panel.

A row of small pushbutton switches provide for operating the low- and high-cut filters, loudness compensation, and stereo/mono selection. One switch permits the tone controls to be bypassed, and two other switches provide a choice of turnover frequencies of 250 or 500 Hz in the bass and 2500 or 5000 Hz in the treble ranges. The tone controls each have 11 detented positions.

Three-position lever switches give the amplifier much of its flexibility. One is a tape-monitor switch for controlling two tape decks; in its center position, the normal program is heard. Another is the tape-copy switch that connects the two decks to copy tapes from either one to the other. Finally, there is the EXT ADPT switch that is similar to the monitor switch except that it is intended for connecting into the circuit (following the tape recorders) such accessories as an equalizer or a quadraphonic adapter. In one of the EXT ADPT switch's positions, two adjacent stereo phone jacks on the front panel are used to connect the accessory device, while the connectors are on the rear apron when the switch is in its alternate position. The EXT ADPT feature can also be used with one or two more tape decks, but it does not offer the tape-copying feature.

At the upper right of the front panel is the large VOLUME control knob. A concentric PRESET ring can be set to provide a light detent at any position of the VOLUME control's rotation for conveniently returning to a previous setting. A small lever to the left of the VOLUME control can be used to reduce the volume by 20 dB for temporary interruptions or while lowering the pickup onto a record surface.

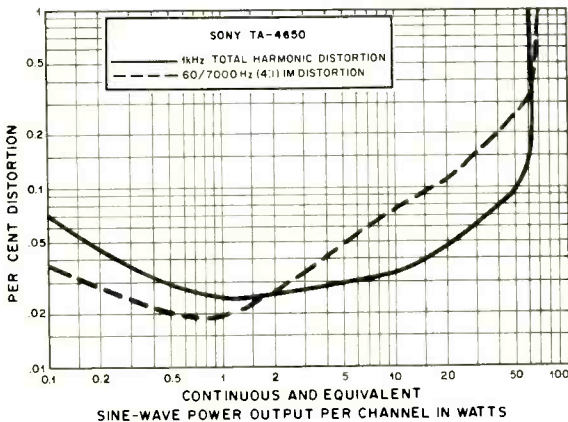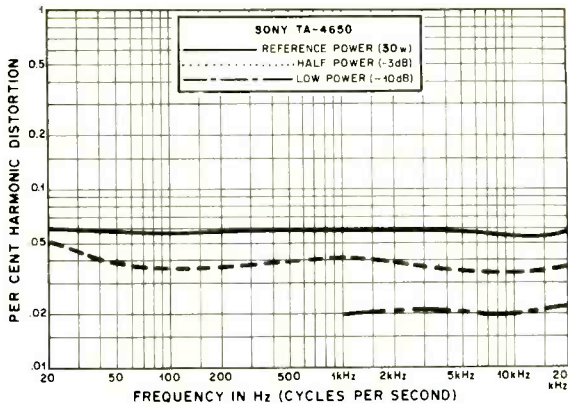The input and output connectors are located on the rear apron of the amplifier. They include a DIN socket for duplicating the functions of the



TAPE 1 inputs and outputs. Insulated springloaded clips are used for the speaker system connectors. The preamplifier outputs and power amplifier inputs are brought out to separate jacks that are normally joined by jumper plugs.

The rear apron also has three accessory ac outlets on it. One of these is unswitched.

**Laboratory Measurements.** When we put the amplifier through its one-hour preconditioning period at 10 watts output power, it became quite warm. However, it displayed no signs of distress. Driving both channels into 8-ohm loads at 1000 Hz, the outputs clipped at 64.4 watts/channel. With 4- and 16-ohm loads, clipping occurred at 75.7 and 39 watts/channel, respectively. It is interesting to note that, when both pairs of speakers are driven simultaneously, they are connected in series so that the amplifier will never have to drive an impedance of less than 4 ohms even if two 4-ohm speaker systems are used.

The 1000-Hz THD, which was below the noise level at outputs of less than 1 watt, measured 0.024% at that level. It increased smoothly to 0.062% at the rated 30 watts and to 0.14% at 60 watts just before clipping occurred. The IM distortion was less than 0.02% at about 1 watt and rose to 0.11% at 30 watts and to 0.36% at 60 watts.

Clearly, Sony has very conservatively rated this amplifier. At the rated 30 watts/channel into 8-ohm loads, the THD was an almost constant 0.06% from 20 to 20,000 Hz. At lower power levels, it was also constant with frequency and measured slightly less than at full power.

The amplifier has a fast-acting relay that disconnects the speaker systems in the event of severe overdriving or an internal malfunction. We tripped it a number of times without causing any damage. The amplifier came on automatically a few seconds after the fault was removed. The relay also provides a turn-on time delay of 5 or 6 seconds to keep transients away from the speaker systems.

An input of 60 mV at the high-level input jacks or 1 mV at the phono jacks drove the amplifier to a reference 10-watt output. The respective noise levels measured -73 and -76 dB. The fact that the phono noise was actually less than the high-level noise probably reflects Sony's use of special low-noise transistors of the company's own design in the phono preamp section. The phono input overloaded at the very high input level of 380 mV.

The tone controls had a rather moderate range of  $\pm 10$  dB at the frequency extremes, but the choice of turnover frequencies gives them better than average flexibility for a bass/treble configuration. The filters had gentle

# Olson Electronics Parts and Accessories

## SALE

### DUAL IN-LINE IC'S

Made in U.S. These IC's are guaranteed against defects. With diagram. Shpg. wt. 1/4 lb.

**LOW AS 29c**

Type 7400 Quad 2-Input Pos. NAND Gate. High speed, diode-clamped inputs.  
 TR-431, Reg. 69c Sale 29c  
 Type 7402 Quad 2-Input Pos. NOR Gate. Low-noise. Propagation delay, 12 ns.  
 TR-432, Reg. 69c Sale 29c  
 Type 7404 Hex Inverter. Low noise, low power dissipation.  
 TR-433, Reg. 79c Sale 29c  
 Type 7410 Triple 3-Input Pos. NAND Gate. Low output impedance. diode-clamped inputs.  
 TR-434, Reg. 69c Sale 29c

Type 7447 BCD to 7-Segment Decoder/Driver. With common anode displays.  
 TR-435, Reg. 2.99 Sale 99c  
 Type 7473 Dual J-K Master Slave Flip-Flop.  
 TR-436, Reg. 1.19 Sale 39c  
 Type 7474 Dual D-Type Edge Triggered Flip-Flop.  
 TR-438, Reg. 69c Sale 39c  
 Type 7475 4-Bit Latch. Temp. stores binary coded info.  
 TR-437, Reg. 1.89 Sale 79c  
 Type 7490 Decode Counter. Binary coded decimal counter with symmetrical divide.  
 TR-439, Reg. 1.89 Sale 79c

### Rechargeable Battery With Charger

6 VDC alkaline rated @ 5 amp/hr. Max. current 1.25 amp. Eveready Reg. #565 4 lbs. 9.98 BA-307. Sale 4.99

**4.99**

### BIG 1 LB. Resistor Kit

Over 400 pieces of 1/2, 1 watt sizes. All color coded. 2 1/2 lbs. RS-239. 99c

**99c**

### 500-ft. Hook-Up Wire

For almost any type of printed circuit or wiring project. 2 lbs. WW-579. Sale 1.69

**1.69**

### PNP Transistors

Big 10 pc kit. For general, io & hi-gain & audio Germanium types. Untested 1/4 lb. TR-445. Sale 39c TR-444. NPN. 39c

**39c**

### 3-6 VDC Motors

Kit / 5 Small 1/2 lb. MO-333. Sale 55c  
 Kit / 4 Med. 1 lb. MO-334. Sale 79c  
 Kit / 4 Ass'd. 2 lbs. MO-335. Sale 99c

**59c**

### Three 60-Min. Cassettes

Pkg 3 quality cassette recording tapes. 60-Min. each 1/2 lb. TA-879. Sale 99c

**99c**

### 12-Digit IC Calculator Chip

40-pin DIP single CAL-Tech #CT-5001 7-seg. decoded display output. overflow lock-out. Specs. Incl.

**1.59**

Reg. 5.98 XM-330. Sale 1.59

### 8-T Blank Tape

Famous manufacturer's high quality low priced tapes 1/2 lb. TA-854. 40-Min. 89c TA-855. 80-Min. 99c

**89c**

### 50-Pc. 1 Amp Diode Kit

Polarity is unmarked but easily identified with ohm meter. 200 PIV rated. 1/2 lb. DI-051. Sale 69c

**69c**

REG. 1.69

### Silicon Rectifiers

1 Amp Epoxy Type Pkg. 5 4 oz.

Reg. Sale  
 DI-028 50 PIV IN4001 89c 39c  
 DI-029 100 PIV IN4002 99c 39c  
 DI-030 200 PIV IN4003 1.19 39c  
 DI-031 400 PIV IN4004 1.39 39c

### Switching Diodes

Pkg. of 10 IN4148 for low current applications. 10 mA-75 PIV 1/2 lb. XM-382. Sale 59c

**59c**

Reg. 1.29

### LED'S 2V 10 mA

Gallium phosphide. Large red, high quality LED. Wt. 1/2 lb. Pkg. 5 PL-233. Sale 59c

**59c**

Reg. 1.19

### FREE Olson Catalogs

WITH THOUSANDS OF ELECTRONIC BARGAINS

Next 7 Issues FREE!

FREE Send Today!

### SCR Assortment

Hobby Pak of asst. values & case types. Pkg. of 25. Untested. Wt. 1 lb. TR-446. Sale 99c

**99c**

Reg. 2.69

**ORDER TODAY!** Send to Olson Electronics, 260 S. Forge St., Akron, Ohio 44327. Allow for postage. C.O.D. 20% Deposit. Ohio Residents Add 4% Sales Tax.

**Olson electronics** Dept. IC  
 260 S. Forge St., Akron, Ohio 44327

NAME \_\_\_\_\_  
 ADDRESS \_\_\_\_\_ APT \_\_\_\_\_  
 CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

6-dB/octave slopes with the -3-dB response points at 30 and 7500 Hz. The loudness compensation boosted the lows, and to a lesser degree the highs, at low volume settings. The RIAA phono equalization accuracy was within  $\pm 0.5$  dB from 100 to 20,000 Hz. It rose to +1.5 dB between 20 and 40 Hz. The equalization was virtually unaffected by cartridge inductance since the equalization components are almost completely isolated from the phono circuits.

**User Comment.** The Model TA-4650 is a notable amplifier both for what it does and for what it does not do. First of all, it obviously has just about all of the operating versatility one could desire. Certainly, one could hardly ask for better electrical performance than

our laboratory tests revealed. What this amplifier does *not* have (and in this respect, it lives up to the advance publicity for V-FET devices) is crossover distortion or any other higher-order harmonics in its output. At normal listening levels of up to 10 or 20 watts output, the distortion is almost pure second harmonic in nature, with a little third harmonic appearing at power levels above 30 watts.

If you are a true believer in the mystical properties of "vacuum-tube" sound, perhaps you will find the sound of this amplifier comparable to that of a very good tube-type amplifier. For our part, we see and hear it simply as a first-rate amplifier, devoid of any identifiable distortion or other sonic properties. It has no flaws or operating vices we could discover. Its sound

quality is certainly as good as there is, and its construction is superior to most other amplifiers on the market.

Judging from the fairly warm idling temperature, the two V-FET devices in each channel operate at a relatively high quiescent current, which lets them avoid the problem of crossover distortion. The exceptional ruggedness and heat dissipation ability of the V-FET is obviously one of its strong points, and Sony has apparently made good use of these characteristics.

Whatever reason Sony might have had in rating this amplifier at 30 watts/channel, it is plain to us that it is really more appropriate to call it a 60-watt/channel amplifier. Therefore, it is certainly a lot of amplifier, even at its moderately high price.

CIRCLE NO. 65 ON FREE INFORMATION CARD

## KOSS PHASE/2 + 2 QUADRAFONE 4-CHANNEL HEADPHONES

*Unusual design, with programmer, provides variable listening characteristics.*



Most 4-channel headphones have two drivers in each earcup, one located ahead of

and the other behind the listener's ear. Sometimes the two drivers in each earcup have different response characteristics to help the listener to distinguish between the front and rear channel sounds. Unfortunately, most attempts at making true quadraphonic sounds in headphones have been unsuccessful, but a few notable exceptions have recently emerged. One is the new Koss Phase/2 + 2 Quadrafone, with phones and control box as part of an integrated system. It comes close to providing a relatively realistic 4-channel sound effect by employing a radically different design approach than is found in other quad-

raphonic phone systems, as will be described later.

The Koss phones are only slightly bulkier than stereo phones. This is due to the small size of the forward earcup extensions. The large areas of the ear cushions make these phones comfortable to wear for extended listening periods. The phones are designed to be driven from sources with impedance ratings between 3.2 and 600 ohms. They are also designed to produce a 90-dB sound-pressure level (SPL) with a 1-volt, 1000-Hz drive signal. The maximum input signal rating is 10 volts. When delivering a 100-dB SPL at 1000 Hz, the phones' THD (total harmonic distortion) is specified at less than 1%.

The Koss Phase/2 + 2 Quadrafone is list priced at \$145.00, which includes the control box.

**General Description.** The front channels of the phones consist of 2" (5.1-cm) dynamic drivers that are positioned directly over the listener's ears. The rear-channel drivers are 1½" (3.8 cm) in diameter and are located in *front* of the drivers for the front channels, in forward extensions of the earcups.

The outsides of the molded plastic earcups are perforated to provide the correct loading to the rear of the drivers. The foam plastic ear cushions provide only slight isolation from outside sounds, giving these phones

much of the "open" sound quality of good nonisolating phones.

The 4' (1.22-meter) cords from the earcups terminate in the small control box that comes with the phones. The box is about the size and shape of a pocket calculator. Exiting from the box is a 10' (3-meter) long coiled cord that goes to the front- and rear-channel phone plugs of an amplifier or receiver. The controller (Koss calls it a "Programmer") contains eight slide switches that permit the listener to alter the spatial and frequency response characteristics of the system over a wide range. There are, in fact, 127 different combinations of switch settings available.

Koss engineers have determined that much of the front-to-rear sound resolution of the human ear depends on the different characteristics of the sound arriving from two directions. (Don't confuse this with the more general concept of directional localization, which is the basis for the various 4-channel matrix systems.) Since the sound from the front carries the primary program information, the front drivers were placed where their full frequency range would be most effective—directly over the ears. Locating the rear-channel drivers behind the ears caused the listener's external earlobes to adversely affect the sound quality. So, putting the drivers forward of the ears and carefully tailoring their frequency response, the sub-



jective effect of a sound source to the rear was achieved in the new phones.

The Programmer has a QUAD COMPARATOR switch whose CH4 position connects the drivers in the phones directly to the corresponding signal inputs. The other switch position, labelled  $\phi 2 + 2$ , is intended primarily for synthesizing 4-channel effects from ordinary 2-channel stereo programs. It can also be used to modify 4-channel programs. In the  $\phi 2 + 2$  mode, two BINAURALATOR switches permit partial blending of the left and right signals, with independent control of the front and rear channels. A QUAD FIELD switch is provided for altering the relative contributions of the front and rear drivers to simulate a basically front-located source ( $2\pi$ ) or a full surround sound ( $4\pi$ ). Four AMBIENCE EXPANDER switches that can be used in either the CH4 or the  $\phi 2 + 2$  mode permit reversing the phase of each driver individually.

**Laboratory Measurements.** Our measurements of these phones were limited to evaluating their performance and to verifying the actual circuit functions of the Programmer switches. Using a Koss-designed coupler, we measured a frequency response of 20 to 20,000 Hz  $\pm 5$  dB, with a slight dip at 2500 Hz. The rear drivers had a similar frequency response but with somewhat lower output level at frequencies above 5000 Hz. They also had a 6-dB rise at 300 Hz, with the curve exhibiting a rapid decline in output at lower frequencies. With a 3-volt drive signal applied, the front drivers generated between 90 and 100 dB SPL over most of the audio range.

The QUAD FIELD and BINAURALATOR switches had little effect on the frequency response, but they made a great difference in the sound. The phase reversal introduced by the AMBIENCE EXPANDER switches had the predictable effect of almost cancelling out the midrange sound in either earcup when its two drivers were operated out-of-phase with each other and had little effect at low frequencies, where the two drivers had dissimilar output levels.

The impedance of the phone system measured a constant 300 ohms. When the BINAURALATOR switch was set to the  $\phi 2 + 2$  mode, the impedance rose to 500 ohms. At a 100-dB SPL output and a test signal frequency of 1000 Hz, the THD from the front-channel drivers measured a mere 0.6%.

**User Comment.** These are very good headphones, with a quality—apart from any 4-channel considerations—that compares favorably with the best dynamic phones we have tested. Their smooth response, wide frequency range, and low distortion figures would earn them a place in the top ranks of headphones solely on the basis of listening quality. Their one major disadvantage is their high impedance, which precludes their use with most preamplifiers and tape decks. These phones must be driven from the outputs of a power amplifier. When we used a low-power receiver to drive them, we had to crank the volume up to near its maximum setting. Thus, we conclude that the driving amplifier should be capable of delivering some 30 or more watts per channel.

We listened to a number of CD-4 records that were chosen for their exaggerated separation and movement of sounds around the listener to judge just how discrete the sound would be from the phones. It was apparent that the front-to-rear directionality of the phones was not nearly as positive as that of the program itself. Although we were able to detect the difference between the front and rear sound, it was not always obvious which was which. However, most 4-channel programs (particularly from matrix-encoded discs) are not sharply directional. Consequently, when we listened to these records, we were very impressed with the spaciousness and "surround-sound" effect obtained. Better still, the phones delivered much the same effect with ordinary stereo programs. The effect was analogous to that obtained from the Dynaquad<sup>®</sup> and basic SQ and RM matrix decoders on stereo programs.

By and large, we feel that the subjective quadraphonic effect imparted by these phones was superior to that of a four-speaker system on the same program material—with a few exceptions. There was often little difference between the sounds of  $\phi 2 + 2$  enhanced stereo and discrete 4-channel programs. Both had the same sense of "liveliness" and ambience that, in our opinion, represent the most important contribution of quadraphonic sound to subjective realism. We must emphasize, however, that these phones (nor any other 4-channel phones) do not sound like a 4-speaker system, any more than stereo phones sound like a stereo speaker system setup.

# FREE EICO CATALOG

## 346 Ways To Save On Instruments, Burglar Alarms, Automotive & Hobby Electronics!

The more you know about electronics, the more you'll appreciate EICO. We have a wide range of products for you to choose from, each designed to provide you with the most pleasure and quality performance for your money. The fact that more than 3 million EICO products are in use attests to their quality and performance.

---

**"Build-it-Yourself" and save up to 50% with our famous electronic kits.**

---

For latest EICO Catalog on Test Instruments, Automotive and Hobby Electronics, Eicocraft Project kits, Burglar-Fire Alarm Systems and name of nearest EICO Distributor, check reader service card or send 50¢ for fast first class mail service.

**EICO—283 Malta Street,  
Brooklyn, N.Y. 11207**

*Leadership in creative electronics  
since 1945.*



CIRCLE NO. 21 ON FREE INFORMATION CARD

The vast number of control switch combinations available on the Programmer invites the listener to try his hand at creating the sound that best suits his tastes. In this respect, the


Programmer is more versatile than any other type of program modifier we have used. Not only can it shift the ambience characteristic, from a spacious to a constricted sound, but it

can move instruments closer to and farther away from the listener, shift them around the listening area, and even make them disappear altogether.

CIRCLE NO. 66 ON FREE INFORMATION CARD
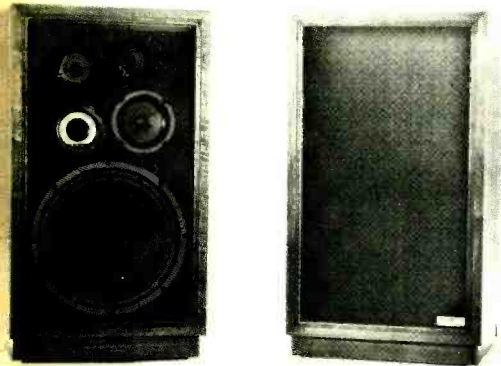
## AUDIOANALYST MODEL A-200X SPEAKER SYSTEM

*Five drivers with switchable level adjustments.*



The Model A-200X floor-standing, sealed-enclosure system is at the top of

Audio Analyst's speaker system line. It contains five drivers: a 12" (30.5-cm) woofer, 5" (12.7-cm) midrange driver, 2" (5.1-cm) cone-type tweeter, and two 1½" (3.8-cm) cone-type tweeters.

The crossovers are at 800, 2000, and 7500 Hz, respectively. The pair of 1½" tweeters is angled for better dispersion than is usually the case in both the horizontal and vertical planes. System resonance is 46 Hz, while impedance is nominally 8 ohms.

Two toggle switches on the rear of the system's oiled-walnut cabinet permit separate level adjustments in the middle- and high-frequency ranges. The speaker system is recommended for use with amplifiers capable of delivering a minimum of 10 watts/channel of power. Consequently, this is a relatively high-efficiency acoustic-suspension speaker system. There is no need for protective fuses when the system is driven by medium- and high-power (up to 100 watts/channel) amplifiers.

Audioanalyst is one of the few speaker system manufacturers to supply a specific frequency response rating for its speaker systems. In the case of the Model A-200X, the response is stated at 38 to 20,000 Hz  $\pm 3$  dB, with the bass response down 10 dB at 28 Hz in a free-air field, where it is not reinforced by room boundaries.

The system measures 27"H  $\times$  15"W

$\times$  12 ¾"D (69  $\times$  38  $\times$  32 cm) and weighs approximately 45 pounds (20.5 kg). Backed by a six-year warranty, it retails for \$259.

**Laboratory Measurements.** We created a frequency-response curve by measuring the averaged smoothed output of the speaker system in a reverberant field (about 12', or some 3.7 m, from the system in a "live" room) at frequencies above a few hundred hertz. At the same time, we measured the woofer response with a microphone placed very close to this driver to eliminate room effects. Splicing together the two curves gave us a composite frequency response curve that closely matched Audioanalyst's specifications when we made allowances for the characteristics of our microphone and test room acoustics.

The bass response matched the rated free-field response almost exactly, with a drop to  $-10$  dB at about 30 Hz. Except for a slight peak at 12,000 Hz (near our microphone resonance), the frequency response of the system was  $\pm 3$  dB from 38 to 18,000 Hz, which is excellent for a live room measurement. This response was measured with both level switches in their up positions for maximum output, which corresponded to the flattest power response. The midrange switch was able to drop the output in the 800-to-2000-Hz range by a couple of decibels, while the tweeter switch reduced the output above 2000 Hz by about 5 dB.

The low-frequency distortion, measured at a 1-watt input, was very low—less than 1% from 100 to below 50 Hz, and only 6% at 20 Hz. Increasing the drive to 10 watts had only a minor

effect on distortion, which was about 2% down to 50 Hz and 9% at 20 Hz. The tone-burst response was good, exhibiting no signs of ringing or spurious outputs.


As claimed, the system's efficiency was relatively high. An input of 1 watt of random noise in the octave centered at 1000 Hz produced a 92-dB SPL at a distance of 1 meter. The system impedance measured 8 ohms or higher—and was 20 ohms at bass resonance—from 20 to 20,000 Hz with both rear-panel switches in their down positions. In their up positions, the impedance dropped above 3000 Hz, to a minimum of about 5 ohms at 13,000 Hz.

**User Comment.** As its wide, smooth frequency response and low distortion suggest, the Model A-200X is a very accurate, as well as a highly listenable, speaker system. We confirmed this by subjecting it to our "live-versus-recorded" listening test, which evaluates speaker system accuracy principally in the frequency range above a few hundred hertz. The Model A-200X proved to be one of the most accurate speaker systems we have ever tested in this manner, with essentially 100% perfect imitation of the "live" sound source. The only part of the test where a difference could be heard was in the reproduction of wire brush sounds that involve the highest audible frequencies. A boost of 2 or 3 dB in the 10,000-to-20,000-Hz range resulted in accurate reproduction of these sounds, which proved to be the nemesis of many other speaker systems we have tested.


When we listened to a variety of recorded music through the speaker

*Tone-burst responses.*


100 Hz

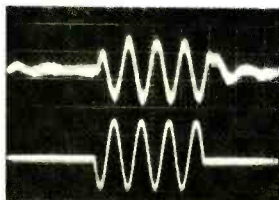

1000 Hz

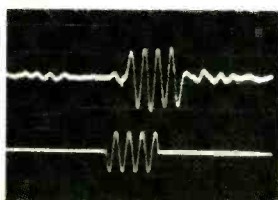

5000 Hz

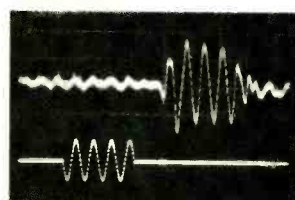

system, making side-by-side comparisons against other fine systems, the essential sound character of the Model A-200X became quite apparent. Because of its excellent overall balance, one is never aware that this is a four-way, five-driver speaker system. The sound is thoroughly integrated and dispersed, with no coloration over most of the audible range.

The chief difference between the Model A-200X and some systems to

which we compared it was in bass response. Even with the speaker system in a free-standing position several feet from a room boundary, the deep bass could often be felt as well as heard.

In general, we would describe the sound of this speaker system as "warm," with a healthy but not excessive output from the lowest bass through the midrange. Since this was balanced nicely by the smooth output at higher frequencies, the system did

not sound at all "bottom heavy," except possibly by comparison with some speaker systems that are less well endowed in the bass registers.

The Audioanalyst Model A-200X is priced to compete with some very fine speaker systems. Judging by its measured performance and audible listening quality, it should be a formidable competitor indeed.

CIRCLE NO. 67 ON FREE INFORMATION CARD

## SBE "FORMULA D" TYPE 26 CB TRANSCEIVER

*Mobile unit employs digital frequency synthesis to eliminate extra crystals.*



**T**HE USE of digital frequency synthesis appears to be the coming thing for multi-channel coverage in CB transceivers. Already, several CB rigs with digital frequency synthesis can be found on the market. One of these is the Linear Systems SBE "Formula D" Type 26 transceiver in which all 23 transmit and receive channels are controlled from a single crystal. This eliminates the need for as many as 14 crystals normally required in traditional CB synthesizers.

The Formula D is an AM transceiver designed for mobile operation. It can operate from any 11.7-to-15.9-volt, positive- or negative-ground mobile electrical system. Built in are reverse-polarity protection, voltage regulation, and line-filter circuits.

The transceiver measures 9 3/8"D x 6 3/4"W x 2 1/2"H (24 x 17 x 6.4 cm). Supplied with a microphone and mobile mounting hardware, it retails for \$199.95.

**The Receiver.** Aside from the frequency synthesizer, the transceiver's design is quite straightforward. A double-conversion scheme is used in the receiver to derive 10.695-MHz and 455-kHz i-f's. The grounded-base r-f amplifier is diode protected, a dual-

gate MOSFET is used as the first mixer. A 455-kHz ceramic filter, located ahead of the i-f stages, provides the selectivity. The voltage-doubling detector is followed by a switchable series-gate automatic noise limiter (anl), two audio stages, and a push-pull power output stage. Designed into the audio system is an a-f tone control.

Measurements indicated a high 0.3- $\mu$ V receiver sensitivity for 10 dB (S + N)/N with 30% modulation at 1000 Hz. Image, i-f, spurious-response, and adjacent-channel rejection measured 90, 66, 46, and 50 dB, respectively.

The overall 6-dB audio response was from 275 to between 2600 and 4000 Hz, depending on the setting of the tone control. Audio output at the start of clipping measured 3 watts at 7% distortion with a 1000-Hz test signal and an 8-ohm load. A 0.5- $\mu$ V r-f input signal produced full output, and the same full output was also available on PA. Two jacks are provided for external speakers.

The voltage-doubling agc held the audio output to within 7 dB with a 20-dB r-f input change at 1 to 10  $\mu$ V


and to 3 dB with an input change of 60 dB at 10 to 10,000  $\mu$ V. The S meter, which doubles as an r-f output indicator on transmit, indicated S9 with only 10  $\mu$ V of input signal. The squelch system was adjustable for 0.3- to 1000- $\mu$ V thresholds.

**Frequency Synthesizer.** The frequency synthesizer consists of digital-counter dividers and a crystal-controlled master clock oscillator that works with a phase-locked loop (PLL). Space does not permit a description of how the complex system functions; so, we will just cover what it does.

As shown in the diagram, the receiver heterodyning signals for the first conversion are obtained from a voltage-controlled oscillator (vco) operating in the range from 16,270 to 16,560 kHz. For example, the 27,115-kHz signal of channel 13 minus the vco frequency of 16,420 kHz yields a first i-f signal frequency of 10,695 kilohertz.

The second conversion is accomplished by using a 10,240-kHz crystal-controlled oscillator so that the 10,695-kHz first i-f minus the

*Diagram shows how digital frequency synthesis works.*

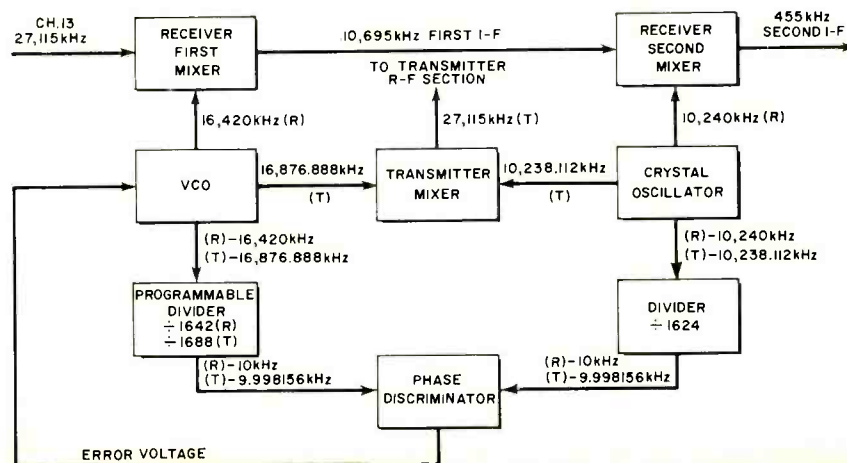

10,240-kHz oscillator signal yields a 455-kHz second i-f. This crystal signal is also divided by a factor of 1024 to produce a standard reference frequency of 10 kHz ( $10,240/1024 = 10$  kilohertz).

In addition, the vco frequency is divided to a second 10-kHz comparison signal by a factor in the range between 1627 and 1656, depending on the channel in use. This is accomplished with the aid of a programmable divider by which the required division for a particular channel is obtained from the channel-selector switch. For example, 16,420 kHz, the frequency of the vco on channel 13, divided by 1642, the channel-13 divisor, equals 10 kHz.

The two 10-kHz signals are compared in a phase discriminator where any frequency or phase difference between them produces an error voltage that corrects the vco frequency in the direction that shifts its derived 10-kHz comparison signal until it is locked in phase with the standard reference. This places the vco on the proper heterodyning frequency for the specific channel.

Suppose that, when the selector switch is set for channel 13, the initial vco frequency is 16,424.926 kHz. Dividing this number by the channel-13 divisor of 1642 yields 10.003 kHz, or 3 Hz above the 10-kHz reference. This causes the error voltage at the discriminator that now shifts the vco frequency to the point where its frequency is divisible by 1642 to exactly 10 kHz (16,420 kHz). A phase-locked condition then takes place and holds the vco on-frequency.

On transmit, the vco and crystal oscillator signals are sum-mixed. For this to result in an on-channel carrier, the vco frequency must be increased by 455 kHz. To demonstrate, 16,420 kHz (vco frequency on channel 13) + 455 kHz = 16,875 kHz. Then 16,875 kHz + 10,240 kHz (crystal oscillator frequency) = 27,115 kHz on channel

13. It is readily apparent that there is no whole-number factor that will divide the new vco frequencies to yield exactly 10 kHz. Now, by shifting the crystal oscillator's frequency downward by 1.888 kHz—to 10,238.112 kHz—and again dividing by 1024, a new standard reference of 9.998156 kHz is obtained. Then, by allowing the new vco frequencies to increase an additional amount in the range of 1.861 to 1.914 kHz (according to the channel) and programming its divider for a factor in the range of 1646 to 1702, the vco comparison signal will also be 9.998156 kHz, again producing a phase-locked condition. In addition, the mixing sum of the vco and crystal oscillator signal frequencies will still come out to the channel frequency.

As a safety precaution, provisions are included for preventing out-of-lock operation. With channel 13 set "on the nose" (done during production by adjustment of the crystal oscillator), the accuracy of the other channels will progressively deviate by up to a maximum of +26 Hz on channel 1 to -27 Hz on channel 23 due to the added variations in the vco frequency required to produce the correct vco comparison signal for the particular channel.

These conditions were verified at an ambient temperature of 75° F. After the transceiver was operating for a while or at ambient temperatures in the 85° to 90° F range, the frequency on all channels decreased by 200 to 250 Hz, well within the legal tolerance.

**The Transmitter.** The carrier goes to two r-f amplifiers and the power amplifier. The latter has a double-pi output network for matching to 50-ohm loads. Included is a 54-MHz TVI trap. The last two stages are conventionally modulated by the receiver's audio output amplifier with automatic modulation control (amc).

The output power from the transmitter measured 4 watts, using a 13.8-volt

dc power source. Modulation (producing a sine-wave signal) limited to 90% to 95% at 5% distortion with a 1000-Hz test signal. With a 6-dB increase in input signal level both positive and negative peaks limited with some clipping at the 100% points, with distortion at 10%. Adjacent-channel splatter was down 40 dB with a 2500-Hz test tone and down 50 dB with a 1000-Hz tone. The overall a-f response was nominally 275 to 7500 Hz.

**User Comment.** The Formula D transceiver's Delta tune system varies the crystal oscillator frequency on receive. The DELTA TUNE has a range of  $\pm 700$  Hz, which is hardly enough to make any practical audible or visual difference in slightly off-frequency signals. The back-lighted r-f/S meter is a reasonably good size, but its calibrations are blue on a black background, making them a bit difficult to distinguish under some conditions. On the other hand, the red meter pointer shows up well against the dark background.

A DISTANCE/LOCAL switch on the transceiver allows the front-end gain to be reduced by almost 30 dB for strong-signal overload protection. When the anl is switched on, impulse noise 60 dB above 0.3  $\mu$ V was attenuated to virtual inaudibility in the presence of the signal. We found it extremely effective in our exceptionally noisy test car.

The very high receiver sensitivity and the fine performance of the anl, coupled with the good audio response and the built-in loudspeaker characteristics that provide very good intelligibility, make this transceiver ideal for use in weak-signal areas and where electrical noise is a problem. In addition, the amc setup during voice modulation ensures a signal of high average power without undue splatter.

CIRCLE NO. 68 ON FREE INFORMATION CARD

## B&K MODEL 520 TRANSISTOR TESTER

*Tests and identifies devices in or out of circuit.*

**T**HERE are a great many in/out-of-circuit transistor testers on the market for troubleshooting modern solid-state equipment and devices. One of the best we have encountered is the latest B&K Model 250 transistor tester that sells for \$150. Using either three clip leads or a front-panel transistor socket, this transistor tester can be used to determine if a transistor is

good or bad, identify the device's basing, determine its composition (silicon or germanium) and its polarity (npn or pnp), and test for leakage.

The tester can also measure the  $I_{CES}$  and  $I_{RES}$  of bipolar transistors, the  $I_{DDS}$  and gate leakage of FET's, and the reverse current leakage of diodes. Furthermore, it can be used to determine if a device under test is bipolar,



POPULAR ELECTRONICS

FET, or SCR. If this last feature does not appear to be much, keep in mind that package styling is similar among these types of semiconductors.

**Using the Tester.** Operation of the transistor tester is simplicity itself, owing to the fact that there are only two switches (and no controls) that need be touched. One switch is for identifying whether the semiconductor under test is silicon or germanium in its IDENTIFY position and to measure current leakage in its LEAKAGE position. The TEST switch is a six-position affair that is used to identify the device's basing.

In use, you simply connect the three color-coded test leads to the three leads of the semiconductor under test in any order whatever for in-circuit tests or plug the device into the front-panel socket for out-of-circuit tests. Then operate the large six-position TEST switch until the tester emits a loud audio tone. At this point, a front-panel LED will come on to identify the device type.

Once the semiconductor is identified according to type, you set the second switch to IDENTIFY whether it is

silicon or germanium. Moving this switch to the LEAKAGE position gives a meter indication of the amount of leakage current in the device under test. The meter scale and ballistics are logarithmic so that leakage currents can be indicated over a range of 0.1  $\mu$ A to 5 mA. The meter also indicates the limits for silicon signal and power and germanium signal and power transistors so that you can see at a glance if the indicated leakage is within tolerance for that particular device.

Unlike other transistor testers, the Model 520 uses an exclusive high-current, low-duty-cycle (5%) pulse technique to make its test. For a good/bad test, the limiting values connected to the device under test is greater than 10 ohms, while the capacitance is up to 5  $\mu$ F for low-beta and 15  $\mu$ F for high-beta transistors.

The Model 520 is housed in an attractive metal cabinet that measures 8"W  $\times$  7"H  $\times$  3 $\frac{1}{2}$ "D (20  $\times$  18  $\times$  9 cm). The instrument weighs 5 pounds (2.3 kg). Rubber feet are attached to the housing for upright use, while a handle/tilt stand can be used on the bench. The color coding is clear and unambiguous. A yellow LED is used


for silicon and a green LED for germanium device types. A pair of red LED's are used as NPN and PNP indicators. The B/C/E indicators on the TEST switch are brightly colored and keyed to the coding of the test clips.

**User Comment.** During a period of several weeks on our workbench, we used the Model 520 to test a number of densely packed printed circuit board assemblies. In an A/B comparison between a run-of-the-mill in/out-of-circuit tester and the Model 520, we noted quite a difference in setup and operation. With the B&K tester, there was no need to properly orient the test leads, and the loud "beep" we heard as we hit the correct lead basing left no doubt about the connections.

With both testers, we were able to isolate bad transistors from the good ones on the pc assemblies and to identify silicon and germanium devices according to whether they were npn or pnp transistors. The Model 520, however, also uncovered a leaky transistor that our other tester failed to catch. Our other tester could not check out FET's, which the B&K tester can.

CIRCLE NO. 69 ON FREE INFORMATION CARD
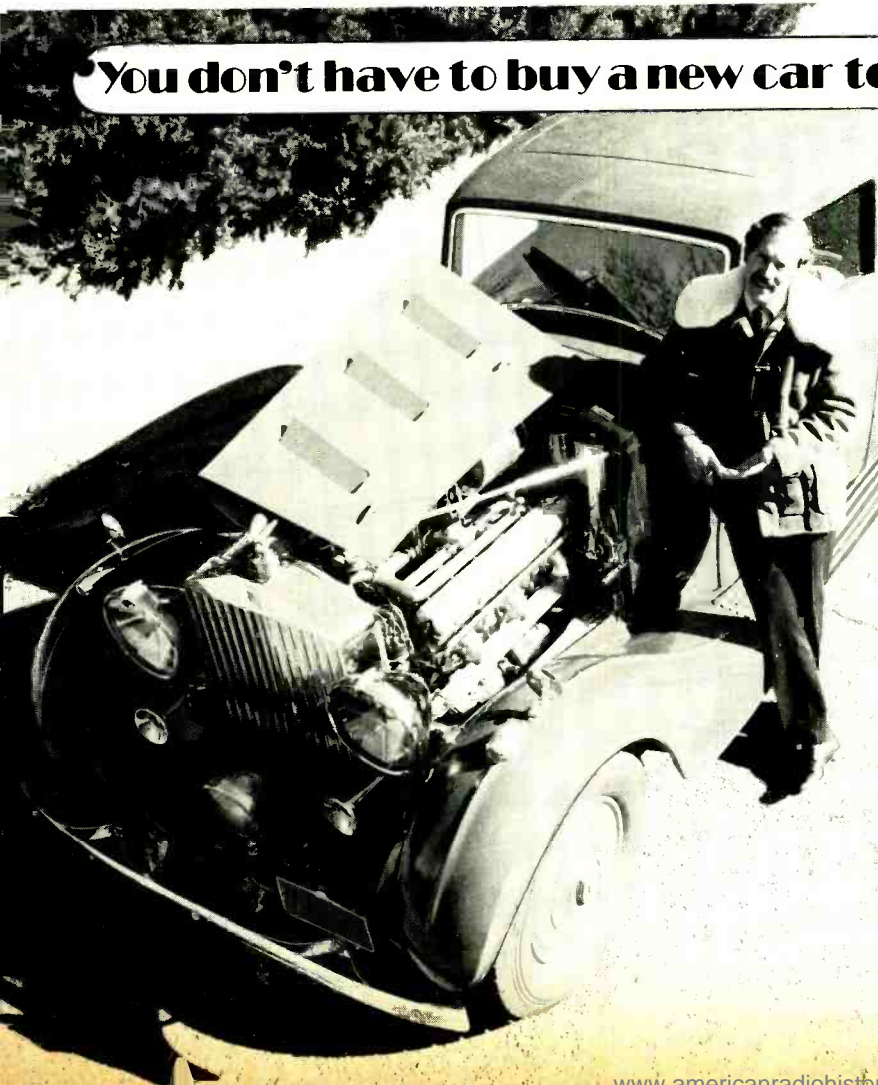
## You don't have to buy a new car to get an electronic ignition.



Let's face it. After 37 years, even a Phantom III can use a lift. That's why I put a Delta Mark Ten B Capacitive Discharge Ignition on my Phantom . . . to give her a spark I'd pit against any '75 model car. I went to Delta because they aren't Johnny-come-latelys. Delta's been making electronic ignition systems for over a decade.

Whatever kind of car you drive, you can give it the same great Delta performance I gave mine.

- Mark Ten B Capacitive Discharge Ignition Systems are manufactured by Delta Products, Inc., a company with a conscience, and with a proven record of reliability both in product and in customer relations.
- The Mark Ten B really does save money by eliminating the need for 2 out of 3 tune-ups. Figure it out for yourself. The first tune-up or two saved pays for the unit, the rest is money in your pocket. No bunk!
- Because the Mark Ten B keeps your car in better tune, you actually can save on expensive gasoline.
- With a Mark Ten B, spark plugs stay clean and last longer . . . fouling is virtually eliminated.



I want to know more about Mark Ten B CDI's. Send me complete no-nonsense information on how they can improve the performance of my car.

Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_




**DELTA PRODUCTS, INC.**

P.O. Box 1147, Dept. PE, Grand Junction, Colo. 81501  
 303-242-9000

Mark Ten B, assembled	\$64.95 ppd	Standard Mark Ten, assembled	\$49.95 ppd
Mark Ten B, kit	\$49.95 ppd	Deltakit@	\$34.95 ppd

CIRCLE NO. 19 ON FREE INFORMATION CARD

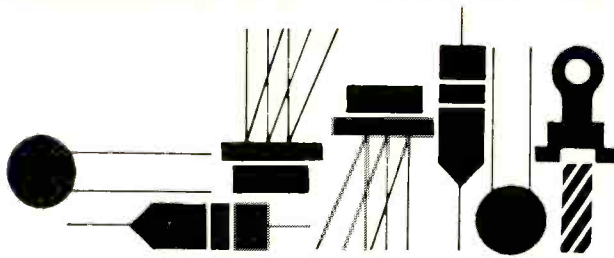

# Solid State

By Lou Garner

## THE GOODFLASHER—PART II

**W**HEN a motion picture is a box-office smash, there's a fine opportunity for a sequel. For example, the resounding success of "The Godfather" resulted in "The Godfather, Part II." But, whereas a few motion picture sequels are planned before the initial film is released, I truly planned—and promised—to present additional applications for the amazingly versatile LM3909 LED flasher/oscillator first discussed in this column last July. (That was a smash hit!)

In fulfillment of that promise, "Solid-State Productions" proudly presents another super-colossal epic in breathtaking black and white: "Goodflasher, Part II," starring LM3909. As customary in Show Biz, credits are in order. I am indebted to Mr. Peter Lefferts, an engineer with the National Semiconductor Corporation (2900 Semiconductor Drive, Santa Clara, CA 95051), who designed, bench-tested and contributed the circuits shown in Figs. 1 through 4.

The LM3909, you may recall, is a monolithic oscillator specifically designed to flash light emitting diodes. Consisting of one pnp double collector and three npn transistors, a zener diode, and nine resistors, the device is packaged in an 8-lead plastic mini-DIP. With a maximum power dissipation rating of 500 mW and a maximum supply rating of 6.4

volts, the LM3909 can deliver current pulses of up to 200 mA. It is available through franchised National Semiconductor electronic components distributors and from some mail order supply houses.

Designed to demonstrate the LM3909's high efficiency and low power requirements, the solar powered oscillator circuit in Fig. 1A may be used as part of a science fair display, as an interesting lab experiment, or simply as a "fun" project. In direct sunlight, the oscillator will deliver a piercing screech, while average daylight will produce a more moderate tone. A low buzz is emitted when the circuit is activated by a 75-watt incandescent bulb placed two or three feet from the solar-cell power supply. With practice, one may be able to "guesstimate" light intensity by the tone of the output signal.

In addition to the LM3909 (IC1), the circuit requires two 1/4- or 1/2-watt resistors (R1 and R2) and a low-voltage, 15- $\mu$ F electrolytic capacitor (C1). The output device is a standard PM loudspeaker with a 25-ohm (or more) voice coil, while the power supply consists of four to six single-junction silicon solar cells (PC1 to PC4), connected in series.

A simple AM broadcast band receiver circuit featuring the LM3909 is illustrated in Fig. 1B. Here, the IC serves as a detector/amplifier rather than in its customary role as a pulse oscillator. Suitable for listening to stronger local stations, the receiver has better sensitivity and greater power output than conventional crystal sets but, of course, can not be compared to multistage superheterodyne designs. It is an excellent project for the novice, however, who has tried crystal and one or two transistor circuits and wants to experiment with IC devices.

Operating power is supplied by a single penlight or flashlight cell (B1), controlled by a spst toggle, slide, or rotary switch (S1). The PM loudspeaker should have a 40-ohm (or better) voice coil. (If you have trouble finding one, use a 4- or 8-ohm coil and a step-down impedance transformer.) Capacitors C2 and C3 may be ceramics, plastic film, or tubular paper types. The single tuned circuit consists of a standard ferrite core broadcast band antenna coil (L1) and a matching variable capacitor (C1).

If desired, a short antenna can be connected to the "high" end of the coil, as shown. Overall sensitivity and selectivity will be improved with a longer antenna, but this should be connected to a tap near L1's "cold" (ground) terminal. If the coil used does not have a separate antenna tap, simply wind a few turns of fine-gauge enamelled wire around the lower end of the coil, attaching one end to ground and the other to the long antenna.

Requiring fewer components than an equivalent UJT configuration, the triac trigger circuit illustrated in Fig. 2A is designed as an interface between TTL logic circuitry and a



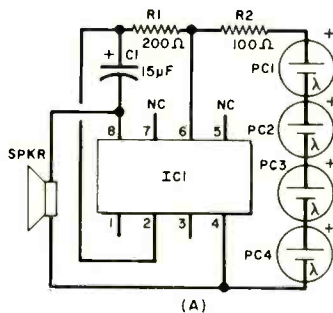
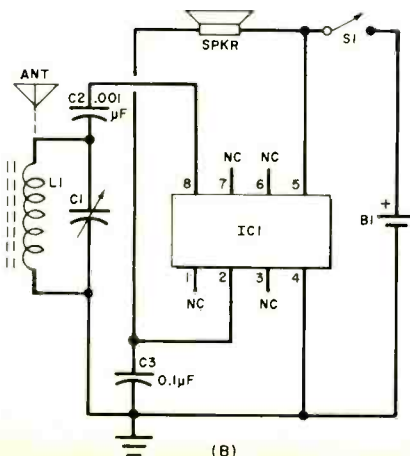


Fig. 1. Applications for LM3909: (A) solar powered oscillator; (B) AM broadcast band receiver.

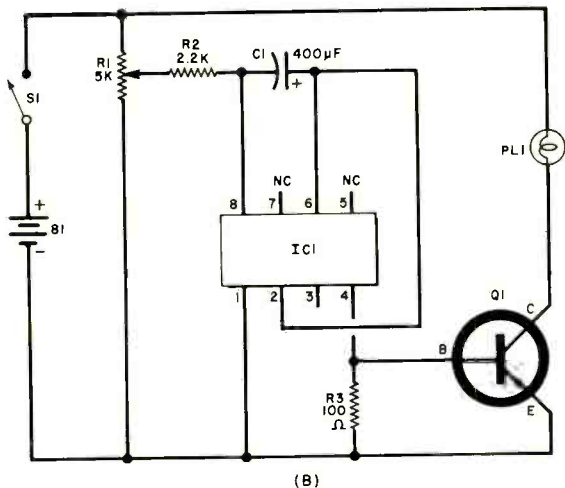

power triac. The circuit delivers a train of 7-kHz, high-current pulses to the triac's gate through isolation transformer *T1* when its input is driven "low" by a lightly loaded TTL gate through series input resistor *R1*.

Fig. 2. (A) Triac trigger and (B) ministrobe circuit.

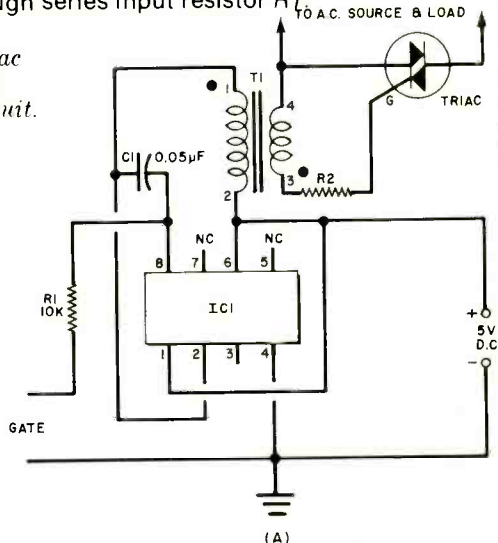


Other than the LM3909 (*IC1*), the circuit requires a standard pulse transformer, *T1* (Sprague 11Z2003), a small 0.05- $\mu$ F ceramic or plastic film capacitor (*C1*) and a 1/2-watt resistor (*R1*) at 10,000 ohms or less. A 1/2-watt gate current limiting resistor (*R2*) will be needed for low-to-medium-power triacs, with its value determined by the device's maximum gate current specification. If a high-power triac capable of handling a 200-mA gate current is used, *R2* will be 1 ohm or less (or can be omitted). As indicated, the circuit is designed for operation on a standard 5-volt dc supply.

Battery operated and thus shockfree, the mini-strobe circuit given in Fig. 2B is ideal for a youngster's toy, but also could be used for advertising displays or caution and warning signal applications. With an effective flashing rate of up to 7 Hz, the unit can provide a strobeflike "flicker" effect in a darkened room. The rate control, *R1*, has a range from "off" to beyond the response time of the incandescent lamp bulb, *PL1*, causing it to appear "on" continuously.

For optimum results, the lamp, a type 1767 bulb (chosen for its rapid response characteristic), should be provided with a reflector. Control *R1* is a 5,000-ohm linear potentiometer. Timing capacitor *C1* is a 3-volt electrolytic. The lamp driver (*Q1*) is a National Semiconductor type U01 npn transistor or similar general-purpose device. Operating
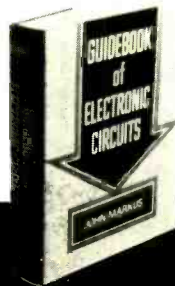
# Find *whatever* circuit you need – instantly



## THE LARGEST COLLECTION EVER

Over 3,600 circuit diagrams, complete with component values, in one handy volume, all clearly indexed and cross-referenced for speedy answers to your immediate design needs.

# GUIDEBOOK OF ELECTRONIC CIRCUITS

By John Markus

1068 pages, \$24.50

Whatever your project—a hi-fi system, a burglar alarm, a solid state metal detector, an automatic timer—you name it, you'll find the circuit that best meets your needs in this, the largest single-volume collection of illustrated circuits ever to be published.

**131 CHAPTERS**, each devoted to a particular type of circuit, present 3,600 individual circuits, all with essential construction and adjustment details, design precautions and other practical data. The advantages and disadvantages of the various circuits are also given so you can decide quickly and easily what best meets your needs at the moment.

**FAST, EASY USE.** The Index has over 10,000 entries that list—and cross-reference—circuits by all their different names, by performance parameters, by applications, and by a host of other relevant categories. Perfect for super-fast looking or leisurely leafing.

**SAMPLE CONTENTS** quadrasonic circuits . . . tape recorder circuits . . . citizens band circuits . . . measuring circuits . . . filter circuits . . . amplifier circuits . . . code circuits . . . telephone circuits . . . signal generator circuits . . . flasher circuits . . . switching circuits . . . and thousands more!

And in case you missed Markus' two previous circuit books, use the coupon below to order examination copies. 92,000 already sold. Absolutely no duplication of circuits in these three volumes.

### SOURCEBOOK OF ELECTRONIC CIRCUITS

By John Markus 888 pp. 8 1/2" x 11" \$23.50

3,000 different circuits with values and exact source citations.

### ELECTRONIC CIRCUITS MANUAL

By John Markus 892 pp. 8 1/2" x 11" \$24.75

3,181 different circuits with values and exact source citations.

At your local bookstore or use coupon below for

**FREE 10-DAY EXAMINATION**

### McGraw-Hill Book Company

1221 Avenue of the Americas, New York, N.Y. 10020



Please send me the book(s) I have checked below for a free 10-day examination. In that time I will either remit the price, plus local tax, postage, and handling, or return the book(s) with no further obligation. I understand that if I remit in full, plus local tax, with this order, McGraw-Hill pays postage and handling, and a 10-day return privilege still applies. This order subject to acceptance by McGraw-Hill.

\_\_\_ Guidebook of Electronic Circuits (040445-3) \$24.50

\_\_\_ Sourcebook of Electronic Circuits (040443-7) \$23.50

\_\_\_ Electronic Circuits Manual (040444-5) \$24.75

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

This offer good only in the U.S. and Canada.


**23-A753-4003-3**
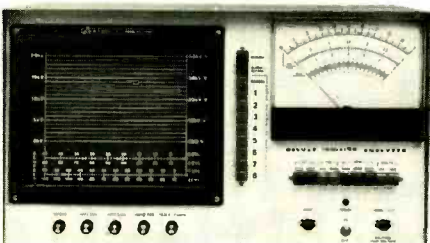
# Your NEW Heathkit Catalog is ready




Now over 400 do-it-yourself electronic kits for home, hobby, and industry. All designed to give you more for your money...more value, more performance, more satisfaction. All designed so even beginners can build them. Send for your free catalog today.

waiting to serve you with more values, more new kits, than ever before


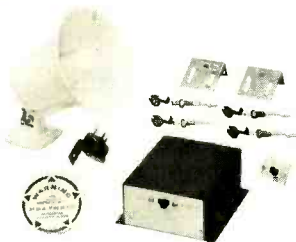
## New Professional 12" Ignition Scope — Kit or Wired

Does more than others for \$1000 less. Spots tough ignition problems on all types of systems in 3, 4, 6, 8 cyl. or 2-rotor Wankel engines; sets itself automatically for no. of cylinders. Big 12" screen has 2 calibrated primary and secondary voltage grids plus dwell angle indications. Special circuit maintains trace length regardless of RPM. Displays "superimposed" patterns, single cyl. pattern, primary or secondary "parade" patterns. "Power balance" feature even helps spot bad valves or rings. 8" meter with tach & DCV ranges. Optional low cost timing light, alternator adaptor & cart. Kit CO-2500 \$379.95; Assembled WO-2500 \$695.



## New Automobile Intrusion Alarm Kit

**Total Protection.** Alarm mounts anywhere; connects to switches on doors, hood, & trunk. Underdash switch arms or disables unit. Adjustable delay time allows you to quickly enter or leave car without triggering alarm, but opening trunk or hood triggers alarm instantly. Alarm sounds car horn in repeated 2-minute cycles. Kit GD-1157 Alarm \$24.95; Kit GDA-1157-1 Siren (gives yelping sound louder than car horn) \$19.95.



## New Programmable Digital Stop Watch Kit

Another "first" from Heath. 2 IC counters, 8 digits & 7 functions with typical accuracy to  $\pm 0.003\%$  and resolution to 1/100th of a second. Function 1 (Start/Stop Elapsed) times individual events while also counting total. Function 2 (Sequential) times each part of event & displays each separately while timing overall event. Function 3 (Total Activity) accumulates total elapsed time of a series, excluding time between events. Function 4 (Split) displays cumulative time to each "split" point while continuing overall event time. Function 5 (Start/Stop Activity) shows separate time for each event & totals all individual times. Function 6 (Programmed Upcount) counts up to "learned" time. Function 7 (Programmed Downcount) counts down from "learned" time. Stop watch can "learn" time from other functions or be programmed up to 9 hours, 59 minutes, 59 seconds. Has jacks for external triggering devices and alarms. Includes nickel-cadmium batteries & charger. Kit GB-1201, \$99.95.



## New Digital Wind Speed & Direction Indicator Kit

**Unique.** Two big, bright digits show wind speed to 99 mph. As you build, choose 2 readout modes: miles, knots, or kilometers per hour; front panel light shows mode in use. 8 incandescent lights show wind direction at principal compass points; adjacent lighted bulbs give 16 point resolution. Remote transmitter boom clamps to TV mast. Styled in black plastic to match Heathkit GC-1005 Digital Clock and ID-1390A Digital Thermometer. Kit ID-1590, \$69.95 less cable.



## New — Two-Way Telephone Amplifier Kits


Now, hands-free telephone use with amplified "talk" and amplified "listen" — with or without dialer. Talk & listen from 10' away. Voice-actuated circuitry switches from talk to listen without feedback or clipped words. Listen button lets you monitor line without built-in microphone activated. Dialer model may be used with or without regular telephone. Includes 4-prong jack & phone coupler connector. Battery powered. Kit GD-1112 (no dial) \$49.95; Kit GD-1162 (w. dial) \$69.95.
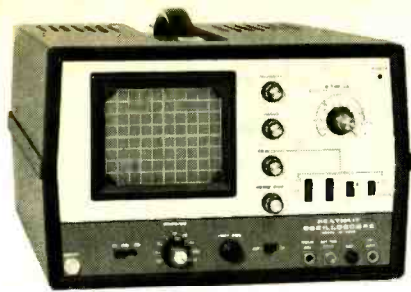
## New Public Address Sound System Kits

Outperforms those costing twice as much. **TA-1620 Control/Amp.** takes 6 low impedance mikes, each with level, bass & treble controls & reverb sw. Has VU meter, 4 switched response "shaper" circuits, exclusive bass filter, 100 rms watts drives 2 speaker columns. **TA-1625 Booster Amp.** 100 rms watts to drive 2 extra speaker columns. **TS-1630 Speaker Column.** Six 8" full-range drivers response tailored for voice; 60 watt rms rating; 12 ohm impedance. Kit TA-1620 \$449.95; Kit TA-1625 \$179.95; Kit TS-1630 \$199.95.







## New DC-5 MHz Triggered Scope — Kit or Wired

**Best scope value today.** Wide bandwidth, 20 mV sensitivity, & stable triggering — ideal for TV, audio and RF servicing. Easy-to-use controls. Trigger circuit (not recurrent type) has normal & automatic modes, switched AC & DC coupling, & front panel external inputs (special TV position allows low freqs. to pass while rejecting high freqs. for easy triggering on complex TV signal. 7 calibrated time bases from 200 ms to 0.2  $\mu$ s/cm. 20 mV/cm vertical sensitivity with 9 calibrated attenuator positions up to 10 v/cm, plus variable control. 5" round flat-face CRT (8 x 10 cm graticle). Lightweight, durable blue plastic cabinet with white panel. Kit IO-4540 \$179.95; Assembled SO-4540 \$275.



## New — Lowest cost Triggered 5 MHz Scope Kit

**The scope everyone can afford,** and it has the performance you need. DC-5 MHz band width, 100 mV vertical sensitivity with X1, X10 & X100 attenuation, AC or DC. Automatic, positive locking horizontal sweep continuously adjustable from 20 ms to 200 ns/cm. Stable displays due to zener regulated amplifiers and sweep. 5" round flat-face CRT with 8 x 10 cm graticle. Simplified controls and switches make it easy to use. Lightweight, durable blue plastic cabinet; white panel. It's the best instrument buy in years. Kit IO-4560 \$119.95

**New catalogs and kits also available at**

**HEATHKIT ELECTRONIC CENTERS —**  
Units of Schlumberger Products Corporation  
Retail prices slightly higher.

ARIZ.: Phoenix; CALIF.: Anaheim, El Cerrito, Los Angeles, Pomona, Redwood City, San Diego (La Mesa), Woodland Hills; COLO.: Denver; CONN.: Hartford (Avon); FLA.: Miami (Hialeah), Tampa; GA.: Atlanta; ILL.: Chicago, Downers Grove; IND.: Indianapolis; KANSAS: Kansas City (Mission); KY.: Louisville; LA.: New Orleans (Kenner); MD.: Baltimore, Rockville; MASS.: Boston (Wellesley); MICH.: Detroit; MINN.: Minneapolis (Hopkins); MO.: St. Louis (Bridgeton); NEB.: Omaha; N.J.: Fair Lawn; N.Y.: Buffalo (Amherst), New York City, Jericho (L.I.), Rochester, White Plains; OHIO: Cincinnati (Woodlawn), Cleveland, Columbus, Toledo; PA.: Philadelphia, Pittsburgh; R.I.: Providence (Warwick); TEXAS: Dallas, Houston; VA.: Norfolk (Va. Beach); WASH.: Seattle; WIS.: Milwaukee.



## New Variable Isolated AC Supply

**What every tech & hobbyist needs.** The IP-5220 isolates equipment under test from the AC power line and provides an AC output which is variable from zero to 140 volts. Great for locating circuit faults caused by high or low voltage or testing equipment with unknown power requirements. Power rating is 360 volt-amperes, continuous. Variable output current rating: 3A. max. Direct output current rating: 10A. Two meters: voltmeter 0-150 VAC; ammeter: 0-1 & 0-3A. Ammeter and variable output socket are fused. Kit IP-5220, \$109.95

## New 21" (diag.) Digital Design Color TV Kit

**All the advanced technology** of digital circuitry in a smaller screen size. **Electronic touch-to-tune** varactor front end (nothing mechanical to wear out) with computer-like programming board for up to 16 channels. **On-screen channel numbers**, adjustable in brightness, position, and duration. **On-screen digital clock**; a low-cost option; programmable in 12 or 24 hour format, displays 4 or 6 digits. **Fixed-filter IF**, a Heath exclusive that assures better pictures longer, never needs instrument alignment. **100% solid state** — more ICs than any other — sophisticated circuitry that results in less interference, better color tints, improved sensitivity, greater noise immunity, improved picture definition. **Black negative matrix 21V picture tube** for brighter, sharper pictures. **Total touch-tune remote control** — low cost option that operates all functions, including recall of time & channel.



## New Oscilloscope Calibrator Kit

For time calibration, it generates a 0.5 second to 1  $\mu$ sec square wave in 1-2-5 sequence accurate to 0.01% with 200 mV peak ( $\leq$  3% overshoot) and  $\leq$  4 ns rise time. Voltage calibration ranges are 1 mV to 100 v. in decade sequence, accuracy within 2%, DC plus variable 2 Hz to 10 kHz in 1-2-5 sequence (internal std. accuracy within 1%). Use it to calibrate scopes up to 35 MHz and voltmeters; it's also a fast rise time squarewave generator and good bench freq. standard. Kit IG-4505 \$44.95

**Easier to build & service** — thanks to extensive modular design and built-in servicing tools including digital-design dot generator, front access slide-out Service Drawer, new picture centering and pin-cushioning correction circuits, and Test Meter. **Enjoy the best in TV design** — now in smaller size at lower cost. Kit GR-2050 \$599.95. Kit GRA-2000-6, remote control, \$89.95. Kit GRA-2000-1, digital clock accessory, \$29.95. Contemporary or Mediterranean cabinets from \$119.95.

**Use coupon below to order your favorite new kit or to get your FREE new Heathkit Catalog.**

HEATH Schlumberger	Heath Company Dept. 10-10 Benton Harbor, MI 49022
<input type="checkbox"/> Please send my free 1975 Heathkit Catalog. <input type="checkbox"/> Enclosed is \$ _____ plus shipping. Please send model(s) _____	
NAME _____	
ADDRESS _____	
CITY _____	STATE _____ ZIP _____
<small>PRICES ARE FACTORY MAIL ORDER, FOB PRICES &amp; SPECIFICATIONS SUBJECT TO CHANGE WITHOUT NOTICE.</small>	
CL-571A	



### IT'S PORTABLE

Industry preferred L.E.D.'s offer, dependable, durable and bright displays. But brightness means high current drain. Well, we've licked the "high current drain-short battery life" problem with our patent pending "auto-off" circuit that blanks the display between measurements. Your benefit? A long useable battery life and a bright easy to read display. And it's tough enough to be portable. Cyclocase case and recessed controls withstand that field use. It's protected electrically, too, up to 2000V DC, for minimum downtime — maximum uptime.

### IT'S COMPLETE

Most portable DVM's sacrifice on features, functions, or accuracy. But not the DVM32. It's accurate with full 3½ digit readout, 5% of reading accuracy and 15 megohm input impedance. Complete functions and ranges from: 1mV to 1999V DC, 1mV to 1000V AC rms, .1 ohm to 19.99 megohm and 1uA to 1.999A, AC and DC, plus Hi and Lo power ohms. It's Fast with 2½ updates a second, plus auto-polarity, decimal and overrange indication.

The DVM32 . . . true portability with complete measuring capabilities.

**DVM32** backed by SENCORE'S 100% MADE RIGHT LIFETIME GUARANTEE

**SENCORE** 3200 Sencore Drive, Sioux Falls, S.D. 57107  
Phone: 1-605-339-0100 TWX: 910-660-0300

CIRCLE NO. 52 ON FREE INFORMATION CARD

sign employs a pair of LM3909's. In operation, IC1 produces a high-pitched signal which is modulated at a low rate by a sawtooth waveform developed by IC2. Again, a high-impedance (25-ohm or more) loudspeaker (or transformer) is used. The capacitors are low-voltage electrolytics, and a single flashlight cell serves as the power source. Diode D1 is type 1N4002. Since this circuit provides continuous operation, a single control switch is adequate.

Suitable for operation at distances of up to 200 feet when used with standard 22-gauge intercom or hookup wire, the dual-station code practice set shown in Fig. 4A is a dandy project for beginners or even for old-timers wishing to improve their skills at "pounding the brass." The two units may be operated room-to-room, room-to-garage or basement, apartment-to-apartment, or even house-to-house in some suburban areas. In addition to its obvious application for code practice, the system could be used in lieu of an intercom for simple communication by means of a pre-established private code. For example, one short buzz could mean "dinner's ready," a long and short "you're wanted on the phone," and so on.

In operation, the LM3909 serves as a simple relaxation oscillator to drive both loudspeakers, which are effectively in series. Its normal narrow pulse output is modified by series resistor R2, lengthening capacitor C1's discharge time and developing a rectangular waveform.

With the two loudspeaker voice coils in series electrically, inexpensive 8-ohm types may be used in this application. The capacitor is a low-voltage electrolytic. Either a penlight or flashlight cell may be used as the power source. On-off switch S1 is optional, for the battery drain is virtually nil until one of the handkeys is closed.

For maximum audio output at minimum current drain, the entire system can be operated in a resonant mode. This may be accomplished by adjusting both the oscillator output frequency and the acoustic characteristics of the enclosures (or cases) to match the natural resonant frequencies of the loudspeakers. The oscillator output frequency may be changed by selecting different values for timing capacitor C1. The acoustic characteristics of the cases may be modified by adding additional holes (other than the openings for the speaker grill). Both hole size and capacitor value must be determined experimentally for maximum output and stability.


Another interesting linear application for the LM3909 is given in Fig. 4B—a low power unidirectional intercom or "remote listener." Here, the device serves as a simple audio amplifier between a remote microphone and a local loudspeaker. Although the circuit's overall gain and audio output are relatively low, so is the power drain, assuring long battery life, even under continuous operating conditions.

power is supplied by two series-connected flashlight cells, B1, furnishing 3 volts, controlled by S1.

Delivering a rapidly rising wail when activated, followed by a slower "coasting down" when its control button is released, the fire siren shown in Fig. 3A may be used in toys or as a sound effects generator. As in the previous circuits, the active device is an LM3909. The capacitors are low-voltage electrolytics. A momentary contact, NO, spst push-button type is used as the control switch, S2. A single flashlight cell (B1) serves as the power source. The PM loudspeaker should have at least a 25-ohm voice coil. If the operator prefers that the output tone stop sometime after the pushbutton is released, an 18,000-ohm, ½-watt resistor should be connected between IC pins 6 and 8.

A whooper siren circuit is illustrated in Fig. 3B. Generating a sound similar to that of the electronic sirens used on many ambulances, police cars and rescue trucks, the de-

Fig. 3. (A) Fire siren and (B) whooper siren circuits.

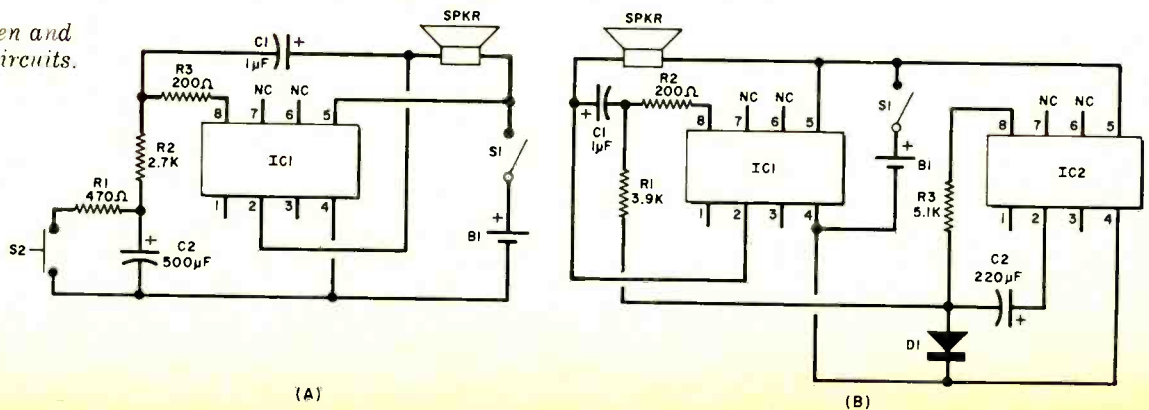

Referring to the schematic, the remote microphone consists of a 3.2-ohm PM loudspeaker and a 3.2-ohm-to-15K matching transformer, *T1*. This can be a small tube-type output transformer used "in reverse." The microphone assembly is connected to the amplifier, *IC1*, through a standard twisted pair up to 50-feet in length. The local loudspeaker should have a high impedance (40-ohm) voice coil (or use a transformer). Capacitors *C1* and *C2* are small ceramic or plastic film types. Operating power is supplied by a single flashlight cell, *B1*.

The additional circuits we've reviewed (Figs. 1 through 4) will hopefully spark your imagination, leading to even more exciting applications in the future.

**Reader's Circuit.** In a letter commenting on the LED flasher circuits discussed in a previous column, reader Edwin C. Hadden (Oakland Park, FL) asks if I know of a circuit capable of flashing two LED's at different rates.


A suitable circuit is illustrated in Fig. 5. Featuring discrete devices, this design was developed several years ago, long before inexpensive timer and flasher IC's, such as the 555, 556, and LM3909, were introduced. Despite the limitations imposed by its early design, the circuit requires but four transistors, four resistors, and two capacitors in addition to its dc power source, yet is capable of flashing two

LED's at widely different rates and includes an optional circuit interlock.

Transistors *Q1* and *Q2* form a complementary relaxation oscillator, with *LED1* serving as *Q2*'s collector load and capacitor *C1* providing the feedback needed to start and sustain oscillation. The circuit's operating rate (frequency) depends upon a number of factors, including the dc source voltage and individual transistor characteristics, but principally upon the *R1-C1* time constant. Similarly, *Q3* and *Q4* form a second complementary relaxation oscillator, with feedback provided by *C2*, and *LED2* serving as *Q3*'s collector load. Operating power is furnished by a common dc source, *B1*, controlled by *S1*. Series resistor *R3* serves a dual role, acting to limit current and thus to protect the LED's. It also introduces a common source impedance to "interlock" the two complementary oscillators.


Different flashing rates for the two LED's may be achieved simply by establishing different operating frequencies for the complementary oscillators, using different values for either the feedback capacitors (*C1* and *C2*) or the corresponding base bias resistors (*R1* and *R4*). If a variable flashing rate is needed, either base bias resistor can be replaced with a fixed resistor in series with a suitable potentiometer. Typically, *R1* could be replaced by a 100K resistor in series with a 500K potentiometer.

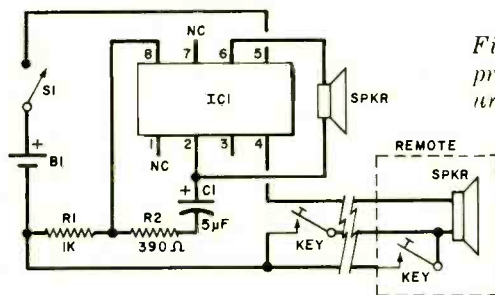The circuit interlock feature provided by *R3* is most effective when one




(A)

Fig. 4. (A) Dual-station code practice set and (B) unidirectional intercom circuit.

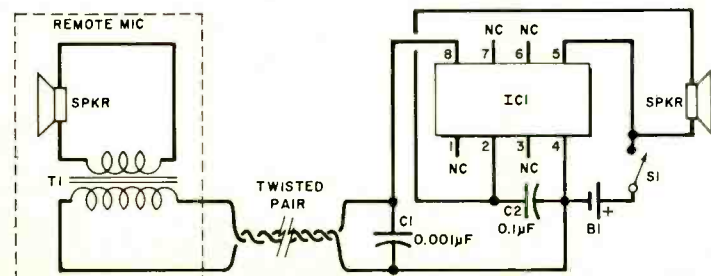

(B)
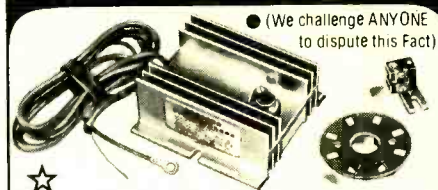
# ALLISON 'OPTO-ELECTRIC' The BEST...the ULTIMATE of ALL Ignition Systems!



● (We challenge ANYONE to dispute this Fact)



Never wears out or needs any Maintenance!



● gives you Maximum Power with continuous PEAK PERFORMANCE

...while reducing Maintenance and Operating Costs!

★ The Allison OPTO-ELECTRIC System eliminates the Points and Condenser, replacing them with an OPTO-ELECTRONIC TRIGGER, using a Light-Emitting Diode and Photo Transistor. The System operates on a beam of Light. As there are NO moving parts in rubbing contact, "Friction-wear" is completely eliminated. Timing adjustments are PERMANENT.

● Gives 40-Times more Timing accuracy than ANY system using "Mechanical" Breaker-Points! UNLIMITED RPM! "Electronically-Controlled" DWELL automatically supplies HIGHEST Performance at both Low and High speeds. Spark strength does not fall off at high RPM. POSITIVE SPARK helps eliminate "Misfire" for faster acceleration and improved Engine Performance. Sparkplugs LAST 3 to 10-Times LONGER.

● Easier Starting under any condition! Smoother running... (NO TIMING FLUCTUATION as with Magnetic Impulse Units). All SOLID-STATE Components UNAFFECTED By Temperature, Moisture, or Vibration! Only Highest grade materials used. Guarantees you Solid, Dependable Performance!

● PERFECT TIMING INCREASES Engine Efficiency and Gas Mileage SAVES Precious Fuel! Allison gives you MAXIMUM Engine Efficiency 100% of the Time... and that's the name of the game for the BEST in GAS MILEAGE AND ECONOMY

★ Perfect Timing and Dwell never change.

● Pays for itself! Eliminates ignition Tune-Ups forever! "INFINITE LIFE" Once installed, Never needs replacing!

★ PROVEN RELIABILITY!  
Each Unit Tested to 15,000 RPM.  
● Road and Race Proven.  
(Opto-Electric Systems won at INDY Two years in a row!)

★ You CAN install the ALLISON System in ALL the U.S. made & Foreign Cars! (4, 6, or 8-Cylinder).

"EASIEST-TO-INSTALL" UNIT ON THE MARKET.  
(Not necessary to dismantle Distributor as with other systems).

★ If you want the BEST, and SAVE! This is IT!

ORDER with CONFIDENCE... SATISFACTION GUARANTEED or Full Refund.

10-YEAR FACTORY WARRANTY! (Free Repair or Replacement).

- Send Check or M/O
- State Make, Year, Engine Size. (Calif. Res. add Tax). (So New... it's Sold ONLY FROM FACTORY DIRECT).
- You may use your MASTER CHARGE or BANKAMERICARD. Send us (1) Your Number. (2) Interbank No. (3) Exp. Date

★ Before buying any other Type ignition system... Send Postcard for our FREE BROCHURE.

★ If you have already installed a C-D ignition system, Modernize and Increase its Efficiency... CONVERT YOUR "C-D" UNIT TO BREAKERLESS! Opto-Electric "TRIGGER UNIT"... Only \$34.95

● Our BEST Salesmen are the users of our ALLISON System!

● America's Oldest and Largest Mfg. of Opto-Electronic Ignition Systems.



**ALLISON**  
AUTOMOTIVE COMPANY

1267-P, East EDNA PL., COVINA, CAL. 91722

CIRCLE NO. 6 ON FREE INFORMATION CARD

# FREE!

## the 1976 Lafayette Electronics Catalog



**The most comprehensive  
consumer electronics  
catalog available!**

**Features Lafayette and Criterion  
Products Plus Major Brands**

Stereo/Quad Hi-Fi Components •  
Tape Equipment • Car Stereo • CB  
and Communications Gear • Police/  
Public Service Scanners • TV/FM  
and Communication Antennas • PA and  
Test Equipment • Tools • Electronic  
Calculators and Watches • Portable  
Radios • Security Systems • PLUS  
an exciting new Parts Line, Tubes,  
Batteries, Hardware and More!

- Stores Coast-to-Coast
- BankAmericard and  
Master Charge

# Lafayette

the electronics shopping center

Mail Coupon  
Today!

**FREE**

Dept. 35105

**Lafayette Radio Electronics**  
111 Jericho Turnpike  
Syosset, L.I., N.Y. 11791

Send me your FREE 1976 Catalog.

Name \_\_\_\_\_ Apt. \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

Zip

Send a 1976 Catalog to my friend.

Name \_\_\_\_\_ Apt. \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

Zip

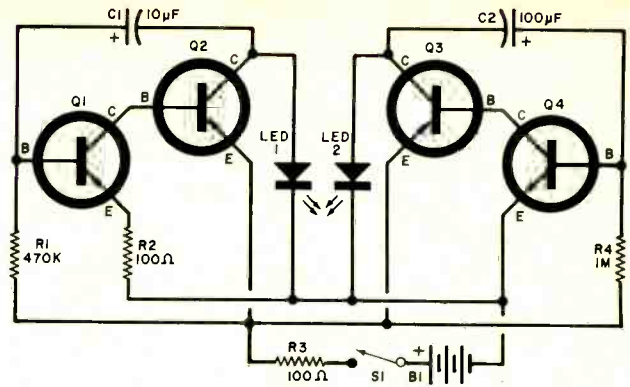


Fig. 5. Simple  
double-flasher  
circuit design.

LED is flashed at a rate which is a multiple of the other. With the values specified in Fig. 5, LED1 is flashed at (approximately) a 1-Hz rate. Then LED2 flashes at a 0.1-Hz rate—once in ten seconds. If the interlock feature is not needed, R3 may be omitted, but fixed small resistors should be connected in series with each LED to limit their respective maximum currents.

While the design is not overly critical, best results are obtained when low-leakage, moderate- to high-gain transistors are used. Small-signal (low-power) types are adequate. In the original model, the npn types, Q1 and Q4, were similar to type 2N170, while the pnp devices, Q2 and Q3, were equivalent to the 2N109. Both LED's were type MV50. The two capacitors were 10-volt electrolytics. A standard 9-volt transistor battery was used.

The double-flasher circuit may be assembled using perf board, point-to-point wiring, or a suitably designed PC board, as preferred, for neither layout nor lead dress are critical. However, some experimentation with component values may be needed to achieve optimum performance and to establish desired flashing rates due to component tolerances and differences in transistor characteristics.


**Device/Product News.** RCA's Solid State Division (Box 3200, Somerville, NJ 08876) has introduced a number of new IC's which are said to offer the performance and reliability characteristics of hermetically sealed devices in low-cost plastic packages. Identified by a "G" suffix, a number of standard circuits are now available in the new "hermetic-in-plastic" packages, including the CA741CG and CA747G op amps, the CA324G quad op amp, the CA339G quad voltage comparator, and the CA3724G and CA3725G high-current npn transistor arrays.

Also from RCA comes news of sub-

stantial price reductions of from 15 to 40 percent on over 100 types of IC's in the firm's extensive COS/MOS line and the addition of 30 new modules, IC's and power devices to the popular "SK" general replacement line. The new "SK" devices include four hi-fi audio modules ranging from 10 to 20 watts, a Darlington preamp, some 16 linear IC's designed for AM and FM radio, stereo, and TV receiver applications, power transistors, op amps, and SCR's.

A family of solid-state current sensors designed to protect highly sensitive electronic equipment against over-current conditions has been announced by the Micro Switch division of Honeywell (11 W. Spring St., Freeport, IL 61032). Designated type ES, the devices use coils which have resistances of a few milliohms to operate Hall-effect sensors. The solid-state sensor is triggered when coil current exceeds a specified level in the 1-to-3 amp range, producing a logic-level digital output signal which, in turn, can be used to actuate "crowbar" circuits or other protective devices. The sensors are designed to respond to over-current conditions in approximately 100 μs, independently of ambient temperature conditions and pre-existing current levels.

Suitable for use in a variety of timing, control and logic applications, a new series of pulse generator modules has been introduced by the Engineered Components Company (3580 Sacramento Drive, San Luis Obispo, CA 93401). Designed to provide precise output pulse widths when triggered by variable width inputs, the new devices are supplied in standard 16-pin DIP's. Twelve models are available, supplying output pulse widths from 5 ns to 100 ns at maximum pulse rates of from 100 MHz (for the 5-ns version) to 5 MHz (for the 100-ns model). All twelve devices operate on a standard 5-volt dc power supply. ♦

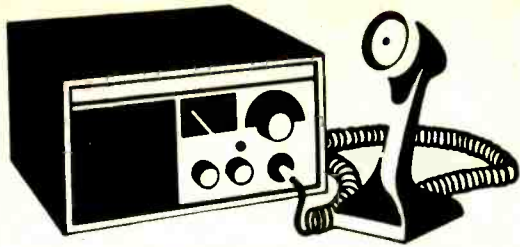

# CB Scene

By Len Buckwalter, K10DH

## HARMONIC TV INTERFERENCE

In a previous column, we dealt with a type of television interference called "fundamental blocking." This time, let's look at another source of TVI—"harmonic interference."

All efficient transmitters produce harmonics, which are signals at integral multiples of the desired or "fundamental" frequency. Thus CB

could zonk the upper end of channel 5, which occupies the frequencies between 76 and 82 MHz.

TV isn't the only service susceptible to harmonic interference from CB transmissions. The fourth harmonic on 108 MHz elbows into the top of the FM broadcast band. Although CB signals use amplitude modulation (to which FM receivers are immune), it's still possible for your voice to be heard on the FM sound systems of both TV and radio receivers through "incidental rectification."

CB's fifth and sixth harmonics fall on 135 and 162 MHz, which are not allocated to TV stations. However, these frequencies are assigned to commercial and government two-way radio services, which should not be interfered with. Further, the seventh and eighth CB harmonics—on 189 MHz and 216 MHz—are potential causes of TVI because they fall within channels 9 and 13.

The biggest source of TV interference, however, is the second harmonic, followed by the third. This is so because the power of a harmonic falls rapidly as its frequency grows higher, and the effects of higher-order harmonics are negligible unless a receiver is extremely close to the CB set.

There are several clues to look for if you suspect TVI is caused by harmonics. They are easy to examine, thanks to the greatest test instrument since the oscilloscope—the TV screen—which, after all, is an oscilloscope of sorts. The most effective

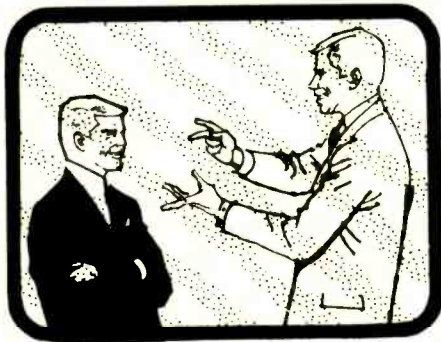


Fig. 1. Cross-hatch interference.

rigs, which have a fundamental of 27 MHz, also produce energy at 54 MHz, 81 MHz, 108 MHz, etc.—the second, third and fourth harmonics.

Harmonics are a problem because they become interfering signals on frequencies which are used by other services. For example, CB's second

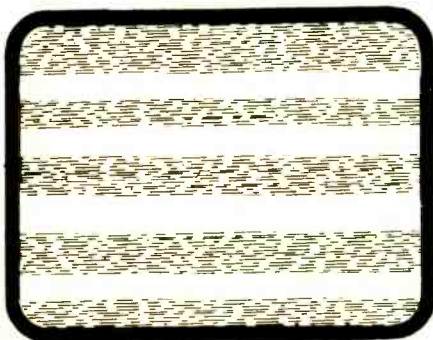


Fig. 2. Sound-bar interference.

harmonic (54 MHz) could affect the picture carrier of television's channel 2 whose video information starts at 54 MHz. The third harmonic (81 MHz)


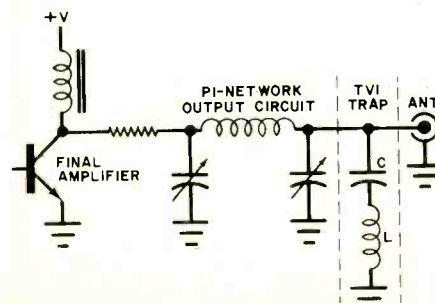



Fig. 3. An LC series wavetrap.

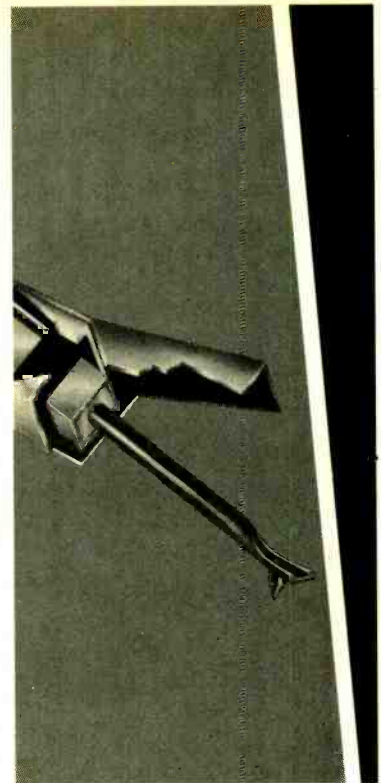
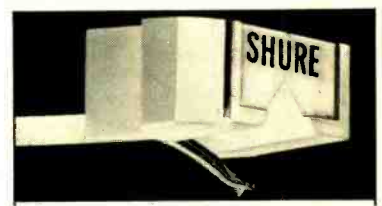
## This protects your most expensive hi-fi investment.

Trying to economize by putting off the replacement of a worn stylus could be like throwing away five dollars every time you play a record. Since the stylus is the single point of contact between the record and the balance of the system, it is the most critical component for faithfully reproducing sound and protecting your record investment. A worn stylus could damage your record collection. Insure against this, easily and inexpensively, by having your dealer check your Shure stylus regularly. When required, replace it immediately with a genuine Shure replacement stylus. It will bring the entire cartridge back to original specification performance.

Shure Brothers Inc.  
222 Hartrey Ave., Evanston, IL 60204  
In Canada: A. C. Simmonds & Sons Limited



Look for the name SHURE on the stylus grip and the words "This Stereo Dynetic® stylus is precision manufactured by Shure Brothers Inc." on the box.

Manufacturers of high fidelity components, microphones, sound systems and related circuitry.  
CIRCLE NO. 53 ON FREE INFORMATION CARD

way of identifying harmonic interference is to note which channels are affected. Only those channels which have a harmonic relationship to the Citizens Band could present problems. If ALL the channels, or one not harmonically related to 27 MHz, show symptoms of TVI, the problem lies elsewhere (most likely in the TV receiver itself). Because the second harmonic falls on 54 MHz, and is the most powerful multiple, TV channel 2 is the one most commonly affected.

Another important sign is the visual pattern of the interference. If the harmonic is potent and the TV re-

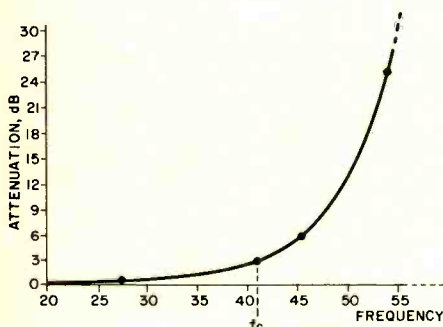


Fig. 4. Low-pass filter response.

ceiver and the transmitter are very close, complete picture "blackout" may occur. Weaker harmonics might cause the picture to be broken up, leaving a jumble of light and dark lines, or cause a "negative" (light and dark areas reversed) to appear. More often though, "cross-hatching"—diagonal bars or lines in the picture—is experienced (Fig. 1). This pattern is caused by heterodyning between the harmonic frequency and the carrier picture frequency. They are wide and few in number if the frequency difference is small, and very fine and plentiful if the harmonic and video carrier are farther apart.

Harmonics can also cause "modulation bars" or "sound bars," a series of dark and light horizontal bands across the screen that step with the syllabic rate of the CB'er's voice. (Fig. 2). It's possible that sound bars may appear when the carrier is modulated even if no cross-hatching is produced by a "dead" carrier.

While it is sometimes possible to treat an individual receiver to eliminate the harmonic-caused interference, this is *not* the course to take. You are merely treating an isolated symptom, and not the source of the disease—the *transmitter*. The FCC clearly specifies that a transmitter output should be as "clean" of harmonics as possible. The minimum fig-

ure to shoot for is 50 dB below power output. In this case, the 4-watt output from a CB transceiver should contain no more than 40 microwatts of harmonic energy.

**Harmonic Suppression.** There are several ways to obtain a high degree of harmonic suppression.

First, manufacturers usually provide an internal trap tuned to 54 MHz to cope with the second harmonic. As shown in Figure 3, it's an LC series trap across the r-f output. The trap offers very low impedance to any 54-MHz output and, in effect, short-circuits them to ground. The fundamental on 27 MHz is virtually unaffected.

If you're causing TVI on channel 2, the trap could be misadjusted or defective. Check your owner's manual—some manufacturers give a standard procedure for tuning the trap. One technique is to watch the interference on a TV set tuned to channel 2 close to the CB rig. As you tune through an access hole on the chassis, adjust the trap for minimum interference to the picture. Some traps use a coil slug which should be adjusted with a plastic tuning tool. Others have a trimmer capacitor that should be tuned with an insulated screwdriver.

The FCC, incidentally, refers to this procedure in its regulations. They state that brief transmissions can be made (with the antenna connected), "when necessary for the detection, measurement, and suppression of harmonics. . . . Test transmissions using a radiating antenna shall not exceed a total of 1 minute during any 5-minute period. . . ." That's time enough to tweak a tuning trap.

A series-tuned trap can only handle one harmonic, the one to which it is tuned. There's another, more flexible approach—an outboard low-pass filter.

Low pass filters as the name implies, are designed to allow all energy below the "cut-off" frequency to flow unimpeded, while frequencies above that frequency are not allowed to pass. Low-pass filters for CB should have a cut-off frequency of about 43 MHz, leaving the CB signal virtually unaffected. The insertion loss, or the amount of desired signal lost in the filter, is often below 0.5 dB (which is negligible).

As we move farther above cut-off, higher frequency signals have an even

more difficult route through the filter. A typical low-pass filter has a frequency response shown in Figure 4. Note that the cut-off frequency ( $f_c$ ), at which the amplitude is reduced by 3 dB (one-half), is 41 MHz. A signal on 54 MHz, on the other hand, is attenuated by a whopping 25 dB to 3/1000 of its original strength). Add that to the harmonic suppression provided internally by the CB manufacturer and almost all interference will vanish.

**Making Filters.** Low-pass filters can either be made at home or bought assembled. There are a large number of commercially available models. They are rather simple, though, and the schematic of a good one is shown in Figure 5. All capacitors (use 100 and 70 pF in parallel to get 170 pF) should be 500-V silver mica components. Given in the schematic are the number of turns for each coil. Wind them with 12 or 14 gauge wire on half-inch (1.3-cm) ID forms, at 8 turns per inch. The dashed lines are metal shields. The entire assembly can be mounted in a 6" x 4" x 2" (15.2 x 10.2 x 5.1 cm) enclosure.

The low-pass filter that you install (whether home-made or a commercial unit) should be inserted in the line close to the transceiver output via a


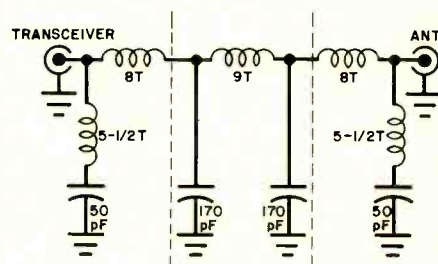


Fig. 5. Typical low-pass filter.

short coaxial jumper. Then connect the antenna feedline to the ANT jack on the filter. Bond the chassis to a good earth ground.

Another solution to the harmonic problem is to use an antenna matchbox. These devices, while designed to provide the correct output impedance for the transceiver, also add a degree of selectivity and harmonic suppression. In fact, a well-designed antenna-matching network can attenuate the harmonics by as much as 40 or 50 dB—all by itself! In many cases, they will clear up the interference, with the added bonus of allowing the final to work into a purely resistive load—the preferred order of things.

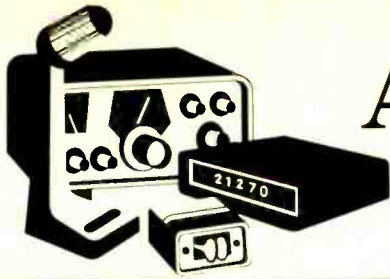

# Amateur Radio

By Herbert S. Brier, W9EGQ

## MORE ON RESTRUCTURING LICENSING

**T**HE COMMENTS and counter proposals made by the American Radio Relay League, Inc. (ARRL) in response to the proposals of the Federal Communications Commission Docket No. 20282 (issuing a new no-code vhf amateur license and reshaping the entire amateur license structure) turned out to be as surprising as the FCC proposals. The ARRL approved of the new vhf license to authorize phone and code operation on 145 to 145.5 MHz and 222 to 225 MHz with a maximum transmitter power input of 50 watts and a license term of five years. However, it could not quite bring itself to vote for the complete elimination of the code test. Instead, it recommended that applicants for the new license be required to identify the code characters with no speed requirement and to pass the standard Novice written examination.

ARRL also recommended that Novice licensees be given the new vhf privileges in addition to their lower-frequency code privileges. The Novice requirements would still include a 5-wpm code test and an elementary written examination. The FCC and ARRL agree that the vhf and Novice exams should be supervised by two volunteer examiners and that their privileges should be renewable. But that is about as far as their agreement goes.

ARRL wants Technician licensees to enjoy all amateur privileges above 29 MHz and Novice privileges below 29 MHz. The FCC goes along with the Novice privileges but wants a new Experimenter's license which would grant all vhf/uhf privileges. ARRL wants the General class requirements reduced from 13 wpm to 10 wpm and a 15-wpm code test added to the Advanced class exam for future licensees. It wants the General, Advanced, and Extra class privileges to remain essentially unchanged, however. In contrast, the FCC would leave the

code tests for the General and Advanced licenses unchanged, but cut their privileges off at 29 MHz for new licensees.

The ARRL and the FCC differ even more widely in their proposed treatment of Conditional and "by-mail" Technician class licensees. The ARRL proposes to freeze them into their present status. The FCC proposes that, except for the physically handicapped, they would be required to pass an appropriate examination before an FCC representative to renew their privileges. I personally feel the FCC proposal is too harsh; while the ARRL proposal would perpetuate privileges that some acquired by chicanery. A more just approach would be that all (except the physically handicapped) who hold conditional-type licenses when the new regulations go into effect shall have five years to pass the new examination. They would not be deemed to have failed it, however, even if they have failed to achieve a passing grade in one or more attempts, until the grace period expires. At that time, their privileges would be reduced one grade. I also oppose any code test for the new vhf license and recommend that its written examination be concerned solely with amateur regulations and operating procedures.

**What Next?** Optimists are hoping that the FCC will wade through the many, many comments it received on these matters and come up with a series of decisions before the end of 1975. If this happens, it will be months after that before the new regulations can be implemented; but it is not too soon now for prospective new licensees and the amateur world to make preparations. The Chicago FM Club (WR9ABY), for example, is actively working on a new repeater to be located in the new 222-MHz sub-band; so that the newcomers will be able to

free

**TRIGGER**  
MONEY-SAVING  
CATALOG



FOR THE MAN IN ELECTRONICS

SEE

**TRIGGER'S GREAT SELECTIONS**

Send for this reliable buying guide to carefully selected:  
**Amateur Gear • Stereo Hi-Fi • Electronic Kits • CB Radio • Tape Recording • Electronic Parts • Antennas • Tubes • Transistors • Tools • Books • Test Gear**

Count on TRIGGER for the best in electronics. Write for this Free Catalog today!

A MONEY-SAVER

SEND FOR IT TODAY!

FREE Catalog

TRIGGER Electronics, Dept. 12-OC  
 7361 North Ave., River Forest, Ill. 60305  
 Send FREE TRIGGER Catalog

Name \_\_\_\_\_  
PLEASE PRINT

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

CIRCLE NO. 60 ON FREE INFORMATION CARD



**LISTEN!**

We're one of the country's largest Mail Order Houses of Stereo Equipment and Musical Instruments.

Our volume buying power enables us to pass the savings on to you. Listen to us ... You can't go wrong.

Fill out this coupon and mail to address below for our latest Free Catalogs.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

AUDIO CATALOG  
 MUSICAL INSTRUMENT CATALOG

PE-10


**STEREO DISCOUNTERS**

7A AYLESBURY ROAD □ TIMONIUM, MD. 21093  
 [301] 252-6880

CIRCLE NO. 58 ON FREE INFORMATION CARD


# CREI—the only home-study college-level training

## and now

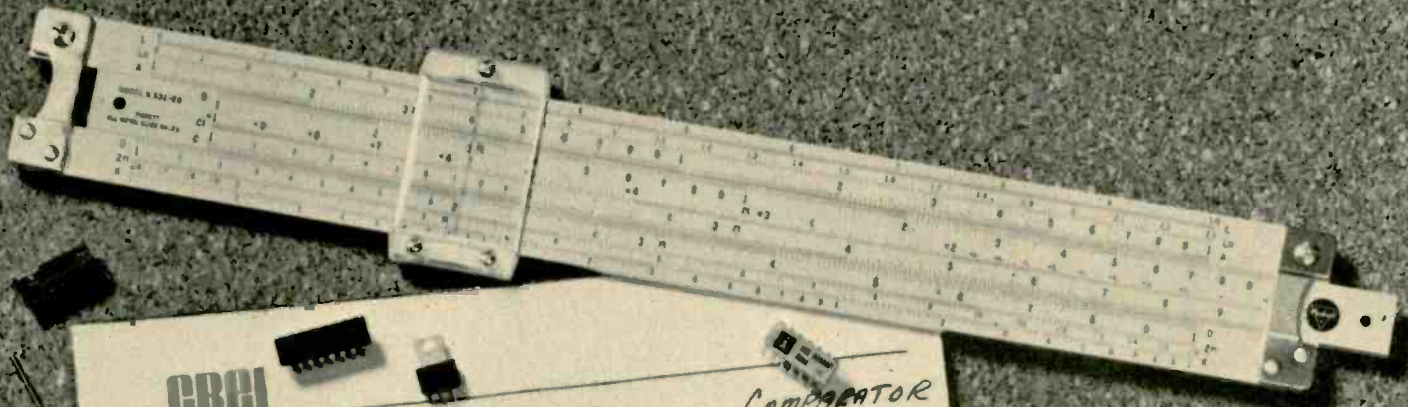

CREI

COMPARATOR  
CONTROLLED  
CLOCK

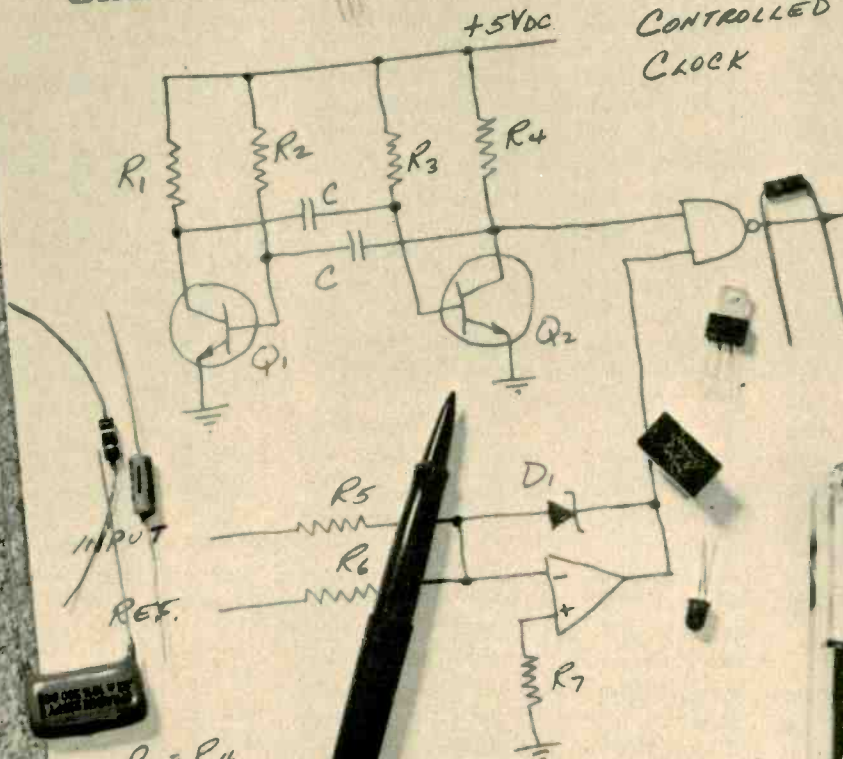

$$R_1 = R_4$$
$$R_2 = R_3 = R$$

$$T = .7RC$$

$$f = \frac{1}{2T}$$





# program which gives you in electronic circuit design

## only CREI offers you a complete college-level Electronic Design Laboratory to speed your learning

**Electronic circuit design**—source of all new development in the application of electronics to new products and services. Without this skill, we would be unable to monitor the heartbeat of men in space. Without it, the computer revolution would never have occurred. And we would have yet to see our first TV show. *Yet, only CREI teaches electronic circuit design at home.*

### ELECTRONIC CIRCUIT DESIGN

A key skill which paces our nation's progress in countless fields—from pollution control to satellite tracking to modern medicine to exploring the ocean's depths. And beyond. A skill which *you* must have to move to the top in advanced electronics.

### CREI programs open up new worlds of opportunity for you.

In addition to electronic circuit design, CREI provides you with a full advanced electronics education in any of thirteen fields of specialization you choose. Communications, computers, space operations, television, nuclear power, industrial electronics—to mention just a few of the career fields for which CREI training is qualifying. With such preparation, you will have the background for a career which can take you to the frontiers of the nation's most exciting new developments. And around the world.

### This free book can change your life. Send for it.

If you are a high-school graduate (or equivalent) and have previous training or experience in electronics, then you are qualified to enroll in a CREI program to move you ahead in advanced electronics.




Send now for our full-color, eighty page book on careers in advanced electronics. In it, you will find full facts on the exciting kinds of work which CREI programs open up to you. And full facts on the comprehensive courses of instruction, the strong *personal* help, and the professional laboratory equipment which CREI makes available to you. All at a surprisingly low tuition cost.

### And when you have it, talk with your employer about it.

Tell him you're considering enrolling with CREI. He'll undoubtedly be happy to know you are planning to increase your value to him. *And he may offer to pay all or part of your tuition cost.* Hundreds of employers and government agencies do. Large and small. Including some of the giants in electronics. *If they are willing to pay for CREI training for their employees, you know it must be good.*

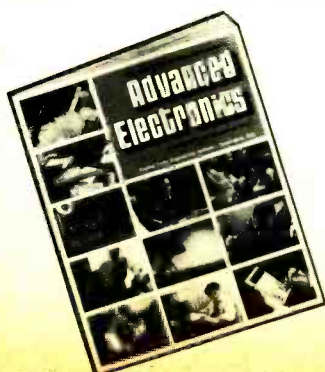**Send for Advanced Electronics today. You'll be glad you did.**



CREI Dept. E-1210F  
3939 Wisconsin Avenue  
Washington, D.C. 20016

Rush me your FREE book describing my opportunities in advanced electronics. I am a high school graduate.

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ ZIP \_\_\_\_\_

If you have previous training in electronics, check here

Employed by \_\_\_\_\_

Type of Present Work \_\_\_\_\_

Veterans and servicemen, check here for G.I. Bill information

# CREI

**CAPITOL  
RADIO  
ENGINEERING  
INSTITUTE**

WASHINGTON, D.C. 20016

# SAVE!

MONEY • TIME • FREIGHT

QUALITY STEREO EQUIPMENT  
AT LOWEST PRICES.

YOUR REQUEST FOR QUOTA-  
TION RETURNED SAME DAY.

FACTORY SEALED CARTONS—  
GUARANTEED AND INSURED.

SAVE ON NAME BRANDS LIKE:  
A.D.C. KLH  
A.R. SHURE  
DYNACO KOSS  
SONY FISHER

PIONEER  
AND MORE THAN 50 OTHERS  
BUY THE MODERN WAY  
BY MAIL—FROM

## ia illinois audio

Department 217S  
12 East Delaware  
Chicago, Illinois 60611  
312-664-0020

CIRCLE NO. 27 ON FREE INFORMATION CARD

### ONE MARK AHEAD OF THE REST....



ADR Audio, one mark ahead of its competitors with the lowest prices of Famous Brand audio components, has now added complete CB & Video depts. All orders promptly shipped from the ADR warehouse in factory sealed cartons, fully warranted, fully insured. Send for our special price quote & newest money saving catalogue. Its your move.

FOR IMMEDIATE QUOTE  
CALL (202) 723-6060

**A.D.R. AUDIO**  
6200 CHILLUM PLACE N.W.  
WASHINGTON, D.C. 20011

CIRCLE NO. 1 ON FREE INFORMATION CARD

use it. Based on the performance of the existing repeater, of which the new one will be a copy, 25-watt mobile stations within a radius of 25 miles of the repeater will be able to work each other with "solid" signals. Therefore, mobile stations on opposite sides of Chicago, 50 miles apart, will be able to communicate with each other easily.

Until the scope of the new vhf examination is announced, it is difficult to tell a prospective licensee exactly what to study. If ARRL's suggestion prevails, however, the written test will be the same for the Novice license. It certainly will not be more comprehensive. If one studies for a Novice license and learns the code at 5 wpm, he will be ahead of the game when the regulations do come into effect.

**New Study Guide.** The spiral-bound *From 5 Watts to 1000 Watts*, a new programmed course in amateur radio recently introduced by Radio Shack, will be useful to a person with no knowledge of electronics who wants to pass a Technician or General class written examination. The book provides the neophyte with an understanding of resistance, conductance, Ohm's Law, horizontal and vertical antennas, capacitance, inductance, frequency, transistors, vacuum tubes, etc. The components are identified by photographs, and their schematic symbols. Their functions are explained with the aid of drawings and schematic diagrams. While *5 Watts to 1000 Watts* is not the equivalent of a full-fledged electronics course, diligent study of it will make it easy to pass the Novice class written test and take the student a long way toward passing the Technician/General written test. For those who are not necessarily studying for an amateur license test, the book might be a good invest-

ment if they are a little hazy on some of the fundamentals.


#### Compact 80/40-Meter Inverted V.

The antenna shown in the diagram is for the 80- and 40-meter bands. It is only 10 feet (30.15 m) longer than a conventional 40-meter dipole, but gives good 2-band coverage. The dimensions were suggested by Art Smith, W6INI. The coils at A are made of #18 wire wound on 1.125" (2.86-cm) OD PVC pipe forms. Cut two 8 3/4" (22.22-cm) pieces of the pipe for the forms and drill two rows of three #42 holes 7 1/4" (18.42 cm) apart in each. Measure two 50' (15.24-m) lengths of the #18 wire for the coils.

Thread one end of one length of wire through one of the rows of holes in one form, allowing 1 1/2" (3.8 cm) of wire to protrude from the form. Close-wind the wire on the form and thread the remaining end through the holes at the other end of the form. Mount a #10 brass or stainless steel eye bolt in each of two PVC pipe caps used to cover the ends of the form. Then insert a #10 solder lug under each outside nut. Drill a #42 hole in each cap adjacent to the lugs. Coat the insides of the caps and the ends of the forms with PVC cement. Position the caps on the ends of the forms so that the ends of the wire protrude through the #42 holes near the solder lugs. Tamp the caps firmly into place and allow the cement to set. Scrape the enamel from the ends of the wire and solder them to the lugs. Use a hot iron, make the connections rapidly, and immediately cool them.

The center insulator can be fabricated from a 5/16" (0.8-cm) piece of plexiglass, an SO-239 coaxial chassis jack and a U clamp to fasten the assembly to the mast. The ends of the antenna can be insulated by lengths of

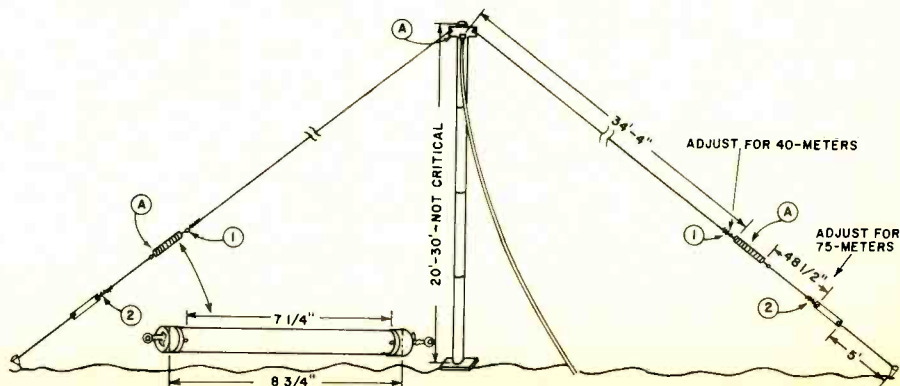*Design for a compact 80/40-meter inverted-V antenna.  
Lead-in is RG-58 or RG-8 depending on length and power.*



plexiglass or standard antenna insulators.

The dimensions in the diagram are approximately correct for the 7.2- and 3.8-MHz phone bands. Assemble the antenna using these dimensions, allowing another 12" (28.5 cm) of wire at points 1 and 2. For the lead-in, use RG-58 for short runs and low power; RG-8 for long runs and high power.

Feed r-f power through an SWR bridge into the antenna at intervals across the 7-MHz band to find the frequency of minimum SWR. Take measurements in smaller frequency increments as the SWR approaches its minimum value, which should be about 1:1 at the resonant frequency of the antenna. If the minimum SWR occurs at a lower frequency than desired, shorten the 7-MHz section of the antenna at points 1. If minimum SWR occurs at too high a frequency, lengthen the antenna. Make the adjustments two or three inches at a time. After 40-meter resonance is established, transfer operations to the 3.5-4-MHz band and adjust lengths at points 2 for minimum SWR at the desired frequency on that band.

After the resonant frequencies of the antenna have been established on both bands, point 1 can be soldered. Proximity to large objects changes the resonant frequency on the 80-meter band, however. Therefore, it is advisable to make it easy to change the lengths at points 2, if the antenna is going to be used in different locations. The center of the antenna should be as high as possible; but if the center height is increased, raise the heights of the ends, too, so that the apex angle does not become too acute.

**CQ World-Wide DX Test.** CW: October 25-26. Phone: November 29-30. Exchange serial numbers and reports with foreign stations on each band. This contest separates the men from the boys. Rules and score sheets from CQ Magazine, 14 Vanderventer Ave., Port Washington, NY 11050.

**ARRL Section Sweepstakes (SS).** CW: November 8-9. Phone: November 22-23. Work as many U.S. and Canadian stations as possible on all bands. Official rules and score sheets from ARRL, 225 Main St., Newington, CN. 06111. IMPORTANT: Include large, stamped return envelope with your requests for data on either contest. Two units of first class postage are suggested. ♦

OCTOBER 1975

## Why any cartridge (even ours) with an elliptical stylus must be considered just a bit old-fashioned.

As a premium stylus, elliptical designs have only one real advantage over a Shibata stylus: lower cost. Which is why we still offer them.

But when it comes to performance, a Shibata stylus is far, far better. It provides the small scanning radius needed to track highs (up to 45 kHz for CD-4), but without the penalty of requiring extremely low stylus force settings.

In fact, even tracking at up to 2

grams, a Shibata stylus is easier on your records than an elliptical stylus trying to track at 1/2-gram! New records last longer, old records sound better, and you can play every kind of two or four-channel record made.

All Audio-Technica top-of-the-line cartridges have genuine Shibata styli. Anything less would be false economy for you . . . and out-dated technology for us. Prove it to yourself today.



**audio-technica**®

AUDIO-TECHNICA U.S., INC., Dept. 105P, 33 Shiawassee Ave., Fairlawn, Ohio 44313  
Available in Canada from Superior Electronics, Inc.


CIRCLE NO. 10 ON FREE INFORMATION CARD

**UNIVERSAL™**

T.M. Audio-Technica. Dual Magnet cartridges are protected by U.S. Patent Nos. 3,720,796 & 3,761,647. Shibata stylus Patent No. 3,774,918.
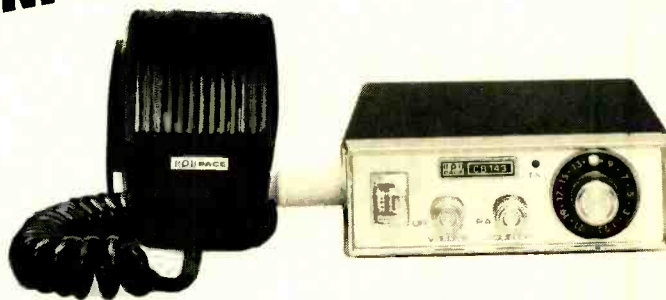
## PACE MAXI-MINI CB

THE LATEST MAXI-MUM TALK POWER WITH  
MINI-MUM SIZE



Pace CB 143 feature-packed: 23 channel synthesized design • (+) or (-) ground  
• separate jack for remote speaker • 'S' meter to monitor incoming signal strength • transmit indicator light • PA system. Only \$129.95.

See your distributor and  
pickup your "Maxi-Mini" today!

**((p)) Pace Communications, Div. of Pathcom Inc., 24049 S. Frampton Ave., Harbor City, Ca. 90710.** Available in Canada from Superior Electronics Inc. Export (all other parts of the world): 2200 Shamus Dr., Westbury, N.Y.

CIRCLE NO. 42 ON FREE INFORMATION CARD

62

# Planning? to move?

Let us know **8 weeks** in advance so that you won't miss a single issue of **POPULAR ELECTRONICS**.

Attach old label where indicated and print new address in space provided. Also include your mailing label whenever you write concerning your subscription. It helps us serve you promptly.

Write to: P.O. Box 2774, Boulder, CO 80302, giving the following information:


- Change address only.
- Extend subscription.  Enter new subscription.
- 1 year \$6.98
- Payment enclosed (1 extra BONUS issue)
- Bill me later

**AFFIX LABEL**

If you have no label handy, print OLD address here.

name please print	address	city	state	zip code
name	address	city	state	zip code

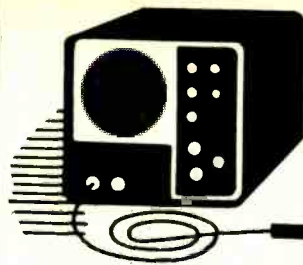Add'l postage per year: Add \$1 for Canada; \$2 for all other countries outside the U.S.



# Test Equipment Scene

By Leslie Solomon

## USING DIODES IN POWER SUPPLIES

**A**CCORDING to my mail, the piece of equipment that most people want to build for their test bench is a power supply. They usually want a supply that is well-filtered, regulated, has a variable output voltage level, and can be used to power a wide variety of equipment.

Questions most often asked about designing a supply involve the rectifier diodes and how to keep them from burning out. The confusion seems to lie in interpreting the diode specifications—particularly the peak inverse voltage (PIV).

There are two ways to apply voltage to a diode—the right way (forward) and the wrong way (reverse). The right way is what is normally seen in a circuit and the wrong way is hardly ever seen, but is important to take it into consideration. For example, if we want a positive output from a simple half-wave rectifier, we would connect the diode anode to one end of the transformer secondary and the diode cathode to the positive lead of the filter capacitor. The other end of the transformer is then the common and is connected to the negative terminal of the filter capacitor. Now, when power is applied, the diode conducts on the positive half cycles and is reverse biased on the negative halves. But there is more to the story than that.


When the diode is properly biased, it conducts and allows the positive half cycles to put a charge on the filter capacitor, making the positive end more and more positive. On the negative half cycle, the diode anode is reverse biased, but the cathode is also reverse biased by the positive voltage on the capacitor. Therefore, the total

voltage across the diode is not just the transformer voltage, but the transformer voltage plus the capacitor voltage. In fact, this voltage is 2.828 times the actual rms value. If the transformer supplies 35 volts rms, then the actual voltage across the diode can reach about 99 volts. If a center-tapped transformer and two diodes are used in a conventional full-wave rectifier/filter circuit, the voltage across the diode would be 1.414 times the rms (50 volts in our example).

So, it can be seen that the PIV rating of the diode must be carefully observed. (It is given in the specifications.) Using just any silicon rectifier is providing an invitation to disaster.

**Choke-Input Filters.** If a choke-input filter is used, it must be kept in mind that, when the diode switches through the zero point of the voltage cycle, the current in the inductor goes to zero. This sudden drop in current causes a large back emf across the diode. (This is how ignition and horizontal-sweep circuits work.) In this case, you must use a diode having a higher PIV and also use the circuit shown at A across the inductor. The approximate value of the transient-suppressing capacitor can be found from  $C = (L \times I^2)/10E^2$ , where C is in microfarads, L is the maximum choke inductance in henries, I is the maximum current through the choke in amperes, and E is the maximum dc supply in kilovolts. The series resistor should be equal to the load impedance connected across the supply.

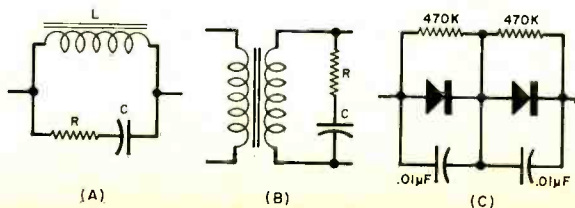Another source of damaging transients is the power transformer itself. Power-line transients and the result-




## DIXIE SAVE ON Brand Name Audio Components

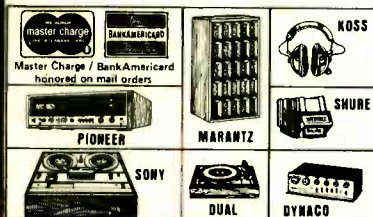**BY MAIL**

Write Today for Our  
**FREE Audio Catalog**

DIXIE is one of the oldest and largest audio component mail order houses in the country. Our prices on brand name components are actually **LOWER** than "Discounters". See our new catalog or call us for a price quote. Everything shipped factory-sealed with full manufacturer's warranty.



**DIXIE HI-FIDELITY** PE-10

5600 Second St., N. E., Washington, D. C. 20011  
Phone: 1-202-635-4900

Please rush me your **FREE** Audio Catalog and complete information. I understand there is no obligation.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_

ing abrupt changes in the magnetizing current in the transformer can cause damage in voltage-sensitive solid-state components. The circuit shown at B is one way to reduce these transients. The approximate value of the capacitor can be found from  $C = (15 \times E \times I)/e^2$ , where C is in microfarads, E is the maximum dc supply voltage, I is the maximum current of the supply in amperes, and e is the rms voltage of the transformer secondary. Here again, the resistor should be equivalent to the load impedance on the supply. (If there is any doubt about this, use 100 ohms.) For transient suppression, it is also possible to use a commercial suppressor such as those in the GE MOV line.

**Current-limiting Resistors.** It is wise to use series current limiting resistors with silicon rectifiers. Knowing the voltage on the transformer secondary and the maximum allowable diode current (from its specifications), you can calculate the value of resistance that will safely limit the current if a direct short were to occur across the rectifier (which happens when the supply is first turned on and the filter capacitors are not charged). Calculate the power and use a resistor of sufficient size to prevent rapid burnout.

If the secondary voltage of the transformer is too high for the PIV of the diodes you have on hand, put two or more diodes in series. To equalize the PIV, connect a resistor of about 470,000 ohms across each diode. To reduce possible transient damage, connect a 0.01- $\mu$ F, 1-kV capacitor across each diode as shown at C. There is another good reason for using these shunt capacitors, which can be explained as follows.


Silicon diodes, such as those used as rectifiers, do not conduct until the applied forward voltage reaches about 0.6 volt. As the input reaches this value, the diode junction suddenly snaps into conduction, producing a small, but steep, waveform. The waveform can have harmonics that go far up into the r-f spectrum, producing signals that can interfere with a radio receiver. Using capacitors across the rectifier diodes suppresses this r-f generation.

If you have a receiver that uses solid-state diodes in the rectifier and you are troubled by strange signals that don't seem to make sense, try connecting a capacitor across each rectifier diode. ♦

# Particular? try these high-performance circuit-builder's delights

**STOP fussin' and cussin' at soldering, heat sinks, short circuits and ruined components. That's a DRAG... when circuit building should be FUN and components should be REUSABLE. Now you can plug in, power up and test your experimental circuits FAST, SAFELY and CONVENIENTLY (and reuse those components) with all the assurance and satisfaction of A P HIGH PERFORMANCE in every circuit-building device. TRY THEM AND SEE!**
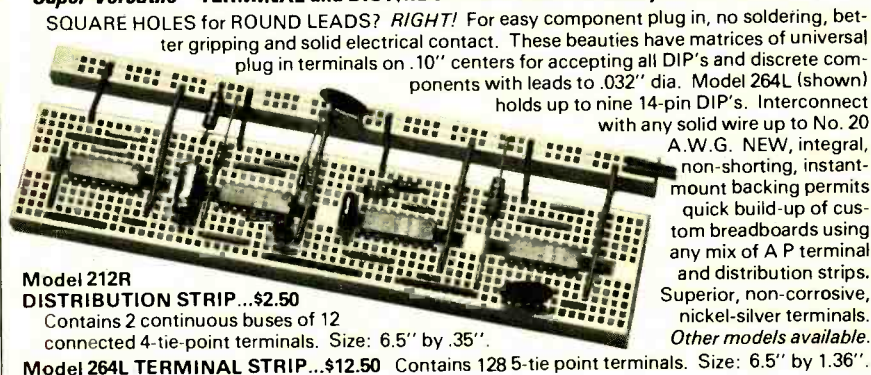
## Super-Versatile™ TERMINAL and DISTRIBUTION STRIPS to build your own breadboards



**SQUARE HOLES for ROUND LEADS? RIGHT!** For easy component plug in, no soldering, better gripping and solid electrical contact. These beauties have matrices of universal plug in terminals on .10" centers for accepting all DIP's and discrete components with leads to .032" dia. Model 264L (shown) holds up to nine 14-pin DIP's. Interconnect with any solid wire up to No. 20 A.W.G. NEW, integral, non-shorting, instant-mount backing permits quick build-up of custom breadboards using any mix of A P terminal and distribution strips. Superior, non-corrosive, nickel-silver terminals. *Other models available.*


**Model 212R DISTRIBUTION STRIP...\$2.50**  
Contains 2 continuous buses of 12 connected 4-tie-point terminals. Size: 6.5" by .35".

**Model 264L TERMINAL STRIP...\$12.50** Contains 128 5-tie point terminals. Size: 6.5" by 1.36".

## HIGH quality... LOW cost... Assemble-it-yourself KIT... SAVE \$\$\$

### A·C·E 200-K All Circuit Evaluator


**MORE SQUARE HOLES...728...count 'em.** Same high-performance features as above! This handy breadboard kit offers excellent circuit-building versatility. Holds up to eight 16-pin DIP's. Universal matrix of solderless, plug-in tie points includes 136 separate 5-tie-point terminals and 2 distribution buses, each consisting of 6 connected 4-tie-point terminals... typically for voltage and ground. Includes two 5-way binding posts, 4 rubber feet. Aluminum base, serving as ground, is gold-anodized for surface protection. *Assembles in 12 min.*

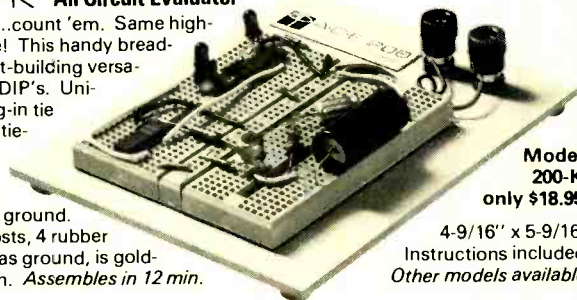

**Model 200-K only \$18.95**

4-9/16" x 5-9/16"  
Instructions included.  
*Other models available.*
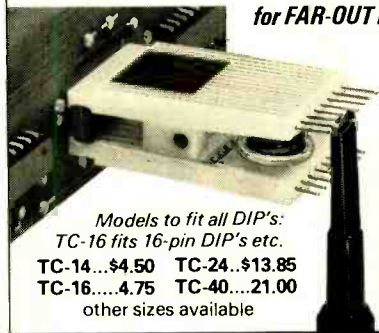
## for FAR-OUT DIP TESTING... Super-Grip™ IC TEST CLIPS



*Models to fit all DIP's:*  
TC-16 fits 16-pin DIP's etc.  
TC-14...\$4.50 TC-24...\$13.85  
TC-16...4.75 TC-40...21.00  
other sizes available

**No more shorting across DIP leads... just clip on an IC TEST CLIP to bring DIP leads out for SAFE attachment of scope probes and other leads.**

Ideal for signal inputs, tracing, troubleshooting, etc. Patented, precision, "contact comb" design guarantees no shorting between DIP leads. Probes can hang "no-hands" free on Test Clip terminals in card racks (photo shows this unique feature). Engineered mechanical clamping plus gold-plated phosphor bronze terminals provide superior electrical contact. *Unequaled as a safe DIP-pulling tool, too!*

*We honor Master Charge & BankAmericard charge orders.*

### ORDER BY MODEL NUMBER

Add proper fees from this chart →  
Add sales tax on OH and CA orders.  
(F.O.B. Painesville on company P.O.'s.)  
Dealer inquiries invited.

SHIPPING/HANDLING	C.O.D.
Up to \$10.00	\$1.00 \$ .70
\$10.01 to \$25.00	1.50 .80
25.01 to 50.00	2.00 .90
50.01 to 100.00	2.50 1.00



*All products guaranteed to meet or exceed published specifications*

## A P PRODUCTS INCORPORATED

Box 110-H • 72 Corwin Drive • Painesville, OH 44077  
or phone 216/354-2101 • or Twx 810-425-2250



## 12 REASONS YOUR CAR NEEDS TIGER CDI

Instant starting in any weather - Eliminates tune-ups - Increases gas mileage - Increases horsepower 15% - Improves acceleration and performance - Spark plugs last up to 70,000 miles - Reduces engine maintenance expense - Amplifies spark plug voltage to 45,000 volts - Maintains spark plug voltage to 10,000 RPM - Reduces exhaust emissions - Dual ignition switch - An Unconditional LIFETIME GUARANTEE. Installs in 10 minutes on any car with 12 volt negative ground - No rewiring - Most powerful, efficient and reliable Solid State Ignition made.

SATISFACTION GUARANTEED or money back

TIGER 500 assembled . . . . . \$53.95  
TIGER SST assembled . . . . . \$42.95  
Post Paid in U.S.A.

Send check or money order with order to:

**Tri-Star Corporation**

P. O. Box 1727 C  
Grand Junction, Colorado 81501

DEALER INQUIRIES INVITED

CIRCLE NO. 59 ON FREE INFORMATION CARD

# free

# BA

## 1976 catalog



**244 PAGE  
RADIO, TV &  
ELECTRONICS  
CATALOG**


Your buying guide for Everything in Electronics . . . Stereo, Hi-Fi, TV's, Radios, Tape Recorders, CB, Kits, Tools, Books and Electronic Parts.

**WRITE FOR YOUR  
FREE COPY NOW!**

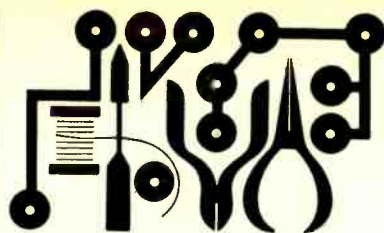**burstein-applebee**

DEPT. PE                      3199 MERCIER ST.  
KANSAS CITY, MO. 64111

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_  
STATE \_\_\_\_\_ ZIP \_\_\_\_\_



# Experimenter's Corner

By Forrest M. Mims

## A PROGRAMMABLE TIMER/COUNTER

**A** FEW years ago, Signetics overwhelmed us all with the introduction of the 555 timer. That chip, as you probably know, is one of the most versatile IC's around, and literally scores of applications for it have been published in POPULAR ELECTRONICS and other magazines.

More recently, Exar capitalized on the 555's popularity by pairing it with a binary counter and putting the whole thing in a 16-pin DIP. They called it the XR-2240 and it is a fully programmable timer/counter with all kinds of fascinating applications. I'm going to describe a few that I've come up with—you will probably think of many others.

With just a few external parts, you can connect the XR-2240 in a free-running mode as shown in Fig. 1. Use anything from 4 to 15 volts for the supply. Current drain is fairly low—about 10 mA for a 9-volt battery. The combination of R and C determines the oscillation period ( $T = RC$ ) of the XR-2240's internal time base. The binary counter outputs (pins 1 through 8) increase T (or reduce the frequency, depending on how you look at it) by factors of 1, 2, 4, 8, 16, 32, 64, and 128. The result is eight square waves with harmonically related frequencies from a single RC timing combination. Figure 2 is a scope photo showing six of the counter outputs from an XR-2240 in its free-running mode ( $R = 1.5$  kilohms and  $C = 0.022 \mu\text{F}$ ). Of course, this is impressive, but you haven't seen anything yet!

You can get some really interesting waveforms by connecting the binary counter outputs together. Some of the possible results are shown in Fig. 3. Exar calls the circuit configuration a binary pattern generator, but I call it a super-deluxe audio "chirper." Just connect a crystal or high-impedance magnetic earphone to the output to hear the chirps. By experimenting

with the binary counter output interconnections and installing resistors of various values between some of the outputs, you will be able to obtain a variety of chirps, buzzes, warbles, and other strange sounds. For even more variations, change values of R and C.

If weird-sounding electronic music doesn't interest you, you can always use the pattern generator in more conventional applications. For example, it makes a nifty marker tone generator for a communications system (such as a long-range laser communicator). While a monotone audio oscillator would do the job, it's hard to miss a chirping marker or mistake it for a heterodyne.

**Waveform Generator.** Another possibility is to use the circuit as a complex waveform generator. I really mean complex, because the XR-2240 can generate all kinds of stepped waveforms. The photo in Fig. 4 shows part of a repetitive, stepped waveform generated by connecting several resistors of different values between the binary counter outputs and the circuit output.

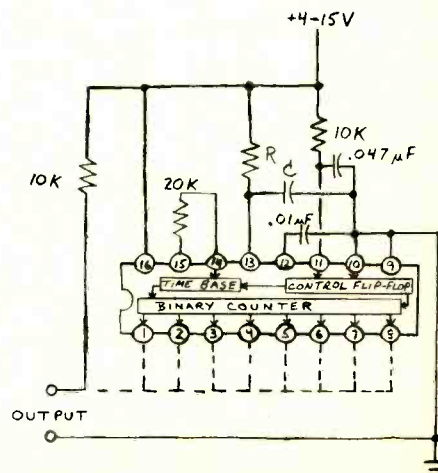


Fig. 1. Schematic of XR-2240 in free-running (astable) mode.

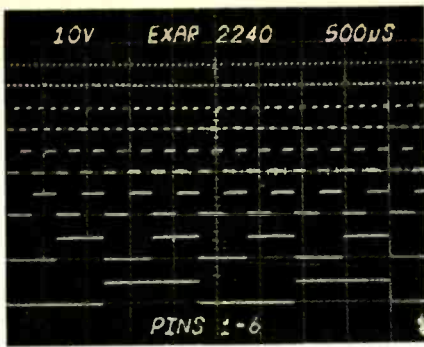


Fig. 2. Output on pins 1 to 6. Scope photos taken with C-59 camera on a Tektronix 7603 scope with 7M13 plug-in readout unit.

If you don't need far-out waveforms like the one in Fig. 4, you can generate more conventional staircases. For a staircase with 255 steps, connect a resistor with a value of about 1000 ohms from pin 8 to the output. Then connect resistors 2, 4, 8, 16, 32, 64, and 128 times that value from pins 7, 6, 5, 4, 3,

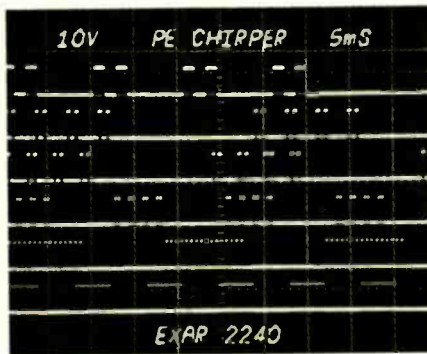


Fig. 3. Six different "chirp" (tone burst) outputs from XR-2240.

2, and 1 (respectively) to the output. You'll have to use precision resistors to get a uniformly spaced staircase. If some values are slightly off, the waveform will be somewhat distorted.

There are lots of other uses for the XR-2240 and they include analog-to-digital conversion, sample-and-hold,

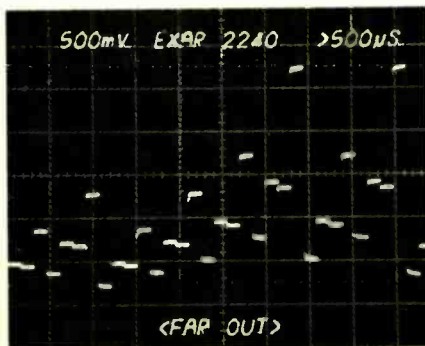


Fig. 4. Complex waveform obtained by connecting resistors to outputs.

harmonic synchronization, and ultra-long "timing" circuits (not true one-shots, but useful nonetheless). The timing properties of the chip are really impressive. For example, the values of R and C in Fig. 1 can be set to provide just one pulse every 10 or 15 minutes. Since pin 8 has a period of 128T, an RC combination which gives a period of 12 minutes would provide an output square wave with a period of  $128 \times 12$  or 1536 minutes. That's more than a whole day. You can get longer delays by connecting more counter outputs to the output bus. The total time delay will equal the sum of the delays available at each counter output pin.

For truly incredible delays of up to 3 years (!), you can cascade two XR-2240's in series. The delays available from the combination can be used to remind you of birthdays and anniversaries, limit your offsprings' phone calls, and dream up assorted science fiction gadgets.

We'll take a closer look at some of the XR-2240 timing applications in a future column. Meanwhile, latch on to a couple of XR-2240's (see the ads in the back of this magazine), and warm up your soldering iron. ♦

## Now...the most enjoyable, do-it-yourself project of your life—a Schober Electronic Organ!

You'll never reap greater reward, more fun and proud accomplishment, more benefit for the whole family, than by assembling your own Schober Electronic Organ.



You need no knowledge of electronics, woodwork or music. Schober's complete kits and crystal-clear instructions show you — whoever you are, whatever your skill (or lack of it) — how to turn the hundreds of quality parts into one of the world's most beautiful, most musical organs, worth up to twice the cost of the kit.

Five superb models, with kit prices from \$575 to around \$2,300, each an authentic musical instrument actually superior to most you see in stores.

Join the thousands of Schober Organ builders — owners who live in every state of the Union. Often starting without technical or music skills, they have the time of their lives — first assembling, then learning to play the modern King of Instruments through our superlative instructions and playing courses.

Get the full story FREE by mailing the coupon TODAY for the big Schober color catalog, with all the fascinating details!

The Schober Organ Corp., Dept. PE-62  
43 West 61st Street, New York, N. Y. 10023

- Please send me Schober Organ Catalog.  
 Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

CIRCLE NO. 51 ON FREE INFORMATION CARD

## FREE McIntosh CATALOG and FM DIRECTORY

Get all the newest and latest information on the new McIntosh Solid State equipment in the McIntosh catalog. In addition you will receive an FM station directory that covers all of North America.



### MX 113

FM/FM STEREO - AM TUNER AND PREAMPLIFIER

**SEND TODAY!**

McIntosh Laboratory, Inc.  
East Side Station P.O. Box 96  
Binghamton, N.Y. 13904  
Dept. PE

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

If you are in a hurry for your catalog please send the coupon to McIntosh. For non rush service send the Reader Service Card to the magazine.

CIRCLE NO. 35 ON FREE INFORMATION CARD

**Hunting for  
a better job?**

**CIE will  
help you get  
the license  
you need**





**A Government FCC License can help you qualify for an exciting, rewarding career in ELECTRONICS, the Science of the Seventies. Read how you can prepare at home in your spare time to pass the FCC Licensing examination.**

If you're out to bag a better job in Electronics, a Government FCC License can give you a shot at job opportunities with *real* futures.

According to the U.S. Office of Education Bulletin (4th Edition): "The demand for people with technical skills is growing twice as fast as for any other group, while jobs for the untrained are rapidly disappearing." There are new openings every year in many different industries for electronics specialists. And you don't need a college education to qualify.

But you *do* need knowledge . . . knowledge of electronics fundamentals. And one of the nationally accepted methods of measuring this knowledge . . . is the licensing program of the FCC (Federal Communications Commission).

**Importance of an FCC License and CIE's Warranty of Success**

If you want to work in commercial broadcasting . . . television or AM or FM broadcasting . . . as a broadcast engineer, federal law requires you to have a First Class Radiotelephone License. Or if you plan to operate or to maintain mobile two-way communications systems, microwave relay stations or radar and signaling devices, a Second Class FCC License is required.

But even if you aren't planning a career which involves radio transmission of any kind, an FCC "ticket" is valuable to have as Government certification of certain technical skills. It's a job credential recognized by some employers as evidence that you really know your stuff.

So why doesn't everyone who wants a good job in Electronics get an FCC License?

It's not that simple. To get an FCC License, you must pass a Government licensing exam.

A good way to prepare for your FCC License exam is to take one of the CIE career courses which include FCC License preparation. We are confident you can successfully earn your license, if you're willing to put forth an effort, because the vast majority of CIE students have. In fact, based on continuing surveys, close to 9 out of 10 CIE graduates have passed their FCC exams!

That's why we can offer this time-tested Warranty of Success: when you successfully complete any CIE career course which includes FCC License preparation, you will be able to pass the Government FCC Examination for the License for which the course prepared you or you will be entitled to a full refund of an amount equal to the cash price of tuition for CIE's Course No. 3, "First Class FCC License," in effect at the time you enrolled. This warranty is good from the date you enroll until the last date allowed for completion of your course.

**CIE HAS CAREER COURSES THAT INCLUDE "HANDS ON" TRAINING**

**ELECTRONICS TECHNOLOGY with LABORATORY** Courses . . . takes beginner from fundamentals to skills required of technician or engineering assistant. Includes Experimental Electronics Laboratory for "hands on" training.

**COLOR TV MAINTENANCE and REPAIR** . . . several CIE courses combine electronics theory with the actual construction, testing and troubleshooting a big screen, stolid state color TV.

**With CIE you learn at home**

With CIE, you learn in your spare time at home . . . or wherever else is convenient. No classroom time, ever. No one to make you go too fast . . . or too slow. With CIE's Auto-Programmed® Lessons you'll pick up facts, figures, and electronics theories you may have considered "complicated" . . . even if you've had trouble studying before.

**You can have attractive job opportunities**

There have already been many exciting developments and breakthroughs in Electronics and some people might assume there will be no new frontiers . . . no new worlds to conquer. Not so.

Electronics is still growing. In nearly every one of the new and exciting fields of the Seventies you find electronics skills and knowledge in demand. Computers and data processing. Air traffic control. Medical technology. Pollution control. Broadcasting and communications. Once you have the solid technical background you need, you can practically choose the career field you want . . . work for a big corporation, a small company or even go into business for yourself.

Yes, Electronics can be the door to a whole new world of career opportunities for you. And CIE training can be your key.

**Send for FREE school catalog**

Discover the opportunities open to people with electronics training. Learn how CIE career courses can help you build new skills and knowledge and prepare you for a meaningful, rewarding career. We have courses for the beginner, for the hobbyist, for the electronics technician, and for the electronics engineer. Whether you are just starting out in Electronics or are a college-trained engineer in need of updating (or anywhere in between), CIE has a course designed for *you*.

Send today for our FREE school catalog and complete package of career information. For your convenience, we will try to have a representative call to assist in course selection. Mail reply card or coupon to CIE . . . or write: Cleveland Institute of Electronics, Inc., 1776 East 17th Street, Cleveland, Ohio 44114. Do it TODAY.

**APPROVED UNDER G. I. BILL**

All CIE *career* courses are approved for educational benefits under the G.I. Bill. If you are a Veteran or in service now, check box for G.I. Bill information.

**CIE Cleveland Institute of Electronics, Inc.**

1776 East 17th Street, Cleveland, Ohio 44114  
Accredited Member National Home Study Council

**Cleveland Institute of Electronics, Inc.**  
1776 East 17th Street, Cleveland, Ohio 44114

Please send me your FREE school catalog and career information package today.

I am especially interested in:

- |  |  |
|--|--|
| <input type="checkbox"/> Electronics Technician  | <input type="checkbox"/> Industrial Electronics  |
| <input type="checkbox"/> FCC License Preparation | <input type="checkbox"/> Electronics Engineering |
| <input type="checkbox"/> Color TV Maintenance    | <input type="checkbox"/> Other _____             |
| <input type="checkbox"/> Mobile Communications   |  |

Print Name \_\_\_\_\_

Address \_\_\_\_\_ Apt. \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_ Age \_\_\_\_\_

Check box for G.I. Bill information.

Veteran       On Active Duty      PE-87



**EDI**

**THE SHOPPING CENTER  
FOR ELECTRONICS**

\*HOBBYISTS ... EXPERIMENTERS ...  
SERVICE TECHNICIANS ... ENGINEERS\*

YOUR SATISFACTION  
IS OUR TARGET!

Top Name Brands ... Low Prices



AMPLE STOCKS - Including those  
hard-to-find Parts whether you  
want a 15v capacitor, or a \$50  
FET-VOM — you can get it at EDI!

**Transistors, ICs, Modules,  
Speakers, Stereo, HI-FI,  
Photo cells and thousands  
of other Electronic Parts ...**

**SEND FOR YOUR  
FREE CATALOG TODAY!**  
(updated 5 times a year)

**ELECTRONIC DISTRIBUTORS, INC.**  
DEPT. PE-1 4900 Elston  
Chicago, Ill. 60630

NAME \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_


CIRCLE NO. 23 ON FREE INFORMATION CARD

**ISO-TIP®**

# QUICK CHARGE


Recharges in 1/3rd the time  
of any other cordless iron.

Complete line of accessories available:



No. 7566 Micro Soldering Tip	No. 7577 Chisel Tip
No. 7535 Regular Tip	No. 7574 Concave Tip
No. 7546 Heavy Duty Tip	No. 7569 "V" Tip
No. 7596 Knife Tip	No. 7573 Tinning Tip
No. 7545 Fine Tip	No. 7572 Blunt Tip
No. 7556 Tuner Extension Tip	

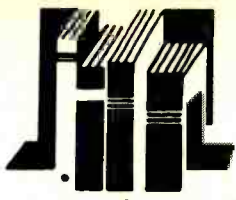**WAHL CLIPPER CORPORATION**  
ORIGINATORS OF PRACTICAL CORDLESS SOLDERING  
Sterling, Illinois 61081 (815) 625-6525  
"Manufacturing Excellence Since 1919"  
CIRCLE NO. 62 ON FREE INFORMATION CARD



## Electronics Library

**RADIO: THEORY AND SERVICING**  
*by Clyde Herrick*

This book covers radio theory and practical servicing information. Each of the thirteen chapters, focusing on broadcast AM, FM and FM stereo, multiband, amateur, two-way, navigation, telephone, space, and special-purpose radios, includes a troubleshooting section and questions to check progress. Component values and circuit details are provided to give the reader a broad view of each type of equipment.  
*Published by Reston Publishing Co., Box 547, Reston, Va. 22090. 310 pages. Hard cover. \$12.95.*

**BASIC TELEVISION  
(REVISED SECOND EDITION)**  
*by Alexander Schure*


This six-volume set introduces the reader to each step in signal processing between the television studio and the home receiver. Both the electronic and physical aspects of the devices used in TV systems are explored. Emphasis is placed on recent developments in color and solid-state circuitry. The volume topics are the transmitter, organization of the TV receiver, TV receiver circuit explanations (Volumes 3-5), and color Television. The series is thoroughly illustrated and will give those with a basic knowledge of electronics an understanding of television systems.  
*Published by Hayden Book Company, 50 Essex St., Rochelle Park, NJ 07662. \$30.50 for the six-volume soft-cover set, \$24.95 for the combined single hard-cover book.*

**SYLVANIA ECG SEMICONDUCTOR GUIDE**  
GTE Sylvania's ECG<sup>®</sup> line of replacement semiconductors is presented in this catalog and cross-reference. The book provides replacement considerations, specifications, biasing, and outline drawings of the ECG products as well as a replacement directory which cross-references almost 106,000 JEDEC types and manufacturers' part numbers to the replacement devices.  
*Published by GTE Sylvania Inc., Electronic Components Group, 100 First Ave., Waltham, MA 02154. 214 pages. \$2.95 soft cover.*

**HOW TO USE INTEGRATED CIRCUIT LOGIC ELEMENTS**  
*by Jack Streater*

For the engineer or technician who has not

# BETTER THAN A THIRD HAND!

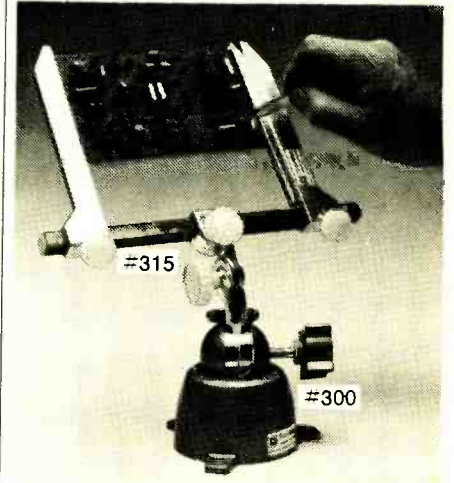

**PANAVISE TILTS, TURNS, AND  
ROTATES TO ANY POSITION.  
IT HOLDS YOUR P.C. BOARD  
EXACTLY WHERE YOU WANT IT.**

Quite possibly the finest new tool you will buy this year. PanaVise is built to exacting professional standards. We guarantee it!

Illustrated is P.C. Board Holder #315 in the #300 Base. This combination has exclusive multiple positioning ability. Boards are gently but firmly locked in place with one arm spring loaded to facilitate quick board changes.

Three other bases and a wide variety of heads are available. All interchangeable! Buy a basic unit, then add on to create your system.

**FREE Write for the latest PanaVise catalog, prices, and dealer listing.**  
*Available through your dealer.*

**PANAVISE®** Dept. 15E  
A Division of Colbert Industries  
10107 Adella Ave., South Gate, CA 90280  
CIRCLE NO. 43 ON FREE INFORMATION CARD

become acquainted with IC logic circuits, this book should provide a practical introduction to forming logic systems from elemental gates. The first two chapters cover number systems, and Boolean algebra with its applications to simple switching circuits. The next two chapters discuss gates and combinational circuits, and bistable elements. Then the logic families (RTL, DTL, TTL, ECL, CTL and MOS) are discussed and compared. Other chapters include breadboarding, testing, and a series of experiments. A glossary of digital terms forms an appendix.  
*Published by Howard W. Sams & Co., 4300 W. 62nd Street, Indianapolis, Ind. 46206.*

# ELECTRONICS MARKET PLACE

**NON-DISPLAY CLASSIFIED: COMMERCIAL RATE:** For firms or individuals offering commercial products or services, \$1.80 per word (including name and address). Minimum order \$27.00. Payment must accompany copy except when ads are placed by accredited advertising agencies. Frequency discount: 5% for 6 months; 10% for 12 months paid in advance. **READER RATE:** For individuals with a personal item to buy or sell, \$1.10 per word (including name and address). No minimum! Payment must accompany copy. **DISPLAY CLASSIFIED:** 1" by 1 column (2-1/4" wide), \$215.00. 2" by 1 column, \$430.00. 3" by 1 column, \$645.00. Advertiser to supply cuts. For frequency rates, please inquire.

**GENERAL INFORMATION:** First word in all ads set in bold caps at no extra charge. All copy subject to publisher's approval. All advertisers using Post Office Boxes in their addresses **MUST** supply publisher with permanent address and telephone number before ad can be run. Advertisements will not be published which advertise or promote the use of devices for the surreptitious interception of communications. Closing Date: 1st of the 2nd month preceding cover date (for example, March issue closes January 1st. Send order and remittance to **POPULAR ELECTRONICS**, One Park Avenue, New York, New York 10016, Attention: Hal Cymes.

## FOR SALE

**FREE!** Bargain Catalog—I.C.'s, LED's, readouts, fiber optics, calculators parts & kits, semiconductor parts, Poly Paks, Box 942PE, Lynnfield, Mass. 01940.

**GOVERNMENT Surplus Receivers, Transmitters, Sniperscopes, Radios, Parts, Picture Catalog** 25 cents. Meshna, Nahant, Mass. 01908.

**LOWEST Prices Electronic Parts.** Confidential Catalog Free, KNAPP, 3174 8th Ave. S.W., Largo, Fla. 33540.

**ELECTRONIC PARTS, semiconductors, kits, FREE FLYER.** Large catalog \$1.00 deposit. BIGELOW ELECTRONICS, Bluffton, Ohio 45817.

**RADIO—T.V. Tubes—36 cents each.** Send for free catalog. Cornell, 4213 University, San Diego, Calif. 92105.

**AMATEUR SCIENTISTS, Electronics Experimenters, Science Fair Students** Construction plans—Complete, including drawings, schematics, parts list with prices and sources. Robot Man — Psychedelic shows — Lasers — Emotion/Lie Detector — Touch Tone Dial — Quadraphonic Adapter — Transistorized Ignition — Burglar Alarm — Sound Meter... over 60 items. Send 50 cents coin (no stamps) for complete catalog. Technical Writers Group, Box 5994, University Station, Raleigh, N.C. 27607.

**METERS—Surplus, new used, panel or portable.** Send for list. Hanchett, Box 5577, Riverside, CA 92507.

**MECHANICAL, ELECTRONIC devices catalog 10 cents.** Greatest Values — Lowest Prices. Fertik's, 5249 "D", Philadelphia, Pa. 19120.

**SOUND SYNTHESIZER KITS—Surf \$12.95. Wind \$12.95.** Wind Chimes \$17.95. Electronic Songbird \$6.95. Musical Accessories, many more. Catalog free. PAIA Electronics, Box J14359, Oklahoma City, OK 73114.

**BUGGED???** New locator finds them fast. Write, Clifton, 11500-L N.W. 7th Avenue, Miami, Florida 33168.

### DISCOUNT PRICES

**B&K, SENCORE, LEADER, RCA EICO, FLUKE and HICKOK**

Test Equipment  
ICC/Servicecenter, RCA and Raytheon Tubes  
Complete line of electronic supplies  
Free Catalog

**FORDHAM RADIO SUPPLY CO., INC.**

558 Morris Ave. • Bronx, N.Y. 10451

**FREE CATALOG, Parts, circuit boards for POPULAR ELECTRONICS projects.** PAIA Electronics, Box C14359, Oklahoma City, OK 73114.

**YOU WILL SAVE BIG MONEY!** Surplus, Clearouts, Bankruptcy, Inventory, Deals. Catalog \$1 (redeemable). ETCOA Electronics, Box 741, Montreal, H3C 2V2, U.S. Inquiries.

**TELEPHONE "BUGGED"?** Countermeasures Brochure \$1.00, Negeye, Drawer 547, Pennsboro, W. VA 26415.

**HEAR POLICE/FIRE Dispatchers!** Catalog shows exclusive directories of "confidential" channels, receivers. Send 10 cent stamp. Communications, Box 56-PE, Commack, N.Y. 11725.

**CONVERT any television to sensitive, big-screen oscilloscope.** Only minor changes required. No electronic experience necessary. Illustrated plans. \$2.00. Sanders, Dept. A-33, Box 92102, Houston, Texas 77010.

**CD IGNITIONS, VHF/UHF monitors, crystals, CB radios.** Southland, Box 3591-B, Baytown, Texas 77520.

**ALPHA/THETA BRAINWAVE biofeedback instruments.** Analog instruments from \$125; digital processing systems from \$225. BioScan, Box 14168-E, Houston, Texas 77021.

**SURPRISE! Build inexpensively, the most Unusual Test Instruments, Futuristic Gadgets using Numerical Readouts!** Catalogue Free! GBS, Box 100A, Green Bank, West Virginia 24944.

**LEARN DESIGN TECHNIQUES.** Electronics Design Newsletter. Digital, linear construction projects, design theory and procedures. Annual subscription \$6.00, sample copy \$1.00. Valley West, Box 2119-B, Sunnyvale, California 94087.

**TELEPHONES UNLIMITED.** equipment, supplies. Catalog 50 cents. Box 1654E, Costa Mesa, Calif. 92626.

**DIGITAL ELECTRONICS!** Highly effective course brings immediate results. \$10.00. Satisfaction or \$11.00 refunded! Plans, Projects, Free Literature. DYNASIGN, Box 60A7, Wayland, Mass. 01778.

**UNSCRAMBLERS:** Fits any scanner or monitor, easily adjusts to all scrambled frequencies. Only 4' square \$29.95, fully guaranteed. Dealer inquiries welcomed. PDQ Electronics, Box 841, North Little Rock, Arkansas 72115.

**RECONDITIONED Test Equipment.** \$0.50 for catalog. Walter, 2697 Nickel, San Pablo, CA 94806.

<p><b>INTEL 8080 CPU</b> \$139.00 8080 8 BIT MICRO PROCESSING CHIP (with data book) \$35.00 2102-2 1024 BIT RAM \$3.95 5202A UV PROM \$19.00 MM5203 UV PROM \$19.00 1702A UV PROM \$19.95</p> <p><b>MINIATURE TRIM POTS</b> 5K, 10K, 25K, 50K, 100K, 200K 100, 500 \$.75 ea. 3/\$2.00</p> <p><b>MULTI-TURN TRIM POTS</b> Similar to Bourns 3010 style 3/16" x 5/8" x 1 1/4" 50, 100, 2000, 10,000 ohms \$1.50</p> <p><b>LIGHT ACTIVATED SCR'S</b> TO-18 200V 1A \$1.75</p> <p><b>PRINTED CIRCUIT BOARD</b> 4 1/2"x6 1/2" single sided epoxy board, 1/16" thick, unetched \$.50 ea. 5/\$2.20 Conductive Elastomer low Profile Calculator keyboard \$6.00</p> <p>2N5460 P FET \$4.45 TIS 73 N JET \$4.45 2N4891 UJT \$4.45 ER900 TRIGGER DIODES 4/\$1.00 2N6028 PROG. UJT \$6.65</p> <p><b>VERIPAX PC BOARD</b> This board is a 1 1/16" single sided paper epoxy board, 4 1/2"x6 1/2". DRILLED and ETCHED which will hold up to 21 single 14 pin IC's or 8, 16 or LSI DIP IC's with busses for power supply connector \$5.25</p> <p>RED/GREEN BIPOLAR LEO \$1.30 MT-2 PHOTO TRANS \$1.60 MV 5053 YELLOW GREEN \$1.60 OR ORANGE LED 35 ea. \$2.00 RED GAP DSL-3 LED \$1.40 14 PIN DIP SOCKETS \$5.40 16 PIN DIP SOCKETS \$5.40 MOLEX PINS 100/\$1.00 1000/\$8.00 8 PIN MINI-DIP SOCKETS \$3.32</p> <p>10 WATT ZENERS 3.9, 4.7 OR 18V \$1.75 EA. 1 WATT ZENERS 5.6 \$1.75 EA. 10, 12, 15, 18 OR 22V \$4.40 EA.</p> <p><b>Silicon Power Rectifiers</b></p> <table border="1"> <tr><th>PRV</th><th>1A</th><th>3A</th><th>12A</th><th>50A</th></tr> <tr><td>100</td><td>.06</td><td>.14</td><td>.30</td><td>.80</td></tr> <tr><td>200</td><td>.07</td><td>.20</td><td>.35</td><td>1.15</td></tr> <tr><td>400</td><td>.09</td><td>.25</td><td>.50</td><td>1.40</td></tr> <tr><td>600</td><td>.11</td><td>.30</td><td>.70</td><td>1.80</td></tr> <tr><td>800</td><td>.15</td><td>.35</td><td>.90</td><td>2.20</td></tr> <tr><td>1000</td><td>.20</td><td>.45</td><td>1.10</td><td>2.75</td></tr> </table> <p><b>REGULATED MODULAR POWER SUPPLIES</b></p> <p>+ 15VDC AT 100ma \$24.95 115VAC INPUT \$19.95 5VDC AT 1A, 115VAC INPUT \$19.95 12V 5A \$24.95</p> <p>IN 4148 (IN914) 14/\$1.00 1103 1024 bit RAM \$4.75 NEC 6003 2048 bit RAM \$9.50 1101 256 bit RAM \$1.75 8223 PROM \$4.75 7489 RAM \$2.45</p> <p>Terms: FOB Cambridge, Mass. Send Check or Money Order. Include Postage. Minimum Order \$5.00. C/D \$2.00.</p>	PRV	1A	3A	12A	50A	100	.06	.14	.30	.80	200	.07	.20	.35	1.15	400	.09	.25	.50	1.40	600	.11	.30	.70	1.80	800	.15	.35	.90	2.20	1000	.20	.45	1.10	2.75	<p><b>TRANSISTOR SPECIALS</b></p> <p>2N6517 NPN Si TO-92 \$4.10 2N5086 PNP Si TO-92 \$4.10 2N4989 PNP TO-66 \$6.00 2N404 PNP GE TO-5 \$5.10 2N3919 NPN Si TO-3 RF \$1.50 MPSA13 NPN Si TO-92 \$3.10 2N3767 NPN Si TO-66 \$5.70 2N2222 NPN Si TO-18 \$5.10 2N3055 NPN Si TO-3 \$5.80 2N3904 NPN Si TO-92 \$5.10 2N3906 PNP Si TO-92 \$5.10 2N3906 NPN Si TO-220 \$5.50 2N6109 PNP Si TO-220 \$5.55 2N3866 NPN Si TO-5 Si RF \$7.75 POWER MJ2252 NPN Si TO-66 \$9.90 2N3638 NPN Si TO-5 \$5.10 2N2218A NPN Si TO-5 \$4.10</p> <p><b>CAPACITORS</b></p> <p>35v at .47 UF TANT 5/\$1.00 35v at 6.8 UF TANT 3/\$1.00 20v at 150 UF TANT \$1.40 6V 30 UF TANT \$5.10 12V 200 UF ELECT \$1.25 200V 4.7 UF ELECT \$3.30</p> <p><b>ARRAY READOUT \$1.65</b> <b>MAN-1 READOUT \$1.75</b> <b>MAN-3 READOUT \$1.00</b> <b>MAN-4 READOUT \$1.30</b> <b>MAN-7 READOUT \$1.25</b> <b>DL747 \$4.50</b></p> <p>DO-33-A 3 DIG. LED \$1.75 4 WATT IR LASER DIODE \$7.95 CD 110 LINEAR 256 X1 BIT SELF SCANNING CHARGED COUPLED DEVICE, WITH DATA \$125.00</p> <p><b>SANKEN AUDIO POWER AMPS</b></p> <p>Si 1010 G 10 WATTS \$6.90 Si 1020 G 20 WATTS \$13.95 Si 1050 G 50 WATTS \$24.95</p> <p><b>LINEAR CIRCUITS</b></p> <p>LM 309K 5V 1A REGULATOR \$1.50 723 40 - 40V REGULATOR \$5.58 301748 -Hi Per Op Amp \$3.30 307 OP AMP \$2.28 CA 3047 - HI PERFORMANCE OP AMP \$9.95 CA 3089 FM IF SYSTEM \$3.25 LM 320 5, 12 or 15V NEGAT REG \$1.50 LM 320 - or - 15V REG \$1.75 741A or 741C OP AMP \$3.31 709C OPER AMP \$2.25 340T-5 8, 12, 15, 18, 24V POS. REG TO-220 \$1.75 101 OPER AMP, HI PERFORMANCE \$1.75 LM 308 Oper Amp., Low Power \$1.05 747 - DUAL 741 \$3.65 555 - DUAL TIMER \$1.30 537 - PRECISION OP AMP \$2.60 LM 3900 - QUAD OP AMP \$4.49 LM 324 - QUAD 741 \$1.70 560 - PHASE LOCK LOOP \$2.00 561 - PHASE LOCK LOOP \$2.00 565 - PHASE LOCK LOOP \$2.00 566 FUNCTION GEN \$2.00 567 - TONE DECODER \$2.00 703 - RF-IF AMP \$4.41 LM 370 - AGC SQUELCH AMP \$1.15 555 - 2 us - 2 HR. TIMER \$6.65 555 - QUAD TIMER \$3.50 FCD 810 OPTO-ISOLATOR \$1.35 1456 OPER AMP \$9.95 1458 DUAL OP AMP \$6.65 LM 380 - 2W AUDIO AMP \$1.29 LM 377 - 2W STEREO AUDIO AMP \$2.50 LM 381 - STEREO PREAMP \$1.69 LM 382 - DUAL AUDIO PREAMP \$1.69 LM 311 - HI PER. COMPARATOR \$9.95 LM 319 - Dual Hi Speed Comp \$1.15 LM 339 - QUAD COMPARATOR \$1.25 8038C IC VOLT CONT. OSC \$4.40</p> <p><b>TRIACS</b></p> <table border="1"> <tr><th>PRV</th><th>1A</th><th>10A</th><th>25A</th><th>1.5A</th><th>6A</th><th>35A</th></tr> <tr><td>100</td><td>.40</td><td>.70</td><td>1.30</td><td>.40</td><td>5.0</td><td>1.20</td></tr> <tr><td>200</td><td>.70</td><td>1.10</td><td>1.75</td><td>.60</td><td>7.0</td><td>1.60</td></tr> <tr><td>400</td><td>1.10</td><td>1.60</td><td>2.60</td><td>1.00</td><td>10.0</td><td>2.20</td></tr> <tr><td>600</td><td>1.70</td><td>2.30</td><td>3.60</td><td>1.50</td><td>15.0</td><td>3.00</td></tr> </table> <p><b>SCR'S</b></p> <table border="1"> <tr><th>PRV</th><th>1A</th><th>10A</th><th>25A</th><th>1.5A</th><th>6A</th><th>35A</th></tr> <tr><td>100</td><td>.40</td><td>.70</td><td>1.30</td><td>.40</td><td>5.0</td><td>1.20</td></tr> <tr><td>200</td><td>.70</td><td>1.10</td><td>1.75</td><td>.60</td><td>7.0</td><td>1.60</td></tr> <tr><td>400</td><td>1.10</td><td>1.60</td><td>2.60</td><td>1.00</td><td>10.0</td><td>2.20</td></tr> <tr><td>600</td><td>1.70</td><td>2.30</td><td>3.60</td><td>1.50</td><td>15.0</td><td>3.00</td></tr> </table> <p>SPOT MIN TOGGLE SWITCH MTA 106 \$1.50 SPOT MIN TOGGLE SWITCH MTA 206 \$2.25 GT7001 Calenda Alarm CLOCK CHIP \$6.75</p>	PRV	1A	10A	25A	1.5A	6A	35A	100	.40	.70	1.30	.40	5.0	1.20	200	.70	1.10	1.75	.60	7.0	1.60	400	1.10	1.60	2.60	1.00	10.0	2.20	600	1.70	2.30	3.60	1.50	15.0	3.00	PRV	1A	10A	25A	1.5A	6A	35A	100	.40	.70	1.30	.40	5.0	1.20	200	.70	1.10	1.75	.60	7.0	1.60	400	1.10	1.60	2.60	1.00	10.0	2.20	600	1.70	2.30	3.60	1.50	15.0	3.00
PRV	1A	3A	12A	50A																																																																																																						
100	.06	.14	.30	.80																																																																																																						
200	.07	.20	.35	1.15																																																																																																						
400	.09	.25	.50	1.40																																																																																																						
600	.11	.30	.70	1.80																																																																																																						
800	.15	.35	.90	2.20																																																																																																						
1000	.20	.45	1.10	2.75																																																																																																						
PRV	1A	10A	25A	1.5A	6A	35A																																																																																																				
100	.40	.70	1.30	.40	5.0	1.20																																																																																																				
200	.70	1.10	1.75	.60	7.0	1.60																																																																																																				
400	1.10	1.60	2.60	1.00	10.0	2.20																																																																																																				
600	1.70	2.30	3.60	1.50	15.0	3.00																																																																																																				
PRV	1A	10A	25A	1.5A	6A	35A																																																																																																				
100	.40	.70	1.30	.40	5.0	1.20																																																																																																				
200	.70	1.10	1.75	.60	7.0	1.60																																																																																																				
400	1.10	1.60	2.60	1.00	10.0	2.20																																																																																																				
600	1.70	2.30	3.60	1.50	15.0	3.00																																																																																																				

Send 20c for our catalog featuring Transistors and Rectifiers; 145 Hampshire St., Cambridge, Mass.



## SOLID STATE SALES

P.O. BOX 74A  
SOMERVILLE, MASS. 02143 TEL. (617) 547-4005

**WE SHIP OVER 95% OF OUR ORDERS THE DAY WE RECEIVE THEM**

# ACE OF THE MONTH SPECIALS



## DUAL POWER SUPPLY KIT

Dual adjustment  $\pm 10$  to  $\pm 16$  volts, regulated, 250 ma. Each supply, short circuit protected. Board size 3" X 6". Ideal for OP AMP and CMOS projects. This kit is complete, all parts are included.

Complete Kit \$24.95  
(includes instructions and schematics)  
Wired & Tested \$29.95



## ASCII COMPUTER KEYBOARDS

These keyboards were manufactured for use on Texas Instrument's line of Silent 700 series data terminals. They are fully encoded with TTL large scale integrated circuits (T.I. TMS-5000 in 28 pin socket). Additional IC's provide a parallel 7 bit, without parity, code plus a strobe signal indicating "valid" data and six other independent outputs for those special keys which are not encoded. The keys are reed type with a format similar to typewriter. Internal circuitry provides for two key rollover and de-bounce. Output is on standard 10 pin double readout connector for data and power input. And 8 pin double readout connector for six special switch functions.

KB-7 - Clare/Pendar 720731-1


T.I. Part number 959326-1 as used on T.I. Silent 700 data Terminals. This is a 64 key full ASCII encoded keyboard.

New \$49.95

Keyboard supplied with wiring diagrams, code tables, and other useful documentation.

## SEMI CONDUCTORS

SN 7410 N	.25	2N 525	.49
SN 741 74N	.49	2N 718	.29
SN 74145 N	1.25	2N 730	.49
SN 74154 N	.98	2N 1307	.49
SN 72 709 N	.49	2N 3054	.75
LM 30 1 AH	.49	2N 3640	.19
IN 746 A	.25	2N 5447	.19
IN 753 A	.25	2N 5449	.19
IN 4751	.35	3N 83	1.49

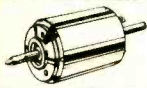

## MOTOR

CAPSTAN DRIVE MOTOR. Super efficient 12 volt DC motor runs on as low as 1/2 volt at 20 ma. Full rating is 12 Volts 250 ma, 2.8 inch of torque at 5000 RPM. Size 1-1/8" DIA X 2" long with 0.118 inch shaft. Also makes excellent tachometer generator at approximately 2 Volts per 1000 RPM. New Guaranteed \$1.95 each 10 for \$12.50

## MEMORY CHIP

SN74S201N 256 BIT RAM with 3 state output  
Plug in replacement for SN74200 & SN74S200.  
\$3.95 ea. 10 for \$25.00  
NEW GUARANTEED

TERMS: We pay postage, unless otherwise specified. Orders over \$50.00 subtract 10% include check or money order, no COD. Texas residents add 5% sales tax.



## ELECTRONIC PARTS

3303 Mangum Road  
Houston, Texas 77018

CIRCLE NO. 3 ON FREE INFORMATION CARD

**SURPRISE! SURPRISE!** Digital Piano Tuning Device tunes musical instruments Accurately! Perfectly! Inexpensively! Construction-Instruction-Plans Complete \$12.95 Airmailed Postpaid! Moonlighting quickly repays \$40 electronics investment! GBS, Box 100P, Green Bank, West Virginia 24944.

PYROTECHNICAL chemicals, casings, fuse, tools, literature, supplies. Catalog-\$1.00, with samples — \$2.00. Westech, Logan, Utah 84321.

ELECTRONIC parts, low prices, free flyer: DARTEK ELECTRONICS, Box 2460, Dartmouth, Nova Scotia, Canada, U.S. Inquiries.

FREE giant bargain electronic catalog listing thousands of components, tubes, transistors, IC's, kits, test equipment. EDLIE'S, 2700-PH Hempstead Tpke., Levittown, N.Y. 11756.

CONSTRUCTION PROJECTS: Laser, \$2.00. TV Camera, \$3.95. Catalog, Technologic, Box 5262, Orchard Lake, Michigan 48033.

ALPHA BRAINWAVE MONITOR—New from EICO Model BW300 Kit, \$34.95; Wired, \$59.95 Postpaid. Send check or money order. M&K Electronic Corp., 135-33 Northern Blvd., Flushing, N.Y. 11354.

## BUILD YOUR OWN TV CAMERA!

— Ideal for home & business —



THE ECONOMIC ANSWER TO HOME MONITORING OF NURSERIES, ENTRANCES, DRIVEWAYS, BUSINESS AND INDUSTRIAL SURVEILLANCE, TV, A NAUTOUR TV PLUS HUNDREDS OF OTHER APPLICATIONS. MODEL XT-1A, SERIES D - KIT FORM \$185; ASSEMBLED \$275. SOLID STATE, WORKS ON ANY TV SET. OPTIONAL SOUND KIT \$28.95. PHONE or WRITE for catalog. Dial 402-987-3771

1301 BROADWAY ATV Research DAKOTA CITY, NE 68701

ALTAIR OWNERS—we have accessory boards, components, memories, etc. Boards, IC Kits for most popular minis. Mini Micro Mart, 1618 James, Syracuse, NY 13203.

## AUDIO PROGRAM CONTROL CENTER



\$14.95 PPD. USA

10 inputs, 4 outputs. Switch TV, Short-Wave, Ham, FM to Stereo Amplifier & Recorder. Listen & Record.

POWERCOM CORPORATION

Box 454 Dept 4 Troy, N. Y. USA 12181

POLICE. Fire monitors, scanners, crystals discount priced. New crystal-less scanners. Box 19224, Denver, CO 80219.

TELETYPE EQUIPMENT for sale for beginners and experienced computer enthusiast. Teletype machines, parts, supplies. Catalogue \$1.00 to: ATLANTIC SALES, 3730 Nautilus Ave., Brooklyn, NY 11224. Tel: (212) 372-0349.

## wanted Citizens Band

### DEALER-DISTRIBUTORS

Send this ad with Letterhead to:

**PAL ELECTRONICS CO.**

2962 W. WELDON - PHOENIX, ARIZ. 85017

FOR A New Electronic Experience, learn to control your brainwaves. Aquarius Electronics, Box 96ZE, Albion, CA 95410.

TEST EQUIPMENT—DISCOUNT PRICES: B&K, Sencore, Leader, EICO, Lectrotech, M&K Electronic Corp., 135-33 Northern Blvd., Flushing, N. Y. 11354.

## GODBOUNT

BOX 2355 OAKLAND AIRPORT, CA 94614

THE "SECRET MICROCOMPUTER COMPANY" IS NATIONAL SEMICONDUCTOR; THEY'VE HIT IN A BIG WAY WITH PACE, A REAL 16 BIT PARALLEL MICROPROCESSOR. 40 PIN DIP PROVIDES 45 CLASSES OF INSTRUCTIONS WITH UP TO 337 INSTRUCTIONS. . . . . \$125

## Get your MITs on a Godbout memory

4K X 8 RAM KIT—ALTAIR PLUG-IN COMPATIBLE. TRI-STATE BUFFERED OUT; ONBOARD REGULATION; INPUTS ARE 1 PPTTL LOAD. MEMORY PROTECT. 4/10<sup>4</sup> PER BIT!

## VECTOR WIRE PENCIL \$9.50

TOOL WRAPS #36 WIRE AROUND LEADS AND TERMINALS; "SOLDER-THRU" INSULATION PERMITS SOLDER BOND. FAST FOR VECTORBOARD WORK!! (+1 lb shp)

SEND STAMP FOR OUR NEW FLYER! TERMS: CAL RES ADD TAX. NO COD. CALL (415) 357-7007 FOR MASTERCHARGE\* OR BANKAMERICARD\* ORDERS

## WAREHOUSE DISCOUNTS ON NATIONALLY ADVERTISED

- C.B. RADIOS
- MONITOR SCANNERS FIRE POLICE IN FACTORY SEALED CARTONS

BUSINESS - RECREATION - PERSONAL SATISFACTION GUARANTEED

WRITE FOR QUOTE  
ELECTRONICS WAREHOUSE, INC.  
6234 LITTLE RIVER TURNPIKE (DEPT. 5)  
ALEXANDRIA, VA. 22312  
OR PHONE: (703) 256-1300

## IMSAI\* AND ALTAIR

OWNERS

INTERCHANGEABLE CPU, MEMORY, and I/O BOARDS

	KIT	ASSEMBLED
8080 CPU BOARD	\$181.00	\$299.00
1K 8111 RAM ON 4K BOARD	165.00	199.00
1K 8111 RAM ON 4K BOARD	60.00	99.00
2K PROM BOARD (with Phone)	175.00	199.00
I/O MODULE (RS 232C, TTY, TTL)	119.00	138.00
COMBINATION WESTERN INTERRUPT & R.T. CLOCK	119.00	138.00

MULTIPROCESSOR/SHARED MEMORY FACILITY

ALLOWS UP TO 3 IMSAI\* 8080s OR ALTAIR 8800s TO SHARE THE SAME MEMORY. \$295.00 KIT and \$335 ASSEMBLED

PERIPHERALS AND CONTROLLERS

FOR IMSAI\* 8080 AND ALTAIR 8800 COMPUTERS

	KIT	ASSEMBLED
32 COLUMN ALPHAMERIC PRINTER!		\$159.00
32 COLUMN PRINTER INTERFACE BD	\$119.00	138.00
FLOPPY DISK DRIVE IN CABINET		109.00
FLOPPY DISK CONTROLLER (11 4 DRIVES)	264.00	439.00
DIABLO II TYPE PRINTER CAB. & P.S.		2695.00
TTY/TELE CONTROLLER BOARD	115.00	142.00
800 LPM LINE PRINTER, CAB. & P.S.		1995.00
LINE PRINTER CONTROLLER	260.00	340.00
80 MEGABYTE DISK CONTROLLER, CABINET AND DEMO.	27,800.00	29,500.00

IMSAI\* 8080 COMPUTER

ALL BOARDS AND SOFTWARE INTERCHANGEABLE BETWEEN IMSAI 8080 AND ALTAIR 8800

BASIC COMPUTER INCLUDES: CPU, I/O, RAM, I/O BOARD, FRONT PANEL CONTROL BOARD, LIGHTS AND SWITCHES, POWER SUPPLY, EXPANDER BOARD & CASE. \$439.00 KIT \$671.00 ASSEMBLED

CHIPS: (FACTORY TESTED, F.R.S.T. RUN, PRIME)

1/02 A	\$17.00	8080	\$99.00
8111 or 2102/1500 ISI	4.00	8224	15.00
8880 (224/8228 SET)	125.00	8228	15.00

## 7400 SERIES TTL PINOUT HANDBOOK

COVERS ENTIRE 7400/7400 SERIES D.I.P. IC'S PIN CONNECTIONS - FUNCTIONAL SPECS

CROSS REFERENCE \$3.95

\*Registered Trademark.

IMS ASSOCIATES INC.  
1922 REPUBLIC AVE. SAN LEANDRO, CALIF. 94577

TERMS: CHECK, M.O., BANKAMERICA, MASTER CHARGE, 25% DEPOSIT ON C.O.D.  
ADD BY POSTAGE AND HANDLING  
CALIF. RESIDENTS ADD 6% SALES TAX  
PRICES SUBJECT TO CHANGE WITHOUT NOTICE

CIRCLE NO. 25 ON FREE INFORMATION CARD

## ALTAIR 8800 USERS!

- DID YOU KNOW . . .
- that our 4K memory board can remember things after you pull the plug!
  - that our I/O module will interface two TV typewriters, with keyboards, a teletype and modem, all at the same time!
  - that all of our modules are 100% compatible with the 8800 computer!
  - that our Software is FREE! or close to it
  - that we deliver on time!!

## INPUT/OUTPUT

This one card will meet all common I/O requirements. Interface your Altair with the TV Typewriter and at the same time a teletype or modem, plus other devices.

- Two parallel input and output ports
- One serial I/O for any teletype and/or EIA RS-232C device, uses a UART
- Two special ports for any imaginable control needs
- Serial data rate from 35 to 9600 baud
- Full I/O handshaking provided

ORDER KIT NO. 3P+S . . . . \$125.

## MEMORIES

Our high speed, low power static read write memory (RAM) allows the 8800 to run at top speed. All our memory IC's are 100% tested to Military STD-883! Each card accepts up to 4096 8 bit words.

ORDER KIT NO. 4KRA

4KRA-4, w/4096 8-bit words . . . \$215.  
4KRA-2, w/2048 8-bit words . . . \$135.

Our PROM card accepts up to eight 1702A or 5203 erasable programmable read only memories. All necessary 8800 interface logic is provided but NO PROM's.

ORDER KIT NO. 2KRO . . . . \$ 50.

Write for assembled unit pricing. Send for our FREE flyer or order now from:

PROCESSOR TECHNOLOGY CO.  
2465P Fourth St., Berkeley, Calif. 94710  
(415) 549-857

Terms: All items postpaid if full payment comes with order. Calif. residents add sales tax. COD orders must include 25% deposit. Discounts: 5% orders over \$375; 10% orders over \$600.

CIRCLE NO. 47 ON FREE INFORMATION CARD  
POPULAR ELECTRONICS

# Altaj Electronic Bargains

PRICES SLASHED! WE WANT YOUR BUSINESS. SATISFACTION GUARANTEED ON EVERY ITEM

## COMPUTER BOARD BONANZA

We bought over 4 tons of assorted boards. Contains TTL, diodes, transistors, etc. 5 board asmt. with 150 to 250 IC's - \$3.95.

C - MOS			
CD4000 - .24	CD4015 - 1.19	CD4026 - 1.49	CD4044 - .59
CD4001 - .24	CD4016 - .59	CD4027 - .59	CD4047 - .59
CD4002 - .24	CD4017 - 1.29	CD4028 - .99	CD4049 - .59
CD4006 - 1.49	CD4018 - 1.49	CD4029 - 1.39	CD4050 - .59
CD4007 - .24	CD4019 - .59	CD4030 - .49	CD4056 - .99
CD4008 - 1.19	CD4020 - 1.59	CD4032 - .24	CD4077 - .39
CD4009 - .59	CD4021 - 1.49	CD4033 - 1.49	74C02 - .29
CD4011 - .24	CD4022 - 1.19	CD4035 - 1.39	74C04 - .29
CD4012 - .24	CD4023 - .24	CD4040 - 1.59	74C107 - 1.29
CD4013 - .59	CD4024 - .99	CD4041 - .89	
CD4014 - 1.49	CD4025 - .24	CD4042 - .79	



**LM300K**  
TO-3 Case. 1 AMP 5 VDC  
Voltage Regulator. Brand New  
By National \$1.19



**3 DIGIT LED READOUT ARRAY**  
Like Litronix DL-33 3 MAN-3 style readouts in one package. Factory new units. Designed for calculators. Special - \$1.39 (3 Digits)



**LITRONIX DL707 READOUTS**  
30 IN. CHAR. Common Anode.  
SPECIAL - \$1.19

**TRANSFORMER SPECIAL #1**  
Miniature size. Primary 115 VAC Secondary 11 VAC NO LOAD. 8 VAC with 400 MA Load. Perfect for clocks or calculators or small power supply.  
99c ea or 6 For \$5

## CALCULATOR CHIP BONANZA PRICES SLASHED!

The newest and easiest to use chips available today. Made by famous US mfg. All are 28 pin DIP. Features: direct LED segment drive, low power consumption, internal keyboard debounce, internal clock oscillator, single supply voltage, internal keyboard encoding, and floating decimal point. Does not require many external components as do older types like CT5001, 5002, 5005, etc. We offer the most sophisticated functions for the lowest price anywhere.  
Chip #1 - 8 Digit, Constant, Six Function (+, -, x, %, √) - \$2.49

## DIGITAL ALARM CLOCK IC

The newest and easiest to use alarm chip on the market today. Features:

1. Single supply voltage.
2. LED Intensity control
3. Simple time set.
4. 4 or 6 Digit LED Display
5. AM-PM indication
6. 24 Hr. Alarm.
7. 10 minute snooze.
8. Outperforms MM5316

Order #70250 - \$4.99

## MM5314 NATIONAL CLOCK CHIP

The most popular clock chip around. We made a huge special purchase of factory fresh, prime units. Lowest price in USA. 24 Pin DIP. 4 or 6 Digits. With Specs. \$3.95

## FLOURESCENT READOUT TUBES

7 Segments. Blue-Green In color. Mfg. by ISE, #D68F. The most popular display used in many imported clocks and calculators. Perfect for use with MM5316 clock chips.  
SUPER SPECIAL 69c ea.  
12 For \$5.95



## DIGITAL WRIST WATCH CRYSTAL

Brand new, mfg. by CTS-KNIGHT. 32.768 KHZ. Standard, most popular type. Special \$1.95



## 6 DIGIT LED READOUTS

Brand new arrays by T. I. Common cathode, properly multiplexed. Six digits plus a negative sign. Perfect for calculators, mini-clocks, stop watches, etc. SUPER SPECIAL \$1.29 ea 3 for \$3

Free 28 Pin Socket with purchase of any clock or calculator chip.  
\$1 VALUE-FREE BONUS

## MOTOROLA MJE 3055

Plastic version of 2N3055. NPN Silicon. 90 Watts 15 Amps. SPECIAL - 69c

## 8008 MICROPROCESSOR

Computer on a chip. 8 Bit Parallel CPU. Can address 16k x 8 bits of memory. With specs. Factory tested units. \$24.95

## DOUBLE DIGIT JUMBO READOUTS

New. Litronix 727. Dual Perfect for giant clocks, etc. \$3.95 each. (2 DIGITS)

## COLOR ORGAN CONTROL MODULE

Completely self-contained. Has SCR circuitry. AC line cord, etc. From a close out by a mfg. of color organs. New, unused. \$1.49

**MOTOROLA SCR**  
2N4443 8 Amp 400PN, Plastic Power Case. 69c

**GE POWER DARLINGTON**  
NPN, Plastic Power Tab Case. VCE0-30 HFE-30,000 TYP. Brand new units, but leads are slightly trimmed for P.C.B.  
#D40C1 - SPECIAL 4 For \$1

## TRANSISTOR BAKER'S DOZEN SALE!

2 million pieces bought for this sale. New, house numbered units by T. I. All prime first quality at a give-away price.

NPN 2N3904 - 13 For \$1

PNP 2N3906 - 13 For \$1

## 2102-1K RAM's for above - \$4.95 or 8 For \$30

## JUMBO LED READOUT

Twice the size of regular readouts. .65 inches. Like Litronix DL747. Outperforms and easier to read than SLA-3, only 20 MA per segment. Our best readout for digital clocks. \$2.95 ea (6 FOR \$15) Common Anode

## 1024 BIT SIGNETICS P-ROM

82S129I-256X4 bipolar, field programmable ROM. Fully TTL compatible. 50 ns. max address access time. Much faster than MOS type units. Perfect for code conversions, microprogrammers, hand-wired algorithms, controllers, etc. With specs. Regular \$35 ea. SPECIAL - 3.95  
BEST MEMORY BUY IN USA!

## IN4004 RECTIFIERS

1 AMP 400PIV - SPECIAL 15/\$1

## 7805 STYLE REGULATORS

TO-220 Plastic Case 5VDC Regulator. Brand New by National - 99c

## FACTORY NEW LED'S

Jumbo Red-Like MV5024-8/\$1  
Jumbo Green-Like MV5222-5/\$1  
Jumbo Yellow-5/\$1  
Mini Red-Like MV50-10/\$1

## LINEAR IC SPECIALS

555V-75c 567V-\$1.95 723CH-59c 741CV-25c  
LM324 by National - Quad 741C in one DIP - \$1.19

## 12VDC REED RELAY

Coil is 500 OHM. SPST-No. \$1.49 Sub-Mini.

## FILTER CAPS

1000 MFD 16VDC upright style. 4 FOR \$1

## PRIME TTL DIP IC'S

7400-16c	7448-89c	74151-75c
7402-16c	7453-16c	74153-89c
7404-16c	7473-37c	74154-95c
7406-24c	7474-37c	74157-99c
7408-16c	7475-65c	74161-99c
7410-16c	7476-39c	74163-1.19
7413-49c	7483-85c	74164-.89
7420-16c	7490-69c	74165-1.49
7427-24c	7492-75c	74174-1.29
7430-16c	7493-75c	74175-1.39
7437-39c	7495-75c	74181-2.75
7438-35c	7496-75c	74192-1.25
7440-16c	74121-38c	74193-1.25
7442-69c	74123-75c	74195-79c
7447-89c	74150-70c	74197-79c

## 8008 FUNCTION GENERATOR

Brand new Voltage controlled oscillator. Has sine, square wave, and triangular outputs \$4.95 each.

## IN148 DIODES

Brand New Units. Same as IN914. Full Leads.

25 For \$1

## MONSANTO COLORED READOUTS

.27 IN. Character. Common Anode

MAN 5 - GREEN - \$1.29

MAN 8 - YELLOW - \$1.29

## PHASE LOCKED LOOP

565A by Signetics. Extremely stable. High linearity, wide frequency range. TTL compatible. Perfect for tone decoders, FSK SCA receivers, frequency multiplication and division - 99c WITH SPECS

## LOOK

## MOS 4 DIGIT COUNTER

An ALTAJ exclusive. These are the latest state of the art, MOS chips. By a famous US mfg. Contains a complete 4 digit counter, including 4 decade counters, latches, multiplexing circuits, display decoders, etc. Features: 5 VDC operation, 25 MW power consumption, both 7 segment and BCD outputs. Perfect for making DVM's, frequency meters, tachometers, stopwatches, or any other device requiring 4 or more digits. Complete with specs. 28 PIN DIP. QTY Limited

SPECIAL - \$12.50  
BACK IN STOCK!

## LED DRIVER IC'S

75491 - Quad segment dr. - 29c  
75492 - Hex digit dr. - 39c

## RCA CA3043 - FM IC

Used in FM stereos. Contains IF Amp, Limiter, FM Detector, and an Audio Preamp and Driver all in one 12 lead TO-5 package. With Spec Sheets.

A \$3.00 Value - 99c

**FORD SOLID STATE MODULES**  
Mfg. by Centralab for Ford car radios. Each module contains 2 transistors plus other components. These modules were used as audio pre-amps. We include specs. - 4 For \$1

**TTL IC ASSORTMENT**  
Various types. Most are marked. Our best selling assortment. Untested but includes many useable devices.  
200 PCS FOR \$3.95

## FM TRANSFORMERS

We bought a load of coils and transformers that were used in Ford AM-FM car radios. Includes 19KHZ, 36KHZ, OSC. Coils, etc. All New. Perfect for experimenters or repairmen. 10 Pc Ass't. - 99c

**TANTALUM CAPS**  
By Sprague. 4.7 MFD 10 VDC. Axial Leads. Perfect for timers.  
10 For \$1

**ALTAJ ELECTRONICS**  
P.O. BOX 38544  
DALLAS, TEXAS 75238


TERMS: Check or money order. No COD. Add 10% Ptg. and Hdq. Tex Res. add 5%.

**NEW KITS! NEW KITS!**

**JAMES ELECTRONICS**

P. O. BOX 822 BELMONT, CALIFORNIA 94002  
(415) 592-8097

**DIGITAL VOLTMETER**

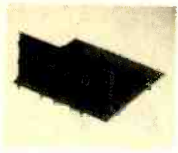

This is a 3 1/2 digit, 0.2 volt Digital Voltmeter, with a .5% full scale accuracy. It is based around the Siliconix LD110, LD111 DVM chip set. The voltmeter uses MAN3 resistors (3" high) to provide a highly readable display. The unit requires the following supply voltages: 12, -12, 5. The unit comes complete with all components to build the unit pictured at the left, that is a complete DVM! less power supply.

**\$39.95 Per Kit**


**LOGIC PROBE**

The Logic Probe is a unit which is for the most part indispensable in trouble-shooting logic families: TTL, DTL, RTL, CMOS. It derives the power it needs to operate directly off of the circuit under test, drawing a scant 10 mA max. It uses a MAN3 readout to indicate any of the following states by these symbols: (H) - 1 (LOW) - 0 (PULSE) - P. The Probe can detect high frequency pulses to 45 MHz. It can't be used at MOS levels or circuit damage will result.



**\$9.95 Per Kit**

**DIGITAL COUNTER**

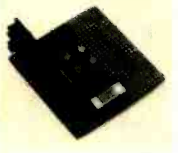


This is a 4 digit counter unit which will count up to 9999 and then provide an overflow pulse. It is based around the Mostek MK5007 digital counter chip. The unit performs the following functions: Count input, RESET, Latch, Overflow. The counter operates up to 250 KHz. The counter is an ideal unit to be used as a frequency counter, where the only extra components needed would be a timebase, divider chain and gate. The unit requires 5V and -12V. The unit comes complete as shown on the left less power supply.

**\$29.95 Per Kit**

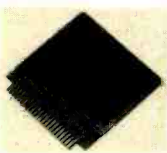**ONE KILOBYTE RANDOM ACCESS MEMORY**

This memory card is for the most part a universal unit that can be used in almost any microcomputer from a HOMEBREW to an ALTAIR-8800. It uses an array of 2102 1k x 1 static random access memories to produce a 1024 x 8 memory compatible with most standard microcomputer systems. We vector everything from the super low noise vector logic card, to fine quality low profile sockets, to the eight 2102's. We even include timing diagrams and tantalum bypass capacitor.



**\$69.95 Per Kit**

**5 VOLT 1 AMP T<sup>2</sup>L SUPPLY**



5 VOLT 1 AMP T<sup>2</sup>L SUPPLY

This is a standard TTL power supply using the well known LM309K regulator IC to provide a solid 1 AMP of current at 5 volts. We try to make things easy for you by providing everything you need in one package, including the hardware for only:

**\$9.95 Per Kit**

**PLASTIC INSTRUMENT CASE**

These cases are fine quality units made by a German manufacturing firm which fit to the dimensions of our DVM and COUNTER kit with room enough left for power supply or batteries. Excellent for many other projects as well. Dimensions 2" x 3-1/8" x 5-7/8"



**\$5.95 Per Case**

Satisfaction Guaranteed. \$5.00 Min. Order. U.S. Funds. Add \$1.25 for Postage — Write for FREE 1975 Catalog California Residents — Add 6% Sales Tax

**JAMES**

P.O. BOX 822, BELMONT, CA. 94002  
PHONE ORDERS — (415) 592-8097

CIRCLE NO. 30 ON FREE INFORMATION CARD

CARBON FILM RESISTORS. Brand new as low as 2-1/4 cents. FREE samples and specifications. COMPONENTS CENTER—PE. Box 134, New York, NY 10038.

RESISTORS: 1/4 and 1/2 watt. 4 cents each, 5 per value, \$5 minimum ppd. Dynamic Electronics, Box 1131, Decatur, AL 35601.

JAPANESE TRANSISTORS. all transistors original factory made. Free catalog. West Pacific Electronics, P.O. Box 25837, W. Los Angeles, CA 90025.

**SAVE ELECTRIC POWER!**

Save up to 80% electrical power with this unique, inexpensive, portable, permanent and legal method applicable for shops, homes, factories, businesses, farms, sites. 100% Refund Guaranteed if not scientifically sound or if it employs gimmicks.

Information \$1.00

**CONSUMERTRONICS CO.**

P.O. Box 1399 Alamogordo, N.M. 88310

FREE FLYER. Semis, Components, Electronic Hardware. Lowest Prices. Vanguard Electronics, Ltd., Box 1193, Edmonton, Alberta, Canada. TSJ 2M5.

UNUSUAL ELECTRONIC PLANS. Projects, Security Equipment, etc. Catalog \$1.00. McCord Electronics, Box 276-PE, Sylvania, Ohio 43560.

**HYBRID AUDIO AMPLIFIER**

EPITEK Model 1240  
12 Watts RMS  
Distortion 0.6% at 12W  
Price: \$6.95 + 50 cents postage.  
(CA Residents add 6% tax)

**ROYER COMPONENTS**  
P.O. Box N  
Bellflower, CA 90706

Send Money Order or COD

MEMORY-2102-1K Static RAM. \$3.75. Quantity discount, computer components, digital clock kits. Send for free list. Digitex, 2603 West Davis, Dallas, Texas 75211.

**PAIA ELECTRONICS, INC.**

The **GNOME** Micro-Synthesizer Kit

- \*VCO \*VCA
- \*VCF \*NOISE
- \*2 Function Generators
- \*Ribbon Controller
- \*32 pg. Using Manual
- \*in a hand-held battery powered package

**\$48.95 plus shipping and insurance 6 lbs.**

The Perfect LOW COST INTRODUCTION TO ELECTRONIC MUSIC SYNTHESIZERS

send for our FREE catalog  
PAIA Electronics, Inc.  
Box C-14359 Oklahoma City, Ok. 73114

**SCHEMATICS!** From TV games to advanced computers. Zodiac Enterprises, Box 2134-A Station A, Champaign, Illinois 61820.

**BUILD THAT ELECTRONIC ORGAN YOU ALWAYS WANTED AT A PRICE YOU CAN AFFORD.** Third edition of "Organ Builder's Guide," pictured product kit line, circuits, block diagrams, design rationale using IC divider and independent generators with diode keying. \$3.00 postpaid. Also, free brochure on keyboards. DEVTRONIX ORGAN PRODUCTS, Dept. C, 5872 Amapola Dr., San Jose, CA 95129.

**VIDEO PING PONG**

PLANS - PC CARDS - KITS ATTACHES TO YOUR TV'S ANT. ONLY 14 IC'S MOSTLY 7400 FAMILY. SEND 50¢ FOR INFO. PACK - REFUNDED WITH FIRST PURCHASE

**D. Duncan Electronics**  
20650 Runnymede Canoga Park Ca 91306

200 MHZ counter kit \$139.95 Cabinet \$15.95, TCXO \$25.00, 500 MHZ Prescaler assembled, ready to operate \$99.95, Davis Electronics, 636 Sheridan Dr., Tonawanda, N.Y. 14150 (716) 874-5848-9.

PERFORATED BOARD TERMINALS. Free Sample and Brochure. R.J.C. Enterprises, Inc., 1780 Monrovia, Costa Mesa, Calif. 92627.

BIOFEEDBACK: EMG, EEG, kits or assembled, accessories. Write for details. EDC, P.O. Box 9161E, Berkeley, CA 94704.

KITS. Beginner digital electronics. Electronic games. From \$7.75. Send stamp. NBL-E, Box 1115, Richardson, Texas 75080.

**STEREO TV**

The TE-200 TELEDAPTER EASILY CONNECTS TO ANY TV & STEREO SYSTEM Using our coupling and matrix circuit, teledapter takes a low impedance output from the television and delivers two HIGH IMPEDANCE CHANNELS OF SIMULATED STEREO, to drive any amplifier. Frequency response is maintained so you can hear the tinkle of bells or booming bass sounds as it happens on TV. With service warranty and hookup instructions \$19.95 ppd. Guaranteed to make your TV 100% more enjoyable.

OUR NEW TE-300 VHF UHF TELEVISION High Fidelity AUDIO TUNER is now available. Completely solid state Recording and amp output jacks. Anodized Aluminum front panel and simulated Walnut Cabinet. 110 volt operation. \$169.95 ppd.

SEND CHECK, M.O. MASTERCHARGE, or BANKAMERICARD NO. and Expiration date TO RHOADES NATIONAL CORP. DEPT NO. 58 BOX 817, HENDERSONVILLE TENNESSEE 37075.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

\*SEND COMPLETE CATALOG

CITIZENS BAND EQUIPMENT. Lowest Discount Prices. Best National Brands. Free List. CRS Communications, 2271 Morris Ave., New York, N.Y. 10453.

DIGITAL IC MANUAL — 3rd Edition — over 3000 latest types / pinout diagrams-cross references, \$6.95 — IC APPLICATIONS MANUAL — Analog / Digital — \$3.95. Electronetics-PE, P.O. Box 127, Hopedale, Mass. 01747.

YOU WANT TO BUILD IT: WE WANT TO HELP. WE SELL CONSTRUCTION PLANS with an Engineering Service. TELEPHONE: Answering Machines, Speakerphones, Carphones, Phonevision, Touch Button Dialers. TELEVISION: VTR, 1" Color TV Set, PONG, \$25.00 Camera, COLOR PROJECTION TV. HOBBYIST: Electron Microscope, \$75 software programmable computer. BROADCAST: Special Effects Generator, Chroma Key, Audio Board, DA's, COURSES: Telephone Engineering \$52.00, Detective Electronics \$29.50, IC Engineering \$65.00. PLUS MUCH MORE NEW Super Hobby Catalog PLUS year's subscription to Electronic News Letter AIR MAILED \$1.00. Don Britton Enterprises, 6200 Wilshire Blvd., Los Angeles, Calif. 90048.

FREE CATALOG. Ultrasonic Devices, LEDs, Transistors, IC's, Keyboards, Unique Components. Low Prices. Chaney's, Box 15431, Lakewood, Colo. 80215.

**FCC LICENSE REPORT**

An FCC License can be your key to a career in Communications Electronics. Our new copyrighted report reveals the best license to get, how to get it—and much more. Order R102-E2, \$3 postpaid.

RBX RESEARCH  
P.O. Box 50406, Nashville, TN, 37205

ALTAIR GOT YOU DOWN? Sell me your used 8800 and recover some of your hard-earned cash. Ken Hopper, 4021 S. Bowman Ave., Indianapolis, IN. (317) 787-8661.

SEMICONDUCTOR AND PARTS Catalogue from the semiconductor specialist. J & J Electronics, Box 1437, Winnipeg, Manitoba, Canada. U.S. Inquiries.

DESIGN your own power supply and regulator circuits. Twenty pages of circuit analysis and design examples. 8-1/2 x 11. \$2.00. Hutch, 10818 Brentway, Houston, Texas 77070.

PROJECT SOUND on Wall — Watch Dazzling Patterns change form to music, oscilloscope like display, easy, cheap to build — \$2 for plans. A. Biener, 149-08 Union Tpke., Flushing, N.Y. 11367.

TELEPHONES and ACCESSORIES. Wide color selection. Free Catalog. Flemco, 20272 37th Ave., N.E., Seattle, Wash. 98155.

CONVERTER gives your Simpson VOM (or any VOM having a 2.5-5-10 voltage sequence) a 10 Megohm input impedance. Precision ±1% resistors in critical circuits. Fully assembled, only \$19.95. ALR Electronics, P.O. Box 706, Flushing, N.Y. 11352.

CB RADIO, Scanners, Antennas. The best for less. Free List. Capitol Sound, Box 3523, Des Moines, Iowa 50322.

UNIVERSAL TTL / DTL / CMOS IC TESTER Tests 16 / 14 Pin Digital IC's! Set Programming Switches, Plug In; Press To Test; Errors Displayed. 151,072 Test Operations / Second. (All ICs TTL; costs less than \$20.00). Circuit is easy to understand and build. DS/PCB Available. Illustrated Plans: \$2.00. NORTHSTAR ENGINEERING, 3617 North Crede Drive, Charleston, WV 25302.

ELECTRONIC ignition: Pointless, Transistor, Capacitor, Vapor inductors, Auburn Sparkplugs. Information 10 cents. Anderson Engineering, Epsom, N.H. 03234.

SUPERDESIGNED: New CB, Experimenter, Computer, Power Sources, Signal Generators, Speech Compressors, More. Free Catalog. Write: Minitron, Box 184, Anoka, Minnesota 55303.

ASIA DIRECTORY — WORLD PRODUCTS INFORMATION. Both just \$1.00. World Trade Inquiries, Box 6224, Spokane, Washington 99207.

















# FREE DATA SHEETS WITH EVERY ITEM 749 IC WITH EVERY \$10 ORDER\*

- REDUCE YOUR PROJECT COSTS
- MONEY-BACK GUARANTEE
- 24-HOUR SHIPMENT
- ALL TESTED AND GUARANTEED

## TRANSISTORS (NPN):

2N3563 TYPE RF Amp & Osc to 1 GHz (pl. 2N918)	6/\$1.00
2N3565 TYPE Gen. Purpose High Gain (TO-92/106)	6/\$1.00
2N3567 TYPE High-Current Amplifier/Sw 500 mA	4/\$1.00
2N3866 TYPE RF Power Amp 1.5 W @ 450 MHz	\$1.50
2N3903 TYPE GP Amp & Sw to 100 mA and 30 MHz	6/\$1.00
2N3919 TYPE RF Power Amp 10-25 W @ 3-30 MHz	\$3.00
2N4274 TYPE Ultra-High Speed Switch 12 ns	4/\$1.00
MPS6515 TYPE High-Gain Amplifier h <sub>FE</sub> 250	3/\$1.00
Assort. NPN GP TYPES, e.g. 2N3694, 2N3903, etc. (15)	\$2.00
2N3638 TYPE (PNP) GP Amp & Sw to 300 mA	4/\$1.00
2N4249 TYPE (PNP) Low-Noise Amp 1µA to 50mA	4/\$1.00

## FET's:

### N-CHANNEL (LOW-NOISE)

2N4091 TYPE RF Amp & Switch (TO-18/106)	3/\$1.00
2N4416 TYPE RF Amplifier to 450 MHz (TO-72)	2/\$1.00
2N5163 TYPE Gen. Purpose Amp & Sw (TO-106)	3/\$1.00
2N5486 TYPE RF Amp to 450 MHz (plastic 2N4416)	2/\$1.00
E100 TYPE Low-Cost Audio Amplifier	4/\$1.00
ITE4868 TYPE Ultra-Low Noise Audio Amp	2/\$1.00
TIS74 TYPE High-Speed Switch 4052	3/\$1.00
Assort. RF & GP FET's, e.g. 2N5163, MPF102, etc. (8)	\$2.00

## P-CHANNEL:

2N4360 TYPE Gen. Purpose Amp & Sw (TO-106)	3/\$1.00
E175 TYPE High-speed Switch 12512 (TO-106)	3/\$1.00

## OCTOBER SPECIALS:

1N4154 DIODE 30 V/10mA-1N914 except 30 V	25/\$1.00
2N2222 NPN TRANSISTOR GP Amp & Switch	5/\$1.00
2N2907 PNP TRANSISTOR GP Amp & Switch	5/\$1.00
2N3553 RF Power Amp 5 W @ 150 MHz, 10 W @ 50 MHz	\$2.00
2N3904 NPN TRANSISTOR GP Amp & Switch	5/\$1.00
2N3906 PNP TRANSISTOR GP Amp & Switch	5/\$1.00
2N5108 RF Power Amp 2 W @ 450, 1 W @ 1 GHz	\$2.50
E101 N-CHANNEL FET Low Current, Low Vp Amp/Sw	3/\$1.00
MPF102 N-CHANNEL FET RF Amp-200 MHz	3/\$1.00
340 T 1A VOLT. REG. Specify 5, 6, 12, 15 or 24 V-W/Ckts	\$1.75
2556 DUAL 555 TIMER 1µsec to 1 hour (OIP)	\$1.00
8038 WAVE FORM GENERATOR ~□ Wave W/Ckts	\$4.50
MM5316 DIGITAL CLOCK Snooze/Alarm/Timer	
Hrs, Mins, Secs, 4 or 6 Digit-With Specs/Schematics	\$5.50

## LINEAR IC's:

308 Micro-Power Op Amp (TO-5/MINI-OIP)	\$1.00
309 K Voltage Regulator 5 V @ 1 A (TO-3)	\$1.50
324 Quad 741 Op Amp, Compensated (OIP)	\$1.75
380 2.5 Watt Audio Amplifier 34 dB (OIP)	\$1.29
555X Timer 1µs-1 hr. Ofc. pinout from 555 (OIP)	\$ .85
709 Popular Op Amp (OIP/TO-5)	\$ .29
723 Voltage Regulator 3-30 V @ 1.250mA (OIP/TO-5)	\$ .58
739 Dual Low-Noise Audio Preamp/Op Amp (DIP)	\$1.00
1458 Dual 741 Op Amp (MINI-OIP)	\$ .65
741 Freq. Comp. OP AMP (DIP/TO-5/MINI-OIP)	3/\$1.00

## DIODES:

ZENERS—400mW, Specify Voltage 3.3, 3.9, 4.3, 5.1, 6.8, 8.2, 9.1, 10, 12, 15, 18, 22, 24, 27 or 33V (+10%)	4/\$1.00
1N3600 TYPE Hi-Speed Sw 75 V/200 mA	6/\$1.00
1N3893 TYPE RECTIFIER Stud Mount 400 V/12 A	2/\$1.00
1N914 or 1N4148 TYPE Gen. Purp. 100V/10mA	15/\$1.00
D5 VARACTOR 5-50 W Output @ 30-250 MHz, 7-70 pF	\$5.00
F7 VARACTOR 1-3 W Output @ 100-500 MHz, 5-30 pF	\$1.00

\*MAIL NOW! FREE DATA SHEETS supplied with every item from this ad. FREE ON REQUEST—749 Dual Op Amp (\$1.00 value) with every order of \$10 or more, postmarked prior to 10/30/75.

ORDER TODAY—All items subject to prior sale and prices subject to change without notice. All items are new surplus parts — 100% functionally tested.

WRITE FOR FREE CATALOG offering hundreds of semiconductors not listed here. Send 10¢ stamp.

TERMS: All orders must be prepaid. We pay postage, \$1.00 handling charge on orders under \$10. Calif. residents add 6% sales tax. Foreign orders — add postage. COD orders — add \$1.00 service charge.

# ADVA ELECTRONICS

BOX 4181 AU, WOODSIDE, CA 94062  
Tel. (415) 851-0455

CIRCLE NO. 4 ON FREE INFORMATION CARD

## BUSINESS OPPORTUNITIES

I MADE \$40,000.00 Year by Mailorder! Helped others make money! Free Proof. Torrey, Box 318-NN, Ypsilanti, Michigan 48197.

FREE CATALOGS. Repair air conditioning, refrigeration. Tools, supplies, full instructions. Doolin, 2016 Canton, Dallas, Texas 75201.

MAILORDER MILLIONAIRE helps beginners make \$500 weekly. Free report reveals secret plan! Executive (1K10), 333 North Michigan, Chicago 60601.

PIANO TUNING LEARNED QUICKLY AT HOME! Musical knowledge unnecessary. Free information. Empire School, Box 450327, Miami 33145.

\$200.00 DAILY in Your Mailbox! Your opportunity to do what mail-order experts do. Free details. Associates, Box 136-J, Holland, Michigan 49423.

FREE BOOK "2042 unique proven enterprises." Work home! Hayling-B, Carlsbad, CA 92008.

GET RICH with Secret Law that smashes debts and brings you \$500 to \$5 Million cash. Free report! Credit 4K10, 333 North Michigan, Chicago 60601.

ELECTRONIC Assembly Business. Big profits. Start home, spare time. Investment, knowledge, experience unnecessary. Free illustrated literature. Barta, Box 248CX, Walnut Creek, Calif. 94597.

P-2

## Wanted Citizens Band

### DEALER-DISTRIBUTORS

Send this ad with Letterhead to:

**PAL ELECTRONICS CO.**

2962 W. WELDON - PHOENIX, ARIZ. 85017

FM RADIO STATION. Start your own. Fantastic income. Frequencies still available. Complete information \$3.00. Concept, Box 106, Lawrence, N.Y. 11559.

DO SIMPLE ADDRESSING—Mailing. Receive \$12.95 orders. Keep \$8.00 profit. Details — Rush stamped envelope. Distributors, Box 9-ZD, East Rockaway, N.Y. 11518.

CB DEALERS WANTED—CSC Distributing, Box 3047, Scottsdale, AZ 85257.

## INVENTIONS WANTED

INVENTORS: Protect your ideas! Free "Recommended Procedure". Washington Inventors Service, 422T Washington Building, Washington, D.C. 20005.

FREE PAMPHLET: "Tips on Safeguarding Your Invention." Write: United States Inventors Service Company, 708-T Carry Building, Washington, D.C. 20005.

## Inventors Wanted

**RECOGNITION, FINANCIAL REWARD, OR CREDIT for "inventing it first" may be yours!** We'll develop your idea, introduce it to industry, publicize it, negotiate for Cash Sale or Royalty Licensing.

Send for **FREE INVENTORS KIT** Includes • Vital information on Protection, Development, Marketing of your Invention • Important "Invention Record Form" • Directory of 500 Corporations Seeking New Products

**RAYMOND LEE ORGANIZATION**  
230 Park Ave. No., New York, NY 10017  
Please rush **FREE INVENTORS KIT A-139**

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

## INSTRUCTION

LEARN ELECTRONIC ORGAN SERVICING at home all makes including transistor. Experimental kit—trouble-shooting. Accredited NHSC. Free Booklet. NILES BRYANT SCHOOL, 3631 Stockton, Dept. A, Sacramento, Calif. 95820.

LEARN WHILE ASLEEP. Hypnotize! Strange catalog free. Auto-suggestion, Box 24-ZD, Olympia, Washington 98501. DEGREE IN ELECTRONICS through correspondence. Free catalog. Grantham, 2000 Stoner Avenue, Los Angeles, California 90025.

INTENSIVE 5 week course for Broadcast Engineers. F.C.C. First Class license. Radio Engineering Incorporated, 61 N. Pineapple Ave., Sarasota, Florida 33577 and 2402 Tidewater Trail, Fredericksburg, VA 22401.

## F.C.C. EXAM MANUAL

PASS FCC EXAMS! Memorize, study—"Test Answers" for FCC 1st and 2nd class Radio-Telephone licenses. Newly revised multiple-choice questions and diagrams cover all areas tested in FCC exams plus "Self-Study Ability Test." \$9.95 postpaid. Moneyback Guarantee.

COMMAND PRODUCTIONS P.O. BOX 26348-P  
RADIO ENGINEERING DIVISION SAN FRANCISCO, CALIF. 94126

SCORE high on F.C.C. Exams. Over 300 questions and answers. Covers 3rd, 2nd, 1st and even Radar. Third and Second Test, \$14.50; First Class Test, \$15.00. All tests, \$26.50. R.E.I., Inc., Box 806, Sarasota, Fla. 33577.

UNIVERSITY DEGREES BY MAIL! Bachelors, Masters, Ph.D's. Free revealing details. Counseling, Box 1162-PE10, Tustin, California 92680.

SELF-STUDY CB RADIO REPAIR COURSE. THERE'S MONEY TO BE MADE REPAIRING CB RADIOS. This easy-to-learn course can prepare you for a career in electronics enabling you to earn as much as \$16.00 an hour in your spare time. For more information write: CB RADIO REPAIR COURSE, Dept. PE105, 531 N. Ann Arbor, Oklahoma City, Okla. 73127.

# HAM SWL CB

they come through LOUD AND CLEAR in the all-new 1976 COMMUNICATIONS HANDBOOK

Here is everything you want to know — need to know about Citizens' Band, Amateur Radio, Shortwave Listening.



DON'T TURN A DIAL. In fact don't even buy a dial or anything else until you've checked out the 1976 Communications Handbook. Whatever your radio specialty — whether you're an old hand or just getting started — this vital "how-to" guide will help you get greater value, greater enjoyment out of every minute you spend with your equipment.

The all-new 1976 COMMUNICATIONS HANDBOOK is scheduled to go on sale nationally November 20, 1975

**YOU CAN RESERVE YOUR COPY NOW AT THE SPECIAL PRE-PUBLICATION PRICE OF ONLY \$1.00 POSTPAID.**

Regular newsstand price is \$1.50, mail order \$1.85.

So to make sure you come through "Loud and Clear" in 1976 . . .

**RESERVE YOUR COPY NOW AND SAVE WITH THIS SPECIAL PRE-PUBLICATION OFFER AVAILABLE TO READERS OF POPULAR ELECTRONICS MAGAZINE ONLY.**

## PRE-PUBLICATION RESERVATION FORM

Communications Handbook PE-1075  
Ziff-Davis Consumer Service Division  
595 Broadway, New York, N.Y. 10012

Enclosed is \$1. Please reserve my copy of the 1976 Communications Handbook at the special prepublication price to be mailed to me on or before November 20, 1975. (Residents of Cal., Col., Fla., Ill., Mich., Mo., N.Y. State, D. C. and Tex. add applicable sales tax.) OUTSIDE U. S. A. \$2 (regular mail order price \$3).

Print Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_

## ADVERTISERS INDEX

READER SERVICE NO.	ADVERTISER	PAGE NUMBER
1	A.D.R. Audio	98
2	A.P. Products Incorporated	101
3	Ace Electronic Parts	110
4	Adva Electronics	122
6	Allison Automotive Company	89
8	Altaj Electronics	111
9	Ancrona Corp	113
10	Audio-Technica U.S. Inc.	99
11	Babylon Electronics	123
	Bell & Howell Schools	54, 55, 56, 57
65	Burstein-Applebee	102
14	CIE Bookservice	13
	CREI Capitol Radio Engineering Institute	94, 95, 96, 97
12	Circuit Specialists Co	114
13	Cleveland Institute of Electronics, Inc	104, 105, 106, 107
15	Cobra, Product of Dynascan Corporation	2
17	Continental Specialties Corp	39-46
18	Delta Electronics Co	120
19	Delta Products, Inc	81
20	Dig-Key Corporation	114
64	Discwasher Inc	FOURTH COVER
	Dixie-Hi Fidelity	100
21	EICO	77
22	Edmund Scientific Co	124
23	Electronic Distributors, Inc	108
46	Electronics Book Service	17
24	Electronics Technical Institute	18, 19, 20, 21
5	Heath Company	84, 85, 86, 87
25	IMS Associates Inc	110
	lasis, Inc	14, 15
27	Illinois Audio	98
28	International Electronics Unlimited	118
29	JS&A National Sales Group	1
30	James	112
31	James	119
33	Johnson Co., E.F.	65-68
32	Lafayette Radio Electronics	90
34	McGraw-Hill Book Company	83
35	McIntosh Laboratory, Inc	103
36	MITS	7
37	Mallory Distributors Products Company	5
38	Midland International	26
39	Mini-Micro Mart	114
	NRI Schools	8, 9, 10, 11
	National Technical Schools	28, 29, 30, 31
40	New-Tone Electronics	120
41	Olson Electronics	75
42	Pace Communications	99
43	PanaVise	108
44	Phase Linear	53
45	Poly Paks	117
47	Processor Technology Co	110
48	Radio Shack	23
49	SAE	6
50	Sansui Electronics Corp	25
51	Schober Organ Corp., The	103
52	Sencore	88
53	Shure Brothers Inc	91
54	Solid State Sales	109
55	Solid State System	121
56	Southwest Technical Products Corporation	SECOND COVER
57	Stanton Magnetics	THIRD COVER
58	Stereo Discounters	93
59	Tri-Star Corporation	102
60	Trigger Electronics	93
61	U.S. Pioneer Electronics Corp	32
62	Wahl Clipper Corporation	108
63	Weller-Xcelite Electronics Division	16

CLASSIFIED ADVERTISING 109, 110, 112, 114, 118, 120, 122, 123

**DRAFTING—Blueprint Reading** (Mechanical, Electronic, Architectural). Home Courses \$25.00. Send \$2.00 first lesson. Prior, Inc., 23-09 169th Street, Whitestone, N.Y. 11357.

**UPDATE** your electronics knowledge and add a FCC first class license. Home study. Free catalog. Genn Tech., 5540 Hollywood Blvd., Los Angeles, CA 90028.

**RECORDING ENGINEER CAREER?** Degree not needed. Details 25 cents. Attainment, Box 45333PE, Dallas, Texas 75235.

**FREE Educational Electronics Catalog.** Home study courses. Write to: Edukits Workshop, Department 710D, Hewlett, N.Y. 11557.

**GET INTO BROADCASTING:** Become a disc jockey, \$4.95. Start your own station, \$14.95. Satisfaction guaranteed. Wilson, Box 5516AL, Walnut Creek, CA 94596.

**UNDERSTAND DIGITAL ELECTRONICS—Calculators.** Microprocessors, clocks. New programmed learning courses. Design of Digital Systems, 6 volumes, only \$14.95. Digital Computer Logic, 4 volumes, \$9.95. Both \$19.95. Unconditional refund if dissatisfied. Cambridge Learning, 300 East 56th Street, New York, N.Y. 10022.

### RECORDS

**OLDIES.** 45rpm. Free Catalog. Corny's Record Shop, Box 166TP, Mason, Ohio 45040.

**FREE RECORD COLLECTION Reviewers wanted.** Anyone qualifies. We ship you new records to review. You pay postage. Records are free. Applicants accepted "first come" basis. Write: Research PE, 6162 Washington Circle, Milwaukee, Wisconsin 53213.

### RUBBER STAMPS

**RUBBER ADDRESS STAMPS.** Free Catalog. 45 type styles. Jackson's, Dept. K, Brownsville Rd., Mt. Vernon, Ill. 62864.

### BOOKS AND MAGAZINES

**FREE catalog aviation/electronic/space books.** Aero Publishers, 329PE Aviation Road, Fallbrook, California 92028.

**FREE book prophet Elijah** coming before Christ. Wonderful bible evidence. Megiddo Mission, Dept. 64, 481 Thurston Rd., Rochester, N.Y. 14619.

**COMPUTERS for Fun!** Read PCC, 6 issues for \$6. Sample \$1. P.O. Box 310, Menlo Park, CA 94025.

**POPULAR ELECTRONICS INDEXES.** Detailed and complete subject indexes available to magazine years 1974, 1973, and 1972. Hundreds of subject references to help you quickly find that special project, article or product test. 1972, 1973, and 1974 editions \$1.50 each. All three editions only \$4.00. INDEX, Box 2228, Falls Church, Va. 22042.

### HYPNOTISM

**SLEEP learning.** Hypnotic method. 92% effective. Details free. ASR Foundation, Box 23429EG, Fort Lauderdale, Florida 33307.

**FREE Hypnotism.** Self-Hypnosis. Sleep Learning Catalog! Drawer H400, Ruidoso, New Mexico 88345.

**AMAZING self-hypnosis record** releases fantastic mental power. Instant results! Free trial. Write: Forum (AA10), 333 North Michigan, Chicago 60601.

### PLASTICS

**CASTOLITE** pours like water, hardens like glass without heat. Crystal clear, colors. Embed flowers, seashells, mementos, anything. Make fine gifts. Reproduce your designs with flexible molds any shape, size. Profitable. Illustrated Manual and Mold Catalog \$1.00. CASTOLITE, Dept. 75L/PE, Woodstock, Ill. 60098.

### BROKERS

**YOUR OLD EQUIPMENT** Collecting dust? **BUYERS & SELLERS Radio Brokerage** — Buyers free, Sellers 10% if you sell. (617) 536-8777 Tuesday, Thursday, 9-5. Box 43, Boston, Mass. 02215.

### MISCELLANEOUS

**WINEMAKERS:** Free illustrated catalog yeasts, equipment. Semplex, Box 12276P, Minneapolis, Minn. 55412.

**YEAR-END SALE** With a \$25 prepaid order we'll include a CT5001 4-function, 12 digit calculator IC with data.



### POTTER BRUMFIELD

Type KHP Relay  
4 PDT 3A Contacts  
24 VDC (650 coil) \$1.50 EA.  
120 VAC (10.5 MA coil) \$1.75 EA.


### DIP SOCKETS

8 PIN PCB \$ .22  
14 PIN PCB .26  
16 PIN PCB .30  
24 PIN PCB .75  
40 PIN PCB 1.25  
14 PIN WIRE WRAP .35

### DIP TRIMMER

-12 turn trimpot which plug into a dip socket  
-5K and 200K  
-1/4" x 1/4" x 1/4"  
-4 leads spaced .3" x .2"  
Each \$1.00 10 for \$8.95

### 2N3055 NPN TRANSISTOR

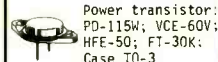

Power transistor:  
PD-115W; VCE-60V;  
HFE-50; FT-30K;  
Case TO-3

Each \$1.15 10 for \$6.95



### 7 Segment Readout

12 bin DIP  
Similar to Litronix DL33  
Digit approx. .1 inch  
Common cathode

Super Special offer  
4 (12 digits) \$5.00

### CARBON RESISTORS

Carbon Resistors 1/2-Watt 5%-full prime  
All values in stock. 10 per value (minimum quantity). 10 for \$ .45

### 2102-2 MOS 1024 BIT MEMORY (DIP)

FULLY DECODED STATIC RANDOM ACCESS MEMORY  
DIRECTLY TTL COMPATIBLE INPUTS AND OUTPUT  
SINGLE 5V SUPPLY - NO CLOCKS OR REFRESH  
**\$5.00 ea. 8 for \$34.95**

### DIODE ARRAY

10 - 1N914 Silicon Signal Diodes in one package. 20 leads spaced .1"; no common connections. Each \$ .25 10 for \$2.25

### Numeric Display 1/4" Single Digit GaAsP LED



COMMON CATHODE WITH RH DECIMAL

**SUPER SPECIAL \$5.99**  
TEN for \$4.95

Compact - 10 digits in 3" panel width  
Highly legible - bright red 4" character easily read within 10 feet over a wide viewing angle (140°)  
Low power - 125 mW per digit at typical brightness

**SPECIAL 8223 PROM**  
8 BIT 32 WORD MEMORY  
\$3.00 EA.  
10 - \$29  
WE PROGRAM FOR \$5 EACH

### RECTIFIER SPECIAL!

1N4007 - 1 AMP - 1000 volt PRV  
\$ .13 each 10 for \$1.00

### SEND FOR FREE FLYER

Mail Orders to:  
P.O. Box 41778  
Sacramento, CA 95841  
Phone: (916) 334-2161

**BABYLON ELECTRONICS**

CIRCLE NO. 11 ON FREE INFORMATION CARD

### Retail Display Plan

All magazine retailers in the United States and Canada interested in earning an allowance for the display and sale of publications of the Ziff-Davis Publishing Company are invited to write for details. Sales Manager, Select Magazines, 229 Park Avenue South, New York, New York 10003.

# LIVE IN THE WORLD OF TOMORROW... TODAY!

And our FREE 164 PAGE CATALOG is packed with exciting and unusual values in electronic, hobby and science items — plus 4,500 finds for fun, study or profit... for every member of the family.

## A BETTER LIFE STARTS HERE

### PRO ELECTRONIC SOUND CATCHER

Parabolic mike w/ 18-3/4" transparent reflecting shield & 2 I.C.'s in amplifier magnifies signals 100x that of omni-direction mikes. Catch sounds never before heard! Highest signal to noise ratio poss. Earphones, tape recorder output, tripod socket; req. two 9v trans. batt. (not incl.)

No. 1649AV (5 1/2 LB.) ..... \$299.00 Ppd.

LOW COST MODEL: NO EARPHONES, ELECTR. CIRC. No. 1665AV ..... \$199.95 Ppd.

LOWER SENSITIVITY ECON. MOD. W/O ELECTR. No. 80,242AV ..... \$89.50 Ppd.



### ELECTRONIC DIGITAL STOPWATCH: \$69.95

A price breakthrough! New pocket size 4 oz. timer acc. to ±2% of last digit (1/100 sec. increments). Compares with others twice the price! Instant error-free readouts to 9999.99 sec. (over 2 3/4 hr). Starts, stops re-starts (accumulates). Mechanical pushbutton & electrical remote on/off w/any 3.5-150v AC/DC source. Plug-in jack. Incls. 9v batt. Solid state.

No. 1943 AV (2 1/4x4 1/4x7/16") ..... \$69.95 Ppd.

DELUXE 2 EVENT STOPWATCH (±0.01% OF LAST DIGIT) No. 1653 AV ..... \$149.95 Ppd.



### FUEL MISER RECLAIMS HEAT

Save your 40% wasted heat to warm a basement, garage or rec room at no extra cost! Instead of going "up the chimney" it goes where you want it. Remove part of furnace exhaust pipe, slip Heat Exchanger in. At 125 fan automat. forces clean air through unit which heats to over 200°F., can be ducted to 20 ft. from unit. 110v AC. Inst.

No. 19,194AV (5/8" DIA.) Shpg. 17 lb. .... \$106.00 FOB

No. 19,195AV (6" DIA.) Shpg. 17 lb. .... \$106.00 FOB


No. 19,198AV (7" DIA.) Shpg. 17 lb. .... \$106.00 FOB



### 3-CHANNEL COLOR ORGAN KIT

Easy to build low-cost kit needs no technical knowledge. Completed unit has 3 bands of audio frequencies to modulate 3 independent strings of colored lamps (i.e. "lows"-reds, "middles"-greens, "highs"-blues. Just connect hi-fi, radio, power lamp etc. & plug ea. lamp string into own channel (max. 300w ea.). Kit features 3 neon indicators, color intensity controls, controlled individ SCR circuits, isolation transformer, custom plastic housing; instr.

Stock No. 41,831AV ..... \$18.95 Ppd

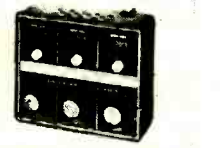

WHEN YOU COME TO PHILADELPHIA BE SURE TO SEE  
★ FREE BICENTENNIAL LIGHT SHOW ★  
IN BARRINGTON, N. J. ONLY 10 MINUTES AWAY AT  
EDMUND FACTORY STORE

### WORLD'S SMALLEST CALCULATOR!



Small but mighty! 8-digit, 4-function electronic calculator does everything big ones do—even has automatic % key... for only \$19.95. Take it anywhere. Fits in your pocket—1/3 size of cigarette pack. 2-oz. dynamo features floating decimal, constant key, lead zero depression, more! Operates on two 1.5v Mallory PX 825 camera batteries (included). 2 x 2.8 x 0.4" w/ plenty of room for most fingers. Another Edmund first with advanced technology.

Stock No. 1945AV ..... \$19.95 Ppd.

### AM RADIO FITS IN/ON YOUR EAR!



Wear it inconspicuously everywhere, listen as you work (lawn, yard, office), watch (game, beach) or wait. Instant music, news, sports. No gimmick-6/10 oz. technological wonder w/integrated circuit, 11 transistors, patented ferrite antenna/tuner/volume dial. Works best outdoors. Uses hearing aid batt. (incl)-up to 100 hrs. playing. New batt. to slip in avail. at drug stores (about 50¢). No lengthy wires, bulky cases, or power-packed!

Stock No. 42,275AV ..... \$14.95 Ppd.

### KNOW YOUR ALPHA FROM THETA!



For greater relaxation, concentration, listen to your Alpha-Theta brainwaves. Ultra-sensitive electrode headband slips on/off in seconds—eliminates need for messy creams, etc. Atch'd to amplifier, filters brainwaves, signals beep for ea. Alpha or Theta wave passed. Monitoring button stimulates Alpha sound; audio & visual (L.E.D.) feedback. Reliable, easy-to-use unit comparable to costlier models. Completely safe. Comprehensive instruction booklet.

No. 1635AV (8 • 3 • 4"; 24 oz.) ..... \$149.50 Ppd.

DELUXE "ON" TIME MONITOR—Measures and records % No. 1652AV ..... (15 • 10 • 6") ..... \$299.50 Ppd.

No. 71809AV LOW COST "STARTER" UNIT ..... \$55.00 Ppd.

DO-IT-YOURSELF KIT ..... No. 61,069AV ..... \$34.95 Ppd.

### LOW COST 7X INFRA-RED VIEWER



For infra-red crime detection surveillance, security system alignment, I.R. detection, laser checking, nite wildlife study, any work req. I.R. detection & conv. to visible spectrum. Self cont. scope w/everything incl I.R. light source.

6v or 12v power. 6032 I.R. converter tube, f/4.5 objective lens, adjust. triplet eyepiece. Focuses from 10' to infinity.

No. 1659AV (11x14 1/4x3") ..... \$275.00 Ppd.

WITHOUT LIGHT SOURCE No. 1648AV ..... \$225.00 Ppd.

### 4 1/4" ASTRONOMICAL TELESCOPE



See moon craters, rings of Saturn, double stars. New equatorial mount, f/10, 1/4 wave mirror (Pyrex). Gives theoretical limit of resolution. Rack & pinion focusing. Aluminum tube, 6X finder, 1" F.L. 45X Kellner achromatic eyepiece and Barlow lens to double & triple power up to 135X. Free Star Chart plus 2 Books.

Stock No. 85,105AV (Shipping Wt. 42 lbs.) ..... \$169.50 FOB

4 1/4" WITH CLOCK DRIVE No. 85,107AV ..... \$189.50 FOB

6" REFLECTOR TELESCOPE (48X to 360X) No. 85,187AV ..... \$249.50 FOB

6" WITH CLOCK DRIVE No. 85,086AV ..... \$285.00 FOB

3" DELUXE REFLECTOR (30X to 90X) No. 80,162AV ..... \$ 89.95 Ppd.

STANDARD 3" REFLECTOR No. 85,240AV ..... \$ 49.95 Ppd.



## MAIL COUPON FOR GIANT FREE CATALOG!

164 PAGES • MORE THAN 4500 UNUSUAL BARGAINS

Completely new 1976 edition. New items, categories, illustrations. Dozens of electrical and electromagnetics parts, accessories. Enormous selection of Astronomical Telescopes. Unique lighting and ecological items. Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Prisms. Hard-to-get-surplus bargains. Ingenious scientific tools. 1000's of components.

EDMUND SCIENTIFIC CO.  
300 Edscorp Building, Barrington, N. J. 08007  
Please rush Free Giant Catalog "AV"

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_



## COMPLETE & MAIL WITH CHECK OR M.O.

EDMUND SCIENTIFIC CO. 300 Edscorp Building, Barrington, N.J. 08007

How Many	Stock No.	Description	Price Each	Total
<input type="checkbox"/>		PLEASE SEND GIANT FREE CATALOG "AV"		
<input type="checkbox"/>		Charge my BankAmericard		
<input type="checkbox"/>		Charge my Master Charge		

Interbank No.

My Card No. Is

Card Expiration Date

30-DAY MONEY-BACK GUARANTEE. Name \_\_\_\_\_  
You must be satisfied or return any purchase in 30 days for full refund. \*\$15.00 minimum City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Add Handling Chg.: \$1.00, Orders Under \$5.00, 50¢, Orders Over \$5.00

I enclose  check  money order for TOTAL \$

Signature \_\_\_\_\_



# Instant Success—the NEW Stanton Gyropoise® turntable



Look at all these  
quality features, many  
of them  
exclusively ours!



1. Gyropoise®—frictionless magnetic suspension of the platter.
2. Die cast aluminum T-Bar for sturdy structure.
3. 2-Speed changer for 33 rpm and 45 rpm playback.
4. 24-Pole synchronous high torque motor.
5. Belt drive for noiseless operation.
6. 12" die cast machined high polish aluminum platter.
7. Unipoise®—single point tone arm suspension.
8. Anti-skate control adaptable to all types of styli.
9. Magnetic hold bar for tone arm convenience.
10. Stylus force slide (range 0 - 4 grams).
11. Stanton state-of-the-art stereo or discrete cartridge.
12. Viscous damped cueing control for featherlight lowering of stylus.
13. Handsome walnut veneer base (comes complete with dust cover).


#### ADDITIONAL FEATURES:

- (a) Comes equipped with low capacitance cables
- (b) Wow and Flutter— $\leq .07\%$  din 45507 weighted
- (c) Rumble— $\leq -60$  dB din 45539 weighted

It's the important exclusive features that make the difference. Only Stanton Turntables have Gyropoise®, the patented frictionless magnetic suspension bearing—thus the platter makes no vertical contact with the body of the structure. This isolation eliminates vertical rumble.

Only Stanton Turntables have Unipoise®, the patented single point tone arm suspension. The arm is supported by a single pivot for both lateral and vertical movement.

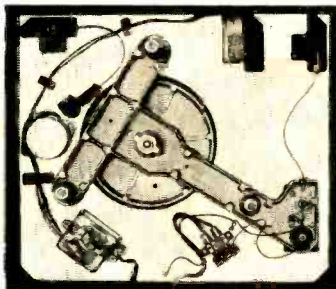Only Stanton Turntables come equipped with a state-of-the-art Stanton cartridge, either the 681 Triple-E calibrated to the tone arm for stereo playback, or the magnificent 780/4DQ for discrete.



Bottom view shows simplicity of design.

See your franchised Stanton dealer for a demonstration of this great new product.



MADE IN U.S.A.

For further information, write: Stanton Magnetics, Inc., Terminal Drive, Plainview, N.Y. 11803

CIRCLE NO. 57 ON FREE INFORMATION CARD

# Two Products You Must Have



Discwasher:  
The Superior  
Record Cleaner.

D'Stat:  
The Static  
Reduction System.

Available at  
Audio Specialists  
world wide.

**Discwasher Inc.**  
909 University.  
Columbia.  
Mo. 65201

# D'STAT

A scientific solution  
to audible static caused  
by electron "Hotspots"  
in phonograph discs.

EXCLUSIVELY DISTRIBUTED BY  
DISCWASHER INC.  
909 UNIVERSITY • COLUMBIA, MO. 65201

CIRCLE NO. 64 ON FREE INFORMATION CARD