

A NEW INDUSTRY STANDARD FOR FM TUNER MEASUREMENT

14278

Popular Electronics

WORLD'S LARGEST-SELLING ELECTRONICS MAGAZINE NOVEMBER 1975/75c

**WHAT YOU SHOULD
KNOW ABOUT HOME
VIDEO DISC SYSTEMS**

**Build a Preregulated
Bench Power Supply
For About \$30**

**How to Make 3-D
Drawings On An
Oscilloscope**

**A Digital Logic
Sensor for Autos**

LAB TESTS:

- Electra Bearcat 101
- Digital Scanner
- Shure M95ED
- Stereo Cartridge
- IAD Dynamic
- Range Expander
- Yamaha CR800


- Stereo
- Lectrote
- TV Colo

692188 JNK 11024082 11LD 00L80
 R JENKINS S 201
 1102 S 45TH ST
 TX 76501

EXCLUSIVE!

The First Motorola AMI '6800' MPU Computer Project

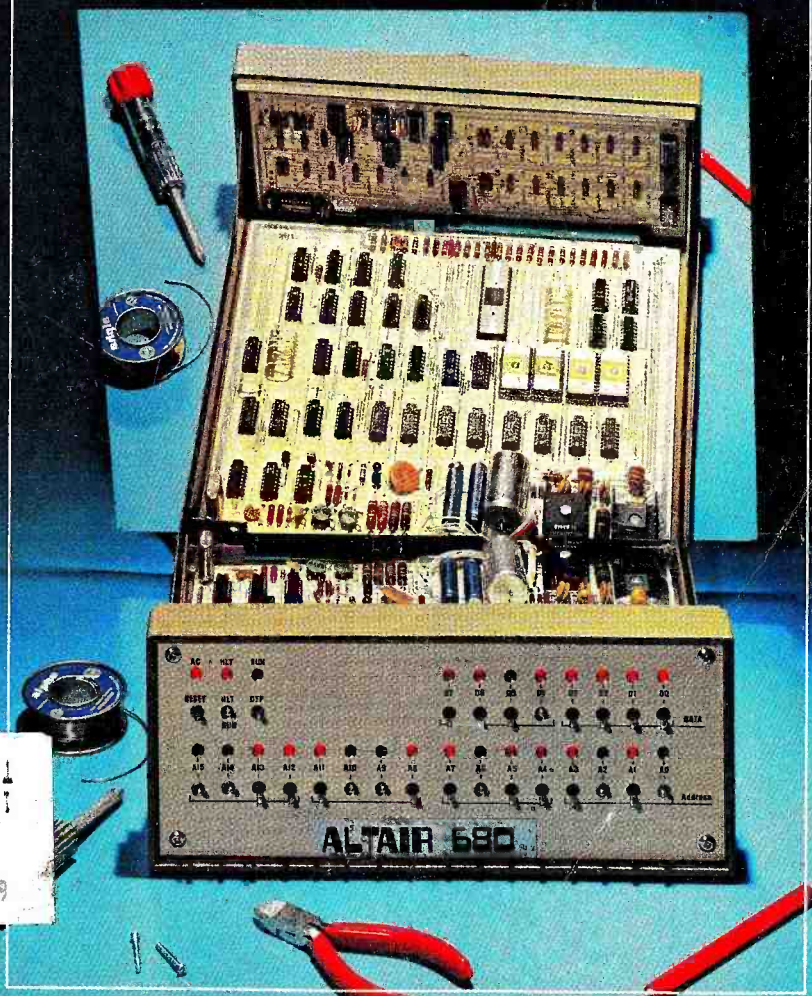- HALF THE PRICE OF ALTAIR 8800
- BUILT-IN TTY INTERFACE
- EASIER TO BUILD ● SMALLER SIZE





CB: What's stopping you?

For less than 50 bucks, you can be into serious Citizens Band radio. Not big, maybe, but in. Because one great thing about Midland CB is that you can get into it, go as pro as you want, and still be assured of the same unquestioned quality and reliability that you'd expect from a company consistently ranking among the top CB names in the world. You've come to demand quality in electronics. Demand it in Citizens Band radio as well.

Whatever you want, whenever you're ready, Midland has it in CB. Specifically: 13 professional walkie talkies, 14 base and mobile transceivers, plus more than 40 helpful CB accessories. So, if you've even thought about getting into CB within the last year, your best bet is to start by checking out what Midland has to offer.

Write for your **FREE 1975 Midland CB brochure**: Midland Communications Division, Dept. PE, Post Office Box 12737, North Kansas City, Missouri 64116. Or circle the number below on the Reader Service Card.

MIDLAND
INTERNATIONAL
Communications Division

CIRCLE NO. 51 ON FREE INFORMATION CARD



If it moves on land or water... Royce has a reliable CB for it!

Here are just two models in Royce's quality line:




The ultimate in miniaturization—**Model 1-580**. Tiny control head mounts in passenger compartment, power unit in trunk.

New and completely unique! 3-piece unit installs in any vehicle. Has (1) control unit slightly larger than king-size cigarette pack—with controls for volume, squelch, PA-CB, S-RF meter, tone, plus speaker. (2) Electronic power unit can be mounted up to 18' away from control center. (3) Royce's exclusive Chan-L-Matic with lighted channel indicator is right on the mike!

Digital readout over 1/2-inch high on new Royce **Model 1-510 Professional CB Mobile Transceiver!**

Now! Digital readout in mobile CB. New Matrix II Switch System replaces conventional mechanical type, gives you a completely electronic system. Fully solid state. Integrated circuits. Chan-L-Matic II System allows remote channel switching from mike. Warn-Tron circuit protects RF final transistor. New bright-dim switch. New semi-leadless chassis minimizes failure from broken wires. Plus so much more!

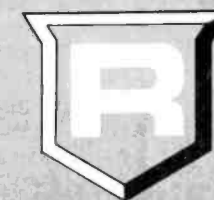
See the whole Royce line at your
CB or marine equipment dealer.
Or, write today for color catalog.



Royce
electronics
corporation

1746 Levee Road
North Kansas City, Mo. 64116
Call: (816) 842-7505 • TELEX: 426-145

CIRCLE NO. 63 ON FREE INFORMATION CARD

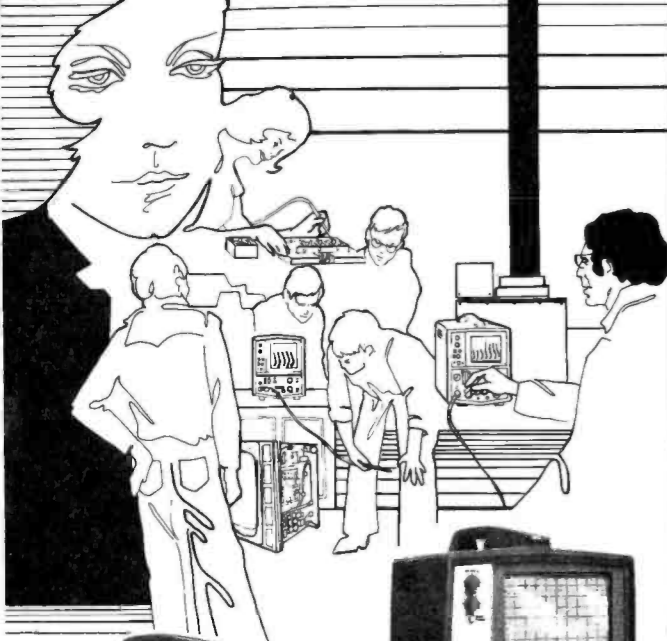

ANNOUNCING the TEKTRONIX T900 Oscilloscopes

from \$695
probes included and more...

Here's important news for engineers, technicians and educators who want the quality, reliability and support associated with TEKTRONIX Oscilloscopes - all at a moderate price. T900* Oscilloscopes are an entirely new line designed for cost savings without sacrifice of basic performance.

This New Line Includes:

- T921—Dc to 15 MHz; single-trace, mono time-base \$ 695**
- T922—Dc to 15 MHz; dual-trace, mono time-base \$ 850**
- T932—Dc to 35 MHz; dual-trace, mono time-base \$1050**
- T935—Dc to 35 MHz; dual-trace, dual time-base with delayed sweep \$1250**
- T912—(Storage model) Dc to 10 MHz, dual-trace mono time-base .. \$1195**

Easy to Use

T900 Oscilloscopes are simple to use. All have a large, bright (8 x 10 cm) crt, beam finder, single knob trigger control, delay line to enable viewing of waveform leading edge, automatic selection of tv line or frame display and functionally color-coded control panels. Convenience is also enhanced by a full complement of accessories including 10X probes (included in price), optional scope stand, camera, rain jacket and more... T900 Oscilloscopes are easy to handle and fit into small spaces. They weigh only 15-18 lbs. and measure only 7" x 10" x 19".

Tektronix Support

T900 Oscilloscopes are warranted against defective materials and workmanship for one year. There are over 37 service centers and 50

field offices across the U.S. Whenever you need help in the selection, operation, application or servicing of T900 Oscilloscopes your local field engineer is available to help you...no extra charge...just extra value.

For a copy of the new T900 Brochure (includes complete specifications), or ordering information write to Tektronix, Inc., P.O. Box 500, Beaverton, Oregon 97077. For immediate information call your local Tektronix field engineer or Tektronix, Inc. (503) 644-0161 extension T900.


*Available presently in U.S.A. only.
**U.S.A. price FOB Beaverton, Oregon.

CIRCLE NO. 73 ON FREE INFORMATION CARD



TEKTRONIX®

committed to
technical excellence

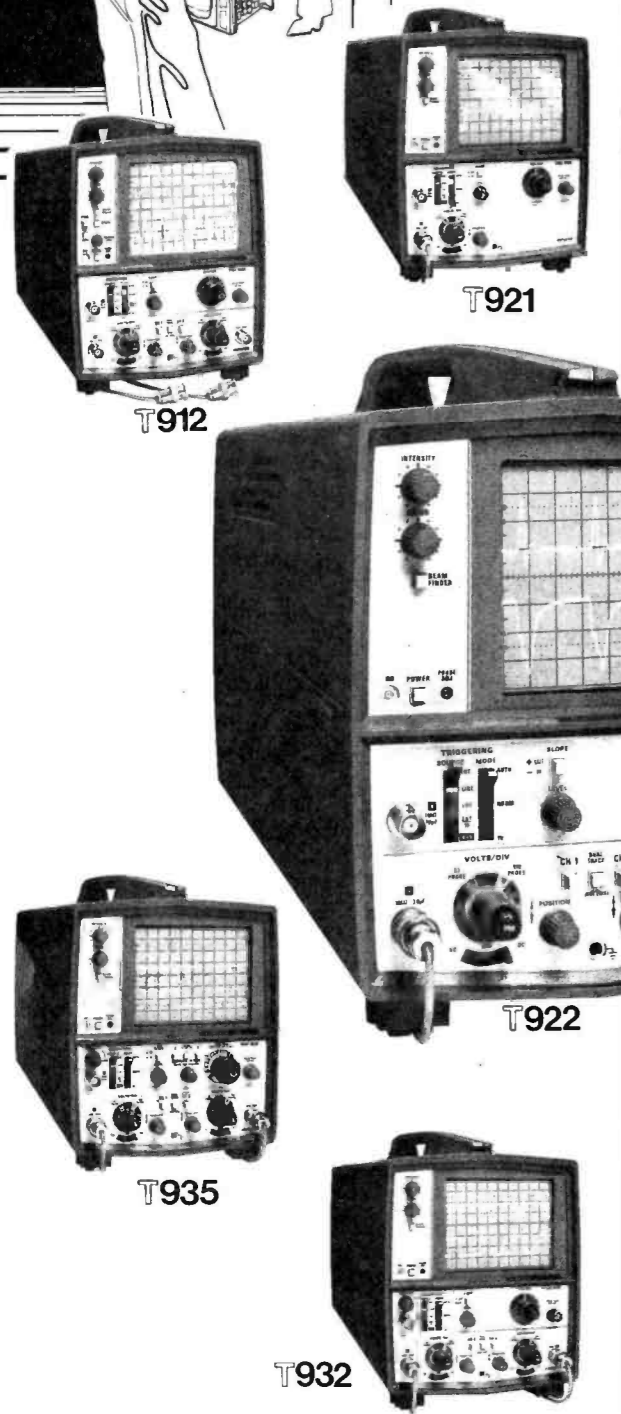

WORLD'S LARGEST SELLING ELECTRONICS MAGAZINE

FEATURE ARTICLES

- HERE COME THE HOME VIDEO DISCS Ken Winslow 38
How three leading video disc systems work.
- A NEW INDUSTRY STANDARD FOR FM TUNER MEASUREMENT, PART I Len Feldman 50
Details on what new FM tuner specifications mean.
- ENGLISH-LANGUAGE SHORTWAVE BROADCASTS FOR NOV. THRU FEB. Richard E. Wood 99

CONSTRUCTION ARTICLES

- THE FIRST MOTOROLA/AMI "6800" MPU COMPUTER PROJECT H. Edward Roberts & Paul Van Baalen 33
Compact size, easy construction, TTY interface, and low cost.
- THE OSCILLOSCOPE GRAPHIC ARTIST Mitchell Waite 53
Generates exciting, three-dimensional patterns.
- BUILD A PREREGULATED POWER SUPPLY G.R. Baumgras 58
Super-stable, multi-purpose supply for the experimenter's workbench.
- BUILD AN AUTOMOBILE LOGIC ALARM Robert Grater 61
Monitors five electrical points; sounds an alarm when wrong conditions occur.

COLUMNS

- STEREO SCENE Ralph Hodges 22
Clearing Up Some Odds And Ends.
- SOLID STATE Lou Garner 88
Calculator Chips For Other Circuits.
- CB SCENE Len Buckwalter 95
Speech Processing.
- DX LISTENING Glenn Hauser 98
What To Look For In a SW Receiver.
- COMPUTER BITS Jerry Ogdin 102
Software Tools.
- TEST EQUIPMENT SCENE Leslie Solomon 104
A Dual-Polarity DC Meter.
- HOBBY SCENE Q&A John J. McVeigh 105
- EXPERIMENTER'S CORNER Forrest M. Mims 109
The Light-Activated SCR.

PRODUCT TEST REPORTS

- IAD MODEL B3A DYNAMIC RANGE EXPANDER 68
- SHURE MODEL M95ED STEREO PHONO CARTRIDGE 72
- YAMAHA MODEL CR-800 AM/STEREO FM RECEIVER 73
- ELECTRA BEARCAT 101 "DIGITAL" SCANNING MONITOR 79
- LECTROTECH MODEL BG-10 COLOR GENERATOR 83

DEPARTMENTS

- EDITORIAL Art Salsberg 4
The Metrication Waiting Game.
- LETTERS 6
- NEW PRODUCTS 12
- NEW LITERATURE 16
- TIPS & TECHNIQUES 106
- OPERATION ASSIST 107
- ELECTRONICS LIBRARY 108
- ADVERTISERS INDEX 127

POPULAR ELECTRONICS, November 1975, Volume 8, Number 5, Published monthly at One Park Avenue, New York, NY 10016. One year subscription rate for U.S., \$6.98; U.S. Possessions and Canada, \$7.98; all other countries, \$8.98. Second Class postage paid at New York, NY and at additional mailing offices. Authorized as second class mail by the Post Office Department, Ottawa, Canada and for payment of postage in cash. Subscription service and Forms 3579; P.O. Box 2774, Boulder, CO 80302. POPULAR ELECTRONICS including ELECTRONICS WORLD, Trade Mark Registered. Indexed in the Reader's Guide to Periodical Literature. COPYRIGHT © 1975 BY ZIFF-DAVIS PUBLISHING COMPANY. ALL RIGHTS RESERVED.

Ziff-Davis also publishes Boating, Car and Driver, Cycle, Flying, Modern Bride, Popular Photography, Skiing and Stereo Review. Editorial correspondence: POPULAR ELECTRONICS, 1 Park Ave., New York, NY 10016. Editorial contributions must be accompanied by return postage and will be handled with reasonable care; however, publisher assumes no responsibility for return or safety of manuscripts, art work, or models. Forms 3579 and all subscription correspondence: POPULAR ELECTRONICS, Circulation Dept., P.O. Box 2774, Boulder, CO 80302. Please allow at least eight weeks for change of address. Include your old address, enclosing, if possible, an address label from a recent issue.

EDGAR W. HOPPER
Publisher

ARTHUR P. SALSBERG
Editorial Director

LESLIE SOLOMON
Technical Editor

JOHN R. RIGGS
Managing Editor

ALEXANDER W. BURAWA
Associate Editor

EDWARD I. BUXBAUM
Art Director

JOHN McVEIGH
Assistant Editor

ANDRE DUZANT
Technical Illustrator

HERBERT S. BRIER
LEN BUCKWALTER
LOU GARNER
GLENN HAUSER
JULIAN D. HIRSCH
RALPH HODGES
ART MARGOLIS
FORREST MIMS
JERRY OGDIN
WILFRED M. SCHERER
Contributing Editors

JOSEPH E. HALLORAN
Advertising Director

JOHN J. CORTON
Advertising Sales

LINDA BLUM
Advertising Service Manager

PEGI McENEANEY
Executive Assistant

STANLEY NEUFELD
Associate Publisher

ZIFF-DAVIS PUBLISHING COMPANY
Popular Electronics
Editorial and Executive Offices
One Park Avenue New York, New York 10016
212-725-3500

Hershel B. Sarbin, President
Furman Hebb, Executive Vice President
Vincent Perry, Financial Vice President and Treasurer
Phillip T. Heffernan, Senior Vice President, Marketing
Edward D. Muhlfeld, Senior Vice President, Sports Division
Philip Sine, Senior Vice President
Frank Pomerantz, Vice President, Creative Services
Arthur W. Butzow, Vice President, Production
Lawrence Sporn, Vice President, Circulation
George Morrissey, Vice President
Sydney H. Rogers, Vice President
Sidney Holtz, Vice President
Charles B. Seton, Secretary
Edgar W. Hopper, Vice President, Electronics Div.

William Ziff, Chairman
W. Bradford Briggs, Vice Chairman

Midwestern Office
The Pattis Group, 4761 West Touhy Ave.,
Lincolnwood, Illinois 60644, 312 679-1100
GERALD E. WOLFE, THOMAS HOCKNEY
Western Office
9025 Wilshire Boulevard, Beverly Hills, CA 90211
213 273-8050; BRadshaw 2-1161
Western Advertising Manager, BUD DEAN

Japan: James Yagi
Oji Palace Aoyama: 6-25, Minami Aoyama
6 Chome, Minato-Ku, Tokyo 407-1930/6821,
582-2851



The publisher has no knowledge of any proprietary rights which will be violated by the making or using of any items disclosed in this issue.



Editorial

THE METRICATION WAITING GAME

Although Congress has not as yet passed a bill dealing with adoption of the metric system in the U.S., the changeover from our present English system is inevitable. After all, about 90% of the world's population with 75% of world trade uses the metric system. And with good reason! It's simpler and faster to deal with multiples and subdivisions of 10 than it is with units of 12.

Of course, the U.S. has been "going metric" for many years, although the use of the system has been more of an incursion than an adoption. For example, we employ the metric system for radio wavelengths, electrical measurements, medical prescriptions, and in photography. We even use it for hi-fi pickup tracking force—2 grams, 1 gram, etc.

Comparing the values of one standard with that of another is always awkward. For instance, 1 gram would translate to 1/28 ounce. In a turnabout, 7 1/2 inches per second, a common U.S. tape recorder speed, is equivalent to 19.05 centimeters per second. Clearly, the nice even numbers occur with the standard that is dominant. The equivalent is generally complicated. For international trade purposes, however, many manufacturers "design" metric. That's why you see many cabinets and enclosures that measure fractionally, such as 14 3/16 inches instead of a nice round 14 1/2 inches. The former measures 36 centimeters on the button!

There are many conversion tables around to compare a value in English to that of metric, and vice-versa. Metric conversion calculators are abundant, too. Moreover, there are factors to simplify conversion that are as easy as π to use ($2.54 \text{ cm} = 1 \text{ in.}$; $1 \text{ kg} = 2.2 \text{ lb.}$). But when you get right down to it, one must eventually choose a system to the exclusion of all others so that even numbers predominate. Most countries employed a changeover period from English to metric, with highway signs reading both miles and kilometers, as an example.


The first country to go metric, France, had a 25-year dual system program starting in 1812 before metric became compulsory in 1837. Our defeated U.S. Metrication Bill had a 10-year changeover period.

Interestingly, Thomas Jefferson, when Secretary of State, recommended in 1790 that Congress introduce a decimal system; President John Quincy Adams advocated adoption of the metric system in 1821; Congress passed a law in 1866 making the metric system legal for those wishing to use it. Nearly 110 years later, however, the U.S. is the only major industrial nation in the world that uses the outmoded English system of weights and measures!

For a country that is a major participant in world trade, the delay in converting to metric is abhorrent. It means that a product cannot be made for universal distribution. Equally distressing, there is no serious move in our schools to teach upcoming generations the system of weights and measures that must ultimately be adopted.

Art Salsberg

4K Computer!

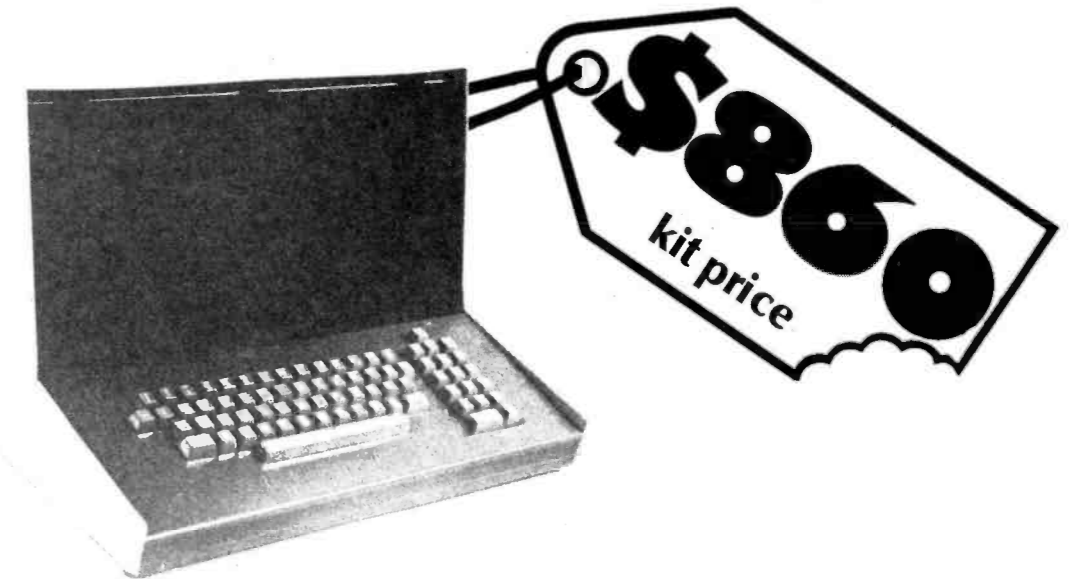

Still, our price goes down a lot easier.

Now's your chance to bite into a complete computer system. We at SPHERE CORPORATION have used the latest micro-processing technology along with some real innovations in mini-circuit design to develop the lowest-cost complete computer systems available. Every system comes complete with TV CRT display, ROM monitor, a real time clock, and typewriter, cursor editing, and numeric keyboards. Every SPHERE SYSTEM has ample memory to run YOUR particular program, whether it's a complicated inventory control system, or keeping detailed track of finances, or monitoring and protecting your home or office... use your imagination! And SPHERE offers manuals with plenty of information for the

first-time computer users. In addition, every SPHERE SYSTEM is expandable as desired. It will run an extended BASIC compiler and/or a most complete line of peripherals. All systems come with complete usage, programming, and application manuals, as well as software supports to make its functions almost limitless. We wanted to make something a lot better; and we did!

The mail order offer you see here is limited. Take advantage of it! If you like, also inquire about our full color graphics CRT display, and SPHERE's most complete line of low-cost peripherals on the market today. Use the coupon below right away!


We make the difference count.

Dear SPHERE:
The facts I read here convinced me!

- Enclosed is my check or money order for \$860.00. Please rush me a SPHERE I System.
- Please rush me more details on your low-cost computer system and peripherals. (Specific questions, if any, are attached.)

Print Name: _____
Address: _____
City: _____
State, Zip: _____

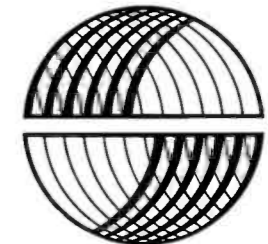SPHERE CORPORATION
791 South 500 West #4
Bountiful, Utah 84010
(801) 295-1368




SPHERE

SPHERE CORPORATION 791 South 500 West #4
Bountiful, Utah 84010 (801) 295-1368

Letters

USING DIODES WITH LOGIC PROBE

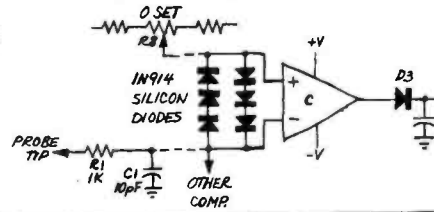In "Build a Universal Logic Probe" (February 1975), it is doubtful that the probe will perform well at frequencies near 10 MHz.



The diodes used to protect the inputs of the comparator IC are the bad guys. The capacitance of a typical zener diode is many times that of a typical switching diode. With the 1000-ohm value of $R1$ and approximately 560-pF capacitance of $D1$ and $D2$, there will be very little 10-MHz square-wave signal amplitude available at the comparator's inputs.

Far better results can be obtained if the zener diodes are each replaced with two or three switching diodes connected across the comparator's inputs as shown in my schematic.—W.E. PARKER, Columbus, Ohio

NOTES ON PROGRAMMING PROCEDURE

The 8223 PROM specifications sheet recommends a 390-ohm burn resistor, as opposed to the 39-ohm value specified in "How To Program Read-Only Memories" (July 1975). The exact magnitude difference between the two values makes me suspicious of the article's procedure.—Mark Coffman, Cincinnati, Ohio

I have a question on one of the steps for programming a PROM (page 30). The note in step 1 states: "NEVER operate S1 when S2 is set to BURN." If this is correct, there is no way to blow the fuses.—David Peterson, Edmonton, Alberta, Canada

It has been our experience that most PROM's need a great deal more burn current than is possible to obtain using a 390-ohm resistor. We experimented with a number of PROM's and found that 39 ohms is the optimum burn resistor value. The 390-ohm value failed to give the desired results. (Perhaps the PROM's we had, from several sources, were manufacturer fall-outs; if so, most of the PROM's our readers will be able to obtain are in this category.)

As for the note in step one of the programming procedure, it should read: "NEVER operate S1 when S2 is set to TEST."

RIPPLE CURRENT IN FILTER CAPACITORS

In "How to Design Your Own Power Supplies" (June 1975), no mention is made of the importance of not exceeding the ripple current rating of the capacitor. This factor cannot be ignored, particularly in low-voltage, high-current power supplies. Failure to consider the ripple current and its heating effect in the capacitor will severely shorten its life.—S.A. Romano, Brooklyn, N.Y.


The author replies that this is a good point to keep in mind if one finds heating in the filter capacitor. The ripple current may be what is causing it. Under normal loads and with full-wave and bridge systems, however, the typical capacitors available to experimenter should not present any problems.

Out of Tune

In "Build a Direct-Reading Logic Probe" (September 1975), in the Parts List, $DIS1$ should be a common-anode unit, not common-cathode.

It's your game.

\$350*
SPECIAL OFFER

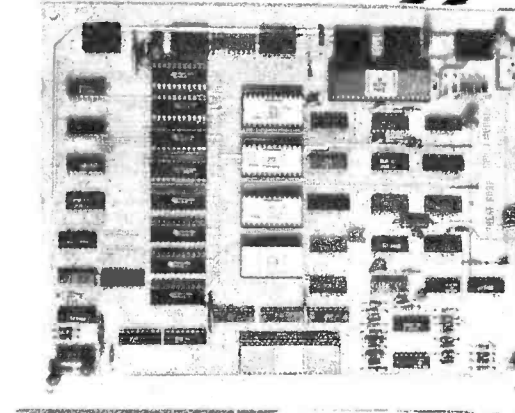

- real-time clock
- 16 digital I/O lines
- 4k RAM
- 512 times 8 PROM
- serial teletype interface
- hardwired ROM monitor (console emulator)

(Complete with usage, programming, and application manuals.)

Still, our price goes down a lot easier.

Take the SPHERE CPU board and you can name a game, play it, and invent your own. It is a totally programmable computer base for fun or serious use. Only real design innovation by the TEAM at SPHERE CORPORATION could make the advances in micro-processing technology that could increase the capabilities and bring the price down. There have been no compromises and no short cuts... look at the features! You might even be interested in the complete 4K computer system kit for \$860.00! In fact, we

at SPHERE have a whole line of fine micro-processing parts, kits, peripherals and even full-blown systems.

Take advantage of the special mail order offer on our CPU board, and get one board at the OEM's 100-quantity price complete with the 3 manuals as listed. Use the coupon and have it delivered right away. It's your game and we at SPHERE CORPORATION make the difference count!

* The Special OEM 100-quantity-price is extended to the hobby user for a single CPU board through mail order only. Offer ends without notice.

We make the difference count.

Dear SPHERE:

The facts I read here convinced me!

Enclosed is my check or money order for \$860.00. Please rush me a SPHERE I System.

Please rush me more details on your low-cost computer system and peripherals. (Specific questions, if any, are attached.)


Print Name: _____

Address: _____

City: _____

State, Zip: _____

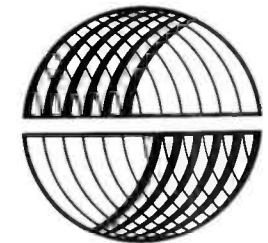SPHERE CORPORATION
791 South 500 West #5
Bountiful, Utah 84010
(801) 295-1368




SPHERE

SPHERE CORPORATION 791 South 500 West #5
Bountiful, Utah 84010 (801) 295-1368

PASS THE WORD... handic® SWEDEN'S SOLID CB IS HERE

"You've got to hear it to believe it!" Because Handic is committed to quality... not to gimmicks, frills or flashing lights. Our 23 channel rigs are designed in Sweden, where the climate is tough and operating conditions tougher... and where CB is more than just a convenience, it's a vital communications link!

With Handic, adjacent channel spillover problems are minimized — 60dB down @ 10KHz, not the usual 45dB down. Spurious emission is filtered down to 0.2 microvolts — 250% better than our own FCC requirements. (If all rigs were Handic, there would be a lot less TVII!) And Handic is required to maintain ±.003% crystal frequency tolerance in Sweden — exceeding our own FCC specs significantly. From "mic" to antenna, this is the kind of sophisticated circuitry found in every Handic rig. Remember, Handic CB's have their own special orange color... symbolic of CB excellence.

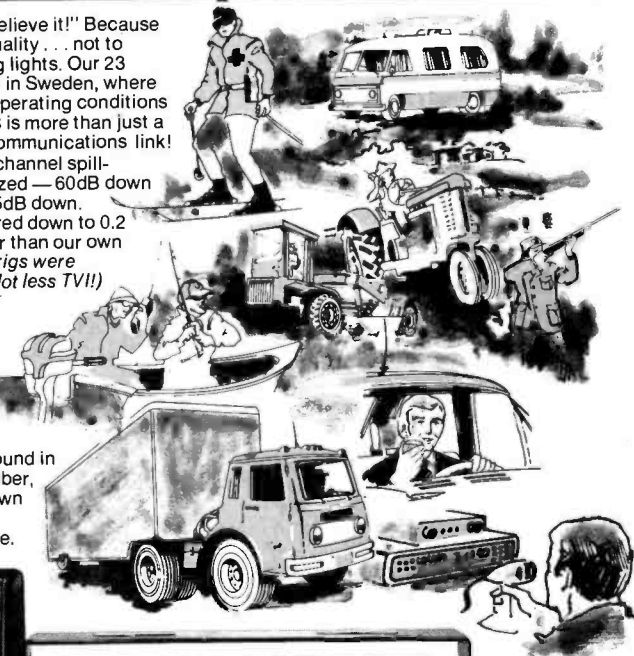

Handic CB radios include: mobile/base transceivers; handheld portables; scanners with FM radio option; antennas; microphones; selective call; and a full line of accessories.

handic U.S.A. Inc.

14340 N.W. 60th Ave., Washington Bldg. Miami Lakes, Fla. 33014 (305) 558-1522
In Canada: Scotcomm Radio Inc., Quebec

THE DEPENDABLE CB FROM SWEDEN

CIRCLE NO. 34 ON FREE INFORMATION CARD

Prepare for a high-paying career in Complete Communications

Including CB design, installation and maintenance...in actual practice



Get 2-way radio training with this solid-state 23-channel transceiver and power supply!



Your CB training will be up-to-the-minute when you experiment with this solid-state transceiver unit. Mount it in your car or use it with your AC power as a base station. You get "hands-on" experience that puts your course theory into practice the practical way.

The field of communications is bursting out all over. In Citizens Band alone, estimates predict a growth in equipment sales from \$514 million in 1973 to \$1.2 billion dollars in 1982! That means a lot of openings in service and maintenance jobs. NRI can train you at home to fill one of those openings...including your FCC license and solid-state 2-way radio service.

NRI's Complete Communications Course will qualify you for a First Class Commercial License or you get your money back! It covers AM and FM Transmission Systems, Teletype, Radar Principles, Marine Electronics, Mobile Communications, and Aircraft Electronics.

You will learn to service and/or adjust CB equipment...using your own 23-channel Johnson Transceiver and AC power supply for hands-on experience as well as your own personal use.

With NRI's training program, you can learn this important skill easily, at home in

your spare time. You get 8 training kits, including your own 3½ digit digital multimeter for digital experiments and precise measurements. You'll learn from bite-size lessons, progressing at your own speed to your FCC license and then into the communications field of your choice.



POPULAR ELECTRONICS

Only NRI offers five choices in TV/Audio Servicing




NRI can train you at home to service and repair commercially-built color and black-white TV, hi-fi equipment, AM-FM radios

Step into the digital age with NRI's Complete Computer Electronics Course



Digital electronics is the career area of the future...and the best way to learn it is with NRI's Complete Computer Electronics Course. You can become a computer or digital technician with NRI's unique and fascinating home training...while you build and use a real digital computer in your home! This is no beginner's "logic trainer". It's a complete programmable digital computer. And it's just one of ten kits you receive, including a professional digital multimeter for experiments it. It's the quickest and al logic, and computer

TV/Audio pro's choose NRI 2 to 1.

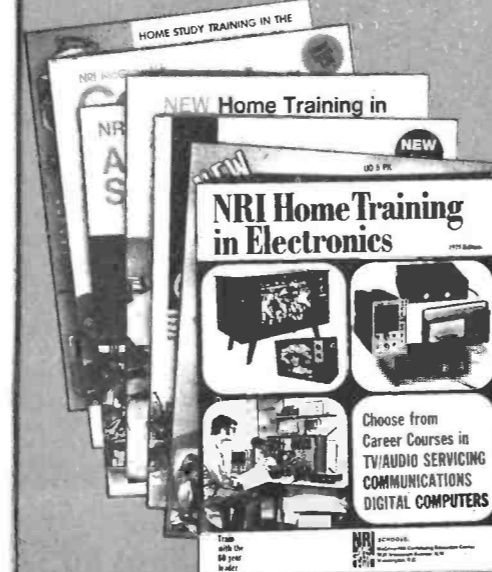

Rush this postage-paid card for your free catalog. No salesman will call.

- | | | |
|--|--|--|
| <input type="checkbox"/> TV/Audio Servicing | <input type="checkbox"/> Industrial & Business Electronics | <input type="checkbox"/> Automotive Mechanics |
| <input type="checkbox"/> Choose from 5 courses | <input type="checkbox"/> Digital Computer Electronics • Electronic Technology • Basic Electronics • Math for Electronics | <input type="checkbox"/> Master Automotive Technician • Tune-Up and Basic Repairs |
| <input type="checkbox"/> Complete Communications | <input type="checkbox"/> License • FCC | <input type="checkbox"/> Auto Air Conditioning & Refrigeration |
| <input type="checkbox"/> Electronics • Aircraft Electronics • Marine Electronics | <input type="checkbox"/> Homeowner & Professional Repairs | <input type="checkbox"/> Basic Air Conditioning |
| <input type="checkbox"/> Electronics | <input type="checkbox"/> Data Processing | <input type="checkbox"/> Servicing • Master Course in Air Conditioning, Refrigeration, & Heating |
| <input type="checkbox"/> Amateur Radio | <input type="checkbox"/> Basic Data Processing & Computer Programming | |
| <input type="checkbox"/> Basic and Advanced Courses | | |

Check here for GI Bill career information

Name _____ Age _____

Street _____ (Please Print)

City/State/Zip _____ Popular Electronics 1-115

STUDENTS IN 60 YEARS E THE NRI WAY...


Discover for yourself the best leader in home study will call. Do it today and your career.

GI BILL

Students are approved for veterans on card for details.

ORDER FOR CATALOG

Name will call

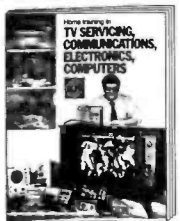

Continuing Education Center
10016

Prepare for a high-paying career in Complete Communications

Including CB design, installation and maintenance...in actual practice



Get 2-way radio training with this solid-state 23-channel transceiver and power supply!



The field of communications is bursting out all over. In Citizens B predict a growth in e \$514 million in 1973 to 1982! That means a lot and maintenance jobs. home to fill one of those c your FCC license and so service.

NRI's Complete Con will qualify you for a Fi License or you get your AM and FM Transmi type, Radar Principles, Mobile Communicati Electronics.

You will learn to serv equipment . . . using y Johnson Transceiver a for hands-on experienc personal use.

With NRI's trainin learn this important sk

McGraw-Hill Continuing Education Center
3939 Wisconsin Avenue
Washington, D.C. 20016

NRI Schools

BUSINESS REPLY MAIL
No postage necessary if mailed in the United States
Postage will be paid by

FIRST CLASS
PERMIT
NO. 20-H
WASHINGTON
D.C.

NRI gives you more training for your money.

Fully Staffed . . . NRI is one of the few home study schools that maintains its own full-time staff of technical writers, editors, development engineers, and instructors. The people who design the kits also design the lessons.

Wide Selection . . . Only NRI offers you a choice of five different courses in TV servicing to match your needs and budget. Plus courses in Communications, Digital Computer Electronics, and more.

Reasonable Costs . . . NRI employs no salesmen. All courses are offered by mail, we pass the savings on to you in the form of more training kits and equipment and savings up to \$650 on comparable courses.

Mail postcard now for free catalog.



Only NRI offers five choices in TV/Audio Servicing



NRI can train you at home to service and repair commercially-built color and black-white TV, hi-fi equipment, AM-FM radios and sound systems. You can choose from 5

courses, starting with a basic servicing course with 65 lessons . . . up to a Master Color TV course, complete with 25" diagonal solid state color TV in handsome woodgrain cabinet. All courses are available with low down payments and convenient monthly payments to fit your budget. And all courses provide professional equipment along with NRI-designed kits for hands-on training. With the Master Course, for instance, you receive your own 5" wide band, solid-state triggered sweep oscilloscope, TV pattern generator, 3½ digit digital multimeter, and a high quality NRI 25" diagonal solid state television receiver expressly designed for color TV training.

YOU PAY LESS WITH NRI TRAINING AND YOU GET MORE FOR YOUR MONEY

NRI employs no salesmen, pays no commissions. We pass the savings on to you in reduced tuition costs and extras in the way of professional equipment, testing instruments, etc. You can pay more, but you can't get better training.

NOVEMBER 1975

Step into the digital age with NRI's Complete Computer Electronics Course



Digital electronics is the career area of the future . . . and the best way to learn it is with NRI's Complete Computer Electronics Course. You can become a computer or digital technician with NRI's unique

and fascinating home training . . . while you build and use a real digital computer in your home! This is no beginner's "logic trainer". It's a complete programmable digital computer. And it's just one of ten kits you receive, including a professional digital multimeter for experiments and precise measurement. It's the quickest and best way to learn digital logic, and computer operation.

NEARLY ONE MILLION STUDENTS IN 60 YEARS HAVE LEARNED AT HOME THE NRI WAY . . .


Mail the insert card and discover for yourself why NRI is the recognized leader in home study training. No salesman will call. Do it today and get started on that new career.

APPROVED UNDER GI BILL


For the career minded, we are approved for veterans benefits. Check box on card for details.

MAIL THE INSERT CARD FOR YOUR FREE NRI CATALOG

No salesman will call

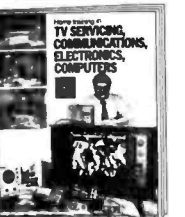

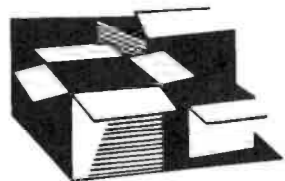NRI SCHOOLS
McGraw-Hill Continuing Education Center
3939 Wisconsin Avenue,
Washington, D.C. 20016



New Products

Additional information on new products covered in this section is available from the manufacturers. Either circle the item's code number on the Reader Service Card inside the back cover or write to the manufacturer at the address given.

ROTEL AM/FM STEREO TUNER

The Model RT-824 AM/FM Stereo Tuner by Rotel has a dual-gate MOSFET front end, an IHF sensitivity of 1.6 μ V, a tuned r-f AM section, and a phase-locked-loop multiplex detector. A wide linear-scale dial and flywheel tuning are included for easy operation. A muting switch selects thresholds of 30 or 50 μ V, or deactivates the muting



circuit. Two tuning meters facilitate proper tuning. The tuner also includes an FM stereo indicator lamp and an amplifier for headphone listening. An FM detector output jack can provide a composite signal for a four-channel decoder. \$359.95.

CIRCLE NO. 86 ON FREE INFORMATION CARD

B.X. & L. AMPLIFIER DELAY SWITCH

The AMP-LAY-SWITCH™ amplifier delay switch by B.X. & L. Industries is a solid-state switching device that automatically turns off an amplifier at a preset time after an automatic turntable has played its last record. Time delays from 0 seconds to two hours are possible. Since both the amplifier and turntable are plugged into the AMP-LAY-SWITCH, the unit can serve as a master switch for the entire system. A manual/delay switch is included. \$79.95. Address: B.X. & L. Industries, Inc., 17905 Sky Park Blvd., Irvine, CA 92707.

ADC "NEW MILFORD I" SPEAKER SYSTEM

The New Milford I is part of a series of loudspeakers developed by Audio Dynamics Corp. According to ADC, the speakers have been engineered with emphasis on "uniform energy response," which considers the listening room as an important speaker parameter. ADC claims that such speakers produce a uniformly flat

energy output/frequency bandwidth characteristic, minimizing problems of critical speaker or listener location within the room. The New Milford I is a 3-way acoustic suspension system employing a 10-inch (25.4-cm), long excursion damped woofer which crosses over at 1500 Hz to a 2½-inch (6.4-cm) damped tweeter. Claimed energy response is 45 to 20,000 Hz \pm 3 dB. A contour control adjusts the half-power (3-dB) tweeter rolloff frequency. Minimum recommended amplifier power is 5 W rms. Measures 22½"H x 13"W x 11"D (57.2 cm x 33 cm x 27.9 cm). Weighs 35 lb (15.9 kg). Simulated walnut grained, non-resonant wood products cabinet. \$99.95.

CIRCLE NO. 87 ON FREE INFORMATION CARD


RCA DUAL-TRACE SCOPE ADAPTER

RCA's new Model WM-541A Dual Trace Adapter converts any triggered or recurrent-sweep oscilloscope to dual-trace operation for servicing audio, digital, and television circuits. The unit can provide additional traces for existing dual-trace scopes. Claimed frequency response is dc to 10 MHz, and display modes are channel A only, channel B only, or both A and B simultaneously (chopped or alternate). Ac and dc coupling are provided for both channels, as well as compensated 6-step (1, 2, 5 ratio) attenuators, separate variable sync-level control with polarity reversing switch, input and output BNC connectors, and vinyl-clad shielded case. COS/MOS integrated circuitry is said to yield a noise level of less than 10 mV, and a maximum signal output of 1 V (p-p). Maximum ac signal input is 50 V (p-p). Input impedance is 1 megohm shunted by 55 pF. The Model WG-400A direct/low capacitance probe is an option. The adapter measures 8¼" x 5¼" x 3¼" (21 cm x 13.3 cm x 8.3 cm) and weighs 3 lb (1.6 kg). \$108.00. Probe, \$15.00.

CIRCLE NO. 88 ON FREE INFORMATION CARD

CIRCUIT-BOARD WIRING KIT

The Solder-Wrap wiring kit, from Applied Manufacturing of Texas, uses a patented wiring wand to dispense heat-strippable wire between components (including IC's) mounted on a special circuit board. Once the wire is routed, connections are heated to remove wire insulation for soldering. This special "hobbyist kit" includes the pencil-shaped wiring wand, a cartridge containing 200 ft. (61 m) of #34 heat-

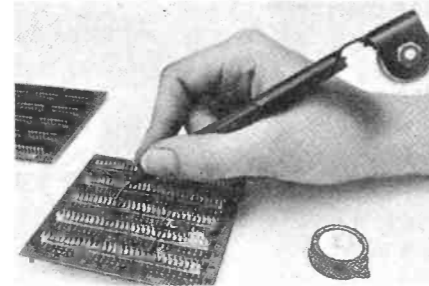

strippable wire, a circuit board with 15 IC positions and 10 insulating channels, and illustrated instructions. \$11.95. Address: Applied Mfg. of Texas, One Main Place, Box 50273, Dallas, TX 75250.

CRAIG CB MOBILE TRANSCEIVER

Craig's new Model 4103 mobile transceiver features a quick-release, anti-theft mounting system, crystal synthesizer providing 23 channels, and a 4-watt r-f output. Also



provided are an r-f gain control, delta tune, ceramic filter, voice compression circuitry, adjustable squelch, anl, and short-circuit protection for output transistors. A three-position ANL/NB/PA switch, a backlit S/R-SWR, and illuminated channel selector facilitate operations. A LED indicates that normal modulation is being achieved. The unit's detachable PTT dynamic mike comes with hanger and hardware. \$199.95.

CIRCLE NO. 89 ON FREE INFORMATION CARD

TELEX CB HEADSET WITH BOOM MIKE

Operating convenience is afforded by the Model CB 1200 boom mike headset by Telex Communications. Designed for the mobile or base station CB operator, it is a single-sided headset (for either ear) so that contact is not lost with the immediate environment. The dynamic, foam-cushioned earpiece is adjustable for maximum comfort. The boom microphone is also adjustable. A built-in FET amplifier, powered by a 1.4-volt mercury battery, matches the mike to any CB transceiver. An in-line PTT switch is supplied with clothing clip. The switch can be depressed momentarily for short messages or locked-in for longer transmissions. \$59.95.

CIRCLE NO. 90 ON FREE INFORMATION CARD

HEATHKIT STEREO MIKE MIXER

Heath's new Model TM-1626 stereo mixer is a low-cost console with stereo outputs, four high/low impedance mike inputs (one with pan control), two auxiliary inputs, and slide controls. Switches above each input level control assign that input to the left or right channel or switch it off. A pan control adjusts the apparent location of the fourth mike anywhere between extreme left and extreme right. A mixer bus allows paralleling of any number of TM-1626 units. A pair of lighted VU meters continuously monitor the outputs over two switch-selected ranges—+4 or 10 dB. Peaks are caught by

POPULAR ELECTRONICS

Another introductory offer to new members of the ELECTRONICS AND CONTROL ENGINEERS' BOOK CLUB

ANY ONE

of these great professional books
for only \$ **1.00**

VALUES FROM \$8.45 to \$37.45

Special \$1.00 bonus book
comes to you with your
first club selection

 404/445 ELECTRONIC CIRCUITS MANUAL by J. Markus Pub. price, \$22.00 Club price, \$15.75	 266/515 INTEGRATED CIRCUITS: A Basic Course for Engineers and Technicians by R. G. Hibberd Pub. price, \$10.25 Club price, \$8.45	 100/810 MOS/LSI DESIGN AND APPLICATION by Carr & Mize Pub. price, \$18.50 Club price, \$13.50	 238/901 APPLICATIONS OF OPERATIONAL AMPLIFIERS by J. G. Graeme Pub. Price, \$16.00 Club Price, \$10.50
 637/458 DESIGNING WITH TTL INTEGRATED CIRCUITS by Texas Instruments Inc. Pub. price, \$19.50 Club price, \$13.50	 388/458 MAGNETIC RECORDING by C. E. Lowman Pub. price, \$14.50 Club price, \$9.75	 287/341 STANDARD HANDBOOK OF ENGINEERING CALCULATIONS by T. G. Hicks Pub. price, \$19.50 Club price, \$14.25	 649/170 OPERATIONAL AMPLIFIERS by Tobey, Graeme & Huelsman Pub. price, \$15.00 Club price, \$11.50
 404/437 SOURCEBOOK OF ELECTRONIC CIRCUITS by J. Markus Pub. price, \$21.50 Club price, \$17.50	 389/756 SEMI-CONDUCTORS MEMORY DESIGN AND APPLICATION by Texas Instruments Inc. Pub. price, \$18.50 Club price, \$13.75	 124/035 HANDBOOK OF PHYSICS, 2/e by Condon and Odishaw Pub. price, \$37.45 Club price, \$14.95	 209/731 STANDARD HANDBOOK FOR ELECTRICAL ENGINEERS, 10/e by Fink and Carroll Pub. Price, \$38.50 Club Price, \$28.50
 491/364 THE DESIGN OF DIGITAL SYSTEMS by J. B. Peatman Pub. Price, \$18.50 Club Price, \$12.95	 353/387 MINICOMPUTERS FOR ENGINEERS & SCIENTISTS by G. Korn Pub. price, \$17.75 Club price, \$10.50		

Save time and money by joining the Electronics and Control Engineers' Book Club



HERE is a professional club designed specifically to meet your day-to-day engineering needs by providing practical books in your field on a regular basis at below publisher prices.

How the Club operates: Basic to the Club's service is its publication, the *Electronics and Control Engineers' Book Club Bulletin*, which brings you news of books in your field. Sent to members without cost, it announces and describes in detail the Club's featured book of the month as well as alternate selections which are available at special members' prices.

When you want to examine the Club's feature of the month, you do nothing. The book will be mailed to you as a regular part of your Club service. If you prefer one of the alternate selections—or if you want no book at all for that month—you notify the Club by returning the convenient card enclosed with each *Bulletin*.

As a Club member, you agree only to the purchase of four books over a two-year period. Considering the many books published annually in your field, there will surely be at least four that you would want to own anyway. By joining the Club, you save both money and the trouble of searching for the best books.

MAIL THIS COUPON TODAY

ELECTRONICS AND CONTROL ENGINEERS' BOOK CLUB
582 Princeton Road, Hightstown, New Jersey 08520

Please enroll me as a member of the Electronics and Control Engineers' Book Club and send me the two books indicated below. I am to receive the higher priced of the two for just \$1, and my first selection at the special Club price. Actual postage, plus 25¢ handling charge will be added (sales tax, also, if applicable). These books are to be shipped on approval, and I may return them both without cost or further obligation. If I decide to keep the books, I agree to purchase as few as four additional books (including this first selection) during the next two years at special Club prices (guaranteed 15% discount, often more).

Write Code No. of
bonus book
here

Write Code No. of
first selection
here

Name _____

Address _____

City _____

State _____ Zip _____

E33283

CIRCLE NO. 31 ON FREE INFORMATION CARD

Hewlett-Packard introduces a third scientific programmable:



the uncompromising HP-25. \$195.00*

Now you have three HP pocket programmables to choose from:

- the \$795.00* HP-65 Fully Programmable, with program recording capability;
- the \$335.00* HP-55 Advanced Scientific Programmable, with 86 preprogrammed functions and digital timer;
- the new, smaller HP-25 Scientific Programmable, with a price that brings programmability within the reach of everyone.

Here's what the new HP-25 offers you:

Keystroke programmability. The four-step answer to repetitive problems:

1. Turn the HP-25 on and switch to PRGM;
2. Enter the keystrokes necessary to solve the problem and switch to RUN;
3. Key in a set of variables and press the R/S (Run/Stop) key;
4. Repeat step three for each iteration.

You save time, gain precision and flexibility. You can verify formulas or test alternate approaches without sacrificing half a morning.

You do it in plain English. You don't need software or a "computer" language. You don't need prior programming experience.

Complete programmability. You can add, check, or change program steps at will. Just use the SST (Single-Step) or BST (Back-Step) key and Display to locate the steps you want to check or change, then enter your changes. The HP-25 displays *all* program steps, so you can *always* tell at a glance where you are in your routine. HP knows you can't edit in the dark.

The HP-25 even has a PAUSE key that lets you write one-second interruptions into your programs, in case you want to pick up intermediate results or verify the progress of a calculation.

In sum, the HP-25 is a complete keystroke programmable calculator, designed by engineers who've done it before. Twice.

Merged key codes. Each step in the HP-25's 49-Step Memory can accommodate multi-keystroke functions, because the keycodes of *all* prefixed functions—including the register arithmetic functions—merge. You gain extra capacity, just in case.

Branching and conditional test capability. You can program the HP-25 to perform direct branches or conditional tests based on eight different logic comparisons.

Eight storage registers and 72 preprogrammed functions and operations. All log and trig functions, the latter in degrees, radians or grads; rectangular-polar and decimal hours-hours/minutes/seconds conversions; mean and standard deviations; summations; register arithmetic on data in *all* registers; an integer/fraction key so you can store two numbers in one register; and all data manipulations.

Fixed decimal, scientific and engineering notation. You know the first two; the third is new to pocket calculators. Engineering notation freezes scientific notation into multiples of $10^{\pm 3}$, so you can convert to milli-, micro-, nano-, etc., without counting decimal places on your fingers.

RPN logic system with 4-register stack. Here's what this time- and error-saver means for you:

- You can evaluate any expression without copying parentheses, worrying about hierarchies or re-structuring beforehand.
- You can solve all problems your way—the way you first learned in Algebra I, the way you now use when you use a slide rule.
- You solve all problems, no matter how complex, one step at a time. You never work with more than two numbers at once.
- You see *all* intermediate answers *immediately*; the HP-25 executes each function immediately after you press the function key.
- You can backtrack when you err, because the HP-25 performs all operations sequentially.
- You can re-use numbers without re-entering them; the HP-25 becomes your scratch pad.

HP quality craftsmanship. One reason Nobel Prize winners, astronauts, conquerors of Everest, America's Cup navigators and over a million other professionals use HP calculators.

Free Applications Program Handbook. The price of the HP-25 includes a 125-page handbook that details solutions to a wide variety of problems. HP also offers many accessories designed specifically to help you get more out of the HP-25.

800-538-7922 (in Calif. 800-662-9862) are the numbers to call for the name of a dealer near you. He'll give you detailed specs, including a list of available accessories, and a "hands-on" demonstration that'll take about 15 minutes. Buy an HP-25, and you'll get them back. Every day you use it.

HEWLETT  PACKARD

Sales and service from 172 offices in 65 countries.
Dept. 254B, 19310 Pruneridge Avenue, Cupertino, CA 95014

615/21


*Suggested retail price, excluding applicable state and local taxes—Continental U.S., Alaska & Hawaii.

NOVEMBER 1975

CIRCLE NO. 35 ON FREE INFORMATION CARD

15

The \$300 alternative.

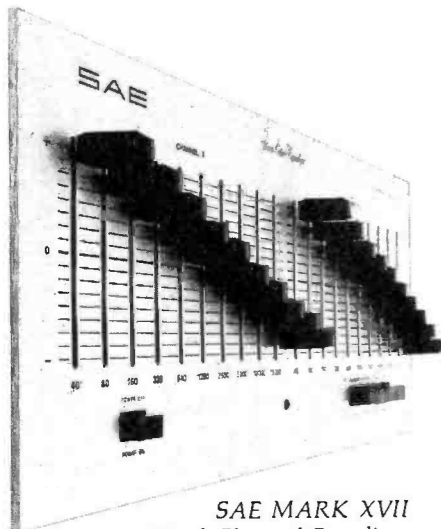

SAE MARK XVII
Dual-Channel Equalizer

Your tone controls are just not designed to compensate for

- Room acoustics
- Speaker placement
- Old or bad recordings

We built the Mark XVII Equalizer to solve these problems and more.

- These are some of the ways:
- Individual Octave Control for each channel
 - Long throw, oil-damped linear slide pots for greater accuracy
 - Dual range operation (controls operate over either $\pm 8\text{dB}$ or $\pm 16\text{dB}$)

Plus

- Capable of driving any system
- Low distortion—less than 0.03% THD and IM
- Low noise—greater than 90dB
- 5-year parts and labor service contract
- SAE's reputation as the finest manufacturer in the audio field

You'd have to look a long time to find an EQ that delivers this much value. SAE innovation has done it.


Components for the connoisseur.



Scientific Audio Electronics, Inc. PE11/75
P.O. Box 60271, Terminal Annex
Los Angeles, California 90060
Please send me the reasons (including available literature) why the SAE MARK XVII Dual-Channel Equalizer is the "\$300 Alternative."

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

CIRCLE NO. 64 ON FREE INFORMATION CARD

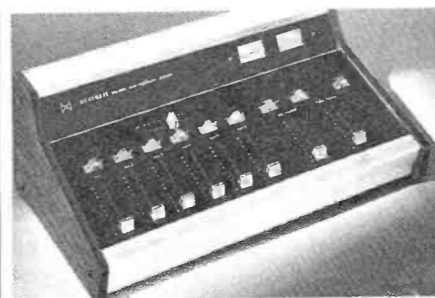

two LED's with adjustable thresholds. Claimed frequency response is 40-20,000 Hz $\pm 1\text{dB}$ with less than 0.5% THD up to 6.5 V output. Overload-resistant inputs are rated at 3.0 V (AUX), 900 mV (HI-Z MIKE) and 60 mV (LO-Z MIKE). \$129.95.

CIRCLE NO. 5 ON FREE INFORMATION CARD

PALM-SIZE CALCULATOR

Edmund Scientific's electronic calculator (Stock No. 1945) fits in your palm, but has an eight-digit readout with floating decimal, four arithmetic functions, automatic percentage key, lead zero suppression, and a constant key. The unit runs on two 1.5-V Mallory PX 825 camera batteries or equivalent (supplied with calculator). Measures 2.8" x 2" x 0.4" (7.1 x 5.1 x 1 cm) and weighs 2 oz (56.8 g). \$19.95.

CIRCLE NO. 91 ON FREE INFORMATION CARD

NON-LINEAR SYSTEMS DMM


A digital multimeter from Non-Linear Systems, the Model LM-3, offers three-digit readout and can be operated from either battery or line power (NiCd batteries and charger included). Small enough to be held in one hand, it has four ranges of ac and dc volts, and five resistance ranges from 1 kilohm to 1 megohm full-scale. Other features are automatic polarity and automatic zero, 10-megohm input impedance on all ranges, and a 0.33-inch (8.4-mm) LED display. Dimensions are 4" x 2.7" x 1.9" (10.2 x 6.9 x 4.8 cm). \$125.00.

CIRCLE NO. 92 ON FREE INFORMATION CARD

TDK HIGH-PERFORMANCE CASSETTE

A new high-fidelity cassette tape, called Super Avilyn, is being introduced by TDK. Avilyn is a patented mix of cobalt, ferric oxide and other proprietary elements. The new tape is said to combine advantages of ferric and chromium tapes, but overcomes inherent problems in both the straight and hybrid formulas currently available. Headwear is said to be the same as that from FeO₃ tapes (much lower than that of CrO₂ formulas). According to TDK, the Avilyn tape has better low- and middle-range response while equalizing the high-frequency response of chromium tapes. Its S/N is 0.5 to 1 dB better than CrO₂, and can be used with the standard chromium playback equalization time constant of 70 μs . The tape will retail for \$3.95 in C-60 format. A C-90 package will be introduced later.

CIRCLE NO. 93 ON FREE INFORMATION CARD

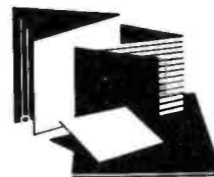

New Literature

JAMES MILLEN SHIELD DESIGN TIP

"Helpful Hints in the Design of a Magnetic Shield" is a 2-page engineering design tip describing how to shield sensitive devices from interference as well as how to shield devices that cause interference. Thickness and types of shielding materials are discussed, and degaussing procedures are given. Address: James Millen Manufacturing Co., Inc., 150 Exchange St., Malden, MA 02148.

ALTEC ENCLOSURE DESIGN MANUAL

"Loudspeaker Enclosures—Their Design and Use" is a 32-page manual containing data for use in designing and constructing enclosures for Altec loudspeakers. It discusses the function of the enclosure, speaker design theory, various types of enclosures, and how to tune a bass reflex port. Price is \$2.00. Address: Altec Corp., 1515 S. Manchester, Anaheim, CA 92803.

NATIONAL CAMERA TOOL CATALOG

The "NC Flasher" (80 pages) includes hard-to-find tools, technicians' supplies, laboratory and workshop equipment, etc. Among new items listed are a low-cost circuit tester, accessories for the "Grabber" test-lead system, and tools and instruments for the photo equipment repair technician. Address: Dept. ORR, National Camera, 2000 W. Union Ave., Englewood, CO 80110.

PROJECTOR-RECORDER BELT CATALOG

A catalog and reference chart from Projector-Recorder Belt Corp. lists over 650 types of belts, wheels, and rubber parts for over 2000 models of audio and video tape players and audio/visual projectors. The company also specializes in servicing belts and other drive parts. Address: Projector-Recorder Belt Corp., 147 Whitewater St., Whitewater, WI 53190.


WOODCRAFTING CATALOG

A 22-page catalog from Garrett Wade Co. describes their line of hardwood workbenches and tools for all types of wood-working projects, including building speaker and hi-fi equipment enclosures and record cabinets. Tools include those for carving, clamping, mitering, and measuring. Workbenches come in a variety of sizes and styles. Address: Garrett Wade Co., Dept. 16, 302 Fifth Ave., New York, NY 10001.

POPULAR ELECTRONICS



THE DESIGN MATE SERIES

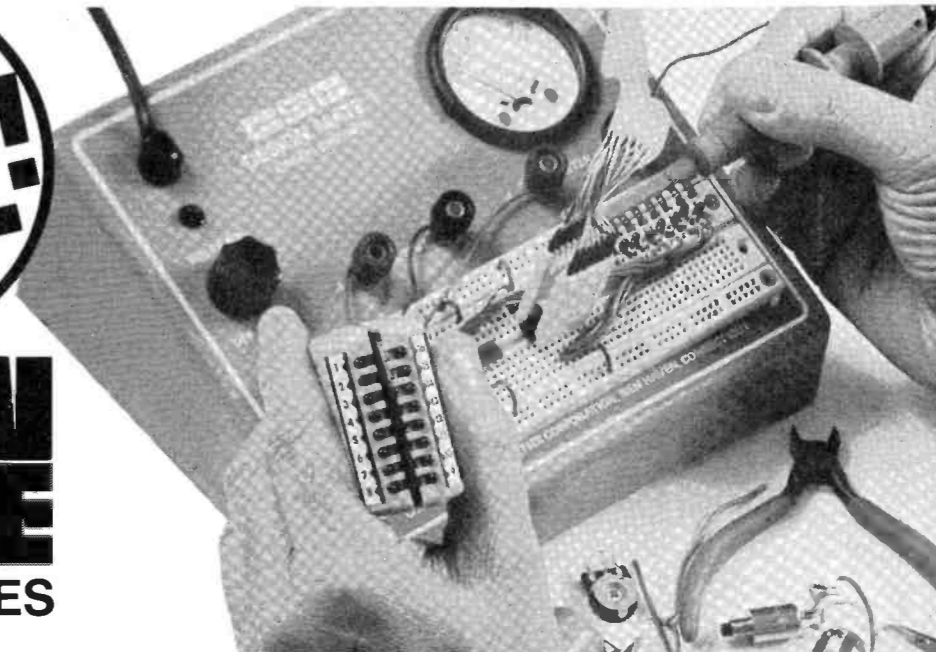

At last! High quality, laboratory-grade test instruments . . . for the professional and hobbyist . . . at prices everyone can afford!

DESIGN MATE 1

CIRCUIT DESIGNER

Now you can build/test electronic circuits WITHOUT SOLDER . . . using solid #22 AWG wire to interconnect discrete components . . . resistors, transistors, linear/digital ICs in TO5 or DIP packages (8-40 pins), and more. Plus, you get 5-15VDC up to 600ma (9 watts) of variable regulated power, with a built-in 0-15V voltmeter to monitor internal power and/or external circuits. Now, that's design flexibility! And look at the low, low price!

49⁹⁵

Add \$2.50 shipping/handling



SPECIFICATIONS


Power Supply: Output: 5-15V @ 600ma. Ripple and Noise: less than 20mv @ full load. Load/Line regulation: <1%. Meter: 0-15V DC. Connectors: 1 QT-59S, 2 QT-59B, 2 power supply 5-way binding posts, 2 meter 5-way binding posts. Wght: 3 lbs. Power Needed: 117V, AC @ 60 Hz 12W.* Patent #235,554.

Each measures 6.75" L x 7.5" W x 3.25" H.; completely assembled, ready to start testing at once. Order your DESIGN MATES today! *220V @ 50Hz available at slightly higher cost.

All DESIGN MATES are made in USA; available off-the-shelf from your local distributor. Direct purchases from CSC can be charged on Bank Americard, Master Charge, American Express. Plus, you get a FREE English/Metric Conversion Slide Rule with each order. Foreign orders please add 10% for shipping/handling. Prices are subject to change.

NOVEMBER 1975

64⁹⁵

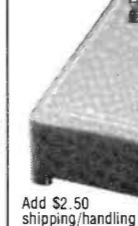

Add \$2.50 shipping/handling

DESIGN MATE 2

FUNCTION GENERATOR

Troubleshooting? Design Testing? DM-2 gives you all the signal source capacity you need . . . at a very modest price. This 3-wave form Function Generator has: short-proof output, variable signal amplitude and constant output impedance. Completely wired, tested, calibrated, ready to test audio amplifiers, op-amp and educational lab designs . . . as well as complex industrial lab projects. Complete with easy-to-read instructions/operations manual, application notes, operation theory and more, DM-2 works hand-in-hand with DM-1 for total versatility.

SPECIFICATIONS

Frequency Range: 1Hz-100KHz (5 ranges: 1-10Hz, 10-100Hz, 100-1000Hz, 1-10KHz, 10-100KHz). Dial Accuracy: Calibrated @ 10Hz, 100Hz, 1KHz, 10KHz, freq. accurate to 5% of dial setting. Wave Forms: Sine <2% THD over freq. range. Triangle wave linearity, <1% over range. Square wave rise/fall <0.5 microseconds — 600 Ω -20pf termination. Output Amplitude: (all wave forms) variable-0.1V-10V peak to peak into open circuit. Output Impedance: 600 Ω -constant over ampli./freq. ranges. Wght.: 2 lbs. Power Needed: 117V, AC @ 60Hz 5W.*

DESIGN MATE 3

R/C BRIDGE

Have you been bugged by color codes or unreadable component markings? Forget it! DM-3, the low cost R/C Bridge, measures true component values . . . in seconds . . . to better than 5%. And, it's all done with only 2 operating controls and a unique solid-state null detector, to zero-in on exact component selection . . . instantly! Completely wired, calibrated and tested, DM-3 includes an extensive instruction/applications manual, and operational theory too.

SPECIFICATIONS

Resistance Range: 10 Ω -100 meg Ω . (6 Ranges: 10-100 Ω , 100-1000 Ω , 1K-10K Ω , 100K-1 meg Ω , 1 meg Ω -10 meg Ω) Capacitance Range: 10pFd-1mFd (5 Ranges: 10-100 pFd, 100-1000pFd, .001-.01 mFd, .01mFd-.1mFd, .1-1mFd.) Null Detector: 2 hi-intensity LEDs-hi/lo markings. Accuracy: <5% of null dial, range switch setting. Wght. 2 lbs. Power Needed: 117V, AC @ 60Hz 3W.*

54⁹⁵

Add \$2.50 shipping/handling



CSC CONTINENTAL SPECIALTIES CORPORATION


44 Kendall Street, Box 1942, New Haven, CT 06509 • 203/624-3103
West Coast Office: Box 7809, San Francisco, CA 94119 • 415/421-8872
Canada: Len Finkler Ltd., Ontario

© Copyright Continental Specialties Corporation 1975

CIRCLE NO. 23 ON FREE INFORMATION CARD

You gain new skills as an electronics troubleshooter in a fascinating learn-at-home program from Bell & Howell Schools. It includes building and experimenting with the new generation color TV.

go exploring.

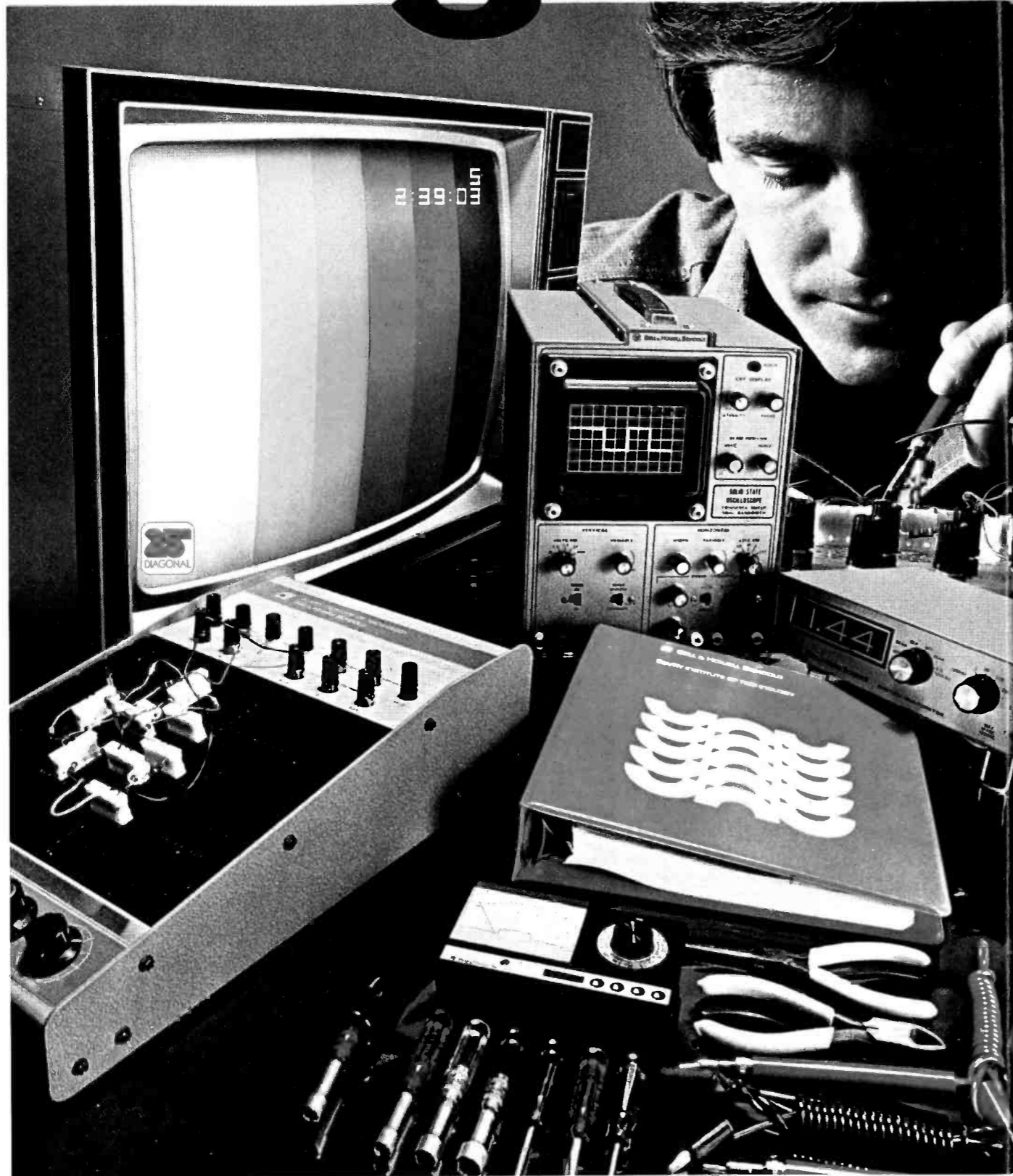

If you're like most men, deep down inside there's still a bit of the boy who loved to go exploring... and who'd love to go again. Well, now you can.

Only this time you'll explore the expanding world of electronics... a world more fascinating than any you ever dreamed of as a boy.

Learn by exploring... Bell & Howell Schools offers an exciting way for you to gain new occupational skills in electronics.

Everybody enjoys learning something new, but why learn it the old way? Classes to go to. Lectures to sit through. And only a bunch of books to keep you interested.

Bell & Howell Schools' adventure in learning is a far cry from all that.

You can probe into electronics and learn exciting new occupational skills right in your own home, in your spare time. On whatever days and whatever hours you choose. So there's no need to give up your present job and paycheck just because you want to learn something new.

What's more, when you're exploring a field as fascinating as electronics, reading about it is just not enough. That's why throughout this program you'll get lots of "hands on" experience with some of today's latest electronic training tools.

You'll be stimulated for hours on end as you build, experiment and learn while using the latest ideas and techniques in this fascinating field.

As part of the program you'll actually learn to build and work with your own electronics laboratory. Using it to put many of today's most dynamic electronic discoveries to the test... including electronic miniaturization.

Among the things you'll discover is how the

you'll build:

1. A design console, for setting up and examining circuits.
2. A digital multimeter for measuring voltage, resistance and current (it displays its findings in big, clear numbers like a digital clock).
3. A solid-state "triggered sweep" oscilloscope—similar in principle to the kind used in hospital operating rooms to monitor heartbeats. You'll use it to monitor the "heartbeats" of tiny integrated circuits. The "triggered sweep" feature locks in signals for easier observation.

Step-by-step you'll build and experiment with Bell & Howell's new generation color TV—investigating digital features you've probably never seen before!

This 25" diagonal color TV has digital features that are likely to appear on all TV's of the future. As you build it you'll probe into the technology behind all-electronic tuning. And into the digital circuitry of channel numbers that appear right on the screen! You'll also build in a remarkable on-the-screen digital clock, that flashes the time in hours, minutes and seconds. Your new skills will enable you to program a special automatic channel selector to skip over "dead" channels and go directly to the channels of your choice.

You'll also gain a better understanding of the exceptional color clarity of the Black Matrix picture tube, as well as a working knowledge of "state of the art" integrated circuitry and the 100% solid-state chassis.

After building and experimenting with this TV, you'll be equipped with the skills that could put you ahead of the field in electronics know-how.

We try to give more personal attention than other learn-at-home programs.

Should you ever run into a problem, we'll be there to help. You mail in your questions, we answer them in 24 hours. Questions that can't wait. These are held in 50 major cities throughout the year where you can meet instructors and fellow students.

Background needed.

All you really need is the thing you've never lost. A boy's love for electronics. Now you can go again, and learn new technical skills all along the way.

Order your postage-paid card today for more details!

For vocational purposes, this program is approved by the state approval agency for Veterans' Benefits.

If you have been removed, write:

Electronics Home Study School
DEVRV INSTITUTE OF TECHNOLOGY
ONE OF THE
BELL & HOWELL SCHOOLS
Belmont, Chicago, Illinois 60641

PLUG IN to the adventure of electronics

Yes, I'd like to hear more about Bell & Howell Schools' fascinating home learning adventure in electronics. See that I receive more information!

Name _____ (Please print)

Address _____

City _____ State _____ Zip _____

Phone _____ Age _____


Taken for vocational purposes, this program is approved by the state approval agency for Veteran's Benefits. Check here for information. 189S1

An Electronics Home Study School
DEVRV INSTITUTE OF TECHNOLOGY
ONE OF THE
BELL & HOWELL SCHOOLS
4141 Belmont, Chicago, Illinois 60641

1-5A0148A


MAIL POSTAGE FREE CARD TODAY!

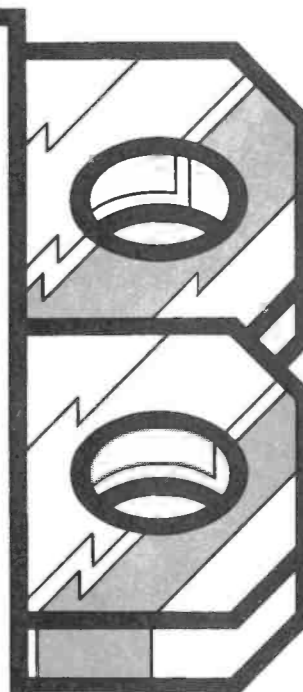Popular Electronics DETACH HERE AND MAIL TODAY



You gain new skills as an electronics troubleshooter in a fascinating learn-at-home program from Bell & Howell Schools. It includes building and experimenting with the new generation color TV.

go exploring.

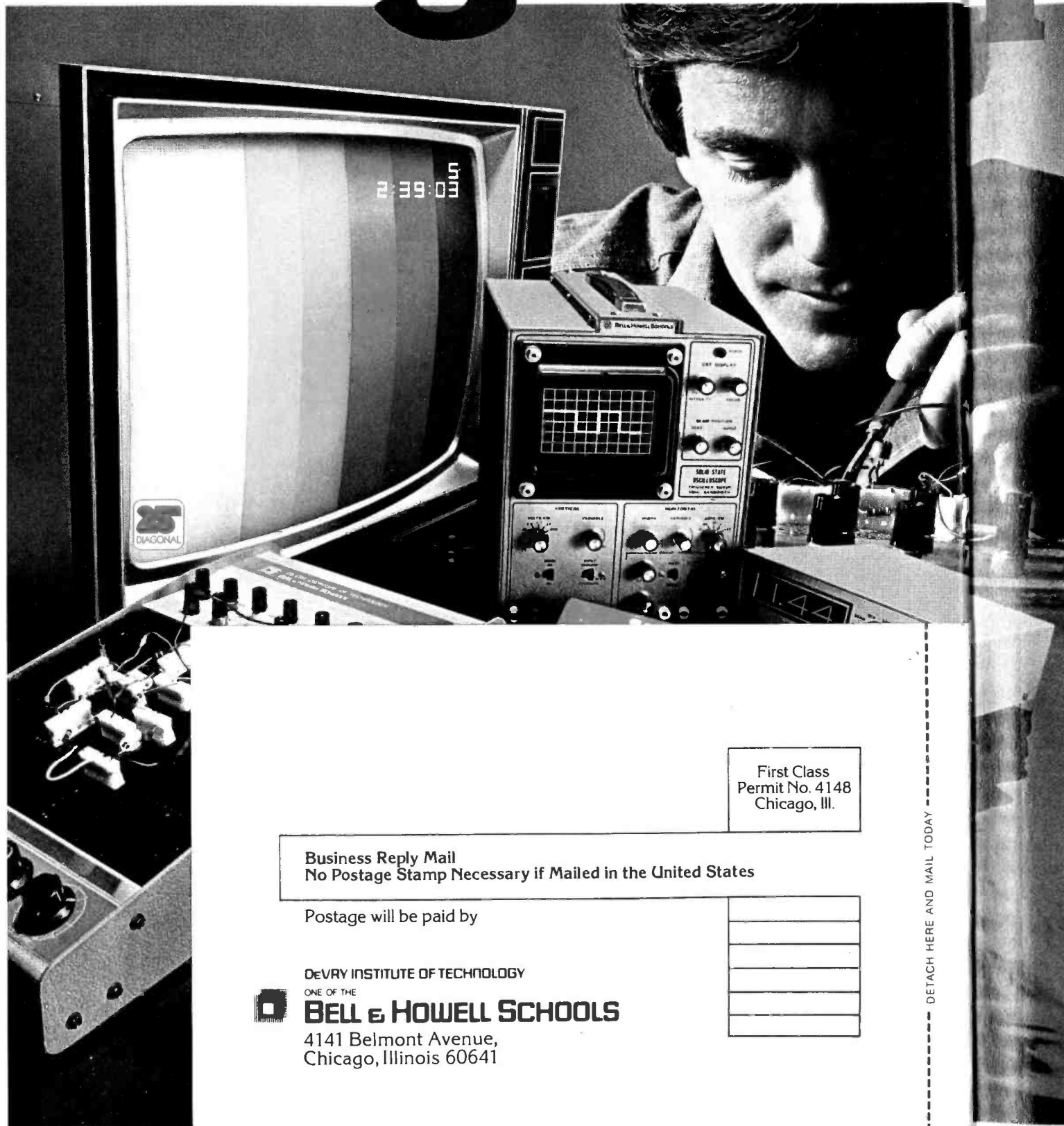

If you're like most men, deep down inside there's still a bit of the boy who loved to go exploring... and who'd love to go again. Well, now you can.

Only this time you'll explore the expanding world of electronics... a world more fascinating than any you ever dreamed of as a boy.

Learn by exploring... Bell & Howell Schools offers an exciting way for you to gain new occupational skills in electronics.

Everybody enjoys learning something new, but why learn it the old way? Classes to go to. Lectures to sit through. And only a bunch of books to keep you interested.

Bell & Howell Schools' adventure in learning is a far cry from all that.

You can probe into electronics and learn exciting new occupational skills right in your own home, in your spare time. On whatever days and whatever hours you choose. So there's no need to give up your present job and paycheck just because you want to learn something new.

What's more, when you're exploring a field as fascinating as electronics, reading about it is just not enough. That's why throughout this program you'll get lots of "hands on" experience with some of today's latest electronic training tools.

You'll be stimulated for hours on end as you build, experiment and learn while using the latest ideas and techniques in this fascinating field.

As part of the program you'll actually learn to build and work with your own electronics laboratory. Using it to put many of today's most dynamic electronic discoveries to the test... including electronic miniaturization.

Among the things you'll discover is how the development of tiny integrated circuits has made possible an electronic calculator small enough to fit into a shirt pocket! And a wristwatch that flashes the time with the push of a button.

You'll investigate the concept of "logic circuits." An idea that has been with us for centuries but only in recent years put to use as the "brain" behind all the new digital consumer appliances we see today.

But more important than anything else is the new occupational skills you'll develop in electronics troubleshooting. While no assurance of income opportunities can be offered, you'll develop skills that could lead you in exciting new directions. Use your training:

1. To seek out a job in the electronics industry.
2. To upgrade your current job.
3. As a foundation for advanced programs in electronics.

You build and perform many exciting experiments with Bell & Howell's Electro-Lab[®] an exclusive electronics training system.

Using our successful step-by-step method,

you'll build:

1. A design console, for setting up and examining circuits.
2. A digital multimeter for measuring voltage, resistance and current (it displays its findings in big, clear numbers like a digital clock).
3. A solid-state "triggered sweep" oscilloscope—similar in principle to the kind used in hospital operating rooms to monitor heartbeats. You'll use it to monitor the "heartbeats" of tiny integrated circuits. The "triggered sweep" feature locks in signals for easier observation.

Step-by-step you'll build and experiment with Bell & Howell's new generation color TV—investigating digital features you've probably never seen before!

This 25" diagonal color TV has digital features that are likely to appear on all TV's of the future. As you build it you'll probe into the technology behind all-electronic tuning. And into the digital circuitry of channel numbers that appear right on the screen! You'll also build in a remarkable on-the-screen digital clock, that flashes the time in hours, minutes and seconds. Your new skills will enable you to program a special automatic channel selector to skip over "dead" channels and go directly to the channels of your choice.

You'll also gain a better understanding of the exceptional color clarity of the Black Matrix picture tube, as well as a working knowledge of "state of the art" integrated circuitry and the 100% solid-state chassis.

After building and experimenting with this TV, you'll be equipped with the skills that could put you ahead of the field in electronics know-how.

We try to give more personal attention than other learn-at-home programs.

1. Toll-free phone-in assistance. Should you ever run into a rough spot during the program, we'll be there to help. While many schools make you mail in your questions, we have a toll-free line for questions that can't wait.
2. In-person "help sessions." These are held in 50 major cities at various times throughout the year where you can talk shop with your instructors and fellow students.

No electronics background needed.

What you really need is the thing you've never lost. A boy's love for exploring. Now you can go again, only this time learning new occupational skills all along the way.

Mail the postage-paid card today for more details!

Taken for vocational purposes, this program is approved by the state approval agency for Veterans' Benefits.

If card has been removed, write:

An Electronics Home Study School
DeVRY INSTITUTE OF TECHNOLOGY
ONE OF THE
BELL & HOWELL SCHOOLS
4141 Belmont, Chicago, Illinois 60641



Simulated TV test pattern.

"Electro-Lab[®]" is a registered trademark of the Bell & Howell Company.


First Class
Permit No. 4148
Chicago, Ill.

Business Reply Mail
No Postage Stamp Necessary if Mailed in the United States

Postage will be paid by

DeVRY INSTITUTE OF TECHNOLOGY
ONE OF THE
BELL & HOWELL SCHOOLS
4141 Belmont Avenue,
Chicago, Illinois 60641

DETACH HERE AND MAIL TODAY

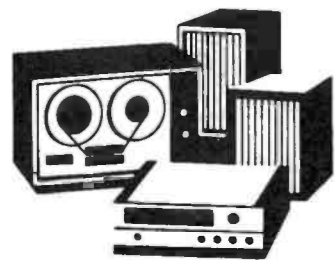

Stereo Scene

By Ralph Hodges

CLEARING UP SOME ODDS AND ENDS

THIS month's column will consist mainly of a few curiosities and conundrums that have kept my mind occupied for the past several weeks, but about which I don't expect to learn much more in the near future. Therefore, it's time to be out with them.

The Omni Question. A long-standing controversy surrounds the use of wide-dispersion or omnidirectional ("omni") loudspeakers in stereo installations. The stereo image provided by omni's, say their detractors, is vague, wandering, diffuse, and sometimes grossly distorted (as when a single instrument, which should have a small, sharply localized apparent source, grows to fill much of the space between the speakers). This is usually attributed to the wealth of reflected sound that omni's provide, creating an incalculable number of secondary sound sources in the vicinity of the speakers where the sound bounces off the walls or ceiling.

Reputedly, the true test of a loudspeaker's stereo capability—and it's certainly a theoretically logical one—is whether a pair of them, reproducing an in-phase mono signal, can develop a "stereo" image that is exactly front-and-center and rock solid, with no lateral spread whatever. This is not an easy test for many speaker systems, as it turns out.

Over the years I've come to share some of these misgivings, although not without reservations. For one thing, the anti-omni faction has handed down a blanket indictment of all such speakers, which instinct and experience tell me is unjust. Omni's differ. There is the Walsh-Ohm sort of device that should behave very much like a vertical line radiator and is inherently omnidirectional in the lateral plane. Then there is the distributed-source configuration in which drivers may be studded on all available surfaces of the cabinet. To a real-time

spectrum analyzer integrating over short time increments, these would appear to be very different types of reproducers. To the ear itself, it's hard to predict what distinctions would be apparent.

But my major quibble with the omni detractors is on theoretical grounds. Oh, I know there's often something interesting going on—whether detrimental or not—when omni's are listened to, but I can't make the pat reflected-sound explanation jibe with what I understand to be the workings of the human ear. To enlarge: in the opinion of such august bodies as the Acoustical Society of America, the localization of a transient sound is likely to depend very much on the difference in arrival times of its very first onset at the two ears. If the left ear hears it a fraction of a millisecond before the right ear, then we're led to conclude that the source is somewhere to the left. In the case of sustained sounds for which onset time differences have not done the trick, we seem to depend on interaural phase differences for whatever localization is possible, provided the sound is below about 2,000 Hz. Above 2,000 Hz, which (interestingly) is the point where the wavelengths approach the distance between our ears, amplitude differences between the two ears appear to be dominant.

Now then, stereo is a contrived illusion that is typically achieved in complex ways, but it is certainly safe to say that, in terms of interaural onset-time differences (before any sound reflections have had a chance to reach us), omni's and more conventional speakers start out on an equal footing, and should "image" equally well.

It is true that a later-arriving reflection that is significantly stronger than the onset sound (not an impossibility if a speaker's free-field frequency response varies much at different angles) can overthrow the original lo-

calization, but such difficulties are not inherent in the omni approach. And when we consider phase and intensity differences, the situation is much the same. Properly worked-out omni's should be equivalent in integrity to conventional designs. But there remains another aspect of speaker behavior having to do with "togetherness" that might have some meaning here.

Time Smear. Because of the design of most crossover networks, and the nature of the drivers themselves, the separate elements of a multi-way speaker system tend not to respond to an input with equal alacrity. Usually the larger drivers are late, so that an input signal with a steep wavefront, like a square wave, would come out with its frequency components broken down according to which driver was handling them, and spread out over an appreciable time base. Not long ago someone dubbed this phenomenon "time smear"—definitely my favorite jargon phrase of the year—and it became a serious consideration in some speaker-evaluation schemes. The point is that a number of omni speakers, most especially the ones with multiple tweeters arranged so that you hear direct radiations from several of them, are going to exhibit more time smear than the usual case, because some tweeters will inevitably be nearer or farther than others. And, of course, the reflected sound they engender will be correspondingly smeared.

Probably it would be better if speakers didn't have any such anomaly, but since the overwhelming number of available products do, it's appropriate to wonder what audible bad effects it has. That is a subject on which it's hard to find agreement. On a signal (a drum beat, perhaps) that involves together the woofer, midrange, and tweeter(s) in what should be a unison response, we're likely to find some frequencies lagging considerably behind, which will sound not so good or perfectly all right, depending on whether you're talking to one "authority" or another.

One predictable effect of omni's documented long ago by Haas, is an increase in perceived loudness. The graph (page 24), which I think has implications for many audible phenomena, indicates that the ear integrates over a time "window" of about 100 milliseconds, so that any

Radio Shack®

A TANDY CORPORATION COMPANY

50%-OFF TAPE SALE*

TO GET YOU INTO REALISTIC SUPERTAPE® (even if you're there already)



CASSETTE



OPEN REEL



8-TRACK

Join the big switch to Supertape and save a neat 50% on your trial order at any participating Radio Shack store or Dealer. It's made in our factory on the newest equipment and to the highest standard we could set. It's internationally sold and acclaimed. Let your recorder and your ears be the judge. Not our advertising. Not theirs. Try Supertape today. There's only one place you can find it . . . Radio Shack!

*At Participating Radio Shack Stores and Dealers Now Through Nov. 30, 1975

Radio Shack's Own tape factory in Fort Worth, Texas



The nation's newest tape manufacturing operation devoted exclusively to audio tape

CLIP COUPONS. BRING TO RADIO SHACK

GET ONE SUPERTAPE CASSETTE AT NO EXTRA COST

when you buy the same cassette at the regular price at any participating Radio Shack store or Dealer. Limit one. This coupon must accompany your in-person purchase. None sent by mail.

STORE # _____
Sale Ends Nov. 30, 1975.

GET ONE SUPERTAPE OPEN REEL AT NO EXTRA COST

when you buy the same reel at the regular price at any participating Radio Shack store or Dealer. Limit one. This coupon must accompany your in-person purchase. None sent by mail.

STORE # _____
Sale Ends Nov. 30, 1975.

GET ONE SUPERTAPE CARTRIDGE AT NO EXTRA COST

when you buy the same 8-track cartridge at the regular price at any participating Radio Shack store or Dealer. Limit one. This coupon must accompany your in-person purchase. None sent by mail.

STORE # _____
Sale Ends Nov. 30, 1975.

sound of about that duration will sound louder the longer it lasts. The delayed arrivals of sound that are an omni specialty—whether caused by reflections or the layout of the drivers—should bring about an extension of the time the sound lasts at the listener's position. It is to this that I'd attribute some of the bright, open quality (particularly in the high frequencies) that we tend to associate with wide dispersion.

As for time smear over several frequency bands, there is no logical reason for an omni's being at all inferior to a conventional speaker. There is some evidence—all of it quite subjective—for such temporal dislocations' causing a subtle change in perceived tonal balance. For example, some experienced listeners have reported noting tonal changes when they moved off the axis of a conventional speaker so that they were slightly closer to some drivers than others. (Of course, the reports state that all other likely causes of this were eliminated.) Also, several speaker designs, some in existence and others still aborning, take the whole matter very seriously.

Assuming there's substance in any of this, it's interesting to speculate on what portions of the signal would dominate; the leading or the lagging ones? As it happens, few omni designs take these considerations into account, and most would be hard pressed to do so. Ultimately this might prove to be a limitation. As things stand now, however, there might very well be something going on.

A New Phase. On a completely different subject, in a conversation with Chuck Wood of Audionics not long ago, I learned of a unique new product that that company is considering. It is an all-pass network that varies the phase of one channel of a phono cartridge, the idea being to get the two channels phase-synchronized as closely as possible and thereby enable your four-channel matrix decoder to

work at its optimum. Harumph, I thought at first, but subsequent investigations have shown a number of cartridges I've checked out to have some phase shift between the two channels. Whether it's enough to be ruinous to matrix-decoder operation I can't say, but my impression is that these boxes need all the help they can get.

More Demo Records. My remarks of some months ago on demonstration records have lured a few more contestants out into the open.

Fulton Electronics, among whose products is the FMI Model 80 (considered by many to be in the top rank of under-\$100 speaker systems), also has a small recording operation at its Minneapolis base. Bob Fulton makes records the way I would if I knew how. Of the five Ark (his label) albums I've sampled, none is less than remarkable. One—*Organ Music from Westminster* (a Minneapolis church, not the British institution)—is unique in my listening experience. No light-voiced Baroque instrument this, but one of the high-pressure roarers that has you checking the ceiling overhead for rickety chandeliers. In fact, the specification shows the swell organ to be the largest section of the instrument, which smacks of nineteenth-century excess. Fortunately, the tone of the organ is not hard or piercing, but is almost dominated by the tremendous low-frequency resources—six 16-foot stops and one 32-foot Bourdon. Fulton has gone after these sounds in a way that all but opens the heavens. The bass is as substantial as a brick wall, and it just rolls over you without remission. Yet the rest remains in focus. I recommend the delightful Mozart selection for openers. I also recommend sturdy woofers.

I could be more enthusiastic about Ark's *Organ Sounds from Mount Olivet* if I hadn't heard the *Westminster* first. The *Olivet* recording is more than adequate in the bass, but of greater interest to me is the upper register, which is very strong yet freer of mod-

ulation effects and plain distortion than I'm used to. I should note that, as in the *Westminster*, some of the repertoire is of less than poignant interest, and unfortunately the organist's manner with J.S. Bach, of which there is nearly a full side, tends to be over-methodical.

It is unusual to find a large-scale work such as Bloch's *Sacred Service* as an original recording effort by a small label, but it is available from Ark, paired with Francis Poulenc's *Gloria*, as performed by orchestral and choral forces of the University of Minnesota. Being a two-microphone pickup (fundamental in Mr. Fulton's recording philosophy, I'm told; also, no Dolby processing—I suspect he doesn't believe in it—so all these records hiss), the recording assigns all soloists to the left channel. And, of course, there are no touch-up mikes to highlight orchestral details, if you've become used to that artifact of multi-track recording. The sound that results is extremely attractive and full-bodied, with a "sweetness" (the only word that comes to mind) of the high frequencies that seems characteristic of all the Ark releases (which wears very well for protracted listening). By great good luck, the Minnesota string section seems to have that rarest of talents among nonprofessional groups: the ability to play together and in tune most of the time. All in all, I don't know which large recording outfit you could turn to for so satisfactory a rendition of this music, or any choral-orchestral work.

The repertoire of the *Armstrong High School Choirs* ranges from Renaissance to late-Romantic sentimentality and the inevitable spiritual; but it has taste, and the Armstrong teenagers do crack ensemble with effortless range and dynamics. The recording is close-up and superlative; it should make you feel warm all over, as well as enabling you to hear the words of almost every voice in the group. *Anoka High School Concert Band (1974)* is just as good technically, but it is a high school band—a healthy cut above the troupes that march on New York's Fifth Avenue on St. Patrick's Day, but distinctly troubled at times by the difficulty of the material selected (a transcription of the Berlioz *Roman Festival Overture*, for example). Catalog and prices available from Fulton Electronics, 4428 Zane Ave N., Minneapolis, MN 55422.

Old-time Dixieland is becoming a

Pioneer's new High Polymer Molecular transducer technology will alter the course of high fidelity.

There's a significant new development in high fidelity that is destined to play a vital role in sound reproduction. It is intimately tied in with the piezoelectric principle.

The piezoelectric effect deals with certain crystal devices that flex when voltages are applied to them. Now, Pioneer has discovered a totally new application of the piezoelectric effect by applying the principle to ultra-thin aluminum coated high polymer film.

By employing this film as a low-mass diaphragm and applying audio signal voltages, the material expands and contracts uniformly generating acoustic energy. For the first time it becomes possible to transform electrical energy to an accurate acoustical equivalent. Such thin-film diaphragms properly mounted are capable of reproducing all music frequencies by means of an incredible "breathing" effect. The ramifications of this unique refinement of the piezoelectric principle are far reaching. Consider such immediate applications as microphones, cartridges, speaker systems and headphones — in fact, any type of electromechanical transducer requiring resonance-free performance.

There have been many attempts to create sound using diaphragm motion. For example, electrostatic speakers and headphones. But in contrast to the electrostatic principle, the new application of the High Polymer Molecular principle as discovered and perfected by Pioneer, requires no dangerous, high polarizing voltages.

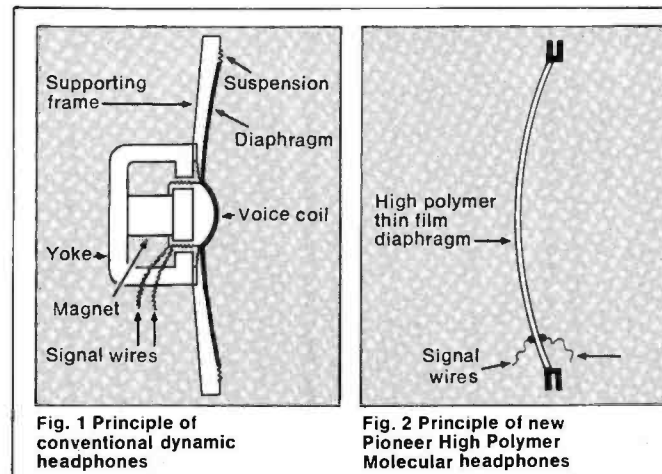


Fig. 1 Principle of conventional dynamic headphones

Fig. 2 Principle of new Pioneer High Polymer Molecular headphones

The first totally new concept in headphones in over a decade.

Pioneer has successfully incorporated the High Polymer Molecular transducer principle in two new headphones that are unlike any others. Conventionally designed headphones use moving coils, miniature loudspeaker elements and other mechanical parts — as shown in Figure 1 — all of which come between you and your music. Pioneer's new SE-700 and SE-500 headphones don't. They employ a single thin-film high polymer piezoelectric diaphragm that reproduces sound directly, as shown in Figure 2. Only the diaphragm moves air — and moves it accurately, in exact conformance with the electrical signal applied directly to it. The accurate, low-distortion signals available from any standard headphone jack on your receiver or amplifier are directly translated to equally precise, low-distortion sound by the action of the high polymer film diaphragm. Nothing, absolutely nothing comes

between you and the original sound.

Even though you may now own a pair of headphones, you owe it to yourself to hear these new piezoelectric high polymer transducer headphones. In fact, compare them with other types. You'll find a lower level of distortion-free sound than has ever been achieved — even at unprecedented volume levels. The experience of listening with these new


Pioneer headphones is a revelation. In addition, the open-back design, light weight and soft, snug fitting earpieces permit hours of comfortable, private listening. You'll come away from your Pioneer dealer thoroughly convinced that Pioneer has altered the course of high fidelity.

SE-700, under \$80*; SE-500, under \$50*. Both come with a 9/16 foot connecting cable, standard phone plug and storage case.

U.S. Pioneer Electronics Corp., 75 Oxford Drive, Moonachie, New Jersey 07074. West: 13300 S. Estrella, Los Angeles 90248 / Midwest: 1500 Greenleaf, Elk Grove Village, Ill. 60007 / Canada: S.H. Parker Co.



PIONEER®
when you want something better

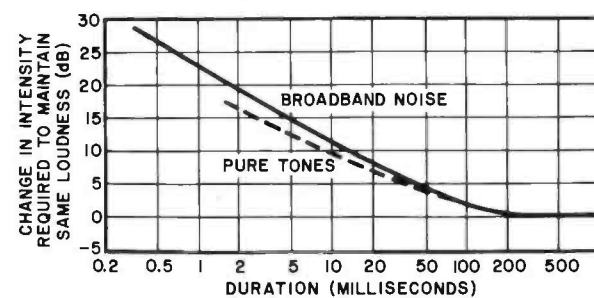

Below 100 ms, short sounds must be more intense to seem as loud as longer sounds. (Courtesy Hewlett-Packard Journal)

specialty of Burwen Laboratories, which incidentally manufactures a compander recording system and a dynamic noise filter for playback-only purposes. Burwen's first record (there have been a couple since, I believe) demonstrates the compander with stunning success. The disc, *Perfectly Clear*, presents the East Bay City Jazz Band and vocalist Jane Campedelli in what is said to be a close approach to traditional New Orleans music making. The record is a real wonder. There is not a sound on it that has not been captured with absolute, crystalline precision, and it's fascinating to follow the sharply etched outlines of the brass timbre into the sinuosity of a virtuoso clarinet. The banjo is a bit remote (it "rustles," as the song says), and the drums are really too far away from the mikes, getting soaked up by the extremely dead acoustic of the recording site. But the recording overall has, of course, no tape noise, and no trace of side effects that I could hear from the operation of the compander system. Nor is there any print-through of groove echo. Recorded levels are on the moderate side to accommodate the extreme peaks (which Burwen claims are there and my scope confirms), but the pressing is the flattest piece of vinyl I've seen in years, and exceptionally quiet. If your system will tolerate high gain settings you can blow yourself into chopped liver with this recording and never hear more than a whisper of noise. The Burwen record is \$10.50 from: Burwen Labs, 209 Middlesex Tpke., Burlington, MA 0183.

As promised, Ambiphon provided a new copy of the Natalie Ryshna piano recording that I found too noisy and otherwise unimpressive in my last report. The new pres-

sing is a great improvement—much superior to the earlier one in terms of discrete noises, and perhaps a bit better in hiss level. Listening to it has set my mind working again on the extremely detrimental effects of noise in any listening situation. At first hearing, the dynamic range of the new pressing seemed much better, but in a later direct comparison with the older version it came out about equal. A tricky business this.


Ambiphon also sent a newer recording by the Tequila Mocking Bird Chamber Ensemble. From the name you'd not expect that the group plays Handel, Vivaldi, and Pachelbel straight, but that appears to be the case. However, they attack this material with violin, tuba, and vibraphone. I question whether the vibes achieve a successful blend with the violin, but the tuba generally works well. God knows the bass line is always audible. The recording is very good. The only thing that keeps it from being exceptional is the lack of a big, spacy acoustic and/or spectacular dynamic range. Ambiphon's address is: P.O. Box 341, Kingsbridge Station, Bronx, NY 10463.

In closing, let me announce that CBS Laboratories, now reorganized as CBS Technology Center, is again offering its full range of test records, many of them remastered with newer equipment. The CBS series is especially valuable to the hobbyist because voice-identified spot frequencies are provided along with the more usual sweep tones that require a chart recorder. Thus a good voltmeter will suffice for reasonably accurate frequency-response measurements. For a catalog and price list write: CBS Technology Center, High Ridge Rd., Stamford, CT 06905. ♦

BUILD YOURSELF A SPEAKER SYSTEM AND SAVE!

You know specs, but you want speakers to speak for themselves. CTS speakers *do*; they sound just the way you like. For example, choose a CTS STARRSÖND™ system. Let CTS dealer/consultants tell you how to install it in an ideal enclosure. You'll know why many famous manufacturers use CTS speakers in their brand-name products! Write, send coupon or circle reader service number for our catalog on speakers for home, musical instruments, auto and other uses. Then visit your CTS dealer and hear them:

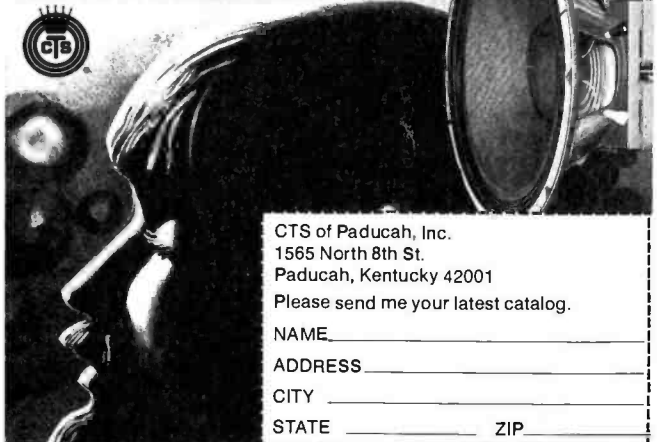The ones that speak for themselves.
CTS OF PADUCAH, INC.
SUBSIDIARY OF CTS CORPORATION, ELKHART, INDIANA



CTS of Paducah, Inc.
1565 North 8th St.
Paducah, Kentucky 42001
Please send me your latest catalog.
NAME _____
ADDRESS _____
CITY _____
STATE _____ ZIP _____

CIRCLE NO. 20 ON FREE INFORMATION CARD

IC troubles?
try these high-performance
Super-Grip™
IC Test Clips

for fast, non-shorting access to all leads on dual-in-line IC packages

No more shorting across DIP leads... just quickly clip on an IC TEST CLIP to bring DIP leads out for safe attachment of scope probes and other leads. Ideal for signal input, tracing, troubleshooting, etc. Patented precision, "contact comb" design guarantees no shorting between DIP leads. Probes can hang "no-hands" free on Test Clip terminals in card racks (unique — see photo). Engineered Mechanical clamping plus gold-plated phosphor bronze terminals provide superior electrical contact. Also unequaled as a DIP removal tool.

11 models to fit all DIP's

Model	Row-To-Row Dim.	Part Number	Price
TC-8	.3 IN.	923695	\$7.35
TC-14	.3 IN.	923698	4.50
TC-16	.3 IN.	923700	4.75
TC-16 LSI	.5/ .6 IN.	923702	8.95
TC-18	.3 IN.	923703	10.00
TC-20	.3 IN.	923704	11.55
TC-22	.4 IN.	923705	11.55
TC-24	.5/ .6 IN.	923714	13.85
TC-28	.5/ .6 IN.	923718	15.25
TC-36	.5/ .6 IN.	923720	19.95
TC-40	.5/ .6 IN.	923722	21.00

TC-16 fits 16-pin DIP's, etc.

We honor M.C. and B.A.C. charges. Add sales tax on OH and CA orders. (F.O.B. Painesville on company P.O.'s.) Dealer inquiries invited

SHIPPING/HANDLING/C.O.D. fees from this chart.

Up to \$10.00	\$1.00	\$.70
\$10.01 to \$25.00	1.50	.80
25.01 to 50.00	2.00	.90

A P PRODUCTS INCORPORATED
All products guaranteed to meet or exceed published specifications
Box 110-H • Painesville, OH 44077 • 216/354-2101

CIRCLE NO. 1 ON FREE INFORMATION CARD



SBE gives you the Digital 1-2 in personal communications!

Digital logic will certainly be the "brain" for future Citizens Band transceivers and scanners. But SBE gives you the digital knockout punch in these product lines right now—is the **only** manufacturer offering a no-crystal scanner monitor receiver and a superlative CB transceiver—both digitally synthesized.



OPTISCAN

And in this corner, **Optiscan!** The non-pareil—the SBE digital sensation! An all band winner: 30-50, 150-170, 450-470, 490-510 MHz.

Optiscan is the only crystal-less monitor that scans any station in the nation by optically reading a

pre-programmed, permanent memory card. Of course it has lockout switches and provisions for Auto./Man. scan.

This is the only championship contender with **NO** cumbersome program switches or gadgetry. You can make a 10 channel program change while driving in your car and still keep your eyes on the road. Merely slide in a proper pre-programmed card. Carry cards programmed for police, fire, marine, other "action" channels wherever you drive. And only the SBE **Optiscan** has both 115 volt AC and 12 volt DC supply built in.

FORMULA D

Now, in the black and silver trunks—SBE's digital CB transceiver phenom, **Formula D**. This unbeaten heavyweight has a great receiver that can take it, a transmitter that can really dish it out, with decisive wins over all CB challengers. Real class too, with 23 digitally synthesized AM channels. Powerful—6 watts in, 4 watts out and AM modulation clout. Everything a champ needs: Audio tone control—Local/DX switch (stops overload from strong signals)—Clarifier—Automatic noise limiter with switch—PA/Loud hailer provisions—Monitor meter for Power out/Received signal strength—Dynamic mic. w/coil cord/plug. A two-fisted slugger with positive or negative ground, 12VDC. You're a sure winner with SBE's digital 1-2!



Send for complete information on this outstanding equipment

SBE
LINEAR SYSTEMS, INC.
220 Airport Blvd., Watsonville, CA 95076


INTERNATIONAL OFFICES
E.S. GOULD
MARKETING CO., LTD.
109 Montee de Liesse,
Montreal, Quebec,
Canada H4T 1S9
LINEAR SYSTEMS, S.A.
5 Rue de Alpes,
P.O. Box 163,
1211 Geneva 1,
Switzerland.

The better the training and the equipment the better you'll be equipped.

Send for FREE illustrated career guide

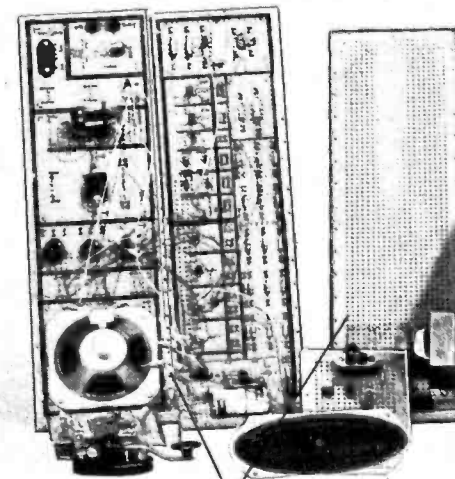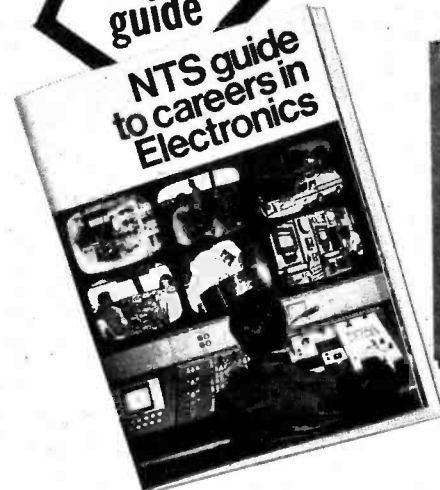

ELECTRO-LAB

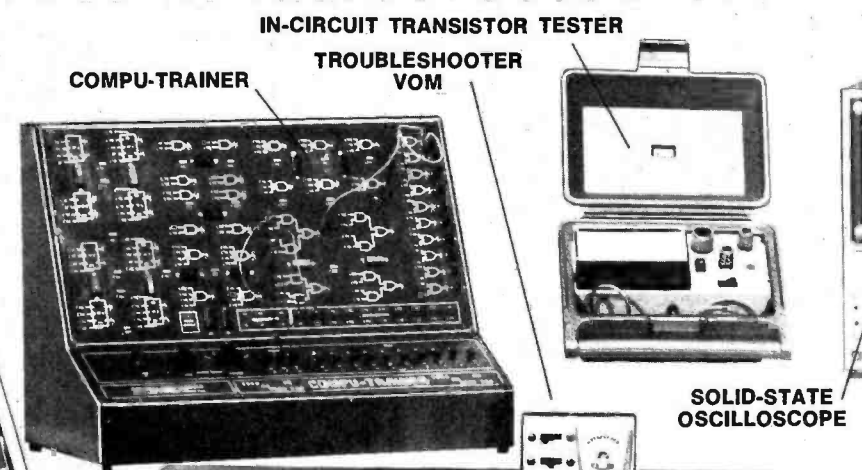

COMPU-TRAINER

IN-CIRCUIT TRANSISTOR TESTER

TROUBLESHOOTER VOM

SOLID-STATE OSCILLOSCOPE



(Simulated TV Reception)



HIGH FIDELITY SPEAKERS

SOLID-STATE STEREO AM/FM/MULTIPLEX RECEIVER


COLOR BAR/DOT GENERATOR

TUBE & TRANSISTOR TESTER

FET-VOM

AM/FM/SW PORTABLE SOLID-STATE RECEIVER

74 sq. in. COLOR MONITOR

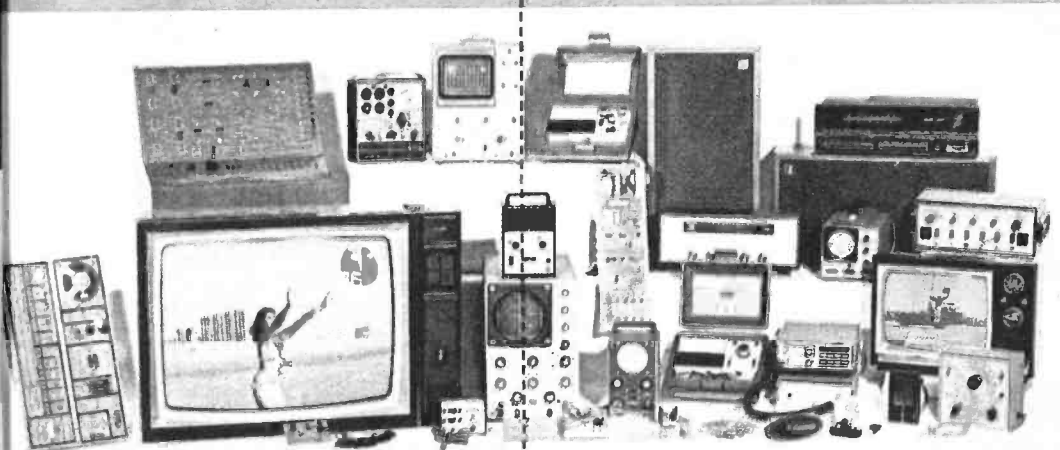

SIGNAL GENERATOR

As an NTS student you'll acquire the know-how that comes with first-hand training on NTS professional equipment. **Equipment you'll build and keep.** Our courses include equipment like the **NTS/Heath Digital GR-2000 Solid State color TV** with first-ever features like silent varactor diode tuning; digital channel selection, (with optional digital clock), and big 315 sq. in. ultra-rectangular screen.

Also pictured above are other units — 5" solid state oscilloscope, vector monitor scope, solid-state stereo AM-FM receiver with twin speakers, digital multi-meter, and more. It's the kind of better equipment that gets you better equipped for the electronics industry.

This electronic gear is not only designed for training; it's field-type — like you'll meet on the job, or when you're making service calls. And with NTS easy-to-read, profusely illustrated lessons you learn the theory behind these tools of the trade.

Choose from 12 NTS courses covering a wide range of fields in electronics, each complete with equipment, lessons, and manuals to make your training more practical and interesting.

Compare our training; compare our lower tuition. We employ no salesmen, pay no commissions. You receive all home-study information by mail only. All Kits, lessons, and experiments are described in full color. Most liberal refund policy and cancella-

The better the equipment the better you'll be equipped.

NTS TRAINING EQUIPMENT FEATURES SOLID-STATE COMPONENTS. PROJECT METHOD COURSES MAKE LEARNING EASIER, FASTER, MORE EXCITING. **FREE** Please rush new color catalog plus complete details on course checked. **NO OBLIGATION. NO SALESMAN WILL CALL.**

- COLOR TV SERVICING
- B&W TV AND RADIO SERVICING
- ELECTRONIC COMMUNICATIONS
- FCC LICENSE COURSE
- ELECTRONICS TECHNOLOGY
- COMPUTER ELECTRONICS
- BASIC ELECTRONICS
- AUDIO ELECTRONICS SERVICING



Name _____ Age _____
 Address _____ Apt. _____
 City _____ State _____

Please fill in ZIP code for faster service
 Check for information on GI Bill
 Check if interested ONLY in Classroom Training in Los Angeles
 Popular Electronics

Dept. 205-115
 90037
 e Lesson.
 L.
 electronics Technology
 mputer Electronics
 sic Electronics
 udio Electronics Servicing
 _____ AGE _____
 _____ APT # _____
 _____ STATE _____
 _____ nation.
 om training in Los Angeles.

The better the training and the equipment the better you'll be equipped.

Send for FREE illustrated career guide

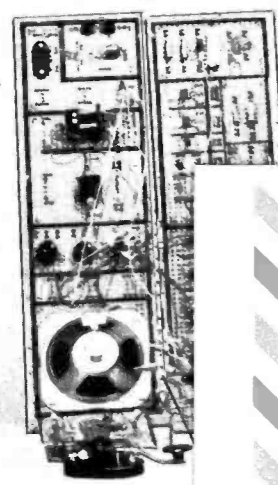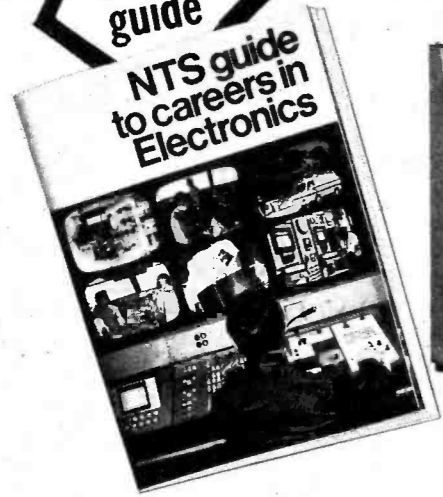

ELECTRO



COMPARE OUR KITS AND LESSONS. COMPARE OUR TUITION.

COMPU-TRAINER

IN-CIRCUIT TRANSISTOR TESTER

TROUBLESHOOTER VOM

SOLID-STATE OSCILLOSCOPE

TUBE & TRANSISTOR TESTER

FET-VOM

AM/FM/SW PORTABLE SOLID-STATE RECEIVER

HIGH FIDELITY SPEAKERS

SOLID-STATE STEREO AM/FM/MULTIPLEX RECEIVER

COLOR BAR/DOT GENERATOR

VECTOR MONITOR SCOPE

74 sq. in. Solid-State B&W TV

SIGNAL GENERATOR

5" OSCILLOSCOPE

DIGITAL MULTIMETER

SOLID-STATE 2-METER FM TRANSCEIVER & POWER SUPPLY

SOLID-STATE POCKET RADIO



NTS/HEATH GR2000 Digital Solid-State Color TV 315 sq. in.

NEW NTS GR 2000 DIGITAL COLOR TV. SOLID-STATE. 25" DIAGONAL. VARACTOR DIODE TUNING. (Simulated TV Reception)



New Fully Illustrated Color Catalog Tells All About These NTS "Extras"

- Job Placement Consultation
- Business Consultation Service
- Student Guidance
- Graduate Association
- Mechanics & Science Bulletins, Plus Much More

APPROVED FOR VETERAN TRAINING Classroom Training Available at Los Angeles

NTS occupies a city block in sunny Southern California with over a million dollars in facilities devoted exclusively to technical training. Check box on reverse side for details.

NATIONAL TECHNICAL SCHOOLS
TECHNICAL-TRADE TRAINING SINCE 1905
Resident and Home-Study Schools
4000 So. Figueroa St., Los Angeles, Calif. 90037

POSTAGE WILL BE PAID BY-
NATIONAL TECHNICAL SCHOOLS
4000 South Figueroa Street
Los Angeles, California 90037

BUSINESS REPLY MAIL
No Postage Stamp Necessary if Mailed in the United States

VIA AIR MAIL

FIRST CLASS
Permit No. 3087
Los Angeles, Calif.

As an NTS student you come with first-hand equipment. Equipment courses include eq Digital GR-2000 Solid-State Color TV features like silent channel selection, (v big 315 sq. in. ultra-

Also pictured above oscilloscope, vector scope AM-FM receiver w meter, and more. It's that gets you better industry.

tion privileges spelled out. Make your own comparisons, your own decision. Mail card today, or clip coupon if card is missing.

NO OBLIGATION. NO SALESMAN WILL CALL

APPROVED FOR VETERAN TRAINING
Get facts on new 2-year extension

NATIONAL TECHNICAL SCHOOLS

TECHNICAL-TRADE TRAINING SINCE 1905
Resident and Home-Study Schools
4000 So. Figueroa St., Los Angeles, Calif. 90037

NOVEMBER 1975

Dept. 205-115

NATIONAL TECHNICAL SCHOOLS
4000 South Figueroa St., Los Angeles, Calif. 90037
Please send FREE Color Catalog and Sample Lesson. NO OBLIGATION. NO SALESMAN WILL CALL.


Color TV Servicing
 B & W TV and Radio Servicing
 Electronic Communications
 FCC License Course

Electronics Technology
 Computer Electronics
 Basic Electronics
 Audio Electronics Servicing

NAME _____ AGE _____
ADDRESS _____ APT # _____
CITY _____ STATE _____

Please fill in Zip Code for fast service
 Check if interested in G.I. Bill information.
 Check if interested ONLY in classroom training in Los Angeles.

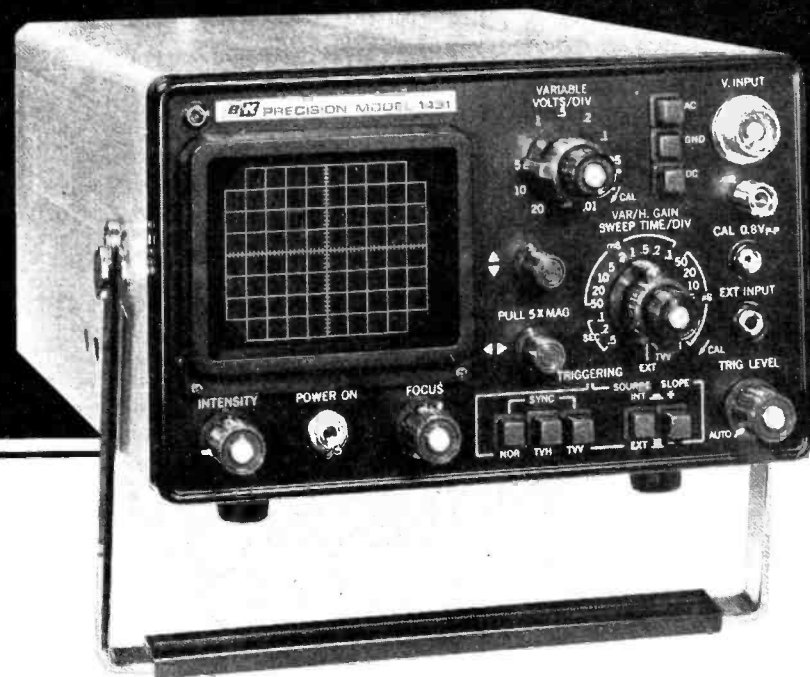**This 10 MHz Triggered Scope
is 1/3 the size
of comparably
performing scopes.**



MODEL 1431 \$399.00

It's a lightweight 13 pounds in your hand and a heavyweight performance wideband scope with a 35 nanosecond rise time on your bench or jobsite. Whether you're servicing or designing industrial equipment or TV, there's the right sweep speed and sync for easiest operation. If you know our Model 1460, the leader in wideband 5" CRT scopes, you know our new 3" Model 1431 which gives you the same high performance in one third the size. (Only 4 3/4" H x 7 7/8" W x 12 7/8" L)

Servicing, production, inspection, quality control and lab applications are all easier with this versatile all solid-state instrument. Triggering is accomplished with only 0.5V peak-to-peak. Ten millivolts per division sensitivity, 0.5 usec/cm to 0.5 sec/cm automatic and triggered sweep in 19 calibrated ranges, and external trigger input are just a few of the reasons you'll like it.

If you have been waiting to buy a portable scope until you could get all the features you'll ever need at a price you want to pay, you've been waiting for Model 1431. Contact your distributor or write Dynascan Corporation.



Shown with optional carrying cover and probe pouch.

B&K PRODUCTS OF
DYNASCAN
1801 W. Belle Plaine Ave.
Chicago, IL 60613 • (312) 327-7270

CIRCLE NO. 15 ON FREE INFORMATION CARD

EXCLUSIVE!

The First Motorola/AMI '6800' MPU Computer Project



*Features compact size, simplified construction,
built-in TTY interface, and low cost.*

BY H. EDWARD ROBERTS & PAUL VAN BAALEN


LARGE-SCALE integration (LSI) has provided many useful IC chips for the hobbyist. One of the latest LSI devices is the microprocessor unit (MPU), which has made it possible to build microcomputers that are fairly easy to assemble at moderate cost. The most popular MPU's are the 8008 and 8080 due to their reasonable cost and wide availability in computer kits.

However, many knowledgeable hobbyists have been looking for a microcomputer built around one of a number of other MPU's available (just as some people would like to try a diesel or steam engine to replace the gasoline motor). Most of these readers have told us they were interested in the Motorola M6800 MPU (for one reason or another). Many also felt that the price of a microcomputer was still too high. POPULAR ELECTRONICS is therefore pleased to introduce the first microcomputer using the 6800 MPU in a design that substantially reduces cost.

THE Altair 680 is a complete microcomputer built around the 6800 MPU available from Motorola and American Micro-Systems, Inc. Measuring a very compact 11 1/16" W x 11 1/16" D x 4 11/16" H (28.1 x 28.1 x 11.9 cm), the 680 is less than one-third the size of the Altair 8800. Although both computers have MPU's with the same memory capacity, the 680's smaller enclosure makes internal expandability significantly less. However, it is more than adequate for most applications. More importantly, the 680 costs less than half the price of the 8800 when the two machines are configured similarly in a minimum system.

Other attributes of the new computer include ease of assembly (only one large pc board), built-in TTY interface, and high speed (4-μs minimum cycle time). The last is some 10 to 50 times faster than earlier small computers built around the 8008 MPU but half the speed of the 8800.

Another meaningful consideration in a 6800-MPU computer design is the raft of instructional material readily available from Motorola Semiconductor Products, Inc., including the "M6800 Microprocessor Programming Manual." Too, the 6800 is TTL compatible and uses just one 5-volt power supply.

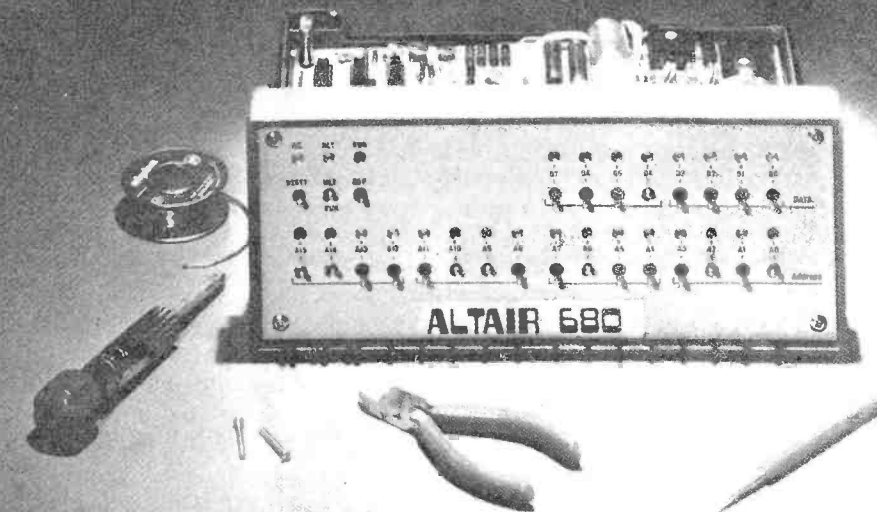

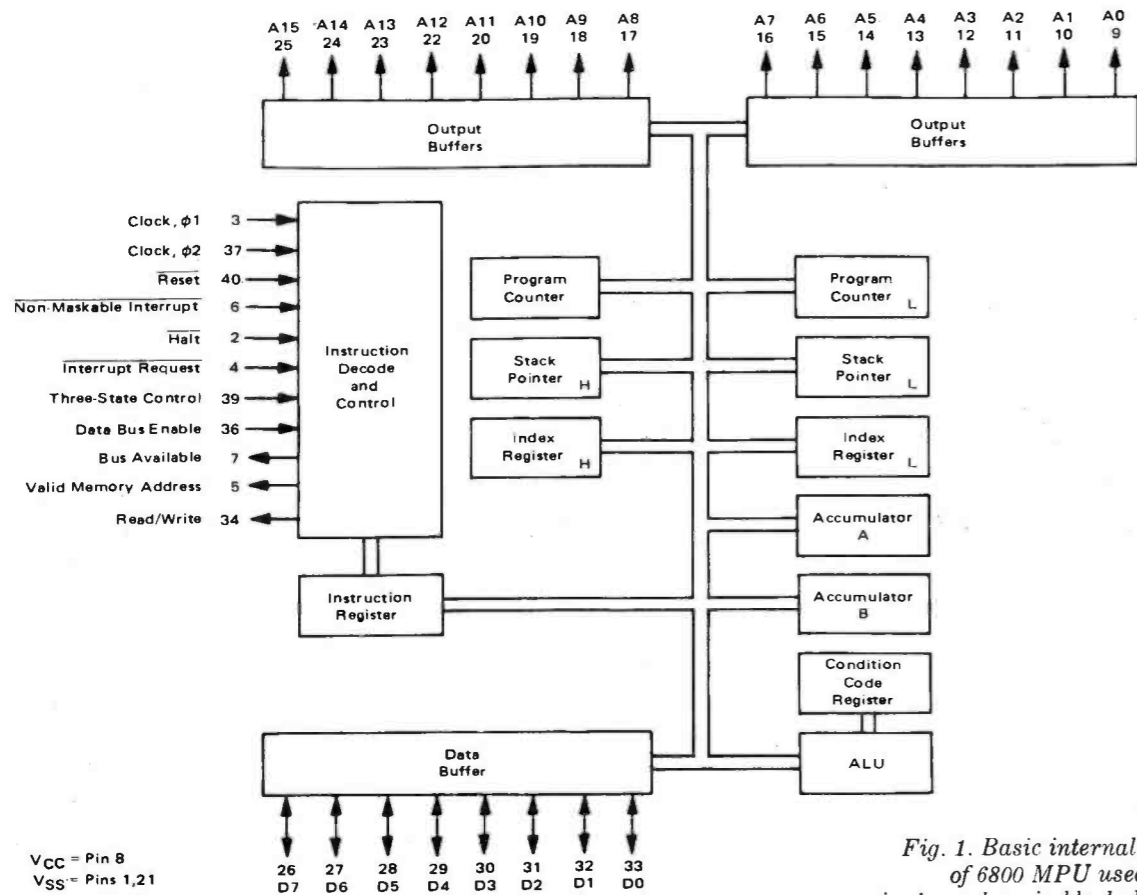


Fig. 1. Basic internal arrangement of 6800 MPU used in computer is shown here in block-diagram form.

Basic System Philosophy. The basic MPU, memory, I/O (input/output), and power-supply circuits in the Altair 680 are located on a single printed circuit board. The addition of a compact power transformer makes this assembly a complete computer system. (Front-panel switch programming can be used, but in the absence of this assembly, PROM's or ROM's must be installed for programming.)

The front-panel assembly contains all the logic needed to reset, halt, or start the processor. Also, any memory cell can be read or written into from the front panel via 16 ADDRESS and eight DATA switches. Mounted on the front-panel circuit board is a 100-contact edge connector that permits the main MPU board to plug directly into the front panel, thus eliminating the need for a wiring harness. (In systems that do not use the front-panel assembly, the MPU board automatically starts running at an address specified by either a PROM or a hard-wired patch.) The front panel contains 27 LED's that indicate the state of each switch. As a safety measure, the POWER switch is located on

the back of the cabinet to obviate the possibility of its being accidentally operated during programming.

The basic computer contains 1024 bytes of memory and has provisions for an additional 1024 bytes of PROM or ROM memory. An I/O channel and interface are also included in the basic system. The I/O channel can be configured to interface RS-232 or a 20-mA or 60-mA TTY loop. This means that anyone who can obtain an old five-level Baudot-type Teletype—such as the MOD-15, MOD-19, etc.—can use it as a computer terminal. (Many such Teletypes are available for less than \$100 and frequently for as little as \$25 nationwide.)

The Altair 680 can be built with either a full-programmability or a "turn-key" front panel. The latter eliminates all controls except restarting the processor. There are a number of applications where this is desirable to eliminate the possibility of having an operator affect the contents of the memory or the computing cycle. An example might be in a sophisticated intruder-detection system where the only control provided for the operator is essentially on/off.

Software. The software associated with the 6800 MPU includes an editor, PROM monitor, and assembler, as contrasted to the editor, assembler, monitor and basic for the Altair 8800 computer.

System Details. The Altair 680 computer is composed of five sections: MPU and clock, memory, control and indication, I/O port, and power supply.

MPU and Clock. As mentioned earlier, the MPU and clock are the new 6800 LSI chip. Its basic internal arrangement is shown in Fig. 1. The main elements are instruction decode and control, instruction register, data and address registers and buffers, 16-bit index register, 16-bit program counter, 16-bit stack pointer, two 8-bit accumulators, condition code register, and ALU (arithmetic logic unit).


The timing and control inputs and outputs for the 6800 chip are:

Phase 1 and phase 2 clock ($\phi 1, \phi 2$)—a nonoverlapping 500-kHz clock at V_{cc} .

Address bus A0 through A15—16 high active outputs that determine address or I/O sections to use.

DISPLAY PARTS LIST

C1, C4—0.33- μ F, 12-V disc ceramic capacitor
 C2, C3—0.47- μ F, 12-V disc ceramic capacitor
 DA00 to DA15, DD00 to DD07, and DS1 to DS3—RL21 light-emitting diode
 ICA, ICB, ICC, ICD, ICE, ICF, ICG, ICH—4449
 ICJ—74L00
 ICK, ICL—26L123
 Following resistors are 1/2-watt, 5%:
 R1 to R16, R20 to R27—1500 ohms
 R17 to R19—20,000 ohms
 R28 to R30, R33 to R37—4700 ohms
 R31 to R38—1000 ohms
 R39, R40—10,000 ohms
 SC1 to SC12—0.1- μ F, 12-V disc ceramic capacitor
 SA00 to SA15, SD00 to SD07, S24—Spdt toggle switch
 S26, S27—Spdt momentary toggle switch
 Misc.—100-contact edge connector

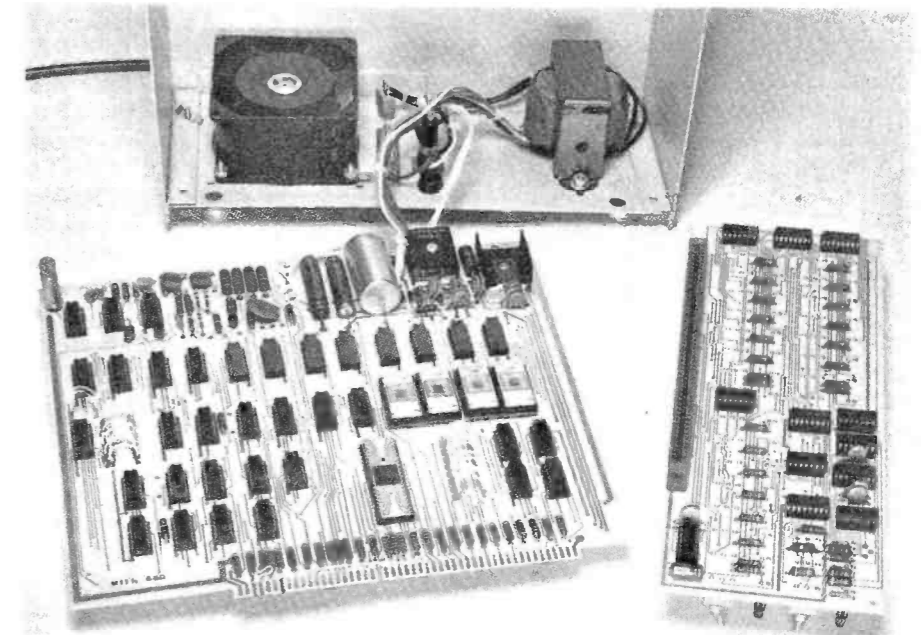

Almost entire computer is assembled on a single large pc board (left). Board at right is for front panel. Boards plug together.

Data bus D0 through D7—eight high active bidirectional lines for transfer to and from memory and peripherals.

Halt signal (\overline{HLT})—low active input that ceases activity in the computer.

Read/write signal (R/W)—in the high state, signals the memory and peripherals that the MPU is in the read condition; in the low state, signals that the MPU is in the write condition.

Valid memory address (VMA)—signals external devices (memory and I/O) that the MPU has a valid address on the memory bus.

Data bus enable (DBE)—enables the bus drivers.

Bus available (BA)—indicates machine has stopped and address bus is available.

Reset (\overline{RES})—resets and starts the MPU from a power-off condition. A positive-going edge on this input tells the MPU to begin the restart sequence.

Interrupt request (\overline{IRQ})—when low, tells the MPU to start an interrupt sequence (save the registers on the stack, set interrupt mask bit high so no other interrupts can occur, and vector to the interrupt address). This type of interrupt can only occur if the interrupt mask bit in the condition code register is low.

Nonmaskable interrupt (\overline{NMI})—

essentially the same as the \overline{IRQ} , except it is not dependent on the condition code register.

The clock is a 2-MHz crystal-controlled oscillator that uses a pair of inverters that drive flip-flops to form a 500-kHz, two-phase clock that is distributed to the MPU, memory, and I/O sections in the computer via inverters and buffers.

Memory. The memory system consists of 1024 words of 8-bit-wide RAM, using 2102-type 1024 \times 1-bit devices, and up to 1024 words of PROM, using ultraviolet-erasable 1702 devices. The basic arrangement is shown in Fig. 2. The low-order address bits are fed to both the RAM's and PROM's.

Front Panel. The front panel assembly contains the RUN/HALT switch, with a LED for each switch position; a reset switch with no LED indicator; and the ac power ON LED indicator (Fig. 3). The 16 ADDRESS switches and eight DATA switches each have their own LED indicator.

The DEPOSIT, RESET, DATA, and ADDRESS switches are enabled only when the RUN/HALT switch is in the HALT position, at which time, a retriggerable one-shot multivibrator drives the halt input of the MPU low. This, in turn, drives the bus-available (BA) signal high and also conditions the other switches. To view the data in any memory location, the RUN/HALT switch must be placed in the HALT position and the ADDRESS switches set to the required address. The data at that

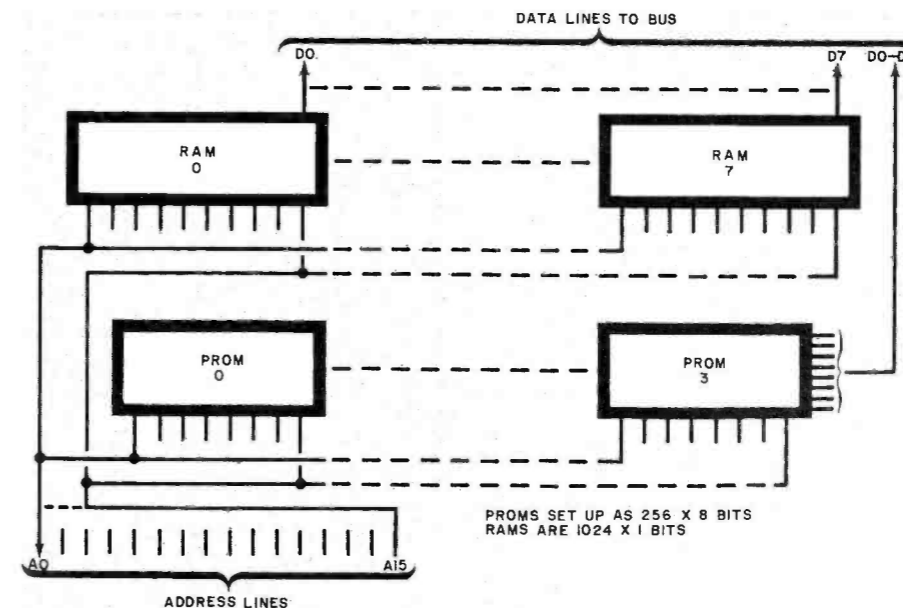


Fig. 2. There are eight RAM's (RAM 0 through RAM 7) and four PROM's (PROM 0 through PROM 3) in the computer's memory system.

ALTAIR COMPUTER COMPARISON CHART

Features	Altair 680	Altair 8800
Maximum word size	24 bits (byte oriented)	24 bits (byte oriented)
Arithmetic unit	8-bit parallel	8-bit parallel
Minimum cycle time	4 μ s	2 μ s
Program instructions	72	78
Maximum memory size	65k bytes	65k bytes
Internal expandability	5 interface cards	250 interface cards
Interrupt	3 levels	8 levels
MPU	6800 (Motorola, AMI)	8080 (Intel, TI)
Approximate system cost (1k memory, I/O, case, P/S)	\$300	\$600
Miscellaneous	Fewer parts 2 printed circuit boards Smaller size Built-in TTY interface	Minimum of 4 pc boards

MAIN BOARD PARTS LIST

BD1—Bridge rectifier (VJ048)
 C1—3300- μ F, 50-V electrolytic capacitor
 C2, C3—100- μ F, 50-V electrolytic capacitor
 C4 to C9—0.33- μ F, 50-V disc ceramic capacitor
 C10, C13—0.1- μ F, 16-V disc capacitor
 C11, C12—0.33- μ F, 16-V disc capacitor
 C14—0.01- μ F, 16-V disc capacitor
 C15—1- μ F, 50-V electrolytic capacitor
 D1, D2, D7 to D12—1N4004 diode
 D3 to D6—1N4739A, 9.1-V zener diode
 F1—1-A, 250-V ac, 3-AG fuse
 ICA—7404
 ICB—7473
 ICC, ICU—7408
 ICD, ICE, ICS—4449
 ICF, ICG—74LS01
 ICH, ICJ, ICK, ICL, ICM, ICN, ICP, ICR—2102
 ICT, ICU, ICGG, ICHH, ICPP, ICRR—74LS30

ICV—74L00
 ICW—74L74
 ICX, ICY, ICTT—4050
 ICZ, ICAA, ICBB, ICC—1702
 ICDD, ICFF—74L04
 ICEE, ICMM—74L10
 ICJ—6800
 ICKK, ICLL, ICSS—74LS05
 ICNN—74LS27
 Q1, Q3, Q4—TIS98
 Q2—EN3907

Except where noted, following resistors are 1/2-watt, 5%:
 R1, R2—33 ohms, 2-watt, 5%
 R3, R4, R5, R7—100 ohms
 R6—130 ohms, 1-watt, 5%
 R8, R11—800 ohms
 R9—220 ohms, 1-watt, 5%
 R10, R28 to R51—7500 ohms
 R12, R15, R16, R17—1000 ohms
 R13—470 ohms
 R14, R20, R21—390 ohms
 R18, R19—330 ohms
 R22—33,000 ohms
 R23, R24, R25, R60—10,000 ohms

R26, R27, R56, R57, R58, R59—not used
 R52 to R55—3000 ohms
 SP1—Spdt toggle switch
 T1—5-volt, 1.2-A transformer
 VR1—7805 regulator
 XTAL—2-MHz crystal

Misc.—Fuse holder (Buss HKP-CC, line cord, fan (IMC 3 $\frac{3}{8}$ "), I/O socket (DB-255), sockets (14-pin, 22; 16-pin, 20; 24-pin, 4; 40-pin, 1), case optional).
 Note—The following are available from MITS, 6328 Linn, N.E., Albuquerque, NM 87108: complete kit (all parts) #680F at \$293; complete kit except for front panel board #680T at \$240; kit #680MPU, including pc board, 6800 MPU, 1k memory, and all main board components except power supply at \$180; front panel and MPU pc boards #680PC at \$48; I/O socket kit at \$29; fan kit at \$16; 256 x 8-bit PROM kit at \$42; construction information package is free, with self-addressed stamped 9" x 12" envelope.

causes an output to the built-in TTY output jack and at the Teletype itself.

Power Supply. The main 5-volt line is generated within the computer by a conventional bridge rectifier, filter capacitor, and IC regulator circuit. A 32-volt winding on the transformer is used to generate the unregulated \pm 16 volts required for the TTY interface system, while a -16-volt line is fed to

four zener-diode-regulated outputs to provide four 9-volt lines for the PROM's.

Construction. The actual-size etching and drilling guides for the computer boards are larger than our page size. Rather than reducing or cutting them up to fit our pages, a free construction package is available. If you

wish to obtain a construction information package, simply send a self-addressed stamped 9" x 12" envelope to the address given at the end of the Parts List.

The construction package contains full-size schematics, full-size etching and drilling guides, component-placement diagrams, and front-panel layout. \diamond

CRAMER ELECTRONICS ENTERS OEM COMPUTER KIT MARKET

THE major reason for the tremendous success of the various computer kits on the market is that they save considerable time. One doesn't have to hunt down the MPU's, memories, etc., that must be accumulated before embarking on a home computer project. It appears that OEM engineers are also spending considerable time in hunting down computer parts. Cramer Electronics, one of the leading U.S. electronic parts distributors, has decided to enter the computer kit business, with emphasis on the OEM market.

Cramer is starting with three kits, separately based on the Intel 8080, Motorola 6800, and Texas Instruments TMS8080 MPU's. Each of the kits

shares a common \$495 price tag.

You get a lot for \$495: complete color-coded schematic diagram; RAM with 1024 (8-bit) bytes, expandable to 65 k bytes; erasable PROM with 1024 (8-bit) bytes; support circuitry, including clock, complete buffering, control and synchronization logic, interrupts, DMA controls; etc. The PROM gives you a program to run at the outset. There are at least four 8-bit-wide input and output ports, with expandability to 512 ports, decoding for 16 of which is included.

The PROM contains a system monitor to permit the computer to be used as soon as it is assembled. Programs can be entered, modified, examined, and executed under switch

control or by typed-in commands. A cassette program, included with the kit, can be used to debug the computer. Finally, a complete user manual gives hints on programming and how to expand the computer.

All together, there are about 190 parts in each kit, adding up to a total catalog value of some \$700. Software is included in the kits to help in programming via front-panel switches and LED's, cassette tape, Teletypewriter, or any RS-232-compatible terminal. Not supplied are printed circuit boards, power supply, and cabinet.

For more information about the new computer kits, write to: Cramer Electronics, Inc., 65 Wells Ave., Newton, MA 02159. \diamond

You don't have to buy a new car to get an electronic ignition.



Most of you know the evaluation of automotive electrical systems... an evaluation characterized only occasionally by efficiency and performance. I know that, and that's why I use the Delta Mark Ten B CDI on all my cars, new and old. And believe me, you don't have to have a new car to appreciate the best electronic ignition available today. Study these features and you'll know what I mean.

1. Mark Ten and Mark Ten B Capacitive Discharge Ignition Systems are manufactured by Delta Products, Inc., a company with a conscience, and with a proven record of reliability both in product and in customer relations.
2. The Mark Ten CDI's really do save money by eliminating the need for 2 out of 3 tune-ups. Figure it out for yourself. The first tune-up or two saved pays for the unit, the rest is money in your pocket. No bunk!
3. Because the Mark Ten CDI's keep your car in better tune, you actually can save on expensive gasoline.
4. With a Mark Ten, spark plugs stay clean and last longer... fouling is virtually eliminated.



No matter what kind of car you drive, it too can use a Delta quality lift.

I want to know more about Mark Ten B CDI's. Send me complete no-nonsense information on how they can improve the performance of my car.

Name _____
 Address _____
 City _____ State _____ Zip _____

DELTA PRODUCTS, INC.
 P.O. Box 1147, Dept. PE, Grand Junction, Colo. 81501
 303-242-9000

Mark Ten B, assembled \$64.95 ppd
 Mark Ten B, kit \$49.95 ppd
 Standard Mark Ten, assembled \$49.95 ppd
 Deltakit® \$34.95 ppd

memory address location will then appear as lighted and unlighted LED's in the DATA display.

To change data in a location, the desired data is written via the DATA switches and entered by operating the DEPOSIT switch. This triggers a one-shot multivibrator, enabling the data information to the data bus and causing the R/W signal to go low. Since the address bus is already connected to the switches by being in the halt state, the write pulse causes the data to be written into the selected RAM address.

When the RESET switch is operated, the CPU resets. This, in turn, initiates a restart sequence. That is, the address bus is pulled to the high state and causes the hard-wired data in the board jumpers to be used as the restart address.

Access to the I/O port is gained by addressing location 17577 (in octal). A sequence of events then occurs that

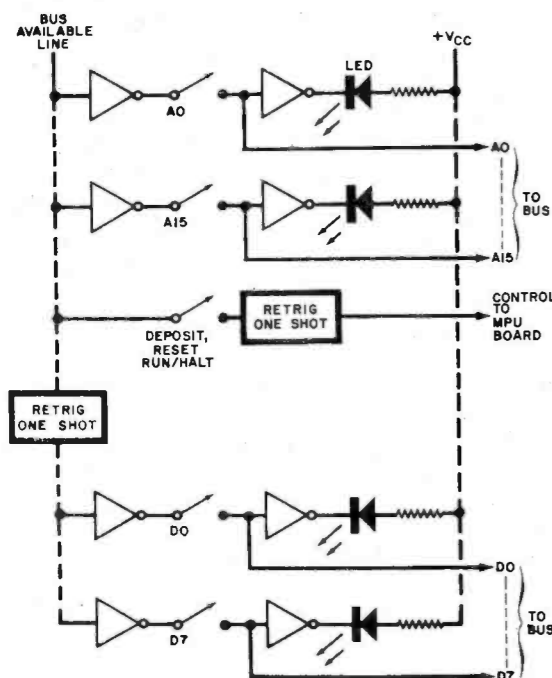


Fig. 3. Front panel contains address and data switches A0 through A15 and D0 through D7, reset switch, and LED indicators.



At bottom right in photo is RCA's VideoDisc player. Engineer is holding typical 12" VideoDisc.

HERE COME THE HOME VIDEO DISCS

How the three leading video disc systems produce sight and sound from a disc resembling the familiar LP record

AFTER several false starts with magnetic tape and optical film and expensive equipment, a practical home-entertainment video playback system that can be used with any TV receiver is on the horizon. RCA, AEG

Telefunken, British Decca, Zenith Radio, N.V. Philips, MCA, Thomson CSF, and others have developed video disc systems, that resemble and can be played like an audio disc. More important, the decks and program

material are relatively inexpensive compared to tape and optical film systems.

If the developers have their way, we will no longer be tied to network and local station programming. Soon,

POPULAR ELECTRONICS

we'll be able to make our own choices of prerecorded video disc color TV programs. In fact, West Germans can now buy a video disc player from a local retailer. They can also choose from an initial selection of 200 video disc programs.

By the end of 1976, it appears that there will be two incompatible systems (produced by RCA and Philips/MCA) in competition for the U.S. consumer dollar. There is also the possibility that other systems, such as West Germany's Teldec system, will join the battle.


The Video Discs. Similar in physical appearance to and played in essentially the same manner as the 12" LP audio record, the video disc will offer just about every form of entertainment imaginable—from motion pictures to plays to opera and even informational and educational programs. Some manufacturers are busily trying to obtain the rights to current-run motion pictures. One manufacturer (Philips/MCA) plans to provide text—illustrations and print—materials that permit the user to scan or read single pages forward, backward, or at random simply by pressing a pushbutton switch.

Although a video disc might look like an audio disc, the similarity is only superficial. By modern high-fidelity audio recording standards, the transient flow of information bits dealt with is calculated to be 300,000 bits/second. Consequently, LP records have the ability to accommodate a density of about 5,000 bits/square millimeter. The result is that a 33 $\frac{1}{3}$ rpm LP disc can easily accommodate 30 to 45 minutes of audio program signal.

The transient information flow required to present a TV picture today is about 100 times more intense than that of sound transmission. A storage medium with the information-density capacity of a video disc would have to offer 100 times more capacity in the same or enlarged surface area for recording the same length (in time) program in video as it does in audio.

An ever-widening variety of dense storage and retrieval techniques and technologies for use with a reasonably sized disc have been demonstrated since 1970. Three leading methods—from RCA, Teldec (Telefunken/Decca), and Philips/MCA—have emerged as of this writing. Because it is the only system currently

NOVEMBER 1975

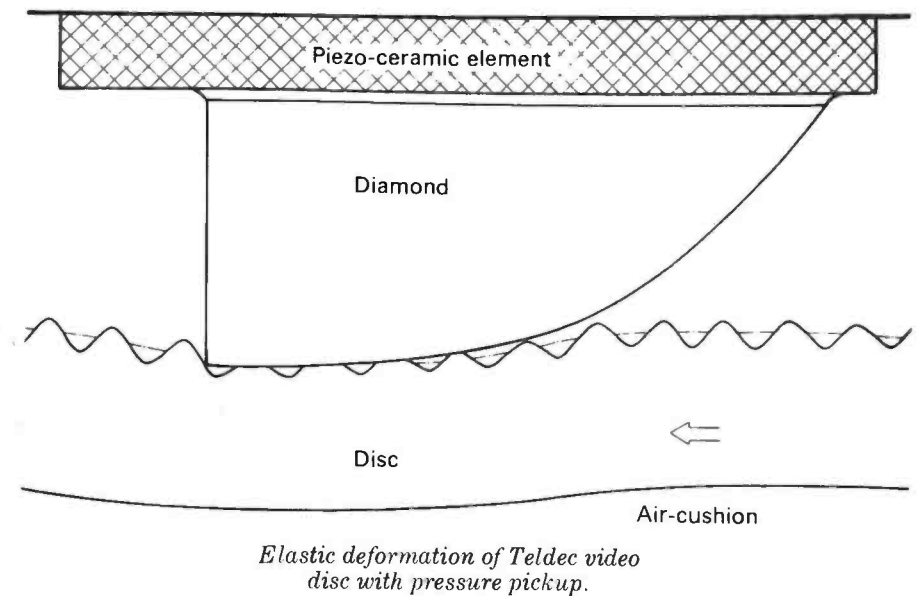

available, we will take a detailed look at Teldec's pioneering work as an example of the problems faced and as a means for comparing the different solutions to the problems. (Teldec's "TeD" system, a cooperative effort between AEG-Telefunken and British Decca, first demonstrated its solution to dense storage technology with a working monochrome system in June 1970.)

The standard LP audio disc contains 250 to 350 grooves/radial inch, with information recovery dependent upon a side-to-side (lateral) stylus excursion. Teldec discovered that, by adopting a frequency-modulation carrier oscillation technique, a single cutting amplitude could be employed during disc mastering to handle the full required frequency range of the video and audio signals within a constant track width. This also permitted the use of an up-and-down (vertical)

stylus excursion method for signal information recovery. Teldec was able to almost eliminate the guard space allowance between the tracks, with the result of raising the number of tracks to 3500/radial inch. This gave the needed 100-fold increase in storage capacity from the same surface area used in audio discs, and it made possible a 12" disc.

The problems of TV's high-frequency range and dense information storage encountered in making the recorded video disc are similarly overcome in retrieving the information from the disc. The stylus for an LP can easily respond as mechanical movement at audio frequencies. However, the mass of the stylus of an audio cartridge is too great to permit such response at the much higher TV frequencies. Needless to say, the various companies have solved the problem in their own special ways.

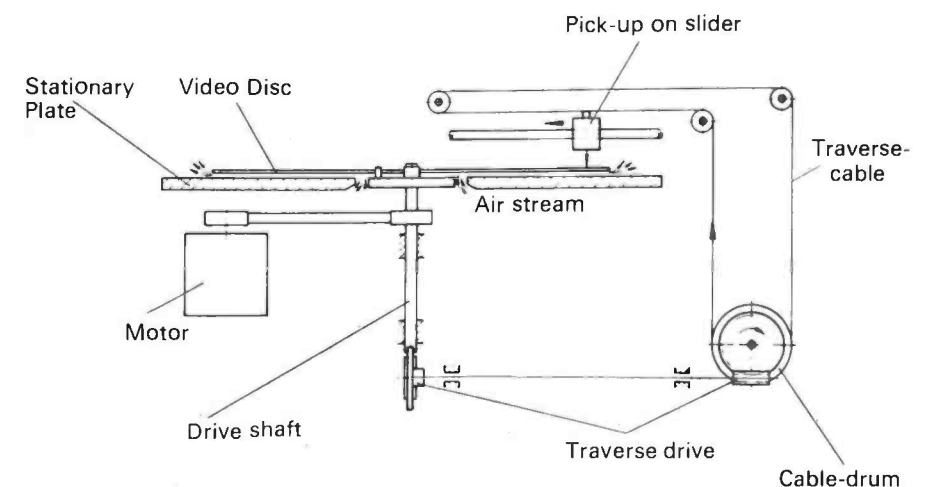


Diagram shows mechanical details of Teldec's disc drive and signal pickup system.

Teldec's "Stylus" Player. In the Teldec system, the information is recorded as deformations in the groove track over which a diamond rides and is sensed as changes in pressure. The stylus tip is in the shape of a sled runner with a gradual radius on the leading edge (relative to disc rotation) and a sharp trailing edge. During playback, the leading edge glides smoothly along the groove over the deformations without damaging them. As the deformations move under the stylus, they become compressed. The sharp trailing edge of the stylus runner passes over the compressed deformations, causing them to spring back to their original shape. In doing so, the signal on the stylus is registered as a constantly varying pressure. The diamond stylus is rigidly fixed to a piezoceramic element that converts pressure variations into electrical picture and sound signals. The sound, recorded in the same fashion as the video, is recovered as pulses that appear during the blanking interval between horizontal line scans.

Consisting of 30 frames/second (equivalent U.S. standards), Teldec's color TV picture is recorded on the disc with each frame occupying one full rotation of the disc. The disc must

rotate at 1800 rpm, which is readily accomplished in synchronization with the power line frequency. Rather than riding on a conventional turntable, the disc is center-positioned on a spindle and is supported on a cushion of air above a stationary platter. Instead of being freely guided by the groove, as with an LP, the video disc's stylus assembly traverses the disc's surface by a simple drum, cable, and pulley arrangement run by the same motor that turns the disc spindle. (The easily scratched disc is not handled by the user. An automatic mechanism extracts it from the protective envelope and returns it after play when the envelope is inserted into the machine by the operator.)

The entire player, with its electrical circuits, is about the size of a large briefcase. It is independent of the TV receiver, providing a modulated r-f sound-and-picture signal on an unused channel through the receiver's antenna terminals.

As the system is currently designed, Teldec's video disc has a playing time of 10 minutes.

P/M's Laser Player. Philips/MCA and RCA have taken the video disc considerably further than Teldec has

to date in terms of playing time. Both companies pack greater numbers of grooves to each inch on their disc. Also, both have developed their own unique information recovery transducer systems that are said to be less expensive per hour of use, cause less wear on the disc, and have longer operating lives. Their discs are also designed to be more rugged and easier to handle than are Teldec's.

N.V. Philips and MCA initially pursued separate development of laser/optical systems but have recently combined their efforts. In March of this year, an impressive demonstration of the joint venture was given. Magnavox, now a subsidiary of North American Philips, is said to be planning to manufacture a U.S. P/M video disc player by the fourth quarter of 1976. The large entertainment conglomerate of MCA will be handling programming and disc mastering and replication for the U.S. market.

The P/M system employs a very precisely controlled laser beam to record information on and recover it from the video disc. In recording, a laser is used to cut minute oblong depressions that represent sound, color, and brightness information. About 0.7-micron wide, the depressions vary by 0.8 to 2.5

microns in length and follow a continuous spiral path. Because of this extremely small size and the fact that the tracks can be spaced less than 2 microns apart, P/M is able to achieve about 12,500 tracks per radial inch. This is almost three times more than is possible with the Teldec approach.


The P/M disc consists of three parts: protective layer, information layer, and highly reflective layer of aluminum.

A laser beam in the player is used as a non-contact optical "reader" to recover audio and video information from the disc. Light from a 1-mW helium-neon laser is focused onto the video disc as a spot 1 micron in diameter. This is reflected back from the aluminum layer through a recovery lens that focuses it on a photo detector. The detector converts the beam into an electronic sound-and-picture signal. The spot of light follows the rotating track and intercepts the depressions that contain the video information. As the light rides over each track depression, the amount of light


reflected back is modulated by the length/depth characteristics of the depressions.

A number of different control and servo systems perform various functions: to select and preserve accurate spot tracking and focus; to maintain time-base stability in case of unevenness of the disc surface due to ir-

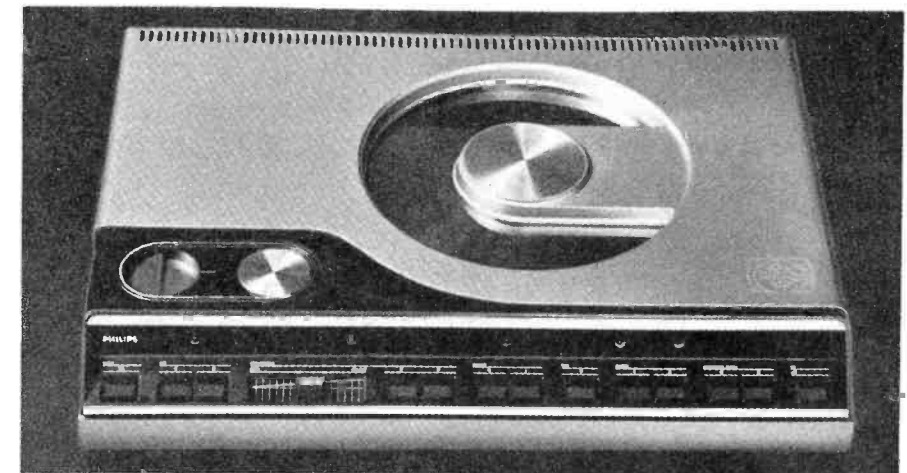regularities or warping and center-hole location eccentricities; and to ignore the accumulation of surface dirt and scratches on the protective transparent coating. Since there is no stylus or physical contact with the disc, the P/M player is a "no-wear" system, and the video disc should theoretically last forever.



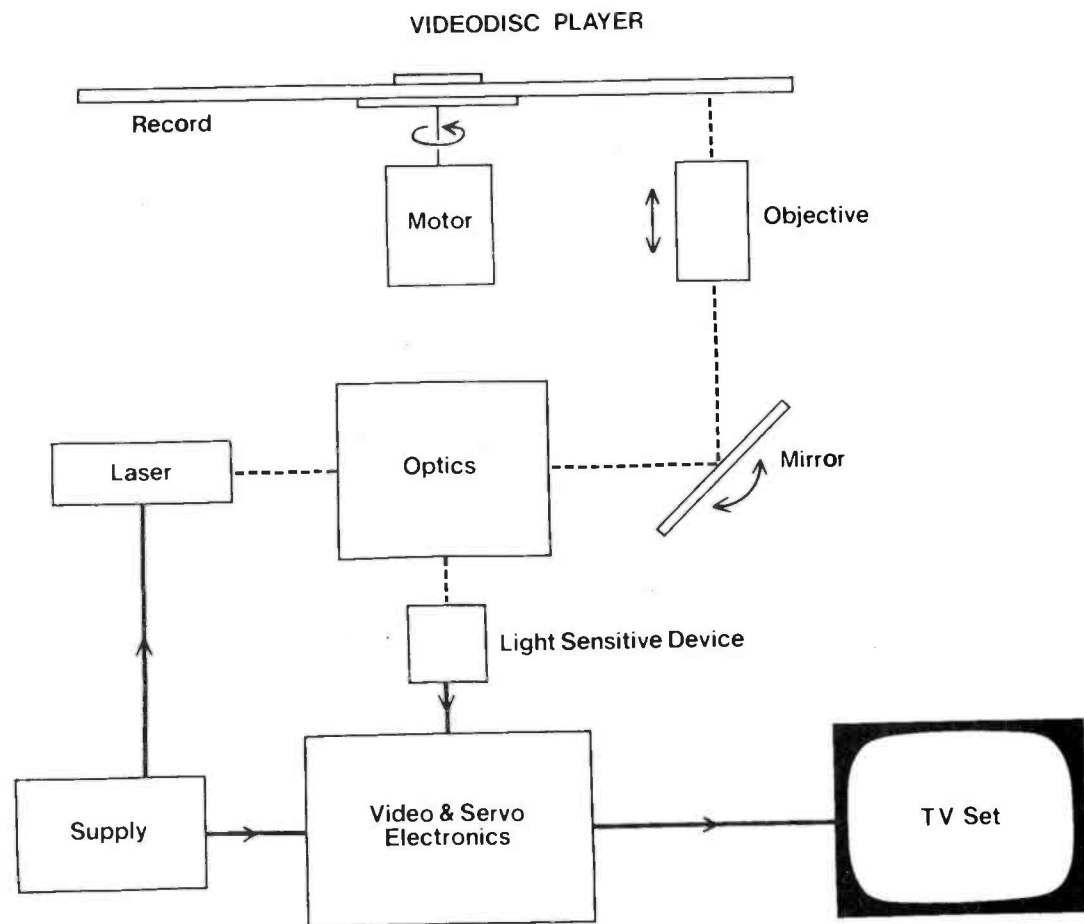Philips/MCA player has controls located on front panel. To left of center is slide-type slow-motion control. Remaining controls on panel are pushbuttons.




Complete Philips/MCA optical laser player system is shown here in block diagram form.

POPULAR ELECTRONICS

NOW!... THE SON OF MEMORY TRANSLATOR...

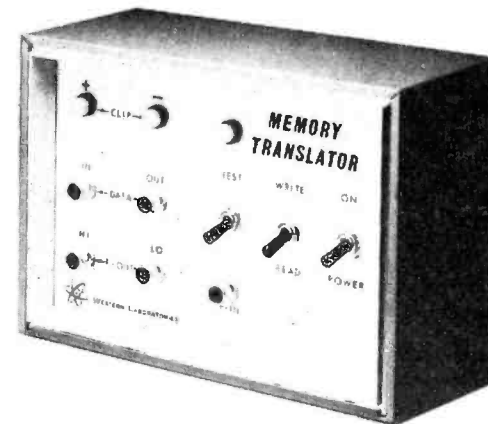(BASED ON THE APRIL 1975 COVER STORY AND CONSTRUCTION ARTICLE)



- 100% portable/micropower operation
- Ready for immediate, direct interfacing with any tape recorder (SMT-12 model)
- FSK modem application (SMT-13)
- 300Hz analog bandwidth
- Digital capability for megabit memories.

COMPLETELY ASSEMBLED AND TESTED!
Both models are available complete for \$169.95 each

Product information available upon request. (213) 793-0148
Western Laboratories, 110 So. Rosemead Blvd., Pasadena, Calif. 91107

CIRCLE NO. 85 ON FREE INFORMATION CARD

In a hurry? try these high-performance A·C·E All-Circuit Evaluators

7 models for fast building and testing of circuits

All solderless plug-in tie-points

photo ACE 227

On all models... simply plug in your components and interconnect with 22-ga. solid wire. All models accept all DIP's, TO-5's and discretes with leads up to .032" diameter.

obsoletes ordinary breadboards

Multiple buses can easily be linked for power and ground distribution, reset and clock lines, shift command, etc. Bases: gold-anodized aluminum. Terminals: non-corrosive nickel-silver. Four rubber feet included.

Order No.	ACE Model No.	Tie Points	DIP Capacity	No. Buses	No. Posts	Board Size (inches)	Price Each
923333	200-K (kit)	728	8 (16's)	2	2	4-9/16 x 5-9/16	\$18.95
923332	208 (assem.)	872	8 (16's)	6	2	4-9/16 x 5-9/16	28.95
923334	201-K (kit)	1032	12 (14's)	2	2	4-9/16 x 7	24.95
923331	212 (assem.)	1224	12 (14's)	8	2	4-9/16 x 7	34.95
923326	218 (assem.)	1760	18 (14's)	10	2	6-1/2 x 7-1/8	46.95
923325	227 (assem.)	2712	27 (14's)	28	4	8 x 9-1/4	59.95
923324	236 (assem.)	3648	36 (14's)	36	4	10-1/4 x 9-1/4	79.95

We honor M.C. and B.A.C. charges. Add sales tax on OH and CA orders. (F.O.B. Painesville on company P.O.'s.) Dealer inquiries invited

SHIPPING/HANDLING C.O.D. fees from this chart:

Up to \$10.00	\$1.00
\$10.01 to \$25.00	1.50
25.01 to 50.00	2.00

All products guaranteed to meet or exceed published specifications

A P PRODUCTS INCORPORATED
Box 110-H • Painesville, OH 44077 • 216/354-2101

CIRCLE NO. 2 ON FREE INFORMATION CARD

NOVEMBER 1975

The disc rotates at 1800 rpm. As a consequence of the 30-frame/second U.S. NTSC TV system, the disc makes one revolution of 360° for each frame. A radial deflection mirror forms part of the laser beam control system. P/M says that the radial deflecting mirror can easily be made to control the beam during the vertical interval to repeat the same track, jump back one or more tracks, or jump forward one or more tracks. Since this occurs during the vertical blanking period of the frame, and provided that not too big a jump is made during this limited time, all manner of still, fixed, and variable slow forward and reverse motion, and random-access effects can be obtained by "playing" the controls. A digital index counter is used to help pinpoint the location of a specific selection or frame.

The disc will be single-sided and will contain up to 30 minutes of program material. Company spokesmen say that they will be able to meet the announced price of \$500 for the player and still be able to offer the stop/slow/variable-frame display system that the player seems so uniquely able to provide.

As announced, the P/M player will offer modulated r-f picture and sound signals through the antenna input of any conventional TV receiver. Two separate 15,000-Hz audio output channels will also be provided for feeding into a stereo audio system.

RCA's "Capacitive" Player. In a number of respects, RCA's capacitive-mechanical video disc system


VIDEO DISC SYSTEM COMPARISON CHART			
	TELDEC	PHILIPS/MCA	RCA
DISC:			
Composition	PVC	Mylar/reflective aluminum	vinyl/metal dielectric/oil
Diameter	8"-10"	8", 12"	12"
Playing time	10 min.	30 min.	60 min. (2 sides)
Speed	1800 rpm	1800 rpm	450 rpm
Tracks/inch	3500	12,500	5555
Information scheme	groove deformations	long longitudinal pits	transverse slots in grooves
Average life	100 plays (min.)	indefinite	100 plays (min.)
Estimated cost	\$4-\$10/disc	\$2-\$10/program	\$10/disc
PLAYER:			
System type/transducer	mechanical contact/pressure	no-contact/optical laser	mechanical contact/capacitive
Estimated price	\$500	\$500	\$400
PICKUP:			
Type	diamond stylus	laser	sapphire stylus
Estimated life	70-100 hours	NA	200 hours (min.)
Replacement price	NA	NA	less than \$10 for stylus/cartridge assembly

NA = Information not available at this writing.

falls between the Teldec and P/M systems in terms of storage-density and playing capability. RCA spokesmen say that a calculated choice was made to design a system that offers a player/disc component system that keeps the difficult parts in the factory

and the noncritical parts in the home. By using a stylus tracking system, a capacitive-sensing signal-detection technique, and a 450-rpm disc speed, RCA believes it has struck the best possible balance in manufacturing, reliability, operational simplicity, low purchase/operating cost, and duration of available playing time. Except for the stylus assembly, the company states that the electrical and mechanical assemblies for the player are largely off-the-shelf items.

Similar to Teldec and unlike P/M, RCA uses a grooved disc that mechanically guides the stylus over the signal track. The grooves are spaced 4.57 microns apart (center to center). There are 5555 grooves per radial inch. The disc itself consists of five layers of material sandwiched together. The vinyl core contains the information slots that vary in length between 0.23 and 1.23 microns. (The slots are cut in the master by a high-resolution electron beam in a vacuum chamber.) Metallic and styrene coatings are then applied to both sides of the disc. Finally, a layer of oil that increases the life expectancy of both the

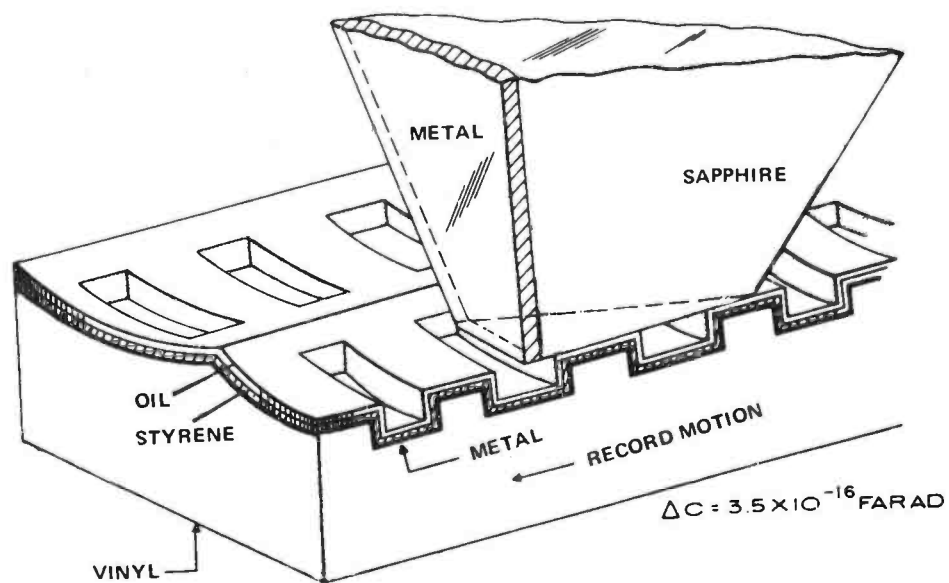

Detail view of RCA's stylus tip and cutaway view of VideoDisc surface. Metal layers on disc and sapphire stylus form two plates of capacitive element.

Carisma*



Model DP-5000

*

(Kar-iz'ma) The ultimate in quality, engineering advancement and appearance of car sound system equipment that sets it apart from all competitors, thereby making it the auto stereo radio line for car enthusiasts seeking the finest in product and performance.

In-Dash Digital Clock/AM/FM MPX Stereo Radio

There's only one AM/FM stereo radio with built-in digital clock, and this is it. Features: large digital readout time piece; solid state and integrated circuitry; FM stereo indicator beacon; quick-set adjustable shafts; vinyl padded faceplate; in-dash installation (under dash also); built-in AFC (Automatic Frequency Control); easy access time setting control.

In-Dash Deluxe Cassette Stereo Tape Player with AM/FM Stereo Radio

Features: touch or lock pushbuttons for fast forward, fast rewind, eject; color-coded indicator beacons for FM, AM stereo broadcast and cassette tape end; pushbutton Mono-Stereo control; quick-set adjustable shafts easy-to-read beveled radio dial; easy in-dash installation.

Model BM-1335

In-Dash Matrix Quad 8-Track Stereo Tape Player with AM/FM Stereo Radio

Features: 5 pushbuttons for AM or FM station selection; fully adjustable shafts for custom installation; positive action slide switches for AM-FM and 2/4 channel quad sound; pushbutton cartridge eject; MPX (stereo) indicator beacon; digital program readout lamps; non-protruding safety cartridge position.

Model BM-1150

Under-Dash Matrix Quad/Stereo 8-Track Tape Player with FM Stereo Radio

Features: 4-channel matrix system separates 2 channel stereo reception into 4 distinct parts for full dimensional sound; fast forward selection; digital program read-out lamps; slide balance control; tape eject button; tape reading lamp; burglar alarm system.

Model BM-1950

In-Dash AM-FM-MPX (Stereo) Radio/8-Track Tape Player


Features: cartridge compartment head adjustment; AM-FM slide bar selector; pushbutton cartridge door; Mono-Stereo slide control; pushbutton local-distance sensitivity control; cartridge compartment Antenna Trimmer; multicolored program indicator beacons.

Model BM-1125

The Model BM-1125 incorporates a new technological advancement in car stereo electronics—an illuminated radio dial in the tape cartridge door. This unit is not just an outstanding AM-FM-MPX Radio. When an 8-Track cartridge is inserted into the tape door the radio dial hinges back, out of the way, and your Stereo Radio becomes an 8-Track Stereo Tape Player.

Now that you know what we look like, drop by your local Boman Astrosonix Dealer and hear what we sound like.

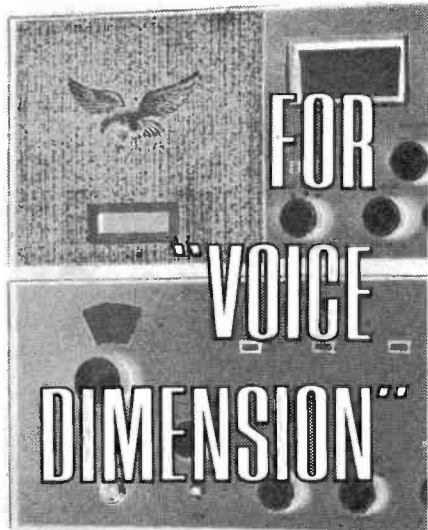Boman Astrosonix
A DIVISION OF
BOMAN INDUSTRIES
9300 HALL ROAD, DOWNEY, CA. 90241 (213) 869-4041



... choose the engineering excellence of a Browning base station or mobile. Its outstanding depth of audio performance lets you go beyond casual fun to full CB enjoyment! Browning's unique "voice dimension" characteristics represent a skillful blending of audio power and fidelity — and are the result of over half a century of adherence to exacting production standards and time-consuming craftsmanship. You may spend a few more dollars — you may even have to wait for delivery — but if you're serious about CB, you'll choose Browning!

For your free full-color catalog, write ...
browning
 Browning Laboratories, Inc.
 1269 Union Avenue
 Laconia, New Hampshire 03246
 Telephone (603) 524-5454

disc and the stylus is applied to both sides of the disc.

The signal is recovered from the disc by capacitively sensing the information elements pressed as transverse slots in the groove. A plow-shaped sapphire stylus, when in contact with the groove, extends about 3 to 10 microns along the groove. A thin coating of metal on the flat trailing edge of the stylus serves as one plate of a capacitor, while the metallic layer in the disc represents the other plate. The styrene coating on the disc serves as the capacitor's dielectric.

As the stylus travels along the groove over the information slots, the capacitive voltage relationship between the insulated plates fluctuates by amounts that depend on whether or not the area immediately beneath the stylus is or is not a slot cavity. The changing capacitance is sensed by a tuned circuit, of which the stylus "plate" is one element, thereby providing the signal information for amplification and processing into a standard video/audio signal.

Variations in disc speed caused by power-line frequency fluctuations, as well as disc imperfections caused by warping and centering problems, must be corrected to insure a steady, fault-free picture. While P/M uses various compensating servo loops, RCA says it has made a special design effort to keep such complexity, with corresponding chances for misadjustment and malfunction, to a minimum. RCA has designed a single servo stylus "arm stretcher" arrangement that consists of a small electromechanical transducer similar to the moving coil in a speaker that continuously drives the stylus arm back and forth along its long dimension according to the variations.

The arm stretcher is housed in a cage driven by a toothed belt to follow the basic groove spiral pitch of the disc. The entire arm sweeps across the disc's surface in a manner similar to that used by Teldec. RCA says that this combination of a belt-driven arm cage and the mechanically tracking stylus, guided by the actual groove spiral, preclude the necessity of holding to difficult mechanical manufacturing tolerances. The player has a built-in one-line horizontal delay for substitution of a preceding picture when a noise or similar defect occurs in an upcoming picture line.

Teldec and P/M have chosen an 1800-rpm playback speed that

equates to one frame every 360° of disc rotation, making it potentially easy to use the disc for still/slow/single-frame viewing. RCA's choice of 450 rpm, equating to four frames per 360° revolution (one frame every 90°), while not precluding these framing effects, makes providing for such features more complex and expensive. The company says that its choice of a 90° frame is critical to greater utility.

RCA is able to design an overall system that can currently offer a combination of the longest playing time with high picture quality. A two-sided disc that will give up to a 60-minute per disc program playing time will be offered with the RCA system.

The slower speed of the RCA player contributes to its ability to offer a less expensive system. The use of a simple stylus arm stretcher is also said to be less expensive than the means adopted by P/M to stabilize signal timing. RCA's lower-speed player enables its more complex stylus assembly to handle the expected amount of disc unbalance, eccentricity, and warp during playback.

While not yet committed to a market entry date, RCA says it could begin to provide players and discs in small retail quantities in the third or fourth quarter of 1976. Prices for the player and individual disc have been tentatively set at \$400 and \$10, respectively. The disc will give some 100 (minimum) plays in normal use, and the operating life of the stylus will be a minimum of 200 hours. A user-replaceable stylus/cartridge assembly is expected to sell for less than \$10. The player's modulated r-f output is set to an unused channel of any TV receiver, and separate outputs to drive a stereo system will be provided.

Conclusion. In this article, we have placed the emphasis on three systems that are almost certain to be available by the end of 1976. However, a host of other systems are under development. These include magnetic card (Sony) and magnetic disc (Bogen) systems that can record and erase and an optical disc system (i/o Metrics) that can record but not erase.

One thing is certain: separately or together, these home video systems will herald a new era in home entertainment. The prices will be right. And if all goes as expected, the programming will be on a par with the best live and film entertainment available anywhere today.

FREE!

The all-new 1976 Lafayette Radio Electronics Catalog



The most comprehensive consumer electronics catalog available. Fully illustrated, the Lafayette catalog features: high fidelity components and accessories of every description; tape equipment, police/public service radios; car stereo; CB and communications equipment; TV/FM and communication antennas; public address; telephones accessories; test equipment; tools; musical instruments and amplifiers; electronic calculators and watches; books; security systems; and an exciting new line of parts, tubes; solid-state devices and hardware plus exclusive Lafayette and Criterion brand products backed by our 55 years of experience. Our modern, complete facilities assure you of continual satisfactory service.

Also see the finest in brand name products which offer outstanding features, performance and reliability at Lafayette's competitive prices.

- Stores Coast to Coast
- Personalized Service and Demonstrations
- Check Your White Pages or Shop by Mail
- Use Your BankAmericard or Master Charge on Mail Orders, Too!



We've got an exciting selection of stereo, quad components and compacts.



We've got everything in car stereo, plus auto test equipment and driving aids.



We're communication specialists, with a wide selection of CB and Ham gear, police and fire receivers, weather radios.



We've got the parts, tubes, hardware you need for hobby and experimenter projects of every type.

Lafayette
 the electronics shopping center

Mail Coupon Today! →

FREE!

Lafayette Dept. 35115
 Radio Electronics, 111 Jericho Turnpike, Syosset, L.I., N.Y. 11791

Send me your FREE 1976 Catalog.

Name Apt.
 Street
 City State
 Zip

Send a 1976 Catalog to my friend.

Name Apt.
 Street
 City State
 Zip

Learning with CIE is

Electronics no picnic.



**It takes work.
And a few sacrifices.
But it's worth it!**

The minute you start your CIE course you'll see why CIE is different than other home-study schools.

Because as a CIE student you'll get the kind of electronics training that prepares you for a career, not just a job. We'll give you a meaningful, well-rounded foundation in electronics theory and practice. And with our

Electronics and some people might assume there will be no new frontiers . . . no new worlds to conquer. Not so.

Electronics is still growing. In nearly every one of the new and exciting fields of the Seventies you'll find electronics skills and knowledge in demand. Computers and data processing. Air traffic control. Medical technology. Pollution control. Broadcasting and communications.

Importance of an FCC License

If you want to work in commercial broadcasting . . . television or AM or FM broadcasting . . . as a broadcast engineer, federal law requires you to have a First Class Radiotelephone License. Or if you plan to operate or to maintain mobile two-way communications systems, microwave relay stations or radar and signaling devices, a Second Class FCC License is required.

because the vast majority of CIE students have. In fact, based on continuing surveys, close to 9 out of 10 CIE graduates have passed their FCC exams!

So if you are serious about getting ahead in Electronics . . . if you are willing to put in the extra work . . . get in touch with us.

We have many *career* courses for you to select from. If you already have some electronics training, you may want to skip our beginner-level courses and enroll in an intermediate program. Or, if you're really hot, there's a tough, college-level course called "Electronics Engineering" that can make you even better.

Send today for FREE school catalog

Send today for our FREE school catalog and complete package of *independent home-study* career information.

For your convenience, we will try to make a representative call to assist in selection. Mail reply card or card to CIE . . . or write: Cleveland Institute of Electronics, Inc., 1776 East 17th Street, Cleveland, Ohio 44114. TODAY.

All Benefits

All career courses are approved for educational benefits under the G.I. Bill. If you are a Veteran or in service now, you can receive a box for G.I. Bill information.

Free School Catalog

Plus Free Booklet on FCC Licenses

Mail attached postcard today for FREE information about career electronics.

YES! I want your FREE "Education-by-Mail" career information.

I am especially interested in:

- | | |
|--|--|
| <input type="checkbox"/> Electronics Technology | <input type="checkbox"/> Industrial Electronics |
| <input type="checkbox"/> FCC License Preparation | <input type="checkbox"/> Electronics Engineering |
| <input type="checkbox"/> Color TV Maintenance | <input type="checkbox"/> Other _____ |
| <input type="checkbox"/> Mobile Communications | |

PRINT NAME _____

ADDRESS _____ APT. _____

CITY _____

STATE _____ ZIP _____ AGE _____
PE-88


Check box for G.I. Bill information.

- Veteran On Active Duty

CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114
Accredited Member National Home Study Council

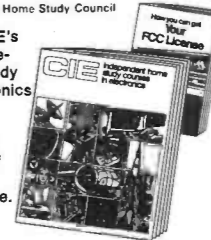Find out about CIE's wide range of independent home study courses in Electronics . . . beginner, intermediate, advanced college level. The value of an FCC License and how to get one. No obligation. FREE.



Electronics, Inc.

Cleveland, Ohio 44114
Home Study Council

Information package today.

Electronics PE-88
Engineering

_____ Apt. _____

_____ Age _____

On Active Duty

A New Industry Standard for FM Tuner Measurement

PART ONE

BY LEN FELDMAN

AFTER an undisturbed 16-year reign, the old "IHF Standard Methods of Measurement for Tuners" (IHF-T-100) has been succeeded by the new "Standard Methods of Testing Frequency Modulation Broadcast Receivers." This new Standard (IHF-T-200 and IEEE Std 185-1975), was produced under the auspices of the IEEE, the IHF, and the EIA. It focuses on some key areas of tuner performance—including stereo—that were inadequately covered by the old Standard. (The old one was developed before stereo FM programming was authorized.) Also, it establishes new reference levels for sensitivity, selectivity, and distortion measurements, among others.

Hopefully, this new set of guidelines will enable manufacturers to relate their products' performances more meaningfully, and allow the consumer to make a well-informed decision when he goes to the marketplace.

The Femtowatt. One of the Standard's more important provisions deals with the basic reference level of signal strength. Previously, the microvolt (10^{-6} V) was used, but now the femtowatt (10^{-15} W) supplants it. Thus, instead of considering the amount of signal voltage developed across the tuner's antenna input, many

measurements will be based on the amount of power delivered to the tuner. By definition, an available signal power level of one femtowatt is the reference 0 dBf—not to be confused with its cousin, dB, which expresses something completely different.

But why power? The previous standard was ambiguous about the true amount of signal delivered to the

Copies of the new "Standard Methods of Testing Frequency Modulation Broadcast Receivers," IEEE Std 185-1975 and IHF-T-200, 1975, are available from the Institute of High Fidelity, 489 Fifth Ave., New York, NY 10017 and from the Institute of Electrical and Electronics Engineers, 345 E. 45th St., New York, NY 10017. 35 pages (8½" x 11), \$6.00 soft cover.

tuner. For example, most signal sources can deliver a higher voltage across an open circuit than across a resistive one, so "open-circuit" microvolts would produce a different result than "terminated" microvolts. Furthermore, tuner inputs are commonly either 75 or 300 ohms, and a standard based on voltage led to a 6-dB hedge due to loading effects.

What really determines signal

strength is the amount of power that's available, which is related to the voltage by the equation $P = E^2/R$. For example, 10 μ V across a 300-ohm input develops 333×10^{-15} W, but the same voltage across 75 ohms produces 1333×10^{-15} W—an increase of about 4 times, or 6 dB! Some manufacturers might quote the 75-ohm figure, which would apparently give them hotter receivers than those whose sensitivity was rated at 300 ohms. Now that everyone is expected to use the new power rating, specification differences based on type of termination will no longer be exaggerated.

Naturally, it will take time for people to get used to the dBf idea, so the IHF suggests that manufacturers publish the "new" figures alongside the old microvolt ones. This should make the transition smoother. The relationship between available power in dBf and open-circuit voltage across a 300-ohm impedance is shown in the nomograph of Fig. 1. Here we see that 0 dBf is equivalent to 1.1 "open-circuit" μ V. Since the units increase exponentially, we'll now be reading sensitivity ratings such as 5 dBf or 1.96 μ V.

Signal generators that are used in FM tuner measurements usually have an output impedance of 50 ohms (unbalanced). To match this to the common 75- or 300-ohm balanced or un-

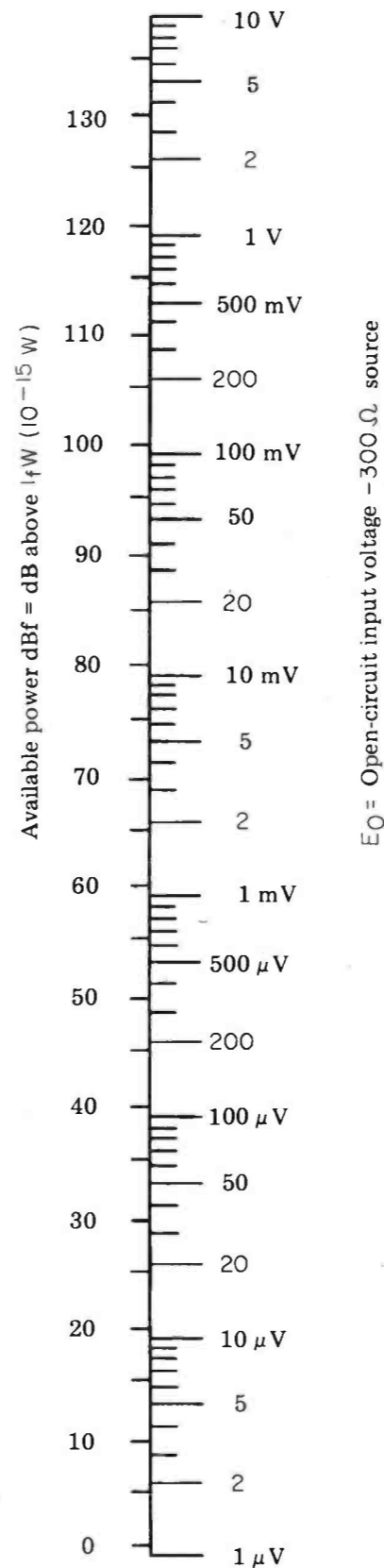


Fig. 1. Voltage/power nomograph relates available power in dBf (left scale) to open-circuit microvolts (right scale).

balanced tuner inputs, the Standard suggests eight dummy antenna configurations (Fig. 2). For each network, E_G is the terminated generator output voltage, usually indicated on a calibrated attenuator. (This works out to be half the open-circuit generator output voltage.) The open-circuit voltage at the receiver input terminals is designated as E_O . Power available to the receiver is P_A , and the power loss incurred by the dummy antenna (in dB) is P_L . Equations relating these variables are given in each case.

For example, suppose we're measuring the sensitivity of a tuner using the dummy antenna in Fig. 2A. With the "old" IHF procedure, we reached the IHF sensitivity when the generator's attenuator read 4.0 μ V. The reading would then be divided by 2, since half the voltage was "dropped" across the resistive network. Thus, the "old" IHF sensitivity would be 2.0 μ V.

In terms of the new Standard, the 4.0 μ V reading is E_O , the "open-circuit" voltage. Accordingly, no division is

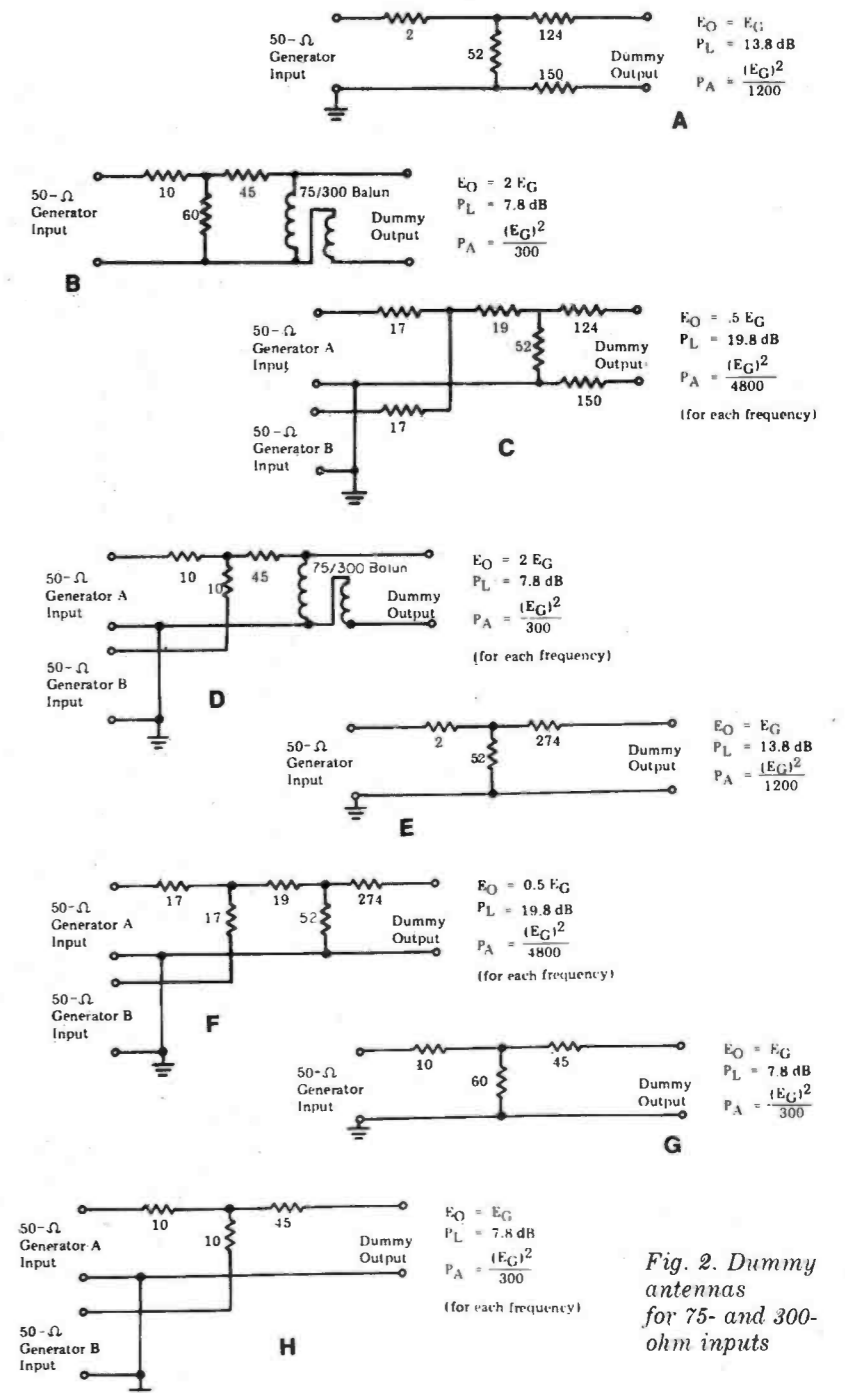


Fig. 2. Dummy antennas for 75- and 300-ohm inputs

required since $E_0 = E_G$ for this network. A glance at Fig. 1 shows us that the "new" sensitivity is about 11 dBf. If greater accuracy is desired, you can calculate the dBf figure using the formula: $\text{dBf} = 20 \log (E_0/1.1)$, where E_0 is expressed in μV . For this particular case, E_0 is $4.0 \mu\text{V}$, so the sensitivity in dBf is $20 \log (4.0/1.1)$ or 11.213 dBf. A chart of dBf values versus generator output in μV is shown as Table I, and includes conversion formulae.

New Mono Specifications. It has become obvious that IHF sensitivity alone does little to point out significant differences between two modern tuners or receivers. Of far greater im-

portance is the nature of the "quieting slope," and more specifically, the point where a S/N ratio of 50 dB is obtained. For this reason, the new Standard requires disclosure of the "50-dB Quieting Sensitivity," expressed in dBf. The familiar "Usable Sensitivity" spec—the level of signal resulting in a combined noise and distortion content of 3% (–30 dB)—will also be included in dBf, because the public is familiar with it, and it takes into account both noise and distortion.

Although only residual noise is measured by the "50-dB Quieting Sensitivity" test (the modulating signal is turned off), it is of great interest

to determine how much harmonic distortion exists at this point. Therefore, a "Distortion at 50-dB Quieting" spec has been established. The distortion readings for this test and those at higher signal levels must be quoted for three frequencies—100, 1000, and 6000 Hz. Previously, THD was most often quoted at 1000 Hz, but it's well-known that most audio products exhibit lowest THD content in the mid-range. Hence, the additional measurements will give a more realistic picture of overall performance.

The Committees that collaborated on the Standard felt that 6000 Hz was the highest practical frequency to conduct this test. Harmonics of higher-frequency fundamentals are not only beyond the range of human hearing, but also extend past the upper limit of FM broadcast audio (15,000 Hz).

Strong Signal Measurements.

Tests formerly conducted at high (1000 "terminated" μV) signal levels, such as "Ultimate S/N," "Ultimate THD," and "Stereo Separation" will now be performed at 65 dBf. That's roughly 1,970 "open-circuit" μV , or 970 "old IHF" (300-ohm) μV —almost the same signal level previously used. Capture ratio is measured in much the same way as before, but the readings must be taken at signal levels of 45 dBf and 65 dBf. The poorer of the two figures must be published as the "rated" capture ratio in dB.

Two Selectivity Specs. "Alternate Channel Selectivity," which spells out the degree of interference from an FM station 400 kHz away from the desired one, will now be measured at 45 dBf (desired signal input), or about 97 "old IHF" μV .

Now, we have another selectivity spec that must also be published—"Adjacent Channel Selectivity." The "numbers" are not going to look too good, of course. Obviously, it's much tougher to suppress signals 200 kHz away than those 400 kHz removed—at least it is when you're trying to maintain sufficient bandwidth for low distortion and good phase linearity. But as the public gets used to seeing "Adjacent Channel" figures in the 20-to-30-dB range, this "embarrassment" should fade away. (This concludes Part One. Next month, we'll examine new methods of curve plotting, and look at the new Stereophonic Specifications.)

Table I. Available Power From Dummy Antennas in Terms of Terminated 50 ohm Generator Output E_G

Impedance Dummy	300 ohms (B),(D)	300 ohms (A),(E)	300 ohms (C),(F)
Impedance Dummy	75 ohms (G),(H)		
dBf			
0	0.55 μV	1.1 μV	2.2 μV
5	0.97 μV	1.9 μV	3.9 μV
10	1.7 μV	3.5 μV	6.9 μV
15	3.1 μV	6.2 μV	12 μV
20	5.5 μV	11 μV	22 μV
25	9.7 μV	19 μV	39 μV
30	17 μV	35 μV	69 μV
35	31 μV	62 μV	120 μV
40	55 μV	110 μV	220 μV
45	97 μV	190 μV	390 μV
50	170 μV	350 μV	690 μV
55	310 μV	620 μV	1.2 mV
60	550 μV	1.1 mV	2.2 mV
65	970 μV	1.9 mV	3.9 mV
70	1.7 mV	3.5 mV	6.9 mV
75	3.1 mV	6.2 mV	12 mV
80	5.5 mV	11 mV	22 mV
85	9.7 mV	19 mV	39 mV
90	17 mV	35 mV	69 mV
95	31 mV	62 mV	0.12 V
100	55 mV	0.11 V	0.22 V
105	97 mV	0.19 V	0.39 V
110	0.17 V	0.35 V	0.69 V
115	0.31 V	0.62 V	1.2 V
120	0.55 V	1.1 V	2.2 V

E_0 = open-circuit voltage

$$= \sqrt{4 \times 10^{-15} R \times 10^{\text{dBf}/10}}$$

R = impedance level


dBf = available power for a 1 fW reference level

$$= 10 \log (E_0^2/4R \times 10^{-15})$$

Note: Letters in parentheses refer to dummy antenna configurations shown in Fig. 2.

THE OSCILLOSCOPE GRAPHIC ARTIST

BY MITCHELL WAITE

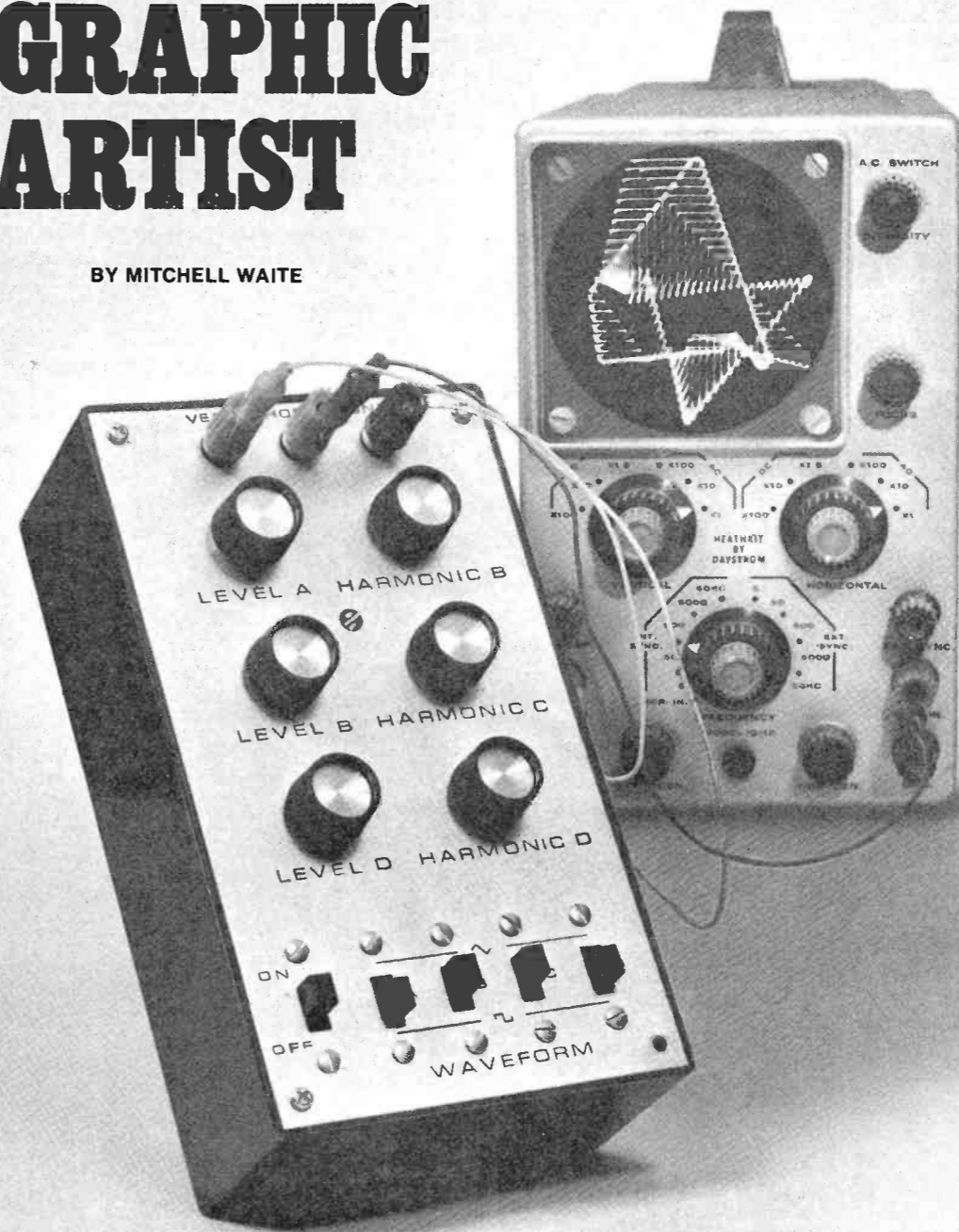

Create exciting,
computer-generated,
three-dimensional
drawings
on your
oscilloscope

A DIM light traces a delicate pattern of geometrical lines on the screen of an oscilloscope. The lines form a rectangle that suddenly tilts back and transforms into a revolving ring of diamonds. You can produce these, plus many more, effects by operating the controls on the Graphic Artist project described here. You can easily make an image rotate in three dimensions, compress and expand, break up into other shapes, or slowly oscillate.

The Graphic Artist is a visual pattern generator that is designed to use the CRT screen of an oscilloscope as a "canvas" and its electron beam as a high-speed "brush." The real-time three-dimensional display on the CRT screen has all the delicate geometric beauty and detail of the computer-generated three-dimensional drawings with which we are all familiar.

The beam in an oscilloscope is forced to follow two complex, harmonically related signals in producing

the geometric patterns. Phase-shift networks, working in concert with a simple modulator, in the Graphic Artist add a signal that produces a depth and volume cue for the scope image.

If you're into electronic music, you might try feeding the output signal of the Graphic Artist into a stereo amplifying system to hear the tones associated with the on-screen images. Even more interesting, you can feed harmonics from a music source into the Artist's circuit in place of the oscillator signals. This allows you to view the patterns created by harmonically related musical notes.

About the Circuit. As shown in the block diagram in Fig. 1, two almost identical signal channels in the Artist are connected to the vertical and horizontal inputs of an oscilloscope. This hookup results in a CRT trace that is known as a Lissajous figure—a

circular-like trace that is proportional to the vertical and horizontal displacement of the scope's electron beam.

Each channel in the Artist consists of two oscillators (A and D) that generate square and triangular waveforms. Added to the signals produced by

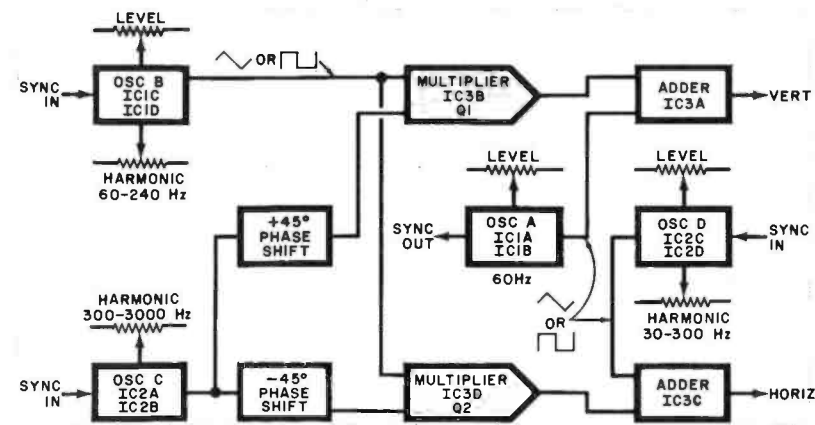


Fig. 1. Block diagram of Graphic Artist.

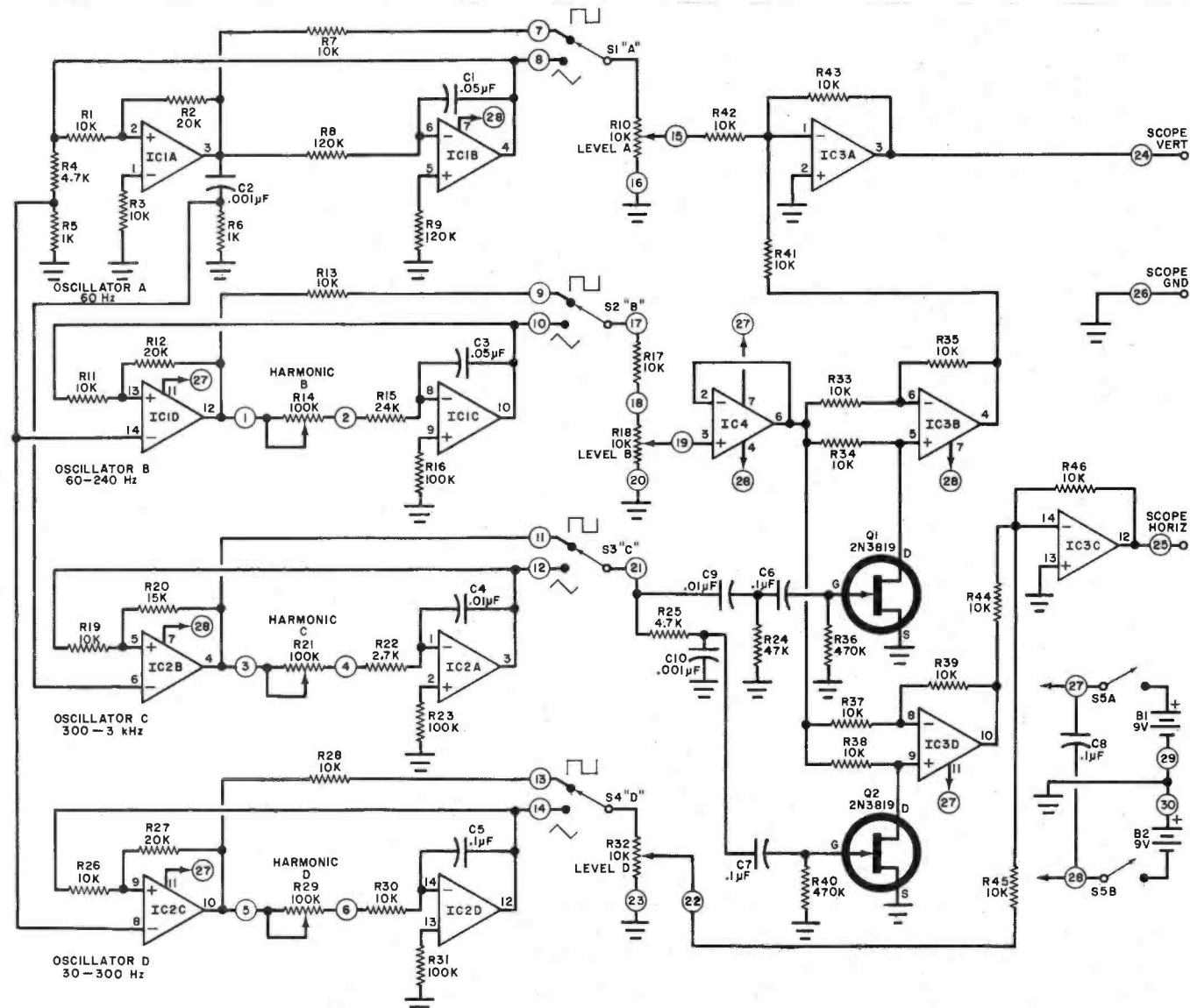


Fig. 2. Oscillators are identical except for frequency-determining elements.

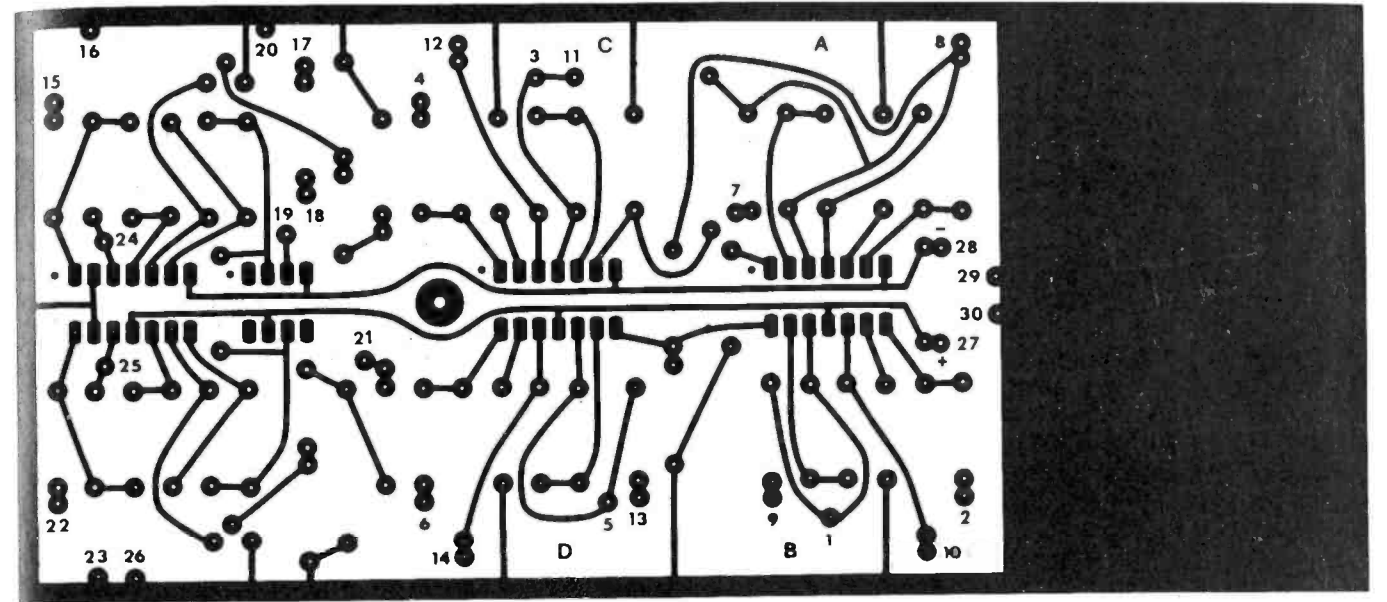



Fig. 3. Etching and drilling (above) and component (right) guides.

PARTS LIST

- B1, B2—9-volt battery
- C1, C3—0.05- μ F Mylar capacitor
- C2, C10—0.001- μ F Mylar capacitor
- C4, C9—0.01- μ F Mylar capacitor
- C5, C6, C7, C8—0.1- μ F 100-volt Mylar capacitor
- IC1, IC2, IC3—Quad 741 operational amplifier integrated circuit (Raytheon RC4136DB)
- IC4—741 operational amplifier integrated circuit
- J1, J2, J3—Five-way binding post
- Q1, Q2—2N3819 junction field-effect transistor

- The following resistors are 1/4-watt 10% tolerance:
- R1, R3, R7, R11, R13, R17, R19, R26, R28, R30, R33, R34, R35, R37, R38, R39, R41, R42, R43, R44, R45, R46—10,000 ohms
 - R2, R12, R27—20,000 ohms
 - R4, R25—4700 ohms
 - R5, R6—1000 ohms
 - R8, R9—120,000 ohms
 - R15—24,000 ohms
 - R16, R23, R31—100,000 ohms
 - R20—15,000 ohms
 - R22—2700 ohms
 - R24—47,000 ohms
 - R36, R40—470,000 ohms
 - R10, R18, R32—10,000-ohm linear taper potentiometer
 - R14, R21, R29—100,000-ohm linear-taper potentiometer
 - S1 thru S4—Spdt slide or toggle switch
 - S5—Dpdt slide or toggle switch
 - Misc.—Printed circuit or perforated board; 7 1/2" L x 4 1/4" W x 2" D (19 x 11 x 5.1 cm) case; knobs (6); battery clips (2); lettering kit; hookup wire; machine hardware; solder; etc.

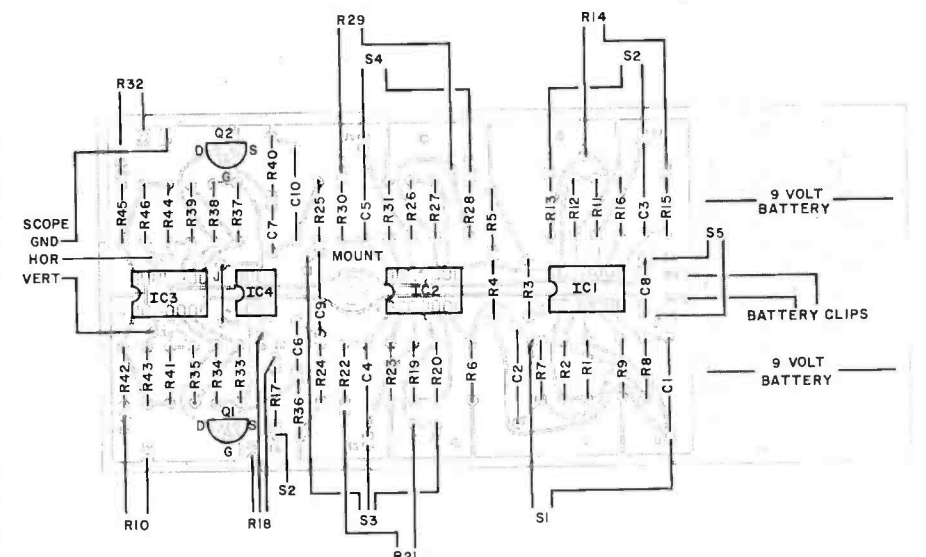Note: The following are available from CalKit, P.O. Box 38, San Rafael, CA 94901: Complete kit #GA-1 (includes components, board, case, but not battery) at \$55; p.c. board #GA-3 at \$7.50. All orders postpaid. California residents, add 6% sales tax.



these oscillators is a common modulated signal derived from oscillators B and C. The overall shape of the Lissajous pattern is set by the signals from oscillators A and D. (For example, a simple rectangle results when triangular waveforms make up these signals.)

The modulation component is comprised of a variable high-frequency carrier from oscillator C and a variable medium-frequency envelope from oscillator B. The carrier is shifted in phase by $\pm 45^\circ$. The $+45^\circ$ component is modulated by waveform B in the multiplier and summed with the waveform from oscillator A in an adder. Likewise, the -45° carrier is modulated by waveform B but is summed with the waveform from oscillator D.

pattern, creating the three-dimensional illusion of volume.

Each oscillator can be switched to generate square waves. Depending on which oscillator is switched to square waves, the pattern will either break up into multiple images or change the character of its surface composition. There are three level controls, which tilt or expand the image and change the relative sizes of the modulating components. The harmonic controls are frequency setting potentiometers that are used to adjust the ratio between the various harmonic signals. The ratios of the signals in turn control the "family" of images you see.

To prevent the patterns from revolving on the screen (this occurs whenever the patterns are derived from uncorrelated oscillators), one of the four oscillators is fixed in frequency. The output from this "master" oscillator is used to synchronize

the remaining oscillators, forcing them to run at an exact multiple of the syncing frequency.






In addition to using the controls on the project, you can also use the vertical- and horizontal-gain controls on the scope to adjust the width and height of the images.

Circuit Details. As shown in Fig. 2, the four oscillators are identical except for their frequency-determining elements. Oscillator A is fixed at approximately 60 Hz by R8 and C1; oscillator B is variable from 60 to 240 Hz; oscillator C is variable from 300 to 3000 Hz; and oscillator D is variable from 30 to 300 Hz. The oscillators are arranged in a classical comparator-integrator configuration.

Taking oscillator A as an example, IC1A uses R1 and R2 to set the trip point at about $\pm V_{cc}/2$. The output of this comparator connects to integrator IC1B, which in turn, connects back to IC1A's input. When IC1A's output is at -9 volts, IC1B linearly charges C1 through R8. Hence, the output of IC1B is a positive-going ramp. As soon as the ramp reaches $V_{cc}/2$, IC1A changes to the positive state and IC1B linearly discharges C1 to initiate a negative-going ramp. When this ramp reaches $-V_{cc}/2$, IC1A trips to the negative state and the cycle repeats itself.

Potentiometers are used to set the frequencies in the three variable-frequency oscillators by varying the charging currents. The outputs from the comparators (IC1D, IC2B, and IC2C) are symmetrical square waves, while the outputs from the integrators (IC1C, IC2A, and IC2D) are triangle waves. Resistor R10 in fixed-frequency oscillator IC1A/IC1B sets the amplitude of the two waveforms. Level controls are provided for all but oscillator C. Oscillator C has no level control because only one signal need be variable if both signals go to the inputs of a multiplier to cause the output of the multiplier to vary.

The square-wave output from oscillator A is differentiated by C2 and R6 to create a sync pulse. This pulse is fed to the inverting (-) input of IC2B to force oscillator C's operating frequency to be an exact multiple of the operating frequency of oscillator A. To sync the remaining oscillators, the triangle-wave output from oscillator A is attenuated by R4 and R5 and fed to the inverting inputs of IC1D in oscillator B and IC2C in oscillator D. The 60-Hz

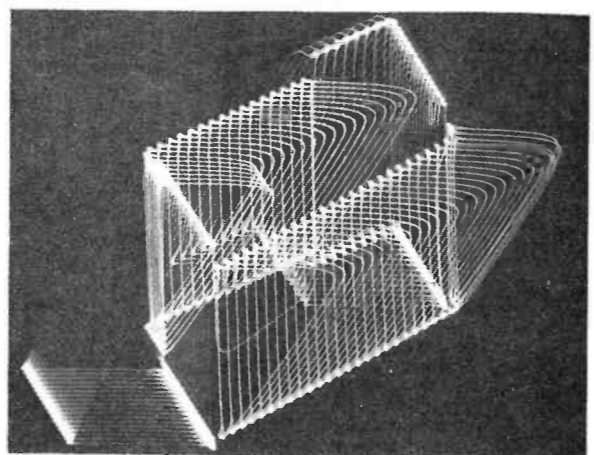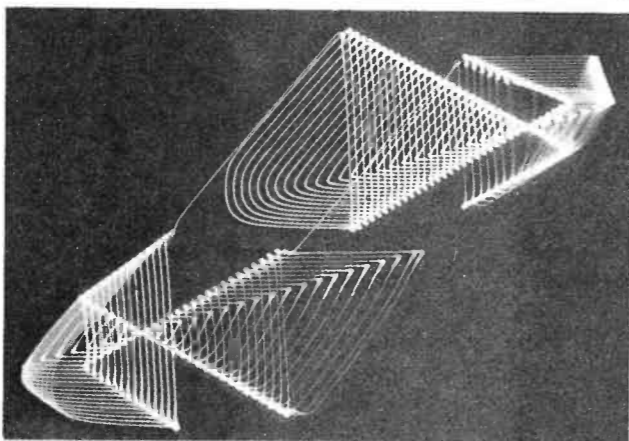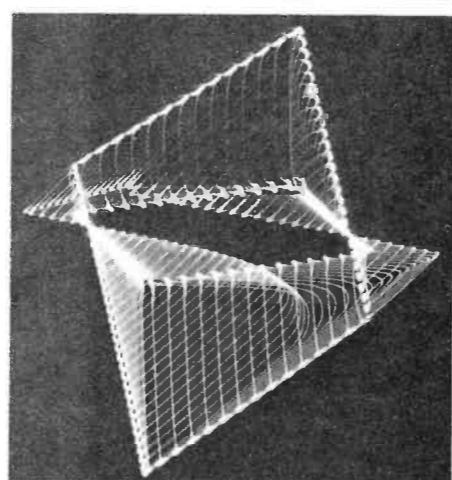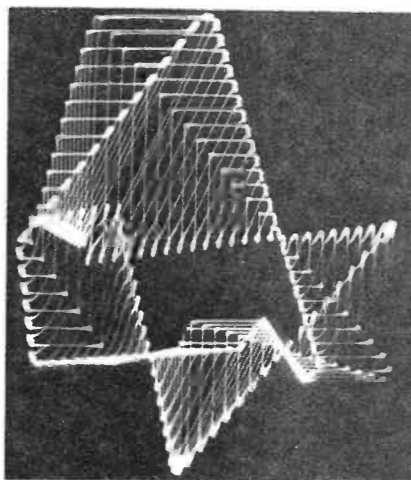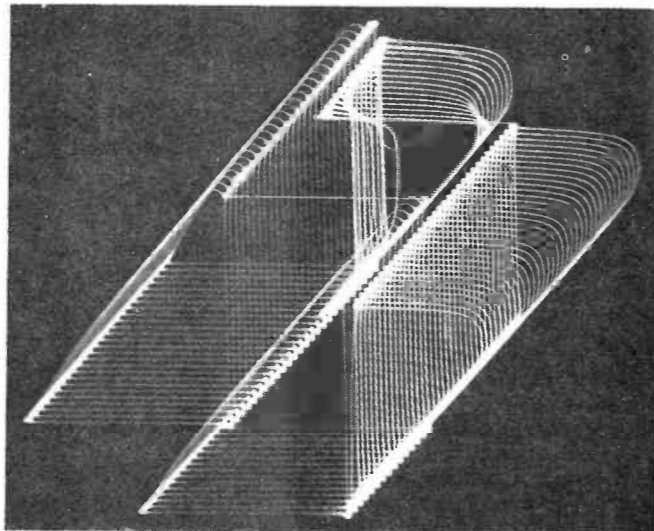

Photos illustrate only five of the countless varieties of waveform displays possible.

triangle wave forces oscillators B and D into exact sync. Resistor R7 in oscillator A makes the square and triangle waves in this oscillator equal in amplitude. Switches S1 through S4 provide means for selecting the desired waveforms.

Integrated circuit IC4 is an op amp follower, used here to reduce the source impedance to chopper-type multipliers IC3B and IC3D. In this type of multiplier, a bipolar transistor or JFET is used to switch the op amp between a noninverting (+) and an inverting (-) unity-gain buffer. Transistor Q1 serves this purpose in this circuit.

When the signal in oscillator C goes positive, Q1 conducts and IC3B reverts to an inverting amplifier. When oscillator C goes negative, Q1 starts to cut off, and IC3B becomes a noninverting amplifier with unity gain. This switching action results in suppression of the carrier, and the output of IC3B is a balanced four-quadrant signal.

The signal from oscillator C is shifted in-phase by +45° in network C9-R24 and by -45° by network

C10-R25. So, the waveform to each JFET (Q1 and Q2) is out-of-phase, resulting in a modulated output from the multiplier also being out-of-phase. Networks C6-R36 and C7-R40 provide dc restoration for Q1 and Q2.

The output from multiplier IC3B is summed with the signal from oscillator A in adder IC3A. The output from multiplier IC3D is summed with the signal from oscillator D in adder IC3C. Finally, the outputs from the two adders are fed to the oscilloscope to form the complex Lissajous patterns.

Power is supplied to the Artist by two standard 9-volt batteries (B1 and B2). Capacitor C8 aids in reducing instability in the IC op amps.

Construction. The project can be built on either printed circuit or perforated board. The actual-size etching and drilling guide and components-placement diagram are shown in Fig. 3. After preparing or buying a ready-to-use pc board (see Parts List for supplier), mount the components on it as shown in the placement diagram, paying particular attention to the orientations of the IC's and transistors. Place B1 and B2 on the blank end of the board, terminals pointing away

Set time LEVEL B control fully counterclockwise (off). Because oscillator B connects to both multipliers, making LEVEL B zero eliminates the modulated component on the screen. You should now see a simple rectangular or square Lissajous pattern. Adjust the horizontal- and vertical-gain controls on the scope so that, when LEVEL A and LEVEL D controls are set to midrange, the image just fills most of the screen.

Slowly turn up LEVEL B. This adds the modulated waveform to the existing pattern. Readjust LEVEL A and LEVEL D for a pleasant balance and to keep the image from drifting off-screen. Adjust HARMONIC B to sync the modulated envelope with the image. In essence, this control sets the number of "lobes" riding on the primary Lissajous pattern.

Next, adjust HARMONIC C so that the high-frequency carrier is in sync with the image. You should now have a display similar to those shown in the photos. The next thing we can do is alter the Lissajous "family" by using combinations of the waveform switches. For example, switching WAVEFORM A to the square-wave position and setting WAVEFORM D to the triangle-wave position causes the

CALCULATE YOURSELF A NICE SAVINGS ON POPULAR ELECTRONICS 33% OFF NEWSSTAND PRICE



FOR NEW SUBSCRIBERS

SAVE \$3⁰¹ with this introductory offer for new subscribers.

Sound like a good deal? It is! You pay only \$5.99 for a year's subscription, instead of the regular yearly price of \$6.98! Punch that up on a calculator and you'll see that's a savings of 33% off annual newsstand price of \$9.00.

So why wait? Plug in to a great deal today. Get 12 issues (1 year) of Popular Electronics for just \$5.99. Or save even more: get 2 years (24 issues) for only \$11.98. Simply fill out, detach and mail the certificate at right.



GOOD FOR \$3.01 OFF

Popular Electronics

P.O. Box 2774, Boulder, Colo. 80302

Send me a full year—12 issues—of Popular Electronics for just \$5.99—33% off annual newsstand price of \$9.00.

CHECK ONE: Please bill me. Payment enclosed (please mail this form in an envelope).

I want to save even more. Send me two years—24 issues—for just \$11.98.

MR./MRS./MS. _____ (please print) 4S04

ADDRESS _____

CITY _____ STATE _____ ZIP _____

Additional postage per year: add \$1.00 for Canada; \$2.00 for all countries outside the U.S.

FOR NEW SUBSCRIBERS ONLY




12 MONTHS FOR \$5.99

the remaining oscillators, forcing them to run at an exact multiple of the syncing frequency.

In addition to using the controls on the project, you can also use the vertical- and horizontal-gain controls on the scope to adjust the width and height of the images.

Circuit Details. As shown in Fig. 2, the four oscillators are identical except for their frequency-determining elements. Oscillator A is fixed at approximately 60 Hz by *R8* and *C1*; oscillator B is variable from 60 to 240 Hz; oscillator C is variable from 300 to 3000 Hz; and oscillator D is variable from 30 to 300 Hz. The oscillators are arranged in a classical comparator-integrator configuration.

Taking oscillator A as an example, *IC1A* uses *R1* and *R2* to set the trip point at about $\pm V_{cc}/2$. The output of this comparator connects to integrator *IC1B*, which in turn, connects back to *IC1A*'s input. When *IC1A*'s output is at -9 volts, *IC1B* linearly charges *C1* through *R8*. Hence, the output of *IC1B* is a positive-going ramp. As soon as the ramp reaches $V_{cc}/2$, *IC1A* changes to the positive state and *IC1B* linearly discharges *C1* to initiate a negative-going ramp.

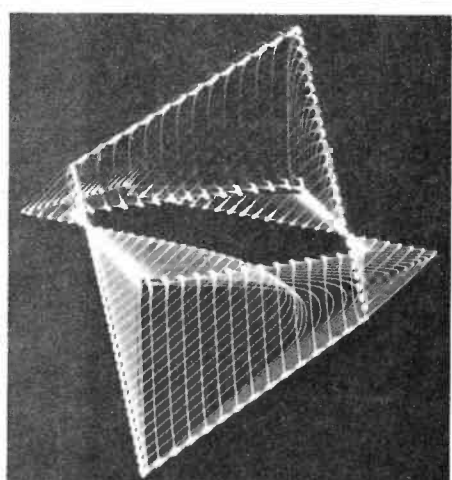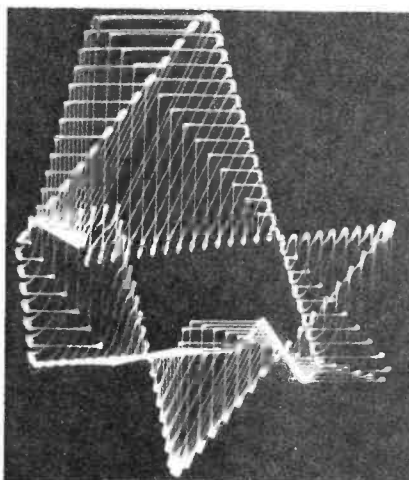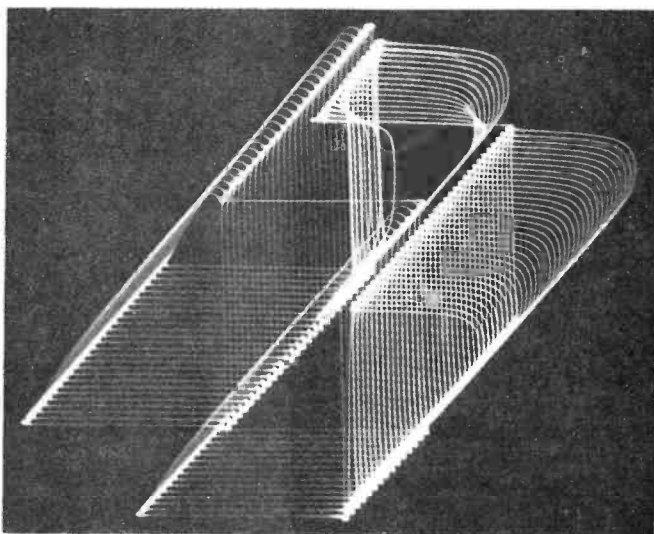

triangle wave forces oscillators B and D into exact sync. Resistor *R7* in oscillator A makes the square and triangle waves in this oscillator equal in amplitude. Switches *S1* through *S4* provide means for selecting the desired waveforms.

Integrated circuit *IC4* is an op amp follower, used here to reduce the source impedance to chopper-type multipliers *IC3B* and *IC3D*. In this type of multiplier, a bipolar transistor or JFET is used to switch the op amp between a noninverting (+) and an inverting (-) unity-gain buffer. Transistor *Q1* serves this purpose in this circuit.

When the signal in oscillator C goes positive, *Q1* conducts and *IC3B* reverts to an inverting amplifier. When oscillator C goes negative, *Q1* starts to cut off, and *IC3B* becomes a noninverting amplifier with unity gain. This switching action results in suppression of the carrier, and the output of *IC3B* is a balanced four-quadrant signal.

The signal from oscillator C is shifted in-phase by $+45^\circ$ in network *C9-R24* and by -45° by network

C10-R25. So, the waveform to each JFET (*Q1* and *Q2*) is out-of-phase, resulting in a modulated output from the multiplier also being out-of-phase. Networks *C6-R36* and *C7-R40* provide dc restoration for *Q1* and *Q2*.

The output from multiplier *IC3B* is summed with the signal from oscillator A in adder *IC3A*. The output from multiplier *IC3D* is summed with the signal from oscillator D in adder *IC3C*. Finally, the outputs from the two adders are fed to the oscilloscope to form the complex Lissajous patterns.

Power is supplied to the Artist by two standard 9-volt batteries (*B1* and *B2*). Capacitor *C8* aids in reducing instability in the IC op amps.

Construction. The project can be built on either printed circuit or perforated board. The actual-size etching and drilling guide and components-placement diagram are shown in Fig. 3. After preparing or buying a ready-to-use pc board (see Parts List for supplier), mount the components on it as shown in the placement diagram, paying particular attention to the orientations of the IC's and transistors. Place *B1* and *B2* on the blank end of the board, terminals pointing away from the components, and fasten them in place with loops of wire passed between the batteries. Temporarily set aside the board assembly.

Next, machine the front panel for the six potentiometers, five switches, three binding posts, and a No. 6 machine screw. The last hole should line up exactly with the large hole in the pc board assembly. Mount the pots, switches, and binding posts in their respective locations (see Fig. 4). Pass a 6-32 x 2" machine screw (to support the circuit board assembly) through the remaining hole, slip over its threads a length of plastic spacer, and follow with a No. 6 machine nut. The spacer should be just long enough that, when the nut is in place, about 1/4" of screw thread is still visible. Label the controls, switches, and binding posts.

Referring back to Fig. 2 and Fig. 3, finish wiring the project.

Operation. The oscilloscope used with the Graphic Artist must have an external horizontal input. Connect test-lead cables from the output binding posts on the Artist to the appropriate inputs on the scope. Set all waveform switches to triangle. Switch on the project and scope.

Set time LEVEL B control fully counterclockwise (off). Because oscillator B connects to both multipliers, making LEVEL B zero eliminates the modulated component on the screen. You should now see a simple rectangular or square Lissajous pattern. Adjust the horizontal- and vertical-gain controls on the scope so that, when LEVEL A and LEVEL D controls are set to midrange, the image just fills most of the screen.

Slowly turn up LEVEL B. This adds the modulated waveform to the existing pattern. Readjust LEVEL A and LEVEL D for a pleasant balance and to keep the image from drifting off-screen. Adjust HARMONIC B to sync the modulated envelope with the image. In essence, this control sets the number of "lobes" riding on the primary Lissajous pattern.

Next, adjust HARMONIC C so that the high-frequency carrier is in sync with the image. You should now have a display similar to those shown in the photos. The next thing we can do is alter the Lissajous "family" by using combinations of the waveform switches. For example, switching WAVEFORM A to the square-wave position and setting WAVEFORM D to the triangle-wave position causes the image to break up into separate shapes. There are 16 combinations for the four waveform switches. Add to this the effects of the six HARMONIC and LEVEL controls, and chances are you will never see the same pattern twice.

After you've familiarized yourself with the operation of the controls (it does take some skill), you might try connecting a pair of stereo headphones to the two output channels. The sounds of the four oscillators mixing and adding produces beat notes that are fascinating in themselves. You can even "play" the sounds by twisting the various controls.

Some very different and interesting effects can be produced by running the Graphic Artist in reverse. Take a signal from an external source, such as an electronic organ, and connect it in place of one of the oscillators. You can do this by disconnecting one waveform switch input and connecting your signal in its place. Choose your notes to be exact even or odd harmonics of oscillator A, which operates at approximately 60 Hz. The images will appear to stop their motion and their actual shape will depend on the particular waveform of the note being played.

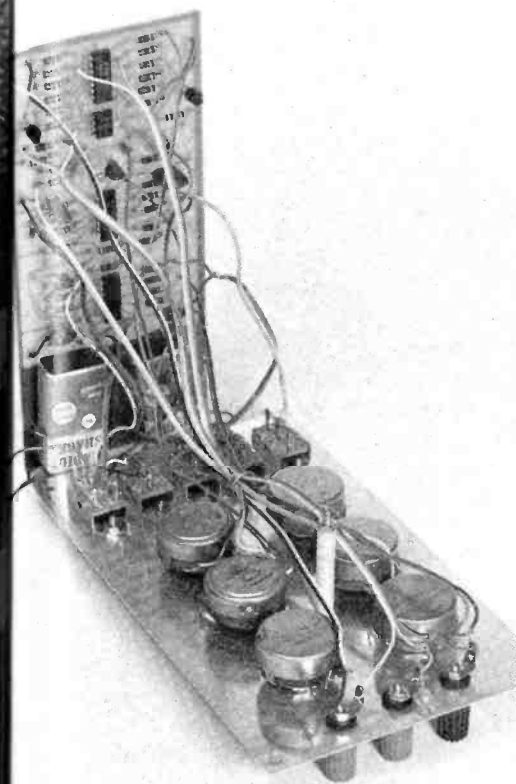


Fig. 4. Construction details.

Check out this savings on Popular Electronics

33% OFF

the newsstand price

Tally up a nice savings! Get a full year of Popular Electronics for just \$5.99. A full year of our test reports on new equipment. Tips on building your own equipment. Plus special stereo, hobby, solid-state and CB features to boot!

So go ahead! Get a full year (12 issues) of Popular Electronics for just \$5.99. Or get two years (24 issues) for only \$11.98—and save even more. Just complete, detach and mail the postpaid reply card at left.

FIRST CLASS
Permit No. 906
Boulder, Colo.

BUSINESS REPLY MAIL

No Postage Stamp Necessary If Mailed In The United States

POSTAGE WILL BE PAID BY

Popular Electronics

P.O. Box 2774
Boulder, Colorado 80302

BUILD A PREREGULATED POWER SUPPLY

Super-stable, multi-purpose supply for the experimenter's workbench

ANYONE who works with modern electronic circuits, whether he is a professional or an amateur, will eventually require a closely regulated variable power supply. While most power supplies are regulated directly from the basic rectified and filtered dc line, tighter regulation can be obtained by using a preregulated approach in the supply's design.

The preregulated power supply described here can be built for about \$15 more than you would have to pay for a conventionally regulated low-current supply. It employs two inexpensive 723 voltage regulator IC's in a circuit that can deliver 3 to 35 volts dc at load currents up to 3 amperes. The design eliminates the need for massive heat sinks and cooling fans.

How It Works. The power supply's circuit shown in Fig. 1 can be functionally diagrammed as an ac source, rectifier bridge, and two voltage regulators in series. The preregulator, by means of SCR1, continuously controls the potential at C1 so that the potential across Q1 remains constant. The output regulator (IC2) is a high-performance circuit that is capable of providing 0.1% regulation.

Synchronized to the 120-Hz rectified ac input, preregulator integrated circuit IC1 is connected as a time-delayed pulse generator that controls the gate of SCR1 to trigger conduction at the exact point required during each half cycle. The bias voltage applied to the inverting input (pin 2) of

IC1 is adjustable via potentiometer R9; it determines the reference level for the supply.

The zener-regulated source at pin 4 of IC1 also supplies current through R14, R15, and R18 to C4 and pin 3 (noninverting input). The current continues to flow until the reference voltage is exceeded. At this point, IC1 turns on. The resulting square-wave pulse from pin 6 of the IC is limited to 9 volts by current-sensing resistors R12 and R13, which is sufficient, at the gate of SCR1, to trigger the SCR into conduction.

The RC time constants in the circuit are controlled by the amount of current flowing through Q3, which, in turn, depends on the error voltage present at the wiper of R10A. A voltage divider consisting of R16 and diodes D7 through D10 applies a relatively constant 2.4 volts to the emitter of Q3 so that when the transistor's base goes above 3 volts there will be a voltage drop across R14 and a corresponding change in the RC time constant. Capacitors C5 and C6 stabilize the operation of Q3 to prevent SCR1 from firing erratically. When R10 is rotated counterclockwise, R17 and D13 protect Q3 and D12 from damage.


The method of synchronizing IC1 to the rectified input is graphically shown in Fig. 2. Triggered into conduction by the positive-going voltage, SCR1 cuts off when the gate signal ceases and C4 discharges sufficiently to reduce to a minimum the holding current to the SCR. The diagram also

reveals why the secondary voltage from T1 must be greater than would be normal in a conventionally regulated power supply. The SCR cannot conduct until its anode is more positive than its cathode. Simultaneously, a minimum latching current must flow. Also, SCR1 must remain conducting until the energy drawn from C1 by the output load is replaced.

Since the potential across C1 will be 41 volts at maximum output, the 18-volt difference allows the time interval necessary for maximum current. This also means that SCR1 fires only near the peak or on the negative-going side of the waveform. Resistors R1 and R2 are bleeders that carry the minimum holding current required by SCR1.

Dual potentiometer R10 establishes feedback to both voltage-regulator IC's. (A wire-wound potentiometer is best used here so that the sections will be more evenly matched. So, if an identical voltage were present across each section of the pot, the wiper voltages would be very nearly the same at any setting.) Potentiometer section R10B samples the output voltage and drives IC2 in the proper direction to maintain 3 volts between wiper and ground. The A section of the pot samples the voltage across C1 and controls the firing of SCR1, also maintaining 3 volts between wiper and ground.

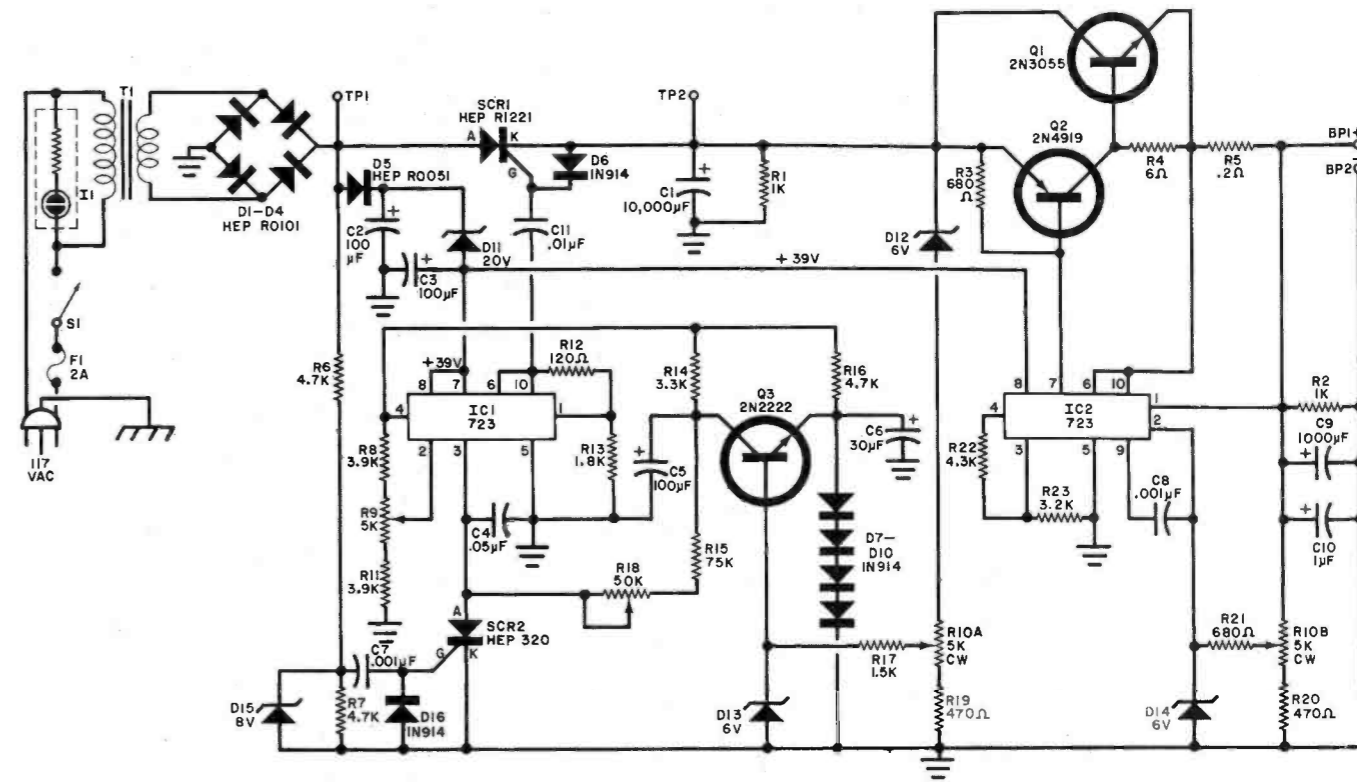Since the potential at the counterclockwise ends of R10A and R10B must be the same, the potential across



- BP1, BP2—Five-way binding post (one black, one red)
 C1—10,000- μ F, 50-volt electrolytic capacitor
 C2, C3—100- μ F, 65-volt electrolytic capacitor
 C4—0.05- μ F disc capacitor
 C5—100- μ F, 10-volt electrolytic capacitor
 C6—30- μ F, 10-volt electrolytic capacitor
 C7, C8—0.001- μ F disc capacitor
 C9—1000- μ F, 50-volt electrolytic capacitor
 C10—1- μ F, 50-volt tantalum electrolytic capacitor
 C11—0.01- μ F disc capacitor
 D1 thru D4—100-PIV, 3-ampere rectifier (Motorola HEP R0101 or similar)
 D5—100-PIV, 1-ampere rectifier (Motorola HEP R0051 or similar)
 D6, D7 thru D10, D16—1N914 diode
 D11—20-volt, 1-watt zener diode (Motorola HEP Z0421 or similar)

- D12—6-volt zener diode (1N429 or similar)
 D13, D14—6-volt zener diode (1N1509 or similar)
 D15—8-volt zener diode (Motorola HEP ZQ217 or similar)
 F1—2-ampere slow-blow fuse
 I1—Neon panel lamp with resistor
 IC1, IC2—723 voltage regulator integrated circuit (in TO-5 can)
 Q1—HEP 704 (Motorola) or 2N3055 transistor
 Q2—HEP 246 (Motorola) or 2N4919 transistor
 Q3—HEP 736 (Motorola) or 2N2222 transistor
 R1, R2—1000-ohm, 2-watt, 10% resistor
 R3, R21—680-ohm, 1/2-watt, 5% resistor
 R4—6-ohm, 1-watt, 5% resistor
 R5—0.2-ohm, 2-watt, 5% resistor
 R6—4700-ohm, 1-watt, 5% resistor

- R7, R16—4700-ohm, 1/2-watt, 5% resistor
 R8, R11—3900-ohm, 1/4-watt, 5% resistor
 R9—5000-ohm miniature pc potentiometer
 R10—5000-ohm dual wire-wound potentiometer
 R12—120-ohm, 1/4-watt, 5% resistor
 R13—1800-ohm, 1/4-watt, 5% resistor
 R14—3300-ohm, 1/4-watt, 5% resistor
 R15—75,000-ohm, 1/4-watt, 5% resistor
 R17—1500-ohm, 1/4-watt, 5% resistor
 R18—50,000-ohm, miniature pc potentiometer
 R19, R20—470-ohm, 1/2-watt, 5% resistor
 R22—4300-ohm, 1% resistor
 R23—3200-ohm, 1% resistor
 SCR1—HEP R1221
 SCR2—HEP 320
 S1—Spst switch
 T1—Transformer, 42V, 3A Secondary
 Misc.—Printed circuit or perforated board; suitable cabinet; heat sink; fuse holder; sockets for IC's (2); etc.

PARTS LIST

Fig. 1. Power supply employs two voltage-regulator IC's for super stability.

C1 will be 6 volts greater than the output because of the action of D12. Any change in the output voltage and/or current will affect the firing-pulse timing at the gate of SCR1, maintaining a constant potential across Q1.

Construction. The easiest way to assemble the power supply is by using a printed circuit board. (See Fig. 3 for actual-size etching and drilling and component placement guides.) Alternatively, you can assemble the circuit on perforated board using solder clips and sockets. Whichever method you use, refer to the table in Fig. 3 for instructions on how to interconnect the circuit board assembly and the com-

SEQUENCE OF EVENTS

- SCR2 fires as C7 charges; C4 then discharges and IC1 cuts off.
 - D15 limits voltage on C7; SCR2 cuts off and C4 begins to charge.
 - C4 has charged above reference level at pin 2 of IC1, causing the IC to conduct; a trigger pulse at pin 6 turns on SCR1 through C11.
 - SCR1 current decreases as C1 voltage increases. When voltage across SCR1 is insufficient to maintain about 10 mA current, SCR1 turns off.
- Note: SCR1 turns on and off at approximately C and D on the curve, when the output load is drawing 3 amperes at 35 volts. With no external load, events C and D occur near the end of the wave as indicated by the unmarked dots.

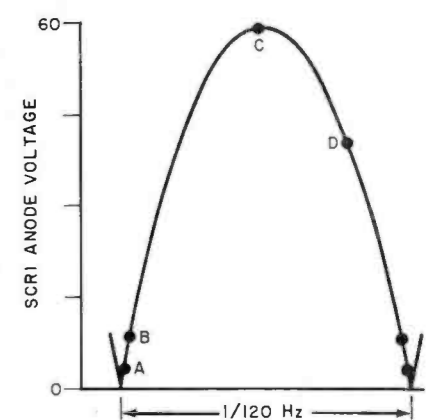


Fig. 2. Events above left are keyed to points on curve.

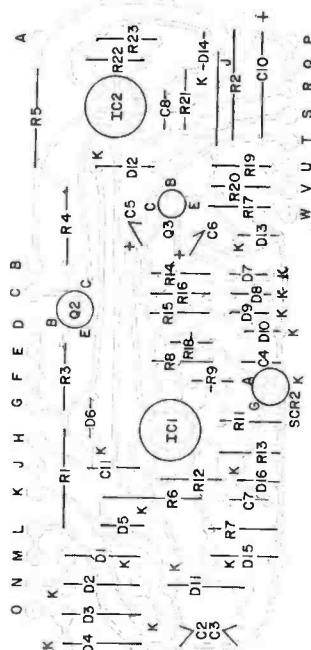
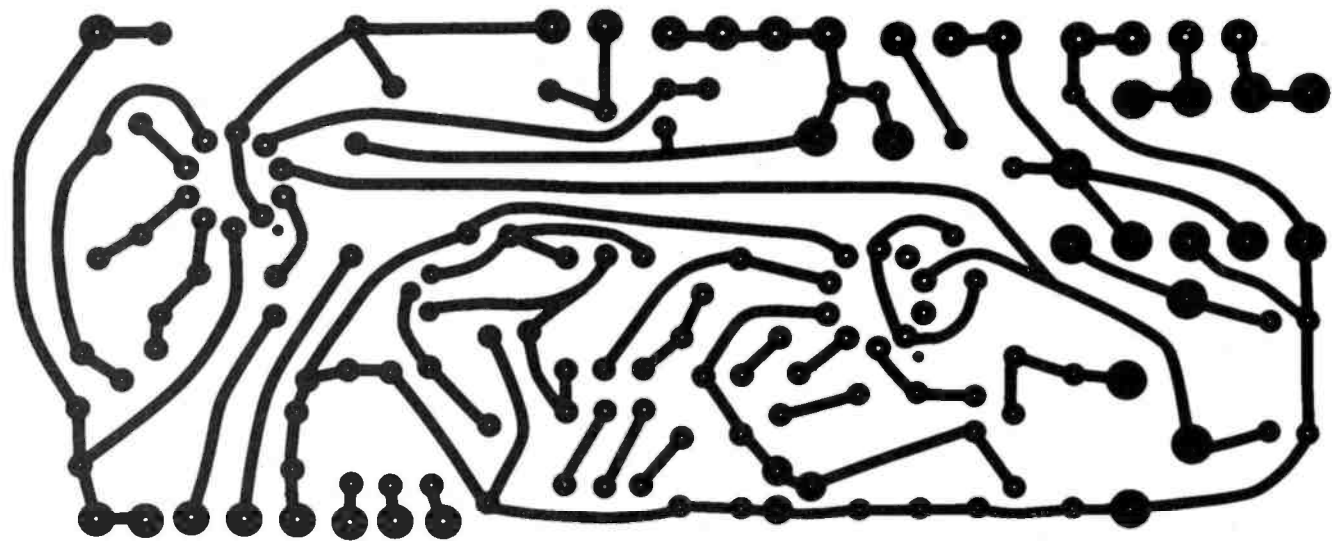


Fig. 3. Actual-size etching and drilling guide is shown above; component-placement diagram is at left; table at right details hookups between board and off-the-board components.

CONNECT

FROM:	TO:	FROM:	TO:
A	C9 +	M	C1 -
B	Q1 E	N, O	T1 S
C	Q1 B	P	BP1
D	Q1 C	Q	R10B CCW
E	TP2	R	R10B WIP
F	C1 +	S	R10A CCW
G	SCR1 K	T	BP2
H	SCR1 G	U	R10A CW
J	SCR1 A	V	R10B CW
K	TP1	W	R10A WIP
L	C9 -		

Mount the off-the-board components, followed by the circuit-board assembly inside the cabinet. Then refer to the table in Fig. 3 and Fig. 1 to complete wiring the system.

Test and Use. To balance out component tolerances, IC1 must be initially aligned. To accomplish this, you will need an oscilloscope, high-impedance multimeter, and an improvised load. Rotate R10 counterclockwise, set R18 to maximum resistance and R9 for maximum voltage gain at pin 2 of IC1 before applying power to the supply. Connect the scope from TP1 to ground and the multimeter from TP2 to ground. Turn on the power.

There should be a small voltage present at TP2, but the scope should indicate that SCR1 is not conducting. Keeping the voltage reference as high as possible at pin 2 of IC1, adjust R18 and R9 until SCR1 fires regularly and the meter indicates 9 volts at TP2. When R10 is rotated fully clockwise, the meter should indicate 41 volts at TP2.

Temporarily short out R5 and momentarily connect a 12-ohm,

120-watt resistor (or an equivalent combination) across the output via BP1 and BP2. If the TP2 reading drops more than 0.2 volt or SCR1 fires intermittently, adjust R9 only enough to correct. Then, with no load connected to the output of the supply, rotate R10 counterclockwise. The reading at TP2 should slowly decrease to 9 volts. If it does not, adjust R9 for a higher voltage at pin 2 of IC1 until it does.

Rotate R10 again and apply the load, compensating for the voltage drop by adjusting R18. There will be some combination of the two adjustments that will permit Q3 to retain control over IC1 throughout the specified voltage and current ranges. To do this, Q3 must always be forward biased. If at any time Q3 does not draw the proper current from R14, it has lost control.

Correct alignment will be achieved when the voltage at the wiper of R10A is the same at any output. As a further test, connect the meter across Q1 and note the voltage change when R10 is rotated clockwise. Any difference would correspond with D12's zener voltage characteristics at bias currents of from 1 to 7mA.

BUILD AN AUTOMOBILE LOGIC ALARM

Simple circuit monitors five electrical points in the car and sounds an alarm when the wrong conditions occur.

BY ROBERT GRATER

MODERN cars have warning systems that monitor various conditions in the engine, lights, etc. One such system is the buzzer that sounds when the driver's door is opened with the key still in the ignition. There are other conditions that can also be monitored if you install the Logic Alarm described here. These include: leaving the headlights on when the ignition is turned off, leaving the ignition on when the oil pressure is low; and leaving the ignition on when the engine is overheated. (As options, the brake and seat-belt warning light circuits can be monitored.) An extra advantage of the Logic Alarm is that the raucous buzzing of most door warning systems can be replaced by a more pleasing audio tone.

12-volt line (negative ground) regulated by a 5-volt zener diode. The IC has four separate gates, each producing an output if its two inputs are in opposite states. A gate will not deliver an output if both inputs are simultaneously high or low.

The 74L86 is used because it is a low-power device requiring only 3 mA. It is not a pin-for-pin replacement for the conventional TTL 7486, which requires more current. The 7486 could be used if the circuit is changed to suit the different pin arrangement, the value of R9 is changed because of greater current flow, and a switch is added to turn off the 12-volt supply when not needed.

The outputs of the four gates pass through diode isolators to a solid-state alarm (another low-power device).

For the headlights-on/ignition-off circuits, the inputs of gate A are held high by the supply through R1 and R2.

With the headlights off, D1 and D2 conduct, maintaining the stable status of gate A. However, with the headlights on and the ignition off, D3 conducts and input 2 to the gate drops, providing an output from the gate.

The oil-pressure (gate B) and temperature (gate C) circuits are identical. One side of each gate is coupled to the ignition through D4 and D6, respectively so that they are in a high state when the ignition is on. The oil-pressure and temperature sensing signals should also be high when the engine is running. Thus there are no outputs from these gates. When the vehicle is first entered and the ignition is turned on (prior to starting the engine), the oil-pressure and temperature sensors will be "cold," and the alarm will sound. This serves as a system test. (If the car has instrument-panel lamps for these functions, the Logic Alarm will provide a warning even if one of the lamps fails.)

Circuit Operation. As shown in Fig. 1, the Logic Alarm uses a single 74L86 low-power quad exclusive-OR gate that receives power from the car's

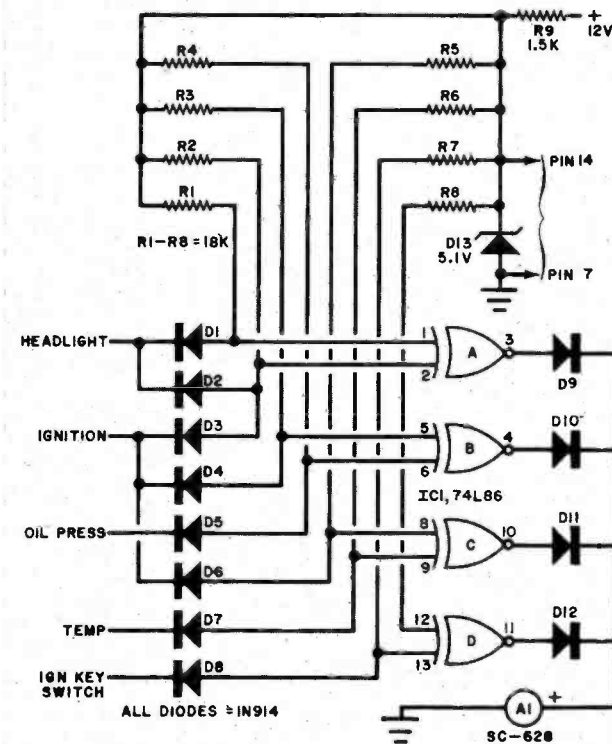


Fig. 1. Points to be monitored are connected to exclusive OR gates through diodes.

PARTS LIST

- A1—Tone generator (Mallory Sonalert SC-628 or similar)
 - D1 to D12—Diode (1N914 or similar)
 - D13—5.1-V, 1/2-W zener diode (HEP ZO-212 or similar)
 - IC1—Quad exclusive OR gate (74L86)
 - R1 to R8—18,000-ohm, 1/4-W resistor
 - R9—1500-ohm, 1/4-W resistor
 - Misc.—14-pin DIP socket, pc or perforated board, wire for connections, mounting hardware, etc.
- Note: The following are available from RGS Electronics, 3650 Charles St., Suite K, Santa Clara, CA 95050: kit of parts including pc board but not Sonalert at \$6.35 including postage and handling; pc board alone at \$2.50.

Note: Components shown from foil side of board.

ponents located off the printed circuit board.

Select a cabinet for the supply that is large enough to accommodate all components without crowding. Machine the front panel for potentiometer R10, lamp/resistor assembly I1, and binding posts BP1 and BP2. Mount the components in their respective holes.

Next, mount Q1 and SCR1 on a 4" x 2 1/2" x 1" (10.2 x 6.4 x 2.5-cm) finned heat sink. Drill mounting holes for this assembly, the line cord, and fuse holder through the rear panel of the cabinet. Mount the fuse holder and heat-sink assembly in place. Line the remaining hole with a rubber grommet for the line cord.

Crown The Known Value...

at an uninflated price!

An honest value isn't hard to find, if you know an honest supplier. CROWN's reputation for providing more recorder value for your dollar is as old as our company. Nothing would ever cause us to change that.

CROWN recorders offer you day-in, day-out worry-free reliability, plus brilliant performance. Both result from simple, rugged design, with only a few moving parts. The CROWN belt drive and massive flywheel almost completely isolate the capstan drive from any vibration or rumble.

CROWN electronic circuits are carefully designed for maximum reliability, and electronic components are thoroughly tested before assembly. Oversize meters and easy-to-handle-controls make operation simple. The result? A professional tape deck, used to produce quality recordings in many a studio.

Each CROWN transport has undergone 100 hours of testing. Each CROWN recorder has its own performance report, signed, not stamped, by a CROWN inspector. And each CROWN recorder is backed by a one-year full warranty on parts and labor; and an additional two-year limited warranty on parts only. We put the CROWN name on these recorders proudly—we believe they've earned it.

Why not talk to your nearby CROWN dealer about the long-term values of a CROWN recorder. And the uninflated price. It could be the year's best buy.

Write us for his name. CROWN, Box 1000, Elkhart, IN 46514



CROWN
WHEN LISTENING BECOMES AN ART
CIRCLE NO. 24 ON FREE INFORMATION CARD


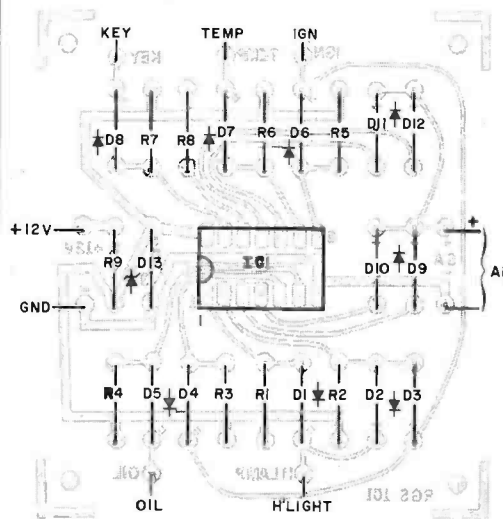


Fig. 2. Etching and drilling guide for pc board is shown below; component layout at left.

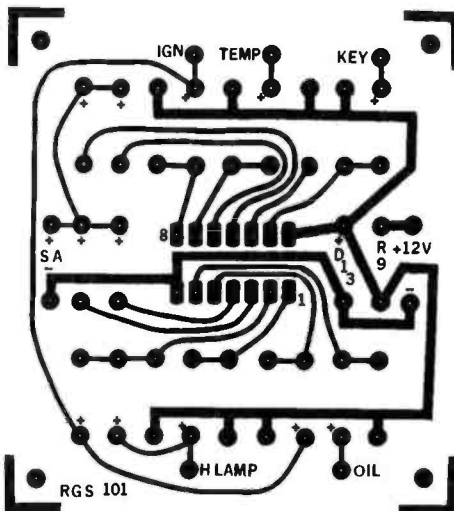

The "you left the key in the ignition" circuit uses gate D, with one input connected to the ignition switch through D8. Thus when the ignition key circuit goes to ground with the key in, one input is low, causing the alarm to sound.

Construction. The Logic Alarm can be assembled on a pc board (Fig. 2) or wired point-to-point on perforated board. The board assembly can be cemented directly to the back of the alarm. The alarm can then be mounted either in a hole cut in the dashboard or in a small enclosure mounted under the dashboard.

Wiring. The headlight sensing point can be picked up either at the fuseblock or the headlight switch—or on the headlight wire using an insulated connection. Use a dc voltmeter to make sure that this point is at 12 volts when the lights are on.

The best place to get at the ignition circuit is at the fuseblock. Use a dc voltmeter to locate a circuit that is at 12 volts when the ignition is on.

The +12 volts used to power the alarm can also be obtained from the fuseblock. The alarm can be wired permanently to the supply since the power consumption is so low. Using the fuseblock to pick off the various signals allows the application of conventional automotive snap-in connectors sold at most automotive supply stores.

The oil-pressure and temperature pickoff points can be made as shown in Fig. 3A, using an insulated connector.

The circuit from the ignition key must be located with the voltmeter and should be at 12 volts with the key in the switch. Fig. 3B shows the buzzer circuit used in most GM cars—others are similar. The buzzer is in the horn relay enclosure and ground is provided through the key switch and door switch. Remove the wire marked with an X in Fig. 3B and connect to it for the ignition key sensing.


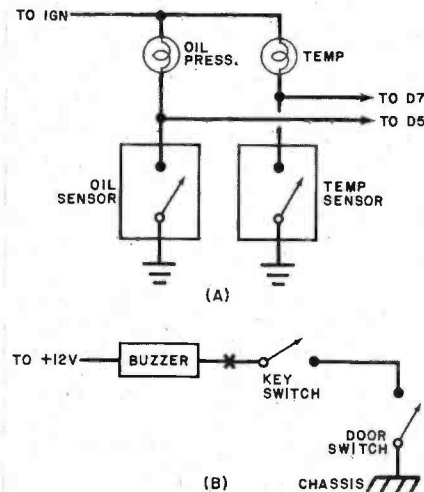


Fig. 3. Circuits for connecting to monitored points.

If Santa had a Altair®...

Santa might be possible!

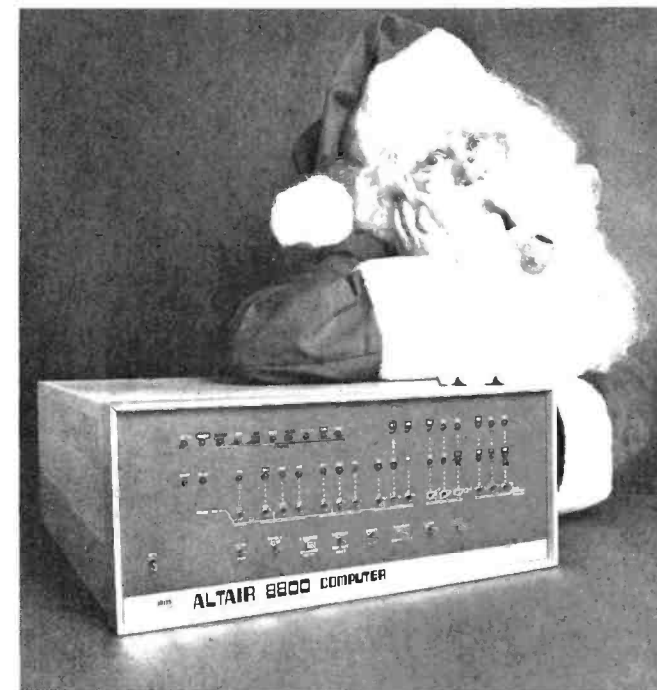

Have you ever wondered how Santa keeps track of all the addresses of all the children in the world? How he knows who gets what?

With an Altair 8800, Santa might have a fighting chance. He might be able to keep up with the ever-expanding toy industry. He might be able to remember who's been naughty and nice.

With an Altair 8800, Santa might be possible. **This Christmas you can do something that's never before been possible.** You can put an Altair under your tree or under the tree of a friend. Or you can start with our special Christmas 75 time payment plan!*

The Altair 8800 is the **NUMBER ONE** hobby computer in the whole world. No other computer offers you the power and versatility—the proven track record—of the Altair 8800 at a comparable price. No other hobby computer offers you the sophistication of Altair BASIC software or the wide variety of Altair modules and peripherals. No other hobby computer offers you the customer support of an Altair (free membership in the Altair Users Club, free access to the Altair Service Department and the Altair Software Library, and a free subscription to the Altair monthly publication, *Computer Notes*).

Order now and avoid the last minute Christmas rush!

* Christmas 75 Time Payment Plan

1K Altair for Just \$68.00 a month!

The Altair time payment plans allow you to be the owner of an Altair 8800 with 1,024 bytes of memory for just \$68.00 a month. Each month (for 8 months) you send in your payment and we send you part of an Altair kit until you have the complete system. The advantages of this plan are **NO interest** or financing charge, **GUARANTEED price** based on today's price, and free, **immediate membership** to the Altair Users Group including subscription to *Computer Notes*.

Our terms are cash with order, BankAmericard or Master Charge. If you send in an early payment we will make an early shipment. By the same token, a late payment will result in a late shipment. (After 60 days past due, the balance of the deal is cancelled. All payments must be made within 10 months).

Total Price: \$544 (Retail price: Altair \$439, Memory \$97, Postage and handling \$8—total \$544)

HARDWARE PRICES:

Altair Computer kit with complete assembly instructions	\$439
Assembled and tested Altair Computer	\$621
1,024 Byte Static Memory Card	\$97 kit and \$139 assembled
2,048 Byte Static Memory Card	\$145 kit and \$195 assembled
4,096 Byte Dynamic Memory Card	\$264 kit and \$338 assembled
Full Parallel Interface Card	\$92 kit and \$114 assembled
Serial Interface Card RS232C	\$119 kit and \$138 assembled
Serial Interface Card (TTL or Teletype)	\$124 kit and \$146 assembled
Audio Cassette Record Interface	\$128 kit and \$174 assembled
COMTER II*	\$780 kit and \$920 assembled

*The Comter II Computer Terminal has a full alpha-numeric keyboard and a highly readable 32-character display. It has its own internal memory of 256 characters and complete cursor control. Also has its own built-in audio cassette interface that allows you to connect the Comter II to any tape recorder for both storing data from the computer and feeding it into the computer. Requires an RS232C Interface Card.

SOFTWARE PRICES:

Altair 4K BASIC	\$350
Purchasers of an Altair 8800, 4K of Altair Memory, and Altair Serial I/O or Audio-Cassette I/O	ONLY \$60
Altair 8K BASIC	\$500
Purchasers of an Altair 8800, 8K of Altair Memory, and Altair Serial I/O or Audio-Cassette I/O	ONLY \$75
Altair EXTENDED BASIC	\$750
Purchasers of an Altair 8800, 12K of Altair Memory, and Altair Serial I/O or Audio-Cassette I/O	ONLY \$150

Altair PACKAGE ONE (assembler, text editor, system monitor)
Purchasers of an Altair 8800, 8K of Altair Memory, and Altair I/O ONLY \$30

NOTE: When ordering software, specify paper tape or cassette tape.

Warranty: 90 days on parts for kits and 90 days on parts and labor for assembled units. Prices, specifications, and delivery subject to change.

MITTS

"Creative Electronics"

MITTS/6328 Linn N.E., Albuquerque, NM 87108 505/265-7553 or 262-1951

MAIL THIS COUPON TODAY!

Enclosed is check for \$_____

BankAmericard # _____ or Master Charge # _____

Altair 8800 Kit Assembled Options

(List on separate sheet)

Include \$8 for postage & handling

Altair Time Payment Plan Please send my order to different address

Please send free literature (List on separate sheet)

NAME _____

ADDRESS _____

CITY _____ STATE & ZIP _____

MITTS/6328 Linn N.E., Albuquerque, NM 87108 505/265-7553 or 262-1951

NOTE: Personal checks take 2-3 weeks for clearance. For immediate processing send money order or use charge card.

Demand for electronics technicians will continue to grow year after year, according to responsible projections, not only in broadcast control (shown here), but in hospitals...industry...offices...schools. Electronics is the field for tomorrow.

16 WAYS TO MOVE AHEAD IN

Choose the one that's right for you, now. The one that can make your future more rewarding, more secure, more enjoyable. These steps to your better tomorrow are available from Electronics Technical Institute...the finest in electronics home study courses and programs!

"Building" is a key word at Electronics Technical Institute. Whether your goal is to get into TV Repair and Service, get your FCC license, move into computers, advance in your present job through learning solid-state technology, or become an electronics draftsman, you build a solid future where the action has to come.

You build that future on a foundation of learning that is useful...practical...step-by-step...hands-on.

You build it from the beginning by a special, simplified, building-block teaching system called *Autotext* (exclusive with Electronics Technical Institute) that makes learning fun. You keep building, combining hands-mind-equipment in the most practical way, so you can "talk shop" or present an idea effectively, and you can also do the job! You've learned by doing, and you gain all the confidence that comes with it.

You build with the concerned personal help of a licensed instructor who knows the subject and wants to know you. You build with the reputation of the school that began as the Marconi Institute back in 1909.

In many phases of building your technical know-how, you use specially developed Project Kits that move in a logical sequence, hands-on, from the first step through completion of basic units. There is no surer way to build solid electronics knowledge and your own confidence in what you can do.

Choose your future...here, and now!

Fundamental Electronics
Get a solid foundation for entering the fast-moving world of electronics where today is great, and tomorrow will be greater. Learn it the simple, easy, step-by-step, programmed way called *Autotext*, exclusive with ETI!

Electronics Drafting
Learn a vitally needed specialty that translates new tech-

ELECTRONICS

nological concepts and developments to the practical drawing board. Become a specialist-in-demand, through ETI's training. Learn it at home...get your future moving now!

Color TV Servicing

There's a real future waiting for the established color television technician. You become that technician through this program that takes you step-by-step to *theoretical and practical* mastery of color TV. Get your tomorrow started today!

Master TV/Radio Servicing

Here is true "master" preparation for a career that can take you as far as you want to go into radio and television servicing, both black and white, and color. The helpful, practical ETI way can be your way to more money, security, success!

Communications

ETI's communications program opens up a whole range of career development possibilities in electronics. Solid-state receivers, solid-state audio equipment, communications equipment, CATV, as well as preparation for FCC-licensed positions in commercial broadcasting and



Digital Technology

Join the digital revolution which is radically altering our lives today and tomorrow. Get solidly trained in the new digital specialties that can lead to a real future as a digital control technician, electronic calculating machine technician, field representative, manufacturer's representative.

Electronics Technology

Learn electronics across the board! You'll be ready for real career advancement with train-

Black and White TV Servicing—Advanced

This can be your own "advance" source to black-and-white TV competence from A to Z. You'll construct a receiver yourself, if you wish. A key to life-time success!

Industrial Instrumentation—Advanced

Move up in the world...the wonderful electronics world! This course opens up a whole range of careers in the industrial field, as instrumentation technician, laboratory technician, process control technician or electronic calculating machine technician. Get ready...and go!

Color TV Servicing—Advanced

Here is the "graduate" course in color TV for those who already know television fundamentals. You'll learn color TV from top to bottom, build your own set if you choose. A great way to build your future!



transistor may be a breakthrough comparable in importance to the development of nuclear energy. Solid-state can mean your solid career development, too, through ETI!

FCC License Preparation


Here is real down-to-earth practical preparation to take your 3rd, 2nd, or 1st class Federal Communication Commission Radio-telephone License examinations. Get yourself ready now for any of the FCC-licensed positions involving broadcasting, mobile communications, microwave communications links, marine communications equipment or in many other positions in solid-state, communications, CATV. Get ready for tomorrow...today!

And it's simple to check it all out right now, with no obligation—and no salesman will call. All it takes to get the colorful new 48-page ETI Career Book is a card or coupon. If you like electronics, you'll enjoy reading about it. You owe it to yourself to get the facts.

The Career Book itself may be worth real money to you, as you make plans for your future and consider the many opportunities open to you through 16 different courses and

programs in electronics.

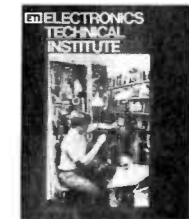To build a future in electronics, the first step is to send for your free ETI Career Book today!



Free! Exciting new 44-page career book!

From Electronics Technical Institute

Tells you how you can change your whole life...

- tells you exactly how you can put your talent to work for a great future!
- tells you 16 ways to get ahead through Electronics Technical Institute courses and career programs! One to meet your needs!
- tells you, in page after page, of today's and tomorrow's most important opportunities in the world of electronics—where the best is yet to come!
- tells you how you can get the most out of learning at your own pace, in your spare time, through the special step-by-step, hands-on, practical teaching methods of Electronics Technical Institute! Explains the exclusive ETI "Autotext" system.



NO SALESMAN WILL CALL
Get all the facts. It's your future, and it's important. There's no obligation of any kind. Send for your exciting free Career Book today!

Tell me how I can get ahead in Electronics through ETI.

I've checked the fields of special interest to me.

- | | |
|---|---|
| <input type="checkbox"/> TV/Audio Servicing
Black and White
Color
Solid-State
CATV
Closed Circuit
Video Recorders
Radio
Hi-Fi Stereo | <input type="checkbox"/> Communications
FCC License
Aircraft
Marine
Mobile Two-Way
Microwave |
| <input type="checkbox"/> Computers
Digital Electronics
Computer Technology
Computer Programming | <input type="checkbox"/> Business and Engineering
Electronics Fundamentals
Electronics Drafting
Industrial Electronics
Advanced Electronics
Industrial Instrumentation
Electronics Technology
Medical Electronics |
- 2-473-115
- Check here for Veterans information.

Name _____ (please print)

Address _____

City _____

State _____ Zip _____

Popular Electronics

Electronics Technical Institute

Technical Home Study Schools

Dept. 2-473-115


Electronics Technical Institute Career Book.

Through ETI, I've checked the fields of special interest to me.

- | | |
|---|---|
| <input type="checkbox"/> Computers
Digital Electronics
Computer Technology
Computer Programming | <input type="checkbox"/> Business and Engineering
Electronics Fundamentals
Electronics Drafting
Industrial Electronics
Advanced Electronics
Industrial Instrumentation
Electronics Technology
Medical Electronics |
|---|---|

(please print)

State _____ Zip _____

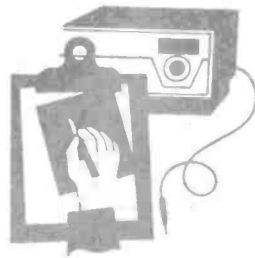

Product Test Reports

ABOUT THIS MONTH'S HI-FI REPORTS

International Audio Designs is an unfamiliar name in the hi-fi marketplace, but the company's Model B3A dynamic range expander should have a wide appeal for audiophiles who wish to restore some of the dynamics lost in their compressed tape and disc recordings and FM broadcasts. The expander can add up to 15 dB of dynamic range to the program. Its gain variations are absolutely undetectable while listening to a program.


When Shure Brothers announces a new phono cartridge, you can be sure that it is designed to fill a definite need in the marketplace. The Model M95ED has the flat, uncolored sound of the highly respected Shure V-15 Type III at a price most critical audiophiles can afford.

Yamaha, a company well-known for its motorcycles, has only recently had its audio products achieve a telling fame on the hi-fi scene. The company's Model CR-800 stereo receiver does almost everything you could require of a deluxe receiver. It performs more like the most refined separate components than like a compact, reasonably priced receiver.

—Julian D. Hirsch

IAD MODEL B3A DYNAMIC RANGE EXPANDER

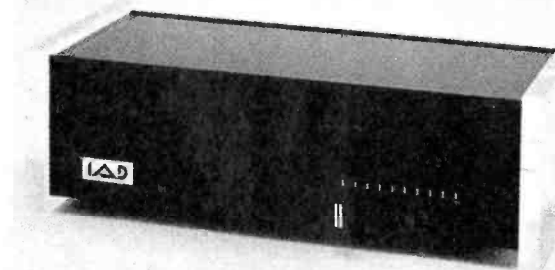Restores dynamics to compressed recorded material.



International Audio Designs has recently introduced a novel dynamic range

expander whose operating parameters (as we'll see) are radically different from those of other expanders we have used. The Model B3A, as with other expanders, is designed to restore some of the program dynamics that are inevitably lost in any compressor-processed recording or broadcast program.

The expander is housed in an attractive black plastic case with thick clear plastic end plates. The case measures 12"L x 5 1/4"D x 3 3/4"H (30.5 x 13.3 x 9.5 cm) and weighs 3 1/2 pounds (1.6 kg).

The manufacturer's warranty covers defects in material and labor for a period of three years from date of purchase. The retail price of the expander is \$279.

Technical Details. The designer of an expander must choose appropriate attack and release time constants, as well as the slope of the expansion (such as 1.5 dB of output change for 1 dB of input signal change). The goal is usually to restore some measure of the compressed dynamics of the program without introducing audible side effects. Almost all expander designs have fallen short of the latter requirement.

If the expansion is accompanied by

"pumping" sounds as the level changes or by transient "fuzz" or "swishes" of background noise, the expander is of little value to the user. By careful design and by limiting the degree of expansion to some extent, these effects can be minimized. It is difficult to eliminate them completely.

IAD has chosen an attack time of 100 ms for the Model B3A, which is relatively slow for some expanders but is fast enough to be effective. On the other hand, a very long release time on the order of 30 seconds renders the reduction in gain following an expansion completely inaudible. As we determined during our tests, the action of the IAD expander is somewhat more complex than this would indicate, but its extremely long release time certainly distinguishes the IAD approach from all others we have seen.

The expander provides a smoothly controllable expansion of as much as 15 dB or more. It can be inserted in the signal path between a preamplifier and a power amplifier or in the tape-monitoring system in an integrated amplifier. With no expansion, the gain of the expander is unity, with each channel's signal passing through an operational amplifier that uses some 80 dB of negative feedback. The input impedance is 47,000 ohms, while the output impedance is 600 ohms.

The maximum output signal level is 9 volts into a high-impedance load or 4 volts into 600 ohms. The maximum rated output is 7.5 volts. Hum and noise are rated to be at least 86 dB below the rated output, with distortion less than 0.05% at any level up to the rated output and 0.005% at outputs of less than 1 volt.

The only operating control on the expander is a slide-type potentiometer that is used to adjust the sensitivity of the expansion circuit. At its minimum setting, there is no expansion. As the pot is moved right toward maximum, increasing amounts of expansion are introduced, depending on the input signal level. Red LED indicators above the control come on at 2-dB intervals that correspond to 1.5 to 13.5 dB of expansion. (The circuits have a somewhat greater range than this.) Although the LED's are sequentially activated by an analog-to-digital converter, the expansion process is smooth and continuous.

There is no power switch on the expander, which is designed to be powered and deactivated when it is plugged into a switched ac outlet of


an amplifying system. With a 2-watt power consumption it is practical to leave the expander on at all times if this proves to be more convenient.

Laboratory Measurements. The output of the expander clipped at 9 volts into a high-impedance load, as rated. The 1000-Hz harmonic distortion was buried in the noise level below 2 volts output, where it measured 0.006% with no expansion being used. At 7 volts output, the THD measured 0.03% at 20 Hz, 0.014% at 1000 Hz, and 0.013% at 20,000 Hz. With full expansion, the THD was 0.04% at 20 and 20,000 Hz and 0.025% at 1000 Hz. The output noise with IEC "A" weighting measured 76 dB below 1 volt, or 91.5 dB below the rated 7.5-volt output.

With no expansion, the frequency response was as flat as our test instruments, measuring ± 0.25 dB from 20 to 20,000 Hz. (IAD's rating is ± 0.3 dB, 5 to 100,000 Hz.) When we applied full expansion, the response appeared to be reasonably flat through the mid-range, being down 1 dB at 200 and 2500 Hz and rolling off to -11 dB at 20 Hz and -12 dB at 20,000 Hz. It was obvious from observing the LED indicators that they did not really represent the response of the expander's amplifiers. Instead, they represent the shaping of the response in its expansion-sensing circuits. Apparently, the expander responds most readily to midrange levels and is less influenced by very low and very high frequencies.

The expander's dynamic behavior was revealed quite clearly when we applied 10-dB increments of input signal level change and plotted the output on a graphic recorder. Starting from a low signal level (our 0-dB reference was below the threshold for the expansion circuit), the first 10-dB increase produced a 12-dB output increase that appeared to be well within the 100-ms rated attack time. The second 10-dB increase stepped the output up by 15.5 dB, while the third 10-dB input increase stepped the output up by 17.5 dB. Hence, a total increase of 30 dB at the input increased the output by 45 dB. On the time scale of the recorder chart, the increases appeared to be instantaneous.

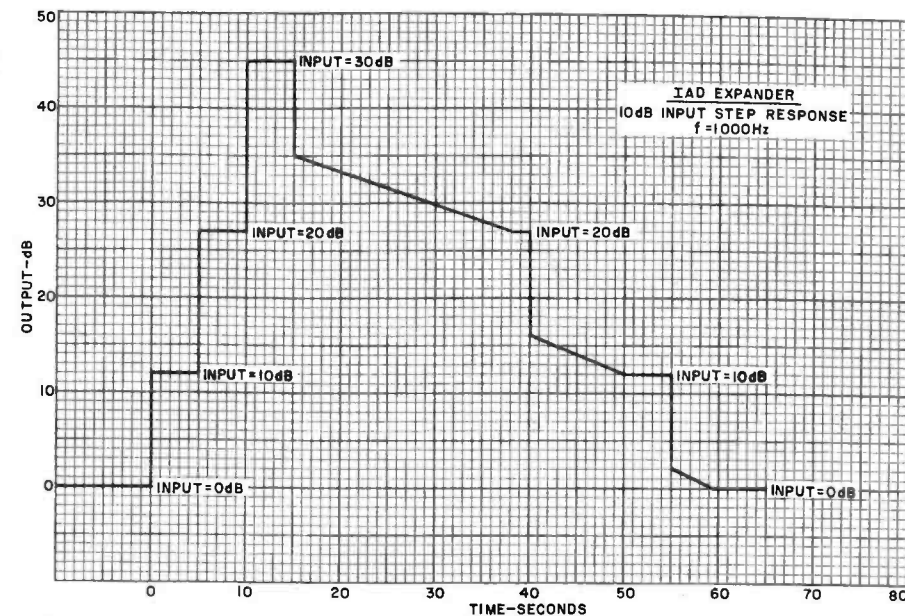When we dropped the input signal level from +30 to +20 dB, the output dropped 10 dB, following the input change. However, the gain of the expander then decreased smoothly by



7.5 dB in the next 22.5 seconds. The next step downward, to +10 dB, also appeared at the output as a 10-dB drop, followed by a 5-dB reduction in the next 10 seconds. Finally, the last reduction, to 0 dB, dropped the output by 10 dB to a +2-dB level, with the output dropping to 0 dB (to equal the input level) in another 4.5 seconds.


User Comment. Our measurements confirmed IAD's claims for the electrical performance of the Model B3A expander. However, the value of the expander can be assessed only by actually operating it in a music system. We connected the expander into several systems and found the tape-monitor connection to be the most practical. Not only does this make the expansion characteristic independent of the volume control setting, but it makes it possible to instantly switch the expander in and out of the system to demonstrate its subjective effect. This is very important if for no other reason than to determine whether or not the expander is really operating.

At no time—regardless of program material, control settings, or other

considerations—were we able to detect the expander in the performance of its function. When none of its LED's were on, switching the expander in and out of the system made no change in the program level. On the other hand, if the LED's indicated considerable expansion, the drop in volume level was dramatic when the expander was bypassed.

The digital operation of the LED's gives the impression that the changes in gain of the amplifiers in the expander also occur in discrete steps. In reality, the changes are so continuous and smooth that one can never detect the expansion action by ear. Depending on where the sensitivity control is set, relative to the program level, one can use the Model B3A as an "upward expander," with the average program level receiving little or no expansion. If you do this, be sure that your amplifier and speaker systems are equal to the task, since 15 dB of expansion will increase the amp's output power by some 32 times compared to what it would be without the expander!

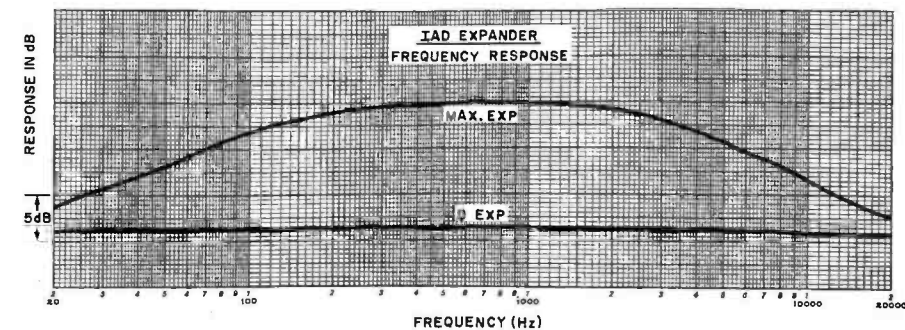An alternate approach is to use a large portion of the expansion at nor-




WINEGARD Chromstar™ THE RUGGEDIZED NEW GENERATION OF TV ANTENNAS!

**40 Models
With Far-Ahead
Features For
Finest Color
Reception Ever!**

**Ask your distributor
for complete information!**

- New Standard Of Excellence In Construction And Performance.
- Anodized and Ruggedized for Weather Protection and Long Life.
- Models To Solve Every Area Reception Problem.
- Most Powerful UHF and VHF Performance Ever.
- New Tri-Linear UHF Director System Extends UHF Reception Distance Up To 30 Miles Farther From Station in Many Areas.

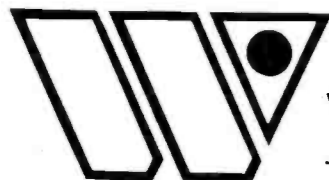**PLUS... New Generation FM Antennas.
High Performance Ruggedized Yagis.
New Solid State Preamplifiers.**



WINEGARD
TELEVISION SYSTEMS

3000 KIRKWOOD
BURLINGTON, IOWA 52601

NEW TRI-LINEAR UHF DIRECTOR SYSTEM*

Increases Gain up to 30%!

Provides broader signal capture area in a more compact configuration.

ORDINARY UHF Director System.




5 1/2"

Uses half-wave directors approximately 5 1/2" long which respond primarily to the high end of the band, with very little gain on the low end.



55"

Boom length required for 12 directors

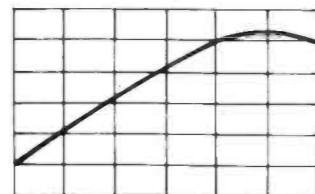


Typical gain curve with ordinary UHF directors. Note low response on low end of band.

WINEGARD High Gain Tri-Linear® Directors



15 1/2"

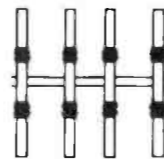Act as 3 half-wave directors on the high end of the band, and re-resonate as a loaded half-wave director on the low end of the band. This results in high linear gain on all UHF channels, giving the antenna sharper directivity and up to 30% more gain over other high gain UHF antennas.



10"

Boom length required for 12 directors



Typical gain curve with Winegard Tri-Linear directors. Note high uniform gain across entire band.

ANODIZED!

Exclusively Winegard! Elements are silver anodized, the boom blue anodized for the best possible protection for aluminum against corrosion and weather.

**FROM WINEGARD
THE FIRST REALLY NEW LINE OF
TV ANTENNAS IN YEARS!**

**Sells Easier/Goes Up Easier/Performs Better/Stays Up Longer
Cuts Down Call-backs./Try One On Your Next Installation.**


Chromstar... a new word for a superior new line of antennas—engineered in the Winegard tradition of integrity, quality, craftsmanship.

Rugged construction and advanced electronics move this new line even farther ahead of other antennas. More powerful performance all down the line. New Tri-Linear director system gives sharper directivity and up to 30% more gain over other high gain UHF antennas. New


features. More benefits. Greater advantages. More of everything for you and your customers, to meet today's demand for years of quality performance.

GET ALL THE FACTS FROM YOUR WINEGARD DISTRIBUTOR, PLUS FREE SPEC CHARTS ON ALL MODELS. Try Chromstar on your next installation and see the *big* difference.

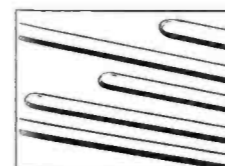
RUGGEDIZED! Chromstar antennas are designed to defy weather and wear—are engineered for extra strength at all points of stress. You can actually see the difference in the rugged construction.



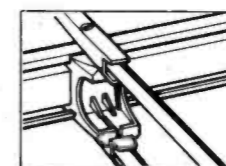
Exclusive 7/8" diameter aluminum tubing for 30% greater strength, better performance, longer life. Winegard is the first and only manufacturer to use this larger diameter.



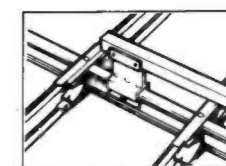
Newtruss-type phasing bars, top and bottom, with more conductive surface, give maximum transfer of signal. Truss-type "bridge" construction more than doubles boom strength.



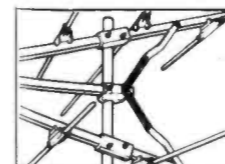
Double boom on longer flat line models for extra strength & rigidity.



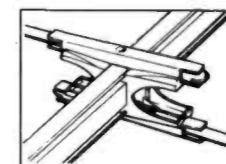New scissors-type struts between upper and lower booms and center boom on wedge models, for extra support, easier installation.



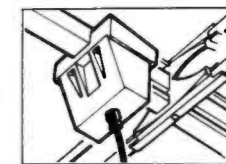High-impact girder design support insulators are moulded of super-tough Noryl G-E plastic. Four positive locks give maximum support and permanent alignment.



Critical-point weather protection! *New compact weatherproof cartridge housing for downlead, preamplifiers and filter modules. New printed circuit downlead module with both twin lead and 75 ohm coax connections. No separate matching transformer required.

TV ANTENNAS MORE PEOPLE LOOK UP TO

mal program levels (turning down the amp's volume control and raising the expander's sensitivity control to restore the lost volume). Then the Model B3A acts as a "downward expander" and in the process reduces noise and hum by as much as 15 dB. In this mode, soft passages may become nearly inaudible. For our purposes, the best mode was an intermediate stage, with the third or fourth LED on at average program levels. This provided a useful amount of expansion as well as some noise reduction.

The effectiveness of the expander depends to a great extent on program

dynamics. With most records and tapes, especially where the program has been allowed to retain some of its dynamic content, the results are nothing short of fantastic. A commercially taped piano solo, for example, was reproduced with its pianissimo portions barely audible, while fortissimo passages drove the amplifier to more than 200 watts/channel output. The sound was highly realistic, since one never had the sense that the system's gain was being manipulated.


It is our opinion that the IAD Model B3A can restore a substantial amount of the compressed dynamics to much

of today's recorded program material. The degree to which its function can be utilized depends to a great extent on the capabilities of the power amplifier and speaker systems with which it is used. We found the expander to be compatible with good 30-watt/channel receivers as well as with super-power amps in the greater than 200-watt/channel class. In any event, we cannot imagine any way in which the expander could degrade any program fed through it if the amplifier and speaker system ratings are not exceeded.

CIRCLE NO. 65 ON FREE INFORMATION CARD

SHURE MODEL M95ED STEREO PHONO CARTRIDGE

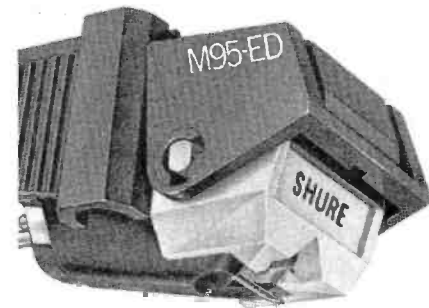Moderately priced, it has "sound" of more costly V-15 Type III.



The new Shure M95ED stereo phono cartridge falls between the company's top-

of-the-line V-15 Type III and its moderately priced Model M91ED. The new cartridge has a pole piece that is similar to the one used in the Type III, although it is not constructed of laminated elements. The design makes possible a lower winding inductance, which results in a flat frequency response that is almost identical to that of the Type III. A low stylus mass of 0.5 mg promises excellent high-frequency "trackability."

The physical appearance of the cartridge is similar to that of the Type III, including an integral swing-away stylus guard as part of the replaceable stylus assembly. The trackability of the cartridge throughout the audio range is such that at its nominal operating force of 1 gram it is about equal to the Type III operating at 0.75 gram.

The retail price of the Shure Model M95ED stereo phono cartridge is \$59.95.

Laboratory Measurements. We installed the cartridge in the tonearm

of a high-quality record player for our tests. Operating the cartridge at a 1-gram tracking force, we soon confirmed that it was able to track very high velocities at low and midrange frequencies on our Cook and Fairchild test records. With another tracking test record, produced by the German Hi-Fi Institute, the cartridge tracked 300-Hz tones recorded at a 60-micrometer amplitude without distortion at 1 gram. At its maximum rated force of 1.5 grams, it was able to track the 90-micrometer band on the record. (Most fine cartridges can track 60 to 70 micrometers, but few can cope with the higher levels.)

High-frequency tracking ability tests using the specially shaped 10,800-Hz tone bursts of the Shure TTR-103 test record revealed the excellence of the cartridge's high-frequency performance. Tracking distortion was on a par with the best cartridges we have tested. A more conventional intermodulation-distortion (IM) measurement with the Shure TTR-102 record that mixes 400- and 4000-Hz tones indicated that the IM was only 2% maximum up to 22.5 cm/s.

The output from the cartridge at 3.54 cm/second was 4.3 mV/channel. The stylus's resonance of about 20,000 Hz revealed itself as a ringing of several cycles on a 1000-Hz square wave from the CBS STR/111 test record.

Initially, we tested the cartridge's frequency response with the standard cable and tonearm capacitance of the record player (200 pF, which is typical

for many players). The response had a peak of about 4 dB at 16,000 Hz. Since Shure recommends a load capacitance of 400 to 500 pF for flattest response, we added capacitance to bring the total to 440 pF and measured the response again. This time it was notably flat, varying ± 1 dB from 40 to 17,500 Hz and dropping to -4 dB at 20,000 Hz. The separation, which was identical on both channels, was better than 30 dB at frequencies below 2000 Hz and gradually reduced to 17 dB at 10,000 Hz and 5 dB at 20,000 Hz.

User Comment. Comparing Shure's specifications for the new cartridge and the slightly less expensive M91ED, the only apparent difference is 2 dB greater "trackability" at 400 Hz for the former. Although this is certainly desirable, it would not in itself warrant the creation of a new cartridge. The real difference, however, is in the sound quality of the two cartridges.

The M91ED has a slightly depressed output in the upper midrange that gives its response curve a "sway-backed" appearance. On the other hand, the M95ED has the same flat response characteristic as the V-15 Type III. Therefore, although it is priced nearer the M91ED, it can sound very much like the costlier Type III.

We compared the M95ED to the M91ED because the two are very close in price. In an A-B comparison, the latter had a warmer, somewhat heavier sound, while the M95ED was brighter and sharper in its apparent definition. It would be impossible to

say that one cartridge sounds better than the other—only that each has a different sound that must be judged by the listener.

If you like the "sound" of the expensive V-15 Type III, the M95ED should be a moderately priced alternative.

CIRCLE NO. 66 ON FREE INFORMATION CARD

YAMAHA MODEL CR-800 AM/STEREO FM RECEIVER

Medium-power unit has superb FM performance.



Ranking next to the top of Yamaha's receiver line is the Model CR-800. This AM/ste-

reo FM receiver is very conservatively rated at 45 watts/channel into 8-ohm loads. The receiver features top-quality performance and a full complement of controls. It has the distinctive Yamaha equipment styling, characterized by a clean, uncluttered satin-aluminum front panel and large dial cutout area.

The receiver measures $17\frac{3}{4}$ "W \times $11\frac{3}{4}$ "D \times $6\frac{1}{4}$ "H (45.1 \times 29.8 \times 15.9 cm) and weighs 31 pounds (14 kg). It retails for \$580.

General Description. The relatively short FM dial scale is linearly calibrated at 0.5-MHz intervals. To the left of the scales are the FM zero-center and AM/FM relative signal strength meters, the latter calibrated logarithmically over a 100-dB range. Three red LED's to the right of the scale indicate when the receiver is on, when a station is tuned in, and when a stereo-FM transmission is being received.

The large tuning knob is located to the right of the dial window. All other controls are located on the lower half of the receiver's front panel. Lever switches are provided for controlling receiver power, a 20-dB audio attenuator for temporary level reduction, stereo/mono switching, and the filters. Three-position, center-off switches are used for the filters.


The low-cut filter provides a choice of 20- or 70-Hz cutoff frequency, with a 12-dB/octave slope. When the high-

cut filter is in its down position, it introduces a 6-dB/octave rolloff beyond 8000 Hz. In the up position, it partially blends the high audio frequencies to reduce noise on stereo programs. The center positions of both switches disable the filters. (Many receivers use a similar system for stereo FM noise reduction, but this Yamaha receiver is the first we have seen to apply it to all program sources.)

The BASS and TREBLE controls have 11 detented positions. The BALANCE control is a center-detented ring concentric with the VOLUME control. A separate LOUDNESS control, also with 11 detented positions, gradually introduces bass and treble boost as it lowers the midrange level. It is used in conjunction with the VOLUME control to provide correct low-level volume compensation that is independent of the setting of the VOLUME control. A separate MICROPHONE volume control, with an OFF position, is provided for adjusting the level from a microphone plugged into an adjacent jack.

The other controls are rotary switches, operated by bar knobs whose settings can be seen at a glance. One switch is for activating either, both, or neither of two pairs of speaker systems connected to the receiver's outputs. Another is for controlling the interface between the receiver and two tape decks. In its center position, the selected program source is heard through the speaker systems. Moving it one position to either side of center permits monitoring of the playback output from either tape deck. An additional two positions per-

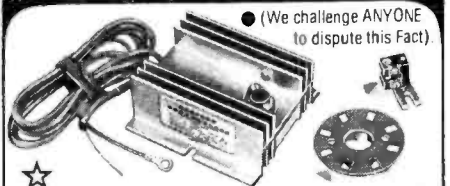ALLISON 'OPTO-ELECTRIC' The BEST...the ULTIMATE of All Ignition Systems!



Never wears out or needs any Maintenance!



gives you Maximum Power with continuous PEAK PERFORMANCE while reducing Maintenance and Operating Costs!

The Allison OPTO-ELECTRIC System eliminates the Points and Condenser, replacing them with an OPTO-ELECTRONIC TRIGGER, using a Light-Emitting Diode and Photo transistor. The System operates on a beam of Light. As there are NO moving parts in rubbing contact, "Friction-wear" is completely eliminated...Timing adjustments are PERMANENT.

- Gives 40-Times more Timing accuracy than ANY system using "Mechanical" Breaker-Points! UNLIMITED RPM!
- "Electronically-Controlled" DWELL automatically supplies HIGHEST Performance at both Low and High speeds. Spark strength does not fall off at high RPM. POSITIVE SPARK helps eliminate "Misfire" for faster acceleration and improved Engine Performance. Sparkplugs LAST 3 to 10-Times LONGER.
- Easier Starting under any condition! Smoother running... (NO TIMING FLUCTUATION as with Magnetic Impulse Units).
- All SOLID-STATE Components. UNAFFECTED By Temperature, Moisture, or Vibration! Only Highest grade materials used... Guarantees you Solid, Dependable Performance!
- PERFECT TIMING INCREASES Engine Efficiency and Gas Mileage. SAVES Precious Fuel! Allison gives you MAXIMUM Engine Efficiency 100% of the Time... and that's the name of the game for the BEST in GAS MILEAGE AND ECONOMY.

Perfect Timing and Dwell never change.

- Pays for itself! Eliminates Ignition Tune-Ups forever! "INFINITE LIFE"...Once installed...Never needs replacing!



PROVEN RELIABILITY!
Each Unit Tested to 15,000 RPM.
Road and Race Proven.
(Opto-Electric Systems won at INDY Two years in a row!)

You CAN install the ALLISON System in ALL the U.S. made & Foreign Cars! (4, 6, or 8-Cylinder).

"EASIEST-TO-INSTALL" UNIT ON THE MARKET.
(Not necessary to dismantle Distributor as with other systems).

If you want the BEST, and SAVE! This is IT!

ORDER with CONFIDENCE... SATISFACTION GUARANTEED or Full Refund.

10-YEAR FACTORY WARRANTY!
(Free Repair or Replacement).

Send Check or M/O State Make, Year, Engine Size. (Calif. Res. add Tax). (So New...It's Sold ONLY FROM FACTORY DIRECT).

You may use your MASTER CHARGE or BANKAMERICARD. Send us (1) Your Number, (2) Interbank No., (3) Exp. Date.

Before buying any other Type ignition system... Send Postcard for our FREE BROCHURE.

If you have already installed a C-D ignition system, Modernize and Increase its Efficiency... CONVERT YOUR "C-D" UNIT TO BREAKERLESS! Opto-Electric "TRIGGER UNIT"...Only \$34.95

Our BEST Salesmen are the users of our ALLISON System!


America's Oldest and Largest Mfg. of Opto-Electronic Ignition Systems.

ALLISON AUTOMOTIVE COMPANY
1267-P, East EDNA PL., COVINA, CAL. 91722

CIRCLE NO. 9 ON FREE INFORMATION CARD 73

400 Heathkit gift ideas

efficient, creative values for everyone

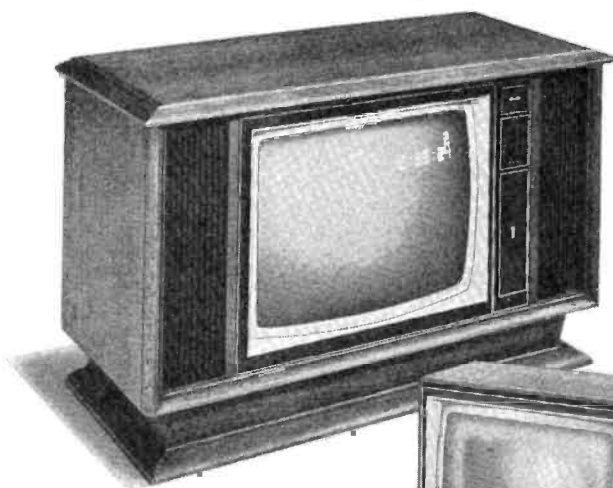

①

Digital-Design Color TVs

Now, enjoy the super performance of Digital-Design TV in 5 picture sizes — 25, 21, 19, 17, 15.



The design the experts say leads the way in advanced technology.

Whatever picture size you choose as best for you, the technical advances of the design that startled the industry are yours in Heathkit Color TV.

On-Screen Channel Numbers

Big, bright, white numbers you can see from any angle, even across the room. Adjustable in brightness. Positionable anywhere on the screen. Adjustable for time duration of up to 1½ minutes or they can remain on all the time, at your option. The numbers change as you change channels. No other channel readout is as convenient.



On-Screen Clock Time

Here's a \$29.95 option that's a marvel of convenience, too. Big ¾" numbers appearing just below the channel numbers tell you the exact time every time you change channels. Right down to the second, if you wish. And it displays in 12 or 24-hour format.


Fixed-Filter for Best Pictures Longer

Unique. Exclusive. Heath-designed circuitry incorporates a fixed L-C type filter with an integrated-circuit IF amplifier to



② **NEW High Fidelity AM/FM Table Radio**

At last, a table radio worth listening to... one that performs like hi-fi components. 5 µV sensitivity; ceramic filters for 60 dB selectivity; and an output power of 5 watts, minimum rms, at less than 1% total harmonic distortion, from 60 to 15,000 Hz into its 8 ohm full range high compliance speaker. The closed cabinet features a teak wood grain vinyl covering and black, molded double-knit jersey front panel. Kit GR-1085, \$99.95

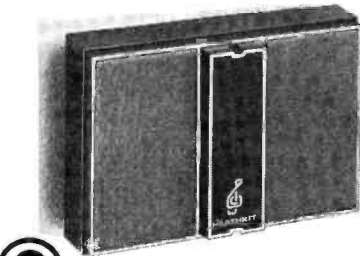

③ **NEW Programmable Electronic "Doorbell"**

Put a song at your doorstep with this unique kit. Program it to play your favorite song. C through C' "keyboard" with plug-in leads for up to 16 notes. Change your tune when you wish to celebrate a season, anniversary, birthday, or special party. One watt sound power; controls for tuning, volume, speed, and decay characteristics. Kit TD-1089, \$44.95



④ **NEW versatile, low cost 5-digit counter**

Measures frequency from 5 Hz to 30 MHz, period to 99.999 seconds, counts events to 99,999, and it will operate on 120 VAC or 12 VDC. As a freq. counter it will resolve to 1 Hz; sensitivity is 15 mV above 50 Hz, 50 mV below 50 Hz. In the period mode, it will resolve to 1 msec. Has Over-range indicator; gate lamp; 3-position input attenuator; 10 MHz time base. Kit IM-4100, \$129.95

produce an ideally shaped bandpass. That means you not only get less adjacent channel interference, but also consistently excellent color pictures year after year because it never needs periodic instrument alignment. These Heathkit Color TVs always look better.

100% Solid-State

And more integrated circuits than any. The only tube in these sets is the picture tube. This sophisticated circuitry gives you less interference, truer colors, more precise, reliable tints, improved sensitivity, greater noise immunity, and better picture definition. Solid long-life performance.

The Differences

Tuning. In the 25v and 21v sizes, you get Total Electronic Touch Tuning. Silent varactor tuners, no moving parts. A programmable digital counter controls the tuning—sweeping up or down the 16 pre-selected channels. And remote control of all functions is just \$89.95. In the small screen sizes, the tuning is all-channel detent type.

One-Button Picture Control in the three

smaller sets restores brightness, contrast, color and tint to pre-set levels at the touch of a button. Child-proof performance.

Latest-design Picture Tubes. In the two larger sets you enjoy brighter pictures with greater contrast thanks to the deluxe Black (negative) Matrix tubes. The three table models use picture tubes with the new precision in-line gun and slotted shadow mask for greater light output and picture realism.

Easier to build and service.

Plug-in circuit modules and wiring harnesses make these sets the easiest to build of all. And the new digital-design Dot Generator, slide-out Service Drawer and Test Meter make self-service easier.

Compare the value.

Send for your free Heathkit catalog, choose the model you prefer. Then compare it with any brand—we think you'll agree you get more for your money with Heathkit Digital-Design Color TV.

For as low as \$399.95, you can enjoy Heathkit Digital Design Color TV.



⑤

MODULUS™

The new total-flexibility music system. For your changing needs.

Heath proudly introduces MODULUS. The totally modular music system that enables you to make of it what you will, change it when you like. With complete freedom. Without obsolescence.

As you like it.

Performance and versatility as in the finest of separate components, yet with the convenience of an integrated receiver.

Your MODULUS custom music system begins with Module I, the AN-2016 Digital AM/FM Tuner/Preamplifier. A superb FM tuner with sophisticated circuitry and exceptional specifications (four ½" LEDs display frequencies; dual JFET, 4-gang tuner with 1.7 µV sensitivity; digital discriminator; LC IF filter with over 100 dB selectivity; phase-locked loop multiplex with over 40 dB separation). AM you'll really enjoy hearing (dual-gate MOSFET tuner and mixer stages; computer-designed 9-pole LC IF filter for no alignment; shielded loop antenna). A superlative preamplifier that functions in stereo or 4-channel modes with specifications unlike any component we've ever offered. Distortion below 0.05% even at full out-

put. Hum and noise are 80 dB below a 0.25 v. input even in the high-level section. A phono preamp with over 94 dB dynamic range—better than most records! Versatile control center. Special speaker protecting circuitry. Four lighted output meters with 40 dB dynamic range. Separate bass, treble, and level controls for front and back channels. Master volume control. 21 pushbutton switches that light when activated. They include: output; inputs (stereo phono, CD-4, aux., tape, tape monitor, dubbing AM and FM); mode (mono, stereo front channels, stereo 4 channels, SQ, and discrete 4-channel); high filter; low filter; loudness; tone flat; squelch defeat; FM Dolby; and power. Use it as a tuner only, as a driver for your present power amps, as a control center for taping, so good you can even use it as a broadcast station monitor. Kit AN-2016, \$599.95

Expand your MODULUS system with your choice of stereo power amplifiers. Module II is the medium power AA-1505. Module III is the high power AA-1506.

35 or 60 watts, min. RMS, per channel into 8 ohms at less than 0.1% distortion from 20-20,000 Hz. Styled to match the Module I tuner/preamp. Add one of either power level for a stereo receiver; add two for a 4-channel receiver. Kit AA-1505, \$159.95; AA-1506, \$179.95

Choose your mode and input. Module IV is the FM Dolby module AD-1504 for reduced noise and greater dynamic broadcast range (\$39.95). Module V is the CD-4 Demodulator for the spacious sound of CD-4 discrete 4-channel records (\$79.95). Module VI is the SQ Decoder for quadraphonic separation of matrixed material; full logic and variable blend (\$49.95). All are housed inside the tuner/preamp module.

A "Living" music system.

MODULUS is designed for you—the way you live—today and tomorrow. It can grow with you, adapt to your changing life style, flex with changing technology. Whatever your desires in music systems, now and later, MODULUS.

NEW HEATHKIT CATALOG

FREE

Heathkit




Please send my

PC-111

HEATHKIT CATALOG

10-11

Name

Address

City

State

Zip

Heathkit

SEND FOR YOUR FREE COPY TODAY!

World's largest electronic kit catalog. A kit for every interest, every budget. Easy credit terms.

• World's largest selection of electronic kits
 • World's most comprehensive assembly manuals
 — written for beginners • Top-quality designs & parts • More features and performance for your dollar • Direct-to-you savings • Nationwide service



NEW 2-Way Telephone Amps

and "talk" and amplified "listen", without dialer. Real hands-free answer—use from 10' away. VOX silently switches from built-in speaker to speaker without clipped feedback squeals. GD-1112 with regular phone. GD-1162 with dial and electronic ringer works extension phone. Easy to build, for use at home or office. Kit GD-1162, \$69.95.

Send today.


Dept. 10-11
MI 49022
Heathkit Catalog,
shipping.



WITHOUT NOTICE. CL-575

400 Heathkit gift ideas


efficient, creative values for everyone

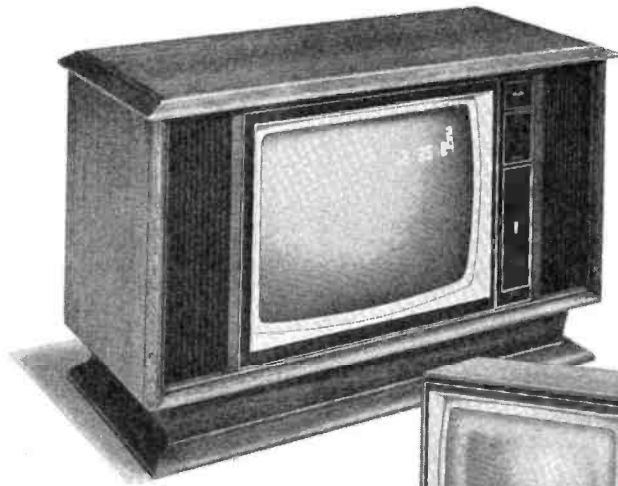

①

Digital-Design Color TVs

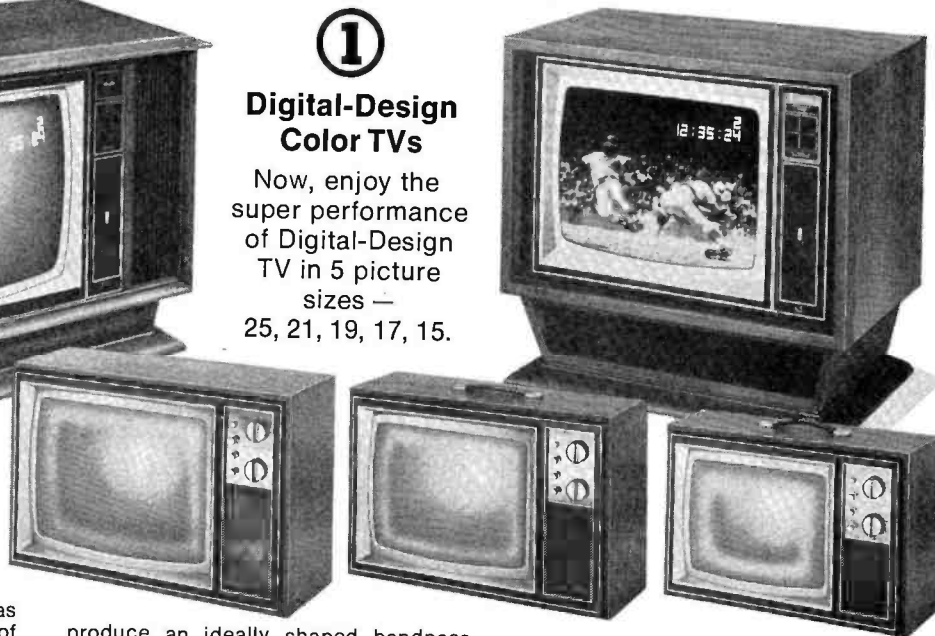Now, enjoy the super performance of Digital-Design TV in 5 picture sizes — 25, 21, 19, 17, 15.



The design the experts say leads the way in advanced technology.

Whatever picture size you choose as best for you, the technical advances of the design that startled the industry are yours in Heathkit Color TV.

On-Screen Channel Numbers

Big, bright, white numbers you can see from any angle, even across the room. Adjustable in brightness. Positionable anywhere on the screen. Adjustable for time duration of up to 1½ minutes or they can remain on all the time, at your option. The numbers disappear as you change channels. No other channel readout is as convenient.

On-Screen Clock Time

Here's a \$29.95 option that's a convenience, too. Big ¾" numbers appearing just below the channel numbers tell you the exact time every you change channels. Right down to the second, if you wish. And it displays in 12 or 24-hour format.

Fixed-Filter for Best Pictures

Unique. Exclusive. Heath-designed circuitry incorporates a fixed L-C type with an integrated-circuit IF amplifier.



② NEW High Fidelity AM/FM Table Radio

At last, a table radio worth listing as one that performs like hi-fi. Comes with 5 μ V sensitivity; ceramic filters for selectivity; and an output power of 5 watts, minimum rms, at less than 1% harmonic distortion, from 60 to 16,000 Hz. The closed cabinet features a teak wood grain vinyl covering and a molded double-knit jersey front. Kit GR-1085, \$99.95.

HEATH COMPANY
BENTON HARBOR, MICHIGAN 49022

Put stamp here. The Post Office will not deliver mail without postage.

produce an ideally shaped bandpass. That means you not only get less adjacent channel interference, but also consistently excellent color pictures year after year because it never needs periodic instrument alignment. These Heathkit Color TVs always look better.

100% Solid-State

And more integrated circuits than any. The only tube in these sets is the picture tube. This sophisticated circuitry gives

smaller sets restores brightness, contrast, color and tint to pre-set levels at the touch of a button. Child-proof performance.

Latest-design Picture Tubes. In the two larger sets you enjoy brighter pictures with greater contrast thanks to the deluxe Black (negative) Matrix tubes. The three table models use picture tubes with the new precision in-line gun and slotted shadow mask for greater light

SEND CARD FOR FREE HEATHKIT CATALOG

Discover the fun and savings of "Do-it-yourself" electronics

OVER 400 KITS TO CHOOSE FROM

- digital design color TV • digital clocks & thermometers • stereo & 4-channel hi-fi • fishing & marine • ham radio • home appliances • calculators • treasure finders • weather stations • auto tuneup • radio control • test instruments • electronic organs • hundreds more.



⑤

MODULUS™

The new total-flexibility music system. For your changing needs.

Heath proudly introduces MODULUS. The totally modular music system that enables you to make of it what you will, change it when you like. With complete freedom. Without obsolescence.

As you like it.

Performance and versatility as in the finest of separate components, yet with the convenience of an integrated receiver.

Your MODULUS custom music system begins with Module I, the AN-2016 Digital AM/FM Tuner/Preamplifier. A superb FM tuner with sophisticated circuitry and exceptional specifications (four ½" LEDs display frequencies; dual JFET, 4-gang tuner with 1.7 μ V sensitivity; digital discriminator; LC IF filter with over 100 dB selectivity; phase-locked loop multiplex with over 40 dB separation). AM you'll really enjoy hearing (dual-gate MOSFET tuner and mixer stages; computer-designed 9-pole LC IF filter for no alignment; shielded loop antenna). A superlative preamplifier that functions in stereo or 4-channel modes with specifications unlike any component we've ever offered. Distortion below 0.05% even at full out-



⑥

NEW 3-Way Speaker

Looks and sounds like it should cost \$100 more! High performance 3-way system has a 10" woofer, 4½" mid-range, 1" dome tweeter. Drives with 10 watts, yet a super-power amp reveals its unusual dynamic range and high power handling capabilities. Enclosure has walnut veneer on all sides and front for use without the black foam grille. Tweeter and front-mounted switch plate are interchangeable for optimum imaging in horizontal or vertical position. Kit AS-1373, \$149.95

⑦

NEW Digital Stopwatch

Programmable — for the time of your sporting life. You program in a time (up to 9 hours, 59 min., 59 secs.) and it will count up to that time or down from it to zero. Or it will count 99 hours, 59 mins., 59:99 secs. in the five other functions which include: Start/Stop Elapsed; Sequential; Total Activity; Split; & Start/Stop Activity. 8 digits & 2 IC counters with accuracy to $\pm 0.003\%$ & resolution to 1/100th second. Jacks for external trigger and alarm. Includes nickel-cad. batteries & charger. Kit GB-1201, \$99.95

⑧

NEW 2-Way Telephone Amps

Amplified "talk" and amplified "listen", with or without dialer. Real hands-free convenience — use from 10' away. VOX control silently switches from built-in microphone to speaker without clipped words or feedback squeals. GD-1112 works with regular phone. GD-1162 with built-in dial and electronic ringer works like an extension phone. Easy to build, convenient for use at home or office. Kit GD-1112, \$49.95; Kit GD-1162, \$69.95.



put. Hum and noise are 80 dB below a 0.25 v. input even in the high-level section. A phono preamp with over 94 dB dynamic range — better than most records! Versatile control center. Special speaker protecting circuitry. Four lighted output meters with 40 dB dynamic range. Separate bass, treble, and level controls for front and back channels. Master volume control. 21 pushbutton switches that light when activated. They include: output; inputs (stereo phono, CD-4, aux., tape, tape monitor, dubbing AM and FM); mode (mono, stereo front channels, stereo 4 channels, SQ, and discrete 4-channel); high filter; low filter; loudness; tone flat; squelch defeat; FM Dolby; and power. Use it as a tuner only, as a driver for your present power amps, as a control center for taping, so good you can even use it as a broadcast station monitor. Kit AN-2016, \$599.95


Expand your MODULUS system with your choice of stereo power amplifiers. Module II is the medium power AA-1505. Module III is the high power AA-1506.

35 or 60 watts, min. RMS, per channel into 8 ohms at less than 0.1% distortion from 20-20,000 Hz. Styled to match the Module I tuner/preamp. Add one of either power level for a stereo receiver; add two for a 4-channel receiver. Kit AA-1505, \$159.95; AA-1506, \$179.95

Choose your mode and input. Module IV is the FM Dolby module AD-1504 for reduced noise and greater dynamic broadcast range (\$39.95). Module V is the CD-4 Demodulator for the spacious sound of CD-4 discrete 4-channel records (\$79.95). Module VI is the SQ Decoder for quadraphonic separation of matrixed material; full logic and variable blend (\$49.95). All are housed inside the tuner/preamp module.

A "Living" music system.

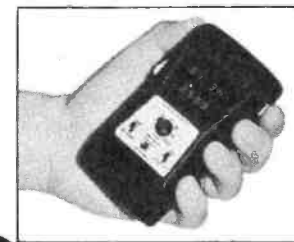MODULUS is designed for you — the way you live — today and tomorrow. It can grow with you, adapt to your changing life style, flex with changing technology. Whatever your desires in music systems, now and later, MODULUS.




392 other gift ideas in the free Heathkit catalog. Send today.

HEATHKIT ELECTRONIC CENTERS — Units of Schlumberger Products Corporation Retail prices slightly higher.

ARIZ.: Phoenix; CALIF.: Anaheim, El Cerrito, Los Angeles, Pomona, Redwood City, San Diego (La Mesa), Woodland Hills; COLO.: Denver; CONN.: Hartford (Avon); FLA.: Miami (Hialeah), Tampa; GA.: Atlanta; ILL.: Chicago, Downers Grove; IND.: Indianapolis; KANSAS: Kansas City (Mission); KY.: Louisville; LA.: New Orleans (Kenner); MD.: Baltimore, Rockville; MASS.: Boston (Wellesley), Boston (Peabody); MICH.: Detroit; MINN.: Minneapolis (Hopkins); MO.: St. Louis (Bridgeton); NEB.: Omaha; N.J.: Fair Lawn; N.Y.: Buffalo (Amherst), New York City, Jericho (L.I.), Rochester, White Plains; OHIO: Cincinnati (Woodlawn), Cleveland, Columbus, Toledo; PA.: Philadelphia, Pittsburgh; R.I.: Providence (Warwick); TEXAS: Dallas, Houston; VA.: Norfolk (Va. Beach); WASH.: Seattle; WIS.: Milwaukee.

HEATH Schlumberger	Heath Company, Dept. 10-11 Benton Harbor, MI 49022
<input type="checkbox"/> Please send my free new Heathkit Catalog. <input type="checkbox"/> Enclosed is \$_____ plus shipping. Please send model(s)_____	
NAME _____	
ADDRESS _____	
CITY _____	STATE _____ ZIP _____
<small>PRICES ARE FACTORY MAIL ORDER, FOB PRICES & SPECIFICATIONS SUBJECT TO CHANGE WITHOUT NOTICE.</small>	
CL-575	

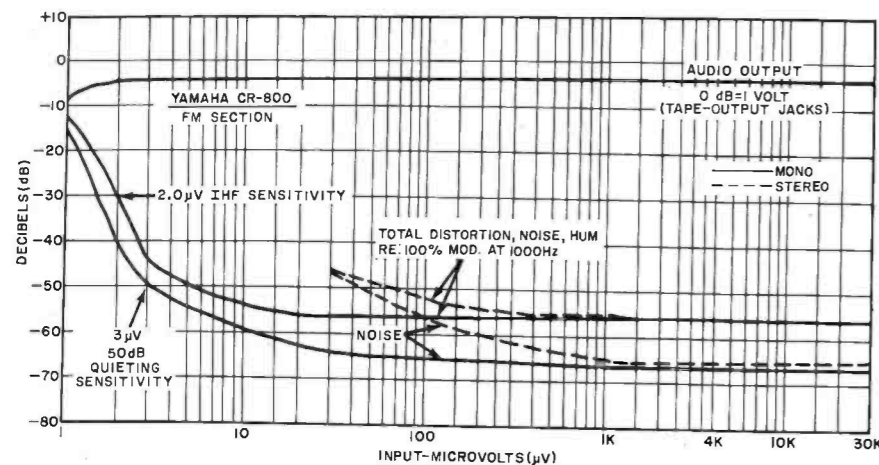


mit connecting the recorders for dubbing from either machine to the other. (The normally selected program source is not heard in this mode.) Finally, the desired program source is selected by a switch with positions for AUX, two magnetic PHONO cartridges, FM with and without interstation noise muting, and AM. A headphone jack is located below the microphone jack.

On the rear apron of the receiver are the various inputs and outputs, plus separate preamplifier outputs and main amplifier inputs that permit independent operation of the two receiver sections or insertion of accessories (active equalizer, active crossover system, etc.) The inputs are normally joined to the outputs in pairs by an adjacent slide switch. The speaker outputs are insulated spring clips. An IF OUT jack is presumably intended for use with a 4-channel FM adapter. In spite of its nomenclature, it is apparently a detected composite stereo signal without deemphasis.

There are antenna inputs for 300- and 75-ohm FM antennas and a wire AM antenna, plus a pivoted ferrite rod

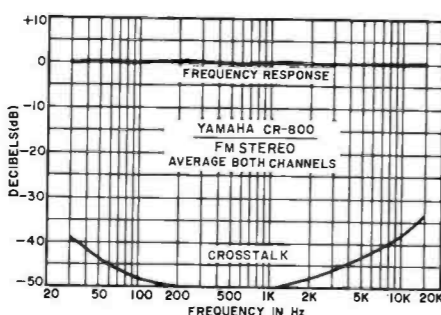AM antenna. Two of the four accessory ac outlets on the rear apron are switched.



Laboratory Measurements. The measured performance of our test receiver speaks for itself. In virtually every respect, the receiver far surpassed its published ratings!

With both channels driven into 8-ohm loads at 1000 Hz, the audio outputs clipped at 61 watts/channel. Into 4- and 16-ohm loads, clipping occurred at 79 and 41 watts/channel, respectively. The THD at 1000 Hz was below the noise level up to several watts output. It measured less than

0.03% from 0.7 to about 60 watts output. The IM distortion was less than 0.03% from 0.1 to 30 watts, reaching 0.05% at 60 watts output. (The conservatism of the receiver's ratings is illustrated by its rated 45 watts/channel from 20 to 20,000 Hz at less than 0.1% THD.)

At the rated 45-watt output, the distortion was less than 0.035% from 20 to 20,000 Hz, typically measuring less than 0.015%. It was roughly the same at half power and even at one-tenth power did not exceed 0.06% over the full audio range.

A reference 10-watt power output required an input of 57 mV at the AUX, 1.2 mV at the PHONO, and 1.1 mV at the MIC inputs. The respective unweighted S/N figures were 80, 78, and 74 dB, referred to 10 watts. These represent exceptionally quiet amplification, especially through the low-level PHONO and MIC inputs. The phono preamp overloaded at a very high 250 mV, while the microphone preamp input overloaded at 700 mV—a new high in our experience with receivers and amplifiers.

The receiver easily handled the one-hour preconditioning period at one-third power before the distortion and power measurements were made. Even more remarkable, it was accidentally subjected to 30 minutes of severe overloading, driven into hard clipping on both channels, without suffering any damage.

The RIAA phono equalization was accurate to within ± 0.5 dB from 30 to 20,000 Hz. It was affected by cartridge inductance to about the same extent as most good amplifiers and receivers, with a reduction of output at 15,000 Hz of 1 to 2 dB, depending on the specific cartridge used.

The filters had the rated characteristics, with excellent low-cut action but a gradual high-frequency rolloff that was of little use in hiss reduction. The tone controls had considerably more range at the low than at the high frequencies, the former with a sliding inflection point and the latter with a hinged characteristic.

The loudness compensation was both unusual and effective. The first few steps of loudness reduction produced only a trace of low- and high-frequency boost. Further operation of the control provided the rather extreme characteristics of most loudness-control systems.

The FM tuner's IHF usable sensitivity measured 2.0 μ V. Its 50-dB quieting sensitivity was 3.0 μ V. The stereo switching threshold (and the muting threshold) was between 15 and 22 μ V. This is somewhat high for such a sensitive tuner, but it does assure that all received signals will be of good quality. The ultimate unweighted S/N ratio was 67 dB in mono and 66 dB in stereo. At 1000 μ V, the distortion was a low 0.15% in both mono and stereo.

The FM capture ratio was an outstanding 0.9 dB, and the AM rejection was far above average at 70 dB. Similarly impressive measurements were obtained for image rejection (79 dB) and alternate-channel selectivity (88 dB). The 19-kHz pilot carrier leakage into the audio outputs was unmeasurable, being more than 85 dB below the 100% modulated program level.

The stereo FM frequency response was literally ruler-flat, with a variation of less than ± 0.3 dB from 30 to 15,000 Hz. This is especially noteworthy in

view of the pilot carrier rejection of the receiver, since most tuners use low-pass filters for rejection to prevent appreciable attenuation at 15,000 Hz. The stereo channel separation exceeded 40 dB from 30 to 7500 Hz and 50 dB from 150 to 1500 Hz. It was still a healthy 33 dB at 15,000 Hz.

The AM frequency response was down 6 dB at 140 and 3200 Hz.

User Comment. As the laboratory tests reveal, this is a receiver that invites the use of superlatives. For example, the FM tuner performance comes close to matching that of the \$1200 Yamaha Model CT-7000 FM tuner and is far better than what we would expect from a receiver at any price. The convenient FM tuning system features afc defeat when the TUNING knob is touched and dimly lights the AFC/STATION LED on the dial when a signal is properly tuned. Releasing the knob permits the afc to gradually come on, bringing the LED to full brilliance. Although afc is certainly not needed to correct for drift, which is essentially nonexistent, it makes the tuning procedure simpler than it would otherwise have been.



The dial calibrations were very accurate and easy to read against the hair line on the movable illuminated plastic indicator. The tuning meter gives a useful indication of relative signal strength, from levels too weak to operate the muting system to the highest that will ever be encountered. All the controls operate smoothly and with positive action, and a total lack of unwanted electrical transients must be experienced to be appreciated.

The FM muting system is one of the best we have used. It had no trace of thumps or noise bursts. As with most stereo receivers, the AM section of the Model CR-800 is below "hi-fi" quality, with the contrast made even more vivid by the superb FM performance of the receiver.

We usually take a dim view of loudness-compensation systems, which tend to make everything sound boomy and unnatural. However, with the system in this receiver, we make an exception. When the control is set to maximum and the volume is set to the loudest level you expect to use, reducing the LOUDNESS control setting preserves a natural frequency balance. At the lowest settings, the compensation becomes rather great. Over most of its range, one is hardly aware of the action of the loudness compensation, which is as it should be.

Obviously, our experience with the Model CR-800 receiver has left us enthusiastic. There are a few other receivers whose quality is similarly above reproach, and we would not attempt to rank them in any order of preference. On the other hand, we can say with assurance that we have never used a stereo receiver whose performance surpasses that of the Model CR-800 in any significant respect. Other receivers might be more powerful or have some features lacking in this one, but none can outrank it in sheer performance and attention to the small details of human engineering that make it such a satisfactory product.

CIRCLE NO. 67 ON FREE INFORMATION CARD

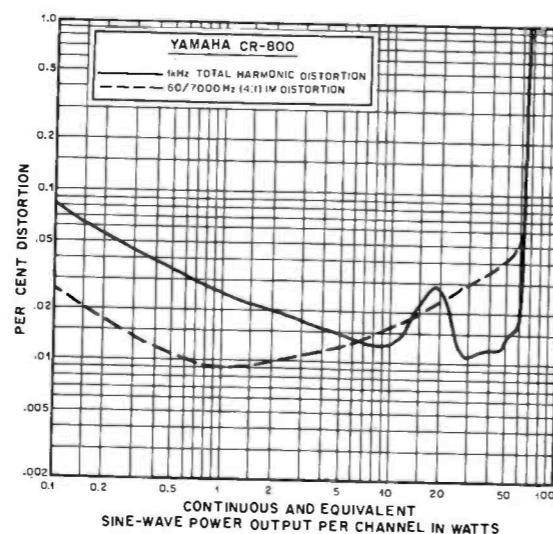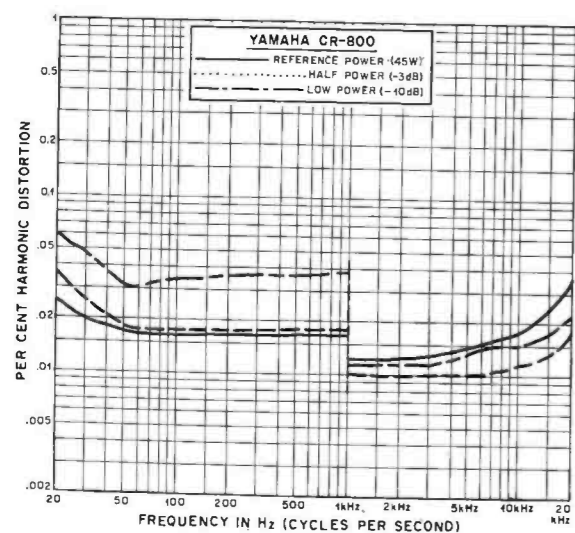

ELECTRA BEARCAT 101 "DIGITAL" SCANNING MONITOR

Vhf-uhf scanner programs 6000 frequencies without plug-in crystals.



THE Bearcat 101 from Electra offers something new in the way of a scanning FM monitor receiver. Highly advanced, it contains the latest

in modern technology, including a computer-type digital frequency-synthesis system that eliminates the need for plug-in crystals. The receiver

provides scanning of 16 frequencies in the 30-to-50-MHz low-vhf, 148-to-174-MHz high-vhf, 416-to-450-MHz uhf, and 470-to-512-MHz T uhf Public Safety bands. Included in the coverage is the 146-to-148-MHz segment of the 2-meter Amateur radio band.

Any 16 out of more than 15,000 possible frequencies in these bands can be set up in any order or band combinations or be changed by the user simply by programming them from the front panel.

In operation, the appropriate r-f circuits for each band are automatically switched in and tuned for each frequency. This ensures peak performance over the entire range of each

Introducing ...the world's lowest cost computer system

JOLT™

JOLT™ is the new, fully-tested microcomputer with the exclusive on-board DEMON™ debug monitor. You can build it, plug it in and talk to it in three hours or less . . . for a price of just \$249!

The basic JOLT™ card includes an 8-bit MOS Technology Model 6502 CPU, which requires no clock, can directly address 65k of memory, has two index registers, 58 instructions with 11 addressing modes, two interrupts and includes both single step and address halt capability. And that's only a part of it.

JOLT's™ CPU card is available IMMEDIATELY* in either kit form or assembled (\$249 for the kit in single quantity and \$348 assembled). Either way, the JOLT™ CPU is completely tested prior to delivery. It comes complete with a terminal interface (TTY or EIA) and a unique software DEbugger/MONitor called DEMON™, for which full documentation is provided. It is very easy to program, and any JOLT™ delivery includes an easy-to-follow assembly instruction manual, showing you exactly how to put everything together . . . correctly. Complete assembly should take you no more than three hours if you choose the CPU in kit form. Besides the JOLT™ CPU — the 6502 from MOS Technology — the basic JOLT™ card has a fully static memory accommodating 512 bytes of the user RAM. The JOLT™ CPU memory also has 64 bytes of interrupt vector RAM. ROM Program memory on the basic card consists of 1k bytes of monitor/debugger with an automatic Power-On bootstrap program — so you can start talking to JOLT™ and it to you as soon as you plug it in to your terminal. On-board Input/Output devices on the JOLT™ CPU card include TTY 20 milliamp current loop and an EIA interface, both full duplex. The card has high speed reader interface lines and 16 fully programmable user I/O lines with full TTL drive.

Nobody, but nobody, except MAI can offer you an on-board debugger/monitor like DEMON™. It's fully documented, too.

The exclusive DEMON™ Debug Monitor really makes JOLT™ one of the most outstanding computer systems offered at any time, at any price. Even without DEMON™ and its superior software features, JOLT™ is the lowest cost computer system in existence. And DEMON™ is a bonus you'll have to use to believe. First, it self-adapts


to any terminal speed from 10-30 CPS. With it, you can display and alter your CPU register and memory locations, plus you can read, write and punch Hex formatted data . . . with Write/Punch BNPF format data for PROM programmers. It has unlimited breakpoint capability along with separate non-maskable interrupt entry and identification. External device interrupts can be directed to any location you choose, or they can be defaulted to DEMON™ recognition. DEMON™ also gives you (1) a completely protected ROM resident debug/monitor; (2) the capability to begin execution at any location in memory; (3) the capability to bypass DEMON™ entirely to permit full control by you over your system; (4) a high-speed 8-bit parallel input option; and (5) it includes user callable DEMON™ I/O subroutines. MOST IMPORTANT, DEMON™ IS INCLUDED AS STANDARD WITH ANY JOLT™ CPU KIT OR ASSEMBLED BOARD!

Obviously, the JOLT™ basic card is a computer in and of itself. But you can add significantly to its capacity and versatility by adding 4k RAM JOLT™ memories — in one card or a whole bunch. A RAM card kit is only \$265 (\$320 assembled). Now.

The JOLT™ memory card is a fully static 4,096-bit Random Access Memory (RAM) with 1 microsecond access time and on-board decoding. It is also available now.*

And the quantity of one price is what you might expect to pay in quantities of 100 . . . very inexpensive!

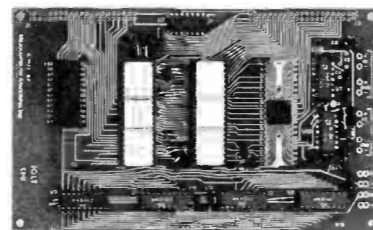There's also a JOLT™ I/O card for you, our Peripheral Interface Adapter. You can't beat the price — single kit 96 bucks — or the function.




Pictured above is the assembled JOLT™ CPU card with DEMON™. Just plug it in and you're ready to go.

The JOLT™ PIA (Peripheral Interface Adapter) I/O card includes two PIA LSI chips, 32 input/output lines, two interrupt lines, on-board decoding and standard TTL drive. It is also fully programmable and available IMMEDIATELY* in either kit or assembled form . . . at a very attractive single unit price (\$140 assembled).

Considering the function and capacity of the JOLT™ Power Supply Card, you probably think the quantity of one price — \$145 — is a misprint. It isn't.

The JOLT™ family also includes a power supply card, which operates at any of

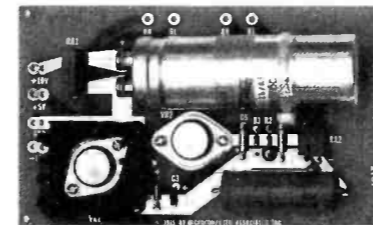three voltages — +5, +12 and -10. The power supply supports the basic JOLT™ CPU card, plus 4,096 bytes of RAM and I/O. The only two words for the price are "dirt cheap." It is available for delivery immediately with a single unit kit price of \$145 (\$190 assembled).



The assembled power supply card shown above powers the JOLT™ CPU, I/O, and RAM Memory cards.

You can also choose a blank JOLT™ universal card. Or several.

The JOLT™ Universal card is completely nude. It's a blank you can use any way you wish, for control panels, T.V. interfaces, keyboards, LED's, or any other interface logic, because the card's holes are drilled to accept 14, 16, 24, or 40 pin sockets and has the same form factor as the other JOLT™ cards. The single unit price is just \$25.

If you think you need extra cables, wires and the like, choose a Super Value JOLT™ Accessory Bag. A \$55 Value for just \$40.

The JOLT™ Accessory Bag includes 25 separate parts, enough hardware to connect one JOLT™ card to another. Order an Accessory Bag for each additional JOLT™ card. The Bag contains such necessary items as flat cable, connectors, cord spacers, hardware, wire, etc.

THE JOLT PLAIN ENGLISH WARRANTY

All components in the JOLT™ family are new and fully tested prior to shipment. Kit components are fully warranted during the first 60 days of ownership. Assembled parts are fully warranted during the first 6 months of ownership. If your properly assembled kit does not work, just ship your order back to Microcomputer Associates Inc. and we'll repair, replace, or refund your money.

20% BONUS

NOW! Special ONE TIME BONUS DISCOUNT. Order one CPU before November 10, 1975 and deduct 20% off of all additional cards and accessories. (Note: Discount does not apply to CPU cards, assembled or unassembled.)

We told you JOLT™ was the world's lowest priced computer system. These prices prove it.

JOLT KITS (ALL PAYMENTS MUST BE IN U.S. DOLLARS)	QUANTITY PRICING				
	1-4	5-19	20-49	50-99	100 up
	JOLT™ CPU	\$249	\$235	\$230	\$225
JOLT™ RAM	265	255	250	245	235
JOLT™ I/O	96	90	88	82	75
JOLT™ POWER SUPPLY	145	135	130	128	115
JOLT™ UNIVERSAL CARD	25	20	18	16	14
JOLT™ ACCESSORY BAG	40	36	34	32	30

JOLT™ ASSEMBLED PRICES (ALL PAYMENTS MUST BE IN U.S. DOLLARS)	QUANTITY PRICING				
	1-4	5-19	20-49	50-99	100 up
	JOLT™ CPU	\$348	\$325	\$320	\$315
JOLT™ RAM	320	305	300	295	280
JOLT™ I/O	140	125	120	115	105
JOLT™ POWER SUPPLY	190	175	170	165	150

ALL JOLT™ KITS ARE DELIVERED COMPLETE WITH A DETAILED AND ILLUSTRATED ASSEMBLY MANUAL

* Order will be shipped within 15 days.

THE NEW JOLT™ FROM MAI IS AVAILABLE ONLY ON A DIRECT BASIS. USE THIS COUPON TODAY TO ORDER FROM



Microcomputer Associates Inc.
111 Main St., Department B
Los Altos, Calif. 94022
Phone (415) 941-1977

©1975 Pehaco Corporation

This coupon will bring you a JOLT™! Complete and return it.

Here is my check, money order or credit card payment for the following JOLT™ products. If a U.S. or Canadian order, please add \$4.86 for shipping, handling and insurance. (Orders to all other countries are priced F.O.B. Los Altos and will be shipped FREIGHT COLLECT.)

Send me immediately:

QUANTITY	PRODUCT	PRICE
_____	JOLT™ CPU KIT	\$ _____
_____	JOLT™ RAM MEMORY KIT	_____
_____	JOLT™ I/O KIT	_____
_____	JOLT™ POWER SUPPLY KIT	_____
_____	JOLT™ UNIVERSAL CARD	_____
_____	JOLT™ ACCESSORY BAG	_____
_____	JOLT™ CPU ASSEMBLED	_____
_____	JOLT™ RAM MEMORY ASSEMBLED	_____
_____	JOLT™ I/O ASSEMBLED	_____
_____	JOLT™ POWER SUPPLY ASSEMBLED	_____
TOTAL		\$ _____
+U.S./CANADA SHIPPING/HANDLING/INSURANCE		4.86
NOTE: CALIFORNIA RESIDENTS, +6% SALES TAX		
TOTAL REMITTANCE (U.S. DOLLARS ONLY)		\$ _____

MAIL Pehaco Corporation, JOLT™ Sales Agents
YOUR Microcomputer Associates Inc. Dept. B
ORDER 111 Main St., Los Altos, Ca 94022
TO: All orders subject to the prior approval of the manufacturer.

20%
BONUS

NOW! Special ONE TIME BONUS DISCOUNT. Order one CPU before November 10, 1975 and deduct 20% off of all additional cards and accessories. (Note: Discount does not apply to CPU cards, assembled or unassembled.)

20%
BONUS

PLEASE CHARGE THE TOTAL TO MY CREDIT CARD:
BANKAMERICARD # _____
MASTER CHARGE # _____ (include 4-digit #)
My credit card expires on _____
SIGNATURE _____
(All credit card orders must be signed!)

I UNDERSTAND THAT ALL U.S. ORDERS WILL BE SHIPPED VIA U.P.S. AND ALL INTERNATIONAL ORDERS WILL BE SHIPPED BY AIR. SEND MY ORDER TO:

NAME _____
ADDRESS _____
ORGANIZATION _____
CITY _____ STATE _____ ZIP _____
PHONE _____ (Include Area Code)

*Make your check payable to: Microcomputer Associates Inc.
International Orders: Payment should be cabled to Account #00417-06355 Bank of America, 215 So. Murphy Avenue, Sunnyvale, California, USA, 94086

band (there are no restrictions as to the band-coverage limits). Each channel can also be set up for automatically providing a one-second rescan delay or no delay at all at a particular channel.

Among the customary features to be found are LED channel indicators, manual/automatic scanning, channel-disable switches, adjustable squelch, volume control, front-facing speaker, telescoping whip antenna, jacks for external antenna and speaker, and terminals for connecting an accessory. A kit consisting of a power converter and mounting hardware is available for mobile installations. Operated from a 117-volt ac line, the receiver draws 30 watts of power.

The receiver measures 9" W x 7 1/4" D x 3 5/8" H (23 x 18 x 9 cm) and weighs 6 1/4 pounds (3.8 kg). Suggested retail price is \$349.95

Technical Details. The receiver employs a single-conversion design, to a 10.8-MHz i-f. Selectivity is provided by a six-pole monolithic crystal filter. High sensitivity, low noise, and good signal-handling capabilities are obtained by use of dual-gate

MOSFET's in the r-f and mixer stages for the vhf bands. Uhf-band operation is optimized by a separate r-f and mixer system that uses bipolar transistors. IC's are used in the i-f, detector, and a-f (including the output) stages.

Each band to which the receiver can be tuned has its own separate r-f circuit. The circuits are automatically selected according to the frequency for which the working channel is set. Tuning to each frequency is accomplished by variable-capacitance diodes that are controlled by the programmed information set up for each channel. Hence, the sensitivity/gain characteristics are uniform over the entire range for which the receiver can be set.

Our measurements, conducted with 50 ohms across the antenna input terminals, indicated 20 dB of quieting with a 0.35-to-0.4- μ V input signal and a usable sensitivity of about 0.25 μ V on the lower bands. The sensitivity dropped off somewhat on the uhf bands.

The maximum extension of the telescopic whip antenna was 22 1/2" (57.2 cm). This is quite short for the 30-to-50-MHz band. However, the efficiency is raised by an antenna-loading inductor that is automatically switched in when this range is used.

Frequency Synthesizer. Custom-designed MOS and TTL IC's are used for scanning at a rate of about 20 channels per second for the frequency-synthesis system. The synthesizer employs the method in which a standard reference signal is derived from a crystal-controlled master oscillator or clock. The local oscillator signal at the receiver's mixer is obtained from a voltage-controlled oscillator (vco).

A vco comparison signal, obtained via a programmable counter-type divider system, is compared against the standard reference in a phase discriminator. Any discrepancy detected creates an error voltage that shifts the vco frequency to the point where these two signals are locked in phase with each other. This results in the proper vco frequency according to the division ratio programmed for the desired channel.

The logic for the switch positions is programmed through a special "non-volatile" memory system that retains the information even after power is removed from the receiver. Therefore, no reprogramming is ever necessary,

unless channel frequencies are to be changed.

User Comment. The receiver is initially programmed at the factory for 16 national frequencies. Reprogramming from a choice of 6000 other assigned Public Safety frequencies is easily accomplished by referring to the manual provided with the receiver. Tables in the manual indicate the required operations for each frequency.

The reprogramming procedure is as follows: You push a READY switch, set all channel switches to their down positions, and operate the MANUAL switch to step the LED indicators to the channel number to be programmed. Then, you push up certain channel switches as indicated in the tables for the desired frequency. (The one-second rescan delay for any particular channel can also be programmed at this time.) Following this, you momentarily depress an ENTER momentary-contact switch. Then, by pressing the READY switch to its up position, and placing the channel switches up for only those channels you want to scan, the receiver is programmed to selectively scan.

Manual or automatic scanning is selected and controlled by a separate lever switch. With manual scanning, any one channel can be kept open until scanning is resumed. There is no priority channel.

The two-meter Amateur frequencies are listed in the manual's tables in multiples of 10 kHz. However, the receiver's selectivity was broad enough to allow reception of local repeaters operating at odd multiples of 5 kHz with the scanner set to the nearest 10 kHz multiple.

Our measured selectivity indicated a 10-kHz adjacent-channel rejection of approximately 40 dB. Operationally, with the 148-to-174-MHz assigned channels at 15-kHz multiples, adjacent-channel interference from our local police transmitter (located some 2 1/2 blocks away) produced only a slight buzzing with low-level audio distortion. It was apparent that no significant problems should be expected in this regard.

Best signal efficiency is obtained from the use of an external outdoor antenna, such as a dipole or ground plane designed for the particular frequency band you plan to use. However, we obtained good readability using only the whip antenna supplied with the receiver at our third-floor in-

door location from signals originating 40 or so miles away.

The output power from the audio section measured 2.5 watts into 8 ohms, with 3% distortion from a 1000-Hz sine-wave signal. At 3 watts

output, the distortion rose to 10%, and the waveform exhibited slight clipping. Audio intelligibility from the front-facing speaker was good to excellent.

CIRCLE NO. 68 ON FREE INFORMATION CARD

LECTROTECH MODEL BG-10 COLOR GENERATOR

Battery-powered, miniature generator for field servicing.

FIELD-SERVICE test equipment has come a long way in less than five years. Test gear that once had to be left back at the shop because of its bulk and weight can now be conveniently carried to a field job. A case in point is the color bar/dot generator used in color TV receiver servicing. Older generators were large and heavy and tied to the ac line. Lugging them along on a call was like lugging around an extra tube caddy. Fortunately, that situation has changed for the better.

Lectrotech, Inc., is currently marketing a Model BG-10 color generator that should make every color TV serviceman jump for joy. Measuring a compact 5 1/2" L x 3" W x 1 1/4" D (14 x 7.6 x 3.2 cm), it is hardly larger than many portable calculators. In fact, it comes in a zipper-type soft vinyl carrying case that resembles many calculator cases.

The color generator is completely independent of ac line operation, using only a pair of 9-volt batteries. The generator's circuit employs low-current-drain CMOS digital IC technology to yield the maximum battery life possible.

The retail price of the generator is \$89.50

Technical Details. The color generator is extremely simple to operate. There are only three switches that need concern the user. One two-position switch selects the row in which a desired pattern is located, while a three-position switch is used to zero in on the desired pattern. The front cover is silk-screened with the six patterns available, which are keyed to the switches with heavy black lines. The patterns available include: single dot, three color bars, single vertical/horizontal lines, full-screen dots, full-screen crosshatch, and 10 color bars.

The third switch is labelled COLOR ON/OFF. This switch must be set to ON whenever the three- or 10-bar pattern is selected and to OFF for any other pattern.

There isn't even a power switch per se. To apply power, a mechanical locking mechanism at one end of the generator's case must be squeezed, while the bottom of the case is being slid out, at which time power automatically comes on. (A plastic "cam" on the upper half of the case passes over a leaf switch when the case is opened, closing the contacts. When the case is shut, the cam disengages and opens the contacts.) When power is on, a LED on the control panel comes on. The locking mechanism prevents the case from accidentally opening and running down the batteries, while a mechanical stop prevents the bottom half of the case from sliding all the way out.

The test leads for the generator are permanently built in. They neatly fold away to fit into a small well in the instrument's case. Since it is necessary to open the case to get at the test leads, power comes on automatically and the instrument is ready to use.

The r-f oscillator in the instrument is factory tuned to TV Channel 4. It can, however, be adjusted with a hex tuning wand to provide an r-f output on either TV Channel 3 or 5 if preferred. Access to the tuning slug is provided through two holes in the side of the case that line up when the instrument is on.

User Comment. This miniature color generator can do virtually everything the full-sized instruments can do. The major advantage to the serviceman is not so much that it performs like an "in-shop" color generator of five years ago, but that it is small enough to be tucked into a tube caddy without taking up vital space for other supplies and tools.

We used it on a number of service calls and can honestly report that it was a great convenience in terms of getting it to the job and its performance on the job. The fact that this is a battery-powered instrument was greatly appreciated, since an ac outlet is often not available.

CIRCLE NO. 69 ON FREE INFORMATION CARD

FREE EICO CATALOG

346 Ways To Save On Instruments, Burglar Alarms, Automotive & Hobby Electronics!

The more you know about electronics, the more you'll appreciate EICO. We have a wide range of products for you to choose from, each designed to provide you with the most pleasure and quality performance for your money. The fact that more than 3 million EICO products are in use attests to their quality and performance.

"Build-it-Yourself" and save up to 50% with our famous electronic kits.

For latest EICO Catalog on Test Instruments, Automotive and Hobby Electronics, Eicocraft Project kits, Burglar-Fire Alarm Systems and name of nearest EICO Distributor, check reader service card or send 50¢ for fast first class mail service.

EICO—283 Malta Street, Brooklyn, N.Y. 11207

Leadership in creative electronics since 1945.



CIRCLE NO. 28 ON FREE INFORMATION CARD

THE DYNAMIC DUO!



Pygmy Portable Amplifier \$39.95

GNOME micro-Synthesizer \$48.95

If you're into electronic music, PAIA's Pygmy Portable Amp and GNOME Micro-Synthesizer are a pair that's hard to beat. And now we offer them together, as a package, at a price that can't be beat — \$84.50 plus 10 lbs shipping — catalog #3741.

DEMO LINE—Use Ma Bell's low night rates to get a one minute demo of PAIA Synthesizers. Our recording equipment also takes catalog requests, charge orders, etc. (405) 843-7396.

— FREE CATALOG —

PAIA ELECTRONICS, INC. Dept. 11-P 1020 W. Wilshire Blvd. Oklahoma City, OK 73116

CIRCLE NO. 56 ON FREE INFORMATION CARD

Communications Engineering


Aeronautical & Navigational

Television Engineering



Computer Engineering

Automatic Control Engineering

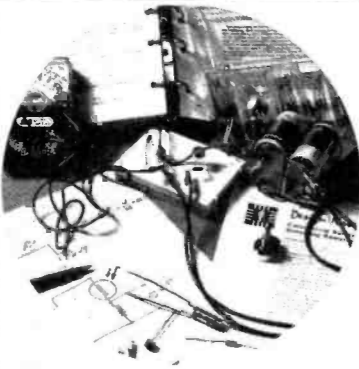

Missile & Spacecraft Guidance


Only CREI offers you a choice of 18 programs in advanced electronics

If you are too busy to go to college to learn advanced electronics, CREI brings college level training to you. CREI programs give you practical engineering training that you can apply in your work to move ahead to higher paying jobs. And CREI lets you specialize in exactly the area of electronics you want. You have a choice, depending on your qualifications, of 18 different programs.

Not only are CREI programs college-level but arrangements are available for you to earn college credit applicable to advanced degrees.

Radar & Sonar Engineering

Digital Communications

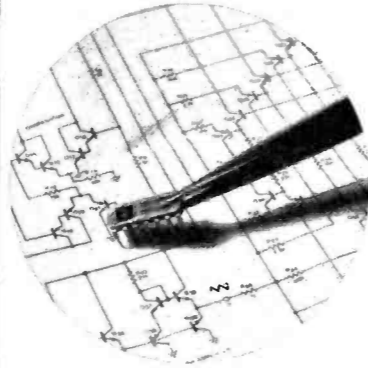

Industrial Electronics


Electronic Systems Engineering

For over 45 years CREI programs have been recognized by leading technical organizations as effective home study training in advanced electronics.


NEW OPTIONAL LAB PROGRAM



CREI now offers a supplementary ELECTRONIC DESIGN LABORATORY PROGRAM to make learning advanced electronics easier and to give you actual experience to use in your work. Only CREI offers this complete college type laboratory program. You learn to actually design electronic circuits. At the same time you get extensive experience in tests and measurements, breadboarding, prototype building and other areas important to your career.

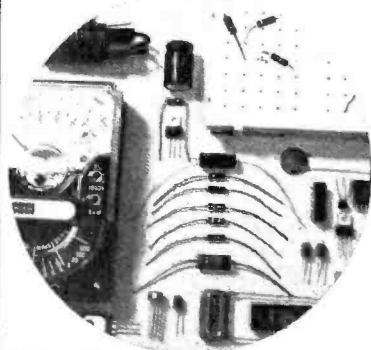

Microwave Engineering

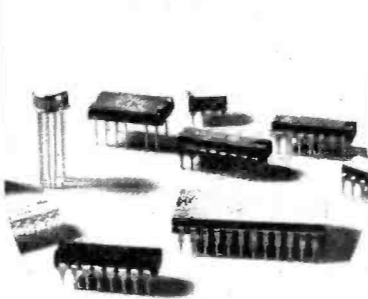

Satellite Communications

Mail This Card for free CREI CATALOG

80 page, full color book describes over 16 college-level electronics engineering programs. (For high school grads or equivalent only.) Check area of interest:

- Communications
- Computers
- Microwave
- Broadcast TV
- Cable TV
- Other

Name _____
 Address _____
 City _____ State _____ ZIP _____
 Phone _____ Age _____
 Employed by _____

Type of Present Work _____
 If you have previous training in electronics, check here
 For GI Bill Information, check here

Accredited Member National Home Study Council

CREI CAPITOL RADIO ENGINEERING INSTITUTE 2
 McGraw-Hill Continuing Education Center
 Washington, D. C. 20016
 E1211F Popular Electronics

Mail This Card for free CREI CATALOG

80 page, full color book describes over 16 college-level electronics engineering programs. (For high school grads or equivalent only.) Check area of interest:

- Communications
- Computers
- Microwave
- Broadcast TV
- Cable TV
- Other

Name _____
 Address _____
 City _____ State _____ ZIP _____
 Phone _____ Age _____
 Employed by _____

Type of Present Work _____
 If you have previous training in electronics, check here
 For GI Bill Information, check here

Accredited Member National Home Study Council

CREI CAPITOL RADIO ENGINEERING INSTITUTE 1
 McGraw-Hill Continuing Education Center
 Washington, D. C. 20016
 E1211F Popular Electronics

ment in a CREI program, you
). You should also be working
 s field.

for CREI's newly published
 advanced electronics. This full
 opportunities for you.


Home Study Council


CREI
CAPITOL
RADIO
ENGINEERING
INSTITUTE


A Division of McGraw-Hill
 Continuing Education Co.
 3939 Wisconsin Avenue,
 Washington, D. C. 20016


If you are too busy to go to college to learn advanced electronics, CREI brings college level training to you. CREI programs give you practical engineering training that you can apply in your work to move ahead to higher paying jobs. And CREI lets you specialize in exactly the area of electronics you want. You have a choice, depending on your qualifications, of 18 different programs.

Not only are CREI programs college-level but arrangements are available for you to earn college credit applicable to advanced degrees.

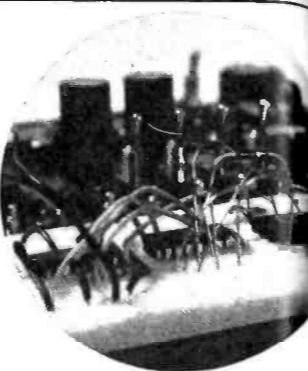Communications Engineering	Aeronautical & Navigational	Television Engineering		Computer Engineering
----------------------------	-----------------------------	------------------------	--	----------------------

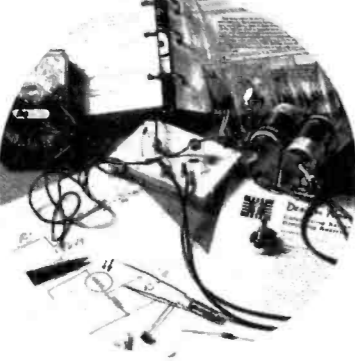Automatic Control Engineering		Missile & Spacecraft Guidance	<h1>Only CREI offers you a choice of 18 programs in advanced electronics</h1>	
-------------------------------	---	-------------------------------	---	--

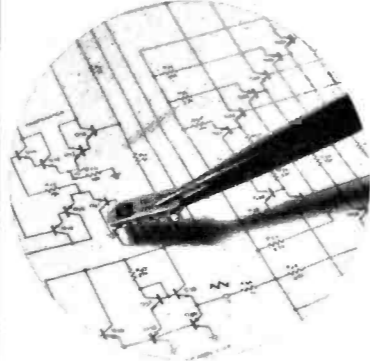Radar & Sonar Engineering	Digital Communications		Industrial Electronics	Electronic Systems Engineering
---------------------------	------------------------	---	------------------------	--------------------------------

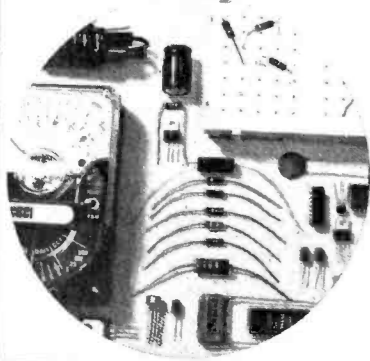	<h1>Nuclear Engineering Technology</h1>			
--	---	--	--	--

Cable Television Engineering	<h1>Special Programs for Non Electronic Engineers</h1>			
------------------------------	--	--	--	--

Only CREI offers you a choice of 18 programs in advanced electronics

For over 45 years CREI programs have been recognized by leading technical organizations as effective home study training in advanced electronics.

NEW OPTIONAL LAB PROGRAM



CREI now offers a supplementary ELECTRONIC DESIGN LABORATORY PROGRAM to make learning advanced electronics easier and to give you actual experience to use in your work. Only CREI offers this complete college type laboratory program. You learn to actually design electronic circuits. At the same time you get extensive experience in tests and measurements, breadboarding, prototype building and other areas important to your career.

Qualifications to Enroll. To qualify for enrollment in a CREI program, you must be a high school graduate (or equivalent). You should also be working in electronics or have previous training in this field.

Send for FREE book. If you are qualified, send for CREI's newly published book describing your career opportunities in advanced electronics. This full color book is filled with facts about career opportunities for you.



Accredited Member, National Home Study Council

CREI, Dept. E1211F
3939 Wisconsin Avenue
Washington, D. C. 20016

Rush me your FREE book describing my opportunities in advanced electronics. I am a high school graduate.

Name _____ Age _____
 Address _____
 City _____ State _____ ZIP _____
 If you have previous training in electronics, check here
 Employed by _____
 Type of Present Work _____
 Veterans and servicemen, check here for G. I. Bill information

CREI
CAPITOL
RADIO
ENGINEERING
INSTITUTE

A Division of McGraw-Hill
 Continuing Education Co.
 3939 Wisconsin Avenue,
 Washington, D. C. 20016


Postage will be paid by
CREI CAPITOL
 RADIO ENGINEERING
 INSTITUTE
 McGraw-Hill Continuing Education Center
 3939 Wisconsin Avenue
 Washington, D. C. 20016

Postage will be paid by
CREI CAPITOL
 RADIO ENGINEERING
 INSTITUTE
 McGraw-Hill Continuing Education Center
 3939 Wisconsin Avenue
 Washington, D. C. 20016

Postage will be paid by
CREI CAPITOL
 RADIO ENGINEERING
 INSTITUTE
 McGraw-Hill Continuing Education Center
 3939 Wisconsin Avenue
 Washington, D. C. 20016

FIRST CLASS
 Permit No. 20-R
 Washington, D. C.

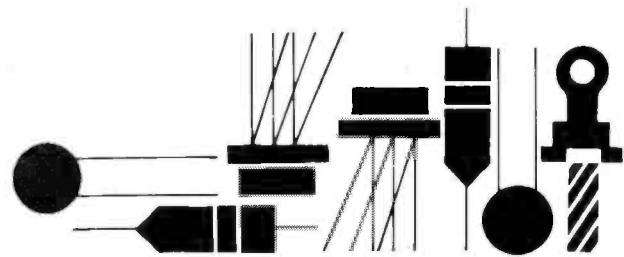FIRST CLASS
 Permit No. 20-R
 Washington, D. C.



Solid State

By Lou Garner

CALCULATOR CHIPS FOR OTHER CIRCUITS

UBIQUITOUS, innocuous and relatively inexpensive, calculator IC's (popularly called "chips" by engineers) are suitable only for the assembly of pocket and desk calculators. Right?

Wrong! More and more circuit designers are using these devices in noncalculator applications and, unlikely as it may seem, one day they may be used almost as extensively in other type of equipment as they are in calculators today. Some calculator chips have such powerful capabilities, in fact, that a number of original equipment manufacturers are considering their use in specialized instrument and control systems in place of minicomputer subsystems and expensive microprocessors. One industry executive has predicted that by 1977 not less than 20% of the total calculator chips manufactured will be used in commercial equipment and systems rather than in conventional calculators.

Calculator chips can be used to assemble computers; specialized types of watches and clocks; laboratory, industrial and service test equipment; medical instruments; process monitors; communications equipment; surveillance and security systems; and automotive, appliance and industrial controls. Under development and scheduled for early release (if not on the market by the time this appears in print) is a miniature combination calculator wristwatch.

Typical of one class of noncalculator applications, an easily duplicated counter circuit featuring a calculator IC is given in Fig. 1. Abstracted from *Calculator Chip Makes A Counter* (application note AN-112) published by the National Semiconductor Corporation (2900 Semiconductor Drive, Santa Clara, CA 95051), this is the simplest of seven circuits featured in the 6-page publication. The other circuits include a higher speed counter, an "up-down" counter and a combination counter/calculator.

Suitable for either pc or perf board assembly, the counter circuit requires only a type MM5736 calculator IC, a type DM75492 digit driver, a type NSA1166 six-digit LED display, three spst switches, and a 6.5-to-9.5-volt dc power source, such as a standard 9-volt transistor battery. Capable of handling counts of up to 999,999, the circuit's average maximum counting rate is approximately 60 Hz, but the actual maximum rate may range from as low as 40 Hz to as high as 150 Hz due to IC chip tolerances. It can be actuated by a pushbutton, mat, or reed switch, by magnetic relays, by a microswitch, or by any of a number of contact arrangements. Therefore, it is suitable for a wide variety of practical applications. Depending on the type of count control switch (S3), the counter can be used, typically, for inventory control, production line counting, recording game scores, or for counting the number of customers entering or leaving a store or business office.

The counting function is achieved simply by using the calculator chip to add "1" repeatedly. This is accomplished by interconnecting the chip's terminals (K3 and D4) which initiate the "addition" step through an external COUNT switch, S3. In practice, the operator first clears the circuit by depressing CLEAR switch S1, then enters "1" into the count by closing the START switch, S2. From this point, each closure of the COUNT switch causes "1" to be added to the total count up to the display's maximum capability.

By definition, a computer is a device or system capable of solving problems by accepting and retaining data, performing prescribed operations on that data, and supplying and/or storing the results of those operations. If the capability of accepting and retaining a planned program of operations is added to a calculator chip, then, in effect, the calculator/programmer combination becomes a basic computer.

Not too long ago, a programmable calculator required


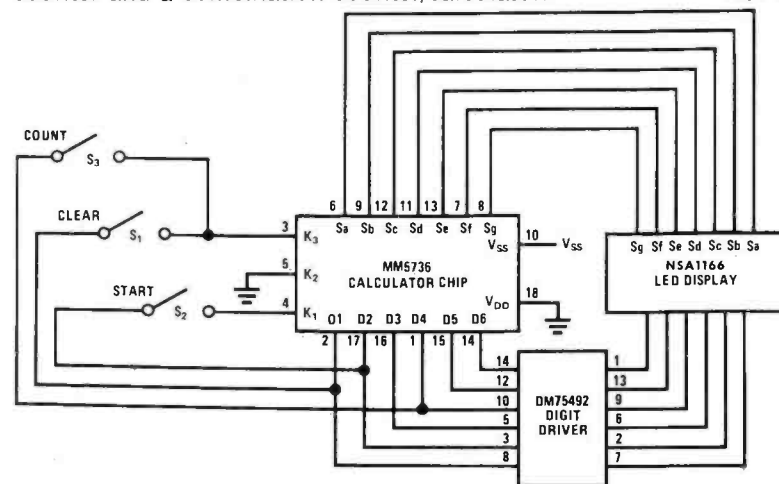


Fig. 1. In this six-decade counter circuit (from a National Semiconductor Application Note), a calculator IC and a digit driver control an LED readout. Depending on the type of counting switch used, the circuit has many different applications.

SWTPC 6800

The Computer System You Have Been Waiting For

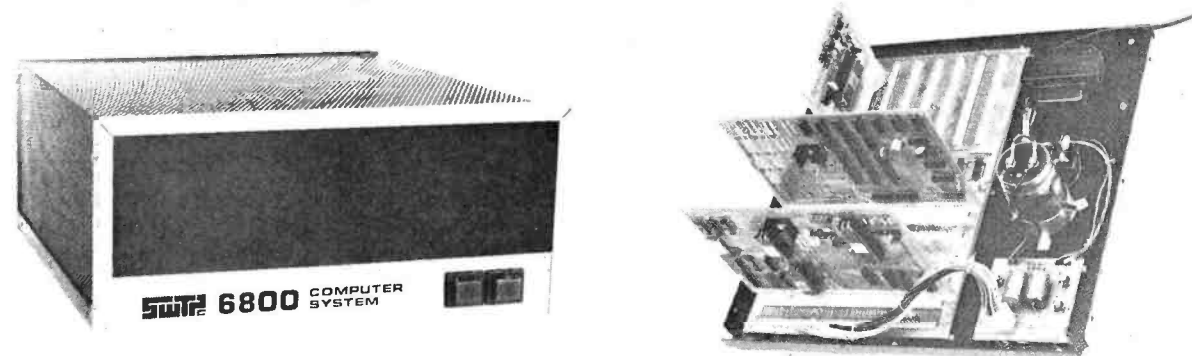A BENCHMARK SYSTEM—Using the MOTOROLA M6800 benchmark microprocessor family.



Southwest Technical Products is proud to introduce the M6800 computer system. This system is based upon the Motorola MC6800 microprocessor unit (MPU) and it's matching family of support devices. The 6800 system was chosen for our computer because this set of parts is currently in our opinion the "Benchmark Family" for microprocessor systems. It makes it possible for us to provide you with a computer system having outstanding versatility and ease of use.

In addition to the outstanding hardware system, the Motorola 6800 has without question the most complete set of documentation yet made available for a microprocessor system. The 714 page Applications Manual for example contains material on programming techniques, system organization, input/output techniques, and more. Also available is the Programmers Manual which details the various types of software available for the system and provides instructions for the programming and use of the unique interface system that is part of the 6800 design. The M6800 system minimizes the number of required components and support parts, provides extremely simple interfacing to external devices and has outstanding documentation.

Our kit combines the MC6800 processor with the MIKBUG[®] read-only memory (ROM). This ROM contains the program necessary to automatically place not only a loader, but also a mini-operating system into the computers memory. This makes the computer very convenient to use because it is ready for you to enter data from the terminal keyboard the minute power is turned "ON". Our kit also provides a serial control interface to connect a terminal to the system. This is not an extra cost option as in some inexpensive computers. The system is controlled from any ASCII coded terminal that you may wish to use. Our CT-1024 video terminal is a good choice. The control interface will also work with any 20 Ma. Teletype using ASCII code, such as the ASR-33, or KSR-33. The main memory in our basic kit consists of 2,048 words (BYTES) of static memory. This eliminates the need for refresh interrupts and allows the system to operate at full speed at all times. Our basic kit is supplied with processor system, which includes the MIKBUG ROM, a 128 word static scratch pad RAM, and clock oscillator bit rate divider; main memory board with 2,048 words, a serial control interface, power supply, cabinet with cover and complete assembly and operation instructions which include test programs and the Motorola Programmers Manual.

If you have a Motorola 6800 chip set, we will sell you boards, or any major part of this system as a separate item. If you would like a full description and our price list, circle the reader service number or send the coupon today. Prices for a complete basic kit begin at only \$450.00.

MAIL THIS COUPON TODAY

Enclosed is \$450.00 or Master C. # _____ Bank # _____
 or BAC # _____ Ex Date _____
 For My SWTPC Computer Kit Send data package

NAME _____
 ADDRESS _____
 CITY _____ STATE _____ ZIP _____

Southwest Technical Products Corp., Box 32040, San Antonio, Texas 78284

FREE

1975 CATALOG OF CIRCUIT DESIGN AND BREADBOARDING EQUIPMENT

Send for your free copy of Circuit Design's new 1975 catalog. In it, you'll find lots of new ideas in solderless breadboarding aids and instrumentation (in kit form or assembled), as well as a host of hard to find components. If you are involved in any aspect of electronics, you can't do without it. For your free copy, write to:

CIRCUIT DESIGN, INC.
Div. of E&L Instruments
P.O. Box 24 - Shelton, Connecticut 06484

CIRCLE NO. 21 ON FREE INFORMATION CARD

COMING UP IN THE DECEMBER

Popular Electronics®

SPECIAL FOCUS ON HI-FI:

- Build a Direct-Drive Electronic Turntable
- How Good Are New Cassette Tapes?
- What's New in Hi-Fi Electronics

PROGRAMMABLE RAM MUSIC BOX

PRODUCT TEST REPORTS:

- Pioneer AM/FM Stereo Tuner
- Tandberg Stereo Cassette Deck
- E.F. Johnson LED-Readout Mobile CB
- Fluke Frequency Counter
- Vector Wiring Pencil

several LSI chips to provide the necessary calculation, memory and programming functions, keyboard de-bounce circuits to prevent false entries, separate segment and digit drivers for the display, a multidigit display, power supply regulation circuits and, of course, a suitable keyboard. As a result, commercial programmable calculators cost as much as several hundred dollars each.

Several months ago, the National Semiconductor Corporation made it possible for equipment manufacturers to design moderately priced programmable calculators when it introduced a series of four special-function single-chip calculator IC's together with a compatible programmer chip capable of converting any of the four chips into a fully programmable "learn mode" calculator. Using these new devices, a programmable calculator can be assembled with only three IC's, a LED display, an appropriate keyboard, a dc power source, and a few small components.

National's five new IC's include the MM5760 slide-rule circuit, the MM5762 business and financial calculator, the MM5763 statistical calculator, the MM5764 international conversion calculator, and the MM5765 calculator programmer. All four calculator chips provide standard arithmetical functions. In addition, the MM5760 offers a complete set of log and trig functions, while the MM5762 provides a single-key computation of present and future value of compound interest, deposit or sinking fund amounts, payment or loan installments, and sum-of-the-digits calculations. The MM5763 includes linear correlation and regression, y-intercept, mean and standard deviation, summation of X or Y values, and related statistical functions. The MM5764 is designed to provide automatic conversions of length, volume, area, or temperature between two different measuring systems, such as British and metric. Finally, the MM5765 programmer circuit, used in conjunction with any of the calculator chips, can provide computational programs of up to 102 steps.

All of the circuits in the new series feature automatic display cutoff to conserve battery power, trailing zero suppression, power-on clear, and a low battery signal display (when used with a suitable digit driver).

Reader's Circuits. Suitable for use in electronic music synthesizers, waveform generators, operational control sequencers, and similar projects, the circuits illustrated in Figs. 2 and 3 were submitted by reader Frank J. Canova, Jr. (725 Myrtle Ave., Green Cove Springs, FL 32043). Each circuit is capable of delivering a repetitive series of different output voltage levels when triggered by a chain of

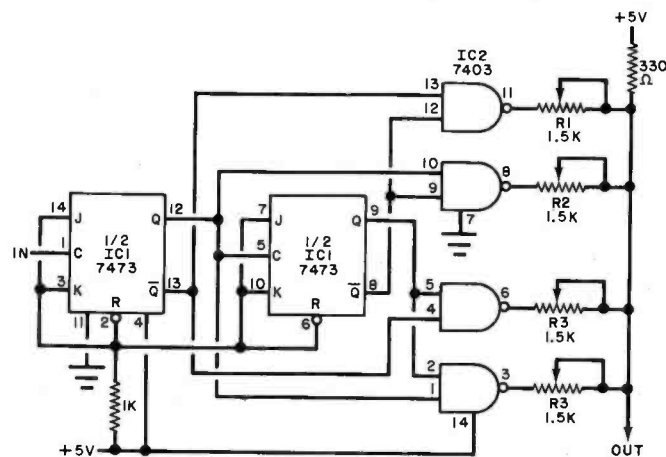


Fig. 2. Circuit provides four output voltage levels.

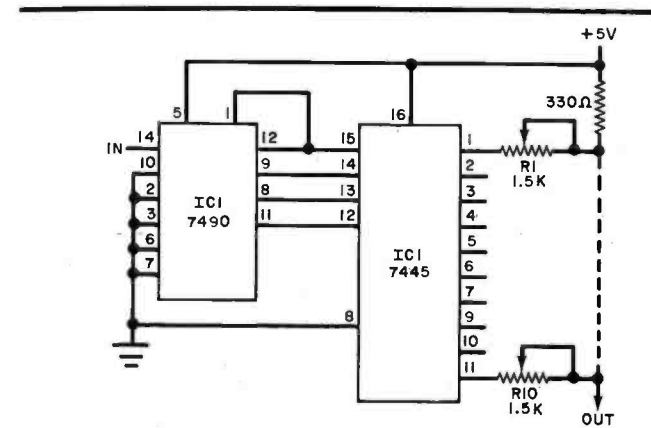


Fig. 3. Ten-step sequence or function generator.

pulse signals from a logic "clock" circuit or relaxation oscillator. Both circuits utilize readily available 7400 series digital logic IC's and both are designed for operation on standard 5-volt negative-ground dc sources.

As shown in Fig. 2, a 7473 dual J-K flip-flop, IC1, and 7403 quad 2-input positive NAND gate, IC2, are used to provide four output voltage levels in sequence when a pulse chain is applied to the circuit's input terminal. Each output voltage is preset (or programmed) by adjusting a potentiometer (R1 to R4) in series with one of the four NAND gate output terminals and the dc source voltage through a 330-ohm resistor. The flip-flops are inter-connected to form a binary counter.

The sequence starts with pins 8 and 13 of binary counter IC1 "high," driving only the top NAND gate on and shunting R1 to ground. At this point, the output voltage, established by the voltage division between the common 330-ohm resistor and R1, is somewhere between 0 and 4 volts (approximately), depending on R1's adjustment. When the first input pulse is applied, the input flip-flop changes state, with pin 12 (IC1) going "high," pin 13 "low." The top NAND gate is switched off, the second NAND gate on, and R2 is connected to ground, changing the output voltage to a level determined by R2. In a similar fashion, the next pulse causes both flip-flops to change state, with pins 13 and 9 of IC1 high and the third NAND gate switched on, all others off, and changing the output voltage to a level determined by R3. Finally, the fourth input pulse switches pin 12 (IC1) high, driving only the last NAND gate on and delivering an output voltage established by R4. The next pulse causes both flip-flops to change state and re-establishes the original conditions, starting a new cycle.

The circuit given in Fig. 3 operates in somewhat similar fashion, but utilizes a type 7490 decade counter and a type 7445 (or 74145) BCD-to-decimal decoder/driver to provide ten adjustable output levels. Again, separate potentiometers, R1 to R10, are used to establish each output voltage level.

Standard components are used in both designs. The potentiometers are 1500-ohm linear-taper types and can be either conventional knob-controlled units or screwdriver-adjusted trimmers, depending on the circuit's intended application. The fixed resistors are half-watt types. Any standard input and output connectors can be used, although shielded (coaxial) types are preferred. For optimum performance, the circuit(s) should be powered by

Particular? try this high-performance circuit-builder's Super-strip™

840 solderless plug-in tie-points
holds up to 9 14-pin DIP's

fastest, most reliable method known...to build, test and modify experimental circuits

8-bus distribution system plus universal .1" by .1" matrix of solderless, plug-in tie points all in one integral device.

Accepts all DIP's and discretes with leads up to .032" dia.

Interconnect with any solid wire up to No. 20 A.W.G.

ORDER BY PART NUMBER
923252 (nickel-silver terminals).....\$17.00
923748 (gold-plated terminals).....\$18.90

We honor M.C. and B.A.C. charges. Add sales tax on OH and CA orders. (F.O.B. Painesville on company P.O.'s.) Dealer inquiries invited

Add fees from this chart.	SHIPPING/HANDLING C.O.D.		
	Up to \$10.00	\$1.00	\$.70
	\$10.01 to \$25.00	1.50	.80
	25.01 to 50.00	2.00	.90

All products guaranteed to meet or exceed published specifications

A P PRODUCTS INCORPORATED
Box 110-H • Painesville, OH 44077 • 216/354-2101

CIRCLE NO. 3 ON FREE INFORMATION CARD

THE COMPLETE PORTABLE DVM



\$198

IT'S PORTABLE

Industry preferred L.E.D.'s offer, dependable, durable and bright displays. But brightness means high current drain. Well, we've licked the "high current drain-short battery life" problem with our patent pending "auto-off" circuit that blanks the display between measurements. Your benefit? A long useable battery life and a bright easy to read display. And it's tough enough to be a portable. Cyclocat® case and recessed controls withstand that field use. It's protected electrically, too, up to 2000V DC, for minimum downtime - maximum uptime.

IT'S COMPLETE

Most portable DVM's sacrifice on features, functions, or accuracy. But not the DVM32. It's accurate with full 3 1/2 digit readout, .5% of reading accuracy and 15 megohm input impedance. Complete functions and ranges from: 1mV to 1999V DC, 1mV to 1000V AC rms, .1 ohm to 19.99 megohm and 1uA to 1.999A, AC and DC, plus Hi and Lo power ohms. It's Fast with 2 1/2 updates a second, plus auto-polarity, decimal and overrange indication.

The DVM32... true portability with complete measuring capabilities.

DVM32 backed by SENCORE'S 100% MADE RIGHT LIFETIME GUARANTEE

SENCORE 3200 Sencore Drive, Sioux Falls, S.D. 57107
Phone: 1-605-339-0100 TWX: 910-650-0300

CIRCLE NO. 80 ON FREE INFORMATION CARD

((p))
**FULL-FEATURE
 PERSONAL 2-WAY
 RADIO**

Styled for the CB'er who is budget minded, yet wants a combination of performance, style and ruggedness for his CB Radio.



PACE CB 144 is a fully synthesized 23 channel AM transceiver offering full legal transmit power. Maximum control at your fingertips: Noise blander switch • Automatic noise limiter switch • RF gain control • PA control • Delta tune • illuminated S/RF meter • transmit indicator light • Plug-in microphone. Operates on 12V DC (+) or (-) ground. Suggested retail price \$189.95

See your distributor today.

62

((p)) **PATHCOM INC. PACE TWO-WAY RADIO PRODUCTS**

24049 S. Frampton Ave., Harbor City, Cal. 90710 Available in Canada from Superior Electronics Inc. Export (all other parts of the world): 2200 Shamus Dr., Westbury, N.Y. 11590.

CIRCLE NO. 55 ON FREE INFORMATION CARD

**Our new cartridges
 will turn your
 good record player into
 a great record player.**

Perhaps you've tried to track your records at the lowest advertised setting for your elliptical stylus. In the hopes of optimizing performance and reducing record wear. But every footstep threatens to bounce the stylus out of the groove. And big crescendos are simply fuzzy. Should you get a better player? No. Get a better stylus.

We have a sensible new approach. A stylus shape that contacts more of the groove wall, to spread tracking force over a greater vertical area. The Shibata

stylus. It safely tracks your records at up to 2 grams while maintaining response to 45,000 Hz, offering great stereo separation, and reducing record wear... even compared with an elliptical stylus at less than a gram.

Put an Audio-Technica Dual Magnet UNIVERSAL cartridge with genuine Shibata stylus in your good old record player today. It's a great combination for better sound today and tomorrow, and tomorrow.



audio-technica INNOVATION / PRECISION / INTEGRITY

AUDIO-TECHNICA U.S., INC., Dept. 115P, 33 Shiloh Ave., Fairlawn, Ohio 44131 Available in Canada from Superior Electronics, Inc.

a well-regulated 5-volt dc supply, with additional filtering provided on each circuit board to prevent possible cross-coupling. Frank recommends a 100- μ F electrolytic capacitor shunted by a 0.1- μ F plastic film or ceramic type, connected as close to the IC power terminals as is practicable.

Neither lead dress nor component layout are critical but soldering to the IC leads should be done with a 30-watt soldering pencil. Beginners may prefer to provide sockets for the IC's. Either pc or perf-board construction is satisfactory.

The completed circuit(s) can be used in any of a variety of applications, depending on the type of equipment involved and the frequency of the input drive signal, as well as upon the adjustment of the individual potentiometers determining the output voltage levels. If used with a music synthesizer, for example, the programmed output signal could serve to control vco (voltage controlled oscillator), vcf (voltage controlled filter), or gain circuits, or even a combination of these. The 10-step version (Fig. 3) is preferred for function generator applications. Here, the circuit can serve to create virtually any waveform that can be approximated by ten distinct voltage levels. As a general (but not inflexible rule) lower frequency drive signals are used in sequencer and music synthesizer applications, higher frequency signals up to the kHz and lower MHz range for waveform generation. An input drive signal of at least two volts amplitude is required for positive operation.

R & D Tidbits. While it may not be the ultimate answer to the nation's energy crisis, the semiconductor solar cell is certainly the simplest device currently available for converting sunlight into electricity. The chief limitations to its widespread use in the past have been its comparatively high cost and relatively low efficiency. However, both of these limitations may become less critical as the result of recent scientific breakthroughs, and the solar cell might well become a serious challenger in the energy race.

A new type of solar cell promising high efficiency at low cost has been developed by a research team at NASA's Jet Propulsion Laboratory in Pasadena, California. The new solar cell—dubbed AMOS, for Antireflection Coated Metal-Oxide-Semiconductor—is made from oxidized


gallium arsenide with an extremely thin, nearly transparent gold film on its surface. Some samples have demonstrated an efficiency of about 15 per cent in terrestrial sunlight, which is better than the average silicon solar cell now in standard use. Perhaps more important, the device is potentially adaptable to production using very low-cost polycrystalline film techniques, with only a modest reduction in efficiency.

Another breakthrough, also with gallium-arsenide photoelectric devices, has been made by a scientific team at Varian Associates, Palo Alto, CA. Using a concave reflector to concentrate the sunlight by a factor of 1000:1, the Varian Associates group has achieved an output of 10 watts from a solar cell measuring only 1 cm in diameter. This was made possible, in part, by gallium arsenide's ability to operate at high temperatures and high current densities beyond the reach of silicon devices. In addition, the Varian units have exhibited efficiencies as high as 23%, and Joe Feinstein, vice president of research at the firm, suggests that efficiencies as high as 35 to 40% may be possible within a few years.

In another area, scientists at Stanford University have been testing a new thick-film CMOS transducer capable of converting sound waves directly into electrical impulses which can be injected into an animal's auditory nerve system. The new transducer performs a function similar to that of the hair cells in the inner ear. Current tests are with cats' ears.

Engineers at the Bell Telephone Laboratories, Murray Hill, New Jersey, have designed and built the first solid-state TV camera that meets the resolution requirements for commercial broadcast use. The experimental camera, measuring only 2.5 x 2.5 x 6 inches, was built to demonstrate the feasibility of high resolution video-telephone systems. Its small size was made possible by the use of a solid-state charge-coupled device (CCD) as the imaging sensor. With an imaging area equivalent in size to the scanned area of a standard one-inch-diameter vacuum tube used in conventional TV cameras, the new CCD has 496 vertical interlaced scan lines and 475 horizontal picture elements and contains a quarter of a million sensing elements, representing a significant improvement in resolution over other known solid-state imaging devices.

**THE
 SOUND VAULT**

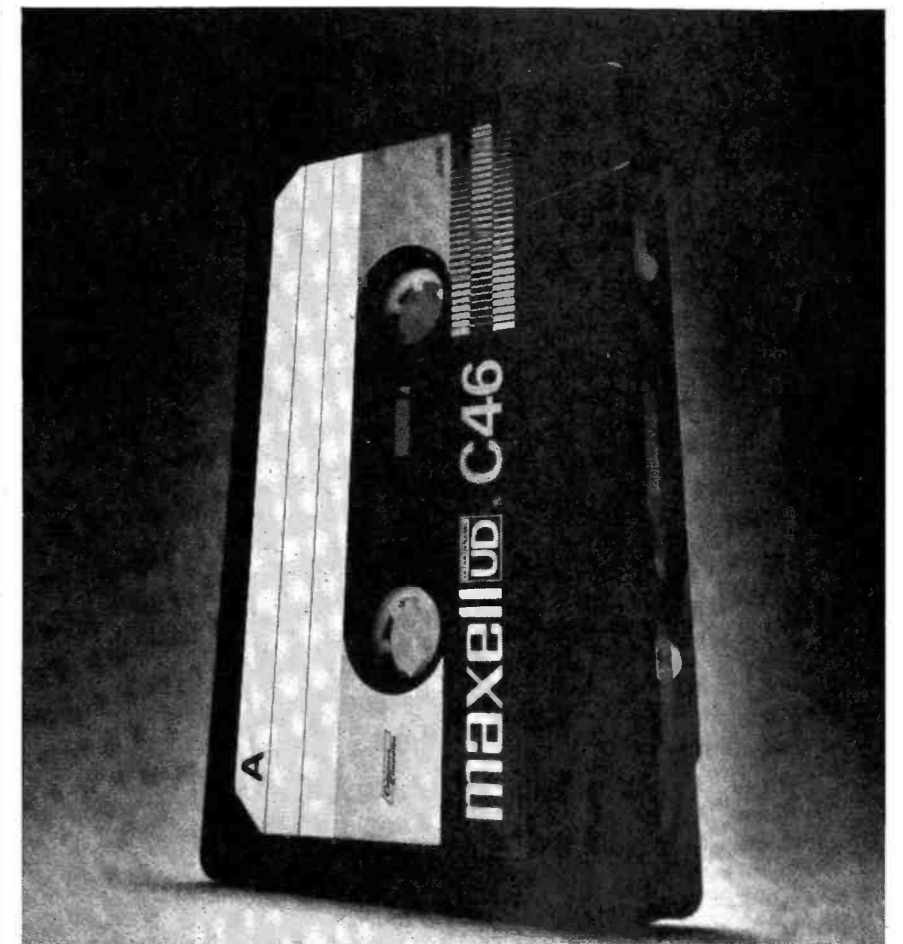

Every UD cassette gives you stainless steel guidepins to keep your recordings secure.

Tough steel pins form part of the internal security system inside every UD cassette.

They make sure your UD tape runs smooth and winds even. (Ordinary cassettes have plastic posts that can wear out and cause wow and flutter.)

These steel pins are another reason

your Ultra Dynamic cassette captures the very best sounds (both high and low) your equipment can produce.

Use Maxell Ultra Dynamic cassettes and you'll always play it safe.

Maxell Corporation of America, Moonachie, New Jersey 07074. Also available in Canada.

maxell
 For professional recordings at home.



CIRCLE NO. 50 ON FREE INFORMATION CARD

TAKE YOUR CHOICE



Mini-Scan™ is the pocket scanner that works a week on just 4 penlight cells.

A breakthrough we call "mini-miser circuitry" makes it possible ... and it's actually 2½ to 5 times more efficient than any other pocket scanner we tested! *Just 4 alkaline penlight cells power it for a full week, 8 hours a day, on a tough 50-50 duty cycle (50% full volume, 50% squelched). And its performance is bred from our experience in public safety two-way radio ... so it also gives you the crispest, clearest messages possible. Just \$119.95 with built-in ferrite antenna (batteries, crystals and optional flexible antenna extra.)

*Test results gladly supplied on request.



Johnson

MINI-SCAN™

... the professional pocket scanner

E. F. JOHNSON CO., WASECA, MINNESOTA 56093

IN CANADA: A. C. SIMMONDS & SONS, LTD.

CIRCLE NO. 42 ON FREE INFORMATION CARD

Measuring 16 x 20 mm, the image sensor is the largest single chip device ever made.

Finally, in fulfillment of another of the predictions made in last January's column, the LEAA (Federal Law Enforcement Assistance Administration) has contracted for the development of a *personal fitness monitor*—essentially a wristwatch-sized solid-state instrument that will instantly tell its wearer his pulse rate, temperature, blood pressure, and other critical information, with a built-in alarm to warn the user if his bodily signs have reached a dangerous level.

Device/Product News. In addition to its new calculator and programmer chips, discussed earlier, the National Semiconductor Corporation has recently introduced a number of other devices which should be of interest to serious experimenters, students, engineers, and hobbyists, including a new display driver, a 12-bit successive approximation register, and a new pair of line drivers.

Combining the best features of both CMOS and bipolar technologies, National's new display driver, the CD4511, incorporates a BCD decoder/driver and an integral latch on a single chip. The decoding functions and the latch are made with a CMOS process, which insures very low input current and power requirements. The output drivers, on the other hand, are constructed with a bipolar process, permitting the CD4511 to source segment currents of up to 25 mA. Logically, the device provides the functions of a 4-bit storage latch, a BCD-to-seven segment decoder, and seven high-current output drivers. Lamp test, blanking, and latch-enable inputs are provided for display testing, turning-off or brightness modulation, and storing the BCD code, respectively.

Designated type MM74C905, National's new CMOS 12-bit successive approximation register contains all of the digital control and storage necessary for building a 12-bit A/D (analog-to-digital) converter. Designed for operation over a supply range of from 3 to 15 volts, the device has a guaranteed noise margin of 1.0 volt. Provision is made for register expansion or truncation, and the circuit can function in either start/stop or continuous conversion modes, selectable by the user.


Manufactured using both CMOS and bipolar processes, National's new

line drivers, types MM88C29 and MM88C30, can operate on 3 to 15 volts, provide a noise immunity of (typically) 45% of the power supply, have an on resistance of only 20 ohms, and are capable of sourcing 80 mA (typ.). Both devices are offered in 14-pin Epoxy-B or ceramic DIP's. The MM88C30 is a dual differential line driver that also performs the dual four-input AND or the dual four-input NAND function.

An all-electronic solid-state tuning system designed primarily for TV sets has been developed by the General Instrument Corp. (New York, NY). Dubbed *Omega*, the new tuner features an MNOS nonvolatile memory, a CMOS D/A converter, and ion-implanted logic. It is approximately one quarter the size of corresponding electromechanical tuners. In operation, a metal-nitride-oxide semiconductor (MNOS) memory digitally stores all the tuning information needed for each TV channel, retaining the memory for up to 10 years, even with power removed. When the operator selects a station, information in the MNOS memory for that channel is coupled to a 14-bit CMOS D/A converter, developing a corresponding analog voltage, which can then be applied to a Varactor diode to tune in the selected station.

Two new npn power transistors, types 2N6465 and 2N6466, have been announced by RCA's Solid State Division (Box 3200, Somerville, NJ 08876). The new devices are complements of pnp types 2N6467 and 2N6468, respectively, and, as such, are useful in complementary-symmetry circuits for audio-frequency linear amplifier applications, as well as in linear modulators, servo amplifiers, and operational amplifiers. The 2N6465 is a 100-volt, 40-watt device with a dc beta of 15-150 measured at 1.5 A collector current, while the 2N6466 offers the same dissipation rating and beta range, but at 120 volts. Both types normally are supplied in hermetic JEDEC type TO-66 packages.

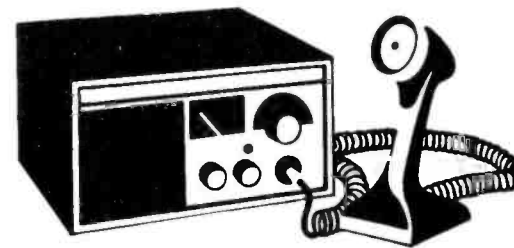Correction. In our September column, we erroneously listed a 416-page Data-book from Unitrode as being free for the asking to anyone who wishes to obtain a copy. This book is available only to Unitrode's customer list as recommended by the company's Sales and Representative Staffs. We sincerely regret any inconvenience our error has caused.



CB Scene

By Len Buckwalter, K10DH

SPEECH PROCESSING

IF YOU make the rounds at a CB coffee break or jamboree, chances are you'll hear conversations about "speech processing" and how it can improve communication intelligibility. Let's examine what it is and what it can do for you.

Voice Signals. Speech processing changes the characteristics of a voice

signal generated by a microphone. Observe that the signal shown in Fig. 1A is sharp, intermittent and non-repetitive. Moreover, there is a large difference between the average and peak values of the waveform. This is also true of the complex signal we get when the signal modulates an r-f carrier (Fig. 1B).

The desired result of the whole

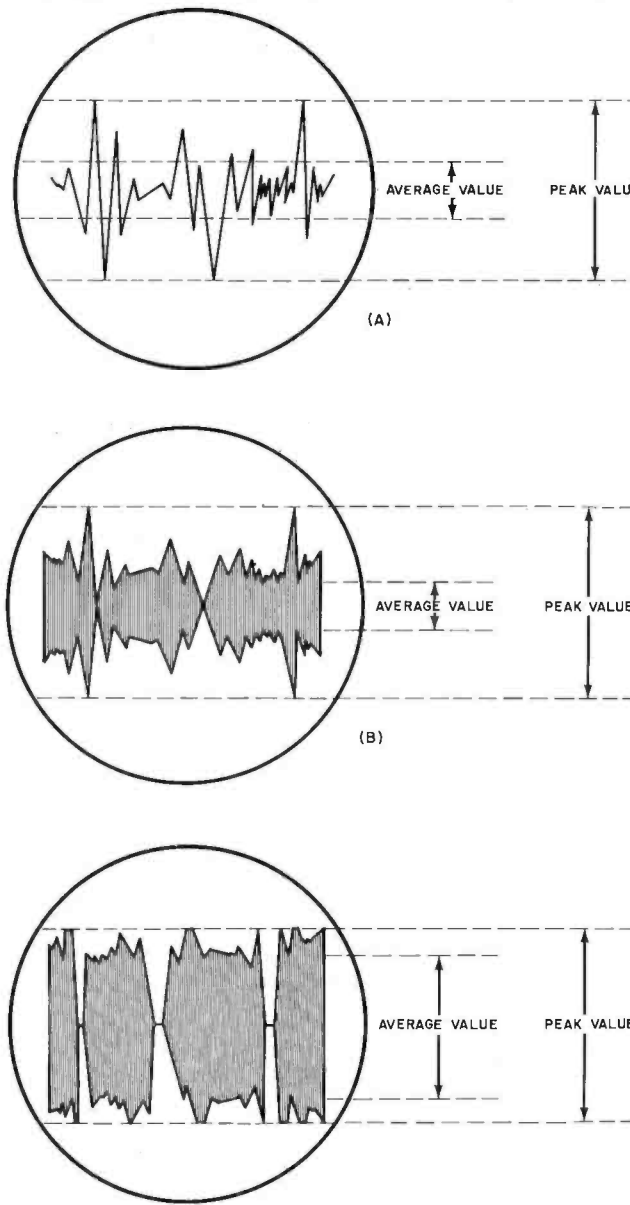


Fig. 1. At (A) is a typical voice signal. Voice peaks are high, but average level of speech is low. At (B) the signal modulates a carrier and the result has strong peaks but a low average modulation level.

Fig. 2. In over-modulated signal, mike gain increases average level of signal but peaks have been clipped.

process—intelligibility—is dependent on the average power output of the transmitter. Typically, human speech that is fully modulating the carrier on, voice peaks will only produce 30% of the peak power most of the time. Thus, the ratio of the average power to the peak power is about 1 to 3. What we end up with is a carrier that loafs along, carrying much less intelligence than it actually could.

If we could find a way of increasing this average/peak ratio, our signal would become a lot more readable.

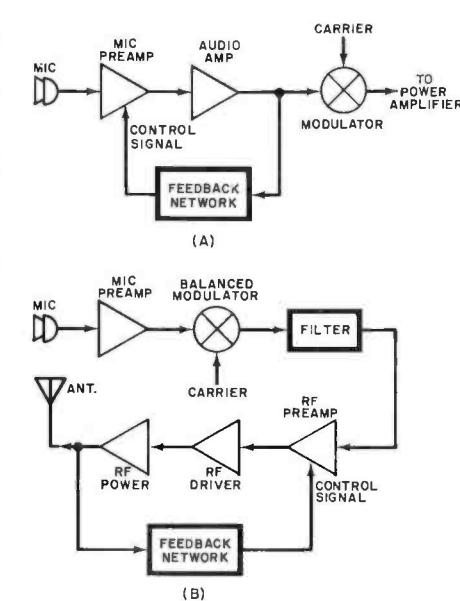


Fig. 3. Two methods of compression: audio and r-f.

One simple way to do this is to crank up the audio gain control. The resulting signal is shown in Fig. 2. Although the average value is a lot closer to the peak, the tops of the waveform are clipped off because the transmitter can't deliver the additional power required. Also, the carrier is interrupted on negative voice peaks. These result in "splatter" onto other channels and poor intelligibility on the desired one. "More modulation means a better signal," is only true when talking about modulation percentages up to the optimum of 100%. Trying to load more information onto the carrier than it can handle causes interference to other CB signals, TV receivers, etc. Also, it's illegal!

Speech processing, however, can increase the average power of the modulated signal without generating a clipped and interrupted wave. There are four basic types that we'll consider: audio compression, audio clipping, r-f compression, and r-f clipping. Each deals with the problem in differ-

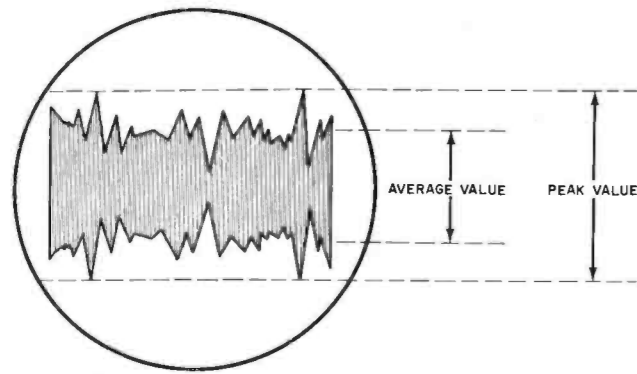


Fig. 4. In compressed modulated waveform, average signal level is high but peaks are compressed to avoid clipping.

ent ways. Predictably, each has advantages, disadvantages, and a varying degree of effectiveness.

Compression. One way of increasing the average degree of modulation is to use a "flexible" amplifier. That is, one with a lot of gain for weak signals, but very little for strong ones. These circuits have been around for a long time, and often assume the alias "automatic gain control" or simply agc. There are two methods of compression: audio and r-f, as shown in Fig. 3.

An audio compression system (Fig. 3A) works on the signal that comes straight from the microphone. This signal is amplified by the MIC PREAMP, and in turn by the AUDIO AMP. As the amplified version appears at the output of the AUDIO AMP, a small portion gets routed into the FEEDBACK NETWORK. In this stage, the sampled signal is rectified and filtered into a dc control voltage, which in turn determines the gain of the MIC PREAMP. When a strong signal appears at the AUDIO AMP output, a high dc level appears at the CONTROL SIGNAL input of the MIC PREAMP, cutting down its gain.

Sounds like a dog chasing its tail, doesn't it? In this case, however, the FEEDBACK NETWORK works fast enough

to control the PREAMP gain while the strong (or weak) signal is still going through it.

A weak signal into the MIC PREAMP will generate a small control voltage, providing lots of amplification. Accordingly, the average level of the modulating waveform will be increased; and, consequently, the carrier will be more fully modulated most of the time (Fig. 4).

A similar compression system operates on the modulated waveform, as shown in Fig. 3B. The r-f compressor (in this case, installed in an SSB transmitter) controls the gain of the r-f amplifiers by sampling a portion of the POWER AMP's output. The FEEDBACK NETWORK converts the r-f sample into a dc control voltage, which determines the gain of the R-F PREAMP. The same type of compression action occurs as in the audio system. The output signal would look like the one in Fig. 4.

Clipping. Another approach to speech processing is clipping, which is performed on either audio or r-f signals. In an audio clipper (Fig. 5A), the mike output is amplified by the MIC PREAMP, and filtered by the low-pass filter. Any audio frequencies above 3000 Hz are shunted to ground, since they don't carry useful information

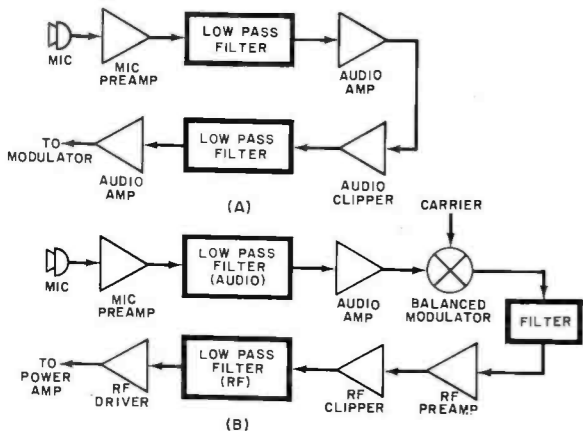


Fig. 5. At (A) audio clipper shapes voice waveform before modulation. R-f clipping (B) processes modulated signal and requires shielding and filter.

and could cause problems. The AUDIO AMP then boosts the signal, and its output drives the AUDIO CLIPPER.

If we compare the output from this stage with Fig. 2, we would see almost the same waveform. This occurs because in most systems the clipper is really an amplifier running wide open. So the signal peaks get clipped off since they're too strong to be reproduced by the amplifier. But wait a minute—didn't the clipping action of Fig. 2 also imply splatter, harmonic radiation, etc.? Yes, but in this case we smooth the waveform by filtering out the audio highs, and then follow up the clipper with another LOW PASS FILTER. This rounds off the clipped corners of the signal, making it much more tolerable. Finally, an AUDIO AMP makes up for filter loss, and drives the modulator as in a conventional system. The output of the AUDIO AMP is shown in Fig. 6. The average value is close to the peak value, and signal peaks are smoothed out.

Clipping can also be accomplished in the r-f portion of a transmitter. Figure 5B shows the processing chain in a typical SSB transmitter. The MIC PREAMP boosts the modulating signal from the microphone. An audio LOW PASS FILTER eliminates highs, and the filtered waveform is boosted again by an AUDIO AMP. Then, the audio signal is combined with a carrier by the BALANCED MODULATOR, and a double sideband, suppressed carrier signal appears at the output. Since we need only one sideband, the FILTER eliminates the undesired one (upper or lower, depending on our preference).

Now we have a single sideband signal, albeit a weak one. The R-F PREAMP gives it a shot in the arm, and an R-F CLIPPER amplifies the signal so much that the tops get closed. As we mentioned before, the sharp corners of a clipped waveform contain many harmonics, so an r-f LOW PASS FILTER shunts the offending components to ground, and smooths out the signal. Finally, an R-F DRIVER adds signal gain to drive the power amp. The resulting waveform is shown in Fig. 6. Again, note that the average/peak ratio is a lot better, and the sharp edges are smoothed out.

Which Is Best? We've examined four methods of speech processing, and all appear to perform the desired function. The average level of modulation is greatly increased, but no spurious

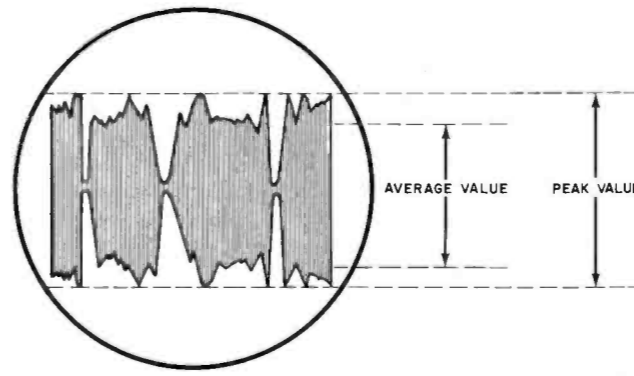


Fig. 6. A clipped and shaped waveform. Average modulation levels are higher, but filtering eliminates splatter.

signals are generated. But which system is best to use, in terms of ease of construction and/or installation, and degree of effectiveness?

In general, audio systems are easier to use, because they work with the existing transmitter circuitry. We can build an audio compressor or clipper in a small box, plug the mike into it and run a cable from the processor output to the mike jack on the transceiver. Audio compressors are simpler to build than clippers, since they don't require filtering stages. R-f systems, on the other hand, have to be inserted at a point within the r-f circuitry of the transceiver, thus requiring some "surgery." In general, r-f clippers are more complex and expensive than compressors, because of the strict filtering requirements.

But in terms of what the CB'er wants most, increased "talk power," r-f systems are superior to audio ones. For a given amount of speech processing, say 20 dB, r-f clipping will increase the signal-to-noise ratio at the receiver by 8 dB (over one S unit). Audio clipping will improve the S/N by about 5 dB, or just under one S unit. Audio and r-f compression will both give an S/N about one dB better than an unprocessed signal.

Transmitter Requirements. In order to get the most out of a speech processor, the transmitter must be designed along certain guidelines. Most important of these concerns the type of tubes or transistors used in the driver and power amplifier stages. Since the average modulation level is a lot higher, these devices will be handling much more power most of the time. This means they'll run hotter, and must be able to dissipate the extra heat generated. Otherwise, thermal effects will reduce their useful lifetimes.

Further, the power supply that supports these active devices must be

"stiff," since the average power demand will be a lot higher. This means that larger filter capacitors, higher-current rectifiers and voltage regulators must be used. Some compact chassis may require a cooling fan to move more air around heat-generating components. And, of course, inboard clippers will necessitate the use of stringent filtering and shielding techniques.

All this adds to the cost of producing a CB rig. Is it worth it? From on-the-air listening experience, speech compressors can do an impressive job of boosting signal readability. An 8-dB (6.3 times) signal boost can make that marginal contact a solid one!

Intelligibility. But copying a message easily is not just a question of signal levels. How clean the received signal is can be just as important. If we compare the original modulating signal (Fig. 1A) to the unprocessed, modulated carrier (Fig. 1B), we can see that the envelope of the waveform is a good replica of the voice signal. The processed signals (Figs. 4 and 6) contain envelopes which are distortions of the original. Inevitably, any speech processing introduces a certain amount of distortion. In most cases though, you'll find that the processed version is still quite recognizable—and more intelligible—than the original.

Most speech processors available to CB'ers are audio compressors—whether they are built-in, add-on accessories, or packaged inside an optional microphone. As we've already seen, clipping is more effective, especially when the r-f method is used. As more and more CB'ers learn of the advantages of speech processing, more effective methods will be included in new transceivers. It's a safe bet that you'll hear an increasing number of properly clipped signals on the air! ♦

THE SILENCER

Your ears are burning with amplified noise. Even though your system is delivering sound accurately, it's also doing an efficient job of pumping out noise... accurately. Ideally, music should be recreated against a dead silent background. The Phase Linear 1000 accomplishes just that with two unique systems: The Auto Correlator Noise Reduction and the Dynamic Range Recovery Systems.

★ It improves the overall effective dynamic range and signal/noise ratio 17.5 dB in any stereo system with any stereo source.


★ The Auto Correlator reduces hiss and noise 10 dB without the loss of high frequencies and without pre-encoding.

★ The Dynamic Range Recovery System restores 7.5 dB of dynamic range without pumping and swishing.

★ Plus, it removes hum, rumble and low frequency noises, without the loss of low frequency music.


★ WARRANTY: 3 years, parts and labor

Even the finest stereo systems are limited in performance by the quality and nature of the recording. With the Phase Linear 1000, these limitations are overcome. Added to any receiver or preamplifier, it gives you the most significant improvement in sound reproduction for the money... more than any other single piece of equipment you could add to your system. Ask your dealer for an audition. The silence is deafening.

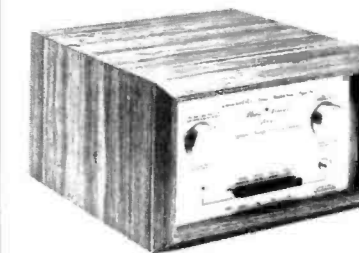

Phase Linear 1000

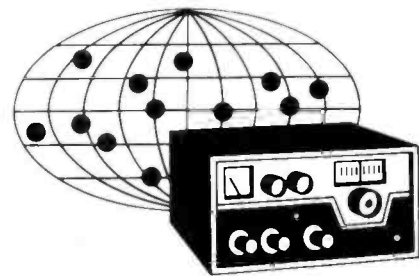Phase Linear Corporation,
20121 48th Avenue W.
Lynnwood, Washington 98036
CIRCLE NO. 58 ON FREE INFORMATION CARD



DX Listening

By Glenn Hauser

WHAT TO LOOK FOR IN A SHORTWAVE RECEIVER

IT'S not too early to start hinting for a new shortwave receiver for Christmas. But unless you pick it out yourself, you may be disappointed. Choosing the best receiver is rather involved. You must know what to look for and how important certain features will be to you.

If you're just starting in DX listening, and not sure how deeply you want to get involved, you may prefer a low-priced portable, to get a feel for what it's all about. The trouble is, the portable may turn you off—unless you realize that most of the problems you have with it can be eliminated with a more expensive receiver.

Image rejection is a common problem in receivers with only one i-f stage. It's possible to be tuned to a station on a desired frequency and also simultaneously pick up both that station and an interloper on another frequency. This interfering "image" signal will be found at a frequency displaced above or below the desired frequency by an amount equal to twice the receiver's i-f. Hence, if you're simultaneously receiving 14-MHz Amateur transmissions and 15-MHz broadcasts, your 455-kHz i-f receiver can't sort out the two signals spaced 910 kHz apart. To minimize such problems, it's best to get a dual- or triple-conversion receiver right at the beginning.

Crowded dials cause frustration. Unless a receiver has adequate *bandspread*, you'll end up sweeping past a host of stations as soon as you touch the tuning dial. But a well-designed receiver with 1-kHz calibration marks spaced 1/8" apart can be a joy to operate. It will allow you to easily home in on a rare station with a high degree of accuracy. Best, but costly,

are the digital frequency synthesizer receivers.

Selectivity is one of the most important characteristics of a good receiver. On better receivers, you can select different bandwidths as required; but lacking this feature, can you separate two strong signals only 5 kHz apart?

Sensitivity is an important consideration, too. Although it's great to have a receiver that can respond to signal levels of a fraction of a microvolt, such sensitivity is useless if masked by receiver-generated noise. An S/N ratio of at least 10 dB is acceptable.

If you want to copy SSB and CW signals, a *bfo* and *product detector* are essential. They also allow you to accurately determine the frequency of AM carriers (by tuning for zero beat).

If you live in an electrically noisy area and/or listen to especially noisy signals, a *noise limiter*—better still, a *noise blanker*—will make broadcasts intelligible.

To Buy or Not to Buy. In some cases, the deficiencies of your present receiver can be compensated for with an add-on accessory. For example, you can boost sensitivity by placing a properly designed FET or IC preamplifier between the antenna lead-in and receiver. A Q multiplier can add selectivity, as can an audio filter and/or an antenna tuner. The antenna tuner is particularly helpful in improving the selectivity of the front end. A crystal-controlled converter can eliminate image problems.

In short, sometimes it's not justified to buy a whole new receiver. In some cases, however, buying a new receiver is unavoidable. Poor mechanical and/or electrical stability, crowded

tuning dials, and a wobbly tuning mechanism demand extensive work beyond the capability of many DX'ers.

Where and What to Buy. We would all like to have a state-of-the-art receiver. But most of us simply can't afford to make a large investment for one of these receivers. What then is a realistic alternative?

There are a handful of fine new SW and general-coverage receivers around that range in price from about \$160 to \$600. The lower in price you go, the less you get in reception and general handling ability. Too, you might consider a used communication receiver that's in good condition. Many have crystal or mechanical filters, concentric tuning mechanisms, notch filters, and rock-solid construction, among other features. Their most desirable attribute is low price, and many of them—especially military surplus receivers—can be obtained for a fraction of their original cost.

If you're looking for one of these receivers, check the ads in amateur radio magazines. Surplus dealers and amateur radio supply houses in your area are also worth a visit. Two points are worth remembering, however. First, try to simulate your actual receiving conditions as close as possible. The best way to do this is to arrange to take the receiver home for a trial period—if the owner agrees.

Among the SW receivers currently used by DX'ers actively reporting to major clubs are the Hammarlund HQ180, HQ145, HQ160, and SP-600; R390 series of military receivers; and Drake SPR4, SW4, and R4B. Some are Amateur-band-only receivers and require additional local oscillator crystals. Others are for SW and broadcast-band only reception. The latter cover the major international bands (13, 16, 19, etc., meters), but they can't be used out-of-band where some rare catches lurk.

Swan On the Air Again. Last summer, Jack Jones in Jackson, Miss., discovered a new Honduran station calling itself "Radio Swan de Honduras" on 6185 kHz. The station takes an anti-communist line and operates 24 hours a day. The mailing address is in San Pedro Sula.

The Brazilian Shuffle. This is not a new dance, but a complicated new set of frequency assignments in the tropical bands—perhaps to show rural sta-

tions the central government is still boss, or just to confuse DX listeners! Here are the changes so far uncovered, thanks to monitoring in Brazil by Jack Perolo, Robert Veltmeijer and Cláudio Moraes, and in Paraguay by Tony Jones. Throw out your old lists, and go by this one when DX'ing Brazil. Best times are 0800-0900 GMT, and sunset to 0200. R=Radio; D=Difusora; Cl=Clube; Cu=Cultura.

kHz		New	Old	Station
2420	2410	R	São Carlos	
2424	2420	R	Carajá	
3205	3265	R	Ribeirão Preto	
3225	4935		Lins RCI	
3235	3255	RCI	Marília	
3245	4825	RCI	Varginha	
3255	3355	RD	Uberlândia	
3255	3305	R	Educadora Cariri	
3265	4885	RCu	Poços de Caldas	
3285	3385	RCI	Teresina	
3287	3375	R	Olinda	
3305	3283	RC1	Fluminense	
3325	3315	R	Gazeta Alagoas	
3335	3345	R	Alvorada Londrina	
3345	3295	R	Educadora Uberlândia	
3365	4825	R	Educadora Parnaíba	
3365	4915	RCu	Araraquara	
3385	4795	R	Congonhas	
4756	3295	R	Ed. Rural Campo Grande	
4765	5035	R	Espírito Santo	
4775	4985	A	Voz do Oeste	
4785	4755	R	Brasil Campinas	
4790v	5025	RD	Aquidauana (varies to 4795)	
4808v	4805	RD	Amazonas	
4815	3365	RD	Paraná/Londrina	
4825	4815	RD	Petrópolis	
4825	4945	R	Ed. Bragança	
4835	4845	RD	Teresina	
4855	4865	RCI	do Pará	
4865	4765	R	Sociedade Feira de Santana	

4915	5035	R	Anhanguera
4925	4855	RD	Taubaté
4935	4945	R	Capixaba
4935	4945	RD	Mearim
4945	5015	RD	Poços de Caldas
4945	5025		Voz de São Francisco
4965	4835	R	Sociedade Triângulo Mineiro
4965	4937	R	Poti
4985 1/2	4995	R	Brasil Central
5015	5055	RCu	de Cuiabá
5015	4975	R	Copacabana
5015	4880	R	Pioneira
5025	3325	R	Borborema
5025	5055	R	Vitória
5035	4985	R	Aparecida
5045	3335	R	Presidente Prudente

This list does not include some stations on the same and other frequencies, which have not moved.

More on RCI. Radio Canada International is solving its QSL versus programming problem by disbanding its shortwave club, dropping DX and mailbag shows after November 1. The new requirement is that QSL seekers fill in details themselves, starting next spring.

Change of Address. When the Executive Editor of the International Radio Club of America, Fr. Jack Pejza, was transferred to a new assignment, ending the club's San Diego HQ, a new group in Seattle stepped forward to keep the club in business. IRCA's new address is Box 21462, Seattle, WA 98111. Samples of the 34-issue-per-year *DX Monitor*, covering all aspects of DX'ing the mediumwave (AM) band, are 50¢ each. ♦

ENGLISH-LANGUAGE SHORTWAVE BROADCASTS FOR NOV. THRU FEB. by Richard E. Wood

TO EASTERN NORTH AMERICA				
TIME-EST	TIME-GMT	STATION	QUAL*	FREQUENCIES, MHz
6:00-7:30 a.m.	1100-1230	London, England	G	5.990 (via Sackville), 15.07
6:00-6:30 a.m.	1100-1130	Tirana, Albania	F	9.48, 11.985
6:00-9:00 a.m.	1100-1400	**VoA, Washington, U.S.A.	G	5.955, 9.73
6:15-7:15 a.m.	1115-1215	Montreal, Canada	G	5.97
6:15-7:45 a.m.	1115-1245	Melbourne, Australia	G	9.58
7:00-7:55 a.m.	1200-1255	Peking, China	F	11.685
7:30-8:30 a.m.	1230-1330	London, England	G	15.07
7:15-10:00 a.m.	1215-1500	HCJB, Quito, Ecuador	G	11.74, 15.115
7:30-8:00 a.m.	1230-1300	Stockholm, Sweden	G	17.71
8:15-8:45 a.m.	1315-1345	Berne, Switzerland	G	15.14
9:00-9:30 a.m.	1400-1430	Stockholm, Sweden	G	17.71
		Oslo, Norway	F	17.795 (Sun. only)
		Helsinki, Finland	G	15.185
10:00-11:15 a.m.	1500-1615	London, England	G	17.84 (via Ascension)
10:00-11:30 a.m.	1500-1630	HCJB, Quito, Ecuador	G	11.74, 15.115, 17.88

CB where the ACTION'S at

Millions of 2-way CB radios are in use—millions of new ones are being sold annually to new CBers and for replacing old units—what a market for repair service. It's the biggest thing in electronics since color TV. There's only one thing wrong with CB growth—the lack of technicians capable of servicing CB radios. That's why many TV shops are expanding into CB and why new CB shops are opening up all over the country. Going CB servicing rates run from \$12 to \$24 per hour.

To get into CB radio servicing, full-time or part-time, you need test equipment, an FCC operator license and to learn how. **To learn how**, you can buy the **CB RADIO REPAIR COURSE** for cash, on a monthly payment plan, or charge the cost to your BankAmericard or Master Charge account.

To make it easy to study, this 70-lesson course employs the **PROGRAMMED** teaching technique and sticks to the target—CB radio. Study at your own pace as you receive the self-examining lessons. We can't guarantee that you will become a CB expert since that depends on you. We promise nothing except information. To get the facts about this course, write a letter or card or mail the coupon below today. No salesman will call.


CB RADIO REPAIR COURSE, INC. Dept. P-115
531 N. Ann Arbor
Oklahoma City, OK 73127

Please send information about your Course to:

Name _____
Address _____
City _____ State _____ Zip _____

CIRCLE NO. 19 ON FREE INFORMATION CARD

A Major Advance...

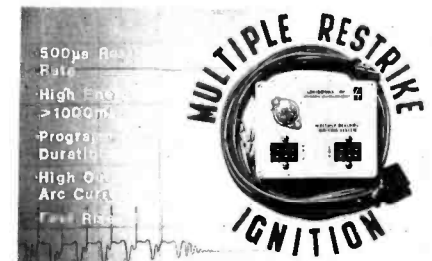

- *INSURES PROPER COMBUSTION
- *EASIER STARTING
- *LONGER POINTS and PLUG LIFE
- *INCREASE MILEAGE up to 40%
- *EASY INSTALLATION (12v neg. gnd.)

Labtronics' Multiple Restrike (M-R) Ignition produces a high energy repetitive spark on each power stroke to effectively ignite the air/fuel mixture. M-R statistically insures more complete combustion - resulting in greater energy and increased efficiency. Send for Labtronics' free literature on the M-R system. Better yet, experience M-R and enjoy the pleasure and the economy of a well-performing engine.

Model VI \$79.95 • 1 Year Warranty •
Model VI-B \$59.95
Brochure 30 Day Money Back Guarantee
P.P.D. in U.S.A. Send Check or Money Order to:
Labtronics, Incorporated
3635 Hillside, Ypsilanti, Michigan 48197

DEDICATED TO EFFICIENCY
CIRCLE NO. 43 ON FREE INFORMATION CARD



Computer Bits

SOFTWARE TOOLS

By Jerry Ogdin

NO MATTER how small the computer, even the most dedicated programmer will rapidly become bored with binary notation.

Some hobbyists use a Teletype as there are several older models on the market at reasonable prices. Even with a Teletype, though, you need some software to convert those key-strokes into something meaningful in memory. If you can't afford a Teletype, you can almost always use an en-

coded keyboard. These are frequently on the surplus market for less than \$25.00.

A terminal is important, but it is only one tool in the computer hobbyist's kit. Once you've written a program and gotten it into storage, you ought to use the cassette interface (HIT) described in September's column. With this tool, you have to "button in" the program bit-by-bit only once. After it is in storage, you can write it out to be taped

and read in the next time you want it. Of course, if your only storage medium is RAM, you'll lose the memory contents when you turn the computer off. So, it's a good idea to copy the latest version of a program out to tape as a backup.

Also, if your only storage medium is RAM, you'll have to reenter the tape reading routine laboriously through the switches (or the terminal) each time the computer power is turned on. That is a good reason for having a small program, called a *bootstrap loader*, kept in read-only memory. This program makes it possible to read data from the tape and then execute that data. Such a read-in program is usually somewhat larger and more powerful, so it reads in several records (perhaps using the bootstrap program as a subroutine), which make up an even larger and more sophisticated program. The effect, then, is to use one group of records to read the next

group in, thus "pulling" the program in by its own bootstraps.

Using a Monitor. The ability to preserve a program for later recall is important, but it doesn't solve two major nuisances: (1) you still have to key in the program bit-by-bit the first time; and (2) every time you make an error in the program, you have to key in the changes, some of which may be traumatic and complex. One of the best ways to solve this kind of inconvenience is to provide a small *monitor*. A monitor is just another computer program, but one that is designed to make computer use more convenient. This program reads characters from a terminal (or a separate keyboard), with these characters specifying the bit patterns to put into memory.

The simplest monitor has three basic *commands*: Load, Dump and Go. A command is a single letter typed at a time when the monitor is not otherwise engaged in some activity. Typical commands are single letters like "L" for Load, "D" for Dump and "G" for Go. When you type in "L" you are directing the monitor program to accept keyboard input and load it into memory; "D" means you want to display contents of memory on your terminal or display device; "G" is your means of transferring control out of the monitor into the program you have previously loaded.

Most programmers now use the hexadecimal number system for communicating with the machine, although there are "pockets" of users of octal. Hex and octal are, of course, just shorthand notations for binary code. Hex digits allow us to specify four bits with one symbol, octal allows three. The hexadecimal digits are 0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, B, C, D, E, and F. (The letters A through F stand for decimal equivalent values 10 through 15, respectively.) The monitor, for utmost simplicity, uses only hexadecimal digits for the specification of addresses and data byte values.

Each of the command letters (L, D or G) is followed by an address that specifies where to start. For the Load command, that address is where the first byte of data from the keyboard will be stored; for Dump, it is the address from which data will begin being displayed; for Go, it is the address that is to be placed into the CPU's program counter. Whenever the Go command's address has been supplied, control is transferred to that

location. Whenever the Dump command's address has been given, data displaying will begin. However, after the Load command's address, the monitor will expect more bytes (one after another) to be loaded into successive locations in memory.

A small monitor for the 8080 microprocessor that you can use as a model is shown opposite. Each command is stopped by resetting the CPU, thus returning control to the top of the monitor. Notice some error correction conventions that have been instituted to save you some time: numbers are assumed to consist of any number of hex digits but if the monitor wants an address, only the least-significant four digits are used. Likewise, for a data byte, only the least-significant two hex digits are preserved. This means that if you've made an error, just keep typing. Hex digits end with any character that is not a hex digit; most people find that the space character is the most convenient.

News Items. The extremely popular 8080, originally from Intel, is now being supplied by other semiconductor makers as well. The TI TMS8080 is identical to the original 8080, which Intel no longer makes. Intel's newer device, the 8080A, is functionally identical but has better current drive capacity. Intel has another part, the 8080A-1, that'll go faster so that AMD's 9080 (which is supposed to run 50% faster than the original Intel part) will have a competitor. So, if you are using the 8080, be sure to check the diagrams to see that your part matches the requirements.

The new MOS Technology 6501 is destined to become a popular CPU among hobbyists, if only because of its dramatically low price (\$20 at press time). The device is modelled after Motorola's 6800, although with some major differences. All of the Motorola support parts like memory I/O chips can be used with the 6501, so you can get on board quickly. The Motorola software, however, cannot be executed on the 6501 without revision.


The 6501 is capable of operation at twice the Motorola part's speed; some parts may operate three times as fast. The introduction of this part is likely to start the real price war that has been brewing in the microprocessor business. Even with the new support chip for the 8008 that Intel has announced, it seems unlikely that it can compete with the 6501 for hobbyist use. ♦

QUICK.... what number is this?



If you have to read your microcomputer like this--bit by bit, from rows of lights--the computer's making you do *its* work. And if you have to use rows of toggle switches to program it, you might wonder why they call the computer a labor-saving device!

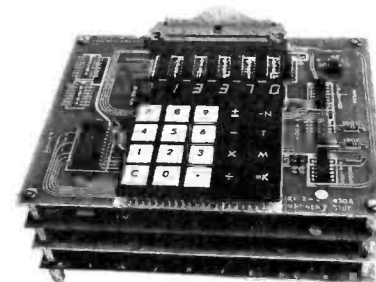Contrast the layout of a typical pocket calculator. A key for each number and function; six easy-to-read digits. Why not design microcomputers like that?



Here they are! The *modular micros* from Martin Research. The keyboard programs the computer, and the bright, fully-decoded digits display data and memory addresses. A Monitor program in a PROM makes program entry easy. And, even the smallest system comes with enough RAM memory to get started!


Both the *MIKE 2* system, with the popular 8008 processor, and the 8080-based *MIKE 3* rely on the *same* universal bus structure. This means that accessories--like our 450 ns 4K RAM--are compatible with these and other 8-bit CPUs. And, systems start at under \$300! For details, write for your...

FREE CATALOG!



MIKE 2 MANUAL...
This looseleaf book includes full information on the *MIKE 2* system, with schematics.

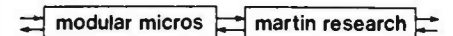
Price for orders received by November 15, 1975... **\$19**
Includes a certificate worth \$10 towards a *modular micro* system, good 90 days. (Offer valid, USA only.) After 11/15: \$25.



Martin Research / 3336 Commercial Ave.
Northbrook, IL 60062 / (312) 498-5060
CIRCLE NO. 49 ON FREE INFORMATION CARD

```
; THIS IS THE POPULAR ELECTRONICS SUPER-
; SIMPLF MONITOR.  COMMANDS ARE:
; D XXXX (DUMP FROM XXXX)
; L XXXX (LOAD FROM XXXX)
; G XXXX (GO TO XXXX)
STACK EQU 03FFH ;YOUR STACK ORIGIN
CRLF EQU 0106H ;YOUR CR, LF ROUTINE
WRCHR EQU 0103H ;YOUR OUTPUT ROUTINE
RDCHR EQU 0100H ;YOUR READING ROUTINE
;
; MONITOR ENTRY POINT
;
0040: 31FF03 PEMON: LXI SP,STACK ;INITIALIZE
CD0601 CALL CRLF ;ISSUE CARRIAGE RETURN,
3E3F MVI A,'2' ; LINE FEED AND ?
CD0301 CALL WRCHR ;AWAIT COMMAND
CD0001 CALL RDCHR ;STRIP OFF PARITY BIT
E67F ANI 07FH
FE4C CPI 'L'
CA6300 JZ LOAD ;"LOAD" COMMAND
FE44 CPI 'D'
CA7400 JZ DUMP ;"DUMP" COMMAND
FE47 CPI 'G'
C24000 JNZ PEMON ;ERROR
; THIS THE THE "GO" COMMAND PROCESSOR. WE
; NOW EXPECT A 16-BIT DESTINATION ADDRESS
; AND THEN TRANSFER TO IT
005F: CDB700 CALL RDNUM
E9 PCHL ;"GO"
; THIS IS THE "LOAD" COMMAND PROCESSOR. THE
; USER IS EXPECTED TO TYPE IN A 16-BIT ADDRESS
; FOLLOWED BY DATA BYTES TO LOAD INTO SUCCESSIVE
; LOCATIONS. ANY NON-HEX CHARACTER SPARATES
; THE BYTES FROM ONE ANOTHER. ANY BYTE THAT IS
; TERMINATED WITH A COLON WILL BE IGNORED.
0063: CDCD00 LOAD: CALL RDNR2 ;GET USER'S ADDRESS
CDB700 CALL RDNUM ;GET A BYTE
FE3A CPI ':'
CA6600 JZ LOAD+3 ;SKIP IF FOLLOWED BY ':'
7D MOV A,L ;GET LAST TWO HEX DIGITS
02 STAX B ;STORE THEM AWAY
03 INX B
C36600 JMP LOAD+3 ;(GET W/ CPU RESET)
; THIS IS THE "DUMP" COMMAND PROCESSOR.
; THE USER IS EXPECTED TO SUPPLY A 16-BIT
; STARTING ADDRESS. WFNNEVER THE LEAST-SIG-
; NIFICANT FOUR BITS OF THE ADDRESS OF THE
; NEXT BYTE ARE ZERO, THE CARRIAGE IS RETURNED
; AND THE ADDRESS IS PRINTED (FOLLOWED BY COLON).
0074: CDCD00 DUMP: CALL RDNR2 ;GET STARTING ADDRESS
79 MOV A,C ;CHECK TO SEE IF
E60F ANI 15 ; NEW-LINE TIME.
C2A200 JNZ MORE ;NO. JUST PRINT
CD0601 CALL CRLF ;START NEW LINE
78 MOV A,B ;GET MSB OF ADDRESS
1F RAR
1F RAR
1F RAR
1F RAR
1F RAR
1F RAR
1F RAR
1F RAR
1F RAR
1F RAR
CDED00 CALL CVTAS
78 MOV A,B ;GET 2ND DIGIT
CDED00 CALL CVTAS
79 MOV A,C ;GET 3RD DIGIT
1F RAR
1F RAR
1F RAR
1F RAR
1F RAR
1F RAR
1F RAR
1F RAR
1F RAR
1F RAR
CDED00 CALL CVTAS
79 MOV A,C ;DO LAST DIGIT
CDED00 CALL CVTAS
3E3A MVI A,' ' ;MARK ADDRESS SPECIALLY
CD0301 CALL WRCHR
```

```
3E20 MVI A,' '
CD0301 CALL WRCHR
00A2: 0A MORE: LDAX B ;FETCH BYTE TO DUMP
1F RAR
1F RAR
1F RAR
1F RAR
1F RAR
CDED00 CALL CVTAS ;ISSUE MSB
0A LDAX B
CDED00 CALL CVTAS
3E20 MVI A,' '
CD0301 CALL WRCHR
03 INX B ;ACQUIRE NEXT CELL
C37700 JMP DUMP+3
; THIS ROUTINE READS ONE OR MORE HEXADECIMAL
; DIGIT CHARACTERS ('0'..'9', 'A'..'F') IN
; AND ACCUMULATES A SIXTEEN-BIT NUMBER IN
; THE (H,L). EACH NEW DIGIT IS SHIFTED INTO
; THE LEAST-SIGNIFICANT FOUR BITS OF THE (H,L).
; CONTROL IS RETURNED WHENEVER THE DEPENDENT
; ROUTINE ("RDHEX") SETS THE CARRY BIT TRUE.
00B7: 210000 RDNUM: LXI H,0 ;START OFF VALUE AT 0
CDD600 CALL RDHEX ;GO GET A HEX DIGIT
DAB700 JC RDNUM ;AWAIT HEX DIGIT
00C0: 29 RDNXT: DAD H ;SHIFT (H,L) LEFT 4
29 DAD H
29 DAD H
29 DAD H
B5 ORA L ;PLACE NEW FOUR BITS IN
6F MOV L,A
CDD600 CALL RDHEX ;GO GET NEXT DIGIT
D8 RC ;THE NUMBER'S FINISHED
C3C000 JMP RDNXT ;GO PROCESS NEXT DIGIT
; THIS ROUTINE READS A NUMBER VIA "RDNUM" AND
; PLACES IT INTO THE (B,C) PAIR
00CD: CDB700 RDNR2: CALL RDNUM ;GET THE VALUE IN (H,L)
44 MOV B,H ;THEN MOVE IT
4D MOV C,L
C9 RET
; THIS ROUTINE READS IN AN ASCII CHARACTER,
; STRIPS OFF PARITY AND EXAMINES IT FOR
; MEMBERSHIP IN THE HEX-DIGIT SET. IF IT IS
; A HEX-DIGIT THE A-REGISTER IS LEFT AT THE FOUR
; BIT VALUE APPROPRIATE AND THE CARRY IS CLEARED.
; ANY OTHER CHARACTER IS LEFT UNTOUCHED AND THE
; CARRY IS SET.
00D3: D630 RDDIG: SUI '0' ;TRANSLATE '0'..'9'
C9 RET
00D6: CD0001 RDHEX: CALL RDCHR ;**ENTRY POINT**
E67F ANI 07FH ;REMOVE PARITY BIT
FE30 CPI '0'
D8 RC ;CHAR LESS THAN '0' (NOT HEX)
FE3A CPI '9'+1
DAD300 JC RDDIG ;IN RANGE 0..9
FE41 CPI 'A'
D8 RC ;BETWEEN 9 AND A
FE47 CPI 'F'+1
3F CMC
D8 RC ;NOT HEX CHARACTER
D637 SUI 'A'-10 ;TRANSLATE 'A'..'F'
C9 RET
; THIS ROUTINE CONVERTS A BINARY NUMBER IN THE
; LEAST-SIGNIFICANT BITS OF THE A-REGISTER TO
; AN ASCII CHARACTER REPRESENTING THE HEX VALUE
; AND THEN ISSUES IT AS OUTPUT.
00ED: E60F CVTAS: ANI 15 ;ISOLATE FOUR BITS
C630 ADI '0' ;SHIFT DIGITS INTO ASCII
FE3A CPI '9'+1 ;SEE IF IT WAS 0..9
DA0301 JC WRCHR
C607 ADI 'A'-'0'-10 ;CONVERT TO 'A'..'F'
C30301 JMP WRCHR
```

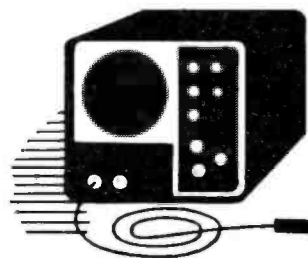

Test Equipment Scene


By Leslie Solomon

A DUAL-POLARITY DC METER

HOW CAN you get a dc meter to indicate upscale with either a positive or negative input, without reversing the leads? It's very simple with an operational amplifier and a few other components as shown in the diagram.

The op amp is connected as a non-inverting dc amplifier using the diode full-wave bridge and the combination of $R1$ and $R2$ to determine the gain. Capacitor $C2$ bypasses any ac component that might be across $R2$. The op amp can be almost any type with a high slew rate. For some op amps, frequency compensation may be required to remove any tendency for the op amp to oscillate at a high frequency, which would produce erratic meter indications.

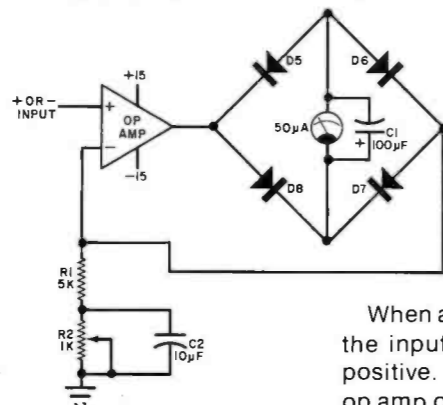Since the op amp is powered by a balanced +15-V and -15-V supply and the inverting (-) input is refer-



enced to the common, a positive-going voltage on the input produces a positive voltage at the op amp output. Conversely, a negative-going input produces a negative output. The amplitude of either output is proportional to the level of the input voltage up to the 15-V limit. The output is referenced to the common.

Obviously, if the input is zero, the output is zero. Actually, there is a very small switching area about the zero point where operation may be erratic; and there may also be a slight offset that can be removed by proper compensation as detailed in the op amp specifications.

When a positive voltage is applied at the input, the output starts to swing positive. Current then flows from the op amp output through $D8$, the meter, $D6$, $R1$, and $R2$ to ground. This current generates a positive voltage at the inverting input of the op amp. When it reaches the same level as the voltage on the noninverting input, the op amp stabilizes and the meter remains at some upscale indication (which can be adjusted by $R2$).

When a negative voltage is applied to the noninverting input, the output of the op amp swings negative and the current is through $R2$, $R1$, $D7$, $M1$, and $D5$. This current produces a negative voltage at the inverting input; and when it reaches the same value as that at the input, the op amp is stabilized. The meter once again settles at an upscale indication. In both cases, the current flows in the same direction through the meter.

Capacitor $C1$ is used to smooth any voltage fluctuations across the meter—especially when the meter is measuring low-frequency ac. Such voltage integration removes flutter from the meter movement.

The voltage difference between the two inputs to the op amp is measured in millivolts so the positive-to-negative transition is very sharp. With some accurately known dc (either polarity) applied to the input, $R2$ can be adjusted to give the correct indication on the meter.


ABOUT OUR STEREO IMAGE



Our fiendishness about quality control is being widely recognized. We, therefore, wish to thank all responsible, from our Spectrum Analyzer and Non-Reflecting Chamber to the Ears with which we test every single component and driver.

Stereo Review has called our product "Superb". Low Density Woofer Cones treated front and back for super-smooth response and Wide Dispersion Tweeters, resulting in exceptional

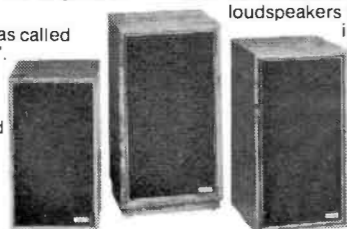stereo imaging, make the Audioanalysts sound magnificently accurate. That's what our sales tell us, despite our selective distribution which we intend to keep limited. So, we'll continue to torture each and every one of our loudspeakers and maintain our image. Beauty, after all, is in the ears of the beholder.



Audioanalyst
P.O. Box 262, Brookfield, Conn. 06804
Monstrous About Perfection

European & Middle East Distributors
Argo Hellas GmbH Frankfurt 6056 Hausenstamm 44 Industrie Strasse, West Germany
CIRCLE NO. 14 ON FREE INFORMATION CARD

Hobby Scene



By John McVeigh


"STEREO" HEADPHONE SOUND

Q. My stereo headphones don't sound "stereo", but rather like two separate sound sources. Why not? Can I build a circuit that will make them sound stereophonic?

—D. Whelan, Jersey City, NJ

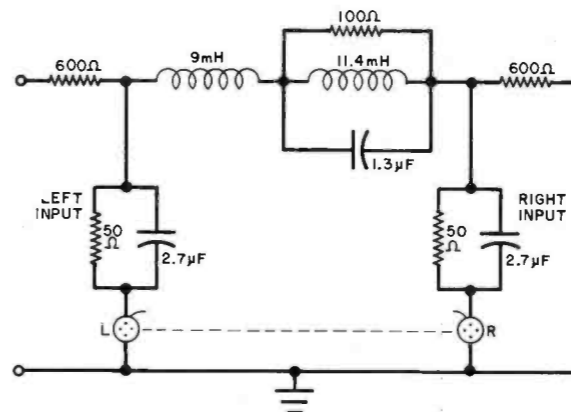A. "Stereo" headphones have two electrically and acoustically separate channels. Loudspeakers, on the other

hand, have a certain amount of acoustical "crosstalk" or blending between them. The circuit shown will electrically introduce the appropriate amount of crosstalk (in both amplitude and phase) to make the headphones sound "stereophonic" rather than "binaural". Be sure to use non-polarized capacitors. If you can't find the required values, use smaller capacitors, paralleling them until the desired capacitance is reached.




FLUORESCENT LAMP FILTER

Q. Whenever I turn on both my AM radio and my fluorescent desk lamp, "hash" comes out of the speaker. Is there any way to eliminate this interference?

—D. Rigg, Southampton, NY

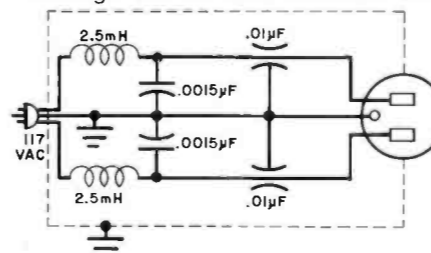A. R-f coming from the lamp can get into the radio by direct radiation or through the ac line cord. The filter



shown, when constructed in a metal box connected to a good ground, will take care of r-f on the line cord. For lamps up to 35 W, use two Miller 6304 coils in parallel for the required 2.5-mH inductors. Bypass capacitors should be 500-WVDC disc ceramics,


and the feedthrough capacitors should be Allen-Bradley CL003-HA503P units or equivalent. If the problem persists, it will be necessary to shield the lamp housing with fine-mesh screening. Ground both the screening and lamp base (if metal).

LED ZERO BEAT DISPLAY

Q. Is there any visual means of detecting when I have "zero-beated" my vfo and a received signal?


—M. Farber, Las Vegas, Nev.

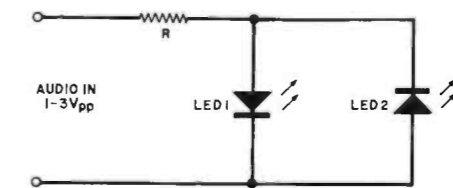A. If your receiver has an S meter, you can adjust for zero beat while watching its needle. As the two frequencies approach each other, the needle will swing back and forth more and more



slowly. At zero beat, the needle will hold one position. The circuit shown will also give a visual display of zero beat. When the vfo has come within 25 Hz of the signal's carrier, the LED's will alternately flicker. At zero beat, neither LED will light up. The circuit can also be used as a polarity checker for dc applications. When the top input terminal is positive, $LED1$ will glow, while $LED2$ turns on when the bottom input terminal is positive. Select R to limit LED current to a safe value, or use a voltage divider.

BETTER THAN A THIRD HAND!

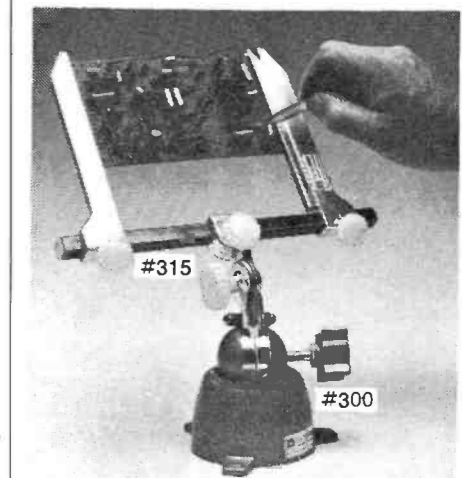

PANAVISE TILTS, TURNS, AND ROTATES TO ANY POSITION. IT HOLDS YOUR P.C. BOARD EXACTLY WHERE YOU WANT IT.

Quite possibly the finest new tool you will buy this year. PanaVise is built to exacting professional standards. We guarantee it!

Illustrated is P.C. Board Holder #315 in the #300 Base. This combination has exclusive multiple positioning ability. Boards are gently but firmly locked in place with one arm spring loaded to facilitate quick board changes.

Three other bases and a wide variety of heads are available. All interchangeable! Buy a basic unit, then add on to create your system.

FREE Write for the latest PanaVise catalog, prices, and dealer listing.

Available through your dealer.


PANAVISE Dept. 15E
A Division of Colbert Industries
10107 Adella Ave., South Gate, CA 90280

CIRCLE NO. 57 ON FREE INFORMATION CARD

ISO-TIP® QUICK CHARGE

Recharges in 1/3rd the time of any other cordless iron.

Complete line of accessories available:

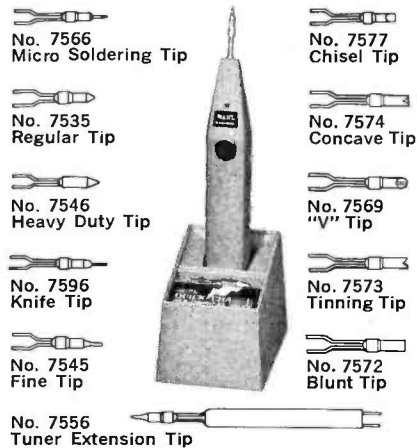

WAHL CLIPPER CORPORATION
ORIGINATORS OF PRACTICAL CORDLESS SOLDERING
Sterling, Illinois 61081 (815) 625-6525
"Manufacturing Excellence Since 1919"

CIRCLE NO. 78 ON FREE INFORMATION CARD

SAVE ON Brand Name Audio Components BY MAIL

Write Today for Our
FREE Audio Catalog

DIXIE is one of the oldest and largest audio component mail order houses in the country. Our prices on brand name components are actually LOWER than "Discounters". See our new catalog or call us for a price quote. Everything shipped factory-sealed with full manufacturer's warranty.



DIXIE HI-FIDELITY PE-11
5600 Second St., N. E., Washington, D. C. 20011
Phone: 1-202-635-4900

Please rush me your FREE Audio Catalog and complete information. I understand there is no obligation.

Name _____
Address _____
City _____
State _____ Zip _____

Tips & Techniques


Tracing Foil Patterns

Etching simple printed-circuit boards from pc blanks can be very easy if you use masking tape to trace the resist pattern. Cover the copper surface of the blank completely with broad masking tape, taking care not to overlap the tape or to leave gaps between each strip. Then trace the outline of the foil pattern on the etching and drilling guide, using a sheet of carbon paper between the tape and the guide. Carefully cut out the tape from the areas to be etched using a sharp knife or razor blade. Then apply the resist using the "stencil" made from the masking tape. When the etch resist is dry, score it with a razor blade where it touches the tape. After the remaining tape is removed, the board is ready to be etched.

—Anthony Barake, Quebec, Canada


An Inexpensive Lamp Dimmer

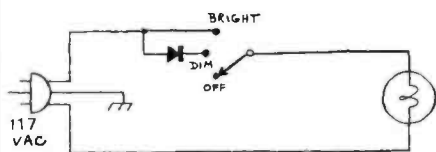If you want more than one light-level output from an incandescent bulb, this circuit is useful. What's more, it can lengthen bulb life considerably, while saving you money on electric bills and make expensive three-way bulbs and dimmers unnecessary. When the power switch is turned to the DIM position the diode allows only positive half-cycles of the ac power to flow



Battery Eliminator For VTVM'S

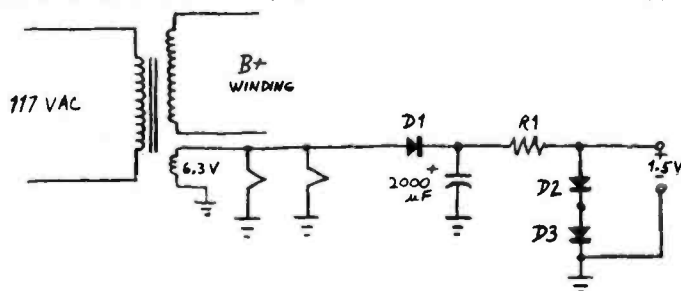If you're tired of replacing the 1.5-volt battery in your VTVM, here's a simple circuit that will eliminate the need for the cell. Diode D1 rectifies the 6.3-V ac filament supply, and a 2000-μF capacitor smooths out the dc. Since the forward voltage drop across a silicon diode is about 0.7 V, con-



through the bulb. In the BRIGHT position, the bulb behaves normally. Be sure to use an adequately rated diode (both PIV and forward current) for the power consumption (in watts) of the light bulb.

—Bill Drislane, Topsfield, MA

IC Breadboards

Breadboarding IC projects is a common practice and many commercial boards are available. However, an inexpensive substitute can easily be made in a pinch. Using 0.1-in. (0.25-cm) grid P-pattern board as a template, drill holes in a piece of perforated board to accept the pins of a 14- or 16-pin DIP. Wire the pins to two rows of spring clips (Vector T-32A or similar). Place extra clips along board edges for use as tie-points. Install push-in flea clips at each corner to elevate the board. Several assemblies can be secured to a larger board for combining subsystems. A strip of masking tape along the terminals permits markings for pin numbers and functions to be made.

—Raymond F. Arthur, New Kensington, PA

Home-Made Adapter Lets You Measure Dwell with Ohmmeter

To use an ohmmeter to measure a car's dwell time, a 1N34 or similar diode must be placed in series with the meter's "hot" test lead. The easiest way to install the diode is to house it in an adapter that can be quickly inserted into and removed from the test setup. This eliminates the need to modify the ohmmeter. To make the adapter, first slot a tip jack to accept the blade of a screwdriver. The next step is to enlarge the barrel of a standard short-barrelled test prod just enough to permit the tip jack to be screwed tightly into it. After prethreading the barrel, solder one lead of the diode to the tip jack (which lead depends on the polarities of the voltages at the meter's test jacks and the car's electrical ground). Use an insulated spacer and finish assembling the adapter.

—Paul E. Griffith

necting two of them in series from the dc supply to ground provides a voltage drop of nearly 1.5 volts. R1, a current-limiting resistor, is composed of two 68-ohm, 2-watt resistors in parallel. All diodes should be 500-mA, 50-PIV or greater units. The electrolytic capacitor ought to have a 15-WVDC rating.

—Donald Wallace, Appalachia, VA

Operation Assist

If you need information on outdated or rare equipment—a schematic, parts list, etc.—another reader might be able to assist. Simply send a postcard to Operation Assist, POPULAR ELECTRONICS, 1 Park Ave., New York, NY 10016. For those who can help readers, please respond directly to them. They'll appreciate it. (Only those items regarding equipment not available from normal sources are published.)

Citi-Phone Model Cd-5 CB transceiver. Tube layout, schematic, and/or service manual. Randy Venable, 2009 Princeton Ave., Bradenton, FL 33507.

United Scientific Laboratories Contact 23 CB transceiver. Schematic and/or service info. R. T. Henley, 139 Mardi Gras, El Paso, TX 79912.

Precision Model E-400 sweep generator, **Amp. Corp. of America** Model ACA-100DC PA amplifier, **Challenger Amp. Co.** Model CH30 PA amplifier. Schematics or manuals. Ray Gill, 3717 Tidewater Trail, Fredericksburg, VA 22401.

Tektronix Model 513D oscilloscope. Schematic and/or service manual. David Mason, 1117 Woodland Dr., Tallahassee, FL 32304.

RCA radios, Models K-80 (Chassis No. RC-415-D) and 812-K, chassis No. 7Y-14(?). **Truetone** radio Model D-727, chassis No. 175E (175EAW). Schematics. Also want source for old radio tubes and **Rider** Radio Schematic Books No. 1-14. Milton Obuch, 1308 N. 4th St., Sayre, OK 73662.

Cathedral-style radio, with "TATRO-A" stenciled on bottom. Circa 1925. Contains 2 #38 tubes, 1 #75, 1 #78, and 1 6A7. **Magnavox** Model 154D 114-ohm speaker. Made to operate off a Delco generator/storage battery power plant. Any restoration information. F. Keith Haywood, Box 537, Angier, NC 27501.

Scott all-wave receiver, serial T-499. Chrome plated, two tweeters and a woofer (electrodynamic), 4 2A3 output tubes, neon regulator with bayonet base, 2 5U4-type rectifiers. Schematic and/or servicing info. Technical Engineering Laboratories, 787 Mesa Way, Richmond, CA 94805.

Capital Model HP-875 tape deck. Parts lists, source(s), schematics. Vaughan Williams, 6356 DeSoto, Detroit, MI 48238.

Lancer Model LA 1010 stereo amplifier. One output transformer (FT-3083445-B 100 6932) needed or source for same. Robert Davenport, 51 Meander Lane, Levittown, NY 11756.

Precision Model 10-12 tube and battery tester with G-104 adapter. Need updated tube roller chart or source for same. Phillip Coulter, 2023 1/2 Wheaton Ave., Millville, NJ 08332.

E.H. Scott navy-type receiver, Model RCH 1czc-46209. Schematic and/or operator's manual. Randall Barbett, 36678 Suffolk Dr., Mt. Clemens, MI 48043.

WWII-vintage VLF receiver (15-600 kHz) Model CFT-46154 serial 649. Operator's manual, parts list, service info, and schematic needed. Tom Dycus, 1507 Katie NE, Albuquerque, NM 87110.

Muskat Model 72MPX10 FM/AM/Tape Player. Schematic and transformer needed. Sam Pope, Sam's TV Service, 717 5th St. SE, Hickory, NC 28601.

Analab 1120 oscilloscope type 700. Schematic diagram. Mihailo Repovic, 39 Pierce Rd., Watertown, MA 02172.

Monroe 820CRT calculator. Readout tube and schematic needed. Earl Leininger, Suite 500, Financial Center, 3443 N. Central Ave., Phoenix, AZ 85012.

Dumont Model 164-E oscilloscope. Schematic and/or service manual. Joseph Lipsky, Rte. 8, Box 264, Brooksville, FL 33512.

Advancetron Model 404A phase meter. User/service manuals and/or schematics. Wesley Kranitz, RR2, Box 823, Lot 357, Pompano Beach, FL 33067.

Superior Instruments Co. Model TD-55 tube tester. Accurate Instrument Co. Model 154 VOM. Service manuals and/or schematics. Frank Waldren, Box 13305, St. Louis, MO 63157.

Nippon Sound Co. AM/FM Stereo Serial No. 1105. Schematic. Richard Gillespie, 6147 Oakbank Dr., Azusa, CA 91702.

RCA CTC9N receiver with remote control CTP7A. Any service information on remote control receiver or transmitter CRK3A. Robert Brandenburg, 1400 Albany St., Apt. 2, Los Angeles, CA 90015.

FREE McIntosh CATALOG and FM DIRECTORY

Get all the newest and latest information on the new McIntosh Solid State equipment in the McIntosh catalog. In addition you will receive an FM station directory that covers all of North America.



MX 113

FM/FM STEREO - AM TUNER AND PREAMPLIFIER

SEND TODAY!

If you are in a hurry for your catalog please send the coupon to McIntosh. For non rush service send the Reader Service Card to the magazine. CIRCLE NO. 47 ON FREE INFORMATION CARD

McIntosh Laboratory, Inc.
East Side Station P.O. Box 96
Binghamton, N.Y. 13904
Dept. PE

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

Revolutionary New Wiring "Pencil" Makes

Interconnections in 1/3 the Time!

- Create Finished Wired Circuits in Hours, Not Days
- For Breadboarding, Prototypes and Production
- Interconnects Circuit Elements in Digital and Analog Circuits

Easy for anyone — just hook up your components using the insulated "solder thru" wire (your choice of blue, red, green or clear). Wire feeds off a replaceable spool thru the P173 tool body and out of a steel tip so fine it easily routes wire around even the smallest I.C. lead. A touch of the iron, with solder, completes the joint.


Available accessory items include P179WS Wire Spacers for neat routing, tenth-tenth Micro-Vectorboards®, circuit Padboards and frames, like the 3677-6 and 51X-1. Order a P173 Now! Supplied with two 250' spools of AWG solder thru wire (1 red, 1 green), complete instructions. **\$950**

At your Vector distributor \$950
Mail orders, add \$2 shipping and handling charge. California residents add 6% sales tax.

NOVEL AND USEFUL HOLIDAY GIFT IDEA!

Vector W P DIVISION
ELECTRONIC COMPANY, INC.
12460 Gladstone Ave. • Sylmar, CA 91342 • (213) 365-9661

need belts?

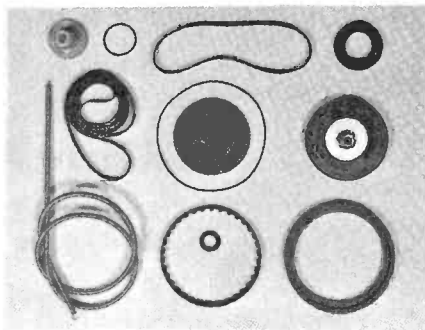


Standard and special belts and tires ready for immediate shipment — fit over 3,000 new and obsolete makes of tape recorders, projectors, dictating machines, video recorders, and turntables. Simplified cross reference system makes ordering easy with **one day service** on most items. Drive tires, wheels, phono idlers also listed. Call or write for **free catalog**. DEALER INQUIRIES INVITED.

PROJECTOR-RECORDER BELT CORP.

319 Whitewater St., Whitewater, WI 53190 — (414) 473-2151
CIRCLE NO. 51 ON FREE INFORMATION CARD

BE A LOCKSMITH

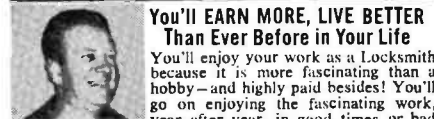

You'll EARN MORE, LIVE BETTER Than Ever Before in Your Life

You'll enjoy your work as a Locksmith because it is more fascinating than a hobby—and highly paid besides! You'll go on enjoying the fascinating work, year after year, in good times or bad because you'll be the man in demand in an evergrowing field offering big pay jobs, big profits as your own boss. What more could you ask!


Train at Home—Earn Extra \$\$\$\$ Right Away! All this can be yours FAST regardless of age, education, minor physical handicaps. Job enjoyment and earnings begin AT ONCE as you quickly, easily learn to CASH IN on all kinds of locksmithing jobs. All keys, locks, parts, picks, special tools and equipment come with the course at no extra charge. Licensed experts guide you to success.

Illustrated Book, Sample Lesson Pages FREE. Locksmithing Institute graduates now earning, enjoying life more everywhere. You, can, too. Coupon brings exciting facts from the school licensed by N. J. State Department of Ed., Accredited Member, Natl. Home Study Council. Approved for Veterans Training.

LOCKSMITHING INSTITUTE
Div. Technical Home Study Schools
Dept. 1473-115 Little Falls, N. J. 07424

LOCKSMITHING INSTITUTE, Dept. 1473-115
Div. Technical Home Study Schools
Little Falls, New Jersey 07424 Est. 1948
Please send FREE illustrated Book—"Your Big Opportunities in Locksmithing," complete Equipment folder and sample lesson pages—FREE of all obligation—(no salesman will call).

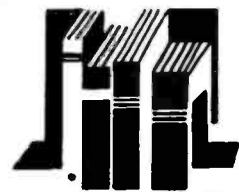Name.....
Address.....
City/State/Zip.....
 Check here if Eligible for Veteran Training
CIRCLE NO. 46 ON FREE INFORMATION CARD



Electronics Library

TOWERS' INTERNATIONAL TRANSISTOR SELECTOR

by T.D. Towers

Over 10,000 transistor types are covered, with specifics on ratings, characteristics, case details, terminal indentities, applications, and manufacturers. Substitution equivalents are given for both U.S. and European transistors. Some Japanese devices are also included. The major portion of the book is arranged in tabular form. Appendices contain explanatory notes, package diagrams, case outlines, manufacturer's house codes, and a list of manufacturers.

Published by Tab Books, Blue Ridge Summit, PA 17214. 138 pages. \$4.95 soft cover.

LOW- AND MEDIUM-FREQUENCY SCRAPBOOK

by Ken Cornell, W2IMB

Produced for the experimenter in communications below 1600 kHz, this book covers receivers, transmitters, coils and coil winding techniques, antennas and FCC regulations. Among its features is information on the nonlicensed bands open to the public, from 160 to 190 kHz, and 510 to 1600 kHz (the AM broadcast band). Power limitations, antenna length, and transmitter design are discussed within the context of government standards. An addendum includes a power mains filter, an audio filter, and an IC crystal-controlled transmitter. FCC rules covering non-licensed communications are reproduced as an appendix.

Published by Ken Cornell, 225 Baltimore Ave., Pt. Pleasant Beach, NJ 08742. 105 pages (8 1/2" x 11"). \$4.75, soft cover.

COMPUTER ALGORITHMS AND FLOWCHARTING

by G. and J. Silver

This work introduces the reader to the special procedures that must be used in setting up computer problems. It concentrates on the logical enumeration and organization of a particular task. This sets the problem in a form (algorithm) that a digital computer can handle. Emphasis is also placed on coding, keypunching and keyboarding, running and debugging, and documentation. The flowchart, or "computer roadmap," is introduced in accordance with the symbols and definitions established by the American National Standards Institute. Many programming applications are included.

Published by McGraw-Hill Book Co., 1221 Ave. of the Americas, New York, NY 10020. 170 pages (8 1/2" x 11"). \$6.96 soft cover.

HAM CB SWL

they come through LOUD AND CLEAR in the all-new 1976 COMMUNICATIONS HANDBOOK

Here is everything you want to know need to know about Citizens' Band, Amateur Radio, Shortwave Listening.



DON'T TURN A DIAL. In fact don't even buy a dial or anything else until you've checked out the 1976 Communications Handbook. Whatever your radio specialty—whether you're an old hand or just getting started—this vital "how-to" guide will help you get greater value, greater enjoyment out of every minute you spend with your equipment.

The all-new 1976 COMMUNICATIONS HANDBOOK is scheduled to go on sale nationally November 20, 1975

YOU CAN RESERVE YOUR COPY NOW AT THE SPECIAL PRE-PUBLICATION PRICE OF ONLY \$1.00 POSTPAID.

Regular newsstand price is \$1.50, mail order \$1.85.

So to make sure you come through "Loud and Clear" in 1976...


RESERVE YOUR COPY NOW AND SAVE WITH THIS SPECIAL PRE-PUBLICATION OFFER AVAILABLE TO READERS OF POPULAR ELECTRONICS MAGAZINE ONLY.

PRE-PUBLICATION RESERVATION FORM

Communications Handbook PE-115
Ziff-Davis Consumer Service Division
595 Broadway, New York, N.Y. 10012

Enclosed is \$1. Please reserve my copy of the 1976 Communications Handbook at the special prepublication price to be mailed to me on or before November 20, 1975. (Residents of Cal., Col., Fla., Ill., Mich., Mo., N.Y. State, D. C. and Tex. add applicable sales tax.) OUTSIDE U. S. A. \$2 (regular mail order price \$3).

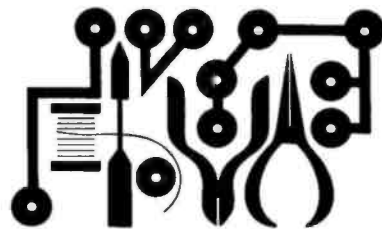Print Name.....
Address.....
City.....
State..... Zip.....



Experimenter's Corner

By Forrest M. Mims

THE LIGHT-ACTIVATED SCR

THE SCR has been around for some time, and most of us have used them in a variety of circuits. There's one SCR, however, that doesn't get much experimenter use. It's the so-called LASCER (Light Activated Silicon Controlled Rectifier).

Lots of the parts dealers now sell LASCER's at bargain-basement prices. Depending on the voltage rating, you can buy good quality units at prices less than 50¢ to about \$1.75. Not bad for a component with lots of practical uses.

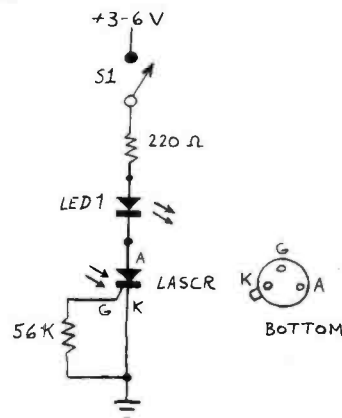


Fig. 1. LASCER test rig.

You can make a simple LASCER test rig in a couple of minutes with an LED, a couple of resistors, a switch, and two flashlight cells. Connect the parts as shown in Fig. 1 and you're in business. First close S1. Normally the LASCER will be off, but an increase in the light level at its sensitive surface will generate a photocurrent which will turn the

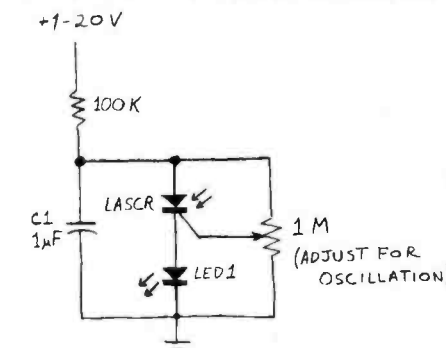


Fig. 2. Relaxation oscillator.

device on. The resulting current will light up the LED. Open S1 to turn the LASCER off.

Figure 2 is a neat little circuit in which the LASCER operates as a low-voltage relaxation oscillator. Capacitor C1 charges to the supply voltage through the 100,000-ohm resistor. The potentiometer is a voltage divider which feeds some of the charge on C1 to the LASCER's gate. When its turn-on voltage is reached, the LASCER switches on and dumps the charge on C1 through the LED. Since C1 is now discharged, the LASCER turns off, C1 begins charging again, and the cycle repeats.

I've operated this circuit from slightly less than one volt! You may have to adjust the light level at the LASCER with a flashlight to start the oscillator at very low voltages.

Like any SCR, the LASCER is a four-layer, three-junction device whose structure is shown in Fig. 3. The anode and gate connections form two terminals of a pnp phototransistor. There is no base lead, so you cannot use a conventional SCR as a transistor. But you can use the anode-gate leads of a LASCER as a pnp phototransistor. To do this, hook up the test circuit in Fig. 4. Toss some light on the LASCER and you've got an instant light meter. I measured 10 µA forward current from a typical LASCER basking in the rays from a #222 lamp 50 mm away.

So far we've just been tinkering around so now let's get down to business with a circuit that really exploits the versatility of the LASCER. The circuit in Fig. 5 (a slave flash) is ideal for supplying filler light for flash photos. If photography isn't your thing, you might want to use the circuit for a novelty device or as a demonstration of how a relatively puny pulse of light can trigger an eye-dazzling flash from a powerful xenon lamp.

The circuit is a conventional strobe, but don't let its simplicity deceive you! Capacitor C1 will be charged to a voltage high enough to vaporize a screwdriver tip, so use care when building the circuit. Mount all the parts on a piece of perf board, use insulated hookup wire, and cover all

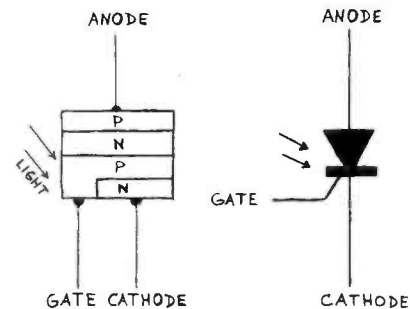


Fig. 3. Structure of LASCER.

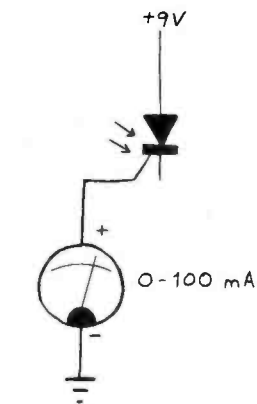


Fig. 4. Light-meter circuit.

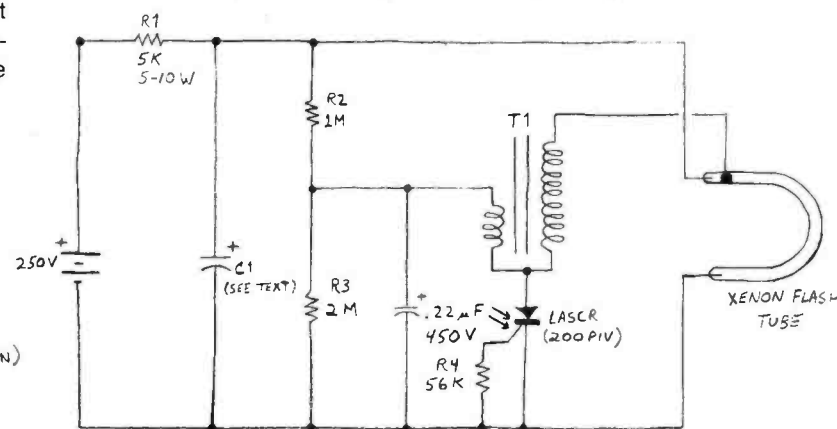


Fig. 5. Slave flash for photography.


THE ALPHA PROFITMETER

AUTO ZERO/POLARITY 3½ DIGIT MULTIMETER KIT

WITH BRIGHT RED LED DISPLAY



ON THE SERVICE BENCH

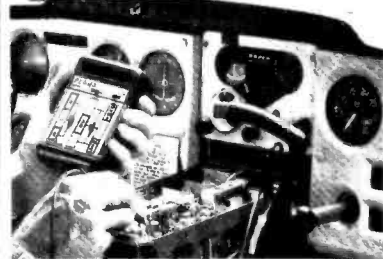

IN THE FIELD

WHEREVER AND WHATEVER THE JOB, YOU'LL NEED ITS BATTERY OPERATED PORTABILITY AND ITS HIGH ACCURACY: .1% DCV & OHMS, 1% CURRENT AND ACV.

\$79.95 +2.95 P&H
Less test leads & batteries



ALPHA ELECTRONICS
DEPT 1 PO BOX 1005
MERRITT ISLAND, FLA. 32952
TO ORDER OR FOR INFORMATION
CALL TOLL FREE
800 - 327 - 2084

SPECIAL OFFER: "PROFIT" AND SAVE \$40.00

NOW, BUY THE PROFITMETER AND GET OUR RALLY IV STOPWATCH KIT FOR \$29.95 OR OUR LED-1 OR DD12/24 (HR/MN/SEC/DATE) DIGITAL WRISTWATCH KIT FOR ONLY \$9.95 WITH THIS AD.

CIRCLE NO. 10 ON FREE INFORMATION CARD

UNBELIEVABLE!

FREQUENCY COUNTER KIT ONLY \$69.95!



FOR: HAMS, CBers, SERVICE TECHS, EXPERIMENTERS!

- 6 DIGITS
- TO 30 MHZ (HAM & CB Bands)
- 100HZ READOUT
- CRYSTAL TIMEBASE
- 1 HZ OPTION 9.95
- M CHG/B.AMER OK
- Wired & Tested 89.95
- ADD \$2.00 Shipping/Handling

HUFCO PO BOX 357 PROVO UT 84601
(801) 224-3355

CIRCLE NO. 36 ON FREE INFORMATION CARD

exposed leads and junctions with sleeving and corona dope for safety. Then house the entire circuit in an insulated enclosure with an aperture for the flash tube.

You can power the circuit with a 300-volt dry battery or a combination of batteries which gives 250 to 300 volts. Buy your battery from a dealer who sells lots of high-voltage batteries to make sure you get a fresh one.

Use an electrolytic capacitor for C1. Several hundred microfarads will give you plenty of light, and you can probably get by with a lot less than that. Use a 450-volt unit and be sure to observe polarity. Use any standard trigger transformer for T1 and any xenon flash tube.

Incidentally, a good source for parts for this project is the cheap flash units originally designed for discontinued Instamatic™ cameras. Several surplus dealers sell these units for about \$10. You might be able to pick up some trade-in flash units at camera stores for a few bucks.

Figure 6 is a scope photo of several half-millisecond flashes from a LASCR triggered slave flash. It's fairly

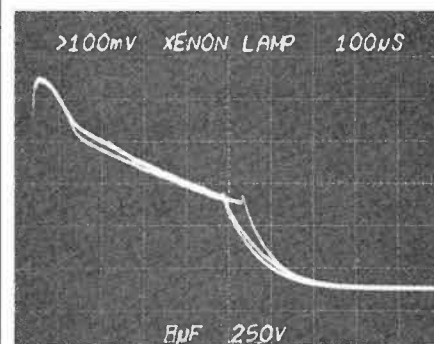


Fig. 6. Scope photo of triggered slave flash.

impressive when you can trigger a brilliant burst of light with just a little penlight.

You can make the LASCR immune to ordinary lights by adding a 1-henry inductor across R4. The choke will appear as a short circuit to steady-state and slow transients, keeping the LASCR off. But a very fast pulse from a master flash unit will bypass the choke (which will appear as an open circuit) and turn on the LASCR.

These are just a few uses for the remarkably versatile and often overlooked LASCR. Pick up a few and try them out. You'll probably come up with some applications of your own.

POPULAR ELECTRONICS

FREE INFORMATION:

Use only one card per person

POPULAR ELECTRONICS PE11753
Use only one card per person.
NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

(Zip Code must be included to insure delivery.) (Void after Jan. 31, 1976)

a. Do you ordinarily use this reader service card for:

(Circle either or both numbers)

1) Immediate Need 2) Future Reference

Please send me 12 issues of Popular Electronics for \$4.89 and bill me.

- | | | | | | | | | | | | | | | |
|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|
| 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 |
| 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 | 26 | 27 | 28 | 29 | 30 |
| 31 | 32 | 33 | 34 | 35 | 36 | 37 | 38 | 39 | 40 | 41 | 42 | 43 | 44 | 45 |
| 46 | 47 | 48 | 49 | 50 | 51 | 52 | 53 | 54 | 55 | 56 | 57 | 58 | 59 | 60 |
| 61 | 62 | 63 | 64 | 65 | 66 | 67 | 68 | 69 | 70 | 71 | 72 | 73 | 74 | 75 |
| 76 | 77 | 78 | 79 | 80 | 81 | 82 | 83 | 84 | 85 | 86 | 87 | 88 | 89 | 90 |

POPULAR ELECTRONICS PE11752
Use only one card per person.
NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

(Zip Code must be included to insure delivery.) (Void after Jan. 31, 1976)

a. Do you ordinarily use this reader service card for:

(Circle either or both numbers)

1) Immediate Need 2) Future Reference

Please send me 12 issues of Popular Electronics for \$4.89 and bill me.

- | | | | | | | | | | | | | | | |
|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|
| 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 |
| 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 | 26 | 27 | 28 | 29 | 30 |
| 31 | 32 | 33 | 34 | 35 | 36 | 37 | 38 | 39 | 40 | 41 | 42 | 43 | 44 | 45 |
| 46 | 47 | 48 | 49 | 50 | 51 | 52 | 53 | 54 | 55 | 56 | 57 | 58 | 59 | 60 |
| 61 | 62 | 63 | 64 | 65 | 66 | 67 | 68 | 69 | 70 | 71 | 72 | 73 | 74 | 75 |
| 76 | 77 | 78 | 79 | 80 | 81 | 82 | 83 | 84 | 85 | 86 | 87 | 88 | 89 | 90 |

POPULAR ELECTRONICS PE11751
Use only one card per person.
NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

(Zip Code must be included to insure delivery.) (Void after Jan. 31, 1976)

a. Do you ordinarily use this reader service card for:

(Circle either or both numbers)

1) Immediate Need 2) Future Reference

Please send me 12 issues of Popular Electronics for \$4.89 and bill me.

- | | | | | | | | | | | | | | | |
|----|----|----|----|----|----|----|----|----|----|----|----|----|----|----|
| 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 |
| 16 | 17 | 18 | 19 | 20 | 21 | 22 | 23 | 24 | 25 | 26 | 27 | 28 | 29 | 30 |
| 31 | 32 | 33 | 34 | 35 | 36 | 37 | 38 | 39 | 40 | 41 | 42 | 43 | 44 | 45 |
| 46 | 47 | 48 | 49 | 50 | 51 | 52 | 53 | 54 | 55 | 56 | 57 | 58 | 59 | 60 |
| 61 | 62 | 63 | 64 | 65 | 66 | 67 | 68 | 69 | 70 | 71 | 72 | 73 | 74 | 75 |
| 76 | 77 | 78 | 79 | 80 | 81 | 82 | 83 | 84 | 85 | 86 | 87 | 88 | 89 | 90 |

Learning more about a product that's advertised or mentioned in an article in this month's issue is as simple as one, two, three. And absolutely free.

1

Print or type your name and address on the attached, postage-paid card. Use only one card per person.

2

Circle the number(s) on the card that correspond to the number(s) at the bottom of the advertisement or article for which you want more information.

(Key numbers for advertised products also appear in the Advertisers' Index.)

3

Simply mail the postage-paid card.

FREE INFORMATION:

HAM SWL

they come through LOUD AND CLEAR in the all-new 1976 COMMUNICATIONS HANDBOOK

Here is everything you want to know — need to know — about Citizens' Band, Amateur Radio, Shortwave Listening.

DON'T TURN A DIAL. In fact don't even buy a dial or anything else until you've checked out the 1976 Communications Handbook. Whatever your radio specialty — whether you're an old hand or just getting started — this vital "how-to" guide will help you get greater value, greater enjoyment out of every minute you spend with your equipment.

The all-new 1976 COMMUNICATIONS HANDBOOK is scheduled to go on sale nationally November 20, 1975.

YOU CAN RESERVE YOUR COPY NOW AT THE SPECIAL PRE-PUBLICATION PRICE OF ONLY \$1.00 POSTPAID.



Regular newsstand price is \$1.50, mail order \$1.85.

So to make sure you come through "Loud and Clear" in 1976... RESERVE YOUR COPY NOW AND SAVE WITH THIS SPECIAL PRE-PUBLICATION OFFER AVAILABLE TO READERS OF POPULAR ELECTRONICS MAGAZINE ONLY.

HERE'S HOW TO ORDER:

Send your remittance in the amount of \$1.00 to Communications Handbook, Consumer Service Division, Dept. PV, 595 Broadway, N.Y., N.Y. 10012. (Residents of Calif., Col., Fla., Ill., Mich., Mo., N.Y. State, D. C. and Tex. add applicable sales tax.) Outside U. S. A. \$2.00 (regular price \$3.00). Your copy will be mailed to you from first-off-the-press copies on or before November 20, 1975.

First Class Permit No. 217 Clinton, Iowa

BUSINESS REPLY MAIL

No postage necessary if mailed in the United States

POSTAGE WILL BE PAID BY

Popular Electronics

P.O. Box 2905 Clinton, Iowa 52732

First Class Permit No. 217 Clinton, Iowa

BUSINESS REPLY MAIL

No postage necessary if mailed in the United States

POSTAGE WILL BE PAID BY

Popular Electronics

P.O. Box 2905 Clinton, Iowa 52732

First Class Permit No. 217 Clinton, Iowa

BUSINESS REPLY MAIL

No postage necessary if mailed in the United States

POSTAGE WILL BE PAID BY

Popular Electronics

P.O. Box 2905 Clinton, Iowa 52732

Wow! INCREDIBLE PRICES

BUY ANY 10 TAKE 15%
BUY 100 TAKE 25%

SN7400	\$.16	SN7462	\$.22	SN74122	.48
SN7401	.16	SN7470	.29	SN74123	.85
SN7402	.16	SN7471	.49	SN74125	.59
SN7403	.16	SN7472	.29	SN74126	.59
SN7404	.19	SN7473	.36	SN74132	1.75
SN7405	.19	SN7474	.36	SN74140	2.10
SN7406	.35	SN7475	.59	SN74145	1.05
SN7407	.35	SN7476	.39	SN74148	2.25
SN7408	.19	SN7478	.79	SN74150	.98
SN7409	.19	SN7480	.52	SN74151	.75
SN7410	.16	SN7481	.59	SN74153	.99
SN7411	.25	SN7482	.89	SN74154	1.35
SN7413	.59	SN7483	.25	SN74155	.95
SN7414	1.65	SN7485	1.25	SN74156	.95
SN7416	.34	SN7486	.37	SN74157	.95
SN7417	.34	SN7488	3.95	SN74158	.95
SN7420	.16	SN7489	2.45	SN74159	.95
SN7421	.22	SN7490	.59	SN74161	1.25
SN7423	.29	SN7491	.59	SN74163	1.35
SN7425	.29	SN7492	.59	SN74164	1.50
SN7426	.25	SN7493	.59	SN74173	1.45
SN7427	.29	SN7494	.95	SN74166	1.50
SN7430	.16	SN7495	.79	SN74174	1.39
SN7432	.25	SN7496	.79	SN74175	1.30
SN7433	.49	SN74100	1.40	SN74176	1.20
SN7437	.34	SN74104	4.40	SN74177	1.20
SN7438	.34	SN74105	.44	SN74181	1.40
SN7440	.16	SN74106	.52	SN74182	.74
SN7441	1.00	SN74107	.44	SN74184	1.98
SN7442	.70	SN74108	.89	SN74185	1.98
SN7444	1.25	SN74112	.89	SN74190	1.40
SN7445	.89	SN74113	.89	SN74191	1.40
SN7446	1.15	SN74114	.89	SN74192	.25
SN7447	.99	SN74121	.49	SN74193	1.25
SN7448	.99			SN74194	1.20
SN7450	.16			SN74195	.85
SN7451	.17			SN74196	1.80
SN7452	.17			SN74197	9.00
SN7453	.17			SN74199	1.75
SN7454	.17			SN74200	4.95
SN7455	.22				
SN7460	.17				

POSTAGE STAMP MOBILE MIKE SPKR \$1.98
This unit is not advertised anywhere! Made for Motorola Communications at the original cost of \$4.50 each (for insertion in their Walkie Talkie Program). It's a 60-ohm imp MIKE. Includes a "A" cell nicad battery hooked up to give you 6-volts for all types of energy uses. The best battery made. Rechargeable.

INDUSTRIAL SPEED CONTROL \$4.95
A \$80 item from G.E. Model 533A (made for Xerox) that controls home, shop and industrial lighting tool! A very elaborate circuit for controlling many electrical and electronic devices. Easily controls speeds of electric drills, brush type motors, etc. 115vac, rated at 1100 watts. With variable speed or dimming control in heavy-duty aluminum case. 3 x 2 3/4 x 2. With diagram and hookups.

PROGRAMMABLE TIMER DELAYS UP TO 5 DAYS \$4.95
XR-2340 14-pin DIP. Consists of a self-contained 8-bit programmable binary counter, oscillator, and controlled flip-flop. 4V to 16V supply. Temp. and power supply stability outperforms all others. Power only 12 mW. @ 4V. Programmable capability 256 steps. 8 separate outputs, one for each counter.

'BEEPER' AND 'DATER' CLOCK ON THE CHIPS
MK50250 BEEPER \$ 8.50
Imagine a chip (MK50250) of alarm, date of the month and direct drive to LED readouts. Both require minimum current drain and voltages, for either 4 to 6 LED readouts, 12 or 24 hours. AM and PM.
CT7001 Alarm and Date... \$6.95

Fabulous POLY PAKS BARREL SALE
25 BARRELS PURCHASED FOR THIS SALE! BUY 'EM FROM THE "BARREL" AND SAVE!

BARREL KIT #1 75 for SN7400 DIP IC'S \$1.98	BARREL KIT #2 75 for SN7401 DIP IC'S \$1.98	BARREL KIT #3 100 for SWITCHING DIODES \$1.98	BARREL KIT #4 "4000" RECTIFIERS 100 for \$1.98	BARREL KIT #5 40 for SCRS, TRIACS, \$1.98	BARREL KIT #6 40 for QUADRACS \$1.98	BARREL KIT #7 25 for \$1.98	BARREL KIT #8 40 for \$1.98	BARREL KIT #9 40 for \$1.98	BARREL KIT #10 40 for \$1.98	BARREL KIT #11 40 for \$1.98	BARREL KIT #12 40 for \$1.98	BARREL KIT #13 40 for \$1.98	BARREL KIT #14 40 for \$1.98	BARREL KIT #15 40 for \$1.98	BARREL KIT #16 40 for \$1.98	BARREL KIT #17 40 for \$1.98	BARREL KIT #18 40 for \$1.98	BARREL KIT #19 40 for \$1.98	BARREL KIT #20 40 for \$1.98	BARREL KIT #21 40 for \$1.98	BARREL KIT #22 40 for \$1.98	BARREL KIT #23 40 for \$1.98	BARREL KIT #24 40 for \$1.98	BARREL KIT #25 40 for \$1.98
---	---	---	--	---	--------------------------------------	-----------------------------	-----------------------------	-----------------------------	------------------------------	------------------------------	------------------------------	------------------------------	------------------------------	------------------------------	------------------------------	------------------------------	------------------------------	------------------------------	------------------------------	------------------------------	------------------------------	------------------------------	------------------------------	------------------------------

9-FUNCTION, 8-DIGIT MEMORY CALCULATOR KIT
It's the easiest multi-function kit today!
KIT INCLUDES: case, 22-key keyboard kit, ON-OFF switch (part of keyboard) PC board, driver and memory calculator chips, 8-digit "bubble" magnifier LED array, array cable, AC adapter jack & wires, battery case, 6 battery card display, instruction and pictorial step-by-step construction booklet. AC/DC too!

"QUAD" TAPE DECK BY TELETYPE PACKARD-BELL
Other features: 4-program indicator lights, automatic or manual program change, push-button channel selector switch, built-in triggering switch that enables you to automatically use 8-track or quad tapes; heavy-duty flywheel for WOW and FLUTTER PROOF sound; flapping front panel tape door mounting front panel flange. Heavy duty cool-proof 115 VAC motor. Requires external 12 VDC supply, for all electronics. Includes schematic, hookups, all cables. Size: 6 1/2 x 3 1/2". IT'S READY TO GO!

4 1/2 DIGIT DIGITAL VOLTMETER DVM CHIP \$14.95
Type MM5330 by National utilizes P channel low-threshold enhancement mode devices and ion implanted depletion mode devices. Provides logic circuit for 4 1/2 digit DVM. To 400 KHz operation. TTL compatible. With instruction sheets and diagram on "how-to-build a 4 1/2 digit DVM". Ideal with our Litronix 1/2" single, 1 1/2" and dual digits. 16-pin DIP.

4-DIGIT AM-PM FLUORESCENT CLOCK PANEL "PANEL OPTICS" \$9.99
YOU ASKED FOR IT! Found only at Poly Paks at this low price! It's ONLY 1 3/4 x 1 3/16 x 3/8" deep panel. Designed especially for our MM-5316 fluorescent driving clock chip. Indicates 4-digits, AM, PM, pulsating second indicator, requires minimum of parts to build. Color: BLUE-GREEN; you can use RED or GREEN filters. Character height: 0.6". Filament voltage is 1.75 VAC or DC @ 160 ma. Anode voltage 26V @ 250 microamps per segment. With spec sheets, clock construction diagrams, P.C. board layouts, specs. A DIGITAL CLOCK BUILDER'S SPECIAL.

NATIONAL LM-340T VR'S \$1.75 Each
Type Volts Sale
LM-340-05T 5V
LM-340-06T 6V
LM-340-12T 12V
LM-340-15T 15V
LM-340-18T 18V
LM-340-24T 24V

MICROPROCESSORS! ROMS! RAMS! MEMORIES!
8008 Microprocessor \$29.95
8080 Super 8080 \$50.00
2102 1024 Static RAM 3.95
1101 256 bit RAM 1.50
1103 1024 bit RAM 2.95
NMS260 1024 RAM 2.95
NMS262 2048 bit RAM 6.50
2513 Character generator 12.50
NMS203Q Erasable PROM 14.95
NMS202Q Erasable PROM 14.95
1702A Erasable PROM 19.95
8223 Programmable ROM 2.95

DOUBLE MEMORY Percent, Constant, Display Restore \$16.95
4-Function Arithmetic 22 KEYS!

RAYTHEON-RCA NATIONAL SIGNETICS LINEAR IC'S

Type	Price	Type	Price
LM300	\$.69	LM562	2.50
LM301	.29	LM565	2.50
LM302	.69	LM566	2.65
LM304	.79	LM567	2.50
LM305	.89	LM703	.49
LM308	1.05	LM703M	.41
LM309H	1.05	LM709	.25
LM309K	1.50	LM710	.29
LM310	1.10	LM711	.29
LM311	.99	LM723	.61
LM318	1.75	LM733	.29
LM319	1.75	LM741	1.75
LM320*	1.25	LM741CV	.31
LM322	1.75	LM747(D)	.69
LM324 (Q)	1.85	LM748	.35
LM339 (Q)	2.45	LM753	1.79
LM340*	1.75	LM1458(D)	.59
LM341-T*	1.75	LM1496	.99
LM350	.69	LM1800	3.50
LM370	1.05	CA3026	.59
LM371	1.05	CA3045	.59
LM373	1.95	CA3054	.59
LM374	1.95	CA3065	.59
LM376	.49	CA3082	.59
LM377	2.50	CA3190	.49
LM380-8	1.10	RC4130(Q)	1.95
LM380	1.20	RC4195	2.10
LM381	1.69	LM4250C	2.10
LM382	1.69	LM7520	.59
LM383	1.95	LM7521	.59
LM384	1.95	LM7522	.59
LM385	.88	LM7523	.59
LM556	2.50	LM7524	.59
LM558(D)	.69	LM7525	.59
LM560	2.50	LM7528	.59
LM561	2.50	LM7529	.59
		LM7535	.59

LED Revolution! 5 for \$1
MONSANTO! XCITON! LITRONIX! OPCOA!

.340x.260	.240x.200
Jumbo Red	Medium Red
Green	Yellow
Yellow	Amber
Amber	Clear
Clear	
Micro Red	.210x.125 Yellow
Micro (Axial) MV-50 style	
MV-50 Clear	10 for \$1.
MV-55 Red	6 for \$1.

7-SEGMENT READOUT SALE!
* Up to 20 mls per seg. at 5V.
* All fit into 14-pin IC socket.

Type	Size	Color	Sale	3 for
MAN-1	.27	Red	\$2.50	\$6.00
MAN-3MA	.12	Red	.69	2.00
MAN-4AB	.27	Red	1.95	5.00
MAN-5	.27	Green	1.50	4.00
MAN-7	.27	Red	1.00	2.50
MAN-8	.27	Yellow	1.50	4.00

LITRONIX "JUMBO'S"
* Singles size: 1 x 3/4 x 5/16
* Duals size: .8 x .9 x .29
* 7-Segment, 25-mils per segment


Type	Size	Color	Sale	3 for
721D	.5	Red	\$5.95	\$15.00
727F	.5	Red	3.95	15.00
746F	.6	Red	3.95	11.00
747	.6	Red	3.95	11.00

POLY PAKS
P.O. BOX 942E, LYNNFIELD, MASS. 01940

NEW KITS! NEW KITS!

JAMES ELECTRONICS
P.O. BOX 822 BELMONT, CALIFORNIA 94002
(415) 592-8097

DIGITAL VOLTMETER

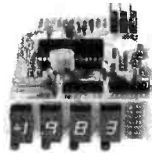

GENERAL DESCRIPTION

The JE901 is a three and one half digit, auto polarity digital voltmeter. In a kit form, it features several options not available in any commercial digital voltmeter. Its low cost is, perhaps, the most important feature, which is achieved by offering it in a kit form. A kit allows the unit to be used by small OEM's where cost effectiveness is an important factor, and by the hobbyist who has to be careful with cost. The unit also features on-card regulator, allowing it to be powered off a single plus and minus fifteen volt, regulated power supply. The unit has a small size of three inches wide, three and three quarters all an inch length, and one and a quarter inch high.

\$39.95 Per Kit printed circuit board

LOGIC PROBE

The Logic Probe is a unit which is for the most part indispensable in trouble shooting logic families: TTL, DTL, RTL, CMOS. It derives the power it needs to operate directly off of the circuit under test, drawing a scant 10 mA max. It uses a MAN3 readout to indicate any of the following states by these symbols: (H) - 1 (LOW) - 0 (PULSE) - P. The Probe can detect high frequency pulses to 45 MHz. It can't be used at MOS levels or circuit damage will result.



printed circuit board
\$9.95 Per Kit

MINI POWER SUPPLIES

These power supplies offer small size, with a wide choice of voltage outputs. They are all capable of delivering 300mA and have dimensions of 1" x 1" x 3". The voltages available are -5V, -5V, +6V, -6V, +12V, -12V. All of these units easily assemble in less than a half an hour, because of the fiberglass printed circuit board construction. Please specify voltage when ordering.


\$9.95 per kit

LOW COST DIGITAL CLOCK KIT

Other companies have offered a low cost digital clock kit, but do not offer important extras such as, printed circuit boards, power supplies cases, etc. We at James are doing just the opposite by offering a complete clock kit, that includes everything down to the line cord. This kit uses .25" FND 70 displays, for HOURS, MINUTES, and SECONDS, in conjunction with the MM5314 clock chip. The printed circuit board is of high quality fiberglass, which is plated. The case is a 6 x 1 1/2 x 1 walnut case with a plexi-glass front, and is similar to the one in our TV WALL Digital clock. It is available without the case for \$16.95.

\$19.95 per kit.

ELECTRONIC ROULETTE

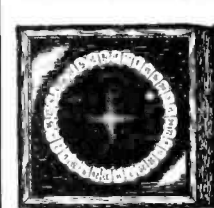

Complete kit with all components case and transformer.

8" x 8" x 1"
A 56 page book on the facts of Roulette included.
\$29.95 Per Kit

ELECTRONIC CRAPS



Complete kit with all components case and transformer.

6 1/2" x 3 1/2" x 1"
A 56 page book on the facts of Craps included.
\$19.95 Per Kit

Satisfaction Guaranteed. \$5.00 Min. Order. U.S. Funds. Add \$1.25 for Postage — Write for FREE 1975 Catalog California Residents — Add 6% Sales Tax

JAMES
P.O. BOX 822, BELMONT, CA. 94002
PHONE ORDERS — (415) 592-8097

CIRCLE NO. 40 ON FREE INFORMATION CARD

ELECTRONIC parts, low prices, free flyer: DARTEK ELECTRONICS, Box 2460, Dartmouth, Nova Scotia, Canada. U.S. Inquiries.

SURPRISE! SURPRISE! Digital Piano Tuning Device tunes musical instruments Accurately! Perfectly! Inexpensively! Construction-Instruction-Plans Complete \$12.95 Airmailed Postpaid! Moonlighting quickly repays \$40 electronics investment! GBS, Box 100P, Green Bank, West Virginia 24944.

PYROTECHNICAL chemicals, casings, fuse, tools, literature, supplies. Catalog \$1.00, with samples — \$2.00. Westech, Loqan, Utah 84321.

FREE giant bargain electronic catalog listing thousands of components, tubes, transistors, IC's, Kits, test equipment. EDLIE'S, 2700-PI Hempstead Tpke., Levittown, N.Y. 11756.

CONSTRUCTION PROJECTS: Laser, \$2.00. TV Camera, \$3.95. Catalog, Technologic, Box 5262, Orchard Lake, Michigan 48033.

CARBON FILM RESISTORS. Brand new as low as 2-1/4 cents. FREE samples and specifications. COMPONENTS CENTER—PE, Box 134, New York, NY 10038.

ALPHA BRAINWAVE MONITOR—New from EICO. Model BW300 Kit, \$34.95; Wired, \$59.95 Postpaid. Send check or money order. M&K Electronic Corp., 135-33 Northern Blvd., Flushing, N.Y. 11354.

wanted Citizens Band
DEALER-DISTRIBUTORS
Send this ad with Letterhead to:
PAL ELECTRONICS CO.
2962 W. WELDON - PHOENIX, ARIZ. 85017

FOR A New Electronic Experience, learn to control your brainwaves. Aquarius Electronics, Box 96ZE, Albion, CA 95410.

TEST EQUIPMENT—DISCOUNT PRICES: B&K, Sencore, Leader, EICO, Lectrotech. M&K Electronic Corp., 135-33 Northern Blvd., Flushing, N. Y. 11354.

GODBOUNT BOX 2355
OAKLAND AIRPORT, CA 94614
REAL 16 BIT PARALLEL MICROPROCESSOR. 40 PIN DIP, 45 CLASSES OF INSTRUCTIONS. SUPPLIED WITH INTER-FACE CHIPS (TTL COMPATIBLE). DATA PACKET: PAGES OF DETAILED INFO ON CHIP ITSELF, SYSTEM ORGANIZATION, SOFTWARE, MORE. A COMPLETE PACE REFERENCE.
PACE \$125 DATA PACKET \$2.50 ONLY.
OEM note: We aren't set up to handle OEM orders; call your NATIONAL distributor or sales office.
SPECIAL! 2102 RAM \$1.95 Fast; 750 ns or less

"Electronic Projects for Musicians" - \$6.95 + shpg
CRAIG ANDERTON'S BOOK TELLS YOU HOW TO BUILD 19 MUSICAL PROJECTS, EVEN IF YOU HAVEN'T BUILT ANYTHING BEFORE. INCLUDES 4 CHAPTERS ON BASIC ELECTRONICS, RECORDING THAT DEMONSTRATES THE PROJECT SOUNDS, & FORWARD BY JOE WALSH. PROJECTS INCLUDE: PREAMP, RING MODULATOR, FILTERS, MINIAMP, HEADPHONE AMP, FUZZES, COMPRESSOR, EXPANDABLE MIXER, MUCH MORE. PRACTICAL, UNDERSTANDABLE, READABLE: THE IDEAL PRIMER FOR MUSIC/ELECTRONICS ENTHUSIASTS, REGARDLESS OF THEIR AGE OR EXPERIENCE. PS: WE ALSO SUPPLY PARTS KITS FOR ALL 19 PROJECTS.
Terms: Cal res add tax. No COD. Call (415) 357-7007 for Mastercharge® or BankAmericard® orders

ALTAIR OWNERS—we have accessory boards, components, memories, etc. Boards, IC Kits for most popular minis. Mini Micro Mart, 1618 James, Syracuse, NY 13203.

AUDIO PROGRAM CONTROL CENTER \$14.95 PPD. USA
10 inputs, 4 outputs. Switch TV, Short-Wave, Ham, FM to Stereo Amplifier & Recorder. Listen & Record.
POWERCOM CORPORATION
Box 454 Dept 4 Troy, N. Y. USA 12181

POLICE, Fire monitors, scanners, crystals discount priced. New crystal-less scanners. Box 19224, Denver, CO 80219.

TELETYPE EQUIPMENT for sale for beginners and experienced computer enthusiast. Teletype machines, parts, supplies. Catalogue \$1.00 to: ATLANTIC SALES, 3730 Nautilus Ave., Brooklyn, NY 11224. Tel: (212) 372-0349.

MEMORY-2102-1K Static RAM, \$2.75. Quantity discount, computer components, digital clock kits. Send for free list. Digitex, 2603 West Davis, Dallas, Texas 75211.

FREE DATA SHEETS WITH EVERY ITEM 749 IC WITH EVERY \$10 ORDER*

- REDUCE YOUR PROJECT COSTS
- MONEY-BACK GUARANTEE
- 24-HOUR SHIPMENT
- ALL TESTED AND GUARANTEED

TRANSISTORS (NPN):

2N3563 TYPE RF Amp & Osc to 1 GHz (pl. 2N918)	6/\$1.00
2N3565 TYPE Gen. Purpose High Gain (TO-92/106)	6/\$1.00
2N3567 TYPE High-Current Amplifier/Sw 500 mA	4/\$1.00
2N3866 TYPE RF Power Amp 1.5 W @ 450 MHz	4/\$1.50
2N3903 TYPE RF Power Amp 10-25 W @ 3-30 MHz	6/\$1.00
2N3919 TYPE RF Power Amp 10-25 W @ 3-30 MHz	\$3.00
2N4274 TYPE Ultra-High Speed Switch 12 ns	4/\$1.00
MP56515 TYPE High Gain Amplifier hFE 250	3/\$1.00
Assort. NPN GP TYPES, e.g. 2N3694, 2N3903, etc. (15)	\$2.00
2N3538 TYPE (PNP) GP Amp & Sw to 300 mA	\$1.00
2N4249 TYPE (PNP) Low-Noise Amp 1µA to 50mA	4/\$1.00

FET's:

N-CHANNEL (LOW-NOISE)	
2N4091 TYPE RF Amp & Switch (TO-18/106)	3/\$1.00
2N4416 TYPE RF Amplifier to 450 MHz (TO-72)	2/\$1.00
2N5163 TYPE Gen. Purpose Amp & Sw (TO-106)	3/\$1.00
2N5486 TYPE RF Amp to 450 MHz (plastic 2N4416)	2/\$1.00
E100 TYPE Low-Cost Audio Amplifier	4/\$1.00
ITE4868 TYPE Ultra-Low Noise Audio Amp	2/\$1.00
T1574 TYPE High-Speed Switch 40Ct	3/\$1.00
Assort. RF & GP FET's, e.g. 2N5163, MPF102, etc. (8)	\$2.00
P-CHANNEL:	
2N4360 TYPE Gen. Purpose Amp & Sw (TO-106)	3/\$1.00
E175 TYPE High-Speed Switch 125Ct (TO-106)	3/\$1.00

NOVEMBER SPECIALS:

1N4154 DIODE 30 V/10mA-IN914 except 30 V	25/\$1.00
2N2222 NPN TRANSISTOR GP Amp & Switch	5/\$1.00
2N2907 PNP TRANSISTOR GP Amp & Switch	5/\$1.00
2N3553 RF Power Amp 5 W @ 150 MHz, 10 W @ 50 MHz	\$2.00
2N3904 NPN TRANSISTOR GP Amp & Switch	5/\$1.00
2N3906 PNP TRANSISTOR GP Amp & Switch	5/\$1.00
2N5108 RF Power Amp 2 W @ 450, 1 W @ 1 GHz	\$2.50
E101 N-CHANNEL FET Low Current, Low Vp Amp/Sw	3/\$1.00
MPF102 N-CHANNEL FET RF Amp-200 MHz	3/\$1.00
340 T 1A VOLT. REG. Specify 5, 6, 12, 15 or 24 V-W/Ckts	\$1.75
2556 DUAL 555 TIMER 1µsec to 1 hour (OIP)	\$1.00
8038 WAVE FORM GENERATOR ~100 ΔWave W/Ckts	\$4.50
MM5316 DIGITAL CLOCK-Snooze/Alarm/Timer Hrs, Mins, Secs, 4 or 6 Digit-With Specs/Schematics	\$5.50

LINEAR IC's:

308 Micro-Power Op Amp (TO-5/MINI-DIP)	\$1.00
309 K Voltage Regulator 5V @ 1A (TO-3)	\$1.50
324 Quad 741 Op Amp, Compensated (OIP)	\$1.75
380 2-5 Watt Audio Amplifier 34 dB (OIP)	\$1.29
555 Timer 1 or 1.5 hr. NE555, LM555, etc. (MINI-DIP)	\$.55
709 Popular Op Amp (OIP/TO-5)	\$.29
723 Voltage Regulator 3-30 V @ 1-250mA (OIP/TO-5)	\$.58
739 Dual Low-Noise Audio Preamp/Op Amp (OIP)	\$1.00
1458 Dual 741 Op Amp (MINI-DIP)	\$.65
741 Freq. Comp. OP AMP (OIP/TO-5/MINI-DIP)	3/\$1.00

DIODES:

ZENERS—Specify Voltage 3.3, 3.9, 4.3, 5.1, 5.8, 8.2	400mW 4/\$1.00
9.1, 10, 12, 15, 18, 22, 24, 27 or 33V (±10%)	1 Watt 3/\$1.00
1N3600 TYPE Hi-Speed Sw 75 V/200 mA	6/\$1.00
1N3893 TYPE RECTIFIER Stud Mount 400 V/12 A	2/\$1.00
1N914 or 1N4148 TYPE Gen. Purp. 100V/10mA	15/\$1.00
D5 VARACTOR 5-50 W Output @ 30-250 MHz, 7-70 pF	\$5.00
F7 VARACTOR 1-3 W Output @ 100-500 MHz, 5-30 pF	\$1.00

*MAIL NOW! FREE DATA SHEETS supplied with every item from this ad. FREE ON REQUEST—749 Dual Op Amp (\$1.00 value) with every order of \$10 or more, postmarked prior to 12/31/75.
ORDER TODAY—All items subject to prior sale and prices subject to change without notice. All items are new surplus parts — 100% functionally tested.
WRITE FOR FREE CATALOG offering hundreds of semiconductors not listed here. Send 10¢ stamp.
TERMS: All orders must be prepaid. We pay postage. \$1.00 handling charge on orders under \$10. Calif. residents add 6% sales tax. Foreign orders — add postage. COD orders — add \$1.00 service charge.

ADVA ELECTRONICS
BOX 4181 AY, WOODSIDE, CA 94062
Tel. (415) 851-0455
CIRCLE NO. 8 ON FREE INFORMATION CARD

WAREHOUSE DISCOUNTS ON NATIONALLY ADVERTISED

- C.B. RADIOS
- MONITOR SCANNERS FIRE POLICE

IN FACTORY SEALED CARTONS
BUSINESS - RECREATION - PERSONAL SATISFACTION GUARANTEED

WRITE FOR QUOTE
ELECTRONICS WAREHOUSE, INC.
6234 LITTLE RIVER TURNPIKE (DEPT. 5)
ALEXANDRIA, VA. 22312
OR PHONE: (703) 256-1300

SAVE TIME AND MONEY! We have 15 years experience selling over 60 brands. Save up to 50% off. We get the best deals from manufacturers, you get the best deals from us! Call now (212) 338-8555 or write: S.C.A., Dept. P.E., 2122 Utica Ave., Brooklyn, N.Y. 11234.

POPULAR ELECTRONICS

DO YOU KNOW ENOUGH ABOUT PSYCHOLOGY? FIND OUT MORE FREE!

A knowledge of psychology can be a real benefit to you. And, chances are, you already know quite a bit about it.

Because you are an avid reader, you obviously have an active and inquisitive mind. You observe people, try to understand them better, perhaps even formulate some informal theories of your own.

You know enough psychology to know that people are endlessly fascinating, that you can do better in life by understanding more about people, and that no matter how much we know, we learn more about human behavior every day.

Find out what you know . . . and what you don't know.

Now you can find out how much you really do know about psychology by taking a test—FREE

The editors of *Psychology Today* have designed a special test to show you the present status of your knowledge of psychology. It's fun to take, and you know the results immediately because you grade yourself with a special answer key. Send in the coupon below and we will rush the test to you . . . FREE. And when we send the test, we will also send a booklet of complete information on a new and easy way for you to expand your knowledge of psychology. Expand your knowledge of psychology with a unique method . . .

Psychology Today Independent Study Program
Offered in cooperation with the University of California Extension

Yes, now you can learn a great deal more about psychology in less time than you'd expect. In only 16 weeks, the *Psychology Today Independent Study Program* can teach you as much about human behavior as a college psychology course.

There are no classes to attend. You study when you have the time and where you choose. And upon successful program completion, you receive 8 college credits from one of the world's most respected learning institutions.


You Get All The Help You Can Use

Everything you need to successfully complete the course is sent to you. You receive a unique series of study manuals to guide you through each major area of psychology step by step. You receive the most complete and exciting introductory textbook available anywhere today—*Psychology Today: An Introduction*—as your basic learning resource. You also receive four long-playing records that bring psychology to life at the spin of a turntable . . . And to help you test your progress, you receive a series of unique self-check quizzes. Each one you take not only shows you things you need to study further, but refers you to the exact pages in the text you should read to study them! Finally, a friendly computer scores the five exams you'll be taking. It tells you what you got right and wrong, and what to re-study.

The materials you work with make the *Psychology Today Independent Study Program* the effective way to learn psychology.

For only \$105.00 you can gain a vast new fund of knowledge that can improve every facet of your life . . . and you can gain 8 college credits. And all this, in the comfort and convenience of your own home and whenever your schedule permits.

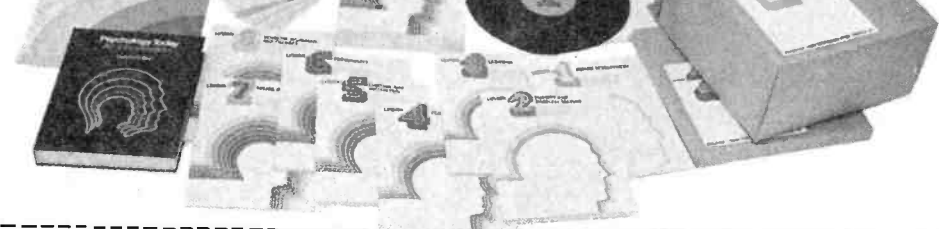So use the coupon today to send for your free quiz and the booklet that will introduce you to a whole new way of understanding people . . . and yourself.



YES!
Please send me complete information about the *Psychology Today Independent Study Program* . . . and include the unique new self-check quiz that has been developed by the editors of *Psychology Today*.
I understand that the booklet and quiz are mine to keep without cost or obligation. And should I decide to enroll in the Program, I understand that you will send me a free copy of one of the 150 pg. *Psychology Today Readers*.

Print Name _____
Address _____
City _____
State _____ Zip _____

Psychology Today Independent Study Program
Rm. 715, One Park Avenue, New York, N.Y. 10016. PE-115

LIVE IN THE WORLD OF TOMORROW... TODAY!

And our FREE 164 PAGE CATALOG is packed with exciting and unusual values in electronic, hobby and science items — plus 4,500 finds for fun, study or profit... for every member of the family.

A BETTER LIFE STARTS HERE

PRO ELECTRONIC SOUND CATCHER

Parabolic mike w/ 18-3/4" transparent reflecting shield & 2 I.C.'s in amplifier magnifies signals 100x that of omni-direction mikes. Catch sounds never before heard! Highest signal to noise ratio poss. Earphones, tape recorder output, tripod socket; req. two 9v trans, batt. (not incl.)
 No. 1649AV... (5 1/2 LB.)\$299.00 Ppd.
 LOW COST MODEL: NO EARPHONES, ELECTR. CIRC. No. 1665AV\$199.95 Ppd.
 LOWER SENSITIVITY ECON. MOD. W/O ELECTR. No. 80,242AV\$89.50 Ppd.



ELECTRONIC DIGITAL STOPWATCH: \$69.95

A price breakthrough! New pocket size 4 oz. timer acc. to ±2% of last digit (1/100 sec. increments). Compares with others twice the price! Instant error-free readouts to 9999.99 sec. (over 2 3/4 hr). Starts, stops re-starts (accumulates). Mechanical pushbutton & electrical remote on/off w/any 3.5-150v AC/DC source. Plug-in jack. Incl. 9v batt. Solid state.
 No. 1943 AV (2 1/4x4 1/4x7 1/4)\$69.95 Ppd.
 DELUXE 2 EVENT STOPWATCH (±0.01% OF LAST DIGIT) No. 1653 AV\$149.95 Ppd.



FUEL MISER RECLAIMS HEAT

Save your 40% wasted heat to warm a basement, garage or rec room at no extra cost! Instead of going "up the chimney" it goes where you want it. Remove part of furnace exhaust pipe, slip Heat Exchanger in. At 125° fan automat. forces clean air through unit which heats to over 200°F., can be ducted to 20 ft. from unit. 110v AC. Inst.
 No. 19,194AV (6" DIA.) Shpg. 17 lb.\$106.00 FOB
 No. 19,195AV (6" DIA.) Shpg. 17 lb.\$106.00 FOB
 No. 19,198AV (7" DIA.) Shpg. 17 lb.\$106.00 FOB



SEE MUSIC IN PULSATING COLOR

New 3-Channel Color Organ adds to music listening pleasure, lets you modulate 3 independent strings of colored lamps with intensity of your music to create an audio "light show." They flash, vary in brightness related to music's rhythm, pitch, volume—pulsating lighting performance to music! Fully assembled & priced half that of others, the Edmund Sound to Light Control is a terrific value. Plug in, turn on!
 No. 42,309AV... (ASSEMBLED)\$17.95 Ppd.
 No. 42,336AV... (UNASSEMBLED)\$13.95 Ppd.



WHEN YOU COME TO PHILADELPHIA BE SURE TO SEE
FREE BICENTENNIAL LIGHT SHOW
 IN BARRINGTON, N. J. ONLY 10 MINUTES AWAY AT
EDMUND FACTORY STORE



WORLD'S SMALLEST CALCULATOR!

Small but mighty! 8-digit, 4-function electronic calculator does everything big ones do—even has automatic % key... for only \$19.95. Take it anywhere. Fits in your pocket—1/3 size of cigarette pack. 2-oz. dynamo features floating decimal, constant key, lead zero depression, more! Operates on two 1.5v Mallory PX 825 camera batteries (included). 2 x 2.8 x 0.4" with plenty of room for most fingers. Another Edmund first with advanced technology.
 Stock No. 1945AV\$19.95 Ppd.

SOLAR ENERGY CUBE!



No. 42,287AV... (4 x 4 x 4")\$19.95 Ppd.

Unique demonstrator dramatically shows how sunlight converts to kinetic energy. Clear plastic Solar Energy Cube placed in the sun with its 3 highly efficient silicon solar cells powers the motor to whirl the propeller! Unit actually produces 1.5v DC, 825ma. Same cells found in our mighty panels. Speed directly related to sunlight available. Nothing to wear out! Great for executives, hobbyists, teachers.



KNOW YOUR ALPHA FROM THETA!

For greater relaxation, concentration, listen to your Alpha-Theta brainwaves. Ultra-sensitive electrode headband slips on/off in seconds—eliminates need for messy creams, etc. Atch'd to amplifier, filters brainwaves, signals beep for ea. Alpha or Theta wave passed. Monitoring button stimulates Alpha sound; audio & visual (L. E. D.) feedback. Reliable, easy-to-use unit comparable to costlier models. Completely safe. Comprehensive instruction booklet.
 No. 1635AV (8 x 3 x 4"; 24 oz.)\$149.50 Ppd.
 DELUXE "ON" TIME MONITOR—Measures and records % No. 1652AV... (15 x 10 x 6")\$299.50 Ppd.
 No. 71809AV LOW COST "STARTER" UNIT\$55.00 Ppd.
 DO-IT-YOURSELF KIT... No. 61,069AV\$34.95 Ppd.



LOW COST 7X INFRA-RED VIEWER

For infra-red crime detection surveillance, security system alignment, I.R. detection, laser checking, nite wildlife study, any work req. I.R. detection & conv. to visible spectrum. Self cont. scope w/everything incl I.R. light source.
 6v or 12v power, 6032 I.R. converter tube, f/4.5 objective lens, adjust. triplet eyepiece. Focuses from 10' to infinity.
 No. 1659AV (11 x 14 1/4 x 3")\$275.00 Ppd.
 WITHOUT LIGHT SOURCE No. 1648AV\$225.00 Ppd.




4 1/4" ASTRONOMICAL TELESCOPE

See moon craters, rings of Saturn, double stars. New equatorial mount. f/10, 1/4 wave mirror (Pyrex). Gives theoretical limit of resolution. Rack & pinion focusing. Aluminum tube, 6X finder. 1" F.L. 45X Kellner achromatic eyepiece and Barlow lens to double & triple power up to 135X. Free Star Chart plus 2 Books.
 Stock No. 85,105AV (Shipping Wt. 42 lbs.)\$159.50 FOB
 4 1/4" WITH CLOCK DRIVE No. 85,107AV\$219.50 FOB
 6" REFLECTOR TELESCOPE (48X to 360X) No. 85,187AV\$249.50 FOB
 6" WITH CLOCK DRIVE No. 85,086AV\$285.00 FOB
 3" DELUXE REFLECTOR (30X to 90X) No. 80,162AV\$ 89.95 Ppd.
 STANDARD 3" REFLECTOR No. 85,240AV\$ 59.95 Ppd.

The right Pickering cartridge for your equipment is the best cartridge money can buy!

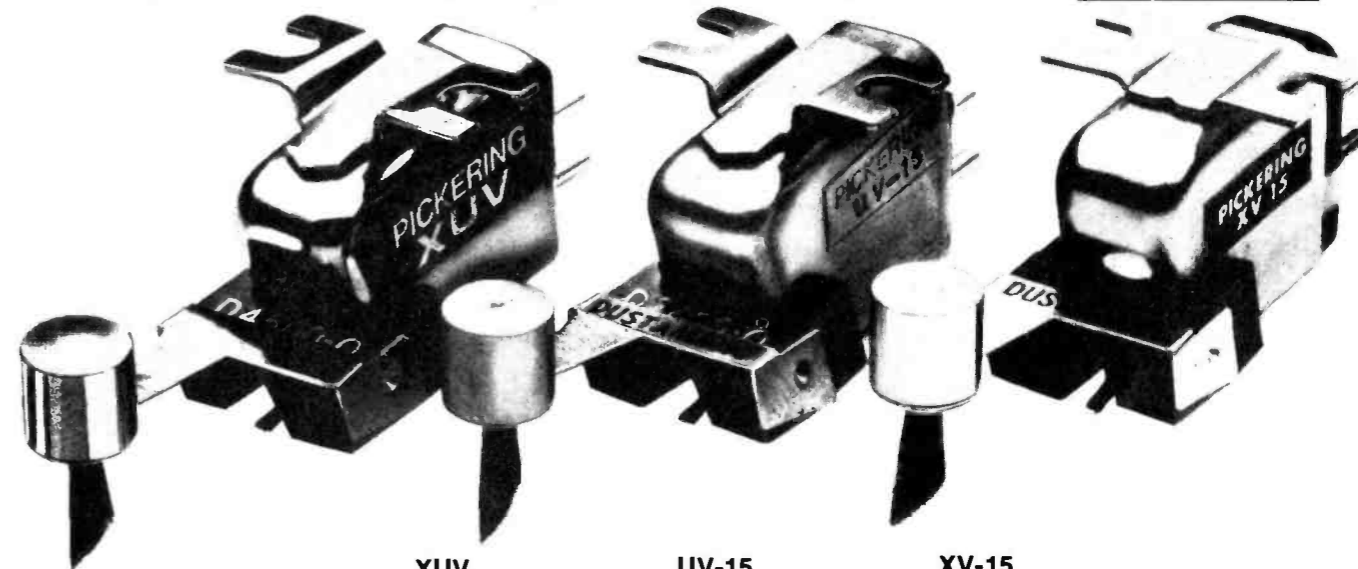They feature low frequency tracking and high frequency tracing ability*!



	XUV STEREO & DISCRETE	UV-15 DISCRETE & STEREO	XV-15 STEREO & MATRIX	
Manual Transcription	XUV/4500Q	UV-15/2400Q	XV-15/1200E XV-15/750E	MANUAL TRANSCRIPTION TURNTABLE
Automatic Transcription	XUV/4500Q	UV-15/2400Q	XV-15/1200E XV-15/750E	AUTOMATIC TRANSCRIPTION TURNTABLE
Manual	XUV/4500Q	UV-15/2400Q	XV-15/400E XV-15/350	MANUAL
Automatic Turntables		UV-15/2000Q	XV-15/400E XV-15/350	AUTOMATIC
Manual/Automatic		UV-15/2000Q	XV-15/200E XV-15/100	MANUAL/AUTOMATIC
Changer			XV-15/200E XV-15/150	CHANGER

Pickering's cartridges have been specifically designed and engineered not only to peak specifications and performance characteristics, but also to achieve total compatability with your music system to help you get the most out of it.

Only Pickering has developed a way for you to be absolutely certain you select the "right" cartridge for your music system. We did it first for stereo by developing our Dynamic Coupling Factor rating system—DCF for short—which identifies pick-up performance in terms of a quantitative measurement. The value of a DCF rating lies not only in its merit to define low frequency tracking ability but also in its measure as an index of high frequency (8 to 50 kHz)

tracing ability. Pickering's DCF-rated pick-ups have exceptional high frequency tracing characteristics, vital for both stereo and discrete 4-channel performance. The Pickering cartridge exactly "right" for maximum performance with your equipment is simple to select because of this rating method.

So, whether stereo or discrete (or both) is your preference, choose the Pickering cartridge exactly right for your equipment.

For further information write to Pickering & Co., Inc., Dept. PE, 101 Sunnyside Blvd., Plainview, N. Y. 11803



"For those who can hear the difference"
 CIRCLE NO. 59 ON FREE INFORMATION CARD

MAIL COUPON FOR GIANT FREE CATALOG!
 164 PAGES • MORE THAN 4500 UNUSUAL BARGAINS
 Completely new 1976 edition. New items, categories, illustrations. Dozens of electrical and electromagnetic parts, accessories. Enormous selection of Astronomical Telescopes. Unique lighting and ecological items. Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Prisms. Hard-to-get surplus bargains. Ingenious scientific tools. 1000's of components.
EDMUND SCIENTIFIC CO.
 300 Edscorp Building, Barrington, N. J. 08007
 Please rush Free Giant Catalog "AV"

Name _____
 Address _____
 City _____ State _____ Zip _____

COMPLETE & MAIL WITH CHECK OR M.O.
EDMUND SCIENTIFIC CO. 300 Edscorp Building, Barrington, N.J. 08007

How Many	Stock No.	Description	Price Each	Total
<input type="checkbox"/>		PLEASE SEND GIANT FREE CATALOG "AV"		
<input type="checkbox"/>		Charge my BankAmericard		
<input type="checkbox"/>		Charge my Master Charge		

Add Handling Chg.: \$1.00, Orders Under \$5.00, 50¢, Orders Over \$5.00

Interbank No. _____
 My Card No. Is _____
 Signature _____
 Card Expiration Date _____
 Name _____
 Address _____
 City _____ State _____ Zip _____

30-DAY MONEY-BACK GUARANTEE. You must be satisfied or return any purchase in 30 days for full refund. *\$15.00 minimum

Would you recommend your turntable to your best friend?

If not, you need a Dual.

If you were to replace any of your present components, would you know exactly what its successor would be? And then buy it without further consideration? Perhaps. But we think it more likely that you would look for more information, either in a music/equipment magazine or from a knowledgeable friend. Probably from both.

Which brings us to turntables . . . and Dual.

Each year we hear from a sampling of Dual owners in response to a lengthy questionnaire. A high percentage tell us they're now on their second Dual. An even higher percentage formerly owned manual turntables. And nearly all rate their Duals as either "excellent" or "good."

Although there are other fine turntables, few match Dual's reputation for quality performance and reliability, and none match Dual's operational versatility. For example, if you want to be able to play records in sequence, you have four single-play/multi-play Duals to choose from. If you simply want fully automatic convenience in a single-play-only turntable, you have two to choose from. And there is now a semi-automatic Dual.

The way a tonearm is moved to and from the record is not critical. Nor is the type of drive system. What is critical is how faithfully the tonearm permits the stylus to follow the contours of the groove and how accurately and quietly the platter rotates. To compromise with quality in these respects can risk damage to your precious records and produce sounds which were never recorded.

Every Dual, from the 1225 to the CS701, provides more precision than you may ever need. Which is why more component owners—audio experts, hifi editors, record reviewers and readers of the music/equipment magazines—own Duals than any other turntable.

There's no better recommendation we can offer you. Or that you can offer to your best friend. Unless you happen to own a Dual yourself.

Dual 1225. Fully automatic, single-play/multi-play. Viscous damped cue-control, pitch-control. 10 $\frac{5}{8}$ " platter. \$139.95, less base.

Dual 1226, with cast platter, rotating single-play spindle, \$169.95.

Dual 1228, with gimballed tonearm, synchronous motor, illuminated strobe, variable tracking angle, \$199.95.

Dual 1249. Fully automatic, single-play/multi-play. Belt drive. 12" dynamically-balanced platter. \$279.95, less base. Full-size single-play models include: Dual 510, semi-automatic, \$199.95; Dual 601, fully automatic, \$249.95. (Dual CS601, with base and cover, \$270.)

Dual CS701. Fully automatic, single-play. D.C. brushless, electronic direct drive motor; tuned anti-resonance filters. \$400, including base and cover.



Dual 1225



Dual 1249



Dual CS701

United Audio Products, 120 So. Columbus Ave., Mt. Vernon, N.Y. 10553

CIRCLE NO. 4 ON FREE INFORMATION CARD

Exclusive U.S. Distribution Agency for Dual

Dual[®]