

# Poptronics®

Formerly **Popular Electronics®** and **Electronics NOW.**

**DIGITAL  
NEW COLUMN  
DOMAIN**

## THE SCATCAT

Teach your pet where not to go in a "startling" and humane way



## Power your projects in a non-polluting way with the Solar-Cell Inverter

Learn how to use a Tunable-Active Filter in your next project



### Also Inside:

- VCR Repair
- Alternative Operating Systems
- High-speed Data Transfer
- Product Reviews



\$4.99 U.S.  
\$5.99 CAN.

# Virtual Lab – Real Results

*Intuitive schematic capture*

*Fast, accurate analog/  
digital simulation*

*Full-featured pcb layout*

*Built-in autorouting*

CircuitMaker 2000 provides all the tools necessary to quickly and easily design circuits, test them in the real world and generate prototype boards – the complete virtual electronics lab solution.

With all the features you'd expect from a professional design system – plus exceptional ease-of-use, you'll spend less time learning and more time designing.

Available in both standard and professional editions, CircuitMaker 2000 gives you full design capability at a price that is simply unmatched by the competition.

Contact us for your Free  
CircuitMaker 2000 brochure



**CircuitMaker<sup>2000</sup>**  
the virtual electronics lab™

Industry standard features  
The accurate analog/digital simulation  
Multi-threaded PCB layout  
Built-in autorouting

FROM  
**\$395**  
New License Price

Upgrade from \$95

*Comprehensive educational and computer-based  
training packages also available*

**CircuitMaker<sup>2000</sup>**  
the virtual electronics lab™

Call your local CircuitMaker sales & support  
center on **800 419-4242**

or visit [www.circuitmaker.com](http://www.circuitmaker.com)

**CircuitMaker**  
the virtual electronics lab™

CircuitMaker and CircuitMaker 2000 are registered trademarks of Protel International Limited.

CIRCLE 133 ON FREE INFORMATION CARD

[www.americanradiohistory.com](http://www.americanradiohistory.com)

# Poptronics®

THE MAGAZINE FOR THE HANDS-ON ELECTRONICS ACTIVIST!

## FEATURES

### 29 TRAIN YOUR PETS WITH THE SCATCAT

Although you might love the four-footed, fur-covered members of your household, they sometimes decide that they're allowed to go wherever they want—even if it's a "no-no" area like the kitchen counter, the dining-room table, the living-room sofa, or if Kitty likes to play "Godzilla" on the toy-train layout! Animals aren't dumb; they're clever enough to realize that they can "get away with it" if you're not around—especially at night. This month's cover story describes a training device that will sound a high-pitched alarm and flash a light whenever an animal enters a "forbidden zone." After a few startling episodes, even the most stubborn pet will "get the hint!"—Russ Shumaker



### 39 SOLAR-CELL INVERTER

Solar cells are a wonderful, non-polluting source of electricity, but the voltage that they put out is too low for most transistor-based circuits. With this device, you can boost the voltage level of any solar cell to usable levels.—Fred Nachbaur

### 42 ALL ABOUT ELECTRONICALLY-TUNABLE ACTIVE FILTERS

Active filters, being one of the fundamental circuits in electronics, are even more valuable if you can change their response with a control voltage. Learn how they are designed and work with this "hands-on" approach using tested designs.—Ron Tipton

## PRODUCT REVIEWS

### 3 GIZMO®

Network Walkman, direct-view HDTV, wireless e-mail, clock radio, still/motion digital camera, THX-certified speakers, music software, portable tablet computer.

## DEPARTMENTS

### 6 NET WATCH

Joe Black uses the Net to buy cellular-telephone service.

### 8 SURVEYING THE DIGITAL DOMAIN

This new column by Reid Goldsborough touches on the subjects that affect every computer user, neophyte and power user alike. This month he takes a quick look at computer viruses and alternative operating systems to the one that came on your computer.

### 14 PEAK COMPUTING

Ted Needleman sets your machine on FireWire as he explores high-speed data-transfer busses.

### 17 PROTOTYPE

Polymers for high-speed communication, new-generation batteries for an electric motorcycle, "intelligent" robot competitions, medical imaging technology, and atom traps.

### 22 Q&A

Michael Covington answers your most perplexing questions.

### 25 SERVICE CLINIC

Sam Goldwasser digs deeper into VCR control problems.

### 60 BASIC CIRCUITRY

Charles Rakes races to the finish line with this marathon of simple circuits.

## AND MORE

2	Editorial
11	Letters
51	New Gear
55	New Literature

### 16 HANDS-ON REPORT

Keyspan 4-Port USB Hub.

65	Poptronics Shopper
98	Advertising Index
98A	Free Information Card

Poptronics (ISSN 1526-3681) Published monthly by Gernsback Publications, Inc. 275-G Marcus Blvd., Hauppauge, NY 11788. Second-Class postage paid at Hauppauge, NY and at additional mailing offices. One-year, twelve issues, subscription rate U.S. and possessions \$24.99, Canada \$33.15 (includes G.S.T. Canadian Goods and Services Tax Registration No. R125166280), all other countries \$33.99. Subscription orders payable in U.S. funds only, International Postal Money Order or check drawn on a U.S. bank. U.S. single copy price \$4.99. Copyright 2000 by Gernsback Publications, Inc. All rights reserved. Hands-on Electronics and Gizmo trademarks are registered in U.S. and Canada by Gernsback Publications, Inc. Poptronics trademark is registered in U.S. and Canada by Poptronix, Inc. and is licensed to Gernsback Publications, Inc. Printed in U.S.A.

Postmaster: Please send address changes to Poptronics, Subscription Dept., P.O. Box 459, Mount Morris, IL 61054-7629

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, Poptronics publishes available plans or information relating to newsworthy products, techniques, and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Poptronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

Larry Steckler, EHF, CET,  
editor-in-chief and publisher

## EDITORIAL DEPARTMENT

Joseph Suda, managing editor  
Evelyn Rose, assistant editor  
Nancy Serenita, editorial assistant

## CONTRIBUTING EDITORS

Joe Black  
Michael A. Covington, N4TMI  
Reid Goldsborough  
Sam Goldwasser  
John Iovine  
Gordon McComb  
Ted Needleman  
Charles D. Rakes  
Teri Scaduto

## PRODUCTION DEPARTMENT

Ken Coren, production director  
Kathy Campbell, production manager  
Michele L. Musé, prepress specialist

## ART DEPARTMENT

Russell C. Truelson, art director

## CIRCULATION DEPARTMENT

Gina L. Gallo, circulation manager

## REPRINT DEPARTMENT

Nancy Serenita, Reprint Bookstore

## BUSINESS AND EDITORIAL OFFICES

Gernsback Publications, Inc.  
275-G Marcus Blvd.  
Hauppauge, NY 11788  
631-592-6720  
Fax: 631-592-6723

President: Larry Steckler  
Vice-President: Adria Coren  
Vice-President: Ken Coren

## SUBSCRIPTION CUSTOMER SERVICE/ ORDER ENTRY

800-827-0383  
7:30 AM - 8:30 PM EST

Advertising Sales Offices  
listed on inside back cover

Cover by Michele Lyn Musé

VISIT US ON THE INTERNET AT:  
[www.gernsback.com](http://www.gernsback.com)

Since some of the equipment and circuitry described in POPTRONICS may relate to or be covered by U.S. patents, POPTRONICS disclaims any liability for the infringement of such patents by the making, using, or selling of such equipment or circuitry, and suggests that anyone interested in such projects consult a patent attorney.

<mailto:popeditor@gernsback.com>

## Copyright Tyranny

This month, I'm going to step aside and turn the podium over to Gary Shapiro, the president of the Consumer Electronics Manufacturers Association. While I only gave one small example of this escalating problem back in June, Gary takes a look at some of the underlying issues and the somewhat chilling direction that we might be heading.

So without further ado, I'll turn things over to Gary.

Joseph Suda  
Managing Editor

Content (or copyright) owners and the consumer-electronics (CE) industry need each other. Hardware needs good content to sell new products. Copyright owners need consumer electronics so consumers can buy and enjoy their content.

But the two industries often have had a strained relationship. The greatest tension occurs because each new technology has been feared by content providers—yet each technology has created vast new revenue opportunities to the content community!

Think back. Movie studios argued that the TV and VCR would reduce their revenues. They fought video rentals and tried to make the VCR illegal. The music industry opposed the analog cassette, the CD, and every other new digital-audio format.

### Limiting Consumer Choices

Today, Hollywood and the recording industry are fighting digital delivery of content. They are using lawsuits, licensing, and withholding of programming to pressure everyone from Website owners to hardware makers to restrict the customer's ability to receive, enjoy, or even modify programs. Thus, consumers are blocked from getting digital-TV programming and are in litigation over access to MP3.

The copyright community envisions a world where consumers pay for every use of a copyrighted work or, as we said in recent Congressional testimony, "the 'play' button will become the 'pay' button."

The threat to consumer rights and technology growth is real. The copyright lobby gives millions of dollars to politicians—much more than other groups. Twice they have successfully persuaded Congress to extend the "limited" constitutional term of a copyright. Before 1978, copyright lasted for 28 years and was renewable (after registration) for another 28 years. In 1978, the term was increased to the life of the author plus 50 years. Today a copyright lasts the life of the author plus 70 years and corporate works, or "works for hire," are protected for 95 years.

In 1995, Congress gave the recording industry the right to control performances of their records. In 1998, Congress passed sweeping legislation that allows copyright owners to lock works in technological protection measures and criminalizes the circumvention of those measures. This continued expansion of the monopoly breadth of copyright owners has not only created complex new regulatory schemes, it has increased the cost of technology, slowed the development of digital television, and kept older works out of the public domain.

### Speak Out

Only rarely will a politician stand up to these copyright tyrants. Recently, Telecommunications Committee Chair Billy Tauzin (R-LA) momentarily stopped the copyright lobbying juggernaut. He said he grew up by learning from Bookmobiles, a possibility that may not exist in a future pay-per-use society. Chairman Tauzin recognized that Congress creates and expands the copyright monopoly, and as copyright owners' rights increase, the "digital divide" widens.

If politicians yield to copyright tyranny, consumers will lose their ability to gain access to information, education, and entertainment. Restrictions on technology (which can even limit fair-use rights or access to non-copyrighted works) also restrict the growth of new technologies and limit the value of broad public access.

We must be aggressive on this issue. Future generations of technology, and ultimately consumers, depend on our action.

# GIZMO®

## Network Walkman

The Walkman for the 21<sup>st</sup> century is Sony's *NW-E3 Network Walkman* digital music player (\$330). Music files are stored on 64MB of embedded flash memory. Measuring just  $3\frac{1}{8} \times 1\frac{1}{4} \times \frac{1}{2}$  inches and weighing in at 1.6 ounces (including a single AAA battery, said to provide up to five hours of continuous playback), the Network Walkman is tiny enough to fit into the change pocket of a pair of jeans. A shuttle switch lets you navigate through audio track information, with details such as title and length displayed on the backlit LCD.

The digital music player allows you to capture and collect your favorite music from the Internet or download CD tracks to your hard drive to create your own digital music collections. An hour of music can be transferred to the NW-E3 in about 90 seconds. The player comes bundled with Sony's PC-based *OpenMG Jukebox* music-management software to organize music and play lists. The player is compliant with the SDMI (Secure Digital Music Initiative) framework for secure digital music downloads.

Sony Electronics Inc., 1 Sony Drive, Park Ridge, NJ 07656-8002; 800-222-SONY; [www.sony.com](http://www.sony.com).

CIRCLE 50 ON FREE INFORMATION CARD



## Pocketful of E-Mail

Receive instant messages and e-mail wirelessly with the VTech *IMprompt2* (less than \$200), a handheld device that's small enough to fit in a pocket.

The portable design provides easy-to-use, one-touch access to e-mail from any standard RJ-11 phone jack through [vtechworld.com](http://vtechworld.com), VTech's service provider. You can opt to receive wireless notification of waiting e-mail or choose from one of several "enhanced" wireless service plans that allow you to instantly receive actual short e-mail messages (limited to 300 characters). SkyTel will provide both wireless messaging and information services for the *IMprompt2*. Flexible rate plans for both wireless and wire-line services will start at less than \$10 a month.

The *IMprompt2* features a filter to keep out unwanted e-mail and a Sender Buddy List that lets you know when you have a message from a specific sender. More than 500 e-mail messages can be stored. Other features include an address book, e-cards, a calculator, and built-in golf and arcade classic games.

VTech Industries, LLC, 101 East Palatine Road, Wheeling, IL 60090-6500; 847-215-9700; [www.vtechworld.com](http://www.vtechworld.com).


CIRCLE 51 ON FREE INFORMATION CARD

## Direct-View HDTV

According to Thomson, its *F38310 HDTV* set, which measures 38 inches diagonally across its widescreen tube, is the world's largest direct-view high-definition television—and its \$3999 suggested retail price makes it one of the most affordable HDTV sets yet. Available in "Venetian Suede" as *RCA F38310* and as the *Proscan PS38000*, the set is capable of displaying more than one million pixels of picture information with a 1080i scanning format. The fully integrated set allows reception of over-the-air analog and digital signals as well as built-in standard DirecTV service and high-def programming from the DirecTV satellite network. The 38-inch Performax picture tube uses a precision-focus HD resolution electron gun and .78mm-pitch Invar shadow mask to support the resolution requirements of HDTV. The set also features up to 20 watts of audio power and the Syncroscan HD component input for easy compatibility with digital cable TV boxes that use YprPb component video connections.

Thomson Consumer Electronics, 10330 North Meridian St., Indianapolis, IN 46290; [www.thomson-multimedia.com](http://www.thomson-multimedia.com).

CIRCLE 52 ON FREE INFORMATION CARD

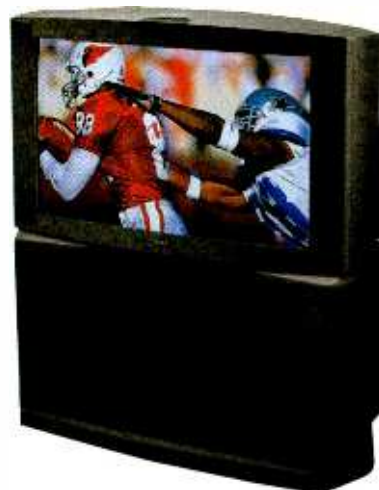



## Digital DualCam

JVC's GR-DVL9800 Digital DualCam (\$1999.95) combines a 680,000-pixel progressive-scan CCD and high-band processing technologies to deliver digital images with 520 lines of horizontal resolution and 480 lines of vertical resolution. The MiniDV camcorder's progressive mode setting allows the progressive-scan CCD to capture all lines in one scan, making it possible to freeze and grab clear, sharp, full-frame still shots for transfer to a PC. A removable card stores still images.

Besides the ability to capture freeze frames, the camera's dual shooting capability provides, in effect, a separate still camera within the camcorder. It allows you to snap still pictures while recording moving images. In digital still camera mode, images can be recorded in resolutions up to 1024 × 768 pixels (XGA).

An i.LINK (IEEE 1394) in/out terminal makes it simple to download still and video images to a similarly equipped computer. Still shots can also be downloaded via a serial connection. The included image-editing and -processing software—JVC's PictureNavigator, Presto! PhotoAlbum, Presto! Mr.Photo, Presto! ImageFolio, and JLIP Video Producer—lets you transform your videos into impressive multimedia productions. A full set of analog inputs and outputs lets you re-record VHS or S-VHS tapes in DV format, and a printer port allows direct connection to JVC's GV-SP2 Digital System Printer.

The DualCam offers 2X/4X high-speed recording at speeds of up to 240 images a second, and "Pro Slow" playback at 1/8 the speed of normal playback. It's equipped with a 3.5-inch LCD monitor as well as a 180,000-pixel color TFT viewfinder. It has a 10X optical zoom for close-in shots and a 200X digital zoom for shooting from a great distance. The progressive super-wide mode is ideal for shooting a panoramic vista.

JVC Americas Corp., 1700 Valley Road, Wayne, NJ 07470; 973-315-5000; [www.jvc.com](http://www.jvc.com).

CIRCLE 53 ON FREE INFORMATION CARD

## Wake-Up Call

Start your day off on the right foot with Philip's AJ3965 CD clock radio (\$89.95). Its "gentle wake" setting gradually increases the volume of the wake-up buzzer or radio station. It starts out barely audible and increases to a volume loud enough to rouse the soundest sleeper. You can select minimum or maximum volume levels, depending on how much of a jumpstart you need each morning. At bedtime, the gentle wake feature works in reverse. It acts as a sleep timer that gradually decreases the volume. The clock radio is equipped with a digital AM/FM tuner. Two separate and independent alarm settings each offer the option of waking to a CD, radio station, or the buzzer. The "weekend sleeper" function instructs the clock's alarm to sound only on weekdays.

Philips Consumer Electronics, 64 Perimeter Center East, Atlanta, GA 30346-6401; 770-821-2400; [www.philips.com](http://www.philips.com).



CIRCLE 54 ON FREE INFORMATION CARD

## Music Management System for PCs

Threefifteen is an extremely powerful yet easy-to-use, desktop PC music-management system developed by Open G, L.L.C. It is an audio-file player, encoder, and digital audio-file manager that offers a total solution for managing, storing, finding, and playing digital music on a personal computer.

The history log shows all songs that have been played all the way through. Using the log, you can choose some or all music played on a single date, and add them to a queue for instant playback or to a mix for future playback.

One unique feature of the software is its search capability that makes it easy to find and queue up music by using keyword search criteria on any combination of song title, album title, genre, and song comments. Available for free download from the Web site for a 30-day free trial, the threefifteen music system sells for \$19.95.

Open G, L.L.C., 1075 Broad Ripple Ave., PMB 315, Indianapolis IN 46220-2034; 317-931-1763; [www.threefifteen.net](http://www.threefifteen.net).

CIRCLE 55 ON FREE INFORMATION CARD



## Personal Computing Tablet

Lightweight and compact, the *Qbe Cirrus Personal Computing Tablet* (\$4745) is a truly mobile computer. (It is an updated and expanded version of the unit we reviewed in "PC Gizmo," January 2000.) The Qbe Cirrus is barely larger than a pad of composition paper and just about as easy to carry around, weighing approximately six pounds and measuring just 14 by 10 by 1.6 inches. The first Aqcess Personal Computing Tablet with a Pentium II 400 MHz processor, it comes equipped with a 12GB hard drive, 128MB of upgradeable memory, 56K modem, and a network card. Additional tools include Internet access along with multimedia features.

TouchPen technology provides handwriting recognition, and the included software provides voice recognition. The voice command will navigate the system, create documents, and send e-mail. At 140 words per minute, the voice function is considerably faster than the most efficient typist. In addition, the digital camera allows users to take photos, shoot a video, and even videoconference. Screen images are provided on the 13.3-inch active matrix color display with resolutions up to 768 by 1024. There's also a Smartcard magnetic strip reader for identification or e-commerce purposes.

Housed in a sturdy case of magnesium, ABS plastic, and rubber, the Qbe Cirrus allows users to perform most tasks while in the field, directing the cursor with a touch of a finger. If preferred, they can plug a mouse into the PS/2 port, open the on-screen keyboard, or even plug in a conventional keyboard. A lithium ion battery allows the user to work up to two hours before plugging the unit into a wall socket or recharging the battery.

Aqcess Technologies Inc., 16800 Aston, Irvine, CA 92606; 888-818-0055 or 949-567-1000; [www.qbenet.com](http://www.qbenet.com).

CIRCLE 56 ON FREE INFORMATION CARD



## Invisible THX



You can enjoy THX-certified sound from speakers hidden within your walls with Atlantic Technology's *THX Ultra-certified System 20*, which includes the *System 20 LCR* front-channel satellite (\$799 each) and the *System 20 SR* switchable Dipole/Bipole surround speaker (\$1199/pair).

The 20 SR can be flush-mounted in a standard two-by-four studded wall with 16-inch centers. Thanks to a clever rotating and tilting midrange/tweeter baffle, the front satellites are certified for both vertical and horizontal installation. The System 20 LCR is a three-way design with a "D'Appolito" (midrange/tweeter/midrange) module that can be rotated 90 degrees. The mid-high baffle can also be tilted 5 degrees up or down to compensate for less-than-ideal placement. Front-mounted high- and mid-frequency level controls allow further tweaking of the sonic balance.



The System 20 SR THX Ultra surround speaker will normally be used as a frequency-enhanced dipole, creating a diffuse, non-directional sound field. Yet it maintains full-range output, as only one woofer operates below

200 Hz. A front-mounted switch changes the System 20 SR to bipole operation (all drivers in-phase) for those few installations where speaker placement issues defeat the benefits of dipole surrounds.

Atlantic Technology advises using its 372 PBM THX Ultra-certified subwoofer to complete a fully THX-certified System 20 installation.

Atlantic Technology, 343 Vanderbilt Ave., Northwood, MA 02062; 781-762-6300; [www.atlantictechnology.com](http://www.atlantictechnology.com).

CIRCLE 57 ON FREE INFORMATION CARD

## Buying Cell Phone Services

If you are now sitting at the six-month point in a 12-month cell-phone service contract, you are likely to be one unhappy camper. Cellular-telephone costs have been dropping—rapidly. Probably under the terms of your existing contract, you are paying more—possibly much more—than the current-rate service would cost.

While I cannot help you get out of your current agreement, I can tell you where you can find help when it's time to find a new cell-phone service supplier. The secret is right there on the Internet. You can check out several places. I have a couple of favorites, and those are the ones we will cover here.

Before we do, I have a couple of personal suggestions. Look for a plan that does not require a contract. This way, if a lower rate comes along that suits your usage, you can switch at the end of the current month. Remember when selecting the number of minutes to check your current

usage. A plan that provides 500 minutes for \$50 is great—if you use almost all of the minutes. When you use those 500 minutes, your cost is ten cents a minute. However, if you use only 250 minutes, your cost doubles to twenty cents a minute. You don't want to cut too close to actual usage unless you first check the cost of additional minutes. You have to weigh that cost against the higher price of a plan that includes more minutes.

If you do a lot of long-distance telephoning, you need to consider those plans that include long distance at no extra charge. If you do a lot of traveling, you need to look for plans that do not have roaming charges. A slightly higher per-minute charge is worth it if you can save several dollars a day in roaming charges.

Now on to the Web!

### point.com

You'll find this site at [www.point.com](http://www.point.com); Fig. 1 shows the opening screen. As you

click on through, you will find three major areas to help you. The first and what I consider the most important is the "PLAN" section. Go here, fill in your zip code or city and state, and you can look at all of the cell-phone plans that are available in your area. Then you can select the features that are important to you—no contract, number of minutes, etc. The site will help search out the plans that fit your parameters. Next, you can select a number of plans you would like to compare. That will give you a side-by-side comparison of the selected plans. I selected four plans to compare. The plan comparison I found is shown in Fig. 2. Note that only three comparisons are visible; to get to the fourth one, you need to click on the "Next 1>" button at the top right.

For an even more complete comparison, one more click is needed—"Expand to see Features" at the lower right. Once you have studied all of the



Plan Comparison

Total Plans: 4 Next 1>

plan	AT&T Wireless	Alltel	Nevada Bell
<b>Plan Details</b>	Wireless \$19.99 Digital	Simply Free 125 Digital Top-Free Plan	Digital PCS Value 652
Monthly Fee	\$19.99	\$29.95	\$29.95
Minutes Included	60	125	150
Peak Airtime Rate	\$0.40	\$0.33	\$0.28
Off-Peak Airtime Rate	\$0.40	\$0.33	\$0.28
Activation Fee	\$25.00	\$30.00	\$25.00
Contract Period	1Yr(s)	1Yr(s)	1Yr(s)
Technology	Digital Cellular (TDMA/800 MHz)	Digital Cellular (CDMA/800 MHz)	Digital PCS (GSM/1900 MHz)
Call Quality	See Map	See Map	See Map
Coverage Maps	See Map	See Map	See Map
Provider Specials	See Details	None	None

Features (Expand to see Features)

Fig. 1. Welcome screen at point.com. You'll find lots of help and many choices here.

Fig. 2. Typical Plan Comparison chart created by the point.com search engine.





Fig. 3. Welcome to decide.com. Just a few more clicks and you're on your way.

**Side by Side**  
Click on a plan to see full details or click on a map for a closer look

AT&T Wireless Services	Sprint PCS	Nevada Bell Wireless	Nextel	Verizon Wireless
Digital Advantage	Free and Clear	Personal Choice	National Business Plan 1000	SingleRate
\$63.99	1000 Promo	1,100		National 900

You selected location is LAS VEGAS, NV  
Click here to change it.

Features

	\$69.99	\$75	\$89.99	\$129.99	\$100
Monthly access charge	\$69.99	\$75	\$89.99	\$129.99	\$100
Minutes included	800	1,000	1,100	1,000	900
Weekend minutes	-	-	1,000	-	-
Natal Direct Connect	-	-	-	Unlimited	-
Off-peak minute package	\$4.99/500, \$9.99/1,000 off-peak mins	\$10/200 off-peak mins	None	\$10/1,000 weekend mins	None
Peak period	7 am-7:59 pm M-F	7 am-8 pm M-F	M-F	None	None
Off-peak period	8 pm-6:59 am M-F, Sa-Su, some holidays	8 pm-7 am M-Th, 8 pm-7 am M	Sa-Su	None	None

Fig. 4. Using the decide.com comparison engine, I got this screen of my five plan choices.

options, you can move on and sign up. If you need a new telephone, continue on to the "PHONE" section and then on to "ACCESSORIES." In just a half-hour or so, you will have gone through all of the possible options, phones, and accessories without having to contact or visit each cellular provider separately.

Elsewhere in this site, you will find promotional offers and some advertising. Don't let that distract you from doing the comparisons you need and selecting the service that does the best possible job for you. You never want to lose sight of the fact that the dollars you are spending are your dollars.

**decide.com**

When you click on through to [www.decide.com](http://www.decide.com), you see the screen in Fig. 3. Again, a variety of options and tools are available to help you find a cell-phone provider. In addition to service

plans, telephones, and accessories, it is possible to select and purchase prepaid long-distance calling cards here.

In a slightly different format, you can again punch in your zip code or city/state information. Then you can examine a variety of available plans including current promotions. If you select and then compare, you'll get a screen like the one in Fig. 4. After selecting the plan, you can move on to a choice of telephones and accessories. Here, I have a suggestion. If you are going to need a new telephone, select one that has an earpiece and micro-

phone attachment, if available. In Las Vegas, where I live, Sprint is offering their customers a free earpiece and mike add-on at no charge. It's a safety feature that provides handy hands-off usage. However, if you are not careful, people around you may think that you are talking to yourself. On the other hand, perhaps that's not so noticeable in this day and age...

**WINDING DOWN**

Knowing the Internet the way I do, I realize that there are likely to be many other sites of use to those looking into new cell-phone providers. If you have any suggestions, pass them on to me and I'll look them over. I can add them into a future column to help other readers. Just e-mail me at the address at the top of the column.

Now back to the net; I've got three weeks to come up with another column! **P**

**HOT SITES**

**Point.com**  
[www.point.com](http://www.point.com)

**Decide.com**  
[www.decide.com](http://www.decide.com)




## COMPUTER VIRUSES AND OPERATING SYSTEMS: CHOOSING YOUR POISON

How many times have you heard a comment like this: "My computer is acting up. It must be a virus." The truth is, most computer glitches are caused by software conflicts or "user error." Viruses do get a lot of publicity, and it's easy to see why. They have an ominous and mysterious aura. How can a machine catch a virus? Can computer viruses, like such human viruses as HIV, be deadly?

Computer viruses are simply small computer programs whose sole aim is to do harm. They're written by disturbed individuals, the kind of sociopaths who indiscriminately slash tires or poison bottles of Tylenol. Like human viruses, computer viruses can replicate, spreading like a disease from one computer to another through shared floppy disks, infected CD-ROM discs, or over the Internet.

Some viruses—more hoaxes than true viruses—are innocuous, doing no more harm than scaring people with a message flashing on their screen that reads "Gotcha!" Other viruses can destroy all the data on your hard drive. Computer viruses can't harm your hardware. The first line of defense, as with every potential computer disaster, is to make regular backups of the vital data stored on your hard drive and to ensure that the backups themselves are reliable.

The next safety step is to consid-

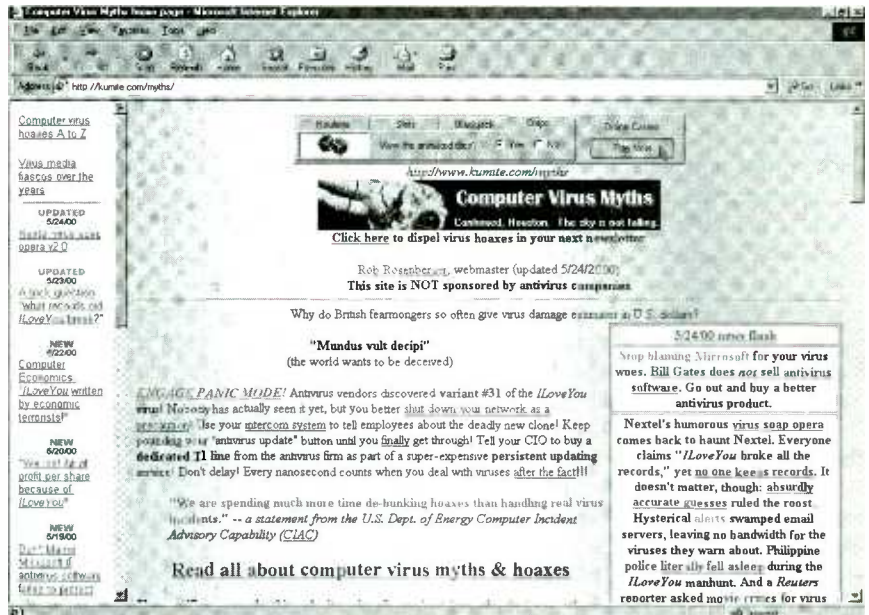


Several Web sites, such as this one, tell the tales behind some of the more well-known virus hoaxes.

er using antivirus software. Some people suspect that new viruses are created and spread by the very companies who develop antivirus programs. After all, there's a lot of money to be made here. Sales of antivirus software are over \$100 million a year, according to market research firm PC Data. According to Ziff-Davis' *Market Intelligence*, five of the ten top-selling utility programs are antivirus packages.

Virus-protection developers do what they can to keep viruses in the mind of the public. A survey by

the National Computer Security Association indicated that 99.33% of medium and large organizations in North America have experienced at least one virus infection, and that every year on average four out of every ten computers in these organizations become infected. That sounds dire indeed. But who paid for the survey? Virus-protection companies.

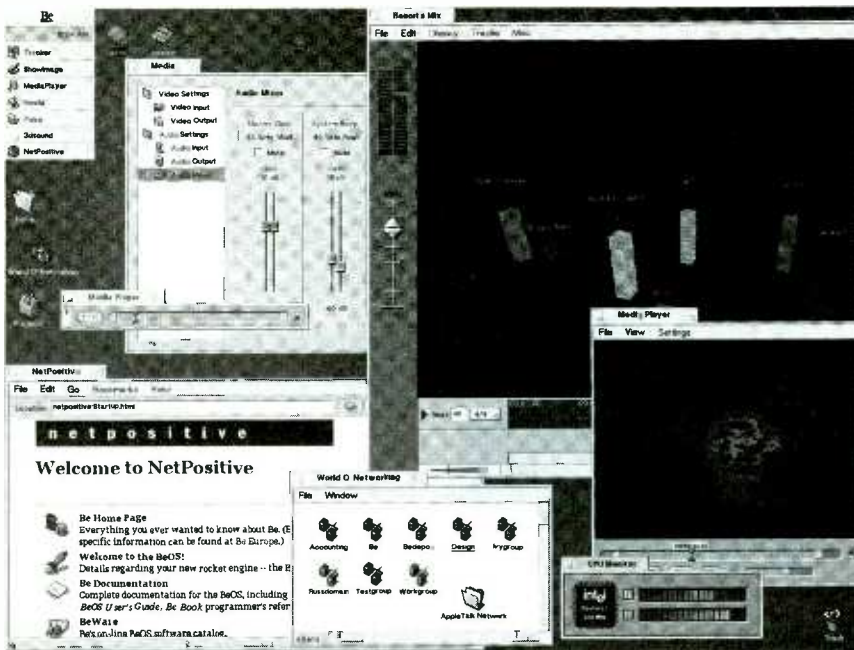It should be pointed out that the National Computer Security Association includes as one of its aims the promotion of ethical practices among



BeOS, from Be, Inc., is an alternative operating system to the one that came bundled on your machine.

virus-protection companies. There's no evidence that a virus-protection company has ever let loose a virus it was studying in its labs. What's more, despite the sensationalism, investing in an antivirus program is still a prudent course of action if you do a lot of program downloading or otherwise try out lots of new software—especially if several people have access to your PC, or if your PC is part of a local-area network. Whether you buy an antivirus program or not, don't become paralyzed by fear of viruses.

Some people avoid the Internet entirely for fear of catching a virus. A few words of reassurance: There's virtually no chance that your computer can become infected by reading e-mail messages. Viruses, as programs, must be run, or "executed," to do their damage and simply reading an e-mail message doesn't run anything except the programs you already have on your system. The situation becomes more complicated with e-mail attachments. These appendages to e-mail messages can potentially include "macro" viruses, which can infect your system and are the fastest growing type of virus. However, you have to initiate action beyond just reading the e-mail message, such as clicking on the attachment with your

mouse, for these mini-programs to do their dirty work.

## WHAT CAN YOU DO?

Fortunately, you have protection here as well. The latest versions of antivirus programs include protection against macro viruses. To be on the safe side, many people simply delete e-mail attachments, particularly if they come from someone they don't know. Even if they seem to come from someone you do know, it can be a good idea to phone the sender to verify this, since some viruses can play tricks here. You might have been sent an

infected attachment without the sender even knowing it.

It's theoretically possible for your system to become infected with a virus by visiting a Web site whose creator coded in land mines in the form of malicious Java applets or ActiveX controls, but there have been no reports of such sites. If one did appear, it would be shut down quickly.

Along with curtailing your activities, the threat of viruses can also make you scramble needlessly. If you receive an e-mail message warning about a hideous-sounding virus, it might be a hoax. The U.S. Department of Energy has created a Web page at [ciac.llnl.gov/ciac/CIACHoaxes.html](http://ciac.llnl.gov/ciac/CIACHoaxes.html) that describes virus and other Internet hoaxes. Another good virus hoax site is Computer Virus Myths at [kumite.com/myths](http://kumite.com/myths). Still, virus infections do occur, and they can cause considerable damage. Norton AntiVirus is the best all-around antivirus program, though McAfee VirusScan has many loyal supporters as well. Both cost less than \$50 for the single-user versions.

Finally, be careful out there. Download files only from reputable Web sites or FTP file repositories. Avoid "pirate" sites and the "Warez" newsgroups where people illegally trade commercial programs. These files are more likely than others to be infected with viruses.

## OPERATING SYSTEMS UPDATE

The recent release of Windows 2000, the successor to Microsoft's business-oriented Windows NT, is forcing many people to look again at their operating-system strategy. Whether you use a personal computer at work or home, its operating system affects your choice of software and hardware peripherals, your ease in loading programs and managing files, and your computer's resistance to crashes and security breaches. If the central processing unit, or CPU, is the heart of your machine pumping out data, the operating system, or OS, is the brain determining where data should go. Here's a run-down on the state of

### POINT AND CLICK

BeOS  
[www.be.com](http://www.be.com)



Computer Virus Myths  
[kumite.com/myths](http://kumite.com/myths)

Corel Linux  
[linux.corel.com](http://linux.corel.com)

Department of Energy Virus Hoaxes  
[ciac.llnl.gov/ciac/CIACHoaxes.html](http://ciac.llnl.gov/ciac/CIACHoaxes.html)

Microsoft Windows 2000  
[www.microsoft.com/windows2000](http://www.microsoft.com/windows2000)

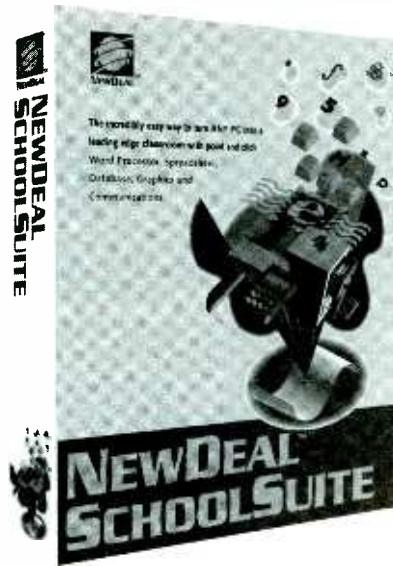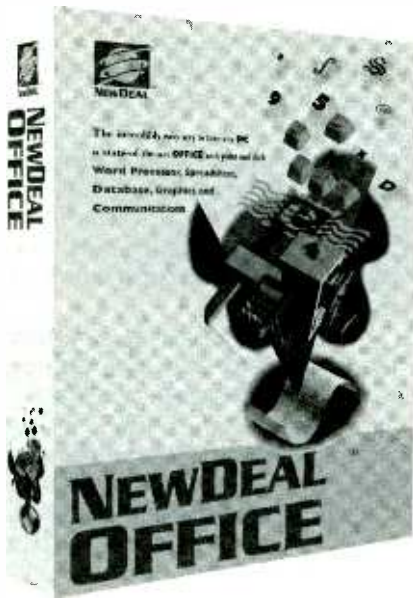NewDeal  
[www.newdealinc.com](http://www.newdealinc.com)



*NewDeal is a combination suite of applications and operating system that can run on a 10 MHz '286 with only 640K of memory. The SchoolSuite has the ability to network together—perfect for that mountain of ancient systems collecting dust in the closet.*

today's operating systems.

**Windows 2000**—This is Microsoft's best attempt yet to bring the enhanced stability and security of Windows NT to the masses. Windows 2000 ([www.microsoft.com/windows2000](http://www.microsoft.com/windows2000)) still doesn't match the stability and scalability of many Unix-based systems, but it's a good upgrade for most users of Windows NT 4.0, with an easier-to-use interface and support for USB peripherals, DVD drives, and Plug-and-Play upgrading. It's not a good choice for most Windows 98 or 95 users. Despite compatibility improvements, Windows 2000 may not support all of your programs or peripherals. You need a relatively recent computer and at least 64 megabytes of memory to run it effectively. It's also expensive, as are all Microsoft OSs—one of the few software categories that hasn't dropped in price over time.

**Windows Millennium**—For most people, the successor to Windows 98 will be a better upgrade. Windows Millennium, abbreviated as Windows ME, is scheduled for release later this year and will improve support for the hottest new technologies, such as the Internet audio format MP3, digital video editing, and home network-

ing. Reports from beta testers, however, indicate that Microsoft may remove some business networking features from Windows ME that exist in Windows 98 and 95; they allege that it's an attempt to force business users to upgrade to the more expensive Windows 2000. When it comes to Microsoft operating-system upgrades, the best decision can sometimes be to wait to upgrade until you buy a new computer that comes preinstalled with the new OS. This saves time and money and avoids potential upgrading glitches.

**Linux**—Microsoft may be the OS Goliath, but there are a few Davids out there, slingshots in hand, with the U.S. Justice Department keeping a benevolent watch on them. The most promising is Linux, the Unix-like OS once strictly for geeks but now moving slowly toward the mainstream. Corel, the Canadian company behind *CorelDraw* and *WordPerfect*, is now distributing Corel Linux ([linux.corel.com](http://linux.corel.com)), an easier-to-use version that looks like Windows 98. More Linux software is available, including Corel's own *WordPerfect for Linux*, though the selection is still dwarfed by the available Windows titles. You also may have problems getting all of

your peripherals to work with Linux systems. Linux is commonly used as a midrange server OS for delivering data and programs over networks. Nevertheless, it will likely show up in the future in more budget-priced computers as well as Internet appliances—inexpensive computer-like devices specifically for connecting to the Net.

**Low-Cost Darkhorse**—Two other inexpensive, upstart OSs, less widely known than Linux, are BeOS and NewDeal. BeOS ([www.be.com](http://www.be.com)) is available as a free download for individuals and, like Linux, will be bundled with some Internet appliances. BeOS was originally the OS for a custom-designed PC (not an IBM clone that we usually associate with the term). When Be found that selling hardware was a money-losing proposition, they targeted their OS to Apple Macintosh users. When Apple backed out of negotiations to buy it, Be shifted focus. Be customized the latest version of BeOS for Windows 98 and 95 users. Unlike Linux, you can use BeOS without having to create a separate partition on your hard disk. Still, unless you use it with an Internet appliance, it's a tool mainly for multimedia experimenters.

NewDeal ([www.newdealinc.com](http://www.newdealinc.com)) can be a good choice if you have a '286 clunker that's headed for a landfill. The product, created by the people behind GeoWorks, a former Windows competitor now used primarily in wireless devices, is a new graphical OS designed for old PCs. Its minimum requirements are just 640 kilobytes of memory, a 10-megabyte hard drive, CGA graphics, and DOS 3.0.

**Old Soldiers**—Once heralded as the successor to DOS, IBM's OS/2 is still around, but it's not being actively marketed or upgraded anymore and is used mainly by IBM's corporate customers. Finally, with its legion of loyal followers, the eminently usable Mac OS continues to improve. Mac OS 9, though still available only for Macs, makes it easier to conduct an Internet search and helps different people using the same Mac keep their desktop and Internet settings separate. P

## Socket To Me

I noticed an error in the article "The PIC Replicator" (**Poptronics**, May 2000) on page 37 regarding information on the PIC Replicator's "Socket Farm."

The error begins in the second sentence of the third paragraph. The text indicates that socket SO1 serves the 18-pin and 28-pin devices and that socket SO2 serves the 40-pin and 8-pin devices. An examination of the PC board and the schematic (which agree) would suggest that the reverse is true. Socket SO1 serves the 40-pin and 8-pin devices, while socket SO2 serves the 18-pin and 28-pin devices. I don't believe that construction and use of the PIC Replicator would be adversely effected, but readers could be confused just the same.

Also, unless I just missed it, the article didn't indicate how to position pin 1 of each device to be programmed in the respective 48-pin socket (SO1 or SO2). That too might be helpful to some readers. As always, this project is great, and I will be building and using it soon.

THOMAS SADDLER

via e-mail

*[You are, of course, correct in that the designation in the text for the PIC Replicator got SO1 and SO2 backwards. Thanks for pointing that out.]*

*While we didn't specifically say where to put the target chips when programming them, the schematic diagram on page 30 shows the relationship between the pins of the chip being programmed and the socket's pins. For example, if you were to program an 8-pin PIC, the schematic shows that you would use SO1; pin 1 of the PIC would be inserted into pin 21 of the socket.*

*If you buy an etched PC board from the source given in the Parts List, it comes with a silk screen that indicates where the target PICs should be inserted. You can see that somewhat in the photograph on page 39.—Editor]*

## PIC Replicator Update

An updated version of the PIC Replicator software (**Poptronics**, May 2000) is up on the [www.edtp.com](http://www.edtp.com) site.

PETER BEST

via e-mail

## Errors Detected

Joseph Carr's article "Non-Linear Configurations For Linear ICs" (**Poptronics**, June 2000) on "op-amp rectifiers" was interesting, but a few items seemed incorrect. I know that Mr. Carr has written many books and articles, so I expect that some of these things occur when an article is prepared for publication.

- On Fig. 3, the current flow convention for I4 (in D4) was opposite to all others.
- On p. 47, the inverting amp gain formula mysteriously changed to  $2Rf/Rin$  (from the correct version:  $Rf/Rin$ ).
- Same area: D2's voltage drop "is

### KEEP IN TOUCH

We appreciate letters from our readers. Comments, suggestions, questions, bouquets, or brickbats ... we want to hear from you and find out what you like and what you dislike. If there are projects you want to see or articles you want to submit—we want to know about them. And now there are more ways than ever to contact us at **Poptronics**.

You can write via snail mail to:

Letters  
**Poptronics**  
275-G Marcus Blvd.  
Hauppauge, NY 11788

Please note the above address is the snail-mail way to get the quickest response. Some readers send letters to our subscription address, and although the mail is forwarded to our editorial offices, it does increase the time it takes to answer or publish your letters.

The e-mail address can be found at the top of the column.

Of course, e-mail is fast.

Check your favorite columns, too. All of our columnists can be reached through the e-mail addresses at the head of each column.

And don't forget to visit our Web site: [www.gernsback.com](http://www.gernsback.com).

about 10.6 to 10.7 volts" should, I believe, read "about .6 to .7 volts."

- Below Fig. 7, the filter description should read "—that has a LONG enough time constant —"
- Dead-band circuits: The author did not show any; I was looking forward to a short piece on Schmitt triggers here.

One small point: the term "voltage follower" is usually reserved for UNITY GAIN, NON-INVERTING amps, typically used as buffers to drive filter sections, or to provide a high input impedance to avoid loading previous stages, or a circuit under test.

Notwithstanding these points, I enjoyed the article. I greatly enjoy **Poptronics**, and was a **Popular Electronics** subscriber as early as the 70s. Keep up the great work.

BRIAN KELLY

North Bay, ON, Canada

## Sorry Wrong Number

*There was a typographical error in the telephone number for Sensory, Inc. in the "New Gear" column in the June issue. The correct number should be 408-744-9000. All the rest of the company information is correct. Our apology for any inconvenience this error may have caused our readers, Sensory Inc., and the neighboring bakery that is getting inquiries for a speech recognition kit.—Editor*

## Out of Business

*We have been advised that Allegro Electronic Systems that was mentioned as the source for the ferrite core step-up transformer in the article "High-Voltage Generation" in our June issue is no longer in business.*

*We always validate our parts sources at the time the article is edited, but unfortunately we cannot guarantee its availability when the magazine gets to the readers.—Editor*

## Information Please

I can find nothing on the step-up transformer (T1) in the "Amazing

Science" column on the Geiger Counter (**Poptronics**, March 2000). Please provide more information.

RICHARD NELSON  
Phoenix, AZ

*[We asked John Iovine that question when preparing the column for publication. He did respond before our deadline, but his e-mail got stuck in the gernsback.com mail server's "bit bucket" and was never forwarded to the editorial office network. The information follows: part number-TR-02, turns ratio-57:1, DC resistance, primary-3.3 ohms, and secondary-117 ohms.—Editor]*

## Robots Rule

No question about it. **Poptronics** definitely has something for everyone who is into electronics! I have subscribed to **Radio Electronics**, **Electronics Now**, and now **Poptronics** since I was 13 years old. Even though I am now 26, it is still exciting when the magazine comes in the mail.

I am especially excited about the new addition "Robotics Workshop." With the ever-growing craze over robotics (myself included), this column will definitely be of great interest. I am looking forward to many more great robotic tips and ideas.

Keep up the great work!

BOBBY JACKSON  
Roebuck, SC

## What is a Synchro?

The "Tech Musings" column on synchros, selsyns and accelerometers (**Poptronics**, May 2000) calls the synchro a three-phase system. It is not. A three-phase system has at any instant three identical voltage amplitudes differing in phase by 120 degrees. The voltages in the synchro system are never equal and at any instant add to zero. They are in fact three single phase voltages, which are either in phase or 180 degrees out of phase with each other.

The term Selsyn is a Sperry trade name, as are Autosyn for Bendix, Telesyn for Ford Instrument Co., and many others. The British call them Magslips.

I enjoy your magazine very much and look forward to many other thought-provoking articles.

DON BURNS  
Comox, British Columbia, Canada

## More on Midi Materials

Michael Covington in his "Q&A" column (**Poptronics**, May 2000) in the

item on Midi Materials seems to have overlooked the ad on page 66 of the same issue: *Advanced MIDI Users Guide* (Catalog # PCP114) from Electronic Technology Today, Inc.

Also, *The Midi Manual* is an excellent source, although there is a typo on page-21, figure-2.13, where the code for "Note-Off" is incorrect. Aside from that it's an excellent book. It is available in most book stores, music stores, and some electronic stores.

There's also a group of MIDI-based equipment manufacturers, a kind of consortium. They would be the best source of MIDI info. After all, it's their standard.

Happy hunting.  
PARTEV SARKISSAN  
via e-mail

*[The moral of the story is check our advertisers first.—Editor]*

## Kirlian Comment

I have an interesting note in relation to the Kirlian photography effect, the subject matter of two columns of "Amazing Science" (**Poptronics**, May and June 2000). The spring issue of *21st Century Science & Technology* (<http://www.21stcenturysciencetech.com/>) has an interview with a Russian biologist, Vladimir Voeikov, who said that Konstantin Korotkov reported to the Gurwitsch Conference the use of the Kirlian effect in Tbilisi, Georgia to diagnose cancer with a 95% accuracy.

WES GORDON  
via e-mail

## A Job Well Done

My compliments on the fine editing of my manuscript, "Two Simple Zener-Diode Testers" (**Poptronics**, May 2000).

However, I did notice some items that might cause a reader some confusion. On page 43 and page 44, "microammeter" should be "milliammeter" since, although it is technically measuring microamps, the current level is beyond most standard microammeters; a milliammeter is a safer bet. This is, of course, a minor terminology correction.

However, the reference to a dual-trace oscilloscope might keep many readers from building these testers. Actually, a regular single-trace scope that has a horizontal input can be used in the same manner. I've used two old sin-

gle-trace scopes this way; and most old scopes have an "H" input, which can be selected by the sweep control.

It is a pleasure to see my work in your magazine.

FRED BLECHMAN

*[In spite of the mistakes, we hope...oops...—Editor]*

## Car Talk

I strongly agree with Tony Neiburg's letter (**Poptronics**, April 2000). We would profit greatly by automobile electric/electrical articles. We need information such as how sensors work and can be tested, what function(s) they perform, and what results when they don't work properly.

Even if today's cars are so complicated that some faults require computer analysis, this is worthless in the hands of someone without the basic knowledge of the automobile system's operation. Also, many troubleshooting procedures don't require any more than a DMM.

FRANKLIN SWAN  
Paw Paw, IL

## Haves & Needs

I have a 1920 Crosley 1-tube regenerative receiver that uses the type 0/A tube. The volume control rheostat does not have the resistance wire wound on it. I intend to rewire this resistance, but I don't know the wire diameter nor what the total resistance of the rheostat was before the wire was removed. (I bought this set at a yard sale.)

I would sure appreciate this information.  
LESTER S. HAUGSDAL  
105 2nd Avenue SW  
Choteau, MT 59422

## Frontier Engineering LLC

Over 20,000 components & electronic products to choose from:

[www.freng.com](http://www.freng.com)

628 S Sunset Longmont CO 80501  
Tel 303 776 6242 Fax 303 776 6080

To learn how to talk with your kids about tough issues, like sex, AIDS/HIV and violence, call

**1-800-CHILD-44**  
and get your free guidebook.



# CD ROM based resources for learning and designing



The internationally renowned series of CD ROMs from Matrix Multimedia has been designed to both improve your circuit design skills and to also provide you with sets of tools to actually help you design the circuits themselves.



only  
**\$50**  
(student/home)

**Electronic Circuits and Components** provides an introduction to the principles and application of the most common types of electronic components and how they are used to form complete circuits. Sections on the disc include: fundamental electronic theory, active components, passive components, analogue circuits and digital circuits.

**The Parts Gallery** has been designed to overcome the problem of component and symbol recognition. The CD will help students to recognize common electronic components and their corresponding symbols in circuit diagrams. Quizzes are included.

**Digital Electronics** details the principles and practice of digital electronics, including logic gates, combinational and sequential logic circuits, clocks, counters, shift registers, and displays. The CD ROM also provides an introduction to microprocessor based systems.



**Analog Electronics** is a complete learning resource for this most difficult subject. The CD ROM includes the usual wealth of virtual laboratories as well as an electronic circuit simulator with over 50 pre-designed analog circuits which gives you the ultimate learning tool. The CD provides comprehensive coverage of analog fundamentals, transistor circuit design, op-amps, filters, oscillators, and other analog systems.

**Electronic Projects** is just that: a series of ten projects for students to build with all support information. The CD is designed to provide a set of projects which will complement students' work on the other 3 CDs in the Electronics Education Series. Each project on the CD is supplied with schematic diagrams, circuit and PCB layout files, component lists and comprehensive circuit explanations.



**PICtutor and C for PICmicro<sup>®</sup> microcontrollers** both contain complete sets of tutorials for programming the PICmicro series of microcontrollers in assembly language and C respectively. Both CD ROMs contain programs that allow you to convert your code into hex and then download it (via printer port) into a PIC16F84. The accompanying development board provides an unrivaled platform for learning about PIC microcontrollers and for further development work.

**Digital Works** is a highly interactive scalable digital logic simulator designed to allow electronics and computer science students to build complex digital logic circuits incorporating circuit macros, 4000 and 74 series logic.

**CADPACK** includes software for schematic capture, circuit simulation, and PCB design and is capable of producing industrial quality schematics and circuit board layouts. CADPACK includes unique circuit design and animation/simulation that will help your students understand the basic operation of many circuits.

**Analog Filters** is a complete course in filter design and synthesis and contains expert systems to assist in designing active and passive filters.

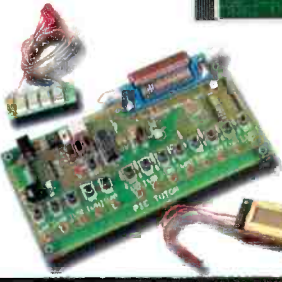


Photo shows PICmicro<sup>®</sup> development kit supplied with institution versions of C for PICmicro<sup>®</sup> and PICtutor.

**Shareware/demo CD ROM with more than 20 programs \$4.99 refundable with any purchase.**

## Order Form

Please circle the products you would like to buy on the table below calculate the total cost, fill in the rest of the order form and send it to us. Please allow 6 weeks delivery.

	Student	Institution
Electronic Ccts. & Comps.	\$50	\$99
Digital Electronics	\$50	\$99
Analog Electronics	\$50	\$99
Electronic Projects	\$75	\$159
PICtutor	\$179	\$350
C for PICmicro	\$179	\$350
Digital Works	\$50	\$99
CADPACK	\$75	\$159
Analog Filters	\$75	\$159
Postage - USA	\$0	\$0
Postage - Canada	\$5	\$5

Name: \_\_\_\_\_  
 Address: \_\_\_\_\_  
 Zip: \_\_\_\_\_ Phone: \_\_\_\_\_  
 Card Type: \_\_\_\_\_  
Mastercard, Visa, or Discover only  
 Card number:            
 I have enclosed my check for \$: \_\_\_\_\_ Signature: \_\_\_\_\_  
 Please charge my credit card for \$: \_\_\_\_\_

Phone your order to us on:  
 631-592-6721  
 or send your order to:  
 CLAGGK Inc.,  
 275-G Marcus Blvd.,  
 Hauppauge, NY 11788  
 Expire date:



Order online NOW from: [www.gernsback.com/poptronics](http://www.gernsback.com/poptronics)

## SETTING YOUR PC ON FIREWIRE

Long before there were even PCs, computer scientists were well aware that one of the greatest limitations to computer system performance wasn't processor speed, but input/output (I/O) and internal bus speed. Moore's Law, postulated by Intel founder Gordon Moore, predicted that component microprocessor density would double every 18 months. That's proven fairly accurate, but there's no equivalent prediction, or improvement, in the way data moves in and out of the system.

The real problem in this area isn't technology—we can make much faster interfaces than we can currently employ, and vendors often do construct these for special purposes. What slows down interface speeds are cost and standards. PC vendors have to have a compelling reason to add more components to their motherboards, while peripheral vendors need assurances that enough PCs will have a new interface to make it worthwhile to incorporate into their products as well.

The last interface to face this test was USB, or the Universal Serial Bus. It started off slow and has taken a few years, but USB is fast becoming truly universal. The original versions of Windows 95 didn't support USB at all, though the service releases of this operating system added supplemental support for the interface. With the release of Windows 98, however, USB support was completely integrated into the operating system. Plug a USB peripheral into a USB port, and Windows 98 usually finds it and looks for a device driver.



Studio DV from Pinnacle transfers full-screen full-video from your digital camcorder to your PC. This high-speed interface is a generation above the USB.

That's worked out well, and you'll now find at least one USB port on most desktops, laptops, and even Apple's Macintosh computers. On the other side of the usage equation, peripheral vendors are incorporating USB interfaces into printers, scanners, and even digital still cameras. For the most part, everyone is very happy with the way USB has turned out.

### NEED MORE SPEED

That "for the most part" is the real kicker. While USB is easy to use and can support up to 127 USB devices on a single PC, it has one limitation that's becoming more evident and annoying the more popular the interface becomes—speed. USB was originally developed to provide a higher-speed interface than those currently in use. Although it's done just that, the data transfer speed hasn't kept up with the growth in data-transfer requirements. Consider the output to an inkjet printer. Several years ago, printer resolution was in the neighborhood of 300 dpi. Today, average print density has jumped to 1200 dpi or higher, and new

inkjets from HP and Lexmark boast 2400 by 1200 dpi. Printing at that high a resolution takes a lot of data, and the interface speed really does begin to put a crimp in system throughput. Similar situations exist when you're scanning at high resolution or downloading image or video files.

Current USB interfaces top out at about 1.5 MB/sec. That's really fast compared to the parallel port's speed of 0.115MB/sec. USB version 2 ports are expected to start showing up in equipment this year, and they double the USB transfer rate to 3 MB/sec. Unfortunately, that just doesn't cut it when you're trying to use one of the new consumer camcorders that record the image digitally, rather than in analog format.

### FIREWIRE INTERFACE

Apple Computer came up with the answer several years ago—a very fast serial type of interface that it called *FireWire*. Apple often doesn't get much of the credit it deserves for the technical innovations it's introduced over the years. From the first Macintosh, Apple standardized on the SCSI interface for its hard disk drives. This interface not only set a level of high performance on disk operations, but enabled the easy connection of image scanners, which were SCSI-only devices when they were first introduced to the consumer market.

After Apple developed and introduced its FireWire interface in the Mac, it submitted the specifications to the IEEE. The specifications were published to the industry, and after the politicking and other spe-



cial interest infighting that usually happens when trying to get a standard established, the Institute finally issued the IEEE-1394 interface standard. Apple's current FireWire interface meets this standard, and the industry as a whole frequently uses Apple's FireWire term to refer to the IEEE-1394 interface.

The IEEE-1394 is a serial interface, in that data is sent over the bus in sequential bits. It even looks a bit like a USB port; while the connector is almost the same size, it is shaped slightly different and polarized so that the cable can only be inserted correctly.

Where FireWire/IEEE-1394 really shines is speed. The absolute transfer speed depends upon the precise implementation of the port, but the maximum speed (which is what vendors usually talk about) is up to 50MB/sec. That's not just a bit faster than even the new USB2 standard, but a *lot* faster.

With this type of data throughput, it's likely that many of the vendors that now support USB on their peripherals will also start to bring out versions with an IEEE-1394 interface. The biggest problem is the same one that slowed down the adoption of USB—not many PCs sport IEEE-1394 ports.

That's changed a bit recently. Many large-screen laptops, those with 14 or 15-inch displays, have added an IEEE-1394 port. And most of Compaq's Presario line now sport two IEEE-1394 ports—one on the front panel of the PC and the other on the rear panel. Sony has also adopted the IEEE-1394, calling theirs an *iLink* port and adding it to almost all of its VAIO models.

The largest incentive to add an IEEE-1394 port to your PC is that it's almost a "must-have" if you've purchased, or intend to purchase, a digital camcorder. Many of the consumer-grade digital camcorders, like the Canon Optura, also will output video in S-Video analog format. If, however, you plug the camcorder into an IEEE-1394 port, not only is the video downloaded much more rapidly, but you can use software on the PC to edit video in the camera, as well as control the camcorder from your PC.



*Evergreen Technologies produces this fireLINE PCI card that provides high-speed data communications between your computer and up to 63 peripherals.*

## BUYING THE BUNDLE

Adding IEEE-1394 FireWire capability to your PC is one of the easier upgrade projects you can undertake. You will, however, need at least a Pentium CPU in your system because both an open PCI expansion slot and overall system performance are needed to support the level of performance that a FireWire peripheral provides.

It's also a good idea to be running Windows 98. Windows 95 wasn't really designed with IEEE-1394 support in mind. Like USB support, if you can get a FireWire port running under Windows 95, it won't be nearly as stable as it will be under Windows 98. In fact, some vendors state Windows 98, Windows NT, or Windows 2000 as a requirement. If your PC meets these requirements, adding IEEE-1394 is as easy as opening up the case, plugging in a PCI card, and installing the requi-

site drivers when Windows 98 finds the new hardware.

IEEE-1394 interface cards are available from a growing number of sources. Adaptec offers a *HotConnect 8920* card with three IEEE-1394 ports on it. The HotConnect operates at 25 MB/sec. As with all IEEE-1394 interfaces, the card can support up to 62 devices by daisy chaining them together (plugging one IEEE-1394 device into another, with at least one of the devices plugged into the interface card).

Evergreen Technologies, best known for its line of CPU upgrades, also now offers an interface card it calls *fireLINE*. The *fireLINE* card also provides a trio of IEEE-1394 connectors and for under a hundred bucks even includes an IEEE-1394 cable. Evergreen Technologies will also be offering a PCMCIA card version of the interface for laptop owners who want to add this capability. Evergreen has a vested interest in promoting IEEE-1394; it already is shipping an external FireWire hard disk drive and has a FireWire CD-RW drive in the works.

Depending on the applications that you intend to run, you may want to purchase just the interface card, as above, or a bundle containing a card and software. Since the most common application requiring IEEE-1394 capability is video editing from a digital video source, a number of popular software applications already contain FireWire support. These include the latest version of Adobe's upscale *Premiere*, as well as the more affordable MGI *VideoWave III* and Ulead's *Video-Studio 4.0*. Add one of the cards and a digital-video source, and you're ready to go.

For this month's upgrade, however, we selected a complete bundle from Pinnacle Systems. The vendor's *Studio DV* is a complete digital-video-editing solution, priced at an affordable \$199. The interface card installs easily—it just plugs in—and an automated installation process on the CD-ROM installs the required drivers and *Studio DV* software. Unlike the two IEEE-1394 cards detailed above, the interface card in the *Studio DV* package has only

*(Continued on page 63)*

VENDOR INFORMATION	
<b>Adaptec, Inc.</b>	691 South Milpitas Blvd. Milpitas, CA 95035 408-945-8600 <a href="http://www.adaptec.com/products">www.adaptec.com/products</a>
<b>Evergreen Technologies, Inc.</b>	808 NW Buchanan Ave. Corvallis, OR 97330 541-757-0934 <a href="http://www.everttech.com">www.everttech.com</a>
<b>Pinnacle Systems, Inc.</b>	280 N. Bernardo Ave. Mountain View, CA 94043 800-474-6622 (800-4PINNACLE) <a href="http://www.pinnaclesys.com">www.pinnaclesys.com</a>



## Keyspan 4-Port USB Hub

*It's easy to add USB ports to any computer with this inexpensive little device.*

If you are using a new PC or Mac, it's more than likely that there is a USB (Universal Serial Bus) jack on its rear panel. This port is a boon. To it, you can connect a variety of new peripherals. I have an HP scanner, an HP color-inkjet printer, and an Iomega Zip drive connected there. However, to do that, I needed to expand the single port. My solution was to obtain a *Keyspan 4-port USB Hub*.

Before going further into the hub itself, let me tell you about one little trick it has made possible. Before I got the color inkjet printer, I was—and still am—using a Panasonic laser printer. I still have that printer connected to the regular printer port. Now it's a cinch to select the desired printer right from the Windows Print menu, with no switch box to deal with.

**Piled Higher and Deeper.** If four USB ports are not enough, you can add more hubs. You can add as many as four 4-port hubs in succession. Therefore, you can end up with 3+3+3+4 or 13 USB ports. If you cascade hubs, any hub that is downstream from a bus-powered hub must be used in its self-powered mode (more details about that later). However, the more devices that you attempt to use at the same time, the slower the connection. In my case, I never use any of the three devices that I have connected at the same time, so it makes no difference at all to me. If I were to print a long document while using my scanner, it would work; both the printer and scanner speeds would be somewhat reduced. How much depends on the specific actions being performed.

My Keyspan hub is housed in a small, somewhat transparent tangerine-colored box that measures a mere  $4\frac{1}{4} \times 3\frac{1}{2} \times 1$  inches that



you can tuck in just about any little corner. They do come in a wide spectrum of seven different colors; you're bound to find one that suits your tastes.

Installing it was a cinch. After taking it out of the box, I plugged the cable that comes with it between the computer and the hub, connected the power supply, and my computer running Windows 98 told me "new hardware detected." A few moments later, it found and installed the software. With the three peripherals plugged in, it was up and running.

**Supplying Power.** An important point here is that the Keyspan hub offers you two different power modes. You can run it as a powered hub (with a power supply plugged into the wall) or you can run it unplugged and let the hub draw its power from the USB port. Of course, you will have to find a place to plug in the little power supply if you want to use it. As a self-powered hub, each downstream port gets 5 volts DC at 500 mA. If it is not plugged in, only 100 mA is available to the peripherals. As I mentioned earlier, if you cascade hubs, any hub that is downstream from a bus-powered hub must be used in its self-powered mode.

All devices connected to the hub are connected via a USB device cable. Full-speed devices (printers and scanners fall into this category) are restricted to a maximum cable length of about 16 feet (5 meters). Low-speed devices

(mice, keyboards, joysticks, and most adapters—USB-to-serial, USB-to-parallel, and USB-to-Ethernet) restrict cable length to about 10 feet (three meters).

There are six LEDs on the top of the hub. Two of them are red. One lights when the hub is operated in its self-powered mode. Both stay dark if the hub operates in the bus-powered mode. The four port LEDs turn green as soon as the hub has registered on the USB.

**Problems, Problems.** I haven't had any problems with the hub, but problems do come up from time to time. Most of them can be cured by disconnecting the hub from its power source for a moment—just unplug and replug the power supply. If one of the devices that you have connected to the hub does not operate as it should, here are some things that you can try: Check to see that the cables are securely connected—you'd be surprised how often a cable manages to work itself loose; also, the hub or the device may have created a power over-limit condition. Usually your computer will alert you to this kind of problem.

Keyspan maintains support for its products. You can go to [www.keyspan.com](http://www.keyspan.com) on the Internet, or during normal business hours, Pacific Time, call 510-222-8802 and ask for technical support. By the way, this \$39 device comes with a five-year warranty.

The Keyspan device works for me. If you need a USB port, take a look at it. For more information, contact Keyspan at either [www.keyspan.com](http://www.keyspan.com) or write to Keyspan, a division of InnoSys, Inc., 3095 Richmond Parkway, Suite 207, Richmond, CA 94806 or circle 80 on the Free Information Card. P

# Prototype

## "Faster Than a Speeding Bullet"

**N**ew polymers developed by chemists and engineers at the University of Washington (UW) and the University of Southern California (USC) appear to achieve speed and capacity increases so great that they will revolutionize telecommunications, data processing, and sensing and display technologies.

The materials are used to create polymeric electro-optic modulators, or "opto-chips." These microscopic devices perform functions such as translating electrical signals—television, computer, telephone, and radar—into optical signals at rates up to 100 gigabytes per second (a gigabyte is 1 billion bytes). Polymeric electro-optic materials can achieve information-processing speeds as great as ten times those of current electronic devices and have significantly greater bandwidths than electro-optic crystals currently in use. In addition, the new materials require a fraction of a volt of electricity to operate, less than one-sixth of what crystals require.

### Real-Time Communications

"These electro-optic modulators will permit real-time communication. You won't have to wait for your computer to download even the largest files," said Larry Dalton, a chemistry professor at both UW and USC, who is the overall leader of the research and has full research teams at both universities.

The breakthrough resulted from research by Dalton; William Steier, a USC electrical engineering professor; Bruce Robinson, a UW chemistry professor; and USC graduate students Cheng Zhang and Hua Zhang. (Their work is described in the April 7 edition of *Science*.)

### Technology With Bandwidth to Burn

Polymeric electro-optic modulators



New polymers that are being developed appear to achieve great speed and capacity increases. Larry Dalton, a chemistry professor at both the University of Washington and the University of Southern California, is the overall research leader in this area at both universities.

can be used for information processing, to steer radio waves and microwaves to and from telecommunications satellites, to detect radar signals, to switch signals in optical networks, and as optical gyroscopes to guide planes and missiles.

They serve as a bridge between electronics and fiber optic, providing huge capacity with very low noise disturbance and very low power requirements. They are being tested for ultra-fast analog-to-digital conversion, optical switching elements in flat-panel displays, and voltage sensing for the electric utility industry,

Dalton said. Currently, the most commonly pursued applications include signal transducers for cable television, directional couplers or routing switches in optical communications networks, and modulators in phased-array radar systems.

"It's a critical decision-determining technology because bandwidth, bandwidth, bandwidth—like location, location, location in real estate—is critical in making decisions in communications technology," Dalton said.

"This technology has bandwidth to burn."



A researcher works with the polymeric electro-optic modulators or "opto-chips" in a clean room.

## Testing and Applications

During testing at Tacan Corp. in Carlsbad, CA, two other co-authors of the *Science* article—lead author Yongqiang Shi (now of Lucent Technologies) and James Bechtel—used the devices to translate electronic cable television signals into optical signals using less than one volt of electricity. Researchers at Lockheed Martin Corp.'s research laboratory in Palo Alto, CA have since replicated those results in tests involving other applications.

Tests indicate that a single modulator measuring one micron (about .000039 inch) can provide more than 300 GHz of bandwidth—enough to handle all of a major corporation's telephone, computer, television, and satellite traffic.

Other applications are so far ranging, Dalton said, that they even create the capability of full three-dimensional holographic projection with little or no image flicker. That makes possible a device such as the science-fictional holodeck, where characters in the "Star Trek: The Next Generation" television series and movies create elaborate holographic worlds in which they live their fantasies.

The research, funded by the National Science Foundation, the U.S. Air Force Office of Scientific Research, and the Office of Naval Research, is aimed at developing new materials based on the principles of condensed-matter theory. Design and molecular synthesis are done at UW; and materials are then sent to state-of-the-art production facilities at USC, where the modulators are fabricated and integrated with both silica fibers and VLSI silicon chips.

The electro-optic modulators in use today are grown as lithium niobate crystals and, rather than being integrated into silicon chips, must be hard wired. Besides having far less capacity and requiring substantially more electrical power than the new materials, they also have greater signal loss because of electronic interference and generate substantially more heat. The special properties of the new polymers, including low heat generation, are particularly important for futuristic device application, Dalton said.



Designer and engineer Bill Dube (left) and another team member assemble a new pack of Bolder TMF cells into the KillaCycle.

## More Power to You

**T**he "KillaCycle" set the current record as the world's quickest electric motorcycle. It was set by 23-year-old Kerry Hogan the first day she drove the bike on a dragstrip on March 18, 2000—10.539 seconds @116.565 mph. Designed, built, and until recently driven by engineer Bill Dube, the KillaCycle does 0 to 60 mph in 2.9 seconds. That's a lot like being shot out of a cannon, according to Dube.



Record-breaking driver Kerry Hogan on the KillaCycle.

The bike is a product of the marriage between state-of-the-art battery technology and old-fashioned "do-it-in-the-garage" workmanship, using a converted '77 Kawasaki KZ100 frame. The batteries are thin-metal-film lead-acid cells, each about the size of a roll of Lifesavers, developed and manufactured by Bolder Technologies, Inc. in Golden, CO, for their new SecureStart automobile jump-starter. Six of these powerful little cells are enough to start a car. The cycle uses 456 of them, interconnected

in such a way as to produce a nominal open-circuit voltage of 304 volts and up to 3000 amps (at about 150 volts). The 92-pound battery pack supplies a peak power of about a third of a million watts during a run down the dragstrip, enabling the two 7-inch-diameter traction motors to churn out well over 300 horsepower.

"Based on the performance I have seen to date, I believe that when the full power potential of TMF cells is exploited, electric vehicles can have a power-to-weight ratio greater than that found in high-performance engines," Dube said. "The TMF cells have the greatest power-to-weight ratio of any battery currently in production. This makes TMF cells ideal for applications requiring high amperage for short periods or the ability to recharge very quickly."

Constructed with an extremely thin lead foil, TMF batteries are wound tightly to achieve the maximum amount of surface area in the smallest volume. More surface area equates to more power. Unique cast-on end connectors transfer the energy efficiently in and out of the battery cell, eliminating the "power bottleneck" common with ordinary batteries. Think of it as a battery built like a capacitor.

Manufactured using inexpensive, readily available raw materials, the batteries have numerous advantages. This technology does not suffer from the memory effect that reduces the capacity

of nickel-cadmium batteries when they are discharged and recharged repeatedly. In high-power applications, such as engine starting and standby-power systems, TMF batteries can do the same amount of work as much larger, commercially available rechargeable batteries. They can be recharged rapidly; have very stable voltage, even during high rate discharge; and their low impedance greatly reduces the amount of heat generated by the battery, simplifying product design.

All batteries lose capacity as the temperature drops. TMF batteries lose significantly less of their room temperature capacity at lower temperatures than other commercially available batteries.

TMF technology is a breakthrough technology enabling new applications that were previously impossible. Designed to quickly and efficiently deliver high bursts of power, TMF cells may enable new applications such as high-performance hybrid electric vehicles. The KillaCycle is one example of such an application, and Dube hopes to continue breaking new records with it. **PT**

## High School Robot Competition

**T**eams consisting of two robots each competed with similar robot buddy pairs during a high school "botball" tournament at NASA Ames Research Center on March 18<sup>th</sup>. There were 26 teams from 19 California high schools participating in the tournament, in which approximately 50 student-made robots attempted to put the most Ping-Pong balls into a moveable target within a set time limit. Each team had two small robots that cooperatively worked together to accomplish the goal, one of which had a bigger computer processor than the other. The machines operated on a smooth, 4- by 8-foot surface.

Organizers designed the event to excite high school students about engineering, science, and mathematics. Teaming up with engineers from businesses and universities, students get a hands-on, inside look at the engineering profession. In six intense weeks, students and engineers work together to brainstorm, design, construct and test their

"champion robot."

"If you talk to the kids, you'll find that they've seen robot wars on TV during which machines try to destroy one another; we don't do that in the botball tournament," said NASA Ames engineer Terry Grant, who volunteered to help students and teachers. He added that the robots are allowed to block each other.

"The challenge is for the team to design their buddy robots to work together," Grant said.

This year's tournament had about 50 percent more participants than a similar contest last year. Schools receive robot kits, each with hundreds of parts as well as sensors, motors, two battery-powered microcomputer/controllers, and programming software.

The botball program teaches students C computer programming, as well as increases their skills and interests in physics and design. Teachers attend a three-day hands-on tutorial to learn how to use the robotics kits.

Students assemble the mini-robots with help from teachers and representatives of the sponsoring organization, but the students themselves program the robots. The robots must operate on their own; no remote control is permitted during the contest. The schools provide desktop computers and workspace. Assembly of the robots requires no machine tools or electronics laborato-



One of the California high school teams participating in the tournament at NASA Ames, in which the student-made robots attempt to put the most Ping-Pong balls into a moveable target within a set time limit.

ries. The schools retain the robotic equipment for educational use.

The program provides hands-on education by connecting students with companies, government agencies, and colleges. The project is co-sponsored by NASA Ames and the non-profit KISS Institute for Practical Robotics, University of Oklahoma, Norman, OK, and numerous other organizations. **PT**

## Looking Forward

**I**n the 21<sup>st</sup> century, particle-atom trapping experiments will provide scientists with more accurate measurements of particle lifetimes and with improved understanding of the weak force, which controls radioactive decay. Weak force is one of the four forces that order the universe. The others are gravity, electromagnetism, and the strong force. Cosmologists eventually will use the data from trapping experiments to refine models of the early formation of the universe.

Atoms and the fundamental units they are made of—electrons, neutrons, and protons—typically zip around the universe at speeds that make them extremely difficult to study. In recent years, however, researchers have slowed atoms to a relative crawl by capturing them in optical and magnetic traps. This ability to trap large numbers of atoms allows researchers to conduct fundamental physics experiments with greater precision than previously possible.

Researchers at Los Alamos National Laboratory developed an atom trap in 1997 that held up to six million radioactive atoms, 100 times as many as any previous effort. The magneto-optical trapping technology uses lasers to trap and cool radioactive rubidium-82 atoms from room temperature down to less than one-millionth of a degree above absolute zero. The process uses six laser beams to trap the atoms as a glowing, millimeter-sized cloud in the center of a chamber. Researchers count the number of atoms in the trap by measuring the amount of fluorescent light emitted by the cloud.

Antiproton trapping research at the Laboratory involves long-standing collaborations with scientists around the world. Los Alamos scientists are partici-

## ► Medical Image Developments

Using medical robotics and imaging combined to improve surgical procedures and success rate is the goal of the Epidaure project. Based in southern France in the Sophia Antipolis INRIA Unit (France's National Institute For Research in Information Technology And Automation), Epidaure is directed by Nicholas Ayache, who leads a team of twenty researchers. Its objective is the design and development of new tools for the analysis of medical images, including tomography, magnetic resonance imaging, ultrasound, and nuclear medicine.

The combination of these tools and images makes it possible to construct virtual models of patients' organs. Surgeons are then able to interact with these models and perform surgical simulations. Using the simulator, the surgeon can manipulate the organ model interactively and virtually repeat the precise surgical movement before intervention without risk to the patient. This tool is particularly suitable for laparoscopic surgery.

Recently, the Epidaure team, in collaboration with outside partners and teams from INRIA, successfully detected and measured changes in multiple sclerosis lesions from cerebral brain images that were acquired at regular intervals. These researchers are on the verge of extracting movement parameters from cardiac images that can be used for the early diagnosis of cardiovascular disease. In collaboration with Ircad, Ayache and his team designed an experimental prototype simulator for liver surgery, pictured above, for the training of manual dexterity in laparoscopic surgery.

In forthcoming work, Epidaure is hoping to develop the modeling of physiological phenomena, such as blood pressure and flow rate, and the use of heads-up display devices for other applications. **PT**



Shown here is an experimental prototype simulator for liver surgery, designed by the Epidaure project for the training of manual dexterity in laparoscopic surgery.

pating in the ATHENA (AnTiHydrogen-ENApparatus) Experiment now under way at CERN, which hopes to produce anti-hydrogen atoms at low energies, capture the atoms in a magnetic trap, and compare the energy levels of antihydrogen to those of hydrogen.

In 1999, Los Alamos researchers were part of a collaboration that successfully confined neutrons in a three-dimensional magnetic trap to determine how long it takes them to decay. Using the reactor at the Center for Neutron Research in Gaithersburg, MD (part of the National Institute of Standards and Technology), neutrons were directed down the beamline into a neutron trap filled with helium chilled to minus 460°F. A fraction of the billions of neutrons created by the reactor beam were confined in the long, narrow trap, which held the neutrons in the supercold liquid helium until they decayed approximately 12 minutes later.

Atom trapping holds the promise for developing sophisticated tools for use in

basic nuclear physics research, cold atomic physics, and ultrasensitive detection for nonproliferation applications. Because the atomic trapping process is extremely selective and sensitive, it can make isotopic ratio measurements in samples as small as 10,000 atoms. This makes it an important tool for nuclear treaty verification and nonproliferation. **PT**

## Reducing Medical Errors


At a time when President Clinton has announced that he will order all hospitals in the United States to take steps to reduce medical errors, Motorola's Healthcare Communications Solutions group has developed a message-alert system that is designed to facilitate the communication needs of physicians. DocLink, in its final stage of development, could significantly increase the timeliness of delivering critical patient information to

physicians.


The DocLink system is a hardware, software, and communications services solution that improves the time-consuming, manual notification process now in place at most health systems and large hospitals. DocLink's clinical information routing system is designed to send clinical information systems' message alerts to clinician's current communications devices, including pagers, cellular telephones, fax machines, office telephones, and personal computers. The system routes each message alert based on the clinician's pre-determined schedule and the alert's priority. Core features include escalation capabilities that route message alerts to another designated clinician if the primary alert recipient doesn't respond to the message; forwarding capabilities to ensure that the message alerts get delivered to the right clinician; and password-protected access to the system. All these features enhance timely delivery of message alerts to clinicians when, where, and how they specify.

The DocLink system has completed its "alpha" test at Washington University School of Medicine and its teaching institution, Barnes-Jewish Hospital. The results of the DocLink system alpha test showed a reduction in cycle time (measured from "drug order start to drug order stop"). The cycle time improved from 27 hours in daily batch processing mode to four hours in real-time, a 33 percent improvement in the pharmacists' response time when he or she concurred with the system-generated message alert. In addition, pharmacist response times were also reduced when the pharmacist did not concur with the alerts because the dose had already been changed, drug discontinued, patient discharged, or the lab result changed.

"Inadequate communication technology is considered one of the factors contributing to the medical errors problem," said Jim Hubbard, business director of Motorola's Healthcare Communications Solutions group. "More effective and timely communication between physicians, labs and pharmacies creates the need for a better system that can assist physicians and hospitals in obtaining critical information on an immediate basis." **PT**

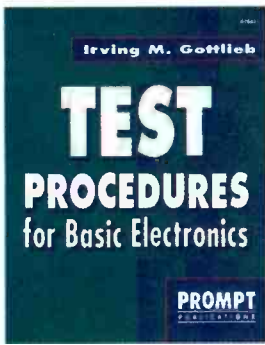


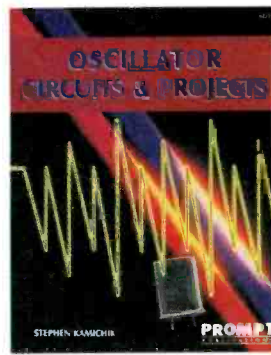Test Procedures for Basic Electronics. #61063. — \$19.95  
Many useful tests and measurements are covered. They are reinforced by the appropriate basic principles. Examples of test and measurement setups are given to make concepts more practical. 7 3/8 x 9 1/4", 356 pp, paperback.




Oscillator Circuits and Projects. #61111. — \$24.95  
A Textbook and project book for those who want to know more about oscillator circuits. You can build and enjoy the informative and entertaining projects detailed in this book. Complete information is presented in an easy-to-follow manner. 7 3/8 x 9 1/4", 249 pp, paperback.

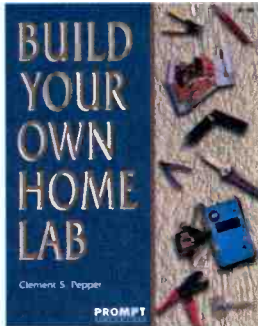
Build Your Own Home Lab. #61108 — \$29.95  
Shows you how to assemble an efficient working home lab, and how to make it pay its own way. Includes projects for creating your own test instruments too. 7 3/8 x 9 1/4", 249 pp, paperback.



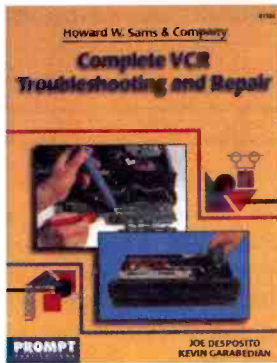Troubleshooting and Repair Guide to TV. #61146. — \$34.95  
Repairing and troubleshooting a TV is very simple and economical with help from the information in this book. It is the most complete and up-to-date TV repair book available, with tips on how to handle the newest circuits. 8 1/2 x 11", 263 pp, paperback.




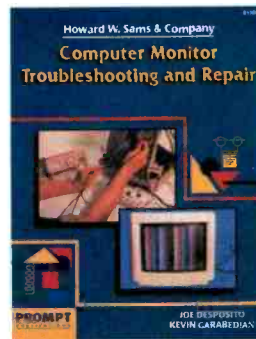Complete VCR Troubleshooting and Repair. #61102. — \$34.95  
Though VCRs are complex, you don't need complex tools or test equipment to repair them. This book contains sound troubleshooting procedures that guide you through every task. 8 1/2 x 11", 184 pp, paperback.




Computer Monitor Troubleshooting and Repair. #61100. — \$34.95  
This book can save you the money and hassle of computer monitor repair by showing you how to fix it yourself. Tools, test instruments, how to find and solve problems are all detailed. 8 1/2 x 11", 308 pp, paperback.

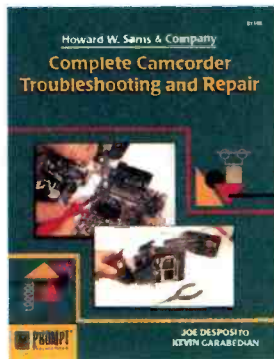Complete Camcorder Troubleshooting and Repair. #61105. — \$34.95  
Learn everything you need to know about the upkeep and repair of video camcorders. Start by examining camcorder troubleshooting procedures, then move into more advanced repair techniques. 8 1/2 x 11", 208 pp, paperback



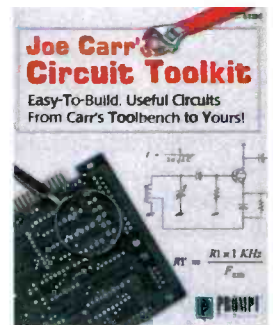Joe Carr's Circuit Toolkit. #61181. — \$29.95  
Easy-to-build, useful circuits from Carr's workbench to you. They will spark new ideas in your day-to-day use of circuits and help solve frustrating problems. 256 pp, paperback. Contact Jim Surface.



Please circle the products you would like to buy on the page above, calculate the total cost, include shipping charges, using in the form below and send it to us. Please allow 4 - 6 weeks for standard delivery.

Name: \_\_\_\_\_  
Address: \_\_\_\_\_  
Zip: \_\_\_\_\_ Telephone: \_\_\_\_\_  
I have enclosed my check for \$: \_\_\_\_\_ Signature: \_\_\_\_\_


Please charge my credit card for \$: \_\_\_\_\_ Number: [ ] [ ] [ ] [ ] [ ] [ ] [ ] [ ] [ ] [ ]

Card Type: \_\_\_\_\_ Expiration Date: [ ] [ ] [ ] [ ] [ ] [ ]  
Mastercard, Visa or Discover only

Note: The delivery address and the address at which the credit card is registered must be the same.

SHIPPING CHARGES IN USA.  
CANADA ADD \$5.00  
1 Book \$ 5.00  
2 Books 8.00  
each add'l book 3.00  
2 Day UPS \$10.00 extra  
Next Day UPS \$20.00 extra

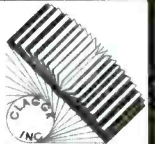Claggk Inc.  
PO Box 12162  
Hauppauge, NY 11788  
Tel: 631-592-6721  
Fax: 631-592-6723  
email: claggk@gemsback.com



SORRY No orders accepted outside of USA & Canada No. of Books Ordered

Total price of books.....\$.....  
Shipping (see chart).....\$.....  
Subtotal.....\$.....  
Sales Tax (NYS only).....\$.....  
Amount Enclosed.....\$.....

All payments must be in U.S. funds! CL04

## Sound Spectrography

**Q** In the February 2000 issue, you answered a question about measuring voice frequency by recommending an oscilloscope or frequency counter. How about a sound spectrograph, such as Spectrogram, available free at <http://www.monumental.com/rshorne/gram.html>? This software works with your sound card to analyze any sound into its component frequencies and will even display the pitch of the dominant tone in standard musical notation.

—Peter Schneider, Worcester, MA

**A** D'oh! I'm especially embarrassed because, for my day job, I'm a computational linguist, and I use such things in the classroom. Usually I use a different piece of software, *SpeechView*, available free from <http://cslu.cse.ogi.edu/toolkit/> (the Oregon Graduate Institute); it's depicted in Fig. 1. Although it doesn't do musical notation, it has more features for analyzing speech and has a cursor that you can place anywhere to read out the pitch of the voice.

Both of these programs are good. *Spectrogram* is smaller and downloads more quickly. *SpeechView* is part of a much larger download (a total of about 28 megabytes) that includes many other software tools.

Thanks also to Joe Heck, who wrote with a similar suggestion.

## Laser Pointer as Remote Control

**Q** I need a circuit to control super-bright LEDs that are used to substitute for candles on a wreath high above the altar of a church. Running wires to it is not feasible, but I need a way to turn it on and off, as well as very long battery life. Also, could I use a pulse circuit to keep the lights from steadily draining the battery?—F. A., West Hartford, CT

**A** Try the circuit shown in Fig. 2, powered by a 6-volt lantern battery. The load can consist of LEDs with resistors or incandescent lamps; you might get a very nice candle effect by running 12-

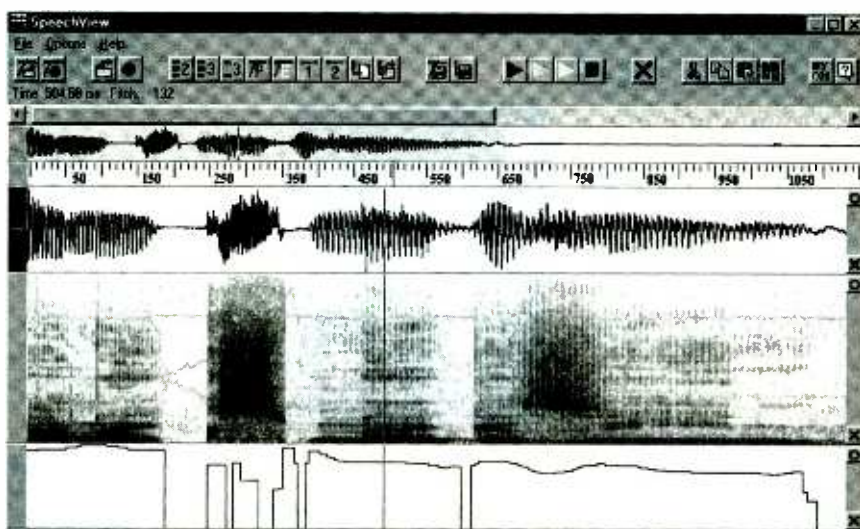


Fig. 1. SpeechView, from the Oregon Graduate Institute, has many different features and tools for analyzing speech and the human voice.

volt lamps on 6 volts.

Turn the lights on and off by hitting one or the other CdS photocell with a laser pointer. In the "off" state, less than one mA is drawn from the battery.

The circuit uses the hysteresis (latching) property of the LM555 IC, but you should actually use a CMOS version of the chip (LMC555, TLC555, or 7555) to save power. When the input is below  $\frac{1}{3}$  of the supply voltage, the output turns on. When the input is above  $\frac{2}{3}$  of the supply voltage, the output turns off. When the input is in between, the output stays in whatever state it was already in.

Thus, when the two photocells are receiving the same amount of light—whatever that might be—the load stays on or off. When you hit one photocell

with the laser pointer, you lower its resistance dramatically and the input voltage swings to +V or ground as the case may be; then, the 555 switches state.

You'll need two photocells that are reasonably well matched. One way to get them is to buy an assortment (such as RadioShack 276-1657) and use an ohmmeter to find two that are alike. At very low light levels, they are unlikely to be well matched no matter how carefully you pick them; resistors R1 and R2 swamp out the unpredictable, high resistance of the photocells in the dark. You may be able to further save battery power by using higher values for R1 and R2, such as 47k or even 220k.

Unfortunately, there's no way to avoid having a steady drain on the battery

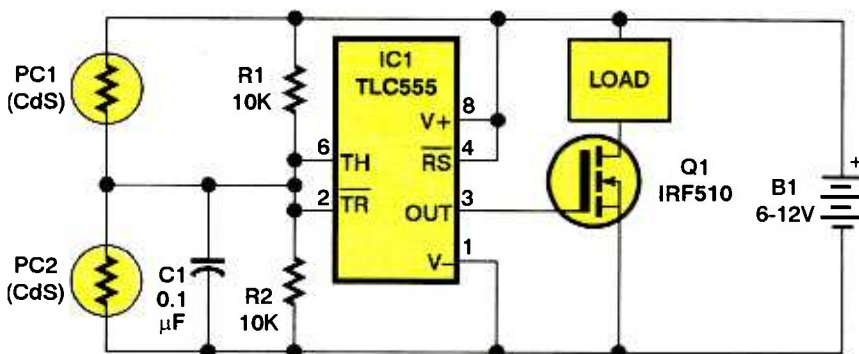


Fig. 2. This simple circuit will let you turn a load on or off depending on which photocell is lit.



when your artificial candles are on. The battery has to supply the energy that comes out of the LEDs in the form of light. Pulse circuits save power by flashing the LED (see this column, last month). If you try to smooth out the pulses with a capacitor, you'll find the voltage is too low—you can't get more energy out than you put in.

## TV Becomes Video Projector?

**Q** *How can I make a video projector by adding a lens to a TV set? I know the picture needs to be upside down and the brightness needs to be increased.—M. K., Plainview, NY*

**A** The short answer is you can't. The brightness of a TV can't be increased very much without burning up the phosphor on the screen. A video projector requires a lot more brightness and hence a special CRT.

To see why, suppose you're projecting onto a screen 5 times the width of the CRT. This is 25 times the original area, so you'll need 25 times as much light—and that's assuming that your lens picks up all of the light emitted by the screen. In real life, the lens picks up only a small fraction, so you need far more brightness than a conventional CRT can deliver.

## Stuck VCR Problem Solved

**Q** *In your February issue, F. A. asked about a Magnavox VCR that seemed to be stuck in play mode. The problem has to do with how the VCR distinguishes ordinary tapes from prerecorded tapes. When an ordinary tape is inserted, the VCR closes the write-protect tab switch to pull a logic line low for normal operation. The switch is located in the lower left-hand area of the chassis under the cassette basket.*

*However, the contacts occasionally oxidize, which means that the switch is never closed. That activates a "feature" of the VCR called AutoPlay. The VCR believes the tape is pre-recorded, automatically playing it as soon as it is inserted. With this feature activated, the tape will automatically rewind at the end, eject, and the VCR will shut down.*

*To solve the problem, the switch can be replaced or its contacts cleaned.*

*—Roy L. Huether, Glendive, MT*

**A** Thanks! We also thank Richard Reed, who wrote in with the same informa-

tion and points out that sometimes the problem is in the tape cartridge rather than the VCR.

## Another Ham Theory

**Q** *Regarding your January column, I think the term "ham" radio came from Hammarlund Manufacturing Company, which made equipment used by early hams.—L. J. H., Portland, OR*

**A** Nice theory, but Hammarlund started a business in 1910 and amateur telegraph experimenters were called "hams" before that, in fact before radio was even invented. See [http://www.arrl.org/why\\_ham.html](http://www.arrl.org/why_ham.html).

I stand by my opinion that "ham radio" is related to "ham actor," which dates from 1882 (if not earlier), or maybe from "ham-handed" or "ham-fisted" (describing an inept telegrapher). There may be historical evidence somewhere that will tell us which is correct. Anyone can guess the origin of a word, but proving that a guess is right is not always easy.

## Zenith Mystery Solved?

**Q** *I'll bet that the late-1980s Zenith TV with the intermittent failure described in your April column is a 25-inch color console. Unplug your television, discharge the picture tube, and pull the main circuit board—the wires are numbered to make it easy to put them back. Look for a shiny tin cover next to the flyback transformer. Unsolder it. Inside it is a 100- $\mu$ F, 25-WVDC capacitor that controls the brightness/contrast voltage to the picture tube. This capacitor has shifted in value, making the high-voltage system shut down. Replace it.*

*—Matthew Martin, Alliance, NE*

*Have your reader check the main circuit board for a burned open (intermittent) solder connection on one lead of a large power diode in the low-voltage power supply.*

*—Larry Jacob, Goodyear, AZ*

*Look for a defective capacitor in the power-supply circuit, probably near the VR chip. An ESR meter is the best troubleshooting tool. Capacitor failures are often temperature-related.—Stan Bogovich, Daytona Beach, FL*

**A** There you have it, folks—three possibilities, two of which involve capacitors. Electrolytic capacitors are the sec-

ond most failure-prone parts in modern equipment. Connectors and solder joints are the first.

## Repairman's Blues

**Q** *I have owned and operated a consumer-electronic repair shop for over 12 years. Lately more than ever, I have been frustrated trying to tackle intermittent problems. Some of these complaints simply would not reveal themselves while the equipment is on the test bench.*

*The real problem in some cases is trying to explain to the customer that there is nothing that I can do to pinpoint the problem because as long as the circuit operates properly, everything tests OK. Sometimes a customer says, "With all that fancy equipment, you should be able to tell what the problem is," or "Maybe you just don't know what you're doing," and "I'll tell all my friends not to come here!"*

*Is there anything that can be said to even the most simple-minded customers to make them understand the situation? If not, can you at least confirm what I've said so I can at least show the customer your magazine?—S. B., Daytona Beach, FL*

**A** You're right—intermittents are very frustrating (try fixing computers, which is what I do a good bit of the time!) I assume that you've tried all the usual things, such as warming the equipment up, raising or lowering the line voltage, and using hair dryers and cooling spray to induce temperature shifts.

Sometimes, simply transporting the equipment will shake up a loose connection and cure the problem, temporarily or permanently. Sometimes the intermittent problem is actually at the customer's site, in a wall outlet or an RF-interference source.

Often, though, intermittents are impossible to track down. There is a solution—simply replace the whole circuit board. It's expensive, but it's how intermittents are handled in industrial electronics. It's also how auto repair is often done. How many cars have had their whole microcontroller system replaced because of one loose connection? The customer doesn't want it diagnosed; he wants it fixed and will pay a high price for it.

Tell the customer that the equipment can be repaired, but it's not cheap. Explain it this way: "One of the parts is just starting to wear out, but because it's not worn out yet, I can't tell which one. The best thing to do is to keep using it until the defective part wears completely out. Then it will be cheap and easy to find and fix. If you want it fixed now,

it will cost more because the problem is not yet identifiable, so I have to replace all the parts that might be at fault. If I test everything, I'll find that lots of parts are showing their age, but I still won't know which one is causing this particular problem."

## Writing To Q&A


As always, we welcome your questions. The most interesting ones are answered in print. Please be sure to:

(1) include plenty of background information (we'll shorten your letter for publication);

(2) give your full name and address on your letter (not just the envelope);

(3) type your letter if possible, or write very neatly; and

(4) if you are asking about a circuit, include a complete diagram.

Questions can be sent to Q&A, **Poptronics Magazine**, 275 G Marcus Blvd., Hauppauge, NY 11788, or e-mailed to [q&a@gernsback.com](mailto:q&a@gernsback.com), but please do not expect an immediate reply in these pages (because of our backlog) and please don't send graphics files larger than 100K. Due to the volume of mail, we regret that we cannot give personal replies. 

## HOW TO GET INFORMATION ABOUT ELECTRONICS

**On the Internet:** See our Web site at [www.gernsback.com/poptronics](http://www.gernsback.com/poptronics) for information and files relating to **Poptronics** and our former magazines (**Electronics Now** and **Popular Electronics**) and links to other useful sites.

To discuss electronics with your fellow enthusiasts, visit the newsgroups *sci.elec.tronics.repair*, *sci.electronics.components*, *sci.electronics.design*, and *rec.radio.amateur.homebrew*. "For sale" messages are permitted only in *rec.radio.swap* and *misc.industry.electronics.marketplace*.

Many electronic component manufacturers have Web pages; see the directory at [www.hitex.com/chipdir/](http://www.hitex.com/chipdir/), or try addresses such as [www.ti.com](http://www.ti.com) and [www.motorola.com](http://www.motorola.com) (substituting any company's name or abbreviation as appropriate). Many IC data sheets can be viewed online: [www.questlink.com](http://www.questlink.com) features IC data sheets and gives you the ability to buy many of the ICs in small quantities using a credit card. You can also get detailed IC information from [www.icmaster.com](http://www.icmaster.com), which is now free of charge although it formerly required a subscription. Extensive information about how to repair consumer electronic devices and computers can be found at [www.repairfaq.org](http://www.repairfaq.org)

**Books:** Several good introductory electronics books are available at RadioShack, including one on building power supplies.

An excellent general electronics textbook is *The Art of Electronics*, by Paul Horowitz and Winfield Hill, available from the publisher (Cambridge University Press, 800-872-7423) or on special order through any bookstore. Its 1125 pages are full of information on how to build working circuits, with a minimum of mathematics.

Also indispensable is *The ARRL Handbook for Radio Amateurs*, comprising over 1000 pages of theory, radio circuits, and ready-to-build projects, available from the American Radio Relay League, Newington, CT 06111, and from ham-radio equipment dealers.

**Copies of past articles:** Copies of past articles in **Electronics Now**, **Popular Electronics** (post 1995 only) and **Poptronics**

are available from our Claggk, Inc., Reprint Department, P.O. Box 12162, Hauppauge, NY 11788; Tel: 631-592-6721.

**Poptronics** and many other magazines are indexed in the *Reader's Guide to Periodical Literature*, available at your public library. Copies of articles in other magazines can be obtained through your public library's interlibrary loan service; expect to pay about 30 cents a page.

**Service manuals:** Manuals for radios, TVs, VCRs, audio equipment, and some computers are available from Howard W. Sams & Co., Indianapolis, IN 46214; (800-428-7267). The free Sams catalog also lists addresses of manufacturers and parts dealers. Even if an item isn't listed in the catalog, it pays to call Sams; they may have a schematic on file which they can copy for you.

Manuals for older test equipment and ham radio gear are available from Hi Manuals, PO Box 802, Council Bluffs, IA 51502, and Manuals Plus, PO Box 549, Tooele, UT 84074.

**Replacement semiconductors:** Replacement transistors, ICs, and other semiconductors, marketed by Philips ECG, NTE, and Thomson (SK), are available through most parts dealers (including RadioShack on special order). The ECG, NTE, and SK lines contain a few hundred parts that substitute for many thousands of others; a directory (supplied as a large book and on diskette) tells you which one to use. NTE numbers usually match ECG; SK numbers are different.

Remember that the "2S" in a Japanese type number is usually omitted; a transistor marked D945 is actually a 2SD945.

**Hamfests (swap meets) and local organizations:** These can be located by writing to the American Radio Relay League, Newington, CT 06111; ([www.arrl.org](http://www.arrl.org)). A hamfest is an excellent place to pick up used test equipment, older parts, and other items at bargain prices, as well as to meet your fellow electronics enthusiasts—both amateur and professional.

## TIPS FOR MAIL ORDER PURCHASE

**It is impossible for us to verify the claims of advertisers, including but not limited to product availability, credibility, reliability and existence of warranties. The following information is provided as a service for your protection. It is not intended to constitute legal advice and readers are advised to obtain independent advice on how to best protect their own interests based upon their individual circumstances and jurisdictions.**

**1. Confirm price and merchandise information** with the seller, including brand, model, color or finish, accessories and rebates included in the price.

**2. Understand the seller's return and/or refund policy**, including the allowable return period, who pays the postage for returned merchandise and whether there is any "restocking" or "return" charge.

**3. Understand the product's warranty.** Is there a manufacturer's warranty, and if so, is it for a U.S. or foreign manufacturer? Note that many manufacturers assert that, even if the product comes with a U.S. manufacturer's warranty, if you purchase from an unauthorized dealer, you are not covered by the manufacturer's warranty. If in doubt, contact the manufacturer directly. In addition to, or instead of the manufacturer's warranty, the seller may offer its own warranty. In either case, what is covered by warranty, how long is the warranty period, where will the product be serviced, is there a charge for service, what do you have to do to obtain service and will the product be repaired or replaced? You may want to receive a copy of the written warranty before placing your order.

**4. Keep a copy of all transactions**, including but not limited to cancelled check, receipt and correspondence. For phone orders, make a note of the order including merchandise ordered, price, order date, expected delivery date and salesperson's name.

**5. If the merchandise is not shipped within the promised time**, or if no time was promised, within 30 days of receipt of the order, you generally have the right to cancel the order and get a refund.

**6. Merchandise substitution** without your express prior consent is generally not allowed.

**7. If you have a problem with your order or the merchandise**, write a letter to the seller with all the pertinent information and keep a copy.

**8. If you are unable to obtain satisfaction from the seller**, contact the consumer protection agency in the seller's state and your local Post Office.

If, after following the guidelines, you experience a problem with a mail order advertiser that you are unable to resolve, please let us know. Write to Advertising Department, Gernsback Publications Inc., 500B Bi-County Blvd. Farmingdale, NY 11735.

Be sure to include copies of all correspondence.

## VCR Control-System Problems

**O**K, now we are ready to look at control-system problems that occur in VCRs. One of the most common problems is when the VCR is alive but will not do anything. Typical symptoms are that the front-panel display is active; the clock, timer, or channels can possibly be set; but all transport-related buttons are totally inert. Perhaps there is no response to any button. The VCR may or may not refuse to accept or eject a cassette.

This could indicate a variety of problems, including motor problems as well as a general power-supply or control-system failure. However, you should first try these possible solutions:

- Check for cockpit errors. Someone may have accidentally set the VCR for timer record or turned on the parental-lock mode. See if you can spot a little clock or key symbol on the display. Is there an “L” (or something else you don’t understand) displayed? Inspect the position of all slide or push-push switches. Timer mode may be set by a pushbutton, push-on/push-off, or slide switch, or from the remote control. Parental lock is usually accessible only from the remote control. Consult the user manual if in doubt about how the thing is supposed to work!
- Cycle the power by unplugging the VCR from the wall (don’t just use its power switch) for a minute or two to see if the microcontroller simply got into a confused state. This is more common than you would think. A random power surge can do it. The VCR may have gotten into a bad (mechanical or electrical) state.
- Unplug the VCR and remove the covers. Rotate the shafts of each of the motors (cassette-loading and tape-loading or main motors depending on your VCR) clockwise a couple of turns (assuming there is no resis-

tance to turning). Now plug it back in and listen for initialization sounds; it should detect that the mechanism has been moved and then reset to a safe position. See if it is now behaving. If it still doesn’t do anything, try several turns counterclockwise instead. If there is still no improvement, there may be a more serious power-supply, motor, or control-system problems.

If any of the previous steps appear to solve the problem, it is quite possible that you will never experience it again. However, a dirty mode switch may have resulted in an overshoot to a bad mechanical state and without cleaning or replacement, the same thing may happen again.

### VCR Clock Does Not Run

The clock runs either off the power line (zero crossings of the 50- or 60-Hz waveform) or from a crystal (possibly a reference derived from one of the other frequencies used elsewhere in the VCR). Conceivably, a bad backup battery or “supercap” might result in the clock remaining in setup or power-fail mode. Unfortunately, this probably isn’t much help since identifying and locating the relevant components will be next to impossible without a schematic.

### VCR Attempts to Play Non-existent Cassette

You turn power on or just plug in the VCR to the AC outlet, and it goes through the whirring sounds of playing a cassette, but there is no cassette present. Try unplugging it for 30 seconds or so and plugging it in again. The microcontroller may just have had a bad day and gotten confused—either a bad reset or a power glitch. If that doesn’t help, there could be a faulty end sensor or a bad LED or light bulb that provides illumination for the end sensors.

If either sensor’s output is the same as when a cassette is present (blocked), it is likely that the microcontroller will be confused. In some designs, this is indistinguishable from a cassette actually being loaded. If the “cassette-in” indicator is on, then this is likely. If a VCR uses an actual light bulb for that central light source and it is not lit when you attempt to load a cassette, then it is burnt out and obviously needs to be replaced. However, the LEDs used in most modern VCRs are of the infrared variety and therefore invisible to the human eye.

With somewhat similar symptoms, it is also possible that the VCR is not able to complete the startup initialization due to a slipping belt, gummed-up lubrication, or other mechanical or motor problem. The clincher would be if you manually load a cassette (by turning the appropriate pulleys, etc. with it unplugged) and then the cassette plays properly and acts normally until you try to eject it. However, don’t try this unless you are sure of how the mechanism works, as it is easy to cause damage.

### Erratic Behavior in Various Modes

You press PLAY; the VCR gets halfway through loading the tape, suddenly aborts, and shuts down. Another scenario is that you put a cassette in, and it is immediately spit out as though it tasted bad to the VCR. Better still is pressing PLAY and the VCR goes into *rewind* mode. Perhaps you pressed REVIEW, and it ejected or attempted to eject the cassette. Before you break out the screwdriver or shotgun, cover up the IR remote sensor and cassette slot. Some types of electronically ballasted fluorescent lights may confuse the remote-control receiver. On the other hand, someone or something may be sitting on the remote hand unit, or it may be defective and continuously issuing a rewind command! Excessive general illumination

may even make its way into the tape start and/or end sensors and trick the VCR into thinking that the tape is at one end. If you are working on the VCR with its cover removed, block any stray light from hitting the area of the tape transport to see if behavior returns to normal. If you have determined that none of the above is the source of the problem, let's see what can be done:

- Eliminate the possible mechanical causes such as slipping belts or a bad idler tire that could prevent the VCR from completing your requested action; it instead shuts down or attempts to return to a safe position.
- Bad connections are a possibility, but not as likely as in a TV or monitor, for example. However, some VCRs (including certain JVC units and clones) ground parts of the circuitry via the circuit board mounting screws; simply tightening these is all that is needed to effect a cure.
- The microcomputer or its associated circuitry could be defective as well, but this is not as common as most people fear.
- A faulty power supply may occasional-

ly result in similar behavior. Its output voltages may be marginal, drop under load, or have excessive ripple due to dried-up filter capacitors.

- A sensor assembly present on most VCRs called the *Mode Switch* or *Mode Sensor* is dirty or bad.

#### VCR Mode (Sensor) Switches

For the microcontroller in a VCR to confirm correct functioning and completion of operations like cassette and tape loading and roller-guide position, some mechanical sensor feedback is normally used. The most important sensor assembly in most VCRs is called the "Mode Switch" or "Mode Sensor." The purpose of the Mode Switch is to inform the microcontroller of the gross position of the mechanism at all times. For example, the Mode Switch may have five positions:

- Tape unloaded and cassette out
- Tape unloaded and cassette in
- Tape half-loaded against A/C head but not around drum
- Tape fully loaded around drum and roller guides at V-Stoppers
- Pinch roller pressed against cap-

stan—play/record position

The microcomputer monitors the outputs of the Mode Switch continuously when it is executing a mechanical operation (some monitor it at all times—even with the power off). If an operation takes too long to move from state to state or an incorrect state transition occurs, the operation will be aborted and an attempt—possibly several—will be made to return the transport to a safe position, unloading the tape and possibly ejecting the cassette.

Most Mode Switches are actually mechanical rotary or linear switches with sliding contacts. However, some VCRs use optical Mode Switches such as IR LEDs, a slotted wheel or sliding mask, and photosensors. These are much less common, and failures are even less likely. Most of the comments that follow apply only to mechanical devices.

If the Mode Switch contacts are dirty or worn, or if it has somehow loosened on its mountings and shifted slightly, one or more of these positions will report back incorrectly or erratically signaling an error condition. For example, a transition from state 1 to state 4 direct-

# New and Pre-Owned Test Equipment

## New Equipment Specials

### SIMCHECK<sup>®</sup> Hsc PLUS – Module Tester

- Tests SIMMs/168 pin DIMMs
- Identifies Module properties
- Stand alone/portable
- Built-in Serial Interface

**Only \$1,995.00**

### AVCOM PSA-37D – Spectrum Analyzer

#### Satellite Downlink – Installation – Maintenance & Service

- Band 1: 10 – 1750 MHz
- Line or Battery Powered
- Band 2: 3.7 – 4.2 GHz
- Built-in DC Block & Power for LNA/LNB's
- Carrying Case Included

**Only \$2,395.00**

### Instek GOS-6103 – Analog Oscilloscope

- 100 MHz Bandwidth
- Time Base Auto-range
- 2 Channel, High Sensitivity
- Includes Two Probes
- Trigger Signal Output
- 2 Year Warranty
- Cursor Readout

**Only \$899.00**

### Leader LF 941 – CATV Signal Level Meter

- ✓ TV/CATV Coverage from 46 - 870 MHz
- ✓ Video/Audio Carrier Measurements

**Only \$489.00**

### Fluke 87 IV – Digital Multimeter

- ✓ Basic DC Accuracy of 0.025% at 50,000 Count
- ✓ True-RMS AC, AC+DC, dBm, & dBV

**Only \$319.00**

## Pre-Owned Oscilloscope Specials

B+K Precision	1466	10 MHz	\$185.00
Tektronix	465	100 MHz	\$599.00
Tektronix	465B	100 MHz	\$729.00
Tektronix	475	200 MHz	\$829.00
Tektronix	475A	250 MHz	\$999.00

- Professionally Refurbished
- Aligned & Calibrated to Original Specifications
- The Industry Standard of Oscilloscopes
- 1 Year Warranty - The Longest Available!!!
- See Website for Complete Specifications

See us on the Web!

[www.testequipmentdepot.com](http://www.testequipmentdepot.com)

**We Buy Surplus Test Equipment**

**Test Equipment Depot**

A FOTRONIC CORPORATION COMPANY

99 Washington St. Melrose, MA 02176

(781) 665-1400 • FAX (781) 665-0780

e-mail: [sales@testequipmentdepot.com](mailto:sales@testequipmentdepot.com)

(1-800-996-3837)



**TOLL FREE 1-800-99-METER**

CIRCLE 313 ON FREE INFORMATION CARD

ly would totally confuse the poor controller. A Mode Switch that shifted out of place (or where other timing relationships in the VCR are messed up) might result in certain operations stopping at the wrong position as well. For example, if the Mode Switch shifts one way, the pinch roller may never quite press against the capstan or the roller guides may not snuggle up to the V-Stoppers as they should in play mode. If it shifts the other way, operations may fail to complete and run against the mechanical stops. Stripped or broken gears may even result.

A dirty or worn Mode Switch can result in cassette- or tape-loading, unloading, or eject operations aborting and resetting or the VCR shutting down. For example, some Emerson VCRs will move part-way when loading and then shut down. Repeated attempts may get them to fully load and play the tape, with other tape-movement operations working properly. However, unloading will result in similar cranky behavior.

Mode Switches are usually linear or rotary slide switches with four or more output terminals. They may or may not be easily accessible. Some are visible once the bottom cover is removed. Others are buried beneath a bunch of mechanical “doohickies” (a sophisticated technical term). Some are held in place by a screw or two and a connector. Others require desoldering and the removal of a whole lot of stuff—all of which must be carefully replaced with exactly the same timing relationships—just to gain access.

Once, you get at them, you can often snap the housing apart and use contact cleaner on the sliding contacts and surfaces. I usually do not use any kind of lubricant as it can gum up on the contact surfaces resulting in erratic outputs; possibly the cause of the original problems in the first place. Some may not come apart, and replacement is the only option if squirting contact cleaner through any visible openings does not help. Note that without disassembly, there is no way of knowing if there is still dirt or gummed-up grease inside or if the contacts are actually pitted. Conversely, if squirting in some contact cleaner does not help, the Mode Switch may still be the problem since you have no way of knowing how far the contact cleaner penetrated or whether it had any effect. Sometimes, bad solder connec-

tions to the Mode Switch are the only problem.

In any event, be very careful about not moving anything and take careful notes on the position of any parts that you disconnect as critical timing relationships are controlled by the gear positions. Stripped gears or other broken parts may result when the mechanism cycles. Also, in certain positions, levers or sliders operated by the mechanism that you remove may spring out of position. You will need to make sure that they get put back into the correct slots in any cams when you are done. Mark all gear positions even if they do not seem to be critical.

There are even some poorly designed VCRs where extraneous light through the vent holes or tape door affect sensors and causes erratic operation. If a bright light is shining on the VCR, block it and see if anything changes!

### **Mechanical Relationships in VCRs**

The complexity of the mechanism in a VCR can be quite intimidating. To avoid total frustration and really messing up your day, take careful notes—before you remove anything mechanical—of the precise relationships of any gear, lever, switch, or anything that might possibly get put back together in a different way. Often there are “timing” marks on the gears just as you would find in a lawnmower or automobile engine. These would be little arrows or holes that will line up with stationary marks or with each other on adjacent gears when the mechanism is in a particular position. Often, it is best to put the mechanism in the position where the timing marks line up because there may be fewer levers, cams, etc. that might be under pressure or tension in this position. Not only will it be easier to take apart, but also fewer things will pop out at you. If there are no apparent timing marks, make your own with a scribe or pen. Sometimes mechanisms that at first appear not to be critical really do control critical timing. When in doubt, make more notes than necessary and include a sketch.

### **Intermittent Behavior**

This may mean that pressing on a circuit board, flexing a cable, or operating the VCR in different orientation affects behavior. Sometimes temperature plays a role as well. If this only hap-

pens while servicing, confirm that excessive light is not affecting the start/end sensors. Do not confuse these sorts of symptoms with those indicating a faulty or dirty mode (sensor) switch.

Unlike TVs and monitors that have high-power circuitry and are prone to cold-solder joints from poor manufacturing or thermal cycling, most of the circuitry in a VCR is low voltage and low power. Although problems with bad connections to these components are relatively rare, visual inspection should still be performed where erratic behavior is noted. Exceptions include:

- Power-supply regulator or switch-mode power transistor (depending on type).
- Motor-driver (power) transistors or ICs—particularly those for the main (capstan/reel) drive and video-head drum.
- RF, video, and audio jacks since they may be stressed mechanically.
- Internal multiconductor (crimp-terminated) cable connectors. These may just deteriorate with age and use. Clean and reseat the connector(s).
- Circuit board ground screws. One or more of the screws holding a circuit board may also be providing a ground connection. These can work loose or corrode. Remove screw, scrape corrosion, and/or tighten.
- Hairline cracks in circuit boards. If the VCR has been dropped, this is very common. Sometimes, these are very difficult to locate visually but locate them you must!
- Broken or shorted wires. Some of the individual wires that are in various signal cables are quite thin and fragile. Overzealous movement of circuit boards while replacing belts or other maintenance operations can easily pinch these resulting in immediate or delayed failure. This may also take place when replacing boards. It seems that the manufacturers seem to make it impossible to squeeze all the wires back in where they came from!

That last point brings up an important caution when working inside any type of equipment: Always try to avoid pulling on the wires when removing a connector. This will minimize a stress that could result in the wire conductor breaking off inside the insulation—

something that's very difficult to locate.

### VCR Does Not Work After Cassette was Forcibly Removed

You were watching your favorite tape when suddenly the VCR emitted a mechanical "eek" and is now dead—or you press EJECT and the VCR shuts down without regurgitating your tape. Worse yet, someone (we will not point fingers) forcibly removed the tape to return it to the video store. Assuming that "forcibly" does not mean that permanent damage was done, then the first place to check, as always, is the idler tire and then all other rubber belts. At this point, it is hard to say whether your problem was compounded by the removal of the tape. If any gears were shifted with respect to one another, parts bent, or springs sprung, then it would be difficult for a technician (let alone someone not familiar with your VCR) to repair it without a service manual.

An error at power on usually means that the microcomputer thinks that it is unable to put the mechanism into a "safe" position. This could be due to slipping belts, broken gears, a bad

motor, shifted sensors, or faulty electronics. The original symptoms may have been a slipping idler preventing the takeup reel from rotating allowing tape to spill into the machine.

Hope you enjoyed the visit. Next time, we will continue with what the VCR expects to happen when you apply power. Until then, check out my Web site: [www.repairfaq.org](http://www.repairfaq.org). I welcome comments (via e-mail only, please) of all types and will reply promptly to requests for information. See you next time! ☐



**American Heart Association**  
Fighting Heart Disease and Stroke



**Research gave him a future**

**Support Research**

# POPTRONIX®

Online Edition

*We're on the web*

## FREE

*We are starting up, but you can watch us grow!*

Projects for beginners to experts!  
New Product information!  
Bookstore—discover what's new!

<http://www.poptronix.com>

**WE'RE WITH YOU EVERY DAY  
24 HOURS A DAY! DROP IN!  
WE'D LOVE TO HAVE YOU VISIT!**

## World Passing You By?



**PRIMER**

Are you interested in Microprocessors & Embedded Control Systems? If not you should be! Look around, just about everything these days has an embedded microprocessor in it. TVs, cars, radios, traffic lights & even toys have embedded computers controlling their actions. The Primer Trainer is the tool that can not only teach you how these devices operate but give you the opportunity to program these types of systems yourself. Examples & exercises in the Self Instruction manual take you from writing simple programs to controlling motors. Start out in Machine language, then move on to Assembler, & then continue on with optional C, Basic, or Forth Compilers. So don't be left behind: this is information you need to know!

- Measuring Temperature
- Using a Photocell to Detect Light Levels
- Making a Waveform Generator
- Constructing a Capacitance Meter
- Motor Speed Control Using Back EMF
- Interfacing and Controlling Stepper Motors
- Scanning Keypads and Writing to LCD/LED Displays
- Bus Interfacing an 8255 PPI
- Using the Primer as an EPROM Programmer
- DTMF Autodialer & Remote Controller (New!)

**Examples Include:**

The PRIMER is only \$119.95 in kit form. The PRIMER Assembled & Tested is \$169.95. This trainer can be used stand alone via the keypad and display or connected to a PC with the optional upgrade (\$49.95). The Upgrade includes: an RS232 serial port & cable, 32K of battery backed RAM, & Assembler/Terminal software. Please add \$5.00 for shipping within the U.S. Picture shown with upgrade option and optional heavy-duty keypad (\$29.95) installed. Satisfaction guaranteed.

EMAC, inc.

1985 - 1998

OVER

12


YEARS

OF SERVICE

11 EMAC WAY, CARBONDALE, IL 62901  
618-529-4525 Fax 457-0110 BBS 529-5708  
World Wide Web: <http://www.emacinc.com>

# KENWOOD

## Analog Oscilloscopes



**800.638.2020**  
[www.prodintl.com](http://www.prodintl.com)

**PRINT™**  
Products International

**CS-4125/4135 Features:**

- High Withstand Voltage to 400V
- Wide bandwidth & fast sweep
- VERT mode / FIX triggering
- One touch X-Y switching
- Relay attenuator

**CS-5355/75 & CS-5370 Features:**

- 2% accuracy
- Delay sweep for expanded waveforms
- Reliable relay attenuator
- 3 signals synchronized on V mode

Model	Description	Sale
PCS-4125	20 MHz, 2 ch	\$399.00
PCS-4135	40 MHz, 2 ch	\$599.00
PCS-5355	50 MHz, 3 ch, delayed sweep	\$799.00
PCS-5375	100 MHz, 3 ch, delayed sweep	\$1,049.00
PCS-5370	100 MHz, 3 ch, delayed sweep with readout & cursors	\$1,299.00

CALL FOR YOUR FREE CATALOG!

- digital multimeters
- function generators
- frequency counters
- oscilloscopes
- power supplies
- signal generators

# TEACH YOUR PET WHO'S BOSS WITH THE SCATCAT!

RUSS SHUMAKER


*If the family pet ventures into or onto forbidden areas of the house when you're not around, like beds, furniture, or kitchen countertops, this device could help.*

The family feline, an indoor cat named Fred, had taken to exploring the tops of the kitchen counters during his nocturnal sojourns. He usually got into something he shouldn't, as well as making the kitchen's sanitary condition questionable. Since this is the work area where the resident techie builds his braunschweiger sandwiches, immediate action had to be taken! At a family meeting called to discuss the problem, solutions included:

- High-voltage electric shock (vetoed!)
- Donating the cat to a tennis-racket factory (vetoed!)
- Falling anvil (vetoed!)
- Scaring the bejeebers out of him. (A contender, but one with severe limitations)

Rather than traumatize him, the majority voted to just startle him a bit. This pretty much ruled out the solutions above or a cranked-up version of the finale to the *1812 Overture*.

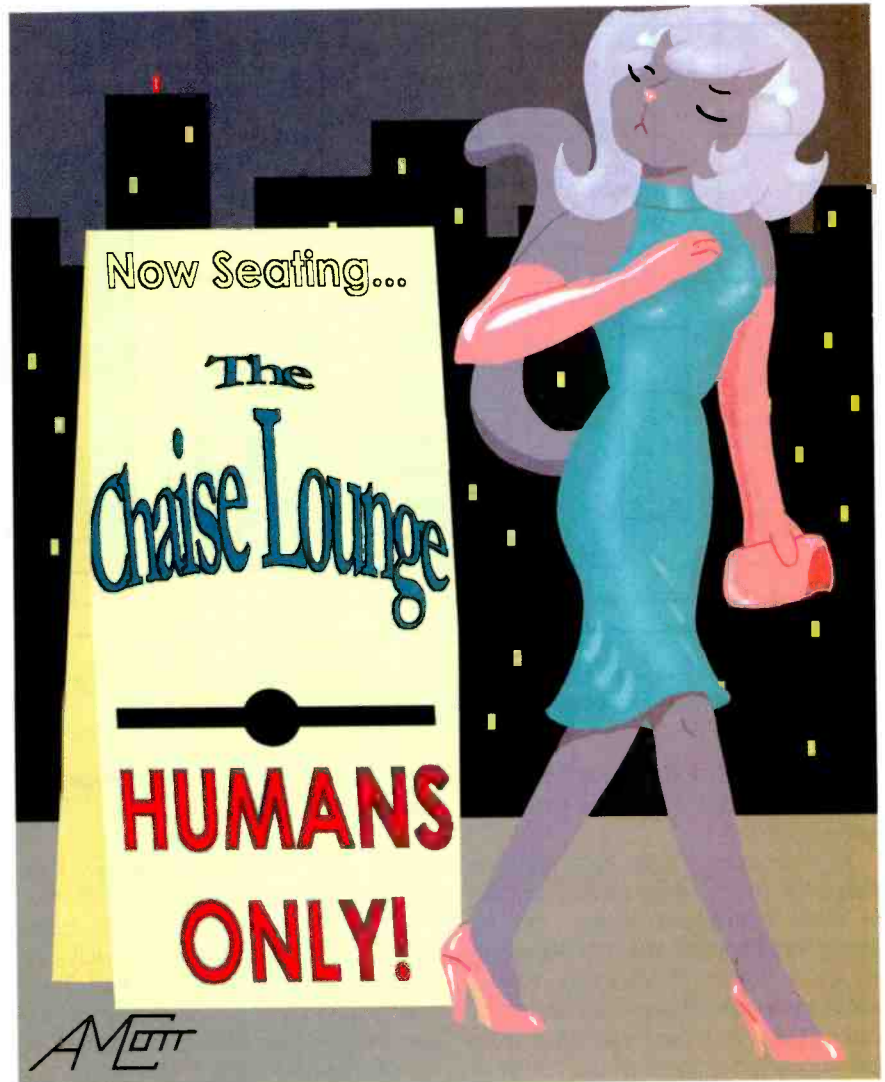Since no one volunteered to stay up and lie in wait for Fred with the primary cat-training device (a Big-Blaster squirt gun), the resident techie rubbed his hands together gleefully, cackled, and took up the challenge. The solution would be electronic, of course. That device, presented here, is appropriately called the *ScatCat*.



**How It Works.** The ScatCat is relatively simple, efficient, and...humane. The pet's presence is detected by a passive-infrared (PIR) motion detector. The detector sends a signal to the main control unit, activating it. The control unit then emits four one-second bursts of high-frequency, low-power sound, accompanied by four one-second flashes of

bright light. That combination is quite startling to cats as well as dogs...especially when they think they're putting one over on you!

The sound bursts are approximately 18 kHz. Since higher-frequency sound is directional and the ScatCat's output is low power, it has not yet awakened any of the family. The light source is a com-

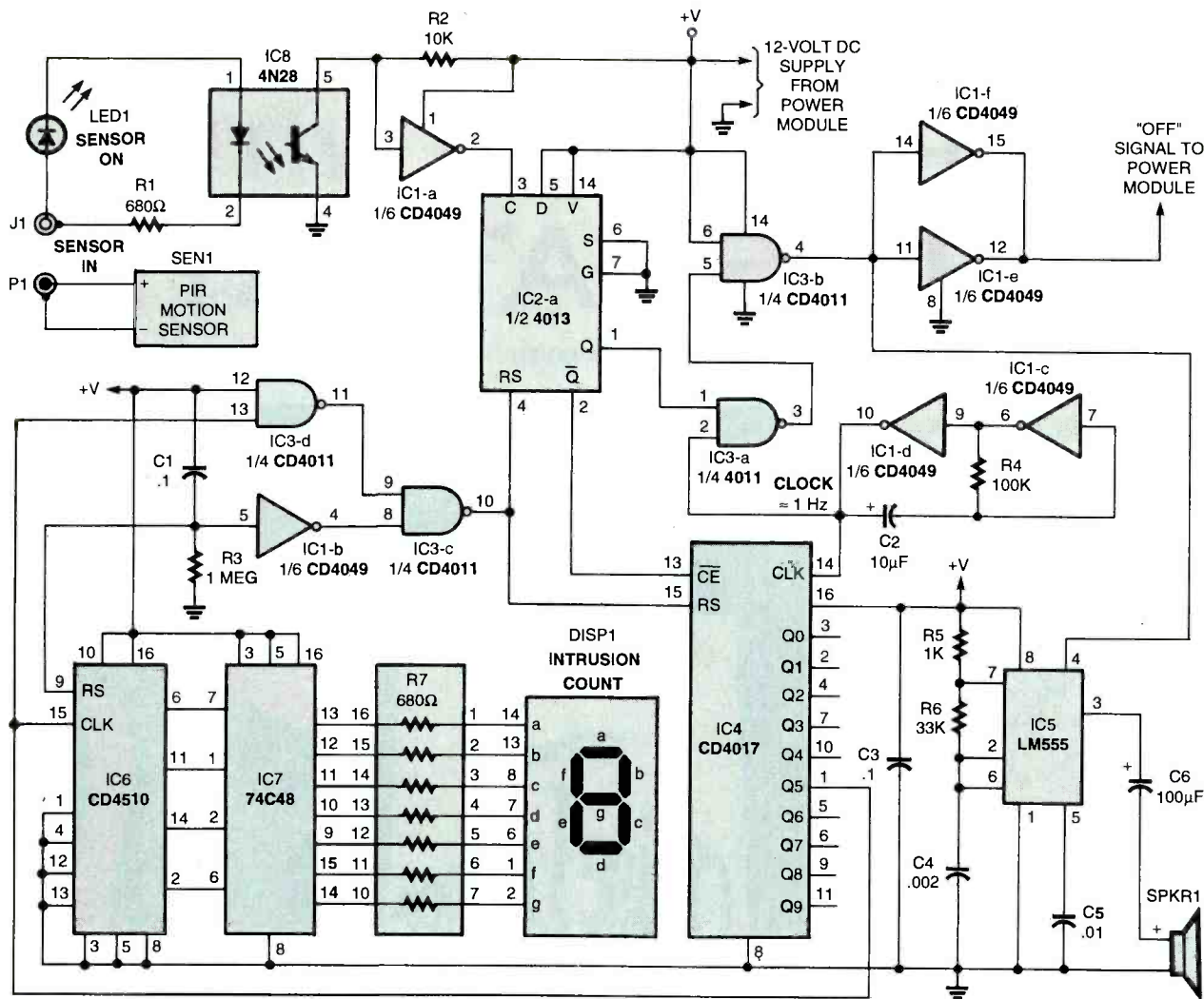


Fig. 1. The ScatCat's control module consists of six simpler sections: On-off control, clock, power-up reset, cycle counter, intrusion counter, and audio-output circuit.

mon 100-watt bulb in a light fixture that plugs into the main control unit.

A clamp-on utility light with a reflector (quite reasonably priced in most hardware stores, and a good addition to the home workshop) is the most versatile, but a table lamp with the shade removed also works. A bare bulb seems to be more effective; more so in a darkened room.

Each time there is an intrusion that activates the unit, a digital-counter readout increments to let you know if your pet is indeed trespassing, and how often. This is the only way to know if the device has been activated and is effective.

The unit also has an internal power-up reset feature to switch off the sound and light outputs and

insure that the counter is reset to zero.

**About the Motion Sensor.** The motion sensor selected for the ScatCat is a self-contained, battery-operated unit that sounds an audible tone when activated. Two reasons made it an ideal choice: Its sensitivity and detection pattern is ideal, and it goes on sale at RadioShack quite regularly. A two-conductor cable replaces its internal speaker. That cable connects the speaker output to the ScatCat's main control. The modification is simple to do, as you'll see later in the construction section.

The sensing medium is dual pyroelectric, which means that it senses body heat as well as motion. Reliable detection occurs when

the subject walks across the beam, rather than towards it; something to keep in mind when setting it up.

The motion detector's detection pattern is a two-dimensional fan-like shape that spreads at a 60-degree angle and is sensitive to a range of about 30 feet. A Fresnel lens sets the pattern. With the detector raised above the floor and the fanout horizontal, a pet can walk on the floor below the sensing area without setting it off. Sensors sold for use in home-security systems call that a "pet" pattern. Positioning the fanout vertically results in a vertical detection-area curtain, which could monitor a doorway.

Outdoor security sensors have a three-dimensional sensitivity pattern. They can be used for this



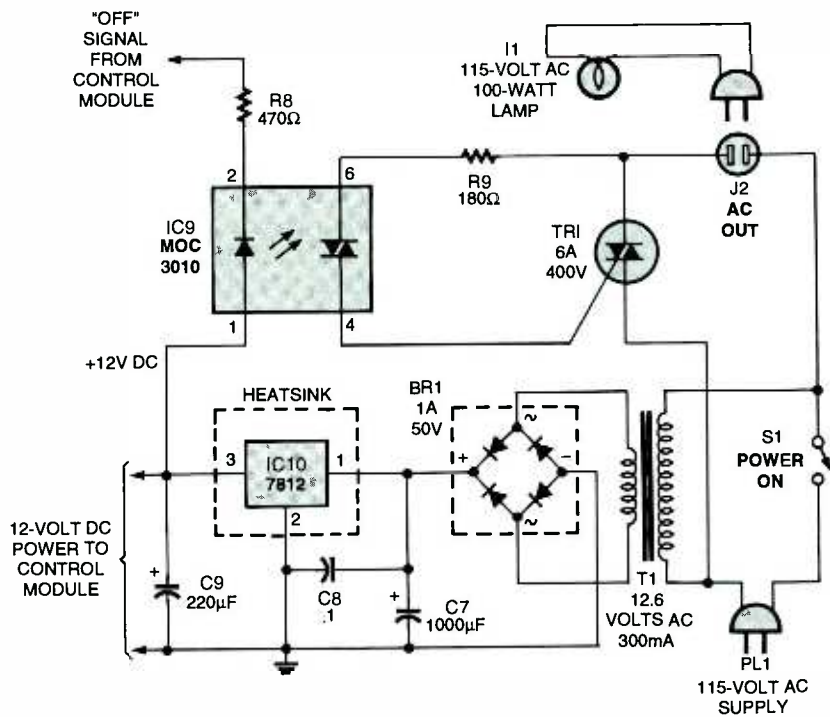


Fig. 2. The power module contains the circuits that deal with AC power: A 12-volt DC supply, which powers the control circuitry; and a solid-state relay circuit, which controls the AC-lamp output.

application if the pattern is taken into account when setting up and aiming the sensor.

There are many motion detectors available at reasonable costs from electronics-surplus vendors. Most can be used with this system. Many have relay-contact outputs. The hookup for a motion sensor with a relay contact output will be discussed later. While we're talking about different types of motion sensors, a break-the-beam "electric-eye" type can also be used with the ScatCat.

The novelty market is awash with big green plastic frogs that "ribbit" when someone passes by. Some are as low as six dollars. Although they don't have a Fresnel lens and the range is somewhat shorter, they most likely have a conical detection pattern, and would probably work. It might be fun to recall high-school Biology 101 (frog dissection), and examine one's "innards." The frog alone might be enough to spook your pets, unless of course you have a Rottweiler, who will probably eat it!

**Circuit Description.** The circuit for the ScatCat's Control Module is shown in Fig. 1. It seems complex at

first glance, but you'll see that it is made from six simpler circuits. Each section will be explained and tied together.

The first section handles on-off control. When SEN1, the PIR motion sensor, is activated, it generates a 6-volt squarewave at about 900 Hz, followed by a 700-Hz squarewave. Originally fed to a speaker, which generated a "bing-bong" tone, that signal is instead sent to the control module through connectors P1 and J1. It then turns on LED1 as a "sensor on" indicator located on the front panel and activates the LED input of optoisolator IC8. A feature of the placement of LED1 in the circuit is that it is powered solely by SEN1, so that the motion detector may be set up and aimed without having to turn on the main unit. That will prevent the sound and light outputs from being activated during the set up.

Optoisolators are current-activated devices and can be used with most sensor inputs with little

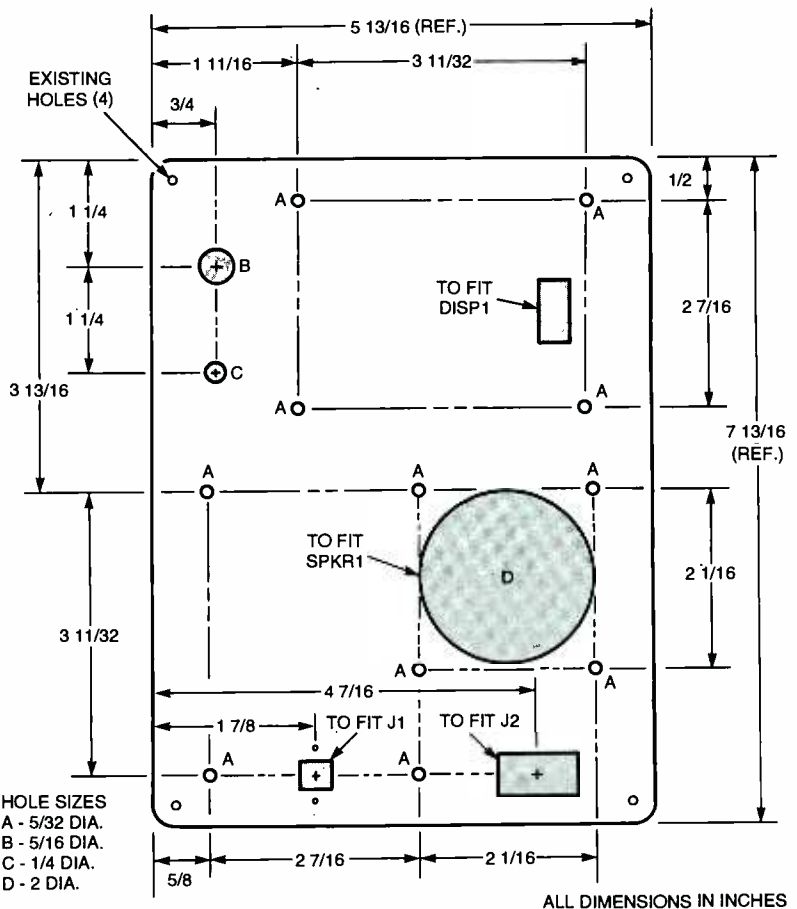


Fig. 3. The ScatCat's front panel needs several holes and cutouts. This arrangement was used in the author's prototype. Some of the cutouts depend on the items that will be mounted in them.

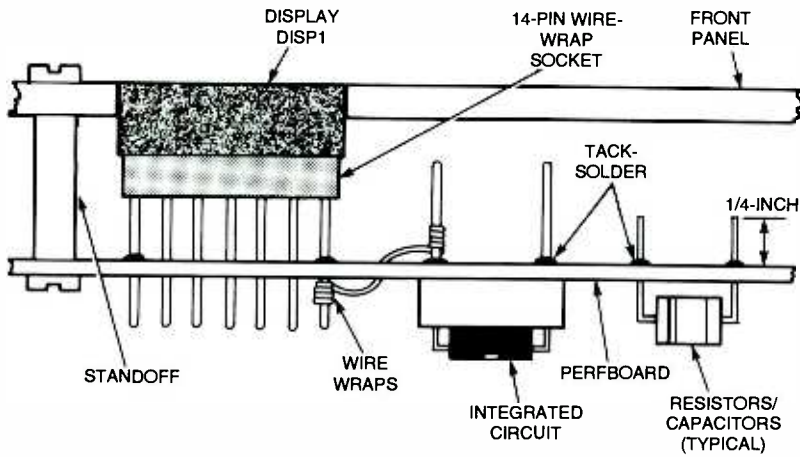


Fig. 4. The circuit boards are mounted to the rear of the front panel as shown here.

regard for voltage levels or common grounding. When using a sensor other than the RadioShack unit specified, select R1 so that IC8's input current is between 10 and 60 milliamperes.

The input to IC1-a is held high through R2. When the output transistor of IC8 is turned on, IC1-a's input is pulled to ground, sending a high pulse to clock IC2-a. The beauty of the flip-flop is that any positive-going signal can set it, be it a squarewave, as it is here, or switched DC—another example of the ScatCat's versatility; any type of motion-sensor input can be used.

The next circuit section is the clock. It is an astable multivibrator consisting of inverters IC1-c and IC1-d, R4, and C2. The 1-Hz squarewave sets the on-off times of the sound and light outputs, and increments the four-cycle on-off count.

The third section is the power-up-reset circuit. Its function is to generate a momentary pulse when power is first turned on, which assures that the light and sound outputs are switched off, and that the counter is reset to zero. The momentary pulse is generated by C1 and R1. When the power is first turned on, the input to IC1-b and the reset input to IC6 are momentarily held high until C1 charges; the pulse is then pulled low by R3.

The momentarily low output of IC1-b connects to one of the inputs of IC3-c. Although that gate is technically a NAND gate (the output goes low when both inputs are high), it can also be thought of as a negative-

input or gate (the output goes high if either input goes low). This isn't tricky quibbling over semantics. Note that we're talking about an active-low pulse from IC1-b.

In any case, the output of IC3-c goes momentarily high, resetting flip-flop IC2-a; its output then goes low. The same reset pulse from IC3-c initializes IC4, setting its active output to pin 3 (designated "Q0").

The fourth circuit, the Cycle Counter, is built around decade counter IC4. Its operation is simple: When the reset input (pin 15) and clock-enable input (pin 13) are both low, the IC will switch its outputs high one at a time with each clock pulse. Normally, the chip will count ten separate outputs before

recycling, but we're using output Q5 to send a pulse to IC3-d, which sends another "power-up" pulse through IC3-c and back to the reset input of IC4. That gives the four-count timing for the four output bursts of sound and light.

When flip-flop IC2-a is reset along with IC4, its output at pin 2 is high, disabling IC4. Although IC4 always sees a clock pulse, this keeps it from incrementing. Each time there is motion-sensor input, IC2-a "sets," enabling IC4 to count the four increments before resetting the circuit with the "fifth" count.

When IC2-a is "on," its other output goes to IC3-a. That gate allows the clock pulses from IC1-c and IC1-d to pass through to IC3-b during an "intrusion." That second NAND gate inverts the clock signal, with IC1-e and IC1-f re-inverting the signal to normal as well as buffering IC3-b's output for greater output current; we'll discuss where that high-powered signal gets used later.

The fifth section is the Intrusion Counter. This consists of a BCD (binary-coded decimal) counter (IC6), a BCD-to-7-segment decoder (IC7), current-limiting resistor network R7, and a common-cathode 7-segment LED display (DISP1).

With each system activation, IC4 counts to four, resetting on the fifth count. That reset pulse also clocks

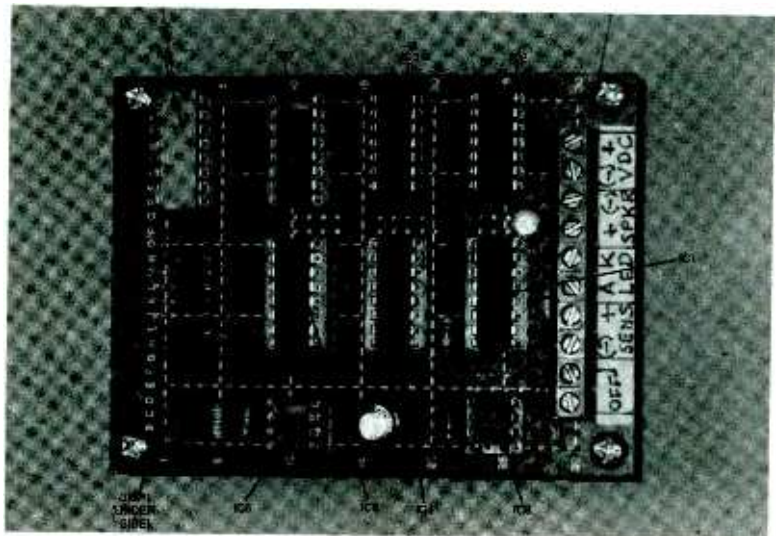


Fig. 5. Here is the control module. Note that DISP1 is mounted on the other side of the board. Using wire-wrap techniques, the locations need not be exact; this photo can be used as a guide in building your own board.

# Distance Education ...

Nearly 70 years of experience with over 150,000 graduates worldwide. At CIE you get a proven, patented, learning method to achieve your career and educational goals.

Choose from a Bachelor or Associate Degree/10 Career Courses or over 30 Micro Courses.

Toll-Free Faculty Assistance and 24 hour priority grading. At CIE you're just a phone call away for one-on-one assistance.

Enroll on-line. Visit CIE's web site at [www.cie-wc.edu](http://www.cie-wc.edu) and take a look at all of our educational offerings and services. You can even take a first lesson.

Visit CIE's Bookstore's web site at [www.ciebookstore.com](http://www.ciebookstore.com) and review our Micro Course offerings and Supplemental Training programs, plus thousands of books, software, tools, test equipment, study guides and videos.

It truly is your one stop training resource center.

## We wrote the book on it ...Since 1934



If you're looking to earn a degree, complete a career course, or upgrade your current skills, CIE's independent study programs may be the right answer for you.

Find out more about CIE by logging on to [www.cie-wc.edu](http://www.cie-wc.edu). In addition to the online enrollment form you'll find everything you need to know about CIE like detailed course descriptions, VA and DANTES benefits, a sample lesson, tuition prices, financial assistance, and it's all just a click away at [www.cie-wc.edu](http://www.cie-wc.edu).

### Call For A Free Catalog

# 1-800-243-6446



*A school of thousands. A class of one. Since 1934.*

Enroll On-line [www.cie-wc.edu](http://www.cie-wc.edu) Shop On Line [www.ciebookstore.com](http://www.ciebookstore.com)

**YES!** I am interested  
Please send me a catalog. PT15

Name: \_\_\_\_\_

Address: \_\_\_\_\_

City: \_\_\_\_\_ State: \_\_\_\_\_ Zip: \_\_\_\_\_

Phone: \_\_\_\_\_

1776 E. 17th St. • Cleveland, OH 44114

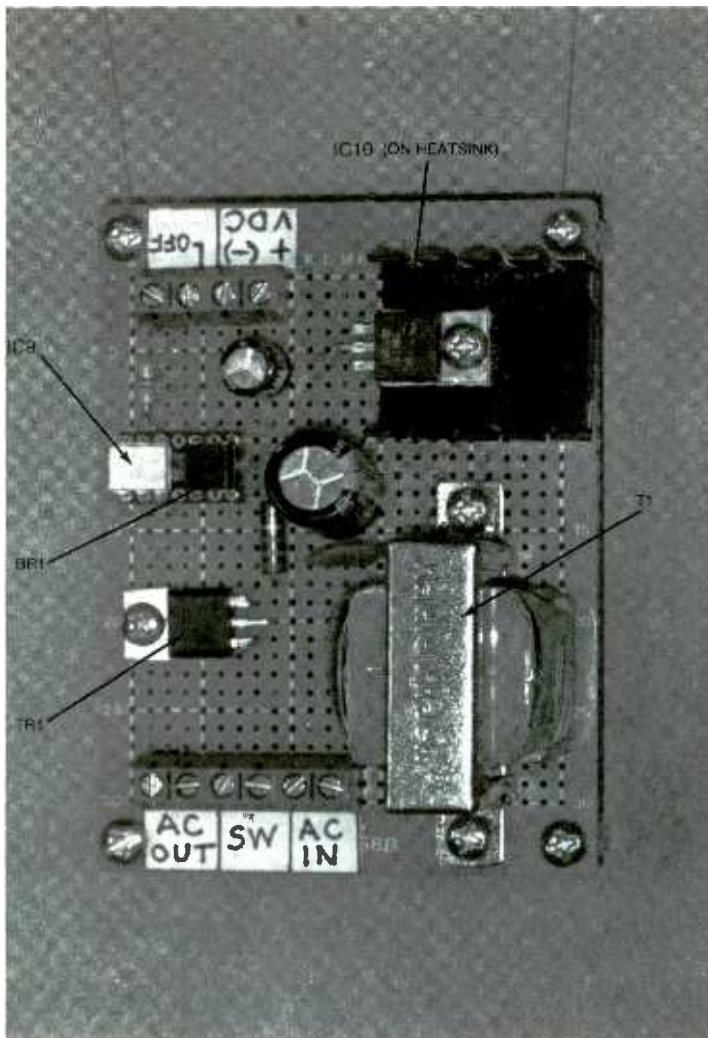


Fig. 6. The power module is built using similar techniques to the control module. Note that you'll have to drill several holes for screw-mounted items, such as T1 and IC10.

IC6, incrementing it each time. The value stored in IC6, therefore, is the number of times that the ScatCat has been set off. The magic of the binary-coded decimal format is that you can't count above nine, making it easy to display the value in a human-readable fashion. The BCD value of IC6 is decoded by IC7 and displayed on DISP1 with R7 limiting the amount of current available to each LED in the display. Without R7, the display (and possibly IC7) would burn out in short order. The reason that we use a resistor network instead of individual 680-ohm resistors is mere convenience; you could substitute standard resistors if you have enough of the right value in your "junkbox."

The last section of the ScatCat's

control module, finally, is the Audio-Output Circuit. It is a standard astable-oscillator circuit built around IC5 and its timing components, and SPKR1, a high-frequency piezo "tweeter" normally used in home-audio speaker systems.

The LM555 operates as a free-running multivibrator; it is activated by IC3-b's "on" signal being applied to pin 4 (enable) of IC5. Each pulse from IC3-b results in an 18-kHz burst from IC5. That signal is coupled through C6 to SPKR1.

**Power Module.** The circuit for the power module portion of the ScatCat is shown in Fig. 2. Optoisolator IC9, together with R1 and R2, form a solid-state relay. The isolated control signal is boosted by TR1 to handle the load connected to J2.

The load, in our case, is I1, a 100-watt light bulb. Note that the ScatCat, through S1, must be turned on for any power to reach I1. The signal to control the solid-state relay comes from IC1-e and IC1-f on the ScatCat's main board (see Fig. 1) that we discussed earlier. The current needed to drive this relay is why we used two gates as a current-boosting circuit. The logic is arranged so that when the "OFF" signal is high, I1 is off.

The rest of the power module circuit concerns, surprisingly, the ScatCat's power supply. Wall current is reduced to 12.6 volts by T1, rectified to DC by BR1, and smoothed by C7. This raw DC voltage is regulated by IC10. Capacitors C8 and C9 help stabilize IC1's operation.

The solid-state relay portion of the circuit could be replaced by a single-piece solid-state relay, such as a RadioShack 275-310.

While IC10 is a precision regulator, there are possible situations where the DC voltage could occasionally exceed the 15-volt maximum limit of the CMOS ICs used in the ScatCat. This could be prevented by using Motorola CMOS chips—which have an 18-volt maximum rating—or by changing Transformer T1 to a unit with a 10-volt output. Those changes would allow IC10, C8, and C9 to be eliminated. The entire DC supply could be removed by using a 9-volt DC wall transformer, such as RadioShack 273-1455. This would, however, provide an additional external plug to contend with.

**Construction.** The ScatCat is simple enough to be built on perfboard using standard construction techniques. Because of that, no PC-board patterns are available. Should you want to use printed-circuit techniques in building the unit, you'll have to design your own patterns.

We'll start actual construction by modifying the motion detector. While these instructions are specific to the unit mentioned in the Parts List, they can be applied to other devices in a general manner; it is up to you as to how to go about modifying any detector that you want to use.

Remove the mounting bracket,

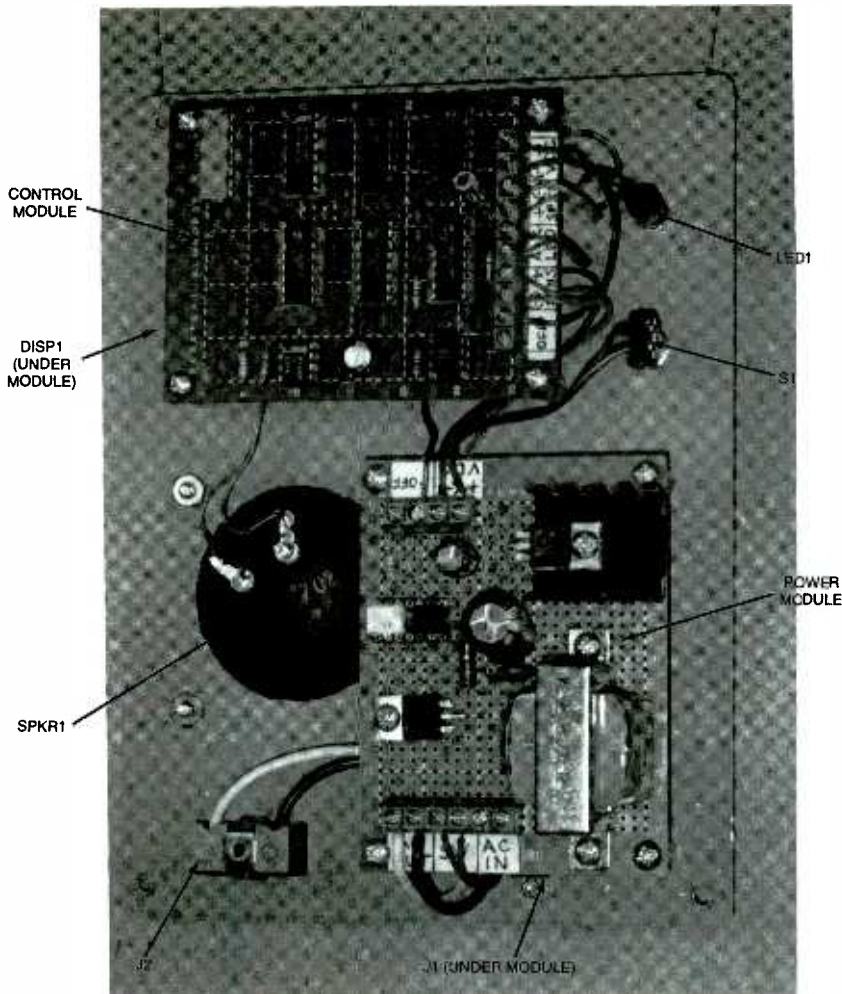


Fig. 7. The completed ScatCat front panel carries all of the various components. Note how they form a neat and handy unit.

open the battery compartment, and remove any battery that might be inside. Open the case by removing the single screw inside the battery compartment. Unsolder the speaker wires from the PC board. In their place, solder a two-foot (minimum) length of small-gauge (minimum) length of small-gauge paired wire, such as intercom twin-pair wire. Two conductors peeled from the edge of a scrap of ribbon cable will work as well. Note the polarity of the connections as marked on the PC board; maintain it through the connectors to the ScatCat's control board. Reassemble the sensor, bringing the new wire pair out through the battery compartment. File a small notch in the edge of the battery cover to allow an exit for the new wire. Reinstall the battery and cover. Insure that the sensor switch is turned off. Add connector

P1 to the free end of the wire, observing the correct polarity.

The enclosure used for the ScatCat prototype is a simple 6- x 8-inch project box. Approximate locations of the various holes needed in the front panel are shown in Fig. 3. Keep in mind that there is nothing sacred here about the size or shape of the enclosure or the component locations. You should hold off cutting the holes for the jacks and DISP1 until you have an actual board to measure from. When you have those measurements, you can cut the rectangular holes by first drilling an appropriately-sized hole and using a nibbling tool (such as RadioShack 64-823) to make the final cuts.

The exact location of the mounting holes for the boards should be measured from the actual board being used; the dimensions shown

should be close enough to get you started. Install DISP1 into a 16-pin wire-wrap socket and insert the socket into a blank board's soldering side at the approximate position indicated in Fig. 3. Mount the board onto the rear of the front panel with standoffs; see Fig. 4. Temporarily place the face of DISP1 against the rear of the front panel. Mark the outline of DISP1 on the back of the front panel, remove the board, and cut out the hole. After cutting, remount the board on the standoffs, set DISP1 so that it is flush with the topside of the front panel, and tack-solder the socket in place.

The control-module board contains all of the circuitry shown in Fig. 1 with the exception of J1, LED1, and SPKR1; we've already taken care of SEN1 and P1. While you can use any layout that you wish, the author's prototype is shown in Fig. 5, with labels showing the locations of some of the major components.

As you did with the socket for DISP1, tack-solder the IC sockets in place. When installing the discrete components (resistors, capacitors, etc.), leave about 1/4-inch of lead protruding when you trim them after soldering. That "pin" will be used to make circuit connections. Details are shown in Fig. 4.

Note that a bank of screw-type terminals are located on the side opposite DISP1; wire connections to the rest of the circuit will be made from there. While using such a terminal is not mandatory, it does make building the project easier when it comes time to do the final wiring.

When all of the components are mounted on the board, make the circuit connections using wire-wrap techniques. Follow the Fig. 1 schematic diagram as you wire the circuit. Work slowly and carefully, double-checking each connection as you go. Care at this point will prevent many frustrating hours of troubleshooting a wiring error later.

Wire wrap was designed with square posts in mind. The wire-wrap style IC sockets have such posts. Note that when you wrap wire around them the corners of the posts "bite" into the wire. The result is a mechanically- and electrically-

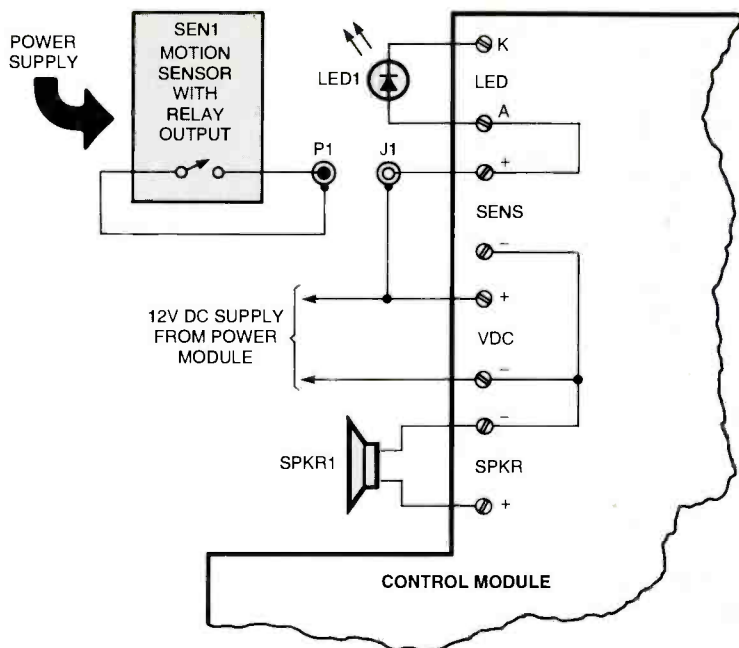


Fig. 8. This alternative wiring arrangement lets you use a motion sensor with a relay output.

solid connection that needs no soldering and can be easily removed for troubleshooting or modification. The only down side to modifying wire-wrap connections is that the wrapped portion of the wire must be cut off and re-stripped; the biting action weakens the wire so that it can only be wrapped once. When

you make wire-wrap connections to the round component leads, you must solder those connections so that they will not degrade over time due to corrosion.

The power-module circuit is built on a second board as shown in Fig. 6. The same comments and suggestions made for the control-mod-

ule board applies to this board as well. Note that IC9 and BR1, a 6-pin and 8-pin DIP component respectively, are placed in a single 14-pin socket. You'll have to drill some holes for screws and nuts to hold T1, IC10, and TR1 in place. Don't forget to use a heatsink on IC1.

Because of the higher currents involved—especially in the power-supply section—use 24- or 26-gauge insulated wire with point-to-point soldered techniques; wire-wrap is not really suitable for these components.

The circuitry for the two modules certainly could have been combined onto a single larger circuit board, but placing AC-power circuitry and DC-control circuitry in close proximity is not a good design practice. In some circuits, AC-to-DC coupling interference can cause circuit malfunction. If there is a mis-wiring or a short circuit, a catastrophic failure could occur. All of the AC is therefore confined to its own board and opto-isolated from the DC circuitry.

All of the ScatCat components are mounted onto the backside of the front panel. See Fig. 7 for the rear view of the author's prototype.

(Continued on page 58)

### PARTS LIST FOR THE SCATCAT

#### SEMICONDUCTORS

- IC1—CD4049 CMOS inverting hex buffer, integrated circuit
- IC2—CD4013 CMOS dual D-type flip-flop, integrated circuit
- IC3—CD4011 CMOS quad 2-input NAND gate, integrated circuit
- IC4—CD4017 CMOS decade counter, integrated circuit
- IC5—LM555 timer, integrated circuit
- IC6—CD4510 CMOS BCD up/down counter, integrated circuit
- IC7—74C48 CMOS BCD-to-7-segment decoder/driver, integrated circuit
- IC8—4N28 optoisolator with transistor output
- IC9—MOC3010 optoisolator with Triac output, integrated circuit
- IC10—LM7812 12-volt, 1-amp positive fixed voltage regulator, integrated circuit
- BR1—Full-wave bridge rectifier, 50-volt, 1-amp, DIP package
- DISP1—Light-emitting diode 7-segment display, common cathode

(RadioShack 276-075 or similar)

- LED1—Light-emitting diode, red
- TR1—Triac, 400-volt, 6-amp

#### RESISTORS

- (All resistors are 1/4-watt, 5% units unless otherwise noted.)
- R1—680-ohm
  - R2—10,000-ohm
  - R3—1-megohm
  - R4—100,000-ohm
  - R5—1000-ohm
  - R6—33,000-ohm
  - R7—680-ohm, 8-resistor network, isolated units (Bourns 4116R-001-681 or similar)
  - R8—470-ohm
  - R9—180-ohm

#### CAPACITORS

- C1, C3, C8—0.1- $\mu$ F, ceramic-disc
- C2—10- $\mu$ F, 16-WVDC, electrolytic
- C4—0.002- $\mu$ F, ceramic-disc
- C5—0.01- $\mu$ F, ceramic-disc

- C6—100- $\mu$ F, 16-WVDC, electrolytic
- C7—1000- $\mu$ F, 35-WVDC, electrolytic
- C9—220- $\mu$ F, 16-WVDC, electrolytic

#### ADDITIONAL PARTS AND MATERIALS

- J1—2-conductor socket to mate with P1
- J2—AC-style receptacle, panel-mount
- SEN1—Infrared motion detector/alarm (RadioShack 49-425 or similar), modified (see text)
- P1—2-conductor plug to mate with J1
- PL1—AC line cord with plug
- S1—Single-pole, single-throw switch
- SPKR1—Piezo-style "tweeter" speaker (RadioShack 40-1383 or similar)
- T1—12.6-volt AC, 300-mA transformer (RadioShack 273-1385 or similar)
- Circuit boards (RadioShack 276-158 or similar), terminal blocks (RadioShack 276-1388 or similar), heatsink for IC10, mounting hardware for LED1, wire-wrap IC sockets, 9-volt battery, wire, case (RadioShack 270-1809 or similar), hardware, etc.

# Get usable solar energy with this SOLAR-CELL INVERTER

*Build this beginner's-level circuit and harness the energy of the sun to power your next electronics project!*

FRED NACHBAUR

Solar-cell technology has come a long way in the past decade. It's not uncommon in areas that have strong year-round sunlight to find homes powered primarily by solar energy. One of the spin-offs of large-scale solar-battery manufacture is that several companies are wiring solar-cell fragments together to form inexpensive packages (small solar arrays) for use by hobbyists and experimenters. Those arrays are usually comprised of several odd-sized chunks of solar cells wired in parallel and enclosed in a plastic frame, complete with lenticular cover to help improve output capability when the cell is not exactly at right angles to the Sun.

Such arrays typically are able to provide output voltages ranging from about 0.5 to 12 volts or more at currents of 0.05 amps or more. Unfortunately, with such low energy outputs, the arrays are of little use in powering most electronic devices. That's where the subject of this article—the *Solar-Cell Inverter*—comes in.

The solar array used in our project measures  $2\frac{1}{2} \times 3\frac{3}{4}$  inches and can supply up to 500 mA at 0.5 volts in full sunlight, representing a respectable output power (about  $\frac{1}{4}$  watt) for such a small package. The half-volt output of the array is adequate to operate low-power DC loads such as small high-efficiency motors. However, there are very few other electronic devices that can be powered by such a low voltage, regardless of the available output current. That's primarily because most electronic devices (such as silicon transistors) require at least 0.6 volts to turn them on, due to the nature of the semiconductor material from which the




device(s) are made.

The most common solution to the low-voltage-output dilemma is to place several identical cells in series, effectively multiplying the output voltage by the number of cells in the series string. But taking that route can get very expensive. Another solution is to use semiconductors that, by their very nature, have a lower forward-bias threshold. Devices (e.g. transistors and diodes) made from germanium are one possibility. Specially designed silicon diodes called "Schottky diodes" are another. Unfortunately, I'm not aware of any "Schottky transistor;" so if amplification or active switching is required, we're

pretty much limited to germanium for our transistors.

Interestingly, germanium was the first material used extensively in the mass-production of solid-state devices. But, in more recent times, germanium has fallen out of favor because of its high leakage currents, temperature dependence, and the relatively expensive manufacturing processes involved. Even so, there has been renewed interest in germanium devices simply because of their ability to operate at very low voltages. Thankfully, they are still available in "substitute" lines such as NTE and ECG, albeit at a much higher cost than in their heyday.

Another source of germanium

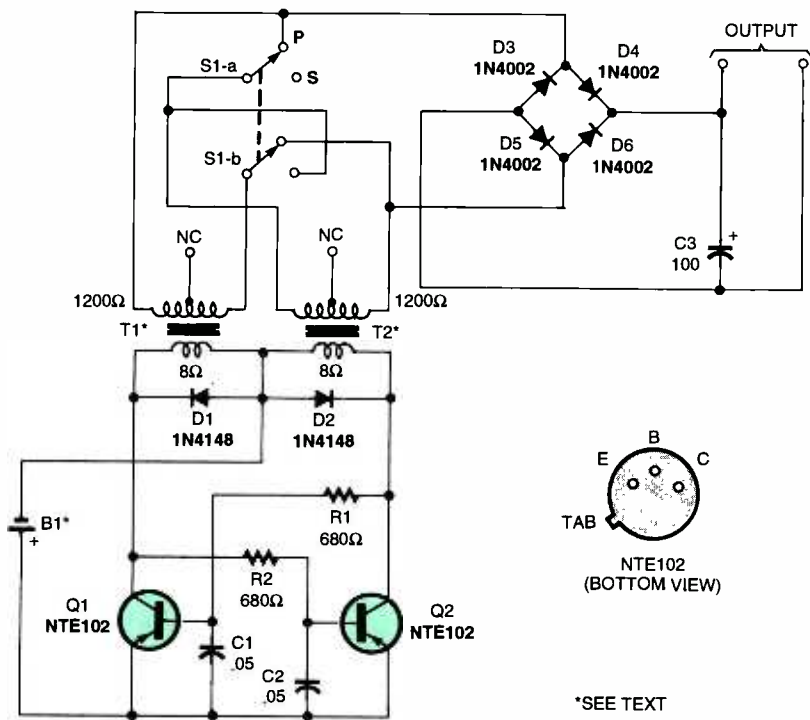

\*SEE TEXT

Fig. 1. The Solar-Cell Inverter can take the low-voltage output from a photovoltaic cell and boost it to a usable level. You can switch the output to increase voltage or current.

transistors is your junk box. The junk boxes of many experimenters are chock full of old "transistor radios," small discrete audio amplifiers, and similar bits of circuitry that include germanium transistors and other salvageable parts. Because the great majority of germanium transistors were of the PNP type, most of the gear that used them used a positive-ground system.

**A Little Background.** The Solar-Cell Inverter is useful for a variety of applications requiring higher voltages than afforded by a single solar cell. The inverter's output voltage can exceed 15 volts in direct sunlight at currents up to several milliamps. That's adequate for powering low-power op-amps and comparators, 555-based timing circuits, and a variety of other devices. With no modifications, the circuit can also be used to directly charge 9-volt NiCd batteries.

The total parts cost of assembling the inverter depends on what you can scrounge from your junk box. The transistors are (or rather, were) very common in the output stages of small audio amplifiers. And it wasn't uncommon to find a pair of them configured for push-pull oper-

ation and used to drive an audio-output transformer. Note that, in this application, we're using the same transformers. However, we're reversing the primary and secondary windings to provide the needed voltage boost.

**About the Circuit.** A schematic diagram of the Solar-Cell Inverter is shown in Fig. 1. The circuit is comprised of a pair of germanium transistors (Q1 and Q2), six diodes (D1-D6), a pair of transformers (T1 and T2), a solar array (B1), and a handful of support components. At the heart of the circuit is an astable multivibrator, better known as a free-running oscillator, formed from germanium transistors—one of the oldest constructs in electronics. To produce an oscillator, the inputs and outputs of the two transistors are cross-wired via two resistor-capacitor (RC) networks, comprised of R1 and C1, and R2 and C2. In that circuit arrangement, a portion of the output voltage of one transistor is diverted to the input of the other—in effect, routing a positive signal (feedback) from the output of one transistor to its counterpart. The result is that one transistor turns on as the other

turns off. The time constant (TC) of the RC networks determines the operating frequency of the oscillator.

The oscillator produces a square-wave output that is applied across the series-connected primary windings of T1 and T2. The negative terminal of B1 (the photocell) connects to the junction of the two transformers. Note that there is a diode connected across each transformer's primary winding. Those diodes act as dampers to prevent inductive kickback (voltage spikes generated by the collapsing electromagnetic field that encompasses the coils of the transformer), especially under no-load conditions, from damaging the transistors as they switch off.

It's rather unfortunate that the transformers commonly available generally have a tap on the high-impedance side (which we don't need), but not on the low-impedance side, where we do need it. However, using two transformers, one for each transistor, can circumvent that problem. The advantage to that arrangement is that it allows a double-pole, double-throw switch to be connected to the outputs of the transformers so that their secondaries can be easily switched from "series" to "parallel" connections and vice versa. The series connection gives the highest output voltage, whereas the parallel con-

### PARTS LIST FOR THE SOLAR-CELL INVERTER

#### SEMICONDUCTORS

- D1, D2—1N4148 general-purpose silicon diode
- D3-D6—1N4002 silicon rectifier diode
- Q1, Q2—NTE102 or ECG102 general-purpose PNP germanium transistor (see text)

#### CAPACITORS

- C1, C2—0.05-µF, polyester-film
- C3—100-µF, 25-WVDC, electrolytic

#### ADDITIONAL PARTS AND MATERIALS

- R1, R2—680-ohm, 1/4-watt, 5% resistor
- T1, T2—1200-ohm primary, 8-ohm secondary audio-output transformer
- S1—Double-pole, double-throw switch (optional; see text)
- Wire, hardware, etc.





Measuring just  $2\frac{1}{2} \times 3\frac{3}{4}$  inches, the solar battery shown here can supply up to 500 mA at 0.5 volts in full sunlight.

nection gives a lower voltage, but delivers a higher current to the load.

The output of the transformers is applied to a full-wave bridge rectifier, comprised of four 1N4002 diodes. The resulting pulsating DC output voltage is then filtered by a 100- $\mu$ F electrolytic capacitor, C3, to remove the ripple from the output voltage.

**Building the Inverter.** There's nothing critical about the construction of the circuit, so feel free to lay it out in any convenient configuration using the assembly method with which you are most comfortable. The author's prototype was assembled on a small section of perfboard, measuring  $1\frac{1}{2} \times 2$  inches, with component inter-connection accomplished through point-to-point wiring. When assembling the circuit, be sure to observe the polarity of all polarized components (the transistors, diodes, and filter capacitor). Don't omit the damper diodes; the circuit will not deliver the rated output without them. Besides, leaving out those components could damage the transistors.

Note that in the schematic diagram (Fig. 1), the transformers have polarity marks (dots) at the primaries and secondaries. To help insure that you don't make polarity errors, mark one side of the transformers with a permanent marker. That's done to prevent the transformers from being wired into the circuit with a phasal difference. That's because a phasal difference (in effect, opposing voltages) across the transformer windings can cause the transformers to overheat and prematurely fail.

The primaries and secondaries of the transformers can easily be dis-

tinguished by their leads: One side of the transformer (the primary) has two wires, while the other side (the secondary) has three. The center tap of the secondary won't be used in this application.

Switch S1 is included in the circuit for experimenting with the circuit. Once you've established which transformer-output configuration works best for your particular project, you can remove it and hard-wire the transformer secondaries as desired. In the author's prototype, the output has a 9-volt battery clip. That setup allows easy connection of a 9-volt, 50-milliamp-hour (mAh) NiCd battery for charging by the Solar-Cell Inverter.

**Testing.** Once the circuit assembly is complete, it's time to check the circuit for the usual construction errors—cold-solder joints, incorrectly wired or polarized (with respect to the other circuit elements) components, etc.—correcting each fault as it is encountered. Powering the circuit while construction errors exist could cause damage to the semiconductors (diodes and transistors) or cause a reverse-polarized electrolytic capacitor to explode!

If all checks out OK, connect the solar cell to the input. Note that the polarity is opposite to what you might be used to! Since we're using PNP transistors, the "common" input (emitters of the transistors) is positive. You might be worried at this point if you're going to have to go to a positive-ground system. Short answer: Not at all. Thanks to the transformers, the input and output of the circuit are completely isolated. Your system ground can be either positive or negative, depending only on your preference.

Connect a DVM (or analog equivalent) set to read voltage to the circuit's output terminals and bring the solar cell close to a light source. The meter should indicate an output voltage of up to several volts or more, depending on the distance between the light source and its intensity. You can also use a milliammeter (in the 20-mA or greater scale) to measure "short-circuit output current." With the component values shown, the circuit will tolerate short circuits at the output indefinitely.


Experiment with the two settings

of the series-parallel switch. In series mode, the circuit will develop over 15 volts open-circuit and in parallel mode about 8 volts.

**Using the Inverter.** In full sunlight, the inverter can charge a 9-volt battery at about 4 milliamps, meaning that full charge will be attained in about 16 hours. Note that the series connection is required for this application.

If you're using the inverter to power other circuits, the parallel connection may be preferred for its higher output-current capability. You should have no trouble powering several low-power op-amps (like the LM358) with no changes to the circuit. If you use a resistive voltage divider to derive your "split-supply ground" for op-amps, your circuit should work over a wide variance of supply voltage, and regulators will not be required.

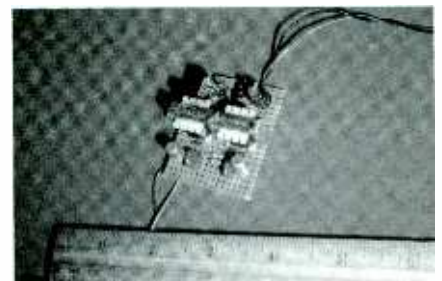For applications requiring a regulated voltage (such as low-power TTL or CMOS logic), you'll have to follow the inverter with a regulator, since the voltage regulation of the inverter is pretty poor. Lower power TO-92 versions of the 7800- (positive) or 7900- (negative) series fixed three-terminal regulators would be ideal.



Shown here is the author's prototype, which was assembled on a small section of perfboard.


The possibilities are only limited by your imagination. Use, for instance, large-value "super-capacitors" (the one-Farad varieties used as battery backup in some computers) as a "reservoir" instead of a battery. Spy on birds, squirrels, and other local wildlife with a small FM transmitter powered by this combination. You could also use a similar arrangement for short-distance telemetry projects. Yet another use is for powering ancillary control circuits in a

(Continued on page 63) 41

# ALL ABOUT ELECTRONICALLY-TUNABLE ACTIVE FILTERS

*Learn about these almost indispensable building blocks of most electronic circuits.*

RON TIPTON

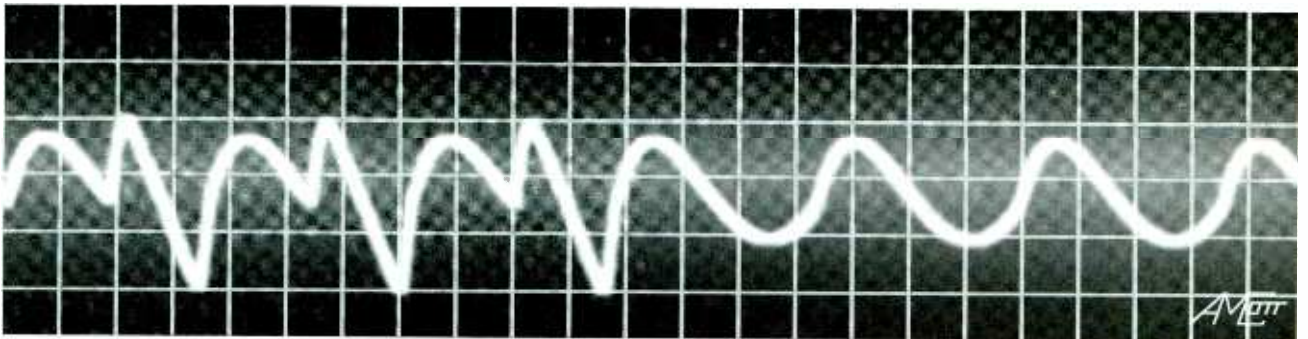

**F**ilters—low-pass, band-pass, high-pass, and band-reject—are used everywhere. Whenever we need to enhance the signal-to-noise ratio of a signal or reject a particular frequency or noise signal, we grab a filter.

Filters come in two basic “flavors:” active and passive. Active filters use “active” components such as op-amps or transistors, along with resistors and capacitors, to replace the bulkier passive filters that are built with inductors and capacitors. Besides being smaller, active-filter designs can have voltage gain (of unity or higher) as opposed to the insertion loss inherent in the passive types. Active filters are available as integrated circuits (ICs), encapsulated modules, or units built from discrete components. With that last variety, you have complete control over the circuit’s response instead of relying on “off-the-shelf” specifications. Often, a fixed-frequency design will do the job, but sometimes a tunable filter is needed.

We’re going to look at five different varieties of tunable filters. The

first three use an analog voltage to control the center, or cutoff, frequency; the last two use a digital input for control.

Although simulation is a useful design tool, all of the response curves shown in this article were measured from actual circuits. They work as described! You can incorporate them into your designs “as is” or you can modify them as needed. For easy reference, I’ve summarized the strong and weak points of each of the five designs in Table 1.

**A FET As A Variable Resistor.** The first problem that we encounter in designing tunable filters is the limited number of active-filter types that permit independent control of the cutoff frequency, gain, and “Q.” State-variable designs are especially suited to tunable filters; we’ll use them in four examples. First, however, there is a special case that I want to cover because it’s a simple and inexpensive way to make a tunable-band-pass filter.

Look at the multiple-feedback (MFB) filter shown in Fig. 1. The cen-

ter frequency can be controlled by varying R2 as demonstrated by the formula

$$f_o = 1 / (2 \times Q - A) \times (2\pi R2 \times C)$$

where A is the gain at the center frequency ( $f_o$ ) and both C1 and C2 are the same value (C).

If we replace R2 with a junction-type field-effect transistor (JFET), the result is shown in Fig. 2. This is a band-pass filter with a voltage-tunable center frequency. With the Q set to 5 and the center frequency tuned to about 2000 Hz, the gain-

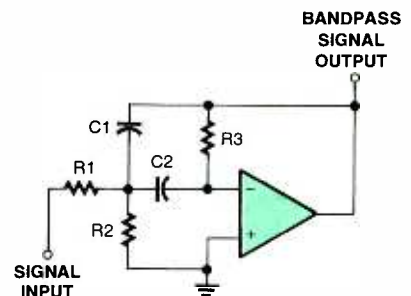


Fig. 1. This multiple-feedback band-pass filter can be tuned for a particular center frequency by varying the value of R2.

TABLE 1  
TUNABLE FILTER COMPARISON TABLE

TYPE	TUNING RANGE	STRONG POINTS	WEAK POINTS
Variable-resistor FET	3:1	Simple, inexpensive	Must block DC-operating voltage
Variable-transconductance op-amp	280:1	Fairly wide tuning range; LM3080 cost less than one dollar	Large DC-offset voltage
Analog multiplier	524:1 (practical range)	Linear-cutoff-frequency tuning; Low output noise	Can't think of any!
Digitally-variable resistor	135:1	Easy-to-use serial tuning	Clock noise may be a problem
Multiplying DAC	366:1	Linear-cutoff-frequency tuning	Output noise and DC offset

vs.-frequency response is shown in Fig. 3.

There aren't too many situations where we can use a JFET as a variable resistor because of the necessary DC operating voltage. In this case, however, capacitors C1 and C2 isolate the DC voltage from the op-amp's input as well as participate in setting the frequency response. In the tunable circuit, R2 is the series combination of R3 and the JFET's

problem because we can tailor the control circuit to match the filter's tuning needs.

So how could we use this "beastie" in a real application? One use is in an adaptive filter according to the block diagram shown in Fig. 5. The output voltage varies the filter's center frequency to maximize the output voltage. That is, the filter tracks in input frequency. When applied to a noisy input signal, the output

will be much "cleaner."

All equations in this article are stated without formal proof. The example circuits work, so that seems to be proof enough. If you want to see where the equations come from, look at one or both books I've listed in the "Resources" sidebar.

I've already mentioned some "filter-centric" terms that you may already be familiar with or at least be able to figure out from the context of this article; terms like cutoff frequency are somewhat self-explanatory. However, there are probably several "newbies" out there that are scratching their heads wondering, "What, exactly, is a 'Q'?"

That's a good question. Aside from the obvious reference to certain characters that appeared in the *Star Trek* television series, the term Q in electronics refers to the "quality factor" of a filter circuit. It is the relationship between a filter's resonant frequency and band-

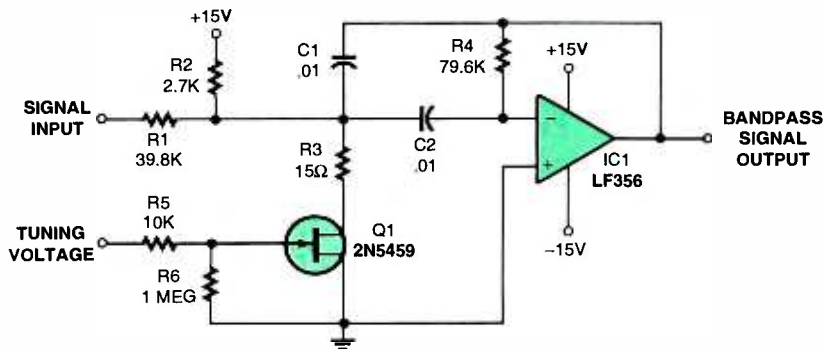


Fig. 2. By substituting a field-effect transistor for R2 of the previous circuit, we get this voltage-tunable band-pass filter. Note that C1 and C2 isolate the FET's supply voltage from the op-amp.

resistance in parallel with R2. This makes the design a bit tedious to do by hand, so I simulated this circuit in *Spice*. I've included the *Spice* file in a file that can be downloaded from the **Poptronics** FTP site. That file, located at [ftp.gernsback.com/pub/pop/tunable\\_filter.zip](ftp.gernsback.com/pub/pop/tunable_filter.zip), includes some other software as well that I'll mention later.

The measured tuning response for this filter is shown in Fig. 4. We can see that it's rather nonlinear, as is the tuning of three of our five examples. The exceptions are the analog and digital multipliers, which we'll get to later. In practice, this nonlinearity isn't much of a

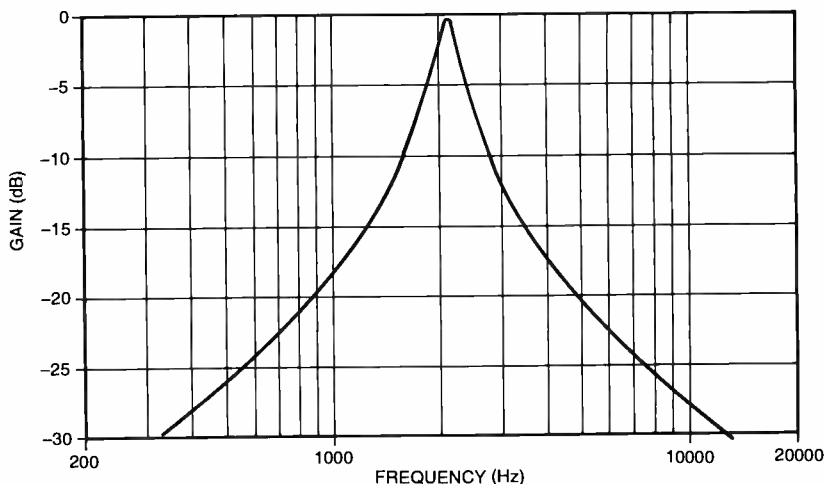


Fig. 3. Here is the response curve of the single-pole voltage-tunable band-pass filter.

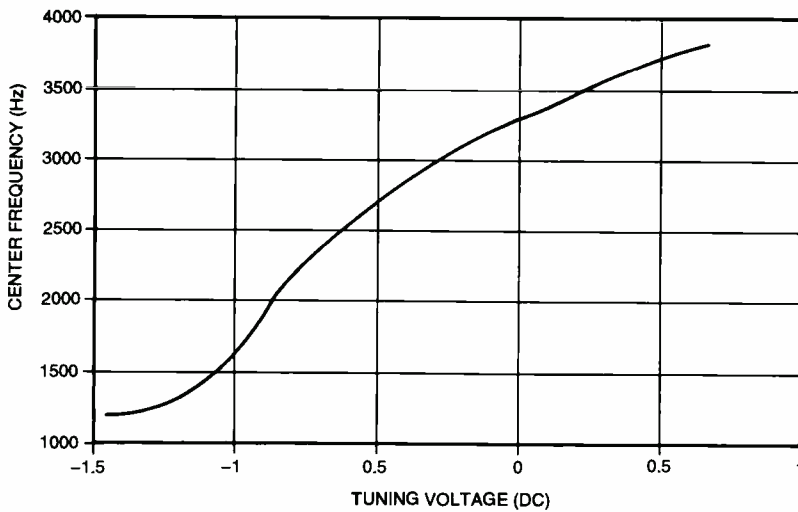


Fig. 4. This graph plots the relationship between the center frequency vs. the tuning voltage for the single-pole band-pass filter. The tuning is linear over short spans only. For example, it's fairly linear from 1500 to 2500 Hz.

width. A bandpass filter can be thought of as a combination of a low-pass and a high-pass filter. The frequencies above the low-pass filter's cutoff and below the high-pass filter's cutoff are the ones that are passed. If you plot the response, you'll see that it can represent a peak or a dip, depending on the direction that the plotline goes. The "steepness" of the slopes indicate the Q factor; the more vertical the slope, the higher the Q. The result is a filter that has greater "sharpness" in passing or blocking the target frequencies.

**State-Variable Low-Pass Filters.** As I've already mentioned, the other four examples use state-variable designs. These come in several

slightly different "flavors," and the two that we're going to look at are shown in Fig. 6. These are both basic 2-pole "building blocks."

Each one uses four op-amps, eight resistors, and two capacitors. These 2-pole blocks can, of course, be cascaded to create any even-order filter that we might need.

In both circuits, the cutoff frequency,  $f_c$ , is given by

$$f_c = 1 / (2\pi R_3 \times C)$$

where  $C=C_1=C_2$  and  $R_3=R_4$ .

If we use a component for  $R_3$  and  $R_4$  whose resistance we can vary, we will have a low-pass filter with a tunable cutoff frequency. The Q and passband gain will be constants unless we choose to make them tunable too. For example, using a variable resistor for  $R_6$  in Fig. 6A would make the Q tunable. That's because the Q is set by the ratio of  $R_6$  and  $R_7$ ; dividing the first value by the second yields the Q of the circuit. Likewise, the gain is set, the same way as in basic op-amp design, by the ratio of  $R_5$  to  $R_1$ ;

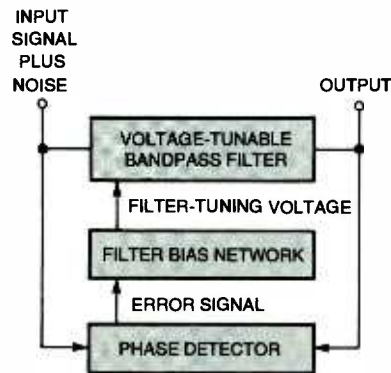
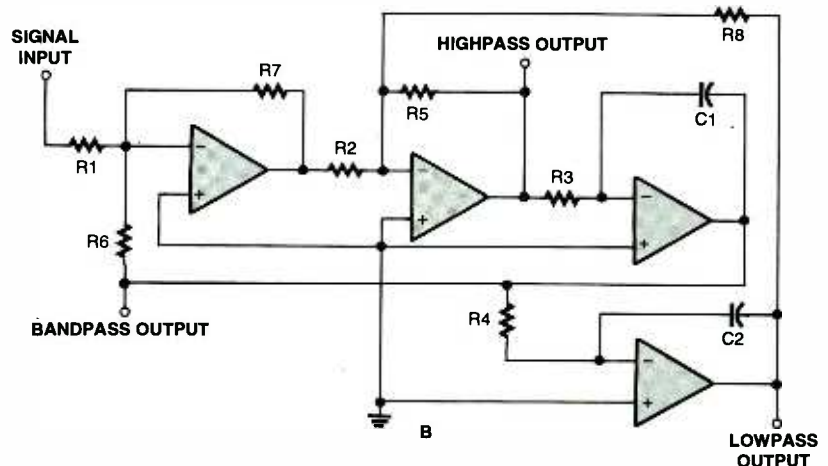
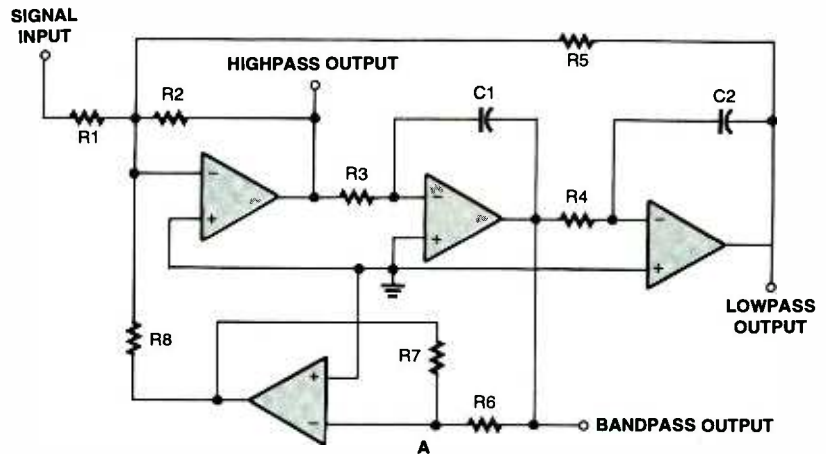


Fig. 5. The block diagram for an input-frequency-tracking filter. When the filter is tuned to the input frequency, there is a 180° phase shift between the input and output signals, resulting in a minimum error signal.

Fig. 6. There is more than one way to design a state-variable 2-pole filter. The circuit shown in (B) is sometimes called a "universal" active filter.

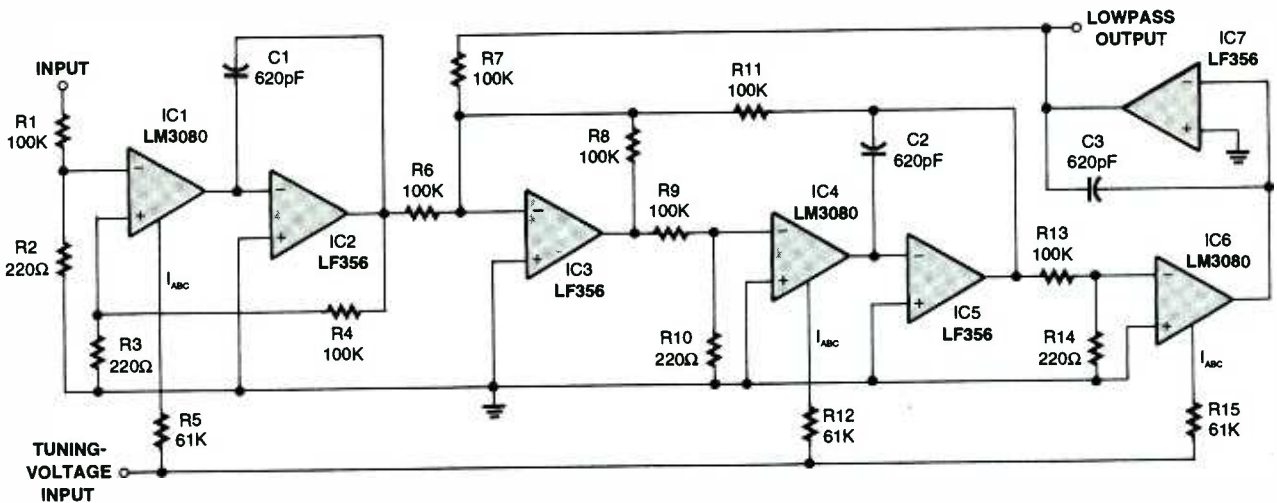


Fig. 7. On this tunable 3-pole Butterworth low-pass filter, the power-supply connections have been omitted for clarity.

again, divide the first by the second for the actual gain value.

The same formulas work for Fig. 6B as well: R5 and R1 set the gain while R6 and R5 set the Q.

One final note: If you want to experiment with the Fig. 6 circuits, you should set R2 and R8 (in Fig. 6A) to the same convenient value; 10K or 100K will do. For Fig. 6B, R2 and R7, and R5 and R8 should match

off frequency.

Although the LM3080 control pin is really a current input, we can use a series resistor as a simple voltage-to-current converter. The 61,000-ohm, 1% resistors in series with pin 5 of each of the LM3080s (as shown in Fig. 7) let us tune the filter with a control voltage between -14.5 volts and +15 volts. Although the circuit uses a dual (plus and minus)

15-volt power supply, we can't drive the control pin all the way to the negative supply voltage. Doing so just turns the LM3080 off, and there will be no signal at the filter output.

I developed this circuit in the mid 1970s to solve a particular design problem. I was developing a piano-tuning aid for the Baldwin Piano and Organ Company, and I used a programmable-frequency divider to generate the tone for each piano key. The divider's output was a squarewave that was "too rich" in harmonics for the application. This called for some low-pass (or band-pass) filtering. I determined that a 3-pole Butterworth (maximally flat amplitude) response with a rolloff of -18 dB per octave was the simplest filter that would do the job.

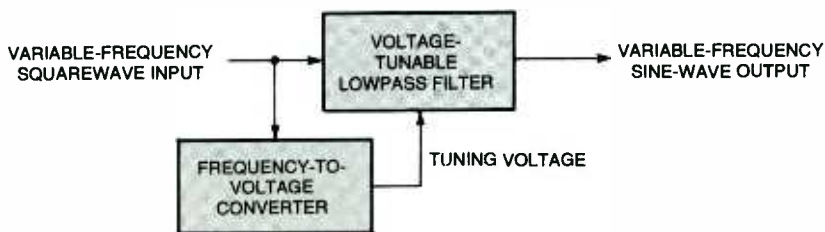


Fig. 8. A voltage-tunable low-pass filter was used to track the input frequency in a piano-tuning aid developed by the author.

each other in value.

In the following examples, we will look at using variable-transconductance op-amps, analog multipliers, digital potentiometers (VRs), and multiplying digital-to-analog converters (MDACs) as the controlled resistor. We'll start with...

#### Variable-Transconductance Op-amps.

The LM3080 (or CA3080) exhibits variable transconductance that is controlled by the current ( $I_{abc}$ ) into pin 5. In other words, the resistance of the op-amp from its input to its output appears to vary with the control current. By substituting an LM3080 for both R3 and R4 of the Fig. 6 circuits, we can tune the cut-

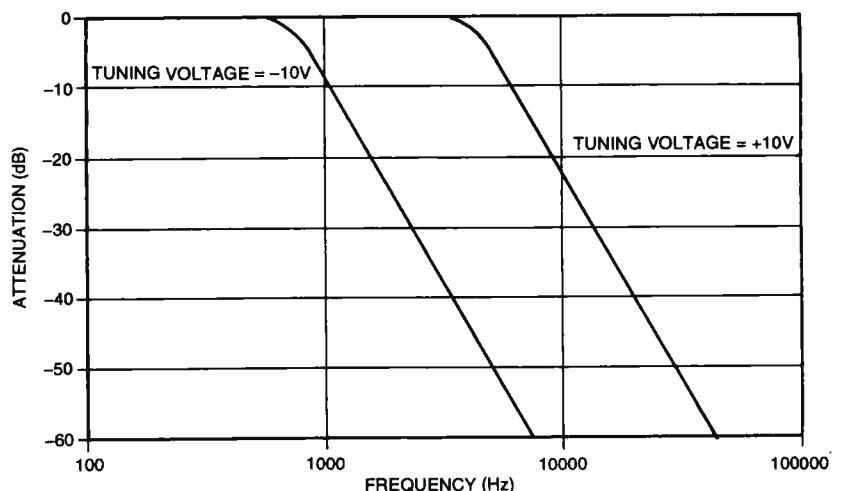


Fig. 9. This graph charts the low-pass frequency response of an LM3080-based 3-pole Butterworth filter. For both tuning-voltage values, there is a -18-dB rolloff per octave.

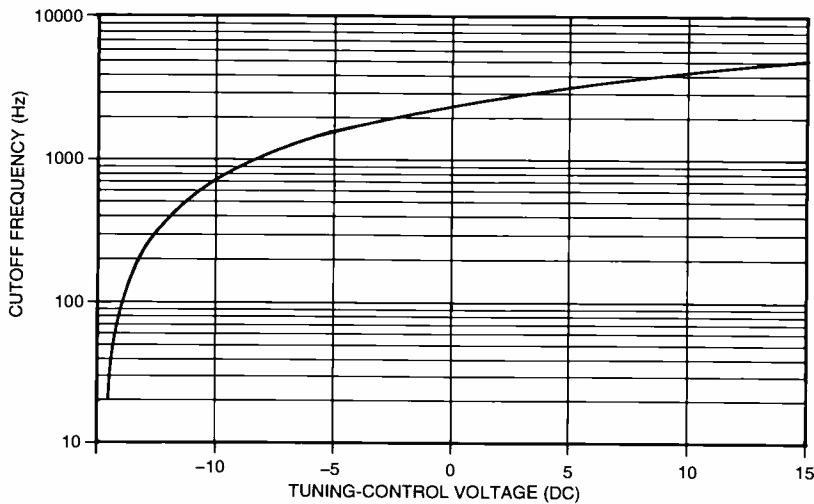


Fig. 10. This cutoff-frequency-tuning curve for the 3-pole Butterworth filter shows how the circuit turns off at tuning voltages below -14.5 volts.

Then I used a frequency-to-voltage converter to tune the filter. This combination, wired in accordance with the Fig. 8 diagram, tracked the divider's output frequency and neatly solved the problem.

Amplifiers IC1 and IC2 form the real (third) pole. The rest of the filter, IC3 through IC7 and associated resistors and capacitors, is just the Fig. 6A circuit; that might not be obvious at first glance. Because the complex pole pair in a 3-pole Butterworth response has a Q of 1, we are able to leave out one op-amp. The 100,000-ohm resistor between the IC7 output and the IC3 input replaces IC4, R6, R7, and R8 in Fig. 6A.

The design equations in Fig. 6 apply here as well, but we need to account for the effective resistance of the LM3080s. At the minimum control current ( $I_{abc}$ ), this resistance is over 12 megohms, which explains how we are able to get a cutoff frequency of 20 Hz with 620-pF values for C1 and C2. The

100,000-ohm/220-ohm voltage divider is needed at each LM3080 inverting input because the gain becomes nonlinear for inputs larger than about 10 millivolts. Notice that the LM3080s are operating open loop—there is no feedback resistor! This lets us get a useful swing of several volts at the filter's output. As you can see, this filter design includes a couple of "tricks" that you may find worth keeping in mind.

I measured the output noise at less than one millivolt rms with a "true" rms voltmeter (an HP 3400A). That represents broadband random noise with some burst or "popcorn" noise—probably from the LM3080s.

The output's DC offset varies with the tuning-control voltage, so the output must be capacitively coupled for most applications.

Response curves for two values of tuning voltage, the tuning voltage vs. cutoff frequency curve, and a photograph of the filter module are included as Figs. 9, 10, and 11.

**Analog Multiplier.** An analog multiplier produces an output voltage that is the product of two input voltages, so we can use a multiplier as a variable resistor to tune our filter. This is perhaps easier to understand by looking at it this way: The control voltage multiplied by the AC signal changes the voltage of the AC signal; that is, it changes the gain. Nevertheless, a gain change at an op-amp's inverting input appears like a change in the value of the series resistor (for constant-feedback impedance).

If we replace R3 and R4 from Fig. 6A with analog multipliers, we get the circuit shown in Fig. 12. The Analog Devices AD633 is a low-cost multiplier with a 1-MHz small-signal bandwidth. Its transfer function is given by

$$\text{Output Voltage} = (\text{X Input} \times \text{Y Input}) / 10$$

and the low-pass cutoff frequency is

$$f_c = V_c / (20\pi R_3 \times C)$$

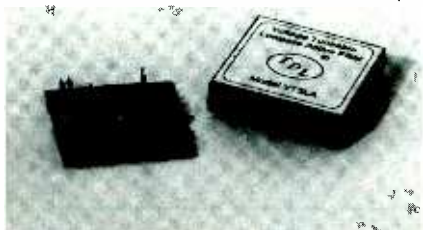


Fig. 11. Here is the author's 3-pole Butterworth low-pass filter module using LM3080s. After the module is potted, it measures  $2 \times 2 \times 1/2$  inches.

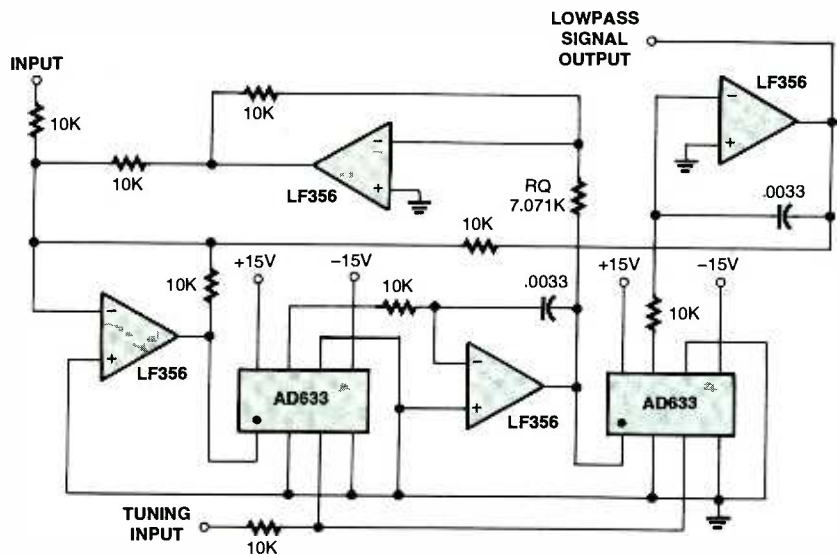


Fig. 12. This 2-pole Butterworth filter uses analog multipliers for cutoff-frequency tuning.

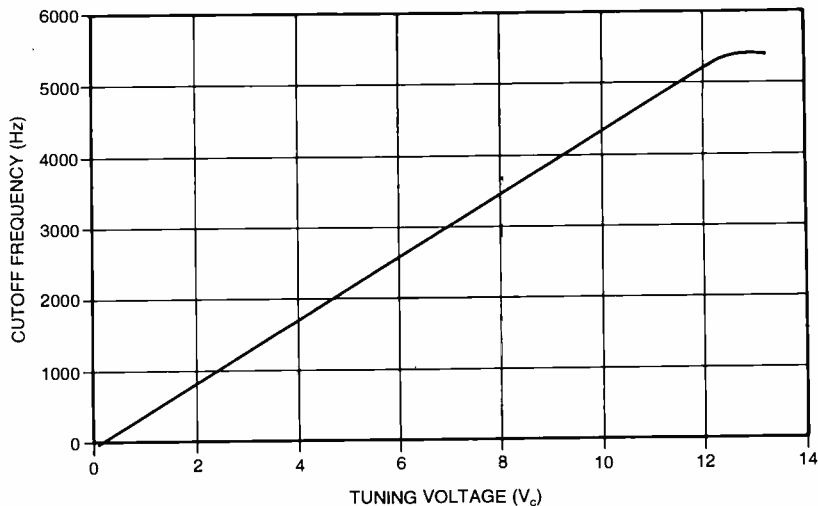


Fig. 13. Here is the measured cutoff-frequency-tuning curve for the 2-pole Butterworth filter using analog multipliers.

where  $V_c$  is the tuning-control voltage,  $R_3 = R_4$ , and  $C = C_1 = C_2$ .

Figure 12 is a 2-pole Butterworth low-pass filter; the design equations in Fig. 6A apply here as well. The measured cutoff frequency tunes from 11 Hz to 5766 Hz as shown in Fig. 13. The tuning is linear up to a  $V_c$  of 12 volts, just as we would expect from the above equation. We can also see another interesting point from this equation: The filter theoretically tunes all the way to zero frequency as  $V_c$  goes to zero. However, the cutoff frequency is 11 Hz at a  $V_c$  of 30 millivolts, so very good control-voltage stability is needed to get lower cutoffs.

This is a "quiet" filter; the output noise is about 300 microvolts rms

with the filter's input either open or shorted. That was measured with a wideband true rms voltmeter; the noise is indeed wide-band random noise with no hint of any single-frequency components. The DC offset was less than 5 millivolts and is primarily set by the op-amps.

A measured frequency-response curve is included as Fig. 14.

**Digital Potentiometer.** A digital potentiometer is ideally a digitally-controlled variable resistor. Real components, such as the 8-bit Analog Devices AD8402 (dual) and AD8403 (quad), are not quite ideal. Their limitations do not really interfere with performance, but they must be kept in mind to assure a successful design.

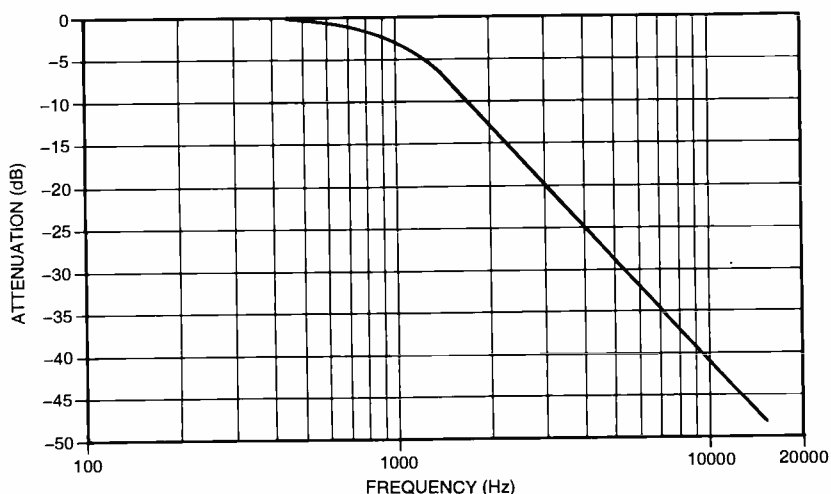


Fig. 14. A plot of the analog-multiplier-based 2-pole Butterworth low-pass filter shows that the rolloff at a tuning voltage of 2.2 volts is -12 dB per octave.

The variable resistor is easy to understand. It is literally a resistor with 256 different values (8-bit selectable). If we replace  $R_3$  and  $R_4$  in Fig. 6A with a 10,000-ohm AD8402, we get the circuit diagrammed in Fig. 15. This is again a 2-pole Butterworth design.

The Fig. 6 design equations again apply, but we have to work with the practical limitations I mentioned above. The first of these is "wiper resistance." The variable resistor has some resistance (about 50 ohms) when the digital input is all zeros. Also, this resistor is a "5-volt IC." That is, it is designed to work between +5 volts and ground; and it works best with op-amps using the same power-supply voltage. This requires a +2.5-volt "virtual" ground to bias the op-amps to the power-supply midpoint. This limits the output voltage swing to  $\pm 2.5$  volts even with

## RESOURCES

There's a bunch of books on filter design. Some are more readable (and useful) than others; two in this category are listed below:

*Active-Filter Cookbook* (D. Lancaster), Synergetics, Thatcher, AZ  
*Electronic Filter Design Handbook* (A.B. Williams and F.J. Taylor), McGraw-Hill

The file mentioned in the text, *tunable\_filter.zip*, is available on a 3 1/2-inch disk from the author for \$5, postpaid. Send check or money order to: TDL Electronics, 5260 Cochise Trail, Las Cruces, NM 88012; 505-382-8175; Fax: 505-382-8810.

All of the components used in the examples are readily available. I've listed some suggested sources below (you should have these catalogs anyway!):

**Digi-Key Corporation**  
 701 Brooks Ave. South  
 Thief River Falls, MN 56701-0677  
 800-344-4539  
[www.digikey.com](http://www.digikey.com)

**Jameco Electronic Components**  
 1355 Shoreway Road  
 Belmont, CA 94002-4100  
 800-831-4242  
[www.jameco.com](http://www.jameco.com)

**Mouser Electronics**  
 2401 Hgwy 287 North  
 Mansfield, TX 76063-4827  
 800-346-6873  
[www.mouser.com](http://www.mouser.com)

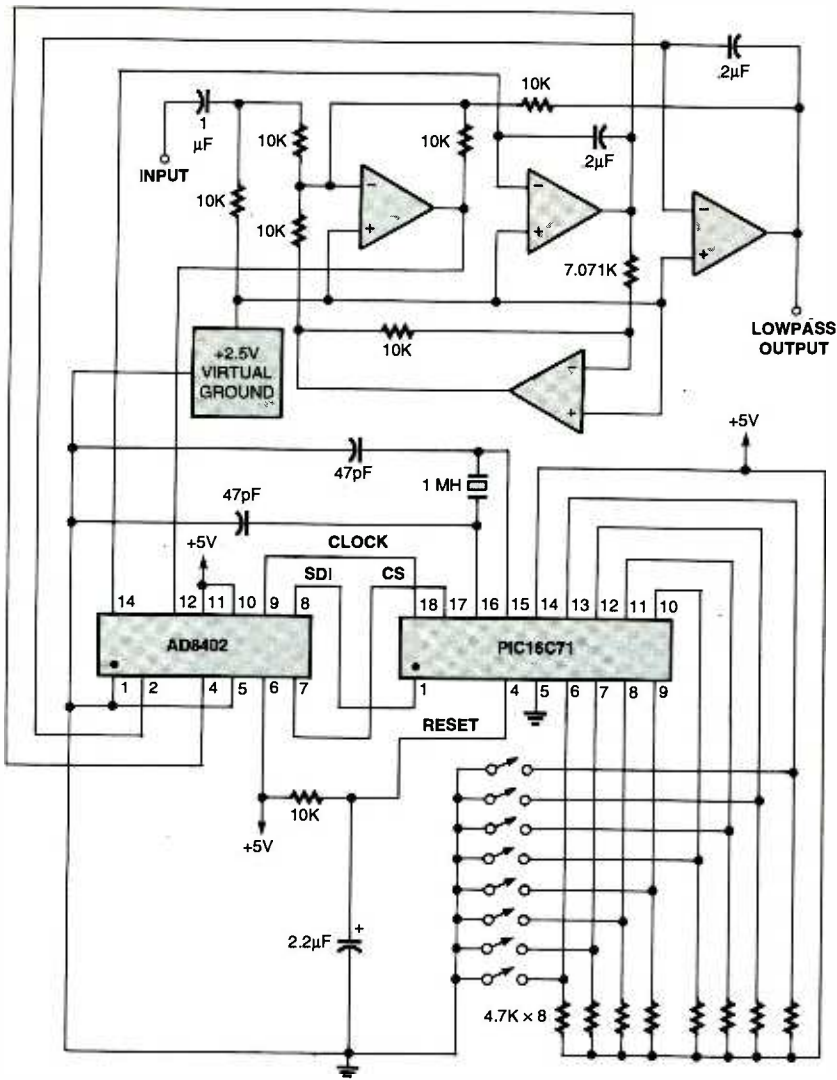


Fig. 15. This 2-pole Butterworth filter uses digital potentiometers to tune the cutoff frequency. Note the use of a "virtual" ground to center the output-voltage swing of the op-amps.

"rail-to-rail" op-amps such as the AD484 that I used in the test circuit.

Both the AD8402 and AD8403 have a 3-wire, SPI-compatible, serial-data input and are very easy to program. For this example, I used a PIC microprocessor from Microchip to read a set of eight toggle switches, generate an 8-bit control byte from them, and program the AD8402 with that value. The C program that I wrote for this proved to be too large for a 16C54 with its 512 bytes of EPROM, so I used a 16C71 with its 1K of program memory. This program is included in the *tunable\_filter.zip* file mentioned before. An assembly language version could possibly be made to fit the smaller memory of the former microcontroller, but it didn't seem worth the effort for this example.

The cutoff-frequency tuning is shown in Fig. 16 as a continuous curve for clarity. It is, of course, a set of 256 discrete frequencies. The frequency response is still the same -12-dB-per-octave rolloff as shown in Fig. 14, so there didn't seem to be any good reason to repeat it.

This filter is somewhat "noisy" because of the microprocessor clock. I measured about 3-millivolts rms output noise that is predominately 1-MHz spikes. If that amount of noise is a problem, one solution would be to put the microprocessor to "sleep" (stopping the clock) except when actually programming the variable resistor. Both the AD8402 and AD8403 have latches that store the last programmed data until it is updated or power is turned off.

The program as written checks the toggle switches every 100 milliseconds and reprograms the variable resistor only if the data has changed, so the 1-MHz spikes are all clock noise.

At first glance, you may think that this filter should have a linear cutoff-frequency-tuning response. After all, each step of the AD8402 is an equal resistance change of about 39 ohms. However, this arrangement doesn't give linear tuning. You can easily verify this by plugging some equal-step resistance values into the cutoff frequency equation from Fig. 6.

**Digital-To-Analog Converter.** A multiplying digital-to-analog converter

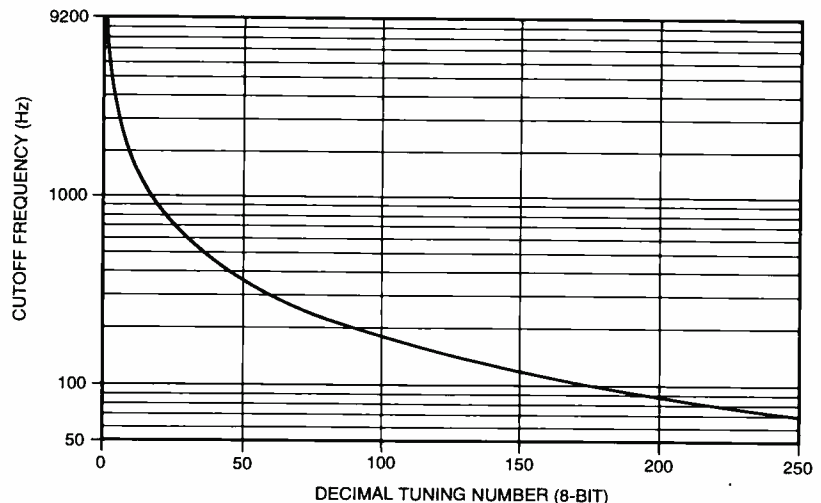


Fig. 16. Although the cutoff-frequency-tuning plot for the 2-pole Butterworth filter using digital potentiometers should have 256 discrete steps, a continuous curve is shown here for clarity.



**TABLE 2**  
**4-POLE PAPOULIS FILTER COMPONENT VALUES**

Component	Section 1	Section 2
R1	20K	10K
R2	10K	10K
R5	20K	10K
R6	11.9K	21K
R7	10K	10K
R8	20K	10K
C1	42-pF	28-pF
C2	42-pF	28-pF
C <sub>c</sub>	-none-	27-pF

(MDAC) is very much like an analog multiplier except the control input is digital data instead of a voltage.

Our final example uses four National Semiconductor 12-bit MDAC's (type DAC1222) to tune the cutoff frequency of a 4-pole low-pass filter. I also decided to use the Fig. 6B "universal" filter this time to show you how to use another response instead of our old, familiar

Butterworth.

In 1958, A. Papoulis published a paper in the *Proceedings of the IRE* on a filter response with a steeper rolloff than a Butterworth but with no amplitude ripple in the pass-band such as you get with a Chebychev response. This was apparently the first English-language publication on this "monotonic" pass-band response, so it got the name

"Papoulis." The Butterworth has a maximally-flat passband.

The 4-pole Papoulis response is given by

$$(s^2 + 1.0995s + 0.43079) \times (s^2 + 0.46338s + 0.94767)$$

and each quadratic term can be built with one of the 2-pole filters shown in Fig. 6. We can then just cascade them to get the 4-pole response.

Each of the above quadratics corresponds to:

$$S^2 + (s \omega / Q) + \omega^2$$

so we can equate coefficients and solve for the normalized frequency and Q for each 2-pole filter section. Since it's normalized, we can write frequency as f rather than  $\omega$ :

$$f_1 = 0.65635, Q_1 = 0.5970$$

$$f_2 = 0.97348, Q_2 = 2.101$$

You don't have to go through this for Butterworth filters because the cutoff frequency of every section (single-pole or 2-pole) is the same as the overall cutoff frequency. This is true for every order Butterworth filter. But the above method of equating coefficients is general and works for Bessel, Chebychev, etc. as well as for Papoulis.

We can use the design equations in Fig. 6B to find the resistances and capacitances, but first we need to look at one characteristic of a practical MDAC. The data book for this chip says the  $V_{ref}$  (voltage-reference) input resistance has a typical value of 15,000 ohms, but can vary from 10,000 to 20,000 ohms. That is too large of a range to get the filter response that we want using four unmatched, off-the-shelf MDACs. The solution is to use a large enough resistor in series with each  $V_{ref}$  input to "pad" out most of the input-resistance difference. Making  $R_{pad}$  equal to ten times the resistance variation ( $10 \times 10,000 = 100,000$  ohms) should do it.

Let's design the filter for a maximum cutoff frequency of 50 kHz. At that frequency, R3 will equal  $R_{pad}$  plus the typical  $V_{ref}$  input resistance, that is, 115,000 ohms. Using

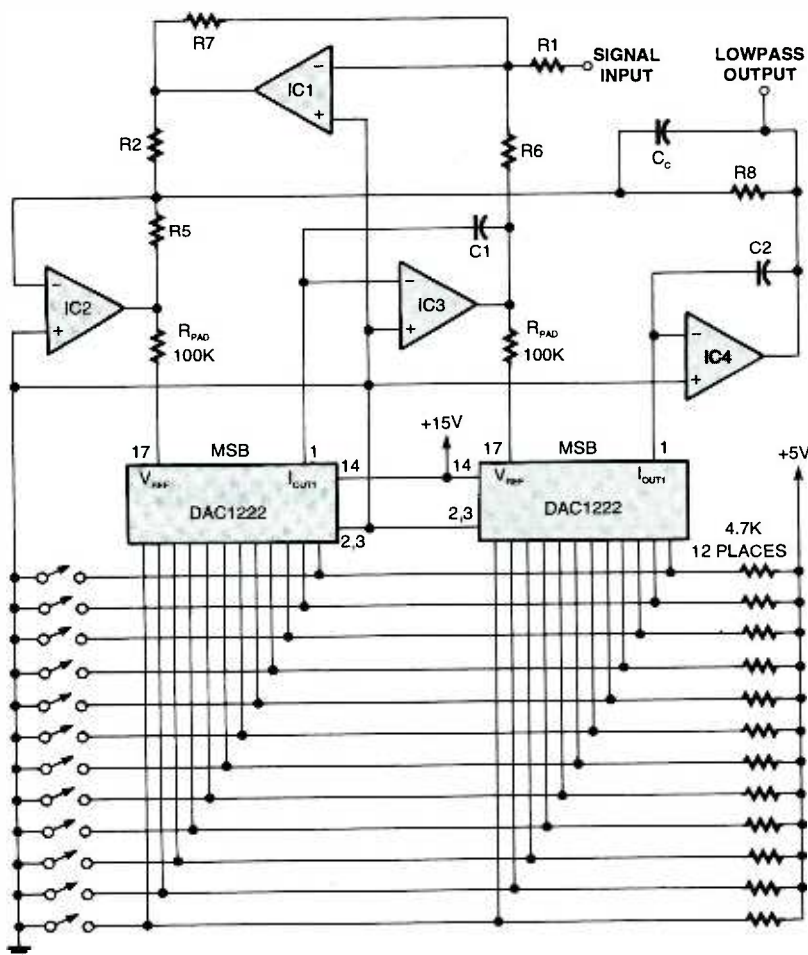


Fig. 17. This 2-pole section of a 4-pole Papoulis filter uses digital-to-analog converters for cutoff-frequency tuning. The second section cascades onto the output of the first.

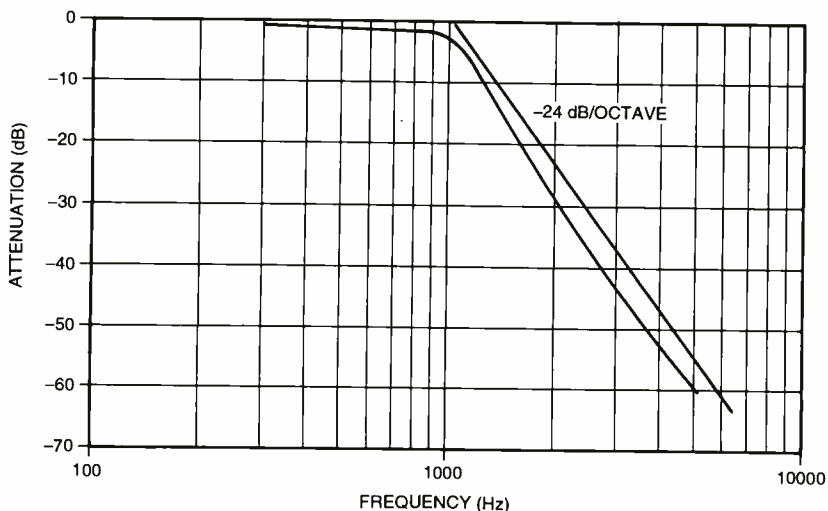


Fig. 18. This plot of the 4-pole Papoulis low-pass filter shows a -24-dB per octave with a DAC setting of 79 (decimal).

the Fig. 6 equations, we get the component values shown in Table 2; those values can be plugged into the Fig. 17 filter-circuit diagram. I used LM318 op-amps, which have a gain-to-bandwidth product of 15 MHz, a pretty fast amplifier. Even so, the second filter section has a  $Q$  of a little over 2, so compensation capacitor  $C_c$  is needed in parallel with  $R_8$  to "tweak up" the bandwidth. Twenty-seven picofarads worked fine in my circuit, but the value will depend on physical layout. If  $C_c$  is too small, the passband at the maximum cutoff frequency won't be flat—it will have a peak greater than unity gain in it. If  $C_c$  is too large, the filter will oscillate at some high frequency—probably

about 1 to 2 MHz—so it's fairly easy to find the right value.

I used one set of pull-up resistors and one set of toggle switches to control all four MDACs. With a digital input of 4095, I measured the maximum cutoff frequency as 55,636 Hz, so the calculated capacitors are a bit too small. I found the minimum cutoff frequency to be 152 Hz at a digital input of 11 (decimal). For inputs of 0 through 10, the filter simply stops working; the MDAC resistance is huge (it's about 38 megohms at an  $f_c$  of 152 Hz).

Figure 18 shows the measured frequency response at a 1-kHz cutoff. The straight line is what we would expect from a 4-pole Butterworth (-24 dB per octave), so the

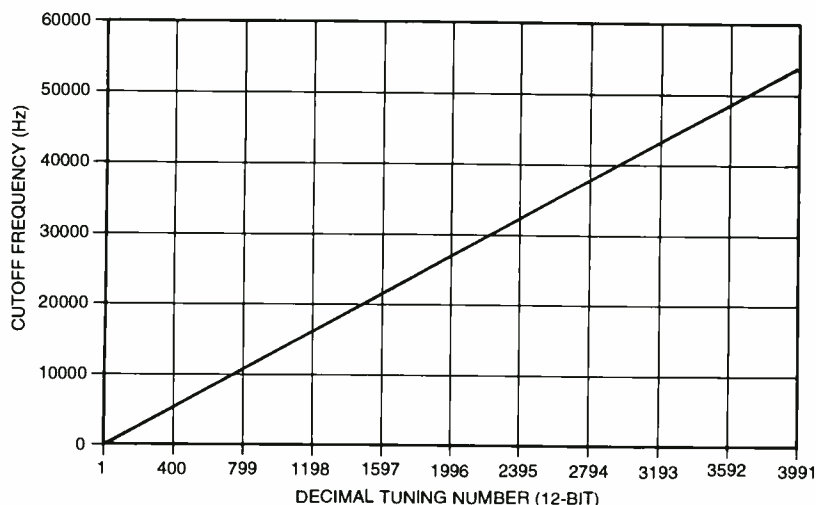



Fig. 19. Note the linearity of the 4-pole Papoulis filter when digital-to-analog converters are used. Although there should be discrete steps, a continuous curve is shown for clarity.

Papoulis is better if we don't need a maximally-flat passband.

The cutoff-frequency tuning is graphed in Fig. 19; you can see that it looks pretty linear. The tuning averages about 13 Hz per digital step, but there is some variation that would probably be improved by using MDACs with better linearity. The DAC1222 has a maximum non-linearity of 0.2%, while it's only 0.05% in the more expensive DAC1220 (which has the same pin-out).

We pay a price for the wide tuning range and good tuning resolution both in output noise and DC-offset level. Both of these vary with the cutoff frequency; that is, they vary with the equivalent resistance of the MDACs. At the minimum  $f_c$  (maximum resistance), the noise is about 6 millivolts rms with 4.3 volts of offset. At an  $f_c$  of 1000 Hz, this decreases to 2 millivolts rms of noise and a 1.6-volts offset. At the maximum  $f_c$  (minimum resistance), the noise is still about 2 millivolts rms, but the offset is down to 60 millivolts.

The MDAC resistance ( $R_3$ ) is so large and the capacitors so small that I built a PC board for this example. This minimizes stray capacitance and other variations. I also simulated the circuit in SPICE to get a "warm, fuzzy feeling" that it would really work! The SPICE model is included in *tunable\_filter.zip*.

These examples will, I think, give you some valuable tools the next time you need a tunable filter! 

## THE COLLECTED WORKS OF MOHAMMED ULLYES FIPS

#166—By Hugo Gernsback.

Here is a collection of 21 April Fools Articles, reprinted from the pages of the magazines they appeared in, as a 74-page, 8½ x 11-inch book. The stories were written between 1933 and 1964. Some of the devices actually exist today.



Others are just around the corner. All are fun and almost possible. Stories include the Cordless Radio Iron, The Visi-Talkie, Electronic Razor, 30-Day LP Record, Teleyeglasses and even Electronic Brain Servicing. Get your copy today. Ask for book #166 and include \$9.99 (includes shipping and handling) in the US (First Class), Canada and Overseas (surface mail), and order from CLAGGK Inc., P.O. Box 12162, Hauppauge, NY 11788. Payment in US funds by US bank check or International Money Order. Allow 6-8 weeks for delivery.

MA05

# NEW GEAR

USE THE FREE INFORMATION CARD FOR FAST RESPONSE

## Mobile E-Mail Device



CIRCLE 60 ON FREE INFORMATION CARD

USERS OF PALM COMPUTING platform-based devices now have the *PocketMail Back Flip* available. It allows them to send and receive e-mail or fax messages from any land-line or wireless phone, without having to connect to a computer. No phone jack, cradle, or cable is needed.

It provides a fast, inexpensive, and easy-to-use mobile e-mail solution. Simply dial a toll-free number, hold the device against a telephone handset, and push the PocketMail button. There is no limit to the number of toll-free calls to access the service or to the volume of e-mail messages sent and received. (Unlimited PocketMail service is \$9.95 a month.)

The BackFlip consists of a small keyboard and a screen that will display eight lines of text. About the size of a calculator, the device measures 3 1/4 by 6 by 1 inches and weighs only 5.5 ounces. It snaps on to the back of the Palm organizer, transferring e-mail messages

directly to the Palm device where they can be read, stored, replied to, or forwarded to another address.

This small device offers many convenient features for the e-mail user on the go. Personalized mailboxes store incoming and outgoing messages. There are nine customizable folders to manage PocketMail messages. Users can access their Palm Address Book to look up previously stored e-mail addresses and fax numbers. The BackFlip handles attachments, sending and receiving vCard and vCalendar attachments. Additional features include SPAM and PocketRules filters and fax functionality.

The PocketMail BackFlip, only available for purchase from the PocketMail Web site, sells for \$99.

### POCKETSCIENCE INC.

2075 de la Cruz Blvd., Suite 100  
Santa Clara, CA 95050  
800-390-5036 or 408-919-7444  
[www.pocketmail.com](http://www.pocketmail.com)

## Desoldering Station

FEATURING A CERAMIC HEATER inside the iron, the *Model 17.510 Digital Soldering Station* maintains the heat at a consistent temperature at all times. This ceramic heating element also enables the iron to heat up and cool down very quickly with less stress on the element than conventional units. It also has a "set" feature that accurately holds the desired temperature.



CIRCLE 61 ON FREE INFORMATION CARD

The unit is ideal for most soldering applications, including surface-mount components. Available with six different tips as accessories, and with a temperature range of 160 to 480 degrees Celsius, the soldering station comes in an ESD-Safe housing.

The 17.510 Digital Soldering Station has a list price of \$132.65.

### AVEN TOOLS, INC.

4595 Platt Road  
Ann Arbor, MI 48108  
800-624-8170 or 734-973-0099  
[www.aventools.com](http://www.aventools.com)

## Piercing Probe

DESIGNED TO ACCURATELY PIERCE wires from .030 to 1/4-inch in diameter, the *Wire-Tap* piercing probe from Precision Instruments, Co. comes in two lengths: 10-inch and 15-inch. Long enough to get into deep crevices, this probe is also small enough to get into those tight spots for isolating one wire in a bundle. Rather than plunging a needle into a wire, the Wire-Tap uses a threading action to precisely control the

amount of penetration. Its silver-plated beryllium copper needle can be removed and resharpened.



CIRCLE 62 ON FREE INFORMATION CARD

The Wire-Tap is meant to be used with multimeters, lab scopes, and graphing multimeters to test automotive, consumer, and industrial electronics. The probe accepts all standard and 4-mm banana plugs, including sheathed and retractable ones.

The Wire-Tap 10-inch probe sells for \$84 and the 15-inch sells for \$89.

### **AUTOMOTIVE ELECTRONICS SYSTEM (AES)**

3849 N. Fine Ave. #102  
Fresno, CA 93727  
559-292-7851  
www.aeswave.com

### **Single-Board Computer**

IDEAL FOR MACHINE CONTROL and for applications that typically call for a BASIC STAMP or PIC controller, the *Jackrabbit (BL1800 series)* is a high-performance single-board computer stocked with I/O, memory, and communication ports. Measuring just 2.5 by 3.5 inches, the Jackrabbit is perfect for embedded control, providing over 40 multifunctional I/O pins that include digital I/O, RS-232/485 serial ports, A/D and D/A converters, and high-voltage outputs. At its core, the Rabbit 2000 microprocessor performs fast number crunching.

Software for the Jackrabbit is developed using Dynamic C, an integrated C-language development package that



CIRCLE 63 ON FREE INFORMATION CARD

includes an interactive compiler, editor, and debugger. The complete development kit includes the Jackrabbit model BL1810 controller, Dynamic C/Rabbit software, manual, schematics, AC adapter prototyping board, programming cable, documentation CD ROM, and additional parts.

The Jackrabbit itself is priced from only \$49 and the complete development kit sells for \$139.

### **Z-WORLD**

2900 Spafford St.  
Davis, CA 95616  
888-362-3387 or 530-757-3737  
www.zworld.com

### **Paperless File System**

EASILY ADAPTED FOR USE BY any type of business that needs to manage, store, and retrieve documents, the *Virtual Paperless 2000* document-storage program is an electronic format for archives and for distribution on a CD or to hard disk. Each CD can store thousands of 8 1/2 by 11 sheets and/or drawings, and all files can be stored as images. The CDs contain their own viewer software, the *Virtual Viewer*, that allows the recipient to find, view, or print files.

The program is easy to implement. Stored files can be viewed in the application's viewer, or a launch button appears to launch the file in its native application. The image-editing tools allow users to edit and clean up the image files using de-speckle, de-skew, and crop, among others.

The *Virtual Paperless 2000* storage program sells for \$495.

### **SIMPLE SOFTWARE, INC.**

P.O. Box 68  
Mogadore, OH 44260  
800-839-9260  
www.simple-software.com

CIRCLE 64 ON FREE INFORMATION CARD

### **Remote-Control Car**

FUN AND EDUCATIONAL TO build, the *RCC7L Radio-Controlled Car Kit* is a complete 7-function R/C car. The RCC7L is fast and has a remote-control range of at least 50 ft. The finished car measures 4.7 by 4 by 1.5 inches and requires one 9-volt and four AA batteries.

Designed as a learning experience in electronics, the kit comes with a manual of well-illustrated step-by-step assembly instructions that are easy to follow. It teaches proper soldering techniques;



CIRCLE 65 ON FREE INFORMATION CARD

and has a theory section, block diagrams, and schematics and other technical information. After every assembly section, there is a simple test to help builders troubleshoot only a small section if problems occur. There is also a master troubleshooting section.

The *RCC7L Radio-Controlled Car Kit* has a list price of \$33.25.

### **ELENCO ELECTRONICS, INC.**

150 W. Carpenter Ave.  
Wheeling, IL 60090  
847-541-3800  
www.elenco.com

### **Inductance Analyzer**

COMBINED INTO A 20-HZ TO 1-MHz tester, the *1910 Inductance Analyzer* features 0.1% measurement accuracy, DC resistance measurements, sequential testing, and internal DC current biasing. The 1910 provides over 27,000 user-programmable test frequencies for inductance measurements up to 1MHz. Within the instrument's internal memory, the tester has the ability to store and recall up to 30 single test setups and 10 sequential setups. Up to six tests can be linked and executed in sequence.



CIRCLE 66 ON FREE INFORMATION CARD

The unit's internal DC bias current source of 0 to 1 Amp allows components to be tested under real operating conditions. Additionally, the unit can display the current through or voltage across the test device, which guarantees the real test conditions.

The 1910 Inductance Analyzer has a list price of \$4995.

### **QUADTECH, INC.**

5 Clock Tower Place

210 East  
 Maynard, MA 01754  
 800-253-1230 or 978-461-2100  
 www.quadtech.com

## Grounding Straps

THE SERIES 2050 HEEL GROUNDING Assemblies in combination with a conductive or dissipative floor offer personnel a way to move between work areas while staying properly grounded. To meet customers' varied needs, the 2056 contains a one-megohm resistor, the 2056-M2 has a two-megohm resistor, and the 2057 comes with a 240k-ohms resistor.



CIRCLE 67 ON FREE INFORMATION CARD

One size fits most shoes. After trimming the conductive ribbon to a desired length, the user inserts the extra-long ribbon between the shoe and sock to complete the ground path.

Prices for the Series 2050 Heel Grounding Assemblies range between \$4.95 and \$9.45.


## 3M ELECTRONIC HANDLING & PROTECTION DIVISION

2892 Cleveland Ave. North  
 Roseville, MN 55113  
 800-814-8709  
 www.3M.com
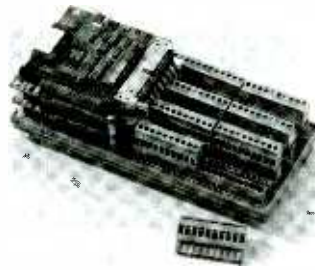
## Ethernet for Smart A/D

THE MODEL 2518/19 IS A COMBINATION of a Smart A/D for sensors with a 10-base-T interface. The combination allows data acquisition of eight or sixteen channels via an Ethernet connection. Each channel is software programmable for a different sensor type.

The Smart A/Ds that are attached to the Ethernet board provide sensor excitation, linearization, software filtering, auto standardization, and alarm monitoring. The unit accepts a wide range of



CIRCLE 68 ON FREE INFORMATION CARD

input power from 12 to 24 VDC. A temperature sensor for each group of eight channels is used as a cold reference for thermocouples.

The prices are \$653 for eight channels and \$949 for sixteen channels.

## SENSORAY

7337 SW Tech Center Drive  
 Tigard, OR 97223  
 503-684-8005  
 www.sensoray.com

## Electronics Trainer

HELPING STUDENTS LEARN how to follow schematic diagrams and make them into working circuits, the *Electro-Trainer* is designed for any electronics, electricity, or automotive vocational course. A wide range of electronics training is available from creating series and parallel circuits; measuring voltage, current, and resistance in series or parallel; working with Ohm's Law; and performing voltage drop calculations.



CIRCLE 69 ON FREE INFORMATION CARD

The panel has 64 milled holes for inserting individual modules during training as well as 7 red and 7 black holes for test leads. All the modules are mounted on white acrylic plastic with silk-screened schematic diagrams and labeling, and they all have banana plugs mounted on the back for inserting and removing from the test board. The unit has a locking top that lifts for convenient storage of the training components and test leads. An illustrated

guidebook is included with explanations, examples, and questions.

The complete Electro-Trainer system sells for \$495 plus shipping and handling.

## IDAHO INSTRUMENTS

624 4<sup>th</sup> Avenue West  
 Twin Falls, ID 83301  
 208-733-5636  
 www.idahoinstrument.com

## Biodegradable Cleaner

A SAFE REPLACEMENT TO aerosol, the *EcoAir VCI-414* water-based, biodegradable, heavy-duty cleaner comes with the convenience of a handy power spray application in a recyclable can. The user can spray the liquid concentrate in any direction, even upside down, to clean and degrease metal and painted surfaces. It clings to ceilings and vertical surfaces, effectively removing dirt, oils, and greases in hard-



CIRCLE 70 ON FREE INFORMATION CARD

to-reach areas

For cleanup of heavily greased or soiled equipment, engine blocks, and tools, the air-powered spray, which provides 100 pounds of compressed air force, penetrates crevices and recessed areas to remove oily residue and dirt. EcoAir cleans and protects both ferrous and non-ferrous metals.


A single spray can of EcoAir VCI-414 sells for \$10.99.

## CORTEC CORP.

4119 White Bear Parkway  
 St. Paul, MN 55110  
 800-4-CORTEC or 651-429-1100  
 www.cortecvci.com
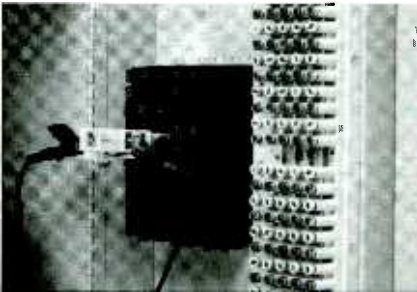
## Telephone Cable Tester

OFFERING TECHNICIANS A QUICK means of troubleshooting telephone cable problems, the *Model 6332 Tel-Line Tester* automatically splits the central office from the field, allowing for fast identification of the problem line. Ideally suited for cable installation and repair, the tester eliminates the need for cutting, stripping, disconnecting, and reconnecting cable pairs.



CIRCLE 71 ON FREE INFORMATION CARD

The Tel-Line Tester plugs into any 5-pin connector block located at a building entrance or central office. To troubleshoot, the technician simply clips a buttset or voltmeter to the appropriate metal tabs and checks the switch to determine whether the problem is located in the field or at the central office. The Tel-Line Test Kit comes complete with tester, looping tool, and craft access wall cord.

The Model 6332 Tel-Line Tester sells for \$555.

### POMONA ELECTRONICS

1500 E. Ninth St.  
Pomona, CA 91766  
909-623-3463  
www.pomonaelectronics.com

# Books that Bridge Theory & Practice

Many electronics enthusiasts discovered that the bridge from classroom theory books to hands-on project building is difficult to span at times without a handy pocket guide. Even the equipment manual to operate a gadget often makes things murkier rather than clearer. A compact text authored by a seasoned expert with hands-on knowledge and a knack of writing in an easy-to-understand style is many times more valuable than the price of ponderous theory and equipment manuals or the parts for a project that could be damaged. Here's a sampler of some titles you may want to own!

**ELECTRONIC HOBBYIST DATA BOOK**—The info you need to transport you from the schematic diagram to project parts. Pin-outs, color codes, truth tables, parts parameters, etc. **Order BP396- \$10.99 Includes S & H**

**PRACTICAL INTRODUCTION TO SURFACE MOUNT DEVICES**—A technology that spun off the automated assembly line into the grasp of experimenters and project builders. **Order BP411- \$9.99 Includes S & H**

**THE PRE-COMPUTER BOOK**—Aimed at the absolute beginner with little or no knowledge of computing. A non-technical discussion of computer bits and pieces and programming. **Order BP115- \$2.99 Plus \$2.00 S & H**

**PRACTICAL OSCILLATOR CIRCUITS**—If your budding project requires an oscillator, you can design it and build it from the many types described here in a hobbyist-friendly style. **Order BP393- \$9.99 Includes S & H**

**PRACTICAL PIC MICROCONTROLLER PROJECTS**—This book covers a wide range of PIC based projects. In most cases the circuits are very simple and they are easily constructed. **Order BP444- \$7.99 Includes S & H**




BP396

BP411

BP115

BP393

BP444

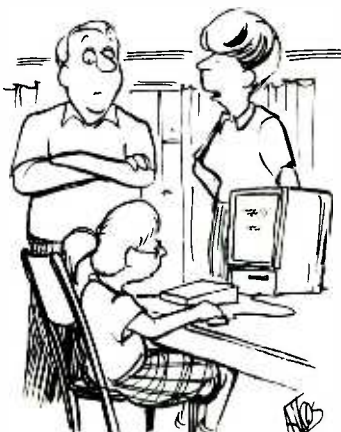

"Like I told you over the phone, Mr. Rolland, your daughter, Kathy, decided to major in computer games."

### Electronics Technology Today Inc.

P.O. Box 240

Massapequa, NY 11762-0240

Number of books ordered

Amount enclosed \$ \_\_\_\_\_

Please send me the following book(s) that I checked:

- BP396 - Electronic Hobbyist Data Book—\$10.99
- BP411 - Practical Introduction to Surface Mount Devices—\$9.99
- BP115 - The Pre-Computer Book—\$2.99 + \$2.00 S & H
- BP393 - Practical Oscillator Circuits—\$9.99
- BP444 - Practical PIC Microcontroller Projects —\$7.99

Most above prices include shipping and handling

ET05

Name/Company \_\_\_\_\_

Address \_\_\_\_\_ Apt. \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_


Sorry, no orders accepted outside the USA and Canada. All payments must be in US funds! NY state residents must include local sales tax. Allow 6-8 weeks for delivery.

# NEW LITERATURE
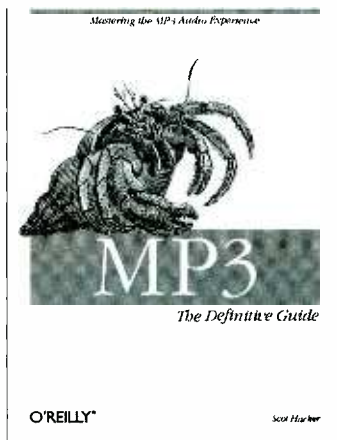
## MP3: The Definitive Guide

by Scott Hacker  
O'Reilly & Associates  
101 Morris St.  
Sebastopol, CA 95472  
800-998-9938 or 707-829-0515  
[www.oreilly.com](http://www.oreilly.com)  
**\$29.95**

A complicated, digital, music-encoding algorithm, MP3 has changed the dynamics of music distribution. According to the author, MP3 "could radically restructure the way we select music." Hacker states "For the first time in history, artists and musicians can potentially be heard by anyone on the planet with Web access, and those artists don't need any part of the recording industry to make it happen."



His book introduces the power-user to all aspects of MP3 technology. It delves into detail on obtaining, recording, and optimizing MP3 files using both commercial and Open Source methods; and it covers four platforms: Windows, Macintosh, Linux, and BeOS. In addition, readers will learn all about the complex legal issues surrounding MP3 files.

## 2000 Technical Library CD-ROM

from Microchip Technology Inc.  
2355 W. Chandler Blvd.  
Chandler, AZ 85224-6199  
480-786-7668  
[www.microchip.com](http://www.microchip.com)  
**Free**

This CD-ROM contains a complete selection of technical documentation on Microchip's PICmicro microcontrollers and associated development tools, analog/interface products, non-volatile memory devices, and related microperipheral products. Giving users the flexibility to edit, compile, emulate, and program PICmicro microcontroller devices from a single user interface, the library includes the most current release of Microchip's popular *MPLAB Integrated Development Environment* software.




All documents are readable in Adobe Acrobat Portable Document Format (.pdf) and run under Adobe Acrobat Reader 3.0 or higher, and WinZip may be used to access the very large files. Copies of these programs can be downloaded from the Web site, which offers both text search and parametric search capabilities.

## Linux Command Summary

by Clarica Grove and Phil Hughes  
Specialized Systems Consultants, Inc.  
P.O. Box 55549  
Seattle, WA 98155-0549  
206-782-7733  
[www.linuxjournal.com](http://www.linuxjournal.com)  
**\$8**

Linux is a free, UNIX-like operating system used by millions of people around the world. The operating system excels in many areas—from end-user concerns, such as stability, speed, and ease of use, to development and networking. A comprehensive reference and learning tool, this book summarizes over 500 Linux commands.

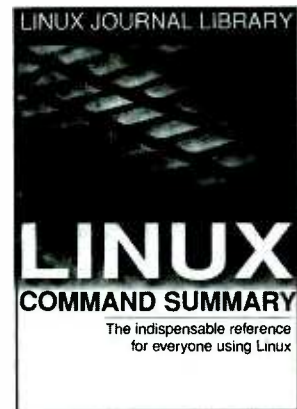Informative for every level of Linux user, the pocket-sized reference guide



contains the same information as large manuals. Sections of the book cover User Commands, System Administration, Configuration Files, and AWK.

## Relay, Circuit Breakers, and Accessories Catalog

from NTE Electronics Inc.  
44 Farrand St.  
Bloomfield, NJ 07003  
800-631-1250 or 973-748-5089  
[www.nteinc.com](http://www.nteinc.com)

### Free

This cross-reference and technical catalog features updated NTE replacements for over 44,000 industry part numbers. Seven new series of relays have been added to their line of U.L. and C.S.A. listed relays and circuit breakers. These include plug-in, multifunctional time-delay, voltage-monitoring, and phase-monitoring relays, as well as alternating relays, solid-state relays, and AC buzzers.



All NTE catalogs, technical specs, and a complete distributor list are available at the Web site.

## Maintaining and Repairing VCRs and Camcorders

by Robert L. Goodman

McGraw-Hill

1221 Avenue of the Americas


New York, NY 10020

800-2MCGRAW

www.books.mcgraw-hill.com

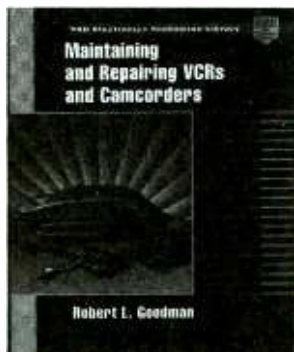
**\$34.95**

Written and illustrated with the technician or advanced hobbyist in mind, this book is designed to eliminate guesswork from VCR and camcorder troubleshooting and repair. An all-in-one resource, this manual shows readers how to perform every type of VCR repair and analysis. All the major brands are covered, including Sony, GE/RCA, Toshiba, JVC, 3M, Magnavox, VCR Plus, Philips, Sencore, RadioShack, and Matsushita. It has all the features to help readers troubleshoot, pinpoint problems, and handle repairs.



There are practical techniques for repairing the latest 8-mm and stereo VHS technologies. The clear, well-illustrated steps make every job easier, as do the case histories that provide solutions to frequently encountered malfunctions.

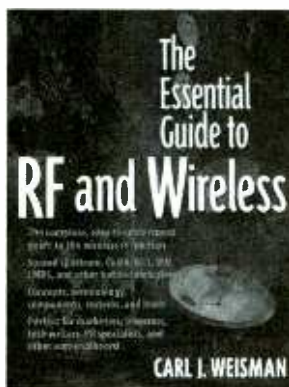Whether you're a customer, investor, hobbyist, professional, or student, this complete guide presents wireless and RF technology at every level. Everything from fundamental concepts, basic terminology, components, and system building blocks to complete systems are all covered.



Topics include spread spectrum and CDMA: how they work and where they're used; wireless local loop (WLL); and ISM-based LANs. The author also looks at Local Multipoint Distribution Service (LMDS): a new alternative for broadband wireless and RF technology. Dozens of charts, diagrams, and photographs make advanced wireless and RF technology easier to understand.

## AutoCAD and Its Applications: Basics, AutoCAD 2000

by Terence M. Shumaker

and David A. Madsen

Goodheart-Willcox Co.


18604 W. Creek Drive

Tinley Park, IL 60477-6243

800-323-0440 or 707-687-5000

www.goodheartwillcox.com

**\$43.96**

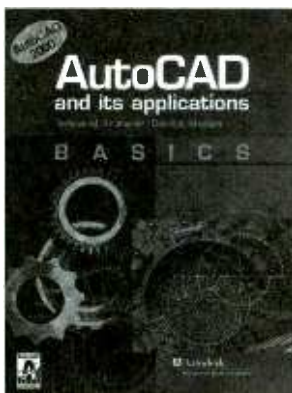

This edition provides comprehensive coverage of introductory and two-dimensional AutoCAD drafting. Organized in an easy-to-understand sequence, the text allows students to progress at a pace that makes them comfortable with the commands and drawing techniques.

There are discussions of every major feature, command, and option. Topics are keyed to the AutoCAD User Guide, and Professional Tips explain how to use AutoCAD efficiently. Hundreds of exercises, questions, and drawing problems help students master AutoCAD.

## Sourcebook for Electronics Calculations, Formulas, and Tables

by Newton C. Braga

Prompt Publications

Howard W. Sams & Company

2647 Waterfront Parkway, East Drive


Indianapolis, IN 46214-2041

800-428-7267

www.hwsams.com

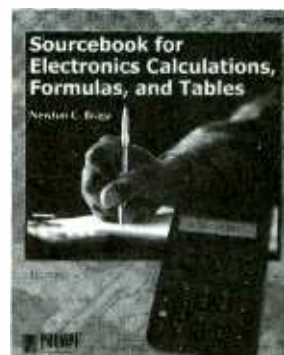**\$34.95**

This book is written for the engineer, student, technician, or hobbyist who designs or needs to understand more about electronic circuits. It contains an assortment of all the basic information necessary to make calculations when designing new projects—a one-stop guide.



Arranged by subject, the information ranges from the simplest elementary operation to the more complex trigonometric and calculus functions. Physical property tables of circuits and materials are included, and many of the formulas are accompanied by application examples. Units, conversions, reduced formulas, and "non-conventional" notations are also included to make design work easier and less frustrating.

## The Essential Guide to RF and Wireless

by Carl J. Weisman

Prentice Hall

One Lake Street

Upper Saddle River, NJ 07458

800-282-0693

www.phptr.com

**\$34.99**



## 2000 Communications Catalog

from Universal Radio, Inc.  
6830 Americana Parkway  
Reynoldsburg, OH 43068-4113  
800-431-3939 or 614-866-4267  
www.universal-radio.com

Free



This catalog (#00-33) covers equipment for the amateur, shortwave, and scanner enthusiast. An extensive selection of antennas, headphones, books, and accessories is also featured.

Among the new items are the TEN-TEC RX-340 and Palstar R30 Communications Receivers, the ICOM IC-R3 and Yaesu VR-500 Wideband Portable Receivers, the Sangean CC Radio, and ICOM 756 Pro HF Amateur Transceiver.

## The ARRL RFI Book

Edited by Ed Hare, W1RF1  
American Radio Relay League  
225 Main Street  
Newington, CT 06111-1494  
888-277-5289 or 860-594-0200  
www.arrl.org.

\$20

There are two kinds of hams: those who don't have interference problems and



those who actually get on the air. The latter type of enthusiast needs the tips in this book. The author and a team of RFI experts have compiled the best advice available on every type of interference, from automotive to TVI, from computers to lamps, from VCRs to stereos, and from intermodes to telephones. If it's a device that can be affected by interference, including the station receiver, readers will find practical cures here.

This extensively rewritten material brings hams and anyone else interested in this subject the most up-to-date and proven techniques for curing all kinds of interference problems. All the chapters from a previous ARRL interference book have been either revised or rewritten. The latest RFI regulations are covered, and the list of suppliers and the bibliography have been updated and expanded.

## Relay & Accessory Guide, 9th Edition (ET-2700-2)

from Philips ECG  
1001 Snapps Ferry Road  
Greeneville, TN 37744  
800-526-9354  
www.ecgproducts.com

Free

This complete and comprehensive reference guide contains 102 different series, including over 800 types of relays, proximity switches, photoelectric sensors, and accessories. It's an easy-to-use reference with its pictorial/tabular selector guide. The two-part replacement directory cross-references over 64,000 U.S., Asian, and European industry part numbers and 281 brand names to ECG replacements.



Complete specifications are provided for new products, with detailed electrical and mechanical data. Among the new

series are miniature and sub-miniature gullwings, inside "L" and through-hole PC mounts, industrial 12-pin plug-ins, and 2-coil motor-reversing contractors. The guide is also available on CD: *Microsoft Windows Cross-Reference Disc Version 2.0* (ET-2604W2.0). **P**

## Practical PIC Microcontroller Projects



This book covers a wide range of PIC based projects, including such things as digitally controlled power supplies, transistor checkers, a simple capacitance meter, reaction tester, digital dice, digital locks, a stereo audio level meter, and MIDI pedals for use with electronic music systems. In most cases the circuits are very simple and they are easily constructed. Full component lists and software listings are provided. For more information about PICs we suggest you take a look at BP394 -- An Introduction to PIC Microcontrollers.

To order Book #BP444 send \$7.99 plus \$3.00 for shipping in the U.S. and Canada only to Electronics Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240. Payment in U.S. funds by U.S. bank check or International Money Order. Please allow 6-8 weeks for delivery. ET10

FREE CONSUMER  
INFORMATION CATALOG.  
Call toll-free 1-888-8 PUEBLO.

Coil Design and  
Construction  
Manual



## YOU CAN WIND YOUR OWN COILS?

There's no trick to it except knowing what you are doing. In a unique, 106-page book you can become expert in winding RF, IF,

audio and power coils, chokes and transformers. Practically every type of coil is discussed and necessary calculations are given with the mathematical data simplified for use by anyone. Get your copy today!

Mail coupon to:

**Electronics Technology Today, Inc.**  
P.O. Box 240  
Massapequa Park, NY 11762-0240

Please send me my copy of *Coil Design and Construction Manual* (BP160). I enclose a check or money order for \$8.99 to cover the book's cost and shipping and handling expenses. NY state residents must add local sales tax.

Name

Address

City  State  ZIP

All orders must be paid in U.S. funds only. Sorry, no orders accepted outside of USA and Canada. Please allow 6-8 weeks for delivery. ET07

## SCATCAT

(continued from page 38)

After mounting the stand-alone items (J1, J2, LED1, S1, and SPKR1), connect suitable lengths of wire to them. After the boards are mounted using screws and threaded standoffs, it is a simple matter to make the appropriate connections to the screw-type terminals on the boards.

Drill a hole in the rear of the case for the line cord. Use a rubber grommet to protect the cord from chafing; wall-socket current will be passing through these wires. Add a cable tie or tie a strain-relief knot in the line cord inside the box.

As an alternative, you could have the line cord pass through the front panel in one corner. While that might not look as attractive, it does make working with the completed unit a breeze; everything comes out when the front panel is removed without worrying about dangling wires being yanked.



The completed ScatCat is ready to teach your pet a lesson about where they shouldn't go!

When you've completed wiring the ScatCat, double-check your work again for any mistakes such as miswirings, wrong components, polarized semiconductors or capacitors installed backwards, and the like. A good approach is to inspect everything and set it aside. Go do something else not related to electronics: Watch television, play a recreational sport, or visit with friends. The idea is to let your mind shift mental gears for a while. After a day or so, go back to the ScatCat and inspect it again. You'd be amazed how many seemingly "simple" errors can be overlooked

when you've been staring at them for hours at a stretch. After taking a break as outlined above, you can approach the unit as if it is new to you.

**Setup and Operation.** If a motion sensor with a relay-contact output is being used, Fig. 8 shows a suggested setup arrangement. Power from the 12-volt supply is connected to J1's "shield" side. That goes to one side of the motion sensor's relay. The other side of the relay feeds back to J1, as well as to the anode of LED1.

If the specified RadioShack unit is being used, insure it has a 9-volt battery installed. Plug P1 into J1 on the control unit's front panel. Turn the incandescent-lamp fixture (with I1) on and plug it into J2. Without turning on the ScatCat, switch SEN1 to its "chime" position; the system won't work in the alarm" position. Wave your hand in front of it; LED1 should light whenever SEN1 is activated, which is handy when setting up and aiming SEN1.

Position the sensor horizontally and aim it toward the area that you want to protect from animal intrusion. Observing LED1 while waving your hand will allow it to be set up to go off exactly where necessary. The sensor should be near the control unit so that the controls can be accessed, and the intrusion counter read, without setting it off yourself.

With LED1 off (no intrusion), turn on the ScatCat with S1. The "Intrusion Count" display on DISP1 should light, indicating "0." Set off the motion sensor. Four one-second high frequency sound bursts will occur, synchronized with four lamp flashes. The "Intrusion Count" display will increment by one count.

**Effectiveness.** Dogs are easy...and trainable. After a few incidents, they don't go there anymore. Cats, as any cat owner will tell you, are not trainable; they can, however, be conditioned. It just takes a little longer. Fred took about four or five days to convince. During this period, the intrusion counts grew fewer and less often. The first night, the counter showed two intrusions.

After he stopped, the ScatCat was left set up for a few more days, just to be sure.

A few weeks later, there was evidence of a cat on the counter again. The unit was set up again to give a little positive reinforcement. After one more intrusion count, he was apparently convinced, and hasn't been back since. Several friends and relatives borrowed the unit, and it has been successful in all cases.


The ScatCat will give pet-owning techies an opportunity to finally outwit their cats! Happy hunting! **P**

## INSIDE CRYSTAL SETS

An easy-to-read book on crystal set theory and construction opens vistas for novices and pros alike. Build radios like Grandpa did, do it better, and know what you are doing. *The Crystal Set Handbook*, published by The Crystal Set Society, is an authentic guide on the topic.

To order *The Crystal Set Handbook*, send \$10.95 plus \$4.00 for shipping in the U.S. and Canada only to **Electronics Technology Today Inc.**, P.O. Box 240, Massapequa Park, NY 11762-0240. Payment in U.S. funds by U.S. bank check or International Money Order. Please allow 6-8 weeks for delivery.

MA03

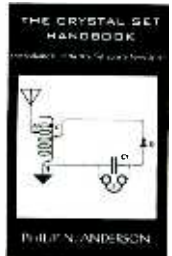

"What high-pitched sound, KA2GUN?  
Your signal sounds fine to me."

# ELECTRONIC TECHNOLOGY TODAY INC.

P.O. Box 240 • Massapequa Park, NY 11762

## INVENTORY BLOWOUT SALE

**30% OFF**

**FREE GIFT**  
With any order over \$15  
(while supplies last)



\* ALL CANADIAN CHECKS MUST CLEAR THROUGH AN AMERICAN BANK

BP07 . . . 100 Radio Hookups . . . . .	\$3.00	BP304 . . . . . Projects for Radio Amateurs and S.W.L.S . . . . .	\$5.99
BP37 . . . . . 50 Projects for Soldering Irons and Triacs . . . . .	\$3.99	BP317 . . . . . Practical Electronic Timing . . . . .	\$6.99
BP48 . . . . . Electronic Projects for Beginners . . . . .	\$2.99	BP320 . . . . . Electronic Projects for Your PC . . . . .	\$5.99
BP56 . . . . . Electronic Security Devices . . . . .	\$3.99	BP321 . . . . . <del>SOLD OUT</del> . . . . .	\$6.99
BP64 . . . . . Semiconductor Technology Elements of Elect Book 3 . . . . .	\$5.99	BP322 . . . . . Circuit Source Book 2 . . . . .	\$6.99
BP74 . . . . . Electronic Music Projects . . . . .	\$3.99	BP329 . . . . . Electronic Music Learning Projects . . . . .	\$6.99
BP76 . . . . . Power Supply Projects . . . . .	\$3.99	BP332 . . . . . A Beginners Guide to TTL Digital ICS . . . . .	\$6.99
BP78 . . . . . Practical Computer Experiments . . . . .	\$2.99	BP333 . . . . . A Beginners Guide to CMOS Digital ICS . . . . .	\$6.99
BP88 . . . . . How to Use OP Amps . . . . .	\$5.99	BP334 . . . . . Magic Electronic Projects . . . . .	\$6.99
BP93 . . . . . <del>SOLD OUT</del> . . . . .	\$2.99	BP355 . . . . . A Guide to the World's Radio Stations . . . . .	\$7.99
BP103 . . . . . Multi-Circuit Board Projects . . . . .	\$2.99	BP359 . . . . . An Introduction to Light in Electronics . . . . .	\$6.99
BP112 . . . . . A Z-80 Workshop Manual . . . . .	\$5.99	BP367 . . . . . Electronic Projects for the Garden . . . . .	\$6.99
BP114 . . . . . The Art of Programming the 16K ZX81 . . . . .	\$3.99	BP370 . . . . . The Superhet Radio Handbook . . . . .	\$6.99
BP115 . . . . . The Pre-Computer Book . . . . .	\$2.99	BP371 . . . . . Electronic Projects for Experimenters . . . . .	\$6.99
BP124 . . . . . Easy Add-On Projects for the Spectrum, ZX81 & ACE . . . . .	\$3.99	BP374 . . . . . Practical Fibre-Optic Projects . . . . .	\$6.99
BP148 . . . . . Computer Terminology Explained . . . . .	\$2.99	BP378 . . . . . 45 Simple Electronic Terminal Block Projects . . . . .	\$6.99
BP154 . . . . . An Introduction to MSX Basic . . . . .	\$3.99	BP379 . . . . . 30 Simple IC Terminal Block Projects . . . . .	\$6.99
BP156 . . . . . An Introduction to QL Machine Code . . . . .	\$3.99	BP384 . . . . . Practical Electronic Model Railways Projects . . . . .	\$6.99
BP187 . . . . . A Prac Ref Guide to Word Pro Amstrad PCW8256/PCW8512 . . . . .	\$7.99	BP391 . . . . . Fault-Finding Electronic Projects . . . . .	\$6.99
BP190 . . . . . More Advanced Electronic Security Projects . . . . .	\$3.99	BP392 . . . . . Electronic Project Building for Beginners . . . . .	\$6.99
BP194 . . . . . Modern OPTO Device Projects . . . . .	\$3.99	BP393 . . . . . Practical Oscillator . . . . .	\$6.99
BP232 . . . . . A Concise Introduction to MS-DOS . . . . .	\$3.99	BP394 . . . . . An Introduction to PIC Microcontrollers . . . . .	\$7.99
BP245 . . . . . Digital Audio Projects . . . . .	\$3.99	BP396 . . . . . Electronic Hobbyists Data Book . . . . .	\$7.99
BP248 . . . . . Test Equipment Construction . . . . .	\$3.99	BP401 . . . . . Transistor Data Tables . . . . .	\$7.99
BP256 . . . . . An Intro to Loudspeakers and Enclosure Design . . . . .	\$3.99	BP411 . . . . . A Practical Intro to Surface Mount Devices . . . . .	\$6.99
BP264 . . . . . A Concise Advanced User's Guide to MS-DOS . . . . .	\$3.99	BP413 . . . . . Practical Remote Control Projects . . . . .	\$7.99
BP267 . . . . . How to Use Oscilloscopes and Other Test Equipment . . . . .	\$5.99	PCP107 . . . . . Digital Logic Gates and Flip-Flops . . . . .	\$10.99
BP272 . . . . . Interfacing PCs and Compatibles . . . . .	\$5.99	PCP112 . . . . . Digital Electronics Projects for Beginners . . . . .	\$10.99
BP290 . . . . . An Intro to Amateur Communications Satellites . . . . .	\$5.99	PCP114 . . . . . Advanced MIDI Users Guide . . . . .	\$10.99
BP297 . . . . . Loudspeakers for Musicians . . . . .	\$6.99	ETT1 . . . . . Wireless & Electrical Cyclopedia . . . . .	\$4.99
BP299 . . . . . Practical Electronic Filters . . . . .	\$6.99		

PRICES DO NOT INCLUDE SHIPPING & HANDLING. ALL SALES ARE FINAL, NO RETURNS

### ORDER FORM

Book No.	Title	Price	No. of Copies	Cost

<b>SHIPPING COSTS</b>		Total Amount \$
\$0.01 to \$5.00 . . . \$2.00	\$20.01 to \$30.00 . . . \$5.00	38% off
\$5.01 to \$10.00 . . . \$3.00	\$30.01 to \$40.00 . . . \$8.00	Subtotal
\$10.01 to \$20.00 . . . \$4.00	\$40.01 to \$50.00 . . . \$7.00	Add shipping cost (see table)
\$50.01 and above . . . \$8.50		Local NY State Sales Tax
		<b>TOTAL COST \$</b>

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

If you wish to use a Credit Card:

MasterCard    Visa   Expire Date \_\_\_\_\_ / \_\_\_\_\_  
Card No. \_\_\_\_\_  
Signature \_\_\_\_\_

Allow 6-8 weeks for order to be fulfilled.

Please return this order form to:  
ELECTRONIC TECHNOLOGY TODAY, INC.  
P.O. Box 240  
Massapequa Park, NY 11762-0240



Telephone Orders: If you wish to place your credit-card order by phone, call 516/592-6722. Automated order taking system functions 24 hours a day. Have your credit-card ready. Sorry, no orders accepted outside of U.S.A. and Canada, New York State Residents must add applicable sales tax. Offer expires 9/30/00.

ET11

## Marathon of Simple Circuits

This month, we're going to sponsor a marathon of simple circuits that hopefully will be the catalyst needed to turn a stalled project into a completed device or to spark an interest in starting a new project. We'll start out by looking at three basic audio circuits and see where that leads us.

### Broadband Audio Amplifier

Our first audio circuit (see Fig. 1) is a two-transistor broadband audio amplifier. The amplifier circuit has a voltage gain of about 60 in the boost position and 15 in the non-boost position. In both gain positions, the amplifier's frequency response is almost flat from 200 Hz to over 100 kHz. Transistor Q1 is connected as a common-emitter amplifier, with resistors R1, R2, and R3 setting the transistor's operating bias. The amplifier's AC voltage gain increases from 15 to 60, when Q1's emitter impedance is lowered by paralleling R5 with R4. Capacitor C4 couples the AC signal through resistor R5, when the boost switch is closed, without changing the transistor's biasing arrangement. The amplifier's output is isolated from external loading by transistor Q2, an emitter-follower amplifier. Almost any NPN audio transistor with a minimum hfe gain of 100 can be used for Q1, and Q2 can be any PNP audio transistor.

This amplifier can supply a 2-volt peak-to-peak output to an external 1000-ohm load or can be used to drive a low-impedance headphone pair if we add a 470-ohm resistor in series with the output.

### Audio-Signal Tracer

Troubleshooting audio equipment or tracing audio signals is as difficult today as it was when grandpa spent his youth working on tube- and early transistor-audio gear. Long before the oscilloscope became an affordable test instrument, the audio-signal tracer was one of the most often used and probably the most

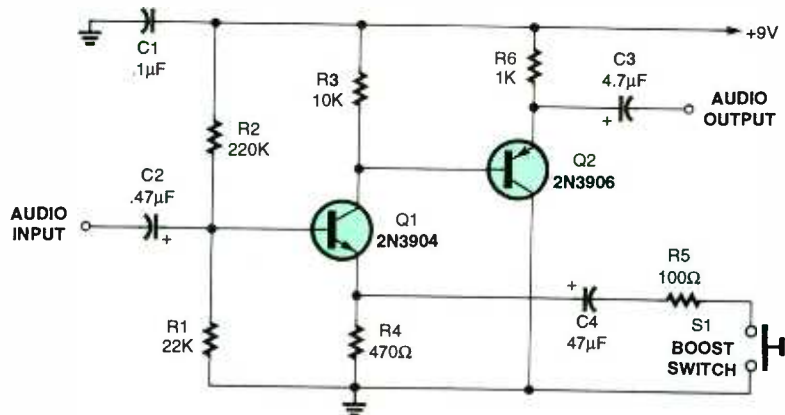


Fig. 1. A simple audio amplifier can be used to drive a low-impedance headphone or to supply a 2-volt peak-to-peak output to an external 1000-ohm load.

valuable test instrument available for the serious-minded technician or home experimenter. Even in today's high-tech world of microelectronics, a modern solid-state version of the time-proven audio tracer is still a useful tool. Our version uses that ever-popular low-voltage audio power amplifier IC, the LM386. This little 8-pin mini-dip IC is designed for battery-powered operation between 4 and 15 volts; the quiescent current is less than 10 mA. The amp's voltage gain can be as high as 200. Best of all, the LM386 is very affordable, going at most electronic retail stores for about a buck-twenty. If the few remaining parts can be salvaged from discarded electronic gear, the audio tracer can be built for less than the cost of a street hot dog.

### Sinusoidal Transistor Phase-Shift Oscillator

Our next circuit is a great companion for the audio tracer. If you are going to be a signal scout, you've got to have a signal to track or you'll go nowhere at all. If your troubleshooting takes you down the path where no signals flow, then build the sinusoidal transistor phase-shift oscillator shown in Fig. 3 and use it to produce your own signal to trace.

### PARTS LIST FOR THE BROADBAND AUDIO AMPLIFIER (FIG. 1)

#### SEMICONDUCTORS

Q1—2N3904 NPN silicon transistor  
Q2—2N3906 PNP silicon transistor

#### RESISTORS

(All resistors are 1/4-watt, 5% units.)

R1—22,000-ohm  
R2—220,000-ohm  
R3—10,000-ohm  
R4—470-ohm  
R5—100-ohm  
R6—1000-ohm

#### CAPACITORS

C1—0.1-µF, ceramic-disc  
C2—0.47-µF, 25-WVDC, electrolytic  
C3—4.7-µF, 25-WVDC, electrolytic  
C4—47-µF, 25-WVDC, electrolytic

#### ADDITIONAL PARTS AND MATERIALS

S1—Single-pole, single-throw, normally-open pushbutton switch

The heart of the oscillator circuit is the RC phase shift network that connects between Q1's base and collector. The network is made up of C1, C2, C3, R1, R2, and R5. Those components

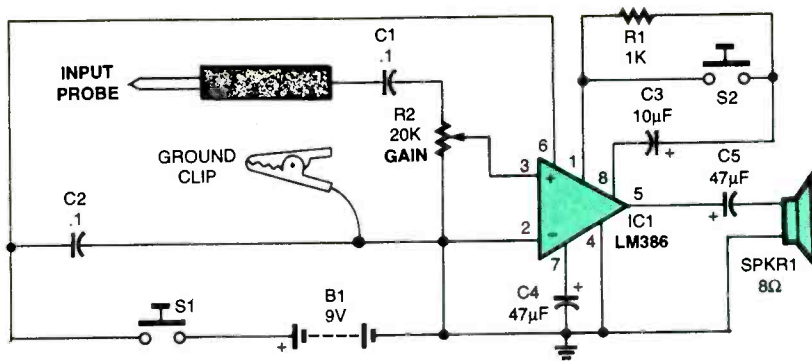


Fig. 2. An audio-signal tracer can be a valuable tool when troubleshooting all kinds of audio circuitry.

### PARTS LIST FOR THE AUDIO-SIGNAL TRACER (FIG. 2)

#### RESISTORS

(All fixed resistors are 1/4-watt, 5% units unless otherwise noted.)

- R1—1000-ohm
- R2—20,000-ohm potentiometer

#### CAPACITORS

- C1, C2—0.1- $\mu$ F, ceramic-disc
- C3—10- $\mu$ F, 25-WVDC, electrolytic
- C4, C5—47- $\mu$ F, 25-WVDC, electrolytic

#### ADDITIONAL PARTS AND MATERIALS

- IC1—LM386 audio power amp. integrated circuit
- S1, S2—Single-pole, single-throw, normally-open pushbutton switch
- SPKR1—8-ohm speaker
- 9-volt battery, case, ground clip, etc.

determine the oscillator's frequency. Resistor R5 serves as the frequency-control potentiometer, which gives the oscillator a tunable frequency range of about 500 to 1000 Hz. Transistor Q1's gain can be adjusted with R6 for maximum output signal with minimum distortion. Transistor Q2 operates as a non-inverting buffer amplifier with R7

acting as a variable output control. The maximum output is about 6 volts peak-to-peak when powered by a 9-volt source.

#### Turn-Signal Reminder

Moving right along to our next entry, we find ourselves far away from the world of audio and into the world of road rage. Often as I travel the highways, I'll find myself following a vehicle that has the turn signal stuck in the ON position flashing for miles and miles. I don't know if it is the constant distraction or just not knowing what that person is going to do next, but in either case it sure can increase the blood pressure and take the fun out of the journey. We may not be able to make the other drivers more attentive to their driving habits, but we can build the turn-signal-reminder circuit in Fig. 4 and become a positive role model for other travelers.

A single CD4049 CMOS hex-inverting-buffer IC is the heart of the reminder circuit. Two of the inverters, IC1-a and IC1-b, are connected in a simple variable-frequency squarewave audio-oscillator circuit. The oscillator drives the remaining four paralleled inverters, which in turn drive the piezoelectric sounder. The anodes of the two

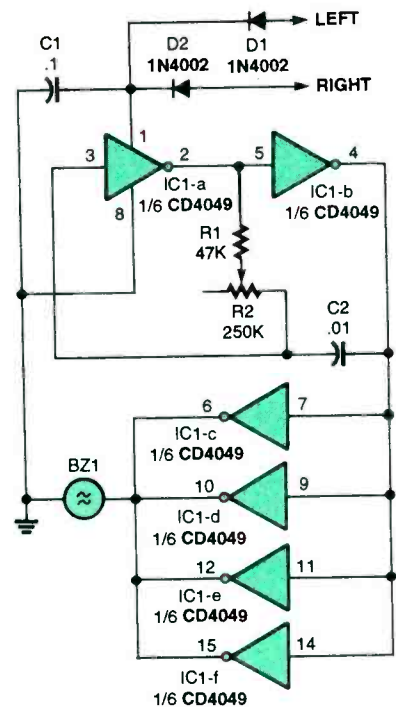


Fig. 4. You won't forget to disengage your car's turn signal if you install this warning device.

diodes, D1 and D2, are connected to the left and right turn-signal outputs, which is normally at zero volts when neither signal is activated. Operating either of the turn signals supplies a pulsing positive voltage to the anode of one of the diodes, powering the circuit and making it emit a beeping audio tone.

Most piezo speakers or sounders produce maximum output power when they are operated at their natural resonant fre-

### PARTS LIST FOR THE PHASE-SHIFT OSCILLATOR (FIG. 3)

#### SEMICONDUCTORS

- Q1—2N3904 NPN silicon transistor
- Q2—2N3906 PNP silicon transistor

#### RESISTORS

(All fixed resistors are 1/4-watt, 5% units unless otherwise noted.)

- R1—10,000-ohm
- R2—4700-ohm
- R3—220,000-ohm
- R4—3300-ohm
- R5—10,000-ohm potentiometer
- R6—100-ohm potentiometer
- R7—5000-ohm potentiometer

#### CAPACITORS

- C1—C3—0.015- $\mu$ F Mylar
- C4—4.7- $\mu$ F, 25-WVDC, electrolytic

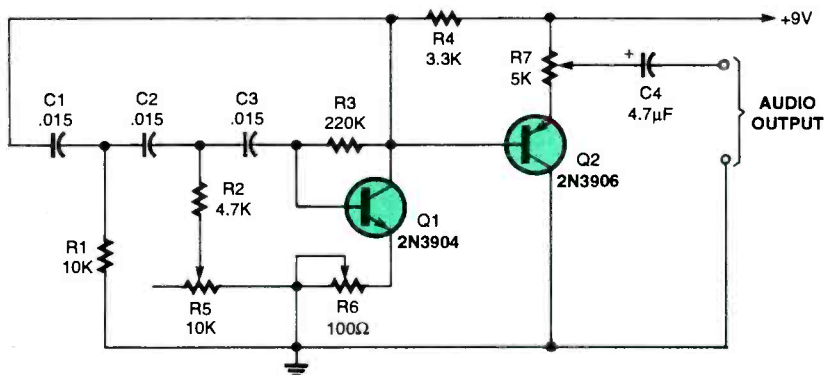


Fig. 3. Signal injectors like this one work hand-in-hand with the audio tracer in Fig. 2.

## PARTS LIST FOR THE TURN-SIGNAL REMINDER (FIG. 4)

### SEMICONDUCTORS

IC1—CD4049 hex-inverting-buffer  
D1, D2—1N4002 1-amp silicon diode

### RESISTORS

(All resistors are 1/4-watt, 5% units  
unless otherwise noted.)

R1—47,000-ohm  
R2—250,000-ohm potentiometer

### CAPACITORS

C1—0.1- $\mu$ F, ceramic-disc  
C2—0.01- $\mu$ F, ceramic-disc

### ADDITIONAL PARTS AND MATERIALS

BZ1—Piezo speaker

quency. Adjust R2 for the loudest output tone. If the natural resonant frequency cannot be reached, try changing the value of C2. Smaller capacitance values will give higher output frequencies, and larger values will produce lower frequencies. Have fun and build one of these for yourself or a forgetful friend.

### Positive-Voltage Booster Circuit

Our next entry, shown in Fig. 5, is a positive-voltage booster circuit. This

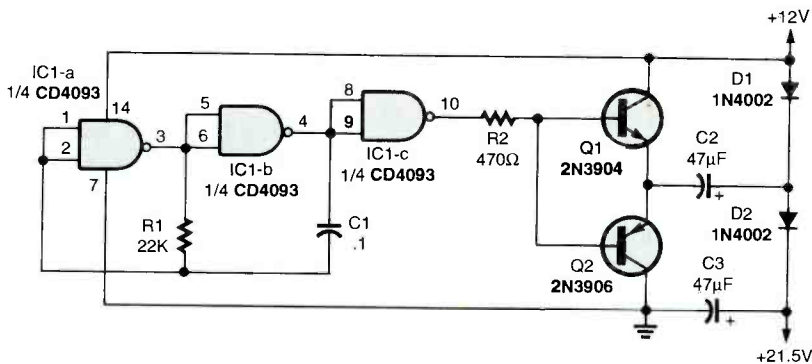


Fig. 5. A positive-voltage booster can increase your operating voltage by as much as 175% and still deliver an output current capacity of 10 to 20 mA.

## PARTS LIST FOR THE POSITIVE-VOLTAGE BOOSTER (FIG. 5)

### SEMICONDUCTORS

IC1—CD4093 CMOS quad 2-input  
NAND Schmitt trigger, integrated  
circuit  
Q1—2N3904 NPN silicon transistor  
Q2—2N3906 PNP silicon transistor  
D1, D2—1N4002 1-amp silicon diode

### RESISTORS

(All resistors are 1/4-watt, 5% units.)  
R1—22,000-ohm  
R2—470-ohm

### CAPACITORS

C1—0.1- $\mu$ F, ceramic-disc  
C2, C3—47- $\mu$ F, 25-WVDC, electrolytic

handy little circuit can increase your operating voltage by as much as 175% with an output current capacity of 10 to 20 mA. Gates IC1-a and IC1-b of a CD4093 dual-input NAND Schmitt-trigger CMOS IC are connected in a squarewave-oscillator circuit with the output buffered by gate IC1-c. The buffered output drives a complementary transistor pair, Q1 and Q2. The square-wave output at the emitters drives the voltage-doubler circuit made up of D1, D2, C2, and C3 to produce a boost output. With a 12-volt supply, the boost circuit will output 21.5 volts at about 10 mA and about 18.5 volts with an output current of 20 mA. Be sure to tie the inputs of the unused gate to circuit ground.

### Variable DC Power Converter

Our next entry in the circuit marathon is a simple variable 5- to 9-volt DC power converter that requires only a single IC and two resistors. Its schematic is shown in Fig. 6. Best of all, with some parts scrounging, the cost should be only a buck or two. The circuit is ideal for use in an automobile or at home with a 12-volt bench supply. The converter can be used to power gadgets that require no more than 1 amp at any voltage between 5 and 9. If the converter were going to be used at or

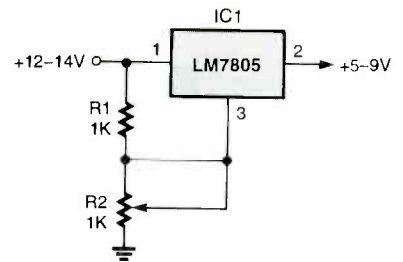


Fig. 6. This DC power converter makes it easy to operate AC devices from a 12-volt car battery.

## PARTS LIST FOR THE VARIABLE DC POWER CONVERTER (FIG. 6)

IC1—LM7805 5-volt voltage regulator,  
integrated circuit

R1—1000-ohm, 1/4-watt, 5% resistor  
R2—1000-ohm potentiometer

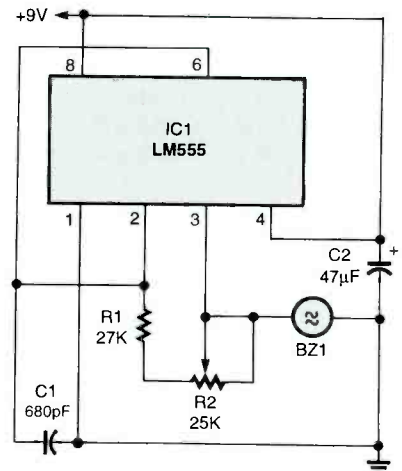


Fig. 7. Here's an ultrasonic "whistle" to help you train your dog.

## PARTS LIST FOR THE ULTRASONIC DOG TRAINER (FIG. 7)

### RESISTORS

(All resistors are 1/4-watt, 5% units  
unless otherwise noted.)  
R1—27,000-ohm  
R2—25,000-ohm potentiometer

### CAPACITORS

C1—680-pF, ceramic-disc  
C2—47- $\mu$ F, 25-WVDC, electrolytic

### ADDITIONAL PARTS AND MATERIALS

IC1—LM555 timer, integrated circuit  
BZ1—Piezo speaker (RadioShack 40-  
1383 or similar)

near its maximum current capacity, it wouldn't hurt to bolt the IC to a piece of aluminum and keep the operation running cool.

### Ultrasonic Dog Trainer

Our next circuit is an interesting and fun device that can be used to confuse, irritate, and hopefully help train your four-legged, tail-wagging friends. Of course, I can't guarantee that Fido will agree with the training part.

When it comes to the sense of smell and hearing, our best friends have us

beat hands down. Just about where our hearing drops off the chart, Fido's is still going strong. The circuit in Fig. 7 will generate ultrasonic frequencies from about 15 kHz to about 45 kHz. The lower frequency end of the range is an excellent area to use in experimenting with training your dog. Your pet's hearing is very sensitive to the high-frequency output so be sure that you keep the exposure time to a minimum.

The heart of the ultrasonic generator is a 555 IC. It is connected in a variable-frequency square-wave oscillator circuit

with its output, at pin 3, driving a 2-inch piezo speaker. The oscillator is tuned to the desired frequency by R2, a 25K potentiometer. A standard 9-volt transistor battery powers the circuit.

That is about all we have time for this month. Between now and our next visit, put some of these basic circuits to work. Revive an old project, or, better yet, create a new one and let me know how it turned out. I can be reached via snail mail at Charles D. Rakes, P.O. Box 445, Bentonville, AR 72712, or via e-mail as listed at the top of the column. **P**

## PEAK COMPUTING

(continued from page 15)

two external IEEE-1394 connectors rather than three. With IEEE-1394's daisy-chaining capability, it doesn't much matter.

Once installed, *Studio DV* operates very much like most video-editing applications. You need to capture the video to your hard disk, select clips from the captured video, arrange them, and add in transition and special effects to make a complete video. When finished, you either save the video in one of the common video formats, perhaps burning it to a CD-R, or output the completed video back to tape.

As with all video-editing applications that provide IEEE-1394 support, using *Studio DV* is a blast. The IEEE-1394 support lets you use the software to control most digital camcorders, such as the Canon

Optura that we used for testing. There's no going back and forth between the camcorder and the PC's keyboard, which makes the whole process a lot smoother. Down-loading the video from camcorder to PC is a whole different experience, as well. Many of the other video capture solutions we've tried over the years have trouble moving full-motion 30-fps video and audio into a PC without dropping frames or losing synchronization with the audio track. That simply didn't happen with *Studio DV*.

However, the way that *Studio DV* differs most from other lower-end editing products is how it handles the capture process. While most other editing programs capture video at full-resolution, *Studio DV* performs the initial video capture at a lower resolution, saving lots of hard disk space. You mark the clips that you want to

actually work with, which can be done even over several different tapes. When you're finished, *Studio DV* will go back to the tapes and recapture only those segments that you actually want to include at a much higher resolution. Therefore, when you are capturing at preview resolution, the video takes up only about 50 MB of space for 20 minutes of captured video. At "real" finished resolution, you'll need about 4 GB of space for the same 20 minutes of high-quality video.

Pinnacle's *Studio DV* provides an easy and complete solution to adding both IEEE-1394 and digital-video-editing capabilities to your PC. Don't be afraid to go a different route if your needs are different. IEEE-1394 interfaces are inexpensive enough and easy to install and run; you should consider one if only to add a high-performance external disk drive. **P**

## SOLAR-CELL INVERTER

(continued from page 41)

"BEAM" robot; see the June, 1997 issue of **Electronics Now** for more information on BEAM robots.

**Modifications.** You can get even higher output voltages by putting two solar cells in series at the input to provide a one-volt source voltage, which would yield an output of up to 30 volts. The inverter hasn't been tested with voltages greater than one volt, so you're on your

own beyond the one-volt mark.

You might want to experiment with the values for the coupling resistors and capacitors. The resistors control the maximum drive available at the bases of the transistors, and the capacitors control the frequency of oscillation. The trade-offs involved here are a bit too complex to easily lend themselves to a theoretical treatment, so the empirical approach is the best here. Be cautious about choosing resistor values too low, however, especially if you are using more than one cell in series

at the input.

If you want to experiment with two or more cells in series, you can switch to silicon transistors such as 2N3904 or 2N4401 NPN units, or 2N3906 or 2N4403 PNP units. If you use NPN transistors, don't forget to reverse your input voltage; the negative side goes to the emitters of the transistors. Don't get too carried away; beyond a certain point, you won't get any higher voltage at the output because of saturation of the transformer cores.

Have fun! **P**

SEE WHAT TAKES SHAPE. EXERCISE.

American Heart Association 

© 1992, American Heart Association

# RETAILERS THAT SELL OUR MAGAZINE EVERY MONTH

## Arizona

Circuit Specialists, Inc.  
220 S. Country Club Dr.  
Bldg 2  
Mesa, AZ 85210

Elliott Elec. Supply  
1251 S. Tyndell Ave.  
Tucson, AZ 85713

## California

All Electronics  
14928 Oxnard Street  
Van Nuys, CA 91411

California Electronics  
221 N. Johnson Ave.  
El Cajon, CA 90202

Electronics Plus, Inc.  
823 4th St.  
San Rafael, CA 94901

Electronics Warehouse  
2691 Main Street  
Riverside, CA 92501

Ford Electronics  
8431 Commonwealth Ave  
Buena Park, CA 90621

HSC Electronics  
6819 S. Redwood Drive  
Cotati, CA 94931

HSC Electronics  
4837 Amber Lane  
Sacramento, CA 95841

Halted Specialties Co.  
3500 Ryder Street  
Santa Clara, CA 95051

Inland Electronic Suppliers  
1012 N. Carpenter Rd.  
Modesto, CA 95351

Kandarian Electronics  
1101 19th Street  
Bakersfield, CA 93301

Mar Vac Electronics  
2001 Harbor Blvd.  
Costa Mesa, CA 92627

Mar Vac Electronics  
1759 E. Colorado Blvd.  
Pasadena, CA 91106

Mar Vac Electronics  
4747 Holt Blvd.  
Montclair, CA 91763

Mar Vac Electronics  
5184 Hollister Blvd.  
Santa Barbara, CA 93111

Mar Vac Electronics  
2537 Del Paso Blvd.  
Sacramento, CA 95815

Mar Vac Electronics  
2000 Outlet Center Dr. #150  
Oxnard, CA 93030

Mar Vac Electronics  
12453 Washington Blvd.  
Los Angeles, CA 90066

Metro Electronics  
1831 J Street  
Sacramento, CA 95814

Minute Man Electronics  
37111 Post St., Suite 1  
Fremont, CA 94536

Orvac Electronics  
1645 E Orangethorpe Ave.  
Fullerton, CA 92631

Sav-On Electronics  
13225 Harbor Blvd.  
Garden Grove, CA 92643

Whitcomm Electronics  
105 W. Dakota 106  
Clovis, CA 93612

## Colorado

Centennial Elec. Inc.  
2324 E. Bijon  
Colorado Springs, CO  
80909

## Connecticut

Cables & Connectors  
2198 Berlin Turnpike  
Newington, CT 06111

## Illinois

BB&W Inc.  
2137 S. Euclid Ave.  
Berwyn, IL 60402

Tri State Elex  
200 W. Northwest Hwy.  
Mt. Prospect, IL 60056

## Indiana

King of the Road Elec.  
409 E. Center Rd.  
Kokomo, IN 46902

## Maryland

Mark Elec. Supply Inc.  
11215 Old Baltimore Pike  
Beltsville, MD 20705

## Massachusetts

Electronic Hook-Up  
104 Main St.  
Milford, MA 01757

"You-Do-It" Electronics  
40 Franklin Street  
Neeham, MA 02494

## Michigan

Norwest Electronics  
33760 Plymouth Rd.  
Livonia, MI 48150

Purchase Radio Supply  
327 East Hoover Avenue  
Ann Arbor, MI 48104

The Elec. Connection  
37387 Ford Road  
Westland, MI 48185

## Minnesota

Acme Electronics  
224 Washington Avenue N.  
Minneapolis, MN 55401

## Missouri

Gateway Electronics  
8123-25 Page Blvd.  
St. Louis, MO 63130

## New Jersey

Lashen Electronics Inc.  
21 Broadway  
Denville, NJ 07834

## New York

LNL Distributing Corp.  
235 Robbins Lane  
Syosset, NY 11791

T&M Elec. Supply, Inc.  
472 East Main Street  
Patchogue, NY 11772

Unicorn Electronics  
Valley Plaza  
Johnson City, NY 13790

## Ohio

Parts Express  
725 Pleasant Valley Drive  
Springboro, OH 45066

Philcap Electronic Suppliers  
275 E. Market Street  
Akron, OH 44308

## Oregon

Norvac Electronics  
7940 SW Nimbus Avenue  
Beaverton, OR 97005

## Texas

Computers Electronics Etc.  
110 E. Medical Center Blvd.  
Webster, TX 77598

Electronic Parts Outlet  
3753 B Fondren  
Houston, TX 77063

Tanner Electronics  
1301 W Beltline  
Carrollton, TX 75006

## Washington

Supertronix Inc.  
16550 W. Valley Hwy.  
Tukwila, WA 98188

**If you'd like to sell our magazine in your store,  
please circle 180 on free information card  
or Contact**

**Gina Gallo at (631) 592-6720 ext 215**



# Poptronics®

# SHOPPER<sup>®</sup>

## The Leader in Micro Video Cameras

### Wireless Camera System



**Color Camera/Transmitter**  
GFC-5001 \$159.95

**4-Channel A/V Receiver**  
GFR-5002 \$119.95

**Features:**

- 2.4 Ghz Wireless CCD Camera with 4-channels selection switch
- Operating frequency of ISM band 2.4 - 2.4835GHz on 4-channels.
- Patch Antennas
- Digital Image Filter to enhance picture clarity.
- Connects to any PC Video capture card, TV or VCR.
- Unequaled quality and reliability.
- 5-minutes to install.

**1-Camera/Receiver Package**  
GFP-5005 \$249.95

**Package Contents:**

- 1-Transmitting Camera & 1-Receiver
- 2-Patch antennas
- 2-Power supplies
- 1-RCA Cable
- 1-Mounting Bracket

### Flat Screen TFT-LCD Monitors



**TFT-4 \$179.95**

4" Screen (Size: 6"(W) x 4.5"(H) x 2"(D))  
An excellent monitor for one camera monitoring or for setting up cameras during installation or maintenance.  
*Several Sizes Available.*



**CM-500cBC \$129.95**  
Aluminum cased Color camera with mounting bracket.

Dimensions: 1.5" Sq



**LP-850w \$169.95**

Built-In Infrared Illuminator, Camera can See in the Dark without Additional Light Source!  
1.4"(Dia.) x 1.8"(L) w/o stand



Color weatherproof video camera.  
**WP-300c \$229.95**  
0.78"(Dia.) x 2.6"(L) w/o stand

### Wireless Transmitter & Receiver

**Transmits From:**

- Surveillance Camera
- Digital Video Disc
- Laser Disc Player
- Satellite Receiver
- Wireless Cable
- Stereo Audio
- VCR
- Cable TV
- CD Player
- Camcorder
- A/V Receiver

**WR-2400 wireless Receiver \$129.95**



Receiver




Transmitter

**WT-2400 wireless Transmitter \$129.95**

Back of Transmitter & Receiver are identical.

### Live Remote Video Server

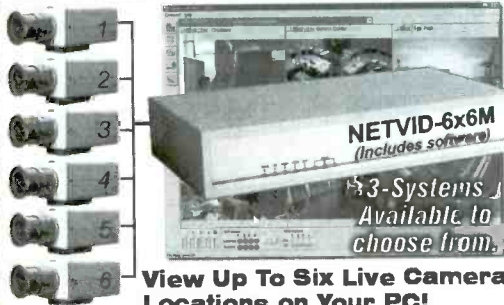

**NETVID-6x6M (Includes software)**

3-Systems Available to choose from.

**View Up To Six Live Camera Locations on Your PC!**

**NETVID-6x6M Server... Works 3-Ways!**

1. Over standard phone line or ISDN.
  2. Internet using Internet Explorer or Netscape Navigator.
  3. PC - LAN/Network.
- PC remote software allows user to dial into NETVID-6x6M Server from any location!  
**Includes: NETVID-6x6M server, Software & Modem. Cameras are Not included.**

**Dial-Up Video Security for:**

- Security/Intrusion • Detect & Photograph Intruders
- Corporate management tool • Beach House, Cabin
- View your home while at work • Save to a Hard Drive



**Polaris Industries**  
[www.polarisusa.com](http://www.polarisusa.com)  
**800.752.3571**

**Free Polaris Video Catalog**

### Camera with Vari-Focal Lens



**Micro "ZOOM" Lens**

**MB-1250HRVF \$199.95**

470 TV Line Color Board Camera with a 4-8mm Vari-focal lens.

1.25 inch sq.



• **MB-1250HRVF \$199.95**  
High-Res Vari-Focal Color Camera

• **MB-1250HRp \$149.95**  
High-Res Pinhole Color Camera

• **MB-1250p \$99.95**  
Low-Res Pinhole Color Camera

### LIPSTICK CAMERAS

**LP-850p \$119.95**

**LP-850i \$109.95**



Length: 1.37" Diameter: .87" B/W Model

B/W Model


Length: 1.9" Diameter: .91"

**Polaris Industries 470 Armour Dr. Atlanta GA 30324 • Tech Info: 404.872.0722 FAX: 404.872.1038**

CIRCLE 300 ON FREE INFORMATION CARD

# ELECTRONIC COMPONENTS

www.mouser.com

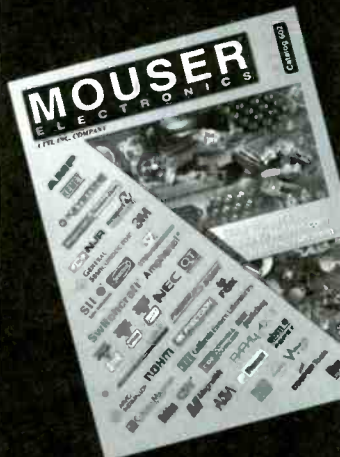

**MOUSER**  
ELECTRONICS

A **ti** COMPANY

sales@mouser.com

(800) 346-6873 • 817-483-6828  
FAX: 817-483-6899

CIRCLE 220 ON FREE INFORMATION CARD

## Accredited B.S. Degree in Computers or Electronics by studying at Home

Grantham College of Engineering  
offers 3 distance education programs:

- B.S.E.T. emphasis in Electronics
- B.S.E.T. emphasis in Computers
- B.S. in Computer Science

-Electronics Workbench Professional 5.0  
included in our B.S.E.T. curriculums  
-Approved by more than 200 Companies,  
VA and Dantes, (tuition assistance avail.)

For your free catalog of our programs dial

1-888-919-8181 Ext. 15


<http://www.grantham.edu>

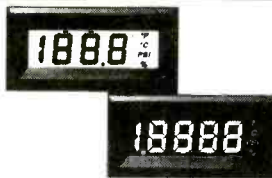**GCE**

Your first step  
to help yourself  
better your future!



Grantham College of Engineering  
34641 Grantham College Road  
Slidell, LA 70460-6815



**KINS**  
Instruments



1-800-

356-4920

### Digital Panel Meters!!

- LCDs • LEDs • 3 1/2 digits • 4 1/2 digits
- loop powered • adjustable voltage input
- bezel mount • surface mount
- miniatures • big digits
- black • red
- amber • green
- negative backlighting
- positive backlighting
- RF resistant EMI resistant
- displayed engineering units • snap-in



We also have Kroy tape  
and shrink tube labeling  
systems and supplies!



Visit our catalog on-line  
[knsinstruments.com](http://knsinstruments.com)

Or call toll free: **800/356-4920**  
Fax: **800/356-1250**



603/627-5144 • Fax 603/624-4710  
PO Box 10158 • Bedford, NH 03110-0158

## Turn Your Multimedia PC into a Powerful Real-Time Audio Spectrum Analyzer

### Features


- 20 kHz real-time bandwidth
- Fast 32 bit executable
- Dual channel analysis
- High Resolution FFT
- Octave Analysis
- THD, THD+N, SNR measurements
- Signal Generation
- Triggering, Decimation
- Transfer Functions, Coherence
- Time Series, Spectrum Phase,  
and 3-D Surface plots
- Real-Time Recording and  
Post-Processing modes

### Applications

- Distortion Analysis
- Frequency Response Testing
- Vibration Measurements
- Acoustic Research
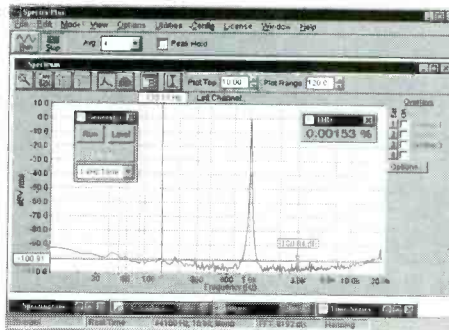
### System Requirements

- 486 CPU or greater
- 8 MB RAM minimum
- Win. 95, NT, or Win. 3.1 + Win.32s
- Mouse and Math coprocessor
- 16 bit sound card



**Priced from \$299**

(U.S. sales only - not for export/resale)

**DOWNLOAD FREE 30 DAY TRIAL!**

[www.spectraplus.com](http://www.spectraplus.com)

**PHS** Pioneer Hill Software  
24460 Mason Rd.  
Poulsbo, WA 98370  
a subsidiary of Sound Technology, Inc.

Sales: (360) 697-3472



**Spectra Plus**  
FFT Spectral Analysis System

Fax: (360) 697-7717

e-mail: [pioneer@telebyte.com](mailto:pioneer@telebyte.com)

## "The Sound Bridge" FM Stereo Wireless Transmitter

The Sound Bridge is a mini FM wireless transmitter that can be used to broadcast stereo sound from any audio source like portable CD players, TVs, electronic games, CD-ROM, even computer soundcards, to your home stereo receiver! Simply plug the unit's audio connector (includes 3.5mm mini stereo plug and standard 1/4" stereo plug) into the headphone or audio output jack of the device you want to broadcast, tune your stereo receiver to 90 MHz (can be adjusted from 89 to 95.5 MHz), and stereo sound is now being broadcast over your sound system with excellent sound quality. Requires two "AAA" batteries, not included. Limited availability.

#249-220 ..... \$14<sup>95</sup> EACH

## 201 PanaVise Jr.

This mini vise is an invaluable bench top companion for the home hobbyist. PV Jr. uses the famous PanaVise design that turns, tilts, and rotates for a full range of movement. Ideal for soldering, gluing, and general work. Features jaws that open to 2-7/8", both vertical and horizontal grooves to hold work, and a fine adjustment knob. Net weight: 1-1/4 lbs.



#365-300 ..... \$19<sup>95</sup> EACH

## DMM and LCR Meter

In addition to functions found in regular DMMs, this meter can also measure inductance in 5 ranges (4mH, 40mH, 400mH, 4H, 40H), capacitance in 5 ranges (4nF, 40nF, 400nF, 4uF, 400uF), frequency in 4 ranges (4kHz, 40kHz, 400kHz, 4MHz), TTL logic test, diode test and transistor hFE test. 5 AC/DC ranges up to 1000V (AC750V), 3 AC/DC current ranges up to 10A and 7 resistance ranges up to 4000 M ohms. Includes test leads, battery, spare fuse, and manual. Net weight: 1 lb.



#390-513 ..... \$85<sup>90</sup> EACH

## 30W Stereo Amplifier Kit

This small amplifier is constructed around the TDA1521 IC, capable of delivering 2x15W RMS (4 ohm) or 2x10W RMS (8 ohm). The IC is thermally and short circuit protected. THD: .07% (1W/1KHz). Frequency response: 7 to 60,000Hz (-3dB). Requires 2x12 VAC, 2A transformer, our #129-050. Net weight: 1 lb.



#320-212 (Kit) ..... \$29<sup>95</sup> EACH

#320-213 (Assembled/Tested) ... \$44<sup>95</sup> EACH

If you haven't received a copy of our current 284 page catalog... have one added to your order or give us a call and we will send one out to you immediately.



## Dayton Loudspeaker Co.<sup>®</sup> 6-1/2" Round Coaxial System

Designed for the home and office, these 6-1/2" round in-walls are ideal for ceiling installations, or for use as rear channel surround speakers.



#300-408 ..... \$69<sup>95</sup> (1-3 PRS) \$62<sup>75</sup> (4PRS-UP)

## D25 Multimedia Speaker System

Two amplified, magnetically shielded speakers with bass, treble, volume and mute controls. Headphone jack and heavy duty 9V, 1 Amp power supply.



#299-510 ..... Compare To \$29.95 \$9<sup>95</sup> EACH

## Color Video Camera With Audio

- ◆ Single chip 1/3" format camera
- ◆ 310 TV line resolution
- ◆ Built-in audio
- ◆ Focusable lens
- ◆ Automatic gain control
- ◆ Auto white balance
- ◆ Pick-Up device: 1/3" CMOS
- ◆ Light sensitivity: 10 Lux
- ◆ Lens: 4.3mm
- ◆ S/N Ratio: >38dB
- ◆ Power: 8-12VDC, 30mA (9VDC adaptor included)



#335-485 ..... \$99<sup>95</sup> (1-3) \$95<sup>50</sup> (4-UP)

## 5" LCD Monitor With Audio

- ◆ Perfect for any portable or fixed audio/video monitoring application
- ◆ True high resolution display: 224,640 dots
- ◆ Durable plastic housing with tilting display
- ◆ Stereo sound with built-in speakers and headphone jack
- ◆ Over 60% more viewing area than a 4" screen
- ◆ Controls for power, volume, tint, brightness and color
- ◆ Video inversion switch for roof mount applications



#205-060 ..... Suggested Resale \$299<sup>95</sup> EACH Regularly \$219<sup>90</sup> EACH

Introductory Price \$199<sup>95</sup> EACH

LARGEST SELECTION OF SPEAKER DRIVERS IN THE COUNTRY!

Visit Us On The Web At  
www.partsexpress.com  
Or Call Toll Free  
1-800-338-0531

725 Pleasant Valley Dr., Springboro, OH 45066-1158 KEY CODE: POM  
Phone: 513-743-3000 ♦ FAX: 513-743-1677 ♦ E-Mail: sales@partsexpress.com

# EARN MORE MONEY!

## Be an FCC LICENSED ELECTRONIC TECHNICIAN!



No costly school. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radiotelephone License." This valuable license is your professional "ticket" to thousands of exciting jobs in Communications, Radar, Radio-TV, Microwave, Maritime, Avionics and more...even start your own business! You don't need a college degree to qualify, but you do need an FCC License.

**No Need to Quit Your Job or Go To School**  
This proven course is easy, fast and low cost! GUARANTEED PASS-You get your FCC License or money refunded. **Send for FREE facts now.**

**Call 1-800-932-4268 Ext. 210**

**Fax 1-415-332-1901**

**Email: [fcc@commandproductions.com](mailto:fcc@commandproductions.com)**

**Visit our Website: [www.LicenseTraining.com](http://www.LicenseTraining.com)**

### COMMAND PRODUCTIONS

FCC LICENSE TRAINING - Dept. 210  
P.O. Box 2824 San Francisco, CA 94126-2824

**Please rush FREE details immediately!**

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_

**Mail This Coupon Today!**

CIRCLE 231 ON FREE INFORMATION CARD

# PIC'n Books

LEARN ABOUT PIC MICROCONTROLLERS



See Table Of Contents: <http://www.sq-1.com>  
Secure Online Ordering Is Available

PIC is a trademark of Microchip Technology Inc.

**SQUARE 1 ELECTRONICS**

Voice (707) 279-8881 Fax (707) 279-8883

<http://www.sq-1.com>

# Fort777.com

The best in electronics anywhere in the galaxy

Here's a tiny sample of the things you'll find at  
[www.fort777.com](http://www.fort777.com)

#### Resistors 1/4W

High quality metal-film.  
Only 9¢ for pack of 10.  
Also 0.6W to 10W available.

#### Capacitors

Ceramic 0.1µF 16V.  
Only 25¢ for pack of 5.  
100's of other types in stock.

White LEDs T-1 and T-1¼  
Only \$2.99 each.

Red, Green, Yellow, Blue  
and super bright available.

#### Diodes & Rectifiers

1N4001 thru 7, 1N914,  
1N4148 all these types:  
Only 25¢ for pack of 10.

#### Connectors

RCA Plug only 15¢ each.  
1/8" Plug mono 35¢ each.  
1/8" Plug stereo 59¢ each.  
1/4" Plug mono 49¢ each.  
BNC Crimp Plug 35¢ each.

#### Computer Accessories

Fully shielded printer cable  
6 feet. Only \$1.99.

#### Motorcycle Intercom

Talk to your passenger in  
comfort. Only \$19.99.

#### Rechargeable Flashlight

Plugs directly to power. Auto  
on if power fails. Night light.  
Only \$11.99.

#### Auto-tuning FM Radio

Super mini, weatherproof,  
twin earphones. Only \$7.99.

#### Audio Patch Cables

Twin RCA-type 3ft 79¢.  
+ gold-plated contacts \$1.19.  
+ gold-plated plugs \$4.99.  
Many other types in stock.

#### TV Flylead

Low-loss RG6 cable, gold-  
plated F male plugs screw-  
on or push-on 3ft \$1.49.

Contact us: [sales@fort777.com](mailto:sales@fort777.com)

Items shown here and on the website [www.fort777.com](http://www.fort777.com) are only available by mail from the website. The address below is for returns and servicing.

Fort777.com North American Service Agents, Frontier Engineering, 628 S. Sunset St., Longmont, CO 80501

DVD Movies  
DVD Music

Weekly  
Specials

Home  
Theater

**BigBang**  
electronics

Auctions

# THE SIGN OF INTELLIGENT LIFE IN THE UNIVERSE ...

Big Bang offers top-quality name-brand electronic equipment and home theater components for lower prices than anywhere else in the galaxy. Make contact Toll Free: 1-888-314-2620 or [www.bigbangelectronics.com](http://www.bigbangelectronics.com).



## TACTILE SOUND

**DON'T JUST WATCH THE MOVIE - FEEL THE MOVIE.**

Tactile Sound is sound you feel. It's the exhilarating rumble of F-16 afterburners, the gentle pluck of a guitar...it's every action and special effect built in to the movie's soundtrack. Now you can experience your favorite movies with your entire body.



**Pioneer • Dennon • MB Quart • Philips • Pioneer • Dennon • MB Quart • Ph**




Rewritable CD Rom

Pronto Intelligent/Universal Remote controls unlimited number of components



PC Camera

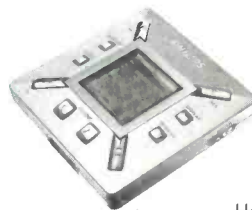
MP3 Player records up to 80 hours of music



HandsFree Cell Phone Holder/Charger
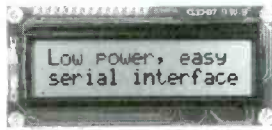
# SERIAL LCDs

Serial LCDs work great with BASIC Stamps® and other microcontrollers. One-wire interface • simple serial protocol • low cost • high quality • in stock



**BPI-216N**  
 • 2x16 text LCD  
 • 2400/9600 bps  
 • \$45 (non-backlit)

**SGX-120L**  
 • Mini graphics LCD  
 • 2400/9600 bps  
 • just \$99



Many other models available—see [www.seetron.com/](http://www.seetron.com/)

Scott Edwards Electronics, Inc.  
[www.seetron.com](http://www.seetron.com) • 520-459-4802



SUPPORTS DEVICES TO 32 MEG

## EPROM+

A device programming system for design, repair and experimentation  
 ♦ EXCEPTIONAL POWER FOR THE PRO  
 ♦ EASY-TO-USE FOR THE NOVICE  
 ♦ INCLUDES STEP-BY-STEP TUTORIAL

**Here's what you get:** A rugged, portable programming unit including the power pack and printer port cable both of which store inside the case. A real printed user and technical manual which includes schematic diagrams for the programming unit plus diagrams for all technology family adapters. \* Comprehensive, easy-to-use software which is specially designed to run under DOS, Windows 3.1, 95 and 98 on any speed machine. The software has features which let you READ, PROGRAM, COPY and COMPARE plus much more. You have full access to your system's disk including LOADING and SAVING chip data plus automatic processing of INTEL HEX, MOTOROLA S-RECORD and BINARY files. For detailed work the system software provides a full screen buffer editor including a comprehensive bit and byte tool kit with more than 20 functions.

**Broad device support:** FIRST GENERATION EPROMS (2708, 1MS2716\*, 25XX) SECOND GENERATION EPROMS (2716-28C080), 40 AND 42 PIN EPROMS\* (27C1024-27C160) FLASH EPROMS (28F, 29C, 29EE, 29F), EEPROMS (2816-28C010), NVRAMS (12XX, X2210/12) 8 PIN SERIAL EEPROMS\* (24, 25, 85, 93, 95, 8001(A) PLUS ER1400/MS8657\* AND ER5901 BIPOLAR PROMS\* (72S/82S), FPGA CONFIGURATORS (17CXXX) MICROCONTROLLERS\* (874X, 875X, 87C5XX, 87C75X, 89C5X) ATMEL MICROS\* (8-40) PIN 89C051, 89SXXX (AVR) 90SXXX PIC MICROS\* 8, 18, 28, 40 PIN (12CXXX-16CXXX, 16FX, 17C) MOTOROLA MICROS\* (68705P3U3/R3, 68HC705, 68HC711)

**\$289**

\*REQUIRES SNAP-IN ADAPTER (ORDER FACTORY DIRECT OR BUILD YOURSELF) \$5.00 SHIPPING • \$5.00 C.O.D. 1 YEAR WARRANTY - 30 DAY MONEY BACK GUARANTEE VISA • MASTERCARD • AMEX  
**ANDROMEDA RESEARCH, P.O. BOX 222, MILFORD, OH 45150**  
 (513) 831-9708 FAX (513) 831-7562 website - [www.arlabs.com](http://www.arlabs.com)

# LASERS

AT GREAT PRICES

Complete Ruby Laser Assembly less than \$300  
 He-Ne Lasers, complete, for less than \$50  
 American 60X Argon Lasers from \$595  
 Laser Diode Modules from under \$40  
 X-Y Scanners from \$79

## FREE CATALOG

- Helium-Neon
- Argon Lasers
- Diode Lasers
- Holography
- Books
- Ruby Lasers
- Scanners
- Lightshow Equipment
- Pointers
- Optics

Email: [mlp@nlenx.com](mailto:mlp@nlenx.com) <http://www.midwest-laser.com>



**Midwest Laser Products**

P.O. Box 262, Frankfort, IL 60423

Phone: (815) 464-0085 FAX: (815) 464-0767


30 Day Satisfaction Guarantee.

VISA / MC Accepted


## Future Horizons Advanced Technology

Po Box 125 Marquette, MI 49855 [www.futurehorizons.net](http://www.futurehorizons.net)


### Traffic Light Buster

 This device will turn traffic lights green in many cities by the touch of a button. Emergency vehicles use this to pass through traffic lights quickly. Can be dash mounted or handheld.  
**TLBU Plans-\$15.00**  
**TLBZ Ready to Use-\$250.00**

### Ambient Power Module

 Low cost circuit provides up to 9 watts of electrical power from free-energy in the air. Can replace batteries in many devices.  
**PWRM Plans-\$20.00**  
**PWRZ Ready to use-\$97.00**

### Ionocraft


 Proven electrical phenomemn produces anti gravity levitation of small craft. Solid State, no moving parts, easily scaled up. Larger craft can exceed lifting efficiency of modern helicopters. Uses HIDZ pwr supply.  
**IONO plans-\$20.00**  
**HIDZ Power supply-\$225.00**




**Lightsaber**  
 Produces brilliant blade of glowing humming light 36" long by the flick of a switch. Virtually identical to those seen in the movies

but this one is REAL. Completely safe. (available in red, green, blue)  
**LIGH Plans-\$20.00**  
**LIGZ 24" Lightsaber-\$140.00**  
**LIGZ-36 36" Lightsaber-\$160.00**

### Cordless Phone Extender

 Learn to extend your cordless phone range to 50 miles. Place calls all around town. Great alternative to cell phones.  
**CPHE Plans-\$20.00**


### Electronic Mind Control

 Control minds with this simple technology. Others will do anything you program them to. Get that raise you always wanted or reprogram your mind.  
**MIND Plans-\$15.00**  
**MINZ Ready to use-\$124.00**

Please add \$5.00 Shipping/Handling, Overseas \$11.00

(906)249-5197 24 hr order only line (906)249-1525 Fax  
 Pay by Visa, MC, Amex, Disc, Chk, Mo, Cash Send \$3 for catalog


# Learn to Hack!

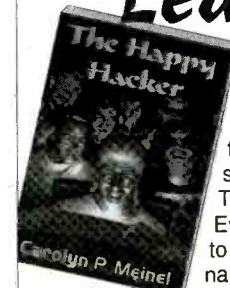

**The Happy Hacker** is nothing less than a step-by-step, easy to follow course on computer hacking. In it you'll learn all the ins and outs of hacking like the pros. You'll also learn how to hack safely, without getting busted or fired. This brand new 3rd edition has it all! Everything from breaking in to computers to hacking web sites, forging email - you name it!

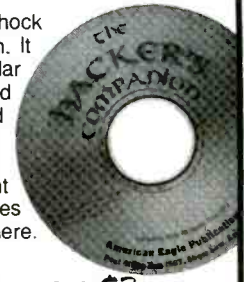**432 PAGE PAPERBACK, \$34.95 SHIPPING \$3**

The Hacker's Companion CD-ROM is chock full of hacking software and information. It includes everything from phones, cellular and satellite hacking to password crackers, war dialers, sniffers and exploit programs. Even a video of dutch hackers breaking into a classified US military computer. An excellent companion to the Happy Hacker, includes many of the programs discussed there. Brand new for the year 2000!



**PC CD-ROM, \$29.95, SHIPPING \$3**

Or call or write for **FREE CATALOG** of hard-to-get information about *computer viruses, computer hacking, security and cryptography*!! Check our web site [www.ameaglepubs.com](http://www.ameaglepubs.com) for lots more about these books and CD's!

**American Eagle Publications, Inc.**  
**P. O. Box 1507, Dept E.**  
**Show Low, AZ 85902**  
**(800)719-4957**

CIRCLE 315 ON FREE INFORMATION CARD

# CEBEK

ELECTRONIC CIRCUITS

TO RECEIVE SALE PRICING,  
You Must Provide This

Source code: **POP76A**

## PRE-ASSEMBLED CIRCUIT MODULES

Prices effective May 23 through October 27, 2000.

Perfect for hobbies, repair, prototype,  
OEM and equipment modification  
Low cost, high quality boards are fully  
assembled and 100% tested at the factory  
Each includes full specifications  
and application information  
These and over 100 additional modules  
stocked exclusively at MCM Electronics  
Complete information at [www.cebek.com](http://www.cebek.com)

### FM Transmitters

- Accepts mic level input
- Transmits from 88-108MHz
- Requires single 9-15VDC supply

Description	Order #	Mfr. #	Reg.	Sale
FM transmitter	28-4850	FM-1	<del>\$14.95</del>	<b>\$10.90</b>
High power FM transmitter	28-4851	FM-2	24.95	<b>22.39</b>
Pre-amplifier with compression	28-6230	PM-9	<del>12.80</del>	<b>10.20</b>

### Digital Message Recorder

- Records any audio signal
- Retains information with power removed
- Includes an electret microphone
- TR-4 and TR-6 have on-board SW amplifiers

Description	Order #	Mfr. #	Reg.	Sale
16 second	28-4855	TR-1	<del>\$34.95</del>	<b>\$28.99</b>
16 second with repeat	28-7854	TR-3	39.95	<b>35.90</b>
16 second with repeat	28-7856	TR-4	<del>52.80</del>	<b>47.20</b>
60 second with repeat	28-6245	TR-6	<del>87.95</del>	<b>79.00</b>

Check

**OUT**

full line catalog at:

1-800-543-4330

[www.mcmelectronics.com](http://www.mcmelectronics.com)

Free Literature

fax: 1-800-765-6960



MCM ELECTRONICS  
650 CONGRESS PARK DR  
CENTERTOWN, OH 45459



### Counters

- Up/down count
- LED display
- Contact closure count and reset input
- Requires single 12VDC supply

Order #	Mfr. #	Description	Reg.	Sale
28-5150	CD-3	Three digit	<del>\$39.95</del>	<b>\$35.50</b>
28-5155	CD-5	Three Digit w/relay output	<del>64.95</del>	<b>58.00</b>
28-4785	CD-9	Two digit	14.95	<b>11.55</b>

### DC Power Supplies

- Includes AC transformer
- Provides tight voltage regulation
- Short circuit protected

Order #	Mfr. #	Output	Reg.	Sale
28-4772	FE-2	12VDC, 300mA	<del>\$14.95</del>	<b>\$11.85</b>
28-4775	FE-4	12VDC, 1A	19.95	<b>16.70</b>
28-4776	FE-7	24VDC, 1A	<del>24.95</del>	<b>20.65</b>
28-4777	FE-11	12VDC, 2A	<del>34.95</del>	<b>29.95</b>
28-4778	FE-13	12VDC, 5A	<del>49.95</del>	<b>44.50</b>

### Audio Pre-Amplifiers

- Use with Cebek or any amplifier with line level input
- Operates from a single 6-18VDC supply
- Gain adjusted via board-mounted potentiometer

Description	Order #	Mfr. #	Reg.	Sale
Microphone preamp, HI-Z	28-7962	PM-1	<del>8.99</del>	<b>\$6.90</b>
Microphone preamp, Low-Z	28-4805	PM-2	8.95	<b>6.50</b>
Preamp for general use	28-7960	PM-4	<del>8.99</del>	<b>7.09</b>
Electric guitar preamp	28-4815	PM-7	8.95	<b>6.49</b>
Voice activation "VOX" relay	28-4825	PM-11	<del>17.95</del>	<b>13.15</b>

### Timer Modules

- Operates from a single 12VDC supply
- Provides precise time delay for a variety of uses
- SPDT, 5A relay output

Description	Order #	Mfr. #	Reg.	Sale
Single event 1-180 second	28-4735	I-1	<del>\$17.95</del>	<b>\$12.45</b>
Single event 2-45 minute	28-4736	I-2	17.95	<b>12.45</b>
Single event 30-240 minute	28-4737	I-3	<del>18.49</del>	<b>13.85</b>
Repeat cycle 0.3-60 second	28-4740	I-10	18.49	<b>13.85</b>
Repeat cycle 1-30 minute	28-4741	I-11	<del>19.95</del>	<b>17.75</b>
Repeat cycle 20-150 minute	28-4742	I-12	18.95	<b>15.85</b>

### Audio Amplifiers

- Perfect for repair and equipment modification
- Operates from a single 12VDC supply
- Accepts line level input

Description	Order #	Mfr. #	Reg.	Sale
0.5W single channel	28-5165	E-13	<del>\$7.49</del>	<b>\$5.60</b>
1W single channel	28-4795	E-1	7.49	<b>5.60</b>
1W two channel	28-5170	ES-1	<del>14.95</del>	<b>11.25</b>
5W single channel	28-4796	E-2	13.95	<b>10.99</b>
5W two channel	28-4800	ES-2	<del>24.95</del>	<b>20.85</b>
15W single channel	28-4797	E-4	19.95	<b>17.20</b>
15W two channel	28-4801	ES-4	<del>39.95</del>	<b>35.60</b>

### Programmable LCD Displays

- Provides one or two line x 16 character display
- Fully programmable with easy menu programming
- Stores up to 14 alpha numeric messages
- EC-3 and EC-4 are backlit

Order #	Mfr. #	Description	Reg.	Sale
28-6135	EC-1	Single line	<del>\$89.95</del>	<b>\$79.95</b>
28-6140	EC-2	Two line	<del>99.95</del>	<b>89.95</b>
28-4765	EC-3	Single line	<del>115.00</del>	<b>103.50</b>
28-4766	EC-4	Two line	<del>140.00</del>	<b>126.00</b>

mcm **Electronics** mcm  
What you want... Today!

SOURCE CODE: POP76A

A Premier Farnell Company

CIRCLE 160 ON FREE INFORMATION CARD


[www.americanradiohistory.com](http://www.americanradiohistory.com)

# Any waveform you want!



- New Features:**
- ✓ 21.5 MHz
  - ✓ .01 Hz steps
  - ✓ multi-unit phaselock

Telulex Inc. model SG-100A

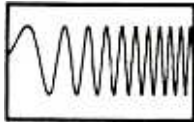


DC to 21.5 MHz linear and log sweeps




Int/Ext AM, SSB, Dualtone Gen.




Int/Ext FM, PM, BPSK, Burst

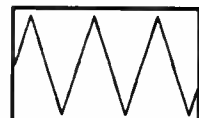


Ramps, Triangles, Exponentials

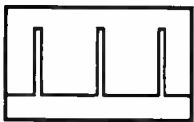


Pulse Generator

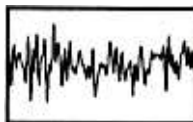

Noise

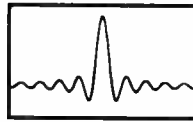

Arbitrary Waveforms

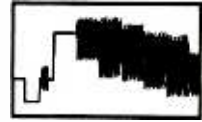

Unlimited Possibilities!

- **Synthesized Signal Generator**  
Clean sinewaves DC-21.5 MHz, .001% accuracy! .01 Hz steps. DC Offset. RS232 remote control.
- **Arbitrary Waveform Generator**  
40 Megasamples/Second. 32,768 points. 12 bit DAC
- **Function Generator**  
Ramps, Triangles, Exponentials & more to 2 MHz!
- **Pulse Generator**  
Digital waveforms with adjustable duty cycle

**Telulex Inc.**

2455 Old Middlefield Way S Tel (650) 938-0240 <http://www.Telulex.com>

Mountain View, CA 94043 Fax (650) 938-0241 Email: sales@Telulex.com

CIRCLE 311 ON FREE INFORMATION CARD


(800)366-0579

(661)295-5577

fax(661)295-8777
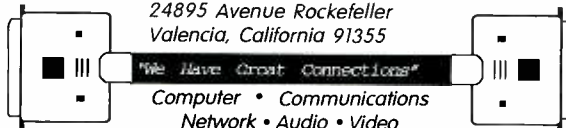
## Roger's Systems Specialist

24895 Avenue Rockefeller  
Valencia, California 91355



### ELECTRONIC CPU SWITCH

- Includes:
- One MiniView KVM switch
  - 2 Sets of Premium Grade KVM Cables
  - One PS/2 to AT keyboard adapter
  - One PS/2 to Serial mouse adapter
  - One User Guide
- Features:
- Keyboard & mouse emulation for error
  - Free PC booting
  - No external power required
  - Works virtually with any operating system
  - Fully hot pluggable

DS-102-KMMPS

- ADAPTORS
- HUBS
- SWITCH BOXES
- PATCH PANELS
- SCSI CABLES
- MOTHERBOARDS
- CPU'S

Case fan system exhaust  
4pin  
**\$12<sup>00</sup>**  
cat.no. TM-FAN-SLOT



**\$99<sup>00</sup>**

**Acer**  
**\$5<sup>00</sup>**  
cat.no. TM-290-PS

SVGA COAXIAL CABLES

### EXTENSIONS, male to female

CC-VGA-4C	6FT	\$6 <sup>00</sup>
CC-VGA-5C	10FT	\$8 <sup>00</sup>
CC-VGA-25CX	25FT	\$16 <sup>00</sup>
CC-VGA-50CX	50FT	\$28 <sup>00</sup>
CC-VGA-100CX	100FT	\$44 <sup>00</sup>

### SWITCH BOX, male to male

CC-VGA-3C	6FT	\$6 <sup>00</sup>
CC-VGA-9C	10FT	\$8 <sup>00</sup>
CC-VGA-11C	25FT	\$16 <sup>00</sup>
CC-VGA50MM	50FT	\$28 <sup>00</sup>
CC-VGA100CX	100FT	\$44 <sup>00</sup>



### Category 5 Patch Cable

TE-038-1.5	3ft. Straight Patch	\$1 <sup>75</sup>
TE-068-1.5	7ft. Straight Patch	\$2 <sup>00</sup>
TE-128-1.5	14ft. Straight Patch	\$4 <sup>00</sup>
TE-258-1.5	25ft. Straight Patch	\$5 <sup>90</sup>
TE-358-1.5	35ft. Straight Patch	\$7 <sup>90</sup>
TE-508-1.5	50ft. Straight Patch	\$8 <sup>90</sup>
TE-758-1.5	75ft. Straight Patch	\$17 <sup>90</sup>
TE-108-1.5	100ft. Straight Patch	\$16 <sup>90</sup>

CIRCLE 308 ON FREE INFORMATION CARD



# CREDIT CARD COMPUTER

**\$14.20** OEM (1000 pc.) price  
**EVAL KIT (Qty 1) \$50**


Includes:

- serial and parallel
- ISA/PC104 bus
- 256kbit nvmem
- BASIC and ASSY
- A to D converter
- Calendar/Clock

NEW, improved version with ...

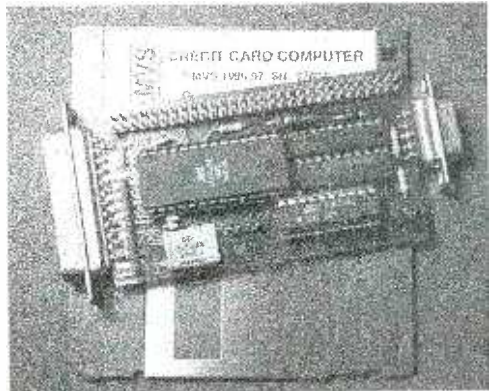**PLUG-N-GO™ !!!**

COMPLETE! No cables or power supply to buy.



## \$95 UNIVERSAL PROGRAMMER



FLASH, EPROM, NVRAM, EEPROM to 8meg (27080). Adapters for micros, PLCC, etc.. Parallel port version for notebooks. FAST and EASY TO USE.

## PC SOLID STATE DISK



\$21 OEM (1k), EVAL \$75  
 FLASH, NVRAM, ROM  
 256K-16M DIP/PCMCIA

## LCD VGA \$27



OEM (1k), eval \$95  
 640x480 controller  
 use with PC or SBC

## PC WATCHDOG!


NO MORE HANGUPS..  
 Reboots PC on hardware  
 or software hangup..  
 oem \$21, eval \$75



## ADC/DAC cards

8/12/16/18bit up to 32 channel for  
 PC or SBC starting at \$14.20 oem

## \$27 MINI PC

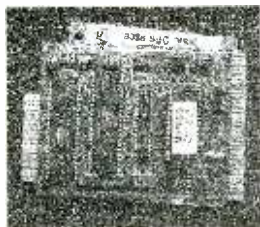

eval \$95, oem \$27 includes:  
 DOS, 3 ser, 2 par, rtc, nvmem,  
 built-in LED display, ISA bus,  
 Keyboard and LCD interface  
**COMPLETE!**  
 Not a "core" or "engine". All  
 utilities and tutorial included.  
 Use Turbo C, Basic, MASM.  
 386 version \$42 oem \$195 eval

## SINGLE CHIP COMPUTER!

**\$1.99** OEM (1K)  
 EVAL KIT  
 (1) \$7.00

- Zero External Components
- Built-in BASIC / Assembly
- RS232 Program Download
- 1K flash, 64ee, 3irq, 2timers
- 15 I/O bits, A/D comparator
- 20mips, faster than pic/8051
- 20 pin DIP part #MV1200



## NEW! 8K SUPER CHIP

Improved BTERP with 40 times the BASIC program capacity  
 - 40 pin DIP part #MV8515 - 32 I/O, 12 irq, 3 timers, bus  
 - 8K flash, 512 ee, 512 nvram - Watchdog with internal osc.  
**\$5.40 OEM (1k), Eval Kit \$19.00**

[WWW.STAR.NET/PEOPLE/~MVS](http://WWW.STAR.NET/PEOPLE/~MVS)

MVS Box 850  
 Merr., NH 03054  
 (508) 792 9507



5yr Limited Warranty  
 Free Shipping  
 Mon-Fri 10-6 EST

**CALL TOLL FREE**  
**(800) 292-7711**  
**Orders Only**

Se Habla Español

# C&S Sales

**Excellence in Service**

**Look For Other**  
**Monthly Specials**  
**On Our Website**

[www.cs-sales.com](http://www.cs-sales.com)

## D/A Trainer

Elenco Model XK-150

**\$89.95**



A low cost, full-function digital/analog trainer that meets the needs of electronic training programs. Rugged construction, can be used as fixed lab equipment or be portable. An economical zipper case is available.

## Soldering Stations

Weller Low Cost Soldering Iron Model WLC-100

**\$34.95**



- Variable power control produces 5-40 watts
- Ideal for hobbyists, DIYers and students.
- Complete with 40W iron.

Weller Soldering Station Model WES50

**\$119**

50 watts of controlled power - designed for continuous production soldering.



## Deluxe Electronic Soldering Station

Elenco SL-5 Series

Electronically controlled, ideal for professionals, students, and hobbyists. Available in kit form or assembled.

Works w/ any iron! Turn any soldering iron into a variable iron.

As Low As  
**\$29.95**

Ordering Information:

- |  |                |
|--|----------------|
| Model SL-5 - No Iron. (Kit SL-5K)                    | <b>\$29.95</b> |
| Model SL-5-40 - Includes 40W UL Iron. (Kit SL-5K-40) | <b>\$35.95</b> |
| Model SL-5-60 - Includes 60W UL Iron. (Kit SL-5K-60) | <b>\$36.95</b> |
- \*\*\* Limited Time Offer \*\*\*  
 FREE SP-1A Solder Practice Kit w/ Kit Order



Features:

- Cushion Grip Handle Soldering Iron (optional) with Grounded Tip for Soldering Static-Sensitive Devices. Easily Replacable. Uses Long-Life, Plated Conical Tip.
- Heavy Steel, Non-Slip Base.
- Iron Holder Funnel - Reversible, left or right side.
- Steel Tray for Sponge Pad.
- Sponge Pad.

## Generators & Counters

B&K 20MHz Sweep/Function Generator with Frequency Counter Model 4040

**\$445**

- 0.2Hz to 20MHz
- AM & FM modulation
- Burst Operation
- External Frequency counter to 30MHz
- Linear and Log sweep

- |                    |        |
|--------------------|--------|
| 21.5MHz Model 4070 | \$1295 |
| 10MHz Model 4017   | \$319  |
| 5MHz Model 4011    | \$249  |

**BK PRECISION**



Four Functions in One Elenco Model MX-9300B

**\$450**

Features:

- One instrument with four test and measuring systems:
- 1.3GHz Frequency Counter
- 2MHz Sweep Function Generator
- Digital Multimeter
- Digital Triple Power Supply - 0-3V @ 2A, 5V @ 2A, 15V @ 1A



Elenco Handheld Universal Counter 1MHz - 2.8GHz Model F-2800

**\$99**



Features 10 digit display, 16 segment and RF signal strength bargraph. Includes antenna, NiCad battery, and AC adapter. C-2800 Case with Belt Clip \$14.95

Elenco RF Generator with Counter (100kHz - 150kHz) Model SG-9500

**\$225**

Features internal AM mod. of 1kHz. RF output 100mV - 35MHz. Audio output 1kHz @ 1V RMS.



SG-9000 ..... \$119.95 (analog, w/o counter)

Elenco Sweep Function Generator w/ built-in frequency counter Model GF-8046

**\$195.95**

This sweep function generator with counter is an instrument capable of generating square, triangle, and sine waveforms, and TTL, CMOS pulse over a frequency range from 0.2Hz to 2MHz.



GF-8025 - Without Counter \$139.95

## Kit Corner

over 100 kits available

Quantity Discounts Available

Model RCC-7K

Radio Control Car Kit

**\$29.95**

- Fun & Easy to Assemble
- 7 Functions
- Radio Control Transmitter included
- Also available as Model AK-870 (No Soldering) \$24.95



Model AK-700

Pulse/Tone Telephone Kit

**\$15.95**



Ideal School Project

Action Lab Kit Model MX-902

- Safe, Solderless, Educational, and Fun!
- Easy-to-read, Illustrated, Lab-Style Manual included.
- Requires 2 "AA" Batteries
- Build your own operating motor - It's easy, it's fun, it's Safe!
- For Ages 10 and up.

**\$24.95**



Model AM-780K

Two IC Radio Kit

**\$11.95**

Also available: Model AM/FM-108K AM/FM Radio Kit \$29.95



Model OWI-007

Robotic Arm (Wired Control)

Teaches the basic robotic sensing and locomotion principles while testing motor skills.

**\$55.95**



300-in-1

Experiment Kit Model MX-908

**\$54.95**

- Everything you need to build 300 exciting electronic projects!
- Easy-to-read, Illustrated, Lab-Style Manual included.
- Requires 6 "AA" Batteries
- For Ages 10 and up.



**Guaranteed Lowest Prices**

UPS SHIPPING: 48 STATES 5%  
 OTHERS CALL FOR DETAILS  
 IL Residents add 8.25% Sales Tax

**C&S SALES, INC.**

150 W. CARPENTER AVENUE  
 WHEELING, IL 60090  
 FAX: (847) 541-9904 (847) 541-0710

**15 DAY MONEY BACK GUARANTEE**  
**2 YEAR FACTORY WARRANTY**



PRICES SUBJECT TO CHANGE WITHOUT NOTICE

CIRCLE 290 ON FREE INFORMATION CARD

**SAME DAY SHIPPING**  
Secure on-line ordering

# C&S Sales


Excellence in Service

CALL OR WRITE FOR OUR FREE

64 PAGE CATALOG!  
(800) 445-3201

## Elenco Oscilloscopes

Free Dust Cover and 2 Probes

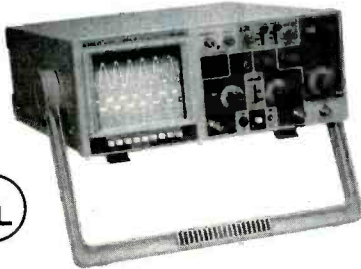

S-1325	25MHz	Dual Trace	\$325
S-1330	25MHz	Delayed Sweep	\$439
S-1340	40MHz	Dual Trace	\$475
S-1345	40MHz	Delayed Sweep	\$569
S-1360	60MHz	Delayed Sweep	\$725
S-1390	100MHz	Delayed Sweep	\$895

### DIGITAL SCOPE SUPER SPECIALS

DS-203	20MHz/10Ms/s	Analog/Digital	\$695
DS-303	40MHz/20Ms/s	Analog/Digital	\$850
DS-603	60MHz/20Ms/s	Analog/Digital	\$950

## Digital Multimeters

### Fluke 87III



**\$319**

Features high performance AC/DC voltage and current measurement, frequency, duty cycle, resistance, conductance, and capacitance measurement.

### Elenco LCR & DMM Model LCM-1950



**\$69**

- Large 1", 3 3/4 digit LCD
- Autorange frequency to 4MHz
- Capacitance to 400µF
- Inductance to 40H
- Resistance to 4000MΩ
- Logic Test
- Diode & Transistor Test
- Audible Continuity Test

### Elenco Model M-1740



**\$34.95**

- 11 Functions
  - Freq. to 20MHz
  - Cap. to 20µF
  - AC/DC Voltage
  - AC/DC Current
  - Buzzer
  - Diode Test
  - Transistor Test
  - Meets UL-124 safety specs.
- Model M-2760 - \$19.95 (9 functions)**

### Dual-Display LCR Meter w/ Stat Functions B&K Model 878



**\$225**

Auto/manual range  
Many features with Q factor  
High Accuracy

### Elenco LCR Meter Model LCR-1810



**\$99.95**

- Capacitance: 1pF to 20F
- Inductance: 1µH to 20H
- Resistance: 01Ω to 2000MΩ
- Temperature to 75°C
- DC Volts 0 - 20V
- Frequency up to 15MHz
- Diode/Audible Continuity Test
- Signal Output Function
- 3 1/2 Digit Display

### Elenco DMM Kit Model M-1005K



**\$19.95**

- 18 Ranges
  - 3 1/2 Digit LCD
  - Transistor Test
  - Diode Test
  - Training Course
- M-1000B (Assembled) \$15.95**

**Quantity Discounts Available**

## B&K Testers

### Deluxe Multi-Network Cable Tester Model 231

**\$75**

- Tests 10BaseT, 100BaseTx, 10Base2, RJ45, RJ11, 356A, TIA-568A, TIA-568B, and Token Ring cables.
- Detects open, short, cross, and continuity.
- Tests Point-to-Point, rather than Pair-to-Pair
- Quick and easy-to-use.
- Tests cables on wall plate or patch panel up to 1,000 ft. away with the remote kit.
- Easy-to-read LED display.



### Multi-Network Cable Tester Model 230

**\$69**

- Auto scans thin Ethernet (BNC), 10BaseT (UTP/STP), 100BaseTx, RJ45, 356A, TIA-568A, TIA-568B, and Token Ring cables in seconds.
- Detects miswiring, polarization, and continuity.
- Also tests the ground of shielded twisted pair cables.
- Tests cables before or after installation with the remote unit.
- LED display for clear indication of problems.



### Remote Network Cable Tester Model 235

**\$195**

- Detects open, short, reversed, crossed, and split.
- Clear LED display for the fault status.
- Simple and easy-to-use.
- Test cable length: Minimum - 4 ft. (1.2m) Maximum - 492 ft. (150m).
- Identify up to 4 different cables at one end by provided remote identifiers.
- Tests: 10BaseT, 100BaseTx, 10Base2 (coax), RJ45, 356A, TIA-568A, TIA-568B, Token Ring, etc.



## CCTV Cameras

Cameras have 420 lines (360 color) of resolution, 0.08 Lux, 3.6mm/F2 90° field of view. Power requirement is 12VDC @ 100mA (order SC-1).

### MONOCHROME CAMERAS



SC-12 - 35mm Lens (1.25"x1.25") **\$69**  
SC-15 - Pin Lens (1.25"x1.25") **\$69**

Add \$10 for lens + Add \$10 for audio

#### Accessories:

SC-1 - 12V 100mA adapter **\$6.95**  
SC-2 - 50' cable with connectors **\$19.95**

### COLOR CAMERAS



SC-20 Pin Lens  
SC-21 3.6mm Lens  
360 Lines 1.25" x 1.25"  
Infrared Sensitive, Audio Included  
**\$109**

Add \$10 for case  
Call for complete catalog.

## Power Supplies

### Elenco Quad Power Supply Model XP-581

**\$79.95**



4 Fully Regulated DC Power Supplies in 1 Unit  
4 DC voltages: 3 fixed - +5V @ 3A, +12V @ 1A, -12V @ 1A  
1 Variable - 2.5 - 20V @ 2A

### B&K High Current DC Power Supply

• Variable 3-14VDC  
• Thermal Function  
• Current Limiting

Model 1686 12A **\$169**  
Model 1688 28A **\$249**



B&K 13.8V Fixed DC Power Supplies  
Model 1680 6A **\$42**  
Model 1682 15A **\$75**

### Elenco Power Supply Kit Model XP-720K

**\$54.95**

- 1.5VDC - 15VDC @ 1A
- -1.5VDC - -15VDC
- 5VDC @ 3A
- 6.3VAC @ 1A & 12.6VAC center tapped @ 1A

XP-720 Fully Assembled **\$85**



### Elenco DC Power Supply Model SPL-603 3A 0-30VDC

**\$79.95**

The SPL-603 is a solid-state DC power supply providing the exact output voltage no matter what current you use. Output fully protected from overload.



**Guaranteed Lowest Prices**

**C&S SALES, INC.**

**15 DAY MONEY BACK GUARANTEE**  
**2 YEAR FACTORY WARRANTY**

UPS SHIPPING: 48 STATES 5%  
OTHERS CALL FOR DETAILS  
IL Residents add 8.25% Sales Tax

150 W. CARPENTER AVENUE

WHEELING, IL 60090

FAX: (847) 541-9904 (847) 541-0710


[www.cs-sales.com](http://www.cs-sales.com)



PRICES SUBJECT TO CHANGE WITHOUT NOTICE

# TiePieScope HS801 PORTABLE MOST

# Reliability

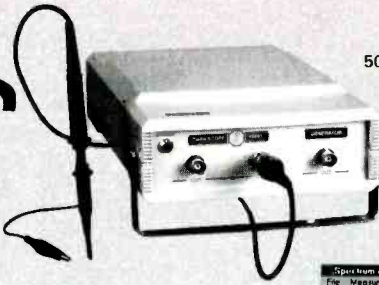


50 MHz ARBITRARY WAVEFORM GENERATOR-  
100 MHz STORAGE OSCILLOSCOPE-  
50 MHz SPECTRUM ANALYZER-  
6 DISPLAY MULTIMETER-  
200 DAYS TRANSIENT RECORDER-

The HS801: the first 100 Mega samples per second measuring instrument that consists of a MOST (Multimeter, Oscilloscope, Spectrum analyzer and Transient recorder) and an AWG (Arbitrary Waveform Generator). This new MOST portable and compact measuring instrument can solve almost every measurement problem. With the integrated AWG you can generate every signal you want.

A user defined toolbar with which over 50 instrument settings quick and easy can be accessed is offered by the versatile software. An intelligent auto setup allows the inexperienced user to perform measurements immediately. Through the use of a setting file, the user has the possibility to save an instrument setup and recall it at a later moment. The setup time of the instrument is hereby reduced to a minimum.

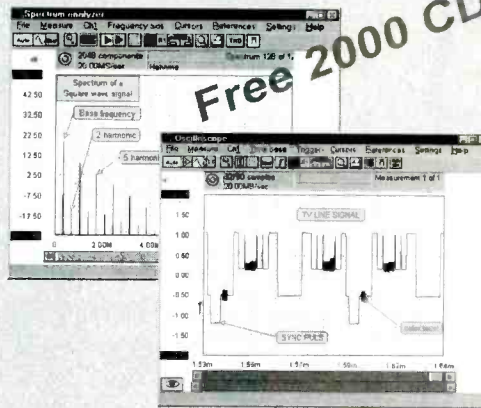Analyzing signals is done with an 8 bit resolution and a maximum sampling speed of 100 MHz. The input range is 0.1 Volt full scale to 80 Volt full scale. The record length is 32K/256K samples. The AWG has a 10 bit resolution and a sample speed of 25 MHz.



Convince yourself and download the demo software from our web page: [www.tiepie.nl](http://www.tiepie.nl). When you have questions and / or remarks, contact us via email: [support@tiepie.nl](mailto:support@tiepie.nl). The HS801 is delivered with a user manual, two probe's, Windows and DOS software.

US dealer:


**Feedback Incorporated:** Tel 800-526-8783;  
Fax 919-644-6470; [www.fb.com](http://www.fb.com)

Outside US:

**TiePie engineering,** P.O. BOX 290, 8600 AG SNEEK,  
The Netherlands.  
Tel: +31 515 415 416 Fax: +31 515 418 819  
Web: [www.tiepie.nl](http://www.tiepie.nl)

CIRCLE 217 ON FREE INFORMATION CARD

# MEMBRANE SWITCHES

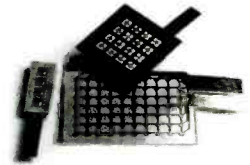

*Stock Layouts!*

*Eliminate tooling costs...*

**\*\*From 2 to 128 keys\*\***

**Optional Stainless Steel Tactile "Clickdomes".**

*Industry \* Hobbyist  
Production \* Prototyping*

Popular tactile types are available as complete *kits*, with bezel, connector & overlay!

4 key DTK-4 kit \$14.67  
12 key DTK-12 kit \$24.43  
many more layouts...

## Sil-Walker

(805) 491-0654

FAX (805) 491-2212

P.O. Box 3220

Camarillo, CA 93011-3220

[silwkr@vcnet.com](mailto:silwkr@vcnet.com)

[www.vcnet.com/silwkr/](http://www.vcnet.com/silwkr/)

MASTERCARD/VISA

ABC ELECTRONICS 315 7TH AVE N. MPLS. MN. 55401  
(612)332-2378 FAX (612)332-8481 E-MAILSURP1@VISI.COM  
WE BUY TEST EQUIPMENT AND COMPONENTS.  
VISIT US ON THE WEB AT WWW.ABCTEST.COM

HP 51501A 100MHZ DIGITIZING SCOPE	\$1300.00	HP 49355A TRANS IMPAIRMENT TEST SET	\$900.00
HP 54201D 300MHZ DIGITIZING SCOPE	\$1000.00	HP 5006A SIGNATURE ANALYZER	\$150.00
HP 54201A 300MHZ DIGITIZING SCOPE	\$1000.00	HP 86602B 1MHZ-1300MHZ RF PLUG	\$400.00
HP 51200A 50MHZ SCOPE WAVEFORM ANALYZER	\$700.00	HP 575 MICROWAVE COUNTER	\$1500.00
HP 3312A 13MHZ FUNCTION GENERATOR	\$250.00	FLUKE 95 50MHZ SCOPEMETER	\$550.00
HP 3379A 100MHZ TTL COUNTER	\$400.00	LECROY 7200 400MHZ O-SCOPE	\$1000.00
HP 3586C LEVEL METER	\$750.00	TEK 475 200MHZ O-SCOPE	\$500.00
HP 436A POWER METER W/O SENSOR & CABLE	\$500.00	TEK 465 100MHZ O-SCOPE	\$400.00
HP 8350B SWEEP OSCILLATOR MAINFRAME	\$2000.00	TEK 496P 1KHZ-1.8GHZ SPLIC ANALYZER	\$3500.00
HP 3437A 3.5DIGIT SYSTEM VOLTMETER	\$250.00	TEK 1240 LOGIC ANALYZER	\$750.00
HP 3455A DIGITAL MULTIMETER	\$250.00	TEK TDS320 100MHZ DIGITAL O-SCOPE	\$1400.00
HP 3456A DIGITAL MULTIMETER	\$400.00	TEK 11401A 500MHZ PROG O-SCOPE FRAME	\$750.00
HP 3330C SYNTHESIZER LEVEL GENERATOR	\$800.00	TEK 7854 400MHZ OSCILLOSCOPE FRAME	\$500.00
HP 5325A SYNTHESIZER FUNCTION GENERATOR	\$1000.00	TEK 7901 400MHZ OSCILLOSCOPE FRAME	\$250.00
HP 5345A 200MHZ COUNTER	\$600.00	TEK 7A26 200MHZ VERTICAL PLUG	\$75.00
HP 8165A PROGRAMMABLE SIGNAL SOURCE	\$1100.00	TEK 7A21 100MHZ VERTICAL PLUG	\$150.00
HP 8558B 181 100K-1500MHZ SPECTRUM ANALYZER	\$1000.00	TEK 7B80 400MHZ TIME BASE	\$75.00
HP 8559B 183 10MHZ-21GHZ SPECTRUM ANALYZER	\$3000.00	TEK 7B92A 500MHZ DUAL TIME BASE	\$125.00
HP 1700A 100MHZ OSCILLOSCOPE	\$250.00	TEK 7512 SAMPLING PLUG	\$250.00
HP 6034A 60VDC -10A POWER SUPPLY	\$750.00	TEK 7L11 10KHZ-1.8GHZ SPLIC ANALYZER	\$1000.00
HP 6209B 10VDC -50A POWER SUPPLY	\$800.00	TEK AM503 CURRENT PROBE AMPLIFIER	\$250.00
HP 6553A 40VDC-12.5A POWER SUPPLY OPT JOI	\$1200.00	WAVETEK 145 20MHZ PULSE FUNCTION GEN	\$400.00
HP 6652A 20VDC-5A POWER SUPPLY	\$500.00	WAVETEK 182A 4MHZ FUNCTION GEN	\$150.00
HP 6613A 45VDC-1.3A POWER SUPPLY OPT JOI	\$750.00	WAVETEK 955 7.5-12.1GHZ MICROSOURCE	\$1100.00

FOR 26 EASY  
WAYS TO HELP  
SAVE THE  
EARTH CALL  
1-800-488-8887.



A Public Service of  
The Ad Council



Earth Share

# Power Tools for Electronic Design Automation


**More Features  
More Power  
Less Money**

Ivex Spice is the latest addition in affordable EDA solutions. Use Ivex Spice with WinDraft Schematics for fast, professional results with un-surpassed ease.

Ivex 650 pin versions have no feature limitations like other low cost products on the market. Fast expert technical support, free 24 hour Knowledge Base on the web, and professional full-featured tools have made Ivex the preferred choice for designers.

For larger designs use these Ivex Products:

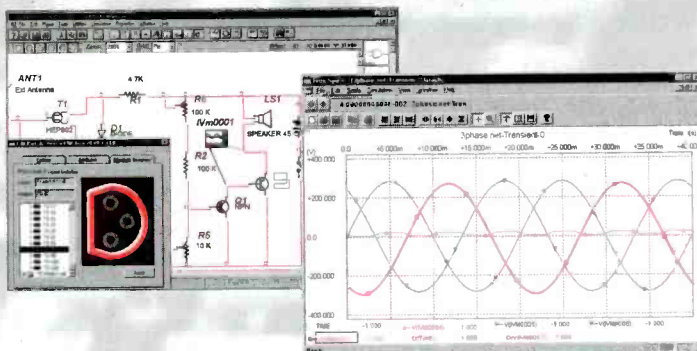WinDraft unlimited: \$495  
WinBoard unlimited: \$495  
Specetra autorouter  
    SP2-1000: \$650  
Ivex View unlimited \$ 99



**WinDraft<sup>®</sup>**  
Schematics **\$250**  
650 pin version

Full Featured 32 bit application  
Powerful hierarchical designs  
Easy single click editing  
Graphical part editor  
Windows functionality  
Advanced Bill of Materials  
User Definable Electrical Rules Check  
Common netlist formats:  
(Accel, Protel, Pads, wirelist, Spice 3f5, & more.)  
Import Orcad/SDT files/parts  
Visual PCB footprint browser  
Over 12,000 parts included

**WinBoard<sup>®</sup>**  
PCB Layout **\$250**  
650 pin version

Multi layer designs (16)  
Surface mount designs  
Advanced Design Rule Check  
Electrical DRC check and Real-Time DRC  
Single click editing  
Graphical part & pad editor  
Hundreds of footprints  
Copper zone pour  
Output Gerber photo plot files

**Ivex Spice/Standard<sup>™</sup>**  
Analog Simulation **\$99**

The Standard Edition includes:  
Multi channel display  
Over 3,000 models  
Uses Spice 3f5 netlist  
Use with WinDraft 3.05+

Seven Analysis types:  
Operating Point,  
DC Sweep, Transient Analysis,  
Fourier, AC Frequency Sweep,  
Small Signal Transfer,  
Sensitivity.

**Ivex Spice/Advanced<sup>™</sup>**  
Analog Simulation **\$299**

The Advanced Edition has all the features of the Standard Edition, with these additional analysis types:

Transient Parameter Sweep,  
AC Parameter Sweep,  
Distortion Analysis,  
Pole-Zero Analysis, Noise  
Analysis and Monte Carlo.

Visit the Ivex web site for complete product information and download full function demos.

**www.ivex.com**

Tel: (503) 531-3555 e-mail: safes@ivex.com

**IVEX<sup>™</sup>**  
DESIGN  
INTERNATIONAL


ADV5\_6

CIRCLE 309 ON FREE INFORMATION CARD
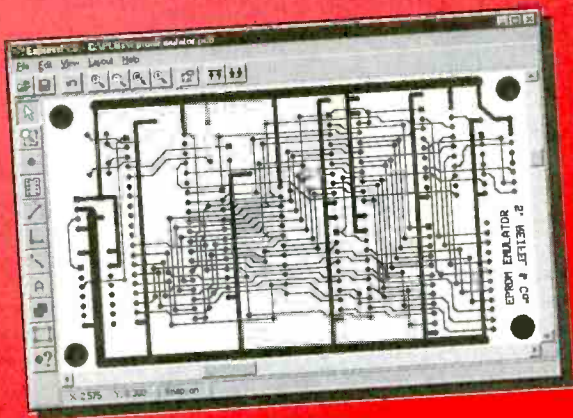
# PCB LAYOUT

Software For Windows - FREE

- 1 Download our board layout software
- 2 Design your 2 sided plated-through PCB
- 3 Send us your layout over the Internet
- 4 In 2-3 business days, UPS delivers your boards, often under \$100



[www.expresspcb.com](http://www.expresspcb.com)

## SECURETEK

DIRECT FROM MANUFACTURER

"WE WILL BEAT ANY COMPETITORS PRICE"

WORLD SMALLEST  
WIRELESS VIDEO CAMERA  
(BLACK & WHITE OR COLOR)  
TRANSMITS VIDEO UP TO 1000FT.

CAMERA SHOWN  
ACTUAL SIZE

WE ALSO CARRY:

- COVERT VIDEO CAMERAS
- COUNTER-SURVEILLANCE PRODUCTS
- CUSTOM MADE VIDEO SYSTEMS
- IN HOUSE ENGINEERING DEPT.

DISTRIBUTOR  
PROGRAM  
AVAILABLE



RUNS ON 9V BATTERY  
FOR UP TO 12 HRS.

CALL FOR CATALOG:

**SECURETEK**

7152 S.W. 47TH STREET  
MIAMI, FLORIDA 33137

TEL. 305.667.4545

FAX. 305.667.1744



[www.securetek.net](http://www.securetek.net)

# DIGITAL STORAGE OSCILLOSCOPES

WITH  
SPECTRUM  
ANALYZER,  
DVM, FREQ.  
COUNTER,  
AND DATA  
LOGGER.

from  
**\$189.**

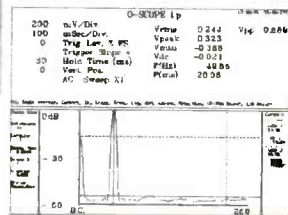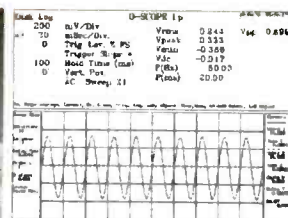PORTABLE  
MODULES  
CONVERT PC'S  
INTO  
MULTIPURPOSE  
TEST AND  
MEASURING  
INSTRUMENTS.



Why lug a scope around? Toss one of our modules into your laptop case or tool kit. For a multi-purpose test device, plug to a PC parallel port and use the PC screen. Continuous, delayed, or triggered sweeps can be frozen on the screen, printed out, or saved to disk. Frequency Spectrums DC to 25 MHz.

Allison now provides PICO TECHNOLOGY Ltd. portable test equipment, including high-speed scopes, and multi channel data loggers. Pico and O-Scope modules accept standard probes and work with 286 or faster PC's.

### FEATURES:

- PORTABLE UNITS TO 25 MHz
- USES PRINTER PORT
- USES STD. PROBES

### OPTIONS:

- PROBE SETS
- AUTOMOTIVE PROBES
- BATTERY PACKS
- SOFT & HARD CASES

O-Scopes Made in U.S.A.

Picos Made in U.K.

Same Day Shipping

Includes Cable, Software & Manuals

O-Scope Ip (DC-50KHz, single trace) .....\$189.

O-Scope II (DC-500KHz, dual trace) .....\$349.

PICO (ADC 200/20) (DC-10MHz, dual trace) .....CALL

PICO (ADC 200/50) (DC-25MHz, dual trace) .....CALL

PICO pc based data loggers from \$99.

Shipping within U.S. UPS Ground \$7.50(Second day \$11.50)

SEND CREDIT CARD INFO., M.O., or CHECK, OR CALL

**1-800-980-9806**

Allison Technology Corporation

2006 FINNEY-VALLET, ROSENBERG, TX 77471

PHONE: 281-239-8500 FAX: 281-239-8006

<http://www.atcweb.com>

# RAMSEY

## Doppler Direction Finder

Track down jammers and hidden transmitters with ease! This is the famous WA2EBY DF'er featured in April 99 QST. Shows direct bearing to transmitter on compass style LED display, easy to hook up to any FM receiver. The transmitter - the object of your DF'ing - need not be FM, it can be AM, FM or CW. Easily connects to receiver's speaker jack and antenna, unit runs on 12 VDC. We even include 4 handy home-brew "mag mount" antennas and cable for quick set up and operation! Whips can be cut and optimized for any frequency from 130-1000 MHz. Track down that jammer, win that fox hunt, zero in on that downed Cessna - this is an easy to build, reliable kit that compares most favorably to commercial units costing upwards of \$1000.00! This is a neat kit!



DDF-1, Doppler Direction Finder Kit ..... \$149.95

## 1 GHz RF Signal Generator



A super price on a full featured RF signal generator! Covers 100 KHz to 999.99999 MHz in 10 Hz steps. Tons of features; calibrated AM and FM modulation, 90 front panel memories, built-in RS-232 interface, +10 to -130 dBm output and more! Fast and easy to use, its


big bright vacuum florescent display can be read from anywhere on the bench and the handy "smart-knob" has great analog feel and is intelligently enabled when entering or changing parameters in any field - a real time saver! All functions can be continuously varied without the need for a shift or second function key. In short, this is the generator you'll want on your bench, you won't find a harder working RF signal generator - and you'll save almost \$3,000 over competitive units!

RSG-1000B RF Signal Generator ..... \$1995.00
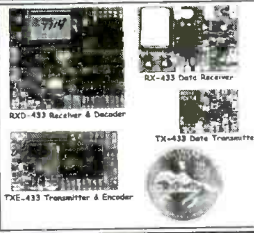
## Wireless RF Data Link Modules

RF link boards are perfect for any wireless control application; alarms, data transmission, electronic monitoring...you name it. Very stable SAW resonator transmitter, crystal controlled receiver - no frequency drift! Range up to 600 feet, license free 433 MHz band. Encoder/decoder units have 12 bit Holtek HT-12 series chips allowing multiple units all individually addressable, see web site for full details. Super small size - that's a quarter in the picture! Run on 3-12 VDC. Fully wired and tested, ready to go and easy to use!

RX-433 Data Receiver..... \$16.95 TX-433 Data Transmitter..... \$14.95  
RXD-433 Receiver/Decoder..... \$21.95 TXE-433 Transmitter/Encoder..... \$19.95



## World's Smallest TV Transmitters



We call them the 'Cubes'... Perfect video transmission from a transmitter you can hide under a quarter and only as thick as a stack of four pennies - that's a nickel in the picture! Transmits color or B&W with fantastic quality - almost like a direct wired connection to any TV tuned to cable channel 59. Crystal controlled for no frequency

drift with performance that equals models that cost hundreds more! Basic 20 mW model transmits up to 300' while the high power 100 mW unit goes up to 1/4 mile. Their very light weight and size make them ideal for balloon and rocket launches, R/C models, robots - you name it! Units run on 9 volts and hook-up to most any CCD camera or standard video source. In fact, all of our cameras have been tested to mate perfectly with our Cubes and work great. Fully assembled - just hook-up power and you're on the air! One customer even put one on his dog!

C-2000, Basic Video Transmitter..... \$89.95 C-2001, High Power Video Transmitter... \$179.95

## CCD Video Cameras



Top quality Japanese Class 'A' CCD array, over 440 line line resolution, not the off-spec arrays that are found on many other cameras. Don't be fooled by the cheap CMOS single chip cameras which have 1/2 the resolution, 1/4 the light sensitivity and draw over twice the current! The black & white models are also super IR (Infra-Red) sensitive. Add our invisible to the eye, IR-1 illuminator kit to see in the dark! Color camera has Auto gain, white balance, Back Light Compensation and DSP! Available with Wide-angle (80°) or super slim Pin-hole style lens. Run on 9 VDC, standard 1 volt p-p video. Use our transmitters for wireless transmission to TV set, or add our IB-1 Interface board kit for super easy direct wire hook-up to any Video monitor, VCR or TV with AV input. Fully assembled, with pre-wired connector.

CCDWA-2, B&W CCD Camera, wide-angle lens ..... \$69.95  
CCDPH-2, B&W CCD Camera, slim fit pin-hole lens. . . \$69.95  
CCDCC-1, Color CCD Camera, wide-angle lens ..... \$129.95  
IR-1, IR Illuminator Kit for B&W cameras ..... \$24.95  
IB-1, Interface Board Kit ..... \$14.95

## AM Radio Transmitter



Operates in standard AM broadcast band. Pro version, AM-25, is synthesized for stable, no-drift frequency and is settable for high power output where regulations allow, typical range of 1-2 miles. Entry-level AM-1 is tunable, runs FCC maximum 100 mW, range 1/4 mile. Both accept line-level inputs from tape decks, CD players or mike mixers, run on 12 volts DC. Pro AM-25 includes AC power adapter, matching case and bottom loaded wire antenna. Entry-level AM-1 has an available matching case and knob set that dresses up the unit. Great sound, easy to build - you can be on the air in an evening!

AM-25, Professional AM Transmitter Kit. .... \$129.95  
AM-1, Entry level AM Radio Transmitter Kit. . . \$29.95  
CAM, Matching Case Set for AM-1 ..... \$14.95

## Mini Radio Receivers



Imagine the fun of tuning into aircraft a hundred miles away, the local police/fire department, ham operators, or how about Radio Moscow or the BBC in London? Now imagine doing this on a little radio you built yourself - in just an evening! These popular little receivers are the nuts for catching all the action on the local ham, aircraft, standard FM broadcast radio, shortwave or WWV National Time Standard radio bands. Pick the receiver of your choice, each easy to build, sensitive receiver has plenty of crystal clear audio to drive any speaker or earphone. Easy one evening assembly, run on 9 volt battery, all have squelch except for shortwave and FM broadcast receiver which has subcarrier output for hook-up to our SCA adapter. The SCA-1 will tune in commercial-free music and other 'hidden' special services when connected to FM receiver. Add our snazzy matching case and knob set for that smart finished look!

AR-1, Airband 108-136 MHz Kit. .... \$29.95 FR-6, 6 Meter FM Ham Band Kit ..... \$34.95  
HFRC-1, WWV 10 MHz (crystal controlled) Kit ..... \$34.95 FR-10, 10 Meter FM Ham Band Kit ..... \$34.95  
FR-1, FM Broadcast Band 88-108 MHz Kit ..... \$24.95 FR-146, 2 Meter FM Ham Band Kit ..... \$34.95  
SR-1, Shortwave 4-11 MHz Band Kit ..... \$29.95 FR-220, 220 MHz FM Ham Band Kit ..... \$34.95  
SCA-1 SCA Subcarrier Adapter kit for FM radio. .... \$27.95 Matching Case Set (specify for which kit) ..... \$14.95

## PIC-Pro Pic Chip Programmer




Easy to use programmer for the PIC16C84, 16F84, 16F83 microcontrollers by Microchip. All software - editor, assembler, run and program - as well as free updates available on Ramsey download site! This is the popular unit designed by Michael Covington and featured in Electronics Now, September 1998. Connects to your parallel port and includes the great looking matching case, knob set and AC power supply. Start programming those really neat microcontrollers now...order your PICPRO today!

PIC-1, PICPRO PIC Chip Programmer Kit ..... \$59.95

**Order Toll-free: 800-446-2295**  
Sorry, no tech info, or order status at 800 number  
**For Technical Info, Order Status**  
**Call Factory direct: 716-924-4560**

**RAMSEY ELECTRONICS, INC.**  
793 Canning Parkway Victor, NY 14564  
See our complete catalog and order on-line with our secure server at:  
**www.ramseyelectronics.com**

## Super Pro FM Stereo Transmitter

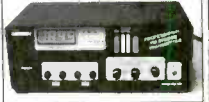

Professional synthesized FM Stereo station in easy to use, handsome cabinet. Most radio stations require a whole equipment rack to hold all the features we've packed into the FM-100. Set freq with Up/Down buttons, big LED display. Input low pass filter gives great sound (no more squeals or swishing from cheap CD inputs!) Limiters for max 'punch' in audio - without over mod, LED meters to easily set audio levels, built-in mixer with mike, line level inputs. Churches, drive-ins, schools, colleges find the FM-100 the answer to their transmitting needs, you will too. Great features, great price! Kit includes cabinet, whip antenna, 120 VAC supply. We also offer a high power export version of the FM-100 fully assembled with one watt of RF power, for miles of program coverage. The export version can only be shipped if accompanied by a signed statement that the unit will be exported.

FM-100, Pro FM Stereo Transmitter Kit ..... \$249.95  
FM-100WT, Fully Wired High Power FM-100..... \$399.95

## FM Stereo Radio Transmitters

No drift, microprocessor synthesized! Great audio quality, connect to CD player, tape deck or mike mixer and you're on-the-air. Strappable for high or low power! Runs on 12 VDC or 120 VAC. Kit includes snazzy case, whip antenna, 120 VAC power adapter - easy one evening assembly.

FM-25, Synthesized Stereo Transmitter Kit ..... \$129.95

Lower cost alternative to our high performance transmitters. Great value, easily tunable, fun to build. Manual goes into great detail about antennas, range and FCC rules. Handy for sending music thru house and yard, ideal for school projects too - you'll be amazed at the exceptional audio quality! Runs on 9V battery or 5 to 15 VDC. Add matching case and whip antenna set for nice 'pro' look.

FM-10A, Tunable FM Stereo Transmitter Kit. .... \$34.95  
CFM, Matching Case and Antenna Set ..... \$14.95  
FMAC, 12 Volt DC Wall Plug Adapter ..... \$9.95

## RF Power Booster

Add muscle to your signal, boost power up to 1 watt over a freq range of 100 KHz to over 1000 MHz! Use as a lab amp for signal generators, plus many foreign users employ the LPA-1 to boost the power of their FM transmitters, providing radio service through an entire town. Runs on 12 VDC. For a neat finished look, add the nice matching case set. Outdoor unit attaches right at the antenna for best signal - receiving or transmitting, weatherproof, too!

LPA-1, Power Booster Amplifier Kit ..... \$39.95  
CLPA, Matching Case Set for LPA-1 Kit ..... \$14.95  
LPA-1WT, Fully Wired LPA-1 with Case ..... \$99.95  
FMA-1, Outdoor Mast Mount Version of LPA-1 ..... \$59.95

## FM Station Antennas

For maximum performance, a good antenna is needed. Choose our very popular dipole kit or the Comet, a factory made 5/8 wave colinear model with 3.4 dB gain. Both work great with any FM receiver or transmitter.

TM-100, FM Antenna Kit ..... \$39.95  
FMA-200, Vertical Antenna ..... \$114.95




**ORDERING INFO:** Satisfaction Guaranteed. Examine for 10 days, if not pleased, return in original form for refund. Add \$6.95 for shipping, handling and insurance. Orders under \$20, add \$3.00. NY residents add 7% sales tax. Sorry, no CODs. Foreign orders, add 20% for surface mail or use credit card and specify shipping method.

CIRCLE 263 ON FREE INFORMATION CARD

# B<sup>2</sup> Spice A/D 2000

**\$299**

## Mixed-Mode Circuit Design

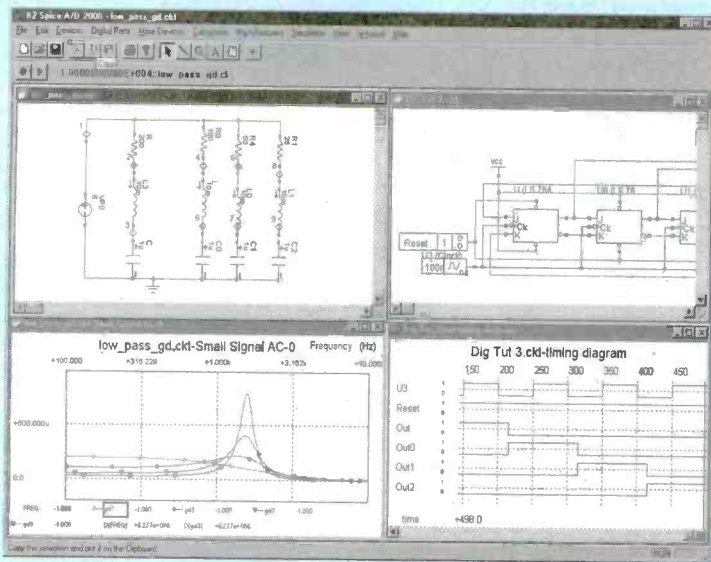

- ◆ Build complex circuits in minutes with our intuitive schematic editor.
- ◆ Turn any circuit into a functional part with just a few simple clicks.
- ◆ Interpret simulation results with customizable graphs.
- ◆ Find exactly the part you need from our database of 4500 parts.
- ◆ Run an Interactive Digital Simulation and view signals in the Timing Diagram

## Competitive Analysis

Characteristics	B <sup>2</sup> Spice A/D 2000	EWB Multisim Personal
PRICE	\$299	\$399
DC Operating point	X	X
DC Parameter Sweep	X	X
Temperature Sweep	X	-
Transient	X	X
Fourier	X	X
Parameterized transient	X	-
AC Analysis (freq sweep)	X	X
Parameterized AC Sweep	X	-
Pole Zero	X	-
Transfer function	X	-
DC Sensitivity	X	X
Distortion	X	X
Noise	X	X
DC Op. Pt. Monte Carlo	X	-
DC Sweep Monte Carlo	X	-
AC Monte Carlo	X	-
Transient Monte Carlo	X	-
Interactive, free running digital logic simulation.	X	-

Visit our web site for a free trial.

**\$99 Lite Version**

Beige Bag Software • [www.beigebag.com](http://www.beigebag.com) • 734.332.0487 • [info@beigebag.com](mailto:info@beigebag.com)

CIRCLE 319 ON FREE INFORMATION CARD

# New Science & Robotic Kits For The Millennium

## BEAMSTER

Beginner Soldering

**OWI-209K**  
\$19.95

Multi-functional; 90° Halogen light head or fluorescent lamp.

## TURBO 2000

Beginner

**OWI-6567**  
\$19.95

Air, motor drive or solar propelled (sold separately) speedster.

## KNIGHT INVADER

Beginner

**OWI-6577**  
\$19.95

Air, motor drive or solar propelled (sold separately) with principles of electricity.

## SUMOROBOT

Beginner

**OWI-9647**  
\$49.95

Retreats or attacks. Sensor system & infrared beam to detect opponents.

## AM RADIO

Beginner Soldering

**OWI-215K**  
\$24.95

Principles of radio wave technology. Tuner & volume control. Easy assembly.

Awards include:



**ROBOTIKITS™**  
**DIRECT**

17141 Kingsview Ave. Suite B, Carson, CA 90746 USA  
Phone: (310) 515-6800 • Toll Free: (877) 515-6651  
Fax: (310) 515-0927  
E-mail: [robotikitsdirect@pacbell.net](mailto:robotikitsdirect@pacbell.net) • Web: [www.robotikitsdirect.com](http://www.robotikitsdirect.com)



Order 24 Hrs. 8a.m. - 4p.m. PST



# A Trained Computer Repairman Charges \$100 An Hour and More... You Can Get That Training!

Foley-Belsaw's Totally New  
Computer Repair Course  
gives you the skills to  
start earning top pay  
**FAST!!!!!!**

You get these Foley-Belsaw  
Exclusives! At no extra cost!

- A+ Certification Test Preparation Tutor™
- Foley-Belsaw CD-ROM Learning Assistant™
- Business Start-up Resource



**SPECIAL BONUS**

Inquire now and your course will come with a complete video archive library of early printer and computer repair techniques... at no additional cost.



**No Experience Necessary!**

Get "hands-on" training in the exciting field of computer repair.

**Train At Home!**

There's not a more complete e- or affordable PC Repair course that will have you trained and job ready in such a short time.

**Fully illustrated, easy to understand course gives you everything you need to succeed.**

The key to your success lies in providing a service that is in great demand. Even if you have no experience, you can become an expert in a few short months. Foley-Belsaw's computer repair course is broken into small, easy to manage lessons. Each lesson is designed with your success in mind. After you complete the course, you'll have the expert knowledge to earn up to \$100 an hour, or more!

**Latest technologies and insider knowledge available only to Foley-Belsaw students!**

Get the hands-on experience you need in Computer Repair. Foley-Belsaw's CD-Rom Learning Assistant™ guides you through each lesson and is always right at your fingertips. The Test Preparation Tutor™ makes preparing for your A+ Certification as easy as turning on your computer. Foley-Belsaw's inside knowledge gives you the practical experience to become a computer repair professional. Get started today!

Take the first step to top pay.  
Call for a **FREE Opportunity Kit** today!  
**1-800-487-2100 Ext #A0114**

or complete this coupon and mail to Foley-Belsaw Institute,  
6301 Equitable Road, Kansas City, MO 64120-1395

**Yes!** Send me one of the following Free Opportunity Kits:

- Computer Repair, Maintenance, Upgrade, 321 NEW!
- Personal Computer Specialist, 325
- Professional Computer Programming, 323
- Professional Saw and Tool Sharpening, 332
- VCR/DVD Service and Repair, 320 NEW!
- Small Engine Service and Repair, 306
- TV/Satellite Dish Service and Repair, 322
- Professional Gunsmithing, 340
- Home Inspection, 342 NEW!
- Networking Specialist, 324
- Locksmithing, 307
- Woodworking, 319
- Upholstery, 308
- AC/Refrigeration, 343
- Electrician, 326

**Satisfaction Guaranteed!**  
**Foley-Belsaw gives you a Free 30-Day Trial.**  
Be careful!  
Most schools charge \$150.00 for this privilege.



World leader in training since 1926, provides at-home, "hands-on" training in high-demand fields.

Name \_\_\_\_\_  
Street \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_  
Phone ( ) \_\_\_\_\_ A0114

CIRCLE 318 ON FREE INFORMATION CARD

**MODERN  
ELECTRONICS**

**CABLE TV  
DESCRAMBLERS**



- ★ **FREE CATALOG!**
- ★ **BEST DEALER PRICING!**
- ★ **DISCOUNTED PRICING!**
- ★ **30 DAY FREE TRIAL!**
- ★ **100% MONEY BACK GUARANTEE**


**COPY RENTAL TAPES WITH  
OUR VIDEO STABILIZER**

**1-800-906-6664**

2609 S. 156th Circle • Omaha, NE 68130  
[www.modernelectronics.com](http://www.modernelectronics.com)



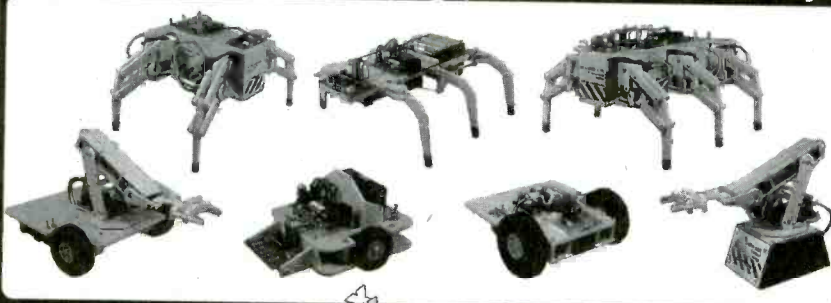**Build Your Own Intelligent Robot, We Make It Easy!**



Lynxmotion, Inc.  
104 Partridge Road  
Pekin, IL 61554-1403  
[www.lynxmotion.com](http://www.lynxmotion.com)



Visit our website or ask for our free catalog!

Tel: 309-382-1816  
Fax: 309-382-1254  
[sales@lynxmotion.com](mailto:sales@lynxmotion.com)  
[tech@lynxmotion.com](mailto:tech@lynxmotion.com)

**MECI** 340 East First Street  
Dayton, Ohio 45402  
*Your Electronics Value Company*

**Tons of  
Electronics**

Get your FREE catalog today and discover some of the best deals in electronics. We have thousands of items ranging from unique hard-to-find parts to standard production components. Call, write or fax today to start your subscription to one of the most unique catalogs in the industry, filled with super values on surplus electronic and hobbyist type items.



Checkout our 10,000 item on-line catalog <http://www.meci.com>

**Order Toll Free** Why pay more?  
**1-800-344-4465** Call today!  
Fax Order Line  
1-800-344-6324

CIRCLE 250 ON FREE INFORMATION CARD



**CCTV OUTLET  
INTERNATIONAL DISTRIBUTORS**



- SECURITY CAMERAS
- WIRELESS TRANSMITTERS
- MONITORS
- OUTDOOR CAMERAS
- HIDDEN CAMERAS
- ALARMS & ACC.
- OUTDOOR HOUSINGS


[WWW.CCTVCO.COM](http://WWW.CCTVCO.COM)

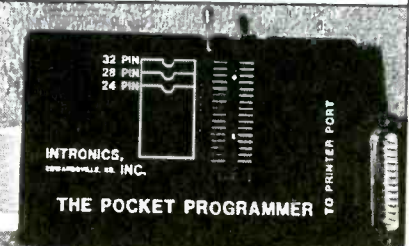**\$34.00**

over 50 brands to choose from  
buy on line or dial toll free  
**1-800-323-8746**



**The Pocket Programmer  
Only \$129.95**



The portable programmer that uses the printer port of your PC instead of an internal card. Easy to use software that programs Eprom, EEprom, Flash & Dallas Ram. 27(C) / 28(C) / 28F / 29F / 29C & 25XX series from 16K to 8 Megabit with a 32 pin socket. Adapters available for Pic, PLCC, 5-Gang, 874X, 875X MCU's, 40-Pin X 16 & Serial Eprom's, 82/74 Prom's and Eprom Emulator to 32K X 8.

**Same Name, Address & Phone #  
for 16 Years... Isn't it Amazing ?**

**Intronics, Inc.**  
Box 13723 / 612 Newton St.  
Edwardsville, KS 66113 Add \$5.00 COD  
Tel. (913) 422-2094 Add \$4.00 Shipping  
Fax (913) 441-1623 Visa / Master Charge

**3 Axis Motion Control System  
Complete, ready to run**

**\$ 295.00 + 12.00 S/H**

Build or adapt CNC mills, CNC routers, Robots, Etc. Includes: 3 Stepping motors (70 oz/in 200 steps/rev). External board (connects to parallel port of a PC). Power supply, Cables, Manual and the MAXNC drive software, with linear, circular and helical interpolation, acceleration deceleration, full contouring, 'G' code programming, screen plot, code generation from CAD (CAM), and more.

For more information,  
phone or write to:

**MAXNC**  
6730 West Chicago  
Suites 2 & 3  
Chandler, AZ 85226  
Ph (480) 940-9414  
Fax (480) 940-2384



**CABLE BOXES**

- **WE'LL BEAT ANY PRICE!**
- **1 YR WARRANTY**
- **FREE CATALOG**
- **30 DAY MONEY BACK GUARANTEE**

[WWW.CATVBXES.COM](http://WWW.CATVBXES.COM)

**1-800-765-4912**

# New MILLENNIUM SALE on Our Best Soldering & Desoldering Tools

**DEN-ON SC7000Z Desoldering Tool**  
**Guaranteed** to be the **BEST** Transportable Desoldering Tool you will ever own. **Base Station Performance** in a Portable Tool. Very High and Quick Vacuum. Quick cleaning filter.

10% off of our  
 Nationally Advertised  
 Low Price of \$395  
 For a Limited Time  
**\$355.50**



Inspect your SMD work with the Stereo Zoom Microscope from Sciencscope. Add different eyepieces and auxiliary lens to get various Magnifications, field of views, and large working distances. Several microscopes listed on our Web site as low as \$495.

**GL-CO-PK4**  
 Regular Price \$1364.00  
**Millennium Price**  
**\$1245.60**



**DEN-ON SS-8200 Temperature Controlled Soldering Pencil** is a hit with everybody who ventures to try it. It is small, lightweight, easy to use, temperature controlled, and has a burn proof cord and long lasting tips. It also has a 200W Ceramic Element that keeps it at a constant temperature.

**Special Millennium Price**  
**\$95.00**



The Best Hot Air Tool available is the **HG3002LCD** by Steinel. Temperature controlled from 120°F to 1100°F. Variable speed motor, Hot and Cool switch. LCD Readout for Accurate Nozzle Temperature control. Regular price \$182.00  
**Now \$163.80**



**EDSYN's 951SX Industrial Grade Temperature Controlled Soldering Station** is by far their most popular Soldering Station. Sold nationally for as much as \$164.95.

**Our Special Price**  
**\$99.00**



**EDSYN's ZD906** includes a Desoldering Tool, a Soldering Pencil and a Hot Air Pencil. Shop air is required. Very small footprint required on your bench. Check out the Specs on our Web Site. 18 Month Warranty Save 10% from our already low price of \$1169.00  
**New Millennium Price**  
**\$1061.10**



Very **REDUCED** Price on the **EDSYN ZD500DX**. Save \$200.00 on one of the Best Industrial Grade Desoldering Stations available. Completely made in the USA by skilled USA workers. 18 Month Warranty. Very Inexpensive to Operate.

Was \$749.95  
**Now \$549.95**



**Contract Manufacturers**  
 This Spot Type Hot Air Rework Station was made for you. Check out the specs. on our web site. **Free Trials Available.** Advertised Nationally for \$5000.

**DEN-ON SD-3000 Millennium PRICE**  
**\$4250.00**



**New Product from EDSYN 971HA SMT Hot Air Station**  
 Precise adjustment for heat and air flow. Air automatically shuts off when pencil is placed in holder. Excellent for SMD work up to 80 pins. Easily converts to Powerful Solder Station w/large selection of tips.


Our Regular Price \$599.00  
**Now \$539.10**



**Capacitor Wizard ESR Meter**  
 Will be on sale for a **Limited Time Only**  
 Advertised elsewhere  
 In this magazine for \$179.95  
**Must Mention this Ad**  
**Now \$159.95**



**Sciencscope Video Inspection System**  
 Ideal for inspection, training, and/or documentation. Magnification to 540x & working distances to 13 inches. Specs are on web site. **Mention this ad for 10% Off regular Price of \$2520.00**  
**CC-97-VS2** Includes single lens Adapter, CCD camera, 3x coupler, digital CCD Camera, 14" monitor, Fiber optic illuminator, Fiber optic ring light, and large boom stand

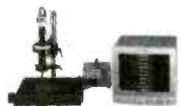

**PDR/Xytronic 710 SolderLight**  
 IR Component Heating w/IR Hand tool  
 IR PCB Preheating W/Bottom Heater  
**All types SMD's and BGA's**  
 See Web Site for Specs.  
**Millennium Madness**  
**\$2395.00**



[www.howardelectronics.com](http://www.howardelectronics.com)

**Visa - M/C - Discover - A/E - COD - Terms to Qualifying Companies**  
**30 Day Money Back Total Satisfaction Guarantee**

**HOWARD ELECTRONIC INSTRUMENTS INC**  
 Your Desoldering Specialists

6222 N. Oliver Kechi, KS 67067  
 Toll Free U.S. and Canada  
**1-800-394-1984**

[www.howardelectronics.com](http://www.howardelectronics.com)  
 sales@howardelectronics.com  
 International (316) 744-1993  
 or Fax (316) 744-1994

CIRCLE 237 ON FREE INFORMATION CARD

# electronic design STUDIO




The new fully integrated electronics CAD system with schematic, simulation, PCB, autorouting and CAD/CAM modules as standard. **New Version 1.2**

- Brings the power of desk top publishing to EDA.
- Publication quality feature rich schematic production.
- New generation dynamic netlist navigator with project management.
- Superb quality CAD/CAM output, including R-274X and Excellon.
- Wizards automate key features.
- Compatible with TINA Pro 5.5.
- No pln limits!

Electronic Design Studio from **\$299**

Price excludes tax and shipping.  
30 DAY MONEY BACK GUARANTEE  
Copyright © 2000.  
Prices & specifications subject to change without notice.

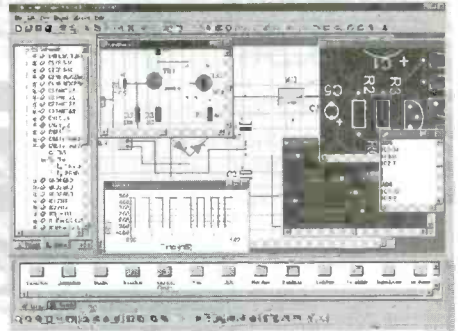**QR**™ Quickroute Systems  
WEB [www.dotqr.com](http://www.dotqr.com)  
Tel 212 937 5200  
Email [sales@dotqr.com](mailto:sales@dotqr.com)  
Fax 212 937 5200



## Tailor made to suit you

## ELECTRONIX EXPRESS

Visit Our Website At  
<http://www.elexp.com>

<p><b>WELLER SOLDERING STATION - MODEL WLC 100</b></p> <ul style="list-style-type: none"> <li>• Variable power control (5 to 40 watts)</li> <li>• Replaceable heating element</li> <li>• Quality light-weight pencil iron</li> </ul> <p style="text-align: right;"><b>\$36<sup>95</sup></b></p> <hr/> <p style="text-align: center;"><b>LOWEST PRICE 20MHZ</b></p> <p><b>instek® OSCILLOSCOPE</b> MODEL GOS-620 Dual Channel - 20MHZ (INCLUDES PROBES)</p> <p style="text-align: right;"><b>\$299<sup>00</sup></b></p> <hr/> <p><b>SCOPE PROBE</b> 60 MHZ SWITCHABLE X1, X10</p> <p style="text-align: right;"><b>\$12<sup>95</sup></b></p> <hr/> <p><b>DIGITAL MULTIMETER</b> 32 Ranges - 3 1/2 Digit MODEL MY-64 AC/DC Volt/Current, Res. Cap., Frequency. Rubber Holster Included</p> <p style="text-align: right;"><b>\$27<sup>95</sup></b></p> <hr/> <p><b>PAD-234</b> DIGITAL/ANALOG TRAINER</p> <p>Complete portable workstation. Variable and fixed power supplies, function generator, digital I/O, rugged design, high impact case.</p> <p>Assembled <b>\$150<sup>00</sup></b>      Kit <b>\$110<sup>00</sup></b></p>	<p><b>instek® FUNCTION GEN.</b> WITH INT/EXT FREQ. COUNTER</p> <p>3 MHz, Digital Display MODEL 8216 <b>\$199<sup>00</sup></b></p> <hr/> <p><b>ALLIGATOR LEADS</b> <b>\$2<sup>10</sup></b> SET OF 10</p> <hr/> <p><b>SWITCHES</b> Mini Toggle SPDT ..... <b>50¢ ea.</b></p> <hr/> <p><b>SOLDERING IRON</b> 3-WIRE HIGH PERFORMANCE #060501 <b>\$5<sup>25</sup></b></p> <hr/> <p style="text-align: center;"><b>HIGH QUALITY TOOLS</b> With Cushion Grips and Return Spring</p> <table style="width: 100%; text-align: center;"> <tr> <td>Needle Nose Pliers <b>\$2<sup>95</sup></b></td> <td>Wire Stripper <b>\$1<sup>50</sup></b></td> <td>Diagonal Cutter <b>\$2<sup>95</sup></b></td> </tr> </table> <hr/> <p style="text-align: center;"><b>DC POWER SUPPLIES</b></p> <p>MODEL HY3003 - DIGITAL DISPLAY Variable output, 0-30 VDC, 0-3 Amp <b>\$89<sup>00</sup></b></p> <p>MODEL HY3003-3 - TRIPLE OUTPUT Two 0-30 VDC, 0-3 Amp variable outputs plus 5V 3A fixed. Digital Display. <b>\$215<sup>00</sup></b></p>	Needle Nose Pliers <b>\$2<sup>95</sup></b>	Wire Stripper <b>\$1<sup>50</sup></b>	Diagonal Cutter <b>\$2<sup>95</sup></b>																																				
Needle Nose Pliers <b>\$2<sup>95</sup></b>	Wire Stripper <b>\$1<sup>50</sup></b>	Diagonal Cutter <b>\$2<sup>95</sup></b>																																						
<p><b>RSR™ TELECOMMUNICATIONS TRAINER</b> HANDS-ON TELEPHONY, LAN, CATV EXPERIENCE WITH ONE SELF-CONTAINED UNIT</p> <table style="width: 100%;"> <tr> <td>T-Comm Trainer (TCM-100) .....</td> <td style="text-align: right;">\$199.95</td> </tr> <tr> <td>Lab Manual / Work Book .....</td> <td style="text-align: right;">26.95</td> </tr> <tr> <td>Component and Supplies Kit .....</td> <td style="text-align: right;">37.95</td> </tr> <tr> <td>Tool Kit .....</td> <td style="text-align: right;">119.95</td> </tr> </table> <p style="text-align: right; font-weight: bold; font-size: 1.2em;">Only <b>\$199<sup>95</sup></b></p> <p style="text-align: right; font-size: 0.8em;">MODEL TCM-100</p>	T-Comm Trainer (TCM-100) .....	\$199.95	Lab Manual / Work Book .....	26.95	Component and Supplies Kit .....	37.95	Tool Kit .....	119.95	<p><b>SOLDERLESS BREADBOARD</b> 830 tie points. MB102PLT model features 3 binding posts and aluminum backplate.</p> <table style="width: 100%; text-align: center;"> <tr> <td>Part No.</td> <td>1-9</td> <td>10+</td> </tr> <tr> <td>MB102</td> <td>5.95</td> <td>5.00</td> </tr> <tr> <td>MB102PLT</td> <td>8.95</td> <td>8.00</td> </tr> </table> <hr/> <p><b>MOTION DETECTOR</b> <b>\$2 ea. - 10 For \$15</b></p> <table style="width: 100%;"> <tr> <td>LM555 10 Min. ....</td> <td style="text-align: right;">22¢ ea.</td> </tr> <tr> <td>LM741 10 Min. ....</td> <td style="text-align: right;">27¢ ea.</td> </tr> <tr> <td>74LS00 10 Min. ....</td> <td style="text-align: right;">18¢ ea.</td> </tr> <tr> <td>7805 Regulator 10 Min. ....</td> <td style="text-align: right;">30¢ ea.</td> </tr> <tr> <td>2N3904 10 Min. ....</td> <td style="text-align: right;">6¢ ea.</td> </tr> <tr> <td>PN2222 10 Min. ....</td> <td style="text-align: right;">6¢ ea.</td> </tr> <tr> <td>Red LED T 1 3/4 10 Min. ....</td> <td style="text-align: right;">6¢ ea.</td> </tr> <tr> <td>Green LED T 1 3/4 10 Min. ....</td> <td style="text-align: right;">7¢ ea.</td> </tr> <tr> <td>Yellow LED T 1 3/4 10 Min. ....</td> <td style="text-align: right;">8¢ ea.</td> </tr> <tr> <td>Photo Cell 10 Min. ....</td> <td style="text-align: right;">65¢ ea.</td> </tr> <tr> <td>100K Pot., 1" Shaft PC Mt. 10 Min. ...</td> <td style="text-align: right;">15¢ ea.</td> </tr> </table>	Part No.	1-9	10+	MB102	5.95	5.00	MB102PLT	8.95	8.00	LM555 10 Min. ....	22¢ ea.	LM741 10 Min. ....	27¢ ea.	74LS00 10 Min. ....	18¢ ea.	7805 Regulator 10 Min. ....	30¢ ea.	2N3904 10 Min. ....	6¢ ea.	PN2222 10 Min. ....	6¢ ea.	Red LED T 1 3/4 10 Min. ....	6¢ ea.	Green LED T 1 3/4 10 Min. ....	7¢ ea.	Yellow LED T 1 3/4 10 Min. ....	8¢ ea.	Photo Cell 10 Min. ....	65¢ ea.	100K Pot., 1" Shaft PC Mt. 10 Min. ...	15¢ ea.
T-Comm Trainer (TCM-100) .....	\$199.95																																							
Lab Manual / Work Book .....	26.95																																							
Component and Supplies Kit .....	37.95																																							
Tool Kit .....	119.95																																							
Part No.	1-9	10+																																						
MB102	5.95	5.00																																						
MB102PLT	8.95	8.00																																						
LM555 10 Min. ....	22¢ ea.																																							
LM741 10 Min. ....	27¢ ea.																																							
74LS00 10 Min. ....	18¢ ea.																																							
7805 Regulator 10 Min. ....	30¢ ea.																																							
2N3904 10 Min. ....	6¢ ea.																																							
PN2222 10 Min. ....	6¢ ea.																																							
Red LED T 1 3/4 10 Min. ....	6¢ ea.																																							
Green LED T 1 3/4 10 Min. ....	7¢ ea.																																							
Yellow LED T 1 3/4 10 Min. ....	8¢ ea.																																							
Photo Cell 10 Min. ....	65¢ ea.																																							
100K Pot., 1" Shaft PC Mt. 10 Min. ...	15¢ ea.																																							
<p><b>PRESS-N-PEEL</b> PC Board Transfer Film</p> <table style="width: 100%;"> <tr> <td>PNP Blue 5 Sheet .....</td> <td style="text-align: right;">\$9.90</td> </tr> <tr> <td>PNP Wet 5 Sheet .....</td> <td style="text-align: right;">9.90</td> </tr> <tr> <td>PNP Blue 20 Sheet .....</td> <td style="text-align: right;">28.95</td> </tr> <tr> <td>PNP Wet 20 Sheet .....</td> <td style="text-align: right;">28.95</td> </tr> </table> <p style="text-align: right; font-weight: bold; font-size: 1.2em;">\$3<sup>95</sup></p>	PNP Blue 5 Sheet .....	\$9.90	PNP Wet 5 Sheet .....	9.90	PNP Blue 20 Sheet .....	28.95	PNP Wet 20 Sheet .....	28.95	<p><b>RESISTOR KIT</b> 1/4 W 5% film. 5 pieces each of 73 values. 365 pieces total.</p>																															
PNP Blue 5 Sheet .....	\$9.90																																							
PNP Wet 5 Sheet .....	9.90																																							
PNP Blue 20 Sheet .....	28.95																																							
PNP Wet 20 Sheet .....	28.95																																							

FREE CATALOG

MORE Low-Priced Items In Our **FREE** 256-Page Catalog

TERMS: Min. \$20 + shipping. School Purchase Orders, VISA, MC, Money Order, Prepaid. NO PERSONAL CHECKS, NO COD. NJ Residents: Add 6% Sales Tax.

In NJ: 732-381-8020  
FAX: 732-381-1006
365 Blair Road • Avenel, NJ 07001-2293  
**800-972-2225**
<http://www.elexp.com>  
email: [electron@elexp.com](mailto:electron@elexp.com)

Poptronics, August 2000

84

CIRCLE 205 ON FREE INFORMATION CARD

www.americanradiohistory.com

Prices effective July 18 through September 1, 2000.

**mcm**

**Electronics**

**mcm**

What you want....Today!™

You Must Provide This Source Code To Receive Discount Pricing: **POP78**

**MCM GOLDLINE®**



**4" Color LCD Monitor Module**

Open circuit board has no case or housing

allowing easy incorporation into automotive seat backs, custom panels and enclosures. Use for automotive multimedia and navigation systems, surveillance and video equipment.

- 3.5mm A/V input
- Resolution: 383 (H) x 234 (V)
- Requires: 12VDC, 500mA
- Dimensions: 3 3/4" x 5" x 1 1/2"

**ORDER**

# **60-9855**

**\$119<sup>00</sup>**



**TENMA Soldering Station**



- Perfect for all types of board level and precision work
- LED bargraph display accurately shows temperature and setpoint
- Temperature range: 300°~790°

Order # 21-147 Reg. \$79.95

**NOW ONLY \$59<sup>95</sup>**



**TP TENMA®**

**13.8VDC 10 Amp Power Supply**

- Perfect for servicing or operating high current autosound products
- Provides 10A output, 14A surge
- Front panel fuse is easily accessible

Order # 72-6623 Reg. \$64.95

**NOW ONLY**

**\$39<sup>95</sup>**



**Clarke Aluminum Tool Case**

Made of lightweight aluminum and designed to take rough field use. Two inside pallets and

adjustable compartments easily carry hand tools, small soldering equipment and test equipment.

- Black finish
- Dimensions: 19" x 14" x 6"

Order # 21-3460 Reg. \$51.50

**NOW ONLY**

**\$34<sup>95</sup>**



**TENMA DMM with Logic Function**

3 1/2 digit LCD display meter measures AC/DC voltage to 600V, AC/DC current to 10A, resistance to 2000Mohm, capacitance to 20µF, transistor h<sub>FE</sub> and provides diode and logic test. Includes holster and test leads.

Order # 72-4025 Reg. \$65.95

**NOW ONLY \$39<sup>95</sup>**



**BATTERY CS3**

**Sealed Lead Acid Battery**

12 volt, 4.5 amp/hour battery is ideal for security and other power back-up applications. 0.25"

tabs accept standard quick-disconnects. Dimensions 3 1/2" x 2 3/4" x 4".

Order # 29-1335 Reg. \$26.95

**NOW ONLY**

**\$14<sup>95</sup>**



**multicomp Automotive 12 Volt Relays**

These high current relays are commonly used for switching high current autosound, security, lighting and other custom applications. Tabs accept standard female quick-disconnects or commonly used four and five pin OEM relay sockets. •Coil voltage: 12VDC 145mA •Dimensions: 1" (H) x 1" (W) x 1" (D) (less mounting tab)

Order #	(1-9)	(10-24)	(25-up)
Contact Type	Contact Current	Contact Current	Pins
26-£33	\$1.19	\$0.99	\$0.85
SPST		40A	Four
26-£34	1.19	0.99	0.85
SPDT		30A	Five



**DEFENDER SECURITY**

**Micro Board CCD Camera**

•Compact open-board black and white camera •Measures 1 1/4" x 1 1/4" x 1 1/8" •CCD image device •380 lines of resolution •NTSC composite video output •12VDC, 330mA

Order # 82-2990 Reg. \$64.95

**NOW ONLY**

**\$49<sup>95</sup>**

**CHECK**

**OUT**

our full line catalog at:



**1-800-543-4330**

**www.mcmelectronics.com**

fax: 1-800-765-6960

Free Literature!



**MCM ELECTRONICS®**  
650 CONGRESS PARK DR.  
CENTERVILLE, OH 45459



**SOURCE CODE: POP78**

**A Premier Farnell Company**

CIRCLE 160 ON FREE INFORMATION CARD

## PIC MICRO TOOLS

### PROGRAM PIC'S IN BASIC!

B2 compatible! Plus can be used within MPLAB IDE. Includes FREE Proto board! Pic n' Basic Pro Compiler \$129.00

**ALLPIC Plus Programmer**  
Program PIC - Scenix - Atmel  
Serial EEPROMS Includes 40  
Pin ZIF Complete \$99.00

**PIC & Scenix Prototyping Boards**  
New Special design makes it easier to  
prototype PIC & Scenix micros than  
any other prototyping boards!  
Starting at \$9.95

**New! Experimenter - Lab Board**  
Several models available! Built in  
Graphics LCD, Servos, Button Matrix,  
EEPROM, Solderless Bread Boards.  
For Beginners to Professionals! All  
boards will work with PIC or Scenix  
Complete Kits Starting at \$49.95

Educational Discounts Available!

VISA • MasterCard • American Express

To Order Call 1-800-773-6698

Send Money orders to: Worldwyde Com,  
33523 Eight Mile Rd #A3-261, Livonia, MI 48152  
Visit us online <http://www.worldwyde.com>

## Monitor Test Equipment

- Sweep rates to 64kHz
- Gray Scale/Color Bars & More
- "AutoScan" (auto rate switching!)
- TV/Stereo/S-Video units
- 6 port "Burn-in" units
- Portable & Bench units
- Video units from \$129.95
- Computer models from \$99.95
- FCC approved units

LOW COST

CMM 1-800-466-4411, 770-662-5633

[WWW.computermonitor.com](http://WWW.computermonitor.com)

Visa-MC-AMX-Discover- On-line ordering

## 35¢ Switches



Premium quality. Rated 6A/125V. All  
hardware included. 1/4" panel hole.  
SPDT or DPDT, on-on or on-off-on.  
100pcs minimum. VISA or Master  
Card. Sorry, no COD. Order Toll-free.

Gateway Products Corporation  
Email: [GtwyPrds@aol.com](mailto:GtwyPrds@aol.com)

# 800-830-9195

## OWN A MACHINE SHOP!

### Do it yourself!

No more waiting to have parts or repairs done.

- Easy to use—Free training.

You'll be doing quality work  
right away.

- Affordable—Six models

starting at \$995.

- Versatile—Work

metal—and wood

or plastic.

- CNC adaptable



"I can fix most anything. Now I don't  
know how I lived without it.  
It paid for itself in no time!"

Enjoy the freedom  
& cost savings of  
owning a benchtop  
machine shop.

FREE  
Info Pak

CALL TODAY!

1-800-345-6342 or write: **Smithy.**

Dept. PE001, PO Box 1517  
Guaranteed to pay its own way Ann Arbor, MI 48106-1517

Visit us at [www.smithy.com](http://www.smithy.com)

## GLOBALTECH DISTRIBUTORS

The Ultimate Electronic Saving Store

Call Today!—1-(800)582-5116

	25ps.	100ps.	500ps.
PIC12C508	1.30	1.20	1.15
PIC16C54	1.40	1.35	1.30
PIC16C56	1.65	1.50	1.45
PIC16C621	2.00	1.95	1.85
PIC16C622	2.25	2.15	1.95
€8HC705C8A	5.50	5.00	4.85
ATF89C52	4.00	3.50	3.15
€2S131	1.50	1.30	1.15
Gall16V8b	1.00	.95	.75
4mhz Res.	.45	.40	.32
20mhz Crystal	.50	.45	.40
CATV Remote	4.25	3.75	3.25
Universal Remote Controls	4.50		

Order@[globaltechdistributors.com](mailto:globaltechdistributors.com)



BEST MICROPROCESSOR STOCK DISTRIBUTOR WORLD WIDE.

## PIC Programmer Kits

Super Value!

\$19.95  
+S&H \$4.95\*

Code:  
CPS96

12C5xx (12C508),  
14000 and 16Cxx (16F84) series  
(except 16C54-58). • All compo-  
nents, PCB and Instructions included. • Parallel port of  
PC is used with straight through (25 pin) cable (not supplie-  
d). • Kit uses shareware which is downloaded from the  
web and registered for \$20. • 40 pin ZIF socket rec-  
ommended (available for \$11.95). • For more info and  
Atmel programmers visit [www.electronics123.com](http://www.electronics123.com)

### Video Camera module

Code:BB004

CMOS Camera Module, Black &  
White, Size: 63"x0.63"x0.59"H.

Low cost, low power and very  
small! Lens: \$4.9, F2.8 FOV 56  
deg x 42 deg EIA 320Hx240V.

Scan: 2:1 interlace, 0.6" DIL

Package: 5 pins. Pin 3 is 1V p-p composite video  
(75 ohm) to standard video monitor. Power  
Supply: 5V +A 0.5V. Current 10mA. Needs regu-  
lated power supply. \*S&H to Canada is \$7.95

\$35.95  
+S&H \$4.95\*

Toll Free: 1-888-549-3749 (USA & Canada)


Tel: (330) 549-3726. Request a FREE catalog or visit us  
at: [www.electronics123.com](http://www.electronics123.com) for more products.  
Amazon Electronics, Box 21 Columbiana OH 44408

## CONTROL YOUR WORLD

Modular, Open Source Automation

Digital Input  
From \$40

Controllers  
From \$75

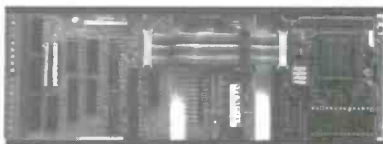

X-10 Control  
From \$47

Event control software included

Build Custom controllers for -

\*\* Home Automation

\*\* Machine Automation

\*\* Security

\*\* Robotics

Low Cost Microcontroller boards, kits & applications

**ZORIN** <http://www.zorinco.com>  
or call (206) 282-6061

## Underground Info!

Hacking • Cracking • Satellite • Cable • Phreaking • Micros  
GameBoy I/O • Smart Cards • Emulation • Hardware • Tools

Plus More! Visit us on the web!

### Books & CD's:

Hackers Anarchy Cook Book 2000 .....	\$39.95
The Hack & Crack Bible Vol.2 .....	\$39.95
Hackers Gold CD Vol.1 .....	\$49.00
Secrets of Dish Network Vol.1 .....	\$49.95
DSS Secrets Vol.4 Book & CD .....	\$49.95
Cable Test Devices Source Code & Plans ..	\$79.00
PSX Secrets w/ MODCHIP Source Code ....	\$69.95
The Ultimate Phreaking Guide .....	\$39.95
Emulator Heaven CD .....	\$49.95
Game Boy I/O - Servos/Relays/Sensors .....	\$49.95

### Hardware:

PIC, Scenix, Atmel Programmer Complete ...	\$99.00
ISO 7816 Smart Card Programmer .....	\$59.95
Smart Cards (from) .....	\$ 6.95
Prototyping Boards PIC & Scenix .....	\$ 9.95

VISA • MasterCard • American Express

To Order Call 1-800-773-6698

Send Money orders to: Worldwyde Com,  
33523 Eight Mile Rd #A3-261, Livonia, MI 48152  
Visit us online <http://www.worldwyde.com>

## The Hack & Crack Bible on CD-ROM

Includes all Software, Documentation,  
Plans, and PCB Layouts!

Unlock the secrets of:

- DSS & Smart Cards  
—Programming & Schematics
- Cable Test Devices
- Sony Playstation  
—Mod Chip CD Backups/Emulation
- Backup Sega & SNES Console Cartridges
- Sega & SNES Emulation on your PC or Mac
- Warz - where to find them on the Internet
- Cellular Hack/Phreak/Mod
- And Much More!

Only  
\$29.95

PIC & Age Compatible CD-ROM

VISA • MasterCard • American Express  
To order, call Worldwyde @ 1-800-773-6698  
21365 Randall Street • Farmington Hills, MI 48335  
Visit us on the web at [www.worldwyde.com/hack](http://www.worldwyde.com/hack)

## Video Scrambler

HIGH PERFORMANCE  
ENCODE/DECODE SYSTEM

CREATE OR RESTORE  
SCRAMBLED VIDEO  
AUTOMATICALLY

MAKES THE PERFECT  
PORTABLE ENCRYPTION  
SYSTEM!

OPERATES ON A STANDARD  
9 VOLT BATTERY

phone:  
(219) 233-3053  
fax:  
(219) 239-1366



MODEL VITR



R.C. Distributing • P.O. Box 552 • South Bend, IN 46624

[www.rcdistributing.com](http://www.rcdistributing.com)

[www.jm-micro.com](http://www.jm-micro.com)

## PIC In-Circuit Emulator

for the PIC16Cxx from \$295

**PIC Programmer** \$155

**80C552 (8051) Development**

Training System \$235

**68HC11 SBC** \$120

**ROMY-16 EPROM Emulator**  
from \$195

**Universal Microprocessor  
Simulator/Debugger (including  
Assembler, and Disassembler)**  
\$100 each CPU

**J&M Microtek, Inc.**

83 Seaman Rd. W Orange, NJ 07052

Tel:(973)325-1892 Fax:(973)736-4567

## CABLE SECRETS!!!

### Build your OWN cable box "test" devices!

Why pay \$100.00 or more for a "test" device that someone else made? Make your own! Includes complete source code and plans for the most commonly used cable boxes. *Unlock all of the channels on your box!*

**Or start your own lucrative business!**

Complete source code ..... \$79.95  
Code for individual boxes ..... \$29.95

## DSS SECRETS — Vol. 2

Step-by-step instructions on programming your own DSS access card. *Unlock all channels on your own card!* This is the most current information on the market! Includes software, plans, and hardware sources. Book & CD-ROM.

**DSS Secrets Vol. 2..... \$49.95**

VISA • MasterCard • American Express

To order, call Worldwyde @ 1-800-773-6698

21365 Randall Street • Farmington Hills, MI 48336

Visit us on the web at [www.worldwyde.com](http://www.worldwyde.com)

## Press-n-Peel Transfer Film

### PC Boards in Minutes

8.5" x 11" Shts.  
\* Or Photocopy  
\*\*Use standard  
household iron

1. LaserPrint\*
2. Press On\*\*
3. Peel Off
4. Etch



Use Standard Copper Clad Board  
20 Shts \$30/ 40 Shts \$50/ 100 Shts \$100  
Visa/MC/PO/CK/MO \$4 S&H/Foreign Add \$7

**Techniks Inc.**


P.O. Box 463, Ringoes NJ 08551

ph. 908.788.8249 fax 908.788.8837

[www.techniks.com](http://www.techniks.com)

Vist Our E-Store On-Line!

## CONTROL IT

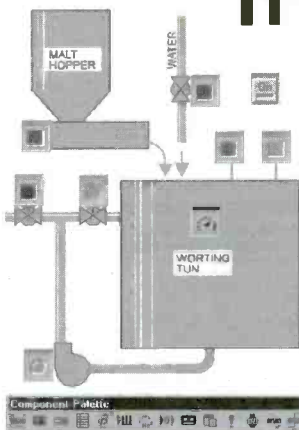

**Intec Automation Inc.**

[www.microcommander.com](http://www.microcommander.com)

## PIC PROJECTS

Book & CD-ROM

Many PIC Projects for Beginners & Experts!  
Includes Software, Documentation, and PCB Layout

Book &  
CD Only  
**\$24<sup>95</sup>**

- LCDs
- X10 — Home Automation
- Keypads
- Serial Port Interface
- On-Screen Displays
- Robotics
- Data Logging
- Serial-Parallel
- And Many More!

### PIC Programmer

Programs all PIC16C55x/6x/7x/8x/9x,  
PIC16F8x, and PIC12C devices.  
Optional ZIF adapters for SOIC & PLCC.  
Includes all necessary software.  
Only \$39<sup>95</sup>

Buy  
Both for  
**\$59<sup>95</sup>**

We accept

VISA • MasterCard • American Express

To order, call Worldwyde @ 1-800-773-6698

21365 Randall Street • Farmington Hills, MI 48336

Visit us on the web at [www.worldwyde.com/pic](http://www.worldwyde.com/pic)

## LASER MODULE



Auto Power Control  
Collimated Laser  
Compact Size  
100,000 hr lifetime  
No Electronics Required

Visible Laser Modules(635-670 nm)  
TTL Modulated Laser Modules  
Line Generator Laser Modules  
Infrared Laser Modules(780-830 nm)

from  
**\$ 29 (US)**

## LASER POINTER



Focus Adjustable  
Elegant Design  
Solid Metal Body

Pen Style Laser Pointer (1500 ft visibility)  
Key Chain Laser Pointer (1500 ft visibility)  
Available in silver and, black finish.

**\$19.95 (US)**

World Star Tech.

Ask for free catalog

Tel:(416)204 8298 Fax:(416)596 7819

<http://www.worldstartech.com> e-mail: [info@worldstartech.com](mailto:info@worldstartech.com)

## 10Hr Phone Recorder \$69

Records both sides of conversation automatically

**Telephone Scrambler \$159 ea. or 2 for \$149 ea.**

Secure phone conversations with this high tech "rolling code" scrambler. Thousands of codes! Easy connection. Requires one at each end.

**Voice Changer Phone \$99**

Disguise your voice with this phone. 16 Pitches. Make your voice deeper or higher. Men can sound like a woman. Easy to use.

**5 Hr. Phone Recorder Touch-tone decoder \$159**

Records both sides of conversation including phone numbers dialed

**Phone Information Recorder \$169**

Records both sides of conversation along with the number dialed

Records name and number of callers (requires Caller ID service)

**PC Telephone Recorder \$119**

Use your PC to record phone calls. Windows 95, Sound blaster

compatible sound card 486 or higher PC required

**Phone Tap detector \$159**

Protect your phone against phone taps, eaves droppers and RF bugs.

**Mini Bug Detector up to 2Ghz \$119**

Detects RF "bugs", Video Transmitters and wireless microphones from

5Mhz to 2 GHz. LED Bargraph and Audible alarm

VISA • MC • Money Orders • US & Canada Only

NO CHECKS • NO COD • Add \$6.95 S/H

[www.mscelectronics.com](http://www.mscelectronics.com)

**MSC Electronics**

PO BOX 461 Jessup, MD 20794

(301) 497-1600

FAX (301) 497-1925



## Smart Cards in BASIC

PROGRAM SMART CARDS IN BASIC!

Complete system! Program your own smart

card applications in easy to use BASIC!

**Smart Card Tool Kit \$79.00**



Security Systems, Time Cards, Emulation  
Access Control for Home, Office, Auto  
Computers, Robotics Programming  
Interface with any application!

**Tool Kit comes complete with:**

- CyberMouse SmartCard Reader/Writer
- Developer Software Package
- Documentation on CD-ROM
- Technical manual in printed form
- 3 Blank Smart Cards Ready to Program

VISA • MasterCard • American Express

To Order Call 1-800-773-6698

Send Money orders to: Worldwyde.com,

33523 Eight Mile Rd #A3-261, Livonia, MI 48152

Visit us online <http://www.worldwyde.com>

# TrailBlazer™

## wireless joystick



- Omni-directional wireless joystick
- 20 feet Operating range
- Integrated wireless mouse controls

**\$49.95 ONLY**

45645 Northport Loop East, Fremont, CA 94538, USA  
 Tel: (510) 623 8832, Fax: (510) 623 8849  
 Email: sales@rfddevices.com  
 Website: www.rfddevices.com

ULTIMA ASSOCIATES

New-Old-Stock, Tubes, Parts, Supplies, Speakers, Books, Transformers, Grill Cloth

2221 S. Maple Ave  
 Tempe AZ, 85283  
 ph. (480) 820 5411  
 fax (480) 820 4643  
 fax (800) 706 6789

www.tubesandmore.com

ANTIQUE ELECTRONIC SUPPLY

XICON JENSEN

Call Today And **SAVE!**

# Unbeatable PRICES!

## CABLE TV

### DESCRAMBLERS CONVERTERS • FILTERS VIDEO STABILIZERS

**FREE** ➤ 30 Day Trial  
**FREE** ➤ Product Catalog  
**FREE** ➤ 1 Year Warranty

**100% MONEY BACK GUARANTEE**



Let us point you in the right direction ...

# Arrow Technologies

Omaha, Nebraska

TOLL FREE  
**888-554-ARROW**  
 888-554-2776


## World's Smallest 68HC11 Microcontroller Module!

**NEW!**

**Applications:**

- telemetry
- microrobotics
- smart toys
- animatronics
- model railroads
- automate your home
- many others!


# MicroStamp11™

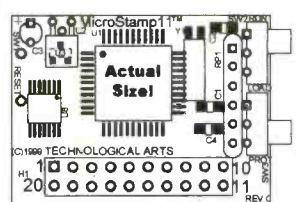

- tiny 1-inch x 1.4-inch 68HC11 module
- 5V regulator, 8MHz crystal
- choice of 8K or 32K EEPROM
- plugs into your breadboard like a DIP
- SCI, SPI, OCS, ICs, timers, & more
- all 14 I/O lines and 2 interrupts brought out to versatile 20-pin connector
- easy code-loading with Docking Module
- Starter Packages: \*  
 with 8K EEPROM (#MS11SP8K).....\$49  
 with 32K EEPROM (#MS11SP32K).....\$60  
 • additional modules from \$34 each

\* includes MicroStamp11, documentation, PC software, serial cable & Docking Module

# MicroGore-11™

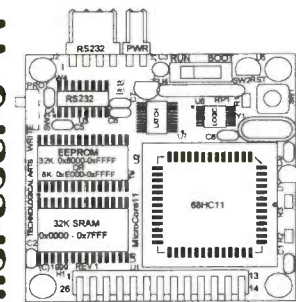


- tiny 2-inch x 2-inch 68HC11 module
- 12 inputs/outputs plus 8 analog inputs
- RS232, 5V regulator, 8MHz crystal
- 32K SRAM plus 8K or 32K EEPROM
- plugs into your breadboard like a DIP
- simple program loading from any PC
- motor driver & accessories available
- ideal for MicroMouse robot competitions

8K Starter Package #MC11SP8K.....\$75  
 32K Starter Package #MC11SP32K.....\$89

## Technological Arts

Many other modules & accessories available. Visit our website at:  
[www.technologicalarts.com](http://www.technologicalarts.com)  
[sales@technologicalarts.com](mailto:sales@technologicalarts.com)  
**Phone: (416) 963-8996**  
**Fax: (416) 963-9179**  
 Add \$5 shipping & handling within Canada & USA  
 Visa • MasterCard • Discover • Amex

## Smart Battery Charger



FOR GEL-CELLS or LEAD ACID BATTERIES.

Features: Precision temperature tracking voltage reference & three mode charging sequence. Standard kit is for 12V @ 1/2 or 1 Amp, user selectable. Can be connected to the battery indefinitely, will not overcharge. Weighs 2 pounds and measures 4"W x 5 1/2"D x 2 1/2"H. Finished enclosure included in kit.

**Complete Kit Only ..... \$59.95**  
**Assembled & Tested ..... \$79.95**  
 CA residents add 7.75% sales tax. S&H: \$6.50 (insured)  
 Foreign orders add 20%. For more info or price list, send legal size SASE (55¢) to:

**A & A Engineering**  
 2521 W. La Palma #K • Anaheim, CA 92801  
 (714) 952-2114 • FAX: (714) 952-3280

## FCC License Preparation

### RADIOTELEPHONE LICENSE

Electronics Tech, Avionics, Marine & Radar  
 Homestudy—Fast-Easy & inexpensive.  
 Manuals-Audio-Video-podisks-Q&As  
**Guarantee Pass-see at www.wptfcc.com**  
 Details-800-800-7555. WPT Publications  
 4701 NE 47ST, Vancouver, WA, 98661

# BUGGED??

Eavesdropping is unbelievably widespread! Electronic Devices with amazing capabilities can be monitoring your telephone and room conversations RIGHT NOW! Are you sure you're safe? **FREE CATALOG** tells you fast! Includes Free Bonus details on fantastic opportunities now open in Counter-Surveillance field. Exciting, immensely interesting and EXTREMELY profitable (up to \$250/hr) full/part-time income. Call Now! **1-800-732-5000**

## PC BOARDS

Low Cost, Precision-Made PC Boards  
 From Your Gerber/NC Drill Files

Put your CAD program to work for you!

**PCB Milling**

- Milling
- Drilling
- Routing

[www.pcbmilling.com](http://www.pcbmilling.com) FAX: (703) 818-0071

## SINGERS! REMOVE VOCALS



(Unlimited, Low Cost, Instantly Available Background Music from Original Standard Recordings! Does Everything Karaoke does... Better and gives you the Thompson Vocal Eliminator Free Brochure & Demo Tape. LT Sound Dept PE 7988 LT Parkway, Lithonia, GA 30058 Internet: <http://www.LTSound.com> 24 Hour Demo/Info Request Line (770)482-2485 • Ext 49 When You Want Something Better Than Karaoke!

## CABLE TV BOXES



(WE'LL BEAT ANY PRICE!)  
 30 DAY TRIAL\* 1YR. WRNTY. \*FREE CATALOG QTY. DISCOUNTS \*DEALERS WELCOME!

# 1-800-785-1145

HABLAMOS ESPANOL

VISA MasterCard Discover C.O.D.

## PRIVATE CABLE SYSTEMS



# AVEN

®

## Delivering Performance With Value

e-mail: info@aventools.com • website: www.aventools.com

### MICROSCOPES

**System 703**  
Stereo Inspection Microscope  
Part #26.703

**Price \$270.00**

- Adjustable interpupillary distance between 2.5" (55mm) and 3/4" (75mm)
- Slide mount objectives for rapid magnification change
- Provides a long working distance of 6" at 10x magnification
- Built-in illuminator with articulating arm allows infinite positioning
- Weighted stand with 9" arm is fully adjustable
- Magnification 5x, 10x, and 20x
- 5 year limited warranty



**System 707**  
Deluxe Stereo Microscope  
Part #26.707

**Price \$266.00**

- Selectable 20x or 40x magnification
- Bottom transmitted and overhead illuminators
- Rotary turret mounted with posture click stop for easy power change
- Precision rack and pinion focus
- 45 degree inclined eye tubes
- Working distance 3.15" at 20x
- Incandescent (12v/10w) and Halogen (12v/10w) lights



### CABLETESTERS

**Multi-Network Cable Tester**  
Part #25.102

**Price \$94.50**

- Quickly tests by auto scanning
- Suitable for thin ethernet (BNC) /10 Base T, (UTP/STP) /356A /TIA 568A /TIA-568B /token ring
- Use attached remot terminator to test cable before or after the cables are installed. Also allows you to test the ground of shielded twisted pair cable.



**Multi-Modular Cable Tester**  
Part #25.022

**Price \$76.82**

- Quickly test by auto scanning modular cables USOC4/USOC6/USOC8 terminating with RJ45, RJ12 and RJ11 modular plug
- Comes with remote terminator, allows you to test installed cables.



### TOOLKITS



**22 PC Aven Personal Computer Tool Kit**  
Part #15.014

**Price \$75.00**



**22 PC Aven Basic Electronic Tool Kit**  
Part #15.019

**Price \$56.60**



**73 PC Aven Master Electronic Tool Kit**  
Part #15.018


**Price \$234.89**

- Includes super drill set
- Aluminum Case



**47 PC Aven Premier Compact Technicians Kit**  
Part #15.004

**Price \$132.83**

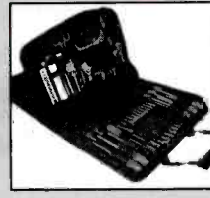

**88 PC Premier Field Service Kit**  
Part #15.006


**Price \$244.90**

- Comprehensive assortment of tools for servicing electronics
- Double-sided case



**Professional Multimeter**  
Part #25.015

**Price \$35.75**

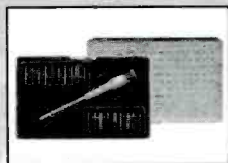

**20 PC Precision Screwdriver Set With Interchangeable Blades**  
Part #13.714

**Price \$15.64**

This useful set contains 19 assorted Slotted/Phillip/Star/Hex/Ball point/Blades. Special quick release designed, make blade changes quick and easy



**Digital Soldering Station**  
Part #17.510

**Price \$132.65**

- Ceramic heater unit for quick start
- Temperature adjustment: 160-480 celcius
- Six different tip sizes available as options
- Perfect for most soldering applications including SMD
- ESD Safe



**Perfectly Balanced Fluorescent Lighting With A Precision 3 Diopter Magnifier Lens**  
Part #26.501

**Price \$77.90**

- 45 inch extension arm
- The shade with handle lets you bring the light where you want
- 3 diopter lens included
- Supplied with 22 watt circline tube
- Color: Ivory
- All metal construction

For your nearest distributor call: #1-800-624-8170  
Fax: #1-734-973-0097 • e-mail: info@aventools.com



Visa/Mastercard Accepted

CIRCLE 235 ON FREE INFORMATION CARD

# spyoutlet.com

## Countersurveillance - Electronic Devices

Purchase your video cameras from  
one of the largest importers in the U.S.

- NEW Waterproof Bullet Cameras • Spy Pinhole Cameras starting at \$79<sup>00</sup> • Wireless Video
- Voice Changer • 3 Hour Micro Recorder • Shotgun Mic • Locksmithing • Bug & Phone Tap Detectors
- Phone Call Register • UV Pens & Powder
- Realtime Telephone Recording Systems:  
12 Hour \$125<sup>00</sup>, 15 Hour \$149<sup>00</sup>
- GPS Vehicle Tracking System (nationwide)  
And much more

www.spyoutlet.com

Printed Catalog send \$5<sup>00</sup>

# SPY OUTLET

2468 Niagara Falls Blvd., Tonawanda NY 14150  
(716) 695-8660 fax (716) 695-7380

## PROGRAMMERS OVER 50 MODELS

ADVANTECH EETOOLS NEEDHAMS DATA I/O ICE TECHNOLOGY HILO SYSTEM GENERAL CHROMA MODULAR CIRCUIT TECHNOLOGY XELTEK



CALL ADVANTECH LABTOOL 629 ICE TECH MICRO/IV 650 EETOOLS ALLMAX + 409 EETOOLS MEGAMAX 509 EETOOLS MEGAMAX4 369 XELTEK SUPERPRO II 409 XELTEK SUPERPRO II P 249 XELTEK SUPERPRO L 165 XELTEK ROMMASTER II 479 MOD-MCT-EMUPA 739 STAG ORBIT-32

599 EETOOLS SIMMAX 795 CHROMA SIMM/SIP 359 MOD-MCT-EMUPA/R 279 MOD-MCT-EMUP/R 49 EPROM 1G TO 512K 69 EPROM 1G TO 1MEG 99 EPROM 4G TO 1MEG 199 EPROM 16G TO 1MEG 89 EPROM 1G TO 8MEG 129 EPROM 4G TO 8MEG 250 EPROM 8G TO 8MEG



## General Device Instruments

Sales 916-393-1655 Fax 916-393-4949 BBS 983-1234  
Web www.generaldevice.com E-Mail icdevice@best.com

## Don't lose sight of Glaucoma.



NATIONAL EYE HEALTH EDUCATION PROGRAM

2539 W. 237th Street, Bldg. F, Torrance, CA 90505  
Order desk only: USA: (800) 872-8878 CA: (800) 223-9977  
LA. & Technical Info: (310) 784-5488 Fax: (310) 784-7590  
http://www.digisys.net/timeline

## TIMELINE INC.

Over 14 years and 32,000 customers and still growing

Minimum Order: \$20.00. Minimum shipping and handling charge \$5.00. We accept cashiers checks, MC or VISA. No personal checks or COD's. CA residents add 8.25% sales tax. We are not responsible for typographical errors. All merchandise subject to prior sale. Phone orders welcome. Foreign orders require special handling. Prices subject to change without notice. 20% restocking fee for returned orders.

### LIQUID CRYSTAL DISPLAYS

**240x64 dot LCD with built-in controller.**  
AND 4021ST-EO. Unit is EL back-lit. \$59.<sup>00</sup> or 2 for \$109.<sup>00</sup> or OPTREX. DMF5005 (non back-lit) \$49.<sup>00</sup> or 2 for \$89.<sup>00</sup>

20 character x 8 line 7/8L x 2 3/4" The built-in controller allows you to do text and graphics.

Alphanumeric—parallel interface			
16x1	\$6.00	20x2	\$8.00
16x1 (lg char)	\$8.00	20x4	\$8.00
16x2	\$6.00	20x4 (lg char)	\$10.00
16x2 (lg char)	\$10.00	24x2	\$8.00
16x4	\$12.00	32x4	\$10.00
		40x1	\$8.00
		40x2	\$20.00
		40x4	\$20.00
		4x2	\$5.00

5V power required • Built-in C-MOS LCD driver & controller • Easy "microprocessor" interface • 98 ASCII character generator • Certain models are backlit, call for more info.

Graphics and alphanumeric—serial interface			
size	Mfr.	price	size
640x480 (backlit)	Epson	\$20.00	480x128
640x400 (backlit)	Panasonic	\$15.00	256x128
640x200	Toshiba	\$15.00	240x128 (backlit)
480x128 (backlit)	ALPS	\$10.00	240x64
			160x128
			Optrex
			Hitachi
			Epson
			Optrex
			Epson
			Optrex

**6" VGA LCD 640X480, Sanyo LMDK55-22 \$19<sup>00</sup>**

### MONITORS

#### Non-Enclosed TTL

Comes with pinout. 12V at 1.4 Amp input • Horizontal frequency 15KHz. • Ability to do 40 and 80 column.  
**5 inch Amber \$19.00 • 7 inch Amber \$19.00**  
**9 inch Amber or Green \$19.00**

**5" COLOR MONITOR \$29.<sup>00</sup>**  
• Flat Faceplate • 320 x 200 Dot Resolution • CGA & Hercules Compatible  
• 12 VDC Operation • 15.75 KHz Horiz. Freq. • 60 Hz Vert. Sync. Freq.  
• Open Frame Construction • Standard Interface Connector • Degaussing Coil included • Mfr. Samtron

2 for \$49<sup>00</sup>

**9" COLOR SVGA MONITOR \$169.<sup>00</sup>** Fully Enclosed - Tilt and swivel type.

### POS & BAR CODE

#### MAGNETIC CARD READER \$19.<sup>00</sup>

Includes: • 20 character dot matrix display with full alpha-numeric capability • keypad with full alpha-numeric entry • separate 7.5 VDC/0.5 Amp power supply • standard telephone interface extension cord • lithium battery and flat-cone speaker.

HP bar code wand (HBCS 2300) \$19.00

### HACKER CORNER

#### Rockwell "Jupiter" GPS Receiver \$69<sup>00</sup>

Miniature (2.75" x 1.5" x .25") 12 channel receiver engine. Supports NMEA 0183 and binary protocols. Supports DGPS input in both protocols. Compatible with active and passive antennas. "Keep-Alive" reduced power capability. Standard 2mm 2x10 interface connector. Complete manual and interface documentation available. Compatible with most laptop software using NMEA interface. Suitable for wide range of GPS applications including: Handheld GPS, Automotive / Marine / Aviation Applications, Amateur APRS and Packet.

#### EMBEDDED 486 COMPUTER \$79.<sup>00</sup>

Complete enhanced Intel 486SX-33 based computer in ultra small (9-7/8" x 6-5/8" x 3-1/8") case. Ideal for embedded operations or as a second computer. Features include: • One 16 bit ISA slot • 3 serial ports plus dedicated printer port • Parallel optical coupled adapter port • Built in IBM PC/AT keyboard port • On board VGA video and port • Uses standard SIMM up to 32 MB • BIOS is PC/AT compatible

Unit has a backup Ni-Cd battery system in case of power failure (5 min. backup time) and lockable front cover to prevent floppy drive access. Mounting / interface provisions for standard 3.5" laptop floppy and 2.5 inch hard drives. Comes with very comprehensive manual.

#### SONY Miniature Color LCD Display \$29<sup>00</sup>

1.8cm (0.7 inch) unit LCX009AKB 827H x 228V \$29<sup>00</sup>

#### CELL SITE TRANSCIVER \$29<sup>00</sup> 2 for \$49<sup>00</sup>

These synthesizers were designed for operation in an AMPS (Advanced Mobile Phone Service) cell site. The 20 MHz bandwidth of the transceiver allows it to operate on all 666 channels allocated. The transmit channels are 870.030-889.980 MHz with the receive channels 45 MHz below those frequencies. A digital synthesizer is utilized to generate the selected frequency. Each unit contains two independent receivers to demodulate voice and data with a Receive Signal Strength Indicator (RSSI) circuit to select the one with the best signal strength. The transmitter provides a 1.5 watt modulated signal to drive an external power amplifier. Channel selection is accomplished with a 10 bit binary input via a connector on the back panel. Other interface requirements for operation are 26 VDC (unregulated) and an 18.990 MHz reference frequency for the digital synthesizer. The units contain independent boards for receivers, exciter, synthesizer, tunable front end, and interface assembly (which includes power supplies and voltage-controlled oscillator). Service manual, schematics and circuit descriptions included.

#### 4 INCH LCD MONITOR \$49.<sup>00</sup>

Compact (4.4" x 3.8" x 1.4") TFT active matrix LCD color monitor including fluorescent backlight. Analog RGB and composite sync input with switchable horizontal / vertical viewing. Low power consumption and long life backlight make it ideal for security and door phone use. Single 8 VDC supply and good resolution allow mobile operations or use with laptops. Standard ribbon cable - Molex connector interface. Complete specifications included.

#### NTSC COMPOSITE 4" LCD MONITOR \$69.<sup>00</sup>


CIRCLE 242 ON FREE INFORMATION CARD

# AMAZING DEVICES
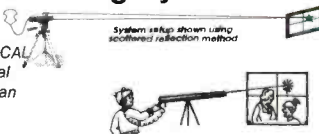
## Laser Window Bounce Listening System

Powerful listening system, yet simple in operation.


You shine a LASER at a window and intercept the reflected beam with our ultra-sensitive filtered OPTICAL RECEIVER. Vibrations on the window from internal sounds and voices are now clearly heard. Range can be up to several hundred meters depending on the output power of the laser and optics used.



- LWB9 Plans and all Data for 3 Laser Window Bounce Systems.....\$20.00
- LWB6K Kit of Complete 100' System with Visible Laser for Demo/Science Project .....\$129.95
- LLR30 Optical RECEIVER with voice filter.....\$99.95
- LLR3K Kit of Optical Receiver.....\$69.95
- LLR40 Higher performance with low noise preamp, basic optics and deluxe headsets.....\$199.95
- CWL10 10 mw ClassIIIB Invisible IR LASER for 500'.....\$199.95
- CWL1K Kit of LASER.....\$149.95
- LM650P5 5 mw ClassIIIA Visible Red Laser Module for up to 100'.....\$19.95
- LM650P10 10 mw ClassIIIB Visible Red Laser Module for up to 200'.....\$69.95
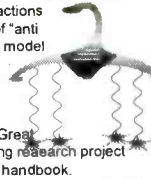
## Gravity Motor

Electrical charge reactions produce the effect of "anti gravity." You build a model craft from simple parts and levitate it with our ion power source. Battery or 115vac operation. Great science or fascinating research project includes our gravity handbook.



- GRA3 Plans/Book.....\$20.00
- GRA3K Power Source Kit.....\$99.95
- GRA30 Assembled Above.....\$149.95

## TAKE CONTROL Using Electronic Hypnosis

Electronic circuitry induces hypnotic as well as ALPHA relaxed mind states. Place subjects under your control.



- HYP2 Plans.....\$10.00
- HYP2K Kit/Plans.....\$49.95
- HYP20 Ready to Use.....\$69.95
- MIND2 Plans for Mind Control.....\$15.00
- MIND2K Kit/Plans.....\$49.95
- MIND20 Ready to Use.....\$79.95

## Thermagnetic Pulser™

Complex Magnetic waves are claimed to produce many health benefits. Board level experimental device is sold for research purposes only.



- THMAG10 Lab Assembled.....\$24.95

## Cybernetic Ear!

Provides that "extra edge" for many listening applications. Enhances 3 to 4x of normal.



- CYBEREAR.....\$19.95

## Mini TESLA Coil

Lights up a 4' fluorescent tube-all without any contact!! Yet only 3" tall!



- MTC1K Kit/Plans.....\$19.95
- MTC10 Assembled.....\$34.95

## Telephone Line Grabber Room Listener Controller and Call Diverter

Listen to your premises. Break in to calls Control household appliances. Remote dial long distance calls-from anywhere!!



- TELCON4 Plans.....\$10.00
- TELCON4K Kit/Plans.....\$129.95
- TELCON40 Ready to Us.....\$169.95

## Tesla Coil

Produces 30" Sparks

Create a spectacular display of nature own lightning. Many amazing experiments possible. See in action on our web site!!



- BTC4 Plans.....\$20.00
- BTC4K kit.....\$799.95
- BTC40 Ready to use.....\$999.95
- Smaller Version (8-10" Sparks)
- BTC3 Plans.....\$15.00
- BTC3K Kit.....\$349.95
- BTC30 Ready to Use.....\$449.95

## Pain Field Pistol

Caution! Do not aim at people!

Blast out rodents with high power ultrasonics. Handheld and battery operated with all controls. Rental units available.



- PPP1 Plans.....\$8.00
- PPP1K Kit/Plans.....\$49.95
- PPP10 Ready to Use.....\$79.95

## Amazing Gravitron

Remarkable true levitation without any tethering or external sources of energy. Winning science project. Includes self starter



- GRV10 - Anti Gravity Top.....\$39.95
- GRV30 - Super Levitator.....\$49.95

## Hover Board

28 pages of data related to the most revolutionary advance in transportation. Cutting edge R&D



- HOVER Plans and Data.....\$25.00

## Transistorized TESLA Coil

Amazing and bizarre effects turn a normal light bulb into a spectacular plasma display!! With adjustable frequency control. Safe 12vdc input



- TCL5 Plans.....\$8.00
- TCL5K Kit/Plans.....\$59.95
- TCL50 Assembled and Tested.....\$99.95

## Attention! High Voltage Modules

Battery powered for hovercraft, plasma guns, anti gravity, force fields, pyrotech




- MIMIMAX4 4KV.....\$19.95
- MINIMAX3 3KV.....\$17.95
- MINIMAX2 2KV.....\$14.95
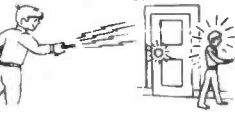
## Ion Ray Guns

Star Wars Technology Directs Energy

Star Wars Technology Demonstrates Weapons Potential, Force Fields, IonMotors, Antigravity etc. Projects electric shocks without contact! Conduct many weird and bizarre experiments. Handheld battery operated and easy to operate.



- IOG719 Plans.....\$10.00
- IOG7K Kit/Plans.....\$99.95
- IOG70 Assembled/Tested.....\$149.95
- Higher Powered Device
- IOG9K Kit/Plans.....\$129.95
- IOG90 Assembled/Tested.....\$199.95

## Semi-Cond Burning Lasers

10mw to 2 Watts of continuous output!! Use for directed beam of heat. illumination source for night vision, laser window bounce IR driver for ultra-bright green lasers.




- CWL5K Kit/Plans minus diode.....\$199.95
- CWL50 Assembled minus diode.....\$299.95
- LD34 CW 3/4 W 980nm diode.....\$249.95
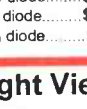
## Nightstar Night Viewer

Sees in total darkness


- 35000x Light Gain
- Over 100 yds Recognition
- Built in IR Illuminator
- 20 degree Field of View
- 20 Hours Battery Life
- Spectral Response 810-840 nm.



- NSTAR10 - Ready to Use.....\$239.95
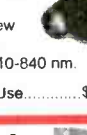
## Jacobs Ladder

Pyrotechnical traveling fiery plasma expands over 3" before evaporating into space. Solid state circuitry with adjustable arc control. 115/230 volt operation. Uses safe high frequency energy.



- JACK1 Plans.....\$8.00
- JACK1K Supply, Mtg Blks, Ladders.....\$149.95
- JACK10 Ready to Use.....\$249.95

## MI FM Voice Transmitter

Crystal clear performance. Many applications. Easy to assemble



- FMV1K Parts and plans.....\$39.95

## 6 Easy FM Xmtr Projects!


- 1 Super Sensitive Ultra Clear 1 Mile+ Voice Transmitter.
- 2 1 Mile+ Telephone Transmitter.
- 3 Line Powered Phone Transmitter Never Needs Batteries!!
- 4 Tracking/Homing Beacon Beeping Transmitter
- 5 Video/Audio Rebroadcaster 1 Mi.
- 6 TV/FM Radio Disrupter. Neat Prank! Discretion Required

Includes Hints Using Wireless Devices.

- COMBOX Parts Above 6 Projects.....\$49.95
- COMBOP Plans Above 6 Projects.....\$10.00
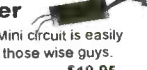
## Shock Force Field Vehicle Object Electrifier

Hand shock balls,wands. Mini circuit is easily hidden. Great payback for those wise guys.



- SHK1K Kit/plan.....\$19.95

## Mind&Brain Controllers

Incredible device Turbo charges memory, Boost mental powers, Controls stress, Speeds up healing processes and Uncover hidden potentials. High quality unit with many features.



- BWPLUS-APOLLO Ready to use.....\$189.95
- BWII- EINSTEIN Lower cost unit.....\$129.95

## Burning Cutting Lasers

Current and Future Weapons System

- We Stock Parts!
- LC3 Plans Poor Mans CO<sub>2</sub> System.....\$15.00
- LC7 Plans Lab CO<sub>2</sub> System 30W+.....\$20.00
- LAGUN2 Plans Nd,Yag, Ruby 6Kw.....\$20.00
- All Three Plans for only.....\$25.00!!

## PLASMA FIRE SABER

Patented Moving Light Concept Defies All Logic as it Appears to Evaporate into Space!! Duplicate the STAR WARS effect

Replaceable Blades, Overide Switch Interactive Sound Module Available on Request

- PFS15K-"C" Kit of 15" Active Length.....\$24.95
- SAB34K "C" Kit of 24" Active Length.....\$39.95
- SAB46K "C" Kit of 36" Active Length.....\$99.95
- \*Please add \$10.00 for special handling



Information Unlimited PO Box 716 Amherst N.H. U.S.A. 03031  
 1 800 221 1705 Orders/Catalogs Only! Fax 1 603 672 5406 Information 1 603 673 4730 Free Catalog on Request  
 Pay by MC,VISA,Cash, Check, MO, COD. Add \$5.00 S&H plus \$5.00 if COD. Overseas Contact for Proforma

CIRCLE 225 ON FREE INFORMATION CARD

# VISION ELECTRONICS



- No Rolls/Jitters/Flickers/Fading
- Works on all TVs, VCRs, Beta, & Cable
- Gold Video Connectors & Cables Included
- 1 Year Warranty
- Money Back Guarantee

**FREE CATALOG!**



## COPY RENTAL TAPES WITH OUR VIDEO STABILIZER

**1-800-562-2252**

2609 S. 156th Circle • Omaha, NE 68130  
www.modernelectronics.com



### EZ-EP DEVICE PROGRAMMER - \$169.95

Check Web!! -- [www.m2l.com](http://www.m2l.com)

**Fast** - Programs 27C010 in 23 seconds

**Portable** - Connects to PC Parallel Port

**Versatile** - Programs 2716-080 plus EE and Flash (28F,29C) to 32 pins

**Inexpensive** - Best for less than \$200

- Correct implementation of manufacturer algorithms for fast, reliable programming.
- Easy to use menu based software has binary editor, read, verify, copy, etc. Free updates via bbs or web page.
- Full over current detection on all device power supplies protects against bad chips and reverse insertion.
- Broad support for additional devices using adapters listed below.


#### Available Adapters

EP-PIC (16C5x, 61.62x, 71, 84)	\$49.95
EP-PIC64 (62-5, 72-4)	\$39.95
EP-PIC12 (12C50x)	\$39.95
EP-PIC17 (17C4x)	\$49.95
EP-51 (8751 C51)	\$39.95
EP-11E (68HC11 E/A)	\$59.95
EP-11D (68HC711D3)	\$39.95
EP-16 (16bit 40pin EPROMs)	\$49.95
EP-Z8 (Z86E02, 3, 4, 6, 7, 8)	\$39.95
EP-SEE2 (93x, 24x, 25x, 85x)	\$39.95
EP-750 (87C750, 1, 2)	\$59.95
EP-PEEL (ICT22v10, 18v8)	\$59.95
EP-1051 (89C1051, 2051)	\$39.95
EP-PLCC (PLCC EPROMs)	\$49.95
EP-SOIC (SOIC EPROMs)	\$49.95
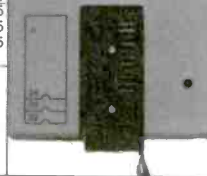
#### M<sup>2</sup>L Electronics

970/259-0555 Fax: 970/259-0777  
250 CR 218, Durango, CO 81301  
CO orders add 7% sales tax.  
<http://www.m2l.com>

**EZ-EP**  
M<sup>2</sup>L ELECTRONICS  
Los Angeles, California



# NetSurf<sup>PRO</sup>

wireless keyboard™

100 feet range

Power indicator



Int.egrated Touchpad

104-key functionality

**\$99**  
only

- 900MHz Wireless RF Technology
- No Line of Sight Requirement
- Encrypted Data Transmission
- Long Battery Life

Ultima Associates, Inc. 45445 Northport Loop East Fremont, CA 94539  
Tel: 510-423-8832 • Fax: 510-423-8849 • Email: Sales@RFDevices.com • URL: www.RFDevices.com

### Low Cost PICmicro Tools

**New! PIC-XI  
Experimenter/  
Lab Board**  
\$49.95 to \$199.95



**EPIC Pocket PICmicro  
Programmer - \$59.95**

Program PICmicros in BASIC!  
**PicBasic Compiler - \$99.95**  
**PicBasic Pro Compiler - \$249.95**

PICProto Boards make  
prototyping with PICmicros  
easy - \$8.95 to \$19.95



**microEngineering Labs, Inc.**

Box 7532 Colorado Springs CO 80933  
(719) 520-5323 fax (719) 520-1867  
<http://www.melabs.com>

### Data Acquisition and Control

The ADR series of interfaces allow control of analog, digital and relay I/O via RS232 or RS485. Visit the web site for specs, applications and programs in VB, C, BASIC etc. (705) 671-2652

[www.ontrak.net](http://www.ontrak.net)

**Ontrak Control Systems Inc.**

### Do You Repair Electronics?

- Repair Databases for TV, VCR, Monitor, UL Audio, FCC, and more.
- Over 76,000 records
- Private user forums
- Live on-line chat rooms

**RepairWorld.com**

Electronics Corp. 11 Federal Sq. Franklin, OH 45324 (937) 878-9878



**One size fits all!**  
**\$333**  
COMPLETE KIT

## CONITEC

### Best for HIGH PERFORMANCE fieldwork

#### One Pocket Sized Tool Does it All

A universal multi-programmer combining performance, flexibility and room for expansion. Optimal for use in the field. Small enough to fit in your pocket, it will output to a wide array of devices.

#### Fast, Versatile Field Programmer

Programs 8-bit and 16-bit EPROMs, EEPROMs, Zero Power RAM's, Flash, Serial EEPROMs / GAL, PALCE, ATF7xxx, 89xxx, PIC12/16/17Cxx / All DIL devices without adapter / Lightning fast parallel data transfer (e.g. 27C512 read/compare 2 sec!)

#### With Expanding Output Capability

Independent power supply with rechargeable battery / Uses PC printer port / Hex, JEDEC, and binary file formats / Hex & fuse-map buffer editor / Split & shuffle for 8-bit, 16-bit and 32-bit targets / Runs under Win3.1, 95, 98, NT / "Remote Control" by DDE scripts / Designed for the future with flexible pin driver technology / New devices added every month / Device list, demo software and lifetime free updates from our website.

GALEP III / cable, batt. and recharger...\$333.00  
PLCC adapt. / 8-bit EPROMs / 16-bit EPROMs / GALs each \$149.00

**GALEP-III**  
Pocket Multiprogrammer

ONLINE ORDERS: [WWW.CONITEC.COM](http://WWW.CONITEC.COM)

CONITEC DATASYSTEMS • 1951 4th Avenue, Suite 301 • San Diego, CA 92101 • Tel: 619-702-4420

### HOT NEW PRODUCTS!!!

**Phone and Internet Voice Changer** - This device is new to the market and provides realistic sounding voices. It allows you to interface directly to your phone jack, or computer via patch cord and mic. Intro price \$129.95



**Phone Manager - Reverse Caller ID.** Now you can keep track of outgoing numbers. Records length, time and date of call. Keep track of the children, the wife, or the phone company. Easy hookup via phone jack. \$79.95



[www.electronickits.com](http://www.electronickits.com) - Over 200 Electronic Gadgets  
Carl's Electronics Inc. [sales@electronickits.com](mailto:sales@electronickits.com)

# ALL ELECTRONICS

C O R P O R A T I O N

QUALITY Parts  
FAST Shipping  
DISCOUNT Pricing



CALL, WRITE, FAX  
or E-MAIL For A  
**Free 96 Page**  
CATALOG.  
Outside the U.S.A.  
send \$3.00 postage.

## 14 Channel FRS Radio

### (Family Radio Service) With CTCSS Subchannels

Fanon / Courier # KF-310. A light-weight, palm-sized FM transceiver. Use it at shopping malls, amusement parks or sports events. Up to a two mile range. Talk with another person who has an FRS radio set to the same frequency as your transceiver. Operates on 14 channels, with 38 CTCSS sub-channels for each channel. Speaker/ microphone jack. Backlit LCD display. Aux. Power jack. Also features VOX voice activation, auto squelch and a power-saver feature which switches on after 8 seconds of inactivity. Operates on 4 AAA alkaline or rechargeable batteries (not included). 1 Year mfg. warranty. FCC approved. **CAT# KF-310**



**\$39<sup>95</sup>** each unit (not per pair)

### Keychain Laser Pointer

2.5" long laser pointer with a keychain and snap-clip. Projects an intense solid red dot up to 500 yards. Perfect for sales meetings, lectures. A great gift item. Includes three LR44 batteries. **CAT # LP-506**



**\$6<sup>50</sup>** each

10 for \$45.00

### Digital On-Timer

Digital timer from Mr. Coffee™. Small modular design, no brand name or logo. Ideal for use in any product that needs to be turned on automatically at a specific time. Operates on 120 Vac. Switch loads up to 10 amps. Can be switched manually. White plastic face. 2.48" X 1.77", with four digit LED clock. Overall size: 2.48" X 2.17" X 1.88" deep behind face. 0.25" qc terminals. Easy to connect and operate. Includes instruction sheet. **CAT# MCT-3**



**\$5<sup>00</sup>** each

## "Ear Bud" Stereo Earphones

Miniature "in-ear" earphones for use with most portable CD, radio and tape players. 3.5 mm stereo phone plug. 32 ohm impedance.



Large Quantity Available

**CAT # HP-6**

**85¢** each

10 for \$7.50  
100 for \$50.00

### Laser Level



Accurate and easy to use for short and long distance leveling. Center the bubble, and anything that intersects the beam is at exactly the same height. Use it to match heights in large rooms or across buildings. Set and align electrical and plumbing fixtures, cabinets and shelves. Rugged, black anodized aluminum housing with pocket clip. Locking push button switch to prevent unintended actuation. Includes two AAA batteries. **CAT # LL-1**

**\$16<sup>95</sup>** each

### 22 UF 450 Vdc



0.63" diameter X 1.6" long axial electrolytic capacitor. **CAT# 22/450VA**

**\$1<sup>25</sup>** each

10 for \$10.00  
100 for \$80.00

### 16 Character X 2 Line LCD with Backlight


Daewoo # 16216L-5-VSO 5 x 7 dot format. 2.56" x 0.54" viewing area. 3.15" x 1.41" module size. LED backlight. Includes hook-up/spec sheet. **CAT# LCD-53**



**\$7<sup>50</sup>** each
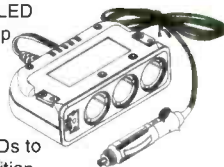
## 3 Outlet Lighter Cord w/ Battery Monitor

Three foot cord with LED lighted, fused, 10 Amp plug at one end and three outlet jacks at other end. Jack assembly has red, yellow and green LEDs to indicate battery condition.



Can be mounted via mounting ears (4.7" centers) or double-sided tape (included). Mounting ears fold out of way if not in use.


**CAT # CLP-44**

**\$3<sup>75</sup>** each

### Ionizer

Seawise Industrial Ltd. Model # SW750. Input: 120 Vac Output: 7.5 KV 60 Hz. The main component in a household ionization unit. 2.2" x 1" x 0.86" thick with a mounting tab that extends 0.75" from the unit. UL recognized. **CAT # SW-750**

**\$4<sup>50</sup>** each

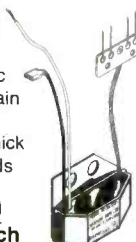

### Blue & White Ultrabrights

BLUE / water clear 1200 mcd 45 degree viewing angle.

**\$3<sup>75</sup>** each

**CAT # LED-58**  
10 for \$30.00


WHITE / water clear 1100 mcd

**\$4<sup>00</sup>** each

**CAT # LED-48**  
10 for \$35.00
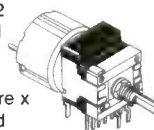
### Motorized Potentiometer Dual 10K Linear Taper

Alps Electric # 726T-10KBX2 Dual 10K linear pot powered by a small reversible 6 Vdc gearhead motor. Pot and motor assembly are 1" square x 1.7" long excluding shaft and bushing. 6 mm flatted shaft is 0.5" long. 9mm threaded bushing. PC pins and mounting tabs for pc board mounting.



**\$4<sup>00</sup>** each

**CAT # MPOT-10K**  
10 for \$35.00

ORDER TOLL FREE **1-800-826-5432**  
Shop ON-LINE **www.allelectronics.com**

MAIL ORDERS TO:  
**ALL ELECTRONICS CORP.**  
P.O. BOX 567 • VAN NUYS, CA 91408-0567

FAX (818) 781-2653 • INFO (818) 904-0524  
E-MAIL **allcorp@allcorp.com**


NO MINIMUM ORDER • All Orders Can Be Charged to Visa, Mastercard, American Express or Discover • Checks and Money Orders Accepted by Mail • Orders Delivered in the State of California must include California State Sales Tax • NO C.O.D. • Shipping and Handling \$5.00 for the 48 Continental United States • ALL OTHERS including Alaska, Hawaii, P.R. and Canada Must Pay Full Shipping • Quantities Limited • Prices Subject to change without notice.

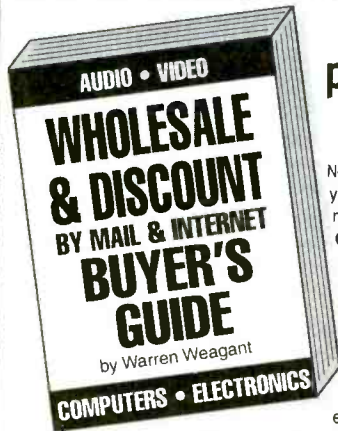**MANUFACTURERS - We Purchase EXCESS INVENTORIES... Call, Write, E-MAIL or Fax YOUR LIST.**



CIRCLE 215 ON FREE INFORMATION CARD

Save up to 90% off list prices on thousands of goods and services!



Why pay retail prices when you don't have to?

No matter what you're looking for, you can get it cheaper with this newly updated for 2000 Buyer's Guide: Audio and Video equipment and materials, Electronic products and surplus, Professional Recording and specialty items, Computers and components, Stereos, CDs, Software, wireless telephone and Communications Equipment and almost anything else you could want.

Here you'll find carefully researched and screened sources that represent the best businesses with the best bargain prices. Plus, you will find unusual companies selling hard-to-find items.

If you're looking for almost anything for yourself, your home or business—chances are you'll find a mail order or internet company listed that sells it at huge wholesale discounts. Company listings include complete address, phone, FAX, Email and Website addresses.

Only  
**\$19.95**  
postpaid



## COMMAND PRODUCTIONS

Post Office Box 2824  
San Francisco, CA 94126  
Call toll free: 1-800-932-4268

## NEW! All 1300 ACTUAL QUESTIONS! FCC Commercial General Radiotelephone Operator License (GROL) Plus Ship Radar

Only **\$18.95** Plus \$4.00 shipping

Compete FCC Element 1, 2 and 8 Question Pools.

Become an FCC licensed

## ELECTRONIC TECHNICIAN

- 347-page Tests-Answers exam Guide covers everything you need to know to get your FCC Commercial Radiotelephone Operator License with Radar Endorsement.
- Newly revised multiple-choice exams cover all word-by-word questions covered on the actual FCC License exam.
- Revised 17th edition has complete information on every commercial radio license examination and how you can qualify...from the publisher specializing in FCC License training since 1969.
- Unconditional **Money Back Guarantee**.



### COMMAND PRODUCTIONS FCC LICENSE TRAINING

Post Office Box 2824 • San Francisco, CA. 94126  
Call Toll Free 1-800-932-4268

CIRCLE 232 ON FREE INFORMATION CARD

## Do Thieves Want Your Computer?

This Year 1.2 Million Desktop Computers Will Be Stolen.  
Protect Your Computer with PC Doberman Security.

Thousands of PCs are equipped with security cards in North America and Europe. PC Doberman is the most comprehensive computer security available. Providing both anti-theft and access control in one package.



- Motion Detection
- Motion Sensitivity Control
- Unauthorized Access Alarm
- Time Lock Access Control
- Anti Password Hacking Alarm
- Minimum Password Length Feature
- Access Control and Disable Mechanism
- Warning or Continuous Motion Alarms at 85 dB
- A Log to keep track of when your PC is used.
- A Real Time Clock

This commercial ISA bus card is easy to install under Windows 3.1, 95 or 98 and DOS. A dozen Windows setup and dialog boxes let you configure the security to suit your needs.

PC Doberman protects your computer at **\$99.95**  
Mention this add and save \$30.00 for only **\$69.95**

For a kit of all parts, PCB, Windows software and build instructions save \$40.00. A great deal at **\$59.95**

Shipping and handling charges of \$6.00 applies on all orders within continental United States and Canada. Elsewhere \$11.00.

Canadians add GST/HST. Ontario residents add PST. All funds in US dollars. Checks or Money Orders accepted.

Microdev 363 Dale Crescent, Waterloo, ON, Canada,  
N2J 3Y6, Tel: 519-746-6819 Fax: 519-746-7292  
sales@microdev.com http://www.microdev.com

## RF Data Modules

### AM Transmitter



- Sub Miniature module
- SAW Controlled
- No adjustable components
- Low current - 2.5mA
- Supply 2.5-12Vdc
- 418MHz or 433MHz
- Range up to 300ft
- CMOS TTL data input
- 7 x 11 x 4mm !
- AM-TX1-xxx .... \$12.60

### AM Receiver



- Compact Hybrid Module
- Very stable
- CMOS/TTL output
- Patented Laser Trimmed
- 5Vdc, 0.8mA (HRR6)
- 2kHz data rate
- Sensitivity -105dBm
- 38 x 12 x 2 mm
- AM-HRR6-xxx... \$16.33

### FM Transceiver



- Only 23 x 33 x 11mm
- Up to 40,000bps data rate
- Up to 450ft. range.
- 5V operation
- 418MHz or 433MHz FM
- 5V CMOS logic interface
- Fast 1mS enable
- Power saving feature
- Carrier Detect output
- BiM-xxx-F ..... \$87.36

### RS232 Transceiver



- 3wire RS232 interface
- 19.2Kbps half duplex
- 418MHz or 433MHz FM
- 7.5-15Vdc, 20mA
- TX/RX Status LED's
- Up to 400ft. range
- 1/4 wave ant. on board
- User data packetizing
- 58 x 40 x 15mm
- CYPHERNET .... \$139.30

### AM Transmitter



- Range up to 250ft.
- SAW controlled stability
- Wide supply range 2-14V
- CMOS/TTL input
- Low current, 4mA typ.
- Up to 4kHz data rate
- Small: 17 x 11mm
- AM-RT5-xxx .... \$12.10



ABACOM  
TECHNOLOGIES

Free Catalog

tel: (416)236 3858  
fax: (416)236 8866  
www.abacom-tech.com  
MasterCard / VISA

**High Performance Auto Ranging DMM** New to our DMM line-up and possibly (probably) the best DMM value you've ever seen! Includes: Analog Bar Graph, Auto-Ranging! Data Hold! Temperature Probe! Frequency Test! Continuity Test! AND MORE!

**ONLY \$29.95**

**NOW IN STOCK!**

**#CSI9903**

**Specifications Accuracy**  
 Vdc: ±1.0% reading +5 digits  
 Vac: ±1.5% reading +8 digits  
 Aac: ±1.2% reading +5 digits  
 Aac: ±1.5% reading +5 digits  
 Resistance: ±1.5% reading +5 digits  
 Frequency: ±3.0% reading +5 digits  
 Temperature: ±1.0% reading +6 digits

**Requires two AAA batteries sold separately.**

Measures:  
 DC Volts: up to 1000V  
 AC Volts: up to 750V  
 AC Amps: up to 20 Amps (AC & DC)  
 Resistance: up to 30M ohm  
 Continuity Check: with audible signal (signal sounds if resistance is less than 20 ohms. Display reads actual resistance).  
 Frequency: (1KHz to 300KHz) displays both digital and bar graph reading.  
 Transistor hFE Test: Display shows approximate hFE value based on test condition of 10uA base current and Vce of approx. 3V.  
 Temperature Test: Measures from 0° to 1832° F (probe supplied!)  
 Diode Test: Tests if diodes are shorted or open  
 Input Impedance: 10Mohm (Vdc/Vac); over 100Mohm on 300 mVdc range

**Removable Hard Drive Rack**  
 For IDE/Ultra DMA Hard Drives

**ONLY \$14.95** any qty.

**#RH-10C-IDE**

Made of ABS 707 fireproof plastic. Use this product to protect sensitive hard drive data, take your hard drive between work and home or even set up different users with their own hard drives that they physically insert every time they use a PC. Other models available from C.S.I. include RH10 series and RH20 series, which are interchangeable within the same interface design (IDE or SCSI). Other Models are Available. See [www.web-tronics.com](http://www.web-tronics.com) under "hard drive and accessories" for more details and pictures.

**Removable Hard Drive Rack with Auto Door and Cooling Fan**

**ONLY \$18.95** any qty.

**#MR-27**

Auto door on the outer frame  
 ABS material of outer frame, High efficiency cooling fan  
 Worldwide patent pulling function handle  
 CE Approved  
 Coating Iron bottom cover  
 For IDE Interface  
 For 1" high 3.5" HDD  
 Not compatible with our RH10 & RH20 series  
 Compatible with our RH17-IDE model.

Details at [www.web-tronics.com](http://www.web-tronics.com)

**2GHz RF Field Strength Analyzer**

**ONLY \$1589**

**#3201**

- Frequency Range: 100KHz to 2,060MHz
- Narrow Band FM (NFM), Wide Band FM (WFM), AM and Single Side Band (SSB) Modulated Signals May Be Measured
- PLL Tuning System for Precise Frequency Measurement and Tuning
- LED Backlight LCD (192x192 dots)
- Built-in Frequency Counter
- Hand-Held and Battery Operated
- All Functions are Menu Selected
- RS232C for PC Interface and Printer

**CTRL - D to bookmark this site**

**www.web-tronics.com**

**Don't forget the dash**

**Circuit Specialists Inc.**

**Easy to Navigate**  
**Includes a Search Engine**  
**That Really Works**  
**New Items Added Constantly**

**In Business Since 1971**

**Mini CCDs (B/W & Color)**

**LOWER PRICES**

Sensational NEW Design for Small Observation Cameras. Smaller and Better!

- Ultra Miniature Design
- Black & White Versions Only 25mm x 25mm
- Color Versions Only 32mm x 32mm
- Available in Standard Lens or Pinhole Lens

All include Pre-Wired Cable Harness for Video & Power  
 12V Regulated Power Supply Required (120mA typical power consumption)  
 0.1 LUX Rating (B/W), 1 LUX (color)  
 CCD Area Image Sensor for Long Camera Life  
 Back Light Compensation Circuit  
 Built-in Electronic Auto Iris Lens

**CCD B&W Board Cameras**

- ASIC CCD Area Image Sensor
- Extremely Low Power Consumption
- 0.5 Lux Min Illumination
- Built-in Electronic Auto Iris for Auto Light Compensation

**LOWER PRICES**

**Detailed Specs on the Web**

VM1030PA-B 30mmx30mmx25mm, Pinhole lens, 12V \$39.00 any qty.  
 VM1030A 30mmx30mmx26mm, Standard lens, 12V \$39.00 any qty.  
 VM1035A 42mmx42mmx25mm, Standard lens, 12V with back light compensation \$49.00 any qty.  
 VMCB21 44mmx38.5mmx28mm, with 6 infra-red LEDs, 12V \$49.00 any qty.  
 VM1036A 32mmx32mmx25mm, Standard lens, 12V, reverse mirror image feature \$49.00 any qty.

**Mini CCDs (B/W & Color)**

**LOWER PRICES**

**Detailed Specs on the Web**

VMCW-H11A 32mmx32mmx30mm, Color CCD with standard lens, pre-wired cabling 12V DC Power \$139.00 / \$129.00 5 or more  
 VMCW-H12A 32mmx32mmx19mm, Color CCD with pinhole lens, pre-wired cabling, 12V DC Power Input \$139.00 / \$129.00 5 or more  
 VMPS-718A 25mmx25mmx30mm, B/W CCD with standard lens, pre-wired cabling, 12V DC Power Input \$59.00 / \$49.00 5 or more  
 VMPS-250A 25mmx25mmx15mm, B/W CCD with pinhole lens, pre-wired cabling, 12V DC Power Input \$59.00 / \$49.00 5 or more  
 VCC-3232 32mmx32mmx30mm, CMOS COLOR, std lens, see web for specs \$79.00 / \$72.00 5 or more

**Bullet CCD Cameras B&W and Color**

**LOWER PRICES**

**Detailed Specs on the Web**

- Smart Rugged Metal Housing
- Extremely Low Power Consumption
- 12 Volt
- CCD Area Image Sensor for Long Camera Life
- Built-in Electronic Auto Iris for Auto Light Compensation
- No Blooming, No Burning
- 0.1 Min Lux Illumination (B&W), 1 Lux Min Lux Illumination (color)

VMBLT1020 B&W, 21mm(D)x55mm(L) \$49.00 any qty.  
 VMBLT1020W B&W Weatherproof, 21mm(D)x58.5mm(L) \$79.00 any qty.  
 VMBLTJC19BW COLOR: Weatherproof, 17mm(D)x88mm(L) \$139.00 any qty.

**COLOR CCD Mini Board Cameras**

**PRICE REDUCTION**

**Detailed Specs on the Web**

- Low Power Consumption
- 1 Lux Illumination
- Internal Synchronization
- 12Volts
- 400 TV Lines
- Built-in Electronic Auto Iris for Auto Light Compensation

VM3010PA 33mmx33mmx18mm, Pinhole lens \$99.00 any qty.  
 VM3011-A 45mmx40mmx24mm, Standard lens, single board \$89.00 any qty.  
 VM3010-A 33mmx33mmx32mm, Standard lens \$99.00 any qty.

**new! Hot Air SMD Rework Station WOW! ONLY \$489**

Similar Systems Cost 100s More!

**ONLY \$489**

**#SR-979**

For technicians, service/repair depots and assembly rework. We also stock a selection of nozzles for QFP, SOP & PLCC devices (see our website for selection details). Hot Air temperature variable from 100°C to 400°C (212°F to 754°F) power consumption: 275w max. Auto cooling feature cools system after shut off to extend service life of heating elements and handle. One year limited warranty from C.S.I. Comes with QFP Nozzle (0.68" x 0.68")

**new! O'Scope Offer ONLY \$299**

**30MHz! ONLY \$299!**

**Industries Best Price!**

See web for specs

**#OSC-1030**

- Dual Channel
- Dual Trace
- Vert Trigger
- 1 Year C.S.I. Warranty!

Manufactured for CSI by a leading O.E.M. manufacturer. See our website for detailed specifications!

**new! 2.4 GHz A/V Sender/Receiver System**

**Now On Sale Order Now**

- Wireless FM transmission of video (color or B/W) and sound (stereo or mono) up to 150 meters (line of sight)
- Directional Antenna Design optimizes performance
- Use with remote cameras or any input (satellite TV, cable etc.) where wireless transmission is desired. View on a TV set.
- Performance through walls varies depending on construction methods etc.
- Each set includes a plug-in power supply for the transmitter & receiver.
- 7 segment LED displays channel (1-4) on receiver & transmitter.

**CSIHTR2400** Includes One Transmitter & One Receiver with Power Supplies \$109.00  
**CSIHTR2400TX** Extra Transmitter/Each Receiver will Monitor up to 4 Transmitters \$89.00

See more detailed specifications at [www.web-tronics.com](http://www.web-tronics.com) in the CCD camera section.

**3000 Series Digital R/O Bench Power Supply**

← Low Cost Single Output ← 3 Amp

**AS LOW AS \$89**

High stability digital read-out bench power supply featuring constant voltage and current outputs. Short-circuit protection and current limiting protection is provided. Highly accurate LED accuracy and stable line regulation make the 3000 series the perfect choice for lab and educational use.

Line Regulation: 2x10<sup>-4</sup> +1ma  
 LED Accuracy: Voltage ±1% +2 digits  
 Current ±1.5% +2 digits  
 Wave Line Noise: ≤1mvrms  
 Dimensions: 291mm x 158mm x 136mm (CSI3003)

**CSI3003: 0-30v/0-3amp Digital R/O Bench PS, 1x10<sup>-4</sup>+5mv Load Regulation \$99.00 5/\$89.00**

**Our Most Sophisticated DMM** We Sold Over 700 Last Year!

with RS-232 Interface & Software, 3-3/4 Digit, 4000 Count, Auto-Ranging with Analog Bar Graph

**NOW ONLY \$129** Reg. \$169

**More Details on our Web Site**

**PROTEK 506**

- K Type Temperature Probe Included
- Pulse Signal for Logic & Audible Test
- Continuity/Diode Test
- Logic Test
- Auto Power OFF/Keep ON Mode
- Fused 20A Input with Warning Beeper
- Data Hold/Run Mode
- Safety Design UL1244 & VDE-0411
- Protective Holster
- Silicon Test Leads

**WIRELESS MOBILE WORKSTATION is a Hackers Bonanza!**  
**Itronix T5000 mobile terminal with 2Meg. PCMCIA Mem card.**



This is a super device we would really like to know more about. Our people are working on it and this is what we know so far: This unit is built like a brick pizzeria. Case is polycarbonate & sealed from rain, dust & drops. It has a 75 key QWERTY keyboard which curiously seems to be mapped one key off. These units were just replaced by a fortune 500 company that was using them in the daily operations. They must require some external input for the correct keyboard mapping. Probably a security measure? The flip up cover holds a transfective Samtron UG24D02 monochrome LCD display that we think is 640 x 240 pixels. Size: 7.3"W x 2.75"H and displays 16 shades of gray also has a white E/L backlight. Each has an Internal Motorola Type RPM4051 Radio Packet Modem with built

in tip up antenna. we believe it operates on the ARDIS or similar network. There is also an RS-232 serial port / bar code wand port & a port for a hand held laser scanner. When powered via the external jack: 10VDC @ up to 800mA. Draws about 175ma after boot. Originally powered by a 7.2V, NICAD pack which has been removed. The battery compartment is external & could easily hold an alternate power source. We believe there is an internal modem as the unit sports an RJ-11 style connector as well tip and ring connections. The 80C552 processor boots MS DOS ROM version 5.00 to an A: > prompt. The screen indicates an internal memory of 640K. A 2meg. PCMCIA memory card is also supplied. Operating temp from -4 to +140F. From there on your own your own. All units are tested for boot up otherwise sold as an experimenters package. **T5100.....\$49ea., or 3 for \$129**

**A VERY COOL COLOR CAMERA, "The ROVING EYE CAM" with Ultra Compact PAN and TILT, AUTO IRIS and AUTO FOCUS to boot!**



Another super quality color conference camera designed as part of a high end system from PictureTel. The unit consists of a camera head attached to a base PC board. The attachment is via a moveable mount. There are two tiny stepper drives which create the pan and tilt motion. The tilt stepper is mounted to the PC board. The pan stepper is unmounted and attaches to the side on your base or enclosure. We assume the camera is controllable via serial commands however we have no info on how to do it. Anyone who can tell us can have some free cameras. Specs: 400 lines @ 1lux, pwr required is 12VDC @ 500mA. size of head is: 5.5" diam. x 3.2"H. The attached PCB is 3W" x 4L" x 1.3"H. Oh, and did we mention it's auto focus and auto

iris too? Composite video output. We think it has 5 video also. Check our web site for further details as they become available. Order now, the price goes up when we get the serial commands. Removed and tested.

**SPECIAL MAY PRICE MINI-R2D2 CAM.....\$149ea. or 2 /\$289, or 5/\$499**

**RESOURCES UN-LTD.**

VISA, MC, AMEX, DISCOVER, COD, ON-LINE  
 ORDER: 800-410-4070 TECH: 603-648-2499  
 FAX: 603-644-7815 E-MAIL sales@resunltd.com  
 \$00 BEDFORD STREET, MANCHESTER, NH 03101

**NEW! LCD COLOR, TFT, ACTIVE MATRIX DISPLAY, Super 5.6" VIEWABLE AREA. Pro System w/Custom Case, 12V gel cell battery, A/V cables & charger.** Finally, exceptional quality & affordable LCD monitor. Perfect general purpose color/B&W monitor. NTSC. Fully compatible with all cameras, camcorders, VCR's etc. Use as a rear view system with any video camera with its built in, mirror image function. Completely enclosed unit. Adj. color, contrast, brightness & volume. Internal stereo speakers! Std. 1/4 x 20 Tripod socket & a tilt down stand for table top. Inputs: audio (L&R) & video on std. 1/8" mini jacks. External 12VDC@600mA on std. barrel connector. 5.6", TFT active matrix LCD, 76.8K Pixels, CCFL backlight, 270cd/m Lumin., 500mW audio out on std. 1/8" jack. 50mV min. std. line level audio in. Size: 6.4"W x 5.25"H x 2.2"D" New, first quality. Pro accessory kit includes: Luggage quality, custom padded case with dual removable straps for shoulder and/or holding at waist level for, hands free viewing. Built into the case is a 12V Gel Cell, rechargeable battery & a complete set of A/V cables. Incl. AC pwr adapter & battery charger. **GM-TFT56,....\$299ea. PRO KIT, GM-ACCYFT...\$45**



**SECURE ON-LINE ORDERING, WWW.RESUNLTD4U.COM**

CIRCLE 246 ON FREE INFORMATION CARD

**CONTROL**  
 RELAYS • LIGHTS • MOTORS  
**MEASURE**  
 TEMPERATURE • PRESSURE • LIGHT LEVELS • HUMIDITY  
**INPUT**  
 SWITCH POSITIONS • THERMOSTATS • LIQUID LEVELS

**MODEL 30 ..... \$79**



- PLUGS INTO PC BUS
- 24 LINES DIGITAL I/O
- 8 CHANNEL, 8 BIT A/D / IN
- 12 BIT COUNTER
- UP TO 14K SMP/SEC

**MODEL 45 ..... \$189**



- RS-232 INTERFACE
- 8 DIGITAL I/O
- 8 ANALOG INPUTS
- 2 ANALOG OUTPUTS
- 2 COUNTERS-24 BIT

**MODEL 100 ..... \$279**



- 12 BIT 100 KHZ A/D
- 4 ANALOG OUTPUTS
- 3 TIMER COUNTERS
- 24 DIGITAL I/O

**MODEL 150-02 .... \$179**



- RS-232 INTERFACE
- TRMS, 20 AMPS
- 12 BIT A/D
- OPTO-ISOLATED
- COMPLETE DMM

**MODEL 40 ..... \$109**



- RS-232 INTERFACE
- 28 LINES DIGITAL I/O
- 8 ANALOG INPUTS
- PWM OUTPUT

**MODEL 70 ..... \$239**



- RS-232 INTERFACE
- 18 BIT A/D
- 5.5 DIGIT
- UP TO 60 SMP/SEC

**Prairie Digital, Inc.**

PHONE 608-643-8599 • FAX 608-643-6754

820 SEVENTEENTH STREET • PRAIRIE DU SAC, WISCONSIN 53578

CIRCLE 219 ON FREE INFORMATION CARD

**Start A Career With High Wages, Excellent Benefits and Job Security!!**

With UCANDO's extraordinary maintenance training programs you can quickly and easily enter a high paying field as a maintenance technician for a very small investment of time and money.




**RC-M ONLY \$165** RC-M is a 15 hour training course on relay ladder logic systems. Includes a 5-part video and workbook. Great Value!

**PLC-M ONLY \$198** PLC-M is a 32 hour training course on PLC systems. Includes (2) 4-part video's and workbook. This training is valuable.



**HYD-M ONLY \$209** HYD-M is a 32 hour course on Fluid Dynamics. Includes (2) 4-part video's and workbook. This Module is a must.

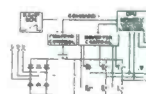**SC-M ONLY \$215** SC-M is a 32 hour training course on AC & DC Servo Controllers. Includes (2) 4-part video's and workbook. Learn everything you need about AC and DC servo Control Systems.



**Electronic Training Videos:** Basic Electronics, Digital Electronics, TV Repair, LASER and Fiber Optic training videos available at very affordable prices starting at Only \$39.95 each.

For information or to place an order call:

**1-800-678-6113**

www.ucando-corp.com

UCANDO VCR Educational Products Corp., Greenville, OH



# CLASSIFIEDS

## BUSINESS OPPORTUNITIES

**\$400 WEEKLY ASSEMBLING** electronic circuit boards/products from home: For FREE information send SASE: Home Assembly-PT Box 216 New Britain, CT 06050-0216.

**EASY WORK! EXCELLENT PAY!** Assemble Products At Home. Call Toll Free 1-800-467-5566 EXT. 1190

## CABLE TV

**CABLE TV Descramblers.** One-piece units. Scientific Atlanta, Jerrold, Pioneer, and others. **Lowest Prices Around. Precision Electronics** Houston, TX Anytime. 1-888-691-4610

**PAY TV AND SATELLITE DESCRAMBLING 2000 EDITION.** \$16.95. Hacking Digital Scrambling Systems III (NEW) \$29.95. Scrambling News Online \$40.00. Pay TV Series CD (Vol. 1-10) \$59.95. Everything listed here \$99.95. Free catalog. **SCRAMBLING NEWS.** 863-646-2564. [www.scrablingnews.com](http://www.scrablingnews.com)

**Descramblers, Converters, Activators, Rft's, Ftg's, Bullet Snoopers. All Options Explained, Best Prices, Services, 2 yr. Warranty, Free Catalog.** 1-800-854-1674 [www.resourceleader.com/aapc](http://www.resourceleader.com/aapc)

**NEW!** Jerrold and Pioneer wireless test units \$125 each, also 75DB notch filters \$19.95 each, quantity pricing available please call **KEN ERNY ELECTRONICS** 24-hour order and information hot line 516-389-3536.

**ROCK BOTTOM..DEALER..DISCOUNTS! 125 CH. VISION MASTER PLUS.. "DECODE'S EVERYTHING PERMANENTLY" TEST CHIPS & ACTIVATORS** 1-888-675-3687—201-386-1145

**ALL CABLE TV BOXES. WE'LL BEAT ANY PRICE. 30 DAY TRIAL 1 YEAR WARRANTY. FREE CATALOG! WWW.CATVBOXES.COM** 1-800-765-4912

## CB-SCANNERS

**CB Radio Modifications!** Frequencies, kits, high-performance accessories, books, plans, repairs, amps, 10-Meter conversions. The best since 1976! Catalog \$3. **CBCI**, Box 1898P, Monterey, CA 93942. [www.cbciintl.com](http://www.cbciintl.com)

## MISC. ELECTRONICS FOR SALE

**T & M ELECTRONICS.** Large variety of electronic parts since 1966. Visit our Web site at [www.tandmelectronics.com](http://www.tandmelectronics.com)

## PLANS-KITS-SCHEMATICS

**ELECTRONIC PROJECT KITS:** \$3.00 catalog. 49 McMichael St. Kingston, ON., K7M 1M8. [www.qkits.com](http://www.qkits.com) — **QUALITY KITS**

**AWESOME KITS:** Ion Propulsion Motor, Stepper Driver, Solar Robot, Scrolling Clock and more! Catalog \$1.00. **LNS Technologies**, PO Box 67243, Scotts Valley, CA 95067 [www.techkits.com](http://www.techkits.com)

**AM Tube Radio Kits.** TRF and Superhets. Visit our website at [www.ghostmoon.bigstep.com](http://www.ghostmoon.bigstep.com)

## REPAIRS-SERVICES

**BRAKE Alert** is a control module that connects to a vehicle's third brake light. Brake Alert senses when the vehicle stops quickly and flashes the third brake light to attract attention to the vehicle behind. Brake Alert can be purchased from web site at [www.brake-alert.com](http://www.brake-alert.com) for \$29.95.

## SATELLITE EQUIPMENT

**FREE Satellite TV Buyer's Guide.** Best Products — Lowest Prices — Fastest Service! Dish Network, DirectTV, C/Ku-band, including 4DTV. Parts — Upgrades — Accessories! **SKYVISION** - 800-543-3025. International 218-739-5231. [www.skyvision.com](http://www.skyvision.com)

## TEST EQUIPMENT

**Browse** our Web site and check out the "Monthly Special". **TDL Technology, Inc.** [www.zianet.com/tdl](http://www.zianet.com/tdl)

**FREE Catalog.** Electronic Test instruments, new and used, wide selection, lowest prices. **GEOMA.** (608) 462-4222.



One tree can make 3,000,000 matches.

One match can burn 3,000,000 trees.

# PCBoards

## PCB Artwork Made Easy!

## PRINTED CIRCUIT DESIGN SOFTWARE

For Windows and DOS  
Layout - Autorouting - Schematic - Circuit Simulation

Visit our Website @ [www.pcboards.net](http://www.pcboards.net)

For free DEMO and Information

**PCBoards** (800) 473-7227  
2110 14th Ave. South (205) 933-1122  
Birmingham, AL 35205

Perfect for the Pro or Hobbyist!

## Poptronics

### Wireless & Electrical Cyclopedia



**ETT1—Wireless & Electrical Cyclopedia** \$4.99. Step back to the 1920's with this reprinted catalog from the Electro Importing Company. Antiquity displayed on every page with items priced as low as 3 cents. Product descriptions include: Radio components, kits, motors and dynamos, Leyden jars, hot-wire meters, carbon mikes and more. The perfect gift for a radio antique collector. To order ETT1, send \$4.99 (includes s&h) in the US and Canada to **Electronic Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240.** US funds only. Use US bank check or International Money Order. Allow 6-8 weeks for delivery. MA11

## SHOPPER

### ELECTRONIC GAMES

**BP69—A number of interesting electronic game projects using IC's are presented.** Includes 19 different projects ranging from a simple coin flipper, to a competitive reaction game, to electronic roulette, a combination lock game, a game timer and more. To order BP69 send **\$4.99 clearance (includes s&h)** in the US and Canada to **Electronic Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240.** US funds only. Use US bank check or International Money Order. Allow 6-8 weeks for delivery. MA07



### Get your copy of the CRYSTAL SET HANDBOOK



Go back to antiquity and build the radios that your grandfather built. Build the "Quaker Oats" type rig, wind coils that work and make it look like the 1920's! Only \$10.95 plus \$4.00 for shipping and handling. **Claggk Inc., PO Box 12162, Hauppauge, NY 11788.** USA Funds ONLY! USA and Canada — no foreign orders. Allow 6-8 weeks for delivery. MA01

### LEARN ELECTRONICS REPAIR

Home study. Learn to repair, service, and install stereos, TVs, VCRs, camcorders, sound/lighting systems. **Free literature: send or call now.**

**CALL 800-223-4542**

The School of Electronics  
430 Technology, Dept. ELJ 341  
PCDI, Norcross, GA 30092



## ADVERTISING INDEX

Poptronics does not assume any responsibility for errors that may appear in the index below.

Free Information Number	Page	Free Information Number	Page
- A & A Engineering	.88	- Lynxmotion	.82
- Abacom Technology	.94	- M <sup>2</sup> L Electronics	.92
- ABC Electronics	.76	160 MCM Electronics	.71, 85
215 All Electronics	.93	250 Mendelsons	.82
- Allison Technology	.78	296 Merrimack Valley Systems	.73
- Amazon Electronics	.86	- Microdev	.94
315 American Eagle Publications	.70	- microEngineering Labs	.92
- Andromeda Research	.70	- Midwest Laser Products	.70
- Arrow Technologies	.88	- Modern Electronics	.82
295 AVEN Tools	.89	220 Mouser Electronics	.66
- Big Bang Electronics	.69	- MSC Electronics	.87
319 Beige Bag Software	.80	- PC Boards	.97
- Carl's Electronics	.92	257 Parts Express	.67
290 C&S Sales, Inc.	.74	- Pioneer Hill Software	.66
- CCTV Outlet	.82	300 Polaris Industries	.65
133 CircuitMaker	.CV2	219 Prairie Digital	.96
233 Circuit Specialists	.95	- Print Products Int.	.28
- CLAGGK, Inc.	.13, 21	- Quick Route Systems	.84
- Cleveland Inst. of Electronics	.35	- RC Distributing Co.	.87
231 Command Productions	.68	263 Ramsey Electronics	.79
232 Command Productions	.94	246 Resources Unlimited	.96
- Computer Monitor Maintenance	.86	- Robotikits Direct	.80
- Conitec Data Systems	.92	308 Roger's Systems Specialist	.72
- EDE Spy Outlet	.90	- Securetek	.78
130 Electronic Workbench	.CV4	- Scott Edwards Electronics	.70
- Electronic Tech. Today	.59	- Sil Walker	.76
205 Electronix Express	.84	- Smithy Company	.86
- EMAC Inc.	.28	- Square 1 Electronics	.68
- Engineering Express	.70	- Techniks	.87
318 Foley-Belsaw	.81	- Technological Arts	.88
- Fort777.com	.68	311 Telulex	.72
- Future Horizons	.70	313 Test Equipment Depot	.26
- Gateway Products	.86	217 Tie Pie Engineering	.76
- General Device Instruments	.90	242 Timeline	.90
- Globaltech Distributors	.86	- UCANDO Videos	.96
- Grantham College of Eng.	.66	- Ultima Associates	.88, 92
237 Howard Electronics	.83	- Vision Electronics	.92
225 Information Unlimited	.91	- World Star Technologies	.87
- Intec Automation	.87	- World Wyde	.86, 87
- Intronics	.82	- Zorin	.86
309 IVEX Design	.77		
- J&M Microtek	.87		
139 Jameco	.CV3		
- KNS Instruments	.66		

## ADVERTISING SALES OFFICES

**Gernsback Publications, Inc.**  
**275-G Marcus Blvd.**  
**Hauppauge, NY 11788**  
**Tel. 631-592-6720**  
**Fax: 631-592-6723**

**Larry Steckler**  
 Publisher (ext. 201)  
 e-mail: advertising@gernsback.com

**Adria Coren**  
 Vice President (ext. 208)

**Ken Coren**  
 Vice-President (ext. 267)

**Marie Falcon**  
 Advertising Director (ext. 206)

**Adria Coren**  
 Credit Manager (ext. 208)

### For Advertising ONLY EAST/SOUTHEAST

**Marie Falcon**  
 275-G Marcus Blvd.  
 Hauppauge, NY 11788  
 Tel. 631-592-6720 x206  
 Fax: 631-592-6723  
 e-mail: mfalcon@gernsback.com

### MIDWEST/Texas/Arkansas/ Oklahoma

**Ralph Bergen**  
 One Northfield Plaza, Suite 300  
 Northfield, IL 60093-1214  
 Tel. 847-559-0555  
 Fax: 847-559-0562  
 e-mail: bergenrj@aol.com

### PACIFIC COAST

**Megan Mitchell**  
 9072 Lawton Pine Avenue  
 Las Vegas, NV 89129-7044  
 Tel. 702-240-0184  
 Fax: 702-838-6924  
 e-mail: mmitchell@gernsback.com

**Subscription/  
 Customer Service/  
 Order Entry**  
 Tel. 800-827-0383  
 7:30 AM - 8:30 PM CST

# JAMECO<sup>®</sup>

ELECTRONIC COMPONENTS

COMPUTER PRODUCTS

1•800•794•9100

[www.jameco.com/pop](http://www.jameco.com/pop)

Click on this URL to receive  
your free shipping and  
special product pricing!



**Free Shipping on Your First Order! Just Mention VIP# PT1**

*Call for details - Certain restrictions apply*

CIRCLE 139 ON FREE INFORMATION CARD

[www.americanradiohistory.com](http://www.americanradiohistory.com)

# The world's most popular simulator just got better.

## MULTISIM SCHEMATIC CAPTURE AND SIMULATION

**NEW  
VERSION 6**

### Flexible Symbol Editor **NEW**

To add or modify symbols for any component.

### Power Meter **NEW**

Works just like with a real Wattmeter.

### 1000 New Components **NEW**

New families include Electromechanical, Connector, Wideband Opamp, and Tiny Logic.

### Editable Footprint Field **NEW**

Add or change default footprint values directly from the schematic.

### New Analyses **NEW**

AC sensitivity and DC sensitivity help determine the stability of your design.

### Multiple Instruments **NEW**

Now you can have more than one copy of an instrument on the screen at once.

### Enhanced Wiring **NEW**

Improved connections to pins and more intelligent autowiring.

### Analysis Wizards **NEW**

Guide you through an analysis, making it easier than ever to take advantage of these powerful functions.

### Virtual Instruments

Includes oscilloscope, function generator, multimeter, bode plotter, word generator, and logic analyzer.

### 9 Powerful Analyses

To analyze circuits in ways just not possible with real instruments. Includes DC, & AC operating point, transient, fourier, noise, DC sweep and Ac & DC sensitivity.

### 5,000 Components

Wide selection of commonly used components, all complete with simulation, symbol and footprint information.

### Full-Featured Schematic Capture

Industry's easiest-to-use design entry is ideal for generating high-quality schematics.

### Changes on the Fly


The world's only simulator that lets you tweak your circuit during simulation for instant feedback.

### Analog and Digital SPICE Simulation

Fast, accurate SPICE simulation with no limit on circuit size.

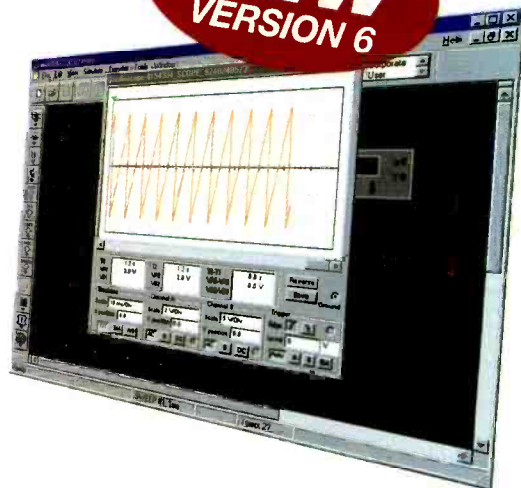
### Custom Model Support

Edit existing models to create new parts, or import components as SPICE models from vendors.



multiSIM \$399

Call for upgrade pricing

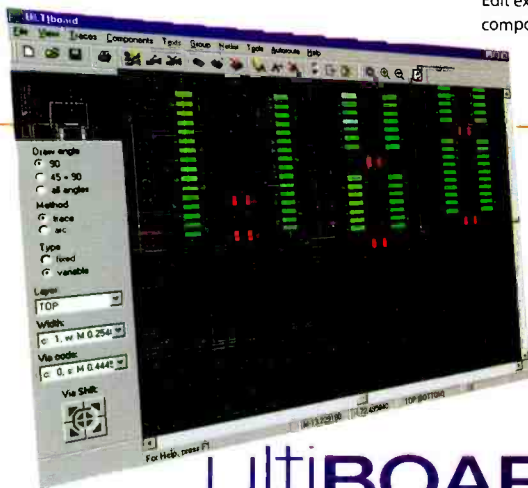

## ULTIBOARD POWERFUL PCB LAYOUT

**Fast Autorouting** Multi-layer autorouter with configurable options for customized performance.

**Real-Time DRC** Automatic Design Rule Check prevents costly errors by monitoring the size and clearance of pads, vias and traces.

**Ideal for all Boards** Built-in board editor to create any shape board up to 50" X 50" in size, with as many as 32 layers.

**Multiple Output Formats** Outputs to the formats you need including Gerber, DXF, plotters, printers, and more.

**Tight Integration with Multisim** Supports forward and back annotation with Multisim, so that the programs share important design information.

**Flexible Editing** Full support of power and ground planes, with or without thermal relief. 'Reroute while move' to move copper without losing connectivity.

ultiBOARD \$399

TO ORDER

For a FREE demo visit [www.electronicworkbench.com](http://www.electronicworkbench.com)

SAVE  
\$1000

Call 1-800-263-5552

Save \$100 when you order the Personal Design Solution  
(Includes Multisim and Ultiboard).



Electronics  
WORKBENCH

DESIGN SOLUTIONS FOR EVERY DESKTOP

CIRCLE 130 ON FREE INFORMATION CARD