

Radio- Electronics

**BUILD YOUR OWN ROBOT:
ASSEMBLING THE ARMS**

\$1.25 SEPT. 1980


Set up a home video system
Solid-state sounder applications
New hi-fi noise reduction system

Build your own wipeout videogame
Inside VHS recorder circuits
New packaging system for projects



**MODULAR PLUG-IN
REMOTE CONTROL**
How it works

A breadboard as big as your ideas.

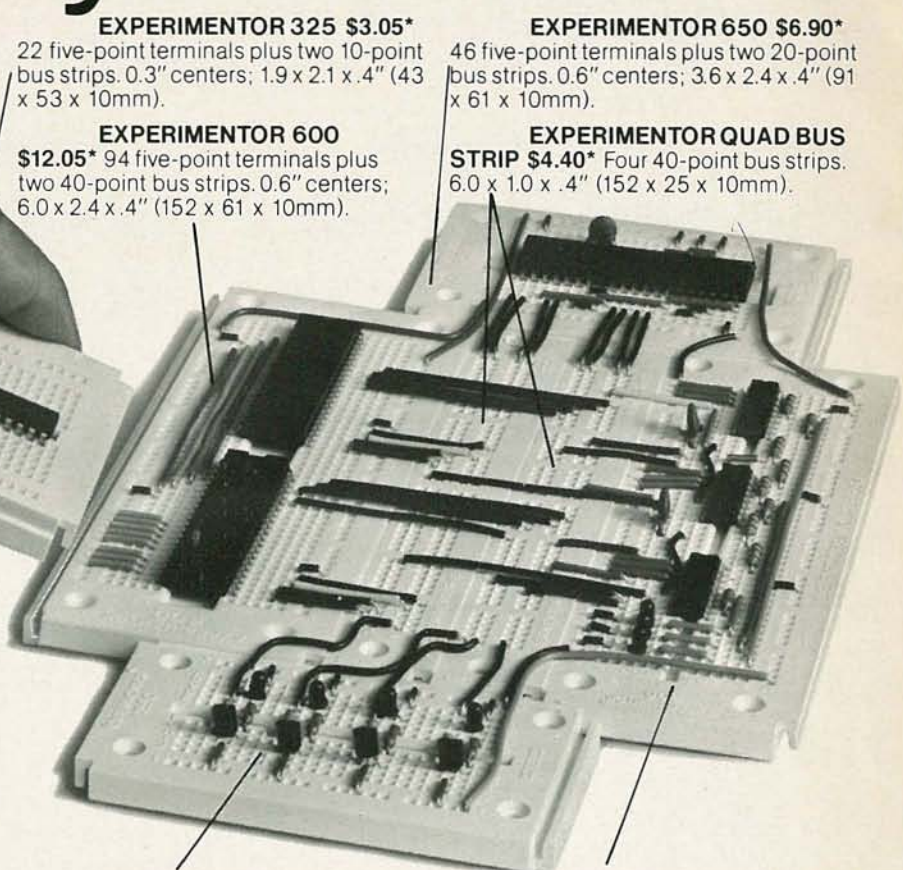

EXPERIMENTOR 325 \$3.05*

22 five-point terminals plus two 10-point bus strips. 0.3" centers; 1.9 x 2.1 x .4" (43 x 53 x 10mm).

EXPERIMENTOR 600

\$12.05* 94 five-point terminals plus two 40-point bus strips. 0.6" centers; 6.0 x 2.4 x .4" (152 x 61 x 10mm).

EXPERIMENTOR 650 \$6.90*

46 five-point terminals plus two 20-point bus strips. 0.6" centers; 3.6 x 2.4 x .4" (91 x 61 x 10mm).

EXPERIMENTOR QUAD BUS STRIP \$4.40*

Four 40-point bus strips. 6.0 x 1.0 x .4" (152 x 25 x 10mm).

Instant hookup for all types of components, with push-in/pull-out ease.

Adaptable for all types of components... DIP-compatible... conform to 0.1" grid; jumpers are #22-30 solid hookup wire.

Mix and match large and small chips in the same circuit. Use 300-series sockets for smaller DIPs; 600-series with 0.6" center channel for full fan-out with larger chips.

Infinite flexibility lets you expand and modify circuits vertically and horizontally, simply by snapping sockets together.

Easy mounting using 4-40 screws from front or 6-32F self-tapping screws from rear. Vinyl-insulated backing lets you fasten to any surface.

EXPERIMENTOR 350 \$6.05*

46 five-point terminals plus two 20-point bus strips. 0.3" centers; 3.6 x 2.1 x .4" (91 x 53 x 10mm).

Marked tie-points simplify translation from breadboards to PC boards or wiring tables.

Ruggedly built of abrasion-resistant materials that withstand 100°C.

EXPERIMENTOR 300 \$10.95*

94 five-point terminals plus two 40-point bus strips. 0.3" centers; 6.0 x 2.1 x .4" (152 x 53 x 10mm).

Quick construction of micro-processors and other circuits—each EXP-4B gives you four bus lines, with 8-, 12-, and 16-line address and data buses easily created by combining Bus Strips.

It's hard to believe how much faster and easier building circuits can be... until you try our Experimentor™ solderless breadboarding sockets. From the largest DIP to the smallest resistor, components plug in and out instantly, without special hardware or jumper cables. So you save

time and money by eliminating soldering and component damage. Start small and expand in any direction your thinking takes you, by snapping sockets together vertically or horizontally. With no limit to your ideas. Get started today, for as little as \$3.05*!

Smarter tools for testing and design.

GLOBAL SPECIALTIES CORPORATION

Call toll-free for details
1-800-243-6077
During business hours

70 Fulton Terr., New Haven, CT 06509 (203) 624-3103, TWX 710-465-1227
OTHER OFFICES: San Francisco (415) 421-8872, TWX 910-372-7992
Europe: Phone Saffron-Walden 0799-21682, TLX 817477
Canada: Len Finkler Ltd., Downsview, Ontario

*Suggested U.S. resale. Prices, specifications subject to change without notice. © Copyright 1980 Global Specialties Corporation.

CIRCLE 39 ON FREE INFORMATION CARD



Bone Fone^{T.M.}

A new concept in sound technology may revolutionize the way we listen to stereo music.

The Bone Fone surrounds your entire body with a sound almost impossible to imagine.

You're standing in an open field. Suddenly there's music from all directions. Your bones resonate as if you're listening to beautiful stereo music in front of a powerful home stereo system.

But there's no radio in sight and nobody else hears what you do. It's an unbelievable experience that will send chills through your body when you first hear it.

AROUND YOU

And nobody will know you're listening to a stereo. The entire sound system is actually draped around you like a scarf and can be hidden under a jacket or worn over clothes.

The Bone Fone is actually an AM/FM stereo multiplex radio with its speakers located near your ears. When you tune in a stereo station, you get the same stereo separation you'd expect from earphones but without the bulk and inconvenience. And you also get something you won't expect.

INNER EAR BONES

The sound will also resonate through your bones—all the way to the sensitive bones of your inner ear. It's like feeling the vibrations of a powerful stereo system or sitting in the first row listening to a symphony orchestra—it's breathtaking.

Now you can listen to beautiful stereo music everywhere—not just in your living room. Imagine walking your dog to beautiful stereo music or roller skating to a strong disco beat.

You can ride a bicycle or motorcycle, jog and even do headstands—the Bone Fone stays on no matter what the activity. The Bone Fone stereo brings beautiful music and convenience to every indoor and outdoor activity without disturbing those around you and without anything covering your ear.

SKI INVENTION

The Bone Fone was invented by an engineer who liked to ski. Every time he took a long lift ride, he noticed other skiers carrying transistor radios and cassette players and wondered if there was a better way to keep your hands free and listen to stereo music.

So he invented the Bone Fone stereo. When he put it around his neck, he couldn't believe his ears. He was not only hearing the music

and stereo separation, but the sound was resonating through his bones giving him the sensation of standing in front of a powerful stereo system.

AWARDED PATENT

The inventor took his invention to a friend who also tried it on. His friend couldn't believe what he heard and at first thought someone was playing a trick on him.

The inventor was awarded a patent for his idea and brought it to JS&A. We took the idea and our engineers produced a very sensitive yet powerful AM/FM multiplex radio called the Bone Fone.

The entire battery-powered system is self-contained and uses four integrated circuits and two ceramic filters for high station selectivity. The Bone Fone weighs only 15 ounces, so when worn over your shoulders, the weight is not even a factor.

BUILT TO TAKE IT

The Bone Fone was built to take abuse. The large 70 millimeter speakers are protected in flexible water and crush resistant cases. The case that houses the radio itself is made of rugged ABS plastic with a special reinforcement system. We knew that the Bone Fone stereo may take a great deal of abuse so we designed it with the quality needed to withstand the worst treatment.

The Bone Fone stereo is covered with a sleeve made of Lycra Spandex—the same material used to make expensive swim suits, so it's easily washable. You simply remove the sleeve, dip it in soapy water, rinse and let the sleeve dry. It's just that easy. The entire system is also protected against damage from moisture and sweat making it ideal for jogging or bicycling.

The sleeve comes in brilliant Bone Fone blue—a color designed especially for the system. An optional set of four sleeves in orange, red, green and black is also available for \$10. You can design your own sleeve using the pattern supplied free with the optional kit.

YOUR OWN SPACE

Several people could be in a car, each tuned to his own program or bring the Bone Fone to a ball game for the play by play. Cyclists,

joggers, roller skaters, sports fans, golfers, housewives, executives—everybody can find a use for the Bone Fone. It's the perfect gift.

Why not order one on our free trial program and let your entire family try it out? Use it outdoors, while you drive, at ball games or while you golf, jog or walk the dog. But most important—compare the Bone Fone with your expensive home stereo system. Only then will you fully appreciate the major breakthrough this product represents.

GET ONE SOON

To order your Bone Fone, simply send your check or money order for **\$69.95** plus \$2.50 postage and handling to the address shown below. (Illinois residents add 6% sales tax.) Credit card buyers may call our toll-free number below. Add \$10 if you wish to also receive the accessory pack of four additional sleeves.

We'll send you the entire Bone Fone stereo complete with four AA cell batteries, instructions, and 90-day limited warranty including our prompt service-by-mail address.

When you receive your unit, use it for two weeks. Take it with you to work, or wear it in your car. Take walks with it, ride your bicycle or roller skate with it. Let your friends try it out. If after our two-week free trial, you do not feel that the Bone Fone is the incredible stereo experience we've described, return it for a prompt and courteous refund, including your \$2.50 postage and handling. You can't lose and you'll be the first to discover the greatest new space-age audio product of the year.

Discover the freedom, enjoyment, and quality of the first major breakthrough in portable entertainment since the transistor radio. Order a Bone Fone stereo at no obligation, today.

JS&A PRODUCTS
THAT
THINK[®]

Dept. RE One JS&A Plaza
Northbrook, Ill. 60062 (312) 564-7000
Call TOLL-FREE 800 323-6400
In Illinois Call (312) 564-7000
© JS&A Group, Inc., 1980

ELECTRONIC BREAKTHROUGH!

Awesome Fingertip Power!

- CASIO C-80 DIGITAL QUARTZ CHRONOGRAPH/CALCULATOR
- THE OLIVETTI WORLD'S SMALLEST PRINTING CALCULATOR/LCD CLOCK



You can call our toll-free number for immediate delivery, and charge just \$69.95 (plus \$2.50 insured shipping) to your credit card. Thirty day money-back guarantee, one-year parts and labor warranty.

Just three more points: the battery's included. There's a tiny light to illuminate the display at night. In fact, it's bright enough to help you find your keys if you drop them in the dark. And when you receive your Casio C-80, resist the temptation to press the keys with your fingernail. Not necessary. Just use your fingertips.

WORLD'S SMALLEST PRINTING CALCULATOR!

Besides all the calculating functions you expect, the Olivetti Logos 9 offers you these added features, plus more, thanks to some new technological breakthroughs.

- Measures only 1 inch by 2½ inches by 4 5/8 inches, with full 12 digit liquid crystal display, with floating or fixed position decimal.
- Exclusive paper cartridge system, simply slide up the calculator top and behold the smallest printing system you've ever seen.
- Clear crisp entries on Olivetti's special cartridge paper. Each cartridge lasts for up to 1,300 entries. (Thirty two rolls...good for three years of use, only \$18.00).
- Incredibly fast printing speed of two lines per second, with print recall. Should your entries exceed unit speed, the Logos 9 will still print each entry.
- Rechargeable batteries (up to 500 recharges per battery).
- Printing head labels all numerical entries with letters. You'll never forget your entries purpose.
- Accumulating memory, plus fully independent memory.
- Digital clock, a totally accurate time-piece.
- Ideal for people who employ, discounts, gross margins, and percentage markups.
- Automatic average: The Logos 9 will automatically compute the average of a group of entries.
- Complete memory recall and display.
- Battery charging and 90 day limited warranty.
- Easy Olivetti service by mail.

Try this amazing pocket calculator today, we're sure that you will agree that the Logos 9 is the most convenient and advanced pocket calculator you've ever seen. If after thirty days, you are not satisfied, return the unit for a prompt refund.

The Olivetti Logos 9 was awarded at the International Consumer Electronic Show 1980 the distinguished position of being the "Most Innovative Product of the Year", and is the best selling pocket calculator in the world. Try it today.

HERE'S HOW TO ORDER AND SAVE

The C-80 Chronograph/Calculator is \$69.95. The Printing Calculator is \$89.95. That adds up to \$159.90. If you order both for yourself (and don't forget gift possibilities) pay only **\$144.95** for a savings of **\$15.00**.

Or order any two and take \$15.00 off their combined price. You can order today by calling one of our toll-free numbers for immediate delivery. You save on insured shipping charges, as well: just \$2.50 for each order, not each item.

30 DAY MONEY BACK GUARANTEE

When you order, you're protected by our 30-day money back guarantee policy. And each item is additionally covered by a one-year parts and labor warranty. All units come with instructions, and batteries are included.

Right now, call toll-free and charge what you want on American Express, Diners Club, Carte Blanche, Master Card, or Visa.

800-526-2801

800-257-7850

In New Jersey call toll free:
800-322-8650

N.J. residents please add 5% sales tax.

You can also mail your order with check or money order to:

INTERNATIONAL SALES GROUP
MERCURY
THE IMAGINATION PEOPLE®

Dept. RE9, Lakewood Plaza
Lakewood, New Jersey 08701

The two wonders on this page are among the best, most wanted, and most useful everyday electronic products in the world.

Each one brings you state-of-the-art function and design and places awesome calculating power at your fingertips. Let's examine these breakthroughs one at a time.

ANATOMY OF YOUR FINGERTIP

The Casio C-80 Chronographic Calculator is the first wrist instrument whose numeric and function command keys are designed so you can operate them with your fingertip. No need to carry a special stylus or look for a pencil with a sharp point whenever you want to calculate something.

The Casio C-80 has an 8-digit read-out. It adds, subtracts, multiplies, divides, and performs chain calculations. Floating decimal tool.

It tells you the time digitally in two zones (accurate within ± 15 seconds a month), and it tells month and date. It's also a stopwatch in hundredths of seconds, with capacity up to 23 hrs., 59 min. 59.99 secs. It gives you both lap and net times as well.

The C-80 weighs much less than metal calculator watches. The case and band are space-age unbreakable plastic, and the LCD face is protected by hard mineral glass.

So far as we know, only one or two stores in New York City have been able to get the C-80. And we've seen it advertised as high as \$75.00 — and that only lets you reserve it, with a long wait for delivery.

CIRCLE 29 ON FREE INFORMATION CARD

SPECIAL FEATURE

- 47 **PLUG-IN MODULAR REMOTE CONTROL**
The BSR System X-10 plugs into AC wall outlets to provide remote control operation of lamps and appliances in your home or office. **Steven A. Clarcia**

BUILD THIS

- 55 **UNICORN-1 ROBOT**
PART 2. Assembling the manipulator arms and "hands."
James A. Gupton, Jr.
- 66 **WIPEOUT VIDEOGAME**
Ten action-packed games in an arcade type videogame. Add on RF modulator and play it on your TV set.
L. Steven Cheairs

TECHNOLOGY

- 4 **LOOKING AHEAD**
Tomorrow's news today. **David Lachenbruch**
- 22 **SATELLITE TV NEWS**
The latest happenings in an exciting new industry.
Gary H. Arlen
- 59 **PIEZOELECTRIC SOUNDER APPLICATIONS**
Solid-state "beepers" have a variety of interesting circuit applications. This should give you a few ideas.
Calvin R. Graf, W5LFM
- 76 **NEW IDEAS**
A winning circuit application from our readers.
- 78 **HOBBY CORNER**
A one-arm bandit circuit plus a new packaging system for projects. **Earl "Doc" Savage, K4SDS**

VIDEO

- 52 **HOW TO HOOK UP HOME VIDEO SYSTEMS**
How to connect a programmable VCR, videogame, pay-TV, cable T.V., and other inputs to a single TV set.
Frank Gates
- 70 **VHS TRANSPORT CIRCUITS**
A look at the circuitry that controls the transport mechanism in VHS videotape recorders and how to troubleshoot it. **Forest Belt**
- 96 **SERVICE CLINIC**
Typical problems with tripler circuits and some not so typical. **Jack Darr**
- 98 **SERVICE QUESTIONS**
R-E's Service Editor solves technicians' problems.

AUDIO

- 61 **NEW NOISE REDUCTION SYSTEM**
The new High-Com II system from Nakamichi provides 18-dB more noise reduction in tape recorders than Dolby B. **Len Feldman**
- 63 **R.E.A.L. SOUND LAB TESTS B.I.C./AVNET MODEL T-3 CASSETTE DECK**
Medium-priced cassette deck rates superb. **Len Feldman**

RADIO

- 86 **COMMUNICATIONS CORNER**
Transceivers with all the operating controls built into the microphone. **Herb Friedman**

EQUIPMENT REPORTS


- 38 **The Defender TS-1 CB Antenna Tuner/Monitor**
- 40 **IET Model RCS-500 R-C Substitution Box**
- 42 **Datong Model AD-170 Active Antenna**
- 43 **Micronta BP-1 Blood Pressure Tester**

DEPARTMENTS


- | | |
|------------------------------|---------------------|
| 122 Advertising Index | 26 Letters |
| 16 Advertising Sales Offices | 105 Market Center |
| 103 Books | 103 New Lit |
| 102 Computer Reports | 83 New Products |
| 16 Editorial | 94 Radio Products |
| 123 Free Information Card | 100 Stereo Products |
| | 7 What's News |

ON THE COVER

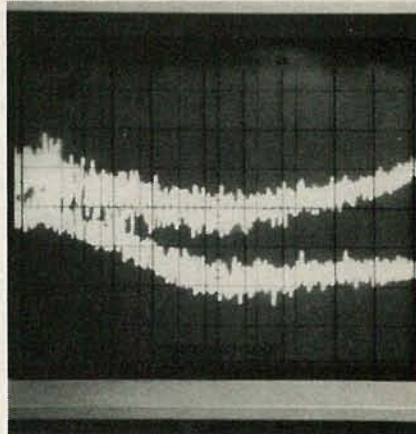You can turn on and off lamps and appliances without ever leaving your armchair with BSR's System X-10. To install the system, you simply plug the various modules into existing AC wall outlets. The system features a hand-held ultrasonic remote control unit and a programmable timer. For a look at the circuitry and how the system works, turn to page 47.



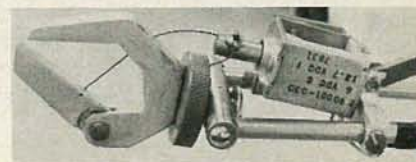NEW NOISE REDUCTION SYSTEM for tape recorders provides 18-dB more noise reduction than Dolby B. For the complete details, turn to page 61.



HANDS FOR THE UNICORN-1 ROBOT are solenoid activated. For details on how to assemble the manipulator arms and hands, turn to page 55.

Radio-Electronics, (ISSN 0033-7862) Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Phone: 212-777-6400. Controlled Circulation Postage Paid at Concord, NH. One-year subscription rate: U.S.A. and U.S. possessions, \$13.00. Canada, \$16.00. Other countries, \$18.00. Single copies \$1.25. © 1980 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

Subscription Service: Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Box 2520, Boulder, CO 80322.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

looking ahead

A 3-disc race: General Electric threw the already complex videodisc race into pandemonium by embracing a third system—VHD (Video High Density), developed by the Japan Victor Company (JVC). The VHD system uses a 10-inch grooveless disc to play two hours (one hour per side) of color and stereo-sound information by reading out capacitance variations in the disc material. The disc revolves at 900 rpm, and has features in common with both other consumer systems. Like the RCA CED (Capacitance Electronic Disc) system, the stylus and disc form the plates of what, in effect, is a variable capacitor; but the RCA system uses grooves to guide the stylus, while VHD employs pilot frequencies that differ between adjacent tracks. Like the Philips-MCA optical system, it's grooveless and is capable of certain special effects, such as fast, slow, and reverse motion. The CED disc revolves at 450 rpm and plays one hour per side. The optical disc spins at 1,800 rpm (30 minutes per side) in the special-effects mode and at a speed varying from 600 to 1,800 in the so-called "constant linear velocity mode" (60 minutes per side). The three systems are totally—and hopelessly—incompatible with each other.

GE's espousal of the VHD system came in talks (nearing completion at press time) to establish three jointly owned companies: 1. With Matsushita (Panasonic and Quasar) and JVC to manufacture players in the United States. 2. With those companies and Thorn EMI of England to press discs here. 3. With the same three companies to acquire rights and develop disc programming. VHD starts up far behind its competitors as a true dark horse. Players for the optical system are already being marketed by Magnavox and Pioneer; discs are being sold by MCA DiscoVision. RCA plans a nationwide launch for the Selecta-Vision CED system early in 1981; Zenith will also sell CED players and both RCA and CBS will press discs. JVC says that the VHD system can be on the American market by the end of 1981 at a price "competitive" to RCA's \$500 target (the Magnavox and Pioneer players are \$775 and \$749, respectively).

Who's on first? RCA was the best-selling color-TV brand in the 1980 model-year (July 1979-June 1980), according to a survey by the industry newsletter *Television Digest*. That was the second consecutive model-year in which RCA was in the No. 1 spot, getting a 21% share of the market to Zenith's 20.5%. GE, with 7.5%, was No. 3 in color, followed by Sears Roebuck, also with 7.5% (but slightly lower in average ranking), Magnavox and Sony, with 7% and 6% respectively. In black-and-white, Zenith easily retained the top spot, registering 16% of the market, with RCA second at 14.85%, GE third with 10%, followed by Sears (9%) and Panasonic (6.65%).

More new VCR's: Videocassette recorders continue to sport a profusion of new features. Both VHS and Beta models under major trade names now include high-speed scan in both directions for easy program-segment selection (and for zipping through commercials) as well as noise-free still-frame, frame-by-frame advance and slow motion, all controlled by a wired remote unit. Akai has introduced the first model with dual soundtracks—a two-

speed VHS portable capable of carrying stereo audio or tracks in different languages. It also is the first model to be marketed in the United States that includes Dolby noise reduction.

JVC has introduced what (at least for the moment) is the lightest and smallest portable VCR available in the United States. It weighs 11.4 pounds and can be back-packed and operated by a hand-held remote control. Meanwhile, the two longitudinal video recorders scheduled for introduction in the home market have been scratched. BASF's unit, which already was in the early stages of pilot production in a California plant, was officially withdrawn and the plant put up for sale. The Toshiba LVR will probably appear first as a data recorder, it may eventually surface again in its video form. At last June's Consumer Electronics Show, Toshiba showed a new version of the LVR that can record two programs simultaneously by using two tracks, but the official word is that until further notice, LVR is no longer a consumer product.

Telecaptions: The experts may argue long and loud over what format for teletext and viewdata should be adopted in the United States, but one form of vertical-interval message transmission is off and running and an unqualified success. This is Telecaptioning, a special service for the hard of hearing, now permitted by the FCC. Captions are prepared by the National Captioning Institute for programs submitted by ABC, NBC, and PBS. CBS chose not to participate, arguing that teletext is better suited for captioning. Sears Roebuck has the exclusive rights to sell decoders which enable TV sets to display the captions, as well as decoder-equipped TV sets, using IC's made by Texas Instruments.

In the first 11 weeks of captioning, Sears sold 17,700 caption decoders, an average of 1,600 per week, but at the end of the period (June 1), sales were running at the rate of 1,800 weekly—matching the current production rate—with a four-week order backlog. The decoders retail for \$250, and a newly introduced 19-inch set with built-in decoder (in Sears' fall catalog) lists for \$520. The decoders have a three-position selector switch, and captioning eventually will be offered in Spanish as well as English, along with "Infodata," a new information service being developed by National Captioning Institute. The Institute is supported by royalties from the sale of decoders.

End of an era: The grand old name in automobile radio—Motorola—has discontinued manufacture of car sound equipment for the general public. The company sold its car radio business to Texstar, which will use the Motorola name in the U.S. and Canada. Motorola also sold its Italian subsidiary Autovox, which makes TV sets, audio and car radio equipment, to a Swiss company, ending its direct involvement in consumer electronics. Its former TV-radio operation is now Quasar Electronics, a subsidiary of Matsushita. Motorola will continue to manufacture automotive electronic equipment, including radios, for sale to car manufacturers.

DAVID LACHENBRUCH
CONTRIBUTING EDITOR

Facts from Fluke on low-cost DMM's

Is this any way to treat a \$139 multimeter?

In the rough world of industrial electronics, even a precision test instrument can get treated like dirt. You need all the ruggedness and dependability you can get in a DMM for field use.

You'll find these qualities and more in the Fluke line of low-cost DMM's. Our DMM's have been dropped from towers, stepped on, and run over by construction equipment. And they've survived because we never cut corners on quality, even on our lowest-priced, six-function Model 8022A Troubleshooter at \$139 U.S.

Take a close look at a low-cost DMM from Fluke and you'll notice tough, lightweight construction that stands up to the hard knocks of life.


Sturdy internal design and high-impact, flame-retardant shells make these units practically indestructible. Right off the shelf, they meet or exceed severe military shock/vibration tests.

Even our LCD's are protected by cast-tempered plastic shields. We use rugged CMOS LSI circuitry for integrity and endurance, and devote a large number of


components to protection against overloading, accidental inputs and operator errors.

We go to these lengths with all our low-cost DMM's to make sure they are genuine price/performance values. You can count on that. Because, that's what leadership is all about.

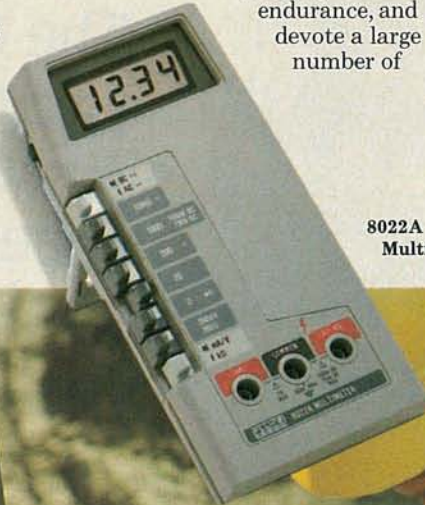For more facts on DMM reliability and where to find it, call toll free **800-426-0361**; use the coupon below; or contact your Fluke stocking distributor, sales office or representative.



8022A
Multimeter

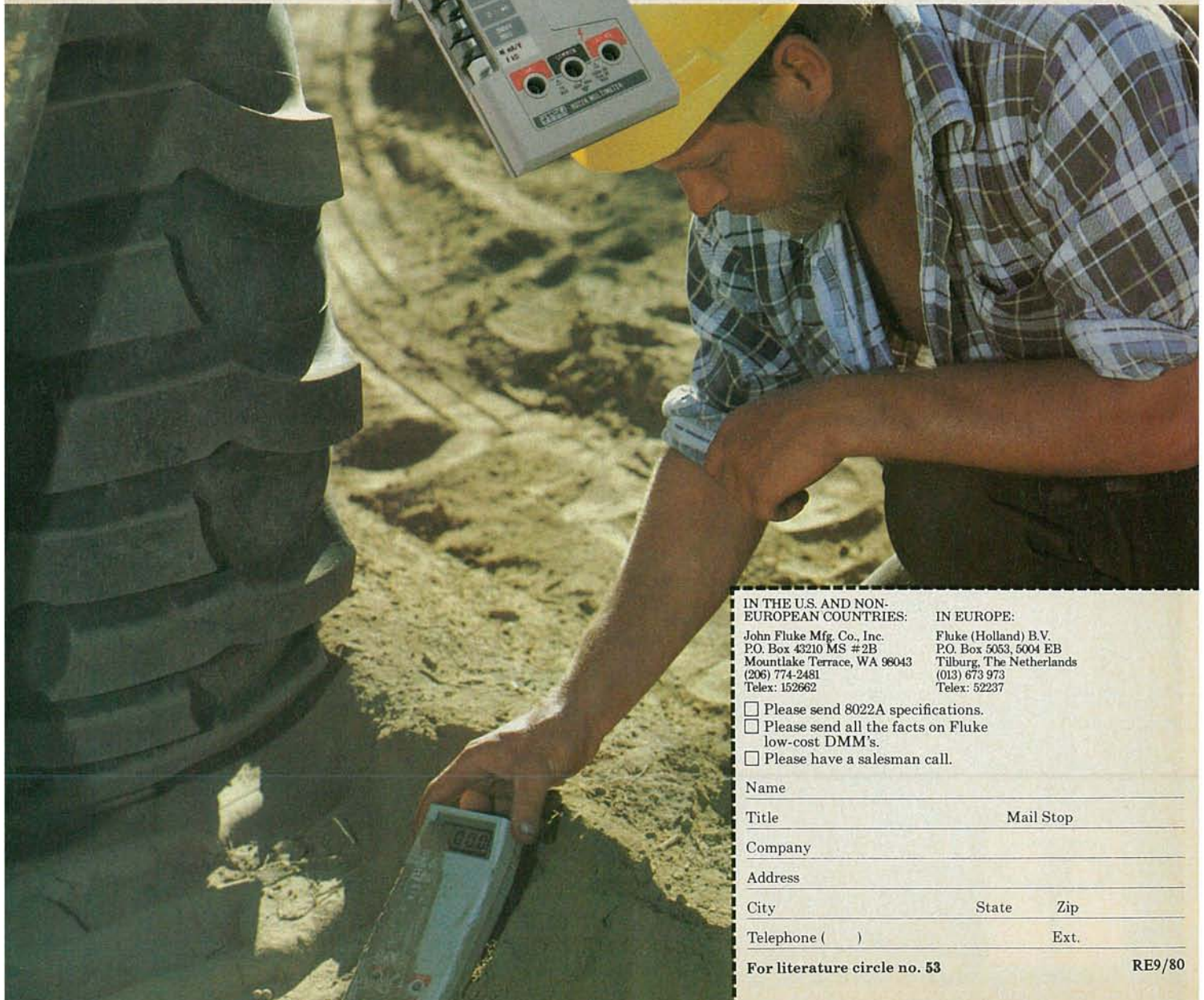

IN THE U.S. AND NON-EUROPEAN COUNTRIES:

John Fluke Mfg. Co., Inc.
P.O. Box 43210 MS #2B
Mountlake Terrace, WA 98043
(206) 774-2481
Telex: 152662

IN EUROPE:

Fluke (Holland) B.V.
P.O. Box 5053, 5004 EB
Tilburg, The Netherlands
(013) 673 973
Telex: 52237

- Please send 8022A specifications.
- Please send all the facts on Fluke low-cost DMM's.
- Please have a salesman call.

Name _____

Title _____ Mail Stop _____

Company _____

Address _____

City _____ State _____ Zip _____


Telephone () _____ Ext. _____

For literature circle no. 53

RE9/80

INTRODUCING HOBBY-BLOX™

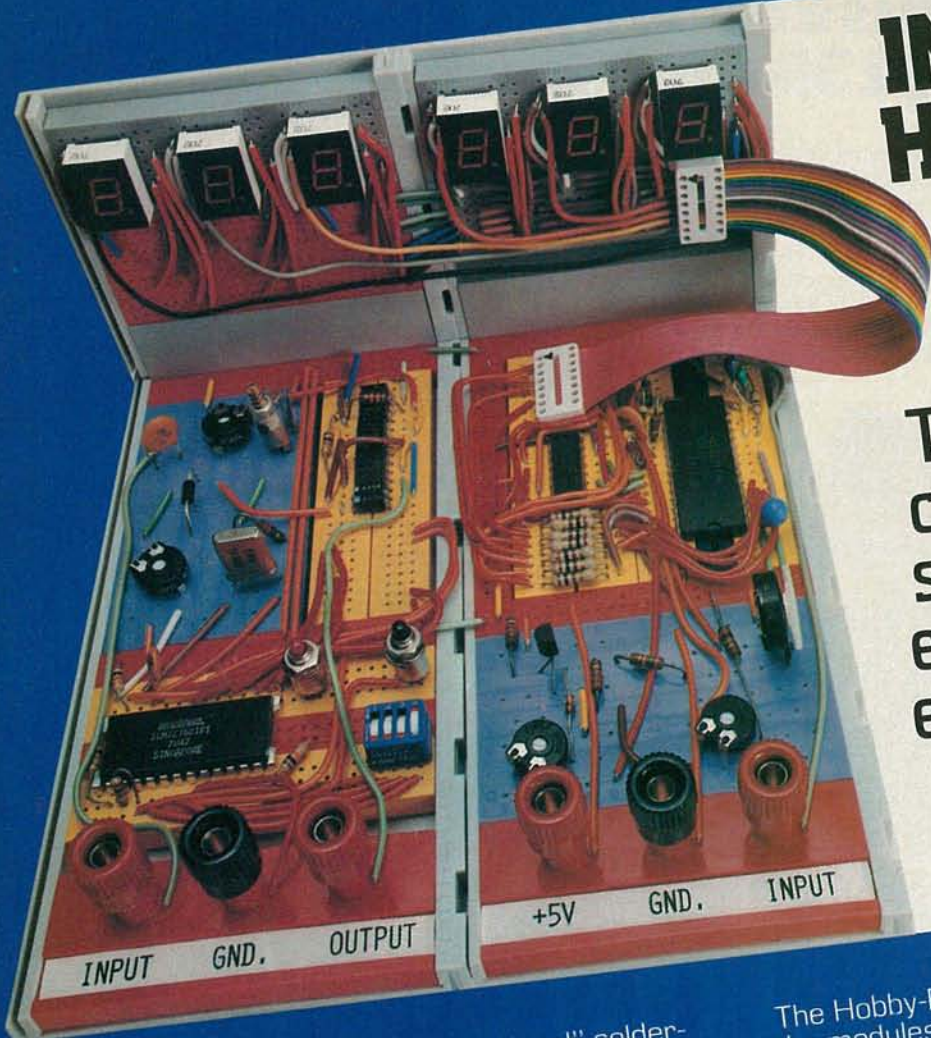The new modular
circuit building
system designed
especially for
electronic hobbyists.



Until now, you had to buy "professional" solderless breadboards for your projects and pay "professional" prices. Now there's Hobby-Blox™, a totally new circuit-building system that's not only economically priced but offers many more advantages to the hobbyist.


At the core of the system are two expandable starter packs (priced under \$7.00), one for discrete component projects, the other for integrated circuit projects. Each comes with a number of Hobby-Blox modules that fit into a tray and an illustrated project booklet. In addition, the system includes 14 separate component packs you can purchase individually — terminal, distribution and bus strips, speaker panels, binding posts, etc. — priced from \$1.29 to \$3.59.

The Hobby-Blox system is easy to use because the modules are color-keyed and letter/number indexed. It's time-saving, because they're solderless. It's compatible with DIP's of all sizes and a wide variety of discrete components. And you save money, because the parts can be reused again and again.

How far can you go with the Hobby-Blox system? Take a look at the example above. Then you'll know why we say, "your only limit is your own imagination!"

For a free catalog and the name of your nearest Hobby-Blox dealer call toll-free (800) 321-9668.

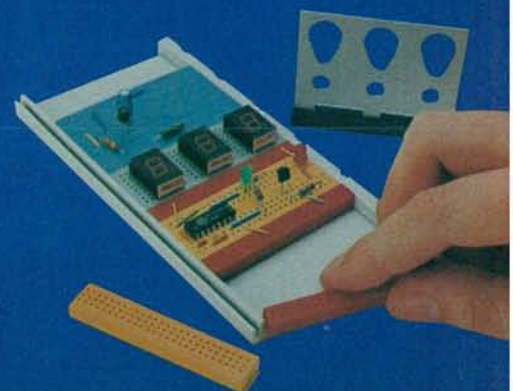Patents Pending
© A P PRODUCTS INCORPORATED 1980
Prices shown are current suggested U.S. resale.



A P PRODUCTS INCORPORATED
1359 West Jackson Street
Painesville, Ohio 44077
(216) 354-2101

In Europe, contact A P PRODUCTS GmbH
Bäumlesweg 21 • D-7031 Weil 1 • W. Germany

CIRCLE 8 ON FREE INFORMATION CARD

Weather "color" radar to get distance control

A new technique that enhances the value of airborne weather radar has been announced by RCA. In 1977 that company pioneered airborne color radar, which gives an airplane pilot information not only of the presence and position of a storm, but of the strength of the precipitation. The colors vary from green, for lightest rainfall, to red, the most intense.

Present radars give excellent information to the pilot trying to fly around a storm. But they can—and often do—underestimate the intensity of precipitation in its remoter areas. That is because signals from those areas are attenuated by the heavy rain in the nearer parts. Thus, if a radar display shows a yellow area behind a red one, it can mean either that the rain is lighter behind the intense storm or that the rain in the red area has so weakened the signal that intense precipitation behind the red area is being understated as yellow.

REACT (Rain Echo Attenuation Compensation Technique) acts as a sort of automatic gain control that compensates for attenuation by water drops in the closer parts of the storm by increasing the gain of the radar receiver for the more distant areas by an amount equal to the two-way attenuation through the nearer ones.

If the return signal is too weak to be seen even with REACT, the radar displays a blue, or "blind" area, which tells the pilot that the intensity of the storm in that area is unknown—it cannot be seen by the radar.

50-inch flat TV "tube" to arrive before 1990?

The concept of a 30 × 40-inch (50-inch diagonal) flat TV display was described by

RCA scientists to the Society of Information Display at their recent conference in San Diego, CA. The new picture-on-the-wall "tube" will have decided advantages in brightness and picture quality over present projection equipment of similar size and will require far less space.

The display would consist of 40 modules, each 1 inch wide and 30 inches high. (Experimental displays of up to five modules have been constructed, but no complete unit has yet been made.) As in earlier concepts of a flat TV tube (*Radio-Electronics*, March 1957, page 43) the electron gun projects its beam parallel to the phosphor screen. To turn the beam (and control vertical scanning) one of a series of horizontal wires—normally held between 250 and 350 volts positive—is switched negative (50 to 100 volts). That repels the beam, "extracting" it and sending it at a right angle through mesh-like beam guides—maintained at 40-80 volts positive—to the phosphor screen, held at about 1300 volts. Vanes on each module scan the beam horizontally across the screen. Program modulation is applied through a series of vertical wires or electrodes.

As to when the new tube (or display) will be perfected, an RCA spokesman says: "While we are optimistic, we are by no means certain as to when all the problems facing us will be overcome. It will probably be close to 1990 before such a flat panel display can be manufactured at a price the home consumer will be willing to pay."

Pocket calculator includes two-hundred-year calendar.

The Toshiba *Time Capsule* liquid crystal calculator, just announced, includes the standard four functions, square root, per-

cent, memory and the rest. But in addition, it is programmed to give you the day of the week in which any date falls—80 years in the past and 120 years in the future. That should be particularly useful to production planners who have to know on what days week-ends and holidays fall, sometimes farther in advance than available calendars show.



THE TOSHIBA LC-840WA CALCULATOR can show, at one time, the calendar for the month, with present date flashing, the time down to the second, and the time for which the alarm has been set.

The little calculator also provides a digital clock service and a 24-hour alarm that can be preset for two times in one day or be preprogrammed up to a month in advance.


As a special feature, the *Time Capsule* can also show the entire calendar, a month at a time, with the present day flashing. The calculator measures 4.9 × 2.7 × 0.3 inches. Suggested retail price is \$59.95.

Magnavox will make no claims on AM stereo broadcasters

Magnavox Consumer Electronics Co. will not assert its AM Stereo broadcast patents against broadcasters or broadcast equipment manufacturers, says Magnavox president Meinken. However, "a reasonable license fee will be charged to receiver manufacturers."

The Magnavox AM Stereo system was approved by the FCC early last April. The company points out that among the advantages of the system are its pilot tone, which can be used to switch the receiver from mono to stereo automatically, at the same time turning on a light that tells the listener the program is in stereo. The pilot tone can also carry a third channel of alphanumeric data, such as call letters or a weather alert.

continued on page 13

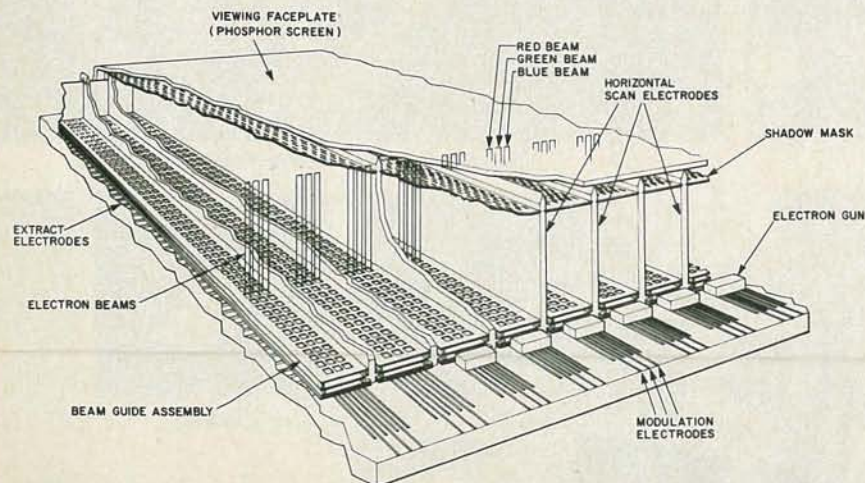

THE FLAT-PANEL TV DISPLAY would consist of 40 modules, each with its own electron gun, beam guides, and modulation electrodes, fastened side-by-side to form a 40-inch-wide and 30-inch-high display. RCA scientists hope that the new "tube" will reach the market some time before 1990.

NRI will train you at home to be an electronics professional in the growing world of communications.

Learn to service, repair, and install everything from microwave antennas
to two-way radios...from radar sets to TV transmitters.

TV Tape Recorders



TV Broadcasting



Antenna Systems




Marine Communications



Aviation Communications & Navigation Systems



Direction Finders, Loran

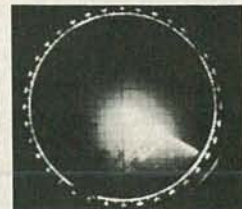

Radar

No other home-study course gives you such complete, professional training in so many fields of communication. No other gives you the actual bench training with kits and demonstration units specially designed for learning. Only NRI gives you the thorough preparation and training you need to achieve professional competence in the wide world of communications.

Learn at Home in Your Spare Time

Learn at your own pace, right in your own home. There's no need to quit your job or tie up your evenings



Mobile Radio



Aircraft Guidance & Landing Systems



Microwave Relay



AM & FM Broadcasting

with night classes. No time or gas wasted traveling to school...NRI brings it all to you. You learn with NRI-pioneered "bite-size" lessons and proven, practical "power-on" training.

Build Your Own 2-Meter, Digitally Synthesized VHF Transceiver or 40-Channel CB

NRI training is "hands-on" training. You get honest bench experience as you build and test this industrial-quality two-way radio and power supply. You reinforce theory lessons as you induce and correct faults, study individual circuits and learn how they interface with others. Or, at your option, you can train with a full forty-channel mobile CB and base-station power supply converter.

You also build and keep for use in your work a transistorized volt-ohm



CB Radio

meter and digital CMOS frequency counter. NRI even gives you special lessons to get your Amateur License so



you can go on the air with your VHF transceiver.

FCC License or Full Refund

In all, you get 48 lessons, 9 special reference texts, and 10 training kits...the training you need to become a professional. And NRI includes training for the required FCC radiotelephone license examination. You pass or *your tuition will be refunded in full*. This money-back agreement is valid for six months after the completion of your course.

Free Catalog, No Salesman Will Call

NRI's free, 100-page full-color catalog shows all the equipment you get, describes each lesson and kit in detail, tells more about the many specialized fields we train you for. It includes all facts on other interesting areas like TV and audio servicing or digital computer electronics. Mail the postage-paid card and see how we can make you a pro.

If the card has been removed, write to:



NRI Schools

McGraw-Hill Continuing
Education Center
3939 Wisconsin Ave.
Washington, D.C. 20016



Digital IC Probe & Logic Pulser

PRB-1 DIGITAL LOGIC PROBE

Compatible with DTL, TTL, CMOS, MOS and Microprocessors using a 4 to 15V power supply. Thresholds automatically programmed. Automatic resetting memory. No adjustment required. Visual indication of logic levels, using LED's to show high, low, bad level or open circuit logic and pulses. Highly sophisticated, shirt pocket portable (protective tip cap and removable coil cord).

Automatic threshold resetting • DE to > 50 MHz

Compatible with all logic families 4-15 VDC • 10Nsec. pulse response

Supply O.V.P. to ± 70 VDC • 120 K Ω impedance

No switches/no calibration • Automatic pulse stretching to 50 Msec.

Open circuit detection • Automatic resetting memory

Range extended to 15-25 VDC with optional PA-1 adapter

PLS-1 LOGIC PULSER

The PLS-1 logic pulser will superimpose a dynamic pulse train (20 pps) or a single pulse onto the circuit node under test. There is no need to unsolder pins or cut printed-circuit traces even when these nodes are being clamped by digital outputs.

PLS-1 is a multi-mode, high current pulse generator packaged in a hand-held shirt pocket portable instrument. It can source or sink sufficient current to force saturated output transistors in digital circuits into the opposite logic state. Signal injection is by means of a pushbutton switch near the probe tip. When the button is depressed, a single high-going or low-going pulse of 2 μ sec wide is delivered to the circuit node under test. Pulse polarity is automatic: high nodes are pulsed low and low nodes are pulsed high. Holding the button down delivers a series of pulses of 20 pps to the circuit under test.

High input impedance (off state) 1 meg ohm • Multi mode-single pulses or pulse trains

Low output impedance (active state) 2 ohms • Automatic polarity sensing

Output pulse width 2 μ sec nominal • Automatic current limiting; 7 amps nominal

Input over voltage protection +50 volts • Automatically programmed output level

Finger tip push button actuated • Circuit powered

Power lead reversal protection • No adjustments required

Multi-family RTL, DTL, TTL, CMOS, MOS and Microprocessors.

PRB 1	DIGITAL LOGIC PROBE	\$56.95	PA 1	HIGH VOLTAGE ADAPTER	\$8.50
PC 1	POWER CORD, Alligator Clips	\$4.95	PT 2	REPLACEMENT PROBE TIP (2)	\$1.50
PC 2	POWER CORD, Micro Hooks	\$9.95	PLS 1	LOGIC PULSER	\$48.95

OK Machine & Tool Corporation

3455 Conner St., Bronx, N.Y. 10475 U.S.A.

Tel. (212) 994-6600 Telex 125091

* Minimum billings \$25.00, add shipping charge \$2.00
New York State residents add applicable tax

what's news

continued from page 7

TV sales off in early 1980— home VTR sales on the rise

Sales of color television sets to retailers in the first 17 weeks of 1980 were 2,811,307, reports the Electric Industries Association. That is a decline of 5.7 percent from the 2,980,951 sets sold during the same period in 1979. Black-and-white sales in the same period were 1,593,733, a decrease of 12.4 percent from the 1,818,667 units sold in the first 17 weeks of last year.

Home video-tape recorder sales to retailers jumped 57.1 percent over last year—189,550 units as against 120,674 sold in the first 17 weeks of 1979.

New energy-saving light bulb

North American Philips Lighting Corporation has developed a new type of light bulb that, when compared with the conventional incandescent lamp, will last 7½ times longer and use 70% less energy. The new lamp is an 11-watt, low-pressure mercury lamp of the fluorescent type, and is similar in size and shape to conventional bulbs; it is designed to fit standard light sockets.

Low-pressure sodium lamps first appeared in Europe, during the 1930's and were about as efficient as mercury vapor lamps, which produced 40 lumens per watt. The new lamps achieve a fourfold increase in efficiency by integrating the development of rare earth fluorescent powders and radical miniaturization. The light in the new bulbs is generated by converting ultraviolet radiation to visible light by means of using fluorescent powder on the inner surface of the bulb wall. The new rare earth powders also opened up the possibility of combining good color-rendering qualities with high efficiency.

The new lamp is expected to replace standard light bulbs for both indoor and outdoor use in private homes, apartments, garages, commercial buildings, and stores. It has low glare, provides excellent contrast, and is not affected by changes in the surrounding temperature. It will be available in 240- and 120-volt versions. 120 volts is the predominant range in the United States and it will be available in the U.S. market early in 1981.

A comparison between the cost, length of life, and performance of a standard 60-watt soft-white incandescent lamp and one of the new SL-18 lamps shows the following: The incandescent lamp has a life expectancy of 1000 hours, while the new lamp has a life expectancy of 7500 hrs. The new lamp costs \$12.00. To obtain the equivalent life span, 7½ incandescent lamps are required at a cost of \$.85 each, for a total cost of \$6.37. During the 7500-hour life span, the incandescents will consume 450 kilowatt-hours while the SL-18 consumes 135 kilowatt-hours. The savings



THE NEW SL-18 is close in size to the standard 60-watt incandescent lamp, and is designed to fit standard light sockets. It will last 7½ times longer than the old-style bulb and consume 70% less energy, reflecting a substantial decrease in the user's electric bills.

in the user's electric bill depend upon the unit cost per kilowatt-hour; at 2¢ per kilowatt-hour, the incandescents cost \$9.00, the SL-18 \$2.70 (\$6.30 saved). At 4¢ per kilowatt-hour, the incandescents cost \$13.50, the SL-18 \$4.05 (\$9.45 saved). At 6¢ per kilowatt-hour, the incandescents cost \$27.00, the SL-18 \$8.10 (\$18.90 saved); and the savings increase where the unit price for energy is higher.

Worldwide, the lamps will immediately be available in four wattages: 11 watts, 13 watts, 18 watts, and 25 watts, as direct replacements for the standard 40-watt, 60-watt, 75-watt, and 100-watt incandescent lamps most widely used today. There can be no doubt that the reduced energy consumption, reflected in lower electric bills, and the longer life of the new bulb will more than offset the higher initial price.

Technologies of the '80's may alter our lifestyles

Westinghouse scientist George F. Mechlin described—at a Pittsburgh press briefing on "Technologies of the '80's: Myths, Facts, and Promises"—seven technologies that will have a significant impact on American society in the next decade. At the same time, he warned against the "myth" that any one of them—or all of them combined—can present a "quick fix" for our present difficulties.

The seven technologies are:

Lasers, already handling fantastic tasks, and beginning to be used to harden metals, read video discs, and separate uranium.

Optics, now able to transmit a million telephone calls for only .001 watt of laser light, and which will make information-processing a billion times faster than is remotely

possible with present technology.

Microprocessors, which will invade every field of industry, transform office procedures, and have a bigger impact on our home life than the changes brought about by TV.

Robotics, to do the dangerous, heavy, hot, and monotonous jobs now handled by human beings.

Solar power, use of which will increase as and when it becomes economical.

Coal conversion, into gas, oil, gasoline or methanol, generating power without the present pollution.

Fuel cells, which will be developed into compact, efficient, and non-polluting energy sources.

But, Dr. Mechlin warned, the very promise of technology has led to several overoptimistic myths that will lead to disillusionment. Most dangerous of those is the Myth of the Quick Fix, which leads many to hope for a near-immediate solution of many present difficulties—particularly of the energy problem.

"An alarming mistake," stated Dr. Mechlin, firmly. "No technical innovation has ever taken hold immediately. Even if a new energy source were discovered tomorrow, it would be unlikely to go 'on line' until the next century."

World's longest single-span fiber- optic video link

The longest single-span fiber-optic video service in use today was completed last April by Times Fiber Communications and is part of Vision Cable's system serving 20,000 cable-TV subscribers in 13 New Jersey communities. The new 2.4-kilometer link, that was completed in only six days, uses no repeaters and carries five channels per-fiber with studio-transmission quality, demonstrating the practicality of Fiber-optic communications.

It consists of three-conductor optical cable and electro-optical equipment manufactured by Times. One fiber-conductor serves as a final leg for televised sports events presented at Madison Square Garden and Nassau Coliseum. The fiber carries the signals from microwave receivers at the headend to the studio for signal-processing and programming. A second fiber returns the program material, along with satellite signals and other studio-originated channels, to the headend for distribution to the subscribers. A third fiber will be used for future programming.

The system is Frequency-modulated and exceeded contract performance specifications, with a measured 53-58 dB signal-to-noise level and no visible degradation of the picture. Vision Cable supplies 130,000 subscribers in the east and north, and additional fiber-optic links are planned for the future.



KEITHLEY

VIZ formerly RCA

TRIPLETT



PHILIPS

HICKOK



New Portable Digital Capacitance Meter

BK PRECISION



Call For Our Price

MODEL 820

- Measures capacitance from 0.1 pF to 1 Farad
- Resolves to 0.1 pF
- 10 ranges for accuracy and resolution
- 4 digit easy-to-read LED display
- 0.5% accuracy
- Special lead insertion jacks or banana jacks
- Fuse protected
- Uses either rechargeable or disposable batteries
- Overrange indication

FLUKE® DIGITAL MULTIMETERS

Model 8022A: The Troubleshooter

\$139

- Six functions
- 3½-digit resolution
- dc voltage
- ac voltage
- dc current
- ac current
- resistance
- diode test
- 0.25% basic dc accuracy
- LCD display
- Overload protection

Model 8020A: The Analyst

\$179

Model 8024A: The Investigator

\$219



NEW

• Seven functions

- dc voltage
- ac voltage
- dc current
- ac current
- resistance
- diode test
- conductance (1/R)
- 3½-digit resolution
- 0.1% basic dc accuracy
- LCD display
- Overload protection
- Free case
- Two year parts and labor warranty

• Nine functions

- dc voltage
- ac voltage
- dc current
- ac current
- resistance
- diode test
- conductance (1/R)
- logic level and continuity detect
- temperature (K-type thermocouple)
- Peak hold on voltage and current functions
- Selectable audible indicator for continuity or level detection
- 3½-digit resolution
- 0.1% basic dc accuracy
- LCD display
- Overload protection

DATA PRECISION Model 938 0.1%, 3½-Digit, LCD DIGITAL CAPACITANCE METER



\$179

- WIDE RANGING — from 199.9 pF full scale (0.1 pF resolution) up to 1999 µF full scale, in eight ranges...virtually every capacitance you'll ever need to measure.
- FAST AND EASY TO USE — Direct reading, pushbutton ranges. Just plug in and read.
- EXCEPTIONALLY ACCURATE — provides ±0.1% basic accuracy.
- TOUGH AND COMPACT — Built to take rough usage without loss of calibration accuracy. Fits and goes anywhere; takes very little bench space; always handy for quick capacitance checkout, matching, calibration, and tracking.
- PORTABLE — Palm-sized, light-weight, operates up to approximately 200 hours on a single 9V alkaline battery.
- EASY READING — big, clear, high-contrast 3½-digit LCD display, a full 0.5" high, readable anywhere.
- VALUE PACKED — Outstanding measurement capability and dependability. Outperforms DC time-constant meters, and even bridges costing 2 to 5 times as much.
- RELIABLE — warranted for 2 full years.

HICKOK

LX304 DIGITAL MULTIMETER

FAST, EASY,
ONE HAND
OPERATION

NEW



AVAILABLE NOW
\$89⁹⁵

New Low Distortion Function Generator

BK PRECISION



Call For Our Price

MODEL 3010

- Generates sine, square and triangle waveforms
- Variable amplitude and fixed TTL square-wave outputs
- 0.1 Hz to 1MHz in six ranges
- Push button range and function selection
- Typical sine wave distortion under 0.5% from 0.1Hz to 100kHz
- Variable DC offset for engineering applications
- VCO external input for sweep-frequency tests

New Sweep/Function Generator

BK PRECISION



Call For Our Price

MODEL 3020

- Four instruments in one package—sweep generator, function generator, pulse generator, tone-burst generator.
- Covers 0.02Hz-2MHz
- 1000:1 tuning range
- Low-distortion high-accuracy outputs
- Three-step attenuator plus vernier control
- Internal linear and log sweeps
- Tone-burst output is front-panel externally programmable

Simpson

BK PRECISION

LEADER

DORIC

Non-Linear Systems

WESTON

DATA PRECISION

PORTABLE OSCILLOSCOPES
BATTERY OPERATED

MS-15



Single Trace 15MHz
Reg. price \$349.
\$299⁹⁵

Non-Linear Systems

S-215



Dual Trace 15 MHz
Reg. price \$465.
\$399⁹⁵

MS-230



Dual Trace 30MHz
Regular price \$598.
\$499⁹⁵

THESE 1980 B&K OSCILLOSCOPES ARE IN STOCK AND AVAILABLE FOR IMMEDIATE DELIVERY



BK PRECISION

- 1479A Dual-Trace 30 MHz
- 1477 Dual-Trace 15 MHz
- 1432 Dual-Trace 15 MHz Portable
- 1476 Dual-Trace 10 MHz
- 1466 Single-Trace 10 MHz
- 1405 Single-Trace 5 MHz

CALL FOR OUR EARLY BIRD SPECIAL LOW PRICE

KEITHLEY

Model 169
BENCH/PORTABLE DMM

- 3½ Digit liquid crystal display
- 0.25% basic accuracy
- 26 Ranges

\$15900



WESTON

The Roadrunner
Model 6100

- 5 Range audible signaling function
- 0.5" LCD display
- 6 Functions
- 29 Ranges

\$13900



**BEEP!
BEEP!**

80MHz Counter with Period Function



MODEL 1820

- 5Hz to 80MHz reading guaranteed—100MHz typical
- Period measurements from 5Hz to 1MHz.
- Period average, auto and manual positions
- One PPM resolution
- Totalizes to 999999 plus overflow
- Elapsed time measurements from .01 to 9999.99 seconds plus overflow
- One-megohm input resistance
- Bright .43" high LED readouts

BK PRECISION

Call For Our Price



THE TEST EQUIPMENT SPECIALISTS
TOLL FREE HOT LINE
800-223-0474



54 WEST 45th STREET, NEW YORK, N.Y. 10036 212-687-2224

ADVANCE ELECTRONICS

PUBLISHER'S LETTER

Home-Study Schools Cancelled GI Bill Not Funded

That could be a minor headline in your local newspaper in the not-too-distant future. Actions now taking place in Congress could make that headline happen.


Radio-Electronics carries a good deal of Home-Study school advertising. It is important to our readers. So when an action occurs that may reduce its availability to many of our readers, we feel it is important enough to tell you the facts.

Here's the story. On June 3, 1980, the Veterans Affairs Committee reported to the budget committee of the House of Representatives and recommended that home-study and flight school instructions no longer be funded through the Veterans Administration. If that recommendation is passed by Congress, Veterans will no longer receive this important benefit.

Why are we so concerned? After all the veteran could still attend a resident school and have his education paid for. There are several practical problems with this answer.

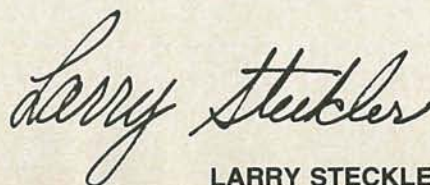1. **There may be no resident school** in the city where the veteran lives.
2. **Even if there is a resident school** in the city where he lives, it may not be convenient for him to reach it after work.
3. **Some resident schools** do not offer the best possible training, and if a veteran can only attend a resident school, his freedom of choice is severely limited.
4. **Correspondence schools permit the student to learn** at his own pace and fit his education into his own schedule. Thousands of veterans have taken home-study school courses and made those courses an important part of their career training. Personally, I got started in electronics by taking a DeForest Technical Training course while I was in the US Army. I finished it after being discharged.
5. **Home-Study schools are much less expensive** than the equivalent resident school. Resident schools can cost from two to five times as much—so eliminating home-study can actually increase the cost of providing benefits.

Radio-Electronics has a vested interest in not losing the advertising dollars we earn each year from correspondence school advertising. But we have an even greater interest in the future of our country and the careers of its veterans. If you agree with our viewpoint, it is urgent that you contact your Congressmen immediately. Let them know that you do not want them to take this extremely important benefit away. Write a letter, a mailgram, or send a telegram right now. Tomorrow could be too late.



LARRY STECKLER
Publisher

Radio- Electronics

Hugo Gernsback (1884-1967) founder

M. Harvey Gernsback, editor-in-chief

Larry Steckler, CET, publisher

Arthur Kleiman, managing editor

Josef Bernard, K2HUF,
technical editor

Jack Darr, CET service editor

Leonard Feldman
contributing high-fidelity editor

Karl Savon, semiconductor editor

Herb Freidman, communications editor

David Lachenbruch, contributing editor

Earl "Doc" Savage, K4SDS, hobby editor

Ruby Yee, production manager

Robert A. W. Lowndes, production
associate

Marie J. Stolfi, production assistant

Gabriele Margules, circulation director

Arline R. Fishman,
advertising coordinator

Cover design by Louis G. Rubsamen

Cover photo by Robert Lewis

Radio Electronics is indexed in *Applied
Science & Technology Index and Readers
Guide to Periodical Literature.*

Gernsback Publications, Inc.
200 Park Ave. S., New York, NY 10003
(212) 777-6400
President: M. Harvey Gernsback
Vice President: Larry Steckler
Secretary/Treasurer: Carol A. Gernsback

ADVERTISING SALES

Larry Steckler
Publisher

EAST

Stanley Levitan
Radio-Electronics
200 Park Ave. South
New York, NY 10003
(212) 777-6400

MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen
The Ralph Bergen Co.
540 Frontage Road—Suite 361-A
Northfield, Illinois 60093
(312) 446-1444

PACIFIC COAST Mountain States

Jay Eisenberg
J.E. Publishers Representative Co.,
8732 Sunset Blvd.,
4th Floor,
Los Angeles, CA 90069
(213) 659-3810
San Francisco, CA 94124
(415) 864-3252

SOUTHEAST

Paul McGinnis
Paul McGinnis Company
60 East 42nd Street
New York, N.Y. 10017
(212) 490-1021



Sabtronics gives you DMM and Frequency Counter kits with more features, better performance and incredibly lower prices

Model 2010A Bench/Portable DMM: \$79.95 kit

Features: 3½ digit LED display • 31 measurement ranges 6-Functions • 0.1% Basic DCV accuracy • Touch-and-hold capability • Hi-Lo Ohms • 40 Hz to 40 kHz frequency response • Auto Zero, Auto Polarity • Overload protected • Overrange indication • Single chip LSI logic • Laser-trimmer resistor network and ultra-stable band-gap reference for better long term accuracy • Built-in NiCd battery charging circuit.

Brief Specifications: DC Volts 100µV to 1000V in 5 ranges; AC Volts 100µV to 1000V in 5 ranges; DC Current 0.1µA to 10A in 6 ranges; AC Current 0.1µA to 10A in 6 ranges; Resistance 0.1Ω to 20MΩ in 6 ranges; Diode Test Current 0.1µA to 1mA in 3 ranges; Input impedance, 10MΩ on AC and DC volts; Power requirement, 4.5 to 6.5 VDC (4 "C" cells) or optional AC adapter/charger.



\$79.95



\$89.95

Model 2015A Bench/Portable DMM: \$89.95 kit

Same features and specifications as Model 2010A except with large, 0.5" LCD 3½ digit display.

Optional Accessories:


- #AC-115, AC adapter/charger \$7.95
- #THP-20, Touch and Hold Probe \$19.95
- #NB-120 NiCd Battery Set \$18.75

Model 8610A Frequency Counter: \$99.95 kit

Features: 8-digit LED display • 10 Hz to 600 MHz guaranteed frequency range (5 Hz to 750 MHz typical) • 3 Gate times • 10 MHz TCXO Time base • Auto decimal point • Overflow indicator • Leading zero blanking • Resolution to 0.1 Hz • Built-in charging circuit for NiCd batteries.

Brief Specifications: Frequency Range, switch selectable, 10 MHz, 100MHz, 600 MHz • Sensitivity, ± 10mV RMS to 100 MHz, ±50mV RMS, 100 MHz to 450 MHz; 90mV RMS 450 MHz to 600 MHz • Impedance, 1 MΩ, 10 MHz and 100 MHz ranges; 50Ω, 600 MHz range • Gate time (switch selectable) 0.1 sec, 1 sec, 10 sec • Temperature stability, 0.1 ppm/°C • Ageing rate < ± 5 ppm/yr • Accuracy, 1 ppm or 0.0001% • Input protection, 150V RMS to 10 kHz (declining with frequency) • Power Requirement, 4.5 to 6.5V DC @ 300mA (4 "C" cells) or optional AC adapter/charger (7.5 to 9V DC @ 300mA).

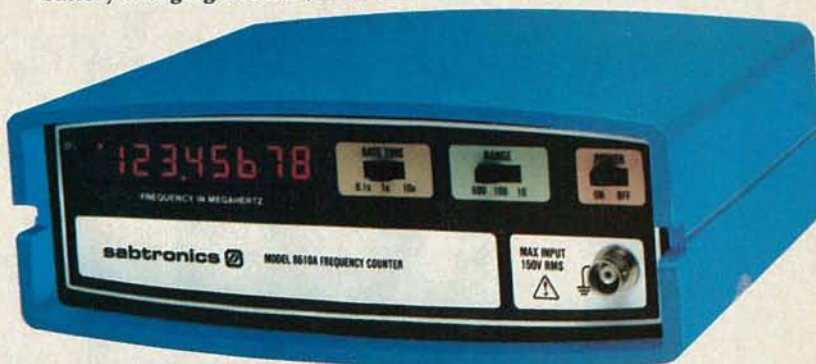Also available Model 8110A, same as 8610A except maximum frequency is 100MHz and without battery charging circuit: \$69.95 kit



\$99.95

(813) 623-2631

sabtronics 
INTERNATIONAL INC.


5709 N. 50th Street, M/S 35, Tampa, FL 33610

In Canada contact: Kumar & Co.
Mississauga, Ont. Canada L5L 1H2

Ordering information

USA—Add \$6.00 per kit for shipping & handling. Personal checks have to clear before goods are shipped (allow 2-3 weeks). For faster delivery send cashiers check or money order. 10% deposit for C.O.D. orders. Florida residents add sales tax. OVERSEAS—Add \$25.00 per kit for airmail delivery. Payment by bank draft in U.S. funds.

**Learning
electronics
is no picnic.**

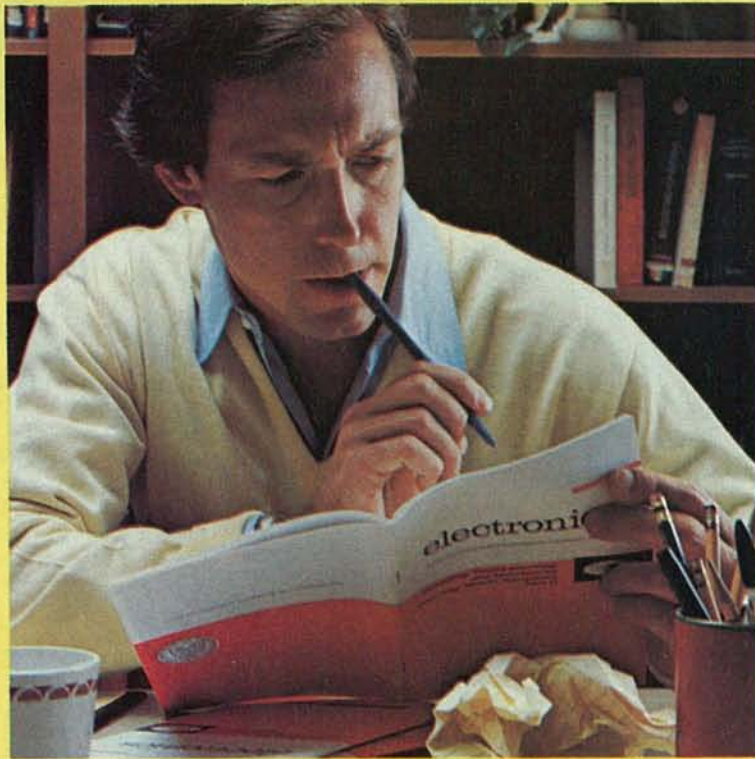

**At any level it
takes work and
a few sacrifices.
But with CIE,
it's worth it.**

Whoever said, "The best things in life are free," was writing a song, not living a life. Life is not just a bowl of cherries, and we all know it.

You fight for what you get. You get what you fight for. If you want a thorough, practical, working knowledge of electronics, come to CIE.

You can learn electronics at home by spending just 12 hard-working hours a week, two hours a day. Or, would you rather go bowling? Your success is up to you.

At CIE, you *earn* your diploma. It is not handed to you simply for putting in hours. But the hours you do put in will be on your schedule, not ours. You don't have to go to a classroom. The classroom comes to you.

Why electronics training?

Today the world depends on technology. And the "brain" of technology is electronics. Every year, companies the world over are finding new ways to apply the wonders of electronics to control and program manufacturing, processing...even to create new leisure-time products and services. And the more electronics applications there are, the greater the need will be for trained technicians to keep sophisticated equipment finely tuned and operating efficiently. That means career opportunities in the eighties and beyond.

Which CIE training fits you?

Beginner? Intermediate? Advanced? CIE home study courses are designed for ambitious people at all entry levels. People who may have:

1. No previous electronics knowledge, but do have an interest in it;
2. Some basic knowledge or experience in electronics;
3. In-depth working experience or prior training in electronics.

You can start where you fit and fit where you start, then go on from there to your Diploma, FCC License and career.

Many people can be taught electronics.

There is no mystery to learning electronics. At CIE you simply start with what you know and build on it to develop the knowledge and techniques that make you a specialist. Thousands of CIE graduates have learned to master the simple principles of electronics and operate or maintain even the most sophisticated electronics equipment.

CIE specializes exclusively in electronics.

Why CIE? CIE is the largest independent home study school that specializes exclusively in electronics. Nothing else. CIE has the electronics course that's right for you.

Learning electronics is a lot more than memorizing a laundry list of

facts about circuits and transistors. Electronics is interesting! It is based on recent developments in the industry. It's built on ideas. So, look for a program that starts with ideas and builds on them. Look to CIE.

Programmed learning.

That's exactly what happens with CIE's Auto-Programmed® Lessons. Each lesson uses famous "programmed learning" methods to teach you important principles. You explore them, master them completely, before you start to apply them. You thoroughly understand each step before you go on to the next. You learn at your own pace.

And, beyond theory, some courses come fully equipped with electronics gear (the things you see in technical magazines) to actually let you perform hundreds of checking, testing, and analyzing projects.

Experienced specialists work closely with you.

Even though you study at home, you are not alone! Each time you return a completed lesson, you can be sure it will be reviewed, graded and returned with appropriate instructional help. When you need additional individual help, you get it fast and in writing from the faculty technical specialist best qualified to

answer your question in terms you can understand.

CIE prepares you for your FCC License.

For some jobs in electronics, you must have a Federal Communications Commission (FCC) License. For others, some employers tend to consider your license a mark in your favor. Either way, your license is government-certified proof of your knowledge and skills. It sets you apart from the crowd.

More than half of CIE's courses prepare you to pass the government-administered exam. In continuing surveys, nearly 4 out of 5 graduates who take the exam get their licenses! You can be among the winners.

Today is the day. Send now.

Fill in and return the postage-free card attached. If some other ambitious person has removed it, cut out and mail the coupon. You'll get a FREE school catalog plus complete information on independent home study. For your convenience, we'll try to have a CIE representative contact you to answer any questions you may have.

Mail the card or the coupon or write CIE (mentioning name and date of this magazine) at: 1776 East 17th Street, Cleveland, Ohio 44114.



Pattern shown on oscilloscope screen is simulated.

CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114

Accredited Member National Home Study Council

YES... I want to learn from the specialists in electronics—CIE. Send me my FREE CIE school catalog plus my FREE package of home study information. **RE-95**

Print Name _____

Address _____ Apt. _____

City _____

State _____ Zip _____

Age _____ Phone (area code) _____

Check box for G.I. Bill bulletin on Educational Benefits: Veteran Active Duty

MAIL TODAY!

satellite tv news

New equipment overflows malls of Cable TV convention

As expected, the 1980 National Cable TV association convention served up a cornucopia of new satellite equipment. The CATV industry has led the way skyward in video programming—and this year's record-breaking gathering indicated that the boom in cable/satellite networking will continue. Not only were there numerous announcements about new programs, but we also saw dozens of new products, including a number of low-priced receivers that seemed more attuned to amateur use for at-home reception.

One item that generated considerable interest (along with jibes about its creating a need for satellite-dish termite exterminators) was a \$750 12-foot antenna built on redwood strips; the antenna kit includes a spherical aluminum screen reflector on the wood struts. Although a working model of the device was not on display, its builders say it does pick up a good signal; it's made by Vidiark Electronics, Box 9363, 3765 South Third Street, Memphis, TN 38109.

Small dishes were the order of the day at the NCTA convention, with such companies as Compact Video Sales (1100 West Chestnut St., Burbank, CA 91506) and familiar giants such as Gardiner Communications, Scientific-Atlanta, and Hughes demonstrating dishes under five-meters across. Hughes also introduced a device that can be added on to an existing antenna to improve its reception capability. Prodelin (PO Box 131, Hightstown, NJ 08520) unveiled its new segmented fiberglass antenna, which is now available in a 10-foot model for \$2,450. Each of the eight petals of the 10-foot model weighs under 15 pounds, which could pave the way for more affordable tracking systems.

Lindsay introduced a 12-foot TV receive-only earth terminal that uses high-tensile aluminum-petal construction. (Lindsay Specialty Products, 50 Mary Street West, Lindsay, Ontario, Canada). U.S. Tower Company (PO Drawer S, Afton, OK 74331) demonstrated its new 3.3-meter dish, priced at \$2,275 including all mounting hardware.

In all we counted well over a dozen dishes on display in the walkways and parking lots surrounding the convention center. Inside the convention hall there were scores of satellite video receivers on display. Rockwell International's Collins Transmission System division showed three new models of its SVR-4 satellite video receivers, with low carrier-to-noise ratios (such as 8.0 dB for the SBR-0A-1 receiver). Other electronic giants, such as Harris Corp., demonstrated new LNA's and video receivers.

Programming galore

Along with the stunning new hardware at the Cable TV convention came a wave of new program announcements. The most overwhelming was the news about *Premiere*, a new all-movie pay-TV service due to begin operations in January 1981. *Premiere* is a joint venture of four major Hollywood studios (Columbia Pictures, MCA-Universal, Paramount Pictures, and 20th Century Fox) and Getty Oil Co., but it will also use films from other studios and producers. *Premiere's* partners plan to offer movies on their own channel at least nine months before they are permitted to be shown on such existing pay-TV circuits as Home Box Office or Showtime—a plan that has prompted other companies to charge that the whole *Premiere* concept is illegal, a violation of antitrust laws.

Whatever the outcome of those legal snarls, the *Premiere* plan itself is massive. Not only would there be about 15 new movies

per month offered via the channel, but they would be bounced on at least two and maybe three satellites. *Premiere* has bought a transponder on Satcom I from Satellite Program Network; that circuit will probably be used for the transmissions to the western time zones. The company has access to a Comstar D2 transponder and to a Westar III circuit, one of which will be used for East-Coast transmissions or all-day service. Since Getty Oil is a major backer of the all-sports ESPN channel, some of *Premiere's* programming may share a transponder with the overflow ESPN service (the main ESPN fulltime network remains aboard Satcom I).

In addition to the *Premiere* bombshell, the cable TV convention poured forth dozens of other program announcements. Home Box Office will start a second pay-TV channel called *Cinemax*, an all-movie channel which will include some foreign movies and older movies. CBS has formed a cable-TV programming subsidiary that will send shows via Westar III to cable systems; the CBS Cable line-up will include new programs never used on the regular CBS broadcast network. Black Entertainment Television will carry an expanded line-up of college football and basketball games starting this fall, and GalaVision, the Spanish-language pay-TV network, has already started its new coverage of professional boxing matches.

In addition, most of the existing program providers using satellites today offered previews of the additional shows they'll carry during the coming year. There will be a variety of special interest shows, ranging from a Ralph Nader consumer-affairs program on Showtime to a show called "Women" (delivered via a new color-slow-scan video process) on Satellite Program Network.

Westar adds more signals

There are at least ten new program services traveling aboard the Westar satellites this summer—including the raw program material being beamed into the brand new Cable News Network headquarters in Atlanta. CNN, the latest brainchild of TV maverick Ted Turner, is the 24-hour-a-day news service that began in June. (After a long legal fight with RCA Americom, CNN has won temporary authority—at least through December—to use Satcom I Transponder #14 to send its all-news programming to cable-TV systems.) However, the programming to Atlanta from CNN bureaus around the country travels via Westar III Transponder 11. Meanwhile Western Union has also lined up a number of other customers, including Hughes TV Network with its heavy dose of sports and special programs (Westar III, Transponder 2) and Spanish International Network (Westar III, Transponder 9). Also on Westar III are CBS (Transponder 6) and ABC (Transponder 10). Satellite Communications Network is on Westar I, Transponder 4.

Around the satellite circuit

Comsat has formalized its plans for a direct-to-home satellite service; it has created a subsidiary called Satellite Television Corp. that will buy and develop programming for the proposed high-power feed. Comsat is still looking for a retail partner to sell and install the necessary small-dish receivers. And the company recently indicated that it is pushing back its target date from 1983 into 1984. Many skeptics believe that it will take much longer than that for the FCC to approve such a complicated venture.

GARY H. ARLEN

Sony Wrote the Book on VTR— Now It's on Tape!

Until now, learning about video recorders meant poring over very technical textbooks—if you could find them. Or enrolling in a highly specialized school.

But with the new Sony Basic Video Recording Course, you can easily learn everything about video tape recording using video itself as a teaching tool. At your own pace, whenever it's most convenient for you. The Sony course clearly demonstrates the theory, operation and characteristics of every major VTR unit. Including EIAJ, Betamax, VHS, U-matic, Quad and SMPTE Types A, B and C.

You'll learn everything from the fundamentals of magnetism to the sophisticated processes used in color recording. And at the end of each lesson you'll find a thorough self-review test, so you can be sure you fully understand each subject before going on to the next one.

You can order a preview tape, individual tapes on a specific subject or the entire course in Betamax or U-matic format.

COURSE CONTENTS:

The course consists of eight color video cassettes ranging from 23 to 30 minutes in length and eight supplementary booklets:

1. ELEMENTS OF MAGNETIC RECORDING, 2. VIDEO RECORDING, 3. SCANNER SYSTEMS, 4. TAPE FORMATS, 5. TAPE TRANSPORTS, 6. SCANNER SERVOS, 7. LUMINANCE PROCESSING, 8. COLOR SIGNAL PROCESSING.

The Sony Basic Video Recording Course will make you an expert on video tape recording. Whether you already own, sell or service video equipment or just have an electronics background and want to understand how it really works—this course is what you've been waiting for.

It would be hard to find a better teacher than the leader in the field—SONY.



Sony Basic Video Recording Course

I'm interested in learning VTR technology. Please send me:

BASIC VIDEO RECORDING COURSE

(8 cassettes/booklets, customized album and binder supplied)

Betamax 1 hr. 2 hr. \$395.00

(Reg. price \$503.00)

3/4" U-matic \$487.00

These prices available for limited time only. (Reg. price \$623.00)

INDIVIDUAL LESSONS

(Price per cassette/booklet)

Betamax 1 hr. 2 hr. \$61.00

3/4" U-matic \$76.00

Circle lesson # and indicate quantity desired in space provided.

1____, 2____, 3____, 4____, 5____, 6____, 7____, 8____,

PREVIEW TAPE

Betamax 1 hr. 2 hr. \$12.50

U-matic \$28.00

Add appropriate sales tax and \$1.75 per cassette (\$14.00 for complete course) for handling and shipping. (UPS in continental U.S. If outside, add \$15.00 for export charges, plus collect freight charges; special handling is extra.) Make check or money order payable to Sony Corporation. If charging to your Sony account, fill in number and enclose purchase order.

For phone orders, call: (213) 537-4300 Ext. 474 or visit your local Sony dealer.


We honor VISA or Master Charge via phone or mail.

Name _____

Address _____

City _____ State _____

Zip Code _____ Phone # _____

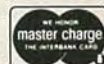

VISA/Master Charge Number _____

Exp. Date _____

Signature _____

Mail to: Sony Video Products Company, Tape Production Services, 700 W. Artesia Blvd., Compton, California 90220.

NOTE: Tapes returnable if defective when received. Please allow two weeks for delivery.

SONY VIDEO COMMUNICATIONS

Sony, Betamax and U-matic are registered trademarks of the Sony Corp.

CIRCLE 33 ON FREE INFORMATION CARD

SEPTEMBER 1980

Heath/Zenith Instruments:



Heath/Zenith instruments are professional units that give you good value for your money. A wide selection to let you choose the unit with the features you need — without paying for a lot of bells and whistles you don't. Manufactured to strict Heath/Zenith standards. Inspected at every step of assembly to assure performance to specifications. They're built to last; built to give

you reliable service. 61 U.S. and Canadian locations offer service, should it ever be necessary. Whether you need a test instrument for electronics service work, manufacturing and design, or serious hobby applications, Heath/Zenith instruments are a good choice. The selection offered here is just part of our total instrument line. Order TOLL FREE 800-253-0570.

NEW

New 10 Hz-225 MHz Frequency Counter



\$159⁹⁵

- 10 mV typical sensitivity
- Single input gives entire range
- Crystal-controlled time base
- 0.1, 1.0 second dual time gates
- Full voltage protection
- Easy-to-read 8-Digit display
- 3.38" H x 7.25" W x 9.0" D

SM-2410 159.95
(\$2.30 shipping & handling)
SMA-2400-1, Antenna 9.95
(\$1.60 shipping & handling)

NEW

New 5 Hz-512 MHz Frequency Counter



\$299⁹⁵

- Ideal for 2-way UHF work
- Ovenized, high-stability, crystal timebase
- 8-Digit resolution
- 10 mV typical sensitivity
- .01, .1, 1, 10 second gate times to fit your needs
- Trigger level control
- Frequency ratio function
- Period function
- 4.25" H x 10.0" W x 13.0" D

SM-2420 299.95
(\$2.75 shipping & handling)
SMA-2400-1, Antenna 9.95
(\$1.60 shipping & handling)

NEW

New Hand-held 512 MHz Counter



\$179⁹⁵

- Easy-to-read 7-digit display
- 10 mV typical sensitivity
- Includes nickel-cadmium batteries
- AC or battery operation
- .1 second and 1 second time gates with automatic decimal point placement
- Leading zero blanking
- Crystal-controlled time base
- Full voltage protection
- 2.0" H x 3.38" W x 8.25" D

SM-2400 179.95
(\$1.90 shipping & handling)
PS-2404 120V Battery Eliminator/
Charger (required) 4.95
(\$1.60 shipping & handling)
PS-2405 240V Battery Eliminator/
Charger (required) 12.95
(\$1.60 shipping & handling)
SMA-2400-1 Telescopic
Antenna 9.95
(\$1.60 shipping & handling)

Hand-held Multimeter gives 0.1% accuracy

\$129⁹⁵

- Measure voltage, current, resistance
- Easy-to-read Liquid Crystal Display
- Five DC voltage ranges — 200mV-1000V
- Five AC voltage ranges — 200mV-750Vrms
- Four DC current ranges — 2mA-2000mA
- Four AC current ranges — 2mA-2000mA
- Six resistance ranges — 200 Ω-20 MΩ
- Uses one 9V battery or 120/240 VAC
- 2.0" H x 3.5" W x 7.5" D

SM-2215 129.95
(\$1.75 shipping & handling)
IMA-2215-1 Leather Carrying Case .. 14.95
(\$1.60 shipping & handling)
PS-2350 120VAC Battery Eliminator .. 4.95
(\$1.60 shipping & handling)
PS-2450 240VAC Battery Eliminator .. 14.95
(\$1.60 shipping & handling)



professional quality, excellent value

General-purpose Power Supply



\$210⁰⁰

- Supplies B+, C- and filament voltages
- 0-400 VDC output at 0-100 mA continuous (125 mA intermittent)
- Output variation less than 1% from no load to full load for 100-400VDC
- Ripple less than 10 mVrms
- Output impedance 10 Ω from DC-1 MHz
- C- Voltage 0 to -100 VDC at 1mA
- Filament voltage 6.3 VAC at 4 amp.
- 5.5" H x 13.38" W x 11.25" D

SP-2717 210.00
(\$4.40 shipping & handling)

Tri-Power Supply



\$185⁰⁰

- Fixed 5 VDC at 1.5A and two continuously-adjustable 0-20 VDC at 500mA
- Interconnect outputs in any combination
- Clutch-coupled 20 VDC supplies for dual-tracking operation
- All outputs short-circuit proof
- Ripple and noise less than 5 mVrms
- Load or live regulation provides less than 0.1% (20 mV) variation on 20V supplies and less than 2% variation on 5V supply
- 4.5" H x 10.75" W x 9.0" D

SP-2718 185.00
(\$3.15 shipping & handling)

Sine-square wave Audio Generator



\$185⁰⁰

- 1 Hz-100 kHz frequency range
- 0.003-10 Vrms sine wave output (10k Ω load)
- 0.003-1 V sine wave output (600 Ω load)
- Meter calibrated in volts and dB
- -62 to +22 dB ranges
- 0.1-10 V square wave output (2000 Ω load)
- 50 nanosecond risetime
- 5.13" H x 13.25" W x 7.0" D

SG-5218 185.00
(\$2.85 shipping & handling)

Dual-trace DC-10 MHz Oscilloscope

\$650⁰⁰


- Two vertical input channels with 10 mV/cm sensitivity
- 11-step attenuator for 10mV/cm to 20V/cm deflection factors
- 19-step horizontal time base from 0.2 sec/cm to 0.2 usec/cm
- Vertical accuracy within 3%
- X5 horizontal expansion
- Calibrated 1V peak-to-peak square wave signal
- 35 ns vertical rise time
- Automatic triggering
- 120/240 VAC, switch-selectable
- 6.9" H x 12.9" W x 19.3" D

SO-4550 650.00
(\$5.50 shipping & handling)



Combination x1, x10 Scope Probe

\$29⁹⁵

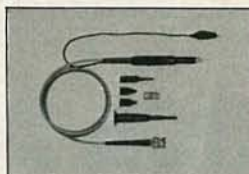

- Switch-selectable x1 and x10 attenuation at probe tip
- Center (ground) switch position allows quick zero level check
- DC to 15 MHz (x1) and DC to 80 MHz (x10) bandwidths
- 4.0 nS (x10) rise time
- Insulating tip, BNC tip adapter, IC tip, insulated compensation capacitor adjustment tool, vinyl case

PKW-105 29.95
(\$1.60 shipping & handling)

Order TOLL-FREE:
800-253-0570

8:00 AM to 8:00 PM Eastern Time M-F. Sorry, toll-free service not available in Alaska, Hawaii or Michigan. Call 616-982-3411, 24 hours a day, seven days a week. TLX: 72-9421

HEATH
ZENITH

Instruments

For information on other Heath/Zenith Instruments write:
Dept. 020-698, Benton Harbor, MI 49022
GX-383

To receive your order faster, charge it!

Use your Visa, MasterCard or Heath Revolving Charge.
Please have your card or account number handy when you call.



61 Service locations throughout the United States and Canada

Heathkit Electronic Centers in the U.S.* and Canada are listed in phone directory white pages.

*Units of Veritechnology Electronics Corporation.



SEPTEMBER 1980

letters

AUDIO POWER LEVEL METER

The Audio Power Level Meter (February, 1980 issue) can be modified to show about twice the dynamic range (55 dB) for those who like "dancing lights" down to background power levels. With 55 dB dynamic range, if the top LED is calibrated to indicate 100 watts, the bottom LED will indi-

cate .003 watt! In this modification, the meter is converted to a single-channel, 20 LED meter, and thus, two are required for stereo. The modification requires replacing R20 with a 1200 ohm, 5%, resistor and R21 with a 4,870 ohm resistor (the previous value of R20), eliminating R15, R17 and the left channel inputs, and rewiring (Fig. 1).

This modification should work with amplifiers capable of 40 watts or more per channel. R2 is still adjusted as described in my article. Adjust R16 by playing music that lights up between 8 and 12 of the LED's and adjusting for a smooth transition from the 10th to 11th LED. (This is hard to describe but easy to do!)

The standard PLM-1 kit can only be used with stereo amplifiers whose outputs include a common ground (virtually all commercial amplifiers). Unfortunately, the Talbot amplifier in your December, 1979 issue does not have a common ground between two output channels, and thus can only be used with two independent PLM's, such as those built with this modification. Also, with this modified monaural PLM, one can be placed on top of each speaker in a stereo system, making it easy for the listener to see.

Discussions with readers has shown me that many people don't realize that the pictures of the PLM-1 in my article were taken from underneath. When turned over, the PLM appears to be in a solid walnut case.

continued on page 32

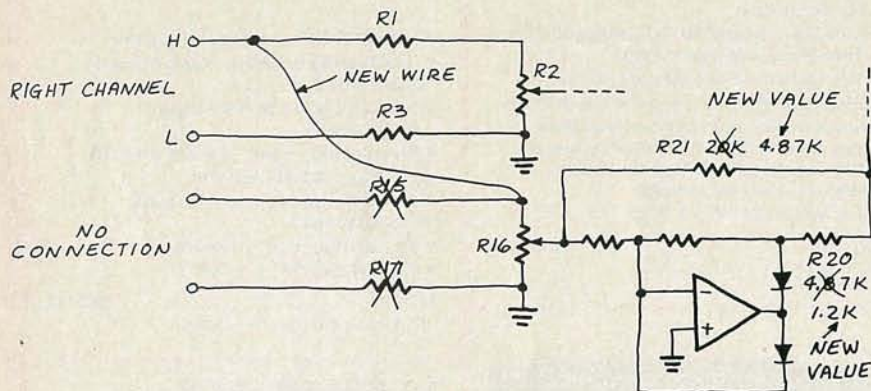


FIG. 1

RCA Permacolor TV Antennas


*Solid Connections
Solid Pictures
Solid Profits*

The best possible TV reception in almost any area. That's what your customers will get with RCA's Permacolor Outdoor TV Antennas. One of the reasons is the use of solid, riveted connections of flexible aluminum — from elements to feed line. These permanent connections provide a positive electrical path for the signal to flow. There's no chance of interruption . . . overcoming a major problem found in other antennas. Plus polypropylene insulators and a weather-resistant blue and gold polyester finish contribute to Permacolor's remarkable performance and long life.


With RCA Permacolor, you can offer your customers a complete line of outdoor TV antennas, including 75

ohm and 300 ohm antenna kits. The RCA name and tradition will assure your customers that the highest quality and performance are built into RCA Permacolor. And they're right. Permacolor brings in a better TV picture for your customers. And a better profit picture for you.

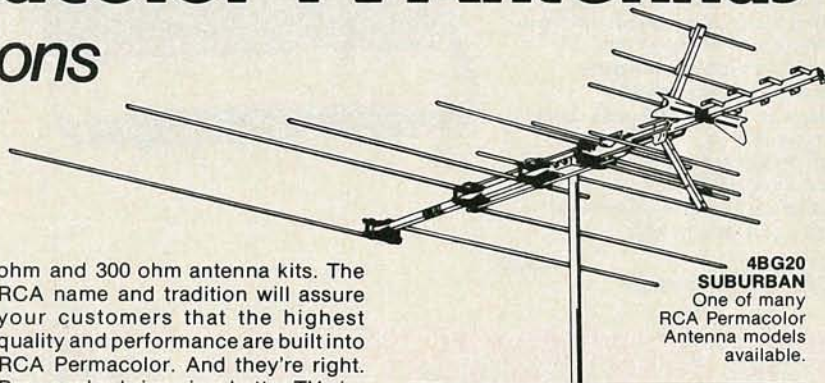For full information, see your RCA Antenna Distributor or write to: RCA Distributor and Special Products Division, Deptford, N.J. 08096, Attn: Sales Promotion Services.




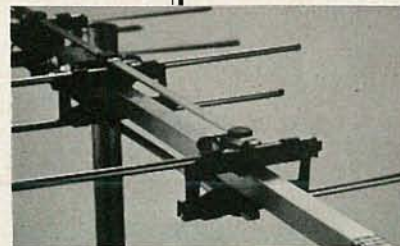**48G20
SUBURBAN**
One of many
RCA Permacolor
Antenna models
available.



SOLID FEED LINE. Solidly riveted connections of flexible aluminum provide a positive path for the signal to flow from the elements to the receiver with virtually no chance of interruption . . . an RCA exclusive.

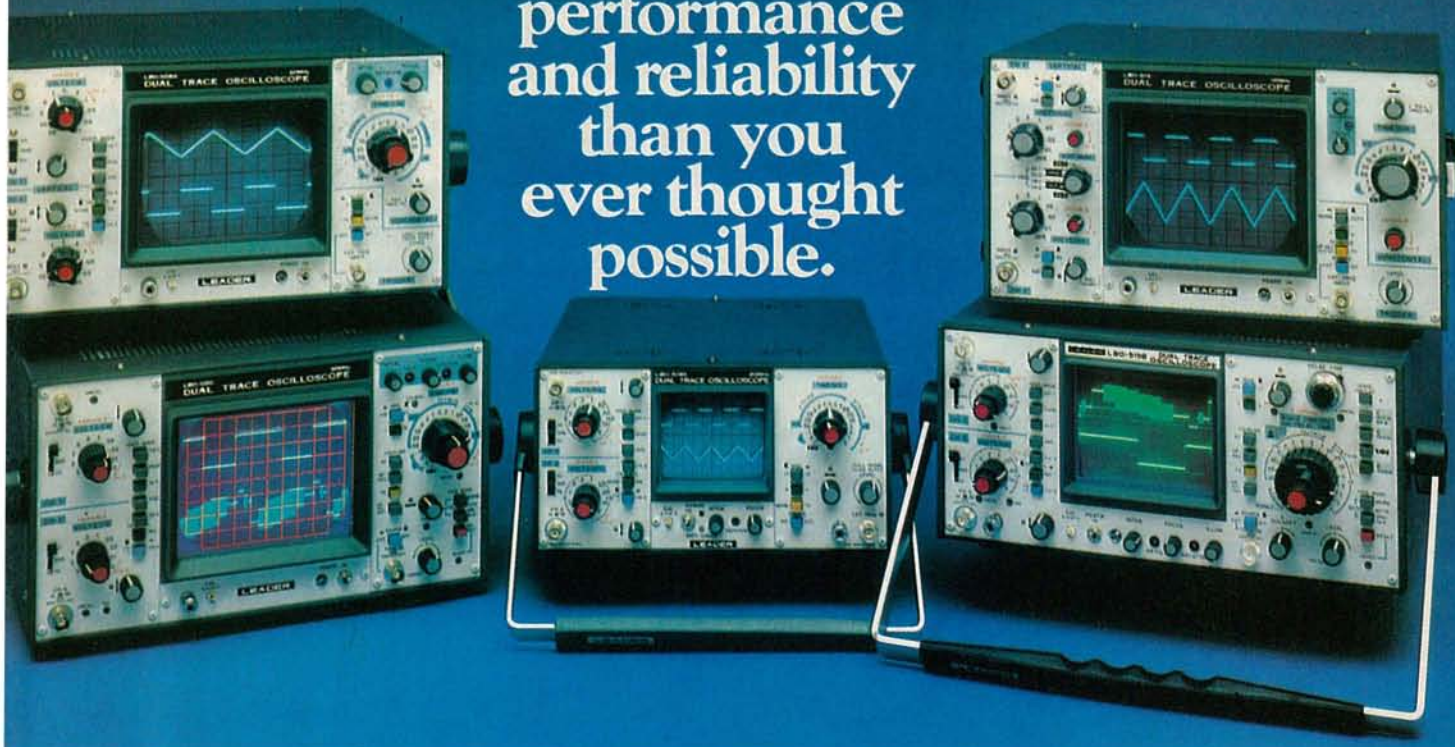10 to 30 MHz oscilloscopes with more performance and reliability than you ever thought possible.



It's easy to see why LEADER oscilloscopes are now specified more than ever. More performance and quality for less cost... with immediate deliveries from over 100 stocking distributors. They also come with the best two-year warranty in the industry... backed by efficient factory service depots on the East and West Coasts.

A full-range of reliable, medium bandwidth oscilloscopes.

LEADER's oscilloscope line includes 11 models, single and dual trace versions, for bench or field use. All models offer comprehensive triggering controls, TTL compatible Z-axis modulation, front panel trace alignment control and convenient, color-keyed front panel layout. Probes are furnished with every oscilloscope and options include probe pouches, carrying cases, front panel covers and rack mounting adapters.

30 MHz delayed sweep - \$1,530.

LBO-515B is a compact, precision oscilloscope at a moderate price. Using a PDA 4-inch CRT with parallax-free internal graticule, it features 5 mV sensitivity and delayed sweep for viewing and measuring complex waveforms. Also has 120 ns signal delay, trigger hold-off and x-y operation at full sensitivity.

30 MHz with signal delay - \$1,100.

LBO-520 combines a 11.7 ns rise time with 5 mV sensitivity and 120 ns signal

The surprising leader.

delay lines. Has single shot triggering, X10 sweep magnifier and bright, sharp PDA CRT. Triggers to 50 MHz.

20 MHz dual and single trace - \$835., \$610.

LBO-508A and LBO-507A give you versatility at low cost. Rise time is 17.5 ns with 1 M Ω (35 pFd) input impedance. Automatic or external triggering, X5 sweep magnifier, 10 mV/cm sensitivity and add/subtract modes.



Oscilloscopes, frequency counters, function generators, video and audio instruments... a LEADER instrument for almost every need.

10 MHz with 1 mV sensitivity - \$645.

LBO-514 has both vertical and horizontal X5 magnifiers. Sensitivity is from 1 mV/cm to 10 V/cm. Sweep speeds from 0.2 s/cm to 0.1 μ s/cm. Auto or normal triggering. Z-axis modulation. (Single trace version, LBO-513, \$495.)

20 MHz battery/ac portable - \$950.

LBO-308S provides lab performance and high reliability in field service applications. Sensitivity is 2 mV with a complete set of triggering controls and 18 sweep ranges to 0.1 μ s/div. with X5 magnifier. Compact, lightweight with 3-inch rectangular, internal graticule CRT. (Optional 2 hour internal battery pack is recharged during ac operation, \$75.00.)

Two-year warranty. Evaluation units.

A history of high reliability permits LEADER to provide a generous 2-year warranty... backed by factory service depots on the East and West Coasts. A free, trial use of LEADER instruments

is available to all qualified companies.

Call toll-free
(800) 645-5104
request:

- an evaluation unit
- our 40-page catalog
- the name of your nearest "Select" distributor
- additional information

When Quality Counts

LEADER
Instruments Corporation

380 Oser Avenue
Hauppauge, N.Y. 11787 (800) 645-5104
Regional Offices:
Chicago, Los Angeles, Dallas.

CIRCLE 67 TO BE CONTACTED
BY LOCAL DISTRIBUTOR

**THESE ARE NOT
HOME-MADE TRAINING DEVICES.
THESE ARE PRODUCTION MODEL
MICRO-SYSTEMS.
NO OTHER HOME STUDY SCHOOL
OFFERS THEM EXCEPT NTS.**



1.

2.

3.

IN FACT, NTS ELECTRONICS PROGRAMS INCLUDE THE WIDEST ARRAY OF SOLID-STATE AND DIGITAL EQUIPMENT EVER OFFERED BY ANY HOME STUDY SCHOOL.



2-Meter FM Transceiver

Now, for the first time, you can learn all about microcomputers by working with your own production model at home. We'll explain the principles of troubleshooting and testing this remarkable instrument and, best of all, we'll show you how to program it to do what you want.

It's the perfect opportunity for you to learn BASIC high level language programming and assembly language programming.

Then, to learn how to localize microcomputer problems and solve them, you'll experiment and test with a digital multimeter and other testing gear.

But most important, you get to assemble and work with today's most sophisticated microcomputers, not home-made training devices. We believe this makes learning a lot more relevant and exciting.

In fact, production-model equipment is featured in all NTS electronics programs.

Our Color TV servicing program boasts the NTS/HEATH digital color TV (25" diagonal) you actually build and keep.

In Communications Electronics you'll build and keep an NTS/HEATH 2-meter FM transceiver, along with digital multimeter and service trainer.

Whichever NTS electronics program you choose, you can count on working with much the same kind of equipment you'll encounter in the field.

Find out more in our full color catalog on the program of your choice.

NTS also offers course in Auto Mechanics, Air Conditioning and Home Appliances. Check card for more information.



Simulated TV Reception



Digital Multimeter

1. **The NTS/HEATH H-89 Microcomputer** features floppy disk storage, "smart" video terminal, two Z80 microprocessors, 16K RAM memory, expandable to 48K. Available in NTS's Master Course in Microcomputers.
2. **The NTS/Rockwell AIM 65 Microcomputer** A single board unit featuring an on-board 20 column alphanumeric printer with 20 character display. A 6502-based unit 4K RAM, expandable. Available in NTS's Microprocessor Technology Course.
3. **The NTS/KIM-1 Microcomputer** A single board unit featuring a 6 digit LED display with an on-board 24 key hexadecimal calculator-type keyboard. A 6502 based microcomputer with 1K of RAM memory, expandable. Available in NTS's Master Course in Electronic and Industrial Technology.

NO OBLIGATION. NO SALESMAN WILL CALL.
APPROVED FOR VETERAN TRAINING.

NTS NATIONAL TECHNICAL SCHOOLS

TECHNICAL-TRADE TRAINING SINCE 1905
Resident and Home-Study Schools
4000 SO. FIGUEROA ST., LOS ANGELES, CA. 90037



NATIONAL TECHNICAL SCHOOLS

4000 South Figueroa Street, Dept. 206-090
Los Angeles, California 90037

Please rush FREE color catalog on course checked below

- | | |
|---|---|
| <input type="checkbox"/> MicroComputers/MicroProcessors | <input type="checkbox"/> Auto Mechanics |
| <input type="checkbox"/> Communications Electronics | <input type="checkbox"/> Air Conditioning |
| <input type="checkbox"/> Digital Electronics | <input type="checkbox"/> Home Appliances |
| <input type="checkbox"/> Industrial Technology | <input type="checkbox"/> Color TV Servicing |

Name _____ Age _____

Address _____

Apt. _____ City _____

State _____ Zip _____

- Check if interested in G.I. information.
 Check if interested ONLY in classroom training in Los Angeles.

LETTERS

continued from page 26

The PLM-1 kit is available from Symmetric Sound Systems, 1608 South Douglas Ave., Loveland, CO 80537 for \$42 postpaid.
JOE GORIN
Loveland, CO

LIGHT

John W. Ecklin's letter in the March 1980 issue concerns the velocity of light and other electromagnetic radiation. His statement "the speed of light is a constant only to the source and may not be a constant to all observers" is interesting.

Consider first the Doppler explanation for spectrum shifts. That explanation was developed first to explain the changed

pitch of sound from a moving source, and was based upon the fact that the relative velocity between sound and its source varies with the motion of the source. The variations caused changes in wavelength to the front and rear which in turn caused the frequency as received to change.

When light was believed to be a wave disturbance moving through an ether substance, it was reasonable to assume a similar effect upon the wavelength of light. After the failure of the Michelson-Morley experiment the wave-ether concept was abandoned. Relativity is based upon the postulate that light moves at a velocity which is an absolute constant, regardless of the motion of the source or receiver. If that is correct, the wavelength of light from a moving source must be the same as if the

source were motionless, and no spectrum shift could occur. Spectrum shifts may result from a change in either wavelength or frequency as received, and neither wavelength or frequency can change under the absolute constant velocity concept.

My reasoning suggests the following: A) We cannot reconcile the Doppler explanation and the absolute velocity concept. B) We cannot return to a simple wave concept because of the failure of the Michelson-Morley experiment. Therefore the only concept which will explain both the results of the Michelson-Morley experiment and spectrum shifts is the particle-photon concept of light. Under the photon concept, we may assume that light moves in full accord with Newton's principles of motion for particles of matter. If so, the addition-of-velocity principle will explain spectrum shifts as due to changes in velocity which change the frequency of light as received. Also when the Michelson-Morley experiment is re-analysed, assuming that light moves as a particle, the failure to detect an interference pattern is in agreement with the particle concept.

Measuring the velocity of light photons is not sufficient to test this matter; what is required is an experiment which will compare, simultaneously, the speed of light from a stationary and a moving source.

M. J. IRESON







Sechelt, British Columbia, Canada

You'll find **MORE** of what you want in Sprague Q-LINE™ capacitors



MORE Types • **MORE** Ratings **MORE** Quality • **MORE** Value

Sprague Q-LINE Capacitors are on display for self-service purchasing at leading electronic distributors. The buying is easy because you can see what's available . . . without waiting, without asking, without searching . . . all pertinent information is clearly spelled out on attractive, color-keyed Blister-Pak packaging, which keeps capacitors visible while protecting them from moisture and dirt. Q-LINE Capacitors give you a broad choice of popular, frequently-needed types and ratings:

Capacitor Type	Number of Ratings	Capacitance Values	Working Voltage Range
 Axial-Lead Electrolytic	62	.47 to 15000 μ F	0-6.3 to 0-450 V
 Vertical-Mounting Electrolytic	33	.47 to 4700 μ F	0-16 to 0-630 V
 Vertical-Mounting Film	63	.0010 to .47 μ F	0-100 to 0-1600 V
 Resin-Coated Solid Tantalum	31	.1 to 680 μ F	0-3 to 0-50 V
 General-Application Ceramic	65	5 pF to 3.3 μ F	0-25 to 0-1000 V
 Epoxy-Dipped Mica	17	10 to 1000 pF	0-500 V

For detailed definition of types and ratings available, write for a copy of Q-LINE Capacitor Listings to Sprague Products Co., Distributors' Division of the Sprague Electric Co., 81 Marshall St., North Adams, Mass. 01247.

Where MORE is more than a promise.



CIRCLE 38 ON FREE INFORMATION CARD a subsidiary of GK Technologies

FCC CERTIFICATION

Regarding the article by Greg Grambor entitled "Servicing Communications Equipment" (May Issue). Mr. Grambor is under the assumption that there is a "required-by-law frequency and modulation certification" that must be performed yearly. What he does not realize is that on September 9, 1976 the Federal Communications Commission put into effect the deregulation proposal of Docket 20665, which eliminated required annual measurements of transmitter power, frequency and modulation. The responsibility of keeping the equipment in compliance with FCC specifications now rests entirely with the user, allowing him to decide when to check the equipment. So contrary to Mr. Grambor's statement, each radio will not generate at least one service call a year.

STEVEN L. NELSON

Webster, MN


With apologies to reader Nelson and others for my coming across a bit of stale source material, I stand corrected. However, it is important to note that, in principle, the idea of every piece of communications equipment generating at least one service call per year remains the same. In the words of Mr. Mannino, the gentleman I interviewed for the article, ". . . any good contractor will advise his customers to have a frequency and modulation check done annually, even though no longer mandated by law. It is both in the interest of the license holder, and good business for the service shop."—Greg Grambor

EINSTEINIAN IMPOSSIBILITIES

In reference to the letter by Anthony Hans Klotz on page 22 of the April 1980 issue: Mr. Klotz has expressed a very common misconception of Dr. Einstein's theory

continued on page 36

Your Toolbox Test Bench

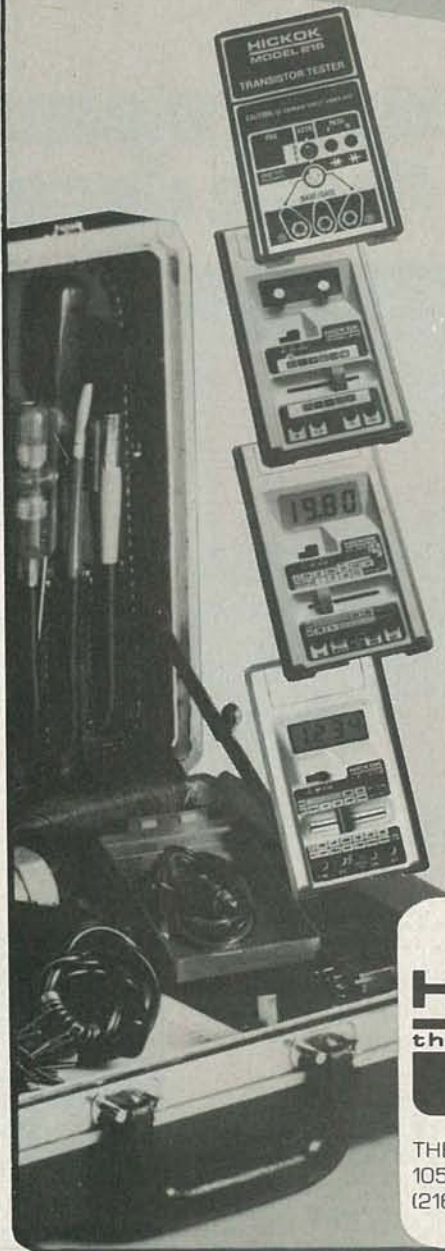

Model 216 Transistor Tester with fast, automatic switching for instant good-bad analysis of NPN's, PNP's, FET's, diodes and SCR's in or out of circuit. \$135.00

Model 240 Video Generator with 10 step gray scale staircase for VTR, CCTV monitor and TV applications. \$159.00

LX304 digital multimeter with automatic decimal point, built in low battery indicator and transistor testing capability. \$89.95

LX303 digital multimeter with easy-to-read LCD display. Only \$79.95

**FOR THOSE ON THE GO
FROM...**


HICKOK 
the value innovator

THE HICKOK ELECTRICAL INSTRUMENT CO.
10514 Dupont Avenue • Cleveland, Ohio 44108
(216) 541-8060 • TWX: 810-421-8286

CIRCLE 47 ON FREE INFORMATION CARD

The Industry challenge: Make it smaller. Make it better. Make it cost less.

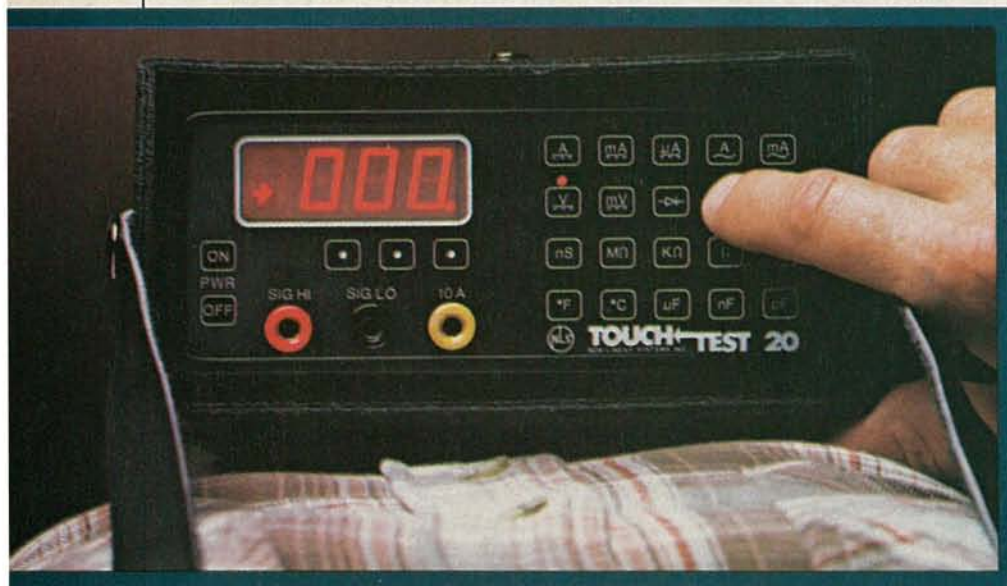How Non-Linear Systems has done it for three decades.



The new Touch Test 20 DMM weighs only 2 lbs. 4 oz. Yet it puts twenty key test functions at your fingertips. Plus exclusive light pressure touch function selection. Shown from above on leather shoulder sling (optional).

When we set out to develop the first digital voltmeter, the new Touch Test 20 digital multimeter and the new MS-230 miniscope, we knew it wouldn't be easy. But we weren't looking for easy answers. We were looking to do it right.

That's why, for nearly three decades, innovation has come first at Non-Linear Systems. And why our contributions to the field of electronics have been so far-reaching.

First DVM to see the light. In 1952, Non-Linear Systems propelled electronics testing out of the Stone Age into the Space

Age by introducing the first digital voltmeter. Suddenly and ingeniously, data was translated into the universal language of numbers on easy-to-scan read-out panels.

With this single idea, Non-Linear Systems set two bold precedents. It made clumsy analog systems a thing of the past. And it committed the company to first rate value and performance through sophisticated, yet simplified electronic test tools.


The remarkable Touch Test 20 DMM. With the Touch Test 20, Non-Linear Systems introduces the 2 lb. 4 oz. test lab. Now, with

20 key test functions at your fingertips (plus the ability to measure 10 electrical parameters and 44 ranges), you can take one lab to the field instead of a cumbersome collection of individual testers.

Another bright idea. The Touch Test 20 is the only DMM with light pressure touch function selection. No more dials to fiddle with. Instead, an LED shows the function you choose. And when you switch, you get an audible bleep and visual blip to let you know.

This small wonder is miniaturization at its best. The new Touch Test 20 is the most innovative portable/bench-type multimeter in the industry today.

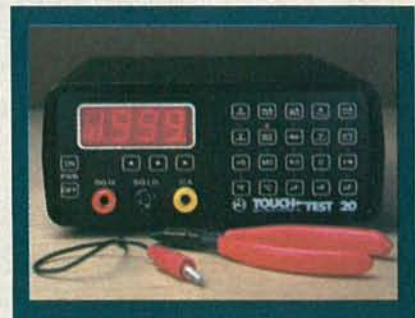Or, you can choose from Non-Linear Systems' eight other



Remarkably light and versatile, the Touch Test 20 DMM is perfect in-shop or on-site.

sophisticated DMMs. And rest assured that you'll be getting the kind of performance and value-packed instrument we've been making for nearly thirty years.

MS-230. A whale of a miniscope.

With our ingenious, new MS-230, 30-megahertz, battery-operated, dual-trace miniscope, portability's suddenly not a problem anymore. At 3 lbs. 10 oz., it's the smallest, lightest miniscope in the field today.

matchless performer.

DPMs are faster, easier to use and more accurate than outmoded pointer meters. What's more, our DPMs have an extremely wide range and acute sensitivity. The model PM-450, for example, has 20,000 counts

Another big plus. Our rugged, solid-state circuitry outperforms pointer systems. Our meters can withstand a shock without requiring the services of a jeweler.

Our versatile DPMs serve a variety of industries. From electronic products, such as ignition analyzers and automated test equipment, to mechanical products using electronic components, such as cars, farm equipment and machine tools.

We serve a variety of customers, too. From design engineers to wholesale and retail distributors.

So if your problem calls for an accurate, dependable DPM, Non-Linear Systems has over 2,000 answers. One to fit your need.

Get the word on us. Non-Linear Systems has been intelligently innovating in the digital instrument industry for nearly three decades. And one reason stands out. Our reach always exceeds our grasp.

To get the whole story, from product facts to philosophy, write for our free 1980 Catalog today. Non-Linear Systems, Inc., Box N, Del Mar, California 92014. Telephone (714) 755-1134, TWX 910-322-1132.



At 3 lbs. 10 oz., the MS-230 is the lightest miniscope around. Now you can take the scope to the problem. Or bring the problem to the scope.

The state-of-the art MS-230 works wonders on site or in the shop. Anywhere there's a need to accurately test or measure electronics equipment.

The versatile MS-230 is perfect for TV repairmen. Services microcomputer systems when the chips are down. Maintains avionics equipment with flying colors. And diagnoses sophisticated medical equipment with the precision of a surgeon.

However, if your budget or needs demand something more economical or less sophisticated, chances are the MS-215 dual-trace or MS-15 single-trace will fit the bill.

Over 2000 DPMs. One commitment: accuracy. The same foresight that distinguishes our miniscopes and DMMs is built into every digital panel meter as well. Whether your job calls for a miniature AC/DC voltmeter, DIN/NEMA frequency monitor, DIN/NEMA temperature meter or digital counter, Non-Linear Systems can oblige with a

full-scale. The PM-450 has no difficulty at all reading the difference between 19.994 and 19.995 volts.

In addition, our DPMs combine a variety of useful features. Like automatic polarity indication.



We offer over 2,000 DPMs — AC/DC voltmeters, DIN/NEMA frequency monitors, DIN/NEMA temperature meters and digital counters.

So there's no need for reversing leads or a reversing switch. A clear, bright plus or minus sign shows the polarity.

Likewise, a programmable illuminated decimal point eliminates the need for memorizing scale factors and the mental arithmetic to apply them.

We offer LED and LCD style readouts. And terminal blocks and edge connectors are available for input and output connections.



Non-Linear Systems, Inc.

Specialists in the science of staying ahead.

© 1980 Non-Linear System, Inc.

002

006/091

Non-Linear Systems, Inc.
Box N, Del Mar,
California 92014

Please send me your free
1980 Catalog.

Name _____

Company _____

Phone _____

Address _____

City _____

State _____ Zip _____

LETTERS

continued from page 32

of Special Relativity. **Radio-Electronics**, unfortunately, has given credence to that misconception by allowing Mr. Klotz's letter to appear without comment. May I explain?

A woman stands beside a highway. A man in an auto drives past her at a constant speed. The speedometer in the auto indicates 60 mph.

The woman, looking at the auto, sees it zip past her. The man, looking out the window of the auto, sees a woman zip past him.

Which of those two observers is correct? The woman says an auto drove past her at 60 mph. The man says he looked out the

window of the auto and saw a woman zip past him at 60 mph.

In everyday life, we automatically assume that it was the woman who was at rest and that the man in the auto was the one in motion. In our day-to-day affairs, such as assumption causes no difficulties. However, when such an assumption was extended to the realm of atomic particles, with their small masses and very high velocities and energies, the assumption rapidly caused severe problems and obvious miscalculations. What to do?

Dr. Einstein provided the answer. He showed with mathematical precision that both the man and the woman are equally correct. It is no more correct to say that the woman was still and the auto in motion than it is to say that the auto was still and

the woman zipped by, unless . . .

Unless a third, *independent observer* is introduced. For example, an astronaut on the moon might look at the man and woman (imagine he has a super-telescope) and say: "Yes, the woman is standing on the earth and the man in the auto is moving over the earth's surface." Thus the motion of the man and woman must be judged *relative* to an observer. Even then, the motion is only relative to that one observer. For example, if the man and the woman were judged by a pilot flying a helicopter at 90 mph in a direction opposite to that of the auto, the pilot's observation would be quite different from that of the astronaut. (The pilot would have to say that the woman was moving past him at 90 mph, while stating that the man in the auto was passing him at 150 mph.)

Returning now to Mr. Klotz's letter, which concerns light beams moving relative to two observers, with one observer moving and the other at rest—Mr. Klotz comes to the conclusion that Dr. Einstein's logic is invalid.

But the argument is deficient in two respects. First, Mr. Klotz cannot have two moving observers (a reference frame, and *M'* in his notation) without an *additional observer* to whom such motion would be relative. To speak of a "moving reference frame" is self-contradictory, as the reference frame, by definition, is arbitrarily considered stationary, in order to judge the motion of the other objects. If a reference frame is indeed that, and is also assumed to be in motion, then two separate problems are being combined invalidly.

Mr. Klotz's second deficiency is in the use of lightbeams in a contradiction of simultaneity. Dr. Einstein had theorized that the speed of light is a universal constant. It is the same relative to any and all observers. In one of the most famous experiments in all physics, Dr. Albert Abraham Michelson confirmed that theory: It is an experimental fact.

To appreciate Dr. Michelson's work, assume that two spaceships are rushing toward each other at $\frac{1}{4}$ the speed of light. One of them is emitting a beam of light while the other tries to measure the speed of that beam.

Now assume that the two spaceships are rushing away from each other at $\frac{1}{4}$ the speed of light, and again one emits a beam of light while the other measures its speed. What results are obtained?

One might assume that the measuring spaceship would measure the light beam at $1\frac{1}{4}$ times the speed of light when the ships are approaching, and at $\frac{3}{4}$ the speed of light when they were retreating. Not so. The speed of light would be read exactly the same in both cases. As said, experimentally confirmed.


Perhaps the simplest way of putting it is this: When Dr. Einstein published his famous papers, it was the year 1905. The ideas he presented therein were called theories. It is still common to refer to them as "theory," though most all of them have been confirmed time and again by direct experiment. Indeed, no modern atomic particle accelerator could function unless its design took Dr. Einstein's "theory" into account.

ED EDWARDS
Midland, MI

R-E

Grab a handful of VIZ value!

More Magic from the Wizard of VIZ

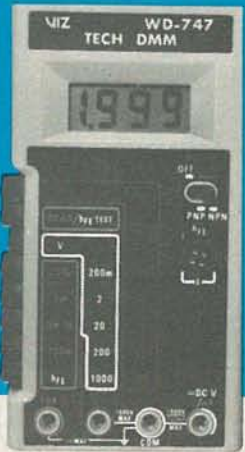

NEW Tech DMM WD-747 \$89.95

More premium quality features per dollar than any other hand-held $3\frac{1}{2}$ DMM! The *only* one with built-in test socket for transistor h_{FE} . Side switches for easy one-hand use. Auto polarity/zero. Large 0.5" LCD digits. Resolution down to 100 μ V. Accuracy

better than 0.8% DCV. 10M Ω input impedance. Full overload protection. All functions color coded. Complete with battery, deluxe test probes and spare fuse. HV probe, multiplier resistor and "LED head" continuity probe available.



0.1% Accurate DMM WD-759 \$159.95

Want top quality? Here's the *only* hand held $3\frac{1}{2}$ DMM with full info LCD readout: Function (V, A or Ω), Amount (numeric value) and whether AC or DC. Also the *only* one with full range high and low power ohms. Features auto polarity/zero, RF shielding, recessed input jacks, high impact case with front guard rail that protects against damage if dropped face down. Supplied with battery, tilt stand, spare fuse (stored inside case). Deluxe test probes have dual banana plug, alligator clip and "no-short" probe tip. Full one-year warranty. AC adapter, "LED-head" continuity probe and carry case available.

Lab accuracy WD-758 with LED readout \$149.95

See your VIZ distributor
Ask about the 7 VIZ bench
DMMs with prices to \$359



VIZ Mfg. Co., 335 E. Price St., Philadelphia, PA 19144

Over 70 test instruments in the line
CIRCLE 44 ON FREE INFORMATION CARD

What would make your business better? We would

You've seen what franchising did for real estate. Franchise companies took struggling independent realtors and put them in the limelight. The result: a greater share of the marketplace.

tronics 2000 is doing the same for the electronics service business. We're selecting a limited number of dealers in each community, giving them our name and high-level training in administrative and marketing techniques. And we're advertising as a single organization. In short, we're building a franchise organization that will stand out in a crowd.

Are you eligible to join? Yes, if you own a service dealership or are planning to start one and if you meet our technical requirements. But you must apply before the quota for your area has been filled.

tronics 2000 could be the lifeline you've been looking for. Call us. Today.

tronics 2000™

equipment reports

The Defender TS-1 CB Antenna Tuner/Monitor



CIRCLE 101 ON FREE INFORMATION CARD

ONE OF THE LEAST UNDERSTOOD PARTS OF A CB station may possibly be the antenna system. There seems to be a general idea that if you go out and buy a new antenna designed for operation on all 40 channels, then you should expect equal efficiency at each channel chosen for your favorite operation. Not so! In most cases an antenna can operate at its best on only one particular channel and as one moves farther and farther away from that design point, there is a loss of efficiency. That has been noticed

especially in mobile units when checking for proper tuning of the antenna and you have found it difficult to get a good SWR reading across the entire band. In most cases you have had to accept a compromise adjustment.

The *Defender TS-1* is designed to allow you to squeeze every last bit of power out of your base rig. It operates by making it possible to adjust your antenna system to the point of optimum match with your transmitter. In other communication fields, that type of unit has been called by various names but it really is an antenna tuning unit. There have been some "add-on" items available for CB, but the *Defender* has built the tuner into an attractive wood-grained cabinet. In addition to the antenna tuner, the *TS-1* also contains a built-in power meter capable of operation on either 5 or 50 watts, an SWR (Standing Wave Ratio) bridge, a modulation meter, and a handy antenna selector switch. The *Defender* is manufactured by The Shakespeare Co., Inc., Columbia, SC 29202.

In operation, the *Defender* is connected to the CB rig through a short piece of 50-ohm coaxial cable and the station antenna is connected to either one of the two antenna connec-

tors on the rear panel of the unit. The unused connector can be terminated in a dummy load (supplied with the *TS-1*) or to a secondary station antenna. At that point, all further adjusting or measuring is accomplished with the front panel controls. For instance, if you wish to check the power output of the transmitter quickly, all that need be done is to set the antenna switch to the position the dummy load is connected to, press the button marked POWER, and read the output power directly on the meter face. Calibration is from 0-5 watts.

By setting the antenna selector switch to the position that connects the antenna to the rig you are now ready either to check the SWR of the system or to continue communicating. Assuming that you would want to test the SWR, all that is required would be first to press the FORWARD button, and adjust the METER ADJUST control for full-scale reading on the meter while keying the transmitter. Then press the REVERSE button (still holding the transmitter in the keyed position); the meter will now indicate the SWR value. The center scale is used for that measurement and is coded in bright red when the SWR exceeds 3 to 1. Of

continued on page 40

BUILD A MASTERPIECE OF SOUND



percussion and sustain. Wersi's famous string orchestra and bass guitar. Exclusive Sound Computer for 32-128 "One Stop Sounds" (total organ presets). Transposer. And lots more.

Build your own masterpiece of sound. No technical knowledge required. Just follow the clearly illustrated, easy to understand instructions. Step by step. Choose from at least 10 models. (Also factory assembled.)

Send \$6.00 with coupon for your Wersi Demo-Package (LP with 104-page color catalog).

WERSI

Wersi Electronics, Inc. Dept. 21
1720 Hempstead Road
Lancaster, PA 17601

Wersi Organs & Kits
Dept. 21
14104 E. Firestone Blvd.
Santa Fe Springs, CA 90670

Enclosed is \$6.00 for my Demo-Package (LP with 104-page color catalog.)

Name _____
Address _____
City _____ State _____ Zip _____

Wersi has combined select features of the electronic music field, added its own creations and years of research by top engineers and musicians, to produce an incomparable line of organs.

Space-age technology. True-to-life voicing with full drawbar system. Polyphonic

CIRCLE 17 ON FREE INFORMATION CARD



**FREE!
NEW
CATALOG
OF
HARD
TO
FIND
PRECISION
TOOLS**

Jensen's new catalog is jam-packed with more than 2000 quality items. Your single source for hard-to-find precision tools used by electronic technicians, scientists, engineers, schools, instrument mechanics, laboratories and government agencies. This popular catalog also contains Jensen's world-famous line of more than 40 tool kits. Send for your free copy today!

JENSEN TOOLS INC.
1230 SOUTH PRIEST DRIVE
TEMPE, ARIZONA 85281

CIRCLE 28 ON FREE INFORMATION CARD

An Extraordinary Offer to introduce you to the benefits of Membership in

ELECTRONICS BOOK CLUB

take any **6** of these 24 unique electronics books **\$2.95** for **ALL SIX**

with a Trial Membership in the Book Club that guarantees to save you 25% to 75% on a wide selection of electronics books




971-196 p.—Miniprocessors; From Calculators to Computers (\$9.95)



1199-476 p.—The Master IC Cookbook (\$15.95)



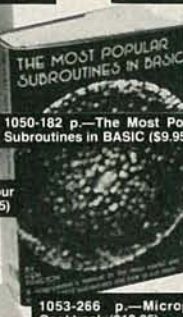1225-322 p.—Master Handbook of Electronic Tables & Formulas—3rd Edition (\$14.95)




1053-266 p.—Microprocessor Cookbook (\$10.95)



1184-616 p.—The Master Guide To Electronic Circuits (\$19.95)



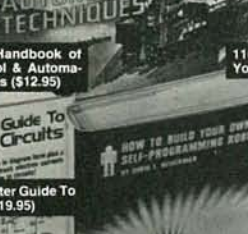801-392 p.—Master Handbook of Ham Radio Circuits (\$12.95)




1241-238 p.—How To Build Your Own Self-Programming Robot (\$12.95)



804-700 p.—Master Handbook of 1001 MORE Practical Electronic Circuits (\$17.95)



1055-140 p.—The BASIC Cookbook (\$7.95)

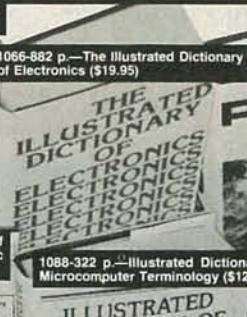



1088-322 p.—Illustrated Dictionary of Microcomputer Terminology (\$12.95)



1123-210 p.—The Laser Experimenter's Handbook (\$9.95)



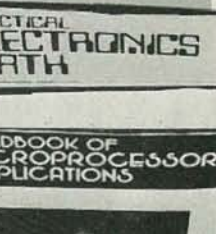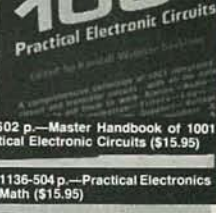800-602 p.—Master Handbook of 1001 Practical Electronic Circuits (\$15.95)



1203-308 p.—Handbook of Microprocessor Applications (\$14.95)

Facts About Club Membership

- The 6 introductory books of your choice carry publisher's retail prices of up to \$107.70. They are yours for only \$2.95 for all 6 (plus postage/handling) with your Trial Membership.
- You will receive the Club News, describing the current Selections, Alternates, and other books, every 4 weeks (13x a year).
- If you want the Selection, do nothing, it will be sent to you automatically. If you do not wish to receive the Selection, or if you want to order one of the many Alternates offered, you simply give instructions on the reply form (and in the envelope) provided, and return it to us by the date specified. This date allows you at least 10 days in which to return the form. If, because of late mail delivery, you do not have 10 days to make a decision and so receive an unwanted Selection, you may return it at Club expense.
- To complete your Trial Membership, you need buy only four additional monthly Selections or Alternates during the next 12 months. You may cancel your Membership any time after you purchase these four books.
- All books—including the Introductory Offer—are fully returnable after 10 days if you're not completely satisfied.
- All books are offered at low Member prices, plus a small postage and handling charge.
- Continuing Bonus. If you continue after this Trial Membership, you will earn a Dividend Certificate for every book you purchase. Three Certificates plus payment of the nominal sum of \$1.99 will entitle you to a valuable Book Dividend of your choice which you may choose from a list provided Members.

May we send you your choice of 6 of these practical time-and-money-saving books as part of an unusual offer of a Trial Membership in Electronics Book Club?

Here are quality hardbound volumes, each especially designed to help you increase your know-how, earning power, and enjoyment of electronics. Whatever your interest in electronics, you'll find Electronics Book Club offers practical, quality books that you can put to immediate use and benefit.

This extraordinary offer is intended to prove to you through your own experience, that these very real advantages can be yours... that it is possible to keep up with the literature published in your areas of interest, and to save substantially while so doing. As part of your Trial Membership, you need purchase as few as four books during the coming 12 months. You would probably buy at least this many anyway, without the substantial savings offered through Club Membership.

To start your Membership on these attractive terms, simply fill out and mail the coupon today. You will receive the 6 books of your choice for 10-day inspection. YOU NEED SEND NO MONEY. If you're not delighted, return the books within 10 days and your Trial Membership will be cancelled without cost or obligation.

ELECTRONICS BOOK CLUB, Blue Ridge Summit, Pa. 17214

ELECTRONICS BOOK CLUB

Blue Ridge Summit, Pa. 17214

Please open my Trial Membership in ELECTRONICS BOOK CLUB and send me the 6 books circled below. I understand the cost of the books I have selected is only \$2.95 for all 6, plus a small shipping charge. If not delighted, I may return the books within 10 days and owe nothing, and have my Trial Membership cancelled. I agree to purchase at least four additional books during the next 12 months after which I may cancel my membership at any time.

800 870 905 1059 1060 1064 1066 1077
1088 1101 1119 1123 1132 1133 1136 1138
1183 1184 1199 1203 1205 1222 1225 8224

Name _____ Phone _____
Address _____
City _____
State _____ Zip _____
(Valid for new Members only. Foreign and Canada add 15%.) RE-90

EQUIPMENT REPORTS

continued from page 38

course, if you are using two (2) antennas connected to the DEFENDER then you could press the selector switch and check the SWR of the secondary antenna. The SWR reading is a good indicator of the efficiency of your antenna system.

The *Defender* will also allow you to tell at a glance just how much "talk-power" your rig is delivering. That function is accomplished by the built-in modulation checker. While keying the transmitter but not talking, press the SET button and adjust the METER ADJUST control for a reading of 100% on the meter. Now, by pressing the TEST button and speaking into the microphone, you will note that the meter will indicate a reading that should increase the

louder you speak. The percentage of modulation is checked by using the bottom scale of the meter. Remember, whenever you exceed the 100% reading while speaking into the microphone, your audio quality will be degraded, and distortion will be noticeable on your signal. The *Defender* operating manual suggests that you constantly monitor the percent modulation at all times in an attempt to keep your voice at the level that will provide the best talk-power on the air.

And now, we come to the antenna-tuning capabilities of the *Defender TS-1*. To make your antenna system present the best load possible to the transmitter, tune your rig to the desired channel and depress the SWR REVERSE button. Set the ANTENNA MATCH switch to the IN position, key the microphone (don't speak), and adjust the TUNE control until a reduction

in the SWR reading on the meter is noticed. When you have found the point of minimum reading, adjust the LOAD knob until once more the reading on the meter is at minimum. By repeating each of those two adjustments—the TUNE and the LOAD controls—until no further reduction is obtained, you may get close to a perfect 1-to-1 match. To check, measure the SWR and you may be happily surprised to find that it is much lower than that which was previously measured on that particular antenna. The match will be best *only* at the channel in use when you tuned the antenna. If you change the operating frequency (channel) then you should either place the matching switch in the OUT position, or, retune the system to the new channel. It should also be pointed out that the adjustment for one antenna will not usually be the same for another antenna. Each time the antenna is changed or there is a switch in the operating channel, to keep the system at optimum, the tuner should be readjusted.

In the model supplied, there is a toggle switch located on the rear panel which allows the *Defender* to be used to make readings up to a maximum of 50 watts of RF power. There are instructions provided for such use. However, all other measurements and checks must be made at 5 watts only.

The *Defender TS-1* is covered by a 1-year limited warranty from the manufacturer. It has specifications that include SWR measurements of 3 to 1 and over, power output measurements of 5 and 50 watts, modulation to 125% can be checked and the antenna tuner can match a 4-to-1 system to provide an SWR of 1.5 to 1 (or less).

In an actual test of the *Defender*, we were able to match two different antenna systems that initially had SWR readings of almost 3 to 1. We obtained an almost perfect match for both antennas. It should be noted that your system may vary from what we obtained. However, if the SWR in your system is reduced by even a small amount, there can be little doubt that your system is providing a more potent signal. And, isn't that really what you are attempting to do in the long run? **R-E**

IET Model RCS-500 R-C Substitution Box




CIRCLE 102 ON FREE INFORMATION CARD

ANYONE WHO HAS GONE THROUGH THE AGONY of trial-and-error component substitution by the "one-at-a-time" connect and disconnect method will appreciate the convenience of the *Model RCS-500* resistance/capacitance substituter from IET.

The *RCS-500* is actually a combination of two separate resistance and capacitance substitution boxes available as the *models RS-200* and *CS-300*.

continued on page 42

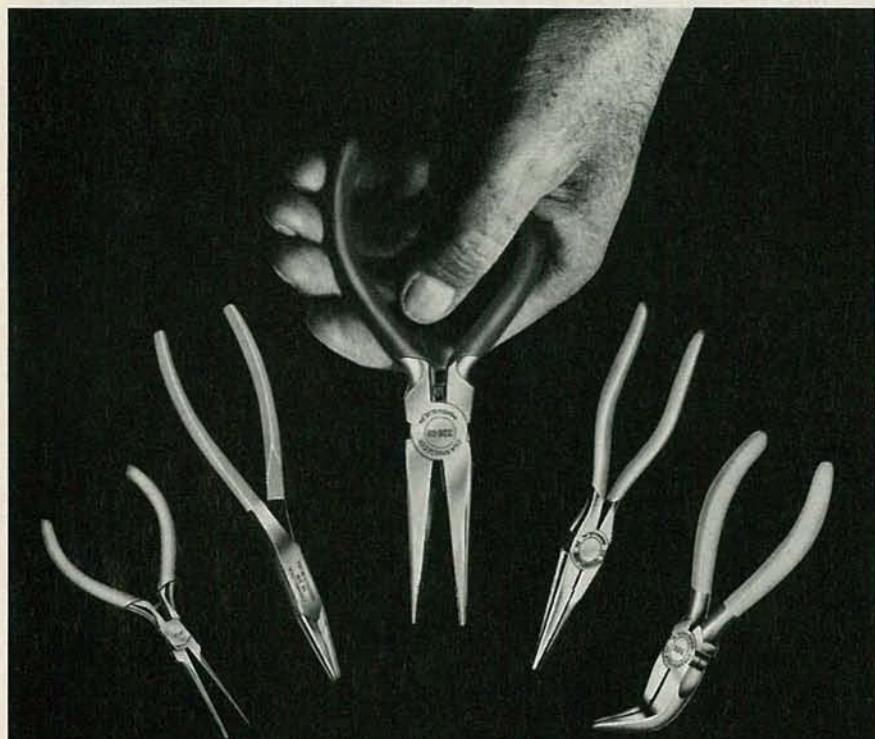

Sometimes It Pays To Have Nosey Friends

... friends that give you a firm grip on fine work in tight places. That make it easy to reach the hard to reach. Long nose pliers by CHANNELLOCK. Slender, perfectly mated jaws with no side wobble. Sharp, hand honed cutters. Beautiful high polished finish. Blue dipped plastic comfort grips. Quality in every detail (at no premium in price). CHANNELLOCK. Be sure that name is on the pliers YOU buy.

CHAN NEL LOCK

CHANNELLOCK, INC. • Meadville, Pennsylvania 16335

Meet The Rest Of The Family. Send For Free Catalog.

CIRCLE 18 ON FREE INFORMATION CARD

HITACHI OSCILLOSCOPES

Single and dual trace, 15 and 30 MHz. All four high sensitivity Hitachi oscilloscopes are built to demanding Hitachi quality standards and are backed by a 2-year warranty. They're able to measure signals as low as 1mV/division (with X5 vertical magnifier). It's a specification you won't find on any other 15 or 30 MHz scopes. Plus: Z-axis modulation, trace rotation, front panel X-Y operation for all four scope models, and X10 sweep magnification. And, both 30 MHz oscilloscopes offer internal signal delay lines. For ease of operation, functionally-related controls are grouped into three blocks on the color coded front panel. Now here's the clincher: For what you'd expect to pay more, you actually pay less. Suggested list price of our top line V-302 dual trace 30 MHz is only \$945.00. The other models comparably less. Check our scopes before you decide.

Hitachi...The measure of quality.

- V-302 30 MHz Dual Trace \$945.00
- V-301 30 MHz Single Trace \$745.00
- V-152 15 MHz Dual Trace \$695.00
- V-151 15 MHz Single Trace \$545.00



HITACHI
Hitachi Denshi America, Ltd.

For more information, contact
Hitachi Denshi America, Ltd.,
175 Crossways Park West, Woodbury, N.Y. 11797
(516) 921-7200.



More sensitive to your input.

EQUIPMENT REPORTS

continued from page 40

The substituter features thumbwheel selection of values, independently obtained from either the resistance or capacitance side of the instrument through separate terminals.

The real beauty of such an instrument is, of course, the capability of dialing in virtually any resistance or capacitance imaginable.

The resistance portion of the box is accurate to 1%. All resistive components are 1/2-watt units, serially tied, allowing for a selection in 1-ohm increments from 1 to 9,999,999 ohms. Residual circuit resistance is 0.4 ohms.

The resistance thumbwheels are conveniently separated and labelled as ohms, kilohms, and megohms. Thus, no mental gymnastics are necessary—merely dial it up and read it!

The capacitor portion of the substituter is just as simple to use. The thumbwheel switches on that side of the instrument are labelled in microfarads, nanofarads, and picofarads.

Capacitance selection begins at 100 picofarads, incrementally advancing in 100-picofarad steps to a maximum value of 99.9999 microfarads. All capacitors below 10 microfarads are rated at 100 volts; those above 10 microfarads will tolerate 25 volts.

Capacitors are parallel-tied, with a residual circuit capacitance of 30 picofarads. Capacitors in this section are specified at 4% tolerance. We decided to check their actual values to see whether they are really that close. Electrolytic capacitors are especially notorious for drifting away from their rated value, and electrolytics are typically rated below their actual capacitances.

Checking the specifications

The instrument we used to check the capacitors was IET's own *CM-500* autoranging digital capacitance meter, certified earlier as being accurately calibrated.

Below 10 microfarads, the capacitors in the *RCS-500* were well within tolerance, with most measuring ± 2 to 3 percent. At 10 microfarads and above, tolerance fell back a little, as was expected, to an accuracy of between 7 to 8 percent. Still, that is better than the usual +50% found on many electrolytics!

Internally, the circuit-board assembly and layout shows the care we have found to be typical of IET craftsmanship. The cabinet is high-impact plastic, heavy-duty thickness, and all functions are clearly labelled.

The model *RCS-500* measures $7.40 \times 4.33 \times 2.36$ -inches and weighs a mere 14.5 ounces. While the *RCS-500* (or the separate resistance and capacitance boxes) are certainly adequate for the vast majority of applications found in servicing and prototype design, a new series of tight-tolerance substituters has been announced. The *RX-201* resistance box uses 0.1% resistors, while the *CS-301* capacitance box features 1% capacitors.

But for most of us, the accuracy of the *RCS-500* resistance/capacitance substitution box is more than adequate.

Remember that when you use a substitution box certain precautions must be taken: Voltage ratings for the capacitors must not be exceeded; nor should switches be continually flipped among high-capacitance values which are connected across B+. That will produce arcing which could gradually break down the contact surfaces of the thumbwheel switches. Also, don't forget that excessive current-flow through resistors will cause them to heat up, often permanently changing their resistances if not totally destroying them.

Properly used, an R-C substitution box of the quality of the IET unit will offer years of trouble-free service. The *RCS-500* digital resistance/capacitance substituter sells for \$185.95. For further information, write IET Labs, Inc., 761 Old Country Road, Westbury, NY 11590. **R-E**

ADVANCE IS PROUD TO INTRODUCE the

KEITHLEY Line of High Quality Digital Multimeters Featuring The New 130 Hand-Held DMM

Take a look at Keithley's new Model 130 measurement problem-solver.

Easy to use


- Two rotary switches instead of eight pushbuttons
- Large, easy to read 1.8cm (.6") LCD digits—larger and sharper than competitors'

Rugged

- High-impact ABS plastic case
- Shock-mounted LCD
- Tough polycarbonate plastic window and front panel

Performance Plus

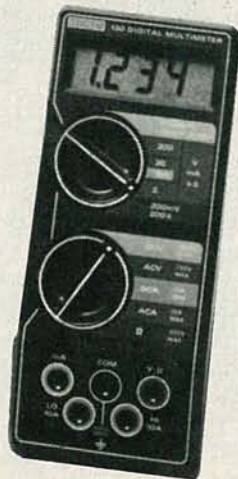- Convenient size and weight—only 10 oz. (7.0" x 3.1" x 1.5")
- 200 hour battery life
- Low battery annunciator
- Easy to maintain—all components on one board
- One-year guarantee on specifications
- Only one calibration adjustment, only once
- 25 Ranges and five functions: DC volts, AC volts, DC amps, ohms
- 100 μ V, 1 μ A, 0.1 Ω sensitivity
- 1000V DC, 750V AC, 10A and 20M Ω upper range limits



\$109

Case \$10.00
Shipping \$3.00

SPECIFICATIONS

	RANGE	ACCURACY
DC VOLTAGE	200mv, 2V, 20V, 200V, 1000V	.5%
AC VOLTAGE	200mV, 2V, 20V, 200V, 750V	1%
DC CURRENT	2mA, 20mA, 200mA, 2000mA, 10A	2%
AC CURRENT	2mA, 20mA, 200mA, 2000mA, 10A	3%
RESISTANCE	200 Ω , 2k Ω , 20k Ω , 200k Ω , 20M Ω	.5%

Datong Model AD-170 Active Antenna



CIRCLE 103 ON FREE INFORMATION CARD

MILITARY RECEIVING INSTALLATIONS HAVE used active antennas for years. Recently, their high performance and reasonable cost have caught the attention of many shortwave listeners. Several manufacturers now offer variations on that unique antenna principle.

Datong, a British firm, offers the *Model AD-170* indoor receiving antenna system that is designed for continuous coverage from 60 kHz through 70 MHz. It consists of several interconnecting parts: antenna preamplifier, wire dipole elements, interface unit, interconnecting cable and power supply.

In application, the wire dipole is suspended

horizontally as high as possible indoors. An attic space, away from electrical wiring or metallic mass, is ideal. The manufacturer advises the user to experiment with a number of mounting configurations, both in direction and polarity. In some cases, vertical mounting of the elements will work better than horizontal mounting.

The AD-170 is designed to feed its signal into a receiver's 50-ohm antenna input. An AC adapter that comes with the unit supplies 12-volts DC at 120 mA. The antenna preamplifier is not waterproof, so a protected installation is required. Transmission line length is only 15 feet, requiring indoor use.

Internally, the AD-170 is nicely laid out. Components are carefully hand soldered onto a glass epoxy circuit board.

Specifications of the antenna system are impressive. Third-order intermodulation products are typically -90-dB relative to 100 mV. Second-order intermodulation distortion is -80-dB relative to 50 mV. Response is essentially flat over its operating frequency range.

The received signal "sees" the AD-170 as a high-to-low impedance converter, capacitively coupled to the signal as 12 picofarads. A switchable preamplifier allows an additional 12-dB gain that is to be used for weak signal reception.

Although the AD-170 is very short (10 feet dipole length), it is equivalent in performance to a full size 16 MHz half-wave dipole. At higher frequencies, performance increases at the rate of 6 dB-per-octave. Below 16 MHz the gain decreases at the same rate, 6 dB-per-octave as compared with a full size half-wave dipole at the frequency of interest. It is easy to see that although the response of the AD-170 is down 18 dB at 2 MHz, a full size 2-MHz dipole would be 250-feet long. This much wire is entirely unnecessary to capture adequate signal for modern high-sensitivity shortwave receivers. In fact, broadcast-band interference would create a real problem with intermodulation in most cases. An antenna needs only to be long enough to present a signal of high enough intensity to override system noise.

We decided to test the overall performance of the AD-170 against a 66-foot reference dipole. The dipole was approximately 15 feet above the soil and the AD-170 was mounted only 8 feet high. Both antennas were mounted in the same direction to cancel directional effects.

A McKay-Dymek DR-33C receiver with a calibrated S-meter was used as the broadband receiver. The antennas were switched through a Daiwa CS-201 UHF coaxial antenna switch. The receiver was tuned to dozens of signals throughout the 100-kHz to 50-MHz range. In virtually every case, the AD-170 was clearly superior to the dipole, often by 10 or 20 dB, sometimes more. The only times that the large reference dipole was ahead was when it was receiving signals near its self-resonant frequency, and even then the difference was only about 5 dB.

Use it as an RDF

As an experiment, we connected two 5-foot lengths of lightweight aluminum rod to the preamplifier. That dipole was then rotated while monitoring a variety of signals throughout the spectrum broadcast through CB. The directional effects were quite pronounced. Variations on that arrangement will probably occur to readers who are interested in erecting a wide frequency coverage direction-finding antenna. The system would also be valuable for

nulling out interference.

We would recommend two improvements to the manufacturer. One would be the availability of a coaxial-cable extension so that the line can be run less directly for cosmetic reasons. Connectors on the interconnecting cable are European, and difficult to find in this country. The second would be a weatherproofing kit consisting of a plastic housing for the little preamplifier and its terminals.

We found the AD-170 to be thoughtfully designed, competently engineered, and reasonably priced. For the apartment dweller, or for the SWL who doesn't have an enormous amount of real estate to erect a large dipole, an active antenna like the AD-170 is hard to beat. The AD-170 active antenna system sells for \$89.00. Available from Gilfer Associates, P. O. Box 239, Park Ridge, NJ 07656. **R-E**

Micronta BP-1 Blood-Pressure Tester

SEVERAL YEARS AGO, MEDICAL EXPERTS BEGAN to realize that premature death might be largely avoided if a certain number of telltale signs were heeded. Those "risk factors" included, among other things, obesity, smoking, stress, and blood pressure.

It is a well established fact that high blood pressure (hypertension) is a major contributor to a shortened life span. Fortunately, it is easily diagnosed; unfortunately, too few Americans bother to have it checked.

Traditionally, blood pressure (BP) is tested by a gadget with the fancy name, sphygmomanometer. That is the familiar inflatable cuff

continued on page 44

STOP TESTING YOUR PATIENCE. START TESTING WITH PALADIN!

Voltage Tester (PA1751)
only \$19.95

ONE PIECE MOLDED BODY FOR DURABILITY

SPECIAL FINGER GUARD FOR OPERATOR SAFETY

ON AND OFF SWITCH

TESTS FROM 4 TO 500 V WITH NO BULB CHANGE

LED VOLTAGE INDICATOR

Continuity Tester (PA1752)
only \$18.50

New Continuity and Voltage Testers With Exclusive Features You Really Need

Up until now voltage and continuity testers very often did more to test your patience than they did voltage. Dimly lit, hard to see indicator lights—fragile bodies that easily cracked or split—poorly designed shapes that brought fingers in touch with live contacts—bulbs that burned out quickly or needed to be changed for higher voltages.

Now Paladin introduces the next generation of testers that can eliminate these and all of your other testing problems. Paladin products are different.

SEE THE DIFFERENCE—The PA1751 Voltage Tester and PA1752 Continuity Tester feature bright, easily read LEDs that have ten times the service life of incandescent bulbs.

These testers feature true ac/dc voltage and continuity measurement capabilities.

FEEL THE DIFFERENCE—These Paladin Testers are molded from tough, durable plastic that ensures their continued operation in any working environment. All of our testers have a specially designed finger guard that prevents the user from inadvertently becoming part of the voltage test.

EXPERIENCE THE DIFFERENCE—The PA1751 and PA1752 Testers are unmatched for performance and economy by any other testers on the market. At only \$19.95 for the PA1751 and \$18.50 for the PA1752 you're not spending more—you're just getting more.

Order your tester today by simply filling out the convenient form below. Be sure to indicate the total number of testers ordered and the total amount enclosed. Send to:

PALADIN CORPORATION
31332 Via Colinas
Westlake, CA 91361
(213) 991-4970

Please send me:

PA1751 Voltage Tester(s)
@ only \$19.95 each.
 PA1752 Continuity Tester(s)
@ \$18.50 each.

Grand total enclosed \$ _____
(Add \$2.00 for postage, handling;
Calif. residents add 6% sales tax)

Bill me Mastercharge VISA

Card account # _____


Signature _____ Exp. Date _____

Name _____

Address _____

City _____ State _____ Zip _____

\$140 Gets It All.

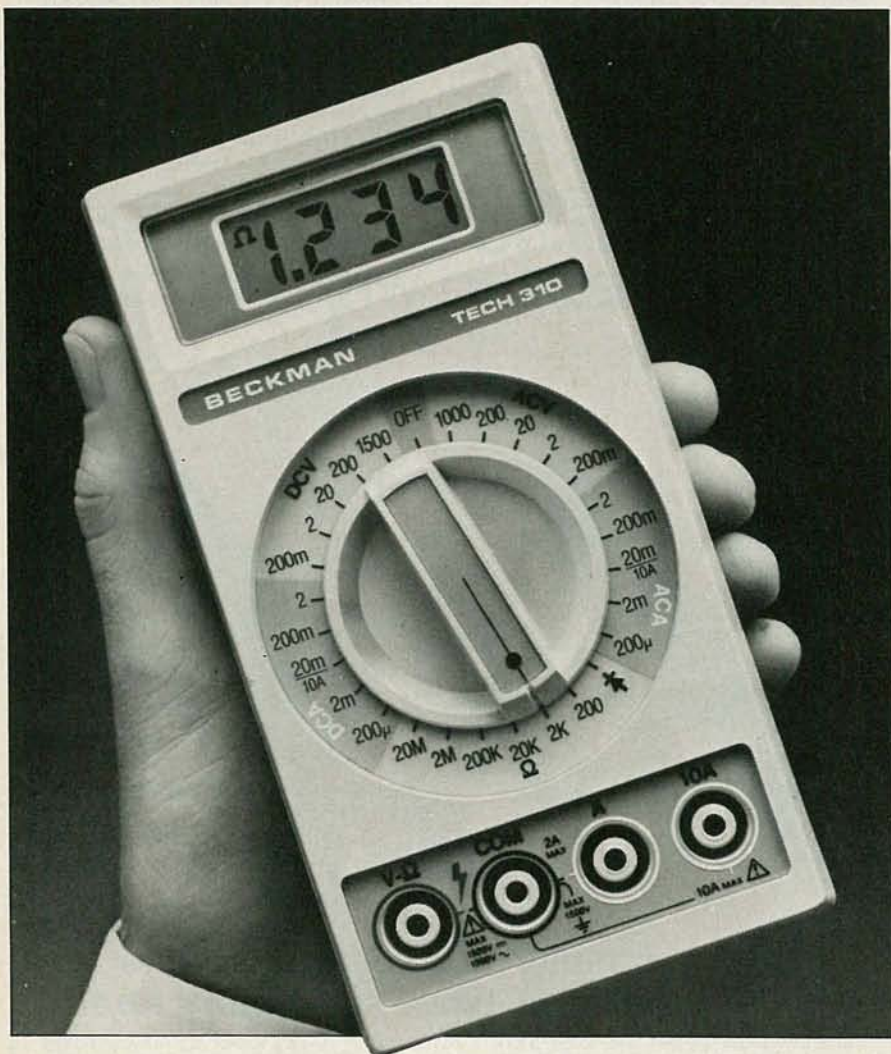

We just knocked down the last reasons for not going digital in a multimeter. Fast continuity measurement. And price.

Beckman's exclusive Insta-Ohms™ feature lets you do continuity checks as fast as the analogs. And Beckman's superior technology and experience let you own this beauty for such a reasonable price.

Of course you get a lot more. Like 7 functions and 29 ranges including 10 amp ac/dc current capability. 0.25% Vdc accuracy. In-circuit resistance measurements and diode/transistor test function. Two years' typical operation from a common 9-volt battery. In other words, all the features you want in one hand-held unit of exceptional good looks and design.

With 1500 Vdc overload protection, 100% instrument burn-in, plus rugged, impact-resistant case, you're assured of the utmost in dependability and long-term accuracy. You get a tough meter that keeps on going, no matter how tough the going gets.

So visit your dealer today and get your hands on the DMM that does it all. Or call (714) 871-4848, ext. 3651 for your nearest distributor.

BECKMAN

CIRCLE 51 ON FREE INFORMATION CARD

EQUIPMENT REPORTS

continued from page 43

aparatus found in every doctor's office, ambulance, clinic, dentist's office, and even some American homes as well. It works in a manner similar to a barometer. The inflated cuff blocks circulation in an artery of the arm, and the meter indicates the amount of pressure necessary to cause the stoppage.



CIRCLE 104 ON FREE INFORMATION CARD

Each time the muscular lower chambers of the heart contract (systole), the forward surge of blood builds up pressure in the arteries. Between beats (diastole), the pressure drops lower. A comparison, or ratio, between the systolic and diastolic pressures is the familiar fraction used to indicate blood pressure. An average, healthy adult might show a blood pressure of 120/80. This means that during the increased pressure of the heart beat, the pressure in the vessel is equivalent to a column of mercury 120 millimeters in height. Between beats, the pressure drops to an equivalent of 80 millimeters of mercury. In fact, the older sphygmomanometers used a column of mercury as the indicator.

Most present-day blood-pressure measuring devices display their measured pressure on a calibrated dial. That instrument is similar to an aneroid barometer.

The use of any conventional blood-pressure tester requires a two-step procedure. First, the cuff has to be wrapped and inflated. Second, a stethoscope is required to detect the cutoff pressure so that the readings can be taken. It is very difficult for an individual to measure his own blood pressure when working under such an arrangement.

Now, Micronta has released a "do-it-yourself" blood-pressure tester available from Radio Shack. The pressure cuff is still there, but it is equipped with a buckle and Velcro combination that makes one-arm application easy. A white dot on the cuff shows the proper location for the artery at the elbow joint of your arm. Under the dot, a small pressure transducer monitors the blood pressure, signalling the electronic circuitry in the instrument.

As with older stethoscope units, the cuff is inflated until arterial pressure no longer supplies an increase of systolic pressure. On the Micronta *BP-1*, that is indicated by an audible "beep" as well as a flashing red LED. A thumb-operated pressure-release button is then activated to reduce pressure until the beep is no longer heard, and the light ceases its flashing; that indicates diastolic pressure. Those two points are read on the gauge, and recorded in the usual fashion. A handy printed

continued on page 84

DON'T LET YOUR COMPUTER TALK DOWN TO YOU.



The more you know about microprocessors, the better you can communicate with your microcomputer. Sams has the latest books on understanding, programming and interfacing the most commonly-used microprocessors like the Z-80, 6502, 6800, 6801 and 8085A.

THESE BOOKS WILL HELP YOU GET MORE RESPECT FROM YOUR COMPUTER.

6502

- PROGRAMMING AND INTERFACING THE 6502, WITH EXPERIMENTS NO. 21651. By De Jong. \$11.95
- 6502 SOFTWARE DESIGN. NO. 21656. By Scanlon. \$9.95

6800 & 6801

- HOW TO PROGRAM & INTERFACE THE 6800. No. 21684. By Staugaard. \$11.95.
- 6801, 68071 and 6803 MICROCOMPUTER PROGRAMMING AND INTERFACING. NO. 21726. By Staugaard. \$12.95

8085A

- 8085A COOKBOOK. NO. 21697. By Titus & Titus. \$12.95

Z-80

- TRS-80 INTERFACING, BOOK 1. NO. 21633. By Titus. \$8.95
- TRS-80 INTERFACING, BOOK 2. NO. 21739. By Titus. \$9.95
- TRS-80 BOOKS 1 & 2. 2-VOLUME SET. NO. 21765. \$17.50
- Z-80 MICROCOMPUTER DESIGN PROJECTS. NO. 21682. By Barden. \$12.95
- Z-80 MICROPROCESSOR PROGRAMMING & INTERFACING, BOOK 1. NO. 21609. By Nichols, Nichols & Rony. \$10.95
- Z-80 MICROPROCESSOR PROGRAMMING & INTERFACING, BOOK 2. NO. 21610. By Nichols, Nichols & Rony. \$12.95
- Z-80 MICROPROCESSOR PROGRAMMING & INTERFACING, BOOKS 1 & 2. 2-VOLUME SET. NO. 21611. \$21.95

HOWARD W. SAMS & CO., INC.
4300 West 62nd Street, P.O. Box 7092
Indianapolis, Indiana 26206
(317) 298-5400

INDICATE QUANTITY IN BOXES ABOVE AND COMPLETE ORDERING INFORMATION BELOW. RETURN ENTIRE AD WITH ORDER.

Total amount of order \$ _____
Add local sales tax where applicable \$ _____
GRAND TOTAL \$ _____

- PAYMENT ENCLOSED (save postage and handling costs)
- CHECK MONEY ORDER
- MASTER CHARGE VISA

Expiration Date _____
Interbank No. _____
Account Number _____
Minimum credit card purchase \$10.00
Name (print) _____
Signature _____
Address _____
City _____ State _____ Zip _____

Offer expires 12/31/80

Prices subject to change without notice. All books available from Sams Distributors, Bookstores and Computer Stores. Offer good in U.S. only. In Canada, contact Lenbrook Industries, Ltd., Scarborough, M1H, 1H5, Ontario, Canada.

Sams BOOKS AD040

Right Out Of Electronic
Counterintelligence . . .

THE HIERONYMUS MACHINE™

Voice Stress Computer

It's almost beyond belief. This tiny solid-state instrument measures 3" x 6" x 1½" and fits in a pocket. Yet it contains sophisticated electronic circuitry, a microphone, and three red diodes. It analyzes the human voice for stress.

Once you learn, in about 30 minutes, how to use the Hieronymus Machine, you will be able to discover whether a person is calm or stressful — merely by monitoring his or her voice.

DEFINITELY NOT A "LIE DETECTOR"

The Hieronymus Machine is not a lie detector. Nor is it a "truth" device. Even the famed polygraph machine is not a lie detector, plain and simple. The polygraph can be used to monitor a person's pulse, respiration, blood pressure, and galvanic skin response, bodily functions affected by stress.

And in the hands of a skilled operator, the polygraph can be used to gain insights about a person's stress levels when talking about certain topics. But a very real part of the polygraph's usefulness is the "Hieronymus Effect," which we'll get to in a moment.

SPIES AND COUNTERSPIES

During wartime, counterintelligence experts wondered if science could come up with something simpler than the polygraph to help ferret out spies. Researchers became attracted to the theory that human voices emit "micro-tremors," low-frequency vibrations that are generally inaudible or masked by other voice components.

An article in **Popular Electronics** (April 1980) describes the theory in detail. But the short story is that after spending millions of dollars, researchers developed a voice stress analyzer. Now, the authors of the definitive article in **Popular Electronics** have perfected a personal voice stress analyzer, which we call the Hieronymus Machine.

WHAT IT DOES, HOW YOU USE IT

The Hieronymus Machine electronically measures changes in voice micro-tremors. The read-out is simple: one red diode indicates normal, two show moderate stress, and three reveal greater stress, ranging from mild to severe anxiety.

You, as the operator, could use the Hieronymus Machine like a thermometer, checking the "fever level" of stress. As you gain skill, your judgment will im-

prove, enabling you to pursue or avoid a line of questioning or discussion that produces stressful responses.

MANY USES AT HOME OR WORK

You can use the Hieronymus Machine at home to have fun with your family. You'll discover how it responds to different people's voices, what effect laughter and singing have on it, and even evaluate politicians' speeches over TV or radio. It works quite well on transmitted voices, as well as over the telephone or with tape recordings.

Next, try it on friends. See how well someone's favorite fish story holds up when you point out that the Hieronymus Machine doesn't believe a word of it. And watch that poker face disappear as the "stress" diode steadily insists you're not getting the whole story.

BIOFEEDBACK FOR YOU

If you're required to talk in front of groups or need to speak convincingly to one person at a time, you can use the Hieronymus Machine to monitor your voice and learn a more relaxed, self-assured, persuasive style of delivery. If you wanted to learn hypnotism, a relaxed voice would be a real asset — and the Hieronymus Machine could help you achieve it.

At work, there are numerous situations in which the Hieronymus Machine could work wonders. Here's how: Hieronymus Bosch was a 15th-century painter known for his startling originality. He was also something of a medical practitioner, and he believed that patients could be cured by passing stones over their bodies. Bosch achieved success because his patients **believed** that a cure was taking place.

Nearer our own time, a couple of science fiction writers concocted a device they named after Bosch: it produced varying sensations in the user depending on where a dial was set, from zero to 100. The amazing thing was that this machine worked on subjects even when it wasn't plugged in — a perfect Hieronymus Effect!

Now we have a true Hieronymus Machine, the Voice Stress Analyzer. It actually works, and among other things of a scientifically verifiable nature, it produces the Hieronymus Effect. In its presence, people suddenly become more forthright. In some cases, with such a machine present, employees being



asked about office theft became very cooperative in answering questions truthfully. Naturally, you'll want to use the Hieronymus Machine in plain sight and tell people what it does. This actually gets more cooperation from them.

30-DAY TRIAL, MONEY-BACK GUARANTEE

The potential uses of the Hieronymus Machine are limited only by your imagination. Try it at no risk for 30 days. We'll send you one or more with complete instructions (9v. battery not included). You'll be able to try it, experiment, even conduct your own "investigation."

Governments and police departments and huge corporations are already using large (briefcase-sized) versions of this kind of machine, and they have to pay \$3,000 or so for theirs. But you can have a personal Hieronymus Machine for only **\$149.95**. If you're not satisfied, send it back (insured) for a full refund, no questions asked. If you want two, the cost is **\$109.95** each. And if you want three or more for business use, it's only **\$99.95** each. You're also protected by a 1-year parts and labor warranty.

EXCLUSIVE BY MAIL FROM MERCURY

The Hieronymus Machine cannot be obtained in stores or from any other source. To order, send check or money order to the address below. Or charge it on American Express, Carte Blanche, Diners Club, Master Charge or Visa. You can also call us toll free:

800-526-2801
or
800-257-7850


In New Jersey, call toll free 800-322-8650. Include **\$2.50** insured shipping charge per Machine. N.J. residents please add 5% sales tax.

Or mail your order to:

NATIONAL SALES GROUP
MERCURY
THE IMAGINATION PEOPLE®

Dept. RE9, Lakewood Plaza
Lakewood, N.J. 08701

Plug-in Remote Control SYSTEM

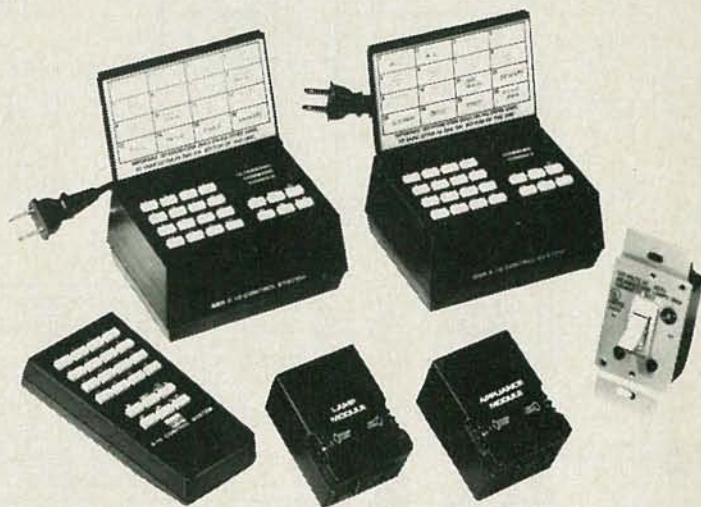

LSI technology now brings us armchair control of electrical devices throughout the home. Here's the inside story on how those controllers work.

STEVEN A. CIARCIA*

"SAVING ENERGY AND SAVING STEPS" are two of the basic selling points in the advertising for the BSR Model X-10 Home Control System. In actuality, the features of this unit combine to make the X-10 one of the most ingenious remote control systems yet introduced to the consumer market.

The X-10 (also sold under the trade names of Sears' Home Control System and Radio Shack Plug'n Power, and in Europe by Busch-Jaeger Electro) incorporates custom-made IC's that allow the user to turn lights or appliances on or off from the comfort of an easy chair. Typical applications can include such things as turning on the outside lights, the TV, and the toaster oven—all with just the push of a few buttons.

If you are too practical to accept that concept on convenience alone, consider energy and security applications as well. The X-10 makes it easier to turn off extra lights and appliances when you are not using them. It can turn on all lights in the event of an emergency, turn everything off when you go to bed, or dim lights in order to reduce power consumption.



FIG. 1—PROGRAMMABLE TIMER permits control of lights and appliances without any human intervention.

The X-10 system components

The X-10 system consists of five separate modules: the Command Controller, Cordless Controller, Lamp Module, Appliance Module, and Wall Switch Module. There is also a new programmable timer unit (see Fig. 1) that provides the system with a semblance of automatic control.

The command controller is the central element in the system. It sends commands to the three types of receiver modules by coded messages sent through the AC power lines. The cordless controller is a remote extension of the command controller and has a matching keyboard. When pointed at the command console from up to 30 feet away, any command that is selected on

it will be transmitted to the command controller and carried out. The communication between the two units is done ultrasonically.

Lamp- and wall-switch modules are essentially the same. They are triac-controlled on/off switches that include dimmers. The lamp module is plugged into a wall outlet in series with the light to be controlled while the wall-switch module replaces a conventional wall switch. Those units are rated at 300 watts. For heavier, or non-resistive loads, a contact-closure-output appliance module is used. It is rated at 15 amps (about 1700 watts).

Inside the command controller

Figure 2-a is a block design of the command console. There are two versions of that unit on the market. One has the ultrasonic receiver/cordless-controller capability; the other hasn't. An internal view of a controller including the ultrasonic circuitry is shown in Fig. 3. At the heart of that, as well as of the other system components, are custom LSI IC's manufactured for BSR by General Instruments Corporation. Fully expanded, the BSR system can accommodate 256 independently addressable receivers. That is accomplished using 16 sets of addresses called "house codes" and 16 "device codes"

* Steven Ciarcia is an engineering consultant and writes the monthly "Ciarcia's Circuit Cellar" and "Ask Byte" columns in *Byte*, a McGraw Hill publication.

Copyright © 1980 Steven A. Ciarcia

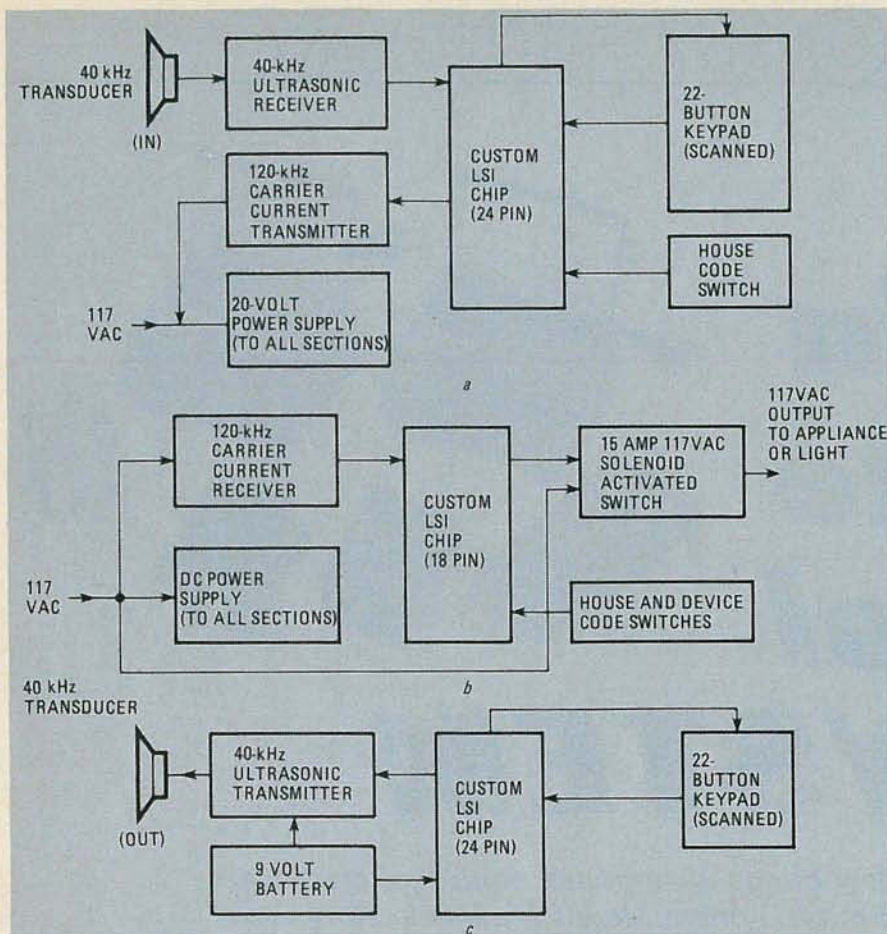


FIG. 2—FUNCTIONAL DIAGRAMS of a command module, b appliance module, and c remote-control transmitter. Text describes operating principles.

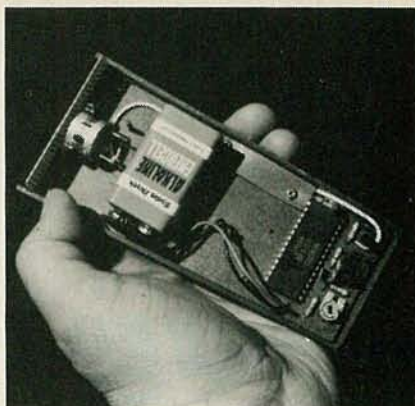


FIG. 3—CONTROLLER MODULE, despite its complexity, is surprisingly small—only $4\frac{1}{2} \times 3\frac{1}{2} \times 2\frac{1}{2}$ inches.


for each house code. The separate house codes allow next-door neighbors to use X-10's without interfering with each other. A thumbwheel switch on the bottom of the command console sets the 4-bit house code. The keyboard selection determines the channel code. This is shown in Fig. 4 and Table 1.

In normal operation the 22-button

keypad, which is wired as a 3×8 matrix, is scanned at a rate of 3.8 kHz. When a button is pressed, its designated function and the house code are combined into a single message. The digital message is directed to the transmitter section where it generates 120 kHz signals that are used to pulse-width modulate the AC line. (See Fig. 5.)



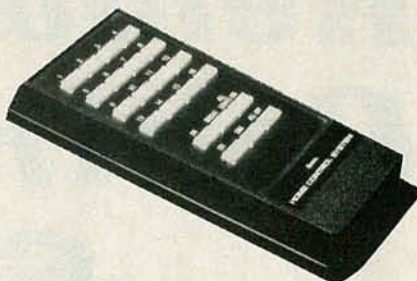HANDHELD remote controller uses a single IC to encode and transmit all commands.



ALL COMMANDS available from main console are also found on remote-control keypad.

In order to synchronize the digitally-encoded serial output (pin 15) with the 60-Hz AC line, the circuit must include zero crossing detection. That is done by feeding the AC line into the trigger input (pin 12) where the switching point is detected within 100 microseconds of zero crossing. (Incidentally, pin 13 provides for 50- or 60-Hz operation.)

The transmitted message, now synchronous with the line, is clocked, a bit at a time, on zero crossing. A command message contains 9 bits of information consisting of the 4-bit house code and 5-bit matrix (keyboard function) code. Each message is transmitted in true and inverted format on successive half-cycles of the AC waveform. That is illustrated in Figs. 6 and 7. A logic-1 bit is three 1-millisecond bursts of 120 kHz signal commencing approximately 200 μ s after the zero crossing of each of the phases. A logic-zero bit is represented by no signal for that half cycle. To synchronize the receivers with the transmitter, a trigger code consisting of three successive logic-1 bits followed by a logic-zero bit is used. The complete message takes 11 full AC cycles (183 ms) to complete.

Actual attachment to the line is by means of a transformer and capacitor coupler. That combination is necessary both for protection and economics. The effective range of this system is generally all the wiring from the controller to the nearest power company step-down transformer. There are usually five or six houses on each transformer and some coordination with respect to the choice of house codes may be

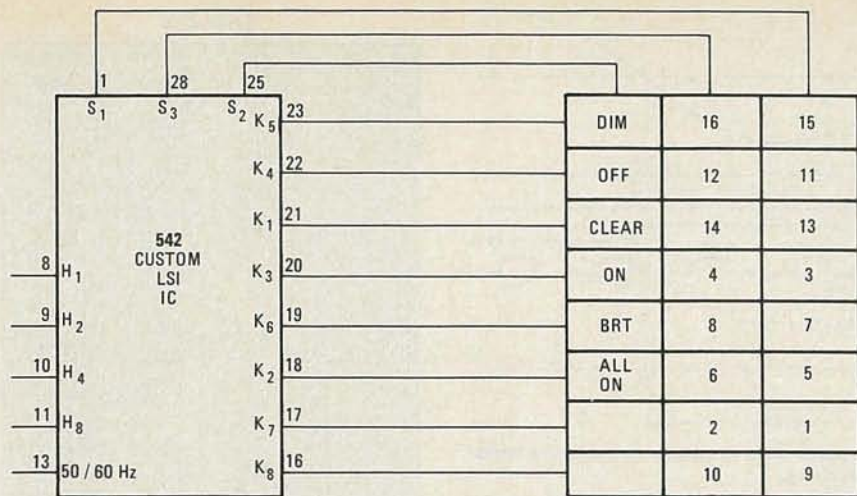


FIG. 4—KEYPAD FUNCTIONS and connections to 542C custom IC. Pin 13 of the IC allows for 50 or 60 Hz operation...at 117 volts AC.

necessary. Also, since the version of the X-10 sold in the U.S. is a 117-volt unit, and most homes derive their 117-volt power from both sides of a 220-volt line, sometimes there can be problems in obtaining consistent operation when receiver modules are used on both the 117-volt lines and relatively few 220-volt appliances are in operation to act as a communication bridge. Placement of the receivers could require some experimentation.

Ultrasonics and the X-10

There is a second method by which

the command console designates a control function and transmits instructions. That is through the ultrasonic handheld controller. When a key is pressed, a code is generated and transmitted as a series of 40 kHz tone bursts. The command console, receiving that information through its ultrasonic receiver section and injecting it into pin 7 of its LSI IC, accepts it as if a button had been pushed on the command console. It then adds the house code and retransmits the house wiring.

Figure 8 and Table 2 show in detail

TABLE 1

House Code	H8	H4	H2	H1
A	1	0	0	1
B	0	0	0	1
C	1	1	0	1
D	0	1	0	1
E	1	1	1	0
F	0	1	1	0
G	1	0	1	0
H	0	0	1	0
I	1	0	0	0
J	0	0	0	0
K	1	1	0	0
L	0	1	0	0
M	1	1	1	1
N	0	1	1	1
O	1	0	1	1
P	0	0	1	1

the communication between the two subsystem components. Each of the 22 buttons has a unique 5-bit code. For example, channel 5 would result in a code of 00010 corresponding to bit positions D8, D4, D2, D1, and F respectively. "All lights on" would be 00011.

The actual message which communicates that selection is approximately 100 ms long and comprised of thirteen 8-ms segments. Each segment consists of a burst of 40 kHz directed to an ultrasonic transducer. A logic-1 is a 4-ms burst and a logic-0 is a 1.2-ms burst. To signify channel 5 the cordless controller first sends a trigger bit to alert the receiver in the command console that a message is coming. That is a 40

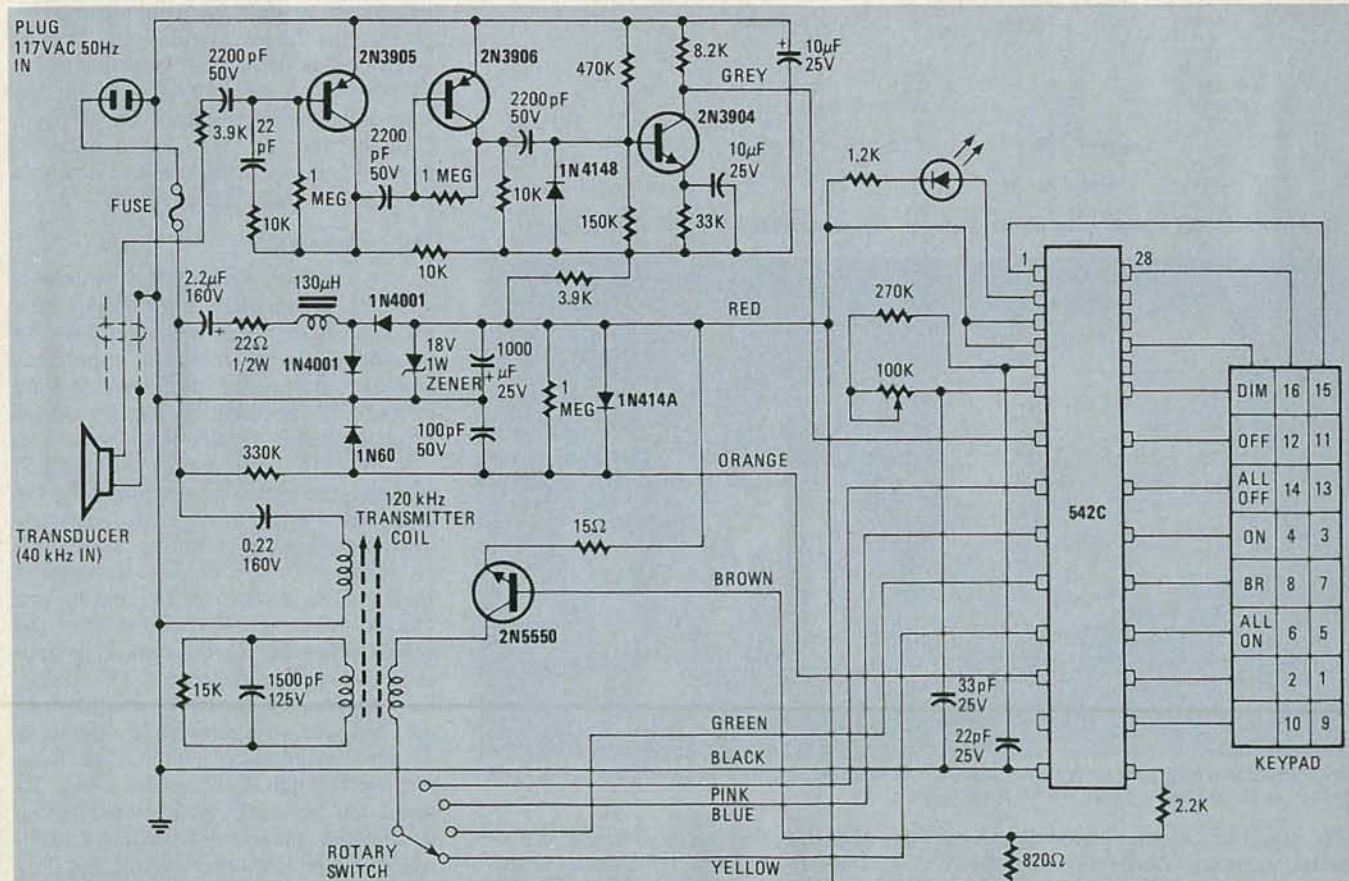


FIG. 5—COMMAND CONSOLE schematic allows you to visualize how information is encoded and transmitted over AC line. Also shown is transducer for use with ultrasonic remote control. (Courtesy BSR [USA] Ltd.)

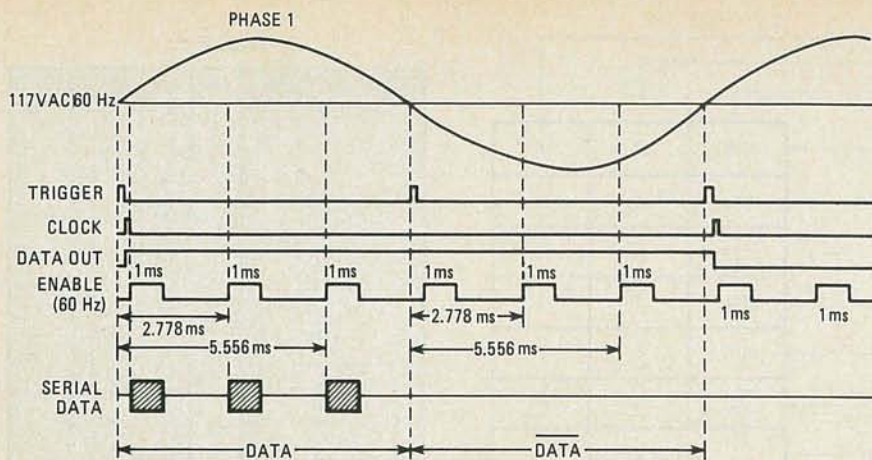


FIG. 6—TIMING DIAGRAM shows how AC line current is pulse-width modulated to transmit information from command console to appliance and lighting modules.

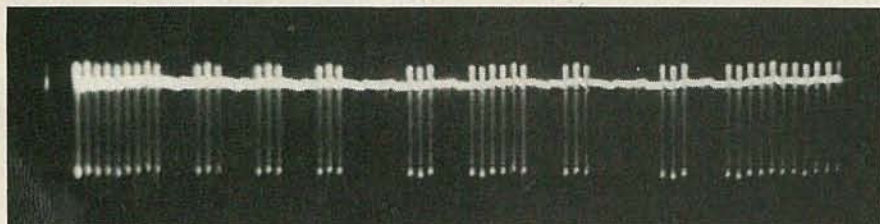


FIG. 7—DEMODULATED 120 kHz signals that make up control message. The three 1-ms bursts signifying a logic "1" are clearly seen.


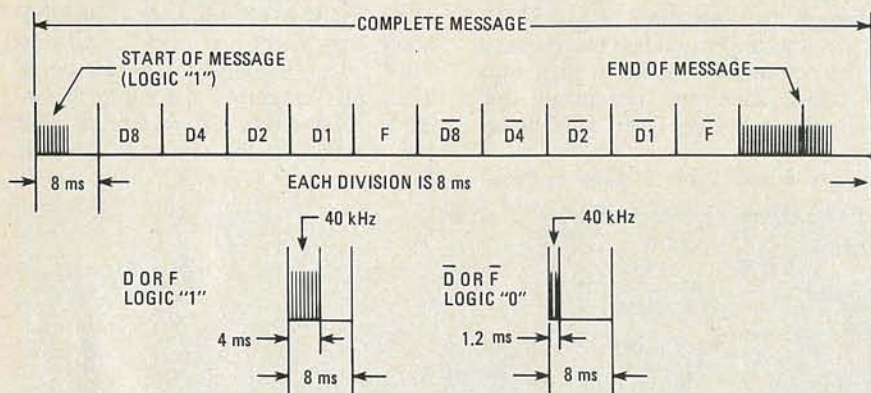


FIG. 8—MESSAGE FORMAT used by the ultrasonic remote controller. Tone bursts are 40 kHz.

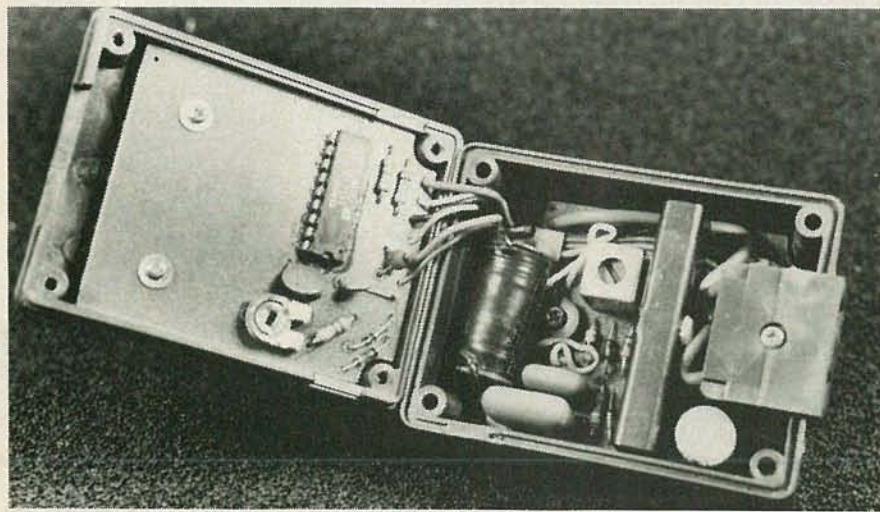

APPLIANCE MODULE interior is tightly packed. The solenoid and 15-amp switch mentioned in the text are at the left of the case; the AC outlet at right.

kHz tone for 4 ms. Next, the 5-bit matrix-selection code is sequentially transmitted as a series of 1.2- and 4-ms bursts of 40 kHz signal. It is followed by a transmission of the logical inver-

sion of the previous 5-bit selection code and then a 12-ms "end of message" burst. All messages use the same format—only the 5-bit selection code varies. Also, since the command console

TABLE 2

Channel Number or Function	Binary Code				
	D8	D4	D2	D1	F
1	0	1	1	0	0
2	1	1	1	0	0
3	0	0	1	0	0
4	1	0	1	0	0
5	0	0	0	1	0
6	1	0	0	1	0
7	0	1	0	1	0
8	1	1	0	1	0
9	0	1	1	1	0
10	1	1	1	1	0
11	0	0	1	1	0
12	1	0	1	1	0
13	0	0	0	0	0
14	1	0	0	0	0
15	0	1	0	0	0
16	1	1	0	0	0
Clear	0	0	0	0	1
All Lights On	0	0	0	1	1
On	0	0	1	0	1
Off	0	0	1	1	1
Dim	0	1	0	0	1
Brighten	0	1	0	1	1

already has a preset house code, that is not sent ultrasonically. The handheld controller is limited to operation on the 16 channels of the single house code set on the command console.

The serial-input capability of the X-10 is not limited to use with ultrasonic data transmission. Specific control of the receivers can be accomplished by injecting a digital command message directly into the serial input pin. At least one personal computer manufacturer is marketing an AC remote-control system using this method. Be advised, though, that the X-10 has a live-wire ground and any attachment to it should be done through optoisolators.

The receivers

The receiver end of the system is quite sophisticated considering that each receiver costs less than \$17. All receivers (lamp modules, appliance modules, and wall switch modules) are essentially the same. A block diagram of an appliance module is shown in Fig. 2-b. Also incorporating a custom LSI IC, the receiver section monitors the AC line, waiting for a coded message corresponding to its unique house code (A through P) and unit device code (1 through 16). To turn on channel 10, one simply press 10 and ON, one after the other. When the appliance module activates, it sounds like a relay energizing. In actuality, the appliance modules use an inexpensive solenoid to operate a 15-amp snap-action switch. The lamp and wall switch modules use a triac instead, and have the capability to brighten or dim in response to control commands. The appliance module has only on/off capability. Schematics of the appliance and lamp modules are shown in Figs. 9 and 10.

HOW TO HOOK UP HOME VIDEO SYSTEMS

*CATV converters and VCR's aren't always compatible.
Here are ways to get around the problem.*

FRANK GATES

YOU HAVE JUST SPENT THIS YEAR'S vacation money on a new video recorder and you are anxious to get it home and hook it up. The dealer assured you that there would be no installation problems—simply follow the directions. He was right as long as you are hooking it up to a conventional house antenna or a 12-channel MATV or CATV system. But what happens if you are a pay-TV subscriber or your cable system offers more than 12 channels? In both situations, some sort of a decoder or channel selector/converter is required for you to be able to receive those additional channels and that is where you start to have installation problems.

You will find that if you want to record the pay-TV channel, you will not be able to watch any other channel at the same time—which defeats one of the biggest features of owning a video recorder. Or maybe you spent a little more for a programmable video recorder and now you find out that the converter or decoder defeats the programmable feature of the recorder. I am going to show you how to overcome those and similar problems, and at the same time get the most out of your home video system.

What is a converter box?

Initially, the most that any cable system could offer its subscribers was 12 channels. That was due basically to two things—line loss with coax cable limited the cable systems to the VHF range of frequencies (or 54-300 MHz) and the home receiver would only tune in 12 of those VHF channels. UHF channels were down-converted to VHF at the cable system's antenna

site and then were delivered to the home receiver through the cable system on a locally unused VHF channel. In short order, all 12 available channels were filled with local VHF or UHF stations.

So what happened when the cable systems added more channels? The only way that a home receiver could get those additional channels was through the use of an external tuning device, thus the converter box.

What that device does is enable the

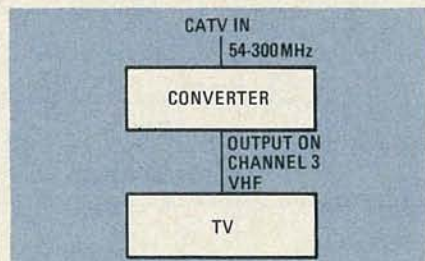


FIG. 1—CABLE-TV INSTALLATION consists of connecting a converter box between the TV set and the cable. The converter outputs all channels on a preselected VHF channel.

home receiver to display the additional cable channels without any modification to the TV set itself. It is simply a tuner/converter that enables you to select manually any incoming VHF channel (54-300 MHz) and convert it to a single conventional VHF channel on your TV tuner (i.e. Channel 3 or 4). In that manner your receiver is able to receive up to 30 or more incoming channels simply by having the converter installed as shown in Fig. 1. With that type of installation, the TV tuner is set to the output channel of the converter box (i.e. Channel 3 or 4) and all channel selecting is done with the converter itself.

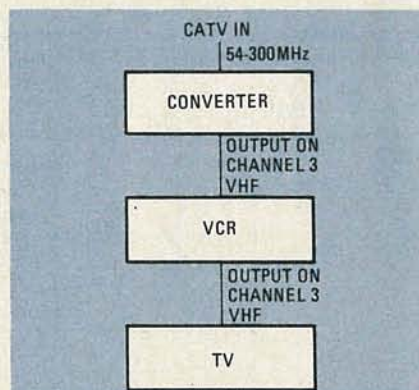


FIG. 2—ADDING A VIDEOTAPE RECORDER to a cable-TV installation consists of connecting the VCR between the converter box and the TV receiver. With that hookup, however, you must watch the same program that the VCR is recording.

Now you install your VCR as shown in Fig. 2. That enables the VCR to record any channel offered by the converter box. Again, all of the incoming VHF channels must go through the converter box and they are delivered to the VCR on the output channel of the converter box, let's say Channel 3. (Notice the absence of any UHF connections. Everything has now been converted to VHF.)

On the front panel of the VCR is a switch that is designed to enable you to monitor all record/playback functions in one position and then switch over and view any of the incoming channels in the other position; thus you have the ability to record one channel and view another at the same time. With the setup shown in Fig. 2, record/playback will be OK but when you try to view any other channel while the VCR is recording you will find that you are unable to do so. This is because when the converter box is installed,



there is only one channel available to the VCR, the output channel of the converter box, Channel 3. So when you switch the VCR/TV switch on the front panel to either position, all you can monitor is the output channel of the converter box.

Now take a look at Fig. 3. A two-way coax splitter has been added to the system and a simple A/B type switch. That will enable you to record one channel and view any other channel from Channel 2 through Channel 13 at the same time. The way that this is possible is that when you have the A/B switch on the A side you have basically the same setup as in Fig. 2. The A path from the splitter enables you to record any of the 30 or more channels that are available on the cable system, and then while the VCR is recording and the switch in the B position, you are able to view any of the Channels 2 through 13 that are now available to the tuner on your TV set.

If you wanted full 30-or-more channel capability on the B path of this system, it would require another converter box to be installed between the two-way splitter and the A/B switch. (I recommend that you spend a few extra dollars and get a good quality A/B switch, one with good isolation; that can save you some headaches in the long run.)

What about the decoders?

Decoders are what the pay-TV stations use to insure that their product is only available to those who are paying for it. There are several different methods that are currently being used

by the various pay-TV stations across the country but how they encode and decode the signal does not affect the way that their device is integrated into the home video system.

Decoding devices can be treated almost the same as a cable TV converter box! In most cases, the decoder is interchangeable with the converter box shown in Fig. 3. The decoder will have a preselected output channel, probably the same channel as the converter box or the VCR, so the setup in Fig. 3 should overcome any of the same problems that were caused by the converter box.

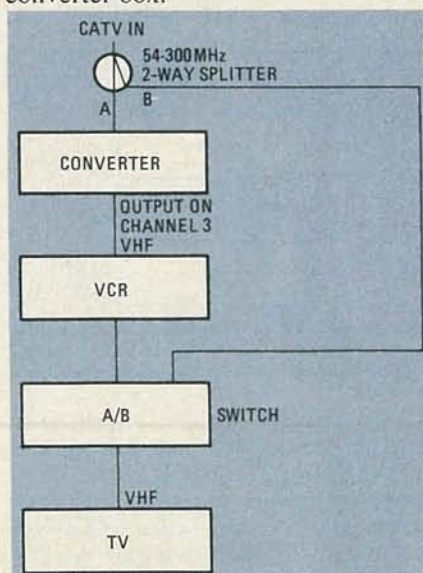


FIG. 3—TWO-WAY SPLITTER AND SWITCH enables you to watch a program different from the one the VCR is recording. However, you can only watch the standard VHF channels.

What about programmable VCR's?

The problem associated with programmable VCR's is common to both the converter box and the decoder. The programmable VCR must have all of the channels available to it on their own separate frequencies for the programmable feature to function properly. If those channels go through any type of converter device (like those that were described earlier), then the VCR's tuner must remain tuned to the output channel of the converter device. None of the installations outlined so far are compatible to a programmable VCR. There are several methods to get around the problem but the simplest and most effective is by using a VHF-to-UHF converter.

What is a VHF-to-UHF converter?

This converter does exactly what the name implies: it converts the entire VHF band up to the UHF band. It is a simple device that replaces most of the components that have been necessary in the first three figures.

Figure 4 shows a VHF-to-UHF converter in use with a programmable VCR. The cable signal feeds into the VHF input of the device; that is all 30 or more channels carried at VHF frequencies on the cable system. The device passes the basic 12 VHF channels, (2 through 13) straight through and on out the VHF output terminal of the device. Now available at the UHF output terminal are all of the 30 VHF input channels (including Channels 2 through 13), now at UHF frequencies.

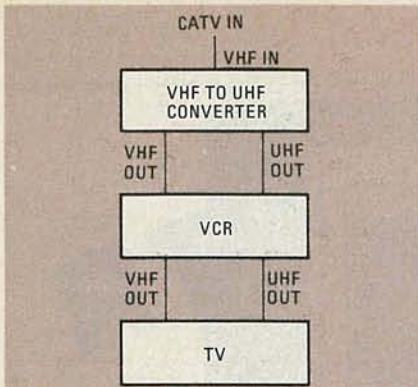


FIG. 4—A VHF-TO-UHF CONVERTER enables you to watch all the cable channels while the VCR is recording a different channel. That connection provides the ideal solution.

There is no longer any need for the cable TV converter box as that device makes all of the cable channels available to the VCR through the VHF/UHF terminals and now the VCR can pass those channels on to the receiver in the same manner. The end result is that now everything works just as it would on your own house antenna or any other 12-channel system. The programmable VCR now has all channels available at frequencies that will enable the programmable feature to work normally. You will need the conversion chart for those additional cable channels that are now available on the UHF tuner; it will tell you that cable Channel A is now UHF Channel 47, and so on. (See Table 1.)

The VCR/TV switch on the front panel of the VCR will now function as it was originally intended. If you had a built-in remote-control device with your TV that had been rendered useless for channel selection since the cable converter box was installed you can dust it off and start using it again also). One source for the VHF-to-UHF converter is ETCO Electronics, North

TABLE 1—WHERE THE CABLE-TV channels are moved to in the UHF band when using a UHF-to-VHF converter

CATV/UHF	CATV/UHF
2=36	7=56
3=37	8=57
4=38	9=58
5=40	10=59
6=41	11=60
	12=61
A=47	13=62
B=48	
C=49	J=63
D=50	K=64
E=51	L=65
F=52	M=66
G=53	N=67
H=54	O=68
I=55	P=69
	Q=70
	R=71

Country Shopping Center, Route No. 9, Plattsburgh, NY 12901.

Cable TV plus off-air pay-TV

Chances are that if you have a cable system plus a local pay-TV channel available, the cable system will already carry that pay-TV channel and make it available to you through a normal converter device that would be compatible with the systems shown earlier or through a UHF-to-VHF converter. A cable system decoder would also be treated in the same manner as the converter box.

In the case where the cable system does not carry the local pay-TV channel, and it is only available through off-air reception and you still want to have the cable system plus the pay-TV channel, you are going to have to use a little of each of the systems that have been discussed so far. (You are also going to be paying a pretty high monthly TV bill.)

Because of all the various possibilities in different areas of the country and the various methods employed, Fig. 5 shows a typical solution to that kind of problem and you can modify or build on to suit the requirements of your particular needs.

In Fig. 5 both pay-TV and cable are kept separate through the entire installation. That prevents any adjacent problems or other problems due to lack of available unused channels to accommodate the preselected output channels of the various devices (VCR, decoder, UHF converter). That type of installation also eliminates the need for any type of manual switching network, another potential source of mixing problems.

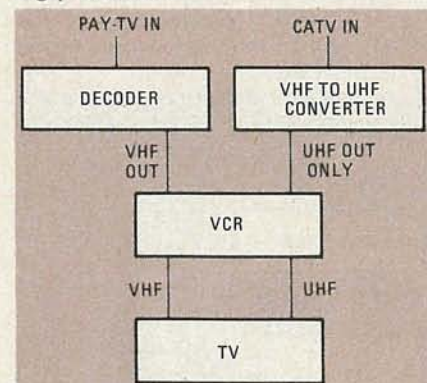


FIG. 5—PAY-TV can be added to a cable-TV installation along with a VCR as shown above. All the features of a programmable VCR are retained.

The pay-TV signal is processed through the decoder and then fed into the VHF input terminals of the VCR. Most off-the-air decoders have two inputs, one for your house system and the other for the off-the-air pay-TV channel. There is a front panel switch that allows you to select either the regular house system or the decoded pay-TV channel that will be on a pre-

selected output channel (i.e., Channel 3). In the installation shown in Fig. 5 you would simply leave the decoder switched to the descramble (premium) position and then whenever the pay-TV channel is broadcasting it would be available to your VCR or TV, decoded on Channel 3 (the preselected output channel of the device). That would also be the only channel on the VHF tuner of both the VCR and the TV.

On the cable side, all of the available cable channels would be up-converted through the VHF-to-UHF converter and would now be available on the UHF tuners of both the VCR and the TV. (See Table 1 for a channel conversion chart.)

There is one additional modification to this type of installation that might be necessary if your home video system is readily accessible to your friends and neighbors. Anyone who is not familiar with that type of installation will have problems operating the TV set. When they switch the tuner over to any conventional VHF channel on the set itself they will find everything is snow except for the single pay-TV channel. All of the remaining channels have been up-converted and are now available only on the UHF tuner. If you feel that it is necessary to have the regular VHF channels back down on the VHF tuner you can do that with just a few modifications to the installation shown in Fig. 5.

Start by inserting a two-way coax signal splitter on the input side of the VHF-to-UHF converter. Leave one leg still attached to the VHF input of the VHF to UHF converter and run the other leg to the input of the decoder device that is normally intended for your house antenna. It will be necessary to move the decoder device to a physically convenient spot near the TV or VCR as you will now have to switch the output of the device back and forth manually from either the pay-TV channel or the VHF Channels 2 through 13. Now you're able to leave the system with the conventional VHF Channels 2 through 13 available on the TV for anyone who wants to watch TV or you can switch back to the setup in Fig. 5 that enables your programmable VCR to select anything (cable or pay-TV) available for recording.


Helpful hints

Keep it simple. The fewer active devices or switches, the more reliable and trouble-free your system will be. If you have two or more pay-TV channels available in your area, or you want to run the output of your VCR to several different rooms in your home (or maybe you have two or more VCR's, or maybe you have all of those), your best bet is to use a centrally located

continued on page 104

BUILD THIS

UNICORN-1 ROBOT

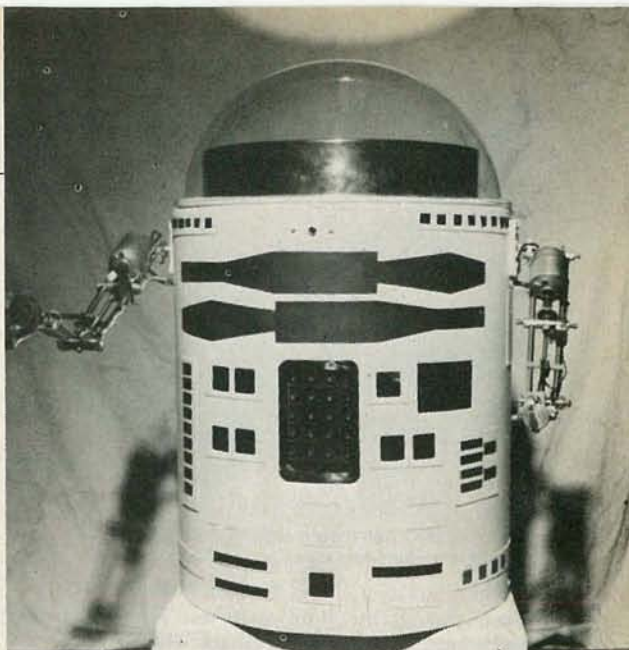

Part II—By the end of this section, your robot's arm will be operational. Here are instructions for completing the arm, and for building several types of hands.

JAMES A. GUPTON, JR.

UNICORN-ONE IS A ROBOT THAT YOU CAN build for between two- and-four hundred dollars, depending on your ingenuity and scrounging abilities. It is fully mobile and has the ability to use its arms and hands. It can be controlled by a cable link to a console, by radio control from a console, or in conjunction with a computer.

The first part of this series described some of the components used in the robot's construction, and covered most of the assembly of its *manipulator(s)* (arms).

In this installment we will complete Unicorn-One's manipulators and build its *end-effectors* (hands). From time to time we will present you with certain options that you may or may not want to include in your version of the robot.

Remember that one of this project's objectives is to build a working robot, but at a reasonable cost. When you start adding frills—which *you* may consider necessities—that cost is going to go up. It might be wisest to start with the essentials, to prove that what you have set out to do *can* be done, and to add the extras later. Unicorn-One was designed with that plan in mind and all the options described—as well as most extras that you'll think of yourself—can be added afterward, with no major alterations to the robot already constructed.

Completion of manipulator

The last part of the manipulator to be fabricated is the *contractor-bar* (we saved the easiest for last). That is simply a bar of aluminum $\frac{1}{4} \times \frac{1}{2} \times$ approximately 6

inches long. The actual length will depend on how far you want the elbow to bend, but we've found that 6 inches is a good size to work with. Use a No. 33 bit to drill a hole close to each end of the rod so it may be connected to the rest of the arm with No. 4-40 screws at the two contractor-bar pivot pieces. See Fig. 9 and Fig. 6 (part 1, last month) for details.

At this point you are probably anxious to see how (and whether) the elbow action of the manipulator works. Before

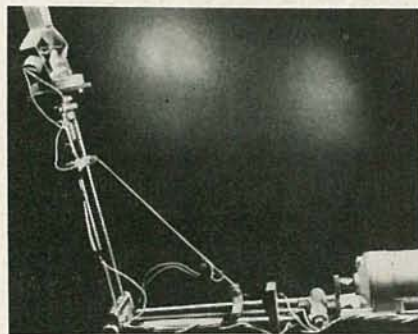


FIG. 9—MANIPULATOR, showing contractor-bar and its attachment to the two pivot pieces.

you power it up, though, there is one more step that must be taken. If you were to turn on the mechanism now there is a very good chance that you would unintentionally allow the threaded rod to travel too far . . . and jam. That could prove extremely embarrassing.

To prevent jamming from taking place, we have to install *limit switches*. Those are lever-type snap-action switches that are placed so that power to the elbow

motor will be cut when the part in motion reaches the desired limit of its travel.

Both upper- and lower-limit switches are used to protect the mechanism during motion in either direction. If power is applied to the elbow motor through one of the limit switches, the threaded rod will turn and cause the forearm to move up or down. When it has gone as far as it can, it will contact the limit switch and stop the motor.

Since we are using DC motors, reversing the current flow in the windings (connecting the power source "backwards") will make them turn in the opposite direction. Therefore, to make the arm move the other way, the other limit switch supplies the motor with current of the opposite polarity.

Almost any size lever-type, N.C. (Normally-Closed) snap-action switch may be used, as long as there is room to mount it. There is no firm rule as to where the limit switches must be located—the objective is to place them so that they will be turned on by some moving part of the arm in time to stop its motion before damage occurs.

Figure 10 shows one possibility for the placement of the upper- and lower-limit switches. Here, the upper-limit switch is attached to the side rod so that its contacts are opened when it is contacted by the upper pivot hinge. The lower is placed so it will contact the side rod when the arm is lowered and the side rod and contractor-bar are nearly parallel. There are other ways of achieving the same results, of course.

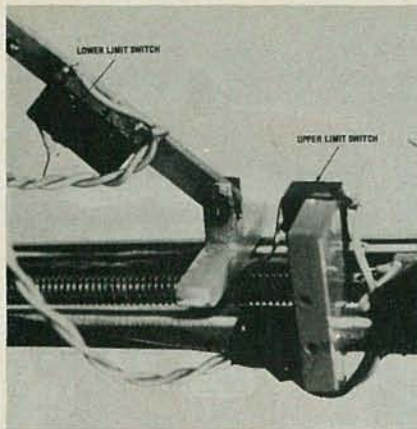


FIG. 10—LIMIT SWITCHES attached to contractor-bar and aluminum block on side rod.

There are two things to bear in mind when placing the limit switches. First, make sure that positive contact will always be made and that there is no possibility that the switch can be turned on accidentally. Second, when taping the switches' wires (and those of the other electrical parts, such as the motors) in place, take care that the tape and wires do not impede the action of any of the moving parts.

The wiring of the limit switches, end-effectors and motors will be covered in some more detail toward the end of this section.

End-effectors

An arm is of little use without a hand at the end of it, so we will present two elementary, but serviceable, types of end-effectors for you to choose from and give you the option of constructing a more complex (and expensive) one, should you so desire.

The two basic hand types we'll describe are the *finger* and the *claw*. Your robot, being ambidextrous, can actually have one of each, using one for one purpose, and one for another.

The grasping action of both types of hand is provided by solenoids—electromagnetic coils with rods through their centers. When a current is passed through the coils, the rod is either pulled into them or pushed out of them. If that rod is connected to part of the hand, the hand will close (in our case) when power is applied to the solenoid. When power is cut, the hand opens by means of a spring which is either part of the solenoid or part of the hand mechanism itself.

Selection of the solenoids is not critical. There are three conditions which must be satisfied: voltage, size, and degree of travel.

The solenoids should be rated to turn on with 12 volts since the robot will almost certainly be using a self-contained 12-volt storage battery when it is operating under its own power. The size of the solenoids will determine the strength of its grip. You may want to use a stronger solenoid in one hand than in the other to allow the robot to perform tasks requiring

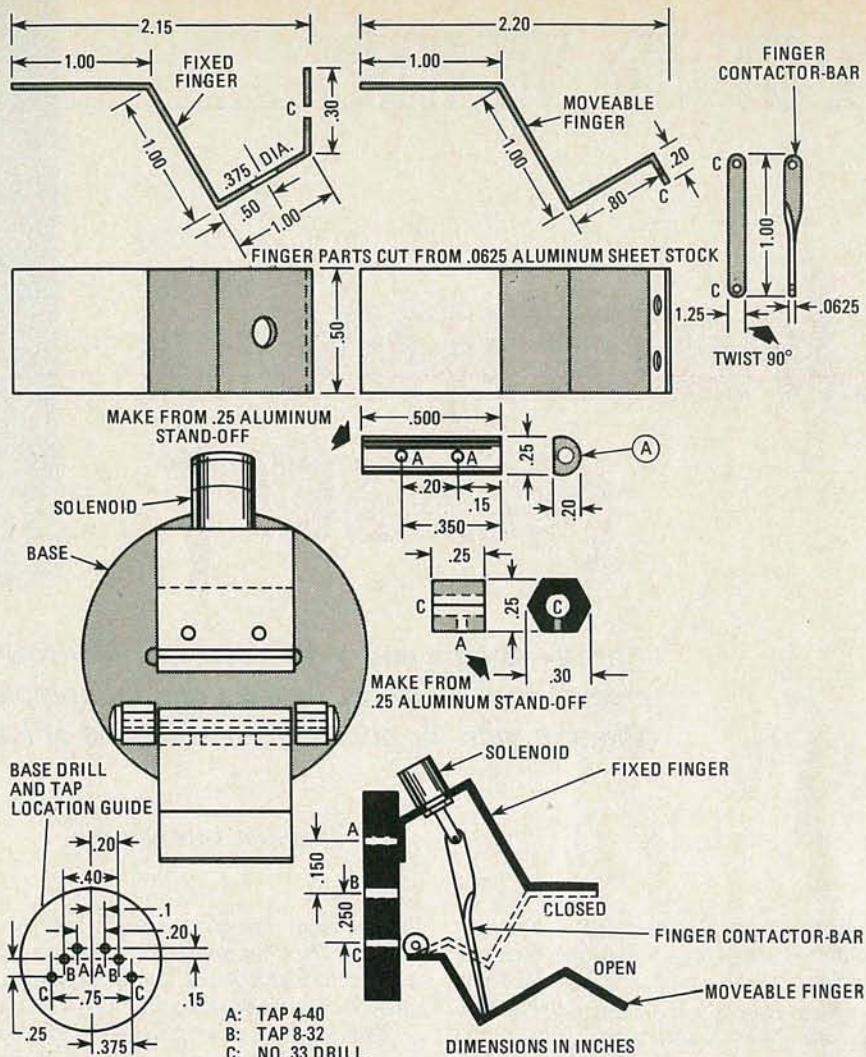


FIG. 11—FINGER-TYPE end-effector assembly drawing. Hinge construction is described in text.

different degrees of delicacy. As for the degree of travel (the distance of the solenoid's rod can move) we've found that a $\frac{1}{2}$ - to $\frac{3}{4}$ -inch rod allows the hand to open far enough for most applications.

Finger-type

Dimensions of the finger-type end-effector are shown in Fig. 11 and one of the completed units in Fig. 12. The material used for that part is $\frac{1}{16} \times \frac{1}{2}$ -inch sheet aluminum. The fixed (upper) finger is made from a piece 3.3 inches long and the movable (lower) finger, from a 3-inch one. The angles should be formed by placing the metal in a vise and bending as evenly as possible. Use a hammer to give uniformity to the surface.

The *finger contractor-bar* is made of $\frac{1}{16} \times \frac{1}{4}$ -inch aluminum, drilled at both ends. The length depends on the solenoid's travel. As shown in Fig. 11, a half-twist is put into that bar. One end of the bar is attached to the solenoid, which is mounted on the outside of the fixed finger, and the other is inserted through a slot sawed in the outside edge of the movable finger and secured with a cotter pin or similar device.

The movable finger is attached to the hinge (refer to Fig. 13) by two No. 4-40 screws. The hinge itself is supported at

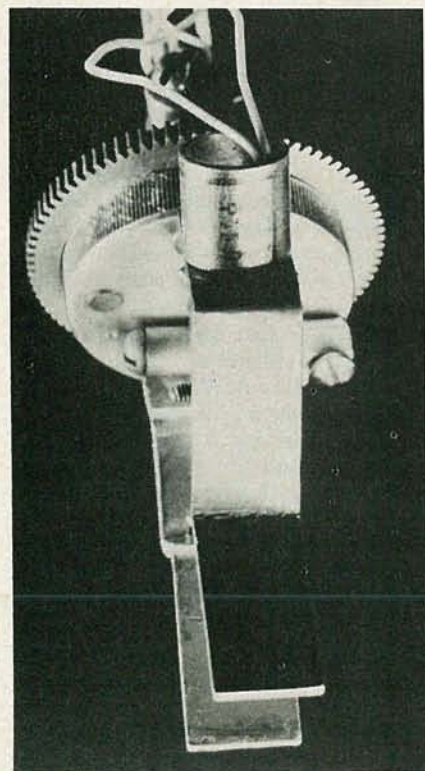


FIG. 12—COMPLETED FINGER-TYPE end-effector. Gear is non-functional, but adds to appearance.

one end by a 1/2-inch diameter piece made from a section of an aluminum stand-off with a long No. 4-40 screw acting as the hinge pin. The finger/hinge assembly is

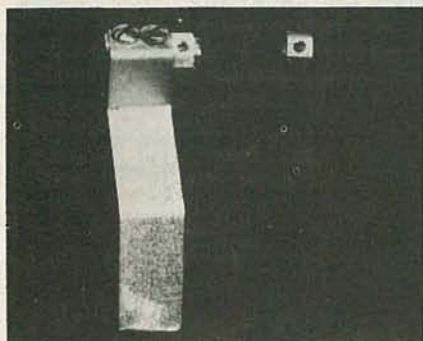


FIG. 13—DETAILS OF HINGE used in finger-type end-effector assembly.

fastened to an end-plate one inch or more in diameter and 1/2 inch thick using No. 8-32 screws and that, in turn, is mounted to the last cross-rod of the manipulator's forearm. The original Unicorn-One used a non-functional gear to build up the end plate and to give the robot a touch of class.

The finished end-effector may be fixed horizontally, vertically, or at any angle in between. Its position depends on the use to which the member will be put.

Claw-type

For heavier-duty applications, you might want to use a claw-type end-effector; that type of hand is shown in Figs. 14 and 15. On 1/4-inch aluminum plate, use a scribe to mark the outline of the two sections. Rough-cut the pieces, taking care to keep to the outside of the outline to allow a margin for error.

Using a hacksaw on the inside angles of the claw may prove to be difficult or even

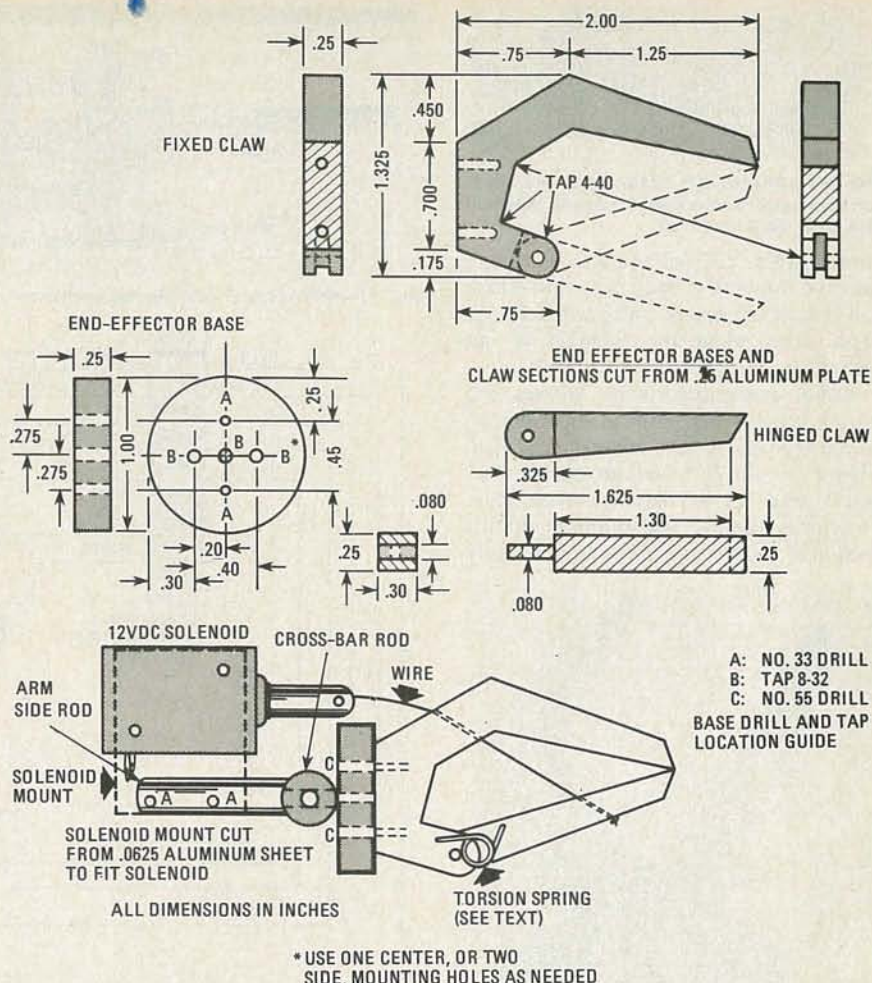


FIG. 14—CLAW-TYPE end-effector assembly drawing. This is a heavier-duty mechanism than the finger-type and you may want one of each.

impossible. Instead, try drilling a closely-spaced series of small holes along the *outside* of the part. Then, using a cold chisel, knock it out and file it to shape, along with the rest of the claw.

Drill two small holes through the two claw sections, in the plane of movement (parallel to the flat sides of the claws), to pass the cable from the solenoid, which can be anchored by a screw to the lower

PARTS LIST					SUPPLIERS	
Item	Size	Quantity	Supplier's part no.	Supplier		
Sheet aluminum	.0625 in. thick	1 X 7.5 in.*	SA625	A	A The Robot Mart Room 1113 19 W. 34th St. New York, NY 10001 (Catalog \$3.00)	G Guardian Electric Mfg. Co. Advertising Dept. 1550 W. Carroll Ave. Chicago, IL 60607 (Write for list of local distributors.)
Sheet aluminum	.250 in. thick	1.5 X 6 in.*	SA250-9	A		
Sheet aluminum	.250 in. thick	0.5 X 6 in.	SA250-3	A		
Solenoid†	Size 50, 1/2 X 1 in. 12 VDC	1	176801-035	F	B Winfred M. Berg, Inc. 499 Ocean Avenue E. Rockaway, NY 11518	H Liberty Controls, Inc. 500 Brookforest Avenue Shorewood, IL 60431
Solenoid†	Size 75, 3/4 X 1 1/2 in. 12 VDC	1	174610-031	F		
Solenoid†	1/2-in. stroke, 12 VDC	1	26	G	F Ledex, Inc. Box 427 Vandalia, OH 45377	I Radio Shack Consult your local telephone directory.
Solenoid†	1/2-in. stroke, 12 VDC	1	L26	H		
Solenoid†	"D"-frame, 12 VDC	1	290001-033	F		
Snap-action switch	Subminiature roller-lever-type, 5-amp	4	275-017	I		
Snap-action switch	Subminiature lever-type, 5-amp	4	275-016	I		
Machine screws	2-56 X 3/8	8				
Machine screws	4-40 X 1/2	11				

NOTES: Items marked with "*" were already specified in the parts list for Part One of this series. Items marked with "†" are to be selected according to the builder's requirements. Components may also be available from suppliers other than those indicated. Some suppliers have minimum order requirements. Inquire before placing order.

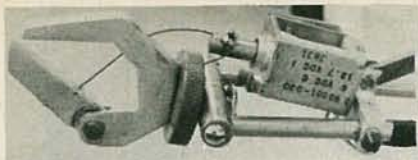


FIG. 15—ASSEMBLED CLAW-TYPE end-effector. Piano wire may be used to connect solenoid and lower portion of claw.

claw. A small hole should also be drilled into the flat side of each claw into which the ends of the spring which will keep the hand open when the solenoid is not turned on.

Robot manipulator-claw springs are not an off-the-shelf item in most places, so you'll probably have to make your own. Figure 16 will give you an idea of what you'll need. If you haven't taken apart any clocks recently, you might try using a section of the type of spring used to close

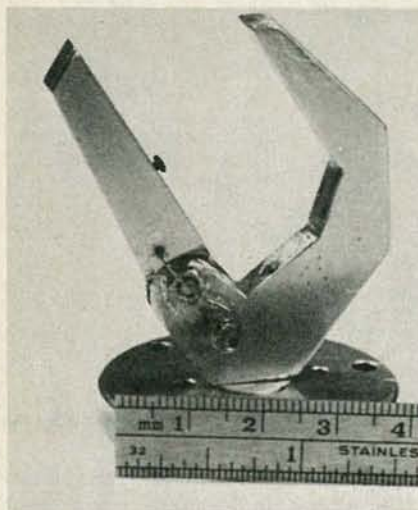


FIG. 16—CLAW-TYPE end-effector showing homemade torsion spring. Text gives details.

screen doors in the summer. Material $\frac{1}{32}$ -in. in diameter seems to work out well.

The tension of the spring will affect the claw's actions. If it's too strong, the claw will not close properly and the robot's grip will suffer, and if it's too weak, there can be problems with keeping it open. If that sounds confusing, bear in mind that the purpose of this particular spring is to hold the claw open, not closed.

Attachment to the manipulator is similar to that for the finger-type end-effector, but you may decide to mount the solenoid (which will probably be larger than the one used for the other) directly on the forearm and feed the cable through to the claw.

You might want to line this hand—or possibly both—with foam rubber or a similar material to give it a better grasp on slippery objects.

A more elaborate type of end-effector is shown in Fig. 17. It also uses the claw-type mechanism but has an additional degree of freedom—a term referring to the different ways a joint can move. (Your own arm, for example, has three degrees of freedom: It can twist, move up and down, and move from side-to-side.)

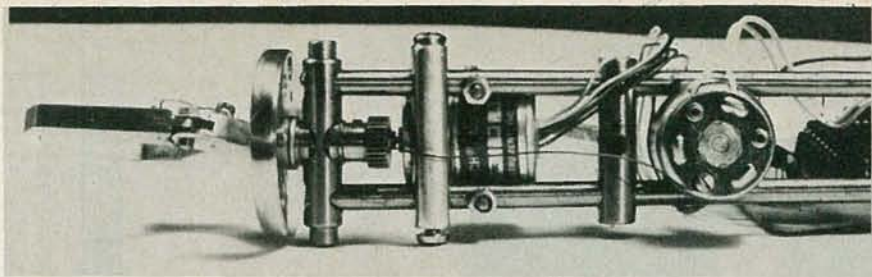


FIG. 17—ROTATABLE end-effector mentioned in text. Stepper motor supplies wrist action.

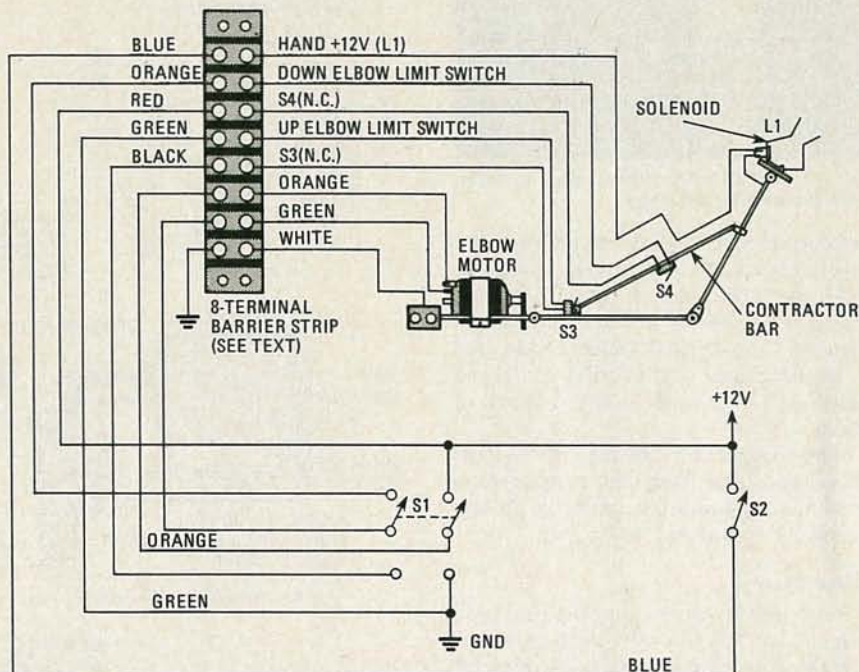


FIG. 18—WIRING DIAGRAM for manipulator and end-effector. Color-code wires in order to avoid confusion.

The added mobility is gained by placing a stepper motor between the arm and the hand. The stepper motor's shaft turns through a small portion of an arc each time a short electrical pulse is applied to it. The result, if enough pulses are applied, is a twist of the wrist—and an added degree of freedom!

Because those pulses are best generated by a digital electronic circuit—which we have not yet discussed—we'll postpone a description of the construction of this type of hand until we start putting together Unicorn-One's electronics. For certain applications, though, it can be indispensable.

Wiring and testing

A wiring diagram for the motor, solenoids, and microswitches, with their associated controls, is shown in Fig. 18. The eight-position terminal strip illustrated is actually part of a 32-position strip, which will terminate all motor and switch connections. Since 32-position terminal blocks are difficult to locate, do the best you can with smaller ones—but allow for at least 32 positions. That will give you several extra positions which you can later use for your own options.

Color-code the wiring to simplify circuit tracing and make sure that everything goes to the right place and that you

have electrical continuity.

Now, with the limit switches installed, you can check out the actual operation of the manipulators and end-effectors. In fact, this is the best time to do so. (If you were to wait any longer, and the arm were attached to the body, you might have to do quite a bit of tearing-apart to get to, and correct, any problem that showed up.)

The parts list shows sources of supply used by the author. There are certain to be others, though, possibly more accessible to you. In fact, many of the materials specified can probably be found, in a form close enough to work with, at your local hardware or building-supplies store. Even closer—and more economical—may be your basement or a nearby junkyard.

The next part of the Unicorn-One series will concern itself with design considerations and construction of the robot's mobility base—the section that gets it from place to place. Also included will be details of the main 32-position terminal strip, which will be the heart of the robot's electrical distribution and control system. The design of that section will permit easy changeover, when you're ready, from manual control by cable-connected console to radio control and, later, to control by microcomputer. **R-E**

PIEZO-ELECTRIC SOUNDER APPLICATIONS

Solid-state "beepers" have a variety of interesting applications. This should give you a few ideas.

CALVIN R. GRAF, W5LFM

IS IT A BUZZER? IS IT A SOUNDER? THOSE are good questions to ask, because the piezoelectric sounder is partly both but unique in its own right. It doesn't buzz, so it's not a buzzer. It doesn't click like the telegraph sounder of days past, so it's not a clicker. But it does sound out with a pure tone when a DC voltage is applied to it, and it operates on the piezoelectric effect. So it is accurately called a piezoelectric sounder.

First introduced by P. R. Mallory about 15 years ago, the sounder was called the Sonalert. It immediately found wide acceptance by the electronic circuit-and-system designer because it emits a near spectrally-pure 2900-Hz tone when a DC voltage between 1 and 28 volts is applied to its terminals. The piezoelectric sounder has been used extensively in applications where a low-current annunciator is needed. Those include wrist watches, alarm clocks, radio beepers, telephone sets, smoke detectors, testing devices, electronic games, intrusion alarms, automobile warning and monitoring, office machines, electronic calculators, timers, and computer peripherals. Many manufacturers produce piezoelectric sounders today. A typical unit is shown in Fig. 1.

A Sound Approach

Sound waves, as you know, are variations in the rate of change in the sound-pressure level. A frequency, or tone, is a measure of the air-pressure variation. A foghorn produces slow variations in air pressure. The whine of a jet engine is produced by many variations in air pressure. A ride in a fast elevator or a passing weather front are also examples of air-pressure



FIG. 1—THE PIEZOELECTRIC SOUNDER is a low-current device that produces an almost pure tone. This is a Sonalert, made by the Mallory Components Group of Emhart Corp.

changes. However, those are not rapid enough for us to hear as sounds, but we do feel the effect on our ears or see the effect on a barometer.

What frequencies are most pleasing to the ear? Research has shown that sound-pressure changes between 700 and 900 Hz are most pleasing to the ear. Those frequencies which attract our attention the most lie between 2000 and 4000 Hz. And you probably well know that a pulsing sound will really get our attention, as compared to a continuous tone.

Ways to sound off

In the army, everyone learns to "sound off" by counting "one, two, three, four." In electronics there are currently three ways to produce an alerting sound.

Electromechanical—The familiar buzzer is probably over 100 years old. That type of audio producer consists of a mechanically-tuned lever with contacts that vibrate back and forth much like a relay using breaker-point switching. The making and breaking of the current, however, generates

radio-frequency interference (RFI) that can be detected beyond 10,000 MHz. The breaker-point lever is connected to a metal disc that vibrates the air to produce a sound. This type emits a buzzing sound and has a high harmonic content that is usually harsh sounding. Others of this type use a small motor to vibrate against a metal or plastic disc to produce a sound.

Speaker-Oscillator—This type of sound producer is a speaker (usually very small and compact) used to deliver sound generated by an electronic oscillator circuit.

Piezoelectric Transducer or Sounder—Truly solid state, this type uses a thin ceramic element bound to a brass disc. The element is connected to a built-in oscillator that drives the ceramic causing it to vibrate a brass disc which flexes and generates a sound wave. This type of sounder is a low-power device that produces a high audio output, and has a long operational life. The piezoceramic sounder by itself (without its transistor driving oscillator circuit) transforms AC voltages to sound-pressure waves. It will also generate an AC voltage across its terminals when stimulated, or vibrated, by a sound-pressure wave. (Is it a speaker or is it a microphone?)

Basic circuits and uses

The basic circuit for the piezoelectric sounder is shown in Fig. 3. It can be used in circuits built around TTL, CMOS, 9-volt transistor batteries, and 12-volt automobile batteries. The sound-output level increases directly with applied voltage, starting near 1 volt and increasing to 20 volts. A higher voltage, approaching 30 VDC, can be used if applied for short periods of

time (a few seconds). The piezoelectric sounder is readily available from many parts sources and its characteristics are shown in Table 1. In Fig. 3, we show a new symbol for the piezoelectric sounder using two wavy lines to indicate that it generates acoustic energy. A single wavy line (sine wave cycle) indicates a generator but without further designation as to whether it is a power generator, an audio generator, or a signal (RF) generator.

Table 1—PIEZOELECTRIC SOUNDER CHARACTERISTICS

Typical Solid-state Piezoelectric buzzer	
Frequency 4.8 kHz
Voltage 1.5 to 20 VDC
Current9 mA at 9 VDC
Size 1 3/8" by 3/8" thick



FIG. 2—THIS SOLID-STATE BUZZER operates with 1.5 to 20 volts DC and delivers a 4.8-kHz signal.

Flashing and sounding circuits

By adding a flasher LED and series-dropping resistor as in Fig. 4, we are able to make the piezoelectric sounder pulse or beep, at the flash rate of the flasher LED. (Be careful and do not confuse the flasher LED with National's LM3909 LED flasher/oscillator.) The 1000-ohm resistor limits the voltage applied to the flasher LED (nominally 5 VDC). In the circuit of Fig. 4, the pulse rate of the sounder is 3 PPS. The pulsating sounder can be used in automobile turn signals and electronic and electrical trouble-shooting. When mounted on the rear of a vehicle and powered from the back-up light circuit it becomes an automotive back-up warning device. The flasher LED is readily available from several manufacturers. The flasher is an IC that switches

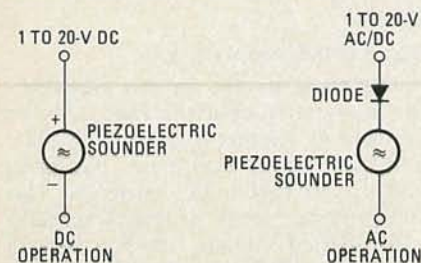


FIG. 3—BASIC CIRCUIT AND SYMBOL for the piezoelectric sounder. Sound energy is produced with as little as 1 mA.

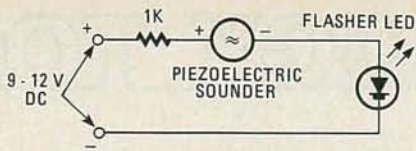


FIG. 4—The PIEZOELECTRIC SOUNDER is made to pulse at a 3 pulse-per-second rate by adding a flasher LED.

Table 2—SOUNDER AND FLASH RATE vs. voltage and capacitance (refer to Fig. 5)

Capacitance, C	Voltage	Flash/Sound Rate
47 μ F	3 VDC	6 pulses in 5 seconds
	6 VDC	4 pulses in 5 seconds
	9 VDC	No output
33 μ F	3 VDC	4 PPS
	6 VDC	2 PPS
	9 VDC	No output
100 μ F	3 VDC	4 PPS (soft note)
	6 VDC	2 PPS
	9 VDC	No output

voltage to a LED at a 3 PPS rate. Current drawn at 5 VDC is about 20 mA. The cost is under \$2.

We vary the pulse of the piezoelectric sounder by connecting a capacitor across it as in Fig. 5. Now the flasher-LED flash rate is sensitive to applied voltage as shown in Table 2.

Light Input to Photocell—When we place a photocell across the piezoelectric sounder, we make the circuit sensitive to ambient light. Figure 6 shows a circuit that will make the sounder and LED pulse at 3 PPS when


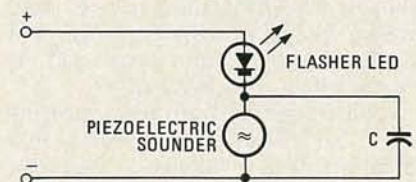


FIG. 5—VARYING PULSE RATES are produced by placing a capacitor across the sounder. (See Table 2.)

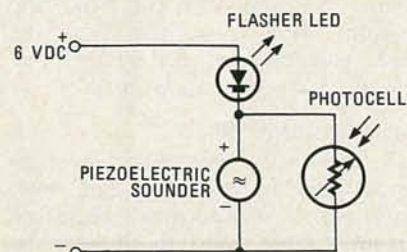

IN LIGHT
LED PULSES 3 PPS
PIEZOELECTRIC SOUNDER SOUNDS AT 3 PPS

IN DARK
LED LIGHTS CONTINUOUSLY
PIEZOELECTRIC SOUNDER SOUNDS CONTINUOUSLY

FIG. 6—ADD A PHOTOCELL to make the pulsing sounder respond to different light levels.

the photocell is illuminated (low photocell resistance), but will remain on continuously in the dark (high photocell resistance). In Fig. 7, we see a circuit arrangement that draws no current in its standby, or dark mode (high photocell resistance), but begins pulsing when the light level reaches a certain level (low photocell resistance). The circuit gets its power from a 9-volt battery.

We will now look at a very simple circuit that uses the low-current characteristics of the piezoelectric sounder. With it, we can check for continuity, or for voltage in a circuit. The few components required for this simple tester can be assembled in the plastic-top cap of a shave cream or other spray can. Use two 24-inch long leads with alligator clips for test leads.

Continuity Tester—The circuit in Fig. 8 is arranged so when the switch is set for CONTINUITY, a small amount of current is drawn through the piezoelectric sounder and the external circuit under test. By shorting the probes, you can establish an audio reference

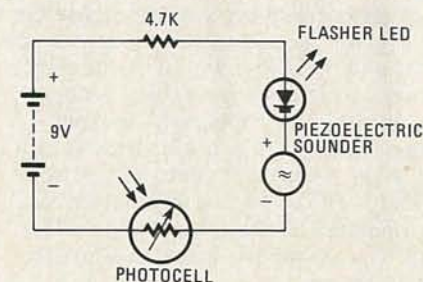


FIG. 7—CONNECT A PHOTOCELL in series to turn the circuit off in the dark (high photocell resistance). Light will cause the sounder to pulse.

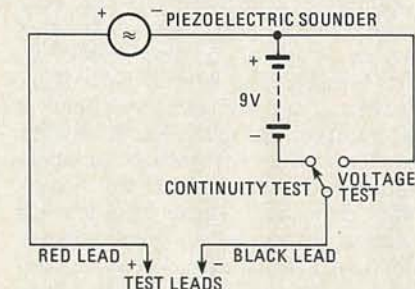


FIG. 8—CONTINUITY/VOLTAGE TESTER using the piezoelectric sounder. Observe correct polarity for voltage tests.

level for zero ohms. An open circuit is obviously infinity and no sound is produced. With a good ear and a good battery, you will be able to hear an indication for 20K to 30K resistance in the circuit under test. That arrangement is good for testing continuity of light bulbs, resistors, diodes, coils, transistors, motors, relays, etc. When you test volume controls for continuity, you can spot a "scratchy" control because the audio level of the tone of the piezoelectric sounder will shift abruptly.

continued on page 99

Better than DOLBY B???

New Noise Reduction System for Tape Recorders

LEN FELDMAN
CONTRIBUTING HI-FI EDITOR

This new noise-reduction system from Nakamichi provides a dynamic range 18 dB greater than Dolby B.

EVERY CASSETTE TAPE-DECK USER OWES a debt of gratitude to Dr. Ray Dolby. His introduction of the Dolby B noise-reduction system more than ten years ago was largely responsible for the wide acceptance of cassette tape recording as a true high-fidelity program storage medium. Although the cassette format delivers much higher performance quality today than it did ten years ago, it is still far from being a "noise-free" system.

The Dolby B noise-reduction system represents a clever choice of compromises that provide a reasonable amount of noise reduction with a minimum of undesirable side effects, at low cost. Those compromises involve limiting the total amount of noise reduction as well as the frequency bandwidth of the system. Until now, the tape-recording enthusiast has had to be content with the 8-to-10 dB of signal-to-noise improvement of the Dolby B system. While modern cassette decks almost universally have built-in Dolby B, tremendous strides in the quality of pre-recorded program sources and a growing interest in live recording demand further improvements in cassette deck performance. Critical listeners often feel that the Dolby system does not provide enough noise reduction for those more esoteric recording applications.

Principles of noise reduction

Nakamichi first became interested in developing a better noise-reduction system several years ago, after evaluating a professional noise-reduction system called Telcom C4D developed by Telefunken of Germany. According to Nakamichi, that system (although

too expensive for consumer applications) provided an unusually large ratio of noise reduction and was particularly free of such undesirable side effects as noise pumping or signal coloration. A cooperative effort between Telefunken and Nakamichi has resulted in a modified consumer version of that noise-reduction system, Nakamichi calls it *High-Com II*. Nakamichi's first commercial version of the system is in the form of a separate add-on device, (see Fig. 1) that can be added to any high-quality cassette deck.



Fig. 1—HIGH-COM II noise-reduction system can be used with any high-quality cassette deck.

Before discussing the specifics of the *High-Com II* noise-reduction system, let us examine the basic principle behind noise-reduction systems. The *comparer* concept that forms the basis of all noise-reduction systems is quite simple. Before recording, the dynamic range of the program is compressed by a circuit, the signal of which is controlled by the signal level itself. Once compressed, the program "fits" on the tape. The weakest signals are amplified and recorded at a level well above the tape noise while strongest signals are compressed and recorded below the level at which distortion occurs because of tape saturation. During playback, the exact converse action takes place: Strong signals are expanded or amplified to compensate for the compression they receive during recording, while the level of weak

signals is reduced, restoring them to the relative intensity they had before recording.

While the basic principle sounds simple, Nakamichi soon discovered that designing a cost-effective noise-reduction system that works well in conjunction with a cassette deck is not an easy task. Each element of the system had to be carefully considered and optimized. If necessary, a compromise between optimum and practical had to be selected.

The ultimate choice of the compression/expansion ratio is a good example. For an expander to be free of noise pumping, most of the recorded signal must be well above the noise floor of the tape. Since the cassette deck's low speed limits the maximum signal levels that can be recorded on the tape, a relatively high compression ratio is needed to maintain a great enough margin between low-level signals and noise. If too high a compression ratio is chosen, however, it becomes difficult to recover the original dynamics during expansion and the entire system becomes very sensitive to slight level variations, such as those caused by inconsistencies in the tape coating itself.

New noise reduction system

In the *High-Com II* system, a 2:1 compression ratio is used to get a 20-dB improvement in signal-to-noise. The 2:1 ratio is maintained throughout most of the dynamic range of the system, except at very low input levels, where the ratio is restored to 1:1. That largely linear-transfer characteristic of the system makes it relatively immune to minor mismatches in level. The 2:1

ratio is not enough, however, to overcome noise pumping completely. That effect is caused by a compander at frequencies other than those of the input signal.

A good example of that is recording a single tone. Noise in the immediate vicinity of the tone's frequency will be masked by the tone signal itself; but noise well above or below that frequency is not masked. It is the modulation of that unmasked noise by the action of the compander that is often noticeable and objectionable. What makes matters even worse is that with 20 dB of basic noise reduction there is less of a constant overall hiss level to mask the noise modulation.

Both the professional Dolby-A and Telcom C4D noise-reduction systems effectively eliminate that type of noise modulation by processing the signal in four frequency bands. In other words, companding action in one frequency range is controlled separately from that in another. Such a complex configuration is far too costly for a consumer version of either system. The Dolby B system combats the problem by limiting its operation to only the high frequencies. The action of Dolby B can be understood by referring to Fig. 2, a sequential trace of residual tape noise, using a spectrum analyzer over the range from 20 Hz to 20 kHz. Vertical

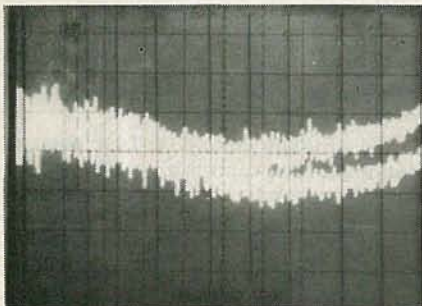


Fig. 2—HOW DOLBY B compensates for high-frequency noise. Action begins above 1 kHz.

sensitivity is 10 dB per box. Note that the two plots (without and with Dolby B turned on) are identical from around 20 Hz to just beyond 1 kHz. At that point the action of the Dolby B system reduces high-frequency noise at a sliding or increasing rate (lower noise trace) out to the limits of the sweep. That makes sense for cassette tape because the overwhelming proportion of noise at the slow tape speed is high-frequency hiss.

However, with 20 dB of noise reduction provided by the *High-Com II* system, it is no longer acceptable to concentrate solely on the higher frequencies. A 20-dB reduction of hiss with no corresponding reduction at low frequencies would only make low-frequency noise equally more audible. The *High-Com II* noise-reduction sys-

tem deals with that problem and minimizes noise pumping still farther by processing the signal in two bands. Using more than two frequency bands would, of course, provide added insurance against noise pumping, but the benefits had to be weighed against the cost. The Telefunken HighCom IC, developed for the *High Com II*, provides a wide selection of attack and release times, and with two bands of processing, an appropriate set of dynamic characteristics could be selected for each frequency range. Comparing the noise-reduction results obtained by using Dolby B (Fig. 2) with those obtained by using the *High Com II* system (Fig. 3), both the increased amount of noise reduction and the fact that some noise reduction is taking place even at mid-to-low frequencies are obvious.

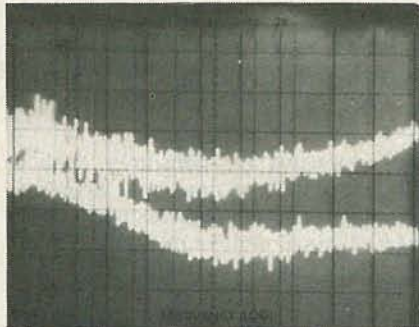


Fig. 3—EFFECT OF High-Com II on residual tape noise. Compare this with Dolby B in Fig. 2.

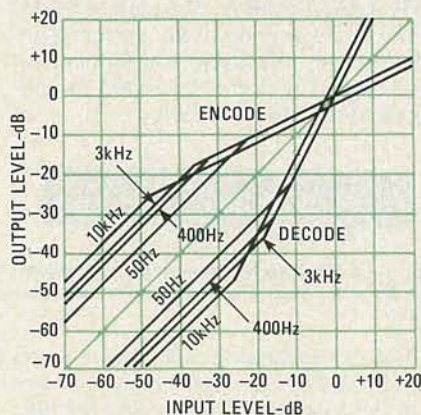


Fig. 4—ENCODING/DECODING and input/output characteristics of the High-Com II system.

Figure 4 shows the encode and decode characteristics of the *High Com II* system and its input/output characteristics. The 0 dB shown is the reference level of the system and the level recorded on the tape for that reference is 200 nWb/m (Nano-Webers Meter—measure of magnetic flux-density). The degree of encoding or decoding is small at low frequencies, increasing as the frequencies get higher. Depending upon frequency, below a certain level the encode-to-decode ratio becomes 1:1, suppressing the breathing noise changes in signal levels cause.

Figure 5 shows the record-play amplitude response and noise analysis of the *High Com II* system coupled to a Nakamichi Model 680 cassette deck using metal particle cassette tape. It was supplied to us by Nakamichi. The pen traces on the lower right corner of the figure show wideband noise levels

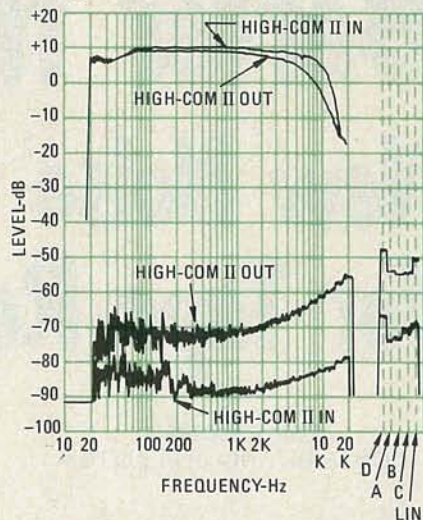


Fig. 5—HIGH COM II record/playback amplitude response and noise analysis.

with various weighting filters. Note that the noise reduction with no weighting filter applied is a full 19 dB. With "A" weighting, the noise reduction is exactly 20 dB, or about 12 dB greater than with the Dolby B system. Actually the increase in dynamic range is somewhat better than 20 dB because, unlike the Dolby B system, the *High Com II* system continues its companding action beyond the reference 0 dB level.

Since 3% total harmonic distortion on that tape deck normally occurs at a true recording level of +6 dB (0 dB equals 200 nWb/m), the 2:1 compression level permits an input level of +12 dB as a maximum. That accounts for the high output of the +10 dB trace in Fig. 5. It would normally be lower because of saturation, but with the 2:1 compression, the actual record level reaching the tape is equivalent to +5 dB. Since the "A" weighted noise with the *High Com II* system turned on is 74 dB below 0 dB, the total dynamic range available, referenced to the 3% total harmonic distortion point, is 74 dB plus 12 dB or 86 dB! That is a full 18 dB better than the dynamic range that is available (referenced to 3% total harmonic distortion level) using Dolby noise reduction.

To preserve high-frequency transients, any compander must have a fast attack time. It must recognize an abrupt change in signal level quickly, or the characteristics of the transient will be altered or destroyed. On the other hand, if the compander has too fast an attack time, it will tend to fol-

continued on page 104

R.E.A.L. SOUND



CIRCLE 106 ON FREE INFORMATION CARD

B.I.C./Avnet Model T-3 Cassette Deck

LEN FELDMAN
CONTRIBUTING HI-FI EDITOR

AS MOST OF YOU KNOW, CASSETTE DECKS ALL operate at a single, standard speed of 1 1/2 inches-per-second. All, that is, except B.I.C./Avnet Corporation's new series of stereo cassette decks, each of which operates at that speed and also at twice that speed, or 3 3/4 ips. Three such two-speed decks are now being marketed by B.I.C./Avnet, and, in all likelihood, even more models (probably higher priced than the first models) are on the way. There are many industry rumors about how B.I.C./Avnet was able to "break with tradition" (not to mention the Philips agreement that presumably governs all cassette-deck manufacturers, since Philips originated the cassette-tape format), and offer speed options in cassette decks. In any case, B.I.C./Avnet has done it and assures everyone that the company is on safe legal ground. We certainly hope so because with increased speed comes vastly increased performance capability.

Of the three two-speed decks now available, we chose to test the third—the top-of-the-line model T-3, which is the first of those decks to offer true three-head operation and its related tape-monitoring capability. In the model T-3, the record and play heads are electrically separate components, but are mounted in a common housing. As a result, no tape azimuth alignment is required, as would be the case when three-head decks use physically separated record and play heads.

A front-panel view of the model T-3 is shown in Fig. 1. The left-hand section of the black front panel contains the cassette compartment; when the STOP/EJECT push-button is depressed, the cassette door opens smoothly and slowly (the action is viscous-damped). Additional piano-key-type tape-transport controls below the cassette compartment include a RECORD switch; REWIND, PLAY, and FAST-FORWARD switches; and a PAUSE switch. Tape motion is controlled by a dual-capstan tape-drive system powered by a two-speed DC servomotor. The POWER on/off push-button is

located in the lower left-hand corner.

To the right of the cassette compartment are a three-digit resettable tape counter, a MEMORY push-button (that permits you to rewind the tape to a preset zero point on the digit counter), and a pair of calibrated peak-reading record-level meters that can accurately read all the way from -40 dB to +5 dB. Note that "0 dB" on those record-level meters corresponds to a level of 200 nanowebers-per-meter (rather than the lower 185 or 160 nW-per-meter often used as 0 calibration points for cassette-deck meters). Keep that in mind when evaluating the headroom figures cited later in this article. An innovatively designed LED indicator is located between the two peak-reading meters. As long as peak record levels are in a safe (or low-distortion) area, the LED glows green. If instantaneous record levels exceed the value considered acceptable by B.I.C./Avnet, the LED magically changes color and glows red, warning the user to back off on record levels or suffer the consequences of over-recording and high distortion levels during playback. Below the two meters are a pair of large, concentrically-mounted record-level controls, while to the right are an output-level control and a separate phone output-level control. The deck can therefore handle headphones with a wide range of sensitivities, and you can adjust the sound level from the headphones without affecting main output level that is being fed to the rest of the system.

The lower edge of the front panel contains a speed-selector switch (with settings for 1 1/2 or 3 3/4 ips); and an equalization-selector switch (with settings for either 120 or 70 μ s). There is a three-position bias-selector switch (marked low, normal, or high, rather than being referred to specific tape types); and a three-position RECORD switch with settings labeled SAFE, READY, and MUTE. In addition, there's a Dolby-mode switch (with a COPY and ON position that lets you use the built-in Dolby circuitry for purposes other than just tape recording and

RADIO-ELECTRONICS AUDIO LAB

R.E.A.L. SOUND

RATES

B.I.C./AVNET T-3 CASSETTE DECK

SUPERB

Copyright © Gernsback Publications Inc., 1979

playback); and an MPX filter switch. That is useful when recording stereo FM programs off-the-air from tuners whose outputs contain significant subcarrier high-frequency products that might upset Dolby operation and calibration, or might beat with the deck's bias oscillator: Three pushbuttons to the right of those switches select source of tape monitoring, introduce a record-calibration test tone, and select microphone or line inputs. (Mixing of microphone and line inputs is not possible with this deck.) Left and right microphone-input jacks, as well as a phone-output jack (stereo) at the lower right, complete the panel layout. Line-input and line-output connections are both made at the rear panel through phono-tip jacks.

Lab measurements

To evaluate and measure the two-speed deck's performance properly, we treated the unit as though it were two separate decks: one operating at a standard 1 1/2-ips speed, the other at the increased speed of 3 3/4 ips. So many performance characteristics change when the speed is increased (all of them for the better, by the way) that we have shown our results for slow and fast operation separately. Table 1 summarizes our results at 1 1/2-ips operation, while Table 2 shows measurements obtained at the higher 3 3/4-ips speed. We made all measurements using TDK-type AD C-90 cassettes as the "standard" sample, while TDK-type SA C-90 cassettes were used for all measurements in the 70-microsecond equalization setting. As mentioned earlier, the manufacturer did not assign generic tape names to the three bias



MANUFACTURER'S PUBLISHED SPECIFICATIONS*:

(*Items shown to either side of slash mark correspond to operation at 1 1/2 ips/3 3/4 ips running speeds.)

Frequency Response (± 3 dB): 70 μ s or CrO₂ tape, 25 Hz-19 kHz/25 Hz-22 kHz. **S/N Ratio. (A-Weighted):** 70 μ s tape, 55/58 dB (Dolby off); 63/67 dB (Dolby on). **Wow-and-Flutter (WRMS):** 0.05/0.035%; unweighted, 0.09/0.06%. **Harmonic Distortion:** 70 μ s tape, 1.8/1.5%, at 0 VU record level. **Fast-Forward or Rewind Speed (C-90):** 45 seconds. **Input Sensitivity:** line, 200 mV. **Output Level:** 2 volts. **Meter Type & Range:** peak reading, -40 to +5 dB. **Power Requirements:** 105/135 volts, 50/60 Hz, 35 watts. **Dimensions:** 17 15/16 W \times 6 7/8 H \times 10 1/8 inches D. **Weight:** 14.8 lbs. **Suggested Retail Price:** \$529.95.

positions on the front-panel switch. They do, however, list recommended bias-switch settings for different brands and grades of tape. In many instances, the settings are *not* the same for high speed as they are for the standard speed. For example, we found (and B.I.C./Avnet recommends) that the high bias setting should be used for TDK-SA tape (whose bias requirements are similar to those of chrome tape) at both low and high speeds. However, for the TDK-AD tape we found that using the low bias setting at slow speed and the high (not the normal) setting at high speed yielded best overall results with respect to frequency response, signal-to-noise (S/N) ratio and distortion.

Since the *Model T-3* is a three-head tape deck, we were able to conduct sweep-frequency measurements (in addition to point-by-point plots or tabulations) of overall record/play response. That was done for the TDK-SA tape at both the slow-speed (Fig. 2) and high-speed (Fig. 3) modes for -20-dB and 0-dB record levels. The frequency-response figures shown in Tables 1 and 2 are those we obtained at the -20-dB record level. The upper traces in Figs. 2 and 3 show a particularly interesting phenomenon: At the slow 1 1/4-ips speed, the typical high-frequency rolloff caused by tape saturation occurs. In contrast, at the 3 3/4-ips speed, response remains virtually flat all the way out to 20 kHz! What that means is enormously increased headroom at high frequencies, in addition to other benefits (abundantly evident when you compare the measured distortion, signal-to-noise, and wow-and-flutter specs shown in Tables 1 and 2).

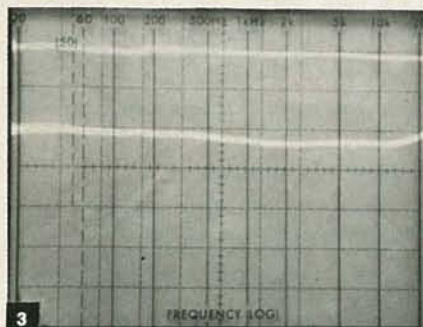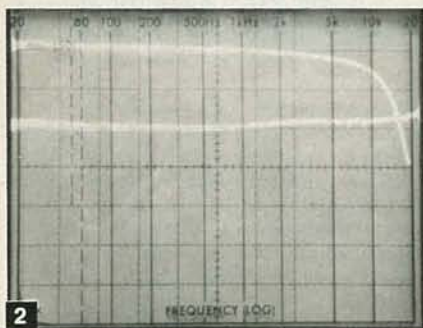

By changing the spectrum analyzer's sweep mode from frequency log (as shown in Figs. 2 and 3) to linear (from approximately 0 Hz to 20 kHz), we were able to display the improvement graphically in both S/N and third-order distortion that is gained by increasing the tape speed to 3 3/4 ips. Figure 4 shows a 1-kHz signal recorded onto the TDK-SA sample tape (this signal appears as the tall spike to the left in Fig. 4). On the right another spike represents

RADIO-ELECTRONICS PRODUCT TEST REPORT

TABLE 1

Manufacturer: B.I.C./Avnet

Model: T-3

CASSETTE TAPE DECK MEASUREMENTS AT 1 1/4 IPS

	R-E Measurements	R-E Evaluation
FREQUENCY RESPONSE MEASUREMENTS		
Frequency response, standard tape (Hz-kHz ± dB)	10-19, 3.0	Excellent
Frequency response, CrO ₂ tape (Hz-kHz ± dB)	10-23, 3.0	Superb
Frequency response, other (see text) (Hz-kHz ± dB)	N/A See Fig 2	N/A
DISTORTION MEASUREMENTS (RECORD/PLAY)		
TDK-SA/TKD-AD		
Harmonic distortion -3 VU (1 kHz) (%)	1.2/1.2	Superb
Harmonic distortion 0 VU (1 kHz) (%)	1.3/1.3	Superb
Harmonic distortion +3 VU (1 kHz) (%)	2.0/1.5	Excellent
Record level for 3% THD (dB)	+4.0/+5.5	Excellent
SIGNAL-TO-NOISE RATIO MEASUREMENTS		
Standard tape, Dolby off (dB)	57	Excellent
Standard tape, Dolby on (dB)	65.5	Excellent
CrO ₂ tape, Dolby off (dB)	57	Very good
CrO ₂ tape, Dolby on (dB)	66	Excellent
MECHANICAL PERFORMANCE MEASUREMENTS		
Wow-and-flutter (% WRMS)	0.045	Superb
Fast wind and rewind time, C-60 (seconds)	45	Superb
COMPONENT MATCHING CHARACTERISTICS		
Microphone input sensitivity (mV)	0.16	
Line input sensitivity (mV)	35.0	
Line output level (mV)	1.9 volts	
Phone output level (mV)	317/8 ohms	
Bias frequency (kHz)	N/A	
TRANSPORT MECHANISM EVALUATION		
Action of transport controls		Superb
Absence of mechanical noise		Excellent
Tape head accessibility		Good
Construction and internal layout		Excellent
Evaluation of extra features, if any		Excellent
CONTROL EVALUATION		
Level indicator(s)		Excellent
Level control action		Very good
Adequacy of controls		Excellent
Evaluation of extra controls		Excellent
OVERALL TAPE DECK PERFORMANCE RATING		
		Superb

TABLE 2

CASSETTE TAPE DECK MEASUREMENTS AT 3 3/4 IPS.

	R-E Measurements	R-E Evaluation
FREQUENCY RESPONSE MEASUREMENTS		
Frequency response, standard tape (Hz-kHz ± dB)	20-23, 3.0	Superb
Frequency response, CrO ₂ tape (Hz-kHz ± dB)	16-24, 3.0 See Fig. 3	Superb
DISTORTION MEASUREMENTS (RECORD/PLAY)		
TDK-SA/TKD-AD		
Harmonic Distortion at -3 VU (1 kHz) (%)	0.8/1.0	Excellent
Harmonic distortion at 0 VU (1 kHz) (%)	1.0/0.8	Superb
Harmonic distortion at +3 VU (1 kHz) (%)	1.0/0.9	Superb
Record level for 3% THD (dB)	+7.5/+11.0	Superb
SIGNAL-TO-NOISE RATIO MEASUREMENTS		
Standard tape, Dolby off (dB)	59	Excellent
Standard tape, Dolby on (dB)	67	Superb
CrO ₂ tape, Dolby off (dB)	61	Superb
CrO ₂ tape, Dolby on (dB)	69	Superb
MECHANICAL PERFORMANCE MEASUREMENTS		
Wow-and-flutter (% WRMS)	0.025%	Superb
Fast wind and rewind time, C-60 (seconds)	45	Superb
COMPONENT MATCHING CHARACTERISTICS		
Microphone input sensitivity (mV)	See Table 1	
Line input sensitivity (mV)	See Table 1	
Line output level (mV)	See Table 1	
Phone output level (mV)	See Table 1	
Bias frequency (kHz)	See Table 1	
TRANSPORT MECHANISM EVALUATION		
Action of transport controls		Superb
Absence of mechanical noise		Excellent
Tape head accessibility		Good
Construction and internal layout		Excellent
Evaluation of extra features, if any		Excellent
CONTROL EVALUATION		
Level indicator(s)		Excellent
Level control action		Very good
Adequacy of controls		Excellent
Evaluation of extra controls		Excellent
OVERALL TAPE DECK PERFORMANCE RATING		
		Superb

RADIO-ELECTRONICS PRODUCT TEST REPORT

TABLE 3

Manufacturer: B.I.C./Avnet

Model: T-3



OVERALL PRODUCT ANALYSIS

Retail price	\$529.95
Price category	Medium
Price/performance ratio	Superb
Styling and appearance	Excellent
Sound quality	Superb
Mechanical performance	Excellent

Comments: With respect to the operation of the model T-3 at 3 3/4 inches-per-second, it is not possible to compare this unusual stereo cassette deck with any other cassette deck available. As of this writing, there is nothing that operates both at the higher 3 3/4 ips speed and standard cassette speed. We expected that the higher-speed performance of this deck would be much better than the 1 1/2 ips performance of more expensive decks, knowing the limitations of slow speed tape recording. What we were not prepared for was the outstanding performance that this deck achieves even when operating at the slower standard speed.

The design engineers could have opted for extended frequency response at the expense of other operating parameters. Instead, they wisely elected to offer a machine in which all the important operating characteristics (i.e., S/N, distortion and frequency response) are beautifully balanced and optimized with respect to each other. At the deck's higher speed, its performance truly equals that of many open-reel machines. Of course, operating at twice the normal speed means that you use twice as much tape. In effect, a nominally labelled C-90 cassette effectively becomes a C-45. To the serious recordist who wants the finest possible recordings, this will pose no great problem. And if you want to be miserly about tape usage, Table 1 confirms that even at low speed the deck maintains a level of performance for which you would have to pay considerably more with other decks.

Aside from the superior measurements shown in Tables 1 and 2, we should note that such recording aberrations as contour effect (the tendency for low-frequency response to waver up to around 150 or 200 Hz) have been all but eliminated (see Figs. 2 and 3). The model T-3's mechanical performance is as impressive as its electrical performance. Although not solenoid-operated, transport control is smooth and positive, and tape handling is safe and reliable. B.I.C./Avnet should be congratulated for taking this bold step in the cassette-deck marketplace.

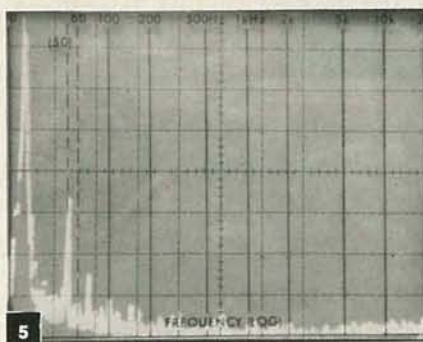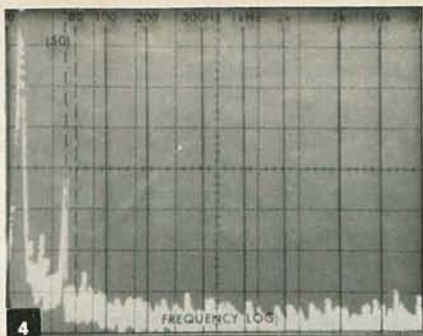

third-order or third-harmonic content (3 kHz, in that instance), while the lower section of the photo displays the random noise content reproduced during playback. In the scope photo of Fig. 5, only the speed was changed, while the 1-kHz recorded signal amplitude and all the gain and sweep settings remained the same. You will note that third-harmonic distortion is measurably lower and overall random noise level is considerably decreased throughout the bandwidth (to 20 kHz).

Summary

Recently, we had occasion to discuss the implications of metal-particle tape with one of the B.I.C./Avnet engineers. As you know, pure metal-particle tape promises to deliver greater headroom (or dynamic range) and improved frequency response especially when it is used in the cassette format. The B.I.C./Avnet engineer pointed out that operating a cassette deck at twice the so-called standard

speed produces exactly the same benefits without having to create new higher-bias circuits, new erase-electronics and heads, and new higher-capacity recording heads. He further indicated that while operating cassette tape at twice the normal speed does indeed use up twice as much tape, the pure metal-particle tape will cost considerably more than even the best grades of cassette tape presently available. He believes therefore that the company's two-speed cassette tape decks negate the actual need for a better tape such as metal-particle tapes. Of course, you can always argue that metal tapes, if used at higher speed in a compatible cassette deck, would yield even further overall improvement in performance.

Our overall product evaluation is contained in Table 3 along with some summary comments regarding this unusual cassette deck. If we have tended to concentrate heavily on the Model T-3's performance at its higher operating speed, that is because we were impressed by the observable differences in performance compared with 1 1/2 ips operation. The B.I.C./Avnet Model T-3 stereo cassette deck is indeed a superb piece of equipment even when compared with ordinary cassette decks operated at the slow 1 1/2 ips speed. Even if you consider this equipment based only on the figures in Table 1, the deck is superb at its price; add the results shown in Table 2 and it becomes a truly incredible machine. **R-E**

Solid State News

Video modulator IC's

Motorola's MC1372 and XC1373 TV video modulators are designed for color TV applications in video games, data terminals, test equipment and videotape recorders. The devices can be driven by the MC6847 video-display generator and other color and video sources.

The MC1372 is a 14-pin device with a chroma subcarrier oscillator using an external 3.58-MHz crystal, a suppressed-carrier double-sideband chroma modulator and an RF modulator.

The lower-cost XC1373, mounted in an 8-pin mini-DIP, has an RF oscillator and dual-input modulator only. It can be used when a composite video source exists in another system.

Both circuits produce signal outputs on

Channel 3 or Channel 4 and can alternatively produce inverted or noninverted video output signals. For details, write to Motorola Semiconductor Products, Box 20912, Phoenix, AZ 85036.

Second-generation VMOS device

Siliconix's second-generation VMOS power FET, the VN84GA, is rated at 12.5 amp and 80 volts which is a six-times current increase over previous transistors. With only microwatt input power, the VN84GA produces up to 80 watts output at low frequencies and a 50-watt output at 30 MHz. The devices do not show any of the secondary-breakdown and thermal runaway characteristics of bipolar transistors. These FET's interface directly with CMOS, TTL, DTL, and MOS families

for use in devices such as solid-state switching regulators, motor controllers, audio amplifiers and micro-processor interfaces.

Using VMOS devices in linear amplifiers up to 30 MHz produces lower distortion because of the linear-transfer characteristics and good high-frequency behavior of the VN84GA, and the low distortion means that only small amounts of feedback are required. The devices can also be used in Class-D audio amplifiers because of their fast switching and zero storage time.

The VN84GA is mounted in a TO-3 package and is priced at \$19.76 in quantities from 1 to 99. Siliconix Incorporated, 2201 Laurelwood Road, Santa Clara, CA 95054. **R-E**

BUILD THIS

WIPEOUT

VIDEOGAME

One integrated circuit equals ten action-packed games. Build this videogame and get in on that action.

L. STEVEN CHEAIRS

BY NOW, NO DOUBT, A NUMBER OF **RADIO-Electronics'** readers associate my name with video games. A fair portion of my articles thus far *have* dealt with that topic—and in the pursuit of the tradition, here is another one. This construction project will provide the reader with ten more black-and-white video games. Both NTSC and CCIR television sets may be used; NTSC is the standard 525-line U.S.A. system and CCIR is the 625-line system used in many foreign countries. Both single-player and two-player games are possible. On-screen automatic scoring has been provided.

Two potentiometers, one for each player, provide for vertical paddle motion. A control voltage, determined by the setting of the potentiometer, charges a capacitor; the charge-level of the capacitor is detected by a Schmitt trigger. Thus the rotation of the pot causes a variation in the voltage across the capacitor that is detected and translated to a player-position on the television screen. The player and his score are color-coded for easy identification. The audio circuit outputs tones to indicate hits of the ball by the player, and impacts with the court border or target obstacles. Game selection is made by using a 10-key switch matrix; either fixed—or momentary-contact—switches are acceptable. Two switches are used to start the ball into motion and to keep it in play during the game. A reset switch is provided to clear the screen to prepare for a new game. Three other switches select skill-level options.

About the games

Five single-player, and five dual-player games are contained on the LSI integrated circuit. Figure 1 shows a typical image for each game. There are three major types of game on that integrated circuit; those are *Wipeout*, *Color Squares*, and *Breakthrough*. The

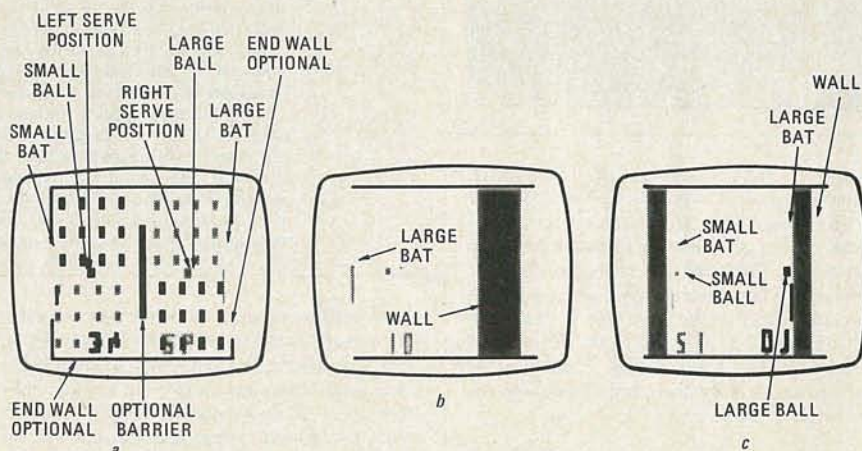



FIG. 1—VIDEO DISPLAYS used by the Ten Action Games. The variations for *Wipeout* and *Color Squares* are shown in a. *Breakthrough 1* and *2* appear in b and c.

first four games that will be described are the wipeout games.

Figure 1-a illustrates the different characters that can be generated when playing the four versions of *Wipeout*

and the four versions of *Color squares*.

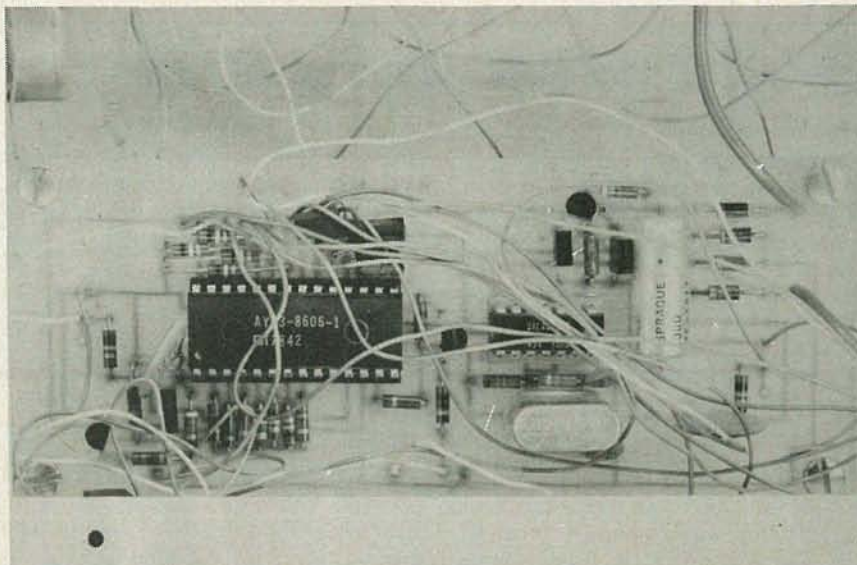Wipeout I is chosen when *select line one* and *strobe line one* are connected, either momentarily or continuously, by switch S9. After game selection and



THE HEART of the Ten Action Games board is the AY-3-8606-1 IC from General Instruments. Many of the components clustered around it are used to set the parameters of the games and display.

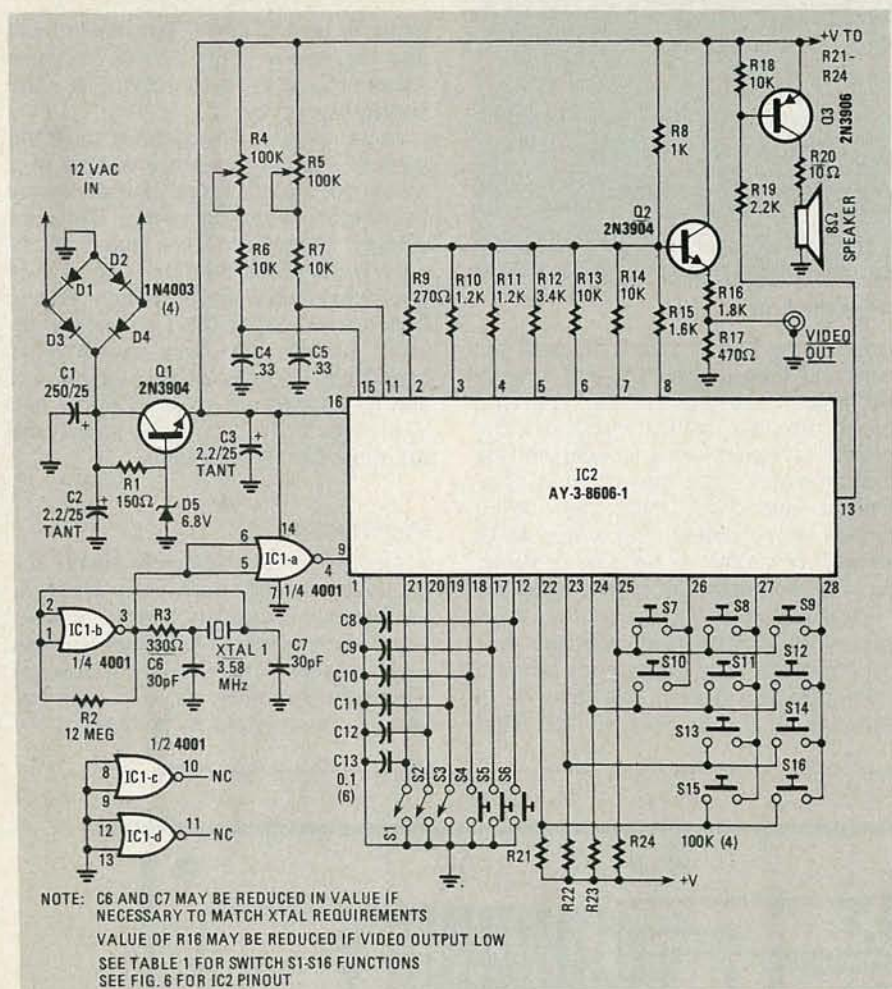
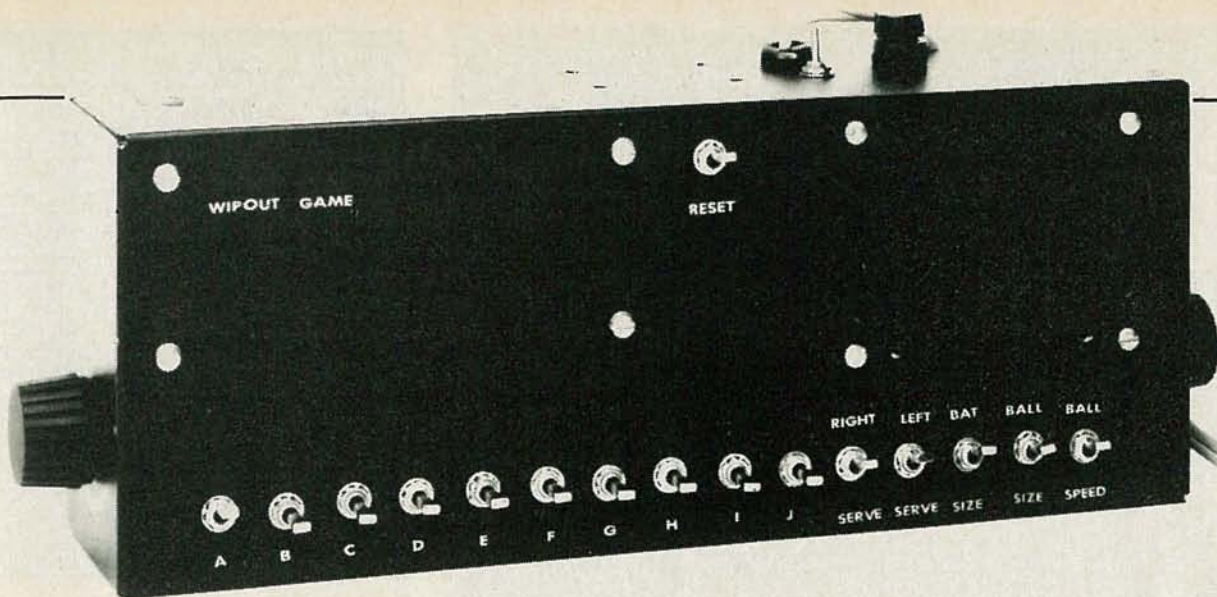


FIG. 2—MAIN SCHEMATIC for the Ten Action Games. A foil pattern is provided in Fig. 4.

game reset, the game is started by pressing either the right or left SERVE button (S5 or S6). The object is to hit every black target-square. The squares disappear as they are hit. No deflection of the ball results from hitting a target-square. The game will end if five consecutive misses occur or if all squares are hit and obliterated. This is a single-player game—the right-hand paddle is used. That paddle is controlled by the

pot connected nearest the LSI IC on the PC board. The score, paddle, ball, and boundary are gray. The score displays the number of targets hit.

Wipeout II is also a single-player game; it uses both the left and right paddles. After selection by S12 (*select 1* with *strobe 2*) and reset (S4), the game begins when either SERVE switch is depressed. It will start with a white ball moving toward the right side of the

screen. If intercepted by the black paddle, the ball changes color to black and rebounds toward the white side. The color-coded score records the targets removed by its color ball.

If *select 1* and *strobe 3* are shorted together by switch S14, then *Wipeout III* is selected. It is a two-player game—both right and left potentiometers and SERVE buttons are used. The game is played much like the previous *Wipeout* game, but the playing area is totally enclosed. After the game is started it will continue until all target squares are removed. The first player to press his SERVE button after reset has control of the ball until his opponent can intercept it, thus gaining control of it for himself.

The last *Wipeout* game, *Wipeout IV*, is chosen by S16's connecting the *select 1* pin to the *strobe 4* pin. It is also a two-player game. The game is played generally the same way as the others but with one major distinction—the screen is divided by a large vertical barrier. Thus the ball can only cross the field near the very top or bottom of the image and an added set of player strategies is gained. For example, once the ball is on a player's side, it may continually be bounced off the barrier to gain up to half the possible points. To win then, one need only pass the ball to the other side of the playing field. At least one more point will be scored in doing so, winning the game.

Color Squares games follow similar lines to the *Wipeout* set with one major exception—the screen is divided into four sections. Two quadrants are color coded as the white player's and two are color coded as the black player's. Target destruction may only occur by ramming one's own color square. The game ends when all targets of one color are removed. *Color Squares I*, selected by connecting *select 2* to *strobe 1* (S8), is a single-player game. *Color Squares*

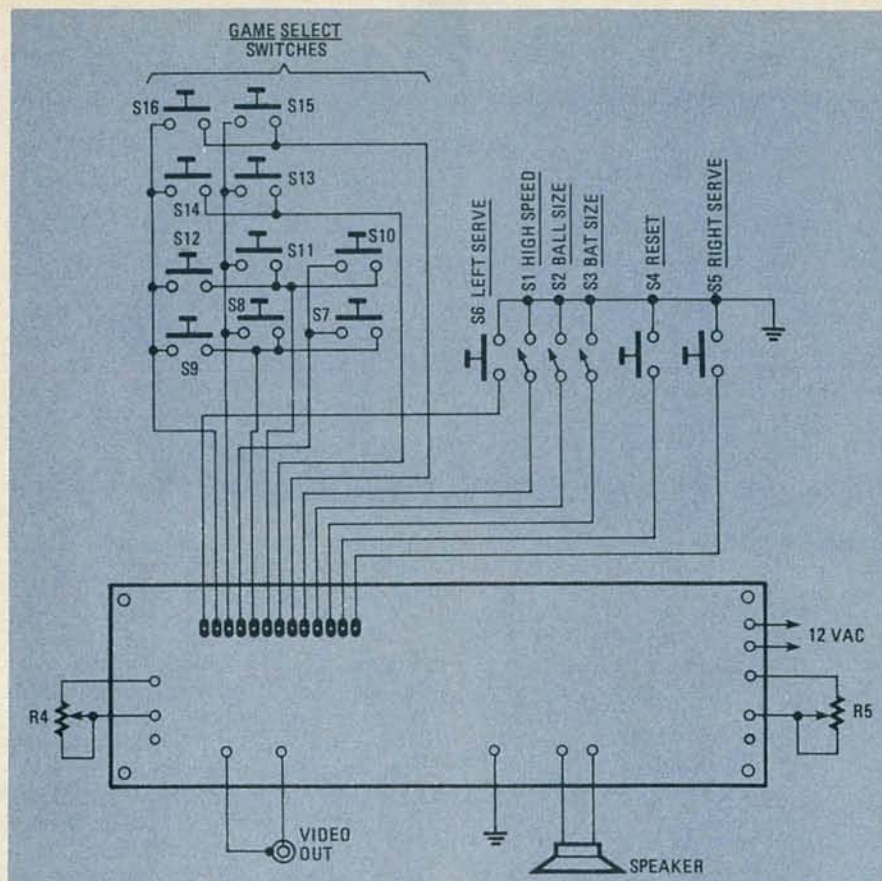


FIG. 3—CONNECTION of case-mounted components to main PC board.

II is similar, but is a two-player version (it uses S11 to connect *select 2* and *strobe 2*). *Color Squares III* (*select 2* and *strobe 3*—using S13) is played much like *Wipeout IV*. *Select 2* and *strobe 4* (S15) turn on *Color Squares IV*. That is a single-player game, with only one paddle; the field is enclosed on three sides.

The remaining two games are *Breakthrough I* and *Breakthrough II*. *Breakthrough I* (Fig. 1-b) is a single-player game selected by switch S7. The ball is served toward the wall opposite the player's paddle. When it hits the wall a block is knocked out. The object of the

game is to knock a hole through the wall and then to pass the ball through the hole. Each time the ball knocks a block from the wall it rebounds. The paddle is maneuvered to intercept the ball and redirect it into the wall. The wall is nine layers thick; only seven misses are permitted. The score, which should be kept as low as possible, records the number of blocks removed.

Breakthrough II (Fig. 1-c) is a two-player game with walls that are four layers thick. The game ends when a breakthrough occurs. Winning is a function of the number of hits. That

TABLE I		
Switch No.	Function	Pin No's.
S1	High speed	21, Gnd.
S2	Ball size	20, Gnd.
S3	Bat size	19, Gnd.
S4	Reset	18, Gnd.
S5	Right serve	17, Gnd.
S6	Left serve	12, Gnd.
S7	Breakthrough I	25, 26
S8	Color Squares I	25, 27
S9	Wipeout I	25, 28
S10	Breakthrough II	24, 26
S11	Color Squares II	24, 27
S12	Wipeout II	24, 28
S13	Color Squares III	23, 27
S14	Wipeout III	23, 28
S15	Color Squares IV	22, 27
S16	Wipeout IV	22, 28

game is turned on by the *select 3* pin and the *strobe 2* line (S10). No game selection occurs when *select 3* or *4* are shorted to *strobe 3*.

Some features are common to all the games. The targets are arranged in a 4×6 array. Each target is eight raster lines high and four dots wide. The score display is sixteen lines high and six dots wide. Each vertical line is two dots wide and each horizontal line is four raster-lines thick. The ball can be either of two sizes, five lines or nine lines high—switch S2—and the bat size and ball speed are selected by S3 and S1, respectively. The audio signals are the same for all the games.

Construction

This project is relatively simple for the beginner. But, even so, a minimum level of skill in construction is assumed. There are a number of sources (such as back issues of *Radio-Electronics*) where the beginner can find information on construction techniques.

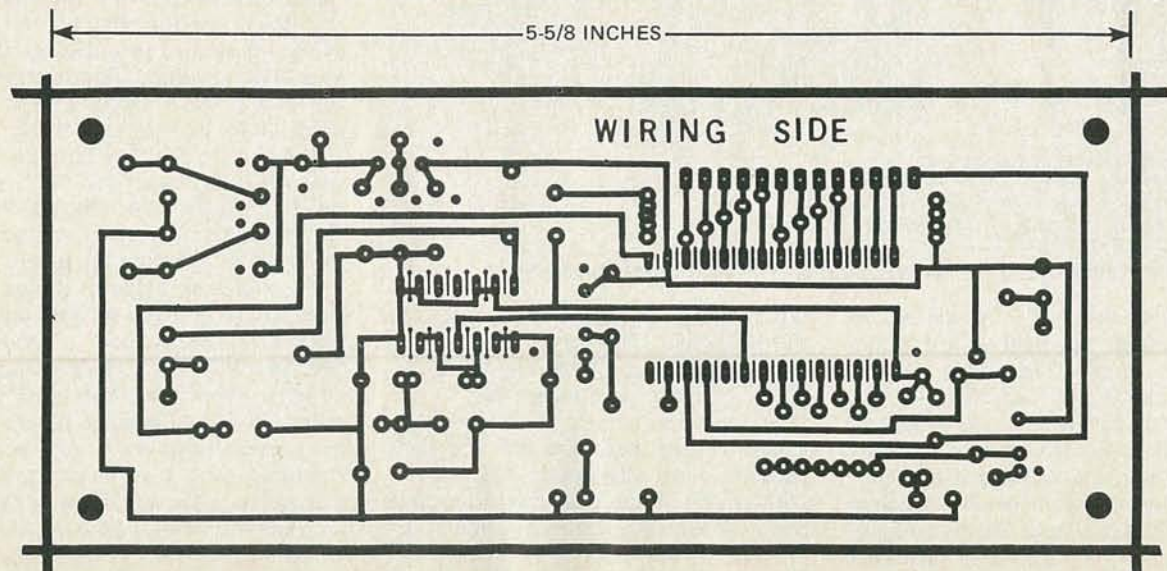


FIG. 4—PC BOARD foil pattern. Dots in corners indicate position of mounting holes.

PARTS LIST

All resistors 1/4 watt, 5% unless otherwise specified

Resistors

R1—150 ohms
 R2—12 megohms
 R3—220 ohms
 R4, R5—100,000 ohm pot, linear taper
 R6, R7, R13, R14, R18—10,000 ohms
 R8—1000 ohms
 R9—270 ohms
 R10, R11—1200 ohms
 R12—3400 ohms
 R15—1600 ohms
 R16—1800 ohms
 R17—470 ohms
 R19—2200 ohms
 R20—10 ohms
 R21-R24—100,000 ohms

Capacitors

C1—250 μ F, 25 volt electrolytic
 C2, C3—2.2 μ F, 25 volt tantalum
 C4, C5—0.33 μ F ceramic
 C6, C7—30 pF ceramic
 C8-C13—0.1 μ F ceramic

Semiconductors

D1-D4—1N4003
 D5—6.8-volt Zener diode
 Q1—2N3904
 Q3—2N3906

IC1—4001 CMOS quad, 2-input, NOR gate

IC2—AY-3-8606-1 (General Instruments) for U.S.-standard video (525-line) or AY-3-8606 for 625-line standard

XTAL1—3.579545-MHz crystal

S1-S3—SPST toggle switch

S4-S16—SPST normally-open (N.O.) pushbutton switch

T1—12-volt, 1-amp transformer

Miscellaneous: case, 8-ohm speaker, line cord, output jack, four spacers, wire, hardware.

The following may be obtained from Quest-Star Electronics Co., 5412 Burntwood Way, Las Vegas, NE 89108: Kit with all parts (no case or hardware), U.S. standard, G1300, \$55.00 or 625-line standard, G1301, \$57.00. PC board only, \$12.00. AY-3-8606 or AY-3-8606-1, \$14.50. For orders of 25 or more contact Quest-Star for prices. Please add \$2.25 for shipping—any excess will be refunded. Nevada residents add 3 1/2% tax. Shipment will be made from stock to six weeks.

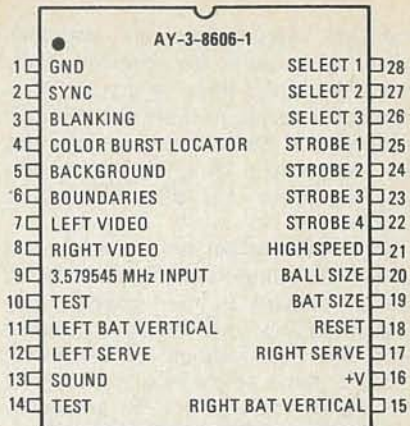


FIG. 6—FUNCTIONAL PINOUT of the AY-3-8606-1 IC. This can help you with the off-the-board wiring and, should it prove necessary, in troubleshooting.


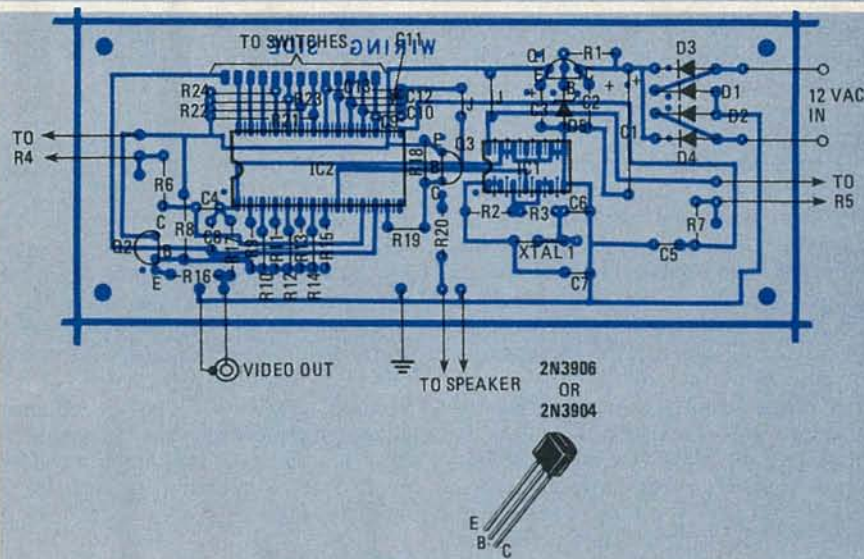


FIG. 5—PARTS PLACEMENT DIAGRAM. Take care to observe all polarities and make sure that jumpers are installed. Do not confuse the 2N3904 and 2N3906 transistors.

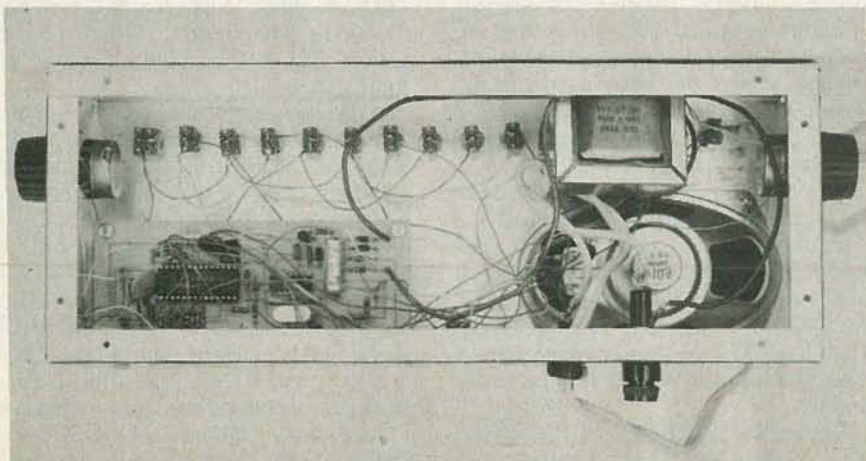

SUGGESTED LAYOUT for the PC board and external components within the case. The array of switches at the top is connected to a row of pads located just above the game IC.

The basic tools one will need are a fine-tip, low-wattage soldering iron (about 27 1/2 watts), a pair of fine-tip pointed-nose pliers, a pair of diagonal-tip wire cutters, and a set of wire strippers. Also, include a spool of rosin-core solder. The game, may be assembled using point-to-point wiring, wire-wrap, or printed-circuit techniques. The printed-circuit approach will be considered here. The other two methods can be undertaken using the parts list and the schematic diagrams shown in Figs. 2 and 3. Table 1 lists the functions of the front-panel mounted switches and their connections.

If the printed-circuit approach is chosen then one can etch his own card using the artwork pattern presented in Fig. 4, or a board layout may be made by referencing the schematic diagram. The simplest course is to buy a ready-made circuit board from the source given in the parts list, Quest-Star Electronics Co.

The first step is to obtain all of the components shown in the parts list; most of those are common items. The main LSI game IC may be a bit difficult to find, but it might be obtained from the same source as the PC board. Also, Quest-Star will provide a complete kit of all parts for those who do not have access to all of the components or who want to simplify their shopping. The complete kit includes all of the electronic components, the PC board, and the required hardware.

Having collected all of the parts, place all of the electronic components on a workbench, desk, or table. Make sure that all of the MOS and CMOS integrated circuits remain in their conductive packaging. Compare the components, now laid out, to the items specified in the parts list and if everything matches then proceed.

Take the enclosure and drill the holes required for the potentiometers, switches, transformer, PC board,

speaker, video-output jack, and line-cord. Next, paint the exterior of the case. After the paint is dry use dry-transfer lettering to label the controls. That should be followed by spraying the case with a clear lacquer to protect the finish. Let the case dry for 12-24 hours.

Mount the corner spacers on the foil side of the printed-circuit board. Install the IC sockets in their proper locations—making sure they are oriented properly; Fig. 5 should be consulted. Place a piece of cardboard on top of the sockets and invert the assembly, keeping an even pressure on both sides. Now solder the sockets into place. Return the assembly to the components-side up position.

Install all of the resistors and capacitors; verify their locations and solder. Next install the diodes, transistors, and voltage regulator. Again verify the orientation and placement of the parts before soldering. Lay the PC card aside until final assembly.

When the case is dry, mount the controls, transformer, line-card, output jack, speaker, and PC card. Wire those components as shown in Fig. 3. Before proceeding verify the wiring! Plug the line cord into an AC wall outlet. Check the voltages at the IC +V pins for the proper DC level—about 5 volts. If they are correct, unplug the cord and discharge the capacitors. Install the IC's in their sockets—observing the proper orientation. The assembly is now complete; if an RF modulator is to be used it may be also installed in the case.

Troubleshooting

This section, I hope, will never be needed but if problems should be encountered use the schematic diagram and the pinouts provided in Fig. 6 to aid in troubleshooting the game circuit. Start by following the checklist below:

1. Are all components in the proper location?
2. Are all components oriented correctly?
3. Is the PC card wired correctly to the external components?
4. Is the power-supply voltage correct?
5. Is a 3.58-MHz clock signal present at pin 9 of the game IC?
6. Is there an audio output?
7. Is there a composite video signal?

If the answer to any of these questions is "no," then investigate that portion of the circuit. For example, if no clock signal is observed, check the oscillator. Troubleshooting in that fashion should enable you to locate and remedy any problems rather quickly.

You should obtain a great deal of enjoyment from both the construction and use of this project. R-E

TROUBLESHOOTING VHS TRANSPORT CIRCUITS

FOREST BELT

THE VHS VIDEOTAPE TRANSPORT MECHANISM is a complex one, and so are the electronic circuits that control it. Let's take a look at how those control circuits work.

A prime key to the operation of the control circuitry lies among several switches. They open and close at what may seem irregular times during the tape-threading process. But the timing is quite specific, as you will see.

Actually, only two switches (see Fig. 1) work oddly. They operate as follows: While the machine is in the STOP mode—that is, before any button is depressed—the play-1 switch is open, and the play-2 switch is closed. When you first press down the PLAY button, the play-1 switch closes. The play-2 switch remains closed, for that initial movement of the PLAY button. However, by the time the PLAY button reaches the bottom of its travel and latches, the play-2 switch has opened.

Later, pressing the STOP button unlatches the PLAY button. As the play linkage leaves the latched-down play position, the linkage closes the play-2 switch . . . and shortly thereafter opens the play-1 switch.

The switches just described initiate the loading operation. To shut off the threading motor when loading has reached its limit, a loading-end switch closes and applies 12 volts to transistor Q612. The switch, having closed when loading is finished, remains closed until the motion of loading actually begins.

Unloading is initiated whenever the PLAY button unlatches, whether it is done manually or by the auto-shutoff solenoid. As you already know, this

action of the PLAY-button linkage closes the play-2 switch and opens the play-1 switch.

Then, when unloading is completed, the unload-end switch closes. That grounds the cathode side of diodes D617 and D618, which redirects voltages around so the motor quits running. The unload-end switch stays closed until such time as the PLAY button again starts a loading operation.

In one variation appearing in recent VHS models, the loading-end switch closes a path to ground instead of to a voltage supply. Of course, circuitry changes somewhat. For operation of the remainder of the section, however, that modification changes practically nothing.

Tape loading

To initiate tape loading, the operator depresses the PLAY button on the front of the machine. Switch play-1 (see Fig. 1) closes immediately. When the button is first pushed, switch play-2 remains closed.

A DC voltage goes through the play-1 switch to a voltage divider (R633-R634) at the base of Q611. That turns Q611 on. The voltage at the collector of Q611 goes low. In digital terms, logic high at the base of Q611 produces a logic low at the collector—a classic inverter action. The low voltage (logic) coupled to the base of Q610 through R632 places a logic high at the Q610 collector and a logic low at its emitter. Both are output points from that stage.

Low bias at the base of Q609 leaves Q609 cut off. A logic high could develop at the collector if there were some path for DC from a supply point. As



Many videotape deck service problems involve the load/unload section. This companion piece to one which appeared several months ago on the Beta mechanism will round out your knowledge and abilities.

you see, however, there is no supply resistor . . . only Q608.

The P collector of Q610 is supplied with 12 volts unregulated through R623 and R624. With no drop across R623, because Q610 is cut off, the base of Q607 stays high, same as the emitter. Lack of forward bias leaves this PNP transistor cut off. Q607 is, in effect, open.

Meanwhile, the play-2 switch has remained closed. (This is still during the first instant of depressing the PLAY button.) The unload-end switch, too, is closed, left that way when the tape last unloaded from the transport mechanism. These two switches create a path to ground for the positive voltage coming through R618. A ground at the cathode of D618 forward-biases D618

and then D619. The voltage at the junction of R618 and D619 stays near zero as long as both switches remain closed.

Hence, Q605 receives no forward bias (logic low) and stays cut off. The resulting low voltage at the emitter of Q605 is seen as a logic low by the base of Q606. So that transistor, too, remains cut off.

A DC supply path exists for the col-

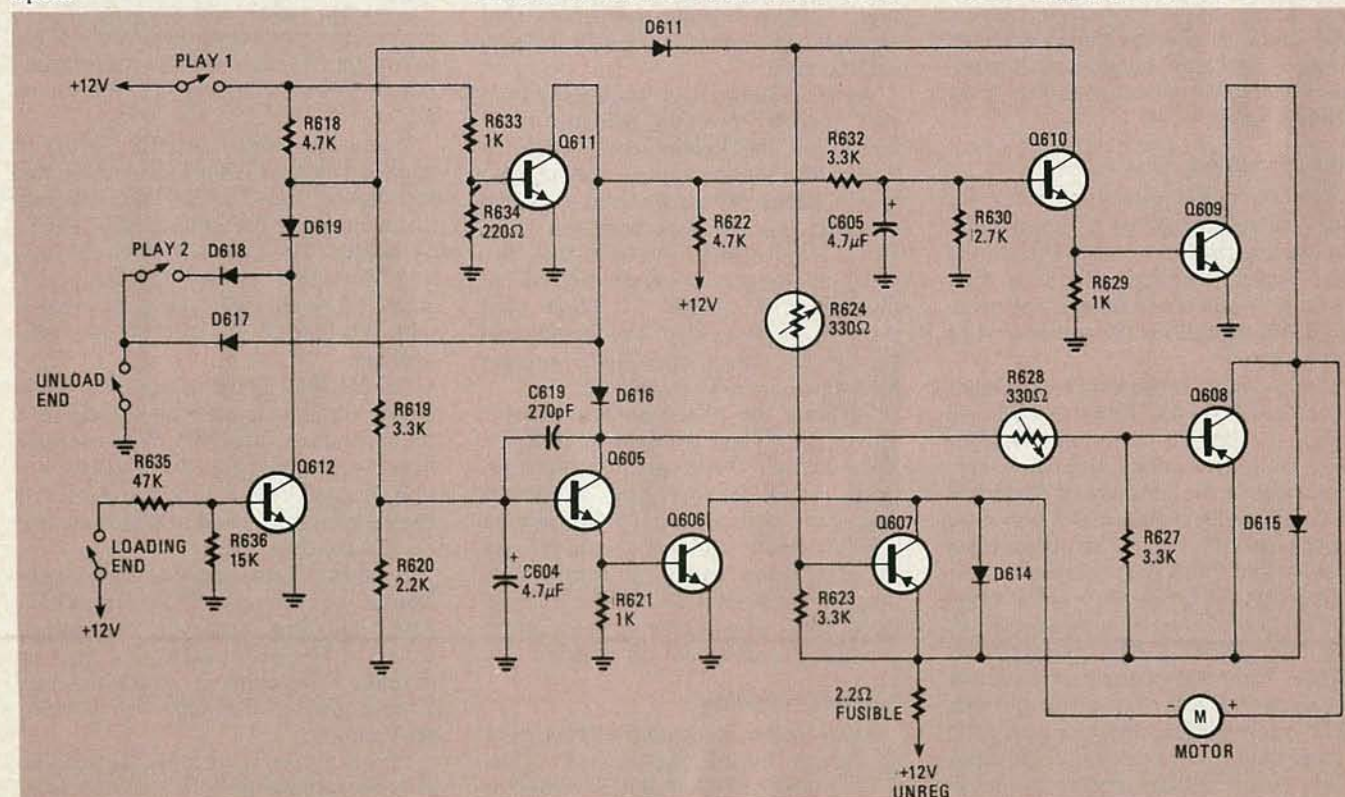


FIG. 1. SWITCHING DIODES AND TRANSISTORS turn threading motor on and off, and apply voltages in reverse for unloading. Limit switches turn the threading motor off at the end of the loading and unloading sequence.

lector of Q605. It starts at the fusible resistor and the 12-volt unregulated line. Resistors R627 and R628 complete the path. But with Q605 cut off, no current flows through those resistors, and no voltage drop occurs. The voltage at the base of Q608 stays at the same level as the emitter, and Q608 remains cut off, too.

All that has taken place in the instant the PLAY button was first pressed downward, closing the play-1 switch. Next, the PLAY button latches at the bottom of its travel. At that extreme, the play-button linkage opens the play-2 switch. Now things begin to happen.

A bias voltage for Q605 now develops across R620. Transistor Q605 turns on. Current flows in the R621-Q605-R628-R627 path from the 12 volts unregulated line. A positive voltage develops across R621, which turns on Q606. The normally-negative motor terminal goes to ground through a conducting Q606.

Current through R627 develops a bias that leaves the base of Q608 less positive than the emitter. That bias turns Q608 transistor on, which applies 12 volts DC to the normally-positive terminal of the loading motor. The motor begins turning, in its "forward" or normal direction. The mechanical loading process thus begins.

The unload-end switch opens as soon as the loading-drive mechanism turns the loading rings. But that has no immediate effect on anything electronic. The play-2 switch opened earlier, when the PLAY button latched. And D617 is reverse-biased anyway, because Q611 is conducting heavily and keeping its collector voltage practically at zero.

End of loading

The threading motor operates the tape-loading mechanism. Eventually, the loading-ring posts reach the limit of their travel, coming up against their V-stops. A protrusion on one ring pushes an arm that closes the end-of-loading leaf switch.

If the switch is the kind that applies 12 volts to R635 and R636, as is shown in Fig. 1, the bias turns on transistor Q612. A highly conductive Q612 acts as a short at the junction of D618 and D619. Diode D619 becomes highly conductive and the voltage at the junction of R618 and D619 goes to zero.

The bias on Q605 ceases and Q605 cuts off. Lack of current through R627 now lets Q608 cut off, removing DC voltage from the positive terminal of the motor. Lack of current through R621 cuts off Q606, which removes the ground path from the negative terminal of the motor. Either change stops the motor from turning.

Note that Q611 stays on. This, through Q610, keeps Q609 and Q607 cut off.

The unload cycle

To initiate unloading in VHS machines, the operator need only press the STOP button. That has no direct electronic effect. It merely unlatches the PLAY button and allows it to return to its up position.

The play-1 switch opens and the play-2 switch closes. The play-2 switch has no effect, because the unload-end switch has remained open ever since loading began.

The play-1 switch, upon opening, removes voltage from R618 and R633. The bias for Q611 disappears. Transistor Q611, which has been on all this time, turns off and triggers a whole chain of electronic events.

The voltage at the collector of Q611 rises to the supply value. The positive voltage (logic high) goes through R632 to the base of Q610, turning Q610 on. Current through R629 places a positive bias on Q609, and that transistor becomes highly conductive. Transistor Q609 thus effectively grounds the normally-positive terminal of the loading motor.

Turning on Q610 brings its collector voltage low. Current flows in supply resistors R624 and R623. The voltage drop across R623 makes the base of Q607 less positive than the emitter. Transistor Q607 turns on, applying the positive 12 volts DC at its emitter to the normally-negative terminal of the motor.

The loading motor, with voltages applied in opposite polarity to "normal," begins turning backward. That starts the threading mechanism unloading the tape.

As the loading rings rotate away from the "loaded" position, pressure is released on the loading-end switch. It opens. But that has no immediate electronic effect. When the play-1 switch opened, voltage was removed from R618. Diode D619 was from that moment no longer forward-biased, so there was no longer a voltage path through Q612 anyway. The loading-end switch just rests open until another loading cycle calls it into use.

Opening the play-1 switch also removes the voltage from the R618-R619-R620 divider. With no positive bias, Q605 cannot conduct. Lack of current leaves no voltage across R621, and no bias for Q606, which stays cut off. By the same token, there's no current flow through R628 and R627; the base of Q608 stays as positive as the emitter and Q608 remains cut off or open.

End of unloading

Some other electronic effects have developed during the unload cycle. Transistor Q611 is off, and its collector voltage increases in the positive direction. That places a positive voltage on the anode of D617. However, it does

not constitute forward bias, because there is no ground return. So far, the unload-end switch is open.

But when the threading mechanism reaches its limit, one loading ring moves an arm that closes the unload-end leaf switch. Now D617 can conduct. And it pulls the voltage at the collector of Q611 to zero.

With bias gone, Q610 turns off, and so does Q609. That removes the ground from the positive motor terminal. Current stops flowing through R624 and R623, leaving Q607 without forward bias either. Transistor Q607 no longer applies a positive voltage to the other motor terminal. The motor stops. Tape has been unloaded. The unload-end switch remains closed until the next load cycle begins.

Safety during threading

Several conditions that trigger automatic-stop have the same effect if they occur during threading. Moisture on the dew detector or a stopped video-head wheel or capstan will prevent loading. The auto-stop mechanism unlatches the PLAY button, letting it return to its up position. That triggers the unload mode and unloading proceeds in the manner just described.

Other safety factors are built into the electronic circuits of the threading/unthreading section. A time-delay sensor, for example, halts loading efforts if anything impedes loading for more than 4 or 5 seconds. Two seconds should be sufficient for normal loading.

You can follow the working of that *misloading* protection arrangement by following Fig. 2, which contains additional control circuitry not shown in Fig. 1.

When the play-1 switch closes, it applies voltage to R638. However, the still-closed play-2 switch grounds out that voltage at the other end of R638, by holding D618 and D620 in conduction. But when the play-2 switch opens (as the PLAY button latches), the ground path through D620 and D618 then disappears.

Diode D621 then conducts. So would D626, which activates auto-stop, were it not for capacitor C606. When voltage first reaches the D621-D626-C606 junction, it goes very low as the capacitor begins charging. Diode D626 therefore cannot conduct.

It takes several seconds for C606 to charge up through R638 and R639. After that time, however, the voltage across C606-R639 increases enough to make D626 conduct. And that sends a logic high to the auto-stop system, activating it.

The purpose is to stop the loading in case something jams the threading mechanism. When loading proceeds as it should, the loading-end switch closes well before C606 reaches any-

ground path through D619, D618, and the unload-end switch keeps the voltage at the base of Q605 low. Anything that ultimately keeps Q606 from conducting can prevent the motor turning. Transistor Q606 acts as an open circuit instead of as a ground connection.

Check the DC voltage at the normally-positive motor terminal. Assuming Q605 conducts as it should, check the bias on Q608, across R627.

If you find that Q608 operates normally, but the voltage at the plus side of the motor is low, check whether a leaky Q609 might be dragging the voltage down at the collector of Q608. Or, Q609 might be turned on. Trace back to find out why, because Q609 should be off during loading. Transistor Q610

should also be cut off. The appearance of bias at the base of Q610 could indicate that D617 or the unload-end switch is open. A defective Q611 would not leave the bias voltage on Q610 high, because a properly functioning D617 and the unload-end switch (still closed, until loading motion actually begins) holds down the voltage coming through R622.

Another possible fault lies in the loading-end stage. Should Q612 short, the D618-D619-D620 junction stays at zero. Diode D619 prevents any voltage from reaching Q605, so Q606 and Q608 remains cut off. Loading therefore cannot occur. (An open or non-operative Q612 leaves the loading motor on. You may hear a squeaking as

the motor pulley rubs the unmoving drive belt.)

Will not unload. The stages involving Q605, Q606 and Q608 must be okay, since the tape loaded. However, an open Q609, Q610 or Q607 might disable the unloading sequence.

Again, start at the motor with your voltmeter. A missing positive voltage at the normally-negative side of the motor indicates that Q607 is not conducting a positive voltage from its emitter to its collector.

A positive voltage at the normally-positive terminal is wrong when the machine is trying to unload. That symptom suggests that Q609 is open or not conducting. A positive voltage at both terminals confirms that Q610 and Q607 are working and that the motor and plug show continuity. Transistor Q607 would stay off if Q610 were open or cut off.

If there is no positive voltage at either side of the motor, you should suspect that Q610 is defective. However, a shorted Q611 or a stuck (closed) unload-end switch could prevent unloading, even though the loading has proceeded normally.

Intermittents. Erratic loading or unloading can give you fits. Once you discover which function fails, the hints already given tell you in which stages the fault might be.

Intermittents tend to fall into two categories. One is a cold-soldered connection between some part and the circuit board. An insulated poking-probe can help you find these. Or, if all else fails, take a hot soldering iron to each connection in the stages likely affected.

The other most common intermittents turn out to be in the connecting plugs. The quickest cure, ordinarily, lies in just unplugging and replugging each connector tightly. But inspect the female side of the plug. A damaged wiper can spoil the connection at one pin; that is not uncommon if someone else has been "into" the machine before you. For your own part, be exceedingly careful when plugging a connector back into the pins of the circuit board. One bent wiper and you're the culprit. That damage can be hard to trace, and the cure just might be a new plug.

Loads, then unloads. This symptom corresponds with automatic shutoff. The PLAY button pops up and the machine unloads. If the tape fails to unthread, you have an unloading problem, too.

Should anything interfere with completion of the loading motion, the loading-end switch does not turn on Q612. After the time-delay interval, shutoff takes over automatically. Hunt for that trouble in the loading sequence, or in any of the sensor stages. **R-E**

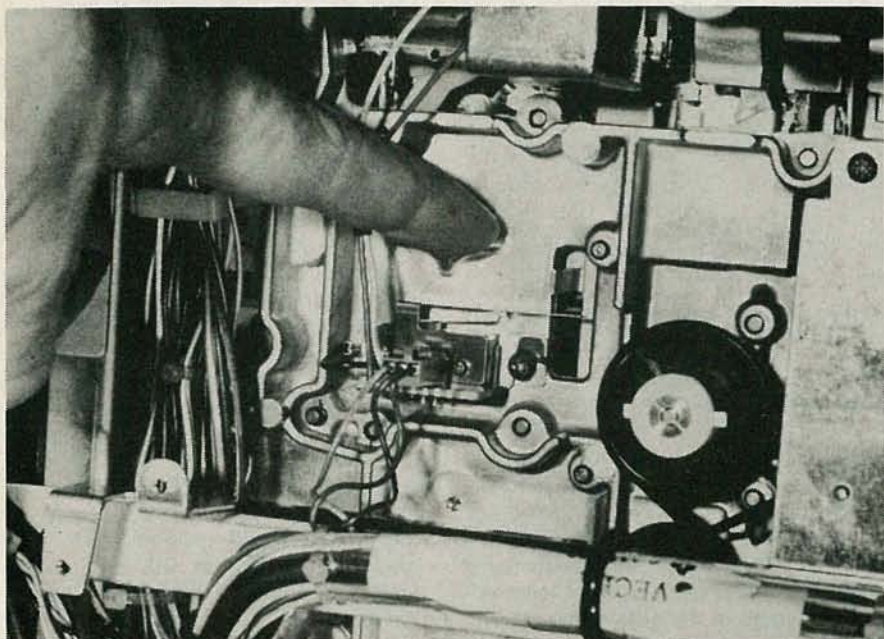


FIG. 4—THE PLAY-1 MICROSWITCH closes when the PLAY button is depressed.


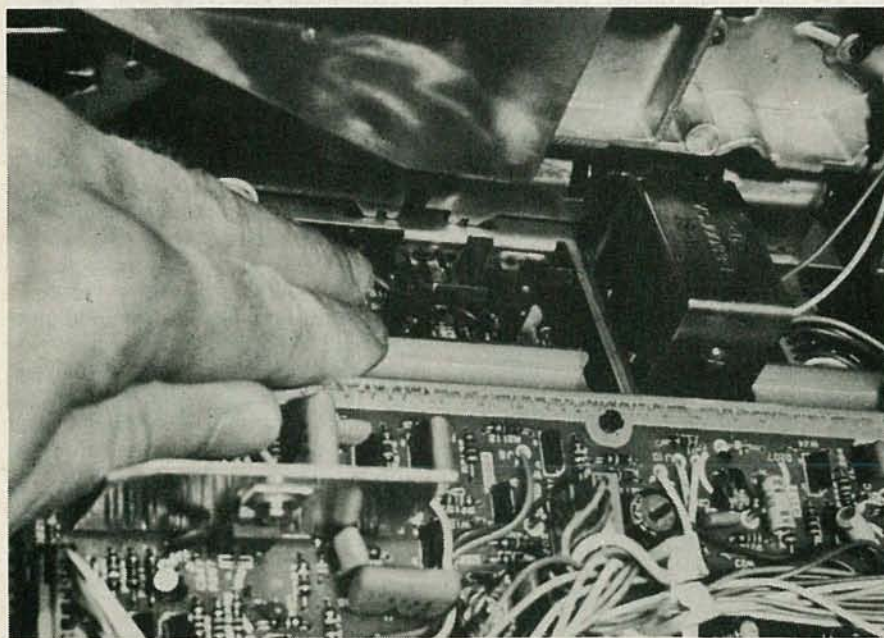


FIG. 5—THE PLAY-2 MICROSWITCH, pushed by a mechanical slide link, opens when the PLAY button latches.

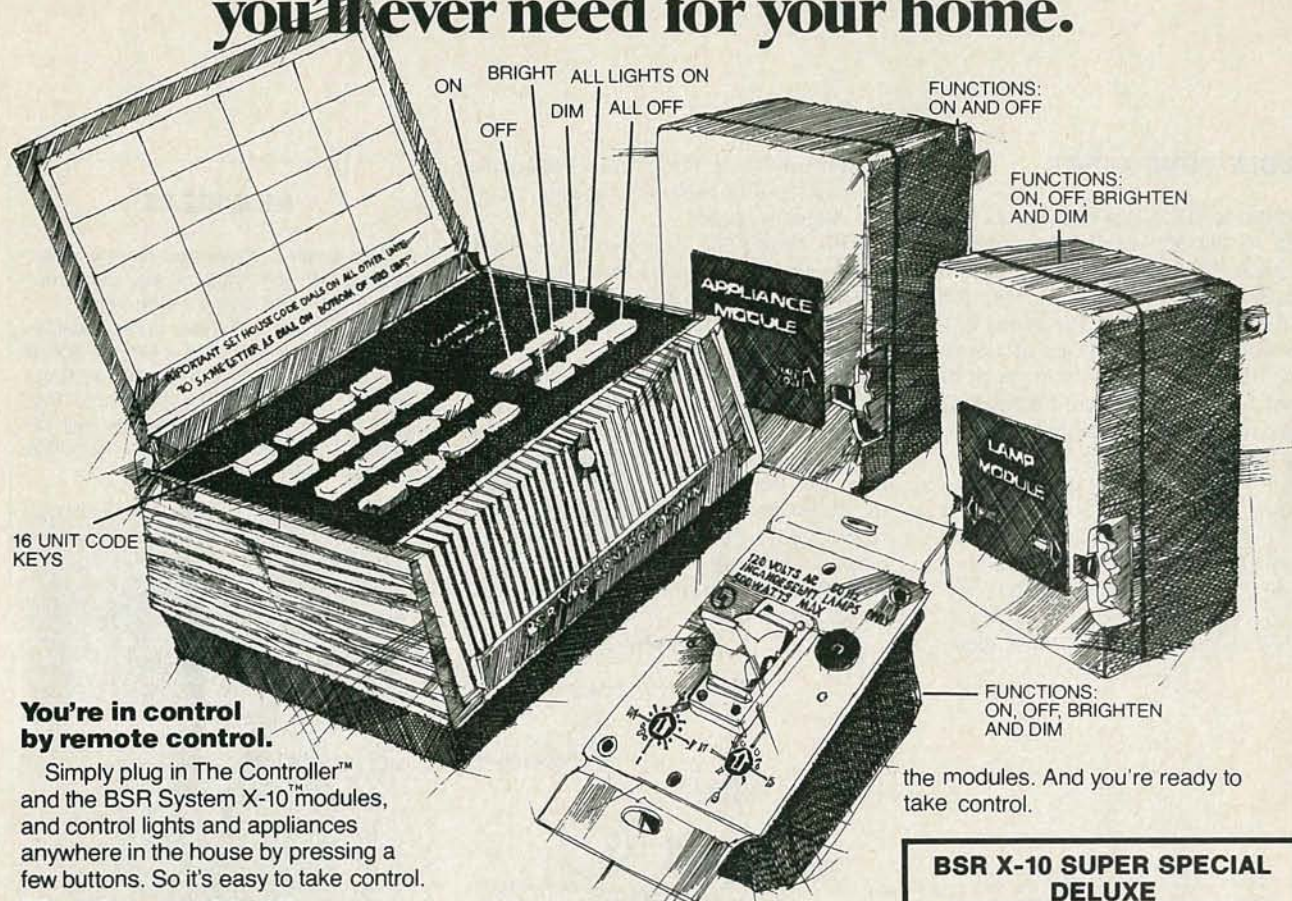An in-depth look at the only "plug-in" remote control system you'll ever need for your home.



You're in control by remote control.

Simply plug in The Controller™ and the BSR System X-10 modules, and control lights and appliances anywhere in the house by pressing a few buttons. So it's easy to take control.

There's no end to all of the control you've got.

You can turn on the TV, radio or stereo in the morning to help you wake up without getting up from bed. Or at night, turn on the lights before going downstairs so you don't have to fumble in the dark. Turn off unnecessary lights and help get your electric bill under control. Or, dim the lights and save energy, too.

And when it's time to turn in, just push a button and turn everything off. And sleep soundly. But, if you hear a strange noise in the middle of the night, you can press a button to turn on all the lights and scare the daylights out of an intruder.

The Controller is designed to control every room in the house.

By pressing the buttons on the Command Console keyboard, command signals are transmitted over

existing household wiring to the module of your choice. The Lamp Module turns on, off or dims any incandescent lamp up to 300 watts. The Appliance Module turns appliances like TVs, window fans or stereos on and off. And the Wall Switch Module is designed to turn on, off or dim any light or lamp up to 500 watts normally operated by a wall switch.

There's even a Cordless Controller that transmits signals to an Ultrasonic Command Console from up to 30 feet away. So there's plenty of control for everyone.

Simplicity is built into the system.



No special wiring is needed. Simply plug The Controller Command Console into any wall outlet in any room of the house.

Then plug your lamps and appliances into the appropriate modules. Plug in

the modules. And you're ready to take control.

BSR X-10 SUPER SPECIAL DELUXE ULTRASONIC CONSOLE

REGULARLY \$49.95
NOW \$29.95

With the purchase of three or more modules

Modules normally \$17.00 ea.

Modules of your choice

3 for \$47.95 6 for \$83.95

Ultrasonic Hand Unit

Normally \$24.95 Now \$18.95

Please add \$3.00 for shipping

TOLL FREE HOT LINE

800-223-0474

THE TIMER™ Automatically Programs Lights, Appliances. Just plug in The Timer and the BSR X-10 modules and you can program up to 8 lights and appliances to go On and Off up to twice a day. UL listed. \$74.95 if purchased separately. If purchased with 3 or more modules \$59.95

NEW



ADVANCE ELECTRONICS

4 West 45 Street, New York, N.Y. 10036 212-687-2224

new ideas

TROUBLE TONE ALERT

I DESIGNED THIS SYSTEM FIVE YEARS AGO for use in my service business, and it works great. I use it to look for intermittent problems on my bench. For example, if I had a color TV whose horizontal output current would go way up at unpredictable times, and I didn't want to sit by and wait for this to happen, I'd hook up the tone alert and let it tell me when the current increase took place.

The Trouble Tone Alert is intended for use with analog meters—just wire a "mini" earphone jack directly across the meter movement, plug it in, and you're all set. The high impedance of the alert keeps it from affecting the accuracy of the meter reading, because most meter

movements are on the order of 1800 ohms and the input impedance of the alert is in the megohm range.

This device is as versatile as your meter, since all it reacts to is the meter-movement driving voltage. It will respond to a change in AC or DC voltage, current, or in resistance.

You tell the Trouble Tone Alert whether to look for an increase or decrease by means of the DPDT switch and adjust the threshold control until the tone from the Sonalert just disappears (with the meter in the circuit being tested, of course). After that you can go about your business and wait for the alert to signal you when your intermittent problem has finally shown up.

John J. Augustine


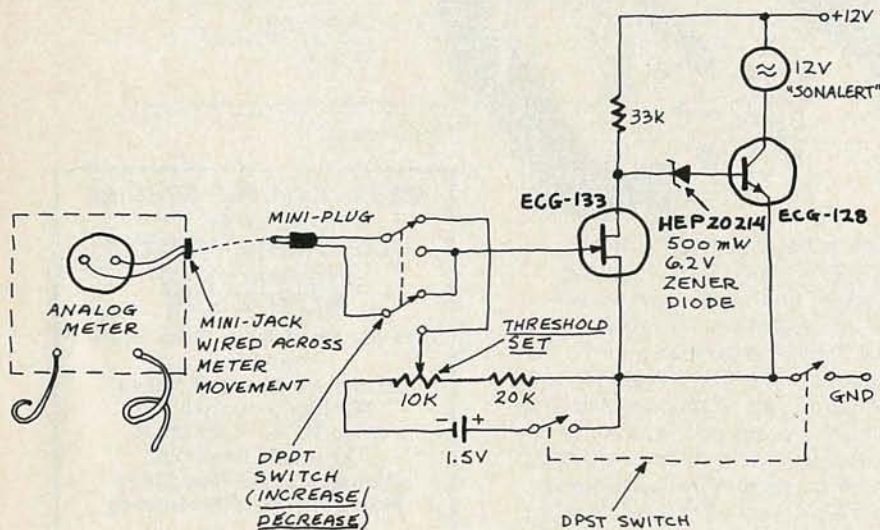



FIG. 1

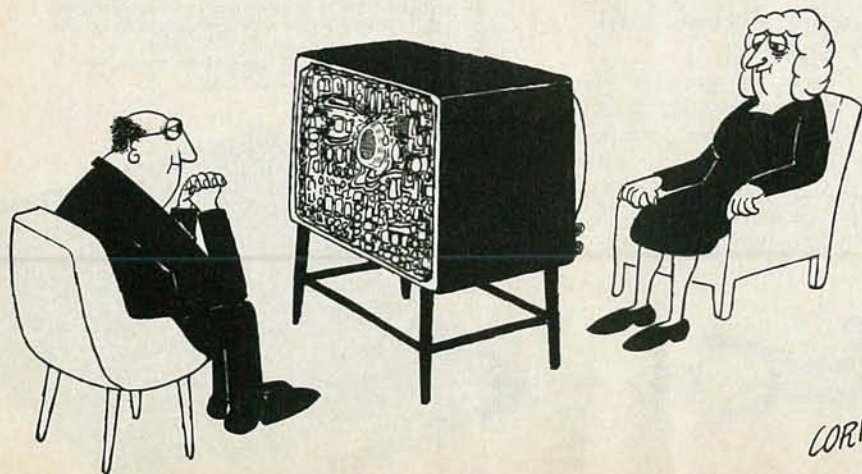

NEW IDEAS

This column is devoted to new ideas, circuits, device applications, construction techniques, helpful hints, etc.

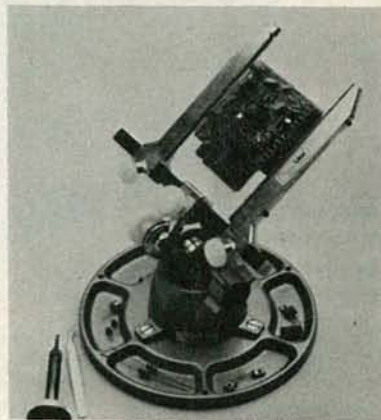All published entries, upon publication, will earn \$25 plus a Circuit Board Holder, Standard Base and Tray Base Mount from Panavise Products, Inc. (See photo below.) Selections will be made at the sole discretion of the editorial staff of **Radio-Electronics**.



I agree to the above terms, and grant **Radio-Electronics** Magazine the right to publish my idea and to subsequently republish my idea in collections or compilations of reprints of similar articles. I declare that the attached idea is my own original material and that its publication does not violate any other copyright. I also declare that this material had not been previously published.

Title of Idea

Signature

Print Name

Date

Street

City

State

ZIP

Mail your idea along with this coupon to:

**New Ideas
Radio-Electronics
200 Park Ave. South
New York, NY 10003**

ADVANCE IS PROUD TO INTRODUCE
The  HITACHI Line of High Quality Oscilloscopes
All Hitachi Instruments
Are Backed by A Two-Year Warranty



Hitachi Oscilloscope V-302
DC-30MHz dual-trace

- | | |
|-------------------------------------|--|
| 1. TV sync-separator circuit | 5. Sweep-time magnifier (10 times) |
| 2. High-sensitivity 1mV/div (5MHz). | 6. Trace rotation |
| 3. Signal delay line | 7. Z-axis input (Intensity modulation) |
| 4. X-Y operation | |

(Also available in single-trace)


- TV sync-separator circuit facilitates rapid video signal measurement.
- Extra-high sensitivity; vertical sensitivity of 1mV/div. now available.
- Built-in signal delay line for leading edge observation of quick-rising waveforms (V-301 and V-302).
- X-Y operation very convenient for measuring phase difference of two waveforms.
- Sweep-time magnifier effective for precise measurement; sweep time magnifying 10 times with one-touch operation.
- Trace rotation system for easily adjusting bright-line inclination caused by terrestrial magnetism.
- Z-axis input provided-possible to use as CRT display.
- 0.2 μ s~0.2s-wide sweep range setting.
- One-touch shifting waveform slopes.
- Five modes of vertical deflection operation (Type V-152 and V-302).
- Panel layout with color-coding of respective functions.

HITACHI V-302 & V-152

Put a proven Hitachi dual-trace oscilloscope on your bench for as little as \$695. Our V-152 15MHz model includes unprecedented sensitivity (1 mV/div)...10X sweep magnification...front panel XY operation...trace rotation...Z-axis input...and more. Need greater bandwidth? Our V-302 model is the only 30MHz dual-trace scope with signal delay line priced under \$1000, with all the above features, to make your testing operations fast, easy, and accurate. Reliability is exceptional too. (As you'd expect from a manufacturer with over 20 years of experience "outscoping" the competition.) So exceptional, in fact, that Hitachi quality is backed by a 2-year warranty...the longest in the industry. Whether you use it for teaching or repairs, for video, audio, or computer testing, you can't find more scope for your dollar than at Hitachi. Call for more details.

- | | | |
|--|--------------|--|
| | Normal Price | Call For
Special Introductory
Price Offer |
| <input type="checkbox"/> V-152 15 MHz Dual Trace | \$695* | |
| <input type="checkbox"/> V-302 30 MHz Dual Trace | \$945* | |
- * Probes included.

Hitachi...The measure of quality.

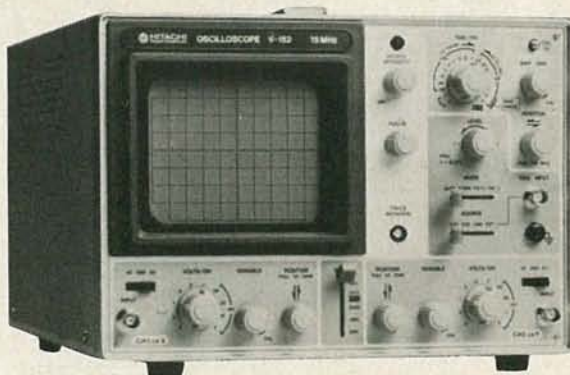

Hitachi Oscilloscope V-152
DC-15MHz dual-trace

- | | |
|------------------------------------|--|
| 1. TV sync-separator circuit | 4. Sweep-time magnifier (10 times) |
| 2. High-sensitivity 1mV/div (5MHz) | 5. Trace rotation |
| 3. X-Y operation | 6. Z-axis input (Intensity modulation) |

(Also available in single-trace)



THE TEST EQUIPMENT SPECIALISTS
TOLL FREE HOT LINE
800-223-0474



ADVANCE ELECTRONICS

54 WEST 45th STREET, NEW YORK, N.Y. 10036 212-687-2224

hobby corner

One-arm bandit circuit plus a new packaging system for your projects.

EARL "DOC" SAVAGE, K4SDS, HOBBY EDITOR

HENRY COOPER OF STERLING HEIGHTS, Michigan, has come up with an interesting circuit for a one-armed bandit. There are a number of such circuits around but his is much simpler than most.

Figure 1 is a "cherries/lemons/oranges" circuit based on the one Henry sent in. When I built his, I managed to eliminate a few more components. The present count seems to be about the minimum number of pieces that will do the job.

each case, the D, E and F segments are on, so he wires them to stay on and doesn't have to worry about controlling them. That leaves only A, B and C segments to control—actually, only two since B and C must go on and off together. The G segment (the center horizontal one) is not used in any of those three displays.

The B and C segments are driven directly by the 7490's. Driving the A segment directly would have it on when it should be off and vice-versa. That is the

want the players to be able to see the readout *before* releasing S1!

A little experience with the bandit may cause you to want to change the odds. That can be done by changing the 7490 output pins used to drive the segments and/or the next 7490. Output pins are 12 (1), 9 (2), 8 (4), and 11 (8). Experiment with various combinations. You don't have to drive the A segment and the next 7490 from the same pin, either.

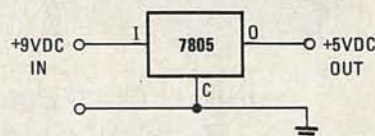


FIG. 2

This little bandit works very well. Build it in a small case such as the *Unibox* mentioned below and it will provide many hours of entertainment. To get it into the smallest possible box and have the greatest convenience, use a small wall-plug-type AC adapter. If you build in the 5-volt regulator shown in Fig. 2, you can use a common 9-volt adapter. Of course, you could also use a 9-volt battery but it won't last long because of the heavy current drain of the readouts.

Thanks, Henry, for sharing your circuit with us.

Packaging your project

As soon as you think you have found an ultimate product—one which cannot be improved—someone comes along and does just that! This time it is small cases/cabinets for electronics projects. Amerex (P. O. Box 2815, Riverside, CA 92516) is the outfit that has made the improvement with their *Unibox* (Figs. 3 and 4).

One would expect the choice of colors and sizes (in this case up to 2 × 4 × 5½ inches) in those tough plastic enclosures. Several other *Unibox* features, however, are not expected.

First, there are epoxy-glass gridboards that mount vertically and/or horizontally inside. Those gridboards are perforated in the standard 0.1-inch hole pattern for easy mounting and wiring of IC's, sockets and other components.

Next, there are red or gray windows for use with LED and other readouts. Then, there are opaque panels that can be used for connectors, switches and so on. The final touch is provided by non-mar-

continued on page 82

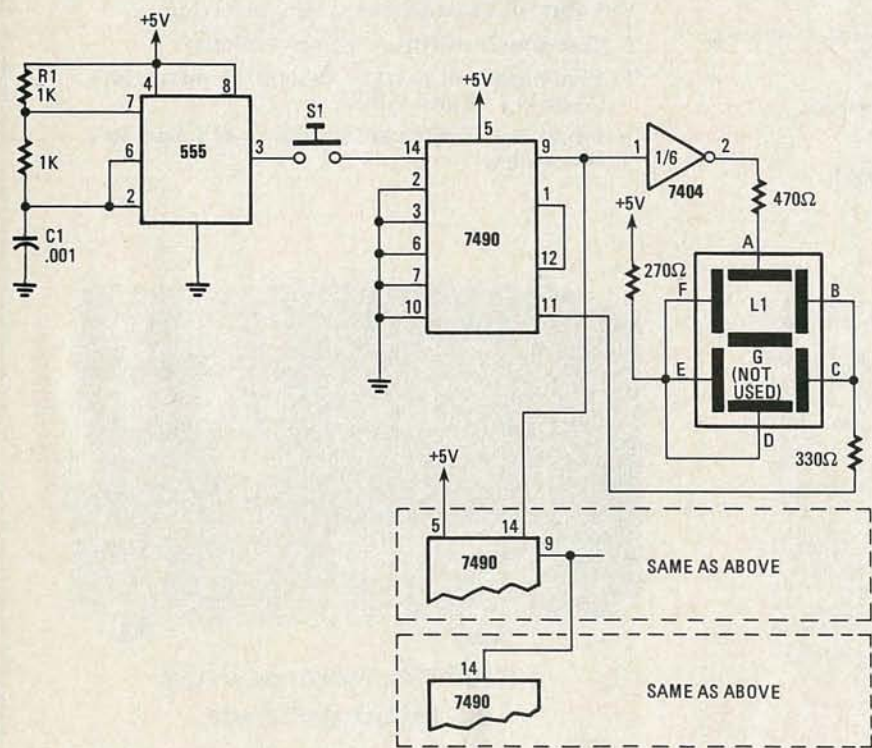


FIG. 1

The readouts are 7-segment common-cathode LED's. Since the circuit wiring is somewhat unorthodox, the LED's are shown in an "exploded" view to prevent confusion.

The 555 serves as a standard astable (free-running) multivibrator that we have discussed before. It drives 7490 counters—one for each "window" LED. That is where the present circuit departs from the usual.

Henry's LED's read "C" for cherry, "L" for lemon and "O" for orange. In

purpose of the inverter (one-sixth of a 7404)—to reverse the on/off action of the A segment.

When building the bandit, you may wish to examine the readout action more closely. As given, you won't be able to see what is happening while S1 is pressed because the 555 is running at a rate of about 500 kHz.

Increasing the value of R1 and/or C1 will slow it down. Don't forget to put it back to high speed when it is operating to your satisfaction. After all, you don't

Innovations

The sharpest picture ever achieved in big-screen projection TV


The new Heathkit Screen Star sets a new standard in picture quality for big-screen projection TV. The finest F1.0 lenses you can buy produce one of the clearest, brightest pictures ever.

Imagine watching all your favorite TV movies and sports events on a big 6-foot diagonal screen. Heathkit's three-tube projection gives you brighter, more vivid color. And it's a lot easier to build than conventional TV's.

A complete computer system in one compact unit

The Heathkit All-In-One Computer takes the guesswork out of selecting a balanced computer system. It includes built-in floppy storage, smart terminal, heavy-duty keyboard, 12-key numeric pad, Z80 CPU, and 16K RAM expandable to 48K—all in one compact unit.

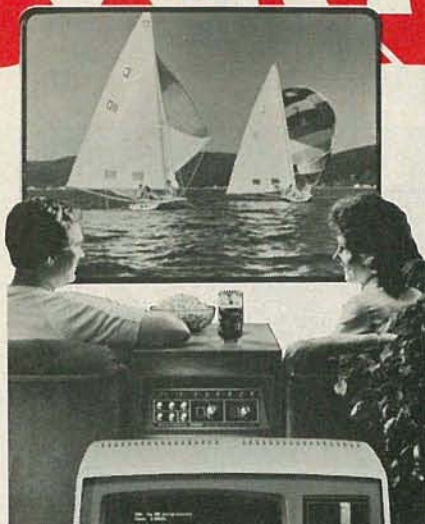Two Z80 microprocessors mean terminal and computer never share power. So both can operate faster on more complex programs. And there's no better way to learn about computers than to build one yourself.



The only computerized home weather station for instant, up-to-the-minute weather reports

Just push a button for reliable weather information anytime you need it with the unique Heathkit Weather Station.

It gives you digital readouts of F or C temperatures, wind speed in miles or kilometers per hour or in knots, wind direction, barometric pressure, date and time of day, even the wind chill factor.

This microprocessor-based weather computer has memory to store data and precision infra-red sensing devices built into the outdoor transmitter. And it's very easy to build.

The finest stereo receiver ever introduced by one of the leaders in audio technology

It's loaded with luxury features that let you adjust your music to your preference.

Special features include a Precision Tuning System (PTS) that automatically corrects mistuning. 5-section FM tuning capacitor gives you maximum rejection of unwanted signals for lower noise, cleaner sound. Digital frequency readout, center tune meter, and flywheel loaded tuning are just a few of the luxury touches. Complete specifications are in the latest Heathkit Catalog.

FREE CATALOG

See all the newest innovations in build-it-yourself kits in the latest free Heathkit Catalog. It contains nearly 400 exciting kits for your home, work or pleasure. Send today.



Send to: Heath Company, Dept. 020-692,
Benton Harbor, MI 49022

Yes, please send me a Heathkit Catalog.
I am not currently receiving your catalogs.

Name _____

Address _____

City _____ State _____

CL-725A Zip _____


Heathkit®

If coupon is missing, write Heath Co.,
Dept. 020-692,
Benton Harbor, MI 49022

Heathkit Products are also sold and serviced at Heathkit Electronic Centers (units of Veritechnology Electronics Corporation) in major cities throughout the U.S. See your white pages.

fact:
five new Shure Cartridges
feature the technological
breakthroughs of the
V15 Type IV

Plus
Unprecedented
stylus protection

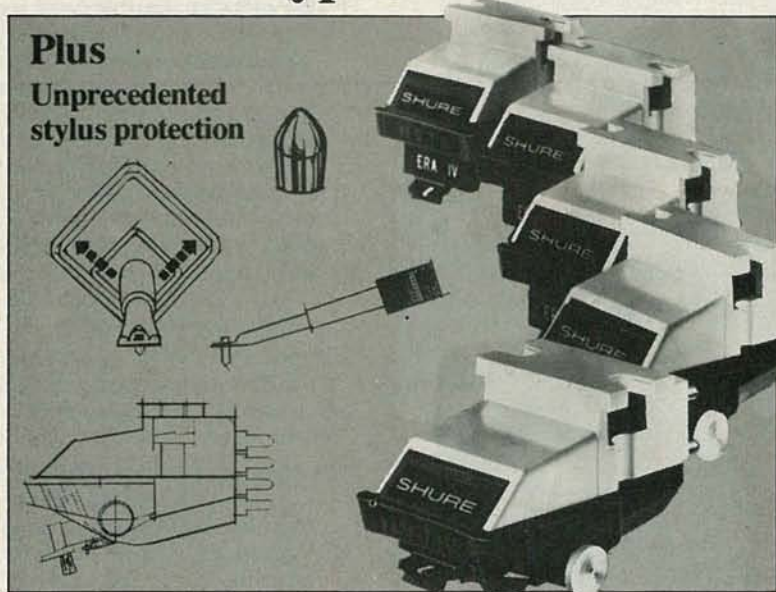

the M97 Era IV Series phono cartridges

Shure has written a new chapter in the history of affordable hi-fi by making the space-age technological breakthroughs of the incomparable V15 Type IV available in a complete line of high-performance, moderately-priced cartridges: the M97 Era IV Series Phono Cartridges, available with five different interchangeable stylus configurations to fit every system and every budget.

The critically acclaimed V15 Type IV is the cartridge that astonished audiophiles with such vanguard features as the Dynamic Stabilizer—which simultaneously overcomes record-warp caused problems, provides electrostatic neutralization of the record surface, and effectively removes dust and lint from the record—and, the unique telescoped stylus assembly which results in lower effective stylus mass and dramatically improved trackability.

Each of these features... and more... has been incorporated in the five cartridges in the M97 Series—there is even an M97 cartridge that offers the low distortion Hyperelliptical stylus! What's more, every M97 cartridge features a unique lateral deflection assembly, called the SIDE-GUARD, which responds to side thrusts on the stylus by withdrawing the entire stylus shank and tip safely into the stylus housing before it can bend.

NEW! M97 Series Era IV Phono Cartridges... Five new invitations to the new era in hi-fi.

Model	Stylus Configuration	Tip Tracking Force	Applications
M97HE	Nude Hyperelliptical	3/4 to 1 1/2 grams	Highest fidelity where light tracking forces are essential.
M97ED	Nude Biradial (Elliptical)	3/4 to 1 1/2 grams	
M97GD	Nude Spherical	3/4 to 1 1/2 grams	
M97EJ	Biradial (Elliptical)	1 1/2 to 3 grams	Where slightly heavier tracking forces are required.
M97B	Spherical	1 1/2 to 3 grams	
78 rpm Stylus for all M97's	Biradial (Elliptical)	1 1/2 to 3 grams	For 78 rpm records.



Shure Brothers Inc., 222 Hartrey Ave., Evanston, IL 60204

In Canada: A. C. Simmonds & Sons Limited

Outside the U.S. or Canada write to

Shure Brothers Inc., Attn: Dept. J6 for information on your local Shure distributor.

Manufacturers of high fidelity components, microphones, sound systems and related circuitry.

CIRCLE 60 ON FREE INFORMATION CARD

HOBBY CORNER

continued from page 78

ring feet which can be added.

Altogether, the Amerex *Unibox* is the neatest and most convenient packaging



FIG. 3

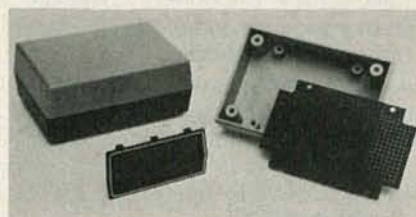


FIG. 4

system I have found for small projects. Prices are quite reasonable, also. If you can't find *Uniboxes* locally, write to Amerex.

The cell connection

Zvi Rozensher of Briarwood, NY has inquired about methods of connecting parallel alkaline cells. As you know, if one is weaker than the others, they will discharge through that weaker one.

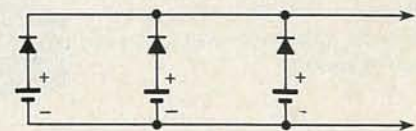


FIG. 5

Of course, the usual way to prevent the discharging is to use diodes as in Fig. 5. However, there is a voltage drop across the diodes. Zvi would like to know if any readers have found another way to connect the cells and avoid that voltage loss.

Circuit handbook

If you do any building at all, you reach a point from time to time when you need a little circuit for some special use. I have accumulated a fair library to search through, when that happens to me. Lately, however, there is one book which I turn to first.

Usually, I find what I need in the new *Archer Engineer's Notebook* (Radio Shack #276-5001 at \$1.99). The 128 pages of that Notebook contain much helpful information and literally hundreds of circuits.


Included are circuits that stand alone, and others that are building blocks for larger projects. A wide variety of TTL, CMOS, and linear IC's are used. One glance through the Notebook will convince you that it would be a very useful addition to your own library.

R-E

new products

More information on new products is available. Use the Free Information Card inside the back cover.

CHART RECORDER, the IR-5207, is an X-Y recorder kit in the test-instrument line. The kit features front-panel input filters with pushbutton controls, an integral paper-hold-down that can be used in horizontal or vertical modes, and "zero" controls that allow the pen to be placed anywhere on the chart with zero input at both coordinates.

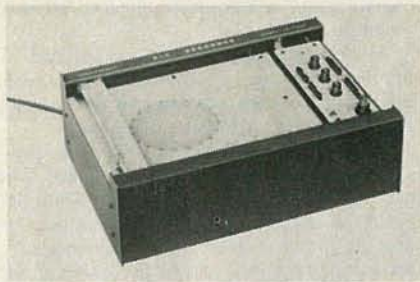

CIRCLE 50 ON FREE INFORMATION CARD

Calibrated 1, 10, 100 mV- and 1 volt-per-inch ranges are selectable from the front panel. Other features are electric pen lift, calibrated X and Y sweep, and remote capability. The IR-5207 uses 8 1/2 by 11 inch paper and two kinds of disposable pens are available. Price is \$479.94.—**Heath Co.**, Dept. 350-260, Benton Harbor, MI 49022.


FUNCTION/SWEEP GENERATOR, model LFG-1300S, provides a wide range of capabilities and is suitable for use in design, testing, and service applications. Housed in an all-metal enclosure, the unit covers frequencies of 0.002 to 2 MHz in 8 ranges and includes linear and logarithmic sweep modes with sweep widths up to 1000:1 and sweep rates of 0.5 to 50 Hz. Waveform outputs include



CIRCLE 151 ON FREE INFORMATION CARD

sine, triangle, sawtooth, and pulses. Output level is continuously variable from 0 to 20 V P-P and a push-button attenuator provides up to 70 dB attenuation in 10-dB steps. An auxiliary connector provides TTL level signals for driving logical circuits. price is \$495.—**Leader Instruments Corp.**, 380 Oser Ave., Hauppauge, NY 11787.

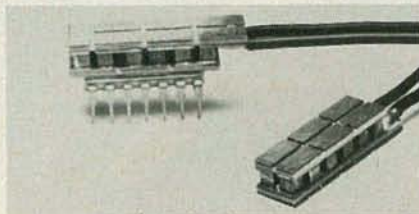
THERMOELECTRIC COOLER, model 801-1029-01-00-00, is designed for use with 8, 14, 16, and 18-lead dual in-line packages (DIP's). When placed between the DIP and a heat sink, it can pump out up to 3.5 watts of heat using a modest input of DC power, thereby allowing a DIP to operate in a hot environment. The unit can heat



CIRCLE 152 ON FREE INFORMATION CARD

as well as cool, so the device can also be used to regulate DIP temperatures to any preset value in the range of ambient $\pm 60^\circ$ Celsius. Price is \$4.90.—**Cambridge Thermionic Corp.**, 445 Concord Ave., Cambridge, MA 02238.

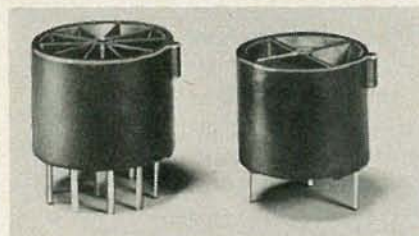BURN-IN SOCKETS, TS-5173, are a line of TO-pattern sockets offered in both standard (150°C with BeCu contacts) and high temperature versions (200°C with BeNi contacts). The series is available with from 3-to-12 gold-plated contacts and features very low insertion force and a center



CIRCLE 153 ON FREE INFORMATION CARD

locating stud for greater mounting rigidity. Price is \$.63 each for 1000 pieces.—**Robinson-Nugent, Inc.**, 800 E. 8th St., New Albany, IN 47150.

CABLE TV ADAPTOR, model 047AE, allows subscribers to tune all cable channels using their TV set's remote control. The system allows reception of cable channels through the set's UHF tuner, which can be operated remotely, thus freeing the viewer from having to get up and go to the cable



CIRCLE 154 ON FREE INFORMATION CARD

converter box everytime he wants to switch to another program. Channels 2 through 13 remain available through the VHF tuner. The system includes the converter, AC adaptor, 75-to-300 ohm transformer and instructions. Price is \$39.95 plus shipping (NY residents add appropriate tax).—**ETCO Electronics Corp.**, North Country Shopping Center, Rte 9 N., Plattsburgh, NY 12901. R-E

RAA DUAL LIMITER

as featured in **MODERN RECORDING**

Craig Anderton's design provides big studio performance at home recording prices with features like "dual" mode which preserves stereo imaging by allowing the signal on one channel to limit both channels.

SPECS: 1 3/4" rack mount package; +12v. @ 25 ma.; -12v. @ 8 ma.; freq. response: 20 Hz. -20 kHz. +1 db.; attack time less than 1 ms.; SNR referenced to 0 db. output greater than -65 db.

No. 6790
DUAL LIMITER KIT \$49.95
Assembled \$74.95 (2 lbs.)

- () I'm sold, send the Limiter kit, \$49.94 plus postage enclosed.
- () Send the assembled limiter \$79.95 plus postage enclosed.
- () Send Free Catalog
- Charge Visa MC Card No. _____
- Name: _____
- Address: _____
- City _____ State: _____ Zip: _____

RAA ELECTRONICS, Dept. 9-R, 1020 W. Wilshire, Oklahoma City, OK 73116

CIRCLE 26 ON FREE INFORMATION CARD

TEST UP TO
100 WATTS/STEREO
200 WATTS/MONO



AUDIO POWER CONTROL
TPC-100 \$140

Now test an amplifier or receiver's maximum power, crosstalk, distortion, and much more. The TPC-100's monitor output provides the interconnection between the amplifier and your test equipment. The TPC-100 distributes 2 channel audio signals into 4, 8, or 16 ohm dummy loads (which are MIL grade non-inductive), or to the external speakers.

To order, or for more information, contact:

testek

6910 HAVENHURST AVENUE/VAN NUYS/CALIFORNIA 91406
213 786-6890

CIRCLE 65 ON FREE INFORMATION CARD



Expand your knowledge Subscribe to **BYTE**

The 1980's are here! The decade of the personal computer has arrived, and **BYTE** has made it happen! **BYTE** — the small systems journal devoted to personal computers — has helped usher in the new era. Leading the personal computer revolution, which is already transforming home and personal life, are **BYTE**'s 160,000 enthusiastic readers. Their enthusiasm has made **BYTE** the largest computer magazine in the world!

To be knowledgeable in the 1980's you need to know how to use personal computers. **BYTE** is your personal guide to the new era. **BYTE** tells you how to build, buy, and use computers for fun, practical purposes, and profit. With help from **BYTE**, you can experiment right in your own home with graphics, word processing, computer music, speech synthesizers, simulations, robotics, personal data base management, business computing — and hundreds of other fascinating hardware and software applications.

Resolve now to expand your computer knowledge.
Subscribe to **BYTE**!

BYTE® the small systems journal
A MCGRAW-HILL PUBLICATION

Fill in and mail the coupon today. Read your first copy of **BYTE**. If it is everything you expected, honor our invoice. If it isn't, just write "Cancel" on the invoice and mail it back. You won't be billed and the first issue is yours at no charge.

Call us toll-free
800-258-5485

BYTE Subscription Dept. P.O. Box 590 Martinsville, NJ 08836
Please enter my subscription for:

- One year \$18 (12 issues) Two years \$32 Three years \$46
 Check enclosed entitles me to 13 issues for price of 12 (North America only)
 Bill Visa Bill Master Charge Bill me (North America only)

Card Number _____ Expiration _____

Signature _____ Name (please print) _____

Address _____

City _____ State/Province/Country Code _____

Foreign Rates (To expedite service, please remit in U.S. Funds)

- Canada or Mexico One year \$20 Two years \$36 Three years \$52
 Europe, one year (air delivered) \$32
 All other countries, one year (surface delivered) \$32. Air delivery available on request.

7890

Please allow 6-8 weeks for processing.

CIRCLE 40 ON FREE INFORMATION CARD

© **BYTE** Publications, Inc. 1980

EQUIPMENT REPORTS

continued from page 44

tablet is included, enabling the user to take hundreds of readings and record them for a variety of individuals.

The instrument is powered by a standard 9-volt transistor radio battery. Because of the additional power consumption required by both LED and audible indicators, use of an alkaline battery is recommended.

Testing the BP-1

Unpackaging the Micronta *BP-1* blood-pressure tester, we found that it included a handy vinyl carrying case, complete with contoured cutouts to support the instrument, a hinged lid, and velcro clasps.

A short review of the manual was most informative. Several paragraphs are devoted to an introduction to hypertension, its causes and statistics, and interpretation of blood pressure readings.

A step-by-step procedure is outlined to familiarize the user with the unit. After reading the instructions and taking a few practice readings, using the instrument is a snap.

Two flexible rubber cables from the pressure cuff are inserted into the instrument. The cuff is placed over the upper arm, white dot located over the brachial artery. That location may be found visually by the presence of a superficial dark vein just to the inside of the elbow joint, palm turned up. Or, it may be detected by feeling for a pulse.

With the pressure cuff in proper position, the Velcro wrap is snugly pressed down, holding the cuff in place. A series of squeezes on the bulb inflates the cuff to a pressure of about 200 millimeters. The instrument is then switched on, and the release button is slightly depressed, allowing the air pressure to drop slowly until the indicators begin to signal.

We found the cuff to be very lenient about slightly improper placement. Virtually identical readings were obtained with the white dot off center by an inch or more. But for a correct reading, the arm *must* be elevated to the same height as the heart (mid-chest height). Too low, and the instrument will show an unrealistic high reading; too high, and the instrument will show an inaccurate low reading. The difference will be a significant amount.

How accurate?

To test the accuracy of the *BP-1*, we took our review sample to a local hospital and checked it against three resident instruments. We found slight differences in measurement among all instruments, but the *BP-1* was well within the range of variability. A further test against a newer instrument is a dentist's office showed identical readings.

While the retail cost of the *BP-1* is higher than most consumer-grade stethoscope sphygmomanometers, it appears to be of quality manufacture; ours was certainly equivalent to the two-piece professional units with which it was compared. The unencumbered one-handed application is a distinct advantage. We find the *BP-1* to be both cleverly designed and realistically priced. The *BP-1* blood pressure tester sells for \$69.95 and is available at Radio Shack stores nationwide. **R-E**



Write: National Committee for
Prevention of Child Abuse,
Box 2866, Chicago, Ill. 60690

Start Computing For Just \$129.95 With An 8085-Based Professional Computer Kit—

Explorer/85

100% compatible with all 8080A and 8085 software & development tools!

No matter what your future computing plans may be, Level "A"—at \$129.95—is your starting point.

Starting at just \$129.95 for a Level "A" operating system, you can now build the exact computer you want. Explorer/85 can be your beginner's system, OEM controller, or IBM-formatted 8" disk small business system... yet you're never forced to spend a penny for a component or feature you don't want and you can expand in small, affordable steps!

Now, for just \$129.95, you can own the first level of a fully expandable computer with professional capabilities—a computer which features the advanced Intel 8085 cpu, thereby giving you immediate access to all software and development tools that exist for both the 8085 and its 8080A predecessor (they are 100% software compatible)—a computer which features onboard S-100 bus expansion—plus instant conversion to mass storage disk memory with either 5-1/4" diskettes or standard IBM-formatted 8" disks.

For just \$129.95 (plus the cost of a power supply, keyboard/terminal and RF modulator, if you don't have them already), Explorer/85 lets you begin computing on a significant level... applying the principles discussed in leading computer magazines... developing "state of the art" computer solutions for both the industrial and leisure environment.

Level "A" Specifications

Explorer/85's Level "A" system features the advanced Intel 8085 cpu, an 8355 ROM with 2k deluxe monitor/operating system, and an 8155 ROM-I/O—all on a single motherboard with room for RAM/ROM/PROM/EPROM and S-100 expansion, plus generous prototyping space.

(Level "A" makes a perfect OEM controller for industrial applications and is available in a special Hex Version which can be programmed using the Netronics Hex Keypad/Display.)

PC Board: glass epoxy, plated through holes with solder mask

- I/O: provisions for 25-pin (DB25) connector for terminal serial I/O, which can also support a paper tape reader... provision for 24-pin DIP socket for hex keypad/display... cassette tape recorder input... cassette tape recorder output... cassette tape control output... speaker output... LED output indicator on SOD (serial output) line... printer interface (less drivers)... total of four 8-bit plus one 6-bit I/O ports • Crystal Frequency: 6.144 MHz • Control Switches: reset and user (RST 7.5) interrupt... additional provisions for RST 5.5, 6.5 and TRAP interrupts onboard • Counter/Timer: programmable, 14-bit binary • System RAM: 256 bytes located at F800, ideal for smaller systems and for use as an isolated stack area in expanded systems... RAM expandable to 64k via S-100 bus or 4K on motherboard.

System Monitor (Terminal Version): 2k bytes of deluxe system monitor ROM located at F000 leaving 0000 free for user RAM/ROM. Features include tape load with labeling... tape dump with labeling... examine/change contents of memory... insert data... warm start... examine and change all registers... single step with register display at each break point, a debugging/training feature... go to execution address... move blocks of memory from one location to another... fill blocks of memory with a constant... display blocks of memory... automatic baud rate selection... variable display line length control (1-255 characters/line)... channelized I/O monitor routine with 8-bit parallel output for high speed printer... serial console in and console out channel so that monitor can communicate with I/O ports.

System Monitor (Hex Version): Tape load with labeling... tape dump with labeling... examine/change contents of memory... insert data... warm start... examine and change all



registers... single step with register display at each break point... go to execution address. Level "A" in the Hex Version makes a perfect controller for industrial applications and can be programmed using the Netronics Hex Keypad/Display.



Hex Keypad/Display.

Hex Keypad/Display Specifications

Calculator type keypad with 24 system defined and 16 user defined keys. 6 digit calculator type display which displays full address plus data as well as register and status information.

Level "B" Specifications

Level "B" provides the S-100 signals plus buffers/drivers to support up to six S-100 bus boards and includes: address decoding for onboard 4k RAM expansion select-able in 4k blocks... address decoding for onboard 8k EPROM expansion select-able in 8k blocks... address and data bus drivers for onboard expansion... wait state generator (jumper select-able), to allow the use of slower memories... two separate 5 volt regulators.



Explorer/85 with Level "C" card cage.

Level "C" Specifications

Level "C" expands Explorer's motherboard with a card cage, allowing you to plug up to six S-100 cards directly into the motherboard. Both cage and cards are neatly contained inside Explorer's deluxe steel cabinet.

Level "C" includes a sheet metal superstructure, a 5-card gold plated S-100 extension PC board which plugs into the motherboard. Just add required number of S-100 connectors

Level "D" Specifications

Level "D" provides 4k or RAM, power supply regulation, filtering decoupling components and sockets to expand your Explorer/85 memory to 4k (plus the original 256 bytes located in the 8155A). The static RAM can be located anywhere from 0000 to EFFF in 4k blocks.

Level "E" Specifications

Level "E" adds sockets for 8k of EPROM to use the popular Intel 2716 or the TI 2516. It includes all sockets, power supply regulator, heat sink, filtering and decoupling components. Sockets may also be used for soon to be available RAM IC's (allowing for up to 12k of onboard RAM).

Order A Coordinated Explorer/85 Applications Pak!

Explorer's Pak (SAVE \$12.50)—Buy Level "A" and Hex Keypad/Display for \$199.90 and get FREE Intel 8085 user's manual plus FREE postage & handling!

Student Pak (SAVE \$24.45)—Buy Level "A," ASCII Keyboard/Computer Terminal, and Power Supply for \$319.85 and get FREE RF Modulator plus FREE Intel 8085 user's manual plus FREE postage & handling!

Engineering Pak (SAVE \$41.00)—Buy Levels "A," "B," "C," "D," and "E" with Power Supply, ASCII Keyboard/Computer Terminal, and six S-100 Bus Connectors for \$514.75 and get 10 FREE computer grade cassette tapes plus FREE 8085 user's manual plus FREE postage & handling!

Business Pak (SAVE \$89.95)—Buy Explorer/85 Levels "A," "B," and "C" (with cabinet), Power Supply, ASCII Keyboard/Computer Terminal (with cabinet), 16k RAM, 12" Video Monitor, North Star 5-1/4" Disk Drive (includes North Star BASIC) with power supply and cabinet, all for just \$1599.40 and get 10 FREE 5-1/4" minidiskettes (\$49.95 value) plus FREE 8085 user's manual plus FREE postage & handling!

Continental U.S.A. Credit Card Buyers Outside Connecticut
CALL TOLL FREE 800-243-7428

To Order From Connecticut Or For Technical Assistance, Etc. Call (203) 354-9375

Netronics R&D Ltd., Dept. RE-9

333 Litchfield Road, New Milford, CT 06776

Please send the items checked below—

- Explorer/85 Level "A" Kit (ASCII Version), \$129.95 plus \$3 p&h.
- Explorer/85 Level "A" Kit (Hex Version), \$129.95 plus \$3 p&h.
- 8k Microsoft BASIC on cassette tape, \$64.95 postpaid.
- 8k Microsoft BASIC in ROM Kit (requires Levels "B," "D," and "E"), \$99.95 plus \$2 p&h.
- Level "B" (S-100) Kit, \$49.95 plus \$2 p&h.
- Level "C" (S-100 6-card expander) Kit, \$39.95 plus \$2 p&h.
- Level "D" (4k RAM) Kit, \$69.95 plus \$2 p&h.
- Level "E" (EPROM/ROM) Kit, \$5.95 plus 50¢ p&h.
- Deluxe Steel Cabinet for Explorer/85, \$49.95 plus \$3 p&h.
- ASCII Keyboard/Computer Terminal Kit (features a full 128 character set, upper & lower case, full cursor control, 75 ohm video output convertible to baudot output, selectable baud rate, RS232-C or 20 ma. I/O, 32 or 64 character by 16 line formats, and can be used with either a CRT monitor or a TV set (if you have an RF modulator), \$149.95 plus \$2.50 p&h.
- Hex Keypad/Display Kit, \$69.95 plus \$2 p&h.
- Deluxe Steel Cabinet for ASCII Keyboard/Terminal, \$19.95 plus \$2.50 p&h.
- Power Supply Kit (± 8V @ 5 amps) in deluxe steel cabinet, \$39.95 plus \$2 p&h.
- Gold Plated S-100 Bus Connectors, \$4.85 each, postpaid.
- RF Modulator Kit (allows you to use your TV set as a monitor), \$8.95 postpaid.
- 16k RAM Kit (S-100 Board expands to 64k), \$199.95 plus \$2 p&h.
- 32k RAM Kit, \$329.95 plus \$2 p&h.
- 48k RAM Kit, \$459.95 plus \$2 p&h.
- 64k RAM Kit, \$589.95 plus \$2 p&h.
- 16k RAM Expansion Kit (to expand any of the above up to 64k), \$139.95 plus \$2 p&h each.
- Intel 8085 cpu User's Manual, \$7.50 postpaid.
- Special Computer Grade Cassette Tapes, \$1.90 each or 3 for \$5, postpaid.
- 12" Video Monitor (10 MHz bandwidth), \$139.95 plus \$5 p&h.
- North Star Double Density Floppy Disk Kit (One Drive for Explorer/85 (includes 3 drive S-100 controller, DOS, and extended BASIC with per-

sonalized disk operating system—just plug it in and you're up and running!), \$69.95 plus \$5 p&h.

- Power Supply Kit for North Star Disk Drive, \$39.95 plus \$2 p&h.
- Deluxe Case for North Star Disk Drive, \$39.95 plus \$2 p&h.
- Experimenters' Pak (see above), \$199.90 postpaid.
- Student Pak (see above), \$319.85 postpaid.
- Engineering Pak (see above), \$514.75 postpaid.
- Business Pak (see above), \$1599.40 postpaid.

Total Enclosed \$ _____ (Conn. res. add sales tax) By—
 Personal Check M.O./Cashier's Check Visa Master Charge (Bank # _____)

Acct. # _____
Signature _____ Exp. Date _____
Print Name _____
Address _____
City _____
State _____ Zip _____
 Send Me Information

By Netronics

ASCII/BAUDOT, STAND ALONE



Computer Terminal

COMPLETE FOR ONLY \$149.95

The Netronics ASCII/BAUDOT Computer Terminal Kit is a microprocessor-controlled, stand alone keyboard/terminal requiring no computer memory or software. It allows the use of either a 64 or 32 character by 16 line professional display format with selectable baud rate, RS232-C or 20 ma. output, full cursor control and 75 ohm composite video output.

The keyboard follows the standard typewriter configuration and generates the entire 128 character ASCII upper/lower case set with 96 printable characters. Features include onboard regulators, selectable parity, shift lock key, alpha lock jumper, a drive capability of one TTY load, and the ability to mate directly with almost any computer, including the new Explorer/85 and ELF products by Netronics.


The Computer Terminal requires no I/O mapping and includes 1k of memory, character generator, 2 key rollover, processor controlled cursor control, parallel ASCII/BAUDOT to serial conversion and serial to video processing—fully crystal controlled for superb accuracy. PC boards are the highest quality glass epoxy for the ultimate in reliability and long life.

VIDEO DISPLAY SPECIFICATIONS

The heart of the Netronics Computer Terminal is the microprocessor-controlled Netronics Video Display Board (VID) which allows the terminal to utilize either a parallel ASCII or BAUDOT signal source. The VID converts the parallel data to serial data which is then formatted to either RS232-C or 20 ma. current loop output, which can be connected to the serial I/O on your computer or other interface, i.e., Modem.

When connected to a computer, the computer must echo the character received. This data is received by the VID which processes the information, converting to data to video suitable to be displayed on a TV set (using an RF modulator) or on a video monitor. The VID generates the cursor, horizontal and vertical sync pulses and performs the housekeeping relative to which character and where it is to be displayed on the screen.

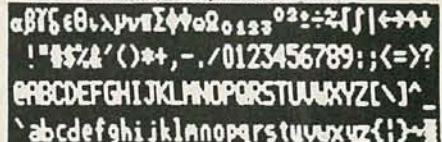Video Output: 1.5 P/P into 75 ohm (EIA RS-170) • Baud Rate: 110 and 300 ASCII • Outputs: RS232-C or 20 ma. current loop • ASCII Character Sets: 128 printable characters—



BAUDOT Character Set: ABCDEFGHIJKLMNOPQRSTUVWXYZ - ? * 3 \$ # () , . 9 0 1 4 1 5 7 ; 2 / 6 8 •
Cursor Modes: Home, Backspace, Horizontal Tab, Line Feed, Vertical Tab, Carriage Return. Two special cursor sequences are provided for absolute and relative X-Y cursor addressing • Cursor Control: Erase, End of Line, Erase of Screen, Form Feed, Delete • Monitor Operation: 50 or 60Hz (jumper selectable)

Continental U.S.A. Credit Card Buyers Outside Connecticut

CALL TOLL FREE 800-243-7428

To Order From Connecticut Or For Technical Assistance, Etc. Call (203) 354-9375

Netronics R&D Ltd., Dept. RE-9

333 Litchfield Road, New Milford, CT 06776

Please send the items checked below—

- Netronics Stand Alone ASCII Keyboard/Computer Terminal Kit, \$149.95 plus \$3.00 postage & handling.
 - Deluxe Steel Cabinet for Netronics Keyboard/Terminal In Blue/Black Finish, \$19.95 plus \$2.50 postage and handling.
 - Video Display Board Kit alone (less keyboard), \$89.95 plus \$3 postage & handling.
 - 12" Video Monitor (10 MHz bandwidth) fully assembled and tested, \$139.95 plus \$5 postage and handling.
 - RF Modulator Kit (to use your TV set for a monitor), \$8.95 postpaid.
 - 5 amp Power Supply Kit In Deluxe Steel Cabinet (± 8VDC @ 5 amps, plus 6-8 VAC), \$39.95 plus \$2 postage & handling.
- Total Enclosed (Conn. res. add sales tax) \$ _____
By—
 Personal Check Cashiers Check/Money Order Visa Master Charge (Bank # _____)
- Acct. # _____
Signature _____ Exp. Date _____
Print Name _____
Address _____
City _____
State _____ Zip _____
 Send Me More Information

communications corner

Transceivers with all the operating controls built into the microphone **HERB FRIEDMAN, COMMUNICATIONS EDITOR**

STARTING WAY BACK IN THE DARK AGES of CB when all transceivers used vacuum tubes, many attempts have been made to place channel selection and other frequently used functions, such as volume and squelch control, in the microphone. (Among other benefits it allows a vehicle's driver to change channels without leaning across the seat, and/or taking his eyes off the road.)

Some early "remote control" designs had RF running all over the place, and they made the "Rube Goldberg" contraptions we used to see in the Sunday comics look like advanced engineering by comparison.

Successful full-feature remote control from the microphone didn't come about until Large-Scale Integration—or LSI as it is more commonly termed—was used for phase-locked oscillators and their control circuits.



FIG. 1

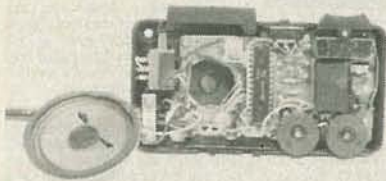


FIG. 2

The phase-locked oscillator generates both the receiver's local oscillator frequencies and the frequencies from which the transmitter's output frequencies are derived. Not very long ago

that was a formidable design with a cost and complexity that limited its use almost exclusively to radio astronomers. But by substituting solid-state devices for vacuum tubes, and then using LSI as a substitute for hundreds of discrete components, almost overnight the phase-locked detector became an IC no larger than your index finger. It was priced well under \$10 in manufacturing quantities. (Actually pennies in today's marketplace.)

Today, we have Large Scale Integration of Large Scale Integration. That's about the only way to describe shrinking a device the size of your index finger to something slightly smaller than half the length of your little finger.

Everything has become so small it's now possible to build virtually all transceiver controls, including channel selection, into the microphone itself, just as Cobra has done in their *model 66GTL* remote (Hideaway) 40-Channel *continued on page 92*

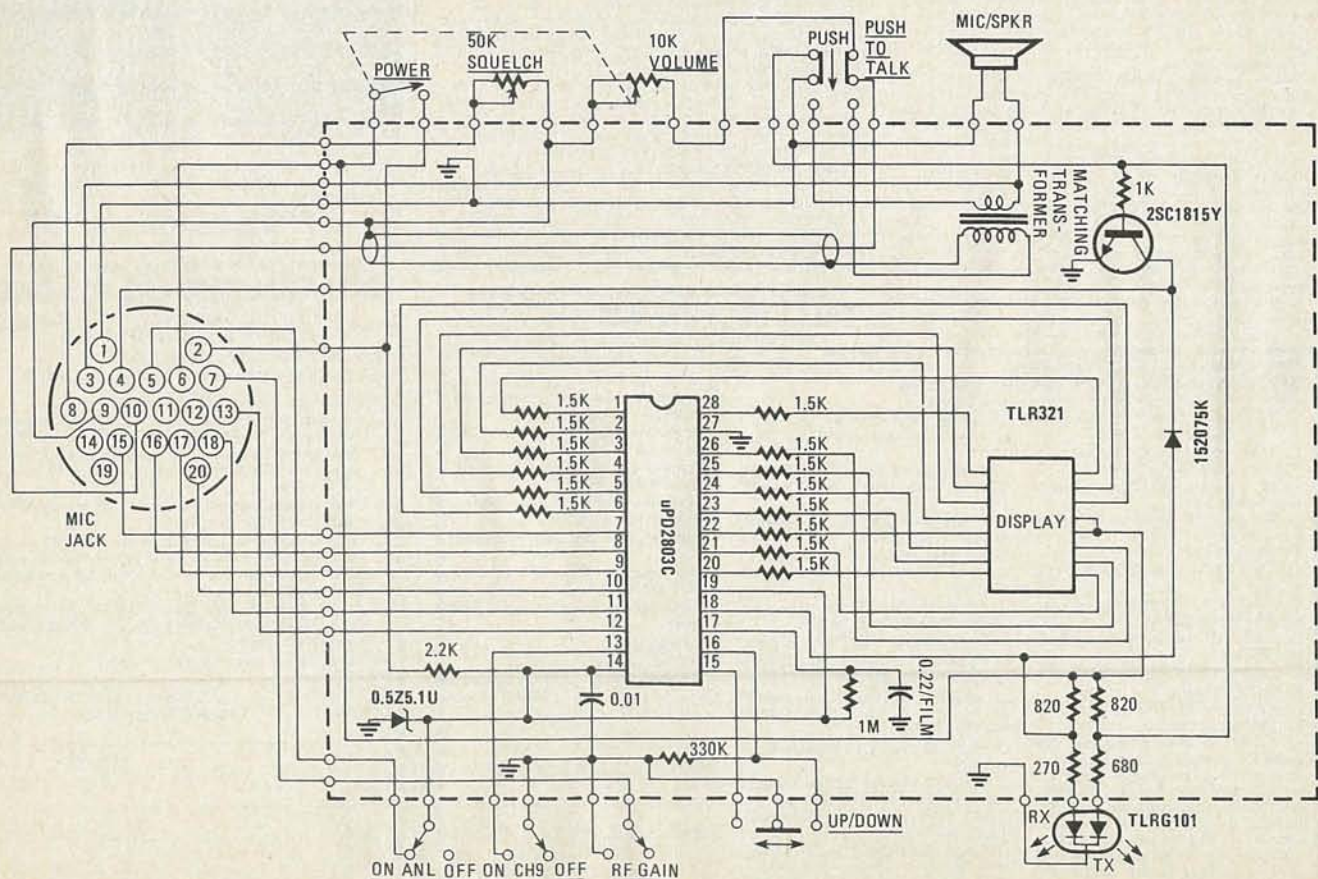


FIG. 3

All new! All construction projects!

Here's the new quarterly magazine you've been waiting for—*Radio-Electronics Special Projects*—page after page of all new, never-before published construction articles on Test Equipment, Computers, Electronic Music, Communications, Automotive and Hobby Projects.

They're the kind of projects you want to build, the kind only *Radio-Electronics* has the expertise to design, and the first issue is filled with brand-new construction articles like these:

Radio-Electronics

Special Projects

\$1.95
WINTER
1980



Bar-Graph Voltmeter

4-Channel Scope Multiplexer
Chord Egg Synthesizer
Car Test Probe





Digital Logic Trainer
TRS-80 I/O Controller
Programmable Sound Generator









Test Equipment

Digital Scope Multiplier—to convert almost any scope into a 4-trace unit.
Frequency Multiplier—to extend the range of your frequency counter.
Safety Cooker—that protects unattended equipment against electrical problems.
Battery Box/Switching Box—a great accessory for any bench.
Car Test Probe—use it to test auto-

motive electrical systems.
Digital IC Tester—to make quick work of testing digital IC's.

Electronic Music

The Chord Egg—to generate an endless series of chords automatically.
Words And Music—a programmable music generator that's ideal for doorbells.
Big Sound For Chord Organs—to enhance the sound

from electromechanical chord organs.

Computers

Digital Logic Trainer—that teaches how microprocessors work.
Save Your Files—cassette tape recorder controller makes using tape as computer memory storage easy.
Programmable Sound Generator—adds sound capability to almost any computer system.

Hobby

Adventures of the IC's—applications for LM3914 and VMOS power FET's.
Digital Do-Nothing Box—lights, counts, teaches binary and digital number systems.

Communications

Digital Readout Add-on For Communications Receivers—to update older receivers easily.
Microphone Acoustic Coupler—a sim-

ple add-on for any communications system. And lots more—all new, and all on your newsstands September 4!

Or...

Use the handy coupon and get your advance copy of *Radio-Electronics Special Projects* (mailed after August 11) delivered right to your door. Make sure you get your copy by ordering ... today!

We will ship your magazine, postpaid in U.S. and Canada, within 6 weeks of receipt of your order. All other countries add \$3 for postage.

I want _____ magazines @ \$3.00 each. First-Class postpaid. (U.S.A. & Canada)

I have enclosed \$ _____. (Foreign, add \$3.00 for Air Mail postage per copy.)

Radio-Electronics
Special Projects

45 East 17th Street
New York, N.Y. 10003

Name		
Street Address		
City	State	Zip



GO WITH MCGRAW-

Join the Electronics and Control Engineers club that saves you BIG money on the



PHASELOCK TECHNIQUES. By F. M. Gardner, 2nd Ed., 285 pp., illus. This edition of the standard working reference shows you not only better methods of analysis and better procedures for deciding on loop parameters, but also the circuits and the results.
582029-3 Pub. Pr., \$21.50 Club Pr., \$16.95

INTRODUCTION TO THE THEORY AND DESIGN OF ACTIVE FILTERS. By L. P. Huelsman and P. E. Allen, 430 pp., illus. Once you add active filter design to your repertoire of specialties, you'll possess a skill that's in great demand today. Here's one of the best texts we know on the theory, design, application, and evaluation of modern active filters and the various techniques used today.
303/543 Pub. Pr., \$25.95 Club Pr., \$19.95

HANDBOOK OF OPERATIONAL AMPLIFIER CIRCUIT DESIGN. By D. F. Stout. Edited by M. Kaufman. 434 pp., 223 illus. Compact, concise, highly concentrated, and containing a storehouse of information, this one-stop volume will help you solve any op amp circuit problem!
617/97X Pub. Pr., \$31.50 Club Pr., \$20.50

ELECTRONIC DISPLAYS. By E. G. Bylander, Texas Instruments Incorporated, 172 pp., illus. The book describes current electronic displays by family types, discussing all aspects of their operation, application, and circuit requirements. You cover photometry and contrast enhancement, together with the fundamentals of such critical components as mounts and drives, interface requirements, and other necessary engineering information.
095/108 Pub. Pr., \$24.50 Club Pr., \$18.50

TRANSISTOR CIRCUIT APPROXIMATIONS. By A. P. Malvino, 3rd Ed., 371 pp. Makes your arrival at an ideal solution to problems you encounter in your transistor work much easier than you ever dreamed. Using the "idealize-and-improve" approach, the book shows you how to arrive at a working degree of accuracy in the shortest length of time.
398/78X Pub. Pr., \$15.95 Club Pr., \$11.95

SEMICONDUCTOR DEVICES AND INTEGRATED ELECTRONICS By A. G. Milnes, 816 pp., 605 illus. The main secret of this book's quick and tremendous success with engineers is the way its logical grouping and handling of the material builds and strengthens your in-depth grasp of the subject, plus its real-world application of just the right amount of theory.
789/487 Pub. Pr., \$26.50 Club Pr., \$20.95

BIT-SLICE MICROPROCESSOR DESIGN. By J. Mick and J. Brick, 320 pp., 230 illus. All in one place—the crucial information you've been needing about the 2900 family of bit-slice microprocessor components! A remarkable "first," this book designs right before your eyes not just one, but two complete 16-bit machines!
417/814 Pub. Pr., \$18.50 Club Pr., \$14.50

MICROCOMPUTER INTERFACING. By B. Artwick, 352 pp., illus., 7 x 9 1/4 format. Here's your passkey to trouble-free, low-cost interfacing! The book gives you the data and describes the techniques you need to conceptualize, select, mate and match, build, and interface microcomputer systems—no matter what the application.
789/436 Pub. Pr., \$18.95 Club Pr., \$14.95

ELECTRONICS DESIGNERS' HANDBOOK. Edited by L. J. Giacoletto, 2nd Ed. 2,344 pp., 1,686 illus. Now doubled in size and with 90% of its material new, this famous classic (first edition by Landee, Davis, Albrecht) has been thoroughly revised and updated to give you not only the *how* and the *why* of all your design work but also the *how much* of every design step you take!
231/494 Pub. Pr., \$62.50 Club Pr., \$46.50

STANDARD HANDBOOK FOR ELECTRICAL ENGINEERS, 11/e. By D. G. Fink and H. W. Beaty, 448 pp., 1,414 illus. A giant in every sense of the word, today's most widely used source of electrical engineering information and data serves you as no other single work available anywhere when you need detailed, accurate, timely, and reliable facts and how-to on the generation, transmission, distribution, control, conversion, and application of electric power.
209/74X Pub. Pr., \$54.50 Club Pr., \$41.95

BE SURE TO CONSIDER THESE IMPORTANT TITLES AS WELL:

DIGITAL FILTERS. By A. Antoniou, 021/171 Pub. Pr., \$26.95 Club Pr., \$20.50

HANDBOOK OF ELECTRONIC SYSTEMS DESIGN. By C. A. Harper, 266/832 Pub. Pr., \$39.50 Club Pr., \$29.50

ELECTRONICS DICTIONARY, 4/e. By J. Markus, 404/313 Pub. Pr., \$24.50 Club Pr., \$19.50

ENGINEERING FUNDAMENTALS FOR PROFESSIONAL ENGINEERS' EXAMINATIONS, 2/e. By L. M. Polentz, 503/80X Pub. Pr., \$22.50 Club Pr., \$16.95

ENGINEERING MATHEMATICS HANDBOOK, 2/e. By J. J. Tuma, 654/298 Pub. Pr., \$24.95 Club Pr., \$19.95


RADIO HANDBOOK, 21/e. By W. Orr, 772/630 Pub. Pr., \$21.50 Club Pr., \$16.60

TRANSFORMER AND INDUCTOR DESIGN HANDBOOK. By W. T. McLyman, 786/755 Pub. Pr., \$35.00 Club Pr., \$26.50

CRYSTAL OSCILLATOR DESIGN AND TEMPERATURE COMPENSATION. By M. E. Frerking, 784/973 Pub. Pr., \$18.95 Club Pr., \$14.95

NATIONAL ELECTRICAL CODE HANDBOOK, 16/e. By J. F. McPartland, 456/909 Pub. Pr., \$19.95 Club Pr., \$14.50

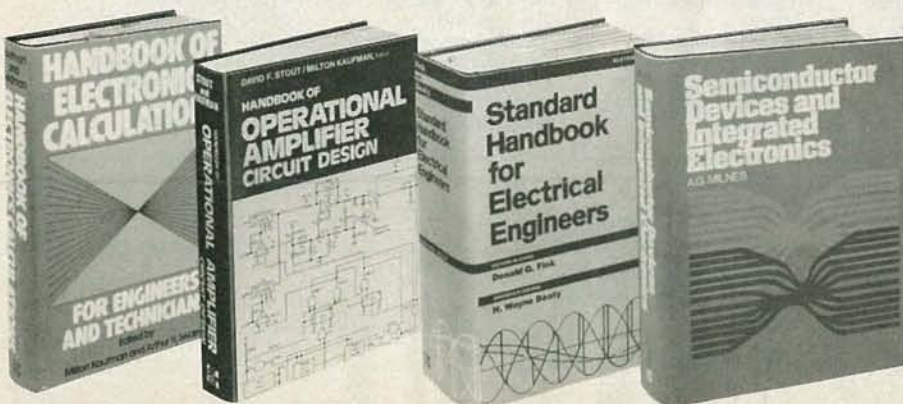NOISE REDUCTION TECHNIQUES IN ELECTRONIC SYSTEMS. By H. Ott, 769/63X Pub. Pr., \$27.95 Club Pr., \$20.95



HILL'S EXPERIENCE!

Book Club — McGraw-Hill's long-established important new books of all publishers!

HANDBOOK OF ELECTRONICS CALCULATIONS FOR ENGINEERS AND TECHNICIANS. Edited by M. Kaufman and A. H. Seidman. 653 pp., 725 illus. This first comprehensive tool of its kind includes hundreds of worked-out problems in analog and digital circuits. Includes more than 700 diagrams, curves, tables, and graphs.
333/920 Pub. Pr., \$24.50 Club Pr., \$18.95

MICROCOMPUTER-BASED DESIGN By J. B. Peatman. Expanded 4th printing, 604 pp., over 400 photos and other illustrations. Do all your best day-to-day designs, as well as your supercreative and special designs, around the new microcomputers and the specific "how-to" help you get here!
491/380 Pub. Pr., \$28.95 Club Pr., \$20.95

MICROELECTRONICS Digital and Analog Circuits and Systems By J. Millman. 881 pp., 700 illus. This giant book takes you step by step from a qualitative knowledge of a semi-conductor, to an understanding of the operation of devices, and finally, to an appreciation of how these are combined to form micro-electronic chips.
423/27X Pub. Pr., \$28.95 Club Pr., \$22.50

ELECTRONIC COMMUNICATION. By Robert L. Shrader. 4th Ed., 801 pp., 870 illus. This thoroughly updated edition offers all the theory and fundamentals you need to prepare yourself for the FCC commercial and amateur grade license examinations—and pass them the first time!
571/503 Pub. Pr., \$19.50 Club Pr., \$15.50

ELECTRONICS ENGINEERING FOR PROFESSIONAL ENGINEERS' EXAMINATIONS. By Charles R. Hafer. 336 pp., illus. Actually two books in one—a quick preparation manual to help you pass your P.E. exams on the first try and a rich source of practical electronics engineering information and know-how.
254/303 Pub. Pr., \$19.50 Club Pr., \$15.50

INTRODUCTION TO RADAR SYSTEMS, 2/e. By M. I. Skolnik. 698 pp., 244 illus. This new edition of a widely used text on radar from the systems engineer's point of view brings you full discussions of the many major changes that have occurred in the field recently.
579/091 Pub. Pr., \$34.95 Club Pr., \$27.95

MICROPROCESSORS/MICROCOMPUTERS/SYSTEM DESIGN. By Texas Instruments Learning Center and the Engineering Staff of Texas Instruments Inc. 634 pp., illus., outsized 7 1/4 x 10 1/4 format. This practical, authoritative guide details the versatile, proved-in-action methods and technical features of the 9900 minicomputer architecture that can be employed to create outstanding products and systems.
637/58X Pub. Pr., \$24.50 Club Pr., \$19.50

ELECTRONICS ENGINEER'S HANDBOOK. Editor-in-Chief, D. G. Fink. 2,104 pp., 2,026 illus. Huge in every sense, this instant-reference volume gives you every latest essential in the field, 2,100 formulas and equations, a 2,500-item bibliography, and every illustration you need to clarify all of modern electronics!
209/804 Pub. Pr., \$57.50 Club Pr., \$40.50

PRINTED CIRCUITS HANDBOOK, 2/e. By C. F. Coombs, Jr. 256 pp., 327 illus. Blueprints every important phase of printed circuitry. Provides the information you need to establish a production facility and control the processes. A virtual encyclopedia in the field, five major sections cover engineering, fabrication, assembly, soldering, and testing.
126/089 Pub. Pr., \$32.50 Club Pr., \$24.50

DESIGN OF SOLID-STATE POWER SUPPLIES. By Eugene R. Hnatek. 2nd Ed., 640 pp., illus. A total revision and expansion of an essential, ready-to-use sourcebook on the design of power supplies, particularly of the switching variety. Incorporates the latest developments in the field while emphasizing the practical, how-to help designers want.
582054-4 Pub. Pr., \$27.50 Club Pr., \$21.50

any one
of these great
professional books

for only **\$1.89**

values up
to \$62.50

Special \$1.89 premium book comes to you with your first club selection

Why YOU should join now!

- **BEST BOOKS IN YOUR FIELD**—Books are selected from a wide range of publishers by expert editors and consultants to give you continuing access to the latest books in your field.
- **BIG SAVINGS**—Build your library and save money too! We guarantee savings of at least 15% off publishers' list prices on every book. Usually 20%, 25% or even higher!
- **BONUS BOOKS**—You will *immediately* begin to participate in our Bonus Book Plan that allows you savings between 70-80% off the publisher's price of many books.
- **CONVENIENCE**—14 times a year you receive the Club Bulletin FREE, fully describing the Main Selection and alternate selections, together with a dated reply card. If you want the Main Selection, you simply do nothing—it will be shipped automatically. If you want an alternate selection—or no book at all—you simply indicate it on the regular reply card and return it by the date specified. You will have at least 10 days to decide. If, because of late mail delivery of the Bulletin you should receive a book you do not want, just return it at the Club's expense.

As a member, you agree only to the purchase of four books (including your first selection) over a two-year period.

MAIL THIS COUPON TODAY

Electronics and Control Engineers' Book Club
PO. Box 582, Hightstown, New Jersey 08520

Please enroll me as a member and send me the two books indicated, billing me for my first selection only at the discounted member's price, plus local tax, postage and handling. If not satisfied, I may return the books within 10 days and my membership will be canceled. I agree to purchase a minimum of 3 additional books during the next 2 years as outlined under the club plan described in this ad. Membership in the club is continuous but cancelable by me at any time after the four book purchase requirement has been fulfilled.

Write Code # of PREMIUM selection here Write Code # of FIRST selection here

Orders from outside the U.S. must be prepaid with international money orders in U.S. dollars.

Signature _____
Name _____
Address _____
City _____
State _____ Zip _____

This order subject to acceptance by McGraw-Hill. All prices subject to change without notice. Offer good only to new members. A postage and handling charge is added to all shipments. E33428

The Most Versatile and Effective Noise Reduction System Ever Produced

Now you can add a state of the art noise reduction system to your component stereo. In kit form, the NR-2* was featured in Radio Electronics (Aug-Sept '79). Len Feldman reported that "the execution of design is excellent" and "results are as good or better than claimed." Available now as a complete unit, this new component can virtually eliminate disturbing noise from all your record, tape or broadcast music.

MORE EFFECTIVE THAN DOLBY*

Significant 4dB improvement over the most respected system on the market today • NR-2* requires no encoding • Removes annoying tape hiss • Actually improves Dolby playback.

MORE VERSATILE THAN DBX* AND HI-COM*

NR-2 does not require specialized encoded discs • Allows total enjoyment of your present record library • Eliminates surface noise.

ENHANCED FREQUENCY RESPONSE

Exhibits a full 12-14 dB improvement S/N Ratio • Enjoy razor sharp highs and thundering lows with equal clarity.

AVAILABLE INDEPENDENTLY

NR-2 plugs right into any existing component stereo system • Makes updating your sound equipment simple and inexpensive.

*NR-2 is the Reg TM of National Semiconductor.
Dolby is the Reg TM of Dolby Laboratories, Inc.
DBX is the Reg TM of dbx, Incorporated.
HI-COM is the Reg TM of Nakamichi.



This extraordinary circuit will be built right into many 1981 OEM stereo systems. Why wait when the NR-2 can be yours now without the needless purchase of an entire receiver. You can immediately begin to enjoy the flawless music reproduction of the future, today!

Advanced Audio Systems, International
4040 Moorpark Ave., Suite 200
San Jose, CA 95117

Yes, I am ready to enjoy this state of the art NR-2 System. Enclosed is my check or money order for \$120.00 for each NR-2 ordered (includes shipping and handling).

If I am not thoroughly satisfied that NR-2 is the ultimate noise reduction system, I may return it within 14 days for a full refund.

Visa Master Charge

Exp. Date _____

Name _____

Address _____

City _____ State _____ Zip _____

CIRCLE 45 ON FREE INFORMATION CARD

COMMUNICATIONS CORNER

continued from page 86

CB mobile radio. And it is done at very little extra cost to the consumer because of LSI.

Figure 1 shows the complete Cobra package consisting of the hideaway *main* unit, that can be concealed easily under the dashboard or under the seat, and the plug-in microphone that contains a combination speaker/microphone and all operating controls. They include the channel selector, volume, and squelch controls, ANL on-off switch, RF gain-control switch, instant channel-9 selector switch, and push-to-talk switch. A two-digit LED indicator is the channel display.

The inside of the mike is shown in Fig. 2. Here we see how the magic is accomplished. The speaker, removed from the case so you can see all of the interior, also serves as the microphone. In addition to the miniature controls and switches along both edges of the microphone, there is a single LSI IC in the center. That IC is the key to full remote control operation.

The IC serves as both the driver for the LED channel indicator and the control for the phase-locked oscillator that is located in the *main* unit—no RF flows back and forth between the microphone and the *main* unit. Each time the channel selector is pushed, up or down to step the channel selector one channel at a time, the IC changes the LED display one channel (up or down). It also sends a coded DC signal to the phase-locked oscillator, that generates the operating frequencies corresponding to the indicated channel selection. The instant channel-9 switch, overrides the normal channel selection and forces the IC to transmit the proper DC control signals needed by the oscillator for channel-9 operation. Simultaneously, the IC changes the LED display to indicate a "9."

The microphone schematic is shown in Fig. 3. IC pins numbered 7 through 12 provide the control signal to the oscillator in the *main* unit. Just about everything else is self-explanatory. Simple? Yes? Low cost? Again, yes. Was this possible four or five years ago? Not with only two IC's in a moderately priced package it wasn't. The technology existed; but without LSI and the cost reduction inherent in the multi-million dollar CB marketplace you'd probably still be reading about "Future applications of the phase-locked oscillator," rather than holding it in the palm of your hand.

Temperature compensation in a frequency counter

TCXO means Temperature-Compensation

Hold everything!

Get a #324 PanaVise Work Center. Here's everything you need to hold everything you work with... in one money-saving package! Write for FREE catalog today.

PANA VISE®
2850 E. 29th St.,
Long Beach, CA 90806

Famous PanaVise standard base tilts, turns, rotates to exact work position.

6-compartment Tray Base Mount with 6 anti-slip feet.

Self-centering wire and Solder Holder* attaches to unit.

Adjustable Circuit Board Holder holds up to 10" board.

FREE 2 Nib Sponges with self-purging slits for easy cleaning.

Solder Iron Holder* with perfect angle for holding constant heat. Attaches to unit.

*Solder wire and solder iron not included.

CIRCLE 58 ON FREE INFORMATION CARD

sated Crystal Oscillator. To anyone even remotely involved with communications equipment it conjures up a vision of a crystal wrapped in a thermostatically controlled heating element to maintain the crystal temperature within very narrow limits to reduce, or eliminate, frequency drift. Virtually all broadcast and non-CB commercial communications transmitters (and some receivers) have a TCXO somewhere in the frequency generating or control chain. Most certainly, every lab-grade frequency counter and/or meter has a TCXO, and even an F.C.C.-approved frequency counter (for transmitter frequency tests) has a TCXO.

Now there's a hand-held 8-digit 50 to 500-MHz frequency counter that sells for only \$169.95 complete with a rechargeable battery pack and charger. It even has a telescopic antenna that can sense signals from hand-held walkie-talkies. Featuring 0.4-inch LED readouts, the unit, the *model 500HH* from DSI Instruments, also features a 1-PPM TCXO.

Since the unit is battery-powered, a logical question is: "How is the TCXO heater powered?" Actually, there's no heater. Nothing in TCXO means that there is a heater; it's simply been assumed that there was, because TCXO's always used a heater for temperature stabilization.

What DSI has done is to design their oscillator so it is within 1-PPM over a relatively narrow temperature range of 17° to 40°C, or 62.6° to 104°F. Just great for indoor use; but no 1 PPM is guaranteed when working on a vehicle or boat out in the cold, or in the hot sun. In a sense, the *500HH* is temperature-compensated for indoor use, but calling it TCXO is an unfortunate choice of words for a device that doesn't have a heated crystal. Unfortunate, because the *500HH* is an excellent device, well worth the money; yet many techs are obviously going to question the use of "TCXO" to describe an oscillator with an unheated crystal.

The *500HH* has two BNC inputs: one for the direct 50-MHz counter; the other through a $\times 10$ prescaler that provides a 500-MHz input. A switch selects either input. A second switch provides power *off* in the center position and a time base of 0.1 sec for MHz, and 1 sec for kHz. The switch automatically corrects the decimal point. To conserve the battery, because LED's eat up a lot of current, all leading zeroes are suppressed.

In actual field tests—indoors of course—the DSI *model 500HH* was within 10 Hz of an F.C.C.-approved frequency counter's reading at approximately 100 MHz. That's about as good an accuracy as you'll ever need for indoor frequency measurements when troubleshooting equipment.

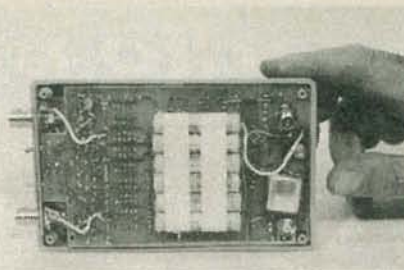


FIG. 4

The unit measures approximately 3-1/2" wide \times 5-7/8" long \times 1-3/16" thick; a nice size for a toolbox. The BNC connectors and switches are along the top edge. The charger/AC power connector is on the rear, as is an access hole to the

crystal's trimmer capacitor. You can take a look at the inside of the counter in Fig. 4.

Overall it's a very convenient and inexpensive frequency meter for the tech or hobbyist on a tight budget. It's simply unfortunate that the temperature range isn't clearly spelled out in °F, a more common reference than °C (at least in this country), and all mention of a non-heated TCXO should be eliminated; the instrument is simply too good for that kind of weasel-wording. Additional information on the *model 500HH* is available from DSI Instruments, Inc., 7924 Ronson Rd., San Diego, CA 92111. **R-E**


Electronics Paperback Book Club

Quality Paperbacks at Affordable Prices

Buy two, get one free!

Select the books you want or join the club now. Either way you earn a free book and can qualify for discounts of up to 20% for the next year.

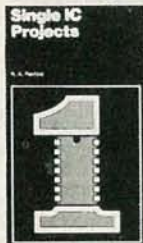Here are 5 great books to start your membership. Select the ones that you want to read.



SINGLE IC PROJECTS \$4.00

Twenty 1-IC circuits that are easy-to-build. Includes low-level audio, audio power amplifiers, timers, operational amplifiers and others. A perboard parts layout is given for each project.



PRACTICAL ELECTRONIC CALCULATIONS & FORMULAE \$5.75

A workshop manual for the electronics enthusiast. It bridges the gap between complicated technical theory and cut and try methods. The book is divided into six sections—Units and Constants; Direct Current Circuits; Passive Components; Alternating Current Circuits; Networks & Theorems; and Measurements.



BEGINNERS GUIDE TO MICRO-PROCESSORS & COMPUTING \$4.50

An introduction to the basic theory and concepts of binary arithmetic, microprocessor operation and machine language programming. The only prior knowledge that has been assumed is basic arithmetic.



ELECTRONIC SECURITY DEVICES \$3.75

A substantial part of the book is concerned with burglar alarms and switch-activated circuits; complete with construction details and perf-board layouts. Any electronic enthusiast should find these circuits easy to build and use.



IC 555 PROJECTS \$3.50

The 555 timer is one of the most useful ICs to come down the pike. Here's a book crammed with applications for it—basic and general circuits, automotive and model railroad circuits, alarms and noise makers plus a section on the 556, 558 and 559 timers.

ORDER FORM

I want to read your books! I've checked off the books I want, and how I want to buy them. Don't forget to include my **FREE** book.

CASH NOW

I've checked off three books that I want to buy. I've included payment for two of them at the full list price. I understand the third book is **FREE**.

\$15 for a 15% discount

I've checked off the book I want **FREE** and have included my \$15 membership fee. I understand that this fee makes me a member of your book club for one year and that during that time I can order as many books as I want and deduct 15% from the list price.

\$25 for a 20% discount

I've checked off the free book and have enclosed my \$25 membership fee. I understand that this fee makes me a member of your book club for one year and that during that time I can order as many books as I want and deduct 20% from the list price. I further understand that I can use my \$25 membership fee as a credit toward future purchases.

Signature _____

Name _____

Address _____

City _____

State _____

Quantity _____

Zip _____

Total Price _____

Title	Quantity	Total Price
<input type="checkbox"/> Single IC Projects \$4.00	_____	_____
<input type="checkbox"/> Practical Electronic Calculations \$5.75	_____	_____
<input type="checkbox"/> Beginners Guide to Microprocessors \$4.50	_____	_____
<input type="checkbox"/> Electronic Security Devices \$3.75	_____	_____
<input type="checkbox"/> IC 555 Projects \$3.50	_____	_____
<input type="checkbox"/> \$15/15% membership	_____	_____
<input type="checkbox"/> \$25/20% membership	_____	_____
Subtotal	_____	_____

MAIL TO: **ELECTRONIC TECHNOLOGY TODAY**

17 Slate Lane
Central Islip, NY 11722

Shipping (25¢ per book)

Sales Tax (NY State residents)

Total _____

No Canadian Orders

Catch the fastest C-meter under \$200 the autoranging B&K-PRECISION 830



Model 830 \$199
Model 820 \$140 (not shown)

B&K-PRECISION was the first company to offer a lab-quality capacitance meter for under \$150, now we're first with autoranging for under \$200. The new 830 is fast, accurate and built with famous B&K-PRECISION dependability.

The 830 offers features that are tough to match at any price, such as 0.1 pF resolution, large 3½-digit LCD display and fuse protection against charged capacitors. Basic accuracy is 0.2%, much greater than the tolerance of most capacitors. Measurement range extends to 199.9 mF.

Simplicity of operation is another strong suit for the 830. For checks limited to a narrow value range, the "range hold" capability can lock the 830 onto one range—an added time saver. This feature, along with its fast reading time, makes the 830 especially valuable for incoming inspection applications.

For applications suited to manual ranging, B&K-PRECISION offers the LED readout 820 at an even lower cost.

With either B&K-PRECISION C-meter you can, measure unmarked capacitors... verify capacitor tolerance... measure cable or switch capacitance... match capacitors for critical applications... measure complex capacitor networks... set trimmer capacitors.

For more information, contact your local distributor and see why B&K-PRECISION is now the leading supplier of digital capacitance meters.

BK PRECISION
DYNASCAN
CORPORATION

6460 West Cortland Street
Chicago, Illinois 60635 • 312/889-9087

Int'l. Sls., 6460 W. Cortland St., Chicago, IL 60635
Canadian Sales: Atlas Electronics, Ontario

CIRCLE 43 ON FREE INFORMATION CARD

radio products

More information on radio products is available. Use the Free Information Card inside the back cover.

RADIO DESKS, model TTY-36 and model TTY-48, are designed for RTTY and computer enthusiasts and will accommodate a complete RTTY station including HF and VHF transceivers, terminal units, and accessories. This easy-to-assemble



CIRCLE 111 ON FREE INFORMATION CARD

desk is made of plywood, has steel legs, and can hold over 200 lbs. Bolts, fasteners, and a wrench are provided. Choice of walnut, teak-stain, or unfinished. Model TTY-36 measures 39" X 30" X 50"; TTY-48 measures 51" X 30" X 50". TTY-36 is priced at \$179.95; TTY-48 is \$199.95. —S-F Amateur Radio Services, 4384 Keystone Ave., Culver City, CA 90230.

CONCEALED-CHASSIS MOBILE CB model 14T276, has all the operating controls located on the microphone. The operating controls include a 40-channel LED readout, electronic channel selector, channel-lock switch, Channel-9 emergen-



CIRCLE 112 ON FREE INFORMATION CARD

cy switch, ANL switch, squelch control and transmit/receive indicator light—all located on the mike. The chassis itself may be mounted behind the dash or under the front seat, or, with an optional 18-foot extension cable, in the trunk of the vehicle. Price is \$207.50. —RCA Distributor & Special Products Division, 2000 Clements Bridge Rd., Deptford, NJ 08096.


DIGITAL SCANNER, the Touch M100, is a fully-synthesized, 10-channel unit for home and mobile use. Its frequency ranges include the low, ama-



CIRCLE 113 ON FREE INFORMATION CARD

teur, and high VHF bands, and UHF band from 440 MHz to 512 MHz. Features include a search mode that can sample an entire bandwidth for calls, channel-one priority, full-function digital display, scan-and-search delay, and a brightness switch for day or night use. Scanning rate is 15 channels per second. The M100 is programmed, and entries made, by means of a backlit, color-coded, pressure-sensitive pad. Price is \$399.95. —Regency Electronics, Inc., 7707 Records St., Indianapolis, IN 46226.

SUPER-FLEXIBLE, HIGH-PERFORMANCE CB antenna, called *The Skinny Stick*, is a 48-inch whip ¼-inch in diameter that can be bent 360° without breaking. Available in black or white, the antenna uses a unique foil band for precision tuning and is retunable. The top-loaded coil provides extra gain on transmit and receive. *The Skinny Stick* fits standard ¼-24 thread-mounts. Power capacity is 150 watts (250 co-phased) and SWR is

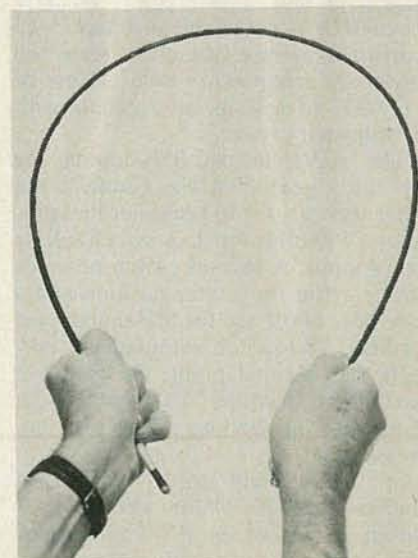

CIRCLE 114 ON FREE INFORMATION CARD

1.5:1 or better. Price is \$12.95. Avanti Research and Development, Inc., 340 Stewart Avenue, Addison, IL 60101. **R-E**

A LIFETIME GUARANTEE AND 11 OTHER REASONS TO BUY AN "OPTOELECTRONICS" FREQUENCY COUNTER

1. SENSITIVITY: Superb amplifier circuitry with performance that can't be matched at twice the price. Average sensitivity of better than 15 mV from 10 Hz to 500 MHz on every model and better than 30 mV from 500 MHz to 1.1 GHz on the Series 8010A and 8013.

2. RESOLUTION: 0.1 Hz to 12 MHz, 1 Hz to 50 MHz, 10 Hz over 50 MHz.

3. ALL METAL CASES: Not only are the heavy gauge aluminum cases rugged and attractive, they provide the RF shielding and minimize RFI so necessary in many user environments.

4. EXTERNAL CLOCK INPUT/OUTPUT: Standard on the 8010/8013 series and optional on the 7010 series is a buffered 10 MHz clock time base input/output port on the rear panel.

Numerous uses include phase comparison of counter time base with WWVB (U.S. National Bureau of Standards). Standardize calibration of all counters at a facility with a common 10 MHz external clock signal, calibrate scopes and other test equipment with the output from precision time base in counter, etc., etc.

5. ACCURACY: A choice of precision to ultra precision time base oscillators. Our ± 1 PPM TCXO (temperature compensated xtal oscillator) and ± 0.1 PPM TCXO are sealed units tested over 20-40°C. They contain voltage regulation circuitry for immunity to power variations in main instrument power supply, a 10 turn (50 PPM) calibration adjustment for easy, accurate setability and a heavily buffered output prevents circuit loads from affecting oscillator. Available in the 8010 and 8013 series is our new ultra precision micro power proportional oven oscillator. With $\pm .05$ PPM typical stability over 10-45°C, this new time base incorporates all of the advantages of our TCXO's and virtually none of the disadvantages of the traditional ovenized oscillator; Requires less than 4 minutes warm-up time, small physical size and has a peak current drain of less than 100 ma.

6. RAPID DISPLAY UPDATE: Internal housekeeping functions require only .2 seconds between any gate or sample time

period. At a 1 second gate time the counter will display a new count every 1.2 seconds, on a 10 second gate time a new count is displayed every 10.2 seconds. (10.2 seconds is the maximum time required between display updates for any resolution on any model listed).

7. PORTABILITY: All models are delivered with a 115 VAC adapter, a 12 VDC cord with plug and may be equipped with an optional ni-cad rechargeable battery pack installed within its case. The optional Ni-Cad pack may be recharged with 12 VDC or the AC adapter provided.

8. COMPACT SIZES: State-of-the-Art circuitry and external AC adapters allowed design of compact easy to use and transport instruments.

Series 8010/8013: 3" H x 7-1/2" W x 6-1/2" D

Series 7010: 1-3/4" H x 4-1/4" W x 5-1/4" D

9. MADE IN U.S.A.: All models are designed and manufactured at our modern 13,000 square foot facility at Ft. Lauderdale, Florida.

10. CERTIFIED CALIBRATION: All models meet FCC specs for frequency measurement and provided with each model is a certificate of NBS traceable calibration.

11. LIFE TIME GUARANTEE: Using the latest State-of-the-Art LSI circuitry, parts count is kept to a minimum and internal case temperature is only a few degrees above ambient resulting in long component life and reliable operation. (No custom IC's are used.) To demonstrate our confidence in these designs, all parts (excluding batteries) and service labor are 100% guaranteed for life to the original purchaser. (Transportation expense not covered).

12. PRICE: Whether you choose a series 7010 600 MHz counter or a series 8013 1.3 GHz instrument it will compete at twice its price for comparable quality and performance.

MODEL 8010A/8013 1.1 GHz/1.3 GHz



MODEL 7010A 600 MHz

MODEL	RANGE (From 10 Hz)	10 MHz TIME BASE			AVG. SENSITIVITY		GATE TIMES	RESOLUTION			EXT. CLOCK INPUT/OUTPUT	SENSITIVITY CONTROL	NI-CAD BATTERY PACK
		STABILITY	AGING	DESIGN	10 Hz to 500 MHz	500 MHz to 1.1 GHz		12 MHz	60 MHz	Max. Freq.			
7010A	600 MHz	± 1 PPM	<1 PPM/YR	TCXO*	15 mV	N/A	(3) 1, 1, 10 sec	1 Hz	1 Hz	10 Hz (600 MHz)	YES OPTIONAL	NO	YES OPTIONAL
8010A	1.1 GHz	± 1 PPM	<1 PPM/YR	TCXO*	15 mV	30 mV	(4) 01, 1, 1, 10 sec	1 Hz	1 Hz	10 Hz (1.1 GHz)	YES STANDARD	YES	YES OPTIONAL
8010.1A	1.1 GHz	± 0.1 PPM	<1 PPM/YR	TCXO*	15 mV	30 mV	(4) 01, 1, 1, 10 sec	1 Hz	1 Hz	10 Hz (1.1 GHz)	YES STANDARD	YES	YES OPTIONAL
8010.05A	1.1 GHz	± 0.05 PPM	<1 PPM/YR	OCXO**	15 mV	30 mV	(4) 01, 1, 1, 10 sec	1 Hz	1 Hz	10 Hz (1.1 GHz)	YES STANDARD	YES	YES OPTIONAL
8013.1	1.3 GHz	± 0.1 PPM	<1 PPM/YR	TCXO*	15 mV	30 mV	(4) 01, 1, 1, 10 sec	1 Hz	1 Hz	10 Hz (1.3 GHz)	YES STANDARD	YES	YES OPTIONAL
8013.05	1.3 GHz	± 0.05 PPM	<1 PPM/YR	OCXO**	15 mV	30 mV	(4) 01, 1, 1, 10 sec	1 Hz	1 Hz	10 Hz (1.3 GHz)	YES STANDARD	YES	YES OPTIONAL

*TCXO = Temperature Compensated Xtal Oscillator.

**OCXO = Proportional Oven Controlled Xtal Oscillator.

SERIES 7010A	
7010A	600 MHz Counter - 1 PPM TCXO \$199.95
7010.1A	600 MHz Counter - 0.1 PPM TCXO \$249.95
OPTION:	
0-H	Handle/Tilt Bail (not shown) \$2.95
1-Cad-701	Ni-Cad Battery Pack & Charging Circuitry Installed Inside Unit \$19.95
C-70	External Clock Input/Output \$35.00
C-70	Carry Case - Padded Black Vinyl \$9.95

SERIES 8010A/8013	
#8010A	1.1 GHz Counter - 1 PPM TCXO \$399.00
#8010.1A	1.1 GHz Counter - 0.1 PPM TCXO \$450.00
#8010.05A	1.3 GHz Counter - .05 PPM Oven \$499.00
#8013.1	1.3 GHz Counter - 0.1 PPM TCXO \$550.00
#8013.05	1.3 GHz Counter - .05 PPM Oven \$599.00

OPTIONS	
#Ni-Cad-801	Ni-Cad Battery Pack & Charging Circuitry Installed Inside Unit \$49.95
#CC-80	Carry Case - Padded Black Vinyl \$ 9.95

ACCESSORIES	
#TA-100	Telescope antenna with right angle BNC \$ 9.95
#P-100	Probe, 50 Ohm, 1X \$13.95
#P-101	Probe, Lo-Pass Audio Usage \$16.95
#P-102	Probe, Hi-Z General Purpose \$16.95
#LFM:1110	Low Frequency Multiplier X 10, X 100, X 1000 For High Resolution of Audio Freq. \$119.95



Optoelectronics inc

5821 N.E. 14th Avenue, Fort Lauderdale, Florida 33334

1-800-327-5912

FROM FLORIDA (305) 771-2051/2

TERMS: Orders to U.S. and Canada, add 5% for shipping, handling and insurance to a maximum of \$10.00. All other orders add 15% O.D. collection fee \$2.00. Florida orders add 4% state tax. Personal checks must clear before goods are shipped.

CIRCLE 4 ON FREE INFORMATION CARD



ELECTRONICS

A DIVISION
OF ALLIANCE
RESEARCH CORPORATION

7241 CANBY AVE. • RESEDA, CALIFORNIA 91335

The Professional's Choice

Test equipment, prime grade original replacements, chemicals, tape heads . . . and MORE!



We feature only quality test equipment: Leader Instruments, Hitachi, Beckman, Hickok, and others.



Leader LB0515B



Hitachi V-302



Beckman 330



Hickok LX 304

SPECIAL OFFER

A top quality 30 Mhz, dual trace, triggered oscilloscope with 1 mV sensitivity and delay line.

FOR UNDER \$800.00! (including 2 probes)

Limited to professional technicians, engineers, and members of the trade. Call in for details and complete specifications.

SHIPPED THE SAME DAY • SHIPPED THE SAME DAY

SENDUST ALLOY HEADS

Metal tape compatible!

Standard configuration stereo.

\$13.50

Longer life.

Best frequency response.



AS-2



AS-3

SENDUST ALLOY
AUTO REVERSE
HEADS

\$20.00 ea.

TAPE HEADS

PERMALLOY HEADS
Cassette stereo

\$4.50



WY032



WY435



WY488

WY802

WY822RP

E721

PERMALLOY
AUTO REVERSE
HEADS

\$7.00

HIGH QUALITY TEST CASSETTES



- PTC 1 Level Test (-10 dB)
- PTC 2 S/N Ratio (0 dB)
- PTC 3 Speed Test (3000 Hz)
- PTC 4 Head Alignment
- PTC 5 Frequency Response
- CT 120 Torque Meter

ORIGINAL JAPANESE REPLACEMENT PARTS IN STOCK!

I.C.s — Prime Grade

These prices are for 1-11 qty!
Call for better price quotes.

AN 306	VCR Chroma	12.00
AN 318	VCR Servo	9.00
AN 7130	Power Amp.	3.00
AN 7150	Power Amp.	3.25
AN 7156N	BTL Amp.	4.00
BA 1310	PLL Demod.	3.50
BA 1320	PLL MPX Demod.	3.50
DA 101	Delco DM98	7.00
HA1366W	Power Amp	2.80
HA1368	Power Amp	2.80
HA1377A	20 Watts Amp	4.90
HA1457	L.N. Preamp	1.80
LA1368	Chroma Processor	3.50
LA1460	Deflection CKT	4.50
LA3155	Equalizer	1.80
LA3160	Preamp	1.60
LA3201	Mini Preamp	1.50
LA4032P	3W Amp	2.25
LA4051P	2.5W Amp	2.50
LA4420	5.5W Amp	2.50
LA4430	4.5W Amp	2.85
LA5110	Regulator	2.00
LB1331	VIR Sig. Processor	6.50
M53273	VCO for CB	1.00
MB3705	4.5W Amp	3.00
MB3712	5.0W Amp	3.85
MB3756	SIL Regulator	3.50
MB8719	Programmable PLL	7.50
S-40W	40W Amp	13.90
S-60W	60W Amp	17.90
S-100WA	100W Amp	27.90
S-200W	200W Amp	45.25
SM5104	PLL Circuit	9.00
STK0029	Darlington HYB	6.00
STK0039	Darlington HYB	7.10
STK0050	Darlington HYB	8.90
STK011	Hybrid 6.5W Amp	4.50
STK013	Hybrid 15W Amp	13.50

I.C.s — Prime Grade

Continued

STK040	Dual 10W Amp	12.00
STK415	2 Ch. Hybrid Amp	9.00
TA7109AP	Amplifier	5.00
TA7205AP	BTL Amp	2.50
TA7217AP	5.8W 4 ohms amp	4.25
TA7222P	5.8W Amp	3.80
TA7227P	BTL Amp	7.00
TA7312P	L.N. Preamp	2.00
TC9106P	C.B. PLL	7.00
UPC671C	Amp	5.00
UPC1181H	BTL Amp	3.50
UPD857C	Ham PLL	7.80
UPD858C	C.B. PLL	6.50
UPD2815	Freq. Synth.	12.50
UPD2816	Freq. Synth.	12.50

TRANSISTORS

— Prime Grade

These prices are for 1-11 qty!

2SA509	50
2SA606	1.45
2SA684	.60
2SA699A	.80
2SA912	.80
2SA912	.80
2SA917	1.80
2SA981	8.00
2SB471	2.00
2SB507	1.50
2SB555	4.60
2SB618	3.00
2SB681	5.75
2SB688	3.30
2SB700	4.00
2SB754	3.75
2SC281	.60
2SC937	8.50
2SC1111	5.20
2SC1209	1.50
2SC1964	3.00
2SC1942	4.50
2SC2001	.50
2SC2086	.60
2SC2101A	11.95
2SC2103A	15.00
2SC2166	2.00
2SD91	1.90
2SD425	3.50
2SD588	3.00
2SD712	1.20
2SD725	6.50
2SD870	7.50
2SD870	7.50
2SD903	6.50
MRF454	22.00
MRF455	15.95
MRF901	3.20

PLUS MANY MORE!

"Our Service Makes The Difference"

Free Catalog to the Trade.
All Others \$1.00 ea.

AIR CORE INDUCTOR

(for crossover network)

20 AWG Wire!

.28 mH	1.60
.5 mH	1.86
1.0 mH	2.75
1.8 mH	3.36
2.5 mH	4.35

CRYSTALS

1-11 **\$3.50 ea.**
12-up **\$3.00 ea.**
20 pF Load Impedance!

7.0025 MHZ	11.3258 MHZ
7.7975 MHZ	11.2850 MHZ
10.240 MHZ	11.2842 MHZ
10.695 MHZ	11.240 MHZ
11.1125 MHZ	11.730 MHZ
11.2858 MHZ	36.570 MHZ

Build your own speaker system!

CROSS OVER NETWORKS



4 ohms or 8 ohms — Made with AIR CORE COILS or FERRITE CORE. Many to choose from. Example: NT406H crossover network: 100 watts input! 3 way, all air core construction for lowest distortion.

ONLY **\$9.00 ea.**

NON POLARIZED ELECTROLYTIC CAPACITORS

For crossover use (axial lead)



uF/V	1-11	uF/V	1-11
1/100	.50	14/100	.60
2.2/100	.50	16/100	.65
3.3/100	.55	22/100	.70
4.7/100	.55	33/100	.95
6.8/100	.55	47/100	1.20
8.0/100	.60	100/100	1.65
10/100	.60	150/100	2.55
12/100	.60	200/100	3.00

We sell exclusively to professionals and members of the trade. Minimum order \$25.00. We pay shipping and insurance on pre-paid orders in the continental U.S.A. C.O.D. orders, VISA/MasterCard welcome!

TO ORDER, CALL TOLL-FREE:
(800) 423-5336 • In Calif. (800) 382-3663
Local (213) 705-0022 • Telex 181011

Are YOU prepared for the ELECTRONIC EIGHTIES ...

... the decade that promises exciting advances in a still-young field?

Not many are. But you could be ... through ETI's advanced home study training methods. It's not an easy field but we make it easier to learn ... and easier on your bank account, too. We're a small school but we're BIG on service and our staff is dedicated to helping you IF you're ambitious, qualified and eager to learn.

Select from our basic courses, career programs or advanced courses. Mix and match to fit your needs and goals.

Send TODAY for our FREE catalog or for faster service, use the toll free telephone number below, day or night.



CALL FREE DAY OR NITE
1 800 621 5809
FROM ILLINOIS 800 972 5858



ETI
ELECTRONICS TECHNICAL INSTITUTE
Dept. 20090
153 West Mulberry St.
Lancaster, Ohio 43130
Ohio License
0683H

ETI Home Study, Dept. 20090
153 West Mulberry
Lancaster, Ohio 43130

Please rush FREE catalog on electronics opportunities and training. I'm interested in:

Basic Career Specialized
 Advanced

Name _____

Address _____

City/State/Zip _____

SERVICE CLINIC
continued from page 96

service questions

HOT SCREEN RESISTOR

I've got an odd problem. The damper tube in this J.C. Penney 4849A got red hot and burned out. While making voltage checks with it out, R904, 220 ohms got very hot. (Note: That is the horizontal output tube screen resistor.) What is the cause?—V.F., Nebraska City, NE.

Crystal ball says that damper tube could have shorted internally; or, the 6GK6 horizontal output tube is shorted. The hot resistor in the screen is *normal!* If you pull the damper tube, you have no plate voltage on the output tube. The screen grid, being the only element supplied with voltage, thinks it's the plate and tries to conduct all the current. In some sets, I've seen that tube looking like a toaster! The screen grid gets red hot!

Current meter in cathode of 6GK6 will tell you whether that stage is taking too much current. With the damper tube out, all current in that stage must flow through the 6GK6 cathode.

ROLL CHARTS FOR TUBE TESTERS

On a question as to availability of new roll-charts for tube testers, I replied, truthfully, that I'd been looking for years and never located a reliable source. John E. Johnson of Thomasville, GA, comes back with this little jewel:

Coletronics Service Inc., 1744 Rockaway Ave., Hewlett, NY 11557, has new charts for Precision Tube-Master Series 10-12, for \$8.95 plus 50¢ shipping. The Hickok Electrical Instrument Co. advised him that for charts for an old TV-7 B/U, to contact: U.S. Navy Supplies, 5801 Tabor Ave., Philadelphia, PA 19120. We pass that along for anyone who might have one of these instruments. Thanks, John.

FOCUS PROBLEM

I'm having a focus problem with an RCA CTC-22. The damper diode was shorted. Changing that restored high voltage but not focus.—L.N., Philadelphia, PA.

I suggest checking all the loads, etc. Since the focus voltage in that chassis comes from the boost voltage, check all of the capacitors around the horizontal efficiency coil and the coil itself.

(Feedback: "I tried those things. The horizontal efficiency coil was shorted! Thanks!")

ODD RASTER DISTORTION

Al Yarborough of Yarborough Electronics, Lexington, NC, sends this along: "Here's field feedback for you. This

Toshiba C-095 had a peculiar raster distortion. The upper left hand corner was expanded diagonally. Blooming was present in that area, too. Not due to high-voltage regulation, either.

"You suggested checking for feedback. In a way, that's what it was! A 100 μ F capacitor in the pincushion stage apparently had a high power factor. It checked OK on an ohmmeter. A capacitor tester showed it as less than 50 μ F. Replacing that fixed it.

"Last question: Years ago, they told us that transistors would do away with intermittents. When are they going to start making those perfect devices?"

Thanks, Al. To your last question, I've been wondering for many years!

HOT RESISTOR

In this GE 25MB chassis, the breaker tripped. I pulled the high-voltage module and that cleared it up. A new module didn't help. Resistor R1318 was high and showed signs of heating. I changed it and the new one overheats. All other modules were checked. What's going on here?—C.C., Amityville, NI.

Resistor R1318 is a series resistor in what seems to be a crowbar circuit in the high-voltage regulator module. It's connected from the +170V line through Q1304, an SCR, to ground. The SCR gate is triggered by sensing the +150-volt regulated DC output. That circuit uses a series Zener diode, and a couple of others. Check the SCR and if it's not shorted, check the trigger diode and others. Something seems to be firing the SCR!

WIGGLE IN SETUP LINE

This Sylvania D-12 had several wrinkles in the left end of the setup lines in with the service switch in the service position. Couldn't think of any reason for it. You suggested it might be something in the deflection yoke. This was a new Thor-darson. Turned out that it had a 680 pF capacitor on the top half of the horizontal winding. Replacing that with 100 pF corrected the wiggle and the other problems. Thanks for the aid. William J. Shinn, New Carlisle, OH.

Thanks to you Mr. Shinn! Definite feedback from the field is a huge help to everyone.

GASSY TUBE?

I replaced the horizontal output and damper tube in this Zenith 12B14C50. Works beautifully. However after about 15 minutes of operation, I see little blue flashes around the bottom of the horizontal output tube. Tried a new one and got same thing. Is that tube gassy?—R.O., Daly City, CA.

This is a very old problem showing up in a new set! There are two things that can cause "blue glow" inside of tubes with high voltages applied. One, of course, is "gas," meaning just a wee bit or

air leakage. The typical symptom of that is a soft cloudy blue glow but looking closely, you'll see that it is *inside* the plate cylinder or rectangle.

A similar thing that's fooled lots of us is really quite different. Check your tube; see if those blue flashes are *actually* on the inside wall of the bulb! See if it flickers too. That is just the opposite of gas: It's called fluorescence and is due to a wee bit of the getter material on the walls. That lights up under a high voltage field, means a very *hard* vacuum!

ODD PROBLEMS

First thing on this Zenith 19CC19 was no red. Changed the IC demodulator and fixed that. Now I've got a weird symptom: good picture in the center of the screen but both sides are bowed in; that area is blank. Controls all work. What is it?—J.V., Punxsutawney, PA.

It sounds to me that you're getting some 60-Hz sinewave blanking into the video. Just for luck, scope the DC power supplies, especially the +25 and +34 volt outputs. I see that the +25 volts come directly from the vertical centering control and the B+. There would normally be a 60-Hz pulse here and it should be filtered out by the 500- μ F electrolytic on this line. Check that one.

LOW VOLTAGES AND VERTICAL PROBLEMS

In this 16M91 Philco, several of the voltages are low and the boost voltage fluctuates quite a lot. Can't get a setup line with the service switch in the service position. Vertical linearity control arcs, too. What are all those?—C.G., Derry, NH.

Easy one first: If your boost voltage is low, chances are your picture tube screens are, too. That could be why no setup lines. Replace that vertical linearity control if it's arcing internally.

For the rest of the problems, that could be something that is common to the whole circuit! In other words, one of the filter capacitors. (From looking at the schematic, it is suspiciously like my own old CTC-15 RCA! So, if I say "filter capacitors", I know whereof I speak. I've been there. Check all of those ground points on the PC board, too.)

Feedback: It was the electrolytic capacitor on the +275-volt line! Bingo.

LOW-VOLTAGE PROBLEM

There are no low voltages from the flyback in this Sears 528. 42000400. No +27.2 volts DC or +28.8 volts at all. The diode, D504, seems to be good. I see a high pulse on the flyback side (anode) but none on the cathode, and no DC voltage. The high-voltage, boost, etc., are very close to normal. Thanks for any help.—G.P., Silver Spring, MD.

You should see pulses on the anode of D504, but you should not see any at all on the cathode. There is a 1,000 μ F capacitor to ground here! From your symptoms, the

only thing I can see is an open diode! If the pulse is present and no DC voltage is developed, the diodes may be open, or the 1,000 μ F capacitor shorted. Your flyback pulse output seems to be normal, since all of the other voltages are in the ballpark. Be sure to use a fast-recovery type diode for D504. Ordinary sinewave types won't last more than 30 seconds!

A DISCO-PICTURE

This J.C. Penney model 2868 came in with an odd symptom. The picture brightness varied like a strobe light in a disco. Also, no color and a small raster. Scoping the DC supply showed a sawtooth of almost 80 volts! After quite a bit of checking, C807 was found open. (Note: That is a 1.0 μ F capacitor, on the base of clipper TR802, from the collector of the sawtooth generator TR801. Part of saw-forming network, on the regulator board.)

That caused the regulator to hunt, and almost go into oscillation. Replacing it cleared up the problem.

Thanks to Dean Carpenter, N5AFT, in Garland, TX, for that helpful hint.

PIEZOELECTRIC

continued from page 60

LED's can be checked easily using the CONTINUITY mode of the tester because the LED will glow when properly connected (correct polarity). When the test leads to the LED are reversed, there will be no sound because the LED is open in that direction. In the same manner, you can test infrared (IR) LED's even though you cannot see the IR LED glow. If you get a sound in both directions, the LED is shorted (the same as for a shorted diode). Sound in one direction shows that the LED or diode is conducting in the forward direction (front-to-back) and no sound in the opposite direction (no conduction) shows that the back-to-front ratio is good.

Voltage Tester—Voltage-level tests can be made by using the piezoelectric sounder in its basic mode, where 1 to 20 volts DC is applied to its terminals. It can be used safely in transistor and TTL circuits, automobile trouble-shooting, checking the general condition of batteries, including watch and calculator batteries, because of its low current drain. It is handy for testing in any circuit where you want a general indication of correct circuit activity and where you use the ear instead of the eye to tell you this condition. Piezoelectric sounder and audio alerting devices are more and more coming into our lives advising us of conditions in the environment surrounding us. May they always beep or sound in your favor!

R-E

BIG 2 1/2" DISPLAY 12:59:46

SOLID STATE CLOCK/CALENDAR KIT

0101 Displays time of day, date or alternates between both automatically. May be connected to 8 ohm speaker for alarm clock. Operates from 120 VAC 60 Hz.

\$49.95 Oak case extra, \$29.95

UNIVERSAL DESIGNER KIT 6100

Indispensable aid to digital IC design. 2 pushbuttons, 2 readouts, 4 switch outputs, 8 LEDs, 2 generators, 2 counters, 5V supply pins.

Breadboard extra. \$59.95 assembled

6101 Digital Logic Course \$29.95

ASK FOR OUR FREE 8-PAGE CATALOG



14905 N.E. 40th, Redmond, WA 98052 (206) 883-9200

- 0101 SOLID STATE CLOCK CALENDAR KIT \$ 49.95
 - 0101 OAK CASE FOR ABOVE 29.95
 - 6100 UNIVERSAL DESIGNER KIT 49.95
 - 6100 ASSEMBLED DESIGNER KIT 59.95
 - QT 59S BREADBOARD 11.00
 - QT 59B BREADBOARD 2.50
 - 6101 DIGITAL LOGIC COURSE 29.95
- ADD \$2.50 PER ORDER POSTAGE AND HANDLING

NAME _____ R-9

ADDRESS _____

CITY, ST, ZIP _____

CARD NO. _____ VISA MSTR CHG

SIGNATURE _____

CIRCLE 25 ON FREE INFORMATION CARD

Why give away \$8,000?

Because...

That's just about how much you pay for a new car nowadays...so why let someone steal it from you! Protect that investment with Gard-A-Car... Within 8 seconds after anyone manages to start your car Gard-A-Car stalls the engine "dead". The thief can't restore it and must flee or be caught! A timed circuit breaker in the unit cuts the power. The control box is operated by flipping the switch "on" when you leave the car and "off" when you return. Easily hidden wherever you want - no holes to drill - only 2 wires to connect. There is no interference with normal car operation. Designed for any ignition system.

And there's more! When you send in your order with the coupon below you save \$2.00 off our regular catalog price of \$21.95 and you will also receive a free copy of our nationally famous 68-page full color security system catalog with over 1,400 items!!

Now Only \$19.95!!

And we pay shipping!



Mail to: Mountain West
4215A N.16th St., Phoenix, AZ 85016

Yes, I want to protect my car from theft please rush me your Gard-A-Car unit. I have enclosed my check for \$19.95 and you will pay shipping. I understand that I will also receive your 68-page full color catalog, absolutely free!

Name _____

Address _____

City _____ State _____ Zip _____

Offer expires 8/31/81

CIRCLE 23 ON FREE INFORMATION CARD

Discone™ Model DCX

MAKE YOUR SCANNER REALLY PERFORM!

...with Hustler multi-band monitor antennas.

Whether it's mobile or base, Hustler has the antenna that provides exceptional scanner performance, resulting from advanced engineering and use of quality materials.

If you want real performance... get Hustler!

Clearly the choice of those who know quality.

See your dealer or write:

HUSTLER INC.

3275 North B. Ave. Kissimmee, Florida 32741

MOM Magnetic Mount

CIRCLE 24 ON FREE INFORMATION CARD

DIGITAL RESISTANCE & CAPACITANCE SUBSTITUTERS



TRULY "HUMAN ENGINEERED" AND ERROR PROOF

RS-200 R-box: 1Ω to 9,999,999Ω; 1% 0.5 watt. ONLY \$89.85
 RS-201: 0.1%. \$179.95
 CS-300 C-box: 100pF to 99,999 μF; 4%, 100 volts. ONLY \$99.95
 CS-301: 1%. \$198.95
 RCS-500 RC-box: Combination unit. ONLY \$185.95
 RCS-502: Combines RS-201 & CS-301. \$369.95

Simply dial the desired impedance or RC value on color coded switches and use.

IET LABS, INC. 761 Old Country Road
 Westbury, N.Y. 11590
 (516) 334-5959

CIRCLE 46 ON FREE INFORMATION CARD

stereo products

More information on stereo products is available. Use the Free Information Card inside the back cover.


AM/FM RECEIVER, model R6, is one of a line of new receivers that feature quartz-locked tuning with digital readout for precise RF reception and a four-function fluorescent metering system. This system gives an accurate readout of AM signal strength, FM signal strength, multipath, and pow-



CIRCLE 131 ON FREE INFORMATION CARD

er output. Other features are a low-noise circuit for increased stability with low distortion, a high-speed amplifier section, and external jacks for signal or tape accessories. *Model R6* produces 60 watts-per-channel into 8 ohms, from 20 Hz to 20,000 Hz with 0.05% THD. Suggested retail price is \$650.—**SAE, Inc.**, 701 E. Macy St., Los Angeles, CA 90012.

SPEAKERS, Mitsubishi model MS-20 and model MS-10, are two-way acoustic air-suspension units that use a unique honeycomb technology in the woofer. The woofers are built of rigid, lightweight aluminum honeycomb material covered with glass-reinforced plastic, thereby reducing distortion caused by unwanted vibration. The system improves low-frequency performance and the airtight seal made from the honeycomb material improves air-suspension performance.

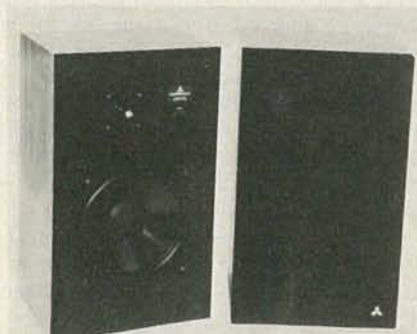

CIRCLE 132 ON FREE INFORMATION CARD

Other features are overload protection circuits and tweeter structures that reduce reverberation. The *MS-20* (shown) can handle power up to 120 watts; *MS-10* up to 100 watts. *Model MS-20* weighs 40 lbs. and measures 14" × 24" × 11" inches. Suggested retail price is \$250. *Model MS-10* weighs 32 lbs., and measures 12" × 22" × 11" inches. Suggested retail price is \$165.—**Melco Sales, Inc.**, 3030 E. Victoria St., Compton, CA 90221.

COMPACT DIRECT-DRIVE TURNTABLE, model SL-10, is a compact quartz unit measuring the same as an LP record jacket. Everything is automatic and the upper and lower halves of the cabinet are sealed during play. To use the *SL-10*, the



CIRCLE 133 ON FREE INFORMATION CARD

user places a record on the turntable, closes the lid to seal it, and presses the start button. The turntable then takes over, determining stylus contact points and the beginning and end of play. With a gimbal suspension and a dynamically balanced tracking arm, the unit can be used in the normal flat position or can be stood upright during record play. A coreless DC motor drives the arm and an optical sensor near stylus tip determines operation. Car battery or any 12V DC power supply can be used, as well as standard AC. Price is \$600.—**Technics**, One Panasonic Way, Secaucus, NJ 07094.

AMPLIFIERS, Model KAC-801 and KAC-727, are two high-power amplifiers designed for car stereo systems. *Model KAC-801* (shown) delivers 50 watts-per-channel into 4 ohms over a range of 20 to 60,000 Hz at 1% total harmonic distortion. Other specifications include a signal-to-noise ratio of 80 dB and a frequency response of 20 to 70,000 Hz. The unit has a built-in DC/DC converter to create the high voltage required to supply the output stages and has an electronic fault-protection circuit to prevent wiring shorts or overloads. Measuring 11" × 2" × 6" inches, the amplifier is designed for trunk installation but can also mount under a car seat.



CIRCLE 134 ON FREE INFORMATION CARD

The *model KAC-727* is an under-dash model that delivers 15 watts-per-channel into 4 ohms from 20 to 50,000 Hz at 1% THD. It also features built-in circuit and speaker protection and uses IC's to minimize load distortion at high power ratings. The amplifier measures 6" × 2" × 6" inches. *Model KAC-801* is priced at \$219; *Model KAC-727* is priced at \$95.—**Kenwood Electronics, Inc.**, Dept. P, 1315 E. Watsoncenter Rd., Carson, CA 90745.

R-E

Sinclair Multimeters

Repeatable Quality at Unrepeatable Prices!
Take advantage of this super special offer of professional quality DMMs.



PDM35


\$39.95

Hand-held 3 1/2 digit LED Multimeter
1% basic DCV Accuracy
16 ranges: DC/AC Volts, DC Current, Ohms.
Resolution 1mV / 0.1nA / 1ohm
Ranges to 1000V / 100mA / 10M
Battery operated (PP3) or AC Adaptor
Complete with test leads and carrying pouch

DM235

Bench/Portable 3 1/2 digit LED Multimeter
0.5% basic DCV Accuracy
21 ranges: DC and AC Volts and Current, Ohms
Resolution 1mV / 1µA / 1ohm
Ranges to 1000V / 1A / 20M
Battery operated (4 'C' cells) or AC Adaptor
Complete with test leads

\$69.95

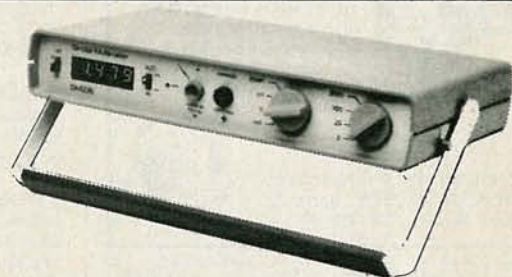

DM350


\$99.95

Bench/Portable 3 1/2 digit LED Multimeter
0.1% basic DCV Accuracy
34 ranges: DC and AC Volts and Current, Ohms
Resolution 100µV / 1nA / 0.1ohms
Ranges to 1200V / 10A / 20M
Battery operated (4 'C' cells) or AC Adaptor
Complete with test leads

DM450

Bench/Portable 4 1/2 digit LED Multimeter
0.05% basic DCV Accuracy
34 ranges: DC and AC Volts and Current, Ohms
Resolution 10µV / 0.1nA / 0.01 ohms
Ranges to 1200V / 10A / 20M
Battery operated (4 'C' cells) or AC Adaptor
Complete with test leads

\$129.95

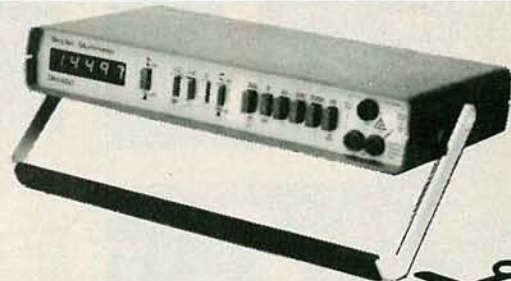

please send me

PDM35 Hand-held DMM @ \$39.95 each : \$ _____
 DM235 Bench/Portable DMM @ \$69.95 each : \$ _____
 DM350 Bench/Portable DMM @ \$99.95 each : \$ _____
 DM450 Bench/Portable DMM @ \$129.95 each : \$ _____
 AC Adaptor for PDM35 @ \$4.95 each : \$ _____
 AC Adaptor for DM235 @ \$4.95 each : \$ _____
 AC Adaptor for DM350 @ \$4.95 each : \$ _____
 AC Adaptor for DM450 @ \$4.95 each : \$ _____

Shipping/Handling at single rate per order : \$ 5.00*
New Jersey residents add appropriate Sales tax: \$ _____

TOTAL : \$ _____

I enclose

Check Money Order Master Charge Visa
 (Allow 2 - 3 weeks clearance time for personal checks)

Credit Card No. _____ Exp. Date _____

NAME _____

STREET _____

CITY _____ STATE _____ ZIP _____

SEND TO: NJS Technology Inc.
P.O. Box 8247
Haledon
New Jersey
07538

Tel. (201) 790 3141

RE

*Continental USA only

SEPTEMBER 1980

"GIVE ME ONE GOOD REASON WHY I SHOULD JOIN NESDA?"

Reason No.1: PROFIT

Haven't you felt frustrated because your profits seem to fly away before you can put them in your pocket?

What you get from your NESDA membership can help you keep more of the money you take in.



WANT 9 MORE GOOD REASONS TO JOIN NESDA?

2. Industry information
3. ServiceShop magazine
4. Electronics Service Industry Yearbook
5. Advocate for better warranty practices
6. Group-rate insurance
7. Technical information
8. Management information
9. Legislative programs with state and nat'l. gov'ts.
10. Low BankCard rates



Don't let your bucks get lost in the shuffle. At NESDA, the bottom line is putting more \$\$\$ in your pocket.

JOIN NESDA

and your local and state associations


Send for more information: NESDA, 2708 W. Berry St. Fort Worth, TX 76109



computer products

More information on computer products is available. Use the Free Information Card inside the back cover.

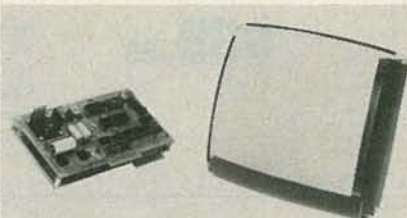TOUCH SCREEN DIGITIZER, TSD-12, eliminates the need for keyboards and light pens at computer terminals. To select an item from the "menu" presented on the screen, all the operator has to do is touch his finger to it.



CIRCLE 121 ON FREE INFORMATION CARD

Applications include: executive data-base interaction, computer-aided instruction, voter registration, banking, and other situations where an operator must interact with a computer data base.

Prices range from \$950 for a unit with parallel unfiltered data output to \$1,200 for one with filtered RS-232 output and power supply. A special one-time evaluation unit with RS-232 interface and power supply is available for \$995. OEM pricing is available upon request.—**TSD Display Products, Inc.**, 35 Orville Drive, Bohemia, NY 11716.

CP/M—COMPATIBLE DESKTOP MICROCOMPUTER series, the *Quay 500* and *520* is based on Quay's 94F/MPS single-board computer with 32K of RAM (expandable to 64K). Both systems use two 5 1/4-inch disc drives with DMA. The model *500* has a storage capacity of 400 kilobytes (for-



CIRCLE 122 ON FREE INFORMATION CARD

matted), single-sided, double density, and the *520* uses double-sided, double-density drives to give over 800 kilobytes of storage.

A parallel and serial port are standard and two additional serial ports can be added. An S-100 bus adaptor is also available.

The systems come with the CP/M Version 2.2 operating system. Prices for the *500* and *520* are \$2,500 and \$3,200, respectively.—**Quay Corporation**, P.O. Box 386, Freehold, NJ 07728.

ADD-ON FLOPPY DISC system, the *H-77*, increases the storage and programming capability of the Heathkit H89 computer. The *H-77* uses standard 5.25-inch, hard sectored, 40-track discettes, each capable of storing 100K of data. Typical sector-access time is less than 250 milliseconds.

Adding the *H-77* to the H89 means that, not only is storage capacity increased, but both sys-

tem and program discs can be run at the same time, giving fast and efficient access to programs and data and making disc duplication simple.

Kit price is \$595 and includes one drive. A second drive, the *H-17-1* is available for \$325. A factory-assembled version, the *WH-87* includes both



CIRCLE 123 ON FREE INFORMATION CARD

drives and is priced at \$1195. An adaptor kit, the *H-88-6* (\$50) is required to install the *WH-77*. All prices are F.O.B. Benton Harbor, MI.—**Heath Company** (a subsidiary of Zenith Radio Corporation), Benton Harbor, MI 49022.

MUSIC SYNTHESIZER for the *TRS-80*, *The Music Box*, is a complete hardware/software tool that enables you to generate music and sound effects using your computer.

The Music Box can play up to four notes simultaneously and has a range of seven octaves. The waveforms generated can be modified so that the music can sound as if played by as many as four different instruments at the same time. In addi-



CIRCLE 124 ON FREE INFORMATION CARD

tion, a variety of sound effects and noises, such as explosions, gun shots, and "phasors," can be produced.

Connection is made to the *TRS-80* keyboard or expansion interface by means of a cable. *The Music Box* includes a volume control, audio amplifier and jack for connection to an external speaker or amplifier. Software is supplied on Level II cassette or disc. A Level II computer with 32K or more of memory is recommended.

Price is \$249 with software and user's manual. Add \$3 for shipping and \$1 more if COD.—**Newtech Computer Systems, Inc.**, 230 Clinton St., Brooklyn, NY 11201. **R-E**

IF YOU'RE AN ADVERTISER WHO NEEDS JUST A LITTLE SPACE LIKE THIS 1/6 PAGE, CALL YOUR NEAREST RADIO-ELECTRONICS SALES OFFICE RIGHT NOW. YOU'LL DISCOVER YOU DON'T HAVE TO SPEND A LOT OF \$\$\$ TO REACH THE PEOPLE WHO DO SPEND A LOT.

NEW YORK
Stan Levitan
212-777-6400

CHICAGO
Ralph Bergen
312-446-1444

LOS ANGELES
J.E. Publishing
213-659-3810

Radio-Electronics



new lit

More information on new lit is available. Use the Free Information Card inside the back cover

ELECTRONICS CATALOG, 55 pages, lists a variety of quality parts from over 40 manufacturers. Covered are regulators, capacitors, resistors, transistors, IC's, soldering irons, and hundreds of other products. Price information and order form included.—**Tri-Tek, Inc.**, 7808 N. 27th Ave., Phoenix, AZ 85021.

CIRCLE 99 ON FREE INFORMATION CARD

MICROCOMPUTER BOOKS, is a 14-page brochure featuring a comprehensive four-volume series introducing microcomputers and books on assembly language and logic design. Descriptions and complete table of contents are provided. Also listed are BASIC software and program manuals, including three business applications programs and 76 short programs with cassette tape for use with the Commodore PET. **Osborne/McGraw-Hill**, 630 Bancroft Way, Berkeley, CA 94710.

CIRCLE 141 ON FREE INFORMATION CARD

COMPUTER ACCESSORIES, *Catalog No. 112*, contains 16 pages of software, computer boards, systems, printers, semiconductors, and PC aids designed for the computer enthusiast, novice, and businessperson. Each product is described in great detail. Quantity and club discounts available.—**Hobby World Electronics**, 19511 Business Center Dr., Northridge, CA 91324.

CIRCLE 142 ON FREE INFORMATION CARD

PERSONAL COMPUTER CATALOG, *No. 6*, contains 20 pages full of books, software, and merchandise for the computer enthusiast. Offered are back issues of popular computer magazines, and books on various subjects including microcomputers, games, business programs, BASIC language, and much more. Their software includes many different games available in cassette or floppy disk form. T-shirts and posters are also featured. Order form enclosed.—**Creative Computing**, P.O. Box 789-M, Morristown, NJ 07960.

CIRCLE 143 ON FREE INFORMATION CARD

HI-FI CATALOG, is an illustrated 32-page booklet describing AM/FM stereo receivers, integrated amplifiers, AM/FM stereo tuners, front-load cassette decks, audio analyzers, direct-drive turntables, and loudspeaker systems. In addition to photographs and descriptions, there is an overall set of tables in the final pages listing specifications so that the reader can compare the claims for one model with another.—**H. H. Scott, Inc.**, 20 Commerce Way, Woburn, MA 01801.

CIRCLE 144 ON FREE INFORMATION CARD

TWO-WAY MOBILE RADIO CATALOG, 1980, is an 8-page illustrated brochure covering base station equipment, remote-control equipment, mobile car telephone equipment, mobile radio equipment, paging equipment, and portable radio equipment, including two-way portable radios.—**Mobile Technical Service Corp.**, 6019 South Kenton Way, Englewood, CO 80111.

CIRCLE 145 ON FREE INFORMATION CARD

ARCHER SEMICONDUCTOR REPLACEMENT GUIDE, 1980 edition, is a 224-page book, featuring cross-reference/substitution listings for over 100,000 devices. It's a comprehensive guide to Radio Shack's complete line of Archer-brand

semiconductors and includes detailed data and pin connections for IC's, diodes, SCR's, LED's, and other devices.

There is information on the care of transistors and integrated circuits, case styles and dimensions, transistor testing, display and optoelectronic devices. A glossary of word symbols, and abbreviations is also included.

The 1980 edition of this replacement guide is \$1.99 and can be obtained from participating Radio Shack stores and dealers throughout the U.S.A.—**Radio-Shack**, 1300 One Tandy Center, Fort Worth, TX 76102.

CIRCLE 146 ON FREE INFORMATION CARD

MINI-SCOPE SELECTION GUIDE 1979, is a full-color, 4-page leaflet presenting photos and brief specifications of mini-scopes (general-purpose, portable oscilloscopes that weigh 15 lbs. or less, are small enough to fit into a tool kit or briefcase, and can operate from self-contained battery power) and mini-scopes with DMM-counters. The back cover gives detailed ordering information and a list of sales representatives in U.S. metropolitan areas.—**Vu-data Corporation**, 7170 Conroy Court, San Diego, CA 92111.

CIRCLE 147 ON FREE INFORMATION CARD

TURNTABLE/CASSETTE CATALOGS, Dual turntables and Dual cassette decks. Each catalog contains 12 illustrated pages. The turntables all feature ULM (*Ultra Low Mass*) tonearms and cartridge systems and models range from single play to fully automatic. The cassette decks feature the new DLL (*Direct Load and Lock*) system. Charts on the back covers give a breakdown of the specific features to be found on each model, and photos shows how they are laid out.—**United Audio**, 120 So. Columbus Ave., Mt. Vernon, NY 10533.

CIRCLE 148 ON FREE INFORMATION CARD

KESTER SOLDER (NEW EDITION) is an illustrated, two-color, 12-page brochure covering Kester's broad line of solders and fluxes. The brochure covers acid and resin-cored solders, flux-cored silver bearing solders, and radiator solder, as well as Kester's half-pound spools of acid-core, solid wire and "44" resin-core solders. Also described are package-goods solders and other carded merchandise—metal mender, TV-radio solder, aluminum-repair solder, solder paste flux, and related chemical products. A special feature is questions and answers about soldering, and a 6-step instruction on soldering procedure.—**Kester Solder**, 4201 Wrightwood Ave., Chicago, IL 60639.

CIRCLE 149 ON FREE INFORMATION CARD


SAMS COMPUTER BOOKS, 1980 *Catalog*, contains 19 illustrated pages in two colors describing one of the industry's largest selection of computer and computer-based items.

The catalog is laid out in five areas for easy reference: Basics, Programming, Computer Technology, Reference, and Computer-related books. The selections are directed to a wide range of people and interests, from the home hobbyist to the technically-oriented professional.—**Howard W. Sams & Co., Inc.** 4300 W. 62nd St., PO Box 7092, Indianapolis, IN 46206. **R-E**

CIRCLE 150 ON FREE INFORMATION CARD

Put Professional Knowledge and a **COLLEGE DEGREE** in your Electronics Career through

HOME STUDY

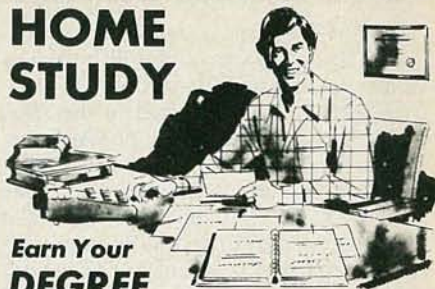

Earn Your DEGREE

by correspondence, while continuing your present job. No commuting to class. Study at your own pace. Learn from complete and explicit lesson materials, with additional assistance from our home-study instructors. Advance as fast as you wish, but take all the time you need to master each topic.

The Grantham electronics degree program begins with basics, leads first to the A.S.E.T. degree, and then to the B.S.E.T. degree. Our free bulletin gives complete details of the program itself, the degrees awarded, the requirements for each degree, and how to enroll. (We are located at 2500 S. LaCienega Bl., Los Angeles, Calif.) Write to our mailing address shown below for *Bulletin R-80*

Grantham College of Engineering
P. O. Box 35499
Los Angeles, California 90035

Worldwide Career Training thru Home Study

Attention
Atari Owners:

Now you can
boost
your 400 or 800
to 16K performance
in just 16 minutes.

Mosaic Electronics has now developed a RAM expansion kit that can up-grade your Atari 400 or 800 to 16K performance. The modification takes just 16 minutes. RAM expansion kit meets or exceeds OEM timing specs, includes all needed hardware and comes complete with pictorially presented instructions.

only \$79
(we pay postage)

Order today and receive our
FREE software catalog.

We can market your Atari software.
Write us for details.

MOSAIC
ELECTRONICS

P. O. Box 748 • Oregon City, OR 97045

Mosaic Electronics is in no way affiliated with Atari.

CIRCLE 56 ON FREE INFORMATION CARD

SEPTEMBER 1980

NOISE-REDUCTION SYSTEM

continued from page 62

low low-frequency signals as continuous level changes and will introduce unacceptable bass distortion.

Spectrum division used in the *High Com II* system solves that problem, too. Since high and low-frequency signals are processed independently, time constants for the high and low-band circuits can be optimized for each particular range of frequencies. The result is extremely accurate reproduction of musical transients, as illustrated by the tone-burst signal (Fig. 6) processed via a *High Com II* system. The frequency within the tone burst was 10 kHz and only a few cycles of that tone were at anything but correct full amplitude after the burst was initiated.

Figure 7 is a dual-exposure oscilloscope photo showing the effectiveness of the *High Com II* system in removing noise components from low-level signals. The upper trace was observed during playback of a 400-Hz signal recorded and played back at a level of -40 dB without the use of any noise reduction. Note that the noise amplitude (blurry thickening of the 400-Hz sinewave) is not much lower than the signal itself. The lower trace represents the playback of a 400-Hz signal recorded at the same input level,

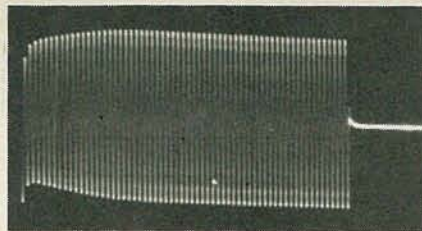


Fig. 6—EXCELLENT TRANSIENT RESPONSE of High Com II illustrated by 10-kHz tone burst.

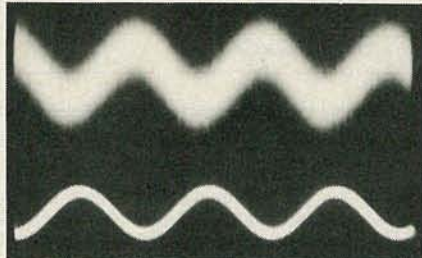


Fig. 7—LOW-LEVEL 400 Hz signal recorded and played back with and without the High-Com II.

but this time recorded and played back using the *High Com II* noise-reduction system.

Nakamichi was probably wise to offer the *High Com II* as an outboard device since it can be connected to any existing cassette deck and, in addition, those listeners who are presently owners of reel-to-reel equipment can also avail themselves of this new noise-reduction system.

R-E

HOW TO CONNECT HOME VIDEO

continued from page 54

patch panel. Run all of your different inputs and output to a central front panel and use bulkhead fittings and jumpers that have been fitted with BNC type connectors or coax push-on fittings. You want them to be secure but easily rearranged depending on how you are currently routing the signals. If you try to use a switching network in this type of system you can expect problems. (Isolation within the switch becomes a critical factor so if you want to use a switching network, spend the money for good quality switches).

You might find that it is necessary to trap out one particular channel to make room in the system for insertion of a pay-TV device or additional VCR. Use a high-Q type trap that will effectively drop out the desired channel without affecting any adjacent channel.

If you use the installations that have been described as guidelines, you should be able to set up your own home video system to meet all of your particular needs.

R-E

Clever Kleps

Test probes designed by your needs — Push to seize, push to release (all Kleps spring loaded).

- Kleps 10.** Boathook clamp grips wires, lugs, terminals. Accepts banana plug or bare wire lead. 4¾" long.
- Kleps 20.** Same, but 7" long.
- Kleps 30.** Completely flexible. Forked-tongue gripper. Accepts banana plug or bare lead. 6" long.
- Kleps 40.** Completely flexible. 3-segment automatic collet firmly grips wire ends, PC-board terminals, connector pins. Accepts banana plug or plain wire. 6¼" long.
- Kleps 1.** Economy Kleps for light line work (not lab quality). Meshing claws. 4½" long.
- Prof 10.** Versatile test prod. Solder connection. Molded phenolic. Doubles as scribing tool. "Bunch" pin fits banana jack. Phone tip. 5½" long.

Write for complete catalog of - test probes, plugs, sockets, connectors, earphones, headsets, miniature components.

Available through your local distributor, or write to:

RYE INDUSTRIES INC.
132 Spencer Place, Mamaroneck, N.Y. 10543
In Canada: Rye Industries (Canada) Ltd.

DON'T FORGET



USE YOUR READER SERVICE CARD

FREE CATALOGS

- Software.** Lists 400 programs on 70 tapes and disks. For education, recreation, and personal use.
- Books.** Lists 100 books, games, records, prints, etc. for educational and personal users of small computers.
- Peripherals.** (ALF music synthesizer and Versa-Writer for the Apple II).

Send 3 15¢ stamps for either catalog or 5 for both. Or send \$2.00 for a sample issue of Creative Computing and both catalogs.

creative computing

DEPT. REHG
P.O. Box 789-M
Morristown, NJ 07960

books

MINIPROCESSORS: FROM CALCULATORS TO COMPUTERS, by David L. Heiserman. TAB Books, Blue Ridge Summit, PA 17214. 196 pp. 5 × 8 1/4 in. Softcover \$5.95; hardcover \$9.95.

This book teaches the computer hobbyist how to turn a calculator into a functional hybrid calculator/computer system (or supercalculator) by adding on memory-control circuit boards, I/O boards, branching and looping systems, etc. You first learn how to build a basic arithmetic calculator, and then proceed step-by-step to a fully programmable system with randomly addressable 256-step memory. Construction techniques are given plus full circuit description, component specs and schematics.

THE MULTITRACK PRIMER, by Dick Rosmini. TEAC Corp. of America, 7733 Telegraph Rd., Montebello, CA 90640. 46 pp. 8 1/2 × 11 in. Softcover \$4.95.

This booklet acquaints readers with multitrack recording and covers all the basics from setup and layout to cue systems and mikes. It covers such topics as designing a basic studio for a one-man keyboard or guitar, and shows you how to build a tent and baffle. The text is accompanied by charts and line drawings.

ALL ABOUT TELEPHONES, by Van Waterford. Tab Books, Blue Ridge Summit, PA 17214. 190 pp. 5 × 8 1/4 in. Softcover \$4.95.

Now that it's legal and possible to own your own telephone system, this book provides an answer to the most common questions, such as how to go about getting your own phone, the types available, and what is or isn't permissible to do according to FCC regulations. Chapter 2 describes how a telephone works and how it is installed. Chapter 4 details the FCC requirements for both owner and telephone company. Other chapters describe types of phones (picturephone, speakerphone, cordless, etc.) security devices and mobile units.

HEAR ALL THE ACTION, by Van Waterford. Howard W. Sams & Co., Inc., 4300 W. 62 St., Indianapolis, IN 46268. 128 pp. 5 1/4 × 8 1/4 in. Softcover \$5.25.

The book guides the hobbyist through the world of international communications via the DX receiver. It starts with a history of DX'ing and a description of radio-wave fundamentals such as frequency, VHF/UHF bands, wavelength, etc. Chapter 2 tells you how to shop for a receiver; Chapter 3 describes accessories and aids; and Chapter 4 deals with antennas. An appendix contains a glossary of terms and lists the abbreviations and codes used in shortwave transmissions.

RADAR DETECTOR HANDY MANUAL, by Van Waterford. Tab Books, Blue Ridge Summit, PA

17214. 79 pp. 5 × 8 1/4 in. Softcover \$2.25.

This handy guide to radar detectors explains the principles, installation and use of these devices, and tells you how to detect highway police radar signals. It also describes how the detectors work, and gives details on radar circuitry. The book includes handy hints on how to avoid speeding violations, plus a chapter on the CB lingo used in reference to police radar.

THE CAMEO DICTIONARY OF CREATIVE AUDIO TERMS. Creative Audio & Music Electronics Organization, 10 Delmar Avenue, Framingham, MA 01701. 100 pp. 5 1/4 × 8 1/4 in. Softcover \$4.95.

This first comprehensive dictionary of creative audio terminology that has ever been compiled is aimed at the reader who is *not* technically inclined. The definitions, from "A-B test" to "zenith adjustment" are brief and clearly presented, with diagrams and tables where needed. The object of the book is to provide fundamental and working knowledge of creative audio terminology to all who are involved in this field and industry; it will be of no less value to the interested reader, too, who may just be curious what some of those words and phrases that audiophiles use are about. The dictionary was compiled by Gary Davis & Associates and the focus is on sound recording, sound reinforcement, and signal processing for the performing artist. R-E

YOU DESERVE IT! GET IT EVERY MONTH!

Come on, treat yourself—and save money, too. Subscribe to Radio-Electronics today, and make sure you get all of the most interesting, most exciting and authoritative electronics reporting in any magazine, month after month. Don't miss a single one of the upcoming issues jam-packed with new-equipment test reports, projects to build, servicing ideas, and news of solid state, computers, hi-fi, hobbies and everything electronic. Save money, too—as much as \$5. off the newsstand price when you subscribe to Radio-Electronics. Come on, you deserve it—check off the money-saving offer you prefer on the handy coupon, and start enjoying Radio-Electronics every month.

Radio Electronics PROTECT YOUR CAR AGAINST AUTO THEFT
\$1.25 MAR. 1980

Build a backyard satellite TV receiver
14 nifty things you can do with a PRAM IC
Build a thunderstorm alarm
New for 1980 TV sets
New super class A hi-fi amplifiers
Circuits that talk back



NIFTY WIRE-WRAP TRICKS

Get The Authority—Every Month

Name (Please print) _____

40J0

Address _____

City _____

State _____

Zip _____

Indicate the offer you prefer:

1 Year—12 issues ONLY \$13.00
(You save \$2.00 off newsstand price.)

Payment enclosed (send one extra issue)

2 Years—24 issues ONLY \$25.00
(Save More! \$5.00 off newsstand price.)

Bill me

Check here if you are extending or renewing your subscription.

Extra Shipping: Canada \$3.00 per year, all other countries \$5.00 per year.

Mail to: **Radio-Electronics**

SUBSCRIPTION DEPT., P.O. BOX 2520 BOULDER, COLO. 80322

High stability crystals for frequency or time. Use the best.

- CB
- 2 meters
- Scanners
- Industry
- Marine VHF
- CB standard
- Amateur Bands
- General Communication
- Micro processor crystals

Send for our latest catalog. Write or phone for more details.

Jan Crystals
2400 Crystal Drive
Ft. Myers, Florida 33907
all phones (813) 936-2397



CIRCLE 16 ON FREE INFORMATION CARD

SEPTEMBER 1980

market center

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services) **\$1.50 per word prepaid (no charge for zip code)** . . . **MINIMUM 15 WORDS**. 5% discount for 6 issues, 10% for 12 issues within one year, if prepaid.

NON-COMMERCIAL RATE (for individuals who want to buy or sell a personal item) **85¢ per word prepaid** . . . no minimum.

ONLY FIRST WORD AND NAME set in bold caps. Additional bold face (not available as all caps) at 10¢ per word. All copy subject to publisher's approval. **ADVERTISEMENTS USING P.O. BOX ADDRESS WILL NOT BE ACCEPTED UNTIL ADVERTISER SUPPLIES PUBLISHER WITH PERMANENT ADDRESS AND PHONE NUMBER.** Copy to be in our hands on the 26th of the third month preceding the date of the issue (i.e., August issue closes May 26). When normal closing date falls on Saturday, Sunday, or a holiday, issue closes on preceding working day.

PASS FCC EXAMS

The Original FCC Tests Answers exam manual that prepares you at home for FCC First and Second class Radiotelephone licenses. Newly revised multiple-choice exams cover all areas tested on the actual FCC exam. Plus "Self-Study" Ability Test. Proven! \$9.95 postpaid. Moneyback Guarantee.



COMMAND PRODUCTIONS Radio Engineering Division P.O. Box 26348 E. San Francisco, CA 94126

EDUCATION & INSTRUCTION

UNIVERSITY degrees by mail! Bachelors, Masters, Ph.D's . . . Free revealing details. **COUNSELING**, Box 317-RE9, Tustin, CA 92680

HOME study degree program in electronics engineering. 75 specialized courses also available. For information write: **CIEE**, P.O. Box 9196, Pittsburgh, PA 15224

THE Illustrated Dictionary of Electronics 868 pps send \$14.98 to: **SDG RESEARCH**, 3947 Delta, Rosemead, CA 91770

WANTED

PRE-WWII and early television sets wanted. Will pay top dollar for any set featured in June Radio-Electronics issue **ARNOLD CHASE**, 9 Rushleigh Road, West Hartford, CT 06117


SONY TC105 tape recorder. **TIM McNEAL**, Box 904, Warsaw, IN 46580

WANTED. Programming manual for Inforex 1302 system computer, write to, **CHRISTOPHER CASEY**, Apt. 240474-A Coffield, Rt. 1, Box 150, Tennessee Colony, TX 75861

PICTURE TUBE MACHINE
We buy and sell NEW and USED CRT rebuilding machinery. **COMPLETE TRAINING.** Buy with CONFIDENCE from the ORIGINAL MFRG.

For complete details send name, address, zip to:

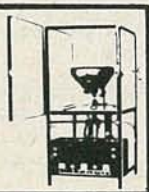LAKESIDE INDUSTRIES
4071 N. Elston Avenue
Chicago, Ill. 60618
Phone: 312-583-6565



To run your own classified ad, put one word on each of the lines below and send this form along with your check for \$1.50 per word (minimum 15 words) to:

Radio-Electronics, 200 Park Avenue South, N.Y., N.Y. 10003

ORDER FORM

PLEASE INDICATE in which category of classified advertising you wish your ad to appear. For special headings, there is a surcharge of \$10.

() Plans/Kits () Business Opportunities () For Sale
() Education/Instruction () Wanted ()

Special Category: \$10

(PLEASE PRINT EACH WORD SEPARATELY, IN BLOCK LETTERS.)

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

PLEASE INCLUDE FOR OUR FILES YOUR PERMANENT ADDRESS AND PHONE NUMBER.

Satellite TV

FOR THE HOME

Sick of Network TV?

Our receiver lets you get over 75 channels of television directly from earth-orbiting cable TV satellites! HBO, Showtime, super stations, sports and movies from around the world.



We don't just sell information! We Manufacture Hardware!

Our 75-page catalog and information book tell the whole story! Inexpensive dishes, high pro-feeds, computer aiming software! Specs, Kits and more! Send \$7.95 today!

24-hour C.O.D Hotline
(305) 339-7600



SPACECOAST RESEARCH
Dept. T, P.O. Box 442, Altamonte Springs, FL 32701

SATELLITE TELEVISION

ANTENNA azimuth and elevation for all Western Hemisphere geostationary satellites. \$3.00 and your latitude and longitude. Free sample SASE. **DAVID FREY**, Box 2591, Satellite Beach, FL 32937

SATELLITE television—New package includes: **Antenna aiming data** computed for your latitude, longitude, (plotted by Compusat), revised listing of U.S. and international geostationary satellites, transponder video frequencies, audio subcarriers, formats, antenna/feedline data and more. All for \$10.00. **COMPUSAT**, 643 South Route 83, Elmhurst, IL 60126



SATELLITE TV FANTASTIC 80 TV CHANNELS

A must for all homeowners and Do-it-yourselfers. Build a Video System the whole family can enjoy! No commercials, FREE movies, sports and Vegas Shows - worldwide, crystal clear reception connects to any TV set. 100 pages (8 x 11) loaded with photos, plans, kits - TELLS EVERYTHING!

Send \$7.95 TODAY! Add \$2.00 for 1st class (air mail). Satisfaction Guaranteed
GLOBAL TV ELECTRONICS, P.O. Box 219-B, Maitland, FL 32751

WHOLESALE TO DEALERS

DEALERS: send letterhead for free wholesale pricelist of CB radio and scanner equipment. **FOUR WHEELER COMMUNICATIONS**, 10-R New Scotland Ave., Albany, N.Y. 12208 (518) 465-4711

GRAPHIC EQUALIZER

TWELVE bands/channel \$100.00 kit still available; see May 1978 R/E cover story or write: **SYMMETRIC SOUND SYSTEMS**, 912 Knobcone PL, Dept. R, Loveland, CO 80537

ATV Research ...specialists in CCTV and computer monitors!

Video monitors - color & B/W * TV Cameras, kits, parts & plans * Video-to-RF modulators * Free catalog. Phone or write. (402) 987-3771

13-RE Broadway Dakota City, NE. 68731

FOR SALE

SCANNER/monitor accessories—kits and factory assembled. Free catalog. **CAPRI ELECTRONICS**, Route 1R, Canon, GA 30520

FREE catalog, IC's, LED's, semi's, parts. **CORONET ELECTRONICS**, 649A Notre Dame W., Montreal, Que., Canada H3C 1H8. U.S. inquiries.

RECONDITIONED test equipment. \$1.00 for catalog. **JAMES WALTER TEST EQUIPMENT**, 2697 Nickel, San Pablo, CA 94806

SAVE up to 50% on name brand test equipment. Free catalog and price list. **SALEN ELECTRONICS**, Box 82-M, Skokie, IL 60077

The World's Hardest I.Q. Test

as featured in *Omni*, April 1979

Qualifying examination for Four Sigma Society

Taken by more than 20,000 people.

\$5, including score report.

Also available:

The Two Cultures Test (\$5)

(Tests knowledge of science and humanities.)

The Vocabulary Gradient Test (\$3)

Send SASE for complete list.

POLYMATH, DEPT. R

P.O. Box 795, Berkeley, CA 94701

MICROWAVE TV downconverter, preamps, parabolic dish antennas, remote tuning. Covers 2000 MHz band. Write for information. **LAB-TRONICS**, Box 171, Rogers, MN 55374

GIANT communications guide. Info thru 1980. Worldwide LW- AM- FM- SW- RTTY- CW- Fax-satellite-VOLMET- marine- NOAA- QSL'S- etc. \$20.00 ppd. **GCG**, 11625 W. McKinley, Fresno, CA 93711

TELEVISION downconverters and decoders \$99.95 up. Details for stamp. **GW ELECTRONICS**, POB 688, Greenwood, IN 46142

OSCILLOSCOPE, DC to 22 MHz, dual trace, Navy equivalent to HP170, \$199. **HAMMOND**, 1013 Lafayette Avenue, Colonial Heights, VA 23834

1. 5 Volt, 3 amp, Regulated Power Supply.

Great for TTL Projects.....\$19.50

2. EMM 4200A, 4K Static RAMs, Ceramic

A local memory boards manufacturer closed. We bought the new memory boards and took these 4200A static RAMs out. They are tested and 90-day guaranteed 100% good.

Prime tested 4200A 4K RAMs \$5.50 ea.

3. Super Saver. Micro PD411, Ceramic 4K x 1 dynamic RAMs..... 8 for \$10.00.

WE BUY SURPLUS ELECTRONIC

INDUSTRIAL INVENTORIES

DELTRONIKS

5151 BUFORD HIGHWAY - 028

ATLANTA, GA 30340

404-458-4690

RAW speakers and finished systems for Hi-Fi and Sound Reinforcement. Also cabinet plans, hardware, grille cloth, crossovers, microphones, accessories, much more. Information-packed catalog, \$1.00. **UNIVERSAL DISCOUNT SOUND**, Dept. RE, 2243 Ringling Blvd, Sarasota, FL 33577

GOVERNMENT surplus receivers, transmitters, sniperscopes, parts, fantastic 72 page catalog 25¢. **MESHNA**, Nahant, Mass. 01908

CABLE TV converters \$39.95. Incredible 96-page catalog free. **ETCO**, Box 762, Plattsburgh, NY 12901

AMAZING ELECTRONIC PROJECTS and PRODUCTS:

Lasers Super Powered, Burning Cutting, Rifle, Pistol, Pocket. See in Dark—Shotgun Directional Mike—Unscramblers—Giant Tesla—Stunwand—TV Disrupter—Energy Producing, Surveillance, Detection, Electrifying, Ultrasonic, CB, Auto and Mech. Devices, Hundreds More—All New Plus INFO UNLTD PARTS SERVICE. Catalog \$1. Information Unlimited, Dept. R8 Box 716 Amherst, N.H. 03031.

RECORDS—tapes! Discounts to 73%; all labels; no

purchase obligations; newsletter; discount dividend certificates; 100% guarantees. Free details. **DISCOUNT MUSIC CLUB**, 650 Main Street, Dept. 3-0980, New Rochelle, NY 10801

VOLCANIC ash

from Mount Saint Helens; glass container filled with ash, plus description. Send \$4.00 to: **ASH**, 5268 35th N.E., Seattle, WA 98105

KEYBOARDS—High quality 61 note single or

dual contact for the organ or synthesizer you are building. Send for information. **DEVTRONIX**, Dept. 70, 6101 Warehouse Way, Sacramento, CA 95826

COMPLETE gear for CB repair shop, including

Score CB 42 analyzer. **TED MARSHALL**, 1605 South Main, Warrenton, OR 97146

Burglar-Fire Protection



Protect Your Life, Home, Business, Auto, etc.

• Our catalog shows how. Install your own alarm systems and devices and save \$\$\$\$. We offer FREE write-in engineering service.

FREE CATALOG Lowest Prices on Reliable, High-Quality Alarm Systems and Devices

Burdex Security Co. Box 82802-RE Lincoln, Ne. 68501

FREE shipping. Liberal discounts. No risk guarantee.

Why pay more for your electronic and computer books. Send stamp for list. **MICRO-POWER BOOKS**, 17095 Bridgeport Road, Dallas, OR 97338

NEW—scope, VOM and more. To best offer.

Write **ERVIN WARREN**, Drawer R, Huntingdon, PA, 16652. Phone 215-444-5879

SCRAMBLED television, encoding/decoding.

New Publication. Theory/circuits. \$9.95. **WORKSHOP**, Box 393 REA, Bethpage, NY 11714

TEST equipment, new and used. Catalog \$1.00.

PTI, Box 8756, White Bear Lake, MN 55110

DIGITAL MULTIMETERS Sinclair PDM35 Reg. \$69.95 Hickok LX303 \$69.50 \$49.95 	MURAPHONE Cordless Telephone System Reg. \$89.95 \$79.95 	Portable VOM Multitester Model \$1995 VMS20 20 KΩ VDC • 10 KΩ VAC 	100 MHz 8-Digit Counter 20 Hz to 100 MHz range LED display Fully automatic Model MAX100 Reg. \$150.00 \$127.50 	6" x 9" 3-Way Speaker 20 oz. ceramic magnet Model BP2000-69TR \$14.95 ea. 						
3 1/2-Digit Portable DMM Model 2800 \$140. 	Beckman TECH310 \$140. 	GTE Flip-Phone™ \$37.95 	HICKOK Digital CB In-Line Tester Reg. \$399.00 \$169.95 Model 388 	ESCC Logic Monitor Automatically displays static and dynamic logic Model LM-1 Works with DTL, TTL, LED display \$59.95 	Telephone Answering Model 1500 \$249.95 Call Control Reg. \$349.95 Model 1400 \$199.95 	CODE-A-PHONE \$249.95 	FREE 8 pc. Tool Set with \$200.00 purchase from this ad. 			
Portable Oscilloscopes 15 MHz Dual Trace Triggered Miniscope Model MS-215 Reg. \$465.45 \$389.95 	Function Generator Model 2001 Reg. \$185.95 \$157.95 Sine-, square-, triangle- and separate TTL square wave output Frequency range: 1Hz-100kHz 	Attache Style Tool Case Model TC100-ST Reg. \$499.95 \$299.95 	Weller Xcelite™ Service Master Tool Kit Model 99-SM Reg. \$79.95 \$49.95 	ESCC 60 Cordless Soldering Iron Model 7800 \$29.95 	Wahl ISORTIP Cordless Soldering Iron Model 7800 \$29.95 	Miniature High Fidelity 3-Way Stereo Speakers Model HF-9 \$69.50 PR Reg. \$149.95 				
15 MHz Triggered Miniscope Model MS-15 Reg. \$349.80 \$289.95 	30 MHz Dual Trace Triggered Miniscope Model MS-230 Reg. \$598.15 \$499.95 	Proto Board with Built-in Power Supplies Regulated Short-proof Reg. \$154.95 \$129.95 Model PB-203A 	ESCC 3 1/2-Digit 0.1% Digital Capacitance Meter Model 3001 9 ranges from 1999 pF to 199.9 μF 0.1% of reading accuracy \$170 	Thermal-Spot Model 800 Circuit Tester \$29.95 	In-Dash Car Stereos 8-Track Tape Player with AM/FM/MPX Radio Model C-777 \$52.50 	Cassette Tape Player with AM/FM/MPX Radio Model CAS-888 \$57.50 				
Logic Probe Compact circuit powered Detects pulses as short as 50 μsec DTL/TTL/HTL/CMOS compatibility \$44.95 Model LP-1 	Proto Preassembled Boards Model PB-104 Fully assembled breadboard contains four QT-59S sockets, seven QT-59B bus strips and four 5-way binding posts \$49.95 	30 MHz LEADER Dual Trace with Delay Line Model LBO-520 \$899.95 	DIGITAL MULTIMETER Simpson 461 Complete with nickel-cadmium batteries, AC charger/adaptor, test leads \$149.95 	BSR X-10 Remote Control for Lights & Appliances 4 Pc Standard Starter Kit • One (1) Standard Command Reg. \$87.95 Complete • Two (2) Lamp Modules • One (1) Appliance Module \$79.50 5 Pc Ultrasonic Starter Kit • One (1) Deluxe Ultrasonic Reg. \$112.95 Command Console • One (1) Hand Held Remote Unit • Two (2) Lamp Modules • One (1) Appliance Unit \$99.95 Lamp Modules \$14.50 Standard Command Console \$36.00 Appliance Modules \$14.50 Ultrasonic Command Console \$59.95 Wall Switch Modules \$14.50 with Hand Held Remote 	Stereo Power Booster Model POW-40 40W stereo \$24.95 	RC Circuit Box 36 resistors (15 1/2 to 10 MΩ) • 18 capacitors (100 pf to 0.22 μf) \$42. includes test leads viz. Model WC 412A 	Magnifier Lamp Precision ground and polished magnification lens Model MG10A \$49.50 	Chess Challenger 7 Reg. \$110.00 \$79.95 Model BBC 	Weller Controlled Output Soldering Station Model WTCPN Reg. \$77.50 \$54.95 	ESCC 30 MHz Portable Frequency Counter Reg. \$130.00 \$65. Model 1627

FORDHAM

855 Conklin St. Farmingdale, N.Y. 11735

• Master Charge
 • BankAmericard
 • VISA • COD
 • Money Order
 • Check
 N.Y. State residents add appropriate sales tax
 200¢ extra

TOLL FREE (800) 645-9518

in N.Y. State call (516) 752-0050

Radio Shack — Your No. 1 Parts Place™

Low Prices and New Items Every Day!

4000-Series CMOS ICs

Low As **89¢**



Type	Cat. No.	Each
4001	276-2401	.99
4011	276-2411	.89
4013	276-2413	1.19
4017	276-2417	1.99
4027	276-2427	1.19
4511	276-2447	1.99
4049	276-2449	.99
4050	276-2450	.99
4066	276-2466	1.59

Schottky ICs

Low As **79¢**

Type	Cat. No.	Each
74LS00	276-1900	.79
74LS02	276-1902	.79
74LS04	276-1904	.79
74LS08	276-1908	.79
74LS32	276-1915	.89
74LS73	276-1918	.99
74LS74	276-1919	.79
74LS75	276-1920	.99
74LS90	276-1923	1.19
74LS123	276-1926	1.49
74LS151	276-1929	1.09
74LS157	276-1930	1.19
74LS161	276-1931	1.59
74LS164	276-1932	1.59
74LS175	276-1934	1.39
74LS193	276-1936	1.69
74LS367	276-1835	1.59


TTL Digital ICs

Low As **69¢**

Type	Cat. No.	Each
7400	276-1801	.69
7402	276-1811	.79
7404	276-1802	.79
7408	276-1822	.79
7447	276-1805	1.19
7448	276-1816	1.29
7473	276-1803	.79
7474	276-1818	.99
7475	276-1806	1.09
7476	276-1813	.89
7490	276-1808	1.09
7492	276-1819	1.19
74154	276-1834	1.49
74192	276-1831	1.59
74193	276-1820	1.49

All 100% Prime from Major Manufacturers. Specs and Pin Out Diagram Included with Each Device.

16-Pin DIP Jumper Cable

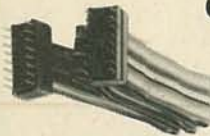

3⁹⁹

Two 16-pin DIP plugs connected by an 18" color-indexed ribbon cable. Simplifies linking up digital circuits.
276-1976 3.99

Barrier Strips

New!

Low As **1¹⁹**



Rugged thermoplastic. Prevent shorts. Ideal for audio equipment, power supplies. Terminals extend 3/16".

Terminals	Cat. No.	Each
4	274-651	1.19
6	274-652	1.49
8	274-653	1.79

Sound Effects Chip



4⁴⁹

28-Pin DIP

SN76477. Music, explosions, phasers, gunshots and more — almost any sound imaginable! Line-level output. 6-15VDC. With data.
276-1765 4.49

3" Solar Cell



9⁹⁹

High Efficiency

Back in Stock! 0.45V at 1 Amp in full sunlight.
276-123 9.99

IC Tool Set



6⁹⁵

Built-In Pin Straightener

Handy insertion and extraction tools handle all 14 to 16-pin devices. Both tools easily grounded.
276-1574 Set 6.95

16K Dynamic RAM

New!

13⁹⁵ Each



16,384 x 1 bits in a 16-pin DIP. Access time: 250 nanoseconds. Refresh: 1 millisecond. Requires +5, +12, and -5VDC. TTL compatible.
276-2505 13.95

Mini Lamps

New!

Only **99¢**

Pkg. of 6



Enlarged to show detail

Long life red incandescents for models, charts, dial lights, more. 6V, 60 mA.
272-1144 6/99¢


Speaker Terminals

New!
1⁹⁹



Just right for hi-fi, instrument or PA speakers. Push-terminals accept up to 16-ga. wire. Also has 2-conductor 1/4" phone jack with sealing plug.
274-624 1.99


Opto Devices

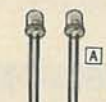

Low As **89¢**

A Emitter/Detector Pair. LED infrared source. Sensitive phototransistor detector.
276-142 1.99
B Phototransistor. Sensitive, fast response silicon.
276-130 89¢

Yellow 0.3" LED Readout

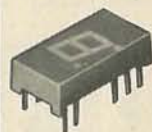

New!
1⁹⁹

Pkg. of 2

Right hand decimal, 3.0V/segment @ 20 mA. Common cathode.
276-067 Pair/1.99

Cases and Cabinet

Save up to **33%**




A Deluxe "Wood Look" Cabinet. Metal, slide-off cover, rubber feet. 2 3/4 x 4 1/4 x 5 1/8". 270-262 (Reg. 5.95) Sale 3.95
B Readout. Holds four 0.6" or eight 0.3" readouts. Removable bracket. 1 1/2 x 3 7/8 x 4 7/8". 270-285 (Reg. 3.95) Sale 2.95
C Clock. For MA-1003 car clock. Blue lens. Accepts 3 switches (not incl.). Bracket, 3 1/2 x 2 1/2 x 2". 270-303 (Reg. 5.95) Sale 3.95

TV RF Modulator Board

Save **29%**

Reg. 16.95
11⁹⁵

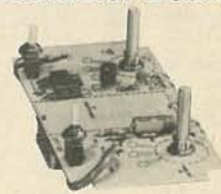


Etched, drilled & labeled PC board with pre-wired RF module and back-of-set ant. switch. Ch. 3 or 4 out. Produces color or b&w video, 30-15,000 Hz hi-fi sound. With instructions. Parts extra.
277-122 Sale 11.95

AC Cooling Fan

Quiet, Efficient

14⁹⁵

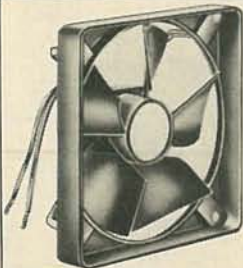

Ideal for cooling hi-fi and ham equipment, power supplies, computers. 70 CFM. For 120VAC. Just 4.63 x 4.63 x 2.47" overall.
273-241 14.95

Regulated 12VDC Supply

29⁹⁵

Circuit Breaker Protected



Powers CBs, ham rigs, auto-sound equipment and more from 120VAC. 2.5A continuous, 5A surge, 2 1/2 x 4 1/2 x 6 3/4" U.L. listed.
22-124 29.95

Prices may vary at individual stores and dealers

NEW 1981 Catalog Available Now! Come in for Your FREE Copy! (None Sent by Mail).

Radio Shack®

A DIVISION OF TANDY CORPORATION • FORT WORTH, TEXAS 76102
OVER 7000 LOCATIONS IN 40 COUNTRIES

CIRCLE 61 ON FREE INFORMATION CARD

SEPTEMBER 1980

109

PLANS & KITS

PRINTED circuit boards from sketch or artwork. Kit projects. Free details. **DANOCINTHS INC.**, Box 261, Westland, MI 48185

SPEAKERS. Save 50%. Build your own speaker system. "Free catalog" write: **MC GEE RADIO**, RE 1901, McGee Street, Kansas City, MO 64108

PROJECTION TV . . . Convert your TV to project 7 foot picture. Results equal to \$2,500 projector. Total cost less than \$20.00. Plans & lens \$16.00. Illustrated information free. **MACROCOMGA**, Washington Crossing, PA 18977

DIGITAL fuel gauge: 2 1/2 digit, 10 led scale. All parts, PCB layout, \$24.00; Digital auto compass/Plans \$3.50 each, information 50¢. **TS RESEARCH**, 970 South Anaheim Blvd, Suite 113, Anaheim, CA 92805

FREE KIT Catalog

AUTORANGE DIGITAL CAP-METER KIT. Still the best for only \$74.95 contains TEST & EXPERIMENTER'S EQUIP.
Phone 415-447-3433
Write or Phone for FREE CATALOG. Average 1 minute Saturday call is 21¢.

DAGE SCIENTIFIC INSTRUMENTS
BOX 1054R LIVERMORE CA 94550

DIGITAL multimeter kits handheld, best quality 0.1% accuracy. The lowest price in America \$67.50 write: **E. G. TRONICS**, 8254 Greenleaf Circle, Tampa FL 33615

TELEVISION alignment—in minutes—while observing revolutionary pattern on screen. Check RF, IF, video, instantly! So simple and inexpensive it's incredible. Complete plans—\$6.00. Free details. **JOHN KOZULKO**, Box 2702R, Clearwater, FL 33517

COMPUTER calculated earth station data. Pad center line \$5.00. Antenna azimuth and elevation \$3.00. Need site latitude, longitude and satellite of interest. Free sample SASE. **KEN'S CATV SERVICE**, P.O. Box 54, Red Ash, VA 24640

AUTHORIZED **TRS-80** DEALER A301

COMPUTER SPECIALISTS



Up to
15% Discount
on **TRS-80's**

26-1051 4K LEVEL I \$424.00
26-1056 16K LEVEL II \$715.00

1-800-841-0860 TOLL FREE

MICRO MANAGEMENT SYSTEMS, INC.
Downtown Plaza Shopping Center
115 C. Second Ave., S.W.
Cairo, Georgia 31728
(912) 377-7120 Ga. Phone No.

NEW plans. Telephone memory dialer, negative ion generator, burglar alarm, \$3.00 each. Subscription television decoder, \$10.00. Plans include detailed instructions and circuit board patterns. **COLLINS ELECTRONICS**, Box 6424, San Bernardino, CA 92408.

DECODE Morse and RTTY signals off the air with new **Morse-a-Word** or **RTTY reader**. Morse keyboard also available. Kits or factory wired. Send for details. **MICROCRAFT**, Box 513R, Thiensville, WI 53092 (414) 241-8144.

MEASURE microfarads, megohms, moonlight, minutes, motion, more with your constant-add calculator and our \$14.62 module. Easy "one-evening" projects. Applications manual \$1.00 (refundable) and large SASE. **KALTEK**, Box 7462-RE, Rochester, NY 14615

SAVE 90%. Build your own minicomputer. Free details. **DIGITRONICS CORPORATION**, 2723E W. Butler Dr., Phoenix, AZ 85021

SUBSCRIPTION TV decoder circuits. Detailed plans \$4.60, **JOE PO** Box 61, Cumberland, RI 02864

BUILD laser using laser diode 1-1200 watts. Plans \$4.00. **LASERTRONICS** (1) 12320 Spring, Portland, Oregon 97225

ELECTRONIC car horn which toots your favorite tune at 15 watts complete with speaker \$69.95 guaranteed, easy installation. Free details. Kit with simple instructions \$24.95, name your tune. **JHC ELECTRONICS**, P.O. Box 1158, Lando-lakes, FL 33539

LOGIC LAB

TTL CMOS linear breadboards, function generator, six supplies, indicators, switches \$99.95. **CASCADE LABS**, 5637 Bayview Avenue, Richmond, CA 94804

HIGHLY PROFITABLE ONE-MAN ELECTRONIC FACTORY

Investment unnecessary, knowledge not required, sales handled by professionals. Ideal home business. Write today for facts!
Postcard will do. Barta-RE-G, Box 248, Walnut Creek, CA 94597.

BUSINESS OPPORTUNITIES

MECHANICALLY inclined individuals desiring ownership of Small Electronics Manufacturing Business—without investment. Write: **BUSINESS-ES**, 92-R, Brighton 11th, Brooklyn, NY 11235

GOLD . . . from electronics, jewelry, scrap. Guaranteed industry procedures, trade secrets. \$5.95 (Texas + 30¢). **AURYTECH**, MS106, 2806 Geraghty, Austin, TX 78707

PROJECTION TV . . . Make \$200.00+ per evening assembling projectors . . . Easy . . . Results equal to \$2,500 projectors . . . Your total cost less than \$15.00 . . . Plans, lens & dealer's information \$14.00 . . . Illustrated information free . . . **MACROCOMGAX**, Washington Crossing, PA 18977

BULLET ELECTRONICS

PO Box 401244R
Garland TX 75040


NPN HIGH VOLTAGE 1.59



VCEO = 450 VDC IC = 3A (5A Peak)
FOR TV HORIZONTAL SECTIONS; HIGH VOLTAGE REGULATORS
REPLACES: 2N5076, 2N5077, 2N5838, 2N5665, BDY94, BU128, 2SC2121, 2N5840, 2SC1046, 2N5466, TIP556 AND MANY OTHERS.

LM3046	(CA3046) Transistor Array	.75
RCA 40430	400V 6A TRIAC TO-66	.75
CA3086	RCA Transistor Array	.80
LM567	Tone Decoder	.99
CD4046	PLL CMOS	.99
LM3302	Quad Comparator	.89
2SC1849	High Freq NPN TO-92	6/1.00
MPS A20	NPN GEN PUR	8/1.00

Sound Effects Kit \$18.50

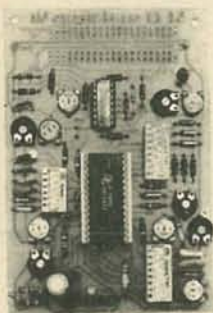

The SE-01 is a complete kit that contains all the parts to build a programmable sound effects generator. Designed around the new Texas Instruments SN76477 Sound Chip, the board provides banks of MINI DIP switches and pots to program the various combinations of the SLF Oscillator, VCO, Noise, One Shot, and Envelope Controls. A Quad Op Amp IC is used to implement an Adjustable Pulse Generator, Level Comparator and Multiplex Oscillator for even more versatility. The 3" x 5" PC Board features a prototype area to allow for user added circuitry. Easily programmed to duplicate Explosions, Phasor Guns, Steam Trains, or almost an infinite number of other sounds. The unit has a multiple of applications. The low price includes all parts, assembly manual, programming charts, and detailed 76477 chip specifications. It runs on a 9V battery (not included). On board 100mA amp will drive a small speaker directly, or the unit can be connected to your stereo with incredible results! (Speaker not included).

• 76477 CHIP IS INCLUDED. EXTRA CHIPS \$3.15 EACH

AY3-8910 PROGRAMMABLE SOUND GENERATOR

The AY3-8910 is a 40 pin LSI chip with three oscillators, three amplitude controls, programmable noise generator, three mixers, an envelope generator, and three D/A converters that are controlled by 8 BIT WORDS. No external pots or caps required. This chip hooked to an 8 bit microprocessor chip or Buss (8080, Z80, 6800 etc.) can be software controlled to produce almost any sound. It will play three note chords, make bangs, whistles, sirens, gunshots, explosions, bleets, whines, or grunts. In addition, it has provisions to control its own memory chips with two IO ports. The chip requires +5V @ 75ma and a standard TTL clock oscillator. A truly incredible circuit.

\$14.95 W/Basic Spec Sheet (4 pages)

60 page manual with S-100 interface instructions and several programming examples, **\$3.00 extra.**

1/2W RESISTOR ASSORTMENT

A good mix of 5% and 10% values in both full lead and PC lead devices. All new, first quality.

(Asst.) 200 pieces/2.00

7 WATT AUDIO AMP KIT

SMALL SINGLE HYBRID IC AND COMPONENTS FIT ON A 2" x 3" PC BOARD (INCLUDED). RUNS ON 12VDC. GREAT FOR ANY PROJECT THAT NEEDS AN INEXPENSIVE AMP. LESS THAN 3% THD @ 5 WATTS. COMPATIBLE WITH SE-01 SOUND KIT. **\$5.95**

ULTRASONIC RELAY KIT

INVISIBLE BEAM WORKS LIKE A PHOTO ELECTRIC EYE. USE UP TO 25 FT. APART. COMPLETE KIT. ALL PARTS & PC BOARDS. **\$21.50**



THE PERFECT TRANSFORMER

117VAC primary, 12VAC secondary @ 200ma
Great for all you CMOS, or low power TTL projects. PC board mount. **99¢ ea.** 3/\$2.50
Size: 1.5" W x 1.25" D x 1.25" H

XAN SUPER DIGITS

.6" JUMBO LED
6920 COMMON CATHODE
6640 COMMON ANODE
.99 7 SEGMENT

NOW A SUPER READOUT AT A SUPER BUY! These are factory fresh prime LED readouts, not seconds or rejects as sold by others. Compare our price and send for yours today, but hurry, the supply is limited!
SPECIFY: COMMON ANODE OR COMMON CATHODE

NEW! MUSIC FOR YOUR EARS

Bullet's **Electronic Music Maker™** Kit has a single 28 Pin Microprocessor Chip with ROM that has been programmed to play the first 6 to 10 notes of the 25 popular tunes listed below. Each tune can easily be addressed individually or played sequentially at the push of a button. The 3 chime sequences are activated at any time by separate switch closures so when used as a doorbell, one door can play songs while two others will play different chimes. The unit has a 5 watt audio amp and will run on either 12VAC or 12VDC. Optional 117VAC transformer is available. Construction is very simple, works with any 8 or 16 ohm speaker, or horn speaker. (Not included.) Tunes can be remotely programmed using a single rotary switch, (not included), if desired.

Complete Kit **\$16.95** Transformer **\$1.35**
(For operation on 117VAC)

Tunes: Toreador * William Tell * Hallelujah Chorus * Star Spangled Banner * Yankee Doodle * America, America * Deutschland Lied * Wedding March * Beethoven's 5th and 9th * Hell's Bells * La Vie En Rose * Star Wars Theme * Clementine * Augustine * Jingle Bells * God Save The Queen * Colonel Bogey * Marcellite * O Sole Mio * Santa Lucia * The End * Blue Danube * Brahms Lullaby * Westminster Chime * Simple Chime * Descending Octave Chime.

PARTS

TL490	Bar/Graph Driver	2.50
7805	5V 1A Regulator	.99
78M05	1/2A TO-5 Reg. 5V (Hse. #)	.60
LM3911	Temp. Transducer	1.10
555	Timer IC	.49
723	Voltage Reg. 14 Pin Dip	.50
7812	1A 12V Reg.	.99
2N6028	P.U.T. W/Specs	.50
IL-1	Opto Isolator W/Specs	.60

- * NO C.O.D.'s
- * SEND CHECK M.O. OR CHARGE CARD NO.
- * PHONE ORDERS ACCEPTED ON VISA AND MASTERCARD ONLY.
- (214) 278-3553**
- * ADD 5% FOR SHIPPING
- * TX. RES. ADD 5% STATE SALES TAX
- * FOREIGN ORDERS ADD 10% (EXCEPT CANADA)
- (20% AIRMAIL) U.S. FUNDS ONLY


catalog free on request

100W CLASS A POWER AMP KIT

Dynamic Bias Class "A" circuit design makes this unit unique in its class. Crystal clear, 100 watts power output will satisfy the most picky fans. A perfect combination with the TA-1020 low T.I.M. stereo pre-amp.

Specifications:

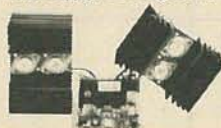- Output power: 100W RMS into 8-ohm
125W RMS into 4-ohm
- Frequency response: 10Hz - 100 KHz
- T.H.D.: less than 0.008%
- S/N ratio: better than 80dB
- Input sensitivity: 1V max.
- Power supply: $\pm 40V @ 5amp$



TA-1000 KIT
\$51.95
Power transformer
\$15.00 each

PROFESSIONAL 10 OCTAVE STEREO GRAPHIC EQUALIZER!!



Graphic equalizer have been used for years in sound studios and concert arenas but were too expensive to be considered for home use. Now we offer you the facility at an affordable price. This unit can extend your control of your Hi-Fi system by minimizing the non-linearities of the combined speaker/room system. Fantastic features as follows:

- 10 double slide controls for two channels
- Cut out rumble, surface noise and hiss
- Minimizes speaker/room non-linearities
- Frequency response from 30Hz to 16KHz
- 10 tone controls plus defeat, monitor and tape selector.
- Control range $\pm 12dB$ in 10 octaves (30Hz, 60Hz, 120Hz, 240Hz, 500Hz, 1KHz, 2KHz, 4KHz, 8KHz, 16KHz.)
- Operating voltage 117V 50/60Hz.

FACTORY ASSEMBLED UNIT, NOT A KIT
SPECIAL PRICE \$117.00 ea

SUB MINI SIZE FET CONDENSER MICROPHONE



Specification:

Sensitivity: $-65dB \pm 3db$
FEQ. Response: 50 Hz - 8 KHz
Output Impedance: 1K ohm max.
Polar Pattern: Omni-directional
Power Supply: 1.5V 10V D.C.
Sound Pressure Level: Max. 120dB
EM4RP \$2.50 ea. or 2 for \$4.50



NEW MARK III 9 Steps 4 Colors LED VU

Stereo level indicator kit with arc-shape display panel!!! This Mark III LED level indicator is a new design PC board with an arc-shape 4 colors LED display (change color from red, yellow, green and the peak output indicated by rose). The power range is very large, from $-30dB$ to $+5dB$. The Mark III indicator is applicable to 1 watt - 200 watts amplifier operating voltage is 3V - 9V DC at max 400 MA. The circuit uses 10 LEDs per channel. It is very easy to connect to the amplifier. Just hook up with the speaker output!

IN KIT FORM \$18.50

SOUND ACTIVATED DISCO LIGHT KIT

Latest design electronic color light organ, with both sound and line input, the three color lights (not included) will change colors with the rhythm of the music; controlled by 3 ranges, low, middle and high. Ideal for party, bar, or home entertainment. Max. controlled output 1000 watts per color (3 colors). Kit includes aluminum cabinet, all electronic parts, P.C. board and transformer.



(Color Organ)
\$45.50 per kit

TY-23

MARK IV 15 STEPS LED POWER LEVEL INDICATOR KIT

This new stereo level indicator kit consists of 36 4-color LED (15 per channel) to indicate the sound level output of your amplifier from $-36dB$ to $+3dB$. Comes with a well-designed silk screen printed plastic panel and has a selector switch to allow floating or gradual output indicating. Power supply is 6V \sim 12V D.C. with THG on board input sensitivity controls. This unit can work with any amplifier from 1W to 200W!

Kit includes 70 pcs. driver transistors, 38 pcs. matched 4-color LED, all other electronic components, PC board and front panel.



MARK IV KIT \$31.50

30W + 30W STEREO HYBRID AMPLIFIER KIT

It works in 12V DC as well! Kit includes 1 PC SANYO STK-043 stereo power amp. IC LM 1458 as pre amp, all other electronic parts, PC Board, all control pots and special heat sink for hybrid. Power transformer not included. It produces ultra hi-fi output up to 60 watts (30 watts per channel) yet gives out less than 0.1% total harmonic distortion between 100Mz and 10KHz.



\$32.50 PER KIT

BATTERY POWERED FLUORESCENT LANTERN

MODEL 888 R

FEATURES

- Circuitry: designed for operation by high efficient, high power silicon transistor which enable illumination maintain in a standard level even the battery supply drops to a certain low voltage.
- 9" 6W cool/daylight miniature fluorescent tube.
- 8 x 1.5V UM-1 (size D) dry cell battery.
- Easy sliding door for changing batteries.
- Stainless reflector with wide angle increasing illumination of the lantern.



\$10.50 EA

STEREO AMPLIFIER



60W
+
60W

COMPLETED UNIT - NOT A KIT!

OCL pre amp. & power stereo amp. with bass, middle, treble 3-way tone control. Fully assembled and tested, ready to work. Total harmonic distortion less than 0.5% at full power. Output maximum is 60 watts per channel at 8 Ω . Power supply is 24 - 36V AC or DC. Complete unit. Assembled \$49.50 ea.
Power transformer \$ 8.50 ea.

5W AUDIO AMP KIT



2 LM 380 with Volume Control
Power Supply 6 18V DC
ONLY \$6.00 EACH

PROFESSIONAL PANEL METERS



- | | |
|-------------|----------|
| A. 0-50UA | 8.50 ea. |
| B. 0-30VDC | 8.50 ea. |
| C. 0-50VDC | 8.50 ea. |
| D. 0-3ADC | 9.00 ea. |
| E. 0-100VDC | 9.00 ea. |

All meters white face with black scales. Plastic cover.

SPECIAL 0.5" LED ALARM CLOCK MODULE

ASSEMBLED! NOT A KIT!

Features: • 4 digits 0.5" LED Displays • 12 hours real time format • 24 hours alarm audio output • 59 min. countdown timer • 10 min. snooze control




ONLY \$7.00 EACH
SPECIAL TRANSFORMER FOR CLOCK
(FREE)

DIGITAL AUTO SECURITY SYSTEM

4 DIGITS PERSONAL CODE!!

SPECIAL \$19.95

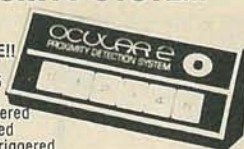

- proximity triggered
- voltage triggered
- mechanically triggered

This alarm protects you and itself! Entering protected area will set it off, sounding your car horn or siren you add. Any change in voltage will also trigger the alarm into action. If cables within passenger compartment are cut, the unit protects itself by sounding the alarm.

3-WAY PROTECTION!

All units factory assembled and tested - Not a Kit!

A NEW LED ARRAY AND DRIVER FOR LEVEL METERS

This series covers a wide range of level indication uses, output and input voltage, time related change, temperature, light measurement and sound level. The problem of uneven brilliance often encountered with LED arrangements as well as design problems caused by using several units of varying size are substantially reduced. 12 LEDs in one bar:

LED ARRAY	
GL-112R3 Red, Red, Red	\$5.50
GL-112N3 Green, Yellow, Red	\$6.50
GL-112M2 Green, Green, Red	\$6.50
GL-112G3 Green, Green, Green	\$6.50



LED DRIVERS

1R 2406G is an I.C. specially designed to drive 12 LED. The number of LED is lineally illuminated according to the control voltage input terminal 21. Operating voltage is 9 12V D.C. \$5.35 EACH

DUEL CHANNEL VU METER
P.C. BOARD AVAILABLE AT \$4.50 EA.

PROFESSIONAL FM WIRELESS MICROPHONE

TECT model WEM-16 is a factory assembled FM wireless microphone powered by an AA size battery. Transmits in the range of 88-108MHz with 3 transistor circuits and an omni-directional electric condenser. Element built-in plastic tube type case; mike is 6 1/4" long. With a standard FM radio, can be heard anywhere on a one-acre lot; sound quality was judged very good.

\$16.50

FLASHER LED

Unique design combines a jumbo red LED with an IC flasher chip in one package. Operates directly from 5V-7V DC. No dropping resistor needed. Pulse rate 3Hz @ 5V 20mA.

2 for \$2.20


BIPOLAR LED RED/GREEN

2 colors in one LED, green and red, changes color when reverse voltage supply. Amazing!
2 FOR \$1.60

LCD CLOCK MODULE!

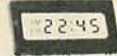• 0.5" LCD 4 digits display • X'tal controlled circuits • D.C. powered (1.5V battery) • 12 hr. or 24 hr. display • 24 hr. alarm set • 60 min. countdown timer • On board dual back-up lights • Dual time zone display • Stop watch function.

NIC1200 (12 hr) \$24.50 EA.
NIC2400 (24 hr) \$26.50 EA



WANT TO BUILD YOUR OWN BLACK MAGIC BOX ON TOP OF THE TV FOR FIRST RUN MOVIES?

We have all the parts including hard to find UHF varactor tuners and P.C. board.
Call us for more information.

FLUORESCENT LIGHT DRIVER KIT



With Case Only
\$6.50 Per Kit

12V DC POWERED
Lights up 8 ~ 15 Watt Fluorescent Light Tubes. Ideal for camper, outdoor, auto or boat. Kit includes high voltage coil, power transistor, heat sink, all other electronic parts and PC Board, light tube not included!

SUPER FM WIRELESS MIC KIT — MARK III



FMC-105
\$11.50 PER KIT

This new designed circuit uses high FET transistors with 2 stages pre amp. Transmits FM Range (88-120 MHz) up to 2 blocks away and with the ultra sensitive condenser microphone that comes with the kit, allows you to pick up any sound within 15 ft. away! Kit includes all electronic parts, OSC coils, and P.C. Board. Power supply 9V D.C.

PRESS-A-LIGHT SELF GENERATED FLASHLIGHT

EXCLUSIVE! \$3.95 ea
Model F-179



Never worry about battery, because it has none! Easy to carry in pocket and handy to use. Ideal for emergency light. It generates its own electricity by squeezing grip lever. Put one in your car, boat, camper or home. You may need it some time!

ELECTRONIC DUAL SPEAKER PROTECTOR



KIT FORM
\$8.75 EA.

Cut off when circuit is shorted or over load to protect your amplifier as well as your speakers. A must for OCL circuits.

"FISHER" 30 WATT STEREO AMP



Super Buy
Only \$18.50

MAIN AMP (15W x 2)
Kit includes 2 pcs. Fisher PA 301 Hybrid IC all electronic parts with PC Board. Power supply ± 16V DC (not included). Power band with (KF 1% ± 3dB). Voltage gain 33dB. 20Hz - 20KHz.

UNIVERSAL PROJECT BOARD

All P.C. boards are made from high quality phenolic, predrilled in different patterns for different purpose. All boards 1/16" single sided copper. Hole spacing is standard 0.1". Fits all kinds of I.C. transistors, capacitors and resistors. Ideal for school projects, engineering designs and prototyping.



SB072

CIRCUIT FIT

BEL-008



M-34

BEL101

BEL202

BEL101	3 1/2" x 6"	\$1.75 EA.
SB072	3 1/2" x 6"	\$1.75 EA.
M-34	3" x 5"	\$1.75 EA.
CIRCUIT FIT	3" x 3 1/2"	\$1.25 EA.
BEL202	3" x 4"	\$1.25 EA.
BEL-008	2 1/4" x 5 1/2"	\$1.25 EA.

PUSH-BUTTON SWITCH



N/Open Contact
Color: Red, White, Blue, Green, Black
3/\$1.00
N/Close also Available
50¢ each
LARGE QTY. AVAILABLE

HEAVY DUTY CLIP LEADS



10 pairs — 5 colors Alligator clips on a 22" long lead. Ideal for any testing.
\$2.20/pack

BATTERIES

PK/\$10.00
2 PK/\$19.00



NICKEL CADMIUM BATTERY PACK 'D' SIZE

ILLUSTRATED LESS COVER

Output: 3.6 Volts @ 3.0 Amp/Hour. Consists of three each 1.2 Volt "D" size Nickel Cadmium Cells stacked and plastic film encapsulated. Tabs are provided at each end for electrical connections. The individual cells can be cut apart if desired. Rated recharge rate is 30 mA, 14-18 hours. Size: 1 1/4" dia. x 7" long. New Shpg. Wt. each pack, 1 lb.

"C" SIZE BATTERY PACK

10 C size ni-cd battery in dng pack, gives out 12.5V D.C. 1.8 amp per hour. All fresh code, pull-out from movie cameras. Can be disconnected to use as single c cells. Hard to find \$15.00 per pack of 10 batteries

ELECTRONIC ALARM SIREN COMPLETE UNIT



AU-999 \$7.50

Ideal for use as an Alarm Unit or hookup to your car back-up to make a reverse indicator. Light Output up to 130dB. Voltage supply 6 12V

SUB MINIATURE TOGGLE SWITCH

SPST 2 FOR 2.80 SPDT 2 FOR 3.20
6 AMP 125V AC CONTACT

TRANSFORMERS ALL 117 VOLT INPUT

30V CT	4 AMP	\$8.50 EA.
36V CT	3 AMP	\$10.50 EA.
48V CT	3 AMP	\$10.50 EA.
24V CT	0.5 AMP	\$3.00 EA.
18V CT	0.5 AMP	\$3.00 EA.
12V CT	0.5 AMP	\$2.50 EA.
6.3V	0.5 AMP	\$2.00 EA.

AC POWER SUPPLY

12V AC	Output	200 MA	\$2.75 EA.
16V CT AC	Output	100 MA	\$2.10 EA.
6V DC	Output	120 MA	\$1.90 EA.
12V DC	Output	100 MA	\$1.90 EA.

ULTRASONIC SWITCH KIT



Kit includes the Ultra Sonic Transducers, 2 PC Boards for transmitter and receiver. All electronic parts and instructions. Easy to build and a lot of uses such as remote control for TV, garage door, alarm system or counter. Unit operates by 9-12 DC. \$15.50

COMPLETE TIME MODULE

0.3" digits LCD Clock Module with month and date, hour, minute and seconds. As well as stop watch function!! Battery and back up light is with the module. Size of the module is 1" dia. Ideal for use in auto panel, computer, instrument and many others!
\$8.95 EACH

SOUND ACTIVATED SWITCH

All parts completed on a PC Board SCR will turn on relay, buzzer or trigger other circuit for 2 - 10 sec. (adjustable). Ideal for use as door alarm, sound controlled toys and many other projects. Supply voltage 4.5V 9V D.C. 2 for \$3.00

FM WIRELESS MIC KIT

It is not a pack of cigarettes. It is a new FM wireless mic kit! New design PC board fits into a plastic cigarette box (case included). Uses a condenser microphone to allow you to have a better response in sound pick-up. Transmits up to 350 ft. With an LED indicator to signal the unit is on #FMM2 KIT FORM \$7.95



REGULATED DUAL VOLTAGE SUPPLY KIT

±4 30V DC 800 MA adjustable, fully regulated by Fairchild 78MG and 79MG voltage regulator I.C. Kit includes all electronic parts, filter capacitors, I.C. heat sinks and P.C. board.

\$12.50 PER KIT

AA SIZE NI-CD SPECIAL SALE

RECHARGEABLE BATTERIES LIMITED QUANTITY AVAILABLE

POCKET SIZE AM-FM RADIO TR-945 with LED TUNING EYE

New design body with see thru speaker grill.
SPECIAL PRICE \$16.50 EACH



TR-945

POWER SUPPLY KIT

0-30V D.C. REGULATED
Uses UA723 and ZN3055 Power TR output can be adjusted from 0-30V, 2 AMP. Complete with PC board and all electronic parts. Transformer for Power Supply, 0-30 Power Supply 2 AMP 24V x 2 \$8.50 \$10.50 each



I.C. TEST CLIPS

Same as the E-Z clips \$2.75
With 20" Long Leads
In Black and Red Colors per pair



SOUND GENERATOR I.C.

Creates almost any type of sound — gun shot, explosion, train, car crash, star war, birds, organ ext. A built-in audio amplifier provides high level output. Operates from one 9V battery, 28 pin dip; we supply the datas. \$2.90 EACH

ELECTRONIC SWITCH KIT

CONDENSER TYPE
Touch On Touch Off
uses 7473 I.C. and 12V relay
\$5.50 each



1 WATT AUDIO AMP

All parts are pre-assembled on a mini PC Board. Supply Voltage 6 9V D.C. SPECIAL PRICE \$1.95 ea.



LOW TIM DC STEREO PRE-AMP KIT TA-10 20

Incorporates brand-new D.C. design that gives a frequency response from 0Hz — 100KHz ± 0.5dB! Added features like tone defeat and loudness control let you tailor your own frequency supplies to eliminate power fluctuation!
Specifications: • T.H.D. less than .005% • T.I.M. less than .005% • Frequency response: DC to 100KHz ± 0.5dB • RIAA deviation: ± 0.2dB • S/N ratio: better than 70dB • Sensitivity: Phono 2MV 47K/Aux. 100MV 100K • Output level: 1.3V • Max. output: 15V • Tone control: bass ± 10dB @ 50Hz/treble ± 10dB @ 15Hz • Power supply: ± 24 D.C. @ 0.5A
Kit comes with regulated power supply, all you need is a 48V C.T. transformer @ 0.5A.

ONLY \$44.50
X'former \$4.50 ea.

SOLID STATE ELECTRONIC BUZZER

Mini size 1" x 3/4" x 3/4"
Supply voltage 1.5V - 12V
Ideal for Alarm or Tone Indicator



\$1.50 each

FORMULA INTERNATIONAL INC.

Shipping & Handling Charges	Under \$50.00 purchase	Over \$50.00 purchase
Inside California	15%	10%
Outside Calif. (includes Mexico & Canada)	18%	20%
Overseas	25%	20%

Minimum Order \$18.00/Calif. Residents Add 6% Sales Tax.
Phone Orders Accepted on Visa or MC ONLY. NO C.O.D./Store Hours 10-7 Mon. thru Sat.

12603 CRENSHAW BLVD., HAWTHORNE, CA 90250
PHONE: (213) 973-1921 • (213) 479-5162

Send \$1.00 For Detailed Catalogue

9/80

MICRO MART

552 Summit Ave.
Westfield, N.J. 07090
(201) 654-6008

MOTION DETECTOR: Features include transparent, optical IC completely assembled on circuit board with necessary capacitors. Extensive specs and application notes included. \$5.00

CRYSTALS—3.579545 MHz 99¢
6.0 MHz 2.95

JUMBO LED's
Green, 7/1.00-Yellow, 7/1.00-Red, 10/1.00
100/13.00 100/13.00 100/9.00
MOUNTING CLIPS—12/1.00

7 SEG Displays (comp. grade)
3"/95¢-6"/1.45 (specify am. or cath.)

AM/FM RADIO CHIP—(#4408) 2.00 or 3/5.00
Complete AM/FM IC-external IF required

DIPPED TANTALUMS
.47 µf 35V (1" leads) 10/1.00

SUPER SUB MINI LYTICS
(1" rad. leads, by Nichicon)
1000µf 50V (1 1/4" L x 1/4" W), 75¢ or 10/6.00
47 µf 25V (7/8" L x 1/4" W), 10/\$1.00
400µf 330V (photo flash or laser circuits)-2/1.00

COMPUTER GRADE TWIST LOCKS
3200µf 50V (ideal for power supplies) 2.00
1000µf 50V—1.00 1000µf 185V—2.00

DISCS—001 1KV 25/1.00, 1.50V 15/1.00

HEAT SENSITIVE SWITCH—4/1.00
self contained unit opens at 150 C

9 DIGIT FLUORESCENT DISPLAY by NEC
complete with driving circuitry-2/5.00

EXTRA LOUD 9V BUZZER—3/2.00

WALL PLUG ADAPTER—5VDC @ 160ma-1.50
6.3V 1.2 Amp Transformer—1.75

MINI AUDIO TRANSFORMERS—3/1.00

DIGITAL MOTION/UNIT COUNTER MODULE
(Fairchild) with large 4 digit display & specs-7.00

8035 Microprocessor, 17.00

INTERFACE CHIP-D8243
16 line I/O extender for all single chip µ Ps 5.75

SUBSCRIPTION TV EDUCATIONAL KIT

If there's a TV channel in your area which you can't tune to and get a proper picture or sound, chances are you're seeing a subscription TV signal. Now you can find the signal. Our 24-page illustrated manual contains a description of how such a system works and includes construction details for building a circuit to restore the audio and video signals to their original state. Our kit is proven to work in many areas of the U.S., but does require use of a scope and is not intended for beginners.

Manual only \$15.00
Drilled and etched PC project board 23.00
Board and manual 35.00
Complete kit 69.00

FREQUENCY COUNTER CHIP

ICM 7225 IPL
(40 pin), with on board dividers, decoders/drivers. 18.95-specs included

ZENER DIODES—20V 1 amp 10/1.00

TV SATELLITE TRANSISTOR


MRF 901 (prime) \$4.50

LINEAR			
LM 323K	5.00	LM 1303	1.50
LM 300H	75	LM 1304	.95
LM 301AN	33	LM 1305	1.15
LM 307H	50	LM 1307	.90
LM 307	35	LM 1307E	.90
LM 308H	95	LM 1310	1.75
LM 308	90	LM 1391	1.50
LM 310	1.05	LM 1414	2.25
LM 311H	85	LM 1800	2.90
LM 317K	5.00	LM 1808	2.75
LM 318H	1.25	LM 1820	1.75
LM 320K-15	1.15	LM 1828	1.75
LM 320K-12	1.15	LM 1830	1.50
LM 324	1.25	LM 1841	1.75
LM 325	1.85	LM 1848	1.75
LM 339J	1.00	LM 1889	4.50
LM 340K-12	1.25	LM 2111	1.60
LM 341P-12	1.25	LM 2113	1.75
LM 343H	3.50	LM 2907	2.40
LM 373	2.95	LM 2917	1.95
LM 377	2.00	LM 3046	1.10
LM 380	1.15	LM 3054	1.50
LM 381	1.50	LM 3064	2.00
LM 384	1.85	LM 3065	1.50
LM 386	1.50	LM 3067	2.50
LM 389	1.50	LM 3070	2.50
LM 390	1.95	LM 3071	2.00
LM 746	2.50	LM 3075	2.75
LM 748CN	.39	LM 3089	1.75
		LM 3900	.75

Terms MICRO-MART accepts Visa, MC, and telephone COD'S. Foreign orders \$50.00 minimum plus shipping-US funds only. Orders under \$10.00 include \$2.00 for shipping/handling. All components guaranteed or money refunded. Immediate shipping. N.J. residents add 5% sales tax.

MICRO-MART • 552 SUMMIT AVE., WESTFIELD, N.J. 07090 • (201) 654-6008

CIRCLE 34 ON FREE INFORMATION CARD

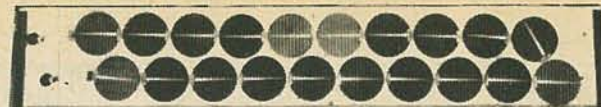

Electricity from the sun.

5 Volt panel 1/4 amp \$50 2.5 Volt panel 1/2 amp \$40

GIANT 3 1/2 inch cell, delivers 1 amp \$8.50

Above cell with special motor & prop, runs in sun \$10.25

Computer video monitor chassis 9 inch, 12 volt used \$40

Computer video monitor chassis 12 inch, new \$50

Hy Gain CB chassis, trunk mount \$9.00



SEE IN THE DARKNESS
IR viewer, portable, new with choice of one lens...close up, telephoto or gen. purpose. Requires 6 volt DC btry. \$250

Parallel ASCII-II Keyboard

Unused \$50.00

Red LED's large 10/\$1.00

Shipping extra on all merchandise

Meshna Inc., PO Box 62, E. Lynn, Mass. 01904

CIRCLE 22 ON FREE INFORMATION CARD

HOME STUDY COURSE ON CASSETTE



Each course below includes a special course book plus two cassettes, for a total course length of 2 1/2 hours. The lecture is completely coordinated to the pages of the book, and cassettes can be played on any standard cassette player.

S1-INTRODUCTION TO MICROPROCESSORS

For Non-Specialists. Course contains: Definitions • Application • Evaluation Terms • System Components • 2.5 hrs.

\$2995

• NO TECHNICAL BACKGROUND ASSUMED •

S2-PROGRAMMING MICROPROCESSORS

For the student who has completed S1. GOAL: To provide an over-all and practical understanding of the concepts of Micro Computer Programming. 2.5 hours.

\$2995



IO120 \$699.00

2114L
1024x4 Static RAM \$450
450 ns

8038C
VCO Waveform Gen. w/sine \$265


TRS-80
16K Memory Add-On \$49.95
KIT with jumpers and instructions



POWER CONTROLLER
8outlet-6switched
EMI filtered
Circuit Breaker \$87.50

EPROM'S

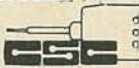2708 \$6.75
1K x 8 450NS
8 FOR \$48.50
2716 \$18.95
16K (2K x 8) 450NS
8 FOR \$142.95
2732 \$49.95
32K (4096 x 8)




Take 20% off 'L5' prices

74LS00	38	74LS160	75
74LS03	34	74LS160	95
74LS04	38	74LS161	100
74LS08	35	74LS162	95
74LS09	38	74LS163	95
74LS10	28	74LS164	115
74LS12	28	74LS165	89
74LS13	28	74LS170	195
74LS15	38	74LS174	90
74LS16	38	74LS175	90
74LS18	39	74LS190	110
74LS19	36	74LS193	95
74LS20	36	74LS195	95
74LS22	39	74LS196	85
74LS23	36	74LS211	140
74LS24	39	74LS240	245
74LS28	39	74LS241	245
74LS30	35	74LS243	230
74LS31	35	74LS244	245
74LS32	35	74LS245	695
74LS33	65	74LS253	95
74LS34	95	74LS257	95
74LS35	115	74LS259	95
74LS36	45	74LS260	85
74LS37	70	74LS269	55
74LS38	70	74LS283	100
74LS39	70	74LS283	185
74LS40	45	74LS289	120
74LS41	48	74LS289	120
74LS42	48	74LS290	120
74LS43	48	74LS290	120
74LS44	50	74LS307	95
74LS45	50	74LS307	95
74LS46	50	74LS307	95
74LS47	50	74LS307	95
74LS48	50	74LS307	95
74LS49	50	74LS307	95
74LS50	50	74LS307	95
74LS51	50	74LS307	95
74LS52	50	74LS307	95
74LS53	50	74LS307	95
74LS54	50	74LS307	95
74LS55	50	74LS307	95
74LS56	50	74LS307	95
74LS57	50	74LS307	95
74LS58	50	74LS307	95
74LS59	50	74LS307	95
74LS60	50	74LS307	95
74LS61	50	74LS307	95
74LS62	50	74LS307	95
74LS63	50	74LS307	95
74LS64	50	74LS307	95
74LS65	50	74LS307	95
74LS66	50	74LS307	95
74LS67	50	74LS307	95
74LS68	50	74LS307	95
74LS69	50	74LS307	95
74LS70	50	74LS307	95
74LS71	50	74LS307	95
74LS72	50	74LS307	95
74LS73	50	74LS307	95
74LS74	50	74LS307	95
74LS75	50	74LS307	95
74LS76	50	74LS307	95
74LS77	50	74LS307	95
74LS78	50	74LS307	95
74LS79	50	74LS307	95
74LS80	50	74LS307	95
74LS81	50	74LS307	95
74LS82	50	74LS307	95
74LS83	50	74LS307	95
74LS84	50	74LS307	95
74LS85	50	74LS307	95
74LS86	50	74LS307	95
74LS87	50	74LS307	95
74LS88	50	74LS307	95
74LS89	50	74LS307	95
74LS90	50	74LS307	95
74LS91	50	74LS307	95
74LS92	50	74LS307	95
74LS93	50	74LS307	95
74LS94	50	74LS307	95
74LS95	50	74LS307	95
74LS96	50	74LS307	95
74LS97	50	74LS307	95
74LS98	50	74LS307	95
74LS99	50	74LS307	95
74LS100	50	74LS307	95

1980 "IC" Master

\$47.95

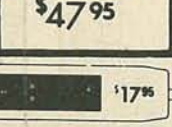

LOGIC PROBE KIT \$17.95

APPLE II Computer with full 48K of memory!



\$1099.00

APPLE EXPANSION KIT
16K Memory Add-On

\$4750

PLEXIGLASS COVER as shown \$24.95

MEMORY ADD-ON KIT INCLUDES INSTRUCTIONS RAMS AND JUMPERS NO TOOLS REQUIRED

5100 MEMORY BOARD

16K STATIC RAM \$249.00

ASSEMBLED & TESTED

California Computer Systems

8212 I/O port \$2.95

VOLTAGE REGULATORS

NEGATIVE POSITIVE
7805/5V 7805/5V 7815/15V
7808/8V 7808/8V 7818/18V
7815/15V 7808/8V 7824/24V
7818/18V 7812/12V

video 100

\$139.00

Leedex Corp.

12" BLACK & WHITE LOW COST VIDEO MONITOR

CONCORD COMPUTER COMPONENTS

1971 SOUTH STATE COLLEGE ANAHEIM, CA. 92806

VISA MASTERCHARGE (714) 937-0637 MINIMUM ORDER \$10.00
CHECK OR M O ADD \$1.50 FOR FRT
NO COD We stock and sell over 12,000 types of semiconductors. CAL RES ADD 6%

CIRCLE 52 ON FREE INFORMATION CARD

We now have available a bunch of goodies too good to bypass. Items are limited so order today

Call Your Phone Order in Today

TERMS: Satisfaction guaranteed or money refunded. COD add \$1.50. Minimum order \$6.00. Orders under \$10.00 add \$7.50. Add 5% for postage, insurance, handling. Overseas add 15%. NY residents add 7% tax.

MINI KITS - YOU HAVE SEEN THESE BEFORE NOW HERE ARE OLD FAVORITE AND NEW ONES TOO. GREAT FOR THAT AFTERNOON HOBBY.

FM MINI MIKE

super high performance FM wireless mike kit! Transmits a stable signal up to 300 yards with exceptional audio quality by means of its built in electret mike. Kit includes case, mike, on-off switch, antenna, battery and super instructions. This is the finest unit available.

M-3 Kit \$14.95
M-3 Wired and Tested 19.95

Color Organ

See music come alive! 3 different lights flicker with music. One light each for, high, mid-range and lows. Each individually adjustable and drives up to 300 W. runs on 110 VAC.

Complete kit, ML-1 \$8.95

Video Modulator Kit

Converts any TV to video monitor. Super stable, tunable over ch 4-6. Runs on 5-15V, accepts std. video signal. Best unit on the market! Complete kit, VD-1 \$7.95

Led Blink Kit

A great attention getter which alternately flashes 2 jumbo LEDs. Use for name badges, buttons, warning panel lights, anything! Runs on 3 to 15 volts. Complete kit, BL-1 \$2.95

Super Sleuth

A super sensitive amplifier which will pick up a pin drop at 15 feet! Great for monitoring baby's room or as general purpose amplifier. Full 2 W rms output, runs on 6 to 15 volts, uses 8-45 ohm speaker. Complete kit, BN-9 \$5.95

CPO-1

Runs on 3-12 Vdc 1 wall out, 1 KHZ good for CPO, Alarm, Audio Oscillator. Complete kit \$2.95

CLOCK KITS

Your old favorites are here again. Over 7,000 Sold to Date. Be one of the gang and order yours today!

Try your hand at building the finest looking clock on the market. Its satin finish anodized aluminum case looks great anywhere, while six .4" LED digits provide a highly readable display. This is a complete kit, no extras needed, and it only takes 1-2 hours to assemble. Your choice of case colors: silver, gold, black (specify).
Clock kit, 12/24 hour, DC-5 \$24.95
Clock with 10 min. ID timer, 12/24 hour, DC-10 \$29.95
Alarm clock, 12 hour only, DC-8 \$29.95
12V DC car clock, DC-7 \$29.95

For wired and tested clocks add \$10.00 to kit price. Specify 12 or 24 hr. format

M Wireless Mike Kit

Transmits up to 300' to any FM broadcast radio. Uses any type of mike. Runs on 3 to 9V. Type FM-2 is added sensitive mike preamp.

M-1 kit \$3.95 FM-2 kit \$4.95

Whisper Light Kit

An interesting kit, small mike picks up sounds and converts them to light. The louder the sound, the brighter the light. Includes mike, controls up to 300 W, runs on 110 VAC. Complete kit, WL-1 \$6.95

Tone Decoder

A complete tone decoder on a single PC board. Features: 400-5000 Hz adjustable range via 20 turn pot, voltage regulation, 567 IC. Useful for touch-tone burst detection, FSK, etc. Can also be used as a stable tone encoder. Runs on 5 to 12 volts. Complete kit, TD-1 \$5.95

Car Clock

The UN-KIT, only 5 solder connections

Here's a super looking, rugged and accurate auto clock, which is a snap to build and completely assembled. You only solder 3 wires and 2 switches, takes about 15 minutes! Display is bright green with automatic brightness control photocell - assures you of a highly readable display, day or night. Comes in a satin finish anodized aluminum case which can be attached 5 different ways using 2 sided tape. Choice of silver, black or gold case (specify).

DC-3 kit, 12 hour format \$22.95
DC-3 wired and tested \$29.95

Universal Timer Kit

Provides the basic parts and PC board required to provide a source of precision timing and pulse generation. Uses 555 timer IC and includes a range of parts for most timing needs.

UT-5 Kit \$5.95

Mad Blaster Kit

Produces LOUD ear shattering and attention getting siren like sound. Can supply up to 15 watts of obnoxious audio. Runs on 6-15 VDC

MB-1 Kit \$4.95

Siren Kit

Produces upward and downward wail characteristic of a police siren. 5 W peak audio output, runs on 3-15 volts, uses 3-45 ohm speaker. Complete kit, SM-3 \$2.95

60 Hz Time Base
Runs on 5-15 VDC. Low current (2.5ma) 1 min/month accuracy TB-7 Kit \$5.50
TB-7 Assy \$9.95

Calendar Alarm Clock

The clock that's got it all: 6-5" LEDs, 12/24 hour, snooze, 24 hour alarm, 4 year calendar, battery backup, and lots more. The super 7001 chip is used. Size: 5x4x2 inches. Complete kit, less case (not available) \$34.95

Under Dash Car Clock

12/24 hour clock in a beautiful plastic case features: 6 jumbo RED LEDs, high accuracy (.001%), easy 3 wire hookup, display blanks with ignition, and super instructions. Optional dimmer automatically adjusts display to ambient light level. DC-11 clock with mtg. bracket \$27.95 kit
DM-1 dimmer adapter \$2.50
Add \$10.00 Assy. and Test

PARTS PARADE

IC SPECIALS

LINEAR	TTL
01 \$1.50 24 \$1.50 80 \$1.50 55 \$1.45 56 \$1.00 65 \$1.00 66 \$1.00 47 \$1.25 45B \$1.50 900 \$1.50 814 \$2.95 1038 \$2.95	74S00 \$1.40 7447 \$1.65 7475 \$1.50 7490 \$1.50 74196 \$1.35
CMOS	SPECIAL
011 \$1.50 013 \$1.50 046 \$1.85 049 \$1.50 059 \$0.00 511 \$2.00 518 \$1.35 639 \$1.75	11C90 \$15.00 10116 \$1.25 7208 \$17.50 7207A \$5.50 7216D \$21.00 7107C \$12.50 5314 \$2.95 5375AB/G \$2.95 7001 \$6.50

Resistor Ass't	Crystals
Assortment of Popular values - 1/4 watt. Cut lead for PC mounting, 1/2" center, 1/8" leads, bag of 300 or more. \$1.50	3.579545 MHZ \$1.50 10.00000 MHZ \$5.00 5.248800 MHZ \$5.00
Switches	AC Adapters
Mini toggle SPDT \$1.00 Red Pushbuttons N.O. 3/\$1.00	Good for clocks, nicad chargers, all 110 VAC plug one end 8.5 vdc @ 20 mA \$1.00 16 vdc @ 160mA \$2.50 12 vdc @ 250mA \$3.00
Earphones	Solid State Buzzers
3" leads, 8 ohm, good for small tone speakers, alarm clocks, etc. 5 for \$1.00	small buzzer 450 Hz, 86 dB, sound output on 5-12 vdc at 10-30 mA, TTL compatible. \$1.50
Slugs Tuned Coils	AC Outlet
Small 3/16" Hex Slugs turned coil, 3 turns. 10/\$1.00	Panel Mount with Leads 4/\$1.00
CAPACITORS	DC-DC Converter
TANTALUM Dipped Epoxy 1.5 uF 25V 3/\$1.00 1.8 uF 25V 3/\$1.00 22 uF 25V 3/\$1.00	+5 vdc input prod. -9 vdc @ 30ma +9 vdc produces -15 vdc @ 35ma \$1.25
ALUMINUM Electrolytic 1000 uF 16V Radial \$3.50 500 uF 20V Axial \$3.50 150 uF 16V Axial \$1.00 10 uF 15V Radial 10/\$1.00	25K 20 Turn Trim Pot \$1.00 1K 20 Turn Trim Pot \$1.50
DISK CERAMIC 01 16V disk 20/\$1.00 1 16V 15/\$1.00 001 16V 20/\$1.00 100 pF 20/\$1.00 047 16V 20/\$1.00	Ceramic IF Filters Mini ceramic filters 7 KHz B. W. 455KHz \$1.50 ea.
FERRITE BEADS	Trimmer Caps
With info and specs 15/\$1.00 6 Hole Balun Beads 5/\$1.00	Sprague - 3-40 pF Stable Polypropylene .50 ea.

READOUTS

Sockets
8 Pin 10/\$2.00 14 Pin 10/\$2.00 16 Pin 10/\$2.00 24 Pin 4/\$2.00 28 Pin 4/\$2.00 40 Pin 3/\$2.00

TRANSISTORS

2N3904 NPN 15/\$1.00 2N3906 PNP 15/\$1.00 2N4403 PNP 15/\$1.00 2N4410 NPN 15/\$1.00 2N4916 FET 4/\$1.00 2N5401 PNP 5/\$1.00 2N6028 4/\$1.00 2N3771 NPN Silicon 1.50 2N5179 UHF NPN 3/\$2.00 Power Tab NPN 40W 3/\$1.00 Power Tab PNP 40W 3/\$1.00 MPP 102/2N5484 4.50 NPN 3904 Type 50/\$2.50 PNP 3906 Type 50/\$2.50 2N3055 1.50 2N2646 UJT 3/\$2.00
--

Diodes	Crystal Microphone	Mini RG-174 Coax
5.1 V Zener 20/\$1.00 1N914 Type 50/\$1.00 1KV 2Amp 8/\$1.00 100V 1Amp 15/\$1.00	Small 1" diameter 1/8" thick crystal mike cartridge 7K5	10 ft. for \$1.00
Coax Connector	9 Volt Battery Clips	Connectors
Chassis mount BNC type \$1.00	Nice quality clips 5 for \$1.00 1/4" Rubber Grommets 10 for \$1.00	6 pin type gold contacts for MA-1003 car clock module price .75 ea.
Parts Bag	Leds	Varactors
Asst of chokes, disc. caps, tant. resistors, transistors, diodes, MICA caps etc. sm. bag (100 pc) \$1.00 lg. bag (300 pc) \$2.50	- your choice, please specify - Mini Red, Jumbo Red, High Intensity Red, Illuminator Red 8/\$1 Mini Yellow, Jumbo Yellow, Jumbo Green 6/\$1	Motorola MV 2209 30 PF Nominal cap 20-80 PF - Tunable range - .50 each or 3/\$1.00

Audio Prescaler

Make high resolution audio measurements, great for musical instrument tuning, PL tones, etc. Multiplies audio UP in frequency, selectable x10 or x100, gives .01 HZ resolution with 1 sec. gate time! High sensitivity of 25 mv, 1 meg input z and built-in filtering gives great performance. Runs on 9V battery, all CMOS. PS-2 kit \$29.95
PS-2 wired \$39.95

600 MHz PRESCALER

Extend the range of your counter to 600 MHz. Works with all counters. Less than 150 mv sensitivity. specify -10 or -100
Wired, tested, PS-1B \$59.95
Kit, PS-1B \$44.95

30 Watt 2 mtr PWR AMP

Simple Class C power amp features 8 times power gain, 1 W in for 8 out, 2 W in for 15 out, 4W in for 30 out. Max output of 35 W, incredible value, complete with all parts, less case and T-R relay. PA-1, 30 W pwr amp kit \$22.95
PA-1, RF sensed T-R relay kit 6.95

MRF-238 transistor as used in PA-1

8-10db gain 150 mhz \$11.95

Power Supply Kit

Complete triple regulated power supply provides variable 6 to 18 volts at 200 ma and +5 at 1 Amp. Excellent load regulation, good filtering and small size. Less transformers, requires 6.3 V 1A 1 and 24 VCT. Complete kit, PS-3LT \$6.95

RF actuated relay senses RF (1W) and closes DPDT relay.

For RF sensed T-R relay TR-1 Kit \$6.95

OP-AMP Special

BI-FET LF 13741 - Direct pin for pin 741 compatible, but 500,000 MEG input z, super low 50 pa input current, low power drain.
50 for only \$9.00 10 for \$2.00

Shrink Tubing Nubs

Nice precut pieces of shrink size: 1" x 1/4" shrink to 1/8". Great for splices. 50/\$1.00

Regulators

7812 \$1.00
7815 \$1.00
7905 \$1.25
7912 \$1.25
7915 \$1.25

Mini TO-92 Heat Sinks

Thermalloy Brand 5 for \$1.00
To-220 Heat Sinks 3 for \$1.00

Opto Isolators - 4N28 type

Opto Reflectors - Photo diode + LED \$1.00 ea.

Molex Pins

Molex already precut in length of 7. Perfect for 14 pin sockets. 20 strips for \$1.00

CDS Photocells

Resistance varies with light, 250 ohms to over 3 meg 3 for \$1.00

7400 TTL

SN7400N .20	SN7472N .29	SN74160N .89
SN7401N .20	SN7473N .35	SN74161N .89
SN7402N .20	SN7474N .49	SN74162N .89
SN7403N .20	SN7475N .49	SN74163N .89
SN7404N .25	SN7476N .50	SN74164N .89
SN7405N .20	SN7477N .50	SN74165N .89
SN7406N .20	SN7478N .50	SN74166N .89
SN7407N .29	SN7479N .50	SN74167N .89
SN7408N .20	SN7480N .50	SN74168N .89
SN7409N .20	SN7481N .50	SN74169N .89
SN7410N .18	SN7482N .50	SN74170N .155
SN7411N .18	SN7483N .69	SN74171N .155
SN7412N .20	SN7484N .69	SN74172N .155
SN7413N .20	SN7485N .69	SN74173N .155
SN7414N .20	SN7486N .69	SN74174N .155
SN7415N .20	SN7487N .69	SN74175N .100
SN7416N .20	SN7488N .69	SN74176N .100
SN7417N .20	SN7489N .69	SN74177N .79
SN7418N .20	SN7490N .69	SN74178N .79
SN7419N .20	SN7491N .69	SN74179N .79
SN7420N .20	SN7492N .69	SN74180N .79
SN7421N .29	SN7493N .65	SN74181N .75
SN7422N .29	SN7494N .65	SN74182N .75
SN7423N .29	SN7495N .65	SN74183N .75
SN7424N .29	SN7496N .65	SN74184N .75
SN7425N .29	SN7497N .65	SN74185N .75
SN7426N .29	SN7498N .65	SN74186N .75
SN7427N .29	SN7499N .65	SN74187N .75
SN7428N .29	SN7500N .65	SN74188N .75
SN7429N .29	SN7501N .65	SN74189N .75
SN7430N .20	SN7502N .65	SN74190N .75
SN7431N .20	SN7503N .65	SN74191N .75
SN7432N .20	SN7504N .65	SN74192N .75
SN7433N .20	SN7505N .65	SN74193N .75
SN7434N .20	SN7506N .65	SN74194N .75
SN7435N .20	SN7507N .65	SN74195N .75
SN7436N .20	SN7508N .65	SN74196N .75
SN7437N .20	SN7509N .65	SN74197N .75
SN7438N .20	SN7510N .65	SN74198N .75
SN7439N .20	SN7511N .65	SN74199N .75
SN7440N .20	SN7512N .65	SN74200N .75
SN7441N .89	SN7513N .65	SN74201N .75
SN7442N .89	SN7514N .65	SN74202N .75
SN7443N .89	SN7515N .65	SN74203N .75
SN7444N .75	SN7516N .65	SN74204N .75
SN7445N .75	SN7517N .65	SN74205N .75
SN7446N .75	SN7518N .65	SN74206N .75
SN7447N .75	SN7519N .65	SN74207N .75
SN7448N .75	SN7520N .65	SN74208N .75
SN7449N .75	SN7521N .65	SN74209N .75
SN7450N .20	SN7522N .65	SN74210N .75
SN7451N .20	SN7523N .65	SN74211N .75
SN7452N .20	SN7524N .65	SN74212N .75
SN7453N .20	SN7525N .65	SN74213N .75
SN7454N .20	SN7526N .65	SN74214N .75
SN7455N .20	SN7527N .65	SN74215N .75
SN7456N .20	SN7528N .65	SN74216N .75
SN7457N .20	SN7529N .65	SN74217N .75
SN7458N .20	SN7530N .65	SN74218N .75
SN7459N .20	SN7531N .65	SN74219N .75
SN7460N .20	SN7532N .65	SN74220N .75

CMOS

CD4000 .39	CD4070 .55
CD4001 .39	CD4071 .55
CD4002 .39	CD4072 .55
CD4006 1.19	CD4073 1.39
CD4007 .25	CD4074 1.39
CD4009 .49	CD4075 1.39
CD4010 .49	CD4076 1.39
CD4011 .39	CD4077 1.39
CD4012 .25	CD4078 1.39
CD4013 .49	CD4079 1.39
CD4014 .39	CD4080 1.39
CD4015 1.19	CD4081 1.39
CD4016 1.19	CD4082 1.39
CD4017 1.19	CD4083 1.39
CD4018 .99	CD4084 1.39
CD4019 .49	CD4085 1.39
CD4020 1.19	CD4086 1.39
CD4021 1.39	CD4087 1.39
CD4022 1.39	CD4088 1.39
CD4023 .29	CD4089 1.39
CD4024 .29	CD4090 1.39
CD4025 .29	CD4091 1.39
CD4026 .29	CD4092 1.39
CD4027 .29	CD4093 1.39

7400

7400 .39	74C01 .29
7401 .39	74C02 .29
7402 .39	74C03 .29
7403 .45	74C04 .29
7404 .49	74C05 .29
7405 .49	74C06 .29
7406 .49	74C07 .29
7407 .49	74C08 .29
7408 .49	74C09 .29
7409 .49	74C10 .29
7410 .49	74C11 .29
7411 .49	74C12 .29
7412 .49	74C13 .29
7413 .49	74C14 .29
7414 .49	74C15 .29
7415 .49	74C16 .29
7416 .49	74C17 .29
7417 .49	74C18 .29
7418 .49	74C19 .29
7419 .49	74C20 .29
7420 .49	74C21 .29
7421 .49	74C22 .29
7422 .49	74C23 .29
7423 .49	74C24 .29
7424 .49	74C25 .29
7425 .49	74C26 .29
7426 .49	74C27 .29
7427 .49	74C28 .29
7428 .49	74C29 .29
7429 .49	74C30 .29
7430 .49	74C31 .29
7431 .49	74C32 .29
7432 .49	74C33 .29
7433 .49	74C34 .29
7434 .49	74C35 .29
7435 .49	74C36 .29
7436 .49	74C37 .29
7437 .49	74C38 .29
7438 .49	74C39 .29
7439 .49	74C40 .29
7440 .49	74C41 .29
7441 .49	74C42 .29
7442 .49	74C43 .29
7443 .49	74C44 .29
7444 .49	74C45 .29
7445 .49	74C46 .29
7446 .49	74C47 .29
7447 .49	74C48 .29
7448 .49	74C49 .29
7449 .49	74C50 .29
7450 .49	74C51 .29

LINEAR

LM100H .89	LM309H .89
LM101H .89	LM310H .89
LM102H .89	LM311H .89
LM191H .89	LM400H .89

74LS00

74LS00 .35	74LS139 .05
74LS01 .35	74LS140 .05
74LS02 .35	74LS141 .05
74LS03 .35	74LS142 .05
74LS04 .35	74LS143 .05
74LS05 .35	74LS144 .05
74LS06 .35	74LS145 .05
74LS07 .35	74LS146 .05
74LS08 .35	74LS147 .05
74LS09 .35	74LS148 .05
74LS10 .35	74LS149 .05
74LS11 .35	74LS150 .05
74LS12 .35	74LS151 .05
74LS99 .35	74LS238 .05
74LS00 .35	74LS239 .05

JE608 PROGRAMMER

2704/2708 EPROM PROGRAMMER



3 separate Display Registers & LED's for Hex, Oct, Bin, 10 LED's 12" 2" for Address Register & LED's for Data Memory Register. The Data Memory Register displays the contents of the RAM from the EPROM Chip.

- Development of microprogram systems by means of a ribbon cable from the programmer panel test socket to the EPROM socket on the microprocessor board.
- Rapid checking verification of program data changes.
- Easy user move data from a master RAM or write into RAM's with ribbon cables.
- Allows manual stepping/manipulation up and down at any address location.
- Stand alone EPROM Programmer assembly.
- 16 Hex Resistorless EPROM Programmer Board assembly with 1 power supply and a LED Test Socket Panel Board assembly. The Test Socket uses force sensitive switches. Power requirements: 115VAC, 60Hz, 800mA.
- Compact desk top enclosure. Color coordinated design's use with light test panels and modules in module brown. Size: 21" x 11" x 2 1/2" H. Weight: 10 lbs.

The JE608 EPROM Programmer is a completely self contained unit which is independent of computer and requires no additional systems for its operation. The EPROM can be programmed from the Hexadecimal Keyboard or from a pre-programmed EPROM. The JE608 Programmer can simulate a programmed EPROM by the use of its internal RAM circuits. This will allow the user to test or pretest a program, for a system, prior to programming a chip. Any changes in the program can be entered directly into the memory circuits with the Hexadecimal Keyboard so that reprogramming the entire program will not be necessary. The JE608 Programmer contains a Program/Board with 28 IC's including power supplies etc. Power requirements: 115VAC, 60Hz, 800mA.

JE608 KIT \$399.95
JE608 Assembled and Tested \$499.95

DISCRETE LEDS

XC556R .200" red	5/51	MV50 .085" red	6/51	XC111R .190" red
------------------	------	----------------	------	------------------

7400

SN7400N	19	SN74123N	59
SN7401N	22	SN74125N	39
SN7402N	22	SN74126N	44
SN7403N	22	SN74128N	59
SN7404N	22	SN74132N	69
SN7405N	23	SN74136N	95
SN7406N	23	SN74139N	95
SN7407N	23	SN74141N	29
SN7408N	26	SN74142N	69
SN7409N	23	SN74143N	295
SN7410N	22	SN74144N	295
SN7411N	29	SN74145N	82
SN7412N	29	SN74147N	195
SN7413N	39	SN74148N	120
SN7414N	59	SN74150N	99
SN7415N	29	SN74151N	87
SN7417N	29	SN74152N	67
SN7420N	22	SN74153N	67
SN7421N	35	SN74154N	119
SN7422N	29	SN74155N	82
SN7423N	29	SN74156N	89
SN7425N	29	SN74157N	69
SN7426N	29	SN74158N	165
SN7427N	29	SN74160N	95
SN7429N	45	SN74161N	99
SN7430N	45	SN74162N	99
SN7432N	29	SN74163N	89
SN7433N	29	SN74164N	97
SN7435N	29	SN74165A	97
SN7439N	29	SN74166N	120
SN7440N	29	SN74167N	129
SN7441N	79	SN74170N	169
SN7442N	57	SN74172N	595
SN7443N	79	SN74173N	79
SN7444N	79	SN74174N	89
SN7445N	79	SN74175N	89
SN7446N	79	SN74178N	85
SN7447N	59	SN74177N	85
SN7448N	79	SN74179N	180
SN7450N	23	SN74180N	75
SN7451N	23	SN74181N	175
SN7453N	23	SN74182N	75
SN7454N	23	SN74184N	195
SN7459N	29	SN74185N	195
SN7460N	23	SN74186N	995
SN7470N	39	SN74188N	190
SN7472N	34	SN74190N	115
SN7473N	38	SN74191N	115
SN7474N	38	SN74192N	85
SN7475N	38	SN74193N	85
SN7476N	38	SN74194N	85
SN7477N	460	SN74195N	85
SN7480N	59	SN74196N	85
SN7481N	110	SN74197N	105
SN7482N	110	SN74198N	139
SN7483N	55	SN74199N	139
SN7485N	65	SN74211N	139
SN7486N	39	SN74251N	95
SN7489N	175	SN74273N	105
SN7490N	39	SN74278N	99
SN7491N	65	SN74283N	215
SN7492N	52	SN74284N	390
SN7493N	49	SN74285N	390
SN7494N	72	SN74290N	125
SN7495N	65	SN74291N	65
SN7496N	72	SN74355N	68
SN7497N	310	SN74366N	68
SN74100N	99	SN74367N	-79
SN74107N	32	SN74368N	-79
SN74109N	53	SN74390N	190
SN74116N	195	SN74393N	190
SN74121N	29	SN74490N	190
SN74122N	39		

74LS00

74LS00N	35	74LS164N	119
74LS01N	28	74LS165N	89
74LS02N	28	74LS166N	248
74LS03N	28	74LS168N	189
74LS04N	39	74LS169N	189
74LS05N	39	74LS170N	189
74LS06N	39	74LS171N	89
74LS09N	39	74LS174N	99
74LS10N	28	74LS175N	99
74LS11N	39	74LS181N	220
74LS12N	39	74LS190N	115
74LS13N	47	74LS191N	115
74LS14N	125	74LS192N	98
74LS15N	39	74LS193N	98
74LS20N	26	74LS194N	115
74LS21N	38	74LS195N	95
74LS22N	38	74LS196N	98
74LS26N	39	74LS197N	89
74LS27N	39	74LS211N	149
74LS28N	39	74LS240N	229
74LS29N	26	74LS241N	249
74LS32N	39	74LS242N	299
74LS37N	79	74LS243N	229
74LS38N	39	74LS244N	295
74LS40N	26	74LS245N	895
74LS42N	110	74LS246N	110
74LS47N	79	74LS248N	110
74LS48N	79	74LS249N	179
74LS51N	26	74LS251N	169
74LS54N	35	74LS253N	98
74LS52N	35	74LS257N	98
74LS53N	45	74LS258N	98
74LS57N	59	74LS259N	295
74LS58N	59	74LS260N	69
74LS59N	45	74LS261N	249
74LS57B	85	74LS266N	59
74LS583AN	99	74LS273N	175
74LS585N	119	74LS275N	449
74LS586N	45	74LS279N	55
74LS590N	75	74LS283N	110
74LS592N	75	74LS290N	129
74LS593N	75	74LS293N	195
74LS595N	88	74LS295N	110
74LS596N	88	74LS298N	129
74LS5107N	45	74LS324N	175
74LS5108N	45	74LS327N	795
74LS5112N	49	74LS348N	195
74LS5113N	49	74LS352N	165
74LS5114N	55	74LS353N	165
74LS5122N	55	74LS363N	149
74LS5123N	119	74LS365N	110
74LS5124N	135	74LS366N	99
74LS5125N	89	74LS367N	99
74LS5126N	89	74LS368N	99
74LS5132N	79	74LS373N	275
74LS5136N	59	74LS374N	275
74LS5138N	89	74LS375N	195
74LS5139N	89	74LS377N	195
74LS5145N	125	74LS395N	195
74LS5148N	79	74LS396N	85
74LS5151N	79	74LS397N	189
74LS5153N	79	74LS399N	195
74LS5154N	249	74LS399N	170
74LS5155N	119	74LS399N	295
74LS5156N	99	74LS424N	295
74LS5157N	99	74LS466N	175
74LS5158N	75	74LS670N	229
74LS5160N	98	81LS95N	199
74LS5161N	115	81LS96N	199
74LS5162N	98	81LS97N	199
74LS5163N	98	81LS98N	199

ADVANCED COMPUTER PRODUCTS

BECKMAN Digital Multimeters

MODELS TECH 300 AND TECH 310



Choice of Models - The TECH 310 has all above features, 7 functions, 20 ranges plus 9 25% Vdc accuracy. The TECH 300 has a 9 25% Vdc accuracy and all the above features, but without Insta-Ohms™ continuity function or the 10 amp current ranges.

TECH 300 Digital Multimeter \$100.00
TECH 310 Digital Multimeter \$130.00
VC-201 Vinyl Carrying Case \$10.00
DC-200 Deluxe Carrying Case \$24.00
HV-211 High Voltage Probe \$35.00
RP-221 RP Probe \$35.00
CI-231 AC Current Clamp \$42.00
DL-241 Deluxe Test Lead \$59.00
TL-242 Spare Test Leads \$5.00 (5 pack)

Apple II. 16K or Apple II. Plus \$990

16K Apple Upgrade Kit \$62.95

Hi-Speed Serial I/O	\$189.00	DS65 Digi-Sector	\$349.00	Integer ROM Card	\$189.00
Centronics Printer I/O	199.95	Apple Graphics Tablet	725.00	Proto Card	21.95
Applesoft II Firmware	189.00	D.C. Hayes Modem II	349.95	M & R Modulator	29.95
Apple Clock	269.00	Disk II w/Controller	575.00	Sanyo Cassette	54.95
Introl X-10 System	269.95	Disk II	475.00	16K Upgrade Kit	62.95
Introl X-10 Controller	179.95	Fiscal Lang. System	450.00	Desktop Plot	98.00
All Music Synthesizer	259.95	Parallel Printer Card	165.00	8" Floppy Controller	350.00
16 Ch. Analog Input	249.95	Communications Card	189.00	Heuristics Speechlab	179.00
2 Ch. Analog Output	184.95	Business Software Pkg.	625.00	Romplus+	169.00
13-Key Keypad	119.95	Corvus 10 Megabyte Drive	4625.00	Superlaker	279.00
Vid-Calc	125.00			Casher	250.00

ATARI 800 & 400 Personal Computer System

ATARI 800 \$750.00
ATARI 400 \$449.00

ATARI 800 Includes: Computer Console, BASIC Lang. Cartridge, Education System Master Cartridge, BASIC Language Programming Manual, 800 Operator's Manual w/Notebook, Atari 410 Program Recorder, 8K RAM Module, Power Supply, TV Switch Box.

Peripherals		Education System Course Program	35.00	Software	
Disc Drive	599.00	U.S. History	35.00	Basic Algebra	35.00
Printer	499.00	U.S. Government	35.00	Basic Algebra	35.00
Program Recorder	89.00	Supervisory Skills	35.00	Basic Game and Program Cassette	35.00
Software - BASIC Cartridge	89.00	World History (Western)	35.00	Guide to BASIC Programming	18.00
Education System Master Cartridge	28.00	Basic Science	35.00	BASIC Game Programs	19.00
Atari BASIC	55.00	Counting Procedures	35.00	Atari Memory	110.00
Assembler/Debug	55.00	Principles of Accounting	35.00	8K RAM Memory Module	110.00
Basicmath	42.00	Physics	35.00	16K RAM Memory Module	225.00
Life	42.00	Great Classics (English)	35.00	Books	
Super Breakout™	42.00	Business Communications	35.00	Bank Databases	
Music Composer	55.00	Basic Psychology	35.00	Disk File Manager	5.00
Super Bag™	55.00	Effective Writing	35.00	Answer Database	
Computer Chess	55.00	Auto Mechanics	35.00	Driving Controller Pak	18.00
Home France	55.00	Principles of Economics	35.00	Physics Controller Pak	18.00

ACP APPLE MUSIC MACHINE WITH 9 VOICES!

• NEW! Uses latest State of the Art LSI Technology!
• Requires only one set for 9 voices • Uses three AT-89-810's to produce line voices (other compatible modules have only 2)
• Includes software • Simulates three ALF Boards
• Plays music generated by the ALF Board • APPLE™ II compatible

3 Times More Powerful Than ALP!

KIT \$189.95
ASSEMBLED AND TESTED \$289.95

THE BONE FONE



• SKIERS
• JOGGERS
• SKATERS
• CYCLERS

You must hear it and feel it to believe it!

AM/FM stereo surrounds and fills your body with sound. No earplugs. You wear it!

\$65.95

FLOPPY DISK DRIVES

MPI B51-5W, 40 tracks	279.00
Shugart 800/801R 8"	475.00
Siemens Shugart Compatible Model	429.00
PERSCI Model 277 Dual	1195.00
WANG/SIEMENS 5 1/4" Drive	290.00
MPI B52 5 1/4" Drive	395.00
WANG/SIEMENS 8 1/2" Drive	395.00
WANG/SIEMENS 8 1/2" Drive	290.00

MONITORS

Sanyo 9"	\$169.95
Sanyo 15"	279.00
Leeds 12"	159.95
Motrola 12", High Resolution, 22 MHz, OEM Model	219.00
#M3000-340	499.00
Zenith 13" Color Monitor	499.00
MGA 13" Color TV	349.00
VAMP 19" Color Monitor	575.00
VAMP 15" Color Monitor	449.00

CONTINENTAL SPECIALTIES

Model 3001 Digital Capacitance Meter	275.00
Model 333 Tri-Mode Comparator	295.00
Model LM-3 40-Channel Logic Monitor	585.00
Model LM-1 Logic Monitor	60.00
Model LM-2 Logic Monitor	147.00
Model 2901 Sweepable Function Generator	186.00
Model 6001 Universal Counter-Timer	350.00
Model 8001 650 MHz Frequency Counter	385.00
MAX-100 100 MHz Portable Frequency Counter	149.00
PS-500 500 MHz Decade Prescaler	70.00
MAX-50 50 MHz Handheld Frequency Counter	77.00
MAX-550 50 MHz Handheld Frequency Counter	165.00
Model 4001 Pulse Generator	835.00
Model B1 Digital Pulser	83.00
Logic Probes	
Model LP-1 Digital Logic Probe	50.00
Model LP-2 Economy Logic Probe	28.00
Model LP-3 High Speed Logic Probe	77.00
Model LP-4 Logic Probe Kit	21.95
Logic Probe Accessories	21
Model LTO-1, LTO-2 Logical Analysis Kits	220.250

Commodore PET AS LOW AS \$775.00

2001-8K	775.00	2003 80-Col Plain Paper Printer	895.00
2001-16K	875.00	2004 Dual Mem. Disk Drive	1250.00
2001-320K (img)	975.00	Pet to IEEE Cable	39.95
2001-320K (img)	1250.00	IEEE to IEEE Cable	49.95
2001-320K (img)	1250.00	2001-320K (img)	1250.00
2002 80-Col Dot Matrix Printer	795.00	C24 External Cassette Deck	95.00

CRAIG LANGUAGE TRANSLATOR AND INFORMATION CENTER

An instant translator of words and phrases from the world's major languages plus a four function calculator plus information center for nutrition, bar and wine guide, guide, etc.

SPECIAL LOW PRICE LIMITED TIME ONLY (UNTIL AUGUST 17) \$119.95

PLUS \$20.00 REBATE FROM CRAIG CRAIG MODULES AVAILABLE FROM \$24.95

The thermostat that uses microprocessor technology to save fuel and money.

PROGRAMMABLE TEMPERATURE CONTROLLER

ACP PRICE \$69.95

A fully automatic electronic thermostat. Easy to install and operate. Compare the cost: TPI's temperature controller is the lowest priced electronic thermostat on the market.

HOME BURGLAR ALARM

ACP PRICE ONLY \$189.00

- No installation
- Protects a whole house
- Turns on lights automatically
- Powerful electric siren
- Exit and entry delay
- Battery back-up

FOR INTERNATIONAL ORDERS:
1401 E. Borchard (714) 953-0804
Santa Ana, CA 92705 TWX: 910-595-1565

SINGLE BOARD COMPUTER SELECTION GUIDE

BOARD	PROCESSOR	ACP PRICE	ENCLOSURE
KIM-1	6502	169.00	Add 29.95
SYM-1	6502	239.00	Add 39.95
Cromemco	Z80	209.00	N/A
SD-SBC100	Z80	439.00	N/A
AIM 65	6502	375.00	Add 49.95
Cosmac Vip	1802	199.00	Inc.

RADIO-ELECTRONICS

RETAIL STORES OPEN MON-SAT

STORE #1	1310 "B" E. Edinger Santa Ana, CA 92705 Showrooms, Retail, Warehouse	STORE #2	674 El Camino Real Tustin, CA 92680 Specializing in Systems
----------	--	----------	---

P.O. Box 17329 Irvine, Calif. 92713
Direct Order Lines: (714) 558-8813
(800) 854-8230 or (800) 854-8241

ADVANCED COMPUTER PRODUCTS

GET YOUR 1980 CATALOG

FIRST TO OFFER PRIME PRODUCTS TO THE HOBBYIST AT FAIR PRICES!

1. Proven Quality Factory tested products only.
2. Guaranteed Satisfaction
3. Over \$1,000,000 Inventory

1980 CATALOG NOW AVAILABLE.

Send \$2.00 for your copy of the most complete catalog of computer products. A must for the serious computer user.

STATIC RAM BOARDS

\$-100 32K (uses 2114)
 ASSEMBLED Kit *Less than \$4 per bit!*
 450ns. 499.00 450ns. 469.00
 250ns. 539.00 250ns. 499.00
 Bare Board 49.95
 Bare Board w/all parts less mem. 99.95

\$-100 16K (\$-100 Compatible)
 Low Power
 2 MHz or 4 MHz
 Assembled & Tested
 2 MHz... \$250.00
 4 MHz... \$265.00

WOW!

LOGOS 18K
 ASSEMBLED
 450 ns. 149.95 KIT 450ns. 125.95
 250ns. 169.95 250ns. 149.95
 Bare PC Board w/Data \$21.95
 *Special Offer Buy 4! 8K 450ns. Kits \$117.00

The VISTA V-60
 Disk Drive System
 Single drive system \$ 369.00
 Two drive system \$ 719.00
 1TB50
 Two drive system \$1499.00
 1TB50
 Two drive cable \$ 18.95
 40 track pitch at NO CHARGE
 Four drive cable \$ 18.95

The VISTA V-200 FOR EXIDY

Price Starting as low as \$1199.00

Item	Capacity	Interface	Shipping	Price
V200 E-20	400	2 Drive	25 Slt.	1199.00
V200 E-22	800	Single Head	25 Slt.	1549.00
V200 E-30	600	3 Drive	32 Slt.	1524.00
V200 E-32	12 MEG	3 Drive	32 Slt.	1999.00

ATTENTION VIDEO HOBBYISTS!!!
 * BOX BUILDERS
 * USE AS REMOTE TUNER/TIMER
 * FULL SCHEMATICS AVAILABLE
 * FOR ONLY \$5.90 - FREE W/PURCHASE

A Recent Special Purchase Allows Us To Present The Following
NEW, UNUSED COMPONENTS
 From The RCA VDT-201
 Videocassette Recorder

1. UHF/VHF Tuner Subassembly with Infrared and Video Demodulator	\$59.95
2. RF Modulator with Audio & Video inputs Channel 3 or 4	\$39.95
3. Digital Color Modem AMP Fluorescent Resistor (9-100)	\$19.95
4. 300 Ohm 50 W Ohm Matching or Subtotal	\$123.34

Save Only **\$74.95**
 Please Call For Volume Discounts

LOW COST FLOPPY DISK SUBSYSTEM
 Shugart 801R Drives (2) VISTA Floppy Controller (9-100), Case, Power Supply & Cable, CP/M Disk Operating System Assembled & Tested... \$149.00
 *CHECK OUR FLOPPY DISK PRICING! ON THIS PAGE (\$179.00 Value)

WATANABE MIPLLOT
 Max. pen speed 50 mm/sec, resolution 10 mm typically, 60 mm. Inset character sizes and 4 degrees of rotation, absolute draw, relative draw, alpha printing done with simple commands.
\$1195.00

IMS STATIC RAM BOARDS
 8K Static \$209.00 450 ns. \$189.00
 16K Static \$449.00 450 ns. \$399.00
 32K Static \$729.00 450 ns. \$629.00

ANADIX PRINTER NEW APPLE VERSION
 Model DP-8000 compact, impact, parallel or serial. Sprocket feed, 80 cols, 84 lines only, bi-directional.
 New only... \$875.00
 DP-8000AP (for Apple) \$875.00

SALE! SD SYSTEMS BOARDS
TAKE 10% OFF! KIT ASSEMB
 SBC 100 Single Board Computer (MHz): \$265.00 \$238.50
 SBC 200 Single Board Computer (MHz): 299.00 269.10
 Z80 Starter System 319.00 287.10
 VDB 8024 Video Display Board 335.00 301.50
 Versa-Floppy II 325.00 292.50
 Exandrom PROM 115.00 103.50
 SD100 Computer System w/4K 699.00 629.10
 SD200 Computer System w/4K 799.00 719.10

8600 MICROMODULE™ PRICE LIST

MODEL NO.	DESCRIPTION	PRICE
9600A	Single Board Microcomputer	\$495.00
9609	Advanced Single Bd. Comp. (6809)	\$595.00
9601	16 Slot Mother Board	175.00
9602	Card Cage	75.00
9603	8 Slot Mother Board	395.00
9604	Power Supply	275.00
9605	DC Input Power Supply	325.00
9610	Utility Proto Board	39.00
9611	Arith. Proc/Memory Module	495.00
9612	Buffered Utility Proto Board	49.00
9616	32K EPROM RAM Module	250.00
9617	EPROM Programming Head	250.00
9620	16 Channel Parallel I/O Module	295.00
9622	Serial Parallel I/O Module	325.00
9627	16K Static RAM Module 470ns	395.00
9629	32K Static RAM 450ns	695.00
9629A	32K Static RAM 200ns	895.00
9630	Card Extender	65.00
9640	Multiple Programmable Timer	395.00
9650	8 Channel Duplex Serial I/O Mod	395.00
9655	Interface Tape Controller	595.00
96103	32/32 I/O Module	275.00
96702	Contact Closure Module	350.00

UNPOPULATED BOARDS (Also Available)

APPLE/EXIDY/EXPANDO TRS 80 16K-UPGRADE KIT

\$54.95 TRS-80/APPLE \$54.95
 MEMORY EXPANSION KITS,
 4116's, 16K (200/250 ns.),
 8 pcs for \$54.95
 w/instructions & jumpers
 Call For Volume Pricing
 * Special: TRS80 Schematic... \$ 4.95
 * Expansion Interface Schematic... \$ 4.95
 * Expansion Interface Connector... 7.95

EXPANDROM II MEMORY KITS
 * Bank Selectable... Uses 4116 200 ns.
 * Write Protect... Power BVDC... ±16VDC
 * Phantom NEW LOW * Up to 4 MHz
 Expando 84 Kit (4116) Assem. & Tested Add \$50.
 16K \$269.00 48K \$435.00
 32K \$349.00 64K \$505.00

HAZELTINE TERMINALS
SALE \$749.00
 Model 1400 \$179.00 Model 1500 \$1085.00
 Model 1410 \$825.00 Model 1510 \$1245.00
 Model 1420 \$945.00 Model 1520 \$1495.00

UV "Eprom" Eraser
 Model UVs-11E \$69.95
 Holds 4 Eproms at a time
 Backed by 45 years experience.
 Model S-52T... \$265.00
 Professional Industrial Model

EMAKO-20.. Reg. \$777.00 **\$599.00**
 UNBELIEVABLE!
 125 Cals, 60 lpm - Vertical
 Formal Unit - 96 Characters - Upper/Lower Case - 4.5" to 9.5" Adjustable - 80 col/40 col double width - Full 96 char. ASCII

EMAKO-22..... \$799.00
 Prints a 132 col/line. Available with parallel or serial output at same price.

MIKA 20..... \$1280.00
 927, 125 cps 136 characters/line
 Full 16" width. Super for business applications requiring large IBM format paper.

BASE II PRINTER
 80 Column Impact Printer
 * 60 Lines Per Minute
 * 115/230 VAC, 50 or 60 Hz
 * 72, 80, 96, 120 or 132 Character/Line
 * Self-Timed
 REG. \$649.00
 ACP PRICE **\$550.00**
 Option "M" Terminal Screen Buffer (1920 Char.) \$50.00
 Option "T" High Speed Paper Advance & Graphics \$50.00
 Option "X" Tractor Feed \$50.00

Z-80/Z-80A/8080 CPU BOARD
 * On board 2708 * 2708 integrated (450ns.)
 * Power on jump * completely socketed
 * Z-80 Assembled and Tested... \$185.00
 * Z-80 Kit... \$129.95
 * Z-80 Bare PC Board... \$ 34.95
 * For 4MHz Speed Add \$15.00
 8080A Kit... \$ 99.95
 8080A Assembled... \$149.95

S-100 MOTHERBOARD SPECIAL
 8 slot expandable w/9 conn.
 reg \$69.95... NOW \$52.95

SIEMENS'S FLOPPY SALE
 * Special buy while supply lasts.
 * 8" Drive with Double-Density
 * 90 Day Warranty
SHUGART 801R \$475.00

ACOUSTIC MODEM
 NOVATION CAT™
 O-300 Baud
 Bell 103
 Answer, Originate \$179.95

DATA BOOKS • COMPUTER BOOKS

1980 IC Master	59.95	Intel MCS 80 Manual	7.95
NSC TTL Data	3.95	Intel MCS 40 Manual	4.95
NSC Linear	4.95	AMD 8080A Manual	5.95
NSC Linear App Notes II	3.95	AMD Schottky Databook	4.95
NSC CMOS	3.95	AMI MCS/LSI Data	7.95
NSC Memory	3.95	GI MCS/LSI Data	4.95
Intel Databook	7.50	Intel Linear Analog Databook	4.95
Intel MCS 80 Manual	7.50	TI Linear Control Data	3.95

SALE • OSBORNE BOOKS • SALE

Understanding Computers	99c	7.95
8080/Microcomputer Experiments	99c	11.95
Beginning BASIC	99c	8.95
Beginners' Glossary & Guide	99c	5.95
Peanut Butter & Jelly Guide to Computers	99c	6.95
8080 Machine Language Programming	99c	9.95
Home Computers Vol. I Hardware	99c	6.95
Home Computers Vol. II Software	99c	11.95
Starfish Simulator	99c	6.95

MICROPROCESSORS

Z8001 16 bit to 8MHz	\$189.00
Z8002 16 bit to 64K	149.00
Z8003 16 bit to 128K	179.00
F-8 (8080)	16.95
F-80	18.95
2101-1	13.95
8080A	8.50
8080A-MHz	19.95
SALE 8088	19.95
8081	14.95
2901A	14.95
2903 4-bit Superdrive	29.95
CP1800	49.95
CP1800A	39.95
6502	11.50
6502C	16.95
IM6100	29.95
6800	11.75
6800 2.0 MHz	11.75
6802P	17.95
8035	19.95
8035A	19.95
8748	69.95
8748A	64.95
8086	69.95

ADVANCED SUPPORT
 AM9511 Arith. Processor 175.00
 9512 Arith. Processor 175.00
 9513 Univ. Timer 79.95
 AM9517 DM Controller 18.95
 AM9519 Universal Interrupt 18.95

Z-80 SUPPORT CHIPS
 Z80-PIO 2.5 MHz 8.75
 Z80-PIO 4.0 MHz 12.95
 Z80-CTD 2.5 MHz 12.95
 Z80-CTD 4.0 MHz 12.95
 Z80-DMA 4.0 MHz 35.95
 Z80-DMA 2.5 MHz 35.95
 Z80-SIO 4.0 MHz 39.40
 Z80-SIO 2.5 MHz 35.95
 Z80-SIO 1.1 4.0 MHz 39.40
 Z80-SIO 2.5 MHz 35.95
 Z80-SIO 2.5 MHz 39.40

8080/8085 SUPPORT
 8155/8156 I/O 24.95
 8755 I/O w/Eprom 84.95
 8201 8255 Ram Control 34.95
 8205/74S 138 Decoder 3.95
 8212 I/O 2.75
 8214 Priority Int. 5.25
 8216 Bus Driver 2.75
 8224 Clock Gen. 2.95
 8224-4 (MHz) 9.75
 8226 Bus Driver 3.95
 8726 I/O 2.75
 8228 Sys. Control 5.50
 8238 Sys. Cont. 5.50
 8241 Prog. I/O 16.95
 8253 Int. Timer 16.95
 8254 Prog. I/O 16.95
 8257 Prog. DMA 6.50
 8258 Prog. I/O 16.95
 8259 Prog. Int. 17.95
 8275 CRT Control 16.95
 8279 Prog. Keyboard 18.95

8000 SUPPORT CHIPS
 6810 128 x 8 Ram 4.75
 6820 PIA 5.95
 6821 8255 Ram Control 6.50
 6828 Priority Int. 9.95
 6834 1-512 x 8 Eprom 16.95
 6845/48/48505 CRT Cont. 49.95
 6847 Color CRT 49.95
 6850 ACIA 5.95
 6852 Serial Adapter 5.95
 6880 Modem 10.95
 6885 Modulator 11.95
 6886 Modem 10.95
 6871A 1.0MHz OSC. 25.95
 6875 1.0MHz OSC. 25.95
 6880 Modem 10.95
 6885 Modulator 11.95
 6886 Modem 10.95
 68047 24.95

1602 SUPPORT CHIPS
 1821 LCD 2K Ram 25.00
 1824 LCD 2K x 8 Ram 25.00
 1824 CD 32 x 8 Ram 9.95
 1852 CD 8 bit I/O 10.95
 1854 Unit Int. 10.95
 1856 CD I/O 8.95
 1857 CD I/O 8.95

5602 SUPPORT CHIPS
 6520 PIA 7.50
 6522 MUX 11.95
 6502-002.003.004.005 21.95
 6525 18.95
 6551 18.95

PROMS
 2708 450 ns. 8.25
 2708-8 650 ns. 7.50
 1702A 4.95
 2732 74.95
 2718 17.95
 2716-9V 12V. 29.95
 2758-9V 29.95
 5208-13.95
 5204AQ 14.95
 IM 5610 3.90
 SALS 8223 32 x 8 2.85
 8281 15 512 x 8 (TS) 16.95
 825128 32 x 8 4.90
 825128 256 x 4 (TS) 4.90
 825130 512 x 4 (IO) 6.50
 82523 6.95
 825131 14.95
 825137 14.95

NOTE: WE PROGRAM PROMS

CHARACTER GEN.
 2513-001 (SV) Upper 9.50
 2513-005 (SV) Lower 10.95
 2512-003 (SV) Lower 14.95
 MCM8571 11.75
 MCM8574 11.75
 MCM8575 14.50
 MCM8575 14.50

UARTS/BAUD RATE
 1R16029 (SV) 12V 3.95
 AY51013 (SV) 12V 4.95
 AY51014 (SV) 1812 15-14V 6.95
 AY51015A (8E3) (SV) 6.95
 1602 6.95
 IM6402 5.95
 IM6403 5.95
 2350 USRT 9.95
 1817B Astro 24.95
 MCM174728 9.95
 4702 14.95
 4701 9.95
 CM 5016 1.95

KEYBOARD ENCODERS
 AY5-2376 13.75
 AY5-3800 13.75
 8001165 9.95
 74C232 9.95
 74C233 9.95

STATIC RAMS

21L02 450ns.	1-24	25-99	100
21L02 250ns.	1.59	1.55	1.15
2111	3.75	3.65	3.65
2112-1	2.95	2.85	2.65
2101-1	2.90	2.70	2.55
2114L-250ns. (4045)	6.95	5.50	6.50
2114L-450ns. (4048)	8.95	5.25	6.75
4044 250 ns.	8.95	7.50	6.25
4044 450ns.	5.95	5.95	4.75
EMM4200A	3.75	3.75	6.25
EMM4200	7.95	7.25	6.25
EMM 4904	12.50	11.50	9.95
5104	7.95	5.95	7.25
AMD01/40/41	10.95	10.25	9.95
AMD01/30/31	12.95	11.95	10.25
6511	1.95	1.75	1.25
P2125/93425 (45ns.)	9.95	8.95	8.25
6508 1K x 1 CMOS	7.95	7.95	7.25
6518 1K x 1 CMOS	7.95	7.95	7.25
74S189 84 bit Ram	3.95	3.25	5.00
2147 Low Power AK Static	19.95	18.95	16.95

64K 1103 1.95
 5282 1.95
 5270 4.95
 5290 12.45
RAMS 6005 7.95
 6004 4.95
 6002 1.50

SOCKETS

# Pins	Le-Pro Solderfill	Wire Wrap 3 Level	Cost
8	15	31	25
14	19	36	59
16	20	42	62
18	24	59	64
20	29	69	99
24	34	79	112
24	38	85	140
28	43	110	149
40	52	128	169
40	60	140	189

ZERO INSERTION FORCE

16 Pin \$5.50 24 Pin \$7.50 40 Pin \$10.25

LED READOUTS

Part No.	LED Color	Description	Price
DL204	Red	Common Cathode	1.25
DL205	Red	Common Anode	1.25
DL206	Red	Common Cathode (+1)	1.25
DL207	Red	Common Cathode (+1)	1.25
DL208	Red	Common Cathode (+1)	1.25
DL209	Red	Common Cathode (+1)	1.25
DL210	Red	Common Cathode (+1)	1.25
DL211	Red	Common Cathode (+1)	1.25
DL212	Red	Common Cathode (+1)	1.25
DL213	Red	Common Cathode (+1)	1.25
DL214	Red	Common Cathode (+1)	1.25
DL215	Red	Common Cathode (+1)	1.25
DL216	Red	Common Cathode (+1)	1.25
DL217	Red	Common Cathode (+1)	1.25</

SOUND EFFECTS GENERATOR BASIC KIT

Now Chaney Electronics makes it possible to build your own sound effects generator without spending a fortune. We supply you with the 1176477 sound chip plus an etched and drilled glass epoxy PC board with schematic and layout instructions. This board makes it simple to build a generator capable of whizzer sounds, locomotive sirens, airplanes, clocks, etc. Does not require DIP switches or other expensive/unusual components. You supply only a few standard resistors, capacitors, switches, pots, speaker, 2N2222 transistor and 3V battery.



BASIC KIT CONTAINING
1176477, PC BOARD
AND INSTRUCTIONS C23889
ONLY \$5.95

2N2222 TRANSISTOR FOR ABOVE C23884 .39 EACH
IF YOU HAVE ALREADY PURCHASED THE 1176477 CHIP YOU MAY BUY THE PC BOARD AND INSTRUCTIONS ONLY. C23885 \$4.00

Strobe Tube & Trigger

2N4081
\$1.75

LED Flasher Kit

Simple to build kit uses one LED transistor and all parts including the PC board. (VW lettering kit not included) C23281 \$2.49

6VDC Xenon Flasher Kit

Battery operated device emits colored bursts of light of approximately 1/4 sec. duration. Compatible with all 6V DC boards. (Line burner) C23886 \$8.00

Digital Counting Module

Made for an electronic counter. Push button one flasher for 100 counts. (VW lettering kit not included) C23887 \$1.79

120 VAC Xenon Strobe Kit

Computer variable rate strobe light kit. Can be used on PC board. Line cord and instructions. C23011 \$7.50

Wheel of Fortune

Popular game device uses LED's, transistors & IC to give the effect of a bright and fast spinning wheel. (VW lettering kit not included) C23888 \$8.99

HIGH OUTPUT SILICON SOLAR CELLS

We now stock a full line of these hard to find cells which convert light directly into electricity. Each cell generates approximately .45 volt and generates current as shown below. Connect cells in series for more voltage and connect cells in parallel for more current. Many other types are listed in our catalog:

SIZE	CURRENT	STOCK #	PRICE
2" 1/4 CELL	100ma	C24154	\$1.75
2" 1/2 CELL	250ma	C24155	\$3.00
2" WHOLE CELL	500ma	C24156	\$5.50
3" 1/3 CELL	300ma	C24157	\$3.25
3" 1/2 CELL	500ma	C24158	\$5.50
3" WHOLE CELL	750ma	C24159	\$8.50
4" WHOLE CELL	1.3 AMP	C24160	\$10.00


RECHARGEABLE AA NIKADS USED-EXCELLENT CONDITION C24161 79¢

CHANEY electronics inc.
• Minimum order \$5.00
• Please include \$1.00 for postage
• Visa, MC and CO accepted
• Phone orders are welcome

P.O. BOX 27038, DENVER, CO. 80227 (303) 781-5750

Send for our free giant catalog of unique items!!!
CIRCLE 20 ON FREE INFORMATION CARD

8 Instruments in 1

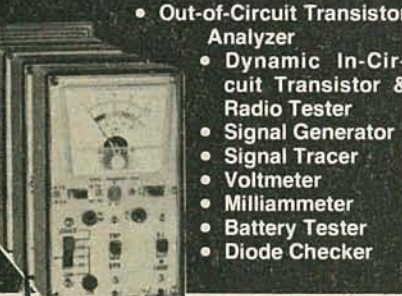

- Out-of-Circuit Transistor Analyzer
- Dynamic In-Circuit Transistor & Radio Tester
- Signal Generator
- Signal Tracer
- Voltmeter
- Milliammeter
- Battery Tester
- Diode Checker

Model **Transistor Analyzer 212**
Factory Wired & Tested — \$35.98
Easy-to-Assemble Kit — \$23.97

Now you can pinpoint defective transistors and their circuit troubles speedily with a single, feature-packed instrument instead of a costly elaborate set-up. Performance-proven by thousands! Checks all transistor types, hi or low power, for DC current gain (beta) to 200 in 3 ranges, and leakage.

Universal test socket accepts all base configurations. Identifies NPN or PNP transistors. Dynamically tests all transistors (oscillator check) and AF, IF, RF circuits.

No external power needed. Measures DC currents to 80 ma. Complete with test leads, instruction manual and transistor listing.

Write for FREE catalog of the world-famous EMC line of test instruments.

EMC ELECTRONIC MEASUREMENTS CORP.
625 Broadway, New York, NY 10012

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

Free Information Number Page

27	AMC Sales	118
—	ATV Research	106
8	AP Products, Inc.	6
13	Active Electronics	107
45	Advanced Audio Systems	92
7,49	Advanced Computer Products	120-121
—	Advance Electronics	14-15,42,75,77
48	All Electronics	118
9	American Antenna	Cover 4
43	B & K Precision Dynascan	94
—	Karel Barta	110
51	Beckman	44
—	Bullet Electronics	110
—	Burdex Security	108
40	BYTE	84
36	CFR Associates	119
20	Chaney Electronics	122
18	Channellock	40
—	CIE—Cleveland Institute of Electronics	18-21
—	Command Productions	106
52	Concord—Computer Components	114
63	Creative Computing	104
—	Dage Scientific	110
—	Deltroniks	108
35	Digi-Key	111
—	EMC—Electronic Measurements	122
—	Electronic Technology Today	93
—	Electronics & Control Engineers' Book Club—McGraw-Hill Book Div.	88-91
3	Electronics Book Club	39
30	Electronics Technical Institute	98
53	Fluke	5
—	Fordham Radio Supply	108
5-6	Formula International	112-113
—	Four Sigma Society	108
39	Global Specialties	Cover 2
—	Global TV Electronics	106
54	Godbout Electronics	118
—	Grantham College of Engineering	103
62,2	Heath	24-25,79-81,Cover 3
47	Hickok Electrical Instruments	33
42	Hitachi Denshi	41
24	Hustler, Inc.	100
46	IET Labs, Inc.	100
—	Information Unlimited	108
55	International Electronics Unltd.	119
—	J S & A	1
14-15	Jameco Electronics	116-117
16	Jan Crystal	105
28	Jensen Tools & Alloys	38
—	Lakeside Industries	106
11,67	Leader	27
29,12	Mercury	2,46
22	Meshna	114
—	Micro Management Systems	110

34	Micro Mart	114
56	Mosaic Electronics	103
23	Mountain West	99
—	NJS Technology	101
—	National Radio Institute (NRI)—Div. of McGraw-Hill	8-11
—	National Technical Schools	28-31
41	Nesda	102
37	Netronics	85
64	Non-Linear Systems	34-35
10	O.K. Machine & Tool	12
4	Optoelectronics	95
66	Ora Electronics	97
26	PAIA	83
25	Pac-Com	99
59	Paladin	43
58	Panavise	92
32	Poly Paks	118
—	RCA	26
61	Radio Shack	109
31	Ramsey Electronics	115
21	Rye Industries	104
—	Sabtronic	17
—	Howard W. Sams	45
60	Shure Brothers	82
19	Solid State Sales	119
33	Sony	23
—	Spacecoast Research	106
38	Sprague Products	32
65	Testek	83
—	Tronics 2000	37
44	VIZ Mfg. Co.	36
17	Wersi Electronics	38

MOVING?

Don't miss a single copy of **Radio-Electronics**. Give us:

Six weeks' notice

Your old address and zip code

Your new address and zip code

ATTACH LABEL HERE


name (please print)

address

city state zip code

Mail to: Radio-Electronics
SUBSCRIPTION DEPT., P.O. BOX 2520,
BOULDER, COLO. 80322

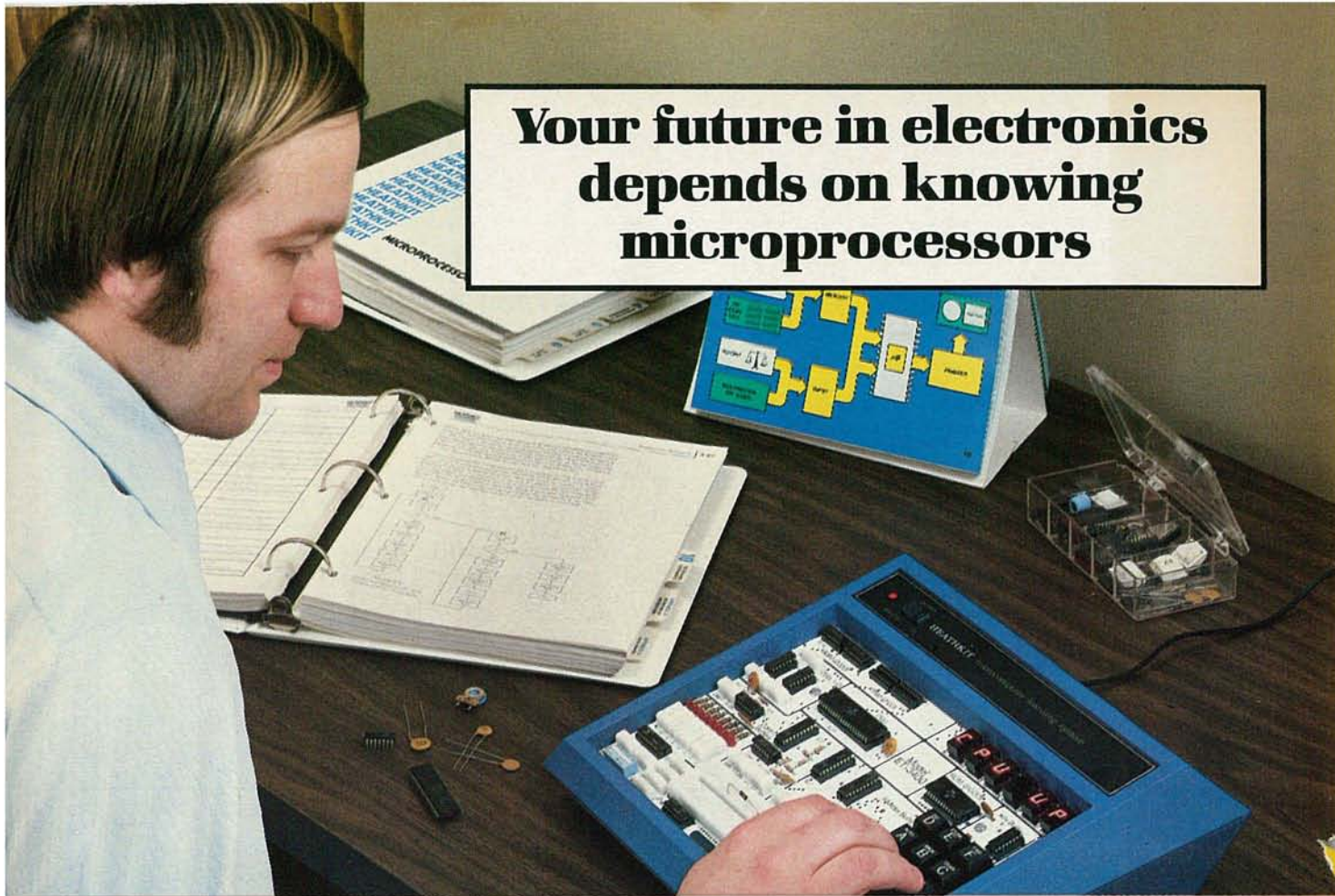Your future in electronics depends on knowing microprocessors



To advance in the electronic-oriented world of today — and tomorrow — you need to understand microprocessors. Now, Heath/Zenith Educational Systems brings everything together in one complete, easy-to-follow self-instructional course on microprocessors — so you can gain the knowledge needed to secure your future in electronics.

Heath/Zenith's Microprocessor Course — as does every program in the Heath/Zenith Electronics Education line — reinforces each concept **FOUR** ways:

1. You **READ** clear, concise text material.
2. You **SEE** large, colorful visuals.
3. You **HEAR** audio cassette tapes which reinforce material presented in the text material and visuals.
4. You **PERFORM** programming and interfacing experiments, which give you hands-on experience in programming and interfacing microprocessors.

Sixty-two different electronic components are included, to make the Heath/Zenith Course an even better value. These parts are used in the hands-on programming and interfacing experiments.

The Heath/Zenith Microprocessor Course is backed by a Microprocessor Trainer, used to perform the experiments. Based on the popular 6800 microprocessor, this Trainer functions as a miniature digital computer. Built-in 1K ROM monitor program controls operation. Six-digit LED display provides address, data readout.

In the experiments, you work with actual components — to gain hands-on experience and confidence, and to make learning more effective.

Here is what you will know when you finish this easy-to-learn course:

Programming — including branching, algorithms and flow-charting.

The 6800 Microprocessor — including architecture, instruction set, addressing modes and interrupts.

Interfacing — with ROM, RAM, displays and switches, D/A and A/D converters; using the Peripheral Interface Adapter (PIA).
Number Systems and Codes, Microcomputer Basics and Computer Arithmetic.

Turn to pages 74 and 75 of the latest Heathkit Catalog for full details on the Microprocessor Course and Trainer — and our complete line of top-quality Heath/Zenith Courses.

If you don't already have a Heathkit Catalog, send for your free copy at one of the addresses below. Or pick up your copy at the nearest Heathkit Electronic Center* in the U.S. and Canada, where Heath/Zenith Educational Courses are displayed and sold.



Start on the road to your future in electronics with the award-winning Heath/Zenith Microprocessor Course.

Don't wait until tomorrow for knowledge you can learn today.

HEATH
ZENITH

Educational Systems

Dept. 020-693, Benton Harbor, MI 49022

In Canada: contact Heath/Zenith Educational Systems, 1480 Dundas St. E., Mississauga, Ontario L4X 2R7

Also at Heathkit Electronic Centers from coast-to-coast.

(*See the white pages of your phone book for the location nearest you. In the U.S., Heathkit Electronic Centers are units of Veritechnology Electronics Corporation.)


ED-140

IF YOU OWN A RADIO, THIS MICROPHONE WILL LET YOU TRANSMIT FURTHER AND CLEARER OR WE'LL GIVE YOU YOUR MONEY BACK!



**Guaranteed to
out perform any mic
on any radio!**

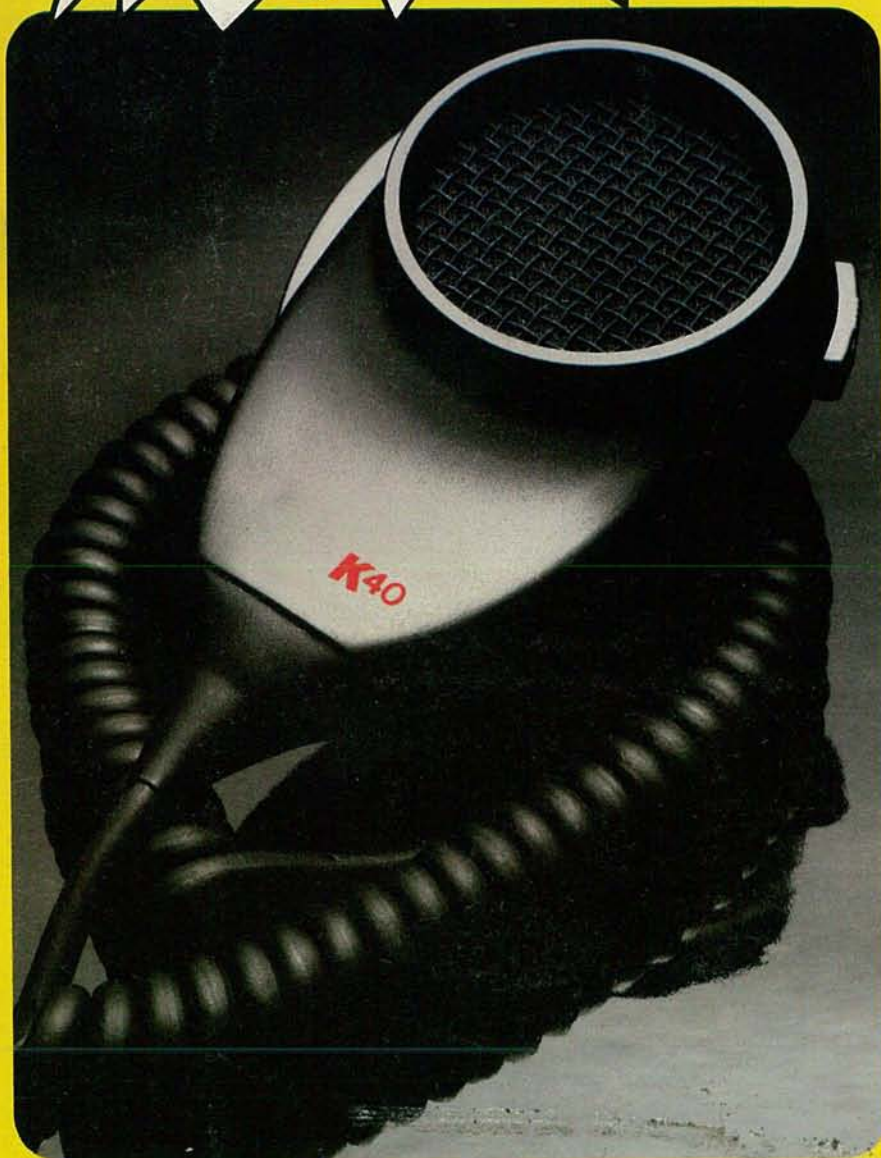A speech processor microcircuit, designed by us, that eliminates splatter, boosts power and recharges its own battery. A patented American invention made in an American town.



CHECK OUT THE EXCLUSIVE FEATURES!



- CLIPS ANYWHERE
- PROCESSES SPEECH WITH COMPUTER CIRCUIT
- SOUND SENSITIVE 2 INCHES OR 2 FEET
- NOISE CANCELLING
- TWO MICS WITH ONE SWITCH
- FRESH CHARGE WITH NO BATTERIES

YOUR DOUBLE GUARANTEE

GUARANTEE I:

The K40 Speech Processor is guaranteed to outperform any microphone it replaces or return it for a complete and full refund within 7 days from the K40 Dealer that installed and tuned it.

GUARANTEE II:

Unconditionally guaranteed for 12 months. Guaranteed against cracking, chipping, or rusting. Guaranteed against mechanical failure. Guaranteed against electrical failure. No exclusions. No gimmicks. For a full 12 months.

\$44.⁵⁰ Suggested Retail

AMERICAN ANTENNA
ELGIN, ILLINOIS 60120
© COPYRIGHT AMERICAN ANTENNA

... Sold exclusively by **3500** American **K40** Dealers throughout the U.S. & Canada.