

Radio- Electronics


**YOUR NEXT CAR—
COMPUTERS UNDER THE HOOD**

\$1.25 JAN. 1981

**Convert your TV into a video monitor
Hi-fi noise reduction techniques
Bells and whistles for your robot**

**How to use universal counter/timers
Designing with majority logic IC's
An easy way to make PC boards**

BUILD YOUR OWN PAY-TV DECODER

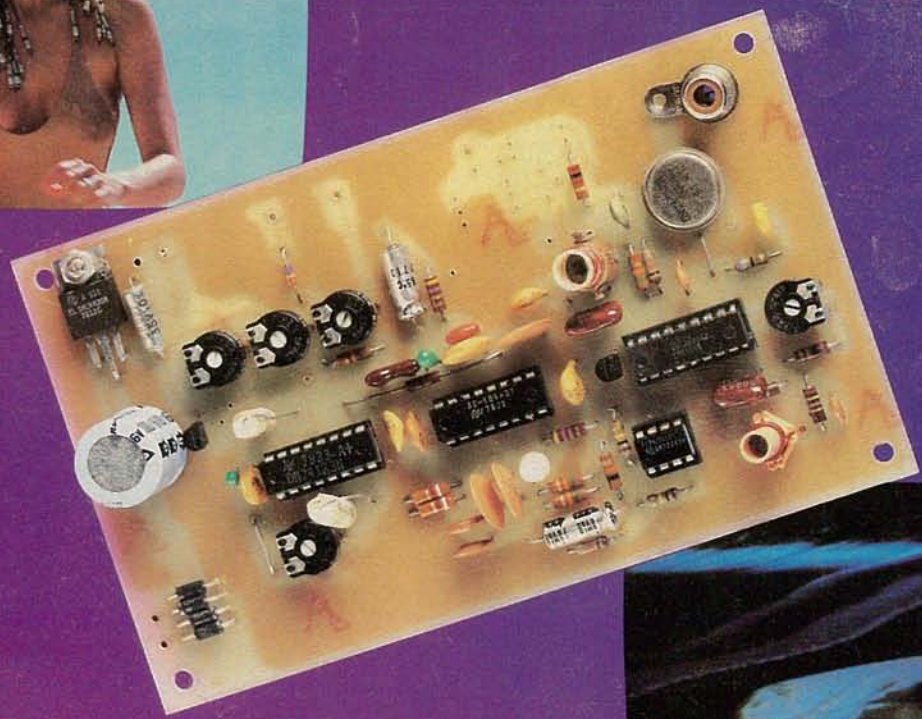

THE NEW DIGITAL

performers.



MODEL 3400
Now only \$125



MODEL 3410
Only \$140



MODEL 4000
Only \$235



MODEL 4200
Only \$270

GO DIGITAL WITH MORE FEATURES FOR THE SAME COST!

When you're shopping for digitals, be sure to check out these Triplet Digital Multimeters. They're loaded with extras that extend multimeter life and make your job a lot easier and safer.

MODEL 3400 . . . Hand size, 3½ digit with handy single range switch. Six functions with 24 ranges including Hi/Lo Power Ohms, auto-zero and auto-polarity. Overload protected to 600V on all ranges. Battery life is 200 hours min. Low battery indicator with 50 hours to spare. Price is now only \$125.

MODEL 3410 . . . All the features of the Model 3400 plus 1000 Volt AC/DC range and overload protection up to 600V on current ranges and up to 1000V on ohms or voltage ranges without fuse blow. Typical battery life of 500 hours. Price is only \$140.

MODEL 4000 . . . Bench type, overload protected with multiple fusing to 1000V on all ranges, RF shielded, auto-zero and auto-polarity. Six functions with 32 ranges, Hi/Lo Power Ohms and 3½ digit, .43" easy-read LED display. Single range selection and pushbutton function selector. Price is only \$235. (Battery version Model 4100)

MODEL 4200 . . . All the features of the Model 4000 plus a true RMS converter that computes the root-mean-square level of a complex AC input signal and displays the digital equivalent. Price is only \$270. (Battery version Model 4300)

MODELS 4100 & 4300 (not shown) . . . Ni-Cad rechargeable battery versions of Models 4000 & 4200. Price of Model 4100 is \$290 . . . Model 4300 is \$325.

Triplet's over 75 years experience is evident in the engineering firsts included in these digital testers. For a free, no-obligation demonstration, contact your Triplet Distributor, Mod-Center or Representative. Triplet Corporation, Bluffton, Ohio 45817.



Triplet performance... a tough act to follow

TTT TRIPLETT

Telephone (419) 358-5015 • TWX: 810-490-2400

CIRCLE 57 ON FREE INFORMATION CARD

CIRCLE 58 ON FREE INFORMATION CARD, IN-PLANT Demonstration

Bone Fone Clone

If you thought the Bone Fone was great, wait until you hear what's new. Here's the latest on the Bone Fone spin-offs.

It started with the Bone Fone. And this very unusual stereo system has created a whole new series of products.

The Bone Fone is an AM/FM stereo radio that drapes around your neck like a scarf. Two speakers, placed near your ears, not only provide excellent stereo separation, but vibrate slightly through your bones to give you the same sensation as standing in front of your home stereo system.

UNEXPECTED APPLICATIONS

Shortly after it was introduced, the Bone Fone became a very popular product for a variety of reasons. A lady in Helena, Montana who bought the unit for her son told us, "It's made a significant contribution to my sanity. No more rock n' roll blasting through the house, the sound goes where my son goes."

A jogger in Rowlett, Texas wrote us "Amazing separation, fantastic stereo response, helps my jogging tremendously. I wasn't really expecting this type of quality through a magazine ad at this price."

But one of the most unexpected letters came from a man in Belle Center, Ohio. "You don't have to be young and jog to enjoy Bone Fone. You see, I'm 73 years old. I just sit and listen."

LETTERS EVERYWHERE

Letters have come from mailmen, roller skaters, skiers, cyclists, motorcycle enthusiasts, hikers and even people who listen to the Bone Fone stereo while walking their dog. The Bone Fone appeals to practically every American.

The Bone Fone was designed by an engineer who wanted to listen to good stereo music without carrying heavy box radios or bulky headphones. Headphones block out all other sounds—even warnings which could be dangerous outdoors, and box radios are heavy and disturb those around you. So he invented the Bone Fone—"the stereo sound you wear around."

Weighing only 17 ounces and powered by

4AA cell batteries the Bone Fone stereo provides a sound that would be impossible to describe in an advertisement. The cliché, "you've got to hear it to believe it," certainly applies here. And for **\$69.95** it's the lowest priced stereo entertainment product available.

But what about the sport enthusiast who can care less about stereo music? Or the person who wants just the news? Or simply the person that just listens to AM radio and doesn't want to spend \$69.95?



The Bone Fone drapes around your neck like a scarf and has a sound that you find incredible when you first hear it.

Enter NUTS! NUTS is the AM version of the Bone Fone for sports nuts, news nuts, jogging nuts or anybody who wants a low cost Bone Fone without FM or stereo. NUTS sells for **\$39.95** complete with two speakers and a strap that firmly attaches the unit to you for any physical activity.

Sitting at a football game, walking your dog, jogging—NUTS gives you a convenient way to listen to music, news and sports without paying a premium for stereo.

But the Bone Fone spinoffs don't end there. There's the Neck Fone—a device you place over your shoulders and plugs into your home stereo system. This lets you enjoy your home stereo without disturbing those around you and without the bulk of headphones. The Neck

Fone sells for **\$34.95**.

So there you have it. Three exciting products—Bone Fone, NUTS, and the Neck Fone—three unusual solutions designed to solve any gift-giving problem.

LOWEST-PRICED STEREO

Compare the Bone Fone price with any box radio, stereo system or even the new \$200 Sony Walkman. The Bone Fone is the lowest-priced quality personal stereo system you can buy. It is also safer than headphones as it leaves you free to hear the sounds around you and keeps you in touch with the environment.

To order any of the above products, simply send your check or money order for the amount listed above plus \$2.50 for postage and handling (Ill. residents add 6% sales tax) to the address below, or credit card buyers may call our toll-free number below. Each unit is backed by a 90-day limited warranty and a service-by-mail facility as close as your mailbox. Service should rarely be required as the units use solid-state components and are designed to take rugged treatment. JS&A is America's largest single source of space-age products—further assurance that your modest investment is well protected.

The Bone Fone started a small revolution. Be part of that revolution with the space-age way to listen to music, news and sports. Order a Bone Fone product at no obligation, today.



Dept. RA One JS&A Plaza
Northbrook, Ill. 60062 (312) 564-7000
Call TOLL-FREE 800 323-6400
In Illinois Call (312) 564-7000

© JS&A Group, Inc., 1984

ITEM NO.
WK-7

CMOS SAFE

IC INSERTION/EXTRACTION KIT

KIT INCLUDES

- MOS-1416 14-16 CMOS SAFE INSERTER
- MOS-2428 24-28 CMOS SAFE INSERTER
- MOS-40 36-40 CMOS SAFE INSERTER
- EX-1 14-16 EXTRACTOR
- EX-2 24-40 CMOS SAFE EXTRACTOR




OK MACHINE & TOOL CORPORATION
 3455 CONNER ST., BRONX, N.Y. 10475 U.S.A.
 PHONE (212) 994 6600 TELEX NO. 125091



PRINTED IN U.S.A.

PATENT PENDING

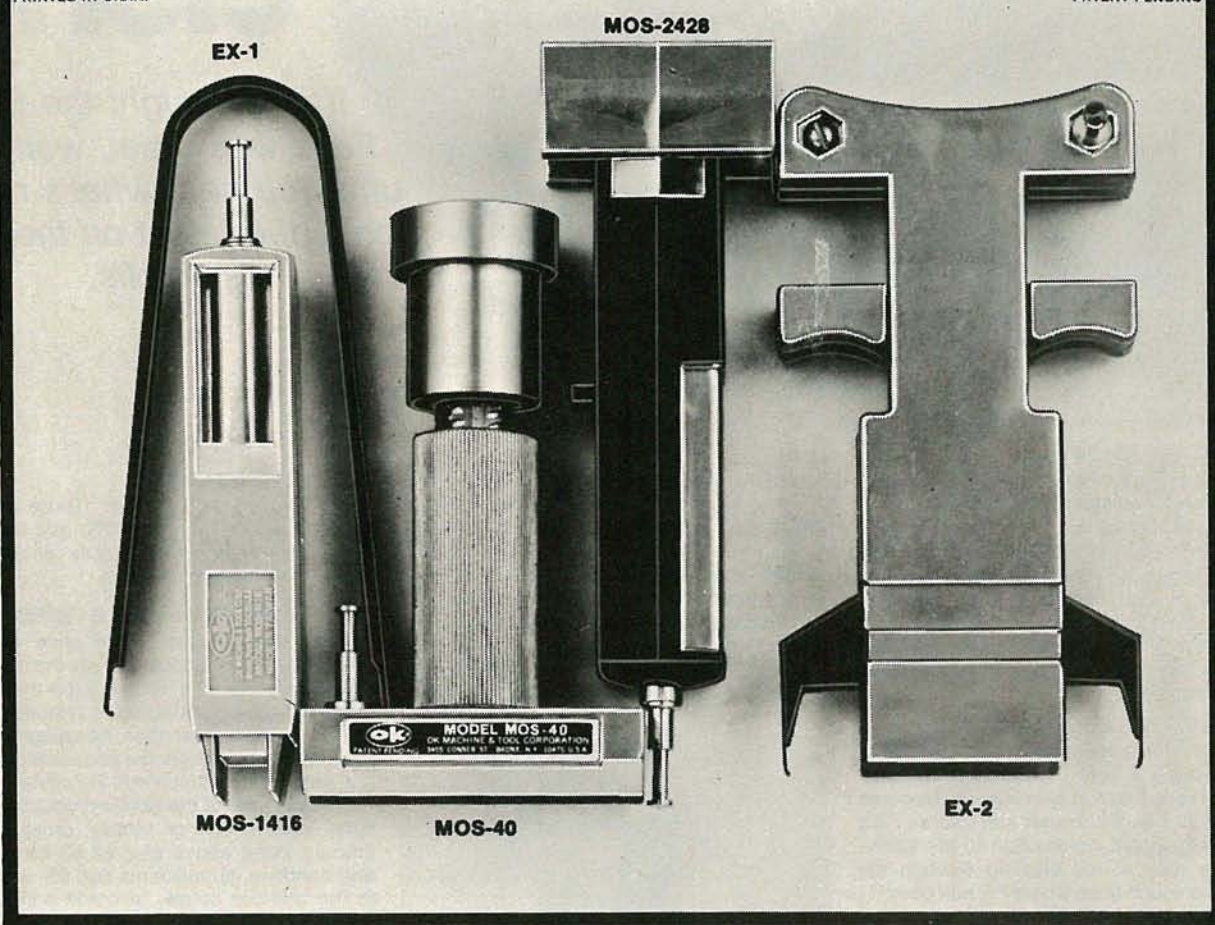

WK-7	COMPLETE IC INSERTER/EXTRACTOR KIT	\$29.95
------	------------------------------------	---------

INDIVIDUAL COMPONENTS

MOS-1416	14-16 PIN MOS CMOS SAFE INSERTER	\$ 7.95
MOS-2428	24-28 PIN MOS CMOS SAFE INSERTER	\$ 7.95
MOS-40	36-40 PIN MOS CMOS SAFE INSERTER	\$ 7.95
EX-1	14-16 PIN EXTRACTOR TOOL	\$ 1.49
EX-2	24-40 PIN CMOS SAFE EXTRACTOR TOOL	\$ 7.95

MINIMUM BILLING \$25.00. ADD SHIPPING CHARGE \$2.00. NEW YORK RESIDENTS ADD APPLICABLE TAX.

OK MACHINE & TOOL CORPORATION 3455 CONNER ST., BRONX, N.Y. 10475 (212) 994-6600/TELEX 125091

CIRCLE 48 ON FREE INFORMATION CARD

**SPECIAL
FEATURES**

- 45 **ELECTRONICS IN YOUR NEXT CAR**
Looking under the hood will reveal advanced engine-control systems, including microprocessors. Here's a look at those new systems and how they function.
Martin Bradley Weinstein
- 56 **UNIVERSAL COUNTERS/TIMERS**
A new breed of test instrument for the technician and experimenter. Here's how they're used and what's available on the market. **Martin Bradley Weinstein**

BUILD THIS

- 41 **PAY-TV DECODER**
Adaptor connects to the video-detector output inside your TV to descramble over-the-air pay-TV signals.
Ray Pichulo
- 49 **COMPUTER/TV INTERFACE**
Adaptor lets you modify your TV set for use as a video monitor. **David E. Cartier**
- 51 **UNICORN-I ROBOT**
Modifying the arms to provide a twist-of-the-wrist function plus adding LED motor-direction indicators.
James A. Gupton, Jr.

TECHNOLOGY

- 4 **LOOKING AHEAD**
Tomorrow's news today. **David Lachenbruch**
- 22 **SATELLITE TV NEWS**
The latest happenings in an exciting new industry.
Gary H. Arlen
- 64 **MAJORITY LOGIC**
Majority-logic IC's can make designing some digital circuits easier. Here's how those IC's work and how you can use them in your digital circuits.
John E. Cunningham
- 68 **HOBBY CORNER**
Another easy way to make circuit boards.
Earl "Doc" Savage, K4SDS
- 73 **NEW IDEAS**
A prize-winning application from a reader.

VIDEO

- 78 **SERVICE CLINIC**
Catastrophic failures in solid-state circuits. **Jack Darr**
- 79 **SERVICE QUESTIONS**
R-E's Service Editor solves technicians' problems.

AUDIO

- 60 **NOISE-REDUCTION TECHNIQUES**
A look at the various devices available for reducing the noise level in your high-fidelity system.
Joseph M. Gorin

**EQUIPMENT
REPORTS**

- 28 **Digital Meter Research DMR-100 dB Meter**
- 30 **B&K-Precision 1650 DC Power Supply**
- 32 **IET CM-500 Capacitance Meter**
- 33 **Harada Model 50 AM/FM Automotive Antenna**
- 35 **Tri-Star Tiger 500 Capacitance Discharge Ignition**

DEPARTMENTS


- | | | | |
|-----|-----------------------|----|-----------------|
| 102 | Advertising Index | 81 | New Lit |
| 74 | Computer Products | 83 | Market Center |
| 12 | Editorial | 76 | Radio Products |
| 103 | Free Information Card | 77 | Stereo Products |
| 24 | Letters | 14 | What's News |
| 72 | New Products | | |

ON THE COVER

Over-the-air pay-TV stations are sprouting up across the country. Those stations broadcast encoded recently-released movies. An adaptor connected internally to your TV set will enable you to decode those over-the-air broadcasts. The lower right-hand corner of the cover shows what the encoded broadcast looks like. The upper left-hand corner of the photo shows Bo Derek in a scene from the recent movie "10".

For a look at how the over-the-air pay-TV encoding system works, and how you can build your own decoder, turn to page 41.

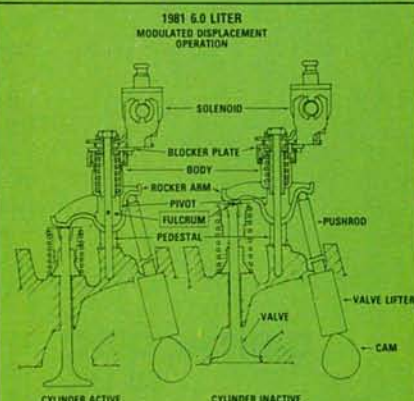*Copyright ©1979 by Orion Pictures Company



YOUR NEXT CAR. A look under the hood and how microprocessors will be controlling the engine in the next generation of U.S. cars.



MAJORITY-LOGIC IC's that will make designing digital circuits easier are available. To find out what majority logic is, and how you can use it, turn to page 64.


Radio-Electronics, (ISSN 0033-7862) Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Phone: 212-777-6400. Controlled Circulation Postage Paid at Concord, NH. One-year subscription rate: U.S.A. and U.S. possessions, \$13.00. Canada, \$16.00. Other countries, \$18.00. Single copies \$1.25. © 1980 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

Subscription Service: Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Box 2520, Boulder, CO 80322.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

looking ahead

INTERACTIVE VCR

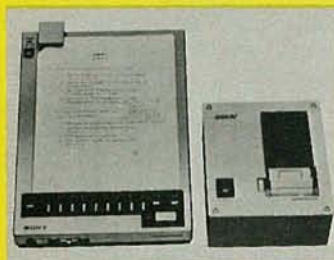

Videocassette recorders can assume many of the interactive features of sophisticated videodisc systems, using Sony's new Video Responder, designed to enhance the users of Betamax and U-matic machines for education and training. It employs a microprocessor that enables the user to respond to questions presented in the program, and provides quick access to chosen segments of the videotape. It also is equipped with a printer that records answers on a paper tape, providing a record of all of the trainee's responses.

Rather than use an alphanumeric keyboard for responses to questions posed on the tape, Sony uses a text holder that resembles a sort of electronic clipboard, on which written questions coordinated with the videotape can be attached. The holder has nine keys for multiple-choice answers. Pressing the wrong answer can automatically cause the tape to speed to the segment that tells the user he's wrong and why, giving the correct answer or encouraging him to try again.

The Video Responder is designed to be used with existing tapes, and makes it possible to re-program them for interactive use.

DISC QUIETER

For some time, Dolby had the noise-reduction field virtually to itself. Then came ANRS, followed by dbx and Telefunken's system. Now comes CBS with its own system designed primarily for use with records, and claimed to eliminate surface noise totally, and to improve dynamic range. CBS says that its new system provides reproduction almost as good as the digital or analog master tape, with an 85dB signal-to-noise ratio. The system will also work with tape recorders.

One major advantage claimed for the new CBS system is complete compatibility—encoded discs or tapes can be played on standard home equipment lacking decoders without sound deterioration. One CBS source estimates that a decoder component for existing stereo systems could be made to sell for about \$50. Built-in decoders would add a lower figure to the cost. CBS plans to use the system in making its own records and is negotiating with other record and equipment manufacturers for adoption of the system. Meanwhile, at Dolby, all is not quiet. The company is talking with its licensees about the imminent introduction of a new consumer noise reduction system, the C-type, which presumably eventually would replace the standard Dolby-B system.

DIGITAL DISC PLUS

JVC's revised entry into the competition for the digital audio disc system of the future turned out to be a major surprise. It carries three channels of audio and provides optional still pictures. Designed as an optional component for its VHD videodisc system, JVC's AHD (audio high density) videodisc is designed as the first consumer digital-TV device. At its original demonstration at Japan's Audio Fair, the disc provided three discrete audio channels and a color picture that changed every seven to ten seconds, although the company says the production model will be able to change pictures every four to five seconds. As displayed, the picture showed photographs of the performers on the record and words to songs. JVC has set no date for commercialization, but is submitting the specifications to Japan's Digital Audio Disc Standardization Committee.

COMPETITIVE PROJECTION



The new General Electric Widescreen 3000, which was designed to be priced in the \$3,500 area, has joined in the general projection-TV price competition with indications it will be competitive with the Sony, Advent and Kloss two-piece systems at just under the \$3,000 level. The GE unit is an improved three-tube version of the company's self-contained rear-projection set. When introduced in New York, one dealer put a pricetag of \$2,800 on it; at the same time, GE had a \$150 factory-rebate promotion on the model, bringing the cost to the customer down to about \$2,650. There seems to be no doubt that projection-TV prices are on the way down—and that may be just what the giant-screen medium needs to bring public acceptance.

TV STEREO PROCEEDS

The choice of a stereophonic sound system for television may be a more harmonious process. An industry-wide EIA subcommittee has been conducting field tests on three proposed systems—backed by the Electronic Industries Association of Japan, Telesonics, and Zenith. If the subcommittee reaches a strong consensus to present the FCC, multichannel sound could be broadcast along with the TV signal as early as 1982. Under the rules of the subcommittee, any system recommended must be capable of accommodating two discrete soundtracks, so it can be used for bilingual broadcasts as well as stereo.

DAVID LACHENBRUCH
CONTRIBUTING EDITOR

A breadboard as big as your ideas.

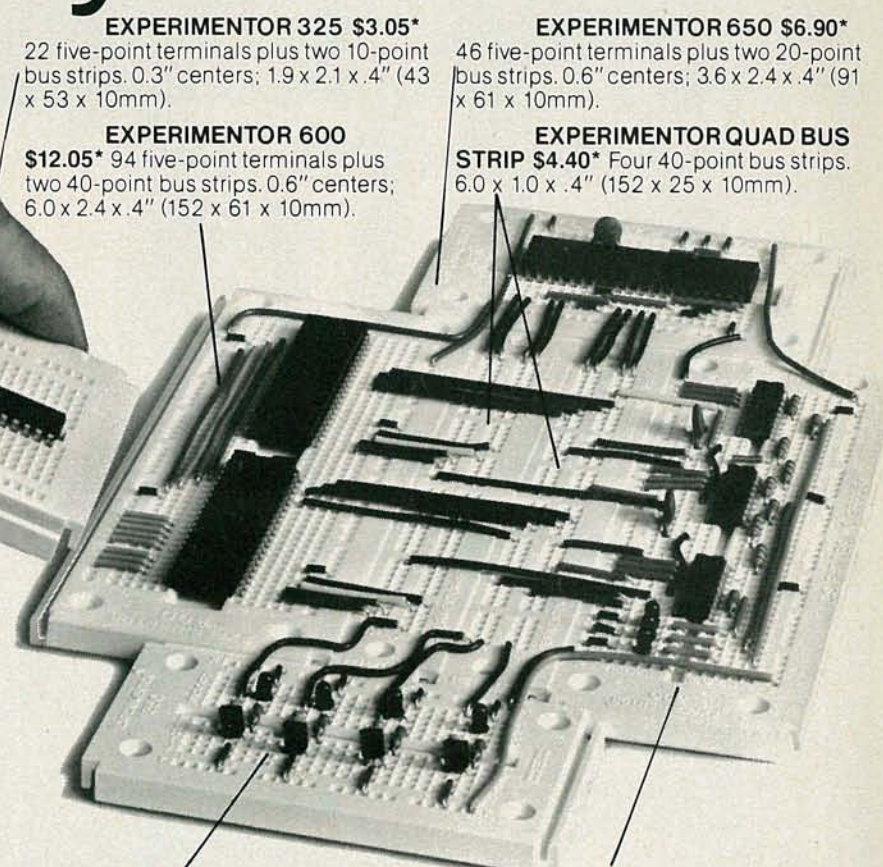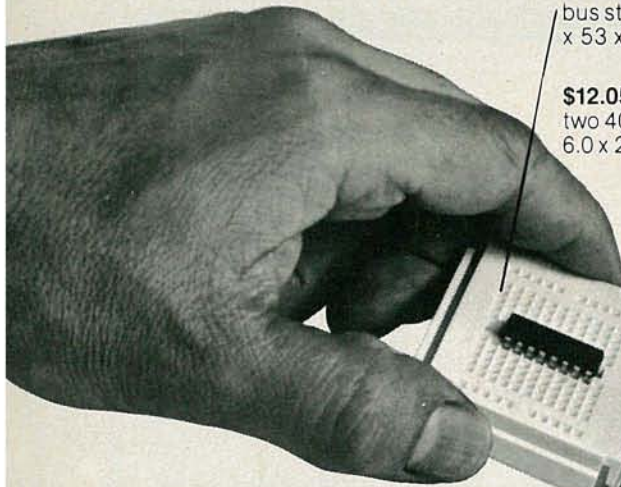

EXPERIMENTOR 325 \$3.05*

22 five-point terminals plus two 10-point bus strips. 0.3" centers; 1.9 x 2.1 x .4" (43 x 53 x 10mm).

EXPERIMENTOR 600

\$12.05* 94 five-point terminals plus two 40-point bus strips. 0.6" centers; 6.0 x 2.4 x .4" (152 x 61 x 10mm).

EXPERIMENTOR 650 \$6.90*

46 five-point terminals plus two 20-point bus strips. 0.6" centers; 3.6 x 2.4 x .4" (91 x 61 x 10mm).

EXPERIMENTOR QUAD BUS STRIP \$4.40*

Four 40-point bus strips. 6.0 x 1.0 x .4" (152 x 25 x 10mm).

EXPERIMENTOR 350 \$6.05*

46 five-point terminals plus two 20-point bus strips. 0.3" centers; 3.6 x 2.1 x .4" (91 x 53 x 10mm).

EXPERIMENTOR 300 \$10.95*

94 five-point terminals plus two 40-point bus strips. 0.3" centers; 6.0 x 2.1 x .4" (152 x 53 x 10mm).

Instant hookup for all types of components, with push-in/pull-out ease.

Adaptable for all types of components... DIP-compatible... conform to 0.1" grid; jumpers are #22-30 solid hookup wire.

Mix and match large and small chips in the same circuit. Use 300-series sockets for smaller DIPs; 600-series with 0.6" center channel for full fan-out with larger chips.

Infinite flexibility lets you expand and modify circuits vertically and horizontally, simply by snapping sockets together.

Easy mounting using 4-40 screws from front or 6-32F self-tapping screws from rear. Vinyl-insulated backing lets you fasten to any surface.

Marked tie-points simplify translation from breadboards to PC boards or wiring tables.

Ruggedly built of abrasion-resistant materials that withstand 100°C.

Quick construction of micro-processors and other circuits—each EXP-4B gives you four bus lines, with 8-, 12-, and 16-line address and data buses easily created by combining Bus Strips.

It's hard to believe how much faster and easier building circuits can be... until you try our Experimentor™ solderless breadboarding sockets. From the largest DIP to the smallest resistor, components plug in and out instantly, without special hardware or jumper cables. So you save

time and money by eliminating soldering and component damage. Start small and expand in any direction your thinking takes you, by snapping sockets together vertically or horizontally. With no limit to your ideas. Get started today, for as little as \$3.05*!

Smarter tools for testing and design.

**GLOBAL
SPECIALTIES
CORPORATION**

Call toll-free for details
1-800-243-6077
During business hours

SEE US AT SOUTHCON BOOTH 744 and 746

70 Fulton Terr., New Haven, CT 06509 (203) 624-3103, TWX 710-465-1227
OTHER OFFICES: San Francisco (415) 421-8872, TWX 910-372-7992
Europe: Phone Saffron-Walden 0799-21682, TLX 817477
Canada: Len Finkler Ltd., Downsview, Ontario

*Suggested U.S. resale. Prices, specifications subject to change without notice. © Copyright 1980 Global Specialties Corporation.

CIRCLE 32 ON FREE INFORMATION CARD

"Here's the best news yet about Fluke Digital Multimeters.

Now you can carry one home."

Right now, in selected electronics supply stores across the country, Fluke is introducing a new line of low-cost DMM's: the Fluke Series D. With their distinctive dark cases and full range of accessories, these five DMM's are designed to meet the test and measurement needs of the uncompromising service technician, home hobbyist, student or working engineer.

Fluke perfected the handheld DMM and set tough standards for accuracy and reliability that have made analog meters obsolete, and other digitals seem clumsy by comparison.

You've probably heard about their superior electrical performance, mechanical

ruggedness and environmental endurance. And now you can see for yourself at your favorite electronics dealer why Fluke DMM's have become the professional's choice the world over.

Series D Handheld Models.

D 800: Fluke's lowest-priced DMM, easy to operate, with six functions, 24 ranges and 0.5% dc voltage accuracy. Guaranteed a full year by Fluke. A sure-fire solution to basic measurement needs. \$125.*

D 802: Basic dc accuracy of 0.1% and conductance for high resistance measurements to 10,000 M Ω make this multimeter a solid price/performance value. \$179.*



If your dealer doesn't carry Series D Multimeters yet, call this number. We'll be happy to tell you who does. **1-800-426-9182**

D 804: A powerful, versatile handheld DMM with nine functions, 26 ranges, 0.1% basic dc accuracy and more. Direct temperature readings in °C with K-type thermocouples; peak hold on voltage and current functions; even an audible indicator for instant continuity and logic level detection. Available January 1981. \$229.*

Series D Bench/Portables.

D 810: By means of a Fluke-built hybrid converter, this multi-purpose DMM delivers True RMS measurements of ac voltage and current with speed and precision. Also features conductance, 0.1% basic dc accuracy, an extra 10A range and diode test. \$259.*

D 811: Same performance features as the D 810 with the added convenience of battery power. Rechargeable "C" size Ni-Cad batteries deliver up to 40 hours continuous operation. \$299.*

Series D Accessories.

A wide range of accessories to extend the measurement capabilities of your Series D Multimeter is available, including temperature and current probes, carrying cases, deluxe test leads and thermocouples.

With Series D Multimeters so easy to find and economical to own, Fluke has made selecting the right DMM much simpler. This is your opportunity to own a Fluke.



From the world leader in DMM's. Now we've designed one for you.



*suggested U.S. list price.
For technical data circle no. 25



Now NRI takes you inside the world's most popular microcomputer to train you at home as the new breed of computer specialist!

NRI teams up with Radio Shack to teach you how to use, program and service microcomputers... make you the complete technician.



It's no longer enough to be just a programmer or a technician. With microcomputers moving into the fabric of our lives (over 200,000 of the TRS-80™ alone have been sold), interdisciplinary skills are demanded. And NRI can prepare you with the first course of its kind, covering the complete world of the microcomputer.

Learn At Home in Your Spare Time

With NRI training, the programmer gains practical knowledge of hardware, enabling him to design simpler, more effective programs. And, with advanced programming skills, the technician can test and debug systems quickly and easily.

Only NRI gives you both kinds of training with the convenience

of home study. No classroom pressures, no night school, no gasoline wasted. You learn at your convenience, at your own pace. Yet you're always backed by the NRI staff and



Training includes TRS-80 computer, transistorized volt-ohm meter, digital frequency counter, and the NRI Discovery Lab with hundreds of tests and experiments.

your instructor, answering questions, giving you guidance, and helping you over the tough spots.

Explore the TRS-80 Inside and Out

NRI training is hands-on training, with practical experiments and demonstrations as the very foundation of your knowledge. You don't just program your computer, you go inside it...introduce and correct faults...watch how circuits interact...interface with other systems... gain a real insight into its nature.

You also build essential test instruments like a transistorized volt-ohm meter and CMOS digital frequency counter. You work with the exclusive NRI Discovery Lab, performing over 60 separate

experiments in all. You learn how your trouble-shooting tools work, and gain greater understanding of the information they give you. Both microcomputer and equipment come as part of your training for you to use and keep.

Send for Free Catalog...No Salesman Will Call

Get all the details on this exciting course in NRI's free, 100-page catalog. It shows all equipment, lesson outlines, and facts on other electronics courses such as Complete Communications with CB, TV and Audio Servicing, Digital Electronics,



eleven different interest areas in all.

Send today, no salesman will ever bother you. Keep up with the latest technology as you learn on the world's most popular computer. If postcard has been used, write to NRI Schools, 3939 Wisconsin Ave., Washington, D.C. 20016.



NRI Schools
McGraw-Hill Continuing
Education Center
3939 Wisconsin Ave.
Washington, D.C. 20016



(TRS-80 is a trademark of the Radio Shack division of Tandy Corp.)

Consumer Electronics 1981

This issue marks the beginning of another new year. On this happy occasion, I'll try my hand at predicting what will happen over the next 12 months and beyond. The only trouble with predicting is that you will either be right on target or miss it entirely. So with a grain of salt, here goes.....


Now that inexpensive voice synthesis is a reality, we will find more and more manufacturers incorporating this new technology into their products. Talking microwave ovens, household appliances, wristwatches, calculators and even talking test instruments are right around the corner. A little farther down the road we will see automobiles with talking dashboards.

This year we will witness the introduction of inexpensive IC's for speech recognition. However, manufacturers will look much more cautiously toward incorporating this technology into their products. They will wait until they've first gained some experience with speech synthesis. Then we will see the introduction of a whole slew of new products incorporating speech recognition. Imagine being able to shout a command to your TV set, having it respond giving a verbal confirmation.

True digital records will become a reality. Before the year is out, we will witness the market introduction of the Philips Optical Compact Disc system. This is a compact laser-based player. The discs are less than 5 inches in diameter with a 60-minute per side playing time. The system provides both a S/N ratio and dynamic range in excess of 90 dB. High-fidelity will never be the same.

Unfortunately, we will not see the introduction of teletext this year. It will remain caught up in FCC red tape and politics.

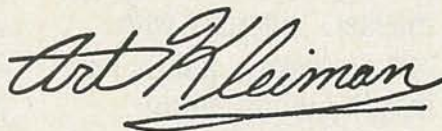No matter how we slice it, whether I'm right on target or out in left field, its going to be another great year for the electronics industry. As consumers, we will be buying higher technology items for our dollar.



ART KLEIMAN
Managing Editor

Radio- Electronics®

Hugo Gernsback (1884-1967) founder
M. Harvey Gernsback, editor-in-chief
Larry Steckler, CET, publisher
Arthur Kleiman, managing editor
Josef Bernard, K2HUF, technical editor
Jack Darr, CET service editor
Leonard Feldman
contributing high-fidelity editor
Karl Savon, semiconductor editor
Herb Freidman, communications editor
Gary H. Arlen, contributing editor
David Lachenbruch, contributing editor
Earl "Doc" Savage, K4SDS, hobby editor
Ruby Yee, production manager
Robert A. W. Lowndes, production
associate
Joan Burwick, production assistant
Gabriele Margules, circulation director
Arline R. Fishman,
advertising coordinator

Cover photo by Robert Lewis

Radio-Electronics is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature*.

Gernsback Publications, Inc.
200 Park Ave. S., New York, NY 10003
President: M. Harvey Gernsback
Vice President: Larry Steckler
Secretary/Treasurer: Carol A. Gernsback

ADVERTISING SALES 212-777-6400

Larry Steckler
Publisher

EAST

Stanley Levitan
Radio-Electronics
200 Park Ave. South
New York, NY 10003
212-777-6400

MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen
The Ralph Bergen Co.
540 Frontage Road—Suite 361-A
Northfield, Illinois 60093
312-446-1444

PACIFIC COAST Mountain States

Jay Eisenberg
J.E. Publishers Representative Co.,
8732 Sunset Blvd.,
4th Floor,
Los Angeles, CA 90069
213-659-3810
San Francisco, CA 94124
415-864-3252

SOUTHEAST

Paul McGinnis
Paul McGinnis Company
60 East 42nd Street
New York, N.Y. 10017
212-490-1021

BK PRECISION**PHILIPS****TRIPLETT****VIZ** formerly RCA**LEADER****HICKOK****HITACHI****Simpson****FLUKE****Non-Linear Systems****KEITHLEY****DORIC****DATA PRECISION****FLUKE****DIGITAL MULTIMETERS****Model 8022A:
The Troubleshooter****\$139**

- Six functions
 - dc voltage
 - ac voltage
 - dc current
 - ac current
 - resistance
 - diode test
- 3½-digit resolution
- 0.25% basic dc accuracy
- LCD display
- Overload protection

**Model 8020A:
The Analyst****\$179****Model 8024A:
The Investigator****\$219****NEW**

- Seven functions
 - dc voltage
 - ac voltage
 - dc current
 - ac current
 - resistance
 - diode test
 - conductance (1/R)
- 3½-digit resolution
- 0.1% basic dc accuracy
- LCD display
- Overload protection
- **Free case**
- Two year parts and labor warranty

- Nine functions
 - dc voltage
 - ac voltage
 - dc current
 - ac current
 - resistance
 - diode test
 - conductance (1/R)
 - logic level and continuity detect
 - temperature (K-type thermocouple)
- Peak hold on voltage and current functions
- Selectable audible indicator for continuity or level detection
- 3½-digit resolution
- 0.1% basic dc accuracy
- LCD display
- Overload protection


DATA PRECISION Model 938

0.1%, 3½-Digit, LCD DIGITAL CAPACITANCE METER

**Reg. \$179.
NOW \$149.**

- WIDE RANGING — from 199.9 pF full scale (0.1 pF resolution) up to 1999 µF full scale, in eight ranges...virtually every capacitance you'll ever need to measure.
- FAST AND EASY TO USE — Direct reading, pushbutton ranges. Just plug in and read.
- EXCEPTIONALLY ACCURATE — provides ±0.1% basic accuracy.
- TOUGH AND COMPACT — Built to take rough usage without loss of calibration accuracy. Fits and goes anywhere; takes very little bench space; always handy for quick capacitance checkout, matching, calibration, and tracking.
- PORTABLE — Palm-sized, light-weight, operates up to approximately 200 hours on a single 9V alkaline battery.
- EASY READING — big, clear, high-contrast 3½-digit LCD display, a full 0.5" high, readable anywhere.
- VALUE PACKED — Outstanding measurement capability and dependability. Outperforms DC time-constant meters, and even bridges costing 2 to 5 times as much.
- RELIABLE — warranted for 2 full years.

KEITHLEY MODEL 130 DIGITAL MULTIMETER

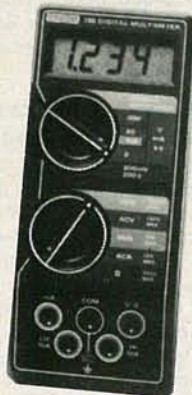**NEW
\$109.**

	RANGE	ACCURACY
DC VOLTAGE	200mV, 2V, 20V, 200V, 1000V	.5%
AC VOLTAGE	200mV, 2V, 20V, 200V, 750V	1%
DC CURRENT	2mA, 20mA, 200mA, 2000mA, 10A	2%
AC CURRENT	2mA, 20mA, 200mA, 2000mA, 10A	3%
RESISTANCE	200Ω, 2kΩ, 20kΩ, 200kΩ, 20MΩ	.5%

New Portable Digital Capacitance Meter

BK PRECISION**MODEL 820**

Call For Our Price

- Measures capacitance from 0.1pF to 1 Farad
- Resolves to 0.1pF
- 10 ranges for accuracy and resolution
- 4 digit easy-to-read LED display
- 0.5% accuracy
- Special lead insertion jacks or banana jacks
- Fuse protected
- Uses either rechargeable or disposable batteries
- Overrange indication

- V-151B 15 MHz Single Trace
- V-152B 15 MHz Dual Trace
- V-202B 20 MHz Dual Trace, High Performance
- V-302B 30 MHz Dual Trace, High Performance
- V-352B 35 MHz Dual Trace, High Performance
- V-550B 50 MHz Dual Trace, High Performance

**Call For
Special Intro
Price Offer****HITACHI**

THE TEST EQUIPMENT SPECIALISTS
TOLL FREE HOT LINE
800-223-0474

54 WEST 45th STREET, NEW YORK, N.Y. 10036 212-687-2224

**ADVANCE
ELECTRONICS**

Heath SOFTSTUFF Programs

Introduced at the PC-80 Personal Computer Conference August 21-24, 1980, the new Heath software line, SOFTSTUFF, is designed for computer users who want quality documented programs to expand the capabilities of their computers for home and business use, says a Heath spokesperson. The Heath Co. has scheduled release of as many as six new programs per month during 1981.

The first releases include a full screen editor and an improved text formatter; CPS, a file transfer utility with on-line access to Micro-NET Information Services available; a sort utility and Macro-80, an assembler from Microsoft.

Available by the beginning of 1981 will be a true CP/M. Languages to be offered include CBASIC 2 and a C compiler. Applications programs for small businesses—among them, Inventory and General Ledger—will also be a part of the first offerings.

The first offerings operate under the Heath Disk Operating System (HDOS). Programs operating under CP/M will have been introduced by 1980's end.

Many of the programs have been developed by members of the Heath Users' Group, while others have been written by a team of Heath software experts. Each program has been tested and evaluated by Heath software engineers. Each product is fully documented. The line will be available through the Heathkit catalog, as well as at the 61 Heathkit Electronic Centers in the

U.S. and Canada. Heath plans to offer the programs through other software retailers—in the U.S., Canada and internationally—in the future.

For details and price information, write for a free catalog to: Heath Company, Dept. 570-690, Benton Harbor, MI 49022. In Canada, write: Heath Company, 1480 Dundas Hwy. East, Mississauga, Ontario, Canada L4X 2R7.

Reader's Digest joins electronic information source

Reader's Digest announces that it has acquired a majority interest in Source Telecomputing Corp (STC), an electronic-information service located in McLean, VA.

By connecting their terminals to the mainframe of Source via telephone, the 7,000 STC subscribers have access to nearly 2,000 programs and data bases. Those include UPI news, financial information, airline schedules, language lessons, a guide to wine buying, point-to-point electronic mail, and many others. The cost is approximately seven cents per minute of connect-time.

New radiosonde

A radiosonde just developed by Atmospheric Instrumentation Research of Boulder, CO, is made of molded pieces of expanded polystyrene plastic fitted together mechanically, using neither adhesives nor fasteners.

The Airsonde, as the manufacturer calls it, measures atmospheric pressure, humidity

and temperature, and transmits the information through a high-frequency radio link to a ground-based computer, which prints out the information. Besides being used by such government agencies as weather stations, NASA (National Aeronautics and Space Administration), NOAA (National Oceanographic and Atmospheric Administration) and others, radiosondes are widely used in industry, by aircraft manufacturers, nuclear generating stations, air-pollution monitoring facilities, and laboratories.

The six parts of the new sonde are the body cavity, which holds the transmitter and other instruments; the cavity door; two wings, so shaped as to cause the craft to gyrate as it is carried upward by a balloon or dropped from an aircraft with a parachute, and two wing tubes. One of those carries a wet-bulb and the other a dry-bulb thermometer. The dry-bulb thermometer measures the air temperature. The difference between it and the temperature registered by the wet-bulb thermometer is used to calculate the relative humidity of the air.

Solar-cell break through

The Department of Energy's Solar Energy Research Institute (SERI) reports development of a thin-film photovoltaic solar cell with an energy conversion of more than 9 percent. The new cell was produced by Boeing's Parts, Materials and Processes Division, under contract to the Solar Energy Research Institute.

The Boeing cell is a Copper Indium Selenide/Cadmium Sulfide (CuInSe/CdS) type, made by evaporating the material onto a low-cost substrate. Thin-film cells are simpler to make and when fully developed, are expected to cost less than 10 percent of the cost of the present dominant silicon cell.

The goal of SERI is to produce thin-film solar cells with an efficiency of 10 percent. Boeing believes it will achieve that 10 percent efficiency in the near future.

Old-time radio get-together

More than 700 radio amateurs, engineers, historians and just enthusiasts gathered at the 1980 National Historical Radio Conference of the Antique Wireless Association last September 25 through 27, at Canandaigua, NY.

Highlights of the Conference (according to each participant's individual taste) were the old tubes and old equipment contests, the historical discussions—ranging from a review of early radio-frequency alternators to a talk on identifying C. D. Tuska radio receivers—or the continuous flea market in the parking lot.

The two auctions, in which members disposed of tubes or equipment they didn't

continued on page 16



THE AIRSONDE BODY, body door, wings and wing tubes, and the tongue-and-groove method of connecting them together.



**Model
3010
\$200**

**Model
3020
\$350**

Generate virtually any wave shape with famous B&K-PRECISION cost-effectiveness!

The new B&K-PRECISION Model 3020 sweep/function generator is the most versatile signal source ever offered by B&K-PRECISION. This one instrument can actually replace a function generator, sweep generator, pulse generator and tone-burst generator. Frequency coverage spans 0.02Hz to 2MHz in seven ranges, with each range providing linear 1000:1 frequency control.

A low-distortion, high-accuracy signal source, the 3020 has the versatility to generate almost any waveform. Examples include sine waves, square waves, TTL square waves, tone-burst, pulses and ramps. All waveform types can be inverted. Internal linear and log sweep capability is also featured. Both modulation and carrier levels can be varied so even a double sideband suppressed carrier test signal can be generated.

For those applications requiring standard function generator signals only, B&K-PRECISION also offers the Model

3010 low distortion function generator. The 3010 generates sine, square, TTL square and triangle waveforms from 0.1Hz to 1MHz in six ranges. An external VCO input is provided for sweep frequency tests. Variable DC offset is also featured for engineering applications. Modestly priced, the 3010 is a stand-out value.

Like other B&K-PRECISION products, the 3020 and 3010 are available for immediate delivery at your local distributor. A ten day free trial is available at many locations.

For additional information and the name of your local B&K-PRECISION distributor, call toll-free 800-621-4627.

BK PRECISION DYNASCAN CORPORATION

6460 W. Cortland Street • Chicago, IL 60635 • 312/889-9087

International Sales, 6460 W. Cortland Street, Chicago, IL 60635 USA: TELEX: 25-3475 Canadian Sales, Atlas Electronics, Ontario

CIRCLE 53 ON FREE INFORMATION CARD

JANUARY 1981 15

what's news

continued from page 14

need (often to buy as much other stuff), were the highlight to many. They were also extremely interesting to many others who bought or sold nothing, offering a clear look at much old equipment that could only be glanced at hurriedly during the preview sessions.

Several Atwater Kent breadboard models sold for over \$300 each, and an ancient marine receiver brought \$825. More than \$18,000 worth of tubes and equipment changed hands at the two auctions. Ten percent of the auction proceeds goes to the Association, enabling it to keep up the A.W.A./Electronic Communications Museum in Holcomb, NY and publish its *Bulletin*, a little quarterly magazine of historical articles and news items of interest to members of the Association.

Next year's Conference will be held at Dearborn, MI.

Bell uses standard approach in optical installation

Southern Bell Telephone has put into operation the first leg of a lightwave telephone system that connects three central offices in the Atlanta (GA) area, where lightwave telephony got its start some five years ago.

The remarkable thing about the installation, from Bell's point of view, is that the system was ordered and installed, and is being operated and maintained by local Bell personnel, using standardized Bell System procedures. To Bell, that opens the

door to general adoption of lightwave at some time in the future.

"Our successful use of standardized Bell-System procedures for ordering and installing this new technology means that the Bell System can now move ahead with larger-scale lightwave systems," states S. E. Jenette, Jr., vice president for Southern Bell in Georgia.

Moving ahead immediately with the new technology, Bell's plans include:

In March 1981, a 40.6-mile system in Pittsburgh, carrying up to 20,000 conversations.

In June, an 8.8-mile system in San Francisco, carrying 40,000 conversations, and a 27.6-mile system in White Plains, NY, carrying 20,000.

In July, a 16.7-mile, 20,000-conversation system in Philadelphia, and in December, a 26.1-mile system in Newark, NJ, also carrying 20,000 conversations.

Pioneer videodisc system now more widely available

Pioneer made its new LaserDisc videodisc system available through more than 400 retail outlets in 46 U.S. cities in October. That laser optical videodisc system consists of prerecorded discs and a player that can be connected to any standard TV set. A low-power laser reads audio and video information from the disc and transmits the picture and sound to the TV set. The audio may also be fed to a stereo-sound system.

The discs, which resemble mirrored LP records without grooves, never wear out, because no needle or stylus is used. They are recorded on both sides. Playing time is 30 or 60 minutes per side, depending on the mode of operation. Each disc contains up to 108,000 individual frames—enough for the entire Encyclopedia Britannica. Suggested retail price for the LaserDisc system is \$749, and videodiscs range from \$5.95 to \$24.95.

Semiconductor use up 23%

The world's consumption of semiconductors will increase from \$14.1 billion in 1979 to \$47.2 billion in 1985, according to Mackintosh Consultants of San Jose, CA. That represents an annual growth of 23 percent. During the same period the worldwide consumption of integrated circuits will grow from \$9 billion in 1979 to \$38 billion in 1985, an average annual increase of 27 percent.

United States companies, Mackintosh believes, will maintain a 63 percent share in worldwide semiconductor production. However, the U.S. share of integrated circuit production will drop from 71 percent in 1979 to 67 percent in 1985.

Worldwide semiconductor manufacturing equipment expenditures will increase from \$1.1 billion in 1979 to \$9.6 billion in 1985, an annual growth of 31 percent.


New home-computer facilities

Dow Jones & Co. put into effect a new price schedule with sharply reduced fees for personal computer users. The new schedule is designed to encourage them to use the Dow Jones News/Retrieval Service, a business and financial news and information base.

The new programming package, *Dow Jones News & Quotes Reporter*, permits users of the Apple II Personal computer to retrieve business and financial news and information quickly and easily from the data base. The software package is available on a diskette that stores the instructions for the Apple computer. Users of other computers may gain access to the Dow Jones data base by operating their computers in a "nonintelligent" mode.

Rates for the personal computer user during non-business hours have been set at 20 cents per minute for access to the news data base and 15 cents per minute for the securities price quotations data base, with a minimum charge of 50 cents. Formerly, personal computer users had access to only the securities price quotations, at a charge of \$3 for the first three minutes and 50 cents per minute thereafter.

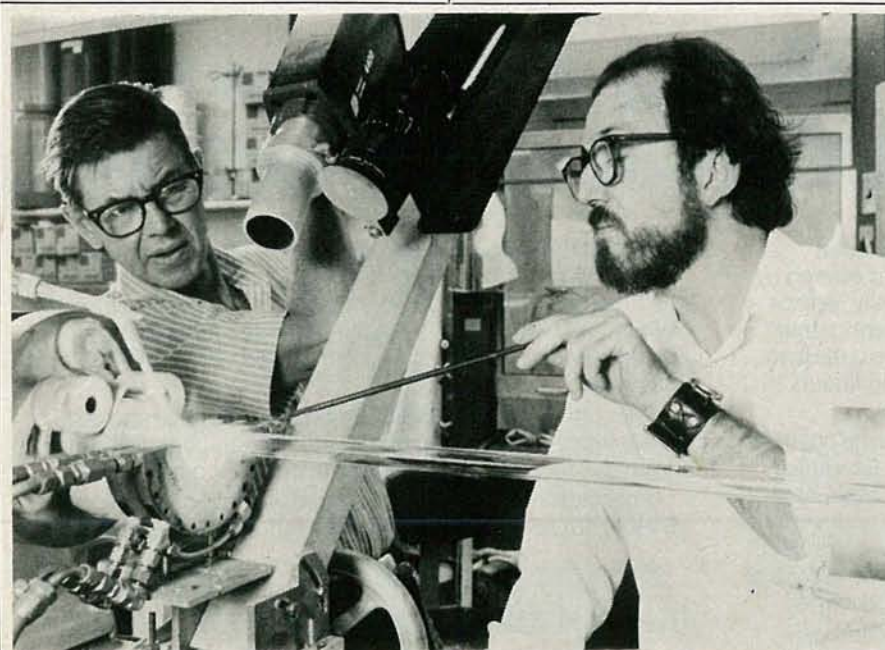
During business hours, the new personal computer rates will be \$1 per minute for news and 75 cents per minute for securities prices, with a minimum charge of \$2. **R-E**



THE ULTRATRANSSPARENT GLASS FIBERS that will carry light signals to and from the three Southern Bell switching offices in Atlanta are fabricated by a process that begins with a silica tube being heated on a glass lathe.



CM-600 Circuit Mount

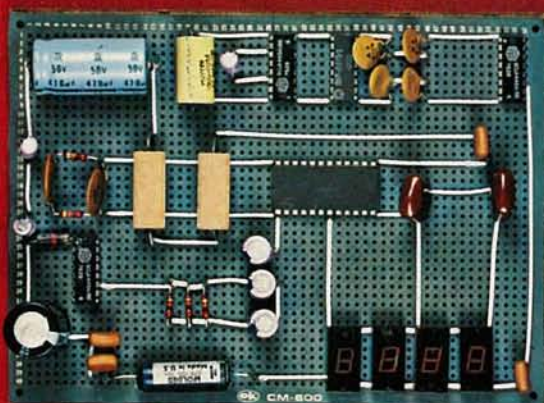

CM-600 \$6.95*
RW-50 \$2.98*

NEW CM-600 SOLDERLESS PROTOTYPE BOARD

CM-600 is a unique system for solderless construction of circuit prototypes, useful to both engineers and hobbyists. The CM-600 is a neoprene board 4½" (114mm) x 6" (152mm) with 2280 holes on .100" (2.54mm) centers. Standard components including DIP's are mounted by simply inserting leads into the holes in the long life neoprene material. Interconnections are easily made using 20 or 22 AWG (0,8 or 0,65mm) wire jumpers. Positive contact is assured by the elasticity of the hole, which compresses the leads together. To remove components or leads, simply pull out. This facilitates easy circuit changes making it ideal for breadboarding experimental circuits. CM-600 also features numbered rows and columns for easy reference.

Accessory Kit RW-50 contains 50 pcs of AWG 20 (0,8mm) insulated jumper wires of assorted lengths from ½" (13mm) to 4" (100mm). Both ends are stripped and bent 90° for easy insertion. In stock directly from

OK Machine & Tool Corporation
3455 Conner St., Bronx, N. Y. 10475 U.S.A.
Tel. (212) 994-6600 Telex 125091

* Minimum billings \$25.00, add shipping charge \$2.00
New York State residents add applicable tax

If you have put off learning more electronics for any of these reasons, act now!

- I don't have the time.
- High school was hard for me and electronics sounds like it may be hard to learn.
- I can't afford any more education.
- I have a family now.
- I'm here. You're there. I've never learned that way before. I'm not sure it will work for me.

Read the opposite page and see how you can get started today!

Be honest with yourself. Are the reasons really excuses? You already know enough about electronics to be interested in reading this magazine. So why not learn more? If you need encouragement, read on and see how excuses can be turned into results.

You don't have the time. Be realistic. All you have in life is a period of time. Use it. Try to know more tomorrow than you do today. That's the proven way to success. CIE studies require just about 12 hours of your time a week, two hours a day. You probably do have the time.

Electronics sounds like it may be hard to learn. You already know something about electronics or you wouldn't be reading this. Now, build on that. CIE Auto-Programmed® Lessons help you learn. Topics are presented in simple, logical sequence. All text is clear and concise for quick, easy understanding. You learn step by step, at your own pace. No classes to attend. Nobody pressures you. You can learn.


You can't afford any more education. Actually, you can't afford NOT to gain the skills that can put you ahead of the others. You know what inflation is doing to you now. Education—learning a skill—is an inflation-fighter that can be yours. If you are not able to pay full tuition now, CIE will lend you funds on a monthly payment plan.

You have a family now. All the more reason why you have the responsibility to advance yourself. For the sake of your family. Do you want them to have what you had or have more than you had? The choice is yours. Electronics is a rewarding career choice. CIE can help you to get started on that career.

You're there. We're here. How does CIE help you learn? First, we want you to succeed. You may study at home, but you are not alone. When you have a question about a lesson, a postage stamp gets you your answer fast. You may find this even better than having a classroom teacher. CIE understands people need to learn at their own pace. When CIE receives your completed lesson before noon any day of the week, it will be graded and mailed back the same day with appropriate instructional help. Your satisfaction with your progress comes by return mail. That's how CIE helps you learn.

NOW, IF YOU AGREE CIE TRAINING CAN WORK FOR YOU, HOW ELSE CAN CIE HELP YOU?

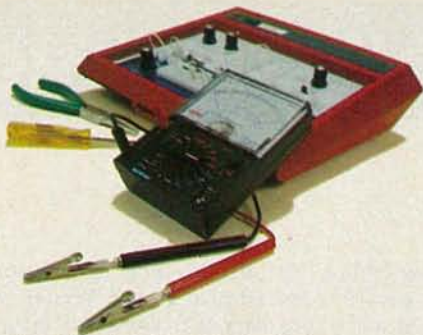Cleveland Institute of Electronics is the largest independent home study school in the world that specializes exclusively in electronics. Although "big" does not always mean "best," it is evidence that CIE is a strong, successful institution with the people and resources to help you succeed.



Step-by-step learning includes "hands-on" training.

The kind of professional you want to be needs more than theory. That's why some of our courses include the Personal Training Laboratory, which helps you put lesson theory into actual practice. Other courses train you to use tools of the trade such as a 5MHz triggered-sweep, solid-state oscilloscope you build yourself—and use to practice troubleshooting. Or a Digital Learning Laboratory to let you apply the digital theory that's essential today for anyone who wants to keep pace with electronics in the eighties.



Your FCC License can impress employers.

For some electronics jobs, you must have your FCC License. For others, employers usually consider it a mark in your favor. Either way, your License is government-certified proof of your knowledge and skills. More than half of CIE's courses prepare you to pass this exam. Surveys show that some 80% of CIE graduates who take the exam are successful.

Find out more! Today. Now.

There's a card with this ad. Fill it in and return. If some other ambitious person has already removed it, use the coupon.

You'll get a copy of CIE's free school catalog, along with a complete package of personal home study information.

For your convenience, we'll try to arrange for a CIE representative to contact you to answer any questions you may have.

If you are serious about a rewarding career, about learning electronics or building on your present skills, your best bet is to go with the electronics specialists—CIE. Mail the card or coupon today or write CIE (please mention the name and date of this magazine), 1776 East 17th Street, Cleveland, Ohio 44114.

This could be the best decision you've made all year.

Associate Degree

Now, CIE offers an Associate in Applied Science Degree in Electronics Engineering Technology. In fact, all or most of every CIE Career Course is directly creditable towards the Associate Degree.

"If you're going to learn electronics, you might as well learn it right!"

*John Cunningham
Senior Technical Director*



CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114
Accredited Member National Home Study Council

YES... I want to learn from the specialists in electronics—CIE. Send me my FREE CIE school catalog...including details about the Associate Degree program...plus my FREE package of home study information.

Print Name _____

Address _____ Apt. _____

City _____

State _____ Zip _____

Age _____ Phone (area code) _____

Check box for G.I. Bill bulletin on Educational Benefits: Veteran Active Duty

MAIL TODAY!

RE-04

satellite tv news

SATELLITE PROGRAMMING STILL GROWING

The never-ending feast of video programming transmitted via satellite continues to grow. Still another pay-TV service began aboard Westar satellites this fall: Golden West Subscription Television, a new subsidiary of Gene Autry's broadcasting company, will send 73 hours per week of movies and other shows to its stations in several cities, starting at 6 pm (Eastern Time) on weekdays and at 1 pm on weekends.

Thanks to a new series of Federal grants totalling \$1.2 million, four organizations will promote the use of satellite networking by public-service groups. Much of that will take the form of specialized teleconferencing, and the next trend will probably be towards originating video at multiple points. (Heretofore, most teleconferences involved one-way video, with telephone-line callbacks; but the increasing number of satellite uplinks makes it more feasible to originate video at several locations.) Most of the programming from those groups will be educational or informational in nature, and almost all of it will be transmitted during daytime hours aboard various satellites—wherever there is room.

Meanwhile, aboard the Westar system, look for more special-interest shows now that the FCC has formally approved "shared use" of public-TV downlinks. Every PBS station in the nation is now equipped with a satellite receiver—and all PBS programs travel via the Westar network. Many of those earth stations can now be used for video transmission by other program distributors to deliver shows to closed-circuit audiences in various cities.

In addition, the FCC recently removed several major cable-TV programming restrictions, which could open the door for the creation of new satellite superstations. Unless the new FCC ruling is overturned when it is appealed to the courts, it will permit TV stations from anywhere in the country to be beamed into a cable-TV system. That means that very popular independent TV stations—or even network affiliates from major cities—could be transmitted to distant CATV systems (probably via satellite) for use.

DIRECT BROADCAST SATELLITES

Direct-to-home broadcast satellites operating in the 12/14-GHz range may still be years away from regular use in the U.S. Nonetheless, plenty of business executives and Washington bureaucrats are spending time this fall making plans for how to operate such a system—or how to fight such services. For example, network-TV executives at ABC began lobbying on Capitol Hill recently in an effort to head off the Federal Communications Commission from making any policy that could hurt current network-TV operations. ABC argues that Congress itself should deal with setting up policy on such an important issue as DBS.

Meanwhile, the FCC itself is in the midst of a study to develop a formal American policy to present at the 1983 WARC (World Administrative Radio Conference), which will determine DBS guidelines for the western hemisphere. The FCC says its preliminary approach is "to foster, not stifle" the potential uses of direct broadcasting satellite.

Another government agency is urging the FCC to adopt a national satellite-planning policy—part of which would include DBS proposals. The National Telecommunications and Information Administration is pushing for a three-phase approach that would eventually lead to long-term planning for satellite orbit/spectrum allocation. And while all those ideas are drifting about Washington, other corporate and government officials are pleading for a DBS policy, which would permit the U.S. "to keep ahead in the area of DBS." One Comsat Executive warned that other nations are rapidly adopting DBS projects—and could soon outpace U.S. activity.

AROUND THE SATELLITE CIRCUIT

TV Ontario, a Canadian educational TV operation, is beaming a direct-to-home signal via Anik B. The programming travels in the 12/14-GHz band, and is intended especially for remote homes in northern Ontario province.

Although Satcom III replacement launch and operation is still about a year away, RCA Americom has already decided who gets the extra spaces aboard that bird, which will become the major cable-TV programming network carrier. In a recent lottery, RCA drew the names of United Video and Warner-Amex Satellite Entertainment Network; those two companies will join the 20 other programmers who will move over from Satcom I when the third RCA bird goes into service.

International satellite communications are expected to double within the next four years, according to a forecast of circuit capacity just prepared by Intelsat, the international satellite organization. The Atlantic Region will continue to be the busiest area, although Pacific-region transmissions will also jump twofold by 1984.

British Broadcasting Corp., is experimenting with satellite networking, to be used mostly for transmitting shows into BBC headquarters.

GARY H. ARLEN
CONTRIBUTING EDITOR

A superb frequency counter is frequently not counted—just because it doesn't have a high price-tag.



The truth is, our 8000B 1 Gigahertz is an excellent counter. In fact, it's preferred by many engineers, technicians, and electronic enthusiasts. Not a single competitor on the market today can surpass our price/performance ratio.

And we've deliberately kept our prices down. First, we've refused to join everybody else in their high mark ups. Instead of "charge what the market will bear," for us it's "charge a fair price." Second, we sell what we manufacture, directly to you. So extra costs of extra steps are automatically eliminated. Third, we have to build a lot of frequency counters to meet the demand. Because we do sell so many, we don't have to charge a high price to make a profit.

And about quality . . . Sabtronics frequency counters always have the most innovative features available. For example, our 8000B 1 Gigahertz Frequency Counter has a 10 Megahertz precision crystal timebase. But most important, the 8000B, using the most advanced LSI circuitry, has a guaranteed sensitivity of 30 millivolts up to 1 Gigahertz, with 20 millivolts typical. The three-stage differential amplifier IC makes this possible. Altogether, the 8000B uses only 6 IC's, making the chance of failure virtually nonexistent.

Three selectable gate times provide the measurement speed you need — and greater resolution. The resolution is further enhanced by our counter's 9-digit display.

Like the 8000B, Sabtronics' 8610B is a high-quality precision frequency counter. It features only 4 IC's, and offers a frequency range up to 600 Megahertz.

The cases of both counters are high strength impact-resistant ABS plastic. Elegant but very rugged. Sabtronics doesn't believe in skimping on the high quality construction that brings excellent performance. But we're not about to charge a high price just because we could get it!

Send in the coupon and order your new frequency counter now. Credit card holders may call.

BRIEF SPECIFICATIONS:

Frequency Range: 10 Hz to 1 GHz (Model 8000B), 10 Hz to 600 MHz (Model 8610B); **Timebase:** Frequency: 10 MHz, Stability: ± 1 ppm (20 to 40°C.), Aging Rate: < 1 ppm/year; **Sensitivity** (adjustable): Input A < 15 mV to 100 MHz, Input B < 30 mV, 100 MHz to 1 GHz (Model 8000B), < 30 mV, 100 MHz to 600 MHz (Model 8610B); **Gate Times:** .1 sec., 1 sec., 10 sec.; **Resolution:** 0.1 Hz to 10MHz, 1 Hz to 100 MHz, 10 Hz to 1 GHz; **Display:** 9-digit LED 0.4"; **Power Requirements:** 4.5 to 6.5 VDC (4 C-cells) or optional AC adapter; **Dimensions:** 8" wide X 6.5" deep X 3" high (203 X 165 X 76 mm), 1.3 pounds (590 g) excluding battery.

Making Performance Affordable

sabtronics 
INTERNATIONAL INC.

Sabtronics International, Inc., 5709 N. 50th Street, Tampa, FL 33610, (813) 623-2631.

Please send me the following:

<input type="checkbox"/> Model 8000B 1 GHz Frequency Counter(s), Assembled @ \$199.00 each	\$ _____
<input type="checkbox"/> Model 8000B 1 GHz Frequency Counter(s), Kit @ \$184.00 each	\$ _____
<input type="checkbox"/> Model 8610B 600 MHz Frequency Counter(s), Assembled @ \$129.00 each	\$ _____
<input type="checkbox"/> Model 8610B 600 MHz Frequency Counter(s), Kit @ \$114.00 each	\$ _____
Shipping and handling, \$6.00 per unit*	\$ _____
10% deposit for C.O.D. orders	\$ _____
Florida residents add 4% Sales Tax	\$ _____

Enclose check money order. (Allow two to three weeks for personal checks to clear.)

Charge: Visa Master Charge

Account No. _____ Exp. Date _____

Name _____

Address _____

City _____ State _____ ZIP _____

*U.S. only. Canada \$7.50; overseas air mail \$25.00. RE



letters

THE COLOR-BAR GENERATOR

I feel that I must comment on the errors, omissions, and inconsistencies in the article, "Affordable NTSC Color-bar Generator" in your April 1980 issue.

Very few TV stations use special color-bar generators since the feature is included as a self-test signal in all professional camera encoders. That explains why they are often called camera-bars.

Figure 1 showed 75% bars but the text discussed 100% video. Chroma is not considered when measuring video levels, since a low-pass filter is used.

White is 12.5% carrier level, not zero modulation, which is the blanking level. Maximum modulation (-87.5%) occurs at white, not sync, which is +40%.

The staircase effect of the Y component of the bars is an artifact of the action of the NTSC color equation and is unrelated to the staircase test signal.

IWQ? You must mean IQ, as used in the industry. The Y signal at the bottom of the split-bar display is always 100% regardless of whether the bars' part is 75% or, less commonly, 100%.

White is, by definition, *not* saturated. The term "saturation" is applicable only to chroma—not luminance.

Several important properties of the bars' signal were omitted completely. They have to do with the way in which the bars are made. Bars are the result of switching red, green, and blue into the encoder in such a way that the first four bars receive full-scale green, the first two, the 5th and 6th receive full red, and the first, 3rd, 5th, and 7th receive full blue. A look at the receiver screen with the beams turned off in pairs shows that clearly.

One of the properties of the process is that the first and 8th bars have zero saturation and all others have 100% saturation, regardless of level changes. Another is that when the primaries are viewed singly, the bar segments will have equal brightness if—and *only* if—the system is free of distortion, the demodulation axis is 90°, and the receiver color controls are set for correct color reproduction. That gives a visual check for hue and saturation settings.

TED DAVIS,
Riverton, IL

I think the differences referred to in Mr. Davis' letter lie in the interpretation. Some of the comments, I do not understand: For example, white is zero modulation; the tips of the horizontal sync pulses are 100% modulation. That is done deliberately to give better sync on a weak signal. With no signal, the screen is white.

The term "IWQ" was taken directly from the instrument manual. (As far as I know, this is the first time I have seen "IQ" used, though it is quite applicable.) The manual uses "IWQ" to mean "minus in-phase chroma/white/quadrature chroma," and, to me, that is the more comprehensible term. (The "Y" confuses me: I keep wanting to call it "yellow.")

I don't know whether the statement that very few TV stations have color-bar generators is valid; but, in my opinion all TV stations should have them. I know of several that do: the color-bar generators are used at the start of the broadcast day for setting up the color cameras so that each has identical response. The most frequent offenders in the "purple people" department is
continued on page 26




Portable Oscilloscopes

15 MHz Triggered Miniscope Model MS-15

15 MHz Dual Trace Triggered Miniscope
Model MS-215

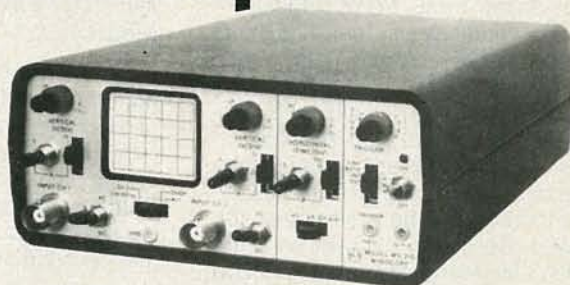30 MHz Dual Trace Triggered Miniscope
Model MS-230



New Touch/Test 20 Multimeter

A portable/bench-type meter than tests and measures 10 electrical parameters, 20 functions & 45 ranges.

MEASURES:

- AC and DC Voltage
- AC and DC Current
- Resistance
- Temperature, °C & °F
- Conductance
- Capacitance
- Performs diode/transistor and continuity tests

FEATURES

- Touch selection and control of functions, ranges and power.
- Large (0.55" high) LED readout.
- In-circuit test capabilities.
- Size: 2.9" H x 6.4" W x 7.5" D.
- Weighs less than 3 lbs.

Order with Confidence and get the Fordham Advantage!

Call for
our prices **TOLL FREE**
(800) 645-9518

in N.Y. State call (516) 752-0050

FORDHAM

855 Conklin St. Farmingdale, N.Y. 11735



- Master Charge
- BankAmericard
- VISA
- COD
- Money Order
- Check
- COD's extra

Innovations

The sharpest picture ever achieved in big-screen projection TV

The new Heathkit Screen Star sets a new standard in picture quality for big-screen projection TV. The finest F1.0 lenses you can buy produce one of the clearest, brightest pictures ever.

Imagine watching all your favorite TV movies and sports events on a big 6-foot diagonal screen. Heathkit's three-tube projection gives you brighter, more vivid color. And it's a lot easier to build than conventional TV's.

A complete computer system in one compact unit

The Heathkit All-In-One Computer takes the guesswork out of selecting a balanced computer system. It includes built-in floppy storage, smart terminal, heavy-duty keyboard, 12-key numeric pad, Z80 CPU, and 16K RAM expandable to 48K—all in one compact unit.

Two Z80 microprocessors mean terminal and computer never share power. So both can operate faster on more complex programs. And there's no better way to learn about computers than to build one yourself.



The only computerized home weather station for instant, up-to-the-minute weather reports

Just push a button for reliable weather information anytime you need it with the unique Heathkit Weather Station.

It gives you digital readouts of F or C temperatures, wind speed in miles or kilometers per hour or in knots, wind direction, barometric pressure, date and time of day, even the wind chill factor.

This microprocessor-based weather computer has memory to store data and precision infra-red sensing devices built into the outdoor transmitter. And it's very easy to build.

The finest stereo receiver ever introduced by one of the leaders in audio technology

It's loaded with luxury features that let you adjust your music to your preference.

Special features include a Precision Tuning System (PTS) that automatically corrects mistuning. 5-section FM tuning capacitor gives you maximum rejection of unwanted signals for lower noise, cleaner sound. Digital frequency readout, center tune meter, and flywheel loaded tuning are just a few of the luxury touches. Complete specifications are in the latest Heathkit Catalog.

FREE CATALOG

See all the newest innovations in build-it-yourself kits in the latest free Heathkit Catalog. It contains nearly 400 exciting kits for your home, work or pleasure. Send today.



Send to: Heath Company, Dept. 020-732
Benton Harbor, MI 49022

Yes, please send me a Heathkit Catalog.
I am not currently receiving your catalogs.

Name _____

Address _____

City _____ State _____

CL-725A Zip _____

Heathkit®

If coupon is missing, write Heath Co.,
Dept. 020-732
Benton Harbor, MI 49022

Heathkit Products are also sold and serviced at Heathkit Electronic Centers (units of Veritechnology Electronics Corporation) in major cities throughout the U.S. See your white pages.

LETTERS

continued from page 24

the film-camera chain. One of my "local stations" is a common offender in that area; they either don't have a color-bar generator, or they aren't using it!

The comment that Fig. 1 shows "75% bars" is mildly incorrect: the drawing says of the last bar "Gray: 75% white." The tip of that bar is at 100 IEEU units, or zero modulation. Full modulation is at the -40 IEEU-unit level, and the black or reference (setup level) is at a +7.5-unit level. The bars in Fig. 3 show the two different chroma levels, at 20 IEEU-unit modulation and 40 IEEU-unit modulation. The text explains why that was done.

All in all, I think the main differences here

lie in the interpretation of certain things, and are perfectly natural. Mr. Davis would agree, I am sure, that the color-bar generator is a very accurate and useful instrument, and should be of great help in TV stations and in the better TV repair shops.

—Jack Darr

THE CONTRACTION EQUATION

For the many readers whose curiosities were stimulated by my exposé on the unreality of Einstein's famous "train-and-simultaneity" thought experiment (Letters, April 1980), I propose another thought-provoker involving simply capacitor plates and measuring rod:

Matter, regardless of what it is—electrons, clocks, measuring rods, starships, you name it—is purported by Einstein's

theory to suffer length contraction in exponential proportion to velocity. The relativistic equation for the "revised" length is

$$L' = L\sqrt{1 - v^2/c^2}$$

where c is the velocity of light and L is the length at rest, which is also unchanged to an observer moving with the matter. If you suspect that it is unreal—that an object cannot be both contracted and not contracted—you are at the heart of the paradoxical nature of Einstein's theory. We are obliged to investigate further.

Consider, then, oppositely-charged capacitor plates attached to each end of a moving measuring rod. Einstein would say: (a) to an observer moving with the rod its length is "normal" and the plates remain separated by a substantial distance; (b) to the "rest" observer, and for v close enough to c , the rod is contracted into a thin disc, so the plates and charges are very close.

As should be obvious to anybody who learned "Electronics I," if (b) is true, and Einstein's equation is consistent with the laws of electronics, the field intensity between the plates is such that the charges must arc across the small gap separating the plates and neutralize them. But, that is rejected by (a)! The situation is self-contradictory.

It is self-contradictory because it is unreal, as mentioned, the culprit being Einstein's contraction hypothesis (b) which is itself unreal, nonexistent. Only (a) represents reality since the plates maintain their charges (presuming that conditions remain stable) and that must realistically be independent of any external observers not partaking in the motion.


Simply because experimental evidence appears to endorse Special Relativity does not guarantee that the theory is physically possible and logically consistent. "Thought experiments" are excellent for identifying its fallacies. But is there any performed experiment contradicting Einstein? Yes. In 1971, the Hafele-Keating Experiment found that, compared with a clock at "rest", a high-velocity cesium-beam clock recorded a time loss, but another flown in the opposite direction recorded a time gain, grew older. The latter was an anomaly contradicting Special Relativity's time dilation predicted for relative motion. Yet, physicists never adequately and honestly admitted that, and texts exclude references to the clock that "aged" faster.

One experimental fact like that proves that the universe does not, in reality, obey rules postulated by Einstein. That happens because those rules were never real originally.

ANTHONY HANS KLOTZ,
Babylon, NY

The equation presented above is the first of the three Lorentz-Fitzgerald Contraction equations, and deals with length. The second deals with time, and the third with mass. The implications of the first equation are that at the speed of light, the length of the object so traveling would be zero in that direction. The third equation, dealing with mass, implies that at the speed of light, the mass of the object would be infinite. It was through his work on the Lorentz-Fitzgerald Contraction equations that Einstein arrived at his famous $E = mc^2$. But there was no specific Einstein contraction theory or equation.—Editor.

R-E

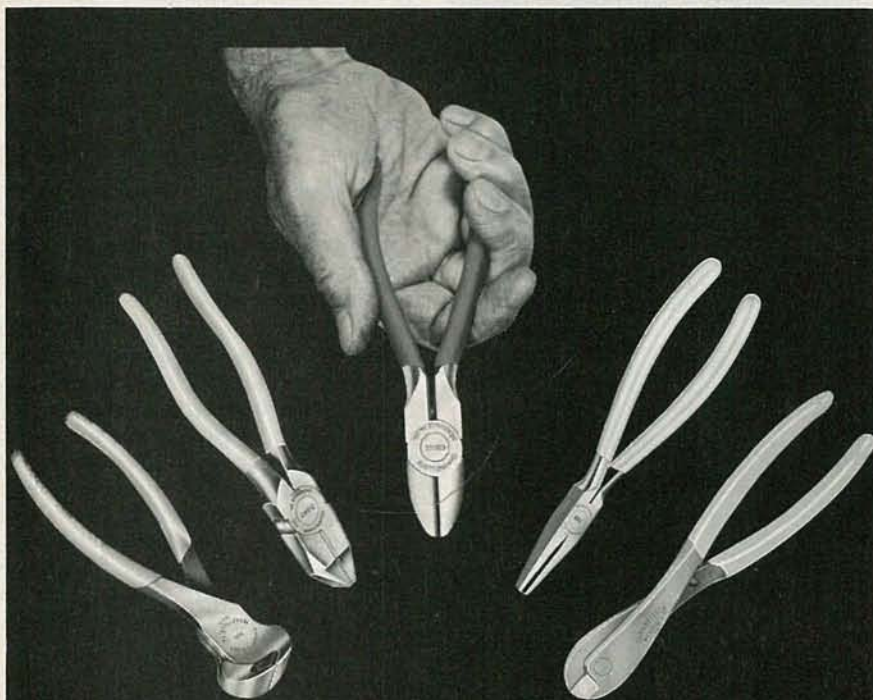

There's Never A Dull Moment With One Of These On The Job


Keen enough to cut a human hair, tough enough to cut piano wire - cleanly, quickly, time after time, year after year. Cutting pliers by CHANNELLOCK. Hand honed, perfectly mated cutters scientifically heat treated to hold their edge. Precision made of highest grade forged steel. Beautiful high polished finish. Blue dipped plastic comfort grips. Quality in every detail (at no premium in price). CHANNELLOCK. Be sure that name is on the pliers you buy.

CHAN NEL LOCK

CHANNELLOCK, INC. • Meadville, Pennsylvania 16335

Meet The Rest Of The Family. Send For Free Catalog.

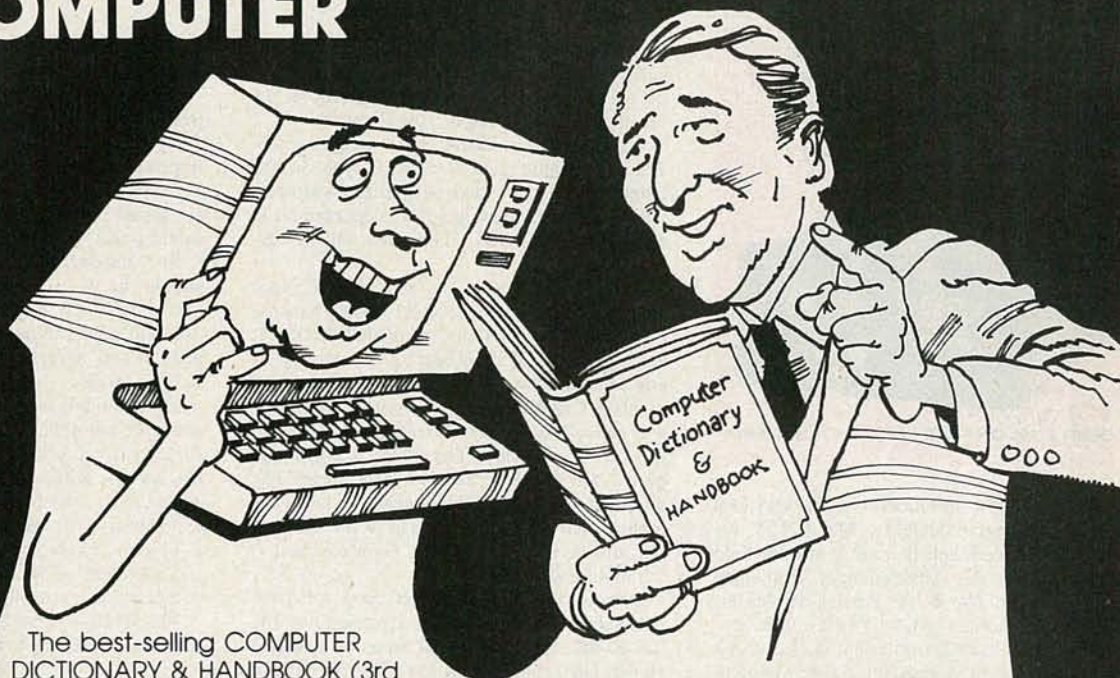CARRY ON AN INTELLIGENT CONVERSATION WITH A COMPUTER



The best-selling **COMPUTER DICTIONARY & HANDBOOK** (3rd Edition) is like a one-volume computer library. Whether you're trying to catch up with computers - or trying to stay ahead - this is the most valuable reference book you can own. This hardbound dictionary and handbook translates computer jargon into language that every teacher, student, scientist, computer operator, engineer, or businessman can understand.

COMPREHENSIVE

The most comprehensive reference available for all phases of computers and computer applications. Includes 14 appendices covering computer-related subjects such as operational control, storage devices, main memory devices, time-sharing principles and procedures, data communications, computer languages, and much, much more.

COMPLETE

Contains over 22,000 definitions, acronyms, and abbreviations dealing with the field of computers and data processing.

By Charles J. Sippl and Roger J. Sippl. 928 pages. No. 21632. \$29.95

AVAILABLE IN A PERSONAL SIZE

The **COMPUTER DICTIONARY** is a personal-size volume that contains much of the information contained in the larger **COMPUTER DICTIONARY & HANDBOOK**. The **COMPUTER DICTIONARY** includes over 12,000 entries - including definitions, acronyms, and abbreviations. Catchwords are used for the first and last entries on each page and shown at the top of each page. Extensive cross-referencing is used. 624 pages. No. 21652. \$12.95.

Mail to: **Howard W. Sams & Co., Inc.**
4300 West 62nd Street
P.O. Box 7092
Indianapolis, IN 46206
(317) 298-5400

ADO56

Account No. _____
Expiration Date _____
Name (print) _____
Signature _____
Address _____
City _____ State _____ Zip _____

• COMPUTER DICTIONARY & HANDBOOK.	No. 21632.	\$29.95	QUANTITY _____
• COMPUTER DICTIONARY.	No. 21652.	\$12.95	_____
	Amount of order	\$ _____	
	*For charge cards, add \$2.00 postage and handling costs	\$ _____	
	Add local sales tax where applicable	\$ _____	
	Total Amount of Order	\$ _____	
• <input type="checkbox"/> PAYMENT ENCLOSED (save postage and handling costs)			
• <input type="checkbox"/> CHECK	<input type="checkbox"/> MONEY ORDER		
• <input type="checkbox"/> VISA*	<input type="checkbox"/> MASTER CHARGE*	Interbank No. _____	

Prices subject to change without notice. All books available from Sams Distributors, Bookstores, and Computer Stores. Offer good in U.S.A. only. In Canada, contact Lenbrook Industries Ltd., Scarborough, MIH, 1H5, Ontario, Canada. Offer expires 4/30/81.

Sams BOOKS®

JANUARY 1981

equipment reports

Digital Meter Research Model DMR-100 Digital dB Meter



CIRCLE 101 ON FREE INFORMATION CARD

DIGITAL METER RESEARCH COMPANY, PO Box 28, Arlington Heights, MA 02175, recently introduced their first entry into the field of specialized audio test equipment. That entry is their model DMR-100 Digital dB Meter. It's a very accurate digital dB meter, with provisions for connecting into an audio circuit at a given point (input, output, etc.), for probing to

read stage gains, or for similar tests. Rated accuracy is 0.1 dB over the full range of 80 dB: -60 dB to +20 dB. At the -60 dB input level 0.1 dB means a resolution of 10 microvolts.

It's easy to use. There isn't a range switch. The main input jack is a BNC-type on the front panel, above two pushbutton switches. One of those switches lets you select readout in either dB or volts DC. The other will be covered later.

On the rear panel, along with the AC input and on-off switch, are two sets of dual banana-plug jacks. One of them is labelled dB INPUT, and can be used for offsetting the display by any amount needed when complex measurements are to be made. An input of +1.0 mV will cause the display to read -0.1 dB from the non-offset value. The offset is adjustable over a ±8 dB range and is highly linear. The dB OUTPUT is a DC voltage proportional to the input-signal level. The voltage is the same as that displayed on the meter. Gain constant is 1.0 mV for 0.1 dB.

Also on the back is a BNC jack for COMPRESSED OUTPUT. As the input varies over the full 80-dB range, this signal varies by less than 10 dB. Distortion is very low. This output can

be used with a scope, or phones or an audio monitor.

The other pushbutton switch on the front panel is used to select between BUFFERED and UNBUFFERED inputs. The buffered input has an impedance of 10 megohms and is useable up to 12 volts, peak input. The unbuffered input has an impedance of only 100K ohms and can be used up to 150 volts, peak.

For production-line testing, this meter should be very useful, especially for final checkout. With a standard input, the DMR-100 will read the output with high accuracy, and let the operator determine whether the units is in-spec.

For audio test work, two DMR-100's may be used; for example, one to meter input and one for output. Or, one unit can read AC signals in dB, and the other the DC level or offset of the signal. The two-meter arrangement can be valuable in such applications as gain-readings in systems where input signal slowly varies or is a function of some other parameter; e.g., compression, expansion, etc.

The DMR-100 has a 3 1/2-digit LED readout, with 0.56-inch high digits. It's housed in a *continued on page 30*

MAKE PROFESSIONAL LOOKING P.C. BOARDS FAST AND EASY

STAMP-IT ETCH-IT

Reduces Printed Circuit Board Art Work From 2 Hours to 10 Min. . .

Simple as A.B.C.

A. Stamp Components on P.C. Board. B. Use Pen to Interconnect Lines. C. Etch Board.

Are you tired of the hours of small, detailed, eye-straining art work that goes into making printed circuit boards? "STAMP IT, ETCH IT" is introducing a NEW product called "STAMP IT, ETCH IT" Kit. This Kit will take the tedious art work and many tiresome hours out of printed circuit board preparation. In just a few short minutes you have a professional looking etched printed circuit board ready for drilling!

The "STAMP IT, ETCH IT" Kit is exactly as the name implies. Following the step by step simple instructions, you can have a printed circuit board and have saved hours of frustration. As easy as you use a rubber stamp to stamp messages on paper, you stamp your component connections on copper clad printed circuit boards.

In your "STAMP IT, ETCH IT" kit we supply all component stamps shown in SE-2 Kit. In the SE-2 kit we also have resist ink enough for months and months of experimenting, ink stamp pad, resist pen, and etching containers. The most revolutionary item in your "STAMP IT, ETCH IT" Kit is . . . The Fool Proof System of etching your printed circuit boards.

With our kits and our etching containers, you are able to etch a printed circuit board as fast as bubble etching machinery and the results are as good or better.



AT LAST . . . COMPLETE LINE OF STAMP-IT ETCH-IT DIP IC SOCKETS A DREAM COME TRUE No Previous PCB Experience Necessary

IC-40 16 PIN	IC-36 16 PIN	IC-28 16 PIN
IC-24 16 PIN	IC-18 16 PIN	IC-16 16 PIN
IC-14 16 PIN	IC-8 8 PIN	

PRICE EACH	FOR COMPLETE KIT ORDER
IC-40 \$4.95	SE-2 KIT
IC-36 4.95	SE-2B KIT
IC-28 3.95	IC-8 1.95
IC-24 3.95	IC-14 3.95
IC-18 3.95	IC-16 3.95
IC-16 3.95	

\$29.95

RAINBOW INDUSTRIES MADE UP A SE-D 400 KIT FOR THE PRINTED CIRCUIT BOARD MAKER WHO WANTS EVERYTHING . . . And Just For You . . . One Complete Package Pictured Below

SE-2 KIT CONTAINS:

- CONNECTOR FINGERS
- 16 PIN DUAL IN LINE IC SOCKET
- 10 PIN ROUND IC SOCKET
- 8 PIN ROUND IC SOCKET
- TO-3 TRANSISTOR SOCKET
- TO-18 TRANSISTOR SOCKET
- LARGE & SMALL DONUT PAD
- RESIST INK
- INK PAD
- RESIST PEN

PLUS

ONLY \$9.95

PLUS 1 LB. POSTAGE

ADDITIONAL STAMPS:

Bread board stamps for all integrated circuits "Great" for experimenters.

Only \$2.95 each or all four \$9.95

#1 DUAL IN LINE #2 FLAT PACK

#3 8-PIN ROUND #4 10-PIN ROUND

- RESIST INK . . . 95c per bottle
- RESIST PEN ea. 95c
- INK PAD ea. \$1.15
- Etching Containers . . . 10 for 95c

SE-2B KIT

SE-D8 KIT

ONE COMPLETE SE-D8 KIT PLUS:

ALL THESE EXTRAS:

- Extra bottle of ink
- Batch of ink thinner and stencil cleaner
- 25 extra etching containers
- Extra ink pad
- Printed Circuit Boards: 2 each 2x4, 2 each 2x4

PLUS:

SE-83 KIT

PLUS:

ALL FOR ONLY \$54.95

ASK FOR SE-D800 KIT

PRINTED CIRCUIT BOARDS

G-10 FIBERGLASS

Size	1 Side	2 Sided
2" x 4"	.25	.35
3" x 6"	.50	.65
4" x 6"	.65	.90
6" x 6"	.90	1.35
6" x 12"	1.50	2.50
12" x 12"	2.95	3.95

See March '79 "Radio-Electronics" Hobby Corner for additional information on Stamp It, Etch It Method.


\$5.00 Minimum Order PLEASE ADD POSTAGE

master charge ORDERS WELCOME PHONE 317-297-2717

CIRCLE 38 ON FREE INFORMATION CARD

ELECTRONICS BOOK CLUB

Are you into

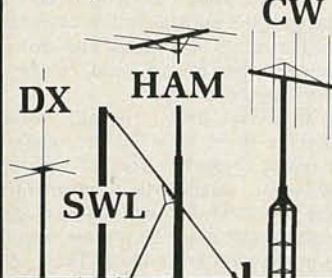

BOOK CLUB

Take 6
great books
for
\$2⁹⁵

(values to \$112.70)

Communications, QSLs, or OSCAR?

Start saving now with discounts up to 75% on hundreds of fact-filled volumes . . . PLUS special Members' Bonus Benefits!



Join now, and get a 1981 Electronics Projects Calendar . . . FREE!! (List \$4.95)

7 very good reasons to try Electronics Book Club . . .

- **Reduced Member Prices.** Save up to 75% on books sure to increase your know-how
- **Satisfaction Guaranteed.** All books returnable within 10 days without obligation
- **Club News Bulletins.** All about current selections—mains, alternates, extras—plus bonus offers. Comes 13 times a year with dozens of up-to-the-minute titles you can pick from
- **"Automatic Order"**. Do nothing, and the Main selection will be shipped to you automatically! But . . . if you want an Alternate selection—or no books at all—we'll follow the instructions you give on the reply form provided with every News Bulletin
- **Continuing Benefits.** Get a Dividend Certificate with every book purchased after fulfilling Membership obligation, and qualify for discounts on many other volumes
- **Bonus Specials.** Take advantage of sales, events, and added-value promotions
- **Exceptional Quality.** All books are first-rate publisher's editions, filled with useful, up-to-the-minute info

ELECTRONICS BOOK CLUB Blue Ridge Summit, PA 17214

Please accept my Membership in Electronics Book Club and send the 6 volumes circled below, plus a free copy of 1981 Electronics Projects Calendar. I understand the cost of the books selected is \$2.95 (plus shipping/handling). If not satisfied, I may return the books within ten days without obligation and have my Membership cancelled. I agree to purchase 4 or more books at reduced Club prices during the next 12 months, and may resign any time thereafter.

802 805 955 1005 1054 1066 1070 1120
1132 1136 1146 1152 1155 1162/1177 1184
1189 1194 1212 1216 1222 1225 1255 8224

Name _____ Phone _____

Address _____

City _____

State _____ Zip _____

(Valid for new members only. Foreign and Canada add 15%.)

RE-181

EQUIPMENT REPORTS
continued from page 28

light blue extruded-aluminum case, with black end-panels and bezels. That means durability, and also shields the meter from external interference that could affect readings. The *DMR-100* is powered by an 18 VAC input, from a wall-mounted plug-in power transformer. That reduces any chance of 60- or 120-Hz interference. The *DMR-100*'s \$250.00 price is quite reasonable for an instrument of its high accuracy and simplicity. **R-E**

**B&K-Precision Model 1650
Tri-Output DC Power
Supply**



CIRCLE 102 ON FREE INFORMATION CARD

IF YOU THINK THAT A DC POWER SUPPLY is nothing but "a transformer + a rectifier + a filter capacitor," well, that is the definition of a DC power supply. However, if you have one like the *model 1650* Tri-Output Laboratory DC power supply (from B&K-Precision, Dynascan Corporation, 6460 West Cortland Street, Chicago, IL 60635) that's something

else . . . like the difference between a moped and an MGB. One of them can do a lot of things the other cannot, and do them a lot more safely.

This is an instrument that can be used in design labs, experimental work, and the like; it's also a handy piece of test equipment to have in an electronics service shop. It's a fully-regulated, current-limited DC power supply with three separate and completely isolated outputs. It has an accurate meter that will read the voltage or current of each output; and that is what makes it a test instrument! Input voltage and current readings are awfully handy in diagnosis.

The *model 1650* has a five-volt output at five amperes for powering any kind of TTL logic circuitry. Five amps will drive a good many TTL gates! The other two outputs are identical twins, with a 0-25 VDC variable output, good up to 500 mA. The outputs can be used separately, with complete isolation, or they can be hooked in series or parallel for higher current-ratings. For a split-rail power supply, like those used for many op-amp circuits, they can be connected back-to-back.

All three outputs use "foldback" current-limiting. If the load current goes above the maximum rating, that automatically reduces the output current to at least 20% below maximum. The current meter will tell you if it happens. That feature not only protects the power supply, but also limits the damage to the equipment under test. All outputs are voltage-regulated, using IC regulators. That holds the voltage to a very tight tolerance anywhere below the maximum load.

An extremely useful feature of the *1650* is the ability of the variable "B" supply to track

the variable "A" supply. This means that, as the "A" voltage is varied, the "B" voltage will change proportionately. The "B" voltage can be set so that it will be any percentage of the "A" voltage.

Somebody put a lot of thought into the design of this power supply. Our normal tendency is to turn a knob clockwise when we wish to increase the output (in this case, the voltage) of the circuit it controls, and that is indeed the case when the "A" and "B" supplies are used independently.

In the TRACKING mode, though, 100%-tracking (where B = A) is at the counter-clockwise end of rotation of the "B" control. This means that, should you inadvertently switch from TRACKING to INDEPENDENT mode, the "B" voltage will never be greater than it was when in the TRACKING mode. Thus, you cannot accidentally overload a circuit being fed from the "B" supply . . . a nice touch.

The tracking function has many uses. In checking subassemblies and other things that have separate or different power supplies, by using 100% tracking you can simulate the effect of low or high supply-voltages on the unit's performance. You can also imitate power supply transients and so on; both voltages will vary at the same time.


The *model 1650* is a well-built and rugged piece of test gear. All controls are plainly marked, and conveniently sized. The panel is well laid-out. Operation is about as simple as it can be made.

The DC outputs all use 5-way binding posts, which can be hooked up to any kind of test-lead. There is also a green jack—for an earth ground—on the front panel. Despite all that,

continued on page 32

B&K PRECISION

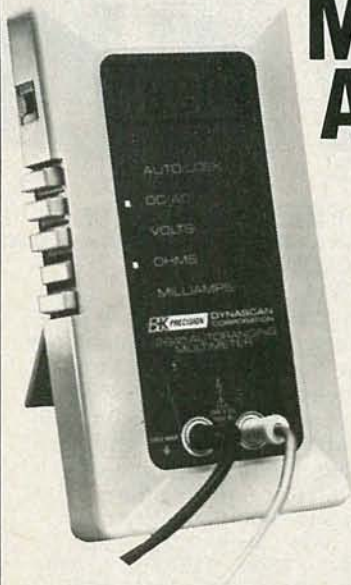Microcomputer-Controlled Autoranging DMM Model 2845



- Computer stabilized accuracy to 0.1%
- Auto-perfection
Selects range for maximum resolution
- Audible continuity indicator
Built-in audible tone generator
- G-MOV overload protection
Provides AC and DC voltage range protection to 1000 VDC or AC peak
- Shielded in RF fields
Accuracy maintained in RF fields


- Long life, high reliability
Four hermetically sealed reed relays perform range switching with virtually no contact wear.
- Microcomputer intelligence
Designed around 4-bit microcomputer. Analyzes stored data and range that provides greatest display resolution. Program memory capacity 1024 x 8 bits of ROM supported by 48 x 4 bits of data memory RAM

... in stock and available for immediate delivery.

Dual Trace 5"
30 MHz Triggered Scope
Model 1479A



Sweep/Function
Generator
Model 3020

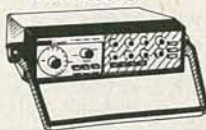

Semiconductor
Transistor Tester
Model 520B



Portable Digital
Capacitance Meter
Model 820



Order with Confidence and get the Fordham Advantage!

Call for
our prices **TOLL FREE**
(800) 645-9518
in N.Y. State call (516) 752-0050

FORDHAM

855 Conklin St. Farmingdale, N.Y. 11735



- Master Charge
- BankAmericard
- VISA ■ COD
- Money Order
- Check
- COD's extra

CIRCLE 40 ON FREE INFORMATION CARD

NOW AVAILABLE!

WATT WIZARD™

POWER FACTOR CONTROLLER CUTS THE COST OF RUNNING ELECTRIC APPLIANCES BY AS MUCH AS 50% -- AND YOU CAN EVEN SEE THE SAVINGS!

For over a year now, in magazines and newspapers the world over, there have been enthusiastic write-ups on a remarkable new device that can cut your electric bill while helping the U.S. save huge quantities of fuel.

"The NASA/Nola power saver," wrote a *Popular Science* senior editor, "was developed by Frank Nola at NASA's Flight Center in a program to reduce power consumption in space-craft motors. Nola calls it a PFC — power-factor controller. I prefer to call it a power saver, however, because that's what it does."

NASA TESTED IT

According to NASA documents, "The device has been tested at Marshall Center on over 40 types of motors, with power savings ranging up to 60%, depending on the loading. The motors tested were both single-phase and three-phase, ranging from 1/2 H.P. to 5 H.P. Most motors will show up to 40 — 50% savings when running lightly loaded or unloaded, and some will show 5-to-7% savings at rated load."

NASA's Technical Support Package showed that "The Power Factor Controller applies to induction type electric motors — the most commonly used type in all major home appliances and the most commonly used by industry."

HOW IT SAVES POWER

Popular Electronics explained it this way: "AC induction motors characteristically run at a nearly constant speed that's fixed by power-line frequency and independent of load and supply voltage. When heavily loaded, the motor draws line current that is nearly in phase with the applied voltage...Under light load conditions, the motor develops less torque by allowing more lag between the voltage and the current. This reduces the power factor while leaving the current essentially the same in magnitude.

"To minimize this waste, Nola's device monitors the motor's power factor and when it detects light load conditions, it reduces the supply voltage..... The current, now more nearly in phase with the voltage, therefore does as much useful work as before, but it and the voltage are smaller, resulting in a net savings of electric power."

THE SAVINGS CAN ADD UP

The cost of electric power keeps going up. In 1980-81 and beyond you'll pay more and more for the privilege of running your electric appliances.

Right now, the typical consumer pays about \$8 per month to operate a 16.5 cu. ft. frost-free freezer...\$10 to run a 17.5 cu. ft. frost-free refrigerator...and

National Aeronautics
and Space Administration
Patent No. 4,052,648


about \$60 for an air conditioner used during summer months. That's what you're paying to run just one of these appliances per year.

Nola's power saver can soon pay for itself, then start reducing your electric bills. Until now, the device has not been available — except for industrial models priced at \$80 or more.

INTRODUCING THE WATT WIZARD

Cynex, an American manufacturer of electrical and electronic products and a prime contractor for the U.S. Army, has been licensed by NASA to manufacture Frank Nola's power saver. Cynex calls it the Watt Wizard.

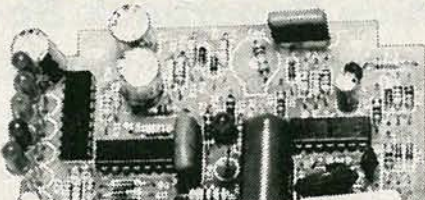The "Watt Wizard" says Ray Beauchea, the firm's **Marketing Director**, regulates the voltage fed into an induction motor making the motors run more efficiently and quieter, while lengthening motor life.



The Watt Wizard features a unique, constant power saving readout. So you can constantly monitor your energy savings.

SIMPLE TO USE

Cynex makes several models of the Watt Wizard (all with solid state design), including the 110 v. AC plug-in model we're offering. It's for single phase fractional H.P. motors (less than 1 H.P.) used in most freezers, refrigerators, fans, swimming pool pumps, vacuum cleaners, sewing machines, etc.

Simply plug the Watt Wizard into any electrical outlet, then plug the appliance into the Watt Wizard. There's no wiring required. Unlike some competitor's models (if and when available), the appliance does **not** have to be turned on before being plugged into the power saver. You can leave the appliance — whether on or off — plugged into the Watt Wizard all the time. Or you can move the Watt Wizard to various locations.

OTHER MODELS AVAILABLE

Air conditioners, washers and dryers require wire-in model. If you lack mechanical skill, you probably need an electrician to install it. We also offer it in 220 VAC single or three-phase.



MERCURY 1980 ©

EXCLUSIVE ADVANCE FEATURES

The Watt Wizard also includes two more unique features which no competitor has. It's fused so if you accidentally overload the device, it won't burn out. Just change the fuse, which is available at any auto supply store.

And Watt Wizard features a unique LED readout, so you can actually tell, at any moment, exactly how much power you're saving — 10%, 20%, 30%, 40% or 50%. This feature is available only on the Watt Wizard.

There's a "power-on" light, too. And the Watt Wizard comes with the manufacturer's 1 year limited warranty.

LOW COST — AND A TAX CREDIT

We're offering the Watt Wizard for only \$39.95, with immediate delivery. Want two? Then its just \$37.95 each. Or splurge and get three at \$34.95 each. Wire-in models for heavy duty motors are \$6 more for each unit. Add just \$2.50 postage/handling for each order (not each unit).

And next year, when you fill out your tax return, you can deduct a full 15% energy tax credit - for additional savings.

30-DAY MONEY-BACK GUARANTEE

Try the Watt Wizard for up to 30 days. If not completely satisfied, return it (insured) for a full refund.

The sooner you send for the Watt Wizard, the more you can save on your electric bills. To order, send your check or money order to the address below. Or charge it to your Visa, MasterCard, American Express, or Carte Blanche credit card. If using your charge card, you can also order via our toll-free phone number:

800-257-7850

(In New Jersey, Call: 800-322-8650)
N.J. residents, add 5% sales tax.

Or mail your order to:

INTERNATIONAL SALES GROUP
MERCURY
THE IMAGINATION PEOPLE®

Dept. RE-1, Lakewood Plaza
Lakewood, New Jersey 08701

CIRCLE 45 ON FREE INFORMATION CARD

JANUARY 1981

31

hafler

STATE OF THE ART COMPONENTS AT AFFORDABLE PRICES

Directly comparable in both sonic quality and test specifications with the most expensive and prestigious equipment, the Hafler amplifier and preamplifier are moderately priced, and further savings can be made by the option of assembling them from kits.

These units are advanced designs using top quality components for consistent performance and long-term reliability. For the kit builder, critical circuits are factory assembled and pre-tested, making a simple, enjoyable assembly project, even for the novice constructor.

Distortion has been virtually eliminated

from these designs, and particular attention has been paid to reduction of all forms of transient and interfacing distortions, so that input sources and loudspeakers do not impair the specified performance.

Detailed literature is available free on request. And, if you send \$1 to cover handling costs, we will send an extensive compilation of test reports by independent reviewers including both laboratory and listening tests. We will also include a kit construction manual (normally \$3) so you can judge the feasibility of assembling our kits.

Available through selected dealers.



DH-200 POWER AMPLIFIER
100 WATTS/CHANNEL

DH-101 PREAMPLIFIER

THE **david hafler** COMPANY
Dept. RE-1 □ 5910 Crescent Boulevard □ Pennsauken □ New Jersey 08109

CIRCLE 36 ON FREE INFORMATION CARD

EQUIPMENT REPORTS *continued from page 30*

the instrument is not big and cumbersome; it takes up very little room. A supply like that can be used for a lot of useful things around a shop, and would be a fine and handy thing to have on hand. Manufacturer's suggested list price is \$325. **R-E**

IET Model CM-500/ Capacitance Meter



CIRCLE 103 ON FREE INFORMATION CARD

THERE WAS A TIME WHEN NEARLY ALL capacitance measurements were made using a balanced bridge. The procedure often required interpolation of values. It was an analog process, often introducing operator error.

Times have changed. Instead of measuring capacitance indirectly by resonating a tuned circuit with the unknown capacitor, digital cir-

ORDER FORM

Electronics Paperback Book Club Quality Paperbacks at Affordable Prices

\$15 for a 15% discount

I've checked off the book I want **FREE** and have included my \$15 membership fee. I understand that this fee makes me a member of your book club for one year and that during that time I can order as many books as I want and deduct 15% from the list price.

\$25 for a 20% discount

I've checked off the free book and have enclosed my \$25 membership fee. I understand that this fee makes me a member of your book club for one year and that during that time I can order as many books as I want and deduct 20% from the list price. I further understand that I can use my \$25 membership fee as a credit toward future purchases.

CASH NOW I've checked off the books that I want to buy.

To order from this ad: Check off the books you want. Total the prices. Add in 25¢ per book for shipping. NY State residents add Sales Tax. Total it up, enclose your check and mail.

- IC 555 Projects (Expanded Edition) **\$4.50**
- Handbook Of IC Equivalents and Substitutes **\$1.95**
- First Book Of Diode Characteristics, Equivalents & Substitutes **\$2.95**
- 28 Tested Transistor Projects **\$2.96**
- 50 CMOS IC Projects **\$2.95**
- A Practical Introduction to Digital IC's **\$2.95**
- Beginners Guide To Building Electronic Projects **\$3.50**
- Essential Theory For the Electronics Hobbyist **\$3.50**
- 1st Book Of Transistor Equivalents and Substitutes **\$1.50**
- 2nd Book Of Transistor Equivalents and Substitutes **\$2.95**
- How To Build Your Own Metal & Treasure Locators **\$2.95**

- 52 Projects Using The 741 **\$2.95**
- 28 Tested Transistor Projects **\$3.50**
- Electronic Calculator Users Handbook **\$2.95**
- Handbook Of IC Audio Preamp and Power Amp Construction **\$2.95**
- 50 Circuits Using Germanium Silicon and Zener Diodes **\$1.95**
- 50 Projects using Relays SCR's and Triacs **\$2.95**
- 50 FET (Field Effect Transistor) Projects **\$3.50**
- Digital IC Equivalents and Pin Connections **\$6.95**
- Linear IC Equivalents and Pin Connections **\$6.95**
- 50 Simple LED Circuits **\$1.95**
- How To Make Walkie-Talkies **\$3.50**
- Popular Electronic Projects **\$3.50**
- Electronic Music and Creative Tape Recording **\$3.50**
- Projects In Opto Electronics **\$3.50**

ORDERING INFORMATION

How many books have you ordered

Total Price

Shipping and Handling (35¢ per book)

Subtotal

Sales Tax (NY State Residents only)

Total Enclosed

MAIL TO:

ELECTRONIC TECHNOLOGY TODAY INC.
17 Slate Lane, Central Islip, NY 11722
No Canadian Orders

Signature

Name

Address

City State Zip

cuitry can measure the fundamental property of a capacitor: its rate of charge.

The new IET *CM-500* autoranging digital capacitance meter does just that. By introducing an accurate pulse-voltage to the unknown capacitor through a known resistance, the rate of charge can be measured directly.

The *CM-500* autorange circuitry automatically selects the appropriate display values for the charge time. Range units include millifarads, microfarads, nanofarads, and picofarads. Since few of us have an intimate familiarity with millifarads and nanofarads, IET has located a conversion table above the display.

Why include millifarads and nanofarads when nobody uses them? The answer lies in the autoranging limits. Picofarads and microfarads, the common units, are six decimal places apart. With only 3½ digits in the display, autoranging would provide very limited accuracy for values that were too high to be measured in picofarads, yet too low to be measured in microfarads.

The display features four half-inch LED's. Measurements to a numerical value up to 1999 may be read before the meter autoranges to the next higher scale. The *CM-500* will measure any capacitance from 1 pF to 200,000 µF with 0.1% accuracy (±1 least-significant-digit). A thumbwheel offset-potentiometer corrects for stray lead-capacitance.

Front-panel provision is made for test leads or capacitor-lead insertion. A plug-in accessory (included) is used for rapid measuring of taped components.

The *CM-500* may be powered by its own internal batteries, or from an optional AC adaptor.

Accurate measurement of capacitors is only the beginning of the *CM-500*'s flexibility. An edge connector can be used to connect the tester with a useful capacitance-limits comparator (model *CLC-502*, optional). With this instrument, a thumbwheel selection of upper and lower limits may be used to tighten up specs on incoming capacitors. This "go/no-go" technique makes accepting and rejecting of components a snap. For quality-control purposes, the optional comparator can pay for itself quickly during bin-sorting of critical components.

Since the accessory *CLC-502* is digital, it introduces no measurement error when plugged into the *CM-500*.

Our bench test

We found the *CM-500* to provide high accuracy, rapid autoranging, and clear readout-visibility. Settling time on large value capacitors was unusually short. A 2200 µF electrolytic was read in only four seconds.

The thumbwheel capacitance-offset control is a little touchy and required some getting used to. It is capable of introducing or subtracting approximately 50 pF, and some gentle persuasion is required to tease the control right to zero.


A pushbutton must be depressed each time a capacitor is measured. Not only does that prolong battery life, but a shorting position on the switch discharges the test capacitors when they are inserted to protect the instrument from overvoltage at the input.

The pulse-generating circuitry is built around a 1-MHz astable multivibrator (crystal oscillator). The squarewave output from this basic clock circuit is then divided down into useful sub-ranges for various capacitances under test. The lowest frequency (500 Hz) is used to measure the highest capacitance (20,000-200,000 µF), while the basic 2-MHz

frequency is used to measure the lowest capacitance (1-2000 pF).

The *CM-500* is ruggedly built, designed for long-term reliability. It carries a list price of \$299 and is manufactured by IET Labs, Inc., 761 Old Country Road, Westbury, NY 11590. **R-E**

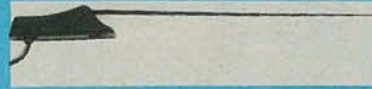Harada Electronic AM/FM Automotive Antenna



CIRCLE 104 ON FREE INFORMATION CARD


THE NAME "HARADA" PROBABLY DOESN'T SPUR instant recognition among most readers, but that company (1900 W. Artesia Blvd., Compton, CA 90220) claims to be the world's largest antenna manufacturer! Judging from their product-line catalog, they may be right.

Harada's specialty is producing original-equipment antennas and accessories for the automotive industry. AM, FM, AM/FM, and motor-driven antennas are available for roofs, gutters, fenders, mirrors . . . just about any spot on your vehicle where you would like to mount an antenna. And they are made for virtually every major automotive manufacturer in the western world.

As we flipped through the interesting Harada catalog, the unit which caught our fancy was the little *EA-50* "Electrona" antenna.

continued on page 34

Beauty Deep Down Inside

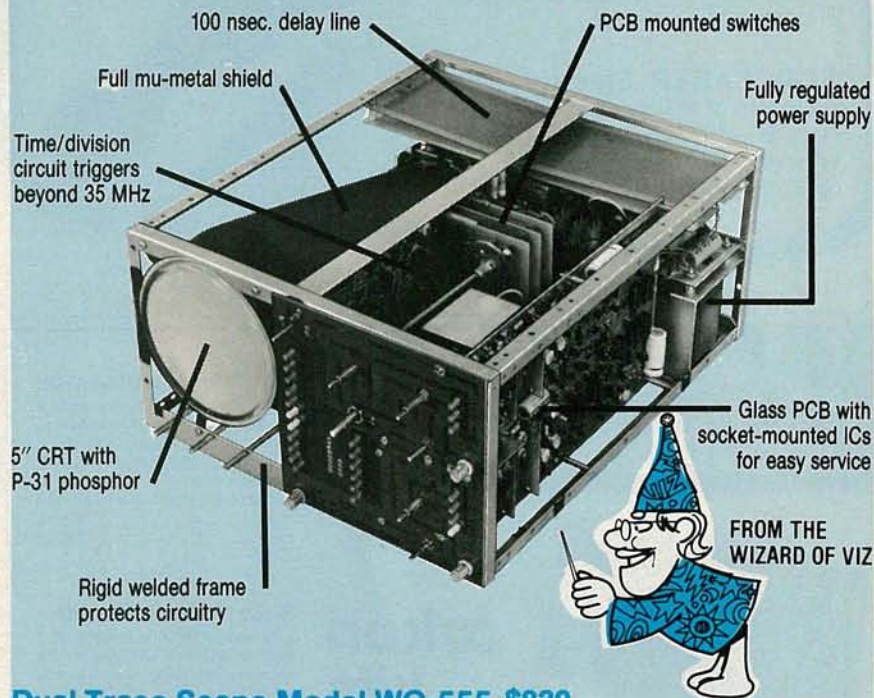

Dual Trace Scope Model WO-555 \$839.

The 15 MHz scope with more accuracy, convenience, versatility and a broader voltage capability (DC thru 600V) than others costing more money. Calibrated X-Y capability. Built-in delay line allows for viewing the full input waveform. "Undershoot and overshoot" can be seen and analyzed. **Unique simplified trig hold** and adjustment control with LED indicator show trig polarity at a glance. Two direct/X10 LoCap probes supplied.

Also available:

Single Trace Scope, WO-527A, \$599.



Beautifully functional
on the outside too

See your local VIZ distributor



VIZ Mfg. Co., 335 E. Price St., Philadelphia, PA 19144

CIRCLE 34 ON FREE INFORMATION CARD

In An Instant. YOU CAN SAFELY PLUG AWAY WITHOUT OVERLOADING OR COMING UP SHORT

You can do it thanks to SGL WABER® multiple outlet strips. There are over 100 versatile models with unsurpassed quality workmanship. Each exceeds National Electrical Code standards and is safety tested. Ideal for organizing your work area and having extra outlets *exactly* where you want them. Over 2,000 electronic distributors carry the SGL Waber line. Send for our free 24-page catalog, today!

SGL WABER Electric
A division of SGL Industries, Inc.
Dept. H—300 Harvard Avenue
Westville, New Jersey 08093
(609) 456-5400



CIRCLE 13 ON FREE INFORMATION CARD

EQUIPMENT REPORTS

continued from page 33

Studying the specifications, we discovered that the little telescoping whip contains a base-mounted preamplifier designed to increase AM and FM signal strengths. Gain is specified as 15 dB on FM, and 10 dB on AM. Fully extended, the antenna is only 16 inches long. For protection, it may be collapsed totally and laid inconspicuously into a recessed groove in its base. A 59-inch cable, terminated with a standard Motorola plug, is supplied. A single red wire also emerges from the bottom of the mounting base to attach to the vehicle's 12-volt power system.

The EA-50 is designed to be mounted as a replacement or supplementary antenna on any of a variety of locations on a vehicle. The illustrated literature which accompanies the antenna shows a number of recommended positions, including front or back fender cowls, rear trunk lid, and roof.

The antenna is supplied with a universal mounting kit, consisting of two different rubber gaskets to align with various flat or contoured surfaces. Because the gaskets are preformed, the cutouts may be used as a drilling template for the antenna mount. Additionally, a full-size printed template appears in the accompanying literature.

Since the antenna depends upon the car-body ground return of the vehicle to complete its 12-volt circuit, a good electrical connection to the metal mounting must be provided by the screws. If the antenna is mounted on a non-conductive surface, an additional wire connection must be provided to ground the unit's base.

Inasmuch as the total current consumption of the EA-50 is only 10 milliamps, it may be connected directly to the automotive battery without fear of running it down! Alternatively, voltage to the positive wire may be switched on and off if desired . . . but frankly, we don't really see a need for it.

After the antenna is installed, the element is extended, and the antenna is positioned by hinging it through several detent positions until the desired angle is attained. The antenna may be collapsed and recessed for protection from vandalism and carwashes.

As with any other antenna, the AM trimmer screw on the car radio should be adjusted for stronger response of a weak signal near the top of the AM band. FM peaking is unnecessary.


The accompanying literature is bilingual (German/English), and provides adequate mounting and operating hints. Suggestions are made for avoiding electrical interference due to grounds.

To check the EA-50's claims, we compared it with a full-size four-foot vertical antenna element. An AM/FM radio using a common antenna input was used to simulate an installation in a vehicle. Testing the antenna using AM broadcasts, and FM as well, we found that the EA-50 gave a good accounting of itself. Its short length was certainly deceiving in terms of ability to deliver strong signals on both bands.

In addition, the antenna worked quite well on signals outside of the bands it was designed for. For example, lower shortwave signals (up to perhaps 10 MHz or so) were quite receivable on the electronic antenna. Similarly, low-frequency signals in the 200-400 kHz range were quite readable using the EA-50.

Scanner buffs will be in for a disappointment, though. The EA-50 has a rather sharp passband for FM-broadcast, and rejects signals

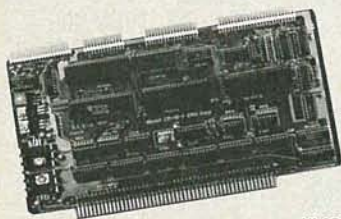Introducing . . . arkon's exclusive line!



CP/IO-1

An S-100 system card, wired and tested that will outperform the mass market systems in versatility, price and speed. It has all the CPU (8080) disc control (1771) and IO (8255) needed for a disc based CPM system. Interfaces, to all common 8" and 5 1/4" drives. (Shugart, Memorex, BASF, Siemens, Wang). Also features EIA RS232 port (110 to 9600 baud), fully vectored interrupts (TMS5501), on board digital data separator, 2K bytes EPROM, 24 fully handshaked IO lines, dual mapped IO, cassette interface on board, fully buffered . . . \$495.00

All ARKON kits are complete with PCB.
Logic Probe Kit, with case . . . \$24.95
RS232 to TTL Converter Kit . . . \$ 9.95
VD-1 Video Modulator Kit . . . \$ 8.95
ETI Sound Generator Kit . . . \$44.95

ASC II KEYBOARD KIT

60 key complete ASCII character set. Highest commercial quality key switches. Uses a KR 2376 ST encoder IC. Output compatible with TTL. Caps lock for upper case alpha characters. Repeat key. Parity and/or data invertable. Positive and negative keypressed and strobe signals. Requires +5V to +30V at 100mA. Complete kit all parts . . . \$99.95

COLOR VIDEO MODULATOR

The ultimate APPLE II color modulator. Provides proper level shifting to clean up the familiar smearing effects of simpler modulators. Available at the same price.
Assembled and tested with die cast case . . . \$49.95
Kit . . . \$24.95

S-100 MOTHER BOARD

Exclusively ARKON's, the A6S100 6 slot mother board, designed for the system builder using modern boards where few slots are required. Provision for semi-active termination.
A6S100 . . . \$24.95
S-100 edge connector . . . \$5. ea/6 for \$25.00.

SUPER S-100 XFORMER

Designed by ARKON, built by HAMMOND. A transformer that fits almost all requirements in building a computer power supply. Transformer no. 120165 uses standard line voltage and provides 3 outputs:
8V at 18A for +5V supply.
28Vct at 4.5A for ±15V supply.
22V at 4.5A for disc drives.
A unique value . . . \$49.95

Send certified cheque, money order, Charge, Master Charge . . . include expiry date, card number and signature. We process only prepaid orders. Minimum order \$10.00 Add 5% (minimum \$2.00) for shipping and handling. Ontario residents add 7% sales tax. All prices subject to change. Dealer inquiries welcome.

409 Queen Street West, Toronto, Ontario Canada,
M5V 2A5. Tel. (416) 868-1315.



CIRCLE 43 ON FREE INFORMATION CARD

outside of that range quite sharply.

We would judge the best application for the EA-50 to be where low-profile reception of AM and FM broadcast signals is desired. As with most other products, this antenna works best (if not exclusively) doing the job for which it was intended—and it does it well. Suggested retail price is \$52.90. **R-E**

Tri-Star Tiger 500 Capacitive Discharge Ignition



CIRCLE 105 FREE INFORMATION CARD

THERE ARE MANY AFTER-MARKET DEVICES sold to improve automotive performances. A prime target for improvement is the ignition system. Various schemes are available, most of them electronic.

The Tiger CDI (Capacitive Discharge Ignition) system uses an electronic-switching approach to increase engine performance. Silicon-controlled rectifiers are used to pulse the ignition coil. Tri-Star, the manufacturer, claims that the system will increase gas mileage up to 15%, reduce maintenance, and improve performance. That's an unbeatable combination if it works!

Theoretically, a capacitive discharge ignition should improve automotive engine performance several ways. It increases spark voltage, enhancing fuel combustion. At the same time, horsepower is increased. Because of the shorter spark time, spark plugs should last at least 50,000 miles. Because switching is done by the CDI system, the points hardly know they are being used. Expect considerable life from them as well. Cold starts should also be improved because of the higher spark voltage of the CDI system.

The CDI ignition is designed to work with a 12-volt ignition system, using either a generator or alternator. Triggering may be provided by breaker-type or breakerless points. Input amperage ranges from .6 to 6 amps, depending upon engine RPM. Output pulse rises to a peak in .3 to .35 μ Sec. There is .15 Joules of power available for each pulse. Minimum firing voltage is 5.5 volts. Output voltage (using the original ignition coil) will be 30,000 volts (engine is cranking and the battery voltage is reduced to 8 volts) to 45,000 volts (500 RPM engine speed). Peak spark current is .175 amps. The Tiger CDI weighs 2 pounds and measures a compact 4½ × 3 × 5 inches.

The Tiger 500 is available both factory-wired, and as an easy-to-assemble kit. The PC board is clearly labelled, parts are high quality, and the assembly manual is excellent. It even provides periodic self-checks to insure proper assembly.

To test the ease of assembly, the kit was given to a high-school student with no previ-

ous kit-building experience. It took him 1½ hours to build. When it was finished, an examination revealed that the product looked professional. Power-switching components are adequately heat-sunked by the die-cast aluminum case.

It took less than a half hour to install the little CDI unit fully on a test vehicle. Directions were reasonably clear, although somewhat sketchy in places. By looking at the accompanying diagram, however, the owner should have no problem completing the installation correctly.

Several alternate installation diagrams are included for a variety of different ignition systems. The diagrams are clear, and the parts are of good quality.

A number of precautionary measures must be taken to insure proper operation of the

Tiger CDI: Proper grounding, removal of interference-suppressor capacitors from the coil, use of standard plugs, and low-resistance ignition wires are a few of them.

Our tests

After the unit was assembled, checked for wiring errors, and installed, it was time to try it out. The test vehicle was a 1975 Toyota Corolla station wagon. Several nearby hills would make an ideal track for time trials.

In all, eight time-trials were run. For each trial, the accelerator was floored at a dead stop at the bottom of each hill. The ignition system was alternated between original Toyota and Tiger 500. The results were generally disappointing. While Tiger literature said that improvements of up to 15% might be realized,

continued on page 104

HOBBY-BLOX™

The modular, circuit building system for electronic hobbyists.

Be careful. Your hobby is about to become an obsession.

The 14 modular units in the solderless, Hobby-Blox™ system are color-coded and cross-indexed. Projects go faster, easier.

For the beginner, there are two starter packs. One for integrated circuits, one for discrete components. Each has its own 10 project booklet.

Once you get into Hobby-Blox, look out. You're going to get hooked.

For a free catalog and the name of your nearest Hobby-Blox dealer, call Toll Free 800 321-9668. In Ohio call collect (216) 354-2101.

Patents Pending.
©AP PRODUCTS INCORPORATED 1980

A.P. PRODUCTS INCORPORATED
9450 Pineneedle Drive
P.O. Box 603
Mentor, Ohio 44060
(216) 354-2101
TWX: 810-425-2250
In Europe, contact A.P. PRODUCTS GmbH
Baumlesweg 21 • D-7031 Weil 1 • W. Germany

Free Project-of-the-Month to Hobby-Blox purchasers!
CIRCLE 17 ON FREE INFORMATION CARD

**THESE ARE NOT
HOME-MADE TRAINING DEVICES.
THESE ARE PRODUCTION MODEL
MICRO-SYSTEMS.
NO OTHER HOME STUDY SCHOOL
OFFERS THEM EXCEPT NTS.**

1.



2.



3.



IN FACT, NTS ELECTRONICS PROGRAMS INCLUDE THE WIDEST ARRAY OF SOLID-STATE AND DIGITAL EQUIPMENT EVER OFFERED BY ANY HOME STUDY SCHOOL.



2-Meter FM Transceiver

Now, for the first time, you can learn all about microcomputers by working with your own production model at home. We'll explain the principles of troubleshooting and testing this remarkable instrument and, best of all, we'll show you how to program it to do what you want.

It's the perfect opportunity for you to learn BASIC high level language programming and assembly language programming.

Then, to learn how to localize microcomputer problems and solve them, you'll experiment and test with a digital multimeter and other testing gear.

But most important, you get to assemble and work with today's most sophisticated microcomputers, not home-made training devices. We believe this makes learning a lot more relevant and exciting.

In fact, production-model equipment is featured in all NTS electronics programs.

Our Color TV servicing program boasts the NTS/HEATH digital color TV (25" diagonal) you actually build and keep.

In Communications Electronics you'll build and keep an NTS/HEATH 2-meter FM transceiver, along with digital multimeter and service trainer.

Whichever NTS electronics program you choose, you can count on working with much the same kind of equipment you'll encounter in the field.

Find out more in our full color catalog on the program of your choice.

NTS also offers course in Auto Mechanics, Air Conditioning and Home Appliances. Check card for more information.



Simulated TV Reception



Digital Multimeter

1. **The NTS/HEATH H-89 Microcomputer** features floppy disk storage, "smart" video terminal, two Z80 microprocessors, 16K RAM memory, expandable to 48K. Available in NTS's Master Course in Microcomputers.
2. **The NTS/Rockwell AIM 65 Microcomputer** A single board unit featuring an on-board 20 column alphanumeric printer with 20 character display. A 6502-based unit 4K RAM, expandable. Available in NTS's Microprocessor Technology Course.
3. **The NTS/KIM-1 Microcomputer** A single board unit featuring a 6 digit LED display with an on-board 24 key hexadecimal calculator-type keyboard. A 6502 based microcomputer with 1K of RAM memory, expandable. Available in NTS's Master Course in Electronic and Industrial Technology.

NO OBLIGATION. NO SALESMAN WILL CALL.
APPROVED FOR VETERAN TRAINING.



TECHNICAL-TRADE TRAINING SINCE 1905
Resident and Home-Study Schools
4000 SO. FIGUEROA ST., LOS ANGELES, CA. 90037



NATIONAL TECHNICAL SCHOOLS

4000 South Figueroa Street, Dept. 206-011
Los Angeles, California 90037

Please rush FREE color catalog on course checked below

- | | |
|---|---|
| <input type="checkbox"/> MicroComputers/MicroProcessors | <input type="checkbox"/> Auto Mechanics |
| <input type="checkbox"/> Communications Electronics | <input type="checkbox"/> Air Conditioning |
| <input type="checkbox"/> Digital Electronics | <input type="checkbox"/> Home Appliances |
| <input type="checkbox"/> Industrial Technology | <input type="checkbox"/> Color TV Servicing |

Name _____ Age _____


Address _____

Apt. _____ City _____

State _____ Zip _____

- Check if interested in G.I. information.
 Check if interested ONLY in classroom training in Los Angeles.

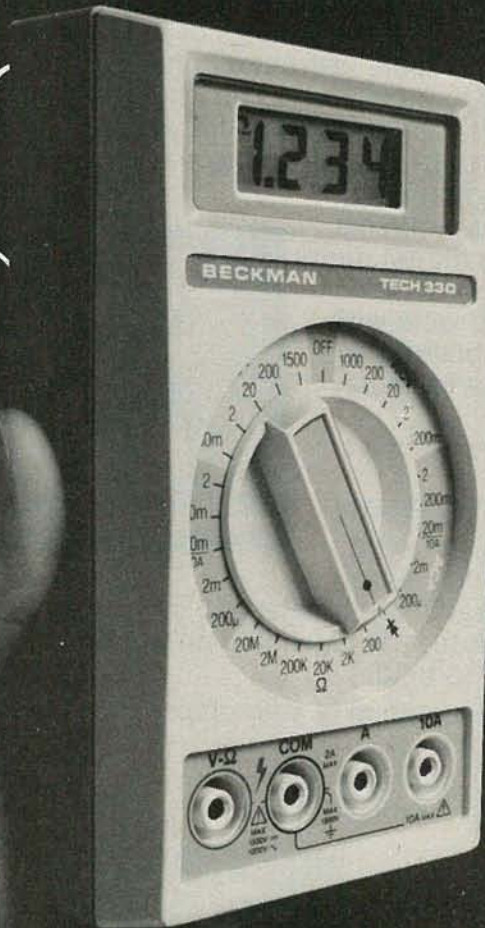Beckman brings a new dimension to hand held Digital Multimeters



True RMS capability at an affordable price

Now you can measure the exact power content of *any signal* – regardless of waveform. Beckman delivers the new TECH™ 330 multimeter with true RMS capability and many more fine performance features for just \$210.

Unlike most multimeters calibrated to read only the true power content of sine waves, the TECH 330 extends its true RMS capability to give you accurate readings of both sine and non-sine waveforms.

True RMS makes a significant difference in accuracy when measuring switching power supplies, flyback power circuits, SCR or TRIAC controlled power supplies or any other circuit generating a non-sine signal.

The TECH 330 also accurately measures the entire audio band up to 20 kHz. But that's not all you can expect from Beckman's top-of-the-line multimeter.

Measurement Comparison Chart

Waveforms (Peak = 1 Volt)	Average Responding Meter	Beckman TECH 330	Correct Reading
Sine Wave 0	0.707V	0.707V	0.707V
Full Wave Rectified Sine Wave 0	0.298V	0.707V	0.707V
Half Wave Rectified Sine Wave 0	0.382V	0.500V	0.500V
Square Wave 0	1.110V	1.000V	1.000V
Triangular Sawtooth Wave 0	0.545V	0.577V	0.577V

You also get 0.1% basic dc accuracy, instant continuity checks, 10 amp current ranges, a separate diode test function, 22 megohm dc input impedance, and an easy-to-use rotary switch.

With so much capability in hand, you'll be able to depend on the TECH 330 for a long time. That's why Beckman designed it tough enough to go the distance.

Enclosed in a rugged water-resistant case, the TECH 330 can take a 6-foot fall onto concrete and still perform up to spec. And to further ensure reliable, trouble-free operation, the TECH 330 gives you 1500 Vdc overload protection, RF shielding, 2000-hour battery life, gold switch contacts, and fewer electronic components to worry about.

Add another dimension to your world of electronics. Visit your Beckman distributor today for more information on the TECH 330 and Beckman's complete line of digital multimeters, starting at \$120.

For your nearest distributor, or a free brochure:

CALL TOLL FREE

24 HOURS A DAY, 7 DAYS A WEEK

1-(800)-821-7700 (ext. 517)

in Missouri 1-(800)-892-7655 (ext. 517)

BECKMAN

CIRCLE 65 ON FREE INFORMATION CARD

BUILD THIS

PAY-TV DECODER

Pay-TV puts cable-quality programming on the air. This is the inside story of the methods used by broadcasters to insure privacy.

D. LANDFEAR

ONE OF THE FASTEST GROWING TV MARKETS today is the subscription-TV, or pay-TV, business. Most pay-TV broadcasters use one of the standard UHF or VHF channels but transmit an encoded, or scrambled, picture. In order to watch those scrambled signals, a subscriber needs to have a decoder attached to his set. Subscription TV is much like cable TV...without the cable.


New pay-TV stations are coming on the air every month; and with over a million subscribers already watching, the prospects for still more stations are indeed good. All of those stations offer approximately the same fare: During prime time they show full-length movies and special-event features, such as night-club acts and sporting events. A special bonus for their monthly subscription fees is that the subscribers are never subjected to commercials.

Pay TV isn't based on any new technology; indeed, the technique of scrambling TV pictures is almost as old as TV itself. In the past there have been at least a dozen different pay-TV schemes that have come and gone because of cost, complexity, or market

NOTE:


The legality of the use of privately-owned devices to decode subscription TV broadcasts is currently the subject of much debate and pending litigation. The subscription companies have taken the position that decoding of broadcasts without payment is "theft of service" and the FCC has issued a notice to the effect that subscription-TV decoders are subject to FCC approval.

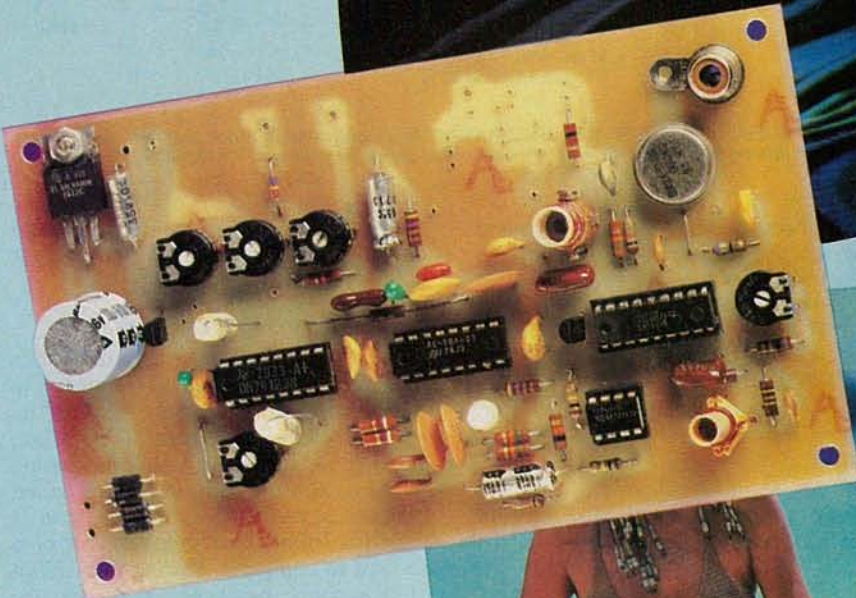This article merely explains how such decoding devices are built and used, and you should obtain independent advice as to the propriety of its use depending upon your individual circumstances.



conditions. However, current technology has played a part in the recent success of those systems: Decoders in use today are a complete receiver which merely attaches to the antenna terminals of the subscriber's set. Contrast that to earlier designs which require connections *inside* the set to the sync, video, audio, and other signals.

Presently, five different encoding schemes have been authorized by the FCC: at least three of them are in use now. All of those systems use essentially the same approach to encoding the signal. Either the audio channel is taken off the main channel and put on a subcarrier, or another audio channel is added somewhere in the composite signal, usually below the video carrier. The video is encoded by removing, suppressing, or masking the sync pulses; that disables the receiver's sync-separator circuit. A viewer who received such a scrambled signal on a normal receiver would see no coherent picture and would probably hear a "barker" or announcer telling him how much he was missing by not being a subscriber!

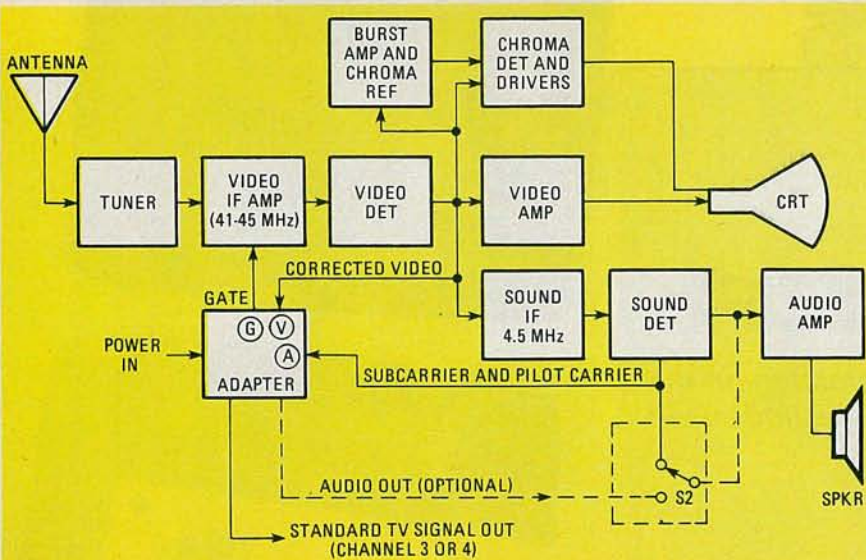

CONNECTION POINTS FOR PAY TV UNSCRAMBLER are indicated in block diagram. A thorough schematic will be necessary for you to locate these points in your own TV receiver.

CONNECTIONS TO TV SET(S)

Connecting the adapter to a TV receiver will require some amount of "digging" and TV knowhow on the part of the builder. There are two possible ways to use the adapter: The TV receiver with the adapter installed can serve as the monitor on which the program is watched; or the program can be watched on a second TV receiver tuned to the channel 3 or 4 output of the adapter's RF modulator.

To install the adapter it will be necessary to find the following connection points in the receiver:

- Power (12 volts or greater)
- Audio-detector output
- Emitter(s) of one or more video IF-gain stages
- Video-detector output

The diagram at the left shows a simplified block diagram of these connections, and each will be discussed next month.

All three of the encoding systems now in use throughout the country make use of one variation or another on that theme. The unscrambler described below works for only one of those three systems but the principles involved are applicable to all of them.

To determine whether the system used in your area is the same as the one discussed here, there are two things you can do. The simplest is to check for the presence of a 5.750-kHz pilot tone at the audio detector of your TV set. If it's there, you're all set. The other is to use your scope (preferably dual-trace) to observe the video waveform. If it matches that shown at the bottom of Fig. 1, once again, you're on the right track.

The significance of the pilot tone and unusual waveform will be made clear below.

How scrambling works

First, let's review the characteristics of a standard TV signal. In order to produce a picture, the entire face of the picture tube is scanned line-by-line, starting at the top left and continuing to the right and down, in what is called a raster scan. Each complete scan is called a frame, and takes 1/30th of a second to complete. During that 1/30th of a second, however, 525 lines are transmitted. Therefore, in one second, there are 525 x 30, or 15,750 lines transmitted. In order to produce a coherent image on the screen, it is neces-

sary to transmit synchronizing (or *sync*) pulses. Those pulses are used to insure that the scan begins at precisely the correct time. Both vertical- and horizontal-sync pulses are used for this purpose.

A vertical-sync pulse defines the beginning of each frame and field (half a frame) and a horizontal-sync pulse defines the beginning of each line. In addition to sync pulses, there is an additional signal called a blanking pulse. To understand the purpose of the blanking pulses, recall how the raster scan goes line-by-line from left to right down the screen. In order for it to get from the end of one line (or one frame) to the beginning of the next, it must sweep back or retrace its path. However, during the brief period when it is doing that, it is necessary to turn off the beam, or blank it. That is the function of the blanking pulse. The sync pulses are superimposed on the blanking pulses.

What happens is that every time the beam sweeps to the end of a line, or frame, it is extinguished or blanked by the horizontal or vertical blanking pulse, respectively, before it is reset to the beginning of the next line, or frame, by the sync pulse.

Now, suppose we alter the characteristics of the sync pulses, or even remove them entirely. What happens? You guessed it—a mess on the screen instead of a picture. The waveforms of a scrambled signal have these characteristics: non-standard sync and blanking pulses. That non-standard signal is compared to a standard signal in Fig. 1, which represents about 1½ lines of video information as viewed on an oscilloscope. The upper trace represents a normal video signal and the lower trace a scrambled one.

Note that in a standard signal, the horizontal-blanking pedestal estab-

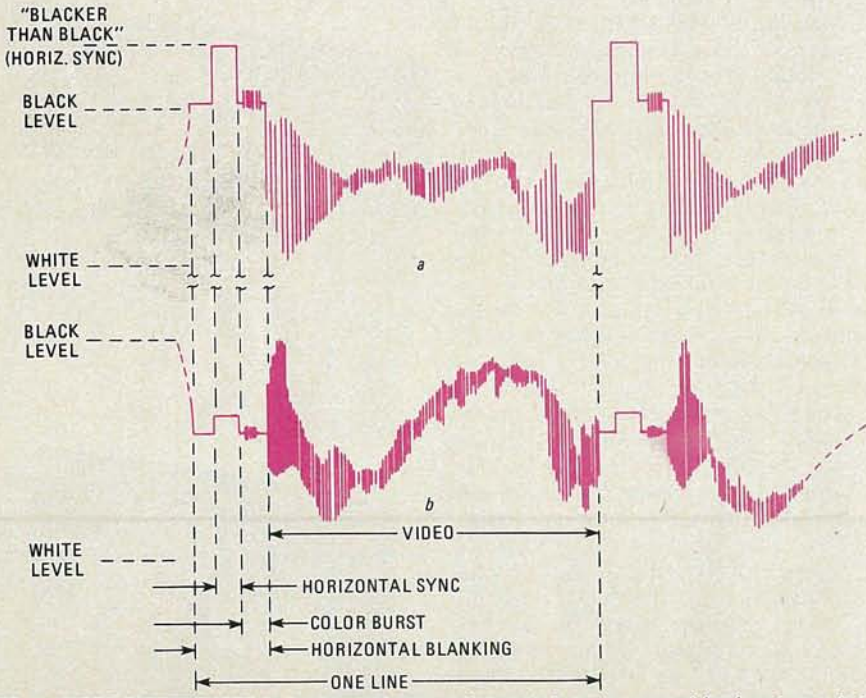


FIG. 1—NOTE DIFFERENCES in horizontal-blanking intervals between normal (top) and encoded (bottom) signals.

PARTS LIST

Resistors 1/2 watt, 5%

R1, R28—470 ohms
 R2—10000 ohms, potentiometer
 R3—22000 ohms
 R4, R5—3900 ohms
 R6, R7—100,000 ohms, potentiometer
 R8, R21—1000 ohms, potentiometer
 R9, R10, R26—15000 ohms
 R11, R27—100,000 ohms
 R12, R13, R20—10000 ohms
 R14-R16—not used
 R17—2200 ohms
 R18, R19—not used
 R22—75 ohms
 R23—100 ohms
 R24, R25—240 ohms
 R29—1000 ohms

Capacitors

C1, C15—10 μ F, electrolytic
 C2, C8—1.0 μ F electrolytic
 C3—0.033 μ F ceramic disc
 C4—0.003 μ F ceramic disc
 C5—470 pF, mica
 C6, C7—0.022 μ F ceramic disc
 C9—0.0047 μ F polystyrene or mylar
 C10—0.0047 μ F polystyrene or mylar
 C11—100 pF ceramic disc
 C12-C14, C27—0.1 μ F ceramic disc
 C16, C17—not used
 C18—22 pF ceramic disc
 C19, C20—0.001 μ F ceramic disc
 C21—56 pF mica
 C22—82 pF mica
 C23, C26, C28-C30—0.01 μ F ceramic disc
 C24—1000 μ F electrolytic
 C25—6.8 μ F tantalum electrolytic

Semiconductors

D1—1N914
 D2—not used
 D3-D6—1N4001
 LED1—jumbo red LED
 IC1—LM1800 PLL FM stereo demodulator
 IC2—74123 dual retriggerable monostable multivibrator
 IC3—LM741 op amp
 IC4—LM1889 TV video modulator
 IC5—7812 12-volt positive regulator
 IC6—78L05 five-volt positive regulator
 Q1—not used
 Q2—MPSA05
 L1—0.068 μ H slug-tuned coil (2 1/2 turns #18 wire on 1/2-inch form) (J.W. Miller 48A77MPC or equivalent)
 L2—7-12 μ H slug-tuned coil (J.W. Miller 23A105RPC or equivalent)
 S1—SPST switch
 S2—SPST or DPST switch
 T1—14-18-volt, one-amp transformer (optional)

Miscellaneous: PC board, phono jack, vestigial sideband filter FL-1 (Plessey SW300 or equivalent—optional), solder, IC sockets, etc.

NOTE: The following are available from Micro-Mart, 552 Summit Avenue, Westfield, NJ 07090 (Tel. 201-654-6008) or Sterling Technology, POB 5929, Incline Village, NV 89450 (Tel. 800-538-9787 except CA. CA residents call 800-662-9238): Etched & drilled, solder-plated PC board with instruction manual, \$20.00; PC board only, \$15.00; kit of all parts with manual, \$69.00. Visa and Mastercard accepted, please add tax where applicable. All prices postpaid within contiguous 48 states.

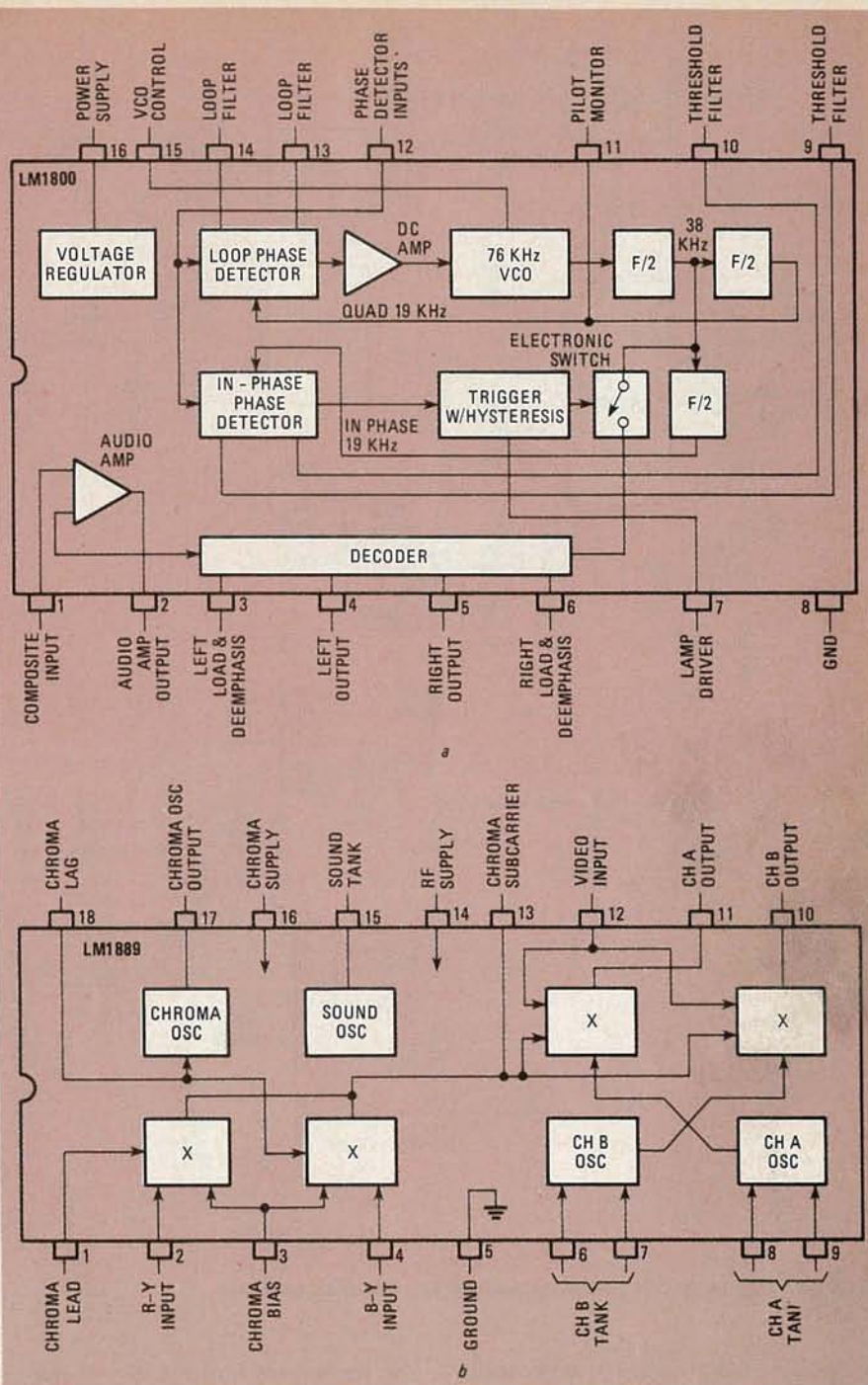


FIG. 2—ALTHOUGH DESIGNED for other purposes, the LM1800 and LM1889 can be used in decoding applications.

lishes the black level for the line. The sync tip is in the "blacker-than-black" region. In the non-standard signal, however, there is no clearly recognizable blanking pulse. Thus, there's no black reference; the video signal itself is seen in the "blacker than black" region by the set, making synchronization impossible. It should also be noted that during the horizontal-blanking interval, a color-synchronization signal is also transmitted. That signal, called the color burst, is used to synchronize the color-detection circuits in the TV set. With a normal signal, the set's circuitry expects to see the color-burst signal during a specified interval. If it doesn't recog-

nize the blanking pulse, then it can't recognize the color-burst signal either; thus, the set's color circuitry is either unsynchronized or doesn't work at all. So just by changing one part of the signal—the blanking pulse—it is possible to destroy not only the picture sync but also the color sync.

All that has been done to the scrambled video signal has been to reduce the horizontal blanking-signal level below the video-signal level. To reconstitute the picture, all that is required is to restore everything to its original levels. That can be accomplished very simply by momentarily increasing the gain of the TV receiver during the horizontal-blanking interval. The trick

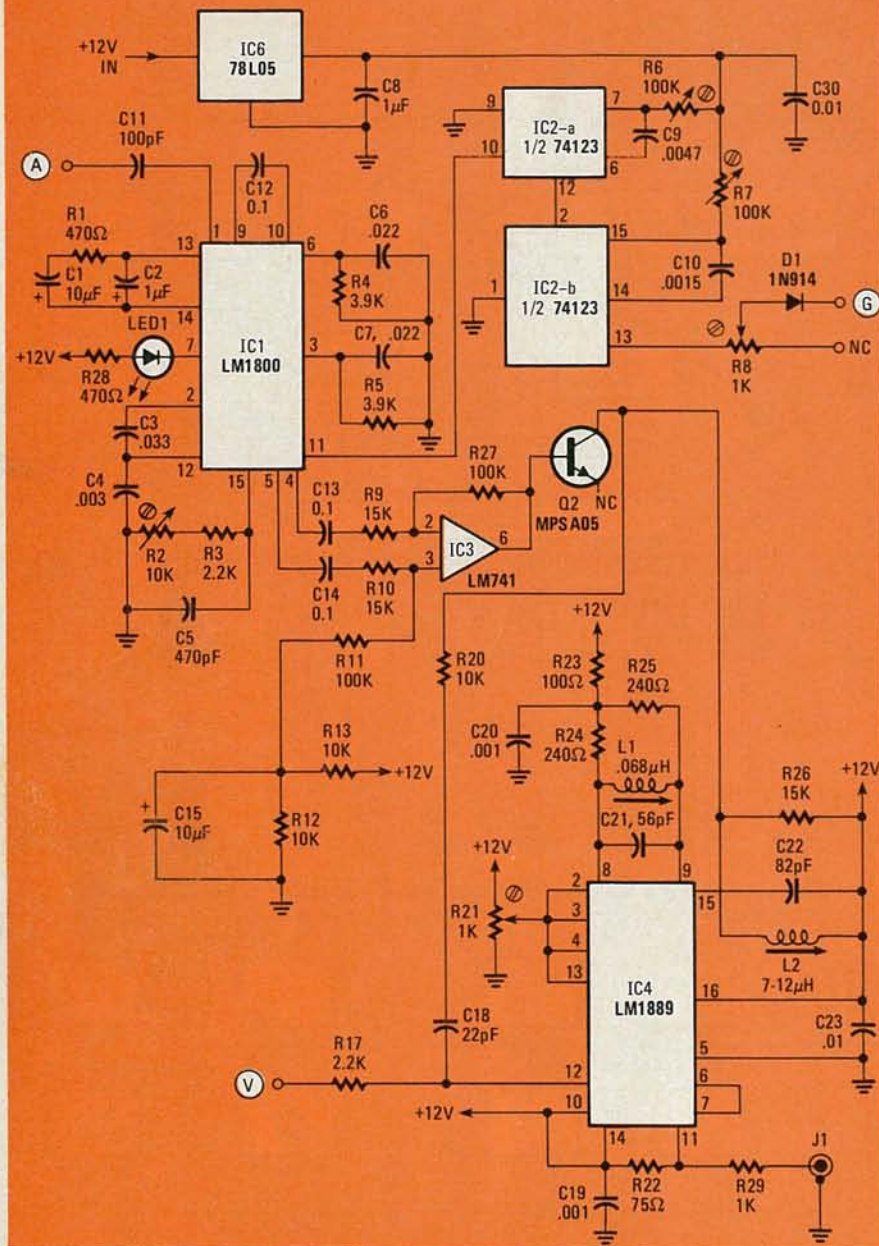


FIG. 3—A SIMPLE PAY-TV DECODER uses just four IC's and a transistor.

is to know exactly *when* to increase the gain. Since the video signal is such that the blanking pulse is almost unrecognizable, perhaps we should look elsewhere.

An unscrambler

Let's digress for a bit and talk about the sound. As you will see, there is a very important correlation between the sound and the restoration of the sync and blanking-pulses. Program audio is transmitted via a 31.5-kHz sub-carrier. The information on that sub-carrier is a double-sideband, suppressed-carrier signal. In order to demodulate it, a reference signal, or pilot carrier, is required. The frequency of that pilot carrier is one-half the modulating-carrier frequency ($31.5/2 = 15.75$ kHz). That number—15.75—is the horizontal-line frequency we talked about earlier, and represents

the number of horizontal-sync pulses generated in one second. Obviously there is some correlation here.

The pilot-carrier signal can be used as a timing reference to recreate the sync and blanking pulses. The pilot carrier generates a 15.75-kHz square-wave signal in a decoder IC such as an LM 1800. That signal in turn is used to trigger two cascaded one-shot multivibrators that produce a gate pulse of exactly the same width and phase as the horizontal-blanking pulse. That gate pulse is used to increase the IF gain of the TV receiver during the horizontal-blanking interval, restoring the sync- and blanking-signal strengths to normal.

The method is the same as the one used to transmit the difference information that produces an FM-stereo signal. And, since the same process is involved, the same hardware can be

used to retrieve the signal. The only difference between the stereo system and this system (other than the choice of frequencies) is in the way the signals are retrieved on the output. In a stereo system, the main-channel signal is added to the sub-carrier signal to produce two separate channels. In the unscrambling application, the main-channel signal is subtracted, and only the subcarrier signal is used.

Block diagrams of both the LM1800 PLL stereo decoder and LM1889 TV video modulator IC's are shown in Fig. 2 to help you understand the workings of the unscrambler.

The circuit

Fig. 3 shows a schematic diagram of a decoder circuit. Assume that the circuit is connected to a TV receiver tuned to a scrambled broadcast. The outputs from the TV's audio and video detectors are connected to points "A" and "V" respectively.

The signal from the TV audio detector is applied to pin 1 of IC1, a PLL FM-stereo demodulator, through C11, a 100-pf coupling capacitor. That capacitor removes most of the main-channel information while allowing the high-frequency subcarrier and pilot carrier to pass through. The pilot carrier is used to phase-lock a 15.75-kHz oscillator that's part of IC1. The free-running frequency of the oscillator is determined by R2, R3, and C5. Phase-lock is indicated by LED1, which lights when lock occurs.


The audio outputs appear at pins 4 and 5 of IC1; they would normally be the left- and right-channel outputs if a stereo signal were being decoded. However, since the intent is to recover only the subcarrier audio, those signals are applied differentially to a 741 op-amp, IC3. The main-channel component is in phase at both the inverting and non-inverting inputs and is cancelled out by IC3. Since the subcarrier signal is 180° out of phase with itself at those two pins, it is not cancelled and appears at the output of IC3.

Next month we will finish discussing how the decoder works and will show you how to construct such a device. We will also provide step-by-step instructions for connecting it to your own TV set. **R-E**



"Now tell me how smart you are!"

ELECTRONICS IN YOUR NEXT CAR

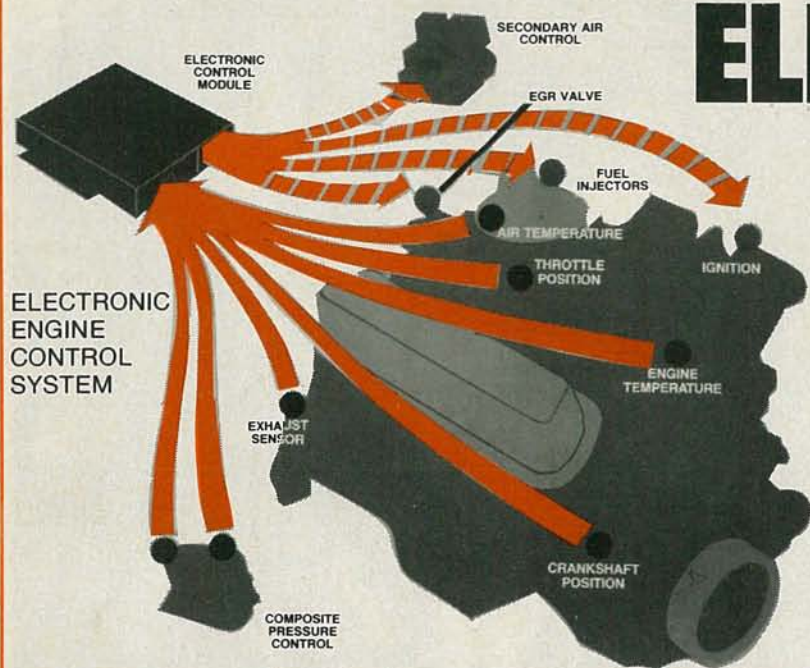

Microprocessor-based technology is making your car's engine a more efficient machine. It's bringing about other improvements, too.

MARTIN BRADLEY WEINSTEIN

FIG. 1—FORD'S MICROPROCESSOR CONTROL UNIT controls carbon monoxide, hydrocarbon, and nitrogen-oxide engine emissions. An oxygen sensor in the engine's exhaust manifold monitors the content of the exhaust and signals the electronic control unit to adjust the air/fuel mixture in the carburetor to maintain the precise mixture for proper operation of the catalyst.

Looking Under the Hood

LAST MONTH, IN PART ONE OF THIS FOUR-part series, we looked at electronics and how it was being applied in the passenger compartment in the new breed of automobiles from Detroit. We looked at digital dashboards and trip computers.

This month, we continue with a look at how electronics is being applied under the hood—engine controls.

Ford claims the "fastest and most versatile interactive electronic control system in the automobile industry... probably two years ahead of its closest competition in the use of electronic control systems."

The New Chrysler Corporation offers what "company engineers believe...is the world's only known continuous-flow method of electronic fuel injection."

Cadillac, the creme de la creme of GM, claims to provide 1981 model buyers "with one of the most advanced engine control, fuel-metering, and emissions-monitoring systems in the automotive industry."

Disregarding for the moment the industry's penchant for claims of superiority, we find some fascinating new approaches to electronic engine control, continued development of some recent trends, and a surprising degree of ingenuity and sophistication.

Here's a closer look at what's changing under the hood, in and around the carburetor, through the ignition system,

and inside the cylinders. You don't have to know much about engines to follow this—and, even if you are an automotive expert, there is a lot to be learned from these new technologies.

The Ford EEC and MCU

Like so many other improvements in the engine compartment, Ford's Microprocessor Control Unit (MCU)—shown in Fig. 1—and Electronic Engine Con-


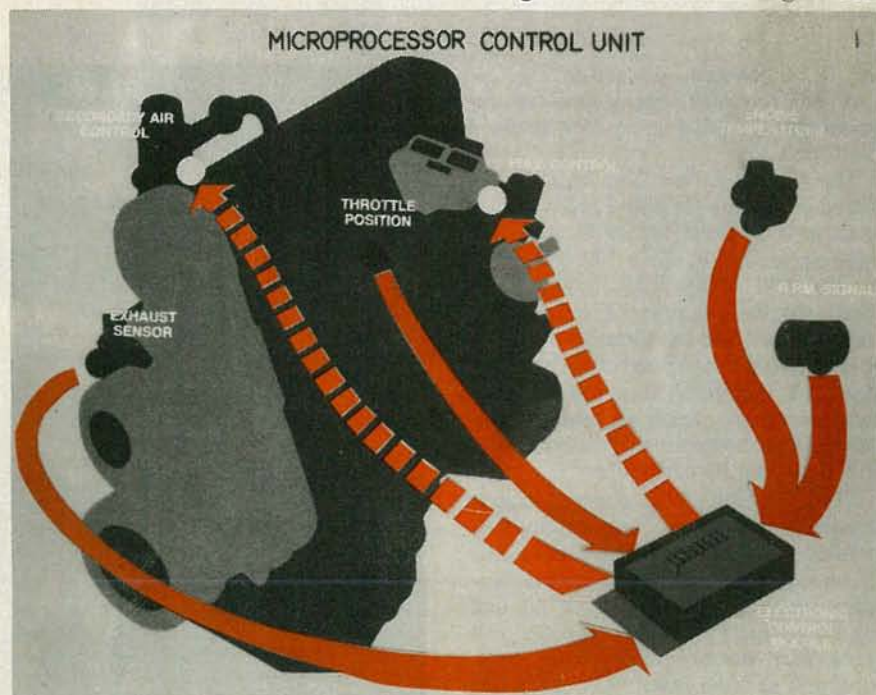


FIG. 2—FORD'S ELECTRONIC ENGINE-CONTROL system senses internal and external engine parameters of the engine, then adjusts the air/fuel mixture, spark timing, and exhaust-gas recirculation for optimum engine performance. At 55 MPH, the system can read seven engine parameters and adjust six engine functions in less than one engine revolution.

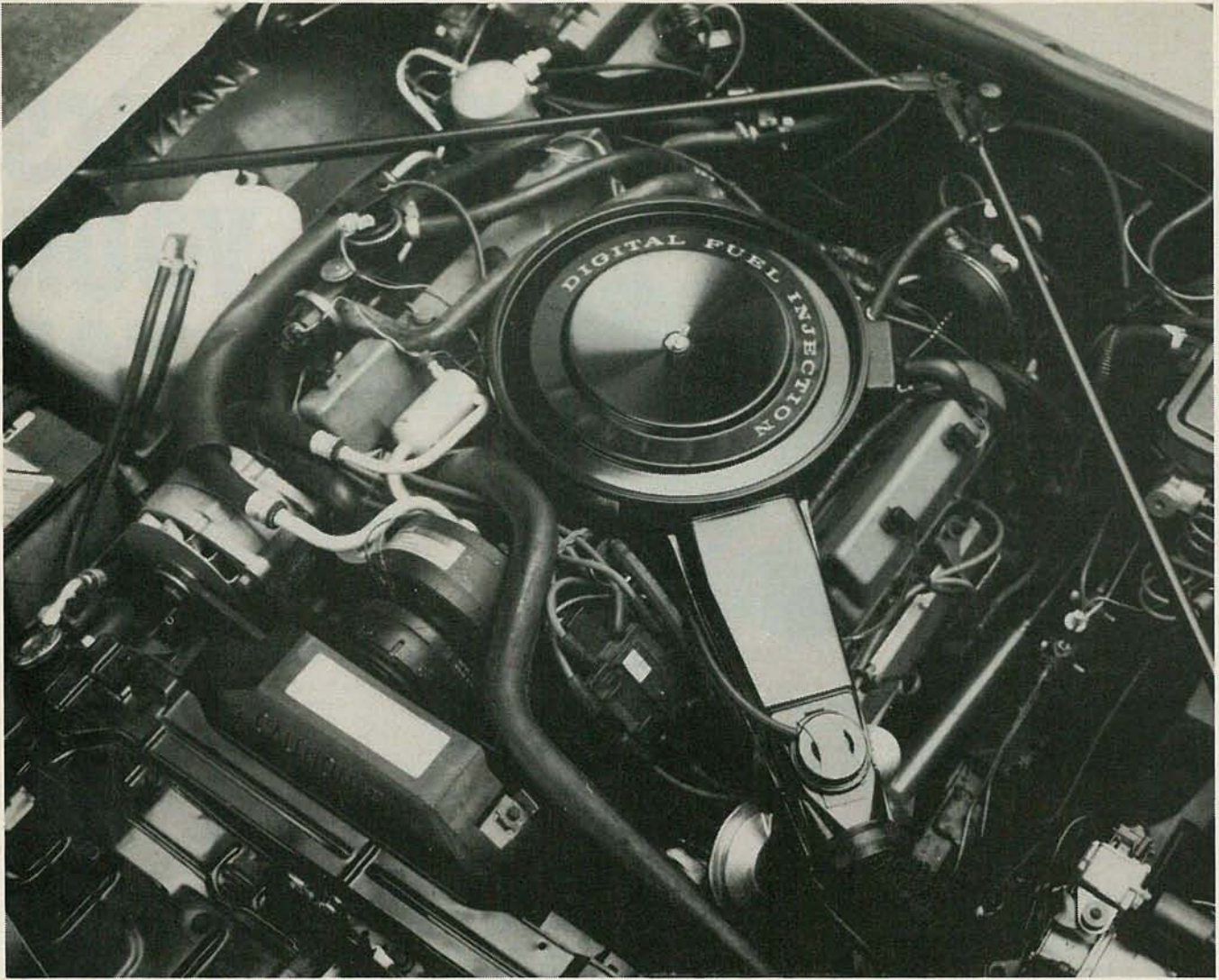

SHOULD ANYTHING EVER MALFUNCTION in this Cadillac engine, an Electronic Control Module will take over and do its best to keep the car running until service can be obtained.

trol (EEC) system—shown in Fig. 2—evolved from stiff federal emission requirements, and even stiffer ones in California.

The MCU evolved from a unit introduced on some 25,000 Ford vehicles sold in California in 1978, and will have appeared on some 597,000 Fords by the end of the 1981 model year. Inputs to the microprocessor include engine speed and temperature, throttle position, and the oxygen content of the gases in the exhaust manifold. The microprocessor analyzes those conditions and controls the fuel-air mixture (lean) in the carburetor.

EEC broadens the scope of engine sensing and control. That system, first available in its third generation as EEC-III on top-of-the-line Ford 5.8-liter engines in 1980, monitors both air and engine temperature, both throttle and crankshaft position, composite pressure, and exhaust gases. It controls fuel injectors, exhaust-gas recirculation (EGR), ignition timing, and air intake.

EEC-IV, which is the next generation system, offers even more im-

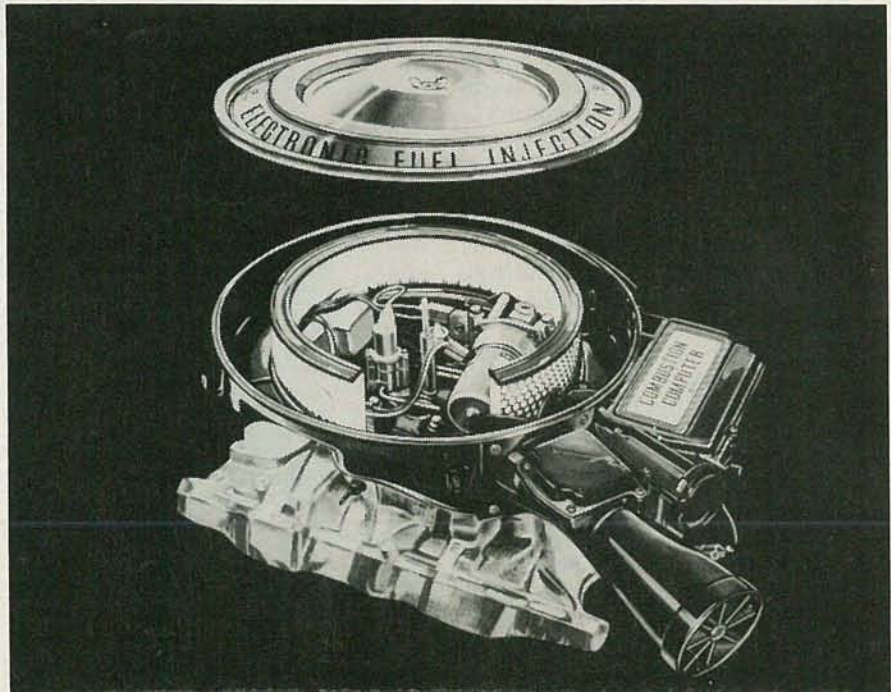


FIG. 3—CHRYSLER'S ELECTRONIC FUEL-INJECTION system replaces the carburetor with a complex pod of electronics, sensors and electromechanical devices.

provements, according to Ford VP John Betti. "It will be several times faster than our present system, have 20% more memory efficiency, and it will accomplish that with two-thirds fewer LSI chips...meeting more stringent emissions standards for oxides of nitrogen...plus Federal tamper-resistance and altitude-compensation standards."

Chrysler's EFI

Remember when Frank Sinatra drove his new 1981 Imperial off the line last summer? That was the first car with Chrysler's "continuous-flow" Electronic Fuel Injection (EFI) system, a rather remarkable accumulation of technology.

EFI controls the amount of fuel pumped from the tank, the mix, and the spark advance; that is based on air and fuel temperature and flow, engine speed, coolant temperature, throttle position, exhaust-gas oxygen content, and more. There's no choke, no separate idlemetering system, no separate wide-open-throttle metering system, no diaphragm-type fuel pump, and no special starting procedure. See Fig. 3.

There are three major parts to the EFI system. In the fuel tank, in addition to the usual plumbing, there's an electric turbine pump and several check valves.

In the air-cleaner assembly, there's an air-flow metering sensor, EGR vacuum sensing, and both metering and ignition-control electronics modules.

Third is the throttle body assembly, including the fuel-control pump and its power electronics, fuel-flow sensing, pressure-regulating valves, spraybars, and an automatic idle speed motor. See Fig. 4.

Here, Chrysler Engine Electrical Engineering Chief Engineer E. W. Meyer, Jr., explains how the system works:

Basically, the computer senses the flow of air into the engine, the flow of fuel and oxygen content in the exhaust gas. It compares those signals to an ideal calibration. When any of the signals is different from the calibration, the computer signals the control-pump motor to deliver more or less fuel, depending on whether the air/fuel mixture is too rich or too lean.

The pump in the gas tank sends fuel to the control pump. The control pump takes a small portion of it (see Fig. 5) and delivers the fuel at 21 pounds-per-square-inch at idle through the fuel-flow sensor and the fuel-delivery regulator valve, into the delivery spraybar, and then through the nozzles of the spraybar and into the engine.

Since the openings are fixed, pressure has to vary to deliver more fuel at higher speeds, up to 60 psi. The spraybar is designed to produce an even flow of fuel at low

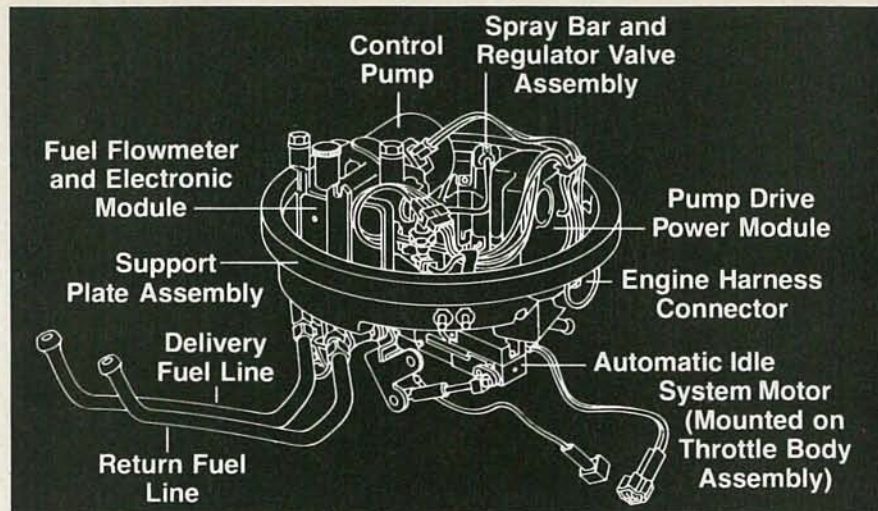


FIG. 4—THE AIR-CLEANER AND THROTTLE-BODY assembly in Chrysler's Electronic Fuel-Injection system contains the fuel-control pump and power electronics, fuel-flow sensing, pressure-regulating valves, spray bars, and automatic idle speed motor.

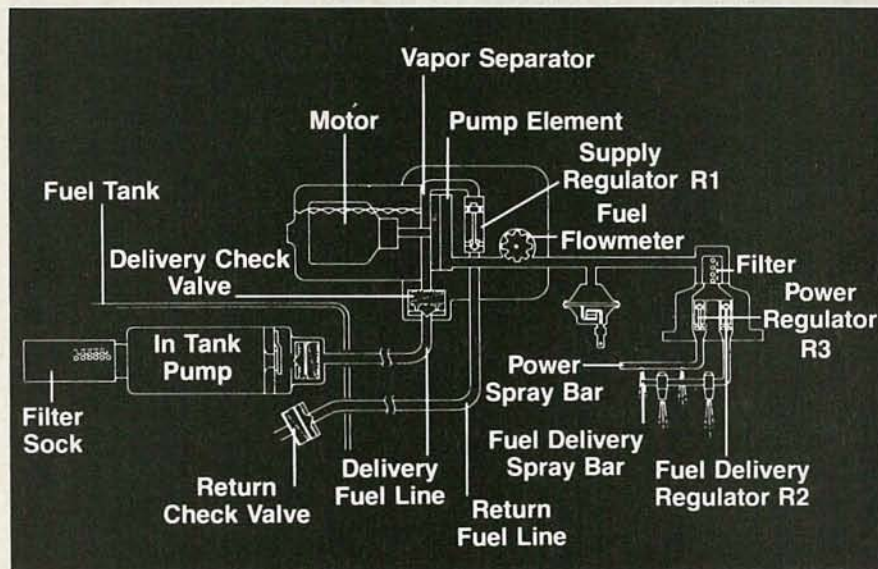


FIG. 5—FUEL FLOW in Chrysler's Electronic Fuel-Injection system is measured, monitored, metered, and manipulated by electronics.

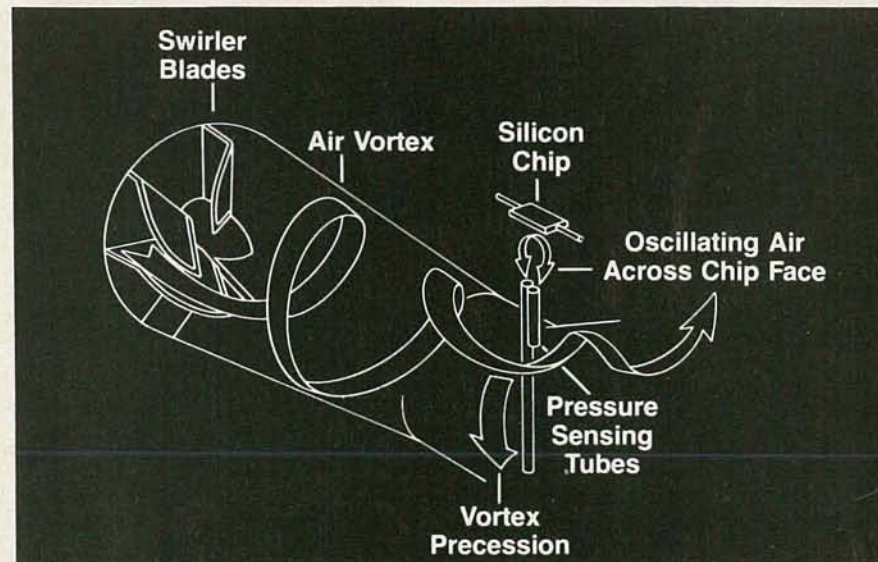


FIG. 6—THE AIR-FLOW SENSOR in Chrysler's Electronic Fuel-Injection system contains blades that swirl the air as it enters a vortex. Centrifugal effects makes the air pressure lower at the center of the vortex, higher at the outside. As the swirling air expands, the low-pressure center begins to rotate around the wall. A silicon pressure-sensor pulses faster as the air flow increases, and slower as the air flow decreases, providing air-flow data to the combustion computer.

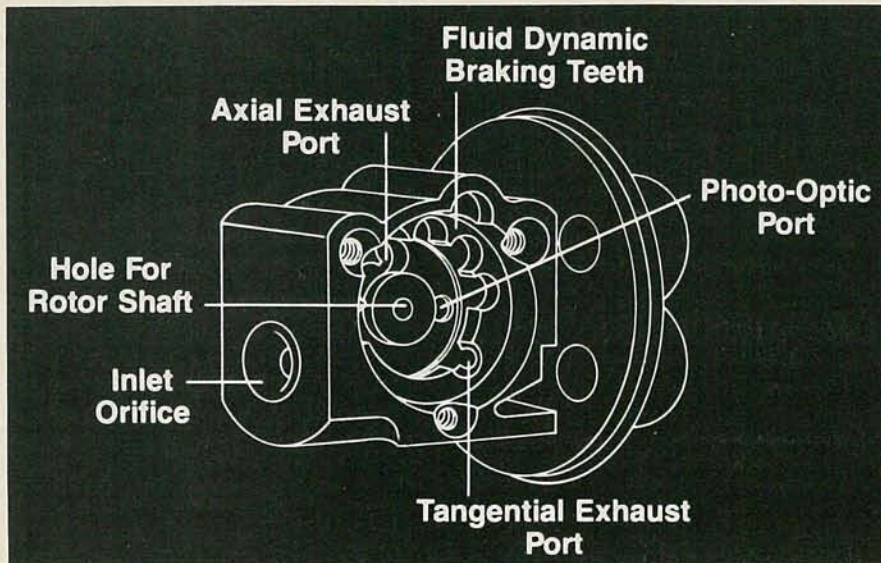


FIG. 7—CHRYSLER'S FUEL SENSOR is essentially a paddlewheel flowmeter with an optoelectronic interrupter providing a pulse rate proportional to fuel-flow rate.

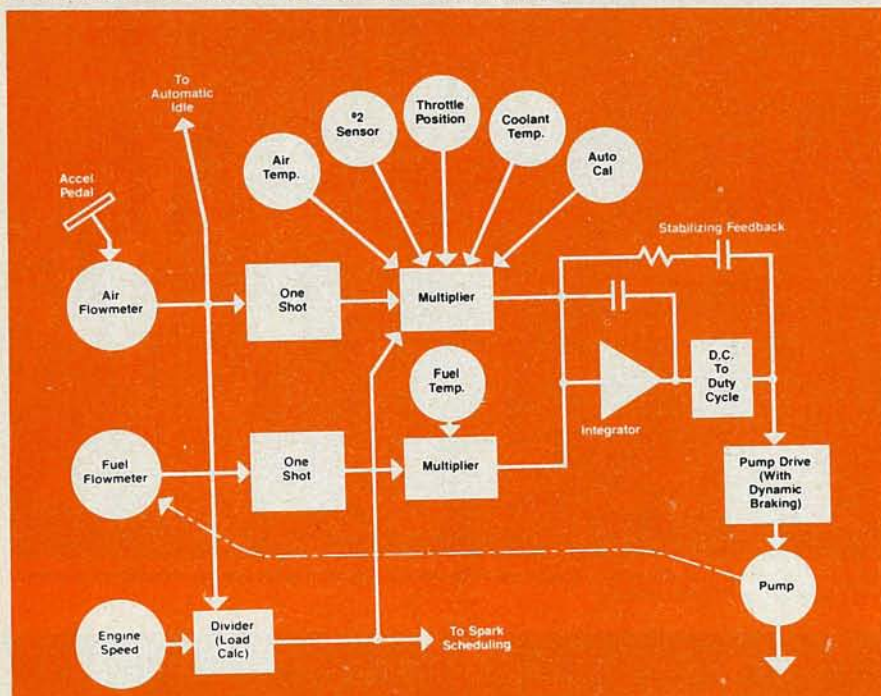


FIG. 8—SIGNAL PROCESSING in Chrysler's EFI system. Block diagram gives you some idea of the complexity of the system. The air and fuel one-shots are of opposite polarity, resulting in a continuously variable net charge on the integrator and extremely fine control of the duty cycle of the drive pulse to the pump-control transistors.

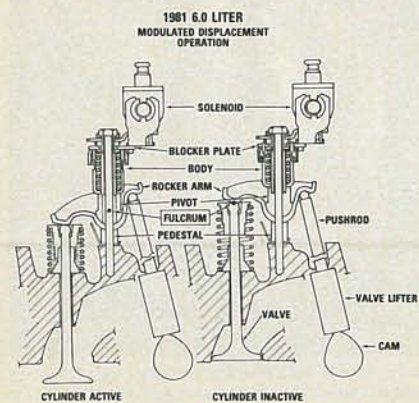


FIG. 9—CADILLAC'S MODULATED DISPLACEMENT system activates 4, 6 or 8 cylinders, as required.

EFI maintains the quality of the air/fuel mixture by arranging the throttle blades and bore in geometrical relationships that make the inducted air shear, entrain, and distribute the fuel evenly to each cylinder.

Chrysler's EFI is on the 1981 Imperial 318 CID V-8 engine. If you're fascinated, stop by a dealer for a look under the hood.

Cadillac's DFI and MD engines

Modulated Displacement (MD) and Digital Fuel Injection (DFI) are the tricks Cadillac's new 6.0-liter engine is up to. It's an eight-cylinder engine—no, six—no, four—hey, hold on there!

MD is an electromechanical system that calls up 4, 6, or all 8 cylinders, depending on driving requirements, based on commands from a controlling microprocessor to four engine-valve selector units. Those are capable of simultaneously deactivating both the intake and exhaust valves of the cylinder. (See Fig. 9.) And modulated displacement is just one factor in that remarkable engine.

Digital Fuel Injection (DFI) uses electronically pulsed fuel injectors under the control of the Electronic Control Module (ECM), central intelligence for all systems under the hood.

The ECM monitors manifold absolute pressure, ambient barometric pressure, engine-coolant temperature, intake-manifold air mixture temperature, engine speed, and throttle position. It computes ignition timing and air/fuel mixture requirements and controls them; and it also relays sensor data both to the cockpit (dashboard) systems (like MPG Sentinel and Cruise Control) and to a service-diagnostics connector.

Idle speed is programmed into the ECM memory and is maintained regardless of whether or not the car is in gear, the air conditioner is on, or any other change in engine loading is introduced. That is said to reduce stalling, improve fuel economy, and eliminate idle adjustments.


The ECM also actively participates in a number of continuous diagnostic-checking routines, which result in one of the industry's most intelligent "idiot lights" ever, one marked simply CHECK ENGINE. The ECM monitors the engine control system, sensors, and actuators for proper operation. Any malfunction, no matter how temporary, is memorized. The CHECK ENGINE light is turned on. Nominal values are substituted for critical sensors until repairs can be made. And when you eventually get the car to the repairman, he can tell what's wrong by instructing the ECM to display the fault code on the digital dashboard display that is normally used as part of the climate-control system.

continued on page 81

speeds. At higher speeds, a second spraybar, the power spraybar, opens to deliver the full amount of fuel at the correct pressure. Fuel that is not needed for a given speed automatically returns to the tank through the return check valve and return fuel line.

The air and fuel sensors report the volume of flow. The air and fuel sensors are shown in Figs. 6 and 7. Three additional sensors change the volume readings to mass readings. Basically, the signals from the two flowmeters trigger one-shot pulses of opposite polarities. Those are fed into an integrator, which controls the pump motor. The block diagram of the signal processor is shown in Fig. 8.

COMPUTER/TV

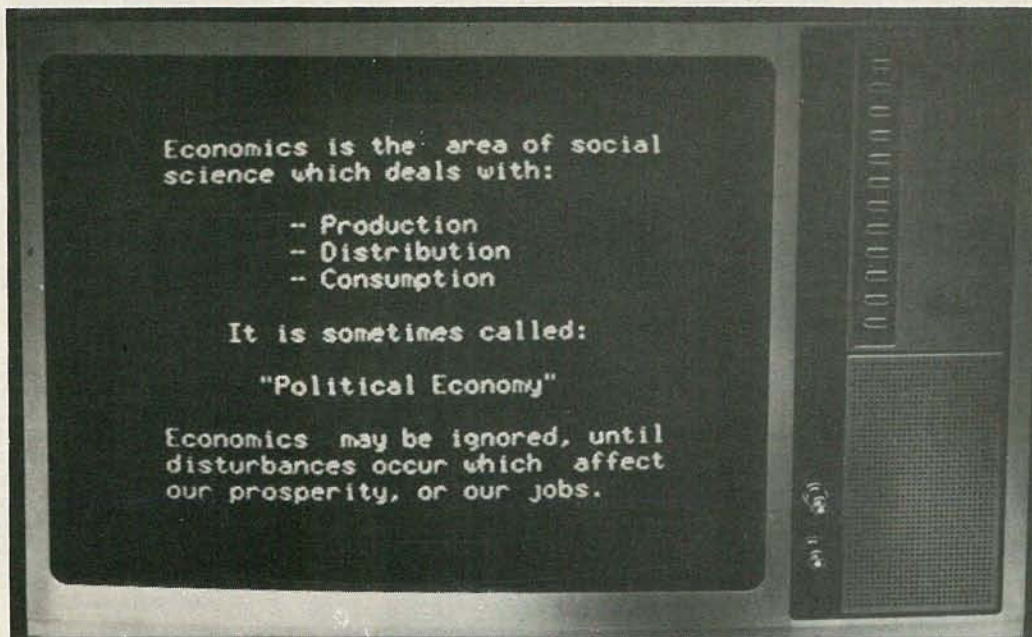

INTERFACE

A SHORT TIME AGO I BUILT A SMALL MICROCOMPUTER. As it neared completion, I realized that, since it had a composite video output, I would need a video monitor to use it. Because of my low budget, I decided to convert a 12-inch black-and-white TV set for this purpose. As is well known, you cannot connect an AC/DC TV set to a transformer-based computer without running the risk of electrical shock or of blowing up one or the other...or all of those. Therefore, I decided to build a circuit that would couple the computer to the TV set using optoisolators to separate the two electrically.

The circuit I designed is simple in concept, inexpensive, and not very critical with respect to parts-replacement or wiring. It can be built using wire-wrap or point-to-point wiring techniques on perforated construction board.

The one sensitive area, however, is the speed of the components used. Because the video rate of a 64-character line, using 5×7 dot-matrix characters with one space between characters (the output of the video board I am using) is about 8 MHz, high-speed components must be used.

Ordinary analog optoisolators won't even begin to do the job—they're much too slow. Instead, I used a *digital* device, the HP-5082-4360, that can run

Any black-and-white TV set can safely serve as a monitor for your computer when you build this inexpensive optically-isolated interface.

DAVID E. CARTIER

at speeds up to 20 MHz. Similarly, the NE529 comparators used in the circuit are high-speed devices.

Theory of operation

To understand how the analog TV signal is turned into a digital one for the optoisolators, refer to Fig. 1. It shows an idealized video waveform of the kind generated by the computer's video-board circuitry. You can see that only three voltage-levels are really involved. The sync level is at or near ground potential—close to zero volts. Black (the background) is at about 0.5 volt and white (the color of the characters) is around one volt. By using

comparators to check the level of the video signal against reference voltages for black, white, and sync, it is possible to separate those three pieces of intelligence and then pass them through the optoisolator circuitry as logic-“highs” and logic-“lows”.

The complete circuit is shown in Fig. 2. The composite video signal from the computer is input at J1 and supplied to the inputs (pin 3) of two NE529 high-speed comparators.

To recover the sync signal, IC1 is referenced by resistor R4 close to—but slightly above—ground potential (about 0.1 volt). That is done because a TTL or CMOS logic “0” actually may be slightly higher than zero volt. Since the sync pulse is the low-level part of the composite video signal, IC1 produces an output pulse for each sync pulse and ignores the video—the video level never gets that low.

On the other hand, IC2 has its reference voltage set higher by R3, to accommodate the video portion of the signal. That resistor is variable so as to make it easy to define the threshold level at which black turns to white.

Two outputs are available from the NE529's, inverted and non-inverted. I used the inverted output to complement the inverted output of the optoisolators. (The two inversions restore the signal to its original polarity.)


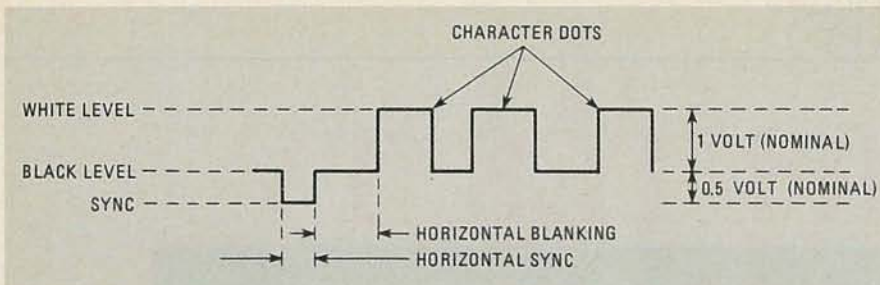


FIG. 1—COMPOSITE VIDEO SIGNAL from computer's video board has three main components: sync, black, and white.

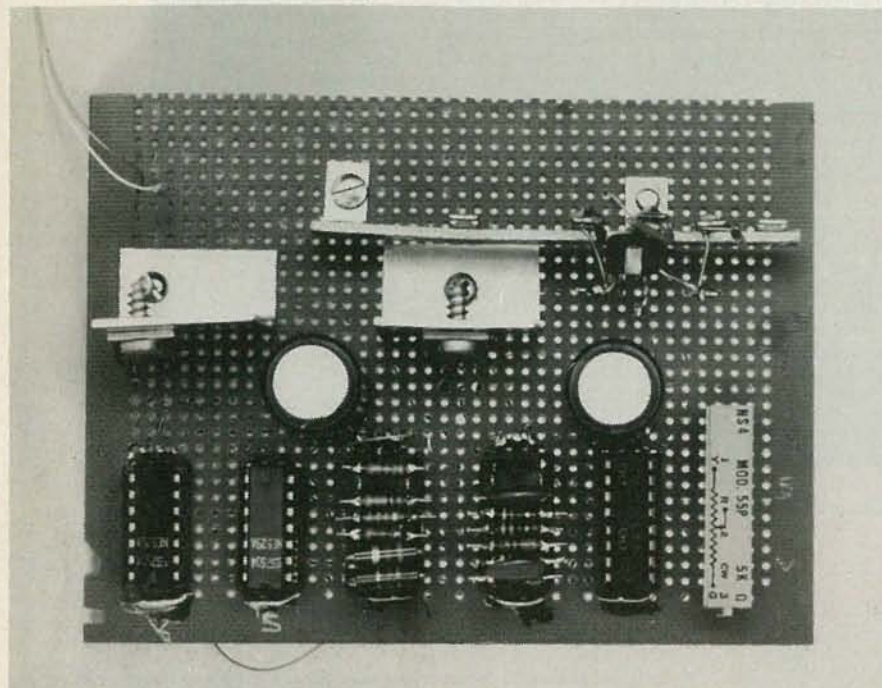

COMPONENT LAYOUT is not critical. Tie-strip at upper-right holds bridge rectifier. Use of DIP headers simplifies mounting and connection of resistors and small capacitors.

PARTS LIST

Resistors ¼ watt, 5%

- R1, R2—4700 ohms
- R3—5000 ohms trimmer potentiometer
- R4—100 ohms
- R5, R6—560 ohms
- R7—3600 ohms
- R8, R10—2200 ohms
- R9—10000 ohms

Capacitors

- C1, C2—1000 μ F, 15 volts, electrolytic
- C3-C5—.1 μ F ceramic disc

Semiconductors

- BR1—full-wave bridge rectifier, 50 PIV, 1 amp
- IC1, IC2—NE529 high-speed comparator (Signetics)
- IC3, IC4—HP-5082-4360 or 6N137 optoisolator (Hewlett-Packard)
- IC5, IC6—7805 five-volt positive voltage regulator
- T1—12.6-volt, 100 mA, center-tapped transformer
- J1—female BNC connector
- S1—SPDT switch

Miscellaneous: perforated construction board, IC sockets, 75-ohm coaxial cable, heat sinks, etc.

NOTE: If unavailable from your usual supplier, the optoisolators may be ordered from: Surplus Electronics, 9600 Baltimore Boulevard, College Park, MD 20740 for \$4.95 each, postpaid. Visa and Mastercard accepted. MD residents add 5% tax.

With the sync and video components of the signal separated and translated to logic states, the individual signals are fed to the optoisolators, IC3 and IC4. Those IC's can sink 13 mA with just 5 mA of input current, and that is well within the drive capabilities of the NE529 comparators.

The video recombining network, *continued on page 80*

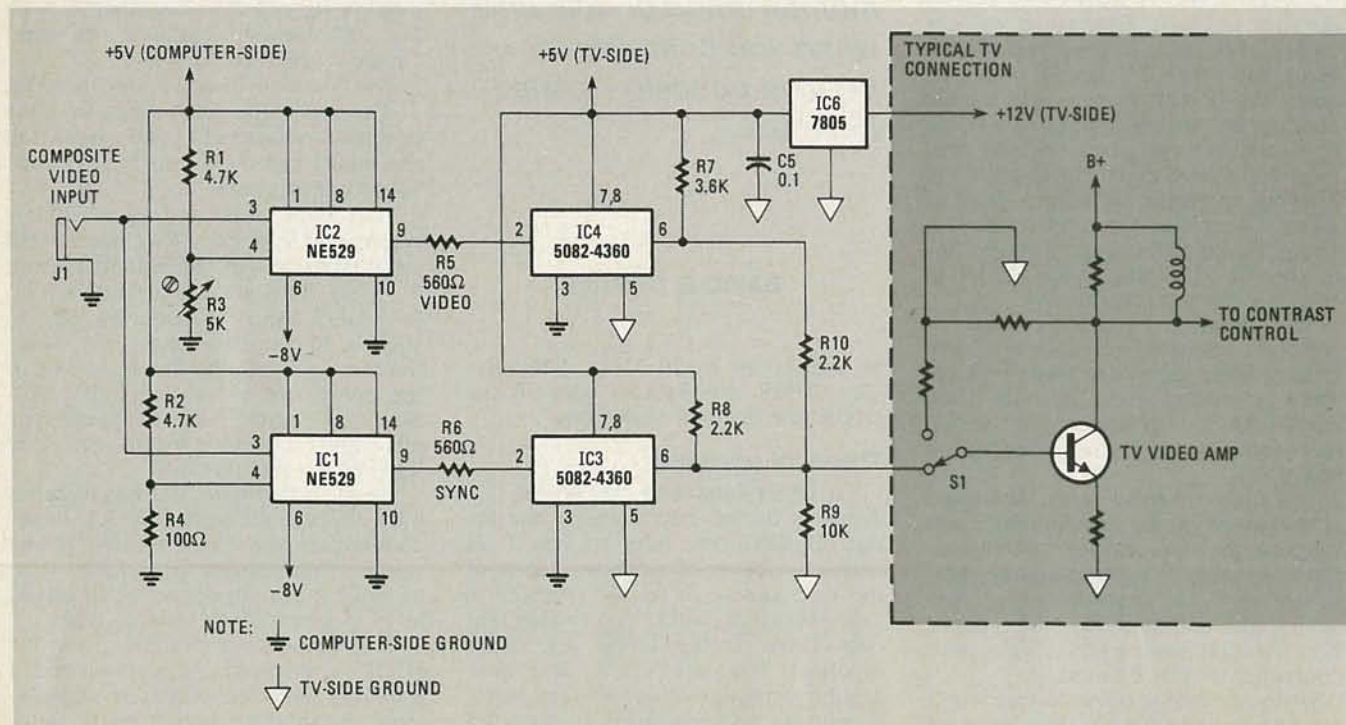


FIG. 2—TWO SEPARATE GROUND SYSTEMS are used by the interface. Make absolutely sure that each ground is made to the proper system!

YOU SHOULD HAVE YOUR OWN VERSION OF Unicorn-1 in action by now, and have probably been using this time to practice controlling the robot.

In this section, we'll not only describe some simple electronic circuits that will give the robot a more impressive appearance but will provide you, as well, with one of the options promised earlier—a rotatable end-effector.

The next installments of this series will provide circuits that can be used either for radio control (R/C) and/or for computer control—the computer being either part of the robot or external to it and transmitting commands via a radio link.

Before we get involved, though, we'd like to correct an error that crept into Part 2 of this series (September 1980) and that was brought to our attention by several readers: The red and green wires between switch S1 and the barrier strip were transposed in Fig. 18. The red wire should go to ground at the bottom-right of the switch, and the green one to +12-volts at the top right.

It's good to see so many readers taking such an interest in the project!

Electronic embellishments

Flashing lights always attract attention and—you can admit it—that's what you'd like your version of Unicorn-1 to do. We'll consider two different LED-indicator circuits: one to show that the arms are in motion, and in what direction they're moving; the other (just) to attract attention by announcing that Unicorn-1 is "alive."

The first circuit, which shows that the shoulder-motors have been activated, is presented in Fig. 42. You'll remember


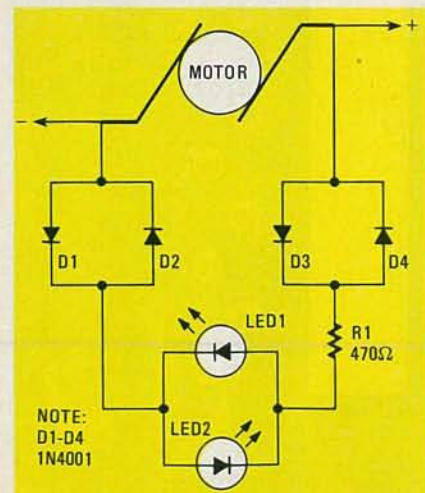


FIG. 42—MOTOR-DIRECTION INDICATOR uses twelve volts. Diodes and resistor reduce voltage and current to safe levels for LED's.

UNICORN-1 ROBOT

Part 6—Add some pizzaz to your robot with two different sets of flashing lights. For the more serious-minded, there's also a twist-of-the-wrist end effector.

JAMES A. GUPTON, JR.

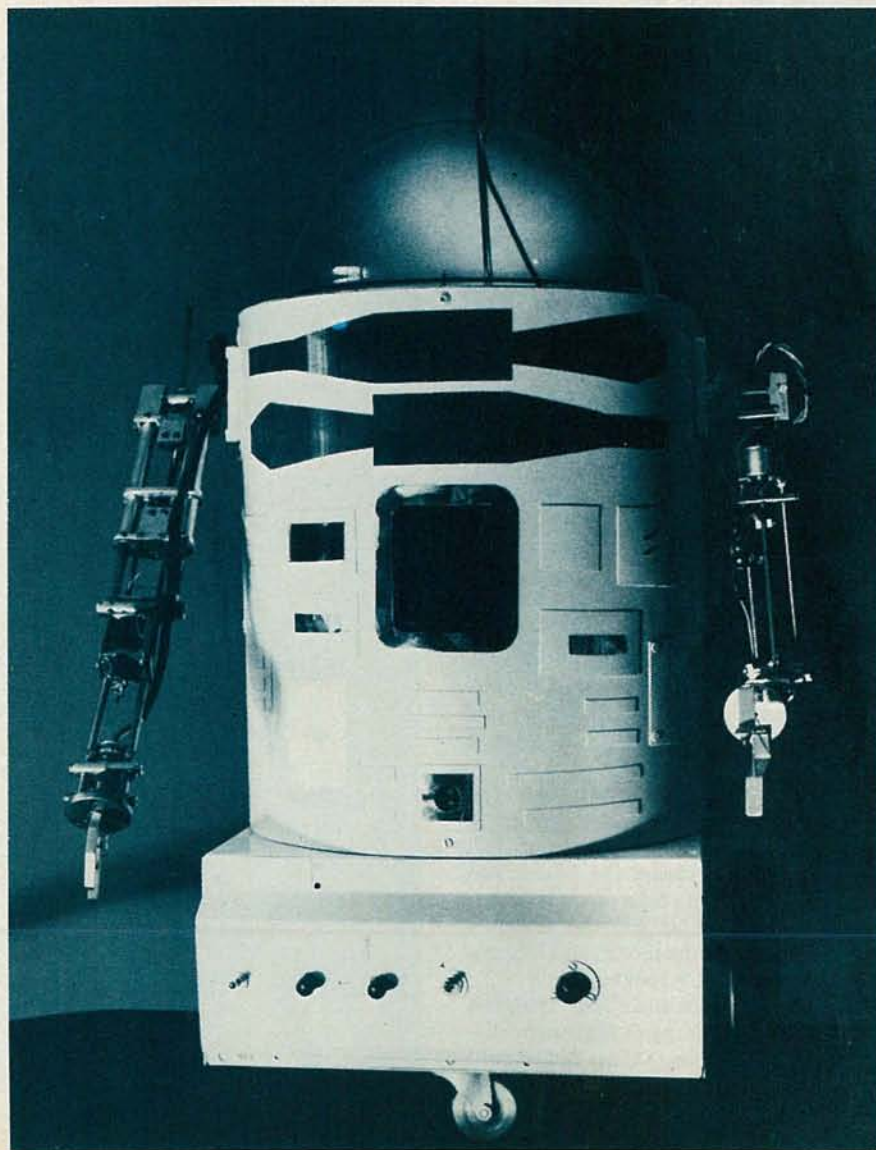

PARTS LIST—MOTOR-DIRECTION INDICATOR

R1—470 ohms, 1/4 watt
 D1-D4—1N4001
 LED1, LED2—jumbo LED's (different colors)

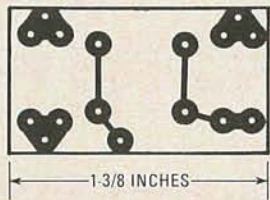


FIG 43—WHEN YOU MAKE THIS BOARD, be sure that pads *do not touch* rectangular border.

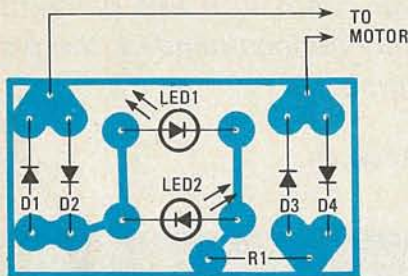


FIG. 44—PC BOARD for motor-direction indicator was designed for rectangular LED's. Circular ones will need their leads bent a bit.

that the direction of motor rotation is changed by reversing the polarity of the current used to power the motor. That circuit detects which way the current is flowing and indicates it via LED's.

Looking at the schematic for the circuit, it can be seen that—if we assume the right-hand terminal to be positive and the other one negative—a stream of electrons will flow through diode D2, LED1, and through D3, causing LED1 to light. (Remember, though, that the current flow is from the positive pole to the negative.) Also bear in mind, as you consider the schematic, that, in a LED—or in any other diode, for that matter—current flows from the cathode to the anode.

Current-limiting resistor R1 is used to prevent burning out the LED's. A value of 470 ohms will be about right to provide the LED with the 20 mA it needs, based on a 12-volt system.

If a command is given to reverse the current flow—where what was previously positive becomes negative—current will then flow through diodes D4, LED2, and D1. Use different colored LED's for LED1 and LED2 so you can tell at a glance which way the motor, and its associated mechanism, is moving.

A foil pattern for the circuit is shown in Fig. 43, and the parts-placement diagram in Fig. 44. Two of those can be built on one board to take care of both arms (see Fig. 45). The LED's used on the board shown in the foil pattern were rect-

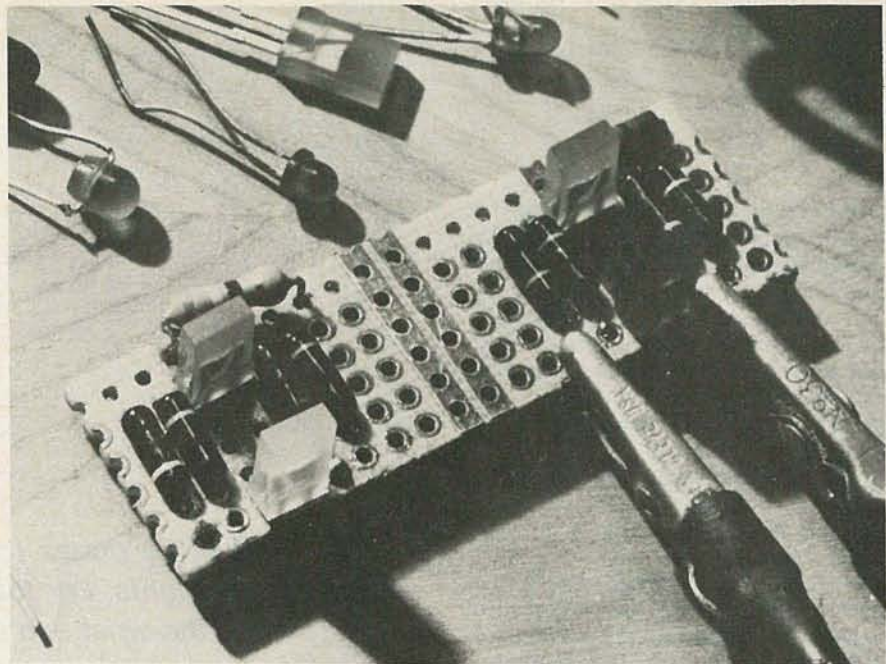


FIG. 45—ONE SMALL PIECE of board holds two complete motor-direction indicators. Current-limiting resistor is visible at top-left of board, above LED.

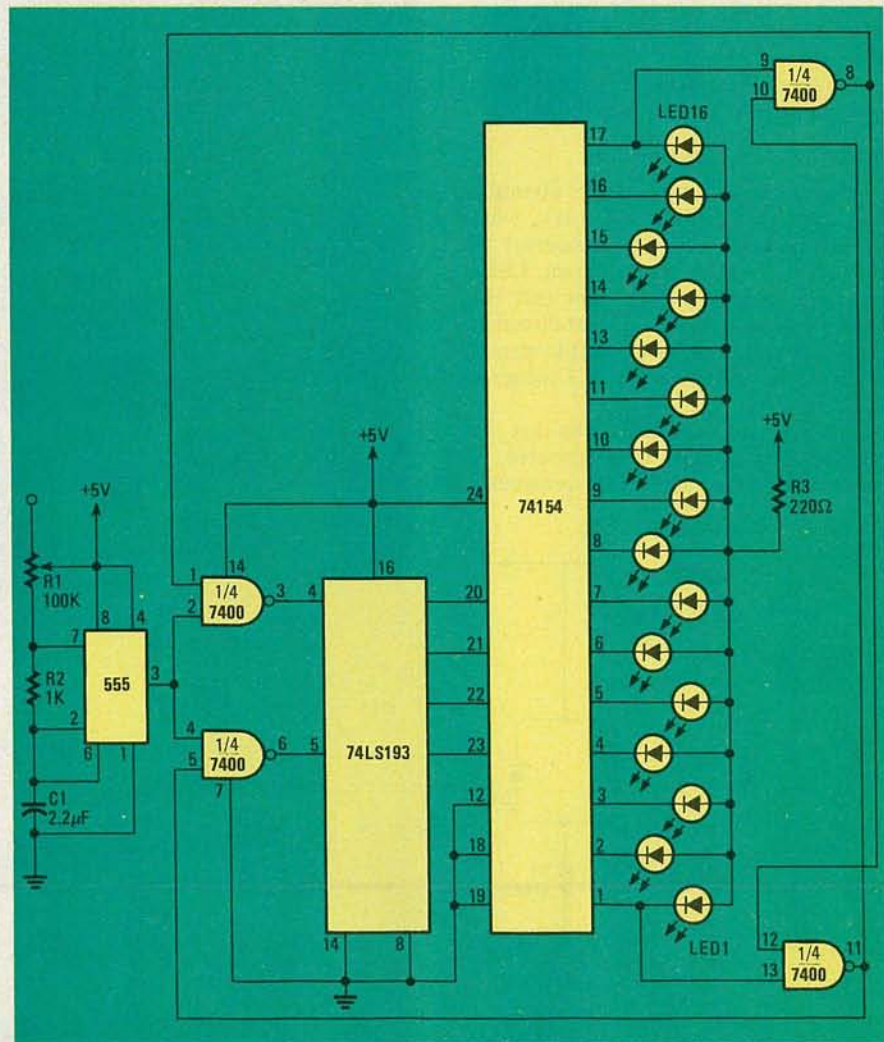


FIG. 46—SEQUENTIAL-FLASHER CIRCUIT uses 74LS193 up/down counter to drive 4-to-16-line decoder.

PARTS LIST—LED FLASHER

All resistors 1/4 watt, 5%

R1—100,000 ohms, trimmer potentiometer

R2—1000 ohms

R3—220 ohms

Capacitors

C1—2.2 μ F, 16 WVDC, electrolytic

Semiconductors

IC1—555 timer

IC2—7400 quad NAND gate

IC3—74LS193 up/down counter

IC4—74154 4-to-16 line decoder

LED1-LED16—jumbo red LED

Miscellaneous: 7805 voltage regulator with heat sink

angular, which explains the wide spacing of the pads. Round LED's would probably be better, since it is easier to drill round holes in the skin for displays than it is to drill rectangular ones.

One of the best attention getters is an array of flashing lights. One such LED circuit appears in Radio Shack's *ARCHER Engineer's Notebook*, and is the one described here. A display that creates a more random pattern was described in *Radio-Electronics'* Hobby Corner department in the December 1980 issue.

The sequential-flasher circuit in the original Unicorn-1 uses four IC's and five external components to operate 16 LED's. Its schematic is shown in Fig. 46. Resistors R1 and R2, working together with capacitor C1, determine the rate at which the 555 timer IC will cause the LED's to light, and R3 is the current-limiting resistor for the LED's.

The LED's are arranged in five columns of three each (see Fig. 47) with the sixteenth LED at the bottom of the middle column. In operation, they will light starting from the bottom-right, going up the column, then jump to the bottom of the next column, etc. When the last LED has lit, the process will reverse itself, working from left to right and finishing up at LED1.

Although a foil pattern and parts placement diagram (Figs. 48 and 49) are provided, the circuit, and the motor-direction indicator, are both easy enough to build on perforated construction board using wire-wrap techniques. If you have never done any wire-wrapping before, this would be a good place to start because of the simplicity of the circuits. (Articles on wire-wrapping techniques and materials appeared in the August 1979 and March 1980 issues of *Radio-Electronics*.)

You'll need nine jumper wires on the LED-sequencer board. Those can be made from wire-wrap wire, stripped at both ends and tack-soldered to the wiring- or foil-side of the board.

A few words about power supplies for those circuits: TTL IC's are very particular about their working voltage—it should be five volts, $\pm 5\%$ (4.75–5.25 volts). While five volts can be derived

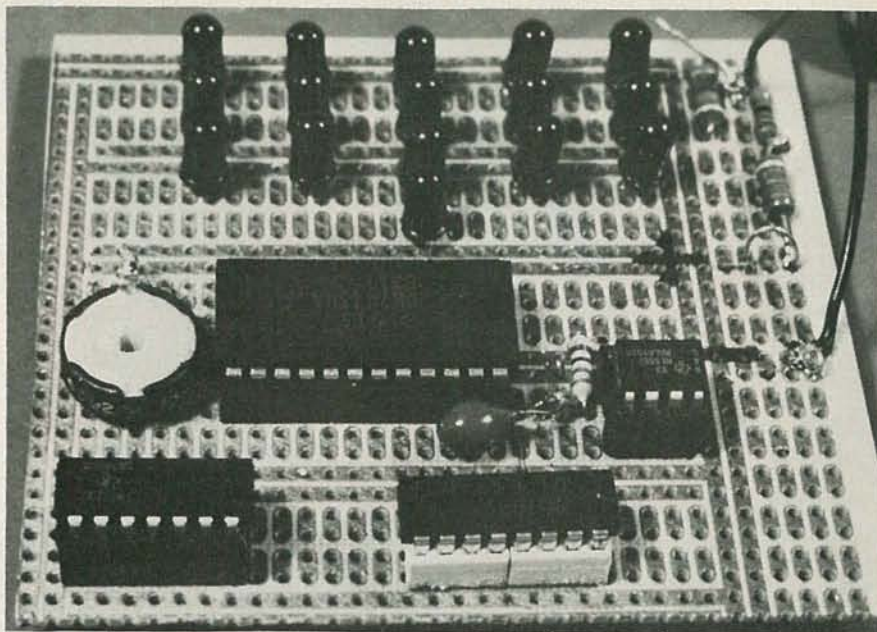


FIG. 47—TRIMMER POTENTIOMETER at left of 74154 IC varies rate at which LED's flash. Mount board so LED's are visible through opening(s) in skin of robot.

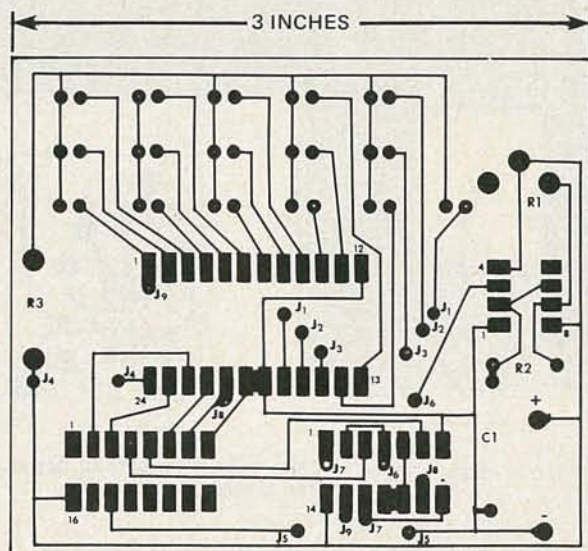


FIG. 48—PC BOARD for sequential-flasher circuit shown in prototype-version above.

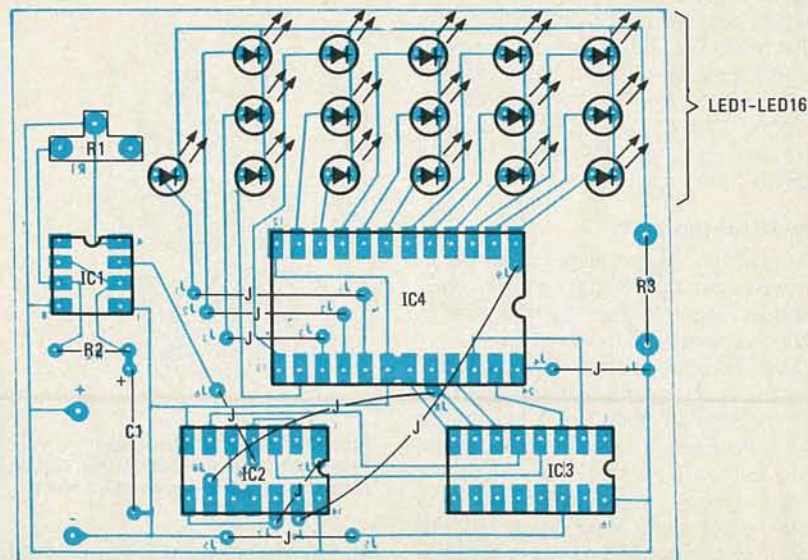


FIG. 49—NINE JUMPER WIRES are required on sequential-flasher board. "Odd" LED at left can be omitted without upsetting anything if symmetrical layout is desired.

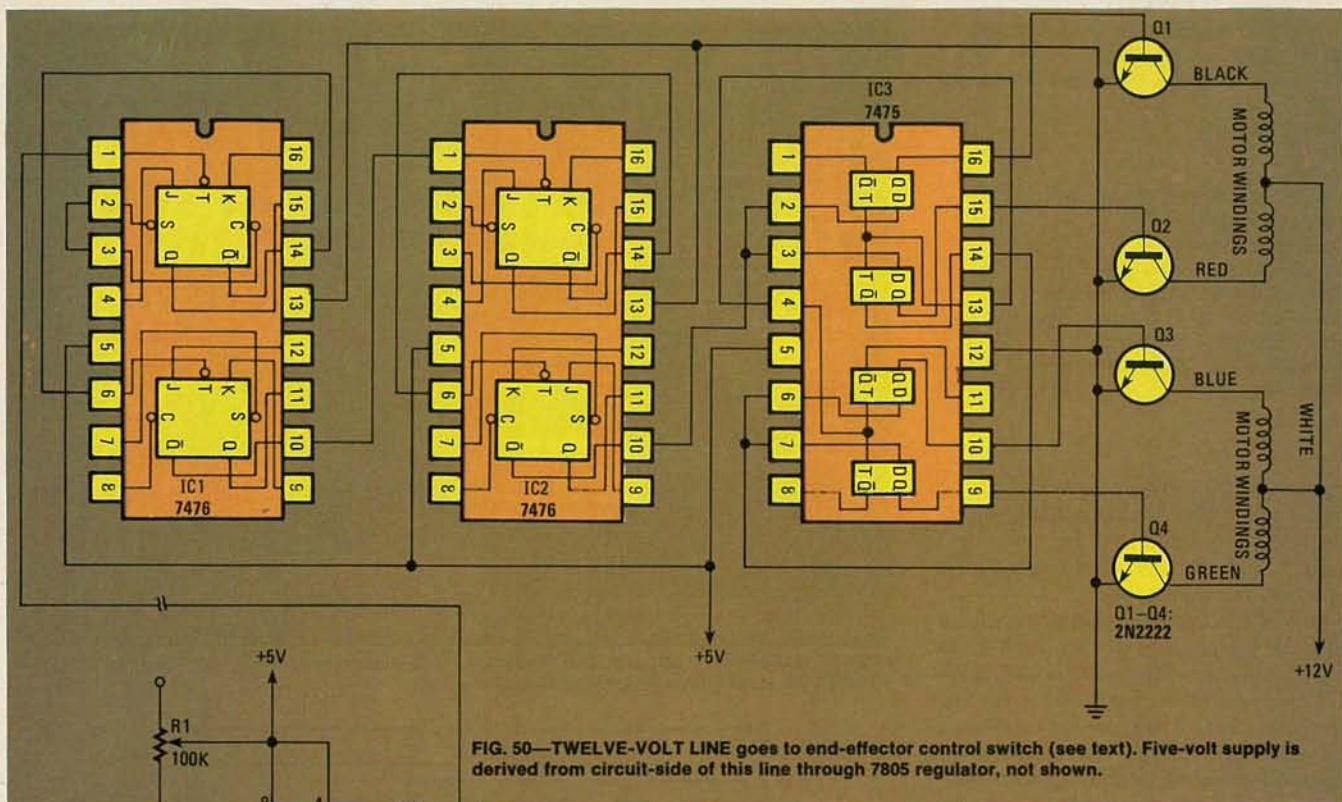


FIG. 50—TWELVE-VOLT LINE goes to end-effector control switch (see text). Five-volt supply is derived from circuit-side of this line through 7805 regulator, not shown.

from the 12-volt supply by means of a dropping resistor, that method leaves itself open to fluctuations, depending on how much of a load the rest of the robot's electrical and electronic parts present to the battery at any given time. It's better to derive the five volts through a 7805 regulator, well heat-sunk to dissipate the heat generated in dropping the twelve volts to five. The addition of an intermediate resistor to drop the 12 volts to eight would ease the load on the regulator.

Other TTL circuits will be described later and they, too, will benefit from a regulated five-volt power supply.

A twist-of-the-wrist

One of the options hinted at earlier in our series was an end-effector (hand) that could be rotated at the "wrist" to give an additional degree of freedom.

That "twist-of-the-wrist" end-effector uses the claw-type mechanism described in Part 2 (September 1980) but, rather than being firmly attached to the manipulator (arm), it is attached to the shaft of a stepper motor. A stepper motor is a motor whose shaft turns just a little bit each time an electrical pulse is applied to its windings.

Figure 50 shows a circuit that gener-

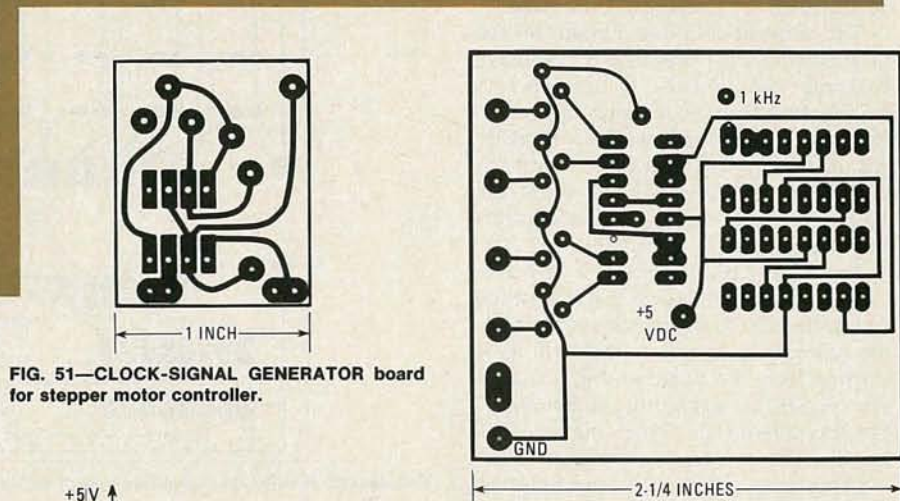


FIG. 51—CLOCK-SIGNAL GENERATOR board for stepper motor controller.

FIG. 53—DIVIDER CHAIN AND LATCHES are located on separate PC board.

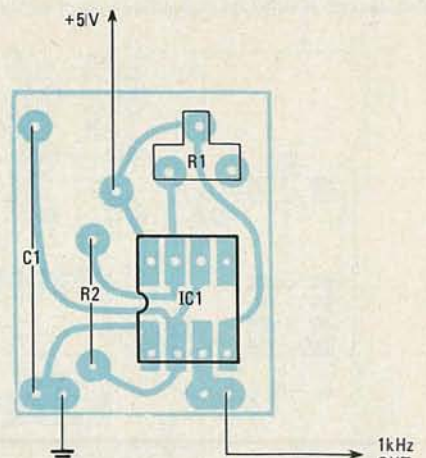


FIG. 52—INTEGRATED CIRCUIT, IC1, is a 555 timer (shown at lower-left in Fig. 50). One-kHz clock signal is fed to second PC board.

ates those pulses and drives the motor. The circuitry actually consists of two parts. The first, used to generate the

pulses, is identical to the 555-IC section of the LED sequencer board, except for the values of R1 and C1, which are chosen to give an output of one kHz.

The second uses two 7476 IC's to divide that one-kHz signal by four (giving an output of 250 Hz), and that output is applied to a 7475 quad latch that feeds driver transistors Q1-Q4. Those transistors are connected so as to provide 12 volts to the four windings of the stepper motor.

Figures 51-54 show foil patterns and parts placement diagrams for the two-board circuit. The 12-volt and 5-volt (through a 7805 regulator, not shown) supplies are derived from the wiring to the solenoid of the end-effector mounted on the stepper motor's shaft.

PARTS LIST—STEPPER MOTOR CONTROLLER

All resistors 1/4 watt, 5%

R1—100,000 ohms trimmer potentiometer

R2—1000 ohms

Capacitors

C1—0.068 μ F, 10 WVDC, any type

Semiconductors

IC1, IC2—7476 dual J-K flip-flop

IC3—7475 quad latch

IC4—555 timer

Q1-Q4—2N2222 or equivalent

Miscellaneous: 7805 voltage regulator with heat sink

PC boards for the above are available from PPG Electronics Co., Inc., 14663 Lanark St., Van Nuys, CA 91402. (213) 988-3525: Motor Direction Indicator and Stepper Motor Oscillator, \$3.00 each, LED Flasher, \$5.00, Stepper Motor Controller, \$5.00. Please add \$1.00 per order for shipping and handling. CA residents add 6% tax. MC and Visa accepted.

PARTS LIST—STEPPER MOTOR ASSEMBLY

Item	Size	Quantity	Supplier's part no.	Supplier
Stepper motor	12 VDC, 0.9°-step	1	Haydon 31612 or 31618, or equivalent	(L)
Shaft	3/16-in. diam. \times 1 inch	1		(K)
Bearing	3/16-in. I.D.	2	B2-9	(A), (B)
Gear	.593-in. diam., 36-T, 64 pitch, 3/16 I.D.	1	P64A19-36	(A), (B)
Note: small mating gear comes with stepper motor				
Solid steel wire	20 gauge	5 inches		(K)

SUPPLIERS

- (A) **The Robot Mart**
Room 1113
19 W. 34th St.
New York, NY 10001
(\$3.00 for catalog)
- (B) **Winfred M. Berg, Inc.**
499 Ocean Avenue
E. Rockaway, NY 11518
- (K) Local hardware or building supplies store
- (L) **Haydon Switch & Instrument, Inc.**
1500 Meriden Rd.
Waterbury, CT 06705
(Write for list of distributors)

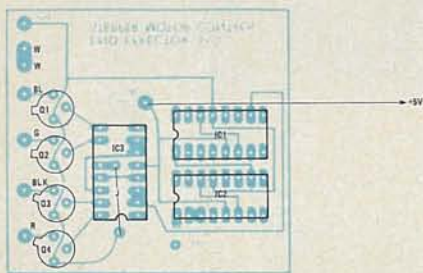


FIG. 54—COLOR CODES shown here should correspond with those on motor wires.

end-effector. The next time the circuit is activated, the end-effector closes again, but the wrist turns the other way.

The end-effector and wrist actions can be made independent of each other by the addition of another switch to the control console.

Several stepper motors that have been found to work well in this application are indicated in the parts list. The attachment of the motor to the robot's end-effector and manipulator is shown in Fig. 55. A

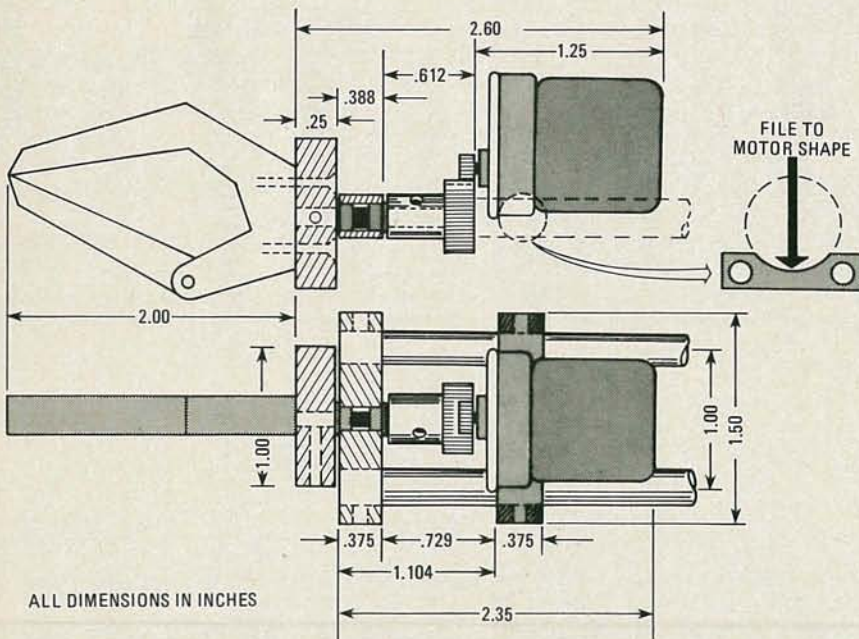


FIG. 55—SMALL GEAR ON STEPPER-MOTOR SHAFT does not have to be purchased separately—it comes with the motor. Note use of bearings through first cross-bar rod.

In practice, when the switch controlling that end-effector is thrown, the "hand" closes and the wrist begins to turn. Returning the switch to the "off" position stops the motor and opens the

9-T (nine-tooth), 64-pitch gear is mounted on the shaft of the stepper motor and drives a 36-T, 64-pitch gear attached to the end-effector mounting flange by means of a 3/16-inch diameter



FIG. 56—COMPLETED rotatable end-effector mounted on forearm shows modified connection to solenoid using solid steel wire.

shaft passed through two flange bearings in the end cross-bar rod. Not shown in the mechanical drawing is a hole bored through the axis of the shaft to pass the wire that operates the claw. Fig. 56 shows the assembled rotatable end-effector with the 20-gauge solid wire pivoted where it is attached to the solenoid to allow free rotation.

To mount the stepper motor and rotatable end-effector, the end cross-bar rod has to be drilled for the bearings and shaft, and the next cross-bar rod up should be filed to accept the shape of the motor. The motor is clamped and/or bolted to the arm assembly.

In the next installment, in preparation for radio- and computer-control, we'll describe motor-control circuits that operate from logic-level signals, and start making radio-control system. **R-E**

UNIVERSAL



THE UNIVERSAL COUNTER/TIMER IS A new breed of test instrument, born of LSI (Large Scale Integration) technology that makes it possible to include the essential central circuits on a single IC, in many cases. To be entirely fair, there were Universal Counter/Timers (or UCT's for short) available before LSI made building them easy, but this is the first time that a number of units have been available for under \$500.

The Universal Counter/Timer makes five basic kinds of measurements:

Frequency: In that mode, the UCT counts the number of selected signal transitions which are appearing at its primary input.

Period: In that mode, the UCT measures the time between successive signal transitions at its primary input. For example, the time between the rising edge of the input signal crossing a 0.5-volt threshold and the next time the input signal rose above 0.5-volt (see Fig. 1) would be displayed in the period mode. Although that might not correspond exactly to the classical explanation of period, it is proper by definition.

Event counter: In that mode, the UCT counts selected input signal transitions until manually "frozen" or reset.

Interval: In that mode, the UCT measures the time between the occurrence of a selected transition of an input signal at its primary input (which starts the measurement) and the occurrence of a selected transition of an input signal at its secondary input (which ends the measurement).

Frequency ratio: In that mode, the UCT counts the number of selected transitions that occur at the primary input between successive selected transitions that occur at the secondary input.

All that talk about selected signal edges or transitions is necessary because of the extensive input-signal conditioning that is provided for at one or both inputs. A *slope-selector* switch determines whether a positive-going transition (or *rising edge*) or a negative-going transition (or *falling edge*) will be used in any measurement. An *attenuator* is usually provided, usually offering factors of attenuation of one (unity), 10 and 100. Also since those inputs are usually DC-coupled, a *trigger level* control selects the threshold level at which the selected edge (rising or falling) is recognized by the counting circuits.

The front panel of a typical UCT is shown in Fig. 2.

We will see that extensive input conditioning makes those delightful instruments all the more useful.

Let's take a look at some hints and tips and application notes to help us get all we can out of our UCT's.

Frequency counter

UCT's are not generally intended for high-frequency use, as they usually provide about a 10-MHz ceiling on their response as frequency counters. On the other hand, they are highly sensitive, offering input impedances on the order of 1 megohm.

Even with its sensitive, high-impedance inputs, a UCT can "pull" the frequency of an oscillator because of the capacitive effects of its connecting

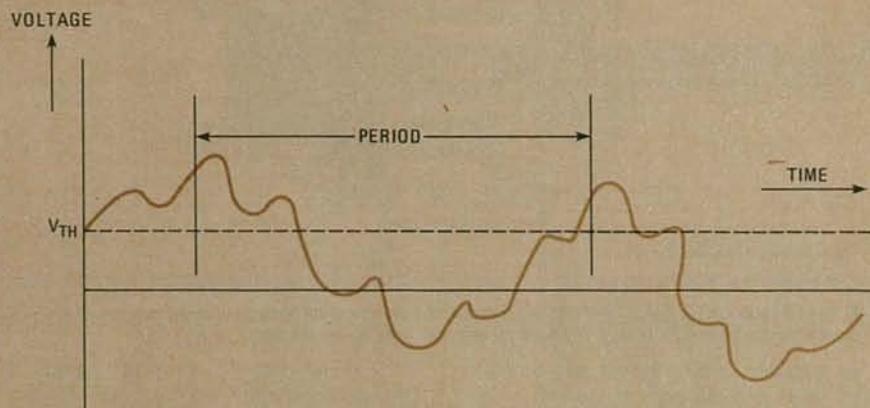


FIG. 1—PERIOD FUNCTION measures time interval between successive signal transitions. (In this example, threshold voltage V_{TH} defines the transition-point.)

COUNTER/TIMERS



DATA PRECISION MODEL 5845 (above) has a pulse-resolution of 15 nS. Low-pass filter maximizes noise-rejection when working with low frequencies.

MODEL 5001 UNIVERSAL COUNTER-TIMER (top of opposite page) from Global Specialties features two inputs, permitting one counting function to modify another.

AUTORANGING MODEL 1820 (below) from B&K Precision, Dynascan Corp. counts from 5 Hz to 80 MHz. Elapsed-time function can be remotely controlled.



When does a counter become a super counter? When it becomes a Universal Counter/Timer, capable of measuring and displaying the occurrence of events in several different ways.

MARTIN BRADLEY WEINSTEIN*

cable (if nothing else) and its input pre-amplifier.

A 10:1 oscilloscope probe (which, happily, readily mates with the BNC input connector usually provided) can minimize circuit loading and oscillator pulling. Better yet, measure the oscillator frequency after a stage or more of buffering instead of at the oscillator whenever possible.

If the oscillator is radiating, as in a transmitter, a short piece of wire—or a telescopic antenna—connected to the UCT may provide adequate coupling for reliable measurements. However, any *direct* connection of the UCT to the transmitter at its antenna can turn the works of both into slag before you can utter a four-letter word.

In many cases (video comes to mind), it may be important to match the UCT input impedance to that of the signal source with a 50-ohm, 75-ohm, 300-ohm or other termination. Because of the high input impedance of the UCT, a termination resistor can be applied directly to its input.

For fast, accurate measurement of very low frequencies, don't measure frequency. Instead, measure period (P), which is the reciprocal of frequency. $F(\text{MHz}) = 1/P(\text{microseconds})$; $F(\text{Hz}) = 1/P(\text{seconds})$. Keep your pocket calculator handy.

Using a microprocessor? Set your UCT up for a 2-volt threshold and your UCT can give you an exact peg on its clock frequency—which may explain why your cycle-counting software doesn't quite get its times right.

*At the time this article was written, the author was Director of Marketing for Global Specialties

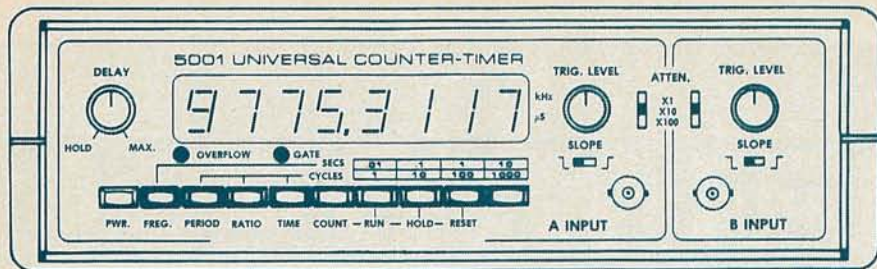


FIG. 2—TYPICAL UCT FEATURES are exemplified by front panel of Global Specialties' model 5001.

For additional accuracy, many UCT's offer multiple gate-times. The longer the gate-time, the longer the wait between display updates but the greater the resolution of the display.

Period measurement

Just as people tend to be either right-handed or left-handed, flip-flops tend to produce one very clean edge and one sloppy edge. And since flip-flops are the most common way that edges are processed in digital circuits (or gates that follow flip-flops—either way, one edge is lots cleaner), there will always be one edge at an output that gives better measurement results than does its opposite.

When the UCT measures frequency, there are lots of events being counted and generally very little noise-induced error, assuming that a non-critical trigger-level was selected. In the period mode, though, the input signal starts and stops the beat-counting of an internal clock.

To improve the odds, most UCT's provide the option of multiple-period averaging. That means they measure either 1 or 10 or 100 or 1000 periods (you decide) and position a decimal point appropriately to preserve the proper display units—seconds or milliseconds or microseconds or nanoseconds or whatever. Using a multiple-period average substantially reduces the susceptibility of measurement accuracy to noise present at the input.

We've seen that low frequencies are easy to measure by using period measurements instead of frequency measurements, and then performing a mathematical inversion. Now you can see why that is both a faster and more accurate technique.

In the frequency-counter mode, it would take 10 seconds to provide 0.1-Hz resolution in measuring a 110.4-Hz signal. But in the period-measurement mode, a 100-cycle average of 9057.971 microseconds is available in less than one second. Say the actual reading is 9057.946 microseconds: that tells us the actual frequency is 110.4003 Hz, which is three accurate digits better than we could do measuring frequency directly.

Want to know the exact speed of a movie projector? An indirect measurement using a UCT is both more con-

venient and more accurate than measurements of mechanical motion made directly. The units of measurement for a film projector are frames per second, which is called its frame rate. The frame rate of most projectors is usually 24. Most of the time, tweaking the speed is only done when things get really bad and Nelson Eddy starts sounding like Rocky the Flying Squirrel—but there are a number of places where precise speed is important.

Your UCT can make the measurement very accurately, as we know, using its period-measurement mode. With no film in the projector and with its motor running and lamp on, a photodetector can be tied to the UCT input to convert the flicker into a measurable signal, as shown in Fig. 3. Depending on the specifics of the detector, some degree of optical filtering, limiting, or shadowing may be desired.

A photovoltaic cell in parallel with a 10 K resistor can be connected to the UCT input directly. Or a phototransistor, photodiode, or photoresistor can be used with the conditioning circuit shown.

Time interval

The first point here is that multiple time-interval averages—available with most UCT's—accumulate errors. The period-measurement mode reduces errors when multiple periods are measured, but the multiple time-interval averaging mode accumulates them. Whenever possible, use the period mode. A device as simple as an OR gate (or flip-flop, or any convenient logic) between the signal coming in and the input to the UCT can often permit time-interval measurements using the period mode. If the time-interval mode is used (remember, a signal at the primary inputs starts the measurement, one at the secondary input completes it), expect some small variance between readings

of identical intervals—that is an inherent error.

Nevertheless, tremendous accuracy and utility are available using the time-interval mode of the UCT. For example, it provides an excellent means of determining pulse parameters—especially pulse width, pulse spacing, pulse period, pulse repetition-rate, and pulse duty-cycle.

The pulses being investigated are fed to both the primary and secondary inputs of the UCT, and appropriate identical thresholds (trigger levels) selected. The selection of identical trigger levels at both inputs is important because it reduces errors due to pulse rise-and-fall-times. For a TTL-level pulse, for example, select a trigger level near 2 volts DC.

To measure pulse width, select the rising edge (using the slope-selector switch) at the primary input, the falling edge at the secondary input. To measure pulse spacing, select the falling edge at the primary input and the rising edge at the secondary input. The other pulse parameters can now be determined by simple calculations:

$$\begin{aligned} \text{Pulse period} &= \\ &\text{Pulse width} + \text{Pulse spacing;} \\ \text{Repetition rate} &= \text{Pulse frequency} = \\ &= \frac{1}{\text{Pulse period}} \\ &= \frac{1}{\text{Pulse width} + \text{Pulse spacing};} \\ \text{Duty cycle} &= \frac{\text{Pulse width}}{\text{Pulse period}} \\ &= \frac{\text{Pulse width}}{\text{Pulse width} + \text{Pulse spacing}} \\ &= \text{Pulse width} \times \text{Pulse frequency} \times 100. \end{aligned}$$

Note that pulse period can be determined using the period-measurement mode of the UCT.

Time-interval measurements are also very important for any study involving rate, time, and distance, since any two of those can always be used to find the third. We'll take a look at the problem in terms of ballistics, but consider that it also applies to timing slot-cars, camera shutters, and lots of other interesting things.

Ballistics got its name because of the rifle balls and ball-shot originally studied—not to mention cannonballs. It's very important for an artilleryman to know where the next shot is going to land. The power charge, the characteristics of the gun, its azimuth and eleva-

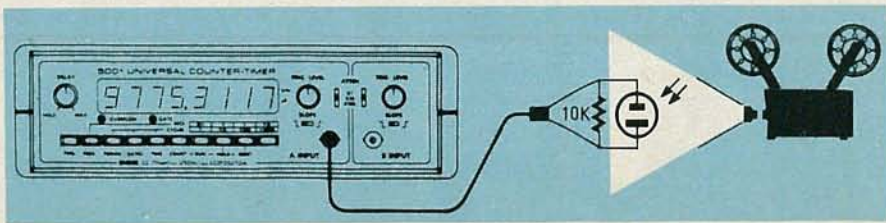


FIG. 3—PROJECTION RATE is determined using UCT to count pulses generated by photodetector.

tion, and the distance to the enemy are the only information real to him. So, to improve the odds, the science of ballistics emerged to make shooting-gallery instinct into hard mathematics.

Originally, an observer with a stopwatch and field glasses would watch as the ball hit a distant target—the distance to the target and the transition time told him what he needed to know.

The UCT helps apply the same principle over much shorter distances and a wider range of speeds, sizes...whatever. Something as simple as a pair of electrical contacts (for a conductive projectile) or a breakable (or frangible) conductor or a microswitch-type rollover (see Fig. 4) can be used where the path of the projectile is precisely known and its flight will not be disturbed by the act of opening or closing the contact.

Note that by using contact *openings* as the significant event (the rising-slope edge using the conditioning circuit shown), you can avoid the problems of contact bounce in most cases.

Even better, non-contact sensing can be used. Photoelectric beam-break arrangements are an excellent and inexpensive alternative to physical contact. Depending on materials, you may also want to look into Hall-effect magnetic sensors, photoreflexive proximity de-

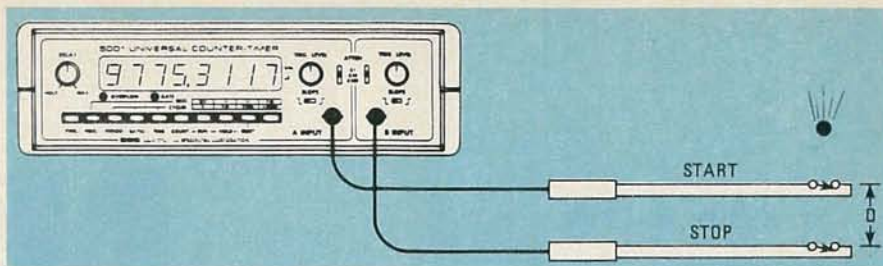


FIG. 4—TIME INTERVAL between opening of two switches can be applied in ballistics calculations.

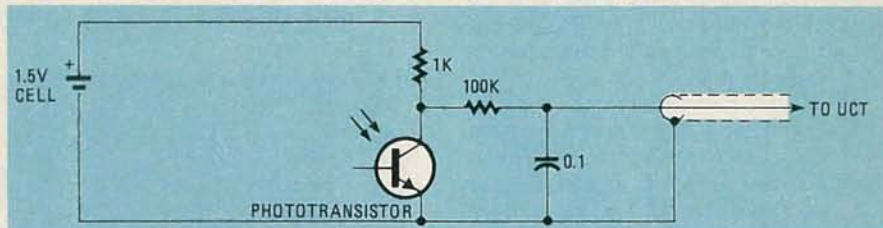


FIG. 5—SIMPLE CONDITIONING CIRCUIT provides clean pulses for input to Universal Counter/Timer.

tectors, etc. A typical photosensitive circuit that can be connected to the input of a UCT is shown in Fig. 5.

Frequency ratio

Many times, the inputs for the UCT will come from transducers that measure real-world phenomena, like flow or rotation or weight or linear speed. The frequency-ratio mode lets you translate the input signals directly into

digital displays in *standard* units—like gallons per minute, RPM, kilometers per hour, etc.

That *scaling* capability (also called *rescaling*) of the frequency-ratio mode happens because the secondary input behaves exactly like the gating circuit of a frequency counter. (Remember, frequency ratio counts the number of events at the primary input during a single cycle at the secondary input.) We could display frequency in Hz simply by using a one-Hz signal one-second cycle-period) at a secondary input; by substituting a different secondary-input frequency, we can make the display do all kinds of tricks.

For example, an encoding disk on a motor shaft might provide 1024 pulses per revolution. A 1024-Hz signal (1/1024-second period) at the secondary input makes the UCT display the actual motor speed in RPS (*Revolutions Per Second*). Want RPM? Divide the secondary input frequency by 60 ($1024/60 = 17.07$ Hz).

Following these rules to determine the correct secondary input frequency:

1. Determine how many pulses you can expect for any event of interest, stated in the units you wish to see displayed. If you know how many pulses are delivered per pint, for example, multiply by 16 to find out how many pulses are delivered per gallon.
2. Express one second in the units of time you wish to see in your displayed reading. For example, 1/60th minute, 1/3600th hour, 1000 milliseconds, etc.
3. Multiply the pulses per event by the time units in seconds to determine the proper frequency to feed into the secondary input.

Event counter

Since the input of the UCT is voltage-responsive, a simple contact closure or

continued on page 100

UNIVERSAL COUNTER-TIMERS

B&K-Precision Dynascan Corp.

6460 West Cortland St.
Chicago, IL 60635

Model 1820

Frequency: to 80 MHz **Period:** 1 microsecond to 200 milliseconds
Interval: .01 to 9999.99 seconds **Event count:** to 999,999 **Price:** \$300
CIRCLE 96 ON FREE INFORMATION CARD

Fluke Mfg. Co.

Box 43210
Mountlake Terrace, WA 98043

Model 1900A

Frequency: to 80 MHz **Period:** 1 microsecond to 200 milliseconds
Event count: to 999,999 **Price:** \$345
CIRCLE 97 ON FREE INFORMATION CARD

Global Specialties

70 Fulton Terrace
New Haven, CT 06509

Model 5001

Frequency: to 10 MHz **Period:** 400 nanoseconds to 10 seconds
Interval: 200 nanoseconds to 10 seconds **Event count:** to 99,999,999
Frequency ratio: to 10 MHz at A, 2 MHz at B **Price:** \$360
CIRCLE 98 ON FREE INFORMATION CARD

Non-Linear Systems

533 Stevens Ave.
Solana Beach, CA 92075

Model RC-5

Frequency: to 10 MHz **Period:** 500 nanoseconds to 10 milliseconds
Interval: 250 nanoseconds to 10 milliseconds **Event count:** to 99,999
Frequency ratio: to 10 MHz at A, 2.5 MHz at B **Price:** \$144
CIRCLE 99 ON FREE INFORMATION CARD

JOSEPH M. GORIN

NOISE

THE GOAL OF HIGH-FIDELITY IS TO MAKE the listener feel as if the music is being created live in front of him. The state of the art is continually advancing towards that idealistic goal.

Sound is a mechanical phenomenon; the plucked string, the struck diaphragm of a drum, the resonance of human vocal cords—all send vibrations into the air. The ear picks up those vibrations, and we have true high-fidelity—a direct-to-ear non-recording. Unfortunately, that can only happen live and in only one place. To allow greater access to excellent, (and therefore rare) music, we record and broadcast it. In the process, it goes through changes in form from acoustical, to electrical, to magnetic (tape), to mechanical (discs), then back to electrical, to acoustical. By the time the music comes out of that complex system, it sounds different. The balance (frequency response) becomes changed by the system (especially the listening room). The music sounds flat because it's all coming from the speakers in front of you. The dynamic range (the ratio of the loudest to softest sounds) becomes squashed in the recording process. Unnatural noises are added. The illusion, though potentially very pleasing, could be much better and more realistic.

Although almost all of the problems induced in the chain described above are mechanically produced, there are electrical remedies available to the hi-fi or electronics enthusiast. Frequency balance can be restored with graphic equalization. The perceived relationship between the room and the listener can be changed with a rear-channel delay unit (ambience synthesizer). The dynamic range can be improved with a dynamic range expander. Surface noises on records, and hiss on tapes, can be reduced with a dynamically-variable



CARVER C-4000 autocorrelation preamplifier.

noise filter. Of all those *signal processing* accessories, to my ears, the expander and filter provide the greatest increase in realism.

I will begin this four-part series of articles by explaining the principles of operation of dynamic range expanders and show how they have been implemented commercially. Next month, I will do the same with noise filters. The following two parts will contain a construction article on a combined expander/noise filter that you can build from scratch, or from a kit, for a fraction of the cost of an assembled unit.

Why expand dynamic range?


Part of the excitement of live music (and part of the musician's intentions) lie in the range of loudness of the parts of the music. Expanding the dynamic range makes the loud sounds louder and the soft sounds softer. Most recordings are compressed intentionally so that the softest sounds are not obscured by the noise level of the recording medium (tape hiss and disc surface noise), and that the loudest sounds

do not overload the medium. (In tape systems, an overload causes tape saturation and distortion; in discs, overload can mean a burned-out cutter-head, excessively-wide grooves, backcutting, or untrackable passages.) In radio broadcasting, compression is almost always applied to give the station a "louder, clearer" sound and to overcome road noise for the motorist-listener. Peak limiting is always available in the system to prevent illegal over-modulation. Those signal-processing activities are the reason that your favorite record almost always sounds better on your own turntable than on the strongest radio station in the area.


Another reason for compression and expansion is for noise reduction. If the noise is only audible for low-level signals, and the low-level signals are attenuated, then the apparent noise will also be attenuated. Thus, the compression applied to the recorded signal can be beneficial.

There are even signal sources that have not been compressed but which benefit from expansion. Live music is

MXR's dynamic expander.

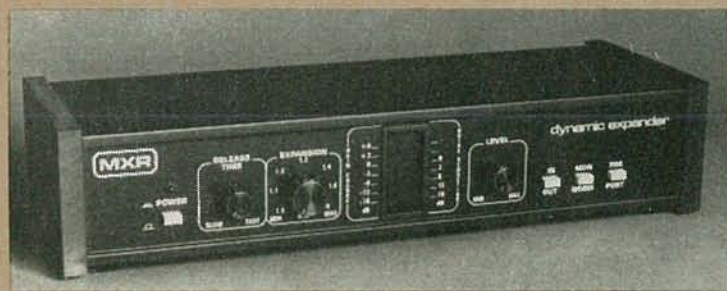

RG DYNAMICS' pro-20.

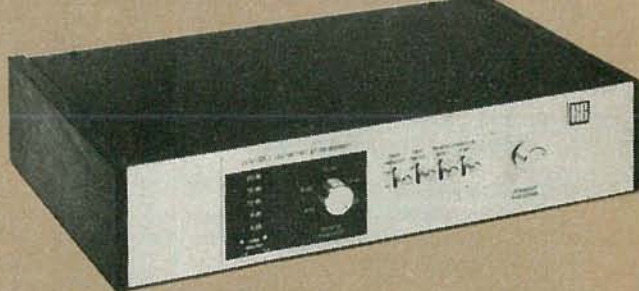

REDUCTION TECHNIQUES

The music that comes out of the speakers of your sound system has usually been processed more thoroughly than cheese spread. The dynamic range expander provides one means of restoring much of the naturalness to your program material.

frequently compressed by the musician to overcome surrounding noise.

By restoring the dynamic range of music, noise filters and expanders (and especially the combination) can create a dramatic improvement in your system—but beware: they are addictive!

How expanders operate

All expanders follow similar straightforward block diagrams with differing details of implementation. As shown in Fig. 1, the work of the expander is done by a device frequently called a VCA (Voltage-Controlled Amplifier), in which the gain is controlled by the voltage (or current) applied to the control terminal.

All the manufacturers of expanders (listed at the end of this installment) have differing implementations of the blocks shown in Fig. 1, each for its own reason. There are three main classes of expanders. First, we have the fixed expanders, as exemplified by the expansion portions of the Heath, Phase Linear, and Carver expanders. They use a conservative, fixed amount of expansion (7, 7.5, and 3.6dB, respectively) as a

portion of their noise-reduction units. Then there are the variable expanders, such as those made by RG Dynamics. They have a variable amount of expansion, and often other controls for different parameters (input/output expansion-slope control, decay time, etc.). A third type is the expander portion of a compressor/expander system intended for noise reduction in tape systems, such as those manufactured by dbx, inc. That type is not optimized for single-ended use (playback of unencoded material) and is thus not applicable to the present discussion. Of

course, the variable-type expanders are more flexible, more expensive—and easier to use to excess (too much expansion always sounds unnatural and too little expansion is of negligible value).

Channel coupling

Most expanders control the gain of both channels together. That reduces the cost of the control circuitry by not requiring two of everything; also, it assures that, regardless of the instantaneous amount of expansion, an instrument placed between the two speakers

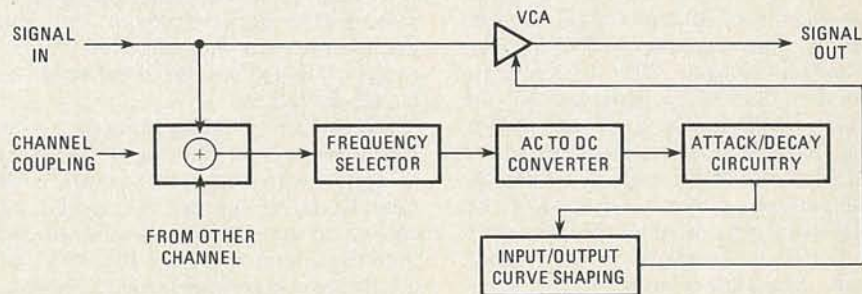


FIG. 1—DYNAMIC RANGE EXPANDERS use a VCA to "ride gain" on the incoming signal.

RG-2 dynamic processor from Pioneer.



MODEL 1BX from dbx.



will not "wander around" because the ratio of its level in each channel will remain constant. If the channels are independent, a strong signal in the left channel can raise the gain of that channel and "pull" a center-stage instrument. Also, if a single instrument is "panned" across the stage, the increased expansion on the dominant side causes an effect very much like increased separation. An advantage of independent channels, though, is that a loud signal in one channel will not change the noise level in the silent channel—an effect that will most likely be noticed only on headphone listening to multi-track recorded music.

Frequency selection

The frequency-selection filter determines which signals affect the expansion most. All the filters attenuate rapidly below 30 Hz to reduce the effect of rumble and other subsonic information. Filtering ultra-sonic signals is also desirable in order to remove FM pilot tones, tape-bias oscillator interference, and other non-musical signals. Typically, however, those are at a very low level and some manufacturers elect not to filter the high end. Besides such obvious criteria, however, there are a number of schools of thought on the shape of the frequency-selection filter. The dbx people are of the broadband school and they suggest that a long, sustained tone will be undesirably modulated by music of changing frequency (but not amplitude) if the frequency filter is not flat. Of course, that situation does not occur often, and it would be hard to detect in an expander of subtle operation (low slope of expansion). Moreover, most musical instruments vary their amplitude with each note. Robert Grodinsky, who designed the products of RG Dynamics, as well as Pioneer's RG-1 (recently updated to the RG-2), believes that the filter should be sensitive to the frequencies where most musical harmonics lie. That will allow more gain when the compressed source is supposed to be loud (lots of harmonics) than when it is soft (fewer harmonics), thus giving more accurate expansion.

AC-DC conversion

Almost all the expanders use precision full-wave detectors to convert the

level of the AC signal to a DC signal suitable for expansion control. A typical circuit is shown in Fig. 2. An explanation of that circuit appears in the February 1980 issue of *Radio-Electronics*. (See "Audio Power Level Meter.") Interested readers are referred to the detailed explanation that is given there. The device is termed "precision" because it is extremely insensitive to the parameters of the diodes, since they are in the feedback loop of the operational-amplifier IC1. The detector is full-wave because it responds identically to peaks of either polarity. That is important if the expander is to respond to rapid asymmetric signals (almost all audio signals are highly asymmetric). The Carver preamp is the only expander to be of the non-precision (passive) half-wave type. At dbx, they use a combination full-wave detector and RMS (Root-Mean-Square) detector.

Attack/decay circuitry

A typical attack/decay circuit is shown in Fig. 3. Voltage V_{IN} is the output of the detector. If a large, fast transient comes along (and music is full of such signals), capacitor C1 will charge up rapidly to a voltage close to the peak value through D1-R2. (Diode D1 is often enclosed in a feedback loop for precision.) Even if the signal is removed, however, C1 must discharge through R1, which is much larger than R2 and allows only a slow discharge rate. That is desirable because the initial edge of a transient should be expanded for enhanced impact. (It is also very likely to have been compressed.) The ear, fortunately, cannot sense the presence of noise immediately following a high-level passage of music, and thus doesn't mind a slow decline in gain. The slow decline prevents the gain from varying rapidly enough to be unpleasant or cause distortion.

RG Dynamics has a special circuit for attack/decay shown in Fig. 4, and used in series with the more conventional type. In that circuit, R2, R3, and C1 are chosen so that C1 charges more slowly than the circuit shown in Fig. 3. Thus, C1 charges up on longer loud passages. Then, at the end of such a passage, the gain declines slowly (about four seconds) so that the reverberant characteristics of the concert hall in which the record-

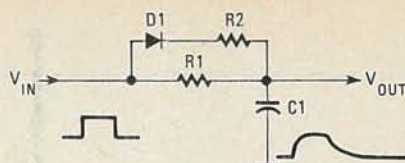


FIG. 3—ATTACK/DELAY CIRCUIT discharges "slowly" to compensate for effects of compression.

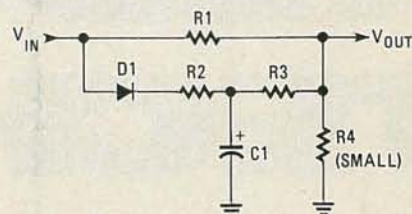


FIG. 4—CIRCUIT USED BY RG DYNAMICS offers longer decay time to long, loud passages.

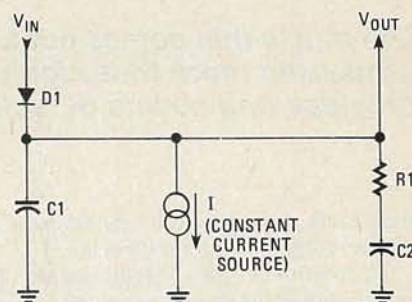


FIG. 5—TWO-STAGE attack/decay circuit is used by dbx for greater flexibility.

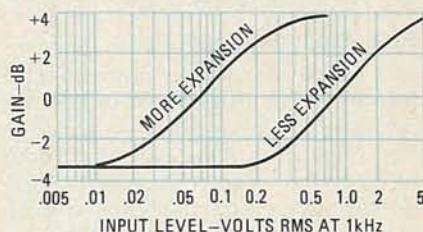


FIG. 6—SLOPE OF EXPANSION should be kept to a minimum to avoid rapid changes in volume.

ing was made are not obscured. If the loud passage is not very long, neither C1 nor the reverberant field of the hall will be expanded. The diode isolates that circuit from the normal path through R1.

The dbx model 1BX also has a special auxiliary circuit that is shown in Fig. 5. It is designed so that a short high-level signal will charge up C1, but not C2; and when the signal dies down, the gain returns to normal (determined by the voltage on C2) rapidly. However, a long, high-level passage will charge up C2, and the gain will decrease slowly because the value of C2 is large (seven times as large as C1). That allows expansion of percussive sounds without varying the expansion of the underlying long-term signal.

Input/output curve shape

In most designs, the shape of the expansion curve (expansion vs. input level) is determined by the implementa-

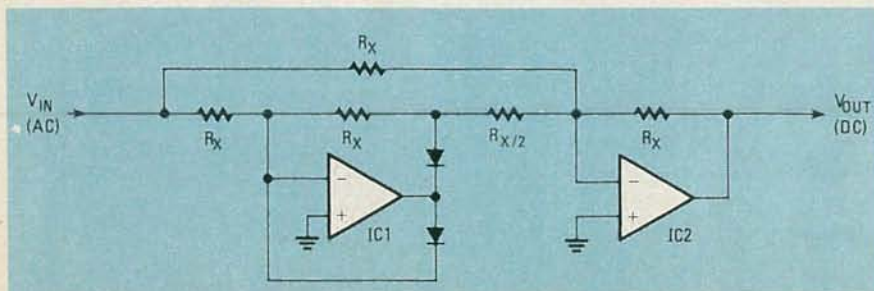


FIG. 2—PRECISION FULL-WAVE detector is first step in generating control signal for VCA.

tion of the other blocks of the circuit, although special shaping circuits can be constructed easily. All the expanders, except the Carver unit, have relatively straight slopes of expansion vs. level. An example is shown in Fig. 6. A slope should be as shallow as possible, be-

cause that minimizes audible gain changing. Also, a modest-size total variation in maximum to minimum gain is desirable for good noise reduction. The way to get the greatest variation with the smallest peak slope is with a straight line. The shape of that curve is

ADDRESSES OF MANUFACTURERS

Carver C-4000 Preamp—\$900 P.O. Box 664 Woodinville, WA 98072 CIRCLE 88 ON FREE INFORMATION CARD	Phase Linear 1000 Series II*—\$400 20121 48th Ave. West Lynnwood, WA 98036 CIRCLE 92 ON FREE INFORMATION CARD
dbx, inc. 1BX—\$260 71 Chapel Street Newton, MA 02195 CIRCLE 89 ON FREE INFORMATION CARD	Pioneer RG-2—\$200 85 Oxford Drive Moonachie, NJ 07074 CIRCLE 93 ON FREE INFORMATION CARD
Heath AD-1304*—\$200 Kit Benton Harbor, MI 49022 CIRCLE 90 ON FREE INFORMATION CARD	RG Dynamics PRO-16—\$300 Skokie, IL 60076 CIRCLE 94 ON FREE INFORMATION CARD
MXR Dynamic Expander—\$300 247 N. Goodman Street Rochester, NY 14607 CIRCLE 91 ON FREE INFORMATION CARD	SSS ASRU**—\$100 Kit 912R Knobcone Place Loveland, CO 80537 CIRCLE 95 ON FREE INFORMATION CARD

* Includes dynamic noise filter—see next month's article.
 ** This unit is the final subject of this article series.

MANUFACTURERS OF EXPANDERS

Manufacturer	Channel Coupling	Frequency Selection	Attack/Decay Circuits	Expansion Fixed Variable	VCA Technique	Features
RG Dynamics	Partial	Midrange "harmonic"	See Text	Variable	Transconductance RCA CA3080	Max. expansion, slope both variable.
MXR	Together	Wideband w/high-treble emphasis	~1.5mS/variable decay	Variable	Transc. Signetics NE571	User variable decay time.
dbx, inc. 1BX	Together	Wideband	See Text	Variable	Transc. Custom dbx circuit.	
Pioneer RG-2	Partial	Midrange	Similar to RG Dynamics	Variable	Unknown	
Phase Linear 1000 Series II	Independent	1.5 kHz and up	Currently being changed.	Fixed—7.5 dB	JFET variable resistor	
Heath	Together	Midrange	.3 mS/300 mS for large changes	Fixed—7 dB	Transc. CA3080	
Carver	Together	70 Hz-2.8 kHz; low-level; wide-band high-level.	30 sec/.25 sec low-level; .7 mS/180 mS high-level	Fixed—3.6 dB	Diode dynamic resistance	
SSS	Together	Midrange	.3 mS-150 mS for large changes	Fixed—9 dB	MOSFET variable resistors	

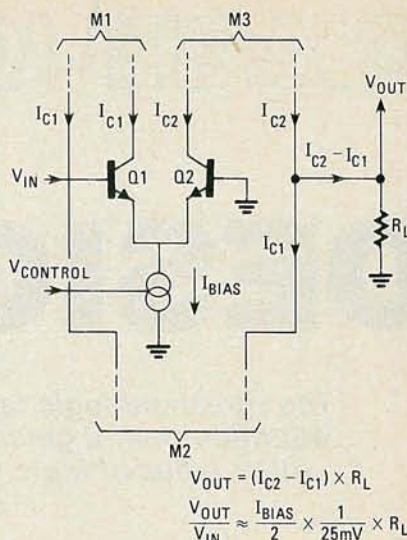


FIG. 7—CURRENT MIRROR PRINCIPLE is illustrated in CA3080 transconductance amplifier.

probably the designer's most basic tool; the shallower it is, the less audible any possible side effects will be. (For example, "breathing", where changes in gain when signals are small cause audible variations in the noise level, and "pumping", where changes in the gain are obvious.)

Voltage-controlled amplifiers

The work of an expander is done by the voltage-controlled amplifier (VCA). Most of the units described use a "transconductance" technique, as shown in Fig. 7. That is typified by RCA's CA3080 operational-transconductance amplifier. A control voltage changes the bias current to differential pair Q1-Q2. The collector current of Q1 goes through current mirrors M1 and M2 (a current mirror "reflects" the input current to its output), and the collector current of Q2 is reflected by M3. The gain of that circuit is due to the transconductance (the ratio of I_{OUT} to V_{IN}) of Q1-Q2 times the load resistance, R_L . Since the transconductance of Q1-Q2 is proportional to I_{BIAS} , the gain is easily controlled.

The drawback of that, and all other VCA's, is that the control element has to be non-linear and it therefore generates distortion. In addition, it will be noisy. (If it were perfectly quiet, the input signal level could be lowered so that the distortion could be dramatically reduced.) The Carver preamp varies the bias on diodes to vary their impedance and change gain, and the Phase Linear 1000 uses FET's as voltage-variable resistors.

Now that you know about what expanders do and how they do it, I expect that you will find my implementation of an expander you can build very interesting. Next month, we will discuss the varied world of dynamic noise-filters.

R-E

DESIGNING With

The threshold-logic family is a relatively unknown one that deserves more attention than it gets. Among its characteristics are the ability to emulate other types of logic gates and to make decisions based on the number of inputs at a given logic level.

JOHN E. CUNNINGHAM

HOW WOULD YOU LIKE A SINGLE INTEGRATED CIRCUIT that could perform all of the logic-gating functions that you have ever heard of, as well as a few that you have probably never heard of? How would you like a gate that would tell when the majority of the inputs assumed a certain state without regard as to which inputs were involved?

Not only can you get such a gate but you can get two of them in a single dual-in-line package which sells for a low price. It is the type MC14530 Majority Logic Gate, made by Motorola.

That IC has been available for several years, but for some reason it seems to have escaped the notice of most experimenters and technicians.

Majority logic is actually a branch of a more general class of logic known as *threshold* logic. Threshold logic is analogous to the response in an animal or human nervous system where the response seems to be based on whether or not a stimulus crosses over a certain threshold. As such, it has been known for many years but has never enjoyed widespread application.

What is majority logic?

Figure 1 shows a sketch of a majority-logic gate. It has five inputs and the output is high whenever any three or more of the inputs are high. It doesn't matter which of the inputs is high—any three will do.

Figure 2 shows a block diagram of the MC14530 Dual 5-input Majority Logic Gate, together with its pin connections. The device is available in a

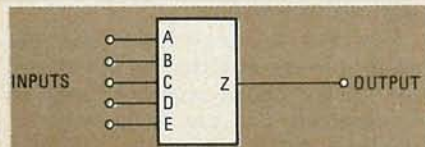


FIG. 1—WHEN the majority of the inputs (A-E) assume a given logic level, so does the output (Z).

16-pin dual-in-line plastic package. The electrical ratings are given in Table 1.

That IC uses CMOS technology and therefore, draws very little current. It can easily be battery-powered. It has the typical CMOS high-noise immunity and can be used in environments where the electrical noise level is high. Like all other CMOS devices, the IC is susceptible to damage from static charges, but it does contain circuitry to protect its inputs.

As shown in Fig. 2, each half of the MC14530 consists of a majority gate of the type shown in Fig. 1 followed by an EXCLUSIVE NOR gate. One input of the latter is brought out to a pin.

The function of the EXCLUSIVE NOR gate is to invert the output of the majority gate by means of a signal applied to input W (pin 6). Thus, if input W is tied to a logical high level, the circuit of Fig. 2 will be a 5-input majority gate. Its output will be high whenever any three or more of the inputs are high. On the other hand, if we connect input W to a logical low level (ground), the circuit will act like what we might call a "minority-logic gate." The output will be low whenever three or more of the inputs are high. The truth table for the EXCLUSIVE NOR gate is shown at the

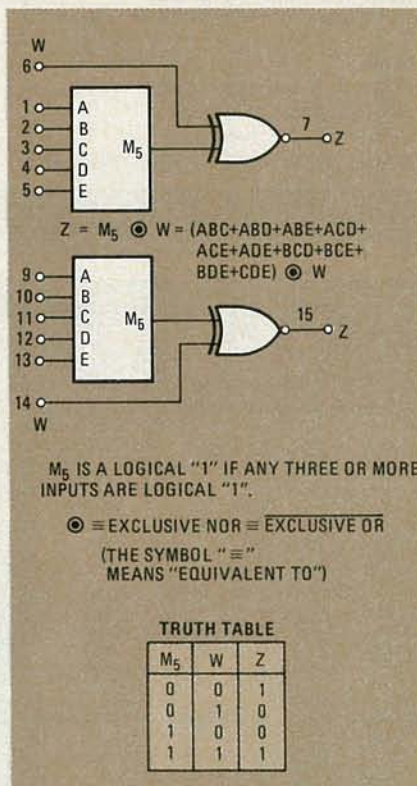


FIG. 2—THE MC14530 consists of two 5-input majority-logic gates, each followed by a NOR gate.

TABLE 1

MAXIMUM RATINGS (Voltages referenced to V_{SS}, Pin 12)

RATING	SYMBOL	VALUE	UNIT	
DC Supply Voltage	MC14530AL MC14530CL/CP	V _{DD}	+18 to -0.5 +16 to -0.5	VDC
Input Voltage, All Inputs	V _{in}	V _{DD}	to -0.5	VDC
DC Current Drain per Pin	I	10		mADC
Operating Temperature Range	MC14530AL MC14530CL/CP	T _A	-55 to +125 -40 to +85	°C
Storage Temperature Range	T _{stg}	-65 to +150		°C

MAJORITY-LOGIC

TRUTH TABLE

INPUTS A B C D E	W	Z
FOR ALL COMBINATIONS OF INPUTS WHERE THREE OR MORE INPUTS ARE LOGICAL "0"	0	1
	1	0
FOR ALL COMBINATIONS OF INPUTS WHERE THREE OR MORE INPUTS ARE LOGICAL "1"	0	0
	1	1

bottom of Fig. 2. Figure 3 shows the truth table for the circuit shown in Fig. 2.

There is no reason why a majority-logic gate must have five inputs. We can easily connect it to act as a 3-input majority gate as shown in Fig. 4. When the gate is connected as shown in Fig. 4-a with input W high, the output Z will be high whenever any two of the three inputs A through C are high. With pin W low, as shown in Fig. 4-b, the output will be low whenever any two of the three inputs are high.

Simulating conventional gates

The MC14530 IC can be used not only as a majority-logic gate, but it can also be made to behave as a 2- or 3-input OR, NOR, AND, or NAND gate. Figure 5 shows how connections are made to make the device behave like any conventional 3-input gate. All that is required is that two of the inputs be permanently connected to predetermined levels. For example, in Fig. 5-a, two inputs are permanently connected to a high-logic level. Now, inasmuch as any two of the five inputs are already high, if any of the remaining inputs go high the output will go high. That is exactly how a 3-input OR gate behaves, so our circuit will behave like a 3-input OR gate.

In Fig. 5-b, input W is connected to ground. That, as we saw earlier, inverts the output so the circuit will now behave like a 3-input NOR gate.

In Fig. 5-c, two of the five inputs are tied to ground. The only way the output can go high is for all of the remaining inputs to go high. That is exactly what happens in a 3-input AND gate. To turn the circuit into a 3-input NAND gate, simply tie input W to ground as shown in Fig. 5-d.

Now we have ways to make the basic circuit behave like any 3-input logic gate. We don't have to stop here. We can also make it behave like any 2-in-

FIG. 3—OUTPUT STATE of the NOR gate is determined by the status of "W" and of the five inputs.



FIG. 4—TYING ONE OF THE five inputs high and one low leaves a 3-input majority-logic gate.

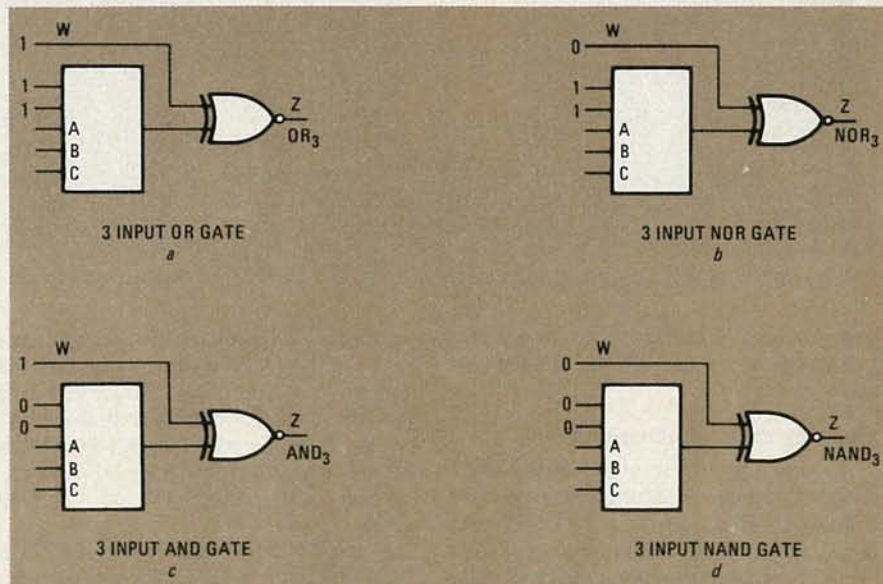


FIG. 5—VARIOUS 3-INPUT logic gates can be formed from a 5-input majority-logic gate.

put gate. The connections are shown in Fig. 6.

In Fig. 6-a, we have simulated a 2-input OR gate by tying two inputs permanently high and grounding another input. If either of the remaining inputs should go high, the output will go high. Thus, we have a 2-input OR gate. To make it into a 2-input NOR gate all we have to do is to ground input W, as shown in Fig. 6-b.

In Fig. 6-c, we have simulated a 2-

input AND gate. Here we have tied two of the inputs low and one of them high. The only way the output can go high is for the remaining two inputs to go high. That, of course, is the AND function. Again to convert the circuit into a NAND gate, all we have to do is to ground input W as shown in Fig. 6-d.

Since the logical function of the gates shown in Figs. 5 and 6 is determined by the logic levels applied to some of the pins, we can change the function of a

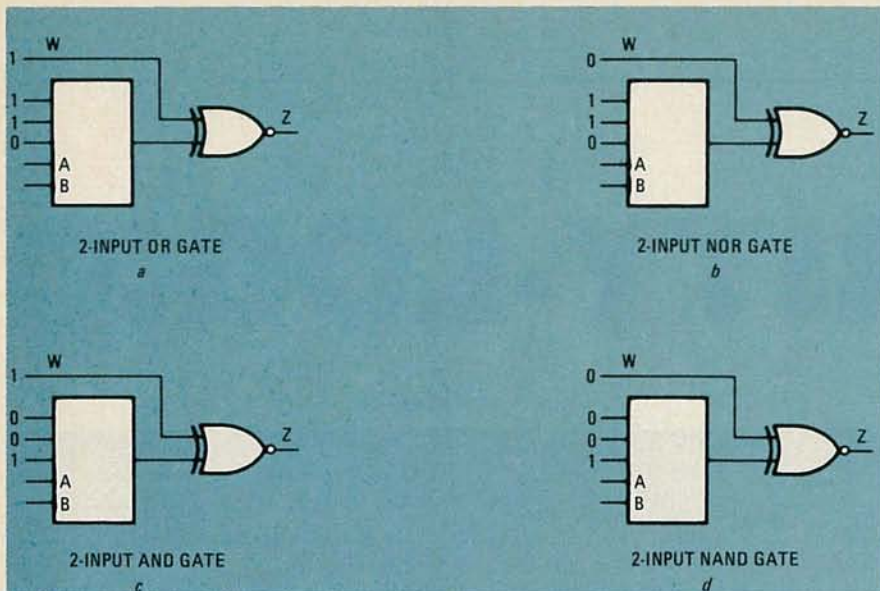


FIG. 6—LOGIC FUNCTION is determined by the logic levels of the "unused" pins.

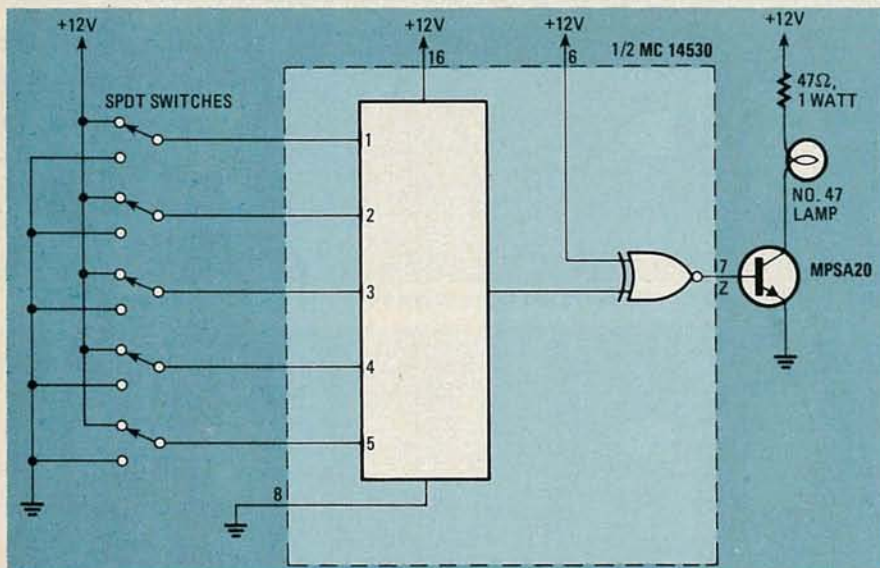


FIG. 7—THE PRINCIPLE OF majority logic is easily applied to a vote where a simple majority rules.

gate while it is in the circuit by simply changing the logic levels applied to those pins.

Majority-logic applications

To make good use of majority logic, most of us have to adopt a new way of thinking. When we think of logic systems and digital circuits, we usually think in terms of the more conventional OR, NOR, AND, or NAND gates. We don't think in terms of majority gates, simply because we haven't been exposed to them.

Many logic-circuit problems can be solved easily using majority logic. Figure 7 shows a secret voting machine for five voters. Each of the voters has a single-pole double-throw switch. When the switch is in the up position it connects one of the inputs of the logic gate to a high logic-level. When the switch is in the down position it connects the input to a low logic-level. Whenever the

majority of the voters set their switches to a high position, the output of the logic gate will go high. Thus, we know that the majority have voted that way, but we have no way of knowing which three (or more) of the five did. The circuit also has possibilities as a simple game.

Figure 8 shows the application of a majority gate to a foolproof security system. One of the most annoying features of intrusion alarms is that they can be tripped by things other than an intrusion, such as failure of a component. The result is false alarms that are annoying and sometimes even dangerous.

The circuit of Fig. 8 minimizes the probability of a false alarm by requiring two out of three intrusion detectors to be tripped before the alarm will sound. Any type of intrusion detector may be used with the system; all that is required is that the output of the alarm

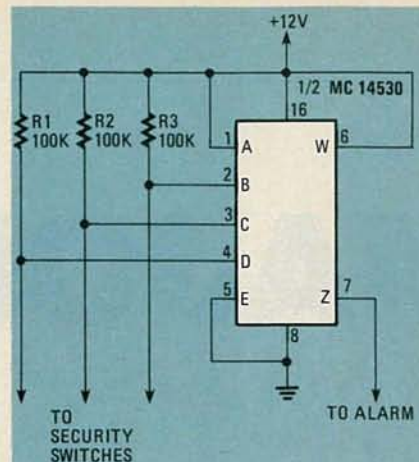


FIG. 8—"FOOLPROOF" SECURITY SYSTEM requires that more than one alarm device be tripped.

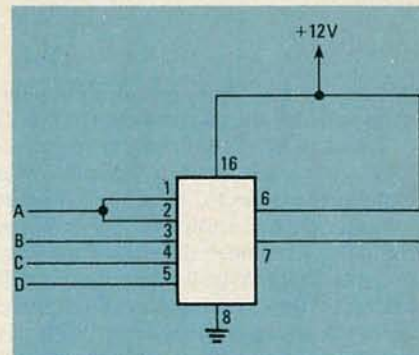


FIG. 9—MAKING TWO INPUTS into one gives that input twice the importance of the others.

be a switch or relay that keeps the output grounded until an intrusion occurs. The intrusion detectors are arranged so that normally an intruder will trip all three upon entering the protected area.

The circuit of Fig. 8 is a 3-input majority gate. The output will go to a high state whenever any two of the input circuits is opened. Thus, if one of the intrusion detectors should fail, it will not cause a false alarm. Similarly, an intruder who skillfully avoids tripping one of the alarms, will sound the alarm upon tripping the other two.

Weighting an input

Another interesting feature of the majority gate is that an input can be "weighted" or made more important than the other inputs. Figure 9 shows a circuit where input A is weighted so that it is twice as important as the other inputs. That is accomplished by simply connecting input A to two of the input pins of the gate.


The output of the circuit of Fig. 9 will go high when inputs B, C, and D go high, or when input A and any one of the other inputs go high. Thus, as far as the circuit is concerned, input A is twice as important as any of the other inputs.

A circuit of that type can be used where one part of a system, such as an intrusion alarm, is more reliable than other parts.

R-E

ELECTRIC BILLS TOO HIGH? GET A

watt saver™

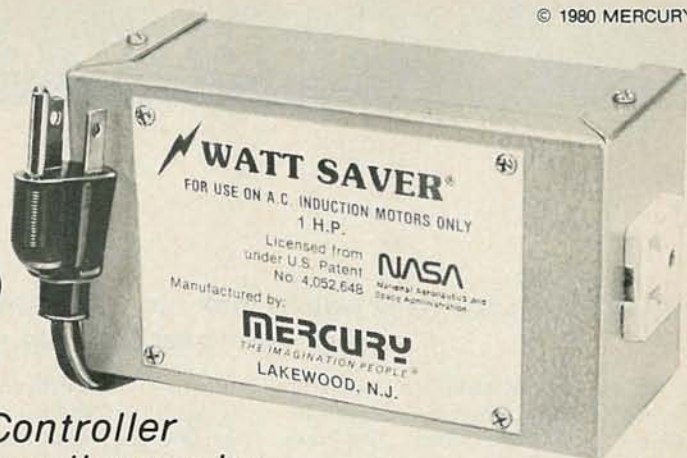

© 1980 MERCURY

Advanced-design Power Factor Controller cuts the cost of running electric appliances by as much as 40%! See for yourself—try it for 60 days!

National Aeronautics and Space Administration
Patent #4,052,648

If you think your electric bills are high now, brace yourself. They'll be even higher next year, and for years to come—even if your use of electricity remains constant—due to utility company rate increases.

Right now, it's probably costing you \$120 to \$160 a year to run a refrigerator...about \$130 for a freezer...and other outrageous sums to power your attic fan, washing machine, sump pump, electric typewriter and/or trash compactor. Even a gas clothes dryer uses expensive electricity (to rotate the drum).

So it makes a lot of sense to use a lot less electric power. And now you can do just that—without cutting down on your use of electric appliances!

INTRODUCING THE WATT SAVER

Our exclusive new Watt Saver is based on an invention developed and patented by the National Aeronautics and Space Administration. "The NASA/Nola power saver," wrote a *Popular Science* senior editor, "was developed by Frank Nola at NASA's Flight Center in a program to reduce power consumption in spacecraft motors. Nola calls it a PFC—power-factor controller. I prefer to call it a power saver, however, because that's what it does."

NASA TESTED IT

According to NASA documents, "The device has been tested at Marshall Center on over 40 types of motors, with power savings ranging up to 60%, depending on the loading. The motors tested were both single-phase and three-phase, ranging from 1/2 H.P. to 5 H.P. Most motors will show up to 40-50% savings when running lightly loaded or unloaded, and some will show 5-to-7% savings at rated load."

NASA's Technical Support Package showed that "The Power Factor Controller applies to induction type electric motors—the most commonly used type in all major home appliances and the most commonly used in industry." Such as those in refrigerators, freezers, washing machines, dishwashers, trash compactors table saws, drill presses, electric typewriters, gas dryers (without electric igniters), fans, grinders, food processing machines, lathes and various types of pumps (e.g., heat, sump, swimming pool).


HOW IT SAVES POWER

Popular Electronics explained it this way: "AC induction motors characteris-

tically run at a nearly constant speed that's fixed by power-line frequency and independent of load and supply voltage. When heavily loaded, the motor draws line current that is nearly in phase with the applied voltage....Under light load conditions, the motor develops less torque by allowing more lag between the voltage and the current. This reduces the power factor while leaving the current essentially the same in magnitude." (The wasted power is given off as heat.)

"To minimize this waste, Nola's device monitors the motor's power factor, and when it detects light load conditions, it reduces the supply voltage....The current, now more nearly in phase with the voltage, therefore does as much useful work as before, but it and the voltage are smaller, resulting in a net savings of electric power."

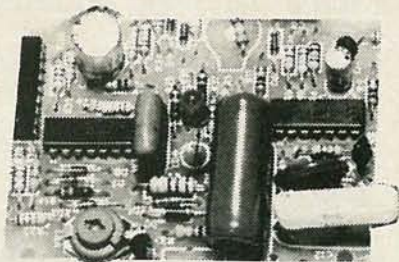Besides saving power, the Watt Saver also allows motors to run cooler—which lengthens their life—and quieter.



Inside the Watt Saver: electronic components work automatically, microsecond by microsecond, to make sure an electric motor receives no more voltage than what's needed to handle the load at any given instant...to save you money!

IT'S SIMPLE TO USE

The Watt Saver—made in the U.S. under license from NASA—is housed in a sturdy metal case (just 5 1/4" W x 3" H x 2" D) with an electrical outlet and a 2-foot cord. Simply plug the cord of your appliance into the Watt Saver, then plug the Watt Saver's cord into any electrical outlet. You can move the Watt Saver to various locations as needed or, better yet, get two or more.

(For air conditioners, order the wired-in model and if you are electrically inclined no electrician is necessary to connect it.)

Whenever the appliance is used, the Watt Saver goes to work instantly. There are no buttons to push, no gauges to watch. The Watt Saver works automa-

tically, to reduce the amount of electric power used and (therefore) to reduce your electric bills—without reducing the efficiency of your appliances!

LOW COST—AND A TAX CREDIT

Although we're the only company in the world offering the Watt Saver, the cost is modest—only \$39.95 for the 110V, 15-amp model that handles motors up to and including 1 H.P. Want two? They're just \$37.95 each. Or splurge and get three at \$34.95 each. Specify plug-in or wired-in models.

We also offer a 220V, 15-amp model for motors up to and including 2 1/2 H.P. The price is \$49.95 for one; \$47.95 each for two or more. Specify plug-in or wired-in.

No matter which model you order or how many units you order, the postage/handling charge is just \$2.50 per order.

And next year, when you fill out your tax return, you can deduct a 15% energy tax credit—for additional savings.

60-DAY MONEY-BACK GUARANTEE

Try the Watt Saver for as long as 60 days. If not completely satisfied, return it (insured) for a full refund.

Naturally, the sooner you send for the Watt Saver, the more you can save on your electric bills. So order today. Send your check or money order to the address below. Or charge it to your Visa, Master Card, Diners Club or Carte Blanche account. If using your credit card, you can order via our toll-free number:

800-526-2801

If it's busy, or no answer, call our other toll-free number:

800-257-7850

(In New Jersey, call: 800-322-8650. N.J. residents: add 5% sales tax.)

Or mail your order to:

NATIONAL SALES GROUP
MERCURY
THE IMAGINATION PEOPLE®

Dept. RE-1, 404 Madison Avenue
Lakewood, N.J. 08701
201-370-0446

CIRCLE 46 ON FREE INFORMATION CARD

JANUARY 1981

67

A look at another easy way to make circuit boards.

EARL "DOC" SAVAGE, K4SDS, HOBBY EDITOR

IN THE AUGUST 1980 ISSUE, WE DISCUSSED the *E-Z Circuit* adhesive materials for making "instant" PC boards. You know that I am impressed with that system, produced and distributed by Bishop Graphics (P. O. Box 5007RE, Westlake Village, CA 91359). This month I want to be sure that you know about two more PC systems that are also covered in their EZ-102 manual/catalog.

The first is called *Cut 'N' Peel*. It is nothing more than a board with a special copper covering. To use *Cut 'N' Peel*, you must first sketch the circuit on the copper. Then, unwanted copper is cut with an *X-acto* or other very sharp knife and simply peeled up off the board.

Of course, with the unwanted copper gone, you are left with your circuit. There you have it—an instant PC board. You are ready to drill the board, and to mount and solder components.

The cutting and peeling may be quite difficult with a complex circuit but it can be done—steady hand, patience, and all that.

In my opinion, that system is well suited to relatively simple circuits. For

others, I'll stick with adhesive copper patterns (pun intended!). In any case, there are two easy, clean, and reliable methods of making prototype one- or two-of-a-kind PC boards, and those methods can even be combined on one board.

What's that?—you need more copies of your board? Then, you may as well get out the etchant. *And* you'll need master artwork. That can be made in a variety of ways. My preference is to use preprinted opaque patterns on clear film (Fig. 1). That system is quick and easy; it not only gives professional-looking results but, perhaps best of all, is forgiving of placement mistakes.

Bishop Graphics offers a complete array of patterns for making original artwork for PC boards. All you have to do is to press them down on clear film in the required configuration and then run traces with the opaque tape. With just a little care, you can come up with a perfect original.

You know, one of the secrets of making a good PC board is to develop a good design (layout) in the first place. Depending upon the circuit, a lot of sketching

and re-sketching may be necessary in order to get the number of jumpers down to a minimum.

Eventually, however, a scale drawing should be made to aid in the actual placement of patterns—either opaque on film, or adhesive copper on a board. Bishop's scale templates are almost indispensable in making those final drawings.

Altogether, the *E-Z Circuit* line is quite comprehensive. Use of those materials can save you a lot of "fussin' and cussin'" when fabricating PC boards.

Pine Wood Derby

Back in March I asked your help for Bill Wisel who was looking for a way to take the "heat" of disputes out of his Cub Scout's Pine Wood Derby heats. Your responses have been both gratifying and intriguing.

Apparently, many of you are or were Scout leaders. There have been more ideas and circuits on that topic than any other since *Hobby Corner* began. In fact, they are *still* coming in. Please accept our thanks and "well done" to each of you who has written.

Unfortunately, all that has come about too late for the 1980 Derby but there is plenty of time for '81. So, let's take a look at some of the responses.

Your answers to Bill's question ranged from the very simple to the very complex—mechanical to IC's; two-lane to six-lane; winner-only to each lane timed; arbitrary timing interval to one-thousandth-of-a-second accuracy! Since the number of circuits we can print is limited, we'll take a look first at the major differences in approach.

Most packs (and leaders!) have limited finances. In spite of using surplus and salvaged parts, an accurately timed, multi-lane finish line is going to be rather expensive. For many readers, however, that is *not* the prime consideration in deciding basic approach.

In determining the number of lanes, several respondents pointed out that those youngsters spend a lot of time building their cars. In order to have the reward of more racing, even for the losers, you have only two lanes and the "best-two-out-of-three heats" rule.

Carl Malmquist of Vestal, NY makes a very good point for *not* actually timing the cars. It is difficult to explain the logic and justice to a youngster who loses one race while having a faster time than the

continued on page 70

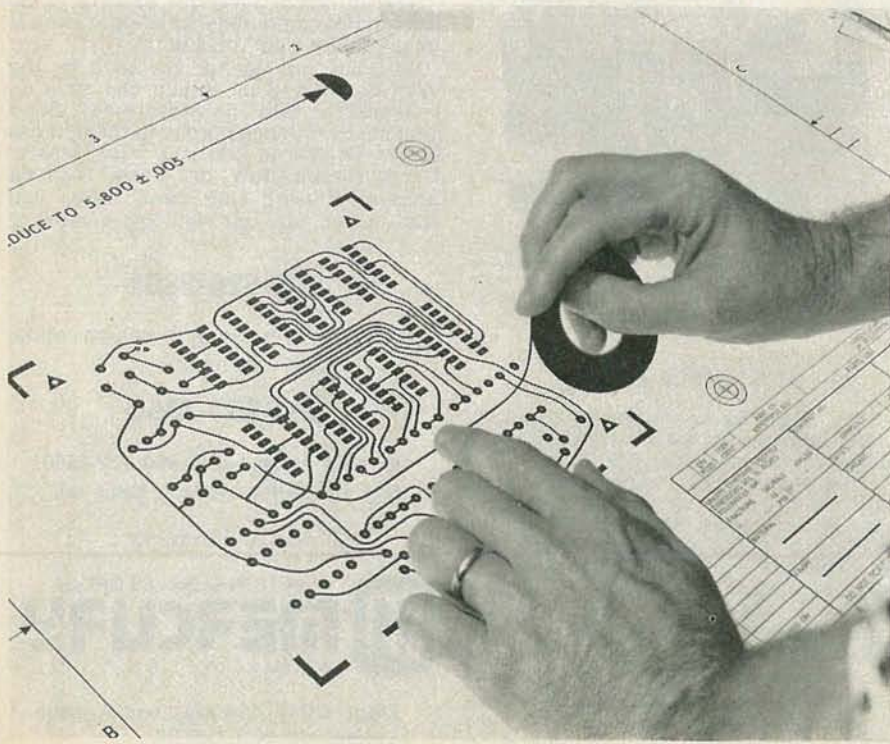


FIG. 1

Start learning and computing for only **\$129.95** with a **Netronics 8085-based computer kit**. Then expand it in low-cost steps to a business/development system with 64k or more RAM, 8" floppy disk drives, hard disks and multi-terminal I/O.

THE NEW EXPLORER/85 SYSTEM

Special! Full 8" floppy, 64k system for less than the price of a mini! Only **\$1499.95!**

(Also available wired & tested. \$1799.95)

Imagine — for only \$129.95 you can own the starting level of Explorer/85, a computer that's expandable into full business/development capabilities — a computer that can be your beginner system, an OEM controller, or an IBM-formatted 8" disk small business system. From the first day you own Explorer/85, you begin computing on a significant level, and applying principles discussed in leading computer magazines. Explorer/85 features the advanced Intel 8085 cpu, which is 100% compatible with the older 8080A. It offers on-board S-100 bus expansion. Microsoft BASIC in ROM, plus instant conversion to mass storage disk memory with standard IBM-formatted 8" disks. All for only \$129.95, plus the cost of power supply, keyboard/terminal and RF modulator if you don't have them (see our remarkable prices below for these and other accessories). With a Hex Keypad/display front panel, Level "A" can be programmed with no need for a terminal, ideal for a controller, OEM, or a real low-cost start.



Level "A" is a complete operating system, perfect for beginners, hobbyists, industrial controller use. \$129.95



Full 8" disk system for less than the price of a mini (shown with Netronics Explorer/85 computer and new terminal). System features floppy drive from Control Data Corp., world's largest maker of memory storage systems (not a hobby brand!)



Level "A" With Hex Keypad/Display.

LEVEL "A" SPECIFICATIONS

Explorer/85's Level "A" system features the advanced Intel 8085 cpu, an 8355 ROM with 2k deluxe monitor/operating system, and an advanced 8155 RAM I/O... all on a single motherboard with room for RAM/ROM/PROM/EPROM and S-100 expansion, plus generous prototyping space.

PC Board: Glass epoxy, plated through holes with solder mask... I/O: Provisions for 25-pin (DB25) connector for terminal serial I/O, which can also support a paper tape reader... cassette tape recorder input and output... cassette tape control output... LED output indicator on SOD (serial output) line... printer interface (less drivers)... total of four 8-bit plus one 6-bit I/O ports... **Crystal Frequency:** 6.144 MHz... **Control Switches:** Reset and user (RST 7.5) interrupt... additional provisions for RST 5.5, 6.5 and TRAP interrupts on-board... **Counter/Timer:** Programmable, 14-bit binary... **System RAM:** 256 bytes located at F800, ideal for smaller systems and for use as an isolated stack area in expanded systems... RAM expandable to 64k via S-100 bus or 4k on motherboard.

System Monitor (Terminal Version): 2k bytes of deluxe system monitor ROM located at F900, leaving 6000 free for user RAM/ROM. Features include tape load with labeling... examine/change contents of memory... insert data... warm start... examine and change all registers... single step with register display at each break point, a debugging/training feature... go to execution address... move blocks of memory from one location to another... fill blocks of memory with a constant... display blocks of memory... automatic baud rate selection to 9600 baud... variable display line length control (1-255 characters/line)... channelized I/O monitor routine with 8-bit parallel output for high-speed printer... serial console in and console out channel so that monitor can communicate with I/O ports.

System Monitor (Hex Keypad/Display Version): Tape load with labeling... tape dump with labeling... examine/change contents of memory... insert data... warm start... examine and change all registers...

single step with register display at each break point... go to execution address. Level "A" in this version makes a perfect controller for industrial applications, and is programmed using the Netronics Hex Keypad/Display. It is low cost, perfect for beginners.

HEX KEYPAD/DISPLAY SPECIFICATIONS

Calculator type keypad with 24 system-defined and 16 user-defined keys. Six digit calculator-type display, that displays full address plus data as well as register and status information.

LEVEL "B" SPECIFICATIONS

Level "B" provides the S-100 signals plus buffers/drivers to support up to six S-100 bus boards, and includes: address decoding for on-board 4k RAM expansion selectable in 4k blocks... address decoding for on-board 8k EPROM expansion selectable in 8k blocks... address and data bus drivers for on-board expansion... wait state generator (jumper selectable), to allow the use of slower memories... two separate 5 volt regulators.

LEVEL "C" SPECIFICATIONS

Level "C" expands Explorer/85's motherboard with a card cage, allowing you to plug up to six S-100 cards directly into the motherboard. Both cage and card are neatly contained inside Explorer's deluxe steel cabinet. Level "C" includes a sheet metal superstructure, a 5-card, gold plated S-100 extension PC board that plugs into the motherboard. Just add required number of S-100 connectors.



Explorer/85 With Level "C" Card Cage.

LEVEL "D" SPECIFICATIONS

Level "D" provides 4k of RAM, power supply regulation, filtering decoupling components and sockets to expand your Explorer/85 memory to 4k (plus the origi-

nal 256 bytes located in the 8155A). The static RAM can be located anywhere from 0000 to EFFF in 4k blocks.

LEVEL "E" SPECIFICATIONS

Level "E" adds sockets for 8k of EPROM to use the popular Intel 2716 or the TI 2516. It includes all sockets, power supply regulator, heat sink, filtering and decoupling components. Sockets may also be used for 2k x 8 RAM IC's (allowing for up to 12k of on-board RAM).

DISK DRIVE SPECIFICATIONS

- 8" CONTROL DATA CORP. professional drive.
- LSI controller.
- Write protect.
- Single or double density.
- Data capacity: 401,016 bytes (SD), 602,032 bytes (DD), unformatted.
- Access time: 25ms (one track)

DISK CONTROLLER/I/O BOARD SPECIFICATIONS

- Controls up to four 8" drives.
- 1771A LSI (SD) floppy disk controller.
- Onboard data separator (IBM compatible).
- 2 Serial I/O ports
- Autoboot to disk system when system reset.
- 2716 PROM socket included for use in custom applications.
- Onboard crystal controlled.
- Onboard I/O baud rate generators to 9600 baud.
- Double-sided PC board (glass epoxy)

DISK DRIVE CABINET/POWER SUPPLY

- Deluxe steel cabinet with individual power supply for maximum reliability and stability.

ORDER A COORDINATED EXPLORER/85 APPLICATIONS PAK!

Beginner's Pak (Save \$26.00!) — Buy Level "A" (Terminal Version) with Monitor Source Listing and AP-1 5-amp Power Supply; (regular price \$199.95), now at SPECIAL PRICE: \$169.95 plus post. & insur.

Experimenter's Pak II (Save \$53.40!) — Buy Level "A" (Hex Keypad/Display Version) with Hex Keypad/Display, Intel 8085 User Manual, Level "A" Hex Monitor Source Listing, and AP-1 5-amp Power Supply; (regular price \$279.35), all at SPECIAL PRICE: \$219.95 plus post. & insur.

Special Microsoft BASIC Pak (Save \$103.00!) — Includes Level "A" (Terminal Version), Level "B", Level "D" (4k RAM), Level "E", 8k Microsoft in ROM, Intel 8085 User Manual, Level "A" Monitor Source Listing, and AP-1 5-amp Power Supply; (regular price \$439.70), now yours at SPECIAL PRICE: \$329.95 plus post. & insur.

ADD A TERMINAL WITH CABINET, GET A FREE RF MODULATOR: Save over \$114 at this SPECIAL PRICE: \$499.95 plus post. & insur.

Special 8" Disk Edition Explorer/85 (Save over \$104!) — Includes disk-version Level "A", Level "B", two S-100 connectors and brackets, disk controller, 64k RAM, AP-1 5-amp power supply, Explorer/85 deluxe steel cabinet, cabinet fan, 8" SD/DD disk drive from famous CONTROL DATA CORP. (not a hobby brand!), drive cabinet with power supply, and drive cable set-up for two drives. This package includes everything but terminal and printers (see coupon for them). Regular price \$1630.30, all yours in kit at SPECIAL PRICE: \$1499.95 plus post. & insur. Wired and tested, only \$1799.95.

Special! Complete Business Software Pak (Save \$625.00!) — Includes CP/M 2.0, Microsoft BASIC, General Ledger, Accounts Receivable, Accounts Payable, Payroll Package; (regular price \$1325), yours now at SPECIAL PRICE: \$699.95.

Please send the items checked below:

- Explorer/85 Level "A" kit (Terminal Version) ... \$129.95 plus \$3 post. & insur.
- Explorer/85 Level "A" kit (Hex Keypad/Display Version) ... \$129.95 plus \$3 post. & insur.
- 8k Microsoft BASIC on cassette tape. \$64.95 postpaid.
- 8k Microsoft BASIC in ROM kit (requires Levels "B", "D" and "E") ... \$99.95 plus \$2 post. & insur.
- Level "B" (S-100) kit ... \$49.95 plus \$2 post. & insur.
- Level "C" (S-100 6-card expander) kit ... \$39.95 plus \$2 post. & insur.
- Level "D" (4k RAM) kit ... \$69.95 plus \$2 post. & insur.
- Level "E" (EPROM/ROM) kit ... \$5.95 plus 50c p&h.
- Deluxe Steel Cabinet for Explorer/85 ... \$49.95 plus \$3 post. & insur.
- Fan For Cabinet ... \$15.00 plus \$1.50 post. & insur.
- ASCII Keyboard/Computer Terminal kit: features a full 128 character set, u&l case, full cursor control, 75 ohm video output, convertible to baudout output; selectable baud rate, RS232-C or 20 ma. I/O, 32 or 64 character by 16 line formats, and can be used with either a CRT monitor or a TV set (if you have an RF modulator) ... \$149.95 plus \$3.00 post. & insur.
- DeLuxe Steel Cabinet for ASCII keyboard/terminal ... \$19.95 plus \$2.50 post. & insur.
- New! Terminal/Monitor: (See photo) Same features as above, except 12" monitor with keyboard and terminal is in deluxe single cabinet kit ... \$399.95 plus \$7 post. & insur.
- Hazeltine terminals: Our prices too low to quote — CALL US
- Lear-Sigler terminals/printers: Our prices too low to quote, CALL US
- Hex keypad/Display kit ... \$69.95 plus \$2 post. & insur.

- AP-1 Power Supply kit ±8V @ 5 amps) in deluxe steel cabinet ... \$39.95 plus \$2 post. & insur.
- Gold Plated S-100 Bus Connectors ... \$4.85 each, postpaid.
- RF Modulator kit (allows you to use your TV set as a monitor) ... \$8.95 postpaid.
- 16k RAM kit (S-100 board expands to 64k) ... \$199.95 plus \$2 post. & insur.
- 32k RAM kit ... \$299.95 plus \$2 post. & insur.
- 48k RAM kit ... \$399.95 plus \$2 post. & insur.
- 64k RAM kit ... \$499.95 plus \$2 post. & insur.
- 16k RAM Expansion kit (to expand any of the above in 16k blocks up to 64k) ... \$99.95 plus \$2 post. & insur, each.
- Intel 8085 cpu Users' Manual ... \$7.50 postpaid.
- 12" Video Monitor (10MHz bandwidth) ... \$139.95 plus \$5 post. & insur.
- Beginner's Pak (see above) \$169.95 plus \$4 post. & insur.
- Experimenter's Pak (see above) ... \$219.95 plus \$6 post. & insur.
- Special Microsoft BASIC Pak Without Terminal (see above) ... \$329.95 plus \$7 post. & insur.
- Same as above, plus ASCII Keyboard Terminal With Cabinet, Get Free RF Modulator (see above) ... \$499.95 plus \$10 post. & insur.
- Special 8" Disk Edition Explorer/85 (see above) ... \$1499.95 plus \$26 post. & insur.
- Wired & Tested ... \$1799.95 plus \$26 post. & insur.
- Extra 8" CDC Floppy Drives ... \$499.95 plus \$12 post. & insur.
- Cabinet & Power Supply For Drive ... \$69.95 plus \$3 post. & insur.
- Drive Cable Set-up For Two Drives ... \$25 plus \$1.50 post. & insur.

- Disk Controller Board With I/O Ports ... \$199.95 plus \$2 post. & insur.
 - Special: Complete Business Software Pak (see above) ... \$699.96 postpaid.
- SOLD SEPARATELY:
- CP/M 1.4 ... \$100 postpaid.
 - CP/M 2.0 ... \$150 postpaid.
 - Microsoft BASIC ... \$325 postpaid.
 - Intel 8085 cpu User Manual ... \$7.50 postpaid.
 - Level "A" Monitor Source Listing ... \$25 postpaid.

Continental U.S.A. Credit Card Buyers Outside Connecticut
CALL TOLL FREE: 800-243-7428

To Order From Connecticut Or For Technical Assistance, call (203) 354-9375

Total Enclosed (Conn res. add sales tax) \$ _____
Paid By: _____
 Personal Check Cashier's Check/Money Order
 VISA Master Charge (Bank No. _____)
Acct. No. _____ Exp. Date _____
Signature _____
Print Name _____
Address _____
City _____
State _____ Zip _____

NETRONICS Research & Development Ltd.
333 Litchfield Road, New Milford, CT 06776

SAVE TIME AND MONEY!

6100

UNIVERSAL DESIGNER

- Save on digital bread boarding
- Easy transition from prototype to wiring diagrams
- Aids digital circuit design

Kit \$49.95

Assembled \$59.95

SELF-TEACHING AID:

6101 DIGITAL LOGIC COURSE \$29.95

- Learn digital logic with 26 self teaching experiments.

0101 SOLID STATE CLOCK/CALENDAR UNIT

BIG 2½" DISPLAY!

- 12/24 hour selectable
- Alarm output

Kit \$49.95

Assembled \$79.95

Oak Case \$29.95

Satisfaction Guaranteed on All Assembled Units

FOR FAST DELIVERY CALL TOLL-FREE EXT. 11
1-800-426-6254

14905 N.E. 40TH, DEPT RE1
 REDMOND, WA 98052 (206) 883-9200

- Please rush me the following:
- | | |
|--|---------|
| <input type="checkbox"/> 6100 UNIVERSAL DESIGNER KIT | \$49.95 |
| <input type="checkbox"/> 6100 UNIVERSAL DESIGNER ASSEMBLED | \$59.95 |
| <input type="checkbox"/> 6101 DIGITAL LOGIC COURSE | \$29.95 |
| <input type="checkbox"/> 0101 CLOCK/CALENDAR KIT | \$49.95 |
| <input type="checkbox"/> 0101 CLOCK/CALENDAR ASSEMBLED | \$79.95 |
| <input type="checkbox"/> OAK CASE | \$29.95 |

ADD \$3.00 PER ORDER POSTAGE & HANDLING

NAME _____

ADDRESS _____

CITY _____ ST _____ ZIP _____


CREDIT CARD NO _____ EXP _____

SIGNATURE _____ VISA MASTERCARD

CIRCLE 8 ON FREE INFORMATION CARD

Put Professional Knowledge and a COLLEGE DEGREE in your Electronics Career through

HOME STUDY

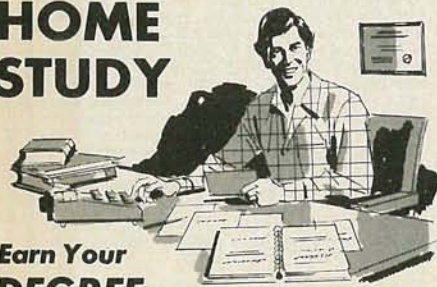

Earn Your DEGREE

No commuting to class. Study at your own pace, while continuing your present job. Learn from easy-to-understand lessons, with help from your home-study instructors whenever you need it.

In the Grantham electronics program, you first earn your A.S.E.T. degree, and then your B.S.E.T. These degrees are accredited by the Accrediting Commission of the National Home Study Council.

Our free bulletin gives full details of the home-study program, the degrees awarded, and the requirements for each degree. Write for *Bulletin R-81*.

Grantham College of Engineering
 2500 So. LaCienega Blvd.

70 Los Angeles, California 90034

HOBBY CORNER

continued from page 68

winner of another.

Two methods of triggering the circuits predominate. About half of the respondents use photocells or phototransistors to detect the car's passage over the finish line. D. R. Fair of Center Valley, PA indicates that a pencil-shaped car may not consistently activate such a trigger. Paul Bradley (Sterling Heights, MI) sent a circuit with trimmer pots on each photo device to adjust them for ambient light conditions.

Mechanical switches are used to trigger circuits by many of you. In some cases, leaf-actuated switches are imbedded in the track. Anthony Saxton of Burnsville, MN mounts his micro-switches behind rubber pads at the end of the track.

As mentioned, the actual circuits varied from mechanical relays to 60-device electronic masterpieces. They can give first place only, first three places, arbitrary or accurate time.

Quite obviously, choices must be made about each of these variables. I suggest to Bill and others that cost and complexity be secondary considerations. Decide first what you *need* and what you *want* in terms of final result. Then plan and build accordingly.

I hope that the discussion above will give you plenty of ideas and food for thought. Space will permit only one reader circuit now. I'll include one or two more soon. By then, you should be ready to start construction. The circuits presented will be chosen to illustrate some of the different approaches, not necessarily because they are better than all the others that were sent in.

Perhaps the simplest circuit was one sent in by Saxton. He uses mechanical switches and relays to pick winner only. Anthony says it has the dual advantage of sufficient accuracy and no overkill.

Figure 2 shows two double-pole relays in a two lane system. Figure 3 shows how three 3-pole relays are connected for a three-lane system. In that same manner, you can expand the setup for any number of lanes. For example, six lanes would require six 6-pole relays. (Any surplus telephone relays out there?) Let's see how Anthony's circuit operates for two lanes (Fig. 2) and then you can figure out any larger one you want.

Suppose the car on Lane 1 flips that momentary switch first. The circuit is complete through lamp L1 and through the coil of relay RY1 via the closed RY2-b contacts. Thus, relay RY1 is energized and that does two things: It closes contacts RY1-a to keep current flowing through L1 and relay RY1 and it also opens contacts RY1-b. In that manner, lamp L1 comes on and stays on.

Now, the second car hits the momentary switch in Lane 2. The circuit to coil

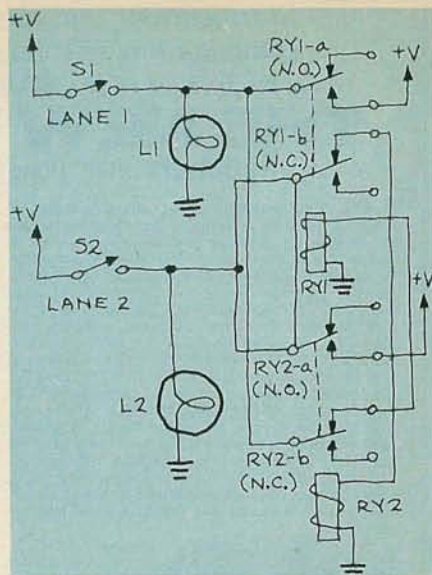


FIG. 2

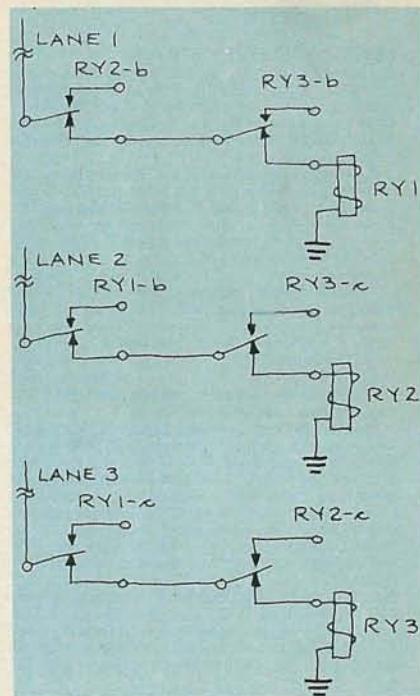


FIG. 3

of relay RY2 is *not* completed because the RY1-a contacts are now open. Thus, relay RY2 does not energize and contacts RY2-a stay open. Since contacts RY2-a are open, lamp L2 does not stay on—it only flashes briefly when the Lane-2 switch is hit.

Of course, if the Lane-2 car is faster, the sequence of events is opposite and lamp L2 lights to the exclusion of L1. A three (or more) lane setup works in the same way and indicates the winner only.

I have given no values for supply voltage, relays, or lamps. The only requirement is that they match. You can even use AC and avoid the need for a power supply.

Next month we'll look at an electronic solution to the problem and talk about some other uses for these circuits. **R-E**

NOW! A MINIATURE TELEPHONICS SYSTEM
EVEN MA BELL DOESN'T MAKE AVAILABLE.

FINGER FONE™

The unique Finger Fone brings you advanced solid-state wizardry with a simple yet intelligent approach to using a telephone. It's the ideal communications instrument for home and office.

Imagine you're a design engineer. You've just been assigned to come up with a smaller, simpler-to-use, more streamlined telephone with basic memory that can handle 99% of the ways people actually use a phone on a day-to-day basis.

You have a research laboratory with a support staff at your disposal. Plus access to the latest transistors, memory chips, and microprocessors. And you are given only one limitation: Keep the consumer's cost under \$100.

Now, since you're something of a maverick, your mind is not trapped in the right way/wrong way syndrome. And you were too independent to take that job with the Bell System a while back. Because you didn't want all your ideas to come out "Bell-shaped."

THE ANATOMY OF DESIGN

So you set to work — but not with wires, bells and whistles. Because your approach is different: You're going to discover how people actually use a telephone today and then design the instrument from the outside in, basing your conception around real communication needs in a way quite unlike anything ever before achieved.

INTRODUCING THE FINGER FONE

When you're finished, you realize you've come up with a minor revolution in design! Your new instrument is actually a miniature telephone: the entire unit measures a scant 2¾" wide, 8¾" long, and 2¾" high (at the speaker end), scarcely any bigger than the handset on an ordinary phone. Your Finger Fone has a nearly standard alphanumeric keyboard plus a couple of special benefits we'll get to in a minute. It also has an omnidirectional microphone, volume selector key, automatically control the volume of incoming voices, with four LED indicator lamps to display each volume level, and even a bright red on-off light.

What's more, it plugs into the new miniconnector Ma Bell provides for all its phones these days — with no additional wires for any other power source (which make the Finger Fone unlike those other multi-wire "speaker-phones" that sell for more but do less).



© MERCURY 1980

Finger Fone: modular, sophisticated, smarter than your present telephone. Comes with an ivory fascia.

WHY PICK A PHONE UP EVERY TIME IT RINGS?

Let's face it, your hands are often occupied when the phone rings. So to answer, you've got to stop at least half of what you're doing. With a Finger Fone, all you do is reach out and tap the "On" key with one finger. And since you needn't pick the instrument up, you can place it conveniently on a desk, counter, or table — or hang it on the wall.

MORE FINGERTIP CONVENIENCE

When Finger Fone announces an incoming call with its pleasant electronic chirp, tap the "On" key and begin speaking. If the caller is someone the whole family wants to hear, simply tap the volume control key and select one of the four sound levels and your caller's voice will be audible to everyone in the room. This benefit is great for the office as well, making it possible to replace an ordinary telephone, separate speakerphone, and their complicated controls.

If you wish to speak with complete privacy, press the volume control key for low level volume. Yes, for strictly private calls you'll have to hold Finger Fone up to your ear. You won't mind, however, because the entire unit is a mere 11¼ ounces, just a featherweight more than ordinary telephone handsets.

YOU HEAR THEM, THEY DON'T HEAR YOU

Need to put your caller on "hold" for a moment? Easy. Tap "hold" key. All five LED indicator lamps will be blinking, indicating your caller is on hold. The other person won't be able to hear you, but you'll be able to hear him or her. We recommend you tell people about this so they don't make unguarded comments they think you can't hear. When you're ready to resume your call, simply tap "off" key, the LED lights will stop blinking, and you can continue.

BUSY SIGNAL? FORGET IT!

Because Finger Fone automatically remembers the most recently dialed "busy" number. When you want to call that number again, tap the "RE" (Recall) key once. Finger Fone dials the number for you, as often as needed until you get a clear line.

WHY WAIT FOR PUSH BUTTON DIALING?

Finger Fone is compatible in areas of the country where push-button dialing is already in use. But if you live in the 30% or so of the country where only rotary-dial phones can be used, wait no longer. Finger Fone automatically converts from musical tones to rotary-dial signals. This way, you can have the speed and advantages of push-button dialing without waiting for your local phone company to install central equipment.

NOW AVAILABLE AT INCREDIBLE LOW COST

Finger Fone costs only **\$89.95** compared with prices of similar-looking telephones (but not similar in performance) costing \$109, \$130 or more. Want two? Then it's only **\$84.95** each. Three? Save even more at **\$82.95** each. Add a **\$2.50** charge to your total order for insured shipping, and if you live in New Jersey, include 5% tax.

MONEY-BACK GUARANTEE

You can try one or more Finger Fones in your own home for 30 days, protected by our unconditional money-back guarantee. If you're not satisfied with Finger Fone for any reason, simply return it (insured) for a full refund, no questions asked. Finger Fone is also covered by a 1-year parts and labor guarantee.

To order Finger Fone, call toll-free now. We're open 24 hours a day. You can charge it on Master Charge, Visa, American Express, Carte Blanche or Diners.

800-526-2801

800-257-7850

In New Jersey, Call: 800-322-8650

N.J. residents please add 5% sales tax. You can also mail your order with check or money order to:

MERCURY
INTERNATIONAL SALES GROUP
THE IMAGINATION PEOPLE®

Dept. RE-1
Mercury Bldg., 404 Madison Avenue
Lakewood, N.J. 08701

CIRCLE 16 ON FREE INFORMATION CARD

JANUARY 1981


71

fact:
five new Shure Cartridges
feature the technological
breakthroughs of the V15
Type IV

the
M97
Era IV
Series
phono
cartridges




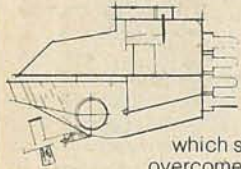Shure has written a new chapter in the history of affordable hi-fi by making the space-age technological breakthroughs of the incomparable V15 Type IV available in a complete line of high-performance, moderately-priced cartridges: the M97 Era IV Series Phono Cartridges, available with five different interchangeable stylus configurations to fit every system and every budget.



Dynamic Stabilizer—which simultaneously overcomes record-warp caused problems, provides electrostatic neutralization of the record surface, and effectively removes dust and lint from the record.

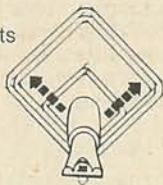
SIDE-GUARD, which responds to side thrusts on the stylus by withdrawing the entire stylus shank and tip safely into the stylus housing before it can bend.



And, the unique telescoped stylus assembly which results in lower effective stylus mass and dramatically improved trackability.

There is even an M97 cartridge that offers the low distortion Hyperelliptical stylus!

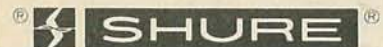NEW! M97 Series Era IV Phono Cartridges... Five new invitations to the new era in hi-fi.




Shure Brothers Inc., 222 Hartrey Ave., Evanston, IL 60204.
 In Canada: A.C. Simmonds & Sons Limited
 Outside the U.S. or Canada, write to Shure Brothers Inc., Attn: Dept. J6 for information on your local Shure distributor.
 Manufacturers of high fidelity components, microphones, sound systems and related circuitry.

CIRCLE 56 ON FREE INFORMATION CARD

new products

More information on new products is available. Use the Free Information Card inside the back cover.

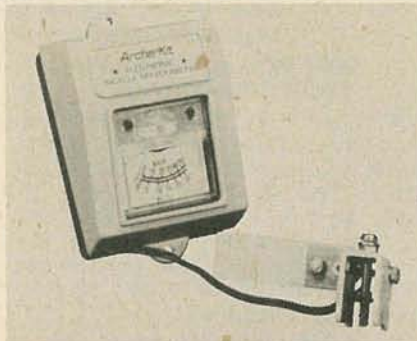
ARCHERKIT, ELECTRONIC BICYCLE SPEED-OMETER, is a kit designed to fit most bikes and has 1/2-inch dual-scale 0 to 60 kilometers-per-hour and 0 to 30 miles-per-hour indication. The unit operates on one 9-volt battery. The speed-



CIRCLE 151 ON FREE INFORMATION CARD

ometer has a rugged 4 x 2 1/2 x 2-inch molded housing and comes complete with mounting bracket, hardware, and step-by-step assembly instructions. Price is \$14.95.—**Radio Shack**, 1300 One Tandy Ctr., Fort Worth, TX 76102.

OSCILLOSCOPE/COMPONENT TESTER, model HM307, is a compact, lightweight single-trace oscilloscope designed for both field service and laboratory applications. It has a built-in component tester that tests common semiconductors and passive components in circuit. (Transistors, diodes, resistors, capacitors, and most other components can be checked.) The model HM307 changes from an oscilloscope to a component tester with the press of a single button while the oscilloscope settings are left undisturbed.

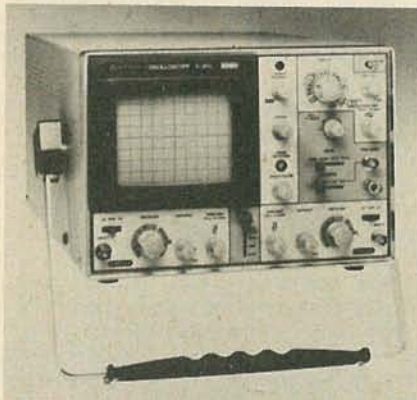

CIRCLE 152 ON FREE INFORMATION CARD

The component tester applies ± 8.6 volts RMS maximum to the device with current limiting to 28 mA; the resulting V/I display instantly reveals most bad semiconductors. No drift compensation is needed, and the model HM307 will trigger on signals as small as 3mV up to 30 MHz. Vertical sensitivity ranges from 5 mV to 20 V/cm in 12 calibrated steps. The time base is from 2 seconds to 0.2 μ sec/cm with auto and external triggering

that ranges from 2 Hz to 30 MHz.

All critical DC voltages are regulated. The input AC transformer can be connected to operate from 110 to 237 volts AC, 50 to 60 Hz. The built-in 1 kHz, 0.2-volt ($\pm 1\%$) squarewave generator is used for checking probe compensation. The model HM307 comes housed in an all-metal low-profile case—4.5 x 8.3 x 10.4 in.—designed for rugged field-service use. There is a handy carry handle and retractable tilt-up stand that pulls down from under the unit. Accessories include x1 probes, x10 probes, x100 probes, demodulator probes, test cables, viewing hood, carrying case, and scope chart. Price \$405.00.—**Hameg, Inc.**, 191 Main Street, Port Washington, NY 11050.

MINIATURE SPEAKER, model S100RA, measures 1 x 3/4 in. and weighs 15.2 grams. The fully-enclosed Alnico magnet weighs 0.209 oz. Nominal power is 0.2 watt and frequency response is 750-10,000 Hz. Voice-coil impedance is 8 ohms but may be varied upon special request.

The S100RA is designed for small-space applications such as in beepers, mobile telecommunications devices, portable medical equipment,



CIRCLE 153 ON FREE INFORMATION CARD

walkie-talkies, and headphones. Cone material is paper and the frame is cadmium-plated steel. Price \$1.00.—**Intervox Speakers**, International Components Corporation, 105 Maxess Road, Melville, NY 11747.

PHASE METER, model 200, has a 0-360° mode for lagging test signals or a $\pm 180^\circ$ mode for signals whose phase relationships vary around zero. The input-voltage range is 35 mV to 250 volts RMS. Input impedance is 1 megohm for all input levels. Frequency range for a 35-mV RMS signal is 20 Hz to 300 kHz, with $\pm 2^\circ$ accuracy over that range. Front-panel calibration controls can also



CIRCLE 154 ON FREE INFORMATION CARD

be used to offset any phase shift in the test setup. Display is three digits, plus sign. An analog output provides 10 mV per degree. Price \$325.—**FSI**, 1894 Commerceter W. No. 105, San Bernardino, CA 92408.


R-E

PLANT WATER GAUGE


THIS PLANT WATER GAUGE CAN EASILY BE constructed on a small piece of perforated construction board. Its case is made from a piece of Styrofoam with a section carved out to hold the nine-volt battery, and a small recess is made into which the underside of the board is pressed. The probes are stuck right through the center of the foam and glued in.

Assemble the gauge following the schematic in Fig. 1 and the drawing in Fig. 2. Be sure to tin the probes with solder to keep them from corroding.

To calibrate the gauge, connect the battery and press the probes gently into a pot containing a plant that is just on the verge of needing water (stick it in so that only an inch of the probe is left visible at the top). Turn the potentiometer until the "OK" LED lights and then turn it back to the point where that LED goes out and the "W," or "Water," LED just comes on. The device should now be properly adjusted.

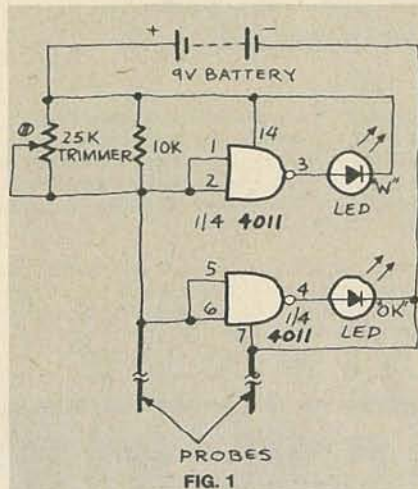

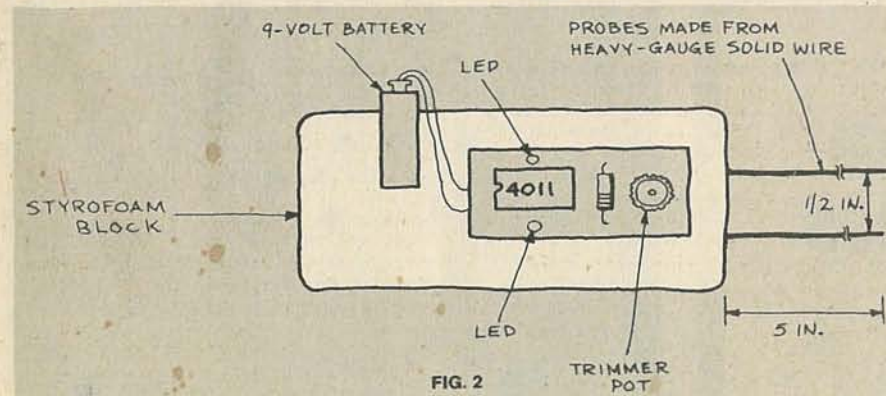
Use this gauge anywhere for indoor plants and you will find it very useful in determining when to water and in preventing overwatering, since it reaches much farther down into the soil than you possibly can with your own fingers.—*Bob Mostafapour*



NEW IDEAS

This column is devoted to new ideas, circuits, device applications, construction techniques, helpful hints, etc.

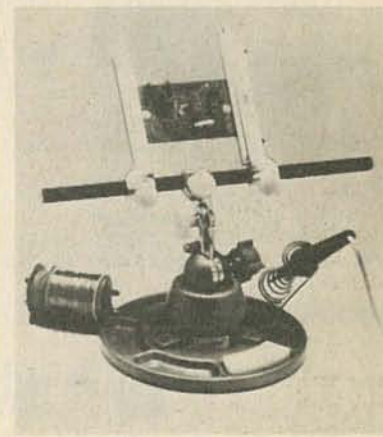All published entries, upon publication, will earn \$25. In addition, Panavise will donate their model 324 Electronic Work Center, having a value of \$49.95. It combines their circuit-board holder, tray base mount, and solder station (see photo below). Selections will be made at the sole discretion of the editorial staff of **Radio-Electronics**.



I agree to the above terms, and grant **Radio-Electronics Magazine** the right to publish my idea and to subsequently republish my idea in collections or compilations of reprints of similar articles. I declare that the attached idea is my own original material and that its publication does not violate any other copyright. I also declare that this material had not been previously published.

Title of Idea

Signature

Print Name

Date

Street

City

State

ZIP

Mail your idea along with this coupon to: **New Ideas Radio-Electronics**,
200 Park Ave. South,
New York, NY 10003

computer products

More information on computer products is available.
Use the Free Information Card inside the back cover.

MICROCOMPUTER WORK STATION, the *CompuDesk*, features a split-level top for optimum positioning of components of a microcomputer




CIRCLE 121 ON FREE INFORMATION CARD

system. It has a compartment with two adjustable shelves and a self-closing door with an attached storage rack for manuals and magazines. The compartment is convection-cooled and a fan

option is offered for high-heat systems. The *CompuDesk* is constructed of birch plywood with a walnut stain finish and formica tops. Price is \$359, plus freight and a \$25 packing charge where applicable.—**ComputerGoods**, P.O. Box 2635, Eugene, OR 97402.

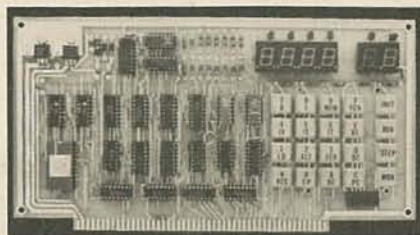S-100 FRONT PANEL for use with 8080 or Z-80 systems features a 20-key matrix and six-digit LED display. The keytops may be ordered blank or with lettering. The *S-100 Front Panel* comes with 256 bytes of RAM and is equipped to take a 2708 or 2716 EPROM, which may be pro-



CIRCLE 122 ON FREE INFORMATION CARD

grammed by the user to meet his particular requirements.

Pre-programmed EPROM's for working in machine language and engraved keyboards are available for either 8080 or Z-80 systems.

Price for a board with blank keytops and less EPROM is \$139.50, assembled and tested. Add \$55 for 8080 or Z-80 firmware.—**Pike Electronics**, 8190 Watsonville Rd., Gilroy, CA 95020.

INTERFACE ADAPTOR, model 488-80B, is designed for interfacing the *GPIB-488* to the Radio Shack *TRS-80 Model I* computer. Any *TRS-80 Model I* with a minimum of 16K RAM and Level II



CIRCLE 123 ON FREE INFORMATION CARD

BASIC can connect to as many as 15 *GPIB-488* peripherals with no extra hardware ports or software drivers required as new devices are added. Peripherals currently available include printers, plotters, digitizers, displays, and measurement and test equipment. A machine-level driver pro-

What would make your business better? We would

You've seen what franchising did for real estate. Franchise companies took struggling independent realtors and put them in the limelight. The result: a greater share of the marketplace.

TRONICS 2000 is doing the same for the electronics service business. We're selecting a limited number of dealers in each community, giving them our name and high-level training in administrative and marketing techniques. And we're advertising as a single organization. In short, we're building a franchise organization that will stand out in a crowd.

Are you eligible to join? Yes, if you own a service dealership or are planning to start one and if you meet our technical requirements. But you must apply before the quota for your area has been filled.

TRONICS 2000 could be the lifeline you've been looking for. Call us. Today. Toll free 1•800•457•4507. In Indiana 1•800•822•4763.

tronics2000

5229 South Highway 57 • P.O. Box 2003 • Bloomington, Indiana 47402 • 812/824-2424

Unless you operate a tracking station for deep-space probes

YOUR BEST BET AMONG ALL-WAVE RECEIVING ANTENNAS IS THE NEW IMPROVED COMPACT OUTDOOR MCKAY DYMEK DA100D

Rooftop, balcony, anywhere outdoors... this tough little four-footer gives very high performance in limited space. Makes most receivers come in better. Equals, and very often outperforms, longwire antennas. For convenience, price, quality, performance... **MCKAY DYMEK DA100** is the name to remember.

add \$5.00 for shipping
calif residents—add 6%
sales tax

For \$139.00 you get:

- lifetime, nonmetallic outdoor case
- neat, newly-designed indoor control
- wide range 50 to 30,000 kHz
- shielded, potted amplifier
- 110-240VAC or 12VDC
- attenuator switch to prevent RF overload
- satisfaction of joining thousands of enthusiastic owners worldwide
 - 30-day trial option
 - plus a dozen or more other features



BUY FACTORY DIRECT • ORDER NOW

MK MCKAY DYMEK CO
111 So College Ave.
P O Box 5000
Claremont, CA 91711



CALL TOLL FREE
800 / 854-7769
Except Calif, Alaska, Hawaii
Local 714/621-6711
TWX 910-581-4990

HIGH STABILITY CRYSTALS FOR FREQUENCY OR TIME USE THE BEST BUY JAN CRYSTALS

- CB
 - CB standard
 - 2 meter
 - Scanners
 - Amateur Bands
 - General Communication
 - Industry
 - Marine VHF
 - Micro processor crystals
- Send 10¢ for our latest catalog.
Write or phone for more details.

Jan Crystals
2400 Crystal Drive
Ft. Myers, Florida 33907
all phones (813) 936-2397
easy to charge



CIRCLE 19 ON FREE INFORMATION CARD

gram provided with this model, on tape or disk, interacts with Level II BASIC, Level III BASIC and Disk BASIC. Price is \$225.00.—Scientific Engineering Laboratories, 11 Neil Dr., Old Bethpage, NY 11804.

MAGNETIC TAPE ERASER, model 24-001, is designed to erase computer cassettes and floppy disks. The device was originally designed to erase video tapes. To operate, the user sweeps the unit over the disk or cassette from which signals are to be removed. The unit's magnetic field then



CIRCLE 124 ON FREE INFORMATION CARD

wipes clean the recorded signals. Measures 5 × 3½ inches and weighs 4 lbs. The model 24-001 operates from a power source of 110 to 120 volts AC and is designed for intermittent duty. The suggested retail price is \$58.50.—Robins Industries Corp., 75 Austin Blvd., Commack, NY 11725. R-E

ILP AUDIO MODULES



- Built-in heatsinks
- Protected circuitry
- No external parts required
- 5 connections
- 5 year warranty!

HY50 Amplifier 30 WATTS RMS \$28.95

High performance amp with rugged aluminum heat-sinks. Measure only 4" × 2" × 1" thick! Mounts with 2 screws. Gives 30 watts RMS at 0.02% distortion. Response 10 — 45 KHz. 4 to 16 ohms. ±25 V/2A.

HY30. 15 watts RMS. Size/specs as HY50. 20 V/2A. 25.95

HY200 Amplifier 120 WATTS RMS \$79.95

High performance amplifier with large heatsink area for cool operation. Fully protected circuitry. Distortion only 0.01% at 120 watts RMS (1 KHz). Response 10 Hz — 45 KHz. S/N ratio 100 db. Only five connections. Amazingly compact — only 4½" × 4" × 2" D. Mounts with 2 screws. Requires ±45 V/3A. 4 to 16 ohms. HY120. 60 W RMS. Specs/size as HY200. ±35 V/2A 59.95

HY400. 240 Watts RMS (4 ohm). Double the power, double heatsink area! Same specs as HY120/200. May be used into 8 ohms at reduced output. ±45 V/4A \$99.95

HY6 Mono Preamp \$25.95

HY66 Stereo Preamp 48.95

Inputs for RIAA phono, tape with monitor, tuner, auxiliary and microphone; full tone control circuitry. Incredible performance: Response DC to 100 KHz, distortion 0.05%, S/N 90 db. Output to 4.5 V RMS. Supplied with edge connectors. Compact. Reliable. Internal voltage regulation — use from 15 to 50 V safely!

Name _____
Address _____
City _____ Zip _____
Please send _____ Amt. _____
Check () M/O () Visa () M/C ()
Number _____ Exp. _____
GLADSTONE Electronics (716) 849-0735
901 Fuhrmann Blvd., Buffalo, N.Y. 14203

CIRCLE 44 ON FREE INFORMATION CARD

HICKOK
the value innovator



Model 333
Model 331

DMM + Vari-Pitch + Logi-Trax = MX-333 World's Fastest Troubleshooter

- 0.1% Basic Accuracy
- LCD Display In Unique Wide Vue Case
- Uses Single 9V Battery
- Compact Size. Rugged Construction
- Overload Protection
- Exclusive VARI-PITCH Audible Output (MX333)
- Fast LOGI-TRAK Logic Function (MX333)
- 20Ω Range (MX333)

... plus these popular sellers in stock and available for immediate delivery.



Compact Video Generator

- Video output for VTR, CCTV and monitor applications
- Adjustable RF channel 2-4
- 11 rock stable patterns • 10 step gray scale staircase • 3 bar and 10 bar gated rainbows
- Adjustable chroma levels (0-150%) • Crystal controlled chroma and timing oscillators for stability from 20' to 125'
- Rugged high impact thermoplastic case and protective cover.


Model 240



Pocket Semiconductor Analyzer

- Automatic, "hands-off" operation — frees both hands for troubleshooting. • Instant GOOD-BAD analysis — including LEAKAGE — of NPN's, PNP's, FET's, diodes & SCR's; in or out-of-circuit. • Rugged, all solid state — no moving parts. • Compact polypropylene case. • Will not damage transistors, diodes, or circuits under test. • Powered by 2 std. 9 V batteries (not inc.)

Model 216

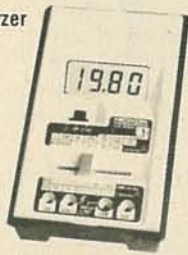

LCD Digital Multimeter

- Automatic polarity, zero and overrange indication
- Easy-to-read 1½" high L.C.D. display
- 1½ year battery life in typical use
- 12 oz. including 9V battery
- Withstands 4 ft. drop without loss of accuracy
- Automatic decimal point, built in low battery indicator, diode and transistor testing capability (LX304 only)

LX 304 LX 303

Order with Confidence and get the Fordham Advantage!

Call for our prices **TOLL FREE**
(800) 645-9518
in N.Y. State call (516) 752-0050

FORDHAM
855 Conklin St. Farmingdale, N.Y. 11735



CIRCLE 41 ON FREE INFORMATION CARD

AMERICA'S BEST SELLING SCANNER JUST GOT EVEN BETTER.

Look what you get with the Bearcat 210XL. Exciting, new space-age styling. No-crystal, pushbutton tuning. New, 18 channel, 6-band coverage of over 6000 frequencies. And features like 2 scan speeds, Automatic Squelch, Search, and Lockout, Direct Channel Access, Selective Scan Delay. And much more. There's never been a Scanner like the Bearcat 210XL.



**"TAKE IT FROM A
SMART OPERATOR."**

Don Adams
**BEARCAT 210XL
SCANNER
\$209.**

THE LOWEST PRICED, FULL-FEATURE, BEARCAT NO-CRYSTAL SCANNER EVER.

Bring home all the real excitement of scanning, and save! Bearcat 160 features a smooth, keyless keyboard for all controls including volume and squelch. Has 5-band, 16 channel coverage. Priority, Selective Scan Delay, Automatic Lockout and Search. And much more. Bearcat is number one in scanning.

**"TAKE IT FROM A
SMART
OPERATOR."**

Don Adams
**BEARCAT
160 SCANNER
\$189.00**



Add \$6.00 per scanner for U.P.S. ground shipping in the continental U.S. or \$12.00 for U.P.S. air shipping. Send your cashier's check or money order to our address below or order by phone if you have a Visa or Master Charge card. Order today!

RADIO-ELECTRONICS

**COMMUNICATIONS
ELECTRONICS™**


854 Phoenix □ Box 1002 □ Ann Arbor, Michigan 48106 U.S.A.
Call TOLL-FREE (800) 521-4414 or outside U.S.A. (313) 994-4444

CIRCLE 61 ON FREE INFORMATION CARD

radio products

More information on radio products is available. Use the Free Information Card inside the back cover.

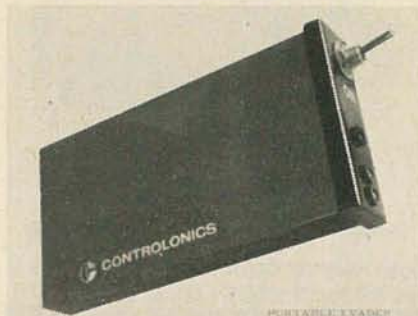
PORTABLE SCRAMBLER, the *Evader*, ensures privacy in two-way radio voice communications. A primary security-level scrambler, the portable *Evader* is compact and mounts directly on the radio using "hook-and-loop" pads. The rugged, water-resistant unit operates from the radio's



CIRCLE 111 ON FREE INFORMATION CARD

power supply. A standard-designation code module is internally wired. The scrambler principle used is audio-band inversion with the code module selecting the inversion frequency. This portable unit is compatible in all codes with all basic *Evader* models. Price is \$547.—**Controlonics Corp.**, 410 Great Road, Littleton, MA 01460.

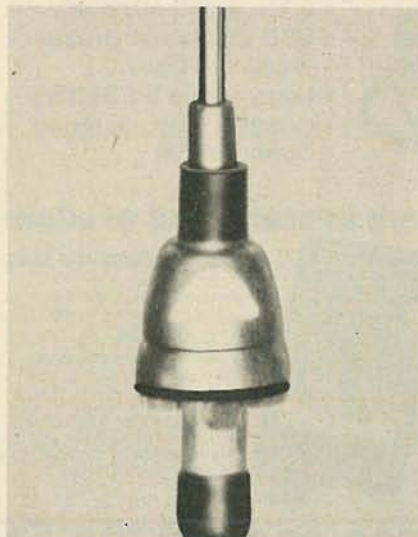CUSTOM ANTENNA, FM-91, fits all General Motors and narrow-fender cars. The antenna has a single stainless-steel mast 31 inches long and a 72-inch cable. Shown is a close-up of the anten-



CIRCLE 112 ON FREE INFORMATION CARD

na's body-mount. Price for the *FM-91* is \$7.37.—**Harada Industry of America, Inc.**, Dept. P, W. Artesia Blvd., Compton, CA 90220.


COMPACT AM/SW RECEIVER, the model *EP-8*, measures only 45 mm × 73 mm × 25 mm (1.77 × 2.95 × 0.98 inches) and weighs only 96 grams



CIRCLE 113 ON FREE INFORMATION CARD

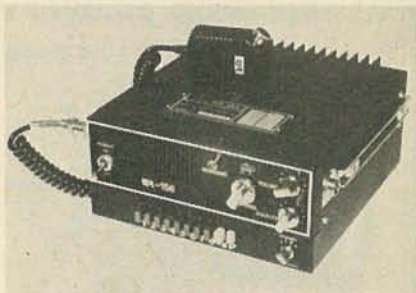(3.5 oz.). The receiver tunes the standard AM broadcast band and shortwave frequencies from 3.9 to 12 MHz. Controls include a BAND SELECT switch, tuning dial, and a volume control coupled with an on/off switch. Power is supplied by two hearing-aid-type batteries (included). The *EP-8* has built-in *Ferrite* rod antennas for both bands. Audio output is by means of an earphone. Price is \$24.95.—**Radios International**, P.O. Box 6053, Richardson, TX 75080.

VHF/FM TRANSCEIVER, model *WR 156*, is a front-mount radio with a frequency range of 150-174 MHz and a frequency spread of 12 MHz. Twelve channels of any TX or RX frequency combination can be programmed with the 12-MHz spread, with full specs eliminating the need for




CIRCLE 114 ON FREE INFORMATION CARD

two separate radios. The performance of each channel in this model is equal to that of a single channel radio. Options available for the *WR-156* include a 12-channel priority scanner, CTCSS encode/decode, DTMF, and time-out timer, plus any signaling system desired. Price range is from \$1,395 to \$2,350.—**WR Communications**, 1165 Harrison St., Seattle, WA 98109. **R-E**

stereo products

More information on stereo products is available.
Use the Free Information Card inside the back cover.

SPEAKER-SELECTOR SWITCH, *The Controller*, is a lightweight, compact unit that allows hookup and independent control of up to five pairs of stereo speakers. Any one pair or up to all five can be played simultaneously. Features include two headphone jacks, built-in amplifier protection, and barrier-type terminals for amp and speaker connections to help prevent short circuits. *The Controller* is compatible with all hi-fi amps, receivers, and headphones that operate into 4-ohms impedance; with a rating of 50 watts contin-

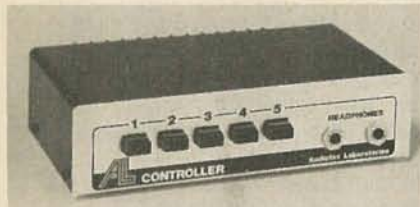

CIRCLE 131 ON FREE INFORMATION CARD

uous per channel, its power is unlimited with the load switch off. Suggested retail price is \$49.50.—**GC Electronics**, 400 So. Wyman St., Rockford, IL 61101.

CLEANING KIT, *model TX250*, is designed for cleaning audio-tape heads, and features *Audio Cleaning Pens*—one for pressure rollers, and one for heads. Each pen holds a *Clean-Wick* that can be cut to the shape needed for each task. The kit



CIRCLE 132 ON FREE INFORMATION CARD

also contains the solvent, ten replacement *Clean-Wicks*, a cutter, a device that elevates the pressure rollers for cleaning, and a rack for the kit materials. Good for about 900 cleanings, the kit is priced at \$27.50.—**Texwipe Co.**, 101 West St., Hillsdale, NJ 07642.


NOISE-REDUCTION SYSTEM, *model SAE 5000A*, removes impulse noises from records. The *SAE 5000A* is capable of removing even smaller pops and clicks than its predecessor while providing a cleaner sound than was previously attainable. Sophisticated logic circuits continually monitor the program material for those audio defects and automatically shut down the audio system upon detection of the impulses. A reconstruction circuit replaces the impulse noise with information extrapolated from the music appearing immediately before and after the impulse so that musical continuity is maintained. Since the entire process takes place in less than



CIRCLE 133 ON FREE INFORMATION CARD

$\frac{1}{1000}$ of a second, the listener remains unaware of it. Both THD and IM in the *SAE 5000A* are rated at less than 0.1%. Signal-to-noise ratio is greater than 90 dB and frequency response is 20 Hz to 20 KHz ± 1 dB. Suggested retail price of the *SAE 5000A* is \$225.—**Scientific Audio Electronics, Inc.**, 701 E. Macey St., Los Angeles, CA 90012.

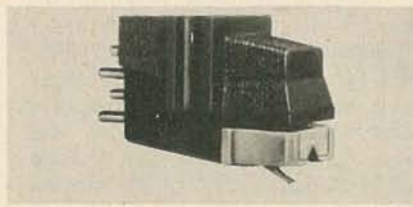STEREO CARTRIDGES, *model M72EJ* and *model M72B*, feature a new stylus assembly with a reduced tip mass that results in high-trackability performance. The cartridges have a tracking-force range of from 1½ to 3 grams, and are compatible with most turntables. The *model M72EJ* (shown), with biradial elliptical stylus is priced at \$51.00; *Model M72B* with spherical stylus is



CIRCLE 134 ON FREE INFORMATION CARD

\$45.70. Prices for stylus assembly alone are: *N72EJ* \$17.45; *N72B* \$14.05.—**Shure Bros., Inc.**, 222 Hartrey Ave., Evanston, IL 60204.

RECEIVER, the *STA-2000*, offers quartz-locked digitally synthesized AM/FM *Dolby* reception. It can scan the entire FM or AM band, stopping automatically, perfectly tuned, at each station. Its fluorescent readout displays the exact station frequency and also serves as a digital clock when the receiver is not in use. Any six FM and any six AM stations may be entered in the receiver's memory for instant access at the touch of a button. A SCAN button makes the microprocessor sample the programming on each station in the



CIRCLE 135 ON FREE INFORMATION CARD

memory for a few seconds, and stops at the touch of the HOLD button. The *STA-2000* is rated at 60 watts-per-channel and carries a price tag of \$599.95.—**Radio Shack**, One Tandy Center, Fort Worth, TX 76102. **R-E**



NOW YOU CAN BUILD YOURSELF AN ORCHESTRA

The most advanced — most versatile organ you ever dreamed of is now within most everyone's reach . . . because you build it yourself the exclusive WERSI way.

Expand your instrument according to your taste and budget. With WERSI's 'Building Block' system, you'll never need to trade organs again!

Superior WERSI quality also available in pianos, synthesizers, amps, rhythm units, etc. . . . kit or factory assembled.

Send \$6 for the exciting Sight and Sound package everyone raves about. You'll receive the famous "WERSITIME 2" 12" LP with accompanying libretto as well as a full color, 104 page manual, widely acclaimed as the encyclopedia of organ builders, introducing you to the Wonderful World of

WERSI world leader in quality do-it-yourself instruments

WERSI ELECTRONICS, INC. Dept. M4
P. O. Box 5318, 1720 Hempstead Road
Lancaster, PA 17601

Please send above demo pack @ \$6.00.

Name _____

Address _____

City _____ State _____ Zip _____

CIRCLE 20 ON FREE INFORMATION CARD

CREATE ANY RHYTHM

new improved memory



Our popular Programmable Drum Set's simple programming system allows even first time users to structure bass, tom, snare, wood-block and clave sounds into any rhythm in any time signature. Versatile memory organization provides simultaneous storage of two separate rhythm patterns each with its own bridge rhythm. Bridges are activated from either the control panel touch plate or optional foot switch and are automatically synchronized to the main rhythm. Improved memory circuitry lets the "save" mode hold rhythm patterns for over one year while battery life for normal operation has been extended to several hundred hours.

In easy to assemble kit or fully assembled.

Send #3750 Drum Set Kit, \$89.95 plus \$3 shipping enclosed.

Send #3750 Drum Set Assembled, \$154.95 plus \$3 shipping enclosed.

Send Free Catalog.

Name: _____

Address: _____

City: _____ State: _____ Zip: _____

VISA: _____ MC: _____ Card No. _____

WERSI ELECTRONICS, DEPT. 1 R, 1020 W. WILSHIRE, OKLA CITY, OK 73116

CIRCLE 55 ON FREE INFORMATION CARD

Catastrophic failures in solid-state circuits can be a troubleshooter's nightmare.

JACK DARR, SERVICE EDITOR

MOST OF US ARE ALL TOO FAMILIAR WITH the catastrophic failure in solid-state TV's, where some part blows up, and takes the horizontal output transistor and several others with it. That problem isn't limited to TV. I just ran across the identical problem in not one, but *two* high-power hi-fi amplifiers. This material was sent to me by Ric Church, the "Hi-Fi Doctor" of Bowling Green, KY. (To be frank, Ric did all the work; I'm just writing it up!)

Catastrophic failure can be a serious problem, and we both thought that it should be brought to the attention of readers so they'd have some ideas about where to start should they have the misfortune to run into it.

The basic problem was the same in both: a Sansui AU20,000 audio amp and a Marantz 2325 receiver. By coincidence, it made its presence known in the left channel on both of them.

The symptoms for both were the same: At very irregular intervals, the units would make a very loud bang out of the left-channel speaker. Along with the bang went the final stage transistors and the woofer of the speaker system went with them. (Even more of a catastrophe than

TV, considering the price of a good woofer!) In Ric's first letter, he gave me a clear description of the problem. I wasn't able to give him too much direct aid, to be honest. I did make some suggestions as to possible causes, tests, and so on. Later, he wrote back, saying he had solved it.

The bang was always at the same volume. That ruled out the preamps. The DC power supply was also eliminated since the problem was only in one channel. Switching the driver boards made no difference, so those were eliminated. The Sansui amplifier contains six transistors in the output stage which has an NPN side and a PNP side. (Marantz is almost the same but only four transistors.) When the bang occurred, it blew only two of the six transistors. The Sansui amplifier would continue to play with the four remaining output transistors and with no bangs. The Marantz blew all of the finals.

I suggested checking at reduced power with a variable-voltage line transformer (and a resistive load to save expensive speakers); also, using heat, cold, and physical jarring to see if the problem could be forced to show up. The reason-

ing was that anything in the signal path or bias circuitry that caused a very sharp transient would do damage when the transient was amplified. It should have been in the input circuits to the finals in order to get the gain needed to do the dirty work. These tests didn't show up anything at all for quite a while.

He finally found it! In the Sansui, it was caused by biasing transistor TR01, a 2SC1364. (See Fig. 1.) Since that is located on the power-output board, swapping other boards did no good. The actual cause was a *momentary* breakdown, which then *healed itself* and the amp went on working. A very rare bird indeed! The component apparently senses output levels and controls bias on the output stages. The breakdown itself caused the transient.

In the Marantz, the problem was basically the same, but the cause was a pair of bias diodes. Same thing; the diodes affect the bias on the high-power output stage. Now, I remember a very similar case, quite a long time ago, in a much smaller amplifier. All of a sudden . . . bang, no output transistors! I found the cause by moving the bias diode, which promptly broke in two in the middle and blew up the two new output transistors I'd just put in. Frankly, at that time I was quite green in dealing with solid-state audio amplifiers and I didn't think that an open bias diode would blow the outputs. Take my word, (and Ric's) for it now, that it *will*.

The Hi-Fi Doctor's recommended cure for that—and one with which I agree—is to locate the parts that could be suspected (bias diodes, bias transistors, etc.) and replace them! The bad parts heal themselves. When making replacements, go through the specs and pick a transistor or diode that *exceeds* the rating of the original part. **Do not** use the same part number or the problem will be back. Since that involves only a very few and comparatively inexpensive parts it would be a logical remedy.

I'll throw this one in from much experience—look the whole area over very closely for any signs of a bad solder joint on the PC boards. A bad joint could easily cause that type of transient; they're noted for it. Also, it would be a very good idea to use high-wattage resistive loads when making tests, instead of the expensive speakers.

Thanks again to Ric for all of the good work, and good luck to all of you if you fall over this kind of problem. **R-E**

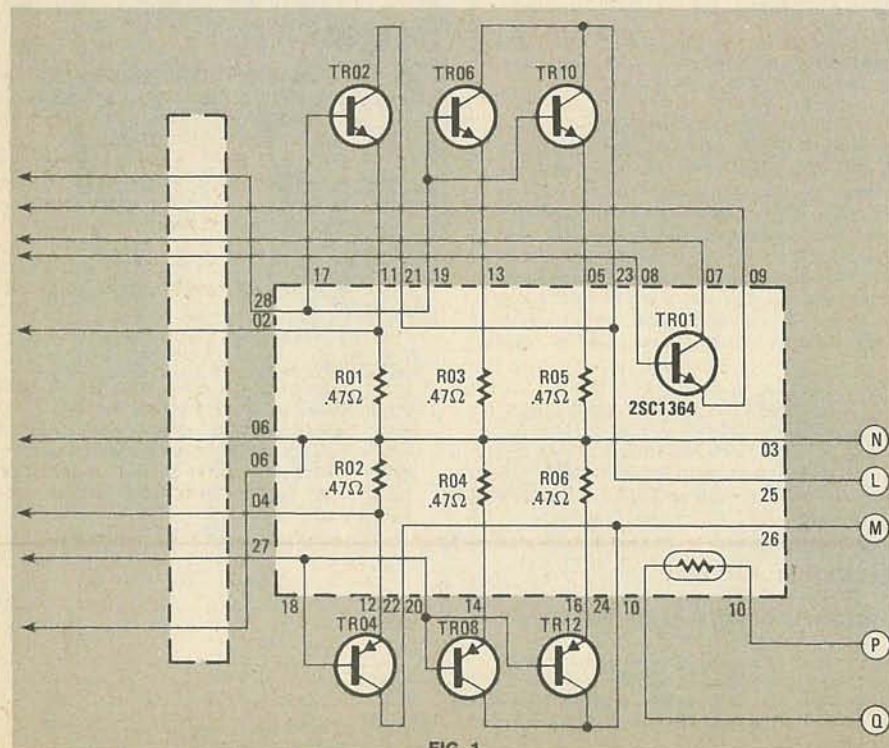


FIG. 1

service questions

COLOR BAR GENERATOR PROBLEMS

Edwin Menendez Inclan of Mexico City sends this feedback note: "I had two problems with my Sencore CG-141 color bar generator. The raster was short, vertically, on all patterns. (On TV signals, raster filled the screen). The other was the complete loss of the single horizontal line or dot pattern. You originally suggested checking or changing TR7, the vertical oscillator transistor. Although the original did not show any leakage, a new one did make the patterns fill the screen. They were vertically unstable, though.

"After much searching, I found that there was a slightly leaky capacitor in the collector circuit of TR7 (.05 μ F at 600 volts). Also, by using a resistance substitution box, I found that a resistor in the same circuit must have changed value. By setting the sub-box to a value that made the line/dot show up, I got it working properly again!"

Thanks, Edwin.

ALL WET

I've got a Panasonic CT-702 that was bought by a friend at a flea-market. Looks as if it had been out in the rain for some time! No sound, no raster. Found a bad SCR and couple of transistors on S-board. No luck. Finally took S-board out and cleaned all the plug-in contacts. Got raster but no sound or picture. Cleaned all contacts on A-board, and got them back. Now, the only problem is that some of the controls don't work properly, such as the Pana-Brite, etc. ABL control doesn't work right. On the S-board, D811 had come in two. Can't find it on the parts list under "diodes."—A.K., Struthers, OH.

Are you sure the guy that bought that thing was really a friend? Anyway, you've done all the right things; I'd suggest pulling all of the plug-in boards and giving them a good cleanup and contact tightening. That can't do anything but good.

D811 is called a diode but it isn't. It's apparently a VDR (Voltage-Dependent Resistor), and is listed only by part number. It is a shunt across TR851, the APF Output, which is just the voltage-regulator transistor. You should be able to get a replacement from Panasonic.

VERTICAL OSCILLATOR TIME-CONSTANT

This Zenith 19CC19's vertical oscillator is running too fast (rolling down). All parts seemed to be in tolerance. Changed C222, .01 μ F; no luck. When I bridged it with another .01 μ F the oscillator locked in. However, the vertical hold now has no

effect at all! What's going on here?—R.A., N. Miami, FL.

The vertical-oscillator frequency here, and in lots of other TV's, is determined by an R-C time-constant developed in the oscillator-input circuitry. You doubled the size of a capacitor; that should indicate that, somewhere in there, one of the resistors in the circuit is off-value! The time-constant is entirely an R-C thing; the value of the resistors and capacitors set it.

Incidentally, the capacitor in question is in the feedback loop from the vertical-output tube plate, so its charging time would set the time of the oscillator stage's "firing" (from the sync). Check or re-

place some of the few resistors in the same circuit; don't overlook any of the other capacitors either!

PARTS WANTED

I need help in finding a flyback for a Broadmoor 6199C color TV. I think the company went out of business some time ago. Can you help?—T.W., Madison, WI.

I've had requests for this sort of thing before, and in a very few cases been able to find something by checking part numbers. Not in this case, unfortunately. If anyone out there has found a source for Broadmoor parts and data, I'd really appreciate getting the information, and so would a whole lot of others. R-E

Radio-Electronics

SPECIAL REPRINT
BUILD A BACKYARD SATELLITE TV RECEIVER



First Printing: Sold Out!
Second Printing—Just Off Press!
Reprints Now Available!

Don't miss out again!

Send away today for your 36-page booklet containing complete reprints of all seven articles in the series on Backyard Satellite TV Receivers by Robert B. Cooper Jr.

This all-inclusive report gives you all the data you need to build your own Backyard Satellite TV Receiver.

■ TELLS ALL ABOUT domestic satellite communications, with full details on how you can pull those elusive TV signals from space.

■ LEGAL REQUIREMENTS, technical specifications, and how you, the home constructor, can meet them. Find out what mechanical and electronics skills you need.

■ RECEIVER CHARACTERISTICS, technical details and specifications, along with examples of actual receivers built at comparatively low cost.

■ ANTENNAE DESIGN... and exactly how you can build a spherical antennae, while keeping total earth station cost for the complete system under \$1,000.

■ THE FRONT END is critical when you build your own system. We help you explore several different approaches to making one that will work for you.

■ RECEIVER-SYSTEM hardware, and how it goes together to bring you direct-from-satellite TV reception in your own home.

To order your copy:

Complete coupon and enclose it with your check or money order for \$6.00. We will ship your reprint, postpaid in U.S. and Canada within 6 weeks of receipt of your order. All others add \$3.00 for postage. New York State residents must add 48¢ sales tax.

Radio-Electronics

Satellite TV Reprints
45 East 17th Street
New York, N.Y. 10003

Please print

(Name)

(Street address)

I want _____ reprints @ \$6.00 each, postpaid.

I have enclosed \$_____ N.Y. State residents

must add 48¢ sales tax.

(City)

(State)

(Zip)

COMPUTER TV

continued from page 50

resistors R8 and R9, is not critical. I found that I could use values ranging from 2K to 10K for R8, and from 5K to 10K for R9, with essentially the same results.

Power supplies

Two separate power supplies are required if the computer-side and the TV-side of the interface are to be completely isolated from each other. The TV-side requires only +5-volts DC. Most TV sets have 12 volts DC available internally somewhere, and that can be reduced to five volts by means of IC6, a 7805 regulator. The TV chassis is used as ground for this end of the circuit.

The computer-side of the interface requires both +5-volts and approximately -8-volts. A simple power supply to deliver those voltages is shown in Fig. 3. A transformer with an output of around 100 mA is adequate for the circuit. The transformer's center-tap should be used as the ground for the entire computer-side of the isolator. Use heat sinks on both of the five-volt regulators to keep them running cool.

Installation and use

The best place to locate the interface board is inside the TV set's cabinet, where accidental contact with the TV's chassis ground will be impossible. Switch S1 can be mounted inconspicuously on the TV set's cabinet. (Make certain that none of its metal

parts are in contact with any of the TV's.) That switch allows you to use the TV set either as a monitor or for its intended purpose.

As suggested by the schematic, the best place to inject the composite video signal from the interface is at the TV's first video-amplifier stage. Refer to your set's schematic or to a Sams Photofact folder. An excellent source of TV-interfacing information is Don Lancaster's *TV Typewriter Cookbook*, published by Howard W. Sams and Co., Indianapolis, IN 46268.

The total cost of this project, including the power supply, should be under \$25. It would be hard to find a monitor at that price! **R-E**

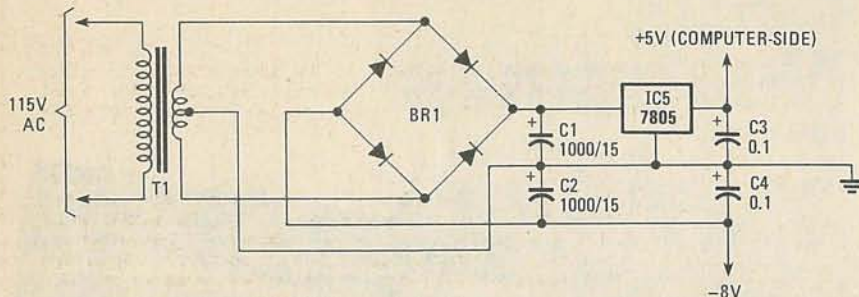


FIG. 3—BIPOLAR POWER SUPPLY is used for the comparators. The -8-volt line need not be regulated.


Put your money where your Heart is.



American Heart Association

WE'RE FIGHTING FOR YOUR LIFE

VIZ LCD Digital Multimeter

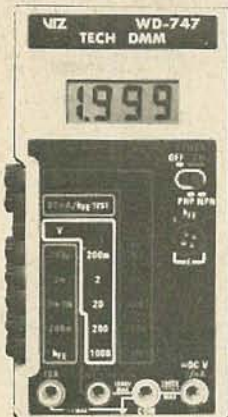

Model WD-747

- Large 3½ digit 0.5" LCD readout.
- Side switches for easy one-hand use.
- Accuracy better than 0.8% DCV.
- Resolution down to 100µV, 100µA DC, 0.1Ω.
- Only DMM with built-in socket for transistor h_{FE} testing.
- 10MΩ input impedance, 10 amp DC range.
- Auto zero polarity. Full overload-protection.
- All functions color coded.
- Rugged orange-colored ABS plastic case.
- Complete with battery, deluxe test probes and spare fuse.

Power Supplies WP-29 Monitor Isotap



- Supply line: 105 to 130V, 48 to 500Hz • Isolated output: 0 to 150V 48 to 500Hz • Leakage: Less than 0.1mA • Power rating (resistive load): 400VA • Meter: Taut band 3½" ±2% • Size: 3½" x 8¼" x 8¾" • Weight: 14½ lb. • Comes with output cable.

WP-708 Triple Output



Two 0-20 VDC supplies, 0-2A full load. May be used in series to provide 0-40 VDC, 0-2A. One 5 VDC (0.4A full load) fixed supply. Two digital voltmeters 0-99.9 VDC with separate inputs on the front panel.

Order with Confidence and get the Fordham Advantage!

Call for our prices **TOLL FREE**
(800) 645-9518

in N.Y. State call (516) 752-0050

FORDHAM

855 Conklin St. Farmingdale, N.Y. 11735



- Master Charge
- BankAmericard
- VISA • COD
- Money Order.
- Check
- COD's extra

What's coming?

At least one manufacturer is in the early-development stages with a 100-bit-wide bit-slice microprocessor. That would allow a great number of operations, both internal and I/O (Input/Output), to happen simultaneously. It allows high throughput at relatively moderate processing speeds.

Self-diagnostics and increased communication capabilities with off-vehicle diagnostic systems are definite trends. The "ideal" under-hood system would have no full-failure modes, would provide back-ups for any faulty component, would alert the driver to any need for service, would tell the mechanic what's wrong, and would stretch every gallon of gas while controlling exhausts utterly.

Most of which we already have, in one form or another.

Now the job is improvement, both in terms of performance and in terms of cost. A thousand, or two thousand, dollars worth of under-hood electronics may save you that in gas and repairs in less than a year, but you still have to put it up to buy the car.

There's more to automotive electronics than engine controls and digital dashboards. Next month, we will take a look at bells and whistles—things that make driving more pleasurable. **R-E**

DON'T FORGET



USE
YOUR
READER
SERVICE
CARD

What would make your business better? We would

You've seen what franchising did for real estate. Franchise companies took struggling independent realtors and put them in the limelight. The result: a greater share of the marketplace.

TRONICS 2000 is doing the same for the electronics service business. We're selecting a limited number of dealers in each community, giving them our name and high-level training in administrative and marketing techniques. And we're advertising as a single organization. In short, we're building a franchise organization that will stand out in a crowd.

Are you eligible to join? Yes, if you own a service dealership or are planning to start one and if you meet our technical requirements. But you must apply before the quota for your area has been filled.

TRONICS 2000 could be the lifeline you've been looking for. Call us. Today. Toll free 1-800-457-4507. In Indiana 1-800-822-4763.

tronics 2000

5229 South Highway 37 • P.O. Box 2003 • Bloomington, Indiana 47402 • 812/824-2424

HAMEG Oscilloscopes

Top Performance In Every Range

HM 307



HM 307 \$405.
Y: Bandwidth DC-10MHz (-3dB) • Sensitivity 5mV-20V/cm (±5%)
X: Timebase 0.2s-0.2μs/cm (±5%) • Triggering 2Hz-30MHz (3mm)
Built-in component tester • Calibrator • Screen 6x6cm • 1kV

HM 312 \$610.
Y: Bandwidth DC-20MHz (-3dB) • Sensitivity 5mV-20V/cm (±3%)
X: Timebase 0.2s-40ns/cm incl. x5 Magn. • Trig. 3Hz-30MHz (4mm)
Dual trace • X-Y Operation • Calibrator • Screen 8x10cm • 2kV

HM 412 \$915.
Y: Bandwidth DC-20MHz (-3dB) • Sensitivity 2mV-20V/cm (±3%)
X: Timebase 2s-40ns/cm incl. x5 Magn. • Trig. DC-40MHz (5mm)
Dual trace • Algebr. addition • X-Y Operation • Screen 8x10cm
Sweep delay • Overscan, Trigger, Delay indications • Trigger filter
Z-Modulation • Calibrator • Graticule illumination • 2kV

HM 512 \$1485.
Y: Bandwidth DC-50MHz (-3dB) • Sensitivity 5mV-50V/cm (±3%)
X: Timebase 5s-20ns/cm incl. x5 Magn. • Trig. DC-70MHz (5mm)
Dual trace • Algebr. addition • X-Y Operation • Screen 8x10cm
Delay line • Sweep delay • After delay triggering • Trigger filter
Single shot + Reset • Overscan, Trigger, Ready, Delay indications
var. Hold-off • Z-Modulation • Graticule illumination • 12kV

HM 812 \$4035.
Y: Bandwidth DC-50MHz (-3dB) • Sensitivity 5mV-50V/div. (±3%)
X: Timebase 5s-20ns/div. incl. x5 Magn. • Trig. DC-70MHz (0.5div.)
Dual trace analog storage with var. Persistence and Auto-Storage
Algebr. addition • X-Y Operation • Screen 8x10div. (7.2x9cm)
Delay line • Sweep delay • After delay triggering • Trigger filter
Single shot • Overscan, Trigger, Ready, Delay, AS indications
var. Hold-off • Z-Modulation • X-Guard circuit • Calibrator • 8.5kV

HM 812 storage



For more information contact:

HAMEG, INC.

88-90 Harbor Rd., Port Washington, N.Y. 11050
516-883-3837/516-883-6428 TWX: 510 223 0889

market center

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services). **\$1.65 per word prepaid (no charge for zip code)** . . . **MINIMUM 15 WORDS**. 5% discount for 6 issues, 10% for 12 issues within one year, if prepaid.

NON-COMMERCIAL RATE (for individuals who want to buy or sell a personal item) **85¢ per word prepaid** . . . no minimum.

ONLY FIRST WORD AND NAME set in bold caps. Additional bold face (not available as all caps) at 10¢ per word. All copy subject to publisher's approval. **ADVERTISEMENTS USING P.O. BOX ADDRESS WILL NOT BE ACCEPTED UNTIL ADVERTISER SUPPLIES PUBLISHER WITH PERMANENT ADDRESS AND PHONE NUMBER.** Copy to be in our hands on the 26th of the third month preceding the date of the issue (i.e., August issue closes May 26). When normal closing date falls on Saturday, Sunday, or a holiday, issue closes on preceding working day.

BUSINESS OPPORTUNITIES

MECHANICALLY inclined individuals desiring ownership of Small Electronics Manufacturing Business—without investment. Write: **BUSINESS-ES**, 92-R, Brighton 11th, Brooklyn, NY 11235

NEW tax loopholes discovered. Everyone eligible. Free sample newsletter. Write: **ULC**, Box 179-CU, Clarkston, GA 30021

CRT rebuilding machinery. Large profits can be made rebuilding picture tubes with our patented equipment. Facts don't lie. Training provided. Phone (312) 583-6565. Write: **LAKESIDE**, 4071 N. Elston, Chicago, IL 60618

PROJECTION TV . . . Make \$200.00+ per evening assembling projectors . . . Easy . . . Results equal to \$2,500 projectors . . . Your total cost less than \$15.00 . . . **Plans, lens & dealer's** information \$14.00 . . . Illustrated information free . . . **MACROCOMGEX**, Washington Crossing, PA 18977

START your own electronic assembly business with our unique plans. Write: **DELCRON**, 32 Fairington St., Catharines, Ont. Canada L2N 5W3

Burglar-Fire Protection

Protect Your Life, Home, Business, Auto, etc.

• Our catalog shows how. Install your own alarm systems and devices and save \$\$\$\$. We offer FREE write-in engineering service.

FREE CATALOG Lowest Prices on Reliable, High-Quality Alarm Systems and Devices

Burdex Security Co. Box 82802-RE Lincoln, Ne. 68501

39⁹⁵ ADD \$2.50 FOR POSTAGE **30 CHANNEL CABLE TV CONVERTER**

FREE! **UNUSUAL 96 PAGE ELECTRONIC PARTS & IDEAS CATALOG!**

ORDER No. 171AE047

BITCO ROUTE 9N, PLATTSBURGH, N.Y. 12901
Tel.: (518) 561-8700.

EDUCATION & INSTRUCTION

THE PA BIBLE from Electro-Voice, a professional guide addressing sound reinforcement and public address applications/specifications from

the club/church/school level up through auditoriums/outside stadiums/road system situations. To receive your copy of this highly regarded tool, including all existing supplements, and to be put on the distribution list for future additions, send \$2.00 to **ELECTRO-VOICE**, Box No. 124, 600 Cecil Street, Buchanan, MI 49107

MAKE hydrogen fuel: Build generators with material from Hardware stores. Illustrated manual; \$10.95 ppd. **NEGEYE ENGINEERING**, Pennsboro, WV, 26415

ELECTRONICS books from world publishers. Lowest prices, ask catalog. **BUSINESS PROMOTION**, Lajpatrai Market, Delhi, India

UNIVERSITY degrees by mail! Bachelors, Masters, PhD's . . . Free revealing details. **COUNSELING**, Box 317-RE 1, Tustin, CA 92680

SUBSCRIPTION television education manual **Two scrambling/decoding systems, theory, circuits. Decoder dealers listed. \$14.95. ABEX, P.O. BOX 26601-R2, San Francisco, CA 94126**

PASS FCC EXAMS TESTS ANSWERS FOR FCC FIRST AND SECOND CLASS COMMERCIAL LICENSE

The Original FCC Tests-Answers exam manual that prepares you at home for FCC First and Second class Radiotelephone licenses. Newly revised multiple choice exams cover all areas tested on the actual FCC exam. Plus "Self Study" Ability Test. Proven! \$9.95 postpaid. Moneyback Guarantee.

COMMAND PRODUCTIONS P.O. Box 26348 E
Radio Engineering Division San Francisco, CA 94126

SATELLITE TELEVISION

SATELLITE television...Howard/Coleman boards to build your own receiver. For more information write: **ROBERT COLEMAN**, Rt. 3, Box 58-ARE, Travelers Rest, SC 29690

ANTENNA azimuth and elevation for all geostationary satellite locations. \$4.00 for Western Hemisphere satellites. \$6.00 for satellites within your horizon. Send accurate lat/long. **DAVID FREY**, Box 2591, Satellite Beach, FL 32937

SATELLITE VISION
SATELLITE VISION
SATELLITE VISION

We manufacture the highest spec 3-meter data & video dish in the world 41db gain! We also sell direct. Immediate delivery or you pick up. Complete details including satellite TV information, aiming service and discount schedule. Send \$1.25 for postage & handling to:

TIGER TENNAS
P.O. Box 561
Casselberry, Florida 32707

BUY DIRECT

Satellite TV

FOR THE HOME

Sick of Network TV?

Our receiver lets you get over 75 channels of television directly from earth-orbiting cable TV satellites! HBO, Showtime, super stations, sports and movies from around the world.



We don't just sell information! We Manufacture Hardware!

Our 94-page catalog and information book tell the whole story! Inexpensive dishes, high pre-feds, computer aiming software! Specs, kits and more! Send \$7.95 today!

24-hour C.O.D Hotline
(305) 339-7600



SPACECOAST RESEARCH
Dept. T, P.O. Box 442, Altamonte Springs, FL 32701

To run your own classified ad, put one word on each of the lines below and send this form along with your check for \$1.65 per word (minimum 15 words) to:

Radio-Electronics, 200 Park Avenue South, N.Y., N.Y. 10003

ORDER FORM

PLEASE INDICATE in which category of classified advertising you wish your ad to appear. For special headings, there is a surcharge of \$10.

() Plans/Kits () Business Opportunities () For Sale
() Education/Instruction () Wanted ()

Special Category: \$10

(PLEASE PRINT EACH WORD SEPARATELY, IN BLOCK LETTERS.)

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

PLEASE INCLUDE FOR OUR FILES YOUR PERMANENT ADDRESS AND PHONE NUMBER.

4Kx16 MEMORY BOARD with 64 IC chips (2102) in sockets. Super deal at \$50 the complete board.

\$29 AUTO SECURITY SYSTEM alarm system \$7.00

SPACE MAN toy module PC board w/musical IC synthesizer chip. ROM has 5 programs, wierd noises blinking LEDs \$3.00 each

DATA STATION CONSOLE w/keyboard 9 inch monitor, power supply. Logic boards broken. \$80
Send for details on this one.

Computer video monitor chassis 9 inch, 12 volt used \$40

Computer video monitor chassis 12 inch, new \$50

8 INCH FLOPPY DISC DRIVE by MPI, with some data. Sold as is but visually OK \$175.00

PIN BALL GAME, solid state, hand held, visual and audio, bumpers, flippers, etc. LED scoring and up to 4 players. Complete PC module w speaker \$10.00

TOUCH PAD solid state w/LSI chip. Bell system compatible. For computers & phones \$24.00

12 VOLT GEL-CELLS 2.5 AH \$14.00 5 AH \$17.00

12 INCH CRT bonded face plate. New with specs.

Made for computers. \$35.00

WALKY TALKIES Govt surplus used condition. 47-55.4 mc range. With schematics. Govt AN/PRC-6 \$25 each 2 for \$45. Ant. \$5 each

ASCII KEYBOARD parallel \$50

RED LED's 10 for \$1.00

MIN ORDER \$10.00

Shipping extra on all merchandise

Meshna Inc., PO Box 62, E. Lynn, Mass. 01904



CIRCLE 15 ON FREE INFORMATION CARD

CFR Associates EXCLUSIVE! SURPLUS COMPUTER BARGAINS

8 INCH FLOPPY DRIVES

Used, removed from systems. Mfd. by MPI Division of Control Data. These are the CDC floppy! Includes schematics & I/O data. Sold 'As-Is' but complete and whole! An incredible BARGAIN, easy to interface with most commercial controllers. Features "hard" sectoring.

Special Price **Only \$229.00..**
Buy 3 and SAVE BIG!! **3/\$599.00**
Plus Shipping



DAISY TERMINALS featuring the DIABLO HyType Daisy Printer. This exciting terminal features: RS232C ASCII, 110-1200 BAUD, KSR operation plus fantastic PLOTTER mode with bi-directional horiz. & vert'l movement, 1/60"H & 1/48"V increments, 15" platen, prints at 10, 15 & 30 cps! Uses plastic printwheel and has many more exciting features. Includes operator's manual & schematics. Used & refurbished.

CASE STYLE **Now Only \$1499.00**
MAY DIFFER Add \$30.00 for Shipping Crate. Pay Shipping On Delivery

* SELECTRIC Typewriter Terminals

USED, off-lease. Features IBM Selectric Printer RS232 I/O. Takes BCD code type elements. Whole and complete. "AS-IS" (may need some adjustments). SEE OUR OCT. 1980 ADVERTISEMENT in this magazine. 15" carriage, type ball included. 110 VAC includes power supply, I/O and printer circuits and more.

Only **\$469.00**
Add \$18.00 for Shipping Crate. Pay Shipping On Delivery



2/\$750

Maintenance Manuals Available.. \$25.00


*IBM Trademark.

GET YOUR COPY OF OUR LATEST FLYER!

Circle the Bingo Card Number or Send a 1st Class Stamp for a Free Copy.

CFR ASSOCIATES, INC.
18 Granite Street
Haverhill, Mass. 01830

617-372-8536
Phone Orders
Welcome

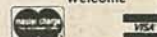

CIRCLE 30 ON FREE INFORMATION CARD

INTERNATIONAL ELECTRONICS UNLIMITED

IMMEDIATE DELIVERY OF QUALITY RESISTORS

CARBON FILM RESISTORS 1/4 & 1/2 watt

CARBON FILM 1/4		PRICING	
1/4watt (R. Ohm R25)	total quantity ea	pk-10	pk-100
.095"dia x .250"long (body)	1-999	\$1.10	45 2.00
1/2watt (R. Ohm R50)	1000-	.10	40 1.80 15.00
.146"dia x .354"long (body)	5000-	.10	30 1.70 14.50
	10000-	.10	25 1.55 13.00

25 or more resistors - not individually packaged - mixed - specify any assortment of values \$0.04ea

.5	3.9	16	68	300	1.2K	5.1K	22K	91K	390K	1.6M	*6.2M
1.0	4.3	18	75	330	1.3K	5.6K	24K	100K	430K	1.8M	*6.8M
1.1	4.7	20	82	360	1.5K	6.2K	27K	110K	470K	2.0M	*7.5M
1.2	5.1	22	91	390	1.6K	6.8K	30K	120K	510K	2.2M	*8.2M
1.3	5.6	24	100	430	1.8K	7.5K	33K	130K	560K	2.4M	*9.1M
1.5	6.2	27	110	470	2.0K	8.2K	36K	150K	620K	2.7M	*10M
1.6	6.8	30	120	510	2.2K	9.1K	39K	160K	680K	3.0M	*11M
1.8	7.5	33	130	560	2.4K	10K	43K	180K	750K	3.3M	*12M
2.0	8.2	36	150	620	2.7K	11K	47K	200K	820K	3.6M	*13M
2.2	9.1	39	160	680	3.0K	12K	51K	220K	910K	3.9M	*15M
2.4	10	43	180	750	3.3K	13K	56K	240K	1.0M	4.3M	(* 1/2w only)
2.7	11	47	200	820	3.6K	15K	62K	270K	1.1M	4.7M	
3.0	12	51	220	910	3.9K	16K	68K	300K	1.2M	5.1M	
3.3	13	56	240	1.0K	4.3K	18K	75K	330K	1.3M	5.6M	
3.6	15	62	270	1.1K	4.7K	20K	82K	360K	1.5M		

Rohm
QUALITY RELIABILITY

METAL FILM RESISTORS

METAL FILM 1/2	total quantity ea	pk-10	pk-25	pk-100	pk-250
RW60 (R. Ohm CR60F) 1/2watt	1-999	\$2.25	1.00	2.00	7.50 17.50
Low temp coef - 50ppm/°C	1000-	.20	.90	1.80	7.00 16.25
.138"dia x .355"long (body)	5000-	.20	.85	1.70	6.50 15.00
color banded	10000-	.20	.80	1.55	6.00 13.75

10 or more resistors - not individually packaged - mixed - specify any assortment of values \$1.54ea

VALUES STOCKED (ohms)

Standard 1/2 metal film values from 10 ohm to 475K ohm	
10.0	12.1 14.7 17.8 22.6 27.4 33.2 40.2 48.7 59.0 71.5 88.7
102	12.4 15.0 18.2 23.2 28.0 34.0 41.2 49.9 60.4 73.2 90.9
105	12.7 15.4 18.7 23.7 28.7 34.8 42.2 51.1 61.9 75.0 93.1
107	13.0 15.8 19.1 24.3 29.4 35.7 43.2 52.3 63.4 76.8 95.3
110	13.3 16.2 19.6 24.9 30.1 36.5 44.2 53.6 64.9 80.6 97.6
113	13.7 16.5 20.0 25.5 30.9 37.4 45.3 54.9 66.5 82.5 100
115	14.0 16.9 20.5 26.1 31.6 38.3 46.4 56.2 68.1 84.5 104
118	14.3 17.4 22.1 26.7 32.4 39.2 47.5 57.6 69.8 86.6 107

and multiples of 10 of the above values to 475K
i.e. 10.0 100 1.0K 10.0K 100K etc (total 448)

Rohm

VOLTAGE REGULATORS **10% OFF ON \$25.00**
15% OFF ON \$50.00

M320T-5	Negative 5 V reg (7905)	1.19	JUMBO LED	
M320T-12	Negative 12 V reg (7912)	1.19	.20"dia, diffused	10/\$1.00 25/\$2.00 100/\$7.50
M320T-15	Negative 15 V reg (7915)	1.19	Red, Clear or White	7/\$1.00 25/\$2.05 100/\$9.75
M340T-5	Positive 5 V reg (7805)	1.19	Green or Yellow	
M340T-8	Positive 8 V reg (7808)	1.19	SUBMINIATURE LED	
M340T-12	Positive 12 V reg (7812)	1.19	.125"dia, diffused	10/\$1.00 25/\$2.00 100/\$7.50
M340T-15	Positive 15 V reg (7815)	1.19	Red or Clear	10/\$1.00 25/\$2.05 100/\$9.75
2N3904	NPN TO-92	10/\$1.50	1N4148	400mw 15/\$1.00 100/\$5.00
2N3906	PNP TO-92	25/\$3.00	1N4001	rectifier 12/\$1.00 100/\$7.00
		100/\$11.00	1N4007	rectifier 10/\$1.00 100/\$9.00

Payment by check, M.O., UPS-COD, M/C or VISA. Add \$1.00 shipping/handling in US, Canada & Mexico. Other countries \$1.00 + 5% of order. California residents add sales tax. Minimum order \$10.00.

INTERNATIONAL ELECTRONICS UNLIMITED
225 Broadway Jackson Ca 95642
phone 209 223 3870

CIRCLE 62 ON FREE INFORMATION CARD

MICRO MART

552 Summit Ave.
Westfield, N.J. 07090
(201) 654-6008

SUBSCRIPTION TV DECODER KIT

Please refer to this month's Radio Electronic's feature article for information regarding our kit.

Complete kit..... \$75.00
Manual & drilled & etched project board..... \$20.00
Additional boards (with one board & manual)..... \$15.00

DIRECT LINE FOR ORDERS ONLY—201-654-6029

7 SEG Displays (comp. grade)
.37"/95±-.6"/1.45 (specify ann. or cath.)
AM/FM RADIO CHIP—(#4408) 2.00 or 3/5.00
Complete AM/FM IC-external IF required

DIPPED TANTALUMS
.47 µf 35V (1" leads) 10/1.00
SUPER SUB MINI LYTICS
(1" rad. leads, by Nichicon)
1000µf 50V (1 1/4" L X 1/4" W), 75¢ or 10/6.00
47 µf 25V (1/4" L X 1/4" W), 10/\$1.00
400µf 330V (photo flash or laser circuits)-2/1.00

COMPUTER GRADE TWIST LOCKS
3200µf 50V (ideal for power supplies) 2.00
1000µf 50V—1.00 1000µf 185V—2.00
DISCS—.001 1KV 25/1.00, 1.50V 15/1.00

HEAT SENSITIVE SWITCH—4/1.00
self contained unit opens at 150 C
9 DIGIT FLUORESCENT DISPLAY by NEC
complete with driving circuitry-2.50

MOTION DETECTOR: Features include transparent, optical IC completely assembled on circuit board with necessary capacitors. Extensive specs and application notes included./\$5.00

CRYSTALS—3.579545 MHz 99¢
6.0 MHz 2.95
JUMBO LED's
Green, 7/1.00-Yellow, 7/1.00-Red, 10/1.00
100/13.00 100/13.00 100/9.00
MOUNTING CLIPS—12/1.00

EXTRA LOUD 9V BUZZER—3/2.00

FREQUENCY COUNTER CHIP
ICM 7225 IPL
(40 pin), with on board dividers,
decoders/drivers. 18.95-specs included

ZENER DIODES—20V 1 amp 10/1.00

LINEAR			
LM 323K	5.00	LM 1303	1.50
LM 300H	.75	LM 1304	.95
LM 301AN	33	LM 1305	1.15
LM 307	.50	LM 1307	.90
LM 309H	.35	LM 1307E	.90
LM 308	.95	LM 1310	1.75
LM 310	1.05	LM 1391	1.50
LM 311H	.85	LM 1414	2.25
LM 317K	5.00	LM 1800	2.90
LM 318H	1.25	LM 1808	2.75
LM 320K-15	1.15	LM 1820	1.75
LM 320K-12	1.15	LM 1828	1.75
LM 324	1.25	LM 1830	1.50
LM 325	1.85	LM 1841	1.75
LM 339J	1.00	LM 1848	1.75
LM 340K-12	1.25	LM 1889	4.50
LM 341P-12	1.25	LM 2111	1.60
LM 343H	3.50	LM 2113	1.75
LM 373	2.95	LM 2907	2.40
LM 377	2.00	LM 2917	1.95
LM 380	1.15	LM 3046	1.10
LM 381	1.60	LM 3054	1.50
LM 384	1.85	LM 3064	2.00
LM 386	1.50	LM 3065	1.50
LM 389	1.50	LM 3067	2.50
LM 390	1.95	LM 3070	2.50
LM 746	2.50	LM 3071	2.00
LM 748CN	.39	LM 3075	2.75
		LM 3089	1.75
		LM 3900	.75

Terms MICRO-MART accepts Visa, MC, and telephone COD'S. Foreign orders \$50.00 minimum plus shipping-US funds only. Orders under \$10.00 include \$2.00 for shipping/handling. All components guaranteed or money refunded. Immediate shipping. N.J. residents add 5% sales tax.

MICRO-MART • 552 SUMMIT AVE., WESTFIELD, N.J. 07090 • (201) 654-6008

Telephone Listening Device

Record telephone conversations in your office or home. Connects between any cassette or tape recorder and your telephone or telephone LINE Starts automatically when phone is answered. Records both sides of phone conversation. Stops recorder when phone is hung up. This device is not an answering service.



Each
\$18.95
Qty. Disc Avail.

Super Powerful

Wireless Mic

10 times more powerful than other mics. Transmits up to 1/4 mile to any FM radio. Easy to assemble kit. 15V battery (not incl.)

Call (305) 725-1000 or send \$18.95 + \$1.00 shipping per item to USI Corp., P.O. Box RE-2052, Melbourne, FL 32901. COD's accept. For catalog of transmitters, voice scramblers and other specialty items, enclose \$2.00 to USI Corp.



size 2x3x1/4

BIOPHYSICAL MONITORING

TELEMETRY transmitter detects arterial pulses with pressure sensitive transducer placed over wrist artery. Each detected pulse transmitted as audio tone, (beep), to standard FM radio. Flashing LED provides visual indication. Completely assembled. Transducer, wrist strap, and battery included. Size: 4.4" x 2.4" x 1.2". Order model BPT-17. \$39.50 plus \$2.00 shipping. **OMNI-TEK**, Box 1318, Longmont, CO 80501

TELEMETRY transmitters: EKG—\$27.50, arterial pulse—\$39.50. Free information. **OMNI-TEK**, Dept. RE, BOX 1318, Longmont, CO 80501

WANTED

BASEBALL cards, other sport and non-sport cards, sports memorabilia of all types. I will buy/sell on consignment. **J. LANNING MYERS**, 6609 Horseshoe Rd. Clinton, MD 20735. 301-868-1510

WE buy sell used vacuum pumps, diffusion pumps and picture tube rebuilding equipment. Phone—(312) 583-6565. Write—**LAKESIDE**, 4071 N. Elston, Chicago, IL 60618

CRYSTAL RADIO
Complete!
\$25.00 ppd.
BOB RYAN
PO Box 3039
Anaheim, CA
92803



AMAZING ELECTRONIC PROJECTS and PRODUCTS:

Lasers Super Powered, Burning Cutting, Rifle, Pistol. Pocket. See in Dark—Shotgun Directional Mike—Unscramblers—Giant Tesla—Stunwand—TV Disrupter—Energy Producing, Surveillance, Detection, Electrifying, Ultrasonic, CB, Auto and Mech. Devices, Hundreds More—All New Plus INFO UNLTD PARTS SERVICE. Catalog \$1. Information Unlimited, Dept. R8 Box 716 Amherst, N.H. 03031.

HIGHLY PROFITABLE

ONE-MAN ELECTRONIC FACTORY

Investment unnecessary, knowledge not required, sales handled by professionals. Ideal home business. Write today for facts! **Postcard will do. Barta-RE-1, Box 248, Walnut Creek, CA 94597.**

PLANS & KITS

PRINTED circuit boards from sketch or artwork. Kit projects. Free details. **DANOCINTHS INC.**, Box 261, Westland, MI 48185

DIGITAL multimeter kits handheld, best quality 0.1% accuracy. The lowest price in America \$67.50 write: **E. G. TRONICS**, 8254 Greenleaf Circle, Tampa FL 33615

SOUND effects synthesizer. Uses voltage controlled circuits to make unlimited sounds. Imitates drum synthesizer. Build it yourself and save. PC board plus complete plans only \$9.95 or send stamp for information. **WAVEFORM PROCESSING**, 7 Bradford Avenue, Pittsburgh, PA 15205

DECODE Morse and RTTY signals off the air with new **Morse-a-Word** or **RTTY reader**. Morse keyboard also available. Kits or factory wired. Send for details. **MICROCRAFT**, Box 513R, Thiensville, WI 53092 (414) 241-8144.

CRYSTAL radio builders . . . \$1.00 brings you two sets plans, details, price list. **BOB RYAN**, P.O. BOX 3039, Dept. R., Anaheim, CA 92803

PICTURE tube restorer. New method. Plans—\$5.00. **PAYETTE ENTERPRISES**, BOX 250, Echo Bay, Ontario POS 1C0

BUILD microcomputer trainer. Send \$5.00 for 2 complete instruction manuals. **PACCOM**, 14905 NE 40th, Dept. PRE120, Redmond, WA 98052

PROJECTION TV. . . . Convert your TV to project 7 foot picture. Results equal to \$2,500 projector. Total cost less than \$20.00. Plans & lens \$16.00. Illustrated information free. **MACRO-COMGE** Washington Crossing, PA 18977

SCRAMBLED TV decoder. Complete circuit/instructions \$10.00. **G&C**, P.O. Box 1055, Dedham, MA 02026

TREASURE finder plans, schematics and pictorials, single and multiple stage \$5.00. **EVANS**, Box 402, Mt. Lookout, WV, 26678

RESISTORS 1/4 watt 5% carbon film factory fresh 1.65 per hundred, 12.00 per thousand. Integrated circuits 4116 dynamic RAM 8 for 34.00, 2716 @ 11.00, 2732 @ 37.00, IC sockets, capacitors, trim pots, and more. Free catalog. **WESTLAND ELECTRONICS**, 34245 Ford Rd., Westland, MI 48185. (313) 728-0650

PLANS: Subscription television decoder, UHF over the air type, \$10.00. **Telephone memory dialer**, stores 32 numbers, \$3.00. **Negative ion generator**, easy to build, \$3.00. We sell complete plan sets which include detailed instructions and circuit board patterns. Parts and kits also available. **COLLINS ELECTRONICS**, Box 6424, San Bernardino, CA 92408

TWELVE bands/channel \$100.00 kit still available; see May 1978 R/E cover story or write: **SYMMETRIC SOUND SYSTEMS**, 912 Knobcone PL, Dept. R, Loveland, CO 80537

ROBOT info—booklet, \$4; basic plans, \$6.50; advanced plans, \$9.45. **OMEGA ENTERPRISES INC.**, "The Robot People", P.O. Box 4143, Dept. RE, Tulsa, OK 74104

SAVE 90%. Build your own minicomputer. Free details. **DIGITRONICS CORPORATION**, 273E W. Butler Dr., Phoenix, AZ 85021

VINTAGE tubes of World War II era . . . never used, in original factory boxes. #957 "acorn" = 18 for \$5.00 postpaid. 1 1/2-volt filament. Supply limited. **BOB RYAN**, P.O. BOX 3039, Anaheim, CA 92803

SUBSCRIPTION TV decoder circuits. Detailed plans \$4.60, **JOE**, PO Box 61, Cumberland, RI 02864


coax & shielded cable

WIRE STRIPPERS

A versatile, compact 3 station stripper. This EXCLUSIVE 3 in 1 SWING BLADE model easily strips miniature coax, RG and shielded cable as well as hook up wires. Can handle constructions up to an O.D. of .265" (6.7mm). FREE catalog tells it all.

FREE WIRE STRIPPING SERVICE

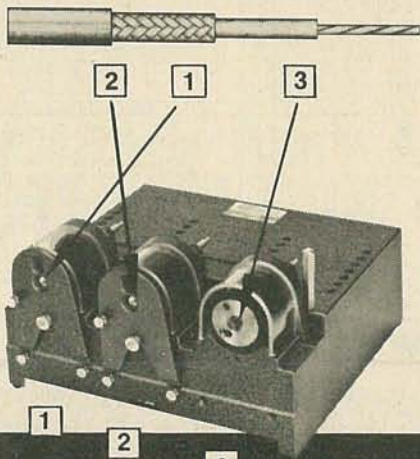Send a 3-5 ft. sample of your cable or wire and strip specifications. Stripped wire will be returned to you with a complete report and recommendations.



CARPENTER
MFG. CO., INC.

Fairgrounds Drive, Manlius, N.Y. 13104
(315) 682-9176

CIRCLE 3 ON FREE INFORMATION CARD

DISCOUNT TRS-80® DEALER A301 COMPUTER SPECIALISTS

FREE
COMPUTER
CATALOG
UPON
REQUEST.



Up to 15% Discount on TRS-80's

26-1051 4K LEVEL I . . . \$ 424.00
26-1056 16K LEVEL II . . . 670.00
26-4002 64K I DRIVE . . . 3466.00

1-800-841-0860 TOLL FREE
MICRO MANAGEMENT SYSTEMS, INC.
Downtown Plaza Shopping Center
115 C. Second Av., S.W.
Cairo, Georgia 31728
(912) 377-7120 Go. Phone No.

FOR SALE

SCANNER/monitor accessories—kits and factory assembled. Free catalog. **CAPRI ELECTRONICS**, Route 1R, Canon, GA 30520

FREE catalog, IC's, semi's, parts. **CORONET ELECTRONICS**, 649A Notre Dame W., Montreal, Que., Canada H3C 1H8. U.S. Inquiries.

SAVE up to 50% on name brand test equipment. Free catalog and price list. **SALEN ELECTRONICS**, Box 82-M, Skokie, IL 60077

GOVERNMENT surplus receivers, transmitters, snooperscopes, parts, fantastic 72 page catalog 25¢. **MESHNA**, Nahant, Mass. 01908

SCR's and TRIAC's

C106D	.34	SCR	5 amp 400V TO-220
TIC116B	.97	SCR	8 amp 200V TO-220
TIC126B	1.09	SCR	12 amp 200V TO-220
TIC216B	.99	Triac	6 amp 200V TO-220
TIC226D	.95	Triac	8 amp 400V TO-220
TIC236D	1.45	Triac	12 amp 400V TO-220
TIC246D	1.45	Triac	16 amp 400V TO-220

Bi-Fet OP AMPS

TL064CN	2.75	Quad low power
TL071CP	.59	Low noise
TL072CP	1.19	Dual low noise
TL074CN	2.35	Quad low noise
TL081CP	.49	J-FET input
TL082CP	.99	Dual J-FET input
TL084CN	1.95	Quad J-FET input

1980 I.C. MASTER

Final sale \$24.95
Subject to prior sale
NEW 1981 EDITION
2 volumes — 3200 pages
now available
regular price \$82.50
Introductory Offer: \$75.00
New section on custom I.C. & microprocessor development systems

PLASTIC POWER TRANSISTORS

TIP29A	.37	TIP41B	.57	TIP122	.72
TIP29B	.38	TIP41C	.59	TIP125	.72
TIP29C	.39	TIP42A	.57	TIP126	.77
TIP30A	.39	TIP42B	.59	TIP127	.84
TIP30B	.42	TIP42C	.64	TIP140	1.44
TIP30C	.42	TIP110	.54	TIP141	1.64
TIP31A	.38	TIP111	.57	TIP142	1.96
TIP31B	.42	TIP112	.64	TIP145	1.84
TIP31C	.45	TIP115	.55	TIP146	1.98
TIP32A	.42	TIP116	.59	TIP147	2.25
TIP32B	.45	TIP117	.64	TIP2955	.83
TIP32C	.48	TIP120	.64	TIP3055	.70
TIP41A	.55	TIP121	.68	FT3055	.59

PROM'S

74S288	\$3.95	256 bit, 16 PIN
74S188	\$3.95	256 bit, 16 PIN
93427/MB7052	\$3.95	1K, 16 PIN
93417/MB7057	\$3.95	1K, 16 PIN
93446/MB7053	\$4.95	2K, 16 PIN
93436/MB7058	\$4.95	2K, 16 PIN
93453/MB7122	\$9.95	4K, 18 PIN
82S185/7128	27.95	8K, 18 PIN
74S478/7132	24.95	8K, 24 PIN
82S191/7138	78.00	16K, 24 PIN

We provide PROM programming.
Please enclose truth table or master PROM.

MOS MEMORIES

Part No.	IC	Capacity	Price
2101-35	1K (256 x 4)	350NS 22 PIN	3.95
2102-25	1K (1K x 1)	250NS 16 PIN	1.09
P2111-45	1K (256 x 4)	450NS 18 PIN	3.95
P2112-35	1K (256 x 4)	350NS 18 PIN	2.85
2114L	Low Power 4K (1024 x 4)	300NS	3.45
2147	4K (4K x 1)	55NS	9.95
2147	4K (4K x 1)	70NS	8.95
UART's			
COM8017/AV5-1013A	Special	40 Khz Single 5V Supply	3.95
1K CMOS RAM			
5101	1K (256 x 4)	450NS 22 PIN Low Power	3.95
4K CMOS RAM			
P6504	4K (4K x 1)	550NS 18 PIN 110MW	7.95
P6514	4K (1K x 4)	450NS 18 PIN 110MW	7.95
SHIFT REGISTERS			
3341APC	FIFO 1 MHz		4.98
3347PC	80 bit		3.95

TTL — LOW POWER SCHOTTKY

74LS00N	.21	74LS20N	.24	74LS55N	.27	74LS95N	.58	74LS138N	.69	74LS162N	.85	74LS193N	.89	74LS248N	1.69	74LS283N	.96	74LS362N	11.95	74LS395N	1.95
74LS01N	.21	74LS21N	.24	74LS73N	.38	74LS96N	.68	74LS139N	.69	74LS163N	.85	74LS194N	.89	74LS249N	.99	74LS290N	.84	74LS365N	.79	74LS447N	1.35
74LS02N	.27	74LS26N	.39	74LS74N	.54	74LS107N	.42	74LS145N	1.25	74LS164N	.64	74LS195N	.68	74LS251N	2.25	74LS293N	.38	74LS366N	.79	74LS490N	.95
74LS03N	.23	74LS27N	.29	74LS75N	.39	74LS109N	.52	74LS147N	2.45	74LS165N	1.27	74LS196N	1.12	74LS253N	.59	74LS298N	1.19	74LS367N	.79	74LS630N	85.00
74LS04N	.27	74LS30N	.19	74LS76N	.39	74LS112N	.42	74LS148N	1.44	74LS166N	1.87	74LS197N	.99	74LS257N	.84	74LS299N	2.65	74LS368N	.79	74LS631N	85.00
74LS05N	.27	74LS32N	.56	74LS78N	.36	74LS115N	.54	74LS151N	4.5	74LS170N	2.75	74LS221N	.88	74LS258N	.68	74LS320N	2.95	74LS373N	1.48	74LS668N	.89
74LS08N	.27	74LS37N	.36	74LS83N	.84	74LS123N	.79	74LS153N	.42	74LS173N	.74	74LS240N	.99	74LS259N	2.95	74LS321N	3.86	74LS374N	1.48	74LS670N	2.65
74LS09N	.32	74LS38N	.36	74LS85N	1.15	74LS124N	.99	74LS155N	.87	74LS174N	.42	74LS241N	.99	74LS260N	.99	74LS322N	4.95	74LS375N	2.95		
74LS10N	.24	74LS42N	.45	74LS86N	.48	74LS125N	.99	74LS156N	1.45	74LS175N	.42	74LS242N	.99	74LS266N	.48	74LS323N	4.95	74LS377N	1.44		
74LS11N	.32	74LS47N	.76	74LS90N	.44	74LS126N	.74	74LS157N	.56	74LS181N	2.38	74LS243N	.99	74LS272N	1.39	74LS324N	1.19	74LS378N	1.19		
74LS12N	.18	74LS48N	1.45	74LS91N	.94	74LS132N	.59	74LS158N	.59	74LS190N	1.25	74LS244N	.99	74LS275N	4.95	74LS324N	2.45	74LS379N	1.95		
74LS13N	.25	74LS51N	.24	74LS92N	.54	74LS133N	2.85	74LS160N	.99	74LS191N	.89	74LS245N	2.25	74LS279N	.68	74LS325N	1.27	74LS390N	1.98		
74LS14N	.48	74LS54N	.24	74LS93N	.42	74LS136N	.48	74LS161N	.85	74LS192N	.68	74LS247N	.89	74LS280N	2.69	74LS326N	1.95	74LS393N	1.87		

Zilog NEW LOW PRICES

Z80-CPU	2.5 MHz	8.45	Z80-SIO/0	4.0 MHz	28.56
Z80-CPU	4.0 MHz	9.45	Z80-SIO/1	2.5 MHz	22.45
Z80-PIO	2.5 MHz	5.98	Z80-SIO/2	2.5 MHz	22.45
Z80-PIO	4.0 MHz	7.65	Z80-SIO/2	4.0 MHz	28.56
Z80-CTC	2.5 MHz	5.98	Z80-SIO/9	2.5 MHz	16.85
Z80-CTC	4.0 MHz	7.65	Z80A-SIO/9	4.0 MHz	21.54
Z80-DMA	2.5 MHz	18.65	Z80-DART	2.5 MHz	14.45
Z80-DMA	4.0 MHz	22.95	Z80A-DART	4.0 MHz	17.60

MICROPROCESSOR CHIP SETS

Part No.	Price	Part No.	Price	Part No.	Price	Part No.	Price
8080A CPU	5.45	8228	4.98	6800 CPU	5.95	6502 CPU	9.45
8085 CPU	9.95	8251	6.95	6802 CPU	11.65	6504 CPU	9.45
8212	2.50	8253	9.95	6810	3.50	6505 CPU	9.45
8214	3.65	8255	5.95	6821	3.50	6520	6.45
8216	2.50	8257	10.95	6850	3.50	6522	9.95
8224	3.45	8259	12.95	6852	3.50	6532	13.95
8226	2.50					6551	13.95

74S SCHOTTKY

74S00N	.48	74S37N	1.29	74S134N	.76	74S168N	4.98	74S241N	4.95	74S373N	3.95
74S02N	.52	74S38N	1.29	74S135N	1.56	74S169N	4.98	74S244N	4.95	74S374N	3.95
74S03N	.52	74S40N	.48	74S138N	1.18	74S174N	1.29	74S251N	1.65	74S412N	2.98
74S04N	.52	74S51N	.52	74S139N	1.18	74S175N	1.29	74S253N	7.65	74S470N	7.95
74S05N	.52	74S74N	.79	74S140N	1.36	74S181N	4.85	74S257N	1.65	74S471N	9.95
74S08N	.52	74S85N	2.20	74S151N	1.19	74S182N	3.98	74S258N	1.65	74S472N	16.85
74S09N	.52	74S88N	1.20	74S153N	1.19	74S189N	15.65	74S260N	1.65	74S474N	26.85
74S10N	.52	74S112N	1.20	74S167N	1.15	74S194N	4.56	74S274N	19.95	74S476N	9.95
74S11N	.52	74S114N	1.20	74S158N	1.29	74S195N	1.89	74S275N	19.95	74S478N	24.95
74S20N	.52	74S124N	2.65	74S161N	3.95	74S201N	12.95	74S280N	2.84		
74S30N	.52	74S132N	1.48	74S162N	4.45	74S225N	9.65	74S283N	3.99		
74S32N	.89	74S133N	1.89	74S163N	3.95	74S240N	4.95	74S299N	6.98		

LINEAR I.C.'s

LM301AN-8	.34	LM324N	.52	LM741CN-8	.32
LM304CH	.89	LM339N	.52	LM747CN-14	.59
LM307N-8	.29	LM348N-14	.99	LM748CN-8	.39
LM309N-8	.52	LM358N-8	.42	LM309N-8	.42
LM309CH	.95	LM555N-8	.29	LM1488N-14	.69
LM309N	1.58	LM556N-14	.48	LM1489N-14	.69
LM310H	1.49	LM723CN	.89	LM3048N-14	.99
LM311N-8	.59	LM723CN-14	.48	LM307N-14	.55
LM317T	1.36	LM723CN-8	1.75	LM3403N-14	.89
(TO-320)		LM733CN-14	1.59	LM3900N	.49
LM318N-8	1.45	LM733CN-8	1.29	LM4136N-14	.99
LM318CH	1.75	LM741CH	.65	ULN2003AN	.89

DUAL-IN-LINE—LOW PROFILE—I.C. SOCKETS

CONTACTS	PRICE	CONTACTS	PRICE
8 PIN	.07	22 PIN	.21
14 PIN	.11	24 PIN	.23
18 PIN	.13	28 PIN	.27
18 PIN	.17	40 PIN	.39
20 PIN	.19		

• LOWEST PRICES ANYWHERE FOR THE HIGHEST QUALITY. AN UNBEATABLE COMBINATION.

CMOS

CD4001BE	.21	CD4026BE	1.98	CD4088BE	.27	CD4519BE	.54
CD4002BE	.21	CD4027BE	.52	CD4099BE	.27	CD4520BE	.69
CD4006BE	.85	CD4028BE	.59	CD4070BE	.39	CD4522BE	.89
CD4007BE	.32	CD4029BE	.84	CD4072BE	.24	CD4526BE	1.25
CD4008BE	.74	CD4030BE	.46	CD4073BE	.29	CD4527BE	1.59
CD4009BE	.52	CD4033BE	1.98	CD4075BE	.29	CD4528BE	.86
CD4010BE	.52	CD4034BE	2.88	CD4076BE	.79	CD4531BE	.86
CD4011BE	.24	CD4035BE	.96	CD4078BE	.32	CD4532BE	1.12
CD4012BE	.24	CD4040BE	.84	CD4081BE	.24	CD4539BE	.84
CD4013BE	.36	CD4041BE	1.79	CD4082BE	.24	CD4543BE	1.98
CD4014BE	.69	CD4042BE	.86	CD4085BE	.58	CD4553BE	2.89
CD4015BE	.69	CD4043BE	.99	CD4086BE	.75	CD4555BE	.64
CD4016BE	.36	CD4044BE	.76	CD4093BE	.75	CD4556BE	.84
CD4017BE	.69	CD4046BE	.84	CD4099BE	1.98	CD4581BE	1.99
CD4018BE	.59	CD4047BE	.8				

100W CLASS A POWER AMP KIT

Dynamic Bias Class "A" circuit design makes this unit unique in its class. Crystal clear, 100 watts power output will satisfy the most picky fans. A perfect combination with the TA-1020 low T.I.M. stereo pre-amp.

Specifications:

- Output power: 100W RMS into 8-ohm
125W RMS into 4-ohm
- Frequency response: 10Hz - 100 KHz
- T.H.D.: less than 0.008%
- S/N ratio: better than 80dB
- Input sensitivity: 1V max.
- Power supply: $\pm 40V @ 5 amp$



TA-1000 KIT
\$51.95
Power transformer
\$15.00 each

PROFESSIONAL 10 OCTAVE STEREO GRAPHIC EQUALIZER!!



Graphic equalizer have been used for years in sound studios and concert arenas but were too expensive to be considered for home use. Now we offer you the facility at an affordable price. This unit can extend your control of your Hi-Fi system by minimizing the non-linearities of the combined speaker/room system. Fantastic features as follows:

- 10 double slide controls for two channels
- Cut out rumble, surface noise and hiss
- Minimizes speaker/room non-linearities
- Frequency response from 30Hz to 16KHz
- 10 tone controls plus defeat, monitor and tape selector.
- Control range $\pm 12dB$ in 10 octaves (30Hz, 60Hz, 120Hz, 240Hz, 500Hz, 1KHz, 2KHz, 4KHz, 8KHz, 16KHz.)
- Operating voltage 117V 50/60Hz.

FACTORY ASSEMBLED UNIT, NOT A KIT
SPECIAL PRICE \$69.50 ea.

SUB MINI SIZE FET CONDENSER MICROPHONE



Specification:

Sensitivity: $-65dB \pm 3dB$
FEQ. Response: 50 Hz - 8 KHz
Output Impedance: 1K ohm max.
Polar Pattern: Omni-directional
Power Supply: 1.5V 10V D.C.
Sound Pressure Level: Max. 120dB
EM4RP \$2.50 ea. or 2 for \$4.50

NEW MARK III 9 Steps 4 Colors LED VU

Stereo level indicator kit with arc-shape display panel!!! This Mark III LED level indicator is a new design PC board with an arc-shape 4 colors LED display (change color from red, yellow, green and the peak output indicated by rose). The power range is very large, from $-30dB$ to $+5dB$. The Mark III indicator is applicable to 1 watt - 200 watts amplifier operating voltage is 3V - 9V DC at max 400 MA. The circuit uses 10 LEDs per channel. It is very easy to connect to the amplifier. Just hook up with the speaker output!

IN KIT FORM \$18.50

2 WATT AUDIO AMP

Pre assembled units. All you need is to hook up the speaker and the volume control. Supply voltage from 9V - 15V D.C. measures only 2" x 3 1/2", making it good for portable or discrete applications. Comes with hook up data.



BUY 2 FOR
\$4.99

MARK IV 15 STEPS LED POWER LEVEL INDICATOR KIT

This new stereo level indicator kit consists of 36 4-color LED (15 per channel) to indicate the sound level output of your amplifier from $-36dB$ to $+3dB$. Comes with a well-designed silk screen printed plastic panel and has a selector switch to allow floating or gradual output indicating. Power supply is 6V - 12V D.C. with THG on board input sensitivity controls. This unit can work with any amplifier from 1W to 200W!

Kit includes 70 pcs. driver transistors, 38 pcs. matched 4-color LED, all other electronic components, PC board and front panel.



MARK IV KIT \$31.50



MARK V 15 STEPS LED POWER OUTPUT INDICATOR KIT

All functions same as Mark IV but this is with heavy duty aluminum front plate and case. Can be easily slot into the front panel of your auto, truck or boat. Operates on 12V DC.



\$41.50 EACH KIT

BATTERY POWERED FLUORESCENT LANTERN

MODEL 888 R

FEATURES



- Circuitry: designed for operation by high efficient, high power silicon transistor which enable illumination maintain in a standard level even the battery supply drops to a certain low voltage.
- 9" 6W cool/daylight miniature fluorescent tube.
- 8 x 1.5V UM-1 (size D) dry cell battery.
- Easy sliding door for changing batteries.
- Stainless reflector with wide angle increasing illumination of the lantern.

\$10.50 EA

30W + 30W STEREO HYBRID AMPLIFIER KIT

It works in 12V DC as well! Kit includes 1 PC SANYO STK-043 stereo power amp. IC LM 1458 as pre amp, all other electronic parts, PC Board, all control pots and special heat sink for hybrid. Power transformer not included. It produces ultra hi-fi output up to 60 watts (30 watts per channel) yet gives out less than 0.1% total harmonic distortion between 100Mz and 10KHz.



\$32.50 PER KIT

5W AUDIO AMP KIT



2 LM 380 with Volume Control
Power Supply 6 18V DC
ONLY \$6.00 EACH

PROFESSIONAL PANEL METERS



Type MU-52E

All meters white face with black scales. Plastic cover.

- A. 0-50UA 8.50 ea.
- B. 0-30VDC 8.50 ea.
- C. 0-50VDC 8.50 ea.
- D. 0-3ADC 9.00 ea.
- E. 0-100VDC 9.00 ea.

SPECIAL 0.5" LED ALARM CLOCK MODULE

ASSEMBLED! NOT A KIT!

Features: • 4 digits 0.5" LED Displays • 12 hours real time format • 24 hours alarm audio output • 59 min. countdown timer • 10 min. snooze control.



ONLY \$7.00 EACH
SPECIAL TRANSFORMER FOR CLOCK
\$2.50

DIGITAL AUTO SECURITY SYSTEM

4 DIGITS PERSONAL CODE!!

SPECIAL \$19.95



- proximity triggered
- voltage triggered
- mechanically triggered

This alarm protects you and itself! Entering protected area will set it off, sounding your car horn or siren you add. Any change in voltage will also trigger the alarm into action. If cables within passenger compartment are cut, the unit protects itself by sounding the alarm.

3-WAY PROTECTION!
All units factory assembled and tested - Not a kit!

SANYO HYBRID AUDIO POWER AMPLIFIER I.C.



Typical ratings

Operating case temp. 85°C.
T.H.D. = 0.5% $f = 20 \sim 20KHz$
Input resistance $P_o = 0.1W 30K\Omega$
Power band width 20Hz - 20KHz
Freq. response 10Hz - 100KHz
Output resistance = 8Ω

With built in protection circuit.

All units come with data sheet.

PART	OUTPUT (W)	SUPPLY VOLTAGE	PRICE
STK040	10W+10W Stereo	$\pm 16V$ D.C.	\$14.50
STK041	15W+15W Stereo	$\pm 20V$ D.C.	\$18.50
STK043	20W+20W Stereo	$\pm 22V$ D.C.	\$22.50
STK054	23 WATTS	$\pm 23V$ D.C.	\$13.50
STK056	30 WATTS	$\pm 22V$ D.C.	\$18.50
STK050	50 WATTS	$\pm 35V$ D.C.	\$26.50
STK070	70 WATTS	$\pm 42V$ D.C.	\$32.50
STK1050	100 WATTS	$\pm 50V$ D.C.	\$40.50

PROFESSIONAL FM WIRELESS MICROPHONE

TCT model WEM-16 is a factory assembled FM wireless microphone powered by an AA size battery. Transmits in the range of 88-108MHz with 3 transistor circuits and an omni-directional electric condenser. Element built-in plastic tube type case; mike is 6 1/4" long. With a standard FM radio, can be heard anywhere on a one-acre lot; sound quality was judged very good.

\$16.50

FLASHER LED

Unique design combines a jumbo red LED with an IC flasher chip in one package. Operates directly from 5V-7V DC. No dropping resistor needed. Pulse rate 3Hz @ 5V 20mA.

2 for \$2.20

BIPOLAR LED RED/GREEN


2 colors in one LED, green and red, changes color when reverse voltage supply. Amazing!

2 FOR \$1.60

LCD CLOCK MODULE!

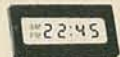• 0.5" LCD 4 digits display • X'tal controlled circuits • D.C. powered (1.5V battery) • 12 hr. or 24 hr. display • 24 hr. alarm set • 60 min. countdown timer • On board dual back-up lights • Dual time zone display • Stop watch function.

NIC1200 (12 hr) \$24.50 EA.
NIC2400 (24 hr) \$26.50 EA.



SANYO UHF VARACTOR TUNER

For UHF CH 14 - 83

Tuning voltage +1V - +28V D.C. Input impedance 75 OHM. I.F. band width 7 - 16 MHz. Noise figure 11.5 dB MAX. Size 2 1/4" x 1 1/4" x 3/4". Supply voltage 15V D.C. Sound I.F. = 58.0 MHz. Video I.F. = 62.5 MHz



All units are brand new from Sanyo.
MODEL 115-B-405A
\$35.00 EACH

FLUORESCENT LIGHT DRIVER KIT



With Case Only
\$6.50 Per Kit

12V DC POWERED
Lights up 8 ~ 15 Watt Fluorescent Light Tubes. Ideal for camper, outdoor, auto or boat. Kit includes high voltage coil, power transistor, heat sink, all other electronic parts and PC Board, light tube not included!

SUPER FM WIRELESS MIC KIT — MARK III



FMC-105
\$11.50 PER KIT

This new designed circuit uses high FET. FET transistors with 2 stages pre amp. Transmits FM Range (88-120 MHz) up to 2 blocks away and with the ultra sensitive condenser microphone that comes with the kit, allows you to pick up any sound within 15 ft. away! Kit includes all electronic parts, OSC coils, and P.C. Board. Power supply 9V D.C.

PRESS-A-LIGHT SELF GENERATED FLASHLIGHT



EXCLUSIVE!! \$3.95 ea
Model F-179

Never worry about battery, because it has none! Easy to carry in pocket and handy to use. Ideal for emergency light. It generates its own electricity by squeezing grip lever. Put one in your car, boat, camper or home. You may need it some time!

ELECTRONIC DUAL SPEAKER PROTECTOR



Cut off when circuit is shorted or over load to protect your amplifier as well as your speakers. A must for OCL circuits.

KIT FORM
\$8.75 EA.

"FISHER" 30 WATT STEREO AMP



Super Buy
Only \$18.50

Kit includes 2 pcs. Fisher PA 301 Hybrid IC all electronic parts with PC Board. Power supply \pm 16V DC (not included). Power band with (KF 1% \pm 3dB). Voltage gain 33dB. 20Hz - 20KHz.

SPACE WAR SOUND GENERATOR BOARD



Brand new preassembled module for a toy factory. The board gives out 6 different selectable space sound with LED light effect. Sounds include UFO take-off, space gun blast, wave, and space chime. 7 LED on the board will work with the sound. Requires 9V battery to operate. Speaker not included. SPECIAL \$3.99 EACH SPEAKER \$1.25 EACH

ELECTRONIC PIEZO BEEP BUZZER



Unique surplus $\frac{1}{2}$ " Dia. piezo ceramic disc on circuit board gives a distinct high freq. buzz. Unit contains an I.C., 2 caps, 6 resistors and is already preassembled. Requires 9V battery to operate. SPECIAL 2 FOR \$2.99

2 BIT COUNTER, WARBLE PULSE ALARM BOARD




This new assembly easily converts to a counter, stop watch, warble and pulse alarm generator by adding a few components. We supply the data and typical applications. Requires 9V battery to operate. SPECIAL 2 FOR \$1.99

PUSH-BUTTON SWITCH



N/Open Contact
Color: Red, White, Blue, Green, Black
3/\$1.00
N/Close also Available
50¢ each
LARGE QTY. AVAILABLE

HEAVY DUTY CLIP LEADS

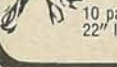

10 pairs — 5 colors Alligator clips on a 22" long lead. Ideal for any testing.
\$2.20/pack

BATTERIES

PK/\$10.00
2 PK/\$19.00



NICKEL CADMIUM BATTERY PACK 'D' SIZE

ILLUSTRATED LESS COVER

Output: 3.6 Volts @ 3.0 Amp/Hour. Consists of three each, 1.2 Volt 'D' size Nickel Cadmium Cells stacked and plastic film encapsulated. Tabs are provided at each end for electrical connections. The individual cells can be cut apart if desired. Rated recharge rate is 30 mA, 14-18 hours. Size: 1 $\frac{1}{4}$ " dia. x 7" long. New. Shpg. Wt. each pack, 1 lb.

"C" SIZE BATTERY PACK



10 C size ni-cd battery in dng pack, gives out 12.5V D.C. 1.8 amp per hour. All fresh code, pull-out from movie cameras. Can be disconnected to use as single c cells. Hard to find \$15.00 per pack of 10 batteries

NI-CD BATTERY SALE



12V Pack 450 MZ/HR Size 3" x 1" x 2" \$8.00 PER PACK
4 AA Pack 450 MA/HR \$3.50 PER PACK

All above batteries are used but late date code and we guarantee to take back all bad ones for exchange.

ELECTRONIC PIN BALL MACHINE



That sounds and plays like the real thing. All units are brand new but without the case. Functions of the game include double flipper control, kicker control, 1-4 players, 3 speed ball control, tilt switch, automatic score, extra bonus cave and many more. All solid state with LED panel, no moving parts. Requires 9V battery to operate, speaker not included.

A perfect gift for yourself or friends.
SPECIAL \$8.99 EACH
SPEAKER \$1.25 EACH

ULTRASONIC SWITCH KIT



Kit includes the Ultra Sonic Transducers, 2 PC Boards for transmitter and receiver. All electronic parts and instructions. Easy to build and a lot of uses such as remote control for TV, garage door, alarm system or counter. Unit operates by 9-12 DC. \$15.50

COMPLETE TIME MODULE



0.3" digits LCD Clock Module with month and date, hour, minute and seconds. As well as stop watch function!! Battery and back up light is with the module. Size of the module is 1" dia. Ideal for use in auto panel, computer, instrument and many others! \$8.95 EACH

SOUND ACTIVATED SWITCH



\$1.75 ea.

All parts completed on a PC Board SCR will turn on relay, buzzer or trigger other circuit for 2 - 10 sec. (adjustable). Ideal for use as door alarm, sound controlled toys and many other projects. Supply voltage 4.5V 9V D.C. 2 for \$3.00

FM WIRELESS MIC KIT



It is not a pack of cigarettes. It is a new FM wireless mic kit! New design PC board fits into a plastic cigarette box (case included). Uses a condenser microphone to allow you to have a better response in sound pick-up. Transmits up to 350 ft.! With an LED indicator to signal the unit is on #FMM2. KIT FORM \$7.95

REGULATED DUAL VOLTAGE SUPPLY KIT



\pm 4 30V DC 800 MA adjustable, fully regulated by Fairchild 78MG and 79MG voltage regulator I.C. Kit includes all electronic parts, filter capacitors, I.C., heat sinks and P.C. board.

\$12.50 PER KIT

AA SIZE NI-CD SPECIAL SALE

RECHARGEABLE BATTERIES LIMITED QUANTITY AVAILABLE

4 FOR \$6.00

SUB MINIATURE TOGGLE SWITCH 6 AMP 125V A.C.

SPDT	\$1.20	
SPDT MOMENTARY	\$1.40	
DPDT	\$1.80	
DPDT MOMENTARY	\$1.80	
DPDT (CENTER OFF)	\$2.20	
3PDT	\$2.20	
3PDT (CENTER OFF)	\$2.50	
4PDT	\$2.80	
4PDT (CENTER OFF)	\$3.80	

POWER SUPPLY KIT

0-30V D.C. REGULATED
Uses UA723 and ZN3055 Power TR output can be adjusted from 0-30V, 2 AMP. Complete with PC board and all electronic parts. Transformer for Power Supply, 0-30 Power Supply 2 AMP 24V x 2 \$8.50 \$10.50 each



I.C. TEST CLIPS

Same as the E-Z clips With 20" Long Leads \$2.75 In Black and Red Colors per pair



SOUND GENERATOR I.C.

Creates almost any type of sound — gun shot, explosion, train, car crash, star war, birds, organ ext. A built-in audio amplifier provides high level output. Operates from one 9V battery, 28 pin dip; we supply the datas. \$2.90 EACH



ELECTRONIC SWITCH KIT

CONDENSER TYPE
Touch On Touch Off uses 7473 I.C. and 12V relay \$5.50 each



1 WATT AUDIO AMP

All parts are pre-assembled on a mini PC Board. Supply Voltage 6 9V D.C. SPECIAL PRICE \$1.95 ea



LOW TIM DC STEREO PRE-AMP KIT TA-10 20

Incorporates brand-new D.C. design that gives a frequency response from 0Hz — 100KHz \pm 0.5dB! Added features like tone defeat and loudness control let you tailor your own frequency supplies to eliminate power fluctuation! Specifications: • T.H.D. less than .005% • T.I.M. less than .005% • Frequency response: DC to 100KHz \pm 0.5dB • RIAA deviation: \pm 0.2dB • S/N ratio: better than 70dB • Sensitivity: Phono 2MV 47K/Aux. 100MV 100K • Output level: 1.3V • Max. output: 15V • Tone control: bass \pm 10dB @ 50Hz/treble \pm 10dB @ 15Hz • Power supply: \pm 24 D.C. @ 0.5A Kit comes with regulated power supply, all you need is a 48V C.T. transformer @ 0.5A.

ONLY \$44.50 X'former \$4.50 ea.



SOLID STATE ELECTRONIC BUZZER

Mini size 1" x $\frac{3}{4}$ " x $\frac{3}{4}$ " Supply voltage 1.5V - 12V Ideal for Alarm or Tone Indicator \$1.50 each



FORMULA INTERNATIONAL INC.

11/80

Shipping and Handling Charges	Under \$50.00 purchase		Over \$50.00 purchase	
	Inside California	Outside Calif. (includes Mexico & Canada)	Inside California	Outside Calif. (includes Mexico & Canada)
Orders	15%	15%	15%	15%
Minimum Order \$10.00/Calif. Residents Add 6% Sales Tax				
Phone Orders Accepted on Visa or MC ONLY, NO C.O.D./Store Hours 10-7 Mon. thru Sat.				

Send \$1.00 For Detailed Catalogue

12603 CRENSHAW BLVD., HAWTHORNE, CA 90250
PHONE: (213) 973-1921 • (213) 679-6152

National Semiconductor Clock Modules

12VDC AUTOMOTIVE/ INSTRUMENT CLOCK



APPLICATIONS:

- In-dash auto clocks
- After-market auto/ RV clocks
- Aircraft/marine cks.
- 12VDC oper. instru.
- Portable/battery powered instruments.

Features: Bright 0.3" green display. Internal crystal time-base. 0.5 sec./day accur. Auto. display brightness control logic. Display color filterable to blue, blue-green, green & yellow. Complete—just add switches and lens.

MA1003 Module \$16.95

MA1023 .77" Low Cost Digital LED Clock Module 8.95
 MA1028 .77" Dig. LED Alarm Clock/Thermometer 18.95
 MA5035 .31" Low Cost Digital LED Clock/Timer 6.95
 MA1002 .5" LED Display Dig. Clock & Xformer 9.95

National Semiconductor RAM SALE



MM5290N-4 (MK4116/UPD416) . . . \$4.95 each
 16K DYNAMIC RAM (250NS)
 (8 EACH \$39.95) (100 EACH \$450.00/lot)

MM5290J-2 (MK4116/UPD416) . . . \$6.95 each
 16K DYNAMIC RAM (150NS)
 (8 EACH \$49.95) (100 EACH \$550.00/lot)

MM5298J-3A \$3.25 each
 8K DYNAMIC RAM (LOW HALF OF MM5290J) 200NS
 (8 EACH \$23.95) (100 EACH \$250.00/lot)

MM2114-3 \$5.95 each
 4K STATIC RAM (300NS)
 (8 EACH \$43.95) (100 EACH \$450.00/lot)

MM2114L-3 \$6.25 each
 4K STATIC RAM (LOW POWER 300NS)
 (8 EACH \$44.95) (100 EACH \$475.00/lot)

EPROM Erasing Lamp



- Erases 2708, 2716, 1702A, 5203Q, 5204Q, etc.
- Erases up to 4 chips within 20 minutes.
- Maintains constant exposure distance of one inch.
- Special conductive foam liner eliminates static build-up.
- Built-in safety lock to prevent UV exposure.
- Compact—only 7-5/8" x 2-7/8" x 2"
- Complete with holding tray for 4 chips.

UVS-11E \$79.50

Jumbo 6-Digit Clock Kit

- Four .630"ht. and two .300"ht. common anode displays
- Uses MM5314 clock chip
- Switches for hours, minutes and hold functions
- Hours easily viewable to 30 feet
- Simulated walnut case
- 115VAC operation
- 12 or 24 hour operation
- Includes all components, case and wall transformer
- Size: 6 1/2" x 3-1/8" x 1 1/4"

JE747 \$29.95

6-Digit Clock Kit

- Bright .300 ht. comm. cath. ode display
- Uses MM5314 clock chip
- Switches for hours, minutes and hold modes
- Hrs. easily viewable to 20 ft.
- Simulated walnut case
- 115 VAC operation
- 12 or 24 hr. operation
- Incl. all components, case & wall transformer
- Size: 6 1/2" x 3-1/8" x 1 1/4"

JE701 \$19.95

Regulated Power Supply

Uses LM309K. Heat sink provided. PC board construction. Provides a solid 1 amp @ 5 volts. Can supply up to ±5V, ±9V and ±12V with JE205 Adapter. Includes components, hardware and instructions. Size: 3 1/2" x 5" x 2 1/4"

JE200 \$14.95

ADAPTER BOARD

Adapts to JE200—±5V, ±9V and ±12V

DC/DC converter with +5V input. Toroidal hi-speed switching XFMR. Short circuit protection. PC board construction. Piggy-back to JE 200 board. Size: 3 1/2" x 2" x 9/16" H

JE205 \$12.95

MICROPROCESSOR COMPONENTS

8080A/8080A SUPPORT DEVICES

IN5290BA CPU	6.30
DP8212 8-Bit Input/Output	1.25
DP8214 Priority Interrupt Control	5.35
DP8216 Bi-Directional Bus Driver	3.49
DP8224 Clock Generator/Driver	3.39
DP8226 Bus Driver	3.49
CP8202 System Controller/Bus Driver	4.95
CP8208 System Controller	4.95
IN5243 I/O Expander for 8-Bit Series	9.35
IN5250 Asynchronous Comm. Element	36.95
CP8251 Prop. Comm. I/O (USART)	7.25
DP8253 Prop. Internal Timer	34.95
DP8255 Prop. Peripheral I/O (PPI)	34.95
DP8257 Prop. DMA Control	34.95
DP8259 Prop. Interrupt Control	34.95
DP8275 Prop. CRT Controller	49.95
DP8279 Prop. Keyboard/Display Interface	39.95
CP8280 Prop. Comm. I/O (USART)	34.95
DP8303 System Timing Element	6.95
DP8304 8-Bit Bi-Directional Receiver	3.95
DP8305 8-Bit Bi-Directional Receiver	2.95
DP8306 8-Bit Bi-Directional Receiver	3.95

6800/6800 SUPPORT DEVICES

MC6800 MPU	14.95
MC6802CP MPU with Clock and RAM	39.95
MC6818A 128-8 Static RAM	4.50
MC6821 Peripheral Inter. Adapt (MC6802)	7.49
MC6828 Priority Interrupt Controller	10.95
MC6828LL 2025-Bit ROM (MC6802)	14.95
MC6850 Asynchronous Comm. Adapter	6.95
MC6862 Synchronous Serial Data Adapter	6.95
MC6860 84800s Digital MC/DEM	23.95
MC6862 24000s Modulator	23.95
MC6865A Quad 3-State Bus Trans. (MC6826)	2.25

MICROPROCESSOR CHIPS

280 (80C) CPU (MC68000) (8MHz)	12.95
2801 (80C1) CPU (MC68000-1) (8MHz)	12.95
CDP1802 CPU	19.95
3900 MPU	34.95
10A2901 ADC CPU—8-Bit Slice (Comp. Temp. Grade)	19.95
MC5502 MPU w/Clock (8K Bytes Memory)	11.95
IN5803N-4 MPU—8-Bit (8MHz)	36.95
IN5803N-4 CPU—Spi. Chip 8-Bit (130bytes RAM)	18.95
IN5804N-4 CPU (2K Bytes RAM)	24.95
IN5807N-4 CPU—64 Bytes RAM	24.95
IN5807N-4 CPU w/Basic Micro Interpreter	29.95
78000 MPU	19.95
IN5800 CPU—16-Bit	29.95
IN5800JL MPU—16-Bit	29.95
TMS9901L MPU—16-Bit	35.95

SHIFT REGISTERS

MM500H Quad 8-Bit Dynamic	.50
MM501H Dual 50-Bit Dynamic	1.00
MM505H Dual 100-Bit Static	2.00
MM505H Dual 64-Bit Accumulator	3.00
MM1402 256-Bit Dynamic	3.95
MM5013 1000-Bit Dynamic/Accumulator	1.95
MM5014 5000-Bit Dynamic	2.95
MM5014H 1000-Bit Dynamic	3.95
MM5024N Octal 80-Bit	3.95
2514N Hex. 32-Bit Static	4.95
2522V Dual 132-Bit Dynamic	2.95
2524V 512-Bit Dynamic	2.95
2525V 1024-Bit Dynamic	2.95
2527V Dual 256-Bit Static	2.95
2528V Dual 256-Bit Static	4.00
2529V Dual 256-Bit Static	4.00
2529N Quad 80-Bit Static	2.95
331C1C File (Dual 80)	6.95

DATA ACQUISITION

AF120-1CN Universal Active Filter 2.5%	5.95
AF120-1CJ Touch Tone Low Pass Filter	19.95
AF120-1CJ Touch Tone Low Pass Filter	19.95
LM324AH Super Gain Op Amp	1.00
LM332C Constant Current Source	1.00
LM332C Temperature Transducer	1.40
LF356N JFET Input Op Amp	1.18
LF399N Sample & Hold Amplifier	2.95
LM399H Temp. Comp. Prec. Ref. (10ppm/C)	4.95
DAC08MLCN 8-Bit A/D Converter (1 LSB)	4.95
DAC08MLCN 8-Bit D/A Converter (0.75% Lin.)	2.25

DATA ACQUISITION (CONTINUED)

AD08MLCN 8-Bit A/D Converter (8-Ch. Multi.)	5.25
AD08MLCN 8-Bit A/D Converter (8-Ch. Multi.)	16.95
DAC108MLCN 10-Bit D/A Conv. Micro. Comp. (0.25%)	11.95
DAC108MLCN 10-Bit D/A Conv. Micro. Comp. (0.25%)	8.95
DAC108MLCN 10-Bit D/A Converter (0.25% Lin.)	6.49
DAC108MLCN 10-Bit D/A Converter (0.25% Lin.)	5.95
CD0403N 4-Ch. 8000 Hz Multiplexer	1.15
AY-5311 20K BAUD UART	5.95

RAM'S

296-1 Static	1.49
306-1 Dynamic	3.99
296-4 Static	3.95
306-4 Static	1.75
306-1 Static	1.75
296-4 Static	3.95
296-4 Static MDS	4.95
306-4 Static 600ns	5.95
306-4 Static 400ns Low Power	6.95
306-4 Static 300ns	7.49
306-4 Static 200ns Low Power	7.95
3628-1 Dynamic 500ns (housemarked)	4.95
38K Dynamic 200ns	4.95
49K Static 70ns	39.95
256-1 Static	3.95
MM5361 1024K Dynamic Fully Decoded	.25
2K-1 Dynamic	.95
MM5362/2307 4096K Dynamic	4.95
MM5362/24138 38K Dynamic 300ns (UPD416)	6.95
MM5362-3A 38K Dyn. 200ns (lower is of MM5362)	1.95
4096K Static	1.95
UPD416/MK4027 4K Dynamic 16-bit	14.95
TMS5004-8N-4 8K Static	34.95
TMS5004S 16K Static	10.95

PROMS/EPROMS

1702A 2K UV Erasable PROM	3.95
2708 8K EPROM	9.95
TMS2716 16K EPROM (4V, +5V, +12V)	17.95
27161 (2716T) 16K EPROM (Single +5V)	17.95
27321 (2732T) 32K EPROM	49.95
2756 8K EPROM (400ns) (Single +5V)	17.95
5103 2048 PROM	14.95
62521 (45180) 22x8 PROM (Open Collector)	19.95
62515 4096 Bipolar PROM	4.95
62512 (45280) 32x8 Tri-State Bipolar PROM	4.95
62518 8K PROM	29.95

ROM'S

25131 (2513) Character Generator (Upper Case)	9.95
25131 (2513) Character Generator (Lower Case)	9.95
2513A Character Generator	10.95
MM5290V 2048-Bit Read Only Memory	1.95

NMOS READ ONLY MEMORIES

MC68M120P 128-8/16 128-8/16 w/Driver	13.00
MC68M130P 128-8/16 Math Symbol & Pictures	13.00
MC68M170P 128-8/16 Alpha Control Char. Gen.	13.00

MICROPROCESSOR MANUALS

M-290 User Manual	7.50
M-COP180 User Manual	7.50
M-360 User Manual	5.00

SPECIAL FUNCTION

D50005CN Dual MOS Clock Driver (BM2)	3.50
D50005CN Dual MOS Clock Driver (DM2)	3.50
IN5177N-1 Flexible Controller	24.95
IN5296N-1 Communication Chip	38.95
MM5367N Microprocessor Real Time Clock	8.95
MM5368N Microprocessor Compatible Clock	11.95
MC68M24N Microcontroller with 64-Digit RAM and Direct LED Drive	6.95
MC68M24N Microcontroller with 64-Digit RAM and Direct LED Drive w/In-Bus Int.	7.49
COPI60N 10-Seq./VAC Fluor. Driver (20-pin pkg.)	3.25

TELEPHONE/KEYBOARD CHIPS

AY-5310 Repertory Dialer	14.95
AY-5300 Repertory Dialer	14.95
AY-5300 CMOS Clock Generator	4.95
AY-5300 Keyboard Encoder (8 keys)	11.95
AY-5300 Keyboard Encoder (16 keys)	7.95
AY-5300 Keyboard Encoder (20 keys)	5.75
AY-5300 Push Button Pulse Dialer	1.95
MM5368N 16/34-Key Serial Keyboard Encoder	8.95

JOYSTICKS



JS-5K 5K Linear Taper Pots \$5.25
 JS-100K 100K Linear Taper Pots \$4.95
 JVC-40 40K (2) Video Controller in case \$5.95

AC and DC Wall Transformers



Ideal for use with clocks, pumps, power supplies or any other type of AC or DC application.

Part No.	Input	Output	Price
AC 250	117V/60Hz	12 VAC 250mA	\$3.95
AC 500	117V/60Hz	12 VAC 500mA	\$4.95
AC 1000	117V/60Hz	12 VAC 1 amp	\$5.95
DV9200	117V/60Hz	9 VDC 200mA	\$3.25
DC 900	120V/60Hz	9 VDC 500mA	\$3.95

CONNECTORS



DB25P	D-Subminiature Plug	\$2.95
DB25S	D-Subminiature Socket	\$3.50
DB51226	Cover for DB25P/S	\$1.75
22/44SE	P.C. Edge (22/44 Pin)	\$2.95
UG88/U	BNC Plug	\$1.79
UG89/U	BNC Jack	\$3.79
UG175/U	UHF Adapter	\$ 4.95
SO239	UHF Panel Recp.	\$1.29
PL258	UHF Adapter	\$1.60
PL259	UHF Plug	\$1.60
UG260/U	BNC Plug	\$1.79
UG104/U	BNC Bulkhead Recp.	\$1.29

TRS-80 16K Conversion Kit

Expand your 4K TRS-80 System to 16K. Kit comes complete with:

- * 8 ea. MM5290 (UPD416/4116) 16K Dyn. Rams (*NS)
- * Documentation for Conversion

TRS-16K2 *150NS \$49.95
 TRS-16K4 *250NS \$39.95

JE610 ASCII Encoded Keyboard Kit



The JE610 ASCII Keyboard Kit can be interfaced into most any computer system. The kit comes complete with an industrial grade keyboard switch assembly (62 keys), IC's, sockets, connector, electronic components and a double-sided printed wiring board. The keyboard assembly requires +5V @ 150mA and -12V @ 10 mA for operation. Features: 60 keys generate the 126 characters, upper and lower case ASCII set. Fully buffered. Two user-definable keys provided for custom applications. Caps lock for upper-case only alpha characters. Utilizes a 2376 (40-pin) encoder read-only memory chip. Outputs directly compatible with TTL/DTL or MOS logic arrays. Easy interfacing with a 16-pin dip or 16-pin edge connector. Size: 3 1/2" H x 14 1/2" W x 9 1/2" D

JE610/DTE-AK (as pictured above) . . . \$124.95
 JE610 Kit 62-Key Keyboard, PC Board, & Components (no case) . . . \$ 79.95
 K62 62-Key Keyboard (Keyboard only) . . . \$ 34.95
 DTE-AK (case only — 3 1/2" H x 14 1/2" W x 9 1/2" D) \$ 49.95

JE600 Hexadecimal Encoder Kit




FULL 8-BIT LATCHED OUTPUT 19-KEY KEYBOARD

The JE600 Encoder Keyboard Kit provides two separate hexadecimal digits produced from sequential key entries to allow direct programming for 8-bit microprocessor or 8-bit memory circuits. Three additional keys are provided for user operations with one having a bistable output available. The outputs are latched and monitored with 9 LED readouts. Also included is a key entry strobe. Features: Full 8-bit latched output for microprocessor use. Three user-definable keys with one being bistable operation. Debounce circuit provided for all 19 keys. 9 LED readouts to verify entries. Easy interfacing with standard 16-pin IC connector. Only ±5VDC required for operation. Size: 3 1/2" H x 8 1/2" W x 8 1/4" D

JE600/DTE-HK (as pictured above) . . . \$99.95
 JE600 Kit 19-Key Hexadec. Keyboard, PC Board & Cmpnts. (no case) . . . \$59.95
 K19 19-Key Keyboard (Keyboard only) . . . \$14.95
 DTE-HK (case only — 3 1/2" H x 8 1/2" W x 8 1/4" D) \$44.95

DESIGNER'S SERIES

Blank Desk-Top Electronic Enclosures

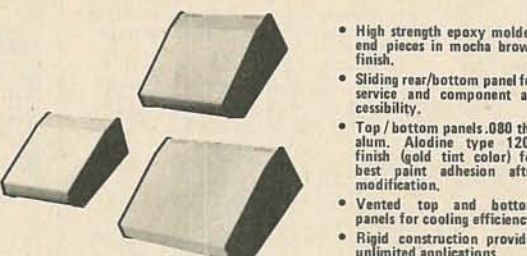

- High strength epoxy molded end pieces in mocha brown finish.
- Sliding rear/bottom panel for service and component accessibility.
- Top / bottom panels .080 thick aluminum. Alodine type 1200 finish (gold tint color) for best paint adhesion after modification.
- Vented top and bottom panels for cooling efficiency.
- Rigid construction provides unlimited applications.

CONSTRUCTION: The "DTE" Blank Desk Top Electronic Enclosures are designed to blend and complement today's modern computer equipment and can be used in both industrial and home. The end pieces are precision molded with an internal slot (all around) to accept both top and bottom panels. The panels are then fastened to 1/4" thick tabs inside the end pieces to provide maximum rigidity to the enclosure. For ease of equipment servicing, the rear/bottom panel slides back on slotted tracks while the rest of the enclosure remains intact. Different panel widths may be used while maintaining a common profile outline. The molded end pieces can also be painted to match any panel color scheme.

Enclosure Model No.	Panel Width	PRICE
DTE-8	8.00"	\$29.95
DTE-11	10.65"	\$32.95
DTE-14	14.00"	\$34.95

\$10.00 Min. Order — U.S. Funds Only
 Calif. Residents Add 6% Sales Tax
 Postage — Add 5% plus \$1 Insurance

Spec Sheets — 25¢
 Send 41¢ Postage for your FREE 1981 JAMECO CATALOG

PHONE ORDERS WELCOME
 (415) 592-8097

Jameco ELECTRONICS

MAIL ORDER ELECTRONICS — WORLDWIDE
 1355 SHOREWAY ROAD, BELMONT, CA 94002
 PRICES SUBJECT TO CHANGE

1/81

7400			
SN7400N	.25	SN74156N	.79
SN7401N	.25	SN74157N	.79
SN7402N	.25	SN74160N	.89
SN7403N	.25	SN74161N	.89
SN7404N	.25	SN74162N	.89
SN7405N	.25	SN74163N	.89
SN7406N	.25	SN74164N	.89
SN7407N	.25	SN74165N	.89
SN7408N	.25	SN74166N	.89
SN7409N	.25	SN74167N	1.25
SN7410N	.25	SN74168N	1.25
SN7411N	.25	SN74169N	1.25
SN7412N	.25	SN74170N	1.95
SN7413N	.40	SN74171N	.99
SN7414N	.40	SN74172N	.99
SN7415N	.40	SN74173N	.99
SN7416N	.40	SN74174N	.99
SN7417N	.40	SN74175N	.99
SN7418N	.40	SN74176N	.99
SN7419N	.40	SN74177N	.99
SN7420N	.40	SN74178N	.99
SN7421N	.40	SN74179N	.99
SN7422N	.40	SN74180N	.99
SN7423N	.40	SN74181N	2.25
SN7424N	.40	SN74182N	.79
SN7425N	.40	SN74183N	2.49
SN7426N	.40	SN74184N	2.49
SN7427N	.40	SN74185N	2.49
SN7428N	.40	SN74186N	2.49
SN7429N	.40	SN74187N	2.49
SN7430N	.40	SN74188N	2.49
SN7431N	.40	SN74189N	2.49
SN7432N	.40	SN74190N	2.49
SN7433N	.40	SN74191N	2.49
SN7434N	.40	SN74192N	2.49
SN7435N	.40	SN74193N	2.49
SN7436N	.40	SN74194N	2.49
SN7437N	.40	SN74195N	2.49
SN7438N	.40	SN74196N	2.49
SN7439N	.40	SN74197N	2.49
SN7440N	.40	SN74198N	2.49
SN7441N	.40	SN74199N	2.49
SN7442N	.40	SN74200N	2.49
SN7443N	.40	SN74201N	2.49
SN7444N	.40	SN74202N	2.49
SN7445N	.40	SN74203N	2.49
SN7446N	.40	SN74204N	2.49
SN7447N	.40	SN74205N	2.49
SN7448N	.40	SN74206N	2.49
SN7449N	.40	SN74207N	2.49
SN7450N	.40	SN74208N	2.49
SN7451N	.40	SN74209N	2.49
SN7452N	.40	SN74210N	2.49
SN7453N	.40	SN74211N	2.49
SN7454N	.40	SN74212N	2.49
SN7455N	.40	SN74213N	2.49
SN7456N	.40	SN74214N	2.49
SN7457N	.40	SN74215N	2.49
SN7458N	.40	SN74216N	2.49
SN7459N	.40	SN74217N	2.49
SN7460N	.40	SN74218N	2.49
SN7461N	.40	SN74219N	2.49

74LS			
74LS00	.29	74LS192	1.15
74LS01	.29	74LS193	1.15
74LS02	.29	74LS194	1.15
74LS03	.29	74LS195	1.15
74LS04	.29	74LS196	1.15
74LS05	.29	74LS197	1.15
74LS06	.29	74LS198	1.15
74LS07	.29	74LS199	1.15
74LS08	.29	74LS200	1.15
74LS09	.29	74LS201	1.15
74LS10	.29	74LS202	1.15
74LS11	.29	74LS203	1.15
74LS12	.29	74LS204	1.15
74LS13	.29	74LS205	1.15
74LS14	.29	74LS206	1.15
74LS15	.29	74LS207	1.15
74LS16	.29	74LS208	1.15
74LS17	.29	74LS209	1.15
74LS18	.29	74LS210	1.15
74LS19	.29	74LS211	1.15
74LS20	.29	74LS212	1.15
74LS21	.29	74LS213	1.15
74LS22	.29	74LS214	1.15
74LS23	.29	74LS215	1.15
74LS24	.29	74LS216	1.15
74LS25	.29	74LS217	1.15
74LS26	.29	74LS218	1.15
74LS27	.29	74LS219	1.15
74LS28	.29	74LS220	1.15
74LS29	.29	74LS221	1.15
74LS30	.29	74LS222	1.15
74LS31	.29	74LS223	1.15
74LS32	.29	74LS224	1.15
74LS33	.29	74LS225	1.15
74LS34	.29	74LS226	1.15
74LS35	.29	74LS227	1.15
74LS36	.29	74LS228	1.15
74LS37	.29	74LS229	1.15
74LS38	.29	74LS230	1.15
74LS39	.29	74LS231	1.15
74LS40	.29	74LS232	1.15
74LS41	.29	74LS233	1.15
74LS42	.29	74LS234	1.15
74LS43	.29	74LS235	1.15
74LS44	.29	74LS236	1.15
74LS45	.29	74LS237	1.15
74LS46	.29	74LS238	1.15
74LS47	.29	74LS239	1.15
74LS48	.29	74LS240	1.15
74LS49	.29	74LS241	1.15
74LS50	.29	74LS242	1.15

74S			
74S00	.50	74S244	3.25
74S01	.50	74S245	1.45
74S02	.50	74S246	1.45
74S03	.50	74S247	1.35
74S04	.50	74S248	1.35
74S05	.50	74S249	1.35
74S06	.50	74S250	1.35
74S07	.50	74S251	1.35
74S08	.50	74S252	1.35
74S09	.50	74S253	1.35
74S10	.50	74S254	1.35
74S11	.50	74S255	1.35
74S12	.50	74S256	1.35
74S13	.50	74S257	1.35
74S14	.50	74S258	1.35
74S15	.50	74S259	1.35
74S16	.50	74S260	1.35
74S17	.50	74S261	1.35
74S18	.50	74S262	1.35
74S19	.50	74S263	1.35
74S20	.50	74S264	1.35
74S21	.50	74S265	1.35
74S22	.50	74S266	1.35
74S23	.50	74S267	1.35
74S24	.50	74S268	1.35
74S25	.50	74S269	1.35
74S26	.50	74S270	1.35
74S27	.50	74S271	1.35
74S28	.50	74S272	1.35
74S29	.50	74S273	1.35
74S30	.50	74S274	1.35
74S31	.50	74S275	1.35
74S32	.50	74S276	1.35
74S33	.50	74S277	1.35
74S34	.50	74S278	1.35
74S35	.50	74S279	1.35
74S36	.50	74S280	1.35
74S37	.50	74S281	1.35
74S38	.50	74S282	1.35
74S39	.50	74S283	1.35
74S40	.50	74S284	1.35
74S41	.50	74S285	1.35
74S42	.50	74S286	1.35
74S43	.50	74S287	1.35
74S44	.50	74S288	1.35
74S45	.50	74S289	1.35
74S46	.50	74S290	1.35
74S47	.50	74S291	1.35
74S48	.50	74S292	1.35
74S49	.50	74S293	1.35
74S50	.50	74S294	1.35

CA-LINEAR			
CA3013H	2.15	CA3099N	3.75
CA3023H	3.25	CA3099F	3.75
CA3031H	1.35	CA3130A	1.39
CA3046N	1.30	CA3140H	1.25
CA3059N	3.25	CA3160H	1.25
CA3060N	3.25	CA3161N	3.50
CA3089H	1.25	CA3096N	.85

CD-CMOS			
CD4000	.39	CD4082	.39
CD4001	.39	CD4083	.39
CD4002	.39	CD4084	.39
CD4003	.39	CD4085	.39
CD4004	.39	CD4086	.39
CD4005	.39	CD4087	.39
CD4006	.39	CD4088	.39
CD4007	.39	CD4089	.39
CD4008	.39	CD4090	.39
CD4009	.39	CD4091	.39
CD4010	.39	CD4092	.39
CD4011	.39	CD4093	.39
CD4012	.39	CD4094	.39
CD4013	.39	CD4095	.39
CD4014	.39	CD4096	.39
CD4015	.39	CD4097	.39
CD4016	.39	CD4098	.39
CD4017	.39	CD4099	.39
CD4018	.39	CD4100	.39
CD4019	.39	CD4101	.39
CD4020	.39	CD4102	.39
CD4021	.39	CD4103	.39
CD4022	.39	CD4104	.39
CD4023	.39	CD4105	.39
CD4024	.39	CD4106	.39
CD4025	.39	CD4107	.39
CD4026	.39	CD4108	.39
CD4027	.39	CD4109	.39
CD4028	.39	CD4110	.39
CD4029	.39	CD4111	.39
CD4030	.39	CD4112	.39
CD4031	.39	CD4113	.39
CD4032	.39	CD4114	.39
CD4033	.39	CD4115	.39
CD4034	.39	CD4116	.39
CD4035	.39	CD4117	.39
CD4036	.39	CD4118	.39
CD4037	.39	CD4119	.39
CD4038	.39	CD4120	.39
CD4039	.39	CD4121	.39
CD4040	.39	CD4122	.39

JE608 PROGRAMMER

2708 EPROM PROGRAMMER



43 segment Display Register 8 LED's for Hex Key entries 16 LED's (0' - F') for Address Register and 8 LED's for Data Memory Register. The Data Memory Register Display also has the EPROM Data Memory Register.

Development of microprocessor systems by means of a ribbon cable from the programmer panel lead to the EPROM socket on the microprocessor board.

Rapid stacking verification of programmed data addresses.

Reads data from a master or RAM's or serial RAM's with keyboard interface.

Allows manual stepping/advance/hold and down at any address location.

Specializes EPROM programming consisting of:

- A 16 Key Hexadecimal Keyboard assembly, Programmer Board assembly with 8 power supplies and a LED's Test Socket Panel Board.
- The Test Socket Board (Type: C.R.H.D. - 2708) with 2708 EPROM's.
- Compact size type enclosure. Color coordinated design case with light blue enamel and metal end caps in white finish. Size: 3 1/2" x 11 1/2" x 5 1/2", Weight: 5 lbs.

The JE608 EPROM Programmer is a completely self contained unit which is independent of computer control and requires no additional systems for its operation. The EPROM can be programmed from the Hexadecimal Keyboard or from a pre-programmed EPROM. The JE608 Programmer can simulate a programmed EPROM by the use of its internal RAM circuitry. This will allow you to test or protect a program for a system, prior to programming a chip. Any changes in the program can be entered directly into the memory circuitry with the Hexadecimal Keyboard so that re-loading the active program will not be necessary. The JE608 Programmer also contains a Programmer Board with 25 IC and including power supplies of: -5V, -12V and +5V. The Hexadecimal Keyboard and LED's Test Socket Panel Board are separate assemblies with the system.

JE608K KIT **\$399.95**
JE608A Assembled and tested **\$499.95**

DISCRETE LEADS

Type	Polarity	Ht	Price	Type	Polarity	Ht	Price
MAN 1	C.A.-red	.270	2.95	DL71	C.A.-red	.600	1.25
MAN 2	5x7 D.M.-red	.300	4.55	DL76	C.A.-red ± 1	.630	1.49
MAN 3	C.C.-red	.125	.25	DL37	C.C.-red	.600	1.49
MAN 4	C.C.-green	.300	1.25	DL50	C.C.-red	.600	1.49
MAN 54	C.C.-green	.300	1.25	DL3B	C.C.-red	.600	1.49
MAN 71	C.A.-red	.300	.75	FND358	C.C. ± 1	.357	.99
MAN 72	C.A.-red	.300	.75	FND359	C.C.	.357	.75
MAN 74	C.C.-red	.300	1.25	FND503	C.C. (FND500)	.500	.99
MAN 52	C.A.-green	.300	1.25	HC507	C.A. (FND510)	.500	.99
MAN 84	C.C.-yellow	.300	.99	HOSP-3401	C.A.-red	.800	1.50
MAN 3520	C.A.-orange	.300	.49	HOSP-3403	C.C.-red	.800	1.50
MAN 3630	C.A.-orange ± 1	.300	.99	5082-7613	C.C., R.H.D.-red	.300	1.25
MAN 3640	C.V.-orange	.300	.99	5082-7620	C.A., L.H.D.-yel.	.300	1.25
MAN 4610	C.A.-orange	.400	.99	5082-7621	C.C., R.H.D.-red	.300	1.25
MAN 6610	C.A.-orange-DD	.560	.99	5082-7730	C.A., L.H.D.-red	.300	.99
MAN 6630	C.A.-orange ± 1	.560	.99	5082-7731	C.A., R.H.D.-red	.300	1.25
MAN 6640	C.C.-orange-DD	.560	.99	5082-7790	C.A., L.H.D.-red	.430	1.75
MAN 6650	C.C.-orange	.560	.99	5082-7791	C.C., R.H.D.-red	.430	1.75
MAN 6660	C.A.-orange	.560	.99	5082-7860	C.C., R.H.D.-red	.430	1.75
MAN 6710	C.A.-red-DD	.560	.99	5082-7900	4x7 spg. dig. RHD	.600	22.00
MAN 6750	C.C.-red ± 1	.560	.99	5082-7902	4x7 spg. dig. LHD	.600	22.00
MAN 6780	C.C.-red	.560	.99	5082-7904	Photo Xistor Opto-Isol.	.900	19.95
DL704	C.C.-red	.300	1.25	47N2	Photo Xistor Opto-Isol.	.900	19.95
DL707	C.C.-red	.300	1.25	LIT-1	Photo Xistor Opto-Isol.	.900	19.95
DL728	C.C.-red	.500	1.45	MOC3010	Optically Isolated Driver	1.25	.00

POTENTIOMETERS

\$2.95 each 2 Watt @ 70°C ± 10% 7/8" Slotted Shaft Linear Taper Meets MIL-R-94

\$1.35 each 3/4 Watt @ 70°C 15 turn pot. Linear taper. Printed circuit. Ruff mount.

Part No.	RVANAY SD-102A	1K	Part No.	RVANAY SD-102A	1K
CMU 1001	RVANAY SD-102A	1K	30P-500hm	30P-500hm	30P-100K
CMU 5021	RVANAY SD-502A	5K	30P-1000hm	30P-100K	30P-200K
CMU 1031	RVANAY SD-103A	10K	30P-500hm	30P-20K	30P

7400

SN7400N	10	SN74123N	50
SN7401N	22	SN74123N	39
SN7402N	22	SN74124N	44
SN7403N	22	SN74128N	59
SN7404N	22	SN74132N	69
SN7405N	23	SN74136N	95
SN7406N	23	SN74138N	95
SN7407N	23	SN74141N	99
SN7408N	26	SN74142N	95
SN7409N	23	SN74143N	2.95
SN7410N	22	SN74144N	2.95
SN7411N	29	SN74145N	62
SN7412N	20	SN74147N	1.90
SN7413N	39	SN74148N	1.20
SN7414N	59	SN74150N	99
SN7415N	29	SN74151N	67
SN7416N	29	SN74152N	67
SN7417N	29	SN74153N	67
SN7418N	29	SN74154N	1.19
SN7419N	29	SN74155N	82
SN7420N	22	SN74156N	89
SN7421N	35	SN74157N	89
SN7422N	29	SN74158N	1.65
SN7423N	29	SN74159N	82
SN7424N	29	SN74160N	95
SN7425N	29	SN74161N	95
SN7426N	29	SN74162N	99
SN7427N	29	SN74163N	99
SN7428N	29	SN74164N	99
SN7429N	29	SN74165N	97
SN7430N	29	SN74166N	1.20
SN7431N	29	SN74167N	1.20
SN7432N	29	SN74168N	1.20
SN7433N	29	SN74169N	1.20
SN7434N	29	SN74170N	1.20
SN7435N	29	SN74171N	1.20
SN7436N	29	SN74172N	5.95
SN7437N	29	SN74173N	5.95
SN7438N	29	SN74174N	89
SN7439N	29	SN74175N	89
SN7440N	29	SN74176N	89
SN7441N	29	SN74177N	89
SN7442N	29	SN74178N	89
SN7443N	29	SN74179N	89
SN7444N	29	SN74180N	89
SN7445N	29	SN74181N	89
SN7446N	29	SN74182N	89
SN7447N	29	SN74183N	89
SN7448N	29	SN74184N	89
SN7449N	29	SN74185N	89
SN7450N	29	SN74186N	89
SN7451N	29	SN74187N	89
SN7452N	29	SN74188N	89
SN7453N	29	SN74189N	89
SN7454N	29	SN74190N	89
SN7455N	29	SN74191N	89
SN7456N	29	SN74192N	89
SN7457N	29	SN74193N	89
SN7458N	29	SN74194N	89
SN7459N	29	SN74195N	89
SN7460N	29	SN74196N	89
SN7461N	29	SN74197N	89
SN7462N	29	SN74198N	89
SN7463N	29	SN74199N	89
SN7464N	29	SN74200N	89
SN7465N	29	SN74201N	89
SN7466N	29	SN74202N	89
SN7467N	29	SN74203N	89
SN7468N	29	SN74204N	89
SN7469N	29	SN74205N	89
SN7470N	29	SN74206N	89
SN7471N	29	SN74207N	89
SN7472N	29	SN74208N	89
SN7473N	29	SN74209N	89
SN7474N	29	SN74210N	89
SN7475N	29	SN74211N	89
SN7476N	29	SN74212N	89
SN7477N	29	SN74213N	89
SN7478N	29	SN74214N	89
SN7479N	29	SN74215N	89
SN7480N	29	SN74216N	89
SN7481N	29	SN74217N	89
SN7482N	29	SN74218N	89
SN7483N	29	SN74219N	89
SN7484N	29	SN74220N	89
SN7485N	29	SN74221N	89
SN7486N	29	SN74222N	89
SN7487N	29	SN74223N	89
SN7488N	29	SN74224N	89
SN7489N	29	SN74225N	89
SN7490N	29	SN74226N	89
SN7491N	29	SN74227N	89
SN7492N	29	SN74228N	89
SN7493N	29	SN74229N	89
SN7494N	29	SN74230N	89
SN7495N	29	SN74231N	89
SN7496N	29	SN74232N	89
SN7497N	29	SN74233N	89
SN7498N	29	SN74234N	89
SN7499N	29	SN74235N	89
SN7500N	29	SN74236N	89

74LS00

74LS00N	35	74LS164N	1.19
74LS01N	28	74LS165N	89
74LS02N	28	74LS166N	2.48
74LS03N	28	74LS168N	89
74LS04N	39	74LS169N	1.89
74LS05N	28	74LS170N	1.99
74LS06N	39	74LS171N	89
74LS07N	39	74LS172N	89
74LS08N	28	74LS173N	99
74LS09N	39	74LS174N	99
74LS10N	28	74LS175N	99
74LS11N	39	74LS176N	1.20
74LS12N	39	74LS177N	2.35
74LS13N	47	74LS178N	1.15
74LS14N	47	74LS179N	1.15
74LS15N	39	74LS180N	98
74LS16N	26	74LS181N	1.15
74LS17N	38	74LS182N	1.15
74LS18N	38	74LS183N	1.15
74LS19N	39	74LS184N	1.15
74LS20N	39	74LS185N	1.15
74LS21N	39	74LS186N	1.15
74LS99N	39	74LS264N	1.15
74LS00N	39	74LS265N	1.15

16K UPGRADE ONLY
\$49.95
 SPECIFY COMPUTER

NEW!
 We Now Have The
Apple Silentype
IN STOCK

With Apple Intelligent Interface Card. Reg. **\$995.00**

Interface Card Has All Software For Hi-Res. Graphics & Pascal Use. **\$549.00**

NOW ONLY

BECKMAN
 Digital Multimeters
 MODELS TECH 300 AND TECH 310

AS LOW AS \$100

TECH 300 has all above features, 7 functions, 29 ranges, plus 0.25% Vdc accuracy. The TECH 310 has 8 0.1% Vdc accuracy and all the above features, but without auto-zero™ continuously function or the 10 amp current range.

TECH 300 Digital Multimeter, \$100
 TECH 310 Digital Multimeter, \$130
 VC-201 Vinyl Carrying Case, \$10
 DC-202 Deluxe Carrying Case, \$24
 HV-211 High Voltage Probe, \$35
 RP-221 RF Probe, \$35
 CR-201 AC Current Clamp, \$42
 DL-241 Deluxe Test Lead Kit, \$10
 TL-242 Spare Test Leads, \$6

NEW!
MUSIC MACHINE 9
 WITH 9 VOICES!

NEW Uses latest State of the Art LSI Technology. Replaces only one slot for 3 voices. Uses three 8128-001's to produce new voices. Plays music generated by the ALF Board. ALF software required. **\$129.95**

ASSEMBLED AND TESTED

FLOPPY DISK DRIVES

MPI BS-15V, 40 tracks, 279.00
 Shugart SA400-5V, 35 tracks, 295.00
 Shugart 800/801R, 8, 475.00
 Siemens Shugart Compatible Model, 2.99
 FDD-120-80, 429.00
 PERSCI Model 77 Dual, 1195.00
 WANG/SIEMENS 5V Drive, 290.00
 MPI BS2 5V Dual, 348.00
 WANG/SIEMENS 282 Dual 5V, 395.00
 WANG/SIEMENS 82, 290.00

CONTINENTAL SPECIALTIES

Model LM-3 40-channel Logic Monitor, 585.00
 Model LM-1 Logic Monitor, 60.00
 Model LM-2 Logic Monitor, 147.00
 MAX-100 100 MHz Portable Frequency Counter, 149.00

Model LP-1 Digital Logic Probe, 50.00
 Model LP-2 Economy Logic Probe, 28.00
 Model LP-3 High Speed Logic Probe, 77.00
 Model LP-1 Logic Probe Kit, 21.95
 Model LTC-1 LTC Logic Analysis Kit, 220/250

Proto Clips
 14-Pin Clip, PC-14, \$ 4.25
 18-Pin Clip, PC-18, \$ 4.50
 24-Pin Clip, PC-24, \$ 4.95
 40-Pin Clip, PC-40, \$14.95

Proto Boards
 PB-6, 16.95
 PB-10, 21.00
 PB-12, 21.00
 PB-13, 43.00

SEMICONDUCTORS
 ☆ SPEAK! ☆
DIGITAL TALKER™
 Speech Synthesis System

The DIGITAL TALKER is a speech synthesis system consisting of multiple N-channel MOS integrated circuits. It contains a speech processor chip (SPC) and speech ROM and when used with external filter, amplifier, and speaker, produces a system which generates high quality speech including the natural inflection and emphasis of the original speech. Male, female, and children's voices can be synthesized.

- Completely independent system, not requiring a processor controller.
- Designed to be easily interfaced to most popular microprocessors.
- 256 possible addressable expressions.
- Male, female, and children's voices.
- Natural inflection and emphasis of original speech.
- Addresses 128K of ROM directly.
- Communicates with static or clocked dynamic ROMs.
- TTL compatible.
- MICROBUS™ compatible.

DIGITAL TALKER™ DT1000. Self contained board that - with just a speaker and a power supply - can rattle off any desired combination of 144 words. **\$485.00**

DIGITAL TALKER™ DT1050. Chip set for building Digitaltalker into your own evaluation design. **\$79.00**

National Semiconductor

ADVANCED COMPUTER PRODUCTS

Apple II. 16K
 or **Apple II. Plus \$990**
DISK SYSTEM SPECIAL

Apple II Plus w/48K Supermod Video Modulator Disk II w/Controller Integer Based ROM Card.
 Reg. \$2,220.00, ACP Price \$1819.00, **SAVE \$401.00**

Hi-Speed Serial I/O	\$189.00	DS65 Dip-Sector	\$349.00	Integer ROM Card	\$189.00
Centronics Printer I/O	180.00	Apple Graphics Tablet	675.00	Photo Card	21.95
Apple II Firmware	189.00	D.C. Hayes Modem II	349.95	A & R Modulator	29.95
Apple Clock	269.00	Disk II w/Controller & Dos. 3.3	595.00	Sony Cassette	54.95
Intro II X-10 System	179.95	Disk II	459.00	16K Upgrade Kit	84.95
Intro X-10 Controller	269.95	Pascal Lang. System	450.00	Desktop Plan	98.00
Alt. Music Synthesizer	259.95	Parallel Printer Card	165.00	Floppy Controller	350.00
16 Ch. Analog Input	249.95	Communications Card	189.00	Heuristics SpeechKit	179.00
2 Ch. Analog Output	184.95	Business Software Pkg.	625.00	Romulus II	159.00
13-Key Keypad	119.95	Convex 10 Megabyte Drive	279.00	SuperTalker	279.00
Visi-Calc	125.00			Cashier	250.00

NEW! California Computer Systems APPLE Clock. Only \$124.95

NEW! Z80 Softcard for APPLE GPM 2.2 & M BASIC 5.0 \$325.00

NEW! California Microproducts Keypad for APPLE \$175.00

NEW! APPLE II-80 CP/M Software Call for Price

ATARI 800 & 400
 Personal Computer System
ATARI 800 \$825.00
ATARI 400 \$449.00

ATARI 800 Includes: Computer Console, BASIC Lang. Cartridge, Education System Master Cartridge, BASIC Language Programming Manual, 800 Operator's Manual w/Notebook, 16K RAM Module, Power Supply, TV Switch Box.

Peripherals		Education System Cassette Program	
Doc. Drive	599.00	U.S. History	29.95
Printer	499.00	Basic I/techy	35.00
Program Recorder	89.00	Basic Algebra	35.00
Software - IBM Cardsets		Supervisory Skills	25.00
Education System Master Cartridge	28.00	Basic History (elementary)	35.00
Alt. BASIC	55.00	Basic Science	35.00
Assembler/Debugger	55.00	Counseling Procedures	35.00
BasicKit	42.00	Principles of Accounting	19.00
Life	42.00	Physics	35.00
Scope Reader™	42.00	Great Classics (English)	35.00
Music Composer	55.00	Business Communications	35.00
Super Bug™	55.00	Basic Psychology	35.00
Convex Chess	55.00		

CPU's & SUPPORT CHIPS

8086	6.95	2114L-3	4.50
8088A	12.95	4116-2	4.95
AMD 2901	13.95	2102-3	6.75
8205	3.95	2102-4	9.90
8216	2.90	MK4027-3	3.50
8228	4.50	MK4026-11	2.95
8251	6.95	TMS4045-25	6.50
8259	9.95	MM5050NL	3.95
8257 (AM9517)	8.95	2101-1	2.45
Z80A SIA	8.95	2107B/8200	3.50
		MM5270	3.45
		MK4008P	1.95
8275	34.95		
MC6845	24.95		
FD1791	34.95		

RAM's

2114L-3	4.50
4116-2	4.95
2102-3	6.75
2102-4	9.90
MK4027-3	3.50
MK4026-11	2.95
TMS4045-25	6.50
MM5050NL	3.95
2101-1	2.45
2107B/8200	3.50
MM5270	3.45
MK4008P	1.95

C/MOS (DIODE CLAMPED)

4001	35	4027	45	4081	35	7427C	50
4002	35	4038	30	4082	48	7428	70
4006	1.10	4030	35	4093	35	7429	1.30
4007	27	4030	35	4099	1.75	7429C	1.40
4008	35	4034	2.25	4021	35	7429C	50
4009	45	4042	35	4014	50	7429C	1.40
4010	45	4040	1.00	4011	35	7429C	35
4012	35	4043	1.00	4015	1.95	7429C	1.75
4013	40	4044	1.30	4016	1.00	7429C	1.75
4014	1.20	4046	1.35	4018	1.20	7429C	1.75
4015	1.00	4048	75	4020	1.00	7429C	1.15
4018	90	4052	1.10	7420A	40	7429C	1.30
4017	1.05	4051	1.10	7420C	27	7429C	1.35
4018	90	4052	1.10	7420A	40	7429C	1.30
4019	1.45	4053	1.10	7420C	27	7429C	1.30
4020	1.10	4056	70	74210	1.30	7429C	1.30
4021	1.10	4059	45	74214	1.30	7429C	1.30
4022	1.00	4071	35	74230	27	7429C	6.95
4023	35	4072	35	74232	27		
4024	75	4076	1.00	74273	35		
4025	35	4077	35				

TRANSISTOR SPECIALS

2N1303 PNP GET-O-5	3.91 00
2N1307 PNP GET-O-5	4.40
2N4004 PNP GET-O-5	3.91 00
HEP 80014 - PNP GET-O-3	8.95
TIP 121 - NPN SIL SWITCHING	6.95
2N6233-NPN SWITCHING POWER	61.95
MRF-8004 a CE R-TRANSISTOR NPN	61.75
2N4908 PNP SI TO-18	61.00
2N5086 PNP SI TO-92	4.91 00
2N5177 NPN SI TO-92	61.75
2N3919 NPN SI TO-92 RF	61.50
2N1420 NPN SI TO-18	3.91 00
2N3904 NPN SI TO-18	61.75
2N2222 NPN SI TO-18	5.91 00
2N2907 NPN SI TO-18	4.91 00
2N5085 NPN SI TO-92	61.75
2N3904 NPN SI TO-92	61.00
2N5096 PNP SI TO-220	61.55
2N5296 NPN SI TO-220	61.55
2N1019 PNP SI TO-220	61.55
TIP 318 NPN SI TO-220	61.55
TIP 328 PNP SI TO-220	61.55
TIP 34 PNP SI	61.55

UART's

AYS-1013	3.75
1602B	3.95
A73-8900	1.95
PT1482B	3.25

ROM's

2708	6.95
2716	16.00
2516	18.00
2532	49.00
8223	3.95
82523	7.95
82512	4.95
825126	2.95
825129	3.25
825130	3.45
825131	3.95
AM9218C	6.95

INTERFACE & DRIVERS

1488	1.40
1489	1.25
8130	2.50
8131	2.50
8830	2.50
8833	2.50
8834	2.00
8837	2.00
8838	2.00
8T380	2.00

PRINTED CIRCUIT BOARD

4" x 6" DOUBLE SIDED EPOXY BOARD 1/16" thick \$6.00 ea. \$52.60

EPOXY GLASS VECTOR BOARD

1/16" thick with 1/10" spacing 4 1/2" x 6 1/2" \$1.95

DATTEL'S DAC-08BC

8 bit DAC - \$9.95

8" DISKETTES HARD SECTOR

\$1.75, 10/\$16.00

74S00-30	74S20	40	74S153	1.10
74S02-30	74S30	40	74S151	1.25
74S05-45	74S32	40	74S157	1.25
74S08-40	74S39	1.90	74S158	1.25
74S11-35	74S112	85	74S174	1.40
74S15-40	74S140	1.00	74S267	1.50
			74S268	1.40

7 WATT LD 65 LASER

25 watt Infra Red Pulse (SQ 2006 equiv.) Laser Diode (Spec sheet included) \$24.95

2N3820 P FET	\$.45
2N5457 N FET	\$.45
2N2646 UJT	\$.45
ER 900 TRIGGER DIODES	4.91 00
2N 6028 PROG. UJT	\$.85

CLOCK CHIPS

MM5387AA	\$5.95
MM5314	\$4.75
MM5316	\$4.95

TANTALUM CAPACITORS

22UF 35 V 5/81.00	10UF 10V	-.40	
47UF 35 V 5/81.00	22UF 10V	-.30	
68UF 35 V 5/81.00	15UF 16V	3/81.00	
1UF 35V	300UF 6V	5/41.00	
2.2UF 20V	5.1UF 100V	33UF 20V	6.70
3.3UF 20V	4.81UF 100V	100UF 15V	5.60
4.7UF 15V	5/81.00		
6.8UF 35V	3/81.00	150UF 15V	5.95

SANKEN AUDIO POWER AMPS

Si 1010 G 10 WATTS	\$ 7.50
Si 1020 G 20 WATTS	\$13.75
Si 1050 G 50 WATTS	\$26.90

200 PRV 1A LASCR .95

RS232 CONNECTORS

DB 25P male	\$3.25
DB 25S female	\$4.25
HOODS	\$1.50

SPECIAL VALUES

ALL 7400 SERIES IC's 15% OFF LIST
ALL REGULATORS 20% OFF LIST

SPECIALS GOOD THRU JANUARY 1981

CRYSTALS \$3.45 ea.	RIBBON CABLE FLAT (COLOR CODED) #30 WIRE
2.000 MHz 6.144 MHz	16 cond. - 40 per foot
4.000 MHz 8.000 MHz	40 cond. - 75 per foot
3.000 MHz 10.000 MHz	50 cond. - 90 per foot
3.57 MHz 18.000 MHz	
5.000 MHz 18.432 MHz	
6.000 MHz 20.000 MHz	

MINIATURE MULTI-TURN TRIM POTS

100, 5K, 10K, 20K, 250K, . . . \$.75 each . . . 3/2.00

ALCO MINIATURE TOGGLE SWITCHES

MTA 106 SPDT	\$1.05
MTA 206 DPDT	\$1.70
MTA 206 P DPDT CENTR OFF	\$1.85
M5D 206 P DPDT CENTER OFF LEVER SWITCH	\$1.85

SCR's TRIAC's

1.5A 6A 35A 110A	PRV 1A 10A 25A
100 45 60 1.40	100 45 80 1.55
200 70 80 1.90 9.00	200 84 1.30 2.10
400 1.20 1.40 2.60 12.00	400 1.30 1.90 3.10
600 1.80 3.00 15.00	600 2.00 2.75 4.30

FP 100 PHOTO TRANS	\$.50
RED, YELLOW OR GREEN LARGE LED's .2"	6/81.00
RED/GREEN BIPOLAR LED's	\$.55
MLED52 P LED	\$.75
MRED48 PHOTO DARL. XTOR	\$.75
TIL-118 OPTO-ISOLATOR	\$.75
IL-5 OPTO-ISOLATOR	\$.80
1 WATT ZENERS: 3.3, 4.7, 5.1, 5.6, 6.8, 8.2, 9.1, 10, 12, 15, 18, or 22V	6/81.00

SFC 3301 - 50 PRV 30A

FAST RECOVERY DIODE (35ns) . . . \$2.25

SILICON POWER RECTIFIERS

PRV 1A 3A 12A 50A 125A 240A	
100 .08 .14 .35 .90 .30 7.00	
200 .70 .20 .40 1.30 4.25 6.50	
400 .09 .25 .65 1.50 6.50 9.80	
600 .11 .30 .80 2.00 8.50 12.50	
800 .15 .35 1.00 2.50 10.50 18.50	
1000 .20 .45 1.25 3.00 12.50 20.00	

IN 4148 (IN914) 15/\$1.00

.1 or .01 of 25V ceramic disc. caps. 16/\$1.00, 100/\$5.00

REGULATORS

LM317T	\$2.50	LM305G	\$.75
LM337	\$2.50	340K-12, 15 or 24V	\$1.50
323K-5V 3A	\$5.75	340T-5, 6, 8, 12, 15	
79HGKC-5V at 5A	6.95	18 or 24V	\$1.10
723	\$.50	320M5	\$.75
350T-5, 12, or 15V	\$1.10	LAS1412-12V 3A	\$3.95

LED READOUTS

FCS 8024-4 digit		DL-707 C.A. 3"	\$.75
C.C. 8" display	\$5.95	DL 747 C.A. 6"	\$1.50
FND 503 C.C. 5"	\$.85	DL 510 C.A. 5"	\$.85
FND 510 C.A. 5"	\$.85	HP3400-8" CC	\$1.95
FD 704-3" C.C.	\$.85		

TTLIC SERIES

7400	17	7450	17	74161	80
74101	17	7472	35	74162	1.20
7402	17	7473	35	74163	95
7403	17	7474	42	74164	85
7404	24	7475	49	74165	85
7405	24	7476	45	74166	1.05
7406	33	7480	45	74167	1.35
7407	35	7483	60	74170	1.60
7408	27	7485	75	74173	1.30
7409	24	7486	42	74174	75
7410	17	7489	60	74183	85
7411	17	7490	50	74175	75
7412	22	7491	55	74177	75
7413	42	7492	50	74180	75
7414	30	7493	50	74181	1.90
7415	33	7494	60	74180	1.30
7417	27	7495	60	74191	1.20
7420	17	7496	60	74192	79
7421	22	74107	35	74193	79
7422	33	74121	35	74194	85
7427	35	74122	39	74195	65
7430	17	74123	42	74196	85
7432	27	74125	45	74197	87
7437	27	74126	45	74279	95
7438	27	74125	45	74279	95
7440	17	74150	1.10	74387	80
7441	25	74151	65	74389	65
7442	50	74153	55	74389	65
7445	70	75154	1.10	75025	1.50
7446	75	74155	75	74911	1.05
7447	75	74157	65	75492	1.05
7448	75	74159	65	8798	1.10

FULL WAVE BRIDGE

PRV 2A 6A 25A	100	1.40	
200	.80	1.30	2.20
400	1.00	1.65	3.30
600	1.30	1.90	4.40

DIP SOCKETS

8 PIN	.17	22 PIN	.30
14 PIN	.20	24 PIN	.35
16 PIN	.22	28 PIN	.40
18 PIN	.25	40 PIN	.60

74LS SERIES

74LS00	28	74LS139	1.30
74LS01	28	74LS14	1.10
74LS02	28	74LS153	1.10
74LS03	28	74LS155	1.10
74LS04	28	74LS156	1.10
74LS05	28	74LS157	1.10
74LS06	28	74LS158	1.10
74LS08	35	74LS161	1.10
74LS09	35	74LS162	1.10
74LS10	35	74LS163	1.10
74LS11	35	74LS164	1.10
74LS12	35	74LS165	1.10
74LS13	35	74LS166	1.10
74LS14	35	74LS167	

ramsey**the first name in Counters!****9 DIGITS 600 MHz \$129⁹⁵ WIRED**

PRICES:

CT-90 wired, 1 year warranty	\$129.95
CT-90 Kit, 90 day parts warranty	109.95
AC-1 AC adapter	3.95
BP-1 Nicad pack + AC Adapter/Charger	12.95
OV-1, Micro-power Oven time base	49.95
External time base input	14.95

The CT-90 is the most versatile, feature packed counter available for less than \$300.00! Advanced design features include: three selectable gate times, nine digits, gate indicator and a unique display hold function which holds the displayed count after the input signal is removed! Also, a 10mHz TCXO time base is used which enables easy zero beat calibration checks against WWV. Optionally, an internal nicad battery pack, external time base input and Micro-power high stability crystal oven time base are available. The CT-90, performance you can count on!

SPECIFICATIONS:

Range:	20 Hz to 600 MHz
Sensitivity:	Less than 10 MV to 150 MHz Less than 50 MV to 500 MHz
Resolution:	0.1 Hz (10 MHz range) 1.0 Hz (60 MHz range) 10.0 Hz (600 MHz range)
Display:	9 digits 0.4" LED
Time base:	Standard-10.000 mHz, 1.0 ppm 20-40°C. Optional Micro-power oven-0.1 ppm 20-40°C
Power:	8-15 VAC @ 250 ma

7 DIGITS 525 MHz \$99⁹⁵ WIRED**SPECIFICATIONS:**

Range:	20 Hz to 525 MHz
Sensitivity:	Less than 50 MV to 150 MHz Less than 150 MV to 500 MHz
Resolution:	1.0 Hz (5 MHz range) 10.0 Hz (50 MHz range) 100.0 Hz (500 MHz range)
Display:	7 digits 0.4" LED
Time base:	1.0 ppm TCXO 20-40°C
Power:	12 VAC @ 250 ma

The CT-70 breaks the price barrier on lab quality frequency counters. Deluxe features such as: three frequency ranges - each with pre-amplification, dual selectable gate times, and gate activity indication make measurements a snap. The wide frequency range enables you to accurately measure signals from audio thru UHF with 1.0 ppm accuracy - that's .0001%! The CT-70 is the answer to all your measurement needs, in the field, lab or ham shack.

PRICES:

CT-70 wired, 1 year warranty	\$99.95
CT-70 Kit, 90 day parts warranty	84.95
AC-1 AC adapter	3.95
BP-1 Nicad pack + AC adapter/charger	12.95

7 DIGITS 500 MHz \$79⁹⁵ WIRED**PRICES:**

MINI-100 wired, 1 year warranty	\$79.95
MINI-100 Kit, 90 day part warranty	59.95
AC-Z Ac adapter for MINI-100	3.95
BP-Z Nicad pack and AC adapter/charger	12.95

Here's a handy, general purpose counter that provides most counter functions at an unbelievable price. The MINI-100 doesn't have the full frequency range or input impedance qualities found in higher price units, but for basic RF signal measurements, it can't be beat! Accurate measurements can be made from 1 MHz all the way up to 500 MHz with excellent sensitivity throughout the range, and the two gate times let you select the resolution desired. Add the nicad pack option and the MINI-100 makes an ideal addition to your tool box for "in-the-field" frequency checks and repairs.

SPECIFICATIONS:

Range:	1 MHz to 500 MHz
Sensitivity:	Less than 25 MV
Resolution:	100 Hz (slow gate) 1.0 KHz (fast gate)
Display:	7 digits, 0.4" LED
Time base:	2.0 ppm 20-40°C
Power:	5 VDC @ 200 ma

8 DIGITS 600 MHz \$159⁹⁵ WIRED

**NEW
READ
RECEIVER
FREQUENCY**

SPECIFICATIONS:

Range:	20 Hz to 600 MHz
Sensitivity:	Less than 25 mv to 150 MHz Less than 150 mv to 600 MHz
Resolution:	1.0 Hz (60 MHz range) 10.0 Hz (600 MHz range)
Display:	8 digits 0.4" LED
Time base:	2.0 ppm 20-40°C
Power:	110 VAC or 12 VDC

The CT-50 is a versatile lab bench counter that will measure up to 600 MHz with 8 digit precision. And, one of its best features is the Receive Frequency Adapter, which turns the CT-50 into a digital readout for any receiver. The adapter is easily programmed for any receiver and a simple connection to the receiver's VFO is all that is required for use. Adding the receiver adapter in no way limits the operation of the CT-50, the adapter can be conveniently switched on or off. The CT-50, a counter that can work double-duty!

PRICES:

CT-50 wired, 1 year warranty	\$159.95
CT-50 Kit, 90 day parts warranty	119.95
RA-1, receiver adapter kit	14.95
RA-1 wired and pre-programmed (send copy of receiver schematic)	29.95

**DIGITAL MULTIMETER \$99⁹⁵ WIRED****PRICES:**

DM-700 wired, 1 year warranty	\$99.95
DM-700 Kit, 90 day parts warranty	79.95
AC-1, AC adaptor	3.95
BP-3, Nicad pack + AC adapter/charger	19.95
MP-1, Probe kit	2.95

The DM-700 offers professional quality performance at a hobbyist price. Features include: 26 different ranges and 5 functions, all arranged in a convenient, easy to use format. Measurements are displayed on a large 3 1/2 digit, 1/2 inch LED readout with automatic decimal placement, automatic polarity, overrange indication and overload protection up to 1250 volts on all ranges, making it virtually goof-proof! The DM-700 looks great, a handsome, jet black, rugged ABS case with convenient retractable tilt bail makes it an ideal addition to any shop.

SPECIFICATIONS:

DC/AC volts:	100uV to 1 KV, 5 ranges
DC/AC current:	0.1uA to 2.0 Amps, 5 ranges
Resistance:	0.1 ohms to 20 Megohms, 6 ranges
Input impedance:	10 Megohms, DC/AC volts
Accuracy:	10.1% basic DC volts
Power:	4 'C' cells

AUDIO SCALER

For high resolution audio measurements, multiplies UP in frequency.

- Great for PL tones
- Multiplies by 10 or 100
- 0.01 Hz resolution!

\$29.95 Kit \$39.95 Wired

ACCESSORIES

Telescopic whip antenna - BNC plug	\$ 7.95
High impedance probe, light loading	15.95
Low pass probe, for audio measurements	15.95
Direct probe, general purpose usage	12.95
Tilt bail, for CT 70, 90, MINI-100	3.95
Color burst calibration unit, calibrates counter against color TV signal	14.95

COUNTER PREAMP

For measuring extremely weak signals from 10 to 1,000 MHz. Small size, powered by plug transformer-included.

- Flat 25 db gain
- BNC Connectors
- Great for sniffing RF with pick-up loop

\$34.95 Kit \$44.95 Wired

ramsey electronics, inc.

2575 BAIRD RD. • PENFIELD, NY 14526



PHONE ORDERS
CALL 716-586-3950

TERMS:

Satisfaction guaranteed - examine for 10 days, if not pleased, return in original form for refund. Add 5% for shipping - insurance to a maximum of \$10. Overseas add 15%. COD add \$2. Orders under \$10, add \$1.50. NY residents add 7% tax.

CIRCLE 7 ON FREE INFORMATION CARD

JANUARY 1981

95

apple II plus
With 48K of memory!
\$1042⁰⁰


With the purchase of the APPLE II select from the below SPECIAL PRICING!

- Base printer...\$599⁰⁰
- Disk II w/corr...\$85⁰⁰
- Disk II.....475⁰⁰
- Sec. Printer Cd...179⁰⁰
- SupRMod.....23⁰⁰
- 3way I/O Select...33⁰⁰
- Video 100 12"...119⁰⁰
- Firmware Card...149⁰⁰
- LHFtoRCA Cable...5⁰⁰



apple II / apple II plus
With 60K of memory!
\$1259⁰⁰

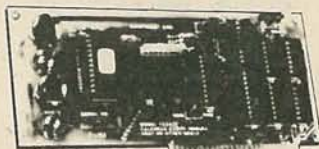- Switch from "APPLESOFT" to "INTEGER BASIC" and back again.
- With Disc Operating System DOS 3.3 run PASCAL program without need for a PASCAL card.



\$124⁹⁵
apple clock/calendar

- Seconds, minutes, hours, day of week, month, date, & year.
 - On board batteries with one year life.
 - Uses MSM5832-crystal controlled.
- California Computer Systems

APPLE EXPANSION KIT
16K Memory Add-On **\$39⁰⁰**
MEMORY ADD-ON KIT
INCLUDES INSTRUCTIONS

video 100



\$125 Lueder Corp.
12" BLACK & WHITE
LOW COST VIDEO
MONITOR

- SN7400N .20
- SN7402N .22
- SN7404AN .22
- SN7408N .24
- SN7410N .22
- SN7412N .28
- SN7413N .35
- SN7414N .49
- SN7416N .29
- SN7417N .29
- SN7423N .28
- SN7425N .25
- SN7430N .23
- SN7437N .29
- SN7438N .24
- SN7440N .22
- SN7442N .57
- SN7443N .78
- SN7445N .78
- SN7451N .20
- SN7454N .20
- SN7474N .32
- SN7475N .32
- SN7482N 1.05
- SN7492N .50
- SN7493N .48
- SN7495N .60
- SN7496N .70
- SN74122N .39
- SN74136N .95
- SN74141N .69
- SN74151N .65
- SN74153N .65
- SN74154N 1.25
- SN74155N .80
- SN74157N .69
- SN74160N .95
- SN74161N .65
- SN74163N .85
- SN74164N .87
- SN74165N .87
- SN74174N .95
- SN74175N .69
- SN74180N .75
- SN74181N 1.15
- SN74393N 1.69

- 74LS00 .20
- 74LS02 .26
- 74LS03 .26
- 74LS04 .26
- 74LS08 .28
- 74LS09 .26
- 74LS10 .26
- 74LS20 .26
- 74LS21 .26
- 74LS22 .26
- 74LS26 .49
- 74LS27 .26
- 74LS30 .28
- 74LS32 .32
- 74LS38 .32
- 74LS42 .65
- 74LS48 .78
- 74LS51 .25
- 74LS54 .35
- 74LS74 .38
- 74LS75 .60
- 74LS83 .44
- 74LS85 .95
- 74LS86 .95
- 74LS90 .69
- 74LS93 .69
- 74LS107 .45
- 74LS112 .38
- 74LS113 .48
- 74LS122 .48
- 74LS123 .95
- 74LS126 .69
- 74LS138 .69
- 74LS151 .44
- 74LS153 .44
- 74LS155 1.15
- 74LS158 .75
- 74LS160 .95
- 74LS161 .95
- 74LS162 .95
- 74LS163 1.60
- 74LS164 .65
- 74LS165 .65
- 74LS170 1.75
- 74LS174 .75
- 74LS175 .75
- 74LS190 .75
- 74LS193 .95
- 74LS195 .95
- 74LS196 .85
- 74LS221 1.40
- 74LS240 1.65
- 74LS241 1.65
- 74LS243 1.45
- 74LS244 1.45
- 74LS245 2.25
- 74LS253 .95
- 74LS257 .95
- 74LS258 .95
- 74LS259 2.85
- 74LS279 .44
- 74LS283 1.00
- 74LS293 1.85
- 74LS298 1.20
- 74LS366 .95
- 74LS367 .55
- 74LS368 .55
- 74LS373 1.39
- 74LS374 1.39
- 74LS386 .65

\$159
BASE 2 PRINTER
TO APPLE COMPUTER
INTERFACE BOARD WITH CABLE

COMPLETE 8085A BASED MICRO-COMPUTER
AND MICROPROCESSOR TRAINING UNIT
YOU GET:

- Fully assembled and tested 8085A Microcomputer with 1K RAM, 1K PROM, & 1K EPROM.
- Programmable I/O, Keyboard unit, CPU card, 20 ma Asynchronous serial port, Display and Operating system.
- 8085A Cookbook: 362 pages takes you from basic concepts to actual design.
- 8080/8085A Software Design Book 1 with detailed examination of all 244 instructions. 336 pages include sample programs using all basic instructions and typical assembly language.

\$295⁰⁰

S-100 MEMORY BOARD

16K STATIC RAM

\$249⁰⁰
FULLY STATIC OPERATION
4K BANK ADDRESSABLE
EXTENDED MEMORY MGMT.
MEETS IEEE PROPOSED
S-100 SIGNAL STANDARDS
4 MHZ OPERATION
ASSEMBLED & TESTED
California Computer Systems

MODEL 8008 IMPACT PRINTER
● Dot resolution graphics in six densities
● 1920 character buffer
● Fully adjustable tractor to 9-1/2"

\$649⁰⁰

base inc. 2^o

Global Specialties

Logic Probes

LP1
Detects pulse widths down to 50 ns, measures rise up to 10 MHz. Separate high and low indicators. LED probe for easy pinpointing. Control indicators: Pulse stretcher, input pulse LED indicator, Memory probe, output pulse LED indicator, low resistor and pull-up resistor. Switch-selectable logic supply (battery or wall). Reverse and anti-voltage protection.

LP2
For many applications, the LP-2 gives best performance. It is individually sized and comes in the LP-1 box for storage, transport and without the Memory probe. Details same as LP-1. Includes 300-ohm and 15-MHz high-impedance. (See note - impedance guards against signal loading.)

LP3
Our highest performance logic probe and LED indicator. It offers an impressive 10-MHz logic level, 100 ns rise time, and 100 ns delay. It is 1/2 inch wide with 300-ohm and 15-MHz high-impedance. (See note - impedance guards against signal loading.)

EPROMS
2708 1Kx8 \$6.75
8 for \$49
2716 2Kx8 12.95
8 for \$110
2732 4Kx8 44.95
2 for \$100
SINGLE SVOLT FOR 2716 & 2732

2114L

1024x4 Static RAM
300nsec \$399
200nsec 475

S-100 16K ADD-ON BARE BOARD WITH DOCUMENTATION AND DETAILED INSTRUCTION BOOK **\$28⁹⁵**

TRS 80

16K Memory Add-On

\$4395
KIT CONTAINS
DIP SWITCHES
AND DETAILED
INSTRUCTIONS

VOLTAGE REGULATORS

NEGATIVE POSITIVE
7905/5V 7805/5V
7908/8V 7808/8V
7915/15V 7812/12V
95c

FRT. CHARGES

amt' frt. chg.
\$10-49 \$200
50-99 400
100-249 700
250-499 800
500-999 1000
1000 up inquire

***note**

555 TIMER 27c

8038C VCO Waveform Gen w/5 wire \$265

LOGIC PROBE KIT \$17⁹⁵



\$8750
No "Glitches", Surges Or Interference

The MPD 117 is the low-cost solution to your power distribution problems. The MPD 117 has a high-performance EMI filter, built-in circuit breaker, two direct and six twist-lead outlets, illuminated "on-off" switch for switched outlets, and is built with rugged UL-approved components and housing in an all-steel chassis with convenient mounting flanges.

Ask about
QUANTITY
DISCOUNT

MSM5832

MICROPROCESSOR
REAL-TIME **\$745**
CLOCK / CALENDAR
GENERAL DESCRIPTION

The MSM5832 is a monolithic, metal-gate CMOS integrated circuit that functions as a real time clock/calendar for use in bus-oriented microprocessor applications. The on-chip 32.768 KHz crystal controlled oscillator time base is counted down to provide addressable 4-bit I/O data of SECONDS, MINUTES, HOURS, DAY-OF-WEEK, DATE, MONTH and YEAR. Data access is controlled by 4-bit address, chip select, read, write and hold inputs. Other functions include 12H/24H format selection, leap year identification and manual - 30 second correction.

SOROC
TECHNOLOGY, INC.

IQ120 \$689

CONCORD COMPUTER COMPONENTS

1971 SOUTH STATE COLLEGE ANAHEIM, CA. 92806
VISA MASTER CHARGE (714) 937-0637 MINIMUM ORDER \$1000
CHECK OR M D ADD FRI
NO COD We stock and sell over 12,000 types of semi-conductors. CAL RES ADD 6%

A Microcomputer for everyone at a Micro Price

The **MicroAce** - a new generation of miniature computers
A COMPLETE COMPUTER for \$149.00 for 1K Kit



Post and Packing FREE


(Add 6% Tax for Shipments inside California)

RAM (expandable to 2K on board) is roughly equivalent to 4K bytes in a conventional computer — typically storing 100 lines of BASIC. (Key words occupy only a single byte.)

The display shows 32 characters by 24 lines.

And Benchmark tests show that the MicroAce is faster than all other personal computers.

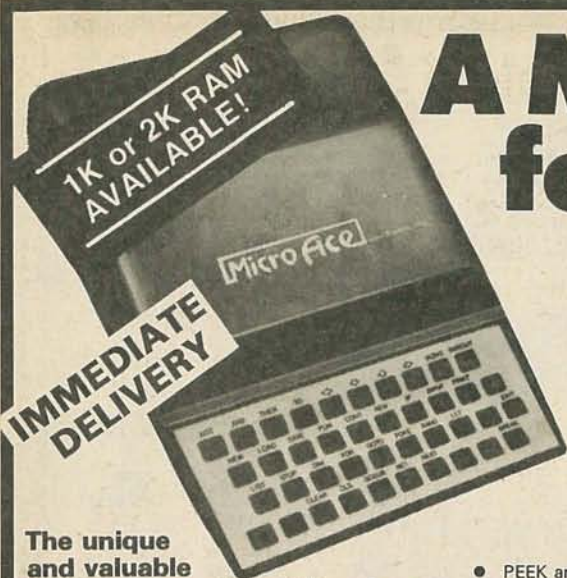No other personal computer offers this unique combination of high capability and low price.



The unique and valuable components of the MicroAce

The MicroAce is not just another personal computer. Quite apart from its exceptionally low price, the MicroAce has two uniquely advanced components: the powerful BASIC interpreter, and the simple teach yourself BASIC manual.

The unique versatile BASIC interpreter offers remarkable programming advantages:

- Unique 'one-touch' key word entry: the MicroAce eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST, etc.) have their own single-key entry.
- Unique syntax check. Only lines with correct syntax are accepted into programs. A cursor identifies errors immediately. This prevents entry of long and complicated programs with faults only discovered when you try to run them.
- Excellent string-handling capability — takes up to 26 string variables of any length. All strings can undergo all relational tests (e.g. comparison). The MicroAce also has string input — to request a line of text when necessary. Strings do not need to be dimensioned.
- Up to 26 single dimension arrays.
- FOR/NEXT loops nested up to 26.
- Variable names of any length.
- BASIC language also handles full Boolean arithmetic, conditional expressions, etc.
- Exceptionally powerful edit facilities, allows modification of existing program lines.
- Randomise function, useful for games and secret codes, as well as more serious applications
- Timer under program control.

- PEEK and POKE enable entry of machine code instructions, USR causes jump to a user's machine language sub-routine.
- High-resolution graphics with 22 standard graphic symbols.
- All characters printable in reverse under program control.
- Lines of unlimited length.

'Excellent value' indeed!

For just \$149.00 (including handling charge) you get everything you need to build a personal computer at home... PCB, with IC sockets for all ICs; case; leads for direct connection to a cassette recorder and television (black and white or color); everything!

Yet the MicroAce really is a complete, powerful, full-facility computer, matching or surpassing other personal computers at several times the price.

The MicroAce is programmed in BASIC, and you can use it to do quite literally anything, from playing chess to managing a business.

The MicroAce is pleasantly straightforward to assemble, using a fine-tipped soldering iron. It immediately proves what a good job you've done: connect it to your TV ... link it to the mains adaptor ... and you're ready to go.

Fewer chips, compact design, volume production—more power per Dollar!

The MicroAce owes its remarkable low price to its remarkable design: the whole system is packed on to fewer, newer, more powerful and advanced LSI chips. A single SUPER ROM, for instance, contains the BASIC interpreter, the character set, operating system, and monitor. And the MicroAce 1K byte

The MicroAce teach-yourself BASIC manual.

If the features of the BASIC interpreter mean little to you—don't worry. They're all explained in the specially-written book *free* with every kit! The book makes learning easy, exciting and enjoyable, and represents a complete course in BASIC programming—from first principles to complex programs. (Available separately—purchase price refunded if you buy a MicroAce later.)


A hardware manual is also included with every kit.

The MicroAce Kit:
\$149.00 with 1K COMPLETE
\$169.00 with 2K

Demand for the MicroAce is very high: use the coupon to order today for the earliest possible delivery. All orders will be despatched in strict rotation. If you are unsuccessful in constructing your kit, we will repair it for a fee of \$20.00, post and packing FREE. Of course, you may return your MicroAce as received within 14 days for a full refund. We want you to be satisfied beyond all doubt — and we have no doubt that you will be.

Z80 A microprocessor chip, widely recognised as the best ever made.

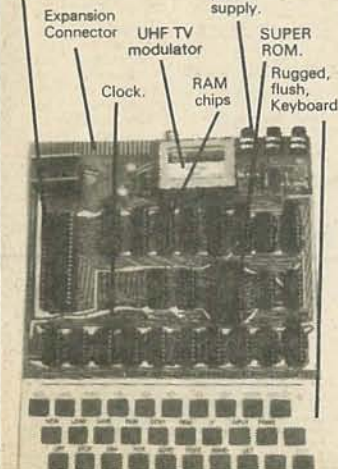Sockets for TV, cassette recorder, power supply.



Your MicroAce kit contains...

- Printed circuit board, with IC sockets for all ICs.
- Complete components set, including all ICs—all manufactured by selected world-leading suppliers.
- New rugged keyboard, touch-sensitive, wipe-clean.
- Ready-moulded case.
- Leads and plugs for connection to domestic TV and cassette recorder. (Programs can be SAVED and LOADED on to a portable cassette recorder.)
- Mains adaptor of 600 mA at 9VDC nominal unregulated.
- FREE course in BASIC programming and user manual.

JOIN THE REVOLUTION - DON'T GET LEFT BEHIND - ORDER YOUR MICRO ACE NOW!!

Send Check, Money Order or quote your Credit Card No. to:
MicroAce 1348 East Edinger, Santa Ana, California, Zip Code 92705.
 or phone (714) 547 2526 quoting your Credit Card Number.

Quantity	Description	Unit Price	TOTAL
	MicroAce Kit 1K	\$149.00	
	MicroAce Kit 2K	\$169.00	
	Manual	\$10.00	
	1K Upgrade Kit	\$29.00	
Shipments inside California add 6% TAX		TOTAL	

- Amex.
- Diners
- Check
- Money Order
- Master Charge
- Visa

Card No. _____

Exp. Date _____

Name _____

Address _____

City _____ State _____ Zip _____

LOWEST PRICES FOR PRIME ICs!

ORDER DESK: 800-325-0101

In addition to the broadest line of digital integrated circuits offered anywhere, I.C.C. offers the complete line of products from the following well known manufacturers of electronic components and subsystems.



I.C.C. has in stock the complete line of AP Products, including the Poweraces, ACE Circuit Evaluators, Super-Strips, DIP Jumpers, PC Board Connectors, and even the NEW Hobby Box. If AP makes it, we have it in stock for immediate delivery. And, best of all, our Volume Discount is applicable to all of them.

O.K. Machine & Tool has one of the widest line of products for wire wrapping, and the associated accessories. These high quality, yet low cost, components include: manual and battery-operated wrapping tools, wire dispensers, Just-Wrap® units, circuit boards, etc. The entire line is available from I.C.C.



Vector is The name in breadboarding, and I.C.C. has the widest range of Vectorboards, Experimenter's Boards, Vector Pins, Terminals and Wrap Posts, Wrapping Tools, and blank Microprocessor Boards for virtually every brand of Microcomputers.

The entire range of 5% and 10%, 1/4 and 1/2 watt, type RGR Mil-Grade resistors manufactured by Allen-Bradley and Stockpile is available from I.C.C. The established reliability levels of 0.01% (Orange fifth band) - 0.01% (Yellow fifth band) failures per thousand hours of operation at 50% rated wattage is your assurance of trouble-free circuit performance.



Pre-Cut and Pre-Stripped (1" from each end) No. AWG 30 wrapping wire in ten colors (Blk, Brn, Red, Org, Yel, Grn, Blue, Vio, Gry, and Wht) and in fifteen different lengths from 1" to 15" in four packages (50, 100, 500, and 1000) are available for low cost, yet fast and reliable circuit and back-panel wiring.

wrapping wire

Volume	Discount	Standard Shipping Charges
\$ 0.01 - \$ 9.99	5%	add \$2.00
\$ 10.00 - \$ 24.99	10%	add \$1.00
\$ 25.00 - \$ 99.99	15%	add \$0.75
\$ 100.00 - \$ 499.99	20%	add \$0.50
\$ 500.00 - \$ 999.99	25%	add \$0.25
\$1000.00 and up	30%	add \$0.00

Shipping on U.S. via Post. Class Mail not used.

INTERNATIONAL COMPONENTS CORPORATION

P. O. BOX 1837
COLUMBIA, MO 65205
PHONE: (314) 474-9485

74xx	74125	80.49	74LS12	80.36	74LS106	51.25	74S189	53.35	74C007	50.75	4009	52.75	LM741C	50.50	
7400	80.20	74126	0.49	74LS13	0.55	74LS171	1.25	74S194	2.15	74C008	1.19	4093	0.99	LM748C	0.35
7401	0.90	74127	0.75	74LS14	1.10	74LS221	1.90	74S200	3.95	74C009	2.15	4099	2.10	LM1458N	0.25
7402	0.30	74147	1.70	74LS21	0.36	74LS244	2.25	74S203	1.45	74C010	6.20	4503	0.95	LM1459C	0.59
7403	0.20	74148	1.20	74LS22	0.36	74LS253	1.01	74S208	1.45	74C011	1.45	4099	0.99	LM1889N	2.25
7404	1.25	74149	0.25	74LS23	0.36	74LS257	0.71	74S212	1.45	74C012	2.25	4504	3.00	LM1311N	1.55
7405	0.20	74151	0.59	74LS27	0.36	74LS258	0.86	74S217	3.90	74C013	2.90	4511	1.15	MC1455P	1.35
7406	0.20	74152	0.59	74LS30	0.34	74LS260	0.38	74S229	4.35	74C014	2.90	4512	1.25	MC1456P	0.95
7407	0.28	74153	0.58	74LS32	0.40	74LS266	0.49	74S237	5.70	74C015	5.70	4518	1.15	MC1457P	0.58
7408	0.20	74156	0.64	74LS36	1.06	74LS269	0.66	74S243	2.90	74C016	2.90	4519	0.62	MC1458C	0.69
7409	0.20	74159	0.69	74LS38	0.36	74LS283	0.99	74S250	2.30	74C017	4.50	4520	1.15	MC1790CP	0.28
7410	0.20	74156	0.69	74LS40	0.34	74LS290	1.05	74S251	3.45	4000	80.35	4527	1.67	MC1710CP	0.29
7411	0.25	74157	0.64	74LS42	0.82	74LS299	0.99	74S261	1.39	4001	0.35	4528	1.50	MC1715CP	0.39
7412	0.25	74158	0.64	74LS44	1.06	74LS305	0.66	74S262	1.39	4002	0.35	4539	1.35	MC1741C	0.35
7413	0.38	74160	0.87	74LS48	1.05	74LS366	0.66	74S263	3.40	4006	1.19	4555	0.89	MC1740CP	1.35
7414	0.70	74161	0.87	74LS49	1.05	74LS367	0.66	74S264	5.00	4007	0.35	4556	1.00	MC1741CP	0.28
7415	0.25	74162	0.87	74LS51	0.34	74LS368	0.66	74S265	1.50	4008	1.06	4562	1.08	MC7805CT	1.20
7416	0.20	74163	0.87	74LS54	0.34	74LS373	2.25	74S266	5.95	4009	0.49	4703	8.25	MC7806CT	1.20
7417	0.20	74164	0.87	74LS55	0.34	74LS374	2.25	74S267	1.55	4010	0.49	4703	8.25	MC7808CT	1.20
7418	0.25	74165	0.87	74LS73	0.45	74LS386	0.53	74S268	2.65	4011	0.35	4704	7.30	MC7812CT	1.20
7419	0.20	74166	1.22	74LS74	0.45	74LS390	1.89	74S269	4.01	4012	0.35	4705	9.25	MC7815CT	1.20
7420	0.20	74167	0.96	74LS76	0.82	74LS400	0.89	74S270	4.01	4013	0.42	4706	8.75	MC7816CT	1.20
7421	0.25	74170	1.58	74LS78	0.48	74LS70	2.45	74S271	4.01	4014	1.05	4720	6.95	MC8012CT	0.77
7422	0.20	74173	1.24	74LS83	1.05	74C00	50.34	0.15	4723	1.50	4723	1.50	MC7945P	1.00	
7423	0.25	74174	0.89	74LS85	1.25	74C002	0.34	0.16	4724	1.50	4724	1.50	MC7949P	0.52	
7424	0.20	74175	0.89	74LS86	0.48	74C003	0.35	0.17	4725	1.01	4725	1.01	MC7951P	0.35	
7425	0.40	74176	0.78	74LS89	0.71	74C004	0.35	0.18	4726	1.01	4726	1.01	MC1324P	0.75	
7426	0.20	74177	0.78	74LS92	0.71	74C010	0.34	0.19	4727	1.05	4005	1.69	MLM5650P	1.20	
7427	0.20	74178	1.90	74LS93	0.71	74C011	0.40	0.20	4728	1.13	4006	0.69	N5558P	0.58	
7428	0.88	74179	1.90	74LS96	0.99	74C012	0.34	0.21	4729	1.13	4016	0.90	N5562A	0.69	
7429	0.59	74180	0.79	74LS107	0.44	74C013	0.46	0.22	4730	1.05	4016	1.17	N5573A	0.66	
7430	0.75	74181	1.95	74LS109	0.44	74C019	0.46	0.23	4731	0.35	4016	1.17	N5581A	0.60	
7431	0.75	74182	1.95	74LS112	0.49	74C020	0.48	0.24	4732	1.00	4024	0.79	N5582A	1.00	
7432	0.75	74184	1.95	74LS113	0.49	74C021	0.48	0.25	4733	1.00	4024	0.79	N5583A	1.00	
7433	0.60	74185	0.95	74LS114	0.49	74C022	0.45	0.26	4734	0.71	4027	0.69	N5584	1.00	
7434	0.65	74188	3.85	74LS123	0.98	74C023	0.48	0.27	4735	0.71	4028	0.88	N5595	0.35	
7435	0.20	74190	0.99	74LS125	0.62	74C024	0.45	0.28	4736	1.13	4029	1.13	N5596A	0.80	
7436	0.20	74191	0.99	74LS126	0.62	74C025	0.45	0.29	4737	1.13	4030	1.13	N5598A	0.50	
7437	0.20	74192	0.80	74LS132	0.91	74C026	0.48	0.30	4738	1.13	4031	1.13	N5599A	1.20	
7438	0.20	74193	0.80	74LS136	0.48	74C027	0.46	0.31	4739	1.13	4032	1.13	N5600	1.20	
7439	0.20	74194	0.87	74LS138	0.53	74C028	0.46	0.32	4740	1.13	4033	1.13	N5601	1.20	
7440	0.20	74195	0.87	74LS139	0.82	74C029	0.70	0.33	4741	1.10	4040	1.20	N5602	1.20	
7441	0.20	74196	0.87	74LS151	0.75	74C030	0.45	0.34	4742	1.10	4041	1.05	N5603	1.20	
7442	0.20	74197	0.87	74LS152	0.75	74C031	0.45	0.35	4743	1.30	4042	0.99	N5604	1.20	
7443	0.20	74198	0.87	74LS153	0.75	74C032	0.45	0.36	4744	1.30	4043	0.99	N5605	1.20	
7444	0.20	74199	1.45	74LS154	1.40	74C033	0.45	0.37	4745	1.30	4044	0.99	N5606	1.20	
7445	0.20	74200	1.09	74LS155	0.89	74C034	0.48	0.38	4746	1.30	4045	0.99	N5607	1.20	
7446	0.20	74201	1.09	74LS156	0.89	74C035	0.48	0.39	4747	1.30	4046	0.99	N5608	1.20	
7447	0.20	74202	1.09	74LS157	0.89	74C036	0.48	0.40	4748	1.30	4047	0.99	N5609	1.20	
7448	0.20	74203	0.99	74LS158	0.75	74C037	0.48	0.41	4749	1.30	4048	0.99	N5610	1.20	
7449	0.20	74204	0.99	74LS159	0.75	74C038	0.48	0.42	4750	1.30	4049	0.99	N5611	1.20	
7450	0.20	74205	0.99	74LS160	0.75	74C039	0.48	0.43	4751	1.30	4050	0.99	N5612	1.20	
7451	0.20	74206	0.99	74LS161	0.75	74C040	0.48	0.44	4752	1.30	4051	0.99	N5613	1.20	
7452	0.20	74207	0.99	74LS162	0.75	74C041	0.48	0.45	4753	1.30	4052	0.99	N5614	1.20	
7453	0.20	74208	0.99	74LS163	0.75	74C042	0.48	0.46	4754	1.30	4053	0.99	N5615	1.20	
7454	0.20	74209	0.99	74LS164	1.15	74C043	0.78	0.47	4755	1.30	4054	0.99	N5616	1.20	
7455	0.20	74210	0.99	74LS165	1.15	74C044	0.78	0.48	4756	1.30	4055	0.99	N5617	1.20	
7456	0.20	74211	0.99	74LS166	1.15	74C045	0.78	0.49	4757	1.30	4056	0.99	N5618	1.20	
7457	0.20	74212	0.99	74LS167	1.15	74C046	0.78	0.50	4758	1.30	4057	0.99	N5619	1.20	
7458	0.20	74213	0.99	74LS168	1.15	74C047	0.78	0.51	4759	1.30	4058	0.99	N5620	1.20	
7459	0.20	74214	0.99	74LS169	1.15	74C048	0.78	0.52	4760	1.30	4059	0.99	N5621	1.20	
7460	0.20	74215	0.99	74LS170	1.15	74C049	0.78	0.53	4761	1.30	4060	0.99	N5622	1.20	
7461	0.20	74216	0.99	74LS171	1.15	74C050	0.78	0.54	4762	1.30	4061	0.99	N5623	1.20	
7462	0.20	74217	0.99	74LS172	1.15	74C051	0.78	0.55	4763	1.30	4062	0.99	N5624	1.20	
7463	0.20	74218	0.99	74LS173	1.15	74C052	0.78	0.56	4764	1.30	4063	0.99	N5625	1.20	
7464	0.20	74219	0.99	74LS174	1.15	74C053	0.78								

The Shack[®] is America's Parts Place[™]!

Low Prices and New Items Every Day!

Speed Up Your Wiring with This Cordless Power Wrapping Tool!



Reg. 21.95
Save 23%
16⁸⁸

So Easy! Why Solder Your Digital Projects?

Makes a perfect wrap every time! Unwraps, too. Built-in wire stripper/cutter. Positive indexing assures identical wraps on 0.025" square posts. Weight-balanced for comfort. Trigger-action on/off switch, carbon-steel tip. Jack for adapter/charger (below). Requires 2 nickel cadmium "C" cells. 276-1571 Sale 16.88


AC Adapter/Charger. U.L. listed.
273-1454 5.95

Subminiature LEDs

1⁵⁹ **New!**
Pkg. of 2

Highly-reflective chrome holders.
Red LED. 276-068 2/1.59
Green LED. 276-069 2/1.59

Cadmium Sulfide Photoresistor

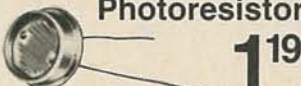

1¹⁹

Wide resistance range—5 megohms (darkness) to 100 ohms (bright light).
Max. power dissipation: 200 mW @ 170V. 276-116 1.19


Sound Generator IC



Linear/I²L Device
Save 20% Reg. 4.49 **3⁵⁹**

SN76477. Build your own synthesizer and create almost any type of sound—including music, explosions, gunshots, steam whistles. Built-in preamplifier provides line-level output. 28-pin DIP. With applications and data.
276-1765 Sale 3.59

Hall Effect Switching Detectors

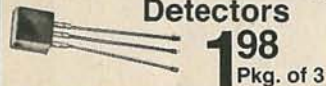

1⁹⁸ Pkg. of 3

Electronically senses magnetic field. 750 gauss "on" threshold. 5-16VDC supply. Similar to type 3006ULN.
276-1646 3/1.98

New! Pushbutton Key-Pad Module



16⁹⁵

Produces 12 Touch-Tone[™] Frequencies

1.5x2" face. Requires 3-5VDC @ 16 mA and 3.58 MHz crystal. With applications, specs.
277-1010 16.95
TV Colorburst Crystal. 3.58 MHz. 272-1310 1.99

Touch-Tone is a registered trademark of AT&T

PC Board and IC Breadboard Sockets

Non-Corrosive Contacts for Reliable Connections—Time After Time!



Low As 3²⁹

A **Experimenter's PC Board.** Design circuits on a socket, then transfer to PC board. Holes match Archer[®] breadboard sockets. 0.3" center with 550 connecting points.
276-170 3.29

B **Modular Breadboard Socket.** Standard 0.3" center for use with up to 40-pin ICs. Boards snap together horizontally or vertically and accept #22-30 solid hookup wire. 2 bus strips with 40 tie-points each and 47 rows of 5 connected tie-points. 550 connections. 2 1/2"x6".
276-174 10.95

C **Modular Breadboard Socket.** Smaller version of above. 270 connections in 2 bus strips of 20 tie-points each with 23 rows of 5 connected tie-points. 2 1/2"x3 3/4". 276-175 6.49

D **Mini-Socket.** 22 rows of 5 tie-points each plus 2 bus strips with 10 connections each. Interlocks with above. 2 1/2"x1 1/8". 276-176 4.49

Infrared Opto-Coupler



New! 1⁹⁹

TIL-111. LED optically coupled to NPN phototransistor. 5 ms switching time. 6-pin DIP. 276-132 1.99

TIL-119/4N31. LED coupled to NPN Darlington phototransistor. DC transfer ratio 300% min. @ 10 mA. 6-pin DIP. 276-133 1.99

VMOS Power FETs



New! 2⁴⁹ 1⁵⁹

Gate-protected transistors for digital, analog, or RF circuits.

A VN67AF. 15W dissipation. TO-202 case. 276-2071 2.49

B VN10KM. 1W dissipation. TO-92+ case. 276-2070 1.59

12VDC DPST Encapsulated Reed Relay



New! 99¢

Encased in protective plastic. Designed to fit printed circuit boards. Contacts rated 1/2 amp at 125VAC. 275-229 99¢

Miniature PC Mount DPDT Switches



Save \$1

Low As 99¢ Each

A Designed for right angle PC board mounting. Center "off". Contacts rated 6A @ 125VAC. 275-665 (Reg. 1.99) Sale 99¢

B Straight mount. Contacts rated 6A @ 125VAC. 275-668 (Reg. 2.19) Sale 1.19

12V, 5A Power Transformer



10⁹⁵

For Projects Or Replacement

Quality, heavy-duty type with steel frame for chassis mounting. Solder lug terminals for easy connections. 120VAC, 5A, 60 Hz primary. 4x2x 2 1/2". 273-1513 10.95

4-Digit LCD Timer/Clock Module



New! 24⁹⁵

- Large Half-Inch LCD Display
- 12 or 24-Hour Format

Just add a few parts and a battery, and you have a versatile nine-function, crystal-controlled timekeeper! Built-in backlight, dual time zones, 24-hour alarm, plus stopwatch, sleep, and control timer functions. 2 1/2"x1 1/2". 1.5VDC operation. 277-1007 24.95

Hobby Project Cases



Low As 1⁵⁹

Made of high-impact plastic, with internal slots to hold PC boards. Blue.

4x2x1 3/16" 270-220 1.59
4x2 1/16x1 1/16" 270-221 1.79
4 3/4x2 1/2x1 3/16" 270-222 1.99
6x3 3/8x1 3/16" 270-223 2.59
7 1/2x4 1/2x2 1/8" 270-224 2.99

Coils and Chokes



1⁹⁸ Pkg. of 100

Ideal for audio and RF circuits. Assortment includes PC chokes, inductors, tuned RF coils.
273-1570 100/1.98

Assorted Ferrites

1⁹⁸ Pkg. of 25

For chokes, RF coils, impedance matching transformers. Includes torroids, ferrite beads, cores, slugs.
273-1571 25/1.98

WHY WAIT FOR MAIL ORDER DELIVERY?
IN STOCK NOW AT OUR STORE NEAR YOU!

Retail prices may vary at individual stores and dealers.

CIRCLE 39 ON FREE INFORMATION CARD

Radio Shack[®]

A DIVISION OF TANDY CORPORATION • FORT WORTH, TEXAS 76102
OVER 7000 LOCATIONS IN 40 COUNTRIES

JANUARY 1981

LONG PLAY 10 HOUR TAPE RECORDER

Top quality AC-DC cassette recorder, modified to provide 5 continuous hours of recording and playback of true fidelity, distortion-free sound on each side of cassette for a total of 10 hours. Unit has many special built-in features. TDK D-C180 cassette supplied.



ONLY \$125.00*

PHONE RECORDING ADAPTER

Record incoming and outgoing calls automatically with this all solid state unit connected to your telephone jack and tape recorder. Starts recording when phone is lifted. Stops when you hang up, making a permanent record. Easily installed. No monthly charges.



\$24.50*

VOX VOICE ACTIVATED CONTROL SWITCH

Solid state. Self contained. Excellent adjustable sensitivity. Voices or other sounds activate and control recorder. Uses recorder mike or remote mike.



\$24.95*

Phone call Adapter \$24.50*, VOX \$24.95*, (* plus \$1.00 ea. shipping & handling), 10 hr. Recorder \$125.00* (* plus \$4.00 shipping & handling). California residents add tax. Mail Order, VISA, M/C, cod's okay, quantity discounts available. Money back guar. Free data.

AMC SALES, Dept. 19 9335 Lubec St., Box 928
Downey, CA 90241, Phone (213) 869-8519

CIRCLE 2 ON FREE INFORMATION CARD

POTTER BRUMFIELD 4 PDT RELAYS

- 14 pin style
- 3 amp contacts
- 24 volt d.c. or
- 120 volt a.c. coil
- Used but fully tested

\$1.50 each
specify coil voltage
LARGE QUANTITIES AVAILABLE




FLAT LEVER HANDLE MINI TOGGLE

S.P.D.T. MINI-TOGGLE
RATED AT 6 AMPS 120 VAC
1/4" - 40 MILLIING
\$1.00 EACH
10 FOR \$9.90



1 OHM 175 WATT WIREWOUND RESISTOR

\$1.75 each
8 1/2" long, 1-1/8" dia.

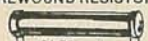

AXIAL ELECTROLYTIC CAPACITORS

8,000 MFD 15VDC \$1.50 ea.
3/78" long x 1.116" diameter
600 MFD, 100 VDC \$1.00 ea.
2.1116" long, 1" diameter
4,700 MFD 16 VDC 2 for \$1.50
2" long, 1" diameter



PHOTO - FLASH CAPACITOR

1100 MFD 330 VOLTS
3 1/4" x 1 1/4"
\$1.50 Each



3 X 5 SPEAKER

3oz. Magnet
8 OHM Impedance
\$2.50 each



LARGE QUANTITIES AVAILABLE

ALL ELECTRONICS CORP.

905 S. Vermont Ave.
Los Angeles, CA 90006
(213) 380-8000

Store & Warehouse Hours
9 AM - 5 PM
Monday thru Friday
Saturday
10 AM - 3 PM

SEND FOR OUR FREE CATALOG

TERMS

- Quantities Limited
- Min. Order \$10.00
- Add \$2.00
- Shipping USA
- Calif. Res. Add 6%
- Prompt Shipping

FLASHER L E D

Litronix FRL-4403

diffused red led with built
in flashing unit T 1 1/4 package
pulse rate 3hz = 5v 20 ma.

2 for \$1.70

COMPUTER GRADE CAPACITORS

ALL ARE BRAND NEW

1,700 MFD.
150 VDC \$2.00
2 1/2 in. dia. x 4 1/4 in.

3,000 MFD.
150 VDC. \$2.00
3 in. dia. x 4 1/2 in.

6,400 MFD. 60 VDC. \$2.50
1-3/8 in. dia. x 4 1/4 in.

22,000 MFD. 15 VDC. \$2.50
2 in. dia. x 2 1/2 in.

22,000 MFD. 50 VDC. \$3.50
3 in. dia. x 4 1/2 in.

CLAMPS TO FIT CAPACITORS 50c ea

22/44 EDGEBOARD CONNECTOR
TIN SOLDER TAIL. 156" x .200"

LARGE QUANTITIES AVAILABLE
\$1.35 each 10 for \$12.50

TRANSFORMERS

115 volt primaries

3 VOLTS @ 200MA. \$1.25

6 VOLTS @ 250MA. \$1.25

12.6 VOLTS C.T. @ 250MA. \$1.50

12.6 VOLTS C.T. @ 1 AMP. \$2.75

16.5 VOLTS @ 3 AMP. \$6.50

50K SLIDE POT \$6.50 each

Knobs for Slide Pots 20c each

audio taper

• 3-1/2 inch long • 2-1/2 inch wide

COUNTERS/TIMERS

continued from page 59

impedance change requires some simple conditioning before the UCT can "read" it. Additional conditioning may be required to get accurate measurements if the signals are plagued by such afflictions as contact bounce, noise, or glitches. Low-pass filters or monostables may be enough.

Even when the input signal is purely electronic (such as how many times a microprocessor interrupt-request flag goes up during a particular program run), a situation may demand some conditioning beyond that afforded by the UCT's own input circuitry.

All that is mentioned here in the interest of tracing those devilish problems down to their source—and saving your capable UCT from undeserved criticism when it counts things "funny." It just counts what it sees.

As you get more experience with your Universal Counter/Timer, you'll be able to pick up or invent a few tricks of your own. If you come up with something interesting, share it with us. It helps to keep life interesting. R-E

BULLET ELECTRONICS

P.O. BOX 401244R
GARLAND, TX. 75040
214 . 278-3553

Sound Effects Kit \$18.50



The SE-01 is a complete kit that contains all the parts to build a programmable sound effects generator. Designed around the new Texas Instruments SN76477 Sound Chip, the board provides banks of MINI DIP switches and pots to program the various combinations of the SLF Oscillator, VCO, Noise, One Shot, and Envelope Controls. A Quad Op Amp IC is used to implement an Adjustable Pulse Generator, Level Comparator and Multiplex Oscillator for even more versatility. The 3 1/4" x 5" PC Board features a prototype area to allow for user added circuitry. Easily programmed to duplicate Explosions, Phaser Guns, Steam Trains, or almost an infinite number of other sounds. The unit has a multiple of applications. The low price includes all parts,

assembly manual, programming charts, and detailed 76477 chip specifications. It runs on a 9V battery (not included). On board 100mW amp will drive a small speaker directly, or the unit can be connected to your stereo with incredible results! (Speaker not included). 76477 is included. Available separately for \$3.15 each.

New! Special Purchase

2N3055 115W NPN POWER TRANSISTOR TO-3

Most popular transistor for power supplies, audio amps, switching, etc.

Limit 20 per customer 50¢ Each



PARTS

1N5350	13V 5W Zener	.25
1N5360	25V 5W Zener	.20
4mz62	6.2V 400MW Zener	.08
1N3890	100V 12A High Speed Diode	1.30
40430	400V 6A Triac TO-66	.75
CD4046	PLL CMOS	.99
LM339/3302	Quad Comparator	.99
MPS A20	NPN Gen Pur TO-92	8/1.00
2SC1849	High Frequency NPN TO-92	6/1.00
CD4511	BCD to 7 Seg Decoder/Latch	.85
CD4026	Decade Counter w/7 Seg Out	1.80
CD4016	Quad Analog Switch	.50

SATISFACTION GUARANTEED ON ALL PARTS AND KITS. EXAMINE FOR 10 DAYS IF NOT PLEASED RETURN IN ORIGINAL FORM FOR REFUND. INSURE FOR AMOUNT IF PRODUCT VALUE IS OVER \$10.

BANKRUPT Game Manufacturer Dumps Computer Backgammon Game

The Engineers designed this one too good, making it too costly to be competitive. Result... Chapter XI. We bought all the parts and can offer the unit as a kit for over 60% off retail!

DISPLAY POINT WILL VERIFY THE NUMBER OF PIECES ON ANY POINT

You get: Double sided glass PC Board

Powerful 8035 Micro Processor Chip
Two 2716 style mask ROMS
RAM Chips, LED readouts,
Keyboard, Instructions
AC Plug transformer

8035 and program ROMS only with schematics. \$12.00



BUILT IN COMPUTER DICE ROLL

CLEAR MOVE ALLOWS TO CLEAR ENTRY TO ALLOW NEW MOVE.

PLUS MUCH MORE!

\$39.95

Includes Case Does not include player pieces

7 Watt Audio Amp Kit \$5.95

SMALL, SINGLE HYBRID IC AND COMPONENTS FIT ON A 2" x 3" PC BOARD (INCLUDED). RUNS ON 12VDC. GREAT FOR ANY PROJECT THAT NEEDS AN INEXPENSIVE AMP. LESS THAN 3% THD @ 5 WATTS. COMPATIBLE WITH SE-01 SOUND KIT.

Overvoltage Protection Kit \$6.95

Protect your expensive equipment from overvoltage conditions. Every computer should have one! Works with any fused DC power source from 10 to 20 volts up to 25 amps.

Super Value Power Transformer

Well made, open frame transformer with mounting ears. Build a +5 and ±12 supply with inexpensive parts. Free schematics of several designs. Primary 117VAC. SEC #1 15VAC @ .5A SEC #2 15 VAC @ .5A SEC #3 8VAC @ 2.5A.

SPECIAL BONUS: Order 2 Get free 723 voltage regulator IC!

\$2.95 Each

THE PERFECT TRANSFORMER

117VAC primary, 12VAC secondary @ 200ma
Great for all your CMOS, or low power TTL projects. PC board mount.


99¢ ea. 3/\$2.50
Size: 1.5" W x 1.25" D x 1.25" H

The Greatest Breakthrough In Electronic Music Ever!

New! The Super Music Maker

\$23.50 (Basic Kit)

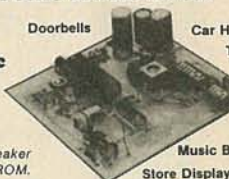Does not include speaker switches or 2708 ROM.



Forget Electronic Music Kits that are a nightmare of numerous IC's... that use hard to find bi-polar PROM's or are limited to just a few notes! The new per Music Maker Kit from Bullet features a single microprocessor IC that is factory programmed with 20 short songs. With the addition of an optional 2708 ROM, it will play up to 1,000 more notes. Unique addressing scheme allows up to 250 notes per song; up to 100 different songs per ROM (total notes less than 1,000). Quality PC board is designed to make assembly easy. If you can program your own 2708's we give complete instructions. Pre-programmed PROM Albums are available with hundreds of song selections For only \$15.00 each. Lists available.

* Operates on *12VDC or 12VAC (transformer required)

* On board 7W power amp drives 8 ohm load

* Envelope control gives decay to notes

"Next tune" switch allows sequential playing of all songs.

ATTRACTIVE PLASTIC CASE * 8 position and 5 position WITH CUSTOM FRONT PLATE DIP switches: Add \$2.50 \$6.50 * 2708 (unprogrammed) \$9.60

Does not include speaker or 2708 ROM. DIP Switches are available separately. Requires 12V AC or DC @ 600 ma.

* NO C.O.D.'s

* SEND CHECK M.O. OR CHARGE CARD NO.


* PHONE ORDERS ACCEPTED ON VISA AND MASTERCARD ONLY.

* ADD 5% FOR SHIPPING

* TX RES. ADD 5% STATE SALES TAX

* FOREIGN ORDERS ADD 10% (EXCEPT CANADA) (20% AIRMAIL) U.S. FUNDS ONLY.

(214) 278-3553

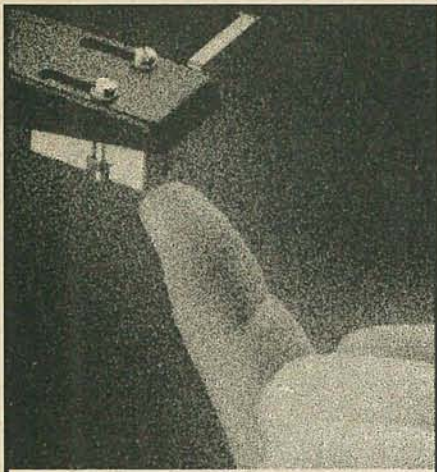

SC-2 gives your cartridge more than The Finger!

The famous SC-1 stylus brush (standard of the record and hifi industries) now has a synergistic fluid called SC-2.

SC-2 Fluid enhances and speeds cleaning and yet protects diamond adhesives, cartridge mounting polymers and fine-metal cantilevers against the corrosive effects of many other "cleaners."

The Discwasher SC-2 System. Stylus care you can finger as clearly superior.



discwasher[®]
PRODUCTS TO CARE FOR YOUR MUSIC

1407 N. Providence Rd.
Columbia, Missouri 65201

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

Free Information Number	Page
2	AMC Sales..... 100
17	A & P Products, Inc..... 35
31	Active Electronics..... 85
—	Advance Electronics..... 13
67,18	Advanced Computer Products..... 92-93
23	All Electronics..... 100
4	American Antenna..... Back Cover
60	Ancrona..... 89
43	Arkon Electronics Ltd..... 34
—	ATV Research..... 102
53	B & K Precision Dynascan Corp..... 15
—	Karel Barta..... 84
65	Beckman Instruments..... 40
—	Bullet Electronics..... 100
—	Burdex Security..... 82
—	CIE—Cleveland Institute of Electronics..... 18-21
30	C.F.R. Associates..... 83
5	Cal-West Supply Co..... 88
3	Carpenter Mfg..... 84
6	Chaney Electronics..... 94
11	Channelock..... 26
—	Command Productions..... 82
61	Communications Electronics..... 76
64	Concord—Computer Components..... 96
—	Crystal Radios..... 84
19	Jan Crystals..... 75
—	Dage Scientific..... 102
35	Digi-Key..... 101
66	Discwasher..... 102
—	EMC—Electronics Measurements..... 88
—	Electronic Technology To-day..... 32
37	Etc..... 88
25	Fluke..... 6-7
33,40,41,42	Fordham Radio Supply..... 24,30,75,80
21,22	Formula International..... 86-87
44	Gladstone..... 75
32	Global Specialties..... 5
—	Global T.V. Electronics..... 102
26	Godbout Electronics..... 94
—	Grantham College of Engineering..... 70
36	David Hafler..... 32
59	Hameg..... 81
29	Heath..... 3 Cover
—	Information Unlimited..... 84
54	International Components..... 98
62	International Electronics Unlimited..... 83
—	JS & A..... 1
9,10	Jameco Electronics..... 89-90
—	McKay Dymek..... 74
45,46,16	Mercury International..... 31,67,71
15	Meshna..... 83
14	Micro-Ace..... 97
—	Micro Management Systems..... 84
—	Micro Mart..... 83
—	NRI National Radio Institute..... 8-11
—	National Technical Schools..... 36-39
47	Netronics..... 69
48,49	O.K. Machine & Tool..... 2,17
8	Paccomm..... 70
55	Paia..... 77
51	Poly-Paks..... 98
39	Radio Shack..... 99
38	Rainbow Industries..... 28
7	Ramsey Electronics..... 95
13	SLG Waber..... 34
—	Sabtronics..... 23
—	H.W. Sams..... 27

56	Shure Brothers..... 72
52	Solid State Sales..... 94
—	Spacecoast Research..... 82
27	Tab Books..... 29
57,58	Triplett..... 2 Cover
—	Tronics 2000..... 74,81
—	USI..... 84
34	VIZ..... 33
20	Wersi Electronics..... 77

EQUIPMENT REPORTS

continued from page 35

our actual tests showed an overall improvement of about 5%. Different vehicles under different driving conditions will undoubtedly find different results.

Because of limitations on time, gas-economy tests were not checked. The Tiger has a reversible plug that allows the user to revert back to the car's original ignition at a twist of the wrist; thus, if failure of the CDI should ever occur, the vehicle will not become disabled. If it should ever be necessary to remove the CDI for service, two simple jumper-wire connections will provide normal operation of the vehicle without having to reconnect the original wiring harness.

Is the installation of the CDI system justified? If the extra few percent horsepower is important, and the additional mileage without replacing points and plugs a major consideration, then the answer may be yes.

The Tiger 500 CDI is available from Tri-Star Corp., PO Box 1727, Grand Junction, CO 81501. The assembled version sells for \$69.95 and the kit version sells for \$59.95. **R-E**

FREE KIT Catalog

FUNCTION GENERATOR KIT \$59.95
Auto-Ranging Gap-meter kit \$79.95
contains TEST & EXPERIMENTER'S EQUIP.
Phone 415-447-3433
Write or Phone for FREE CATALOG.
Average 1 minute Saturday call is 21¢.

DAGE SCIENTIFIC INSTRUMENTS
BOX 1054R LIVERMORE CA 94550

ATV Research ...specialists in CCTV and computer monitors!
Video monitors - color & B/W • TV Cameras, kits, parts & plans • Video-to-RF modulators
* Free catalog, Phone or write. (402) 987-3771
13-RE Broadway Dakota City, NE. 68731

Enjoy Satellite TV Now



Better than Cable TV—Over 200 TV and radio services. Why waste money? Learn the whole story and build a video system the family can enjoy. No commercials, **FREE** movies, sports and Vegas shows—worldwide, crystal clear reception connects to any TV set. Big (8x11 in.) book loaded with details, photos, plans, kits—**TELLS EVERYTHING! Satisfaction Guaranteed.**

Send \$7.95 TODAY! Add \$2.00 for 1st class (air mail) or call our 24 hour C.O.D. rush order line (305) 862-5068.

GLOBAL ELECTRONICS,
P.O. Box 219-E, Maitland, Florida 32751

Brainchild

Yesterday — Remember the first Heathkit Analog Computer (1957)? Or the Heathkit Single-Sideband Transmitter (1958)? How about the Heathkit Multiplex Adapter for FM stereo reception (1960)?

Each was a ground-breaking innovation for its day. Each was a Heathkit brainchild.


Today — Today's brainchildren include the popular Heathkit All-In-One Computer, a complete computer system with disk storage, smart terminal, two Z80 microprocessors — all in one compact unit.

Also rising fast, the Heathkit Screen Star, a new projection TV that brings together the best in video technology to create the sharpest color picture ever on a six-foot diagonal screen.

Heath imagination applied to micro-processor electronics created the Heathkit Weather Computer. It monitors current weather, tracks changes, stores data — and puts it all at your fingertips.

Tomorrow — Tomorrow's brainchild, like today's and yesterday's, will combine the newest and the best in electronics to create a new state-of-the-art.

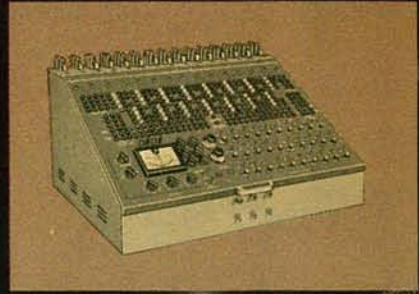On the drawing boards right now are new designs for amateur radios, audio components, computers, color TV's, test instruments and new educational programs — all in easy-to-build, money-saving kits. They'll be appearing soon in Heathkit Catalogs and at Heathkit Electronic Centers. It's one catalog you don't want to be without.



Heathkit®

SEND FOR FREE CATALOG

Write to Heath Co., Dept. 020-734,
Benton Harbor, MI 49022.

Heathkit



VISIT YOUR HEATHKIT STORE

In the U.S. and Canada visit your nearby Heathkit Electronic Center where Heathkit products are displayed, sold and serviced. See the white pages of your phone book. In the U.S., Heathkit Electronic Centers are Units of Veritechnology Electronics Corp.

GX-379

CIRCLE 29 ON FREE INFORMATION CARD



In one year our **K40** antenna has become the largest selling CB antenna in the world!

1. It's more expensive ...

2. It's made better...

3. It's proven best!

\$42.50 suggested retail

And when you pay more, you expect more!

MORE PERFORMANCE:

The K40 is guaranteed to transmit further or receive clearer than any antenna it replaces. We know it will. We've tested it with 771 CB'ers just like you for one year.

MORE FLEXIBILITY:

You can fit your K40 to any mounting surface. It will fit any vehicle you'll ever own! That includes choppers, dune buggies, gutters, mirror mounts, luggage racks, trunks, hatchbacks, through roofs, semis, pick ups and RV's.

MORE QUALITY:

It's not imported. It's not made in Taiwan, Korea or Japan. It's American made in an American town. It's made with better materials that cost more and by professional people we pay more. And we designed it right here in the U.S.A.

*Including optional mounts at extra cost.

... This Antenna is so DYNAMITE you receive a ...

DOUBLE GUARANTEE

GUARANTEE I: The K-40 will transmit farther and receive more clearly than the antenna it replaces or the customer will receive a prompt and full refund from the Registered K-40 Dealer who installed and tuned it.

GUARANTEE II: Unconditionally guaranteed for 12 months. Guaranteed against cracking, chipping, or rusting. Guaranteed against mechanical failure. Guaranteed against electrical failure. Guaranteed against accidental breakage. No exclusions. No gimmicks. For a full 12 months.



...Here's what the leading CB publications said.

CB TIMES: "... it's not often that a product bursts onto the market scene, dominates and improves CB'ing for everyone. American Antenna and the K40 are doing it—repeated tests showed the K40 could out-perform the major competitive brands."

RADIO-ELECTRONICS: "The results of our tests showed that, in three different positions of the monitoring receiver, the model K40 equaled or out-performed the competitive antenna. Apparently, American Antenna's advertising is not merely Madison Avenue showmanship."

PERSONAL COMMUNICATIONS: "... an impressive 95% of the trials, the K40 out-performed the existing mobile antennas. We had to try one for ourselves. ... in every case, the K40 either equaled or out-performed its competitor."

"No ifs, ands, or buts! The K40 Antenna from American Antenna would have to be just about the best antenna around."

CB MAGAZINE: "Introduced in October, 1977, the K40 quickly became the top seller and in mid 1978, became the number one selling antenna in the nation."

...Here's what CB'ers all across the country said.

ANTENNA SPECIALISTS: "... truck driver and CB'er for 10 years ... 50% further than my M410 'Big Momma'."

—J.H. Collett, 207 McFee, Bastrop, LA

AVANTI: "I'm an electronic technician with a Second Class FCC license ... I was able to transmit 70% further and tune the SWR 75% lower than my Avanti."

—H.R. Castro, VRR, Monserrante D-67, Salinas, Puerto Rico

PAL: "... 20% better in transmission and reception than my 5/8 wave Pal Firestik."

—John A. Blum, Box 446, Zellenople, PA

SHAKESPEARE: "... I've been a CB'er for three years and the K40 is the best I've ever had. Better in reception and transmission than my Shakespeare."

—H. Bachert, Jr., 15 King Rd., Park Ridge, NJ

HUSTLER: "Compared to my Hustler XBLT-4, the K40 can consistently transmit 40% further and the reception was better. The K40 is the perfect way to complete a CB system."

—Jerome R. Brown, 7800 S. Linder, Burbank, IL



(SPECIAL NOTE) IF YOU'RE A BEGINNER:

Our K40 Dealers will be happy to sell you any of the older style and less expensive antennas that are great bargains for any beginning CB'er.

AMERICAN ANTENNA
ELGIN, IL 60120

© COPYRIGHT AMERICAN ANTENNA 1979

**K40
POWER!**

... Sold exclusively by 3500 American K40 Dealers throughout the U.S. & Canada.

CIRCLE 4 ON FREE INFORMATION CARD