

48783

**BUILD A TIMEX/SINCLAIR EXPANSION
TO ENHANCE THE ZX81
OPERATING SYSTEM**

\$1.50 JULY 1983
U.K. 85p
DGS

Radio- Electronics®

COMPUTERS - VIDEO - STEREO - TECHNOLOGY - SERVICE

What's coming in
NAVIGATION SYSTEMS
for your car

Build a
TALKING ALARM CLOCK
and listen to the time

How to use
LOW-N-C SIGNALS
for frequency calibration

Build a
DASHBOARD DMM
for your car

All about
TRANSCONDUCTANCE AMP IC's
and how to use them



PLUS:

- ★ Videogames ★ Hobby Corner
- ★ Drawing Board ★ Service Clinic
- ★ New Idea ★ State-Of-Solid-State





affordable precision

Excellence by Design

BBC has been building multimeters and other instrumentation for European engineers and technicians for over 7 decades. And now, twelve advanced technology BBC meters with a complete line of accessories are available in the U.S. Prices range from under \$50.00 to \$595.00. No other manufacturer offers you comparable price and performance values.

Forms that Follow Function

To achieve a family of "hands free" instrumentation designed for heavy-duty use in a wide variety of environments, BBC relied on the industrial design skills of the Porsche Design Studios. You'll like the results.

The unique folding design lets you adjust the viewing angle. Extra large LCD displays make the meters easy to read. The exclusive function and range switch is logically laid out. And the folding meters even turn off automatically when you close the case.

Accuracy Where it Counts

Precision is a tradition at BBC. The 3½ digit folding models feature 0.1% basic dc accuracy. For higher precision measurements, the model MA 5D delivers 0.05% basic dc accuracy and 30,000 counts.

Precision Values

Some of the best news about BBC meters is that you can get them for less than you've been paying for old technology meters. They are built to the world's highest safety standards, VDE/DIN, and are backed by one of the strongest warranties in the industry.

Local Availability

BBC has worked hard to make these meters available through leading U.S. distributors and representatives. There is an outlet close to you. And, if your instrumentation supplier doesn't carry BBC yet, we'll gladly tell you who does. Call toll free: **1-800-821-6327**. (In CO, 303-469-5231)

BBC-METRAWATT/GOERZ

6901 W. 117th Avenue
Broomfield, CO 80020
Telex 45-4540
(303) 469-5231

- Send me information on BBC meters.
- I'd like to be on your mail list.

Fast-Response Coupon



Name _____

Title _____

Company _____

Address _____

City _____ State _____ Zip _____

Telephone (_____) _____

Engineering Excellence in Test and Measurement



CIRCLE 60 ON FREE INFORMATION CARD


Double Your Troubleshooting and Testing Productivity . . . Or Your Money Back!

Six-digit readout: Automatically tracks every CRT test. We call it digital autotracking. It's patent pending.

Bright dual-trace CRT: 60 MHz (-3 dB); 100 MHz (-12 dB).

Delta PPV, Time, Freq: Measure any part of a waveform for PPV, time or frequency using Delta measurements. Just dial in the waveform section you want to measure and push.

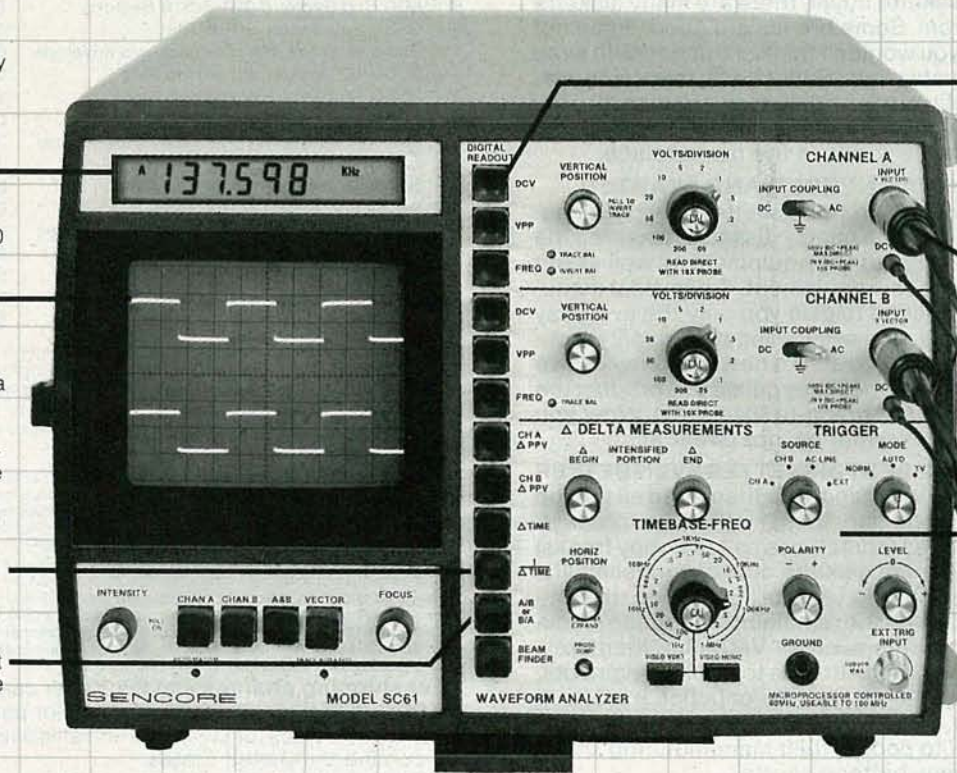Simplify Freq ratio tests: Automatically compare input/output ratio of multiply/divide stages from 1:1 to 1:999,999 with the push of a button.



Autotracking DCV, PPV, Freq: Measure DCV to .5%; PPV to 2%; freq. to .001%. Just push a button for either Channel A or B.

One probe input: One probe input per channel for all measurements - digital and scope - with 5 mV to 2000 V measuring range. (2 lo-cap probes provided.)

Super sync: ECL provides rock-solid sync trigger circuits with only 4 controls; includes TV sync separators for video work.

U.S. Patent Pending
Financing Available

The first scope with push button digital readout. If you use general purpose oscilloscopes for troubleshooting or testing, we can double your present productivity with the SC61 Waveform Analyzer, the first instrument to turn every conventional scope measurement into an automatic digital readout.

No more graticule counting. Connect only one probe to view any waveform to 100 MHz. Then, just push a button to read DCV, PPV, frequency and time — automatically!

There are no graticules to count or calculations to make, which speeds every measurement.

The digital readout is from 10 to 10,000 times more accurate as well.

Plus you have everything you want to know about a test point, at the push of a button, which speeds troubleshooting tremendously.

A special Delta function even lets you intensify parts of a waveform and digitally measure the PPV, time or frequency for just that waveform section.

And it's neat. No more tangled leads, piles of probes or dangling cords. The SC61 is an entire test station in one unit.

The one and only. There are other scopes with digital readout, but none of them completely automate every conventional scope measurement so you can automatically analyze any waveform without counting one single graticule. Totally automatic waveform analyzing at the push of a button. It will make all the difference in your productivity.

Double your productivity. When we say the SC61 will double your productivity, we're being conservative. We've seen cases of

three, four, even ten time increases in productivity with this first-of-its-kind, automated oscilloscope. Every situation is different, however, so try the SC61 and judge for yourself. Here's our offer.

Money back guarantee. If the SC61 does not at least double your productivity during the first thirty days, you may return it for a full refund, including freight both ways.

Call today. Get the entire SC61 Waveform Analyzer story. Call toll-free today, and ask for our eight page color brochure. It could be the most productive call you make this year!

Phone Toll-Free
1-800-843-3338

Alaska, Hawaii, Canada and
South Dakota call collect
(605) 339-0100

SENCORE
3200 Sencore Drive, Sioux Falls, SD 57107

CIRCLE 70 ON FREE INFORMATION CARD
CIRCLE 71 FOR DEMONSTRATION

ULTRA Diskettes

Now...Diskettes you can swear by, not swear at.

Lucky for you, the diskette buyer, there are many diskette brands to choose from. Some brands are good, some not as good, and some you wouldn't think of trusting with even one byte of your valuable data. Sadly, some manufacturers have put their profit motive ahead of creating quality products. This has resulted in an abundance of low quality but rather expensive diskettes in the marketplace.

A NEW COMPANY WAS NEEDED AND STARTED

Fortunately, other people in the diskette industry recognized that making ultra-high quality diskettes required the best and newest manufacturing equipment as well as the best people to operate this equipment. Since most manufacturers seemed satisfied to give you only the everyday quality now available, an assemblage of quality conscious individuals decided to start a new company to give you a new and better diskette. They called this product the *Ultra* diskette, and you're going to love them. Now you have a product you can swear by, not swear at.

HOW THEY MADE THE BEST DISKETTES EVEN BETTER

The management of *Ultra* Magnetics then hired all the top brains in the diskette industry to make the *Ultra* product. Then these top bananas (sometimes called floppy freaks) created a new standard of diskette quality and reliability. To learn the "manufacturing secrets" of the top diskette makers, they've also hired the remaining "magnetic media moguls" from competitors such as Verbatim, Memorex, Dyan and many more. Then all these top-dollar engineers, physicists, research scientists and production experts (if they've missed you, send in your resume to *Ultra*) were given one directive...to pool all their manufacturing know-how and create a new, better diskette.

HOW ULTRA DISKETTES ARE MANUFACTURED

The *Ultra* Magnetics crew then assembled the newest, totally quality monitored, automated production line in the industry. We know that some of *Ultra*'s competitors are still making magnetic media on equipment that is old enough to vote. Since all manufacturing equipment at *Ultra* is new, it's easy for *Ultra* to consistently make better diskettes. You can always be assured of ultra-tight tolerances and superb dependability when you use *Ultra*. If all this manufacturing mumbo-jumbo doesn't impress you, we're sure that at least one of these other benefits from using *Ultra* diskettes will:

- TOTAL SURFACE TESTING** - For maximum reliability, and to lessen the likelihood of disk errors, all diskettes must be totally surface tested. At *Ultra*, each diskette is 100% surface tested. *Ultra* is so picky in their testing, they even test the tracks that are in between the regular tracks.
- COMPLETE LINE OF PRODUCTS** - For a diskette to be useful to you and your computer, it must be compatible physically. *Ultra* Magnetics has an entire line of 5 1/4-inch and 8-inch diskettes.
- SPECIALLY LUBRICATED DISK** - *Ultra* uses a special oxide lubricant which is added to the base media in the production of their diskettes. This gives you a better disk drive head to media contact and longer head and disk life.
- HIGH TEMPERATURE/LOW-MARRING JACKET** - A unique high temperature and low-marring vinyl jacket allows use of their product where other diskettes won't work. This special jacket is more rigid than other diskettes and helps eliminate dust on the jacket.
- REINFORCED HUB RINGS** - Standard on all *Ultra* mini-disks, to strengthen the center hub hole. This increases the life of the disk to save you money and increase overall diskette reliability.
- DISK DURABILITY** - *Ultra* disks will beat all industry standards for reliability at well over millions and millions of revolutions. They are compatible with all industry specifications as established by ANSI, ECMA, ISO and JIS.
- CUSTOMER ORIENTED PACKAGING** - All *Ultra* disks are packaged 10 disks to a carton and 10 cartons to a case. The economy bulk pack is packaged 100 disks to a case without envelopes or labels.
- LIFETIME WARRANTY** - If all else fails, remember, all disks made by *Ultra* Magnetics, (except bulk pack) have a lifetime warranty. If your *Ultra* disks fail to meet factory specifications, *Ultra* Magnetics will replace them under the terms of their warranty.
- SUPERB VALUE** - With *Ultra*'s automated production line, high-quality, error-free disks are yours without high cost.



SAVE ON ULTRA DISKETTES

Product Description	Part #	CE quant. 100 price per disc (\$)
8" SSSD IBM Compatible (128 B/S, 26 Sectors)	81726	1.99
8" SSDD IBM Compatible (128 B/S, 26 Sectors)	81701	2.49
8" DSDD Soft Sector (Unformatted)	82701	3.19
8" DSDD Soft Sector (1024 B/S, 8 Sectors)	82708	3.19
5 1/4" SSSD Soft Sector w/Hub Ring	50001	1.79
5 1/4" Same as above, but bulk pack w/o envelope	00153	1.39
5 1/4" SSSD 10 Hard Sector w/Hub Ring	50010	1.79
5 1/4" SSSD 16 Hard Sector w/Hub Ring	50016	1.79
5 1/4" SSDD Soft Sector w/Hub Ring	51401	1.89
5 1/4" Same as above, but bulk pack w/o envelope	00096	1.49
5 1/4" SSDD 10 Hard Sector w/Hub Ring	51410	1.89
5 1/4" SSDD 16 Hard Sector w/Hub Ring	51416	1.89
5 1/4" DSDD Soft Sector w/Hub Ring	52401	2.79
5 1/4" Same as above, but bulk pack w/o envelope	00140	2.39
5 1/4" DSDD 10 Hard Sector w/Hub Ring	52410	2.79
5 1/4" DSDD 16 Hard Sector w/Hub Ring	52416	2.79
5 1/4" SSQD Soft Sector w/Hub Ring (96 TPI)	51801	2.49
5 1/4" DSQD Soft Sector w/Hub Ring (96 TPI)	52801	3.49

SSSD = Single Sided Single Density; SSDD = Single Sided Double Density; DSDD = Double Sided Double Density; SSQD = Single Sided Quad Density; DSQD = Double Sided Quad Density; TPI = Tracks per inch.
For less than 100 diskettes, add 10% to our quantity 100 price.
For additional compatibility info call *Ultra* Magnetics at 408-728-7777.

The Small Print

To get the fastest delivery from CE of your *Ultra* computer products, send or phone your order directly to our Computer Products Division. Be sure to calculate your price using the CE prices in this ad. Michigan residents please add 4% sales tax or supply your tax I.D. number. Written purchase orders are accepted from approved government agencies and most well rated firms at a 30% surcharge for net 30 billing. All sales are subject to availability, acceptance and verification. All sales are final. Prices, terms and specifications are subject to change without notice. All prices are in U.S. dollars. Out of stock items will be placed on back order automatically unless CE is instructed differently. Minimum prepaid order \$50.00. Minimum purchase order \$200.00. International orders are invited with a \$20.00 surcharge for special handling in addition to shipping charges. All shipments are F.O.B. Ann Arbor, Michigan. No COD's please. Non-certified and foreign checks require bank clearance.

For shipping charges add \$8.00 per case or partial-case of 100 8-inch discs or \$6.00 per case or partial-case of 100 5 1/4-inch mini-discs for U.P.S. ground shipping and handling in the continental United States.

Mail orders to: Communications Electronics, Box 1002, Ann Arbor, Michigan 48106 U.S.A. If you have a Master Card or Visa card, you may call and place a credit card order. Order toll-free in the U.S. Dial 800-521-4414. In Canada, order toll-free by calling 800-265-4828. If you are outside the U.S. or in Michigan, dial 313-994-4444. Telex 810-223-2422. Order your *Ultra* diskettes from Communications Electronics today.

Copyright ©1983 Communications Electronics™

Ad #050583



Order Toll-Free!
800-521-4414

In Michigan 313-994-4444

ULTRA
MAGNETICS
diskettes

COMMUNICATIONS
ELECTRONICS™

Computer Products Division

854 Phoenix □ Box 1002 □ Ann Arbor, Michigan 48106 U.S.A.
Call TOLL-FREE (800) 521-4414 or outside U.S.A. (313) 994-4444

SPECIAL FEATURE

- 43 **ALL ABOUT AUTOMOTIVE NAVIGATION SYSTEMS**
Computer-aided navigation is expected to play a big part in the car of the future. But, as this report shows, that future is not all that far away. **Danny Goodman**

BUILD THIS

- 47 **EXPAND YOUR TIMEX/SINCLAIR OPERATING SYSTEM**
Upgrade your computer with 8K of battery-backed-up CMOS RAM. **Paul W.W. Hunter**
- 51 **TALKING ALARM CLOCK**
Part 2. With this fun project you'll never have to tell time again. **Lee Glinski**
- 59 **DIGITAL VOLTMETER FOR YOUR CAR'S DASHBOARD**
This easy-to-build project helps keep an eye on your car's electrical system. **Fred L. Young Sr. and Fred L. Young Jr.**

TECHNOLOGY

- 4 **VIDEO ELECTRONICS**
Tomorrow's news and technology in this quickly changing industry. **David Lachenbruch**
- 10 **SATELLITE/TELETEXT NEWS**
The latest happenings in communications technology. **Gary H. Arlen**
- 12 **VIDEOGAMES**
A new generation of videogames. **Danny Goodman**
- 63 **USING LORAN-C FOR TIME AND FREQUENCY CALIBRATION**
All about the Loran-C navigational system and how it works. **R.W. Burhans**

CIRCUITS AND COMPONENTS

- 55 **TRANSCONDUCTANCE OPERATIONAL AMPLIFIERS**
What they are, and some practical examples of how to use them. **Thomas Henry**
- 68 **HOW TO DESIGN ANALOG CIRCUITS**
An in-depth look at positive- and negative-feedback circuits. **Manny Horowitz**
- 74 **NEW IDEAS**
An award-winning project from one of our readers
- 76 **HOBBY CORNER**
Some questions from the mailbag. **Earl "Doc" Savage, K4SDS**
- 78 **DRAWING BOARD**
More on voltage regulators. **Robert Grossblatt**
- 80 **STATE OF SOLID STATE**
Power MOSFET amplifiers. **Robert F. Scott**

VIDEO

- 82 **SERVICE CLINIC**
A dish full of bugs. **Jack Darr**
- 82 **SERVICE QUESTIONS**
R-E's Service Editor solves technicians' problems.

RADIO

- 90 **COMMUNICATIONS CORNER**
Communications and the disabled. **Herb Friedman**

COMPUTERS

- 88 **COMPUTER CORNER**
What's new in microcomputers. **Les Spindle**

EQUIPMENT REPORTS

- 24 **Philips Model PM 3215 50-MHz Dual-Trace Oscilloscope**
- 30 **Vector P184-7 Slit-N-Wrap Tool**
- 33 **Kensington Microware System Saver Protection Device for Apple II Computers**
- 38 **Soar Corporation 8050 Digital Multimeter**

DEPARTMENTS

- | | |
|---------------------------------|-------------------|
| 8 Advertising and Sales Offices | 106 Market Center |
| 136 Advertising Index | 95 New Books |
| 137 Free Information Card | 39 New Products |
| 20 Letters | 6 What's News |

ON THE COVER

To most drivers, one of the most exasperating experiences is getting lost in completely unfamiliar territory. But an independent California inventor and a giant Japanese automobile manufacturer are hard at work trying to make that situation a thing of the past. If their efforts are successful, it won't be long until a common automotive accessory will be a navigational computer complete with a video display. This month, we'll preview the future and take a look at both systems. The story begins on page 43.



This upgrade for the Timex/Sinclair 1000 adds 8K of non-volatile RAM. The add-on can be used to increase the system/user memory, or more usefully, for the permanent storage of machine-language routines—thus, in effect, expanding the operating system. Find out more about it starting on page 47.

COMING NEXT MONTH

On Sale July 19

A special section devoted to electronics and photography. Among the things we'll look at are:

- The Sony Mavica system
 - Autofocus and autoexposure electronics
 - Electronics in the darkroom
- And lots more!**

Radio-Electronics, (ISSN 0033-7862) Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Second-Class Postage Paid at New York, N.Y. and additional mailing offices. One-year subscription rate: U.S.A. and U.S. possessions, \$14.97; Canada, \$17.97; Other countries, \$22.47 (cash orders only, payable in U.S.A. currency.) Single copies \$1.50. © 1983 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

Subscription Service: Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Box 2520, Boulder, CO 80322.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

VIDEO ELECTRONICS

DAVID LACHENBRUCH
CONTRIBUTING EDITOR

New VCR Standard

A new VCR standard that eventually is expected to replace the three current half-inch home formats (Beta, VHS, and the European Video 2000) has been approved by a Standardization Conference of 122 Japanese, European, and American companies, whose representatives have been meeting in Tokyo for more than a year.

The new "8mm Video" standard was established to avoid the Beta-vs.-VHS problem that has plagued the home-VCR industry since its inception. In order to avoid disrupting the market, member companies, in the past, have insisted that the new standard was designed only for use in portable camera-VCR combinations; but with the issuance of the specifications, many conference members have dropped that pose. Although initially the system is designed to record for only 90 minutes on one cassette (in the NTSC color system), the standard is obviously flexible enough to accommodate much longer recording times.

The recording medium is an 8-mm-wide cassette tape. The cassette itself measures 95 × 62.5 × 15-mm, slightly smaller in length and width than a standard audio cassette and just a touch thicker than the thickest part of such a cassette. The tape can be either the metal-powder or metal-evaporated type, and the system uses helical scan with a head drum 40mm in diameter.

Three separate audio systems are specified in the new 8mm specifications — a standard longitudinal track, an FM-stereo helical system multiplexed with the video signal of the type used in Beta Hi-Fi recorders, and a helical PCM (Pulse Code Modulation) track. The FM sound system is compulsory, the other two optional. A cue track is also reserved.

The cassette itself is designed for maximum simplicity and low cost, without tape guides and with a wide mouth to accommodate many different loading systems. It has two lids to keep out dust, and recognition holes for automatic detection of tape type and thickness, as well as grips for an auto-changer.

Sources in the Standardization Conference say that an increase in recording time to four hours by means of slower tape speed and thinner tape is easily possible now. Development in the future of new heads and new tape formulations (including the perpendicular or vertical-domain recording system, now in advanced stages of development) will make possible further increases in record/play time.

In Japan, there are widespread forecasts that 8mm VCR's will begin to appear before the year is over, but in any event the American market could see the first portables in 1984. Assuming that longer-playing versions are approved by the Standardization Conference, home decks could show up in about three years, and at that point the new format should begin to take over from Beta and VHS.

The 8mm standard was approved by the conference for both NTSC and PAL color systems, with different parameters — the PAL version has a record/play time of one hour. At the last minute, France's Thomson-CSF proposed that a baseband recording system, "timeplex," be used for any SECAM models. Therefore the conference approved no SECAM standard, but earmarked the French proposal for further study.

The agreement on a new standard format has great implications on the future of the entire video field, laying the groundwork for a new, far more flexible and potentially lower-cost system and eventually ending the standards war.

DIGITAL TV

It can now be definitely reported that color-TV sets using all-digital signal processing will be available, at least in token quantities, in 1984. In the United States, they're expected to be available from General Electric and Zenith, with offerings also possible from Sharp and Sony. All are customers of ITT for its set of seven VLSI digital IC's. The first digital sets may well be in the form of component TV, because they will be designed for add-ons to make possible features not available with analog TV's. One of the first add-ons is expected to be a ghost eliminator. The new digital TV's also are expected to enhance the capabilities of home computers (since they are essentially computers themselves). With the development of low-cost frame-store accessories, the digital TV's will have the potential ability to simulate high-definition television by doubling the number of lines in the picture, inserting "derived" lines between the transmitted ones. Other features could be stop-motion and picture-in-picture (for viewing two channels simultaneously). While digital sets are imminent, those special effects probably won't be along for several years.

R-E

"I built this 16-bit computer and saved money. Learned a lot, too."

Save now by building the Heathkit H-100 yourself. Save later because your computer investment won't become obsolete for many years to come.

Save by building it yourself. You can save hundreds of dollars over assembled prices when you choose the new H-100 16-Bit/8-Bit Computer Kit – money you can use to buy the peripherals and software of your choice.

H-100 SERIES COMPUTER SPECIFICATIONS:

USER MEMORY:
128K-768K bytes*

MICROPROCESSORS:
16-bit: 8088
8-bit: 8085

DISK STORAGE:
Built-in standard
5.25" disk drive,
320K bytes/disk

KEYBOARD:
Typewriter-style,
95 keys, 13
function keys,
18-key numeric pad

GRAPHICS:
Always in graphics mode.
640h/225v resolution;
up to eight colors
are available**

COMMUNICATIONS:
Two RS-232C Serial
Interface Ports and
one parallel port

* 128K bytes standard.
** Optional.

DIAGNOSTICS:
Memory self-test
on power-up

AVAILABLE SOFTWARE:
Z-DOS (MS-DOS)
CP/M-85
Z-BASIC Language
Microsoft BASIC
Multiplan
SuperCalc
WordStar
MailMerge
Data Base
Manager
Most
standard
8-bit CP/M
Software

The H-100 is easy to build – the step-by-step Heathkit manual shows you how. And every step of the way, you have our pledge – "We won't let you fail." Help is as close as your phone, or the nearest Heathkit Electronic Center.†

And what better way to learn state-of-the-art computing techniques than to build the world's only 16-bit/8-bit computer kit? To run today's higher-speed, higher-performance 16-bit software, you need an H-100. It makes a big difference by processing more data faster.

Dual microprocessors for power and compatibility. The H-100 handles both high-performance 16-bit software and most current Heath/Zenith 8-bit software.

Want room to grow? The H-100's standard 128K byte Random Access Memory complement can be expanded to 768K bytes – compared to a 64K standard for many desktop computers.

And the industry-standard S-100 card slots support memory expansion and additional peripheral devices, increasing future upgradability of the H-100.

High-capacity disk storage, too. The H-100's 5.25" floppy disk drive can store 320K bytes on a single disk. The computer also supports an optional second 5.25" and external 8" floppy disk drives. And an optional internal Winchester disk drive will be available soon.

For more information, circle the reader service number below. Better yet, visit your Heathkit Electronic Center for a demonstration!

The H-100 gives me the most for my computer dollar!



Heathkit
Heath
Company

Heathkit Electronic Centers are units of Veritechnology Electronics Corporation.
Heath Company and Veritechnology Electronics Corporation are subsidiaries of Zenith Radio Corporation.

CIRCLE 16 ON FREE INFORMATION CARD

WHAT'S NEWS

Cellular radio system to begin in U.S.A.

The FCC has allocated 666 channels to a new "cellular" two-way radio service, which, with its greatly more efficient use of the radio spectrum than the current mobile telephony system, will make a car telephone available to anyone almost anywhere in the United States.

In a cellular system, an area such as a city is not covered with a single high-powered transmitter, as is done today. Instead, the area is divided up into sections, or "cells," each with a low-power transmitter whose range is pretty much limited to the area of the cell. Since adjacent cells are on non-interfering frequencies, the same frequency can be "re-used" for several widely separated cells in a large city or metropolitan area, increasing greatly the number of phone calls that may be handled in a given area.

The FCC opened applications for cellular system licenses, and as of March, 1983, had already granted permits to cellular mobile

telephone systems in nine U.S. metropolitan areas. Service is expected to start within two years.

A cellular system is made up of four elements (plus the regular telephone system). Those are the Mobile Telecommunications Switching Office (MTSO); a base station (transmitter/receiver), with its antennas, in each cell; wire or microwave connecting links between base stations and the MTSO, and the mobile radios, which may be vehicle-mounted or hand carried.

When a telephone user wishes to make a call, he simply dials the number of the mobile subscriber, as he would any other call. (He need know nothing of the whereabouts of the car he is calling.) The call then goes to the mobile unit's MTSO, which sends a paging signal over all the base stations in the area. The mobile unit, which monitors a nearby base station continuously, responds automatically to the paging signal and establishes contact with the base station. The MTSO then switches the call to one of the traffic channels of

that base station, and the subscriber's phone rings.

If the mobile subscriber travels out of the cell during a call, communications are automatically switched over to the base station of the cell into which he moves.

The subscriber in a mobile vehicle simply dials the number he wants, as he would on his home phone.

The service is expected to cost subscribers anywhere from \$75 to \$150 per month. That would include an access fee of between \$10 and \$50 per month, plus charges for actual use. Those might run from 12 cents per minute in off-peak hours to 40 cents per minute in peak periods.

OK Industries forms electronics division

OK Industries, a New York-based manufacturer of production equipment for the electronics and telecommunications industries, has formed an Electronics Division. The new division is putting out a broad range of bench and

field test instruments, with the idea of offering "truly superior laboratory instruments at prices within the reach of even the 'smallest' user."

The first product from the new division is a 1-MHz function generator with both frequency and amplitude modulation; it will sell at \$250.

900-MHz personal radio may be on the way

The FCC has issued a Notice of Proposed Rulemaking to implement a new personal radio-communications service (PRCS), proposed by General Electric, in the 900-MHz frequency band. G.E. hopes that the FCC will issue a Final Report and Order within the next few months.

The FCC proposal is for a system that will consist of a base station connected to the telephone network, and one or more units that can be installed in cars. The user in a car will then be able to place calls to any telephone, or be reached in the car from any telephone, provided he is within the system's range.

The FCC notice proposes to set aside 8 MHz in the 900-MHz band for the new service. That reservation would permit 133 channels of 30 kHz each for two-way PRCS communications.

New TV space camera


RCA has developed a new telephone camera tube that can detect objects the size of a soccer ball 22,000 miles away.

Serving as the "eye" of a special camera of the Ground-based Electro-Optical Deep Space Surveillance System (GEODSS), it can see objects 10,000 times dimmer than the faintest ones visible to the naked eye.

The new Silicon-Intensifier Target (SIT) tube, type C21146H, is the largest of its type that RCA has ever made. Its 32mm of usable area is twice that of the targets now used in the surveillance cameras that provide the resolving capability of the GEODSS equipment. The target has four times as many silicon diodes as older types.

The GEODSS system answers the need for advanced tracking

continued on page 8

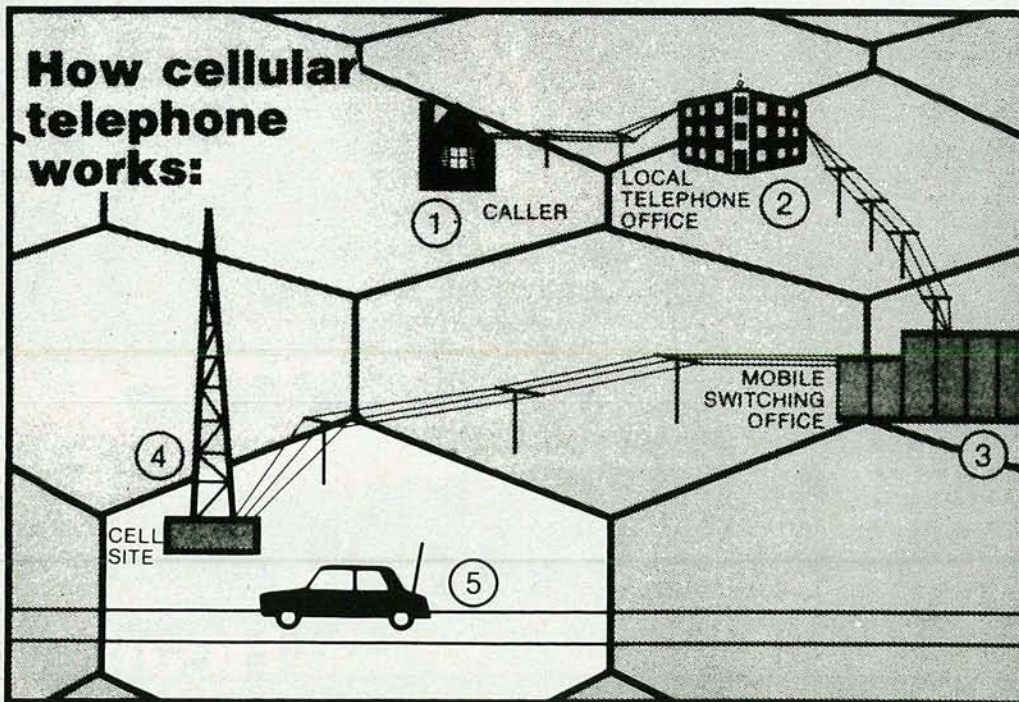

CELLULAR NETWORK OVER PART OF A CITY. The call is routed from the caller's home via the local telephone exchange to the Mobile Telecommunications Switching Office, a complex automatic device that locates the car, makes the connection, and then switches the call from cell to cell as the car moves through the area.

Now. Tektronix 60 MHz Performance is just a free phone call away!

Wide-range vertical sensitivity:
Scale factors from 100 V/div (10X probe) to 2 mV/div (1X probe). Accurate to $\pm 3\%$. Ac or dc coupling.

Two high-sensitivity channels: dc to 60 MHz bandwidth from 10 V/div to 20 mV/div; extended sensitivity of 2 mV/div at > 50 MHz.

Sweep speeds:
from 0.5 s to 50 ns. To 5 ns/div with X10 magnification.

Delayed sweep measurements:
Accurate to $\pm 3\%$ with single time-base 2213; to $\pm 1.5\%$ with dual time-base 2215.

Complete trigger system. Includes TV field, normal, vertical mode, and automatic; internal, external and line sources; variable holdoff.

Probes included. High-performance, positive attachment 10-14 pF and 60 MHz at the probe tip.



Tektronix 2213 60 MHz OSCILLOSCOPE

These easy to order scopes are proof that it's not expensive to have advanced, 60 MHz performance from Tektronix on your bench. It's just practical! Feature for feature, the Tek 2213 and 2215 set a price/performance standard unmatched among portable scopes. And are backed by the industry's first three-year warranty on all labor and parts, including the CRT.

So advanced they cost you less: \$1200* for the 2213! \$1450* for the dual time base 2215! These low costs are the result of a new design concept that utilizes

fewer mechanical parts than any other scope.

Yet there's no scrimping on performance and reliability. You have the bandwidth for digital and analog circuits. The sensitivity for low signal measurements. The sweep speeds for fast logic families. And delayed sweep for fast, accurate timing measurements.

Scope. Probes. Three-year warranty and expert advice. One free call gets it all! You can order, or obtain literature, through the Tektronix National Marketing Center. Technical personnel, expert in oscil-

loscope applications, will answer your questions and can expedite delivery. Direct orders include probes, operating manuals, 15-day return policy, full Tektronix warranty and worldwide service back-up.

**Order toll free:
1-800-426-2200
Extension 12**

In Oregon call collect:
(503) 627-9000 Ext. 12

*Price F.O.B. Beaverton, OR. Price subject to change.

Tektronix
COMMITTED TO EXCELLENCE

CIRCLE 74 ON FREE INFORMATION CARD

WHAT'S NEWS

continued from page 6

methods. That need is caused by the ever-increasing number of objects in space. (An estimated 15,000 pieces—satellites and debris—are now drifting in orbit.) It uses two 40-inch telescopes for deep space tracking and a 15-inch instrument for scanning lower altitudes. Each telescope is coupled to a camera containing one of the new low-light-level SIT camera tubes.

Pictures from the TV cameras are converted into digital pulses and fed into a computer, which examines the data to sort out stars from moving objects. The computer software also contains a catalog of known stars and orbiting satellites for identification and location purposes.

Class A power amplifier for car stereo

Visonik of America, Inc., a manufacturer and distributor of automotive-sound products, has introduced the first Class-A power amplifier specifically intended for car-stereo applications. That amplifier, the model A265, boasts an output of 65 watts-per-channel with total harmonic distortion claimed to be less than 0.01% from 20 Hz to 20 kHz.

The chief advantage Class-A operation is that it eliminates the distortion introduced by the push-pull action of more conventional Class-B amplifiers. Among the unit's circuit features are full complementary symmetry, just 30 dB of negative feedback, and a wide open-loop bandwidth for a high slew-rate and low TIM distortion. The amplifier also includes an exclusive *Perma-Tect* circuit. That circuit monitors the output current and voltage across the output transistors; and, should those levels become excessive, the circuit limits the power without interfering with the signal. In addition, the amplifier has thermal breakers to prevent overheating. According to a company spokesman, that combination makes the amplifier "virtually unblowable."

The A265 offers a variable low-level (100-550mV) input for use with almost any program source. A Molex harness is included for easy installation.

Sanyo LCD TV

Sanyo has developed 3 and 4-inch liquid crystal TV's, using a newly developed liquid-crystal display (LCD) and amorphous silicon thin-film transistors (aSiTFT) that

are designed for switching.

The display on the 4-inch model is 60 × 80 mm (about 2 $\frac{3}{8}$ × 5 $\frac{3}{32}$ inches) and exterior dimensions are 253 × 30 × 113 mm (approximately 10 × 1 $\frac{7}{32}$ × 4 $\frac{15}{32}$ inches)—truly pocket sized.

The new switching transistor is said to provide greater reliability than previous approaches, and the new TN (twisted nematic mode) crystal produces better contrast and a wider view angle. The display boasts are 220 × 240 pixels.

The liquid-crystal displays are being rapidly developed for use in TV sets, office machines, etc., but picture clarity and driving systems remain problems.

"Telephone on an chip"

High reliability and reduced component count are among the features of the new telephone technology introduced by American Telecommunications Corporation, a subsidiary of Comdial. ATC is a supplier of telephones, answering machines, and automatic dialers to the Bell system, as well as to major independent telephone companies and retailers.

Evidence of that new technology can be seen in two ATC products. The *Allegro* is a compact residential phone that features a 10-number memory dialer, automatic redial, and a true hold button. The other new phone, the *Voice Express 41* is designed for business applications. It combines an improved speakerphone, a 41-number automatic dialer, clock, call timer, and security features. Both phones incorporate a new IC that is essentially a complete telephone. That IC is part of ATC's effort to reduce the cost and complexity of manufacturing telephones that meet Bell-system standards.

According to Robert E. Lee, ATC Vice President of Engineering, the company's goal is to totally automate telephone assembly. By using sophisticated robots to assemble the telephones, Comdial hopes to obtain the distinct technology and cost advantage it feels is needed to compete with imported low-cost, and often lower-quality, telephones.



THE ALPHASONIK A265 Class-A power amplifier delivers 65 watts-per-channel into a 4-ohm load. It features Visonik's exclusive *Perma-Tect* protection circuitry.

Radio-Electronics

Hugo Gernsback (1884-1967) founder

M. Harvey Gernsback, editor-in-chief

Larry Steckler, CET, publisher

Arthur Kleiman, editor

Josef Bernard, K2HUF, technical editor

Carl Laron, WB2SLR, associate editor

Brian C. Fenton, assistant editor

Jack Darr, CET, service editor

Robert F. Scott, semiconductor editor

Herb Friedman, communications editor

Gary H. Arlen, contributing editor

David Lachenbruch, contributing editor

Earl "Doc" Savage, K4SDS, hobby editor

Danny Goodman, contributing editor

Dan Rosenbloom, production manager

Robert A. W. Lowndes, production associate

Joan Roman, circulation director

Arline R. Fishman, advertising coordinator

Cover photo by Robert Lewis

Radio-Electronics is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature*.

Gernsback Publications, Inc.
200 Park Ave. South
New York, NY 10003
President: M. Harvey Gernsback
Vice President: Larry Steckler

ADVERTISING SALES 212-777-6400

Larry Steckler
Publisher

EAST/SOUTHEAST

Stanley Levitan
Radio-Electronics
200 Park Ave. South
New York, NY 10003
212-777-6400

MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen
Radio-Electronics
540 Frontage Road—Suite 325
Northfield, Illinois 60093
312-446-1444

PACIFIC COAST Mountain States

Marvin Green
Radio-Electronics
413 So. La Brea Ave.
Los Angeles, Ca 90036
213-938-0166-7




R-E


YOU SELECT FULL MANUAL
OR FULL AUTORANGING

500 HOUR BATTERY LIFE

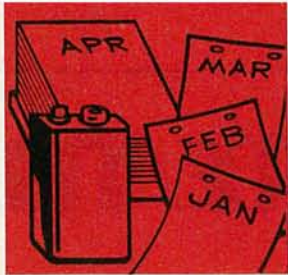HIGH CONTRAST LCD
SHOWS MEASUREMENT
AND FUNCTION





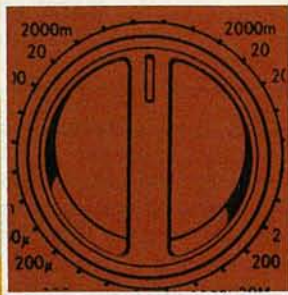0.25% dc volt
accuracy
Continuity beeper
Diode test
Transient and
overload protected
High energy fuse



EASY TO USE... RELIABLE
SINGLE-ROTARY SWITCH
CONTROL

OTHER NEW
DMM MODELS
PRICED
FROM
\$75.00

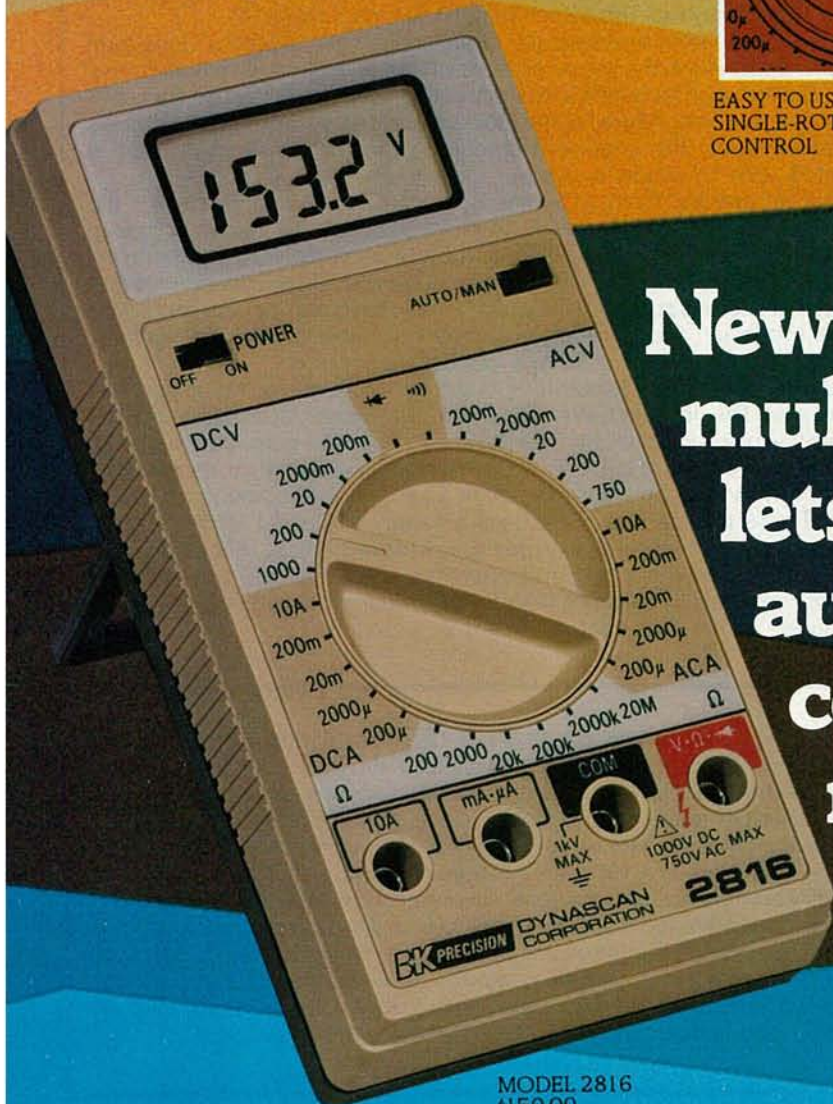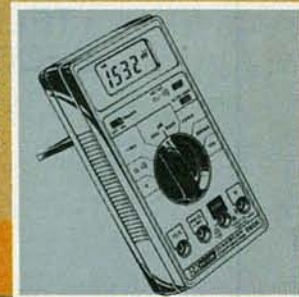

New! A digital multimeter that lets you choose autoranging convenience or manual control

MODEL 2816
\$150.00

To learn more about the 2816
and the complete line of new B&K-PRECISION
DMMs, see your local distributor or call
[1 312 889-9087].

B&K PRECISION DYNASCAN
CORPORATION

6460 West Cortland Street • Chicago, Illinois 60635 • 312/889-9087

International Sales, 6460 W. Cortland St., Chicago, Illinois 60635
• Canadian Sales, Atlas Electronics, Ontario

South and Central American Sales, Empire Exporters, Plainview, NY 11803

CIRCLE 42 ON FREE INFORMATION CARD

SATELLITE/TELETEXT NEWS

GARY ARLEN
CONTRIBUTING EDITOR

TELETEXT DECODERS

The CBS Television Network has started a teletext service called Extravision. The service will be broadcast by the almost 200 CBS affiliated stations (90 percent as this is being written), making it the first national broadcast teletext service. Extravision transmits 100 pages of national and local information and advertising as well as closed captioning of some programs. The service uses the North American Broadcast Teletext Standard (NABTS).

Time Inc. and Matsushita Electric Industrial Co. (Panasonic) have signed a "long-term technology agreement" under which the two companies will co-develop hardware for home-information systems. The first such product is a low-cost decoder for Time's teletext service—with the hoped-for \$150 device being offered under the Panasonic name. The first test models of the unit will be available late this year, with production runs set to begin in 1984 at Matsushita's automated color-TV factory in Japan.

The teletext decoder will use the "North American Broadcast Teletext Specification," the technical format that Time Inc., CBS, NBC and A.T.&T. have adopted. It will be able to pick up Time's full-channel teletext feed, now being tested, as well as vertical blanking-interval teletext, such as the feeds being planned by the television networks. The decoder will include an extension unit to permit add-ons such as a full alphanumeric keyboard, printer, and floppy disks for data storage. In addition, the terminal can accommodate joysticks for videogames, an audio cassette recorder, and a modem for two-way service.

The decoder will also be able to handle software for the customized information services that Time plans to transmit. The decoder's interactive capability makes faster access possible, and the unit will include provisions that allow it to be used for general-purpose computing. Time's teletext service will be offered to cable TV systems, starting with companies operated by its subsidiary American TV and Communications. In addition to news and other typical information services, Time's teletext project includes a variety of innovative recreational activities that take advantage of the high-quality graphics of the technology. For example, a youth-oriented section of the service includes an electronic version of "Mr. Potatohead," that allows children to compose a face by selecting features they would like to insert and placing them over the face outline on the TV screen.

VCR'S AND TELETEXT

EECO (1601 E. Chestnut Ave., Santa Ana, CA 92701), a California company that produces tape-editing equipment and mini-computer systems, is testing *Pictureware*, a system that will permit home videocassette-recorders to record and transmit videotex or teletext signals. *Pictureware* is an interactive still-frame video technology that uses a VCR and a decoder box to compress images, text, and audio onto videotape; material can then be retransmitted in high-speed bursts. The equivalent of a 100-page teletext magazine with 75 color pages of near video-picture quality can be transmitted in about seven seconds—about the time it takes to cycle such a group of pages through a standard vertical blanking-interval sequence. The system becomes interactive through the use of phone lines or two-way cable. EECO sees the target price for the decoder needed to receive the videotex and teletext signals at about \$300. A modified VCR, needed to pick up the digital data, will cost about \$100 more than an unmodified one. EECO plans to begin marketing its *Pictureware* system in 1984.

AROUND THE TELETEXT CIRCUIT

In an apparently unprecedented marketing maneuver, Zenith says its will build and sell teletext receivers in a local market if a TV-station owner in that community commits to offering British-format teletext for at least five years. The unusual offer would presumably encourage broadcasters to begin a service knowing that a supply of receivers will be available in their communities. Zenith, which has long favored the "sturdy" British technology, is presumably also willing to deal with broadcasters working in other teletext formats. The company has already been the primary supplier of teletext receivers for other field trials of teletext.

RCA Laboratories has received a patent for a system that will increase the legibility and color contrast of teletext material by modifying the video signal. The system, primarily for use in set-top teletext decoders, is said to improve color definition and clarity.

R-E

MAKE THE A P CONNECTION

NOW YOUR SINGLE SOURCE FOR ALL YOUR ELECTRONIC
CIRCUIT BUILDING, TESTING AND INTERCONNECTION NEEDS.

**Introducing Our Complete Line of
Interconnection Products and
Accessories...Featuring Our New
Insulation Displacement Connectors.**

No matter what your requirements in interconnection products, we have just what you are looking for. DIP, Socket, and Card-Edge IDC connectors, all styles and sizes of Headers and D-Submin in both IDC and solder versions. Also flat cable in both gray and rainbow in a wide range of widths.

Brand New Low Cost IDC Assembly Tool
So sensationally low-priced it won't put a "crimp" in your budget.

Famous A P Quality and Price

Every A P product is built with time-proven quality and dependability. And best of all...each one is very competitively priced.

Your Single Source

A P makes hundreds of electronic circuit building and testing devices as well as a complete line of interconnection products and accessories. Everything from Breadboards, Super-Strips, Test Clips and Poweraces to Headers, Connectors and Cable.

A P has it all for you!



A P PRODUCTS INCORPORATED • 9450 Pineneedle Drive • P. O. Box 540 • Mentor, Ohio 44060 • [216] 354-2101 • TWX: 810-425-2250
In Europe, contact A P PRODUCTS GmbH • Baumlesweg 21 • D-7031 Weil 1 • West Germany

For the name of your nearest distributor call Toll Free 800-321-9668. (In Ohio call collect 216-354-2101.)

CIRCLE 56 ON FREE INFORMATION CARD

VIDEOGAMES

Future games

DANNY GOODMAN, CONTRIBUTING EDITOR

THE ARRIVAL OF SO-CALLED THIRD-generation home-videogame systems like the Atari 5200 and Colecovision, plus Coleco's announcement of a "fourth generation" tape-loading peripheral, leads me to speculate about what kind of home videogames we're likely to be playing in the late 1980's. I'm not talking about science-fiction gadgetry—stuff like holographic projections coming from your R2-D2 robot. I'm talking about the application of technologies that we have today, buried behind locked laboratory doors—technology that needs only a little refinement to be both practical and affordable.

Interactivity between game play and player will be the area where we will see the greatest changes in the years ahead. This interactivity will take many forms.

Late last year, the world was treated to a glimpse of the interactive future when Sega/Gremlin (555 Millrose, Los Angeles, CA 90038) demonstrated an arcade game that superimposed a shoot-'em-up space chase on a videodisc-scene backdrop that looked like outtakes from a low-budget *Star Wars* imitation. If a player successfully hit an alien ship, the disc would jump to a scene of an explosion in space. The game play and background are not particularly well integrated in this early commercial attempt, but the concept is a valid one.

Videodiscs, by themselves, are just now offering interactive adventures such as *Murder, Anyone?* from Vidmax (36 East 4th St., Cincinnati, OH 45202). In that game, the viewer's response to clues causes the story to jump from one character's account of the crime to another's. As a viewer enters a response into a remote control keypad, the microprocessor-controlled videodisc player accesses the proper segment of the disc.

But that's nothing compared to the possibilities of integrating more traditional videogame play-screens with the high-resolution effects of a videodisc scene. With game-console-generated graphics linked to the videodisc frame counter (there are 54,000 individually addressable frames on a disc), we might have the effect of walking down a corridor in an adventure maze-game. Suddenly a game-generated object—how about a treasure chest—appears on the floor in the distance. As we walk toward it, the chest, in

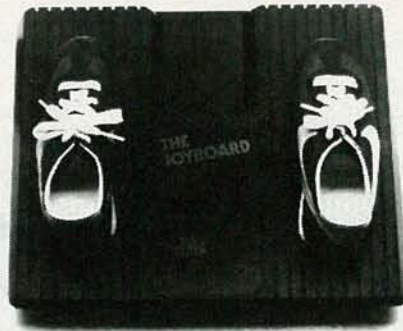


FIG. 1

proper perspective, gets larger. When we're standing directly in front of the chest, we have arms (from the disc) reach down and pick it up. Together, the chest and arms recede out of sight below the screen as though we actually had picked it up. Other game-generated objects could be picked up by the same disc-generated arms later in the game.

Another interactive trend we'll see involves increased use of our other senses. Right now, only our senses of sight and hearing are stimulated by a videogame. For now, we'll have to live with the graphics-resolution limitations of the home color-TV. Better-quality speech synthesis is about all we can expect from the current selection of systems. But stereo sound-effects will be the next step in attempted realism. For example, we'll be able to hear enemy ships approaching from off-screen to the left or right.

Beyond that, the sense of touch opens the way for game development into the late 1980's. Small solenoids will be built into a hand controller to give your palm a little "kick" when you catch a fly ball in a baseball game, or vibration when you're at the control of a race car.

We can even see special environmental videogame-chairs that partially enclose us in a sensory barrage of surround sound and that have motorized or vibrating seats to stimulate the sensations of flying a B-17 through flack or piloting the Millennium Falcon through hyperwarp. Most joystick-type controls would be in the armrests; a steering controller and two foot-pedals would swing in front of us from one side for games requiring that kind of control. The enclosure could adequately contain vapors from scented air

and release them in synchronization with changing screens. For example, as you walked through dark, musty caverns of an adventure maze-game, only your keen sense of smell would help you distinguish between several look-alike scenes.

Are these ideas far fetched? Hardly. Coleco has already demonstrated the kicking hand controller, but decided to hold off for a while. And a new company in the add-on business, Amiga, has shown a foot-operated floor controller (the *Joyboard*, shown in Fig. 1) that lets you stand up and recreate the motions of skiing down a mountain in conjunction with a skier's-eye-view of a slalom course. There's even a prototype environmental chamber that spins you around and gives you a real sense of motion as you pilot your craft. Those are but the simple first steps toward future homebound simulations of real-life and imagined adventures.

U.S. Games' Eggomania for Atari 2600



CIRCLE 101 ON FREE INFORMATION CARD

U.S. Games	Eggomania									
GRAPHICS	■	■	■	■	■	■	■	■	■	■
SOUND	■	■	■	■	■	■	■	■	■	■
EASE OF LEARNING	■	■	■	■	■	■	■	■	■	■
CHALLENGE	■	■	■	■	■	■	■	■	■	■
VALUE	■	■	■	■	■	■	■	■	■	■
	1	2	3	4	5	6	7	8	9	10
	Poor		Fair		Good		Excellent			

U.S. Games (1515 Wyatt Drive, Santa Clara, CA 95054) is dedicated to produc-

continued on page 14

Slashes Fordham Lowers Prices on **B&K PRECISION** Test Equipment

Now Fordham is passing on to customers the hugest savings possible on test instruments. To help celebrate the opening of our new 40,000 square foot facility on Long Island, we've purchased an extra large inventory of B&K Precision products.

We're offering the quality of name brand products and the benefits of our volume purchasing power. While supplies last we guarantee these unbelievably low prices.

3 1/2 Digit LCD Autoranging DMM

Model 2845
Reg. \$175.00 **Now \$79⁹⁵ each**

B&K PRECISION


- Fully automatic, auto-ranges on all functions.
- Range lock holds any range.
- 0.1% accuracy.
- Fast reading.
- 0.5" LCD display.
- Autozeroing.
- Autopolarity on all ranges.
- Audible continuity indicator.
- Varistor and fuse over-load protection.
- RF shielded.
- Meets UL 1244 safety standards.



8-Trace, 4 Channel 100 MHz Dual Time Base Scope

Model 1500
Reg. \$2575.00 **Now \$1489⁰⁰ each**

B&K

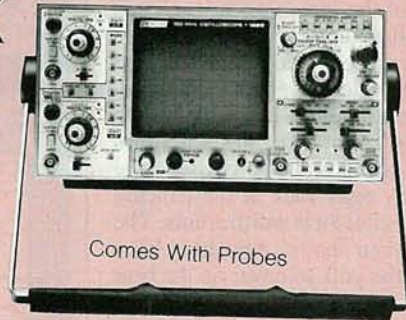

Comes With Probes

- 100 MHz response, 3.5nS rise time • 2nS/div. sweep rate with 10X magnifier • Trigger views or four separate inputs • Dual time base • 1M ohm inputs or 50 ohm inputs • 1mV/div sensitivity to 100 mHz • CH 1 frequency counter output • Delayed sweep, 20 nS to 0.5 seconds • Alternate timebase
- Switching power supply • Selectable chop frequencies • Voltage and current probe calibrators.

Low Distortion Function Generator

Model 3010
Reg. \$220.00

Now \$187⁵⁰ each



- Generates sine, square and triangle waveforms • Variable amplitude and fixed TTL squarewave outputs • 0.1 Hz to 1 mHz in six ranges • Typical sine wave distortion under 0.5% from 0.1 Hz to 100 kHz • Variable DC offset for engineering applications
- VCO external input for sweep-frequency tests.

Dynapeak Transistor Tester

Model 520B
Reg. \$239.00

Now \$199⁷⁵ each



- Fast testing • Hi/Lo drive • Works in-circuit when others won't • Identifies leads of bipolars and FET's • Random lead connection • Audible test OK 'beep'
- Automatic NPN/PNP and Si/Ge identification.

CRT Restorer/Analyzer

Model 467
Reg. \$495.00

Now \$420⁷⁵ each



- Restores color and b/w picture tubes like new! Uses the most powerful restoration method known with minimal danger to the CRT • Exclusive multiplex test technique tests all three guns of color CRT's simultaneously under actual operating conditions, even CRT's with common G1 and G2, with real dynamic tests • Instant, automatic tracking.

FOR ORDERING OR PRICING ON OTHER TEST EQUIPMENT

**Call Toll Free
(800) 645-9518**

N.Y.S. (800)832-1446

FORDHAM

260 Motor Parkway, Hauppauge, N.Y. 11788



■ Master Charge ■ VISA ■ COD
■ Money Order ■ Check
\$50.00 minimum order
COD's extra (required 25% deposit)

N.Y. State residents add appropriate sales tax.

ADD FOR SHIPPING AND INSURANCE	
\$250.00 \$4.50
\$251.00 to 500.00 6.50
501.00 to 750.00 8.50
751.00 to 1000.00 12.50
over 1000.00 15.00

VIDEO EQUIPMENT QUALITY • LOW PRICES OFF-THE-SHELF DELIVERY from FORDHAM of course.

**BUY
OF THE
MONTH**



MODEL V-1880

BP STABILIZER/IMAGE ENHANCER/RF CONVERTER/ VIDEO FADER/2-WAY DISTRIBUTION AMPLIFIER

OUR PRICE \$135.00 each

Most versatile video processor. Contains five units in one: stabilizer (video guard remover); image enhancer; video to RF converter; video fader; and dual output distribution amplifier.

Stabilizer Will correct entire range of copy guard distortion such as jitter, vertical roll or black bar travelling through picture.

Enhancer Lets you attain best picture for your own preference.

RF Converter Allows your TV set to receive video and audio signals from your image enhancer, guard stabilizer, video camera, computer, VCR, etc. The direct video signal from any video component can be fed into the V-1880 and converted to a usable RF signal that can go to your TV antenna terminals.

Video Fader Used to produce professional fade ins and fade outs.

BP VIDEO GUARD STABILIZER MODEL V-1875



OUR PRICE \$45.00 each

Has self contained A&B and bypass switch. Many movies, concerts and special programs for sale or rental are copy guarded. This removes copy guard and allows you to make copies. Many TV sets will not play prerecorded tapes because copy guard causes picture to roll and jitter, turn to snow or disappear. Video Guard Stabilizer removes copy guard from signal.

BP VIDEO GUARD STABILIZER/ RF CONVERTER MODEL V-1877



OUR PRICE \$69.95 each

Same as above but with a built-in RF Converter that gives the model V-1877 an RF output which can be fed directly to the antenna terminals of a TV set. This enables you to remove the copy guard from a pre-recorded tape and view it on a TV using only a VCR.

Use as an RF Converter only. Used in conjunction with your TV, you can feed direct audio and video signals from any video device such as video camera, computer, portable VCR, etc.

BP VIDEO COMMAND CENTER MODEL V-4803

OUR PRICE \$59.95 each

A switcher that can accept 6 inputs and direct them to 3 outputs. Utilizes switch similar to one used on home VCR's. You avoid signal loss incurred by using splitters.



JERROLD 60 CHANNEL CORDLESS TV CONVERTER MODEL DRX-3-105

CALL FOR PRICES



- Receive up to 60 TV channels • Remote TV Control • Attach to any age or model TV in minutes. • No tools required. • On/Off button. • Channel selection. • Channel Stepping. • Fine Tuning.

JERROLD JRX TV REMOTE CONVERTER MODEL JRX-3C105 (SWITCH)

OUR PRICE \$79.95 each

Consists of two units - a receiver and transmitter. 20 ft. connecting cord is detachable at one end to help you position the unit. May be attached to any age or model TV in minutes. No tools required.

- Receive up to 36 channels. • Remote TV control.



BP VIDEO CONTROL CENTER MODEL V-4802

OUR PRICE \$19.95 each

Provides remote control access of all Video, TV or Cable, inputs to TV or Big Screen TV from one location by flipping switch.

- One output, your TV set or Big Screen TV
- Four inputs • Completely passive, i.e. no AC power required to operate • Auxiliary input and output provides added flexibility.



BP UHF CONVERTER FOR TV AND VTR

MODEL V-5736
OUR PRICE \$24.95 each
5 FOR \$100.00

Use your VCR to its maximum capability. Record VHF, UHF, Cable or Pay TV while watching any other mode.

- FEATURES** • 36 channels
- Allows complete programming of VTR • Super-color quality
- Watch or record any combination of selectable channels. • Receives midband, superband/Pay and all VHF channels on UHF.
- For Beta/VHS type recorders or TV set • Record and use TV's remote control.



BP IMAGE ENHANCER MODEL V-1860

Dramatically improves performance of video cameras and VCR's, (off-the-air or second generation recordings), by compensating for deterioration of detail and sharpness. Includes video distribution amplifier with two video outputs, allowing you to make two copies at once without loss in signal level.

OUR PRICE \$59.95 each



BP RF CONVERTER/MODULATOR MODEL V-1885

OUR PRICE \$39.95 each

Allows your TV to receive video and audio signals from image enhancer, guard stabilizer, video camera, computer, VCR, etc. The outputs of many video components cannot be directly hooked up to the VHF antenna terminals on your TV set. This problem is solved by using the Model V-1885 RF Converter. Converts video signal from any video component to adjustable RF signal at antenna terminals. Allows your VCR output to feed two TV sets at the same time, with virtually no signal loss.



FORDHAM
260 Motor Parkway, Hauppauge, N.Y. 11788

- Master Charge
- VISA
- COD
- Money Order
- Check

N.Y. State residents add appropriate sales tax.

COD's extra (required 25% deposit)

ADD FOR SHIPPING AND INSURANCE:	
\$250.00\$4.50
\$251.00 to 500.00 6.50
\$501.00 to 750.00 8.50
751.00 to 1000.00 12.50
over 1000.00 15.00

TOLL FREE (800) 645-9518
in N.Y. State call 800-832-1446

Only NRI Gives You This Kind of Training and Equipment.

Only NRI Gives You So Much Professional Preparation For a TV/Audio/Video Servicing Career.

Build this 25" Heath/Zenith Color TV with 112 channel tuning system, infrared remote control, advanced sound system, and in-set space phone.

Get complete, thorough instruction in the theory, servicing, and repair of TV, VCR, video disc players, audio equipment, AM/FM receivers, antenna systems, home video cameras, projection TV, and more with 65 easy-to-digest, bite-size lessons.



See servicing techniques demonstrated in close-up detail. Graphic presentations make theory and systems come alive on NRI Action Videotapes covering VCRs, disc players, and TVs.

Perform challenging state-of-the-art electronic experiments and demonstrations using your NRI Discovery Lab®.

Learn how to diagnose problems using a professional 3½-digit digital multimeter. Exclusive NRI Action Audio instructions talk you through its complete operation and use.

Learn servicing and adjustment techniques with this 6-hour, remote control videocassette recorder you get as part of your training.

Only NRI gives you so much practical training with equipment you own and keep. You learn by doing. That's the way to make it interesting, that's the way to make it enjoyable, that's the way to get the hands-on experience and know-how you need.

Hands-On Training For Real Bench Experience and Priceless Confidence

You start with experiments and demonstrations on the unique NRI Discovery Lab. You learn basic circuit wiring and soldering techniques, and then quickly move on to more advanced concepts as you come to understand electronic theory, solid-state devices, digital systems, and microprocessors. You learn by actually building and observing the operation of circuitry you'll be working with in real-life situations.

Exclusive NRI Training On Videotape

In addition to profusely illustrated lessons, you get NRI's Action Audio cassette to "talk" you through the use and operation of the professional digital multimeter you receive as part of your equipment. Even more exciting are your NRI Action Videocassettes... videotaped lessons that show you graphic presentations of electronic systems, vivid closeups of servicing techniques and professional "shortcuts" to study and replay as often as you want.

You Get TV, VCR, DMM and More Equipment To Keep

You also build your own 25" Heath/Zenith color TV, a state-of-the-art unit that includes infrared remote control, a Time Control Programmer, and the incredible Advanced Space Phone that lets you telephone from your chair. Using the videocassette recorder that's included as part of your training, you learn how to adjust, service and re-

pair these fast-selling units. Your front-loading VCR features up to 6-hour recording capacity, remote control, and programmable touch-button tuning.

The digital multimeter you receive is a truly professional instrument. You use it in the experiments throughout your course and as a key servicing tool on the job. Using the meter along with the NRI Discovery Lab, you'll learn how to measure voltage, current and resistance and how to diagnose all types of servicing problems.

Advanced Systems Demand Advanced Technicians for Service and Maintenance

The art of TV/Audio/Video servicing has taken quantum leaps into the future. Now, successful technicians must understand advanced concepts like digital control, electronic tuning, laser video discs, microprocessors, and more. NRI gives you the training you need for success... state-of-the-art concepts and practical, hands-on experience working with the kind of equipment you'll encounter on the job.

7 Decades of Teaching Electronics Skills At Home

NRI is the oldest, largest, and most successful school of its kind in the world. It has pioneered and refined the teaching techniques that make learning at home the NRI way

one of the most economical and effective methods ever conceived. You learn at your convenience as a class of one, backed by skilled NRI instructors and carefully designed lessons that take you a step at a time toward your goal. No time away from your job, no night school grind, no classroom pressures. Yet your training is thorough and complete, with a foundation of hands-on experience unequalled by any other training organization.



Send For Free Catalog Covering 12 Electronics Courses

Our 104-page catalog gives you all the details. In it, you'll find a summary description of every lesson, and photos and specifications for every item of equipment included in your course. You'll also learn about other fascinating career opportunities in the world of electronics... Microcomputers, Industrial Electronics including robotics, Communications, and more.

Mail the postage-paid card today for your free copy. See how completely and how thoroughly NRI gets you started on your tomorrow today.



NRI SCHOOL OF ELECTRONICS
McGraw-Hill Continuing Education Center
3939 Wisconsin Avenue
Washington, DC 20016

LETTERS

Address your comments to: Letters, **Radio-Electronics**,
200 Park Avenue South, New York, NY 10003

PRIVACY IN COMMUNICATIONS

Recently, I picked up a copy of **Radio-Electronics** quite by chance, and was so impressed that I subscribed the next day. Keep up the great work.

I would like to comment on the article, "Ensuring Privacy in Communications" in the "Communications Corner" department for January 1983. The writer seems to be conveying a false impression — a misunderstanding that even many amateur radio operators have: that by adding a sub-audible or dual tone signal to your transmission you can ensure privacy from the casual listener.

Tone-squelch systems do not prevent people with scanners from hearing what you say. The tone squelch simply keeps other radios (in a fleet, for example) that have a squelch-muting circuit from being bothered by any except properly encoded signals. A radio without that mute circuitry will pick up every-

thing transmitted over a given frequency, whether or not the transmission has a tone added to it. Since scanners, and the majority of monitoring radios, are not equipped with muting, the tone in no way protects the privacy of the communication. Even radios *with* such muting circuits are usually taken off mute when the microphone is picked up, enabling a listener to hear all the transmissions.

DAN PETERSON
Hemet, CA

ANTIQUE RADIOS

I enjoyed reading Mr. Richard Fitch's recent article about restoring antique radios (**Radio-Electronics**, March 1983). Having repaired many pre-war radios, and some early TV sets, I know the feeling of accomplishment that results from getting one of those treasures playing again.

I'd like to offer a hint that might make

troubleshooting an old chassis a bit easier.

When smaller tube-radios became available (and later, when television appeared on the scene), many an old model was retired while still in good working order. But alas, 40 years later, when the old unit is dusted off and plugged in, all that issues from the speaker is a thin, garbled audio strongly overridden by a loud AC hum.

Here's the problem in almost every case that I've come across: The electrolytic capacitor in the power-supply circuit has dried out. Unlike the paper/foil and mica capacitors in the set, the electrolytics *do not* have an unlimited shelf life. The liquid electrolytic can evaporate away, leaving the caps virtually ineffective.

Two things result: First, the filtering of the pulsating DC from the vacuum-tube rectifier becomes very poor. All that's left to provide a modicum of filtering is the field coil on the

GET THE SAME VIDEO TRAINING THE PEOPLE AT SONY GET.


Now you can be trained by Sony even if you aren't employed by Sony.

Because we're making our vast library of training videotapes available to you. The very tapes that teach our own engineering, service and sales personnel.

The tapes cover the products and concepts of video and its related technologies. You can learn the basics of video recording. Color systems. Digital video and electronics. Television production. And more.

Plus you can learn how to service cameras, VTR's, and other video products. As professionally as Sony does.

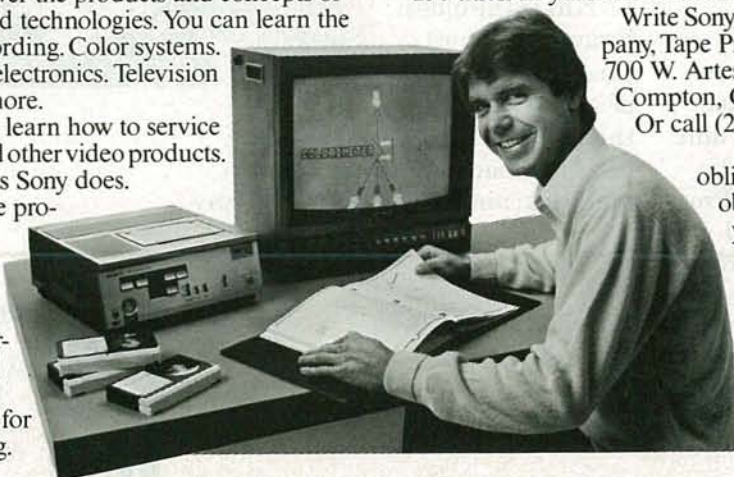The tapes are produced entirely by Sony and contain up-to-the-minute information. They communicate clearly and simply. And some of them are even programmed for interactive learning.



And learning through video can be done at your own pace, in the convenience of your home, shop or school. Reviewing is quick and easy. And the tapes are always available for reference.

Send for your catalog, which lists more than 250 titles. In your choice of 3/4" or 1/2" formats.

Write Sony Video Products Company, Tape Production Services, 700 W. Artesia Boulevard, Compton, California 90220. Or call (213) 537-4300.

Of course, there's no obligation. Except the obligation you have to yourself: to find out about the best training available in one of the country's fastest-growing, most lucrative fields.

SONY
Video Communications
Sony is a reg. trademark of Sony Corp.

CIRCLE 28 ON FREE INFORMATION CARD

wabash[®] diskettes for as low as \$1.29 each!

Now get Wabash Quality at a CE Price

For over 17 years, Wabash has been making high quality and dependable computer products. Wabash diskettes are made to provide error-free performance on your computer system because every diskette has been totally and hypercritically tested. Since you can now buy Wabash computer products directly from CE, the world's largest distributor of magnetic media, you can now get maximum savings on every order. You can even order toll-free.

New Wabash Six Year Warranty

The quality of Wabash diskettes is stressed throughout the entire manufacturing process. After coating, all Wabash diskettes go through a unique burnishing process that gives each diskette a mirror-smooth appearance. Wabash then carefully applies a lubricant that is specially formulated to increase diskette life. Then, to keep out foreign particles, a unique heat seal bonds the jacket and liner together to help prevent contamination. After 100% hypercritical testing and certification, Wabash then packages each diskette, (except bulk pack) in a super strong and tear resistant Tyvek[®] envelope. The final Wabash product is then shrink-wrapped to insure cleanliness and reduce contamination during shipment. Wabash diskettes are so very reliable that Wabash now offers a six year warranty in case of defects in materials or workmanship on all diskettes purchased directly from Communications Electronics.

New...Wabash Diskette Duplication Services

Communications Electronics has teamed up with Wabash to provide a single-source solution for the diskette duplication requirements of software developers, OEM's and distributors. All service is in-house, to give you fast, dependable service. In most cases, delivery can be completed in five days. Whether you require 100, 1,000, or 10,000 copies per week, call CE first for a no obligation price quote. For additional information, please write us on your letterhead with your requirements.

SAVE ON WABASH DISKETTES

Product Description	Part #	CE quant. 100 price per disk (\$)
8" SSSD IBM Compatible (128 B/S, 26 Sectors)	F111	1.89
8" SSSD Shugart Compatible, 32 Hard Sector	F31A	1.89
8" SSDD IBM Compatible (128 B/S, 26 Sectors)	F131	2.39
8" DSDD Soft Sector (Unformatted)	F14A	2.99
8" DSDD Soft Sector (256 B/S, 26 Sectors)	F144	2.99
8" DSDD Soft Sector (512 B/S, 15 Sectors)	F145	2.99
8" DSDD Soft Sector (1024 B/S, 8 Sectors)	F147	2.99
5 1/4" SSSD Soft Sector w/Hub Ring	M11A	1.49
5 1/4" Same as above, but bulk pack w/o envelope	M11AB	1.29
5 1/4" SSSD 10 Hard Sector w/Hub Ring	M41A	1.49
5 1/4" SSSD 16 Hard Sector w/Hub Ring	M51A	1.49
5 1/4" SSDD Soft Sector w/Hub Ring	M13A	1.79
5 1/4" Same as above, but bulk pack w/o envelope	M13AB	1.59
5 1/4" SSDD 10 Hard Sector w/Hub Ring	M43A	1.79
5 1/4" SSDD 16 Hard Sector w/Hub Ring	M53A	1.79
5 1/4" DSDD Soft Sector w/Hub Ring	M14A	2.69
5 1/4" Same as above, but bulk pack w/o envelope	M14AB	2.49
5 1/4" DSDD 10 Hard Sector w/Hub Ring	M44A	2.69
5 1/4" DSDD 16 Hard Sector w/Hub Ring	M54A	2.69
5 1/4" SSQD Soft Sector w/Hub Ring (96 TPI)	M15A	2.59
5 1/4" DSQD Soft Sector w/Hub Ring (96 TPI)	M16A	3.69
5 1/4" Tyvek Diskette Envelopes - Price per 100 Pack	TE5	12.00

SSSD = Single Sided Single Density; SSDD = Single Sided Double Density;
DSDD = Double Sided Double Density; SSQD = Single Sided Quad Density;
DSQD = Double Sided Quad Density; TPI = Tracks per inch.

Quantity Discounts Available

Wabash diskettes are packed 10 disks to a carton and 10 cartons to a case. The economy bulk pack is packaged 100 disks to a case without envelopes or labels. Please order only in increments of 100 units for quantity 100 pricing. With the exception of bulk pack, we are also willing to accommodate your smaller orders. Quantities less than 100 units are available in increments of 10 units at a 20% surcharge above our 100 unit price. **Quantity discounts** are also available.

Order 500 or more disks at the same time and deduct 1%; 1,000 or more saves you 2%; 2,000 or more saves 3%; 5,000 or more saves 4%; 10,000 or more saves 5%; 25,000 or more saves 6%; 50,000 or more saves 7%; 100,000 or more saves 8%; 500,000 or more saves 9% and 1,000,000 or more disks earns you a 10% discount off our super low quantity 100 price. Almost all Wabash diskettes are immediately available from CE. Our efficient warehouse facilities are equipped to help us get you the quality product you need, when you need it. If you need further assistance to find the flexible disk that's right for you, call the Wabash compatibility hotline. Dial toll-free 800-323-9868 and ask for your compatibility representative. In Illinois or outside the U.S. dial 312-593-6363 between 9 AM to 4 PM Central time.

Buy Wabash Diskettes with Confidence

To get the fastest delivery from CE of your Wabash computer products, we recommend you phone your order directly to our Computer Products Division and charge it to your credit card. Be sure to calculate your price using the CE prices in this ad. Written purchase orders are accepted from approved government agencies and most well rated firms at a 30% surcharge for net 30 billing. For maximum savings, your order should be prepaid. All sales are subject to availability, acceptance and verification. All sales are final. All prices are in U.S. dollars. Prices, terms and specifications are subject to change without notice. Out of stock items will be placed on backorder automatically unless CE is instructed differently. Minimum *prepaid* order is \$50.00. Minimum *purchase order* \$200.00. All shipments are F.O.B. Ann Arbor, Michigan U.S.A. No COD's please. Non-certified and foreign checks require bank clearance.

For **shipping charges** add \$8.00 per case or partial case of 100 8-inch flexible disks or \$6.00 per case or partial case of 100 5 1/4-inch mini-diskettes for U.P.S. ground shipping and handling in the continental U.S.A.

Mail orders to: Communications Electronics, Box 1002, Ann Arbor, Michigan 48106 U.S.A. If you have a Visa or Master Card, you may call and place a credit card order. Order toll-free in the U.S. Dial 800-521-4414. In Canada, order toll-free by calling 800-265-4828. If you are outside the U.S. or in Michigan dial 313-994-4444. Telex anytime 810-223-2422. Order your Wabash diskettes today.

Copyright ©1983 Communications Electronics™

Ad #U12483



Order Toll-Free!
800-521-4414

In Michigan 313-994-4444

wabash
error-free
diskettes

COMMUNICATIONS
ELECTRONICS™

Computer Products Division

818 Phoenix □ Box 1002 □ Ann Arbor, Michigan 48106 U.S.A.
Order TOLL-FREE 800-521-4414 or outside U.S.A. 313-994-4444

FORDHAM CUTS PRICES ON HITACHI SCOPES

CALL FOR PRICES

CALL FOR PRICES

MINI-PORTABLE DUAL TRACE



Model V-209

3-way power supply, compact, light weight package • High sensitivity 1 m V/div at 10 m Hz and fast sweep times 50 ns/div • Built-in TV sync separation circuit/TV-V & TV-H modes • Auto-focus • Comes with probes.

20 MHz Dual Trace



Model V-202F

.55" square CRT • Vertical sensitivity 5 m V/div to 5 V/div and 1 m V/div to 1 V/div with 5X amplifier • Display modes Ch1, Ch2, Dual, Add, Diff. • Comes with probes.

Model V-203F - Same as above but with Delayed Sweep.

35 MHz DUAL TRACE



Model V-352F

Vertical sensitivity 5 m V/div to 5 V/div and 1 m V/div to 1 V/div with 5X amplifier • Trigger modes Automatic, Normal, TV(+), TV(-) • Comes with probes.

Model V353F - Same as above but with Delayed Sweep.

60 MHz DUAL TRACE DELAYED SWEEP



Model V-650F

High sensitivity • 1 mV/div (10MHz) • 5 ns/div sweep rate • 3rd channel display (trigger view) • Variable trigger hold-off • Full TV triggering • Single sweep • Automatic focus correction • Comes with probes.

100 MHz QUAD TRACE DELAYED SWEEP



Model V-1050F

Large, bright 8x10 cm screen • Quad trace operation/Ch1, Ch2, A trigger and B trigger • High sensitivity 500 μ V/div (5 MHz) • Full TV triggering • Comes with probes.

FREE DVM \$80 Value



BP Model DVM-532

Full autoranging 3-1/2 digit LCD • Built-in continuity buzzer • Easy to read, 1/2" digit LCD display • Overload protection • Low battery indication.

*With purchase of an oscilloscope from this ad.

CALL FOR SPECIAL INTRODUCTORY PRICES
TOLL FREE (800) 645-9518 in N.Y. State 800-832-1446

FORDHAM

260 Motor Parkway, Hauppauge, N.Y. 11788



- Master Charge
- VISA
- COD
- Money Order
- Check

electrodynamic speaker (which does double-duty as a choke in most of the old circuits). That isn't enough to prevent a loud hum in the speaker. Second, there's usually an electrolytic capacitor used to bypass the cathode resistor in the audio-output stage. When that goes, the AC gain of the stage is reduced to a fraction of its former level.

Solution? Replace *all* the old electrolytics. The values are almost always marked clearly, and modern equivalents are readily available. Some early electrolytics are rectangular in shape, like a matchbox covered with wax; others are enclosed in metal cans attached to the chassis, so keep that in mind when hunting for them in your old set. When replacing, just be sure to use capacitors of equal or higher voltage, and watch out for polarity. The exact capacitance value is usually not critical, and deviations of 25 or even 50 percent will often work satisfactorily.

So if you have an old set with those symptoms, try my suggestions first; they may save you a lot of time and trouble.

DAVID B. WARD
Madison, NJ

ON NIKOLA TESLA

I would like to thank you for publishing my letter to the Editor in your November 1982 issue of *Radio-Electronics*. I believe that we owed that tribute to Nikola Tesla for his many accomplishments and few rewards. I am also sure that your readers have appreciated it. It is a great credit to your magazine to be so responsive to your readers.

May I now point to a slight discrepancy between my letter and the published version, which, I am afraid, may cause confusion among the experts. My letter said: "Of course, the General Electric Company, which originally followed Edison and the DC approach, abandoned it later and followed Tesla's AC direction to grow into the giant of today." The published version read: "That company had followed Edison and the DC approach, at first; later, it turned to follow Tesla's AC direction."

The substitution of "that company" for "the General Electric Company" unfortunately changes the meaning completely, since from the context, "that company" refers to Westinghouse Electric.

I would appreciate it very much if you will once again spare me some of your valuable space and publish my correction.

Once again, my thanks for publishing the tribute to Nikola Tesla, the inventor *extraordinaire*.

SLOBODAN ĆUK, PH.D.
Assistant Professor of Engineering,
California Institute of Technology

Our apologies for the transcription error through which the proper antecedent to the phrase "that company" was omitted. Editor

VIDEO TRANSMISSION

Just a note on the letter that appeared in the January 1983 *Radio-Electronics* by Mr. Peter K. Onnigan about video transmission via FM radio stations.

By his statements and incomplete reasoning, Mr. Onnigan would have us believe that high-resolution video can't be transmitted over 10-kHz telephone lines or via 3-kHz bandwidth radio-communications links. Well, maybe not *moving* pictures, but ...

RONALD S. MOODY
Bremen, GA

R-E

Not Just Another Pretty Breadboard.



So you thought Global Specialties was *just* the leading manufacturer of Solderless Breadboarding Systems? Look again. Over the past 10 years Global's developed more than 40 bench-crafted quality test and design instruments . . . Just for you.

Take your pick . . . We offer Capacitance Meters, benchtop and portable, and an array of complementary instruments to meet your specific needs. We've got 8 Frequency Counters to choose from, starting with our inexpensive MAX-50 and MAX-100 and capped with our recently-introduced 6002, 1 GHz model. Our Universal Counter-Timer family includes the new, widely-acclaimed, handheld 5000 Counter-Timer.

We also make logic probes and pulsers with frequency and pulse width ranges to suit any

application or budget. Global's popular Function and Pulse Generators are designed with the same quality as our NBS-certified Frequency Standard. And a broad range of accessories, hardware and cases round out the Global product line.

Of course, we still manufacture the largest selection of Breadboards and prototyping equipment anywhere . . . Simple Quick Test elements with our patented interlocking system . . . Experimentor Modules which combine sockets and bus strips in popular arrays . . . prototyping systems which provide uncomplicated translation from design to finished product . . . Mounted solderless assemblies, including Global's PB-105 Superboard, 50% larger than any other, and our powered proto-boards offering a wide

selection of power options.

You depend on us for the best in breadboards . . . Depend on us for the best in test and design instruments. Your pocket won't take a beating either. Global provides the specifications and features you require *now* . . . at prices you can afford *today*.

Remember . . . We're not just another pretty breadboard. If you need something for Test or Design, we've probably got it. So give us a call Toll-Free . . . TODAY.



GLOBAL SPECIALTIES CORPORATION

70 Fulton Terr., New Haven, CT 06509
(203) 624-3103 TWX 710-465-1227

OTHER OFFICES:


San Francisco (415) 648-0611, TWX 910-372-7992,
Europe: Phone Saffron-Walder 0799-21682,
TLX 851-817477

Call toll free for details 1-800-243-6077 during business hours

CIRCLE 31 ON FREE INFORMATION CARD

EQUIPMENT REPORTS

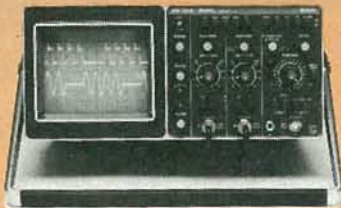Philips Model PM 3215 50-MHz Dual-Trace Oscilloscope



CIRCLE 103 ON FREE INFORMATION CARD

Philips		PM 3215									
OVERALL PRICE											
EASE OF USE											
INSTRUCTION MANUAL											
PRICE/VALUE											
		1	2	3	4	5	6	7	8	9	10
		Poor			Fair			Good			Excellent

YOU CANNOT BE INVOLVED WITH electronics—by profession or even as a hobbyist—without eventually needing an

oscilloscope. And today's advancing technology often demands an oscilloscope with a wide bandwidth. If you have

found that to be true in your experience, and if you are contemplating an oscilloscope purchase, one unit you should not overlook is the *PM 3215* from Philips Test and Measuring Instruments, Inc. (85 McKee Drive, Mahwah, NJ 07430).

General overview

The *PM 3215* is a dual-channel scope with a 50-MHz bandwidth. It is relatively lightweight (less than 18 pounds) and measures 17.5 × 11.8 × 5.4 inches. (Those measurements do not include the front protective cover, the controls, or the handle.) The handle, with its nine locking positions, doubles as a stand for the scope.

The inclusion of a battery input (22–27 volts DC at 1.1 amp maximum) along *continued on page 28*

New Simpson Test Instruments for the 80's FAST PROFITABLE BENCH OR FIELD SERVICING

Three new DMMs offer high accuracy, beeper, diode test, transient protection and double fusing.

The **470TM** is our new low-cost full-function hand-held (calculator style) DMM with 25 ranges.

The **467E** hand portable DMM has peak hold, true RMS and 26 ranges.



The **360 Series 3** digital VOM (with world famous 260[®] styling) has 28 ranges, bright LED display, rechargeable batteries.

Our **Model 165** Handi-VOM is a pocket-size unit with 22 ranges including dB, large 3 1/4" meter, convenient one-knob selector switch.

The **Deluxe Test Lead Kit** (Catalog No. 00818) has everything you need for fast, convenient test setups, measurements and trouble-shooting.

Order Them from
Your Local
Electrical/
Electronics
Distributor

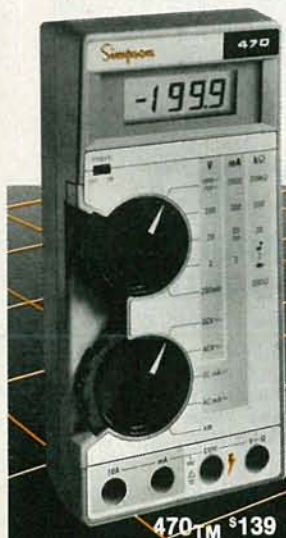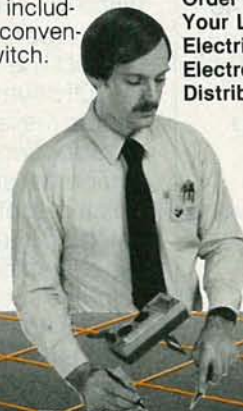Simpson
INSTRUMENTS THAT STAY ACCURATE
SIMPSON ELECTRIC COMPANY
A Katy Industries, Inc. Subsidiary
853 Dundee Avenue, Elgin, IL 60120
(312) 697-2260 • Cable SIMELCO • Telex 72-2416



470TM \$139



467E \$225



Deluxe Test Lead Kit \$57



165 Handi-VOM \$78



360 Series 3 \$275

CIRCLE 91 ON FREE INFORMATION CARD



The ELECTRONICS BOOK CLUB

18 years experience

Hundreds of time- and money-saving ideas for hobbyists, experimenters and technicians!



Select 6 fact-filled volumes for only \$2.95 (total value up to \$115.70)



1536
List \$13.95



1406
List \$17.95



1467
List \$16.95



1000
List \$13.95



1211
List \$14.95



1468
List \$18.95



1277
List \$19.95



1497
List \$15.95



1451
List \$18.95




1199
List \$18.95



1062
List \$14.95



1474
List \$15.95

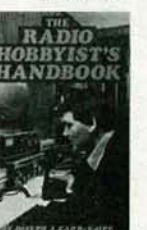

1346
List \$19.95



1465
List \$15.95




1332
List \$16.95



1436
List \$16.95



1473
List \$18.95

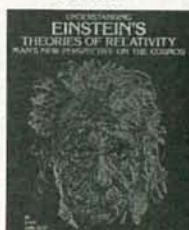

1505
List \$18.95



1296
List \$18.95



1113
List \$11.95



1276
List \$15.95



1486
List \$17.95



1160
List \$13.95



1435
List \$15.95

7 very good reasons to try Electronics Book Club Blue Ridge Summit, PA 17214

- **Reduced Member Prices.** Save 20% to 75% on books sure to increase your know-how
- **Satisfaction Guaranteed.** All books returnable within 10 days without obligation
- **Club News Bulletins.** All about current selections—mains, alternates, extras—plus bonus offers. Comes 13 times a year with dozens of up-to-the-minute titles you can pick from
- **"Automatic Order."** Do nothing, and the Main selection will be shipped automatically! But... if you want an Alternate Selection—or no books at all—we'll follow the instructions you give on the reply form provided with every News Bulletin
- **Continuing Benefits.** Get a Dividend Certificate with every book purchased after fulfilling membership obligation, and qualify for discounts on many other volumes
- **Bonus Specials.** Take advantage of sales, events, and added-value promotions
- **Exceptional Quality.** All books are first-rate publisher's editions, filled with useful, up-to-the-minute information



ELECTRONICS BOOK CLUB Blue Ridge Summit, PA 17214

Please accept my membership in Electronics Book Club and send the 6 volumes circled below, billing me \$2.95 plus shipping and handling charges. If not satisfied, I may return the books within ten days without obligation and have my membership cancelled. I agree to purchase 4 or more books at reduced Club prices (plus shipping/handling) during the next 12 months, and may resign any time thereafter.

1000	1062	1113	1160	1199	1211
1276	1277	1296	1332	1346	1406
1435	1436	1451	1465	1467	1468
1473	1474	1486	1497	1505	1536

Name _____ Phone _____

Address _____

City _____

State _____ Zip _____

Valid for new members only. (Orders outside U.S. or Canada must be prepaid in International Money Orders in U.S. dollars. Canada must remit in U.S. dollars.) This order subject to acceptance by Electronics Book Club. RE-783



QUALITY KITS

\$2.00 REBATE!

Buy one or more of Jim-Pak's electronic kits and receive a \$2.00 factory rebate for each kit you purchase from one of the authorized Jim-Pak distributors shown on the opposite page. Just remit the coupon below along with your ORIGINAL sales slip and receive a \$2.00 rebate direct from the Jim-Pak factory for each kit purchased.

5VDC - 1 Amp REGULATED POWER SUPPLY KIT



120VAC input. Includes components, hardware and instructions.

JE200


±5 to ±15VDC ADJUSTABLE REGULATED POWER SUPPLY KIT



120VAC input. Output per supply 5VDC @ 500mA, 10VDC @ 750mA, 12VDC @ 500mA, 15VDC @ 175mA. LED "On" indicator.

JE215

DIGITAL THERMOMETER



JE300

Dual sensors - switch controls for indoor/outdoor or dual monitoring. Extends to 500'. Range: -40°F to 199°F. Calibrate for Fahrenheit/Celsius. .8" ht. display. AC adapter included.


6-DIGIT CLOCK KIT (.300" Ht.)



JE701

115VAC - 12 to 24 hour operation. Includes components, case and wall transformer. Viewable to 20 feet. 6 1/2" x 3 3/8".

SOLAR CELL PANEL KIT

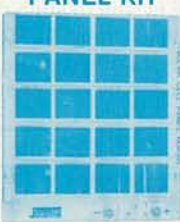

JE305

Output: 10VDC to 100mA in series. 5VDC to 200mA in parallel. Contains 20 solar cells. Power line taps select from 0.5VDC to 10VDC in 0.5VDC increments. Provides currents for small battery power applications.


JUMBO 6-DIGIT CLOCK KIT (.800" Ht.)



JE747

115VAC, 12 to 24 hour. Viewable to 30 feet. Includes components, case and wall transformer. 6 1/2" x 3 3/8".


FUNCTION GENERATOR KIT



JE2206B

Three waveforms: sine, triangle, square. Range from 1Hz to 100kHz. Output amplitude from 0 volts to over 6 volts. Uses a 12V or a ±6V split supply.

ASCII ENCODED KEYBOARD KIT



JE610

60 Keys generate the 128 characters, upper and lower case ASCII set. Fully buffered. Two user-definable keys provided for customer applications. Caps lock for upper case only alpha characters. Utilizes a 2376 (40-pin) encoder read only memory chip. Outputs directly compatible with TTL/DTL or MOS logic arrays. Parallel output. Easy interfacing with a 16-pin DIP or 18-pin edge connector. Interfaces into most computer systems. Requires +5V @ 150mA and -12V @ 10mA. Size: 1 1/2" H x 6 1/2" W x 13 1/4" L.

• REBATE COUPON • REBATE COUPON • REBATE COUPON • REBATE COUPON • REBATE COUPON • REBATE COUPON • R

Please send my refund for \$ _____ for _____ kits. I have enclosed my ORIGINAL sales slip.

NOT VALID WITHOUT ORIGINAL SALES RECEIPT.

EXPIRES JULY 31, 1983

ONE REBATE PER CUSTOMER

Send directly to JIM-PAK, 1355 Shoreway Road, Belmont, California 94002

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

PHONE () _____

• REBATE COUPON • REBATE COUPON • REBATE COUPON • REBATE COUPON • REBATE COUPON • REBATE COUPON •

See your local JIM-PAK distributor listed on the opposite page.

EQUIPMENT REPORTS

continued from page 24

with its light weight and compactness, protective panel cover, and handle, indicates that Philips wanted the *PM 3215* to be at home either on a laboratory bench or in the field.

The CRT display has an internal graticule (an 8- × 10-cm grid) with continuously variable illumination. Those features reduce parallax error and help to make reading the scope non-fatiguing, especially if you use the scope for long periods of time.

When the scope is first turned on, the blue trace appears within 10 seconds, and the unit is ready for immediate use, although a 30-minute warmup time is suggested in the manual. The trace comes on about 4/10 of a division below where it was when the unit was turned off. However, after the 30-minute warmup period, it has returned to its previous position and there is negligible drift in the trace thereafter.

The unit comes supplied with two passive probes with an attenuation factor of 10 (and a compensation range from 14 to 40 pF—full probe-compensation instructions are included in the manuals). A handy zero- or ground-check button is included on the probe shell. The probes

also come with a variety of accessories. They include a spring-loaded test clip, extra probe tips, and special caps for the probe tips that help to make measurements on dual in-line packages or in densely wired circuits easier. An adapter for making measurements of wire-wrapped circuits is also included with the probes.

A look at the controls

The front panel is well organized and laid out in a neat, compact manner with the controls appearing where you would want—and expect—they to be. The controls can be grouped into three main sections. The first section includes the power and CRT controls. The second section contains the vertical-channel controls, and the third contains the triggering and horizontal-channel controls. We'll look at each section in more detail, starting with the first, which is located to the right of the CRT screen.

The ILLUM control acts as the power switch as well as the continuously variable graticule-illumination control. An LED immediately above that control indicates POWER ON. Other controls in this section include those for trace intensity and focus. A screwdriver-adjustable TRACE ROTATION control is included to allow you to align the trace with the horizontal graticule lines. Also included in this section is an output terminal, labeled CAL, which is the source of a 1.2-volt

squarewave having a frequency of about 2 kHz. That can be used for vertical-channel calibration or when compensating probes.

The second section includes two columns of controls for the "A" and "B" vertical channels. They include BNC input-jacks, above each of which are two pushbuttons—one grounds the input and the other selects AC or DC input-coupling. Above each set of pushbuttons is a AMPL/DIV which consists of two concentric knobs. The outer knob—with 12 click-stop positions from 2 mV/div to 10 V/div in a 1-2-5 sequence—selects the vertical-channel multiplier. The inner knob has a click-stop CAL position and can be used to continuously vary the vertical-channel scale multiplier. A POSITION control is located above each AMPL/DIV knob allows you to vary the vertical position of the display.

Centered above each of the two columns of controls for the "A" and "B" vertical channels is a 5-position pushbutton switch that is used to select the vertical-display mode. Your choices include looking at signals on channel "A" only or channel "B" only (positions A and B respectively), or looking at both (ALT or CHOP—chosen depending on the sweep rate that is in use). You can also look at the sum of the signals at the "A" and "B" inputs or, by pulling out the channel-B POSITION control, you can in-

THIS CATALOG IS YOUR KEY TO INCREASED EFFICIENCY AND PRODUCTIVITY. AND BECAUSE IT'S FREE, YOU'VE ALREADY STARTED TO REDUCE COSTS!

This is our current catalog... The Wire Handlers. It's filled with wire handling tools designed and engineered to make your life easier. The tools are unique... unique in design, and unique in the way they perform.

You may know about our Wire Strippers...but we also offer the finest power electric desoldering tools, termination kits, wire and cable cutters, slitters, crimpers, and low cost voltage testers, available. Ask for your copy of The Wire Handlers today! Just send your business card.



 **PALADIN CORPORATION**

Suite 106, 31332 Via Colinas, Westlake Village, CA 91362
Call [213] 991-4970.

CIRCLE 93 ON FREE INFORMATION CARD



HEADACHE SORTING HEX KEYS?


Cure it
With Bondhex™
Key Cases!

- Compact
- Self locking/quick release
- Easy to carry
- Oil resistant plastic
- Easy size identification
- Color coded yellow-inch red-metric



Cases available with:
Balldriver™ or Chamfered L-Wrenches

WRITE OR PHONE FOR FREE INFORMATION

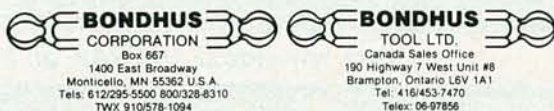

CIRCLE 17 ON FREE INFORMATION CARD

The Bearcat® 100. The first no crystal hand-held scanner.



Now you can have the one scanner you've always wanted—a no crystal, fully synthesized hand-held scanner. The incredible, Bearcat 100.

Push button programming.

The Bearcat 100 works just like the full size, no crystal Bearcat Scanners. Push button controls tune in all police calls, fire calls, weather warnings, and emergency information broadcasts, the split second they happen. Automatically.

All the features you want.

16 channels for storing frequencies. 8 band cover-

age—including high, low, UHF and "T" public service bands; both the 70 cm and 2 meter amateur bands; plus, for the first time ever, both the military and federal government land mobile bands. Both automatic and manual search, lockout, scan delay, direct channel access. Even a liquid crystal display. Flexible antenna, ear-phone, AC adapter/battery charger and carry case are included.

Your Bearcat Dealer wants to hand you an earful.

See your Bearcat Dealer now for a demonstration of the amazing Bearcat 100. Get complete information about the world's first hand-held, no crystal scanner.

SCAN's 30,000 members know what others miss! Insider news. Frequency info. Tech tips. Awards. SCAN Magazine ... and more! Send \$10 for 1-year membership to the Scanner Association of North America, 111 East Wacker Drive, Chicago, IL 60601.

BEARCAT® SCANNERS

Electra Electra Company
Division of Masco Corp. of Indiana
300 East County Line Road
Cumberland, Indiana 46229

© 1983 Masco Corp. of Indiana.

To find out more about where to buy the Bearcat 100 or other Bearcat Scanners, call 800-S-C-A-N-N-E-R toll free.

CIRCLE 5 ON FREE INFORMATION CARD

vert the signal on channel-B and can thus look at the difference of the two signals.

The third control-grouping contains a BNC input-jack for the trigger source or for the source of horizontal deflection. The source is selected by a 4-position pushbutton switch (A, B, EXT, or EXT ÷ 10). Above the pushbuttons is the TIME/DIV control, which, like the AMPL/DIV control, consists of two knobs. The outer knob adjusts the sweep rate from 0.1 μs/div to 0.5 sec/div in a 1-2-5 sequence. As before, the center control allows you to continuously vary the sweep rate. The DEFLECT position of the TIME/DIV control allows you to use the scope in the horizontal-deflection mode. The horizontal deflection can be increased by a factor of ten by pulling out the horizontal channel's POSITION control.

Along the top of the third control-grouping is a 5-position pushbutton switch that selects the trigger mode and the polarity of the trigger. A LEVEL control lets you vary the level of the waveform on which the scope will trigger.

Other features

Located on the back panel is a BNC input for Z-axis (intensity) modulation. That allows you to feed a periodic signal to the control grid of the CRT, which will brighten or dim the trace and give a third, Z, dimension. Periodically brightened spots can be used as markers to time-

calibrate the main waveform. A signal that is applied to the external Z-axis input can also be used to cut off the CRT at selected parts of the trace (much like the retrace blanking signal that is fed to the Z amplifier).

The PM 3215 is very well documented. There are three manuals supplied—an operation manual, a service manual, and a manual for the attenuator probes. All of the manuals are very well written. The operating manual is 87 pages long and is written in three languages (about 25 pages for each). The operating manual includes a brief check-out procedure that is especially useful.

The service manual (written entirely in English) is over 100 pages long. It is comprehensive and includes full schematics, circuit descriptions, corrective-maintenance procedures, printed-circuit board layouts, parts lists, and more. In short, the manuals give you all the information that you need to operate and service the scope. However, if you do not wish to make your own repairs or adjustments, there is also a list of worldwide sales- and service-centers.

All in all, the PM 3215 is a high-quality 50-MHz dual-trace scope that would be a welcome addition to just about any benchtop. The suggested \$1195 list price is just about what you would expect to pay for such a professional piece of test equipment. **R-E**

Vector P184-7 Slit-N-Wrap Tool



CIRCLE 104 ON FREE INFORMATION CARD

Vector	P184-7										
OVERALL PRICE											
EASE OF USE											
INSTRUCTION MANUAL											
PRICE/VALUE											
	1	2	3	4	5	6	7	8	9	10	
	Poor			Fair				Good			Excellent

TWO MOTORIZED WIRE-WRAPPING TOOLS, the P184-7 (shown in photo above) and P180-7 Slit-N-Wrap tools from Vector (12460 Gladstone Avenue, P.O. Box 4336, Sylmar, CA 91342) represent a logical extension of their line of convenient and effective wire-wrapping tools. Of course, those two models make the same reliable connections as Vector's

FIRST QUALITY COMPONENTS - NOT MAIL ORDER "SECONDS"

Send for Free Catalog - over 1100 parts.

ARIES ZERO INSERTION FORCE SOCKETS -



can actuated, true zero insertion - tin plated solder tail pins - capable of being plugged into dip sockets, including wire wrap.

Stock No.	No. Pins	1-9	10-49	50
11055	24	4.98	\$4.35	\$3.90
11056	28	5.15	4.50	4.05
11057	40	6.81	5.95	5.35
11058	64	12.02	10.50	9.45

IC-KOOLERS™ from UNTRACK™ dissipate over 2 watts of heat from IC's, producing longer life and better performance. Just push IC-Kooler on - heat is collected from top and bottom of IC and dissipated. Won't shake loose!

Stock No.	No. Pins	Price
22225	14	\$.29
22226	16	.29
22227	18	.29
22228	20	.29

WILD ROVER

Touch switch capsule. Operating motion is 005" without the use of a levered arm. Extremely fast on and off with low noise. Normally open - rated 115 VAC, 1.6 amp-30 milliohm resistance - .615 radius by .160 thick.

Stock No.	Price
12098	1-9 \$1.42
	10 & Up \$1.26



DIGITAL MULTIMETER
Single rotary switch operation. Large, easy to read, 5" 3 1/2" digit display. 800 hours operating life with single 9v battery. Seven functions - (DC Volts, DC Amps, Ohms, AC Volts, AC Amps, Diode and Resistor Junction, Audible Continuity Check).

Stock No. 62503
\$79.95
Full 1 year warranty

Stock No. 62504 Carryover case with best look **\$9.95**

TI WIRE WRAP SOCKETS

Tin plated phosphor bronze contact - 3 wrap

Stock No.	No. Pins	1-99	100-499	500-999
11301	8	\$4.40	\$3.66	\$3.30
11302	14	.59	.54	.45
11303	16	.64	.58	.48
11304	18	.73	.66	.55
11305	20	.99	.90	.75
11306	22	1.12	1.02	.85
11307	24	1.25	1.14	.95
11308	28	1.52	1.38	1.15
11309	40	2.05	1.86	1.55

TI LOW PROFILE SOCKETS

Tin plated copper alloy 688 contact pins with gas tight seal.

Stock No.	No. Pins	1-24	25-99	999
11201	8	\$1.0	\$0.9	\$0.8
11202	14	.14	.13	.12
11203	16	.16	.15	.14
11204	18	.18	.17	.15
11205	20	.20	.18	.16
11206	22	.22	.20	.18
11207	24	.24	.22	.20
11208	28	.28	.26	.25
11209	40	.40	.37	.33

60/40 ROSIN CORE SOLDER

Stock No.	Dia.	Length (feet)	Weight (oz.)	Price
50075	0.62	9	1.5	\$1.16
50076	0.62	25	4	2.39
50077	0.62	50	8	4.25
50078	0.32	33	1.5	1.31
50079	0.32	88.5	4	2.47
50080	0.32	175	8	4.57

ELPAC POWER SUPPLIES - DC/DC CONVERTERS

SINTEC Stock No.	ELPAC Part No.	Input Voltage (VDC)	Output Voltage (VDC)	Output Current (mA)	Dimensions (HxWxD) in Inches	Price
13825	CB3801 3-0-7.0	12±0.6	0-25	.48x.51x3.05	\$ 7.95	
13826	CB3811 3-0-7.0	12±0.6	0-25	.48x.51x3.05	7.95	
13827	CB3802 3-0-7.0	15±0.7	0-20	.48x.51x3.05	7.95	
13828	CB3812 3-0-7.0	15±0.7	0-20	.48x.51x3.05	7.95	
13829	CB3804 3-0-7.0	28±0.7	0-10	.48x.51x3.05	7.95	
13830	CB3814 3-0-7.0	28±0.7	0-10	.48x.51x3.05	7.95	

ELPAC POWER SUPPLIES - SOLV SERIES FULLY REGULATED

SINTEC Stock No.	ELPAC Part No.	Output Voltage	Current Rating	Dimensions (HxWxD) in Inches	OVP Price
13801	SOLV15-5	5	3.0A	4-7/16x4-1/2	Fixed included \$39.95
13802	SOLV15-12	12	1.5A	4-7/16x4-1/2	Fixed included 39.95
13804	SOLV15-15	15	1.2A	4-7/16x4-1/2	Fixed included 39.95
13806	SOLV15-24	24	0.75A	4-7/16x4-1/2	Fixed included 39.95
13808	SOLV30-5	5	6.0A	5-5/8x4-7/8x3-1/8	OVP-4 59.95
13809	SOLV30-12	12	4.0A	5-5/8x4-7/8x3-1/8	OVP-4 59.95
13810	SOLV30-15	15	3.3A	5-5/8x4-7/8x3-1/8	OVP-4 59.95
13812	SOLV30-24	24	2.0A	5-5/8x4-7/8x3-1/8	OVP-4 59.95

OK MACHINE AND TOOL

IC INSERTION/EXTRACTION KIT
Includes DIP IC extractors and inserters to accommodate all ICs from 14 to 40 pins. Tools that engage conductive surfaces are CMOS safe and include grounding lugs. Stock No. 13309 **\$37.74**

SOCKET WRAP ID
DIP socket-sized plastic panels with numbered holes in pin locations. Slip onto socket before wire wrapping to identify pins. Also write on them for location, IC part number, function, etc. Simplifies initial wire wrapping, troubleshooting and repair. **\$1.82 per pack**

IC EXTRACTOR
One-piece, spring steel construction. Will extract all LSI, MSI and SSI devices with 8 to 24 pins. Stock No. 13313 **\$2.10**

Special of the Month!

HIGH PERFORMER II UHF-TV PREAMPLIFIER
Adds gain to UHF Reception
59002 Kit \$37.50
59003 Assembled Unit \$59.50
For more detailed information call for catalog

MODUTEC

Miniclamp AC Volt-Ammeter allows singling one conductor out of many without disarrangement.
Stock No. AC Amperes Price
13730 0-25A \$39.50
13731 0-50A 39.50
13732 0-100A 39.50

ACCESSORY LINE SPLITTER allows fast readings of AC power consumption of plug in equipment without separation of leads.
Stock No. 13727 **\$9.95**

POCKET SIZED BATTERY TESTER for all types of small batteries from .135v to 4.5v.
Stock No. 13733 **\$13.95**

VOLT-I-CATOR automotive diagnostic meter plugs into lighter socket and indicates battery condition and charging rates.
Stock No. 13736 **\$15.95**

AC VOLTAGE TESTER plugs into any 110v service receptacle to check line voltage over 50-150 VAC.
Stock No. 13735 **\$14.95**

VOM-MULTITESTER versatile Volt-Ohm-Milliammeter in small package.
Stock No. 13729 **\$13.95**

SINTEC co. Drawer Q Milford NJ 08848-9990



TOLL 800-526-5960
FREE in NJ (201) 996-4093

We accept VISA, MC, C.O.D., CHECK, or M.O. INCLUDE SHIPPING CHARGES - \$10.00 to \$100.00 \$100.00 to \$250.00 \$250.00 to \$500.00 over \$500.00 - \$5.00

CIRCLE 82 ON FREE INFORMATION CARD

HITACHI

NLS Non-Linear Systems

HICKOK

WESTON

DATA PRECISION

KEITHLEY

AWS A.W. SPERRY INSTRUMENTS INC.

FLUKE

PHILIPS

BK PRECISION

VIZ R&A

TRIPLETT

Simpson


LEADER

HITACHI

A 30 MHz SCOPE AT A 15 MHz PRICE

\$549⁹⁵

DUAL TRACE W/DELAY

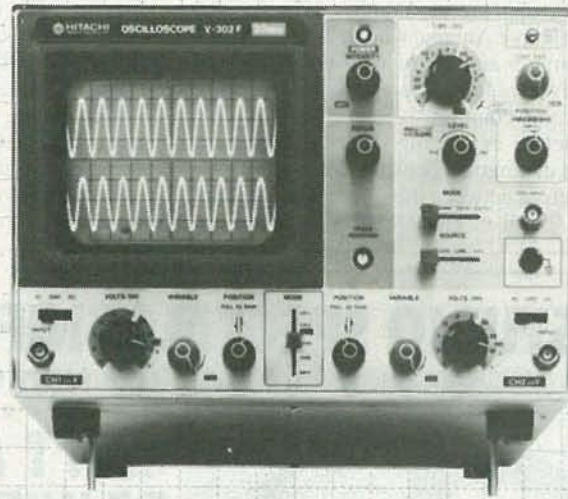

Price does not include probes.
Probes \$50. a pair when purchased with scope.
\$10. shipping within continental U.S.

BK PRECISION

INDUSTRIAL TRANSISTOR TESTER



\$199⁹⁵
WAS \$249.
MODEL 520B

- Now with HI/LO Drive
- Works in-circuit when others won't
- Identifies all three transistor leads
- Random lead connection
- Audibly and visually indicates GOOD transistor

BK PRECISION

POWER SUPPLIES



\$299⁹⁵
WAS \$359.

- Isolated 0-50VDC, continuously variable; 0-2A in four ranges
- Fully automatic shutdown, adjustable current limit
- Perfect for solid state servicing



\$319⁹⁵
WAS \$390.

- Functions as three separate supplies
- Exclusive tracking circuit
- Fixed output 5VDC, 5A
- Two 0 to 25VDC outputs at 0.5A
- Fully automatic, current-limited overload protection

All Hitachi Oscilloscopes feature 2 year parts and labor warranty.

WE CARRY A FULL LINE OF HITACHI OSCILLOSCOPES
CALL FOR OUR PRICES

BK PRECISION

FUNCTION GENERATORS



MODEL 3010 **\$179⁹⁵**
WAS \$229.

MODEL 3020 **\$319⁹⁵**
WAS \$394.

MODEL 3010

- Sine, square and triangle output
- Variable and fixed TTL outputs
- 0.1 Hz to 1MHz in six ranges
- Push button range and function selection
- Typical sine wave distortion under 0.5% from 1 Hz to 100kHz

SWEEP FUNCTION MODEL 3020

- Four instruments in one package—sweep generator, function generator, pulse generator, tone-burst generator
- Covers 0.02Hz-2MHz
- 1000:1 tuning range
- Low-distortion high-accuracy outputs

BK PRECISION

CAPACITANCE METERS



\$189⁹⁵
WAS \$238.

MODEL 830

- Automatically measures capacitance from 0.1pF to 200mF
- 0.1pF resolution
- 0.2% basic accuracy
- 3 1/2 digit LCD display



\$159⁹⁵
WAS \$192.

MODEL 820

- Resolves to 0.1pF
- 4 digit easy-to-read LED display
- Fuse protected against charged capacitors
- Overrange indication

BECKMAN DIGITAL MULTIMETERS



300 310 320
330 350 360

ALL IN STOCK
CALL FOR PRICES



TOLL FREE HOT LINE
800-223-0474

THE TEST EQUIPMENT SPECIALISTS

26 WEST 46th STREET, NEW YORK, N.Y. 10036 212-730-7030

ADVANCE ELECTRONICS

other *Slit-N-Wrap* tools but they also have some desirable features that can be especially advantageous.

With the *P184-7* and *P180-7*, there will be no more over-wrapped or under-wrapped connections. You simply dial-in the desired number of wraps, and each time the trigger is squeezed, the tool delivers that pre-set number of turns and then stops! Anyone who does more than a minimum amount of wire-wrapping will really appreciate the value of an automatic turns-counter.

Before examining those tools farther, let's distinguish between them. The only difference between them is the type of wire that they use. The *P180-7* is set up for use

with 28-gauge copper wire coated with polyurethane and nylon insulation. That is the "standard" wrapping wire, which also may be soldered without stripping. The *P184-7* uses 28-gauge silver-plated copper wire with a Tefzel (Kynar and Teflon) insulation. The Tefzel is a bit thicker (.005 inches), but it takes the best features of its component parts, resulting in a tough insulation that helps to reduce crosstalk. Other than using different types of wire, both models are alike.

Certainly, *Slit-N-Wrap* is a well-known wire-wrapping technique. Using that method, it is unnecessary to strip the insulation from the wrapping wire before it is applied to the wire-wrap post. The

tool automatically slits the insulation as the wire is wrapped but the insulation remains intact between wraps. Thus, it is possible to wire from post-to-post (daisy-chain style) without cutting the wire and starting fresh at each one or having to worry about wires shorting to each other.

The amount of tension on the wrapping wire is very important. Too little tension will result in a poor electrical and mechanical connection. Too much tension can cause wire breakage and poor mechanical stability. Vector provides explicit and easily-followed instructions for properly setting the two adjustments which determine the tension on the wire as it is fed through the tool. Once those adjustments are made, the tension need be checked only occasionally. During our tests, the tension remained constant after the initial adjustment.

Setting the number of turns to be made is only a matter of setting a small dial on the top of the machine. For 28-gauge wire, 7 turns are recommended. Available settings range from 3 to 9 and ∞ , which is a free-running mode that causes the tool to wrap continuously without counting or stopping—as long as the trigger is held. In addition, there is a small three-position toggle switch that engages or disengages the electronic counting-mechanism or disengages the trigger to prevent accidental turning when you are working on the tool.

Another convenient feature of the tools is that the free end of the first wrap need not be held—it is automatically secured. That provides a further advantage not only in convenience, but in speed as well.

So that you can keep track of the wiring in wire-wrapped circuits—it can get rather unwieldy at times—the insulated wire is available in different colors. At this time, four different wire colors are available with polyurethane-nylon insulation, while six colors are available with Tefzel insulation. The tools are designed to make changing the wire quite painless. Even changing the slitting-wrapping bit is easy, though with an anticipated life of 7,000 seven-turn wraps, the typical operator would not need to do that for some time.

During our testing of the *P184-7*, it was found to be fast and effective. Further, the pistol-like tool was balanced and shaped to reduce fatigue even when used for long periods of time.

The tools are packaged in complete kits. In addition to the wrapping tool, each contains an AC power supply, a large roll of wire, a cutting-format tool, and an adjustment tool. Also included are a weight for adjusting wire tension, a small supply of wrap posts, an Allen wrench and spare set-screws, and even a push pin that may come in handy when threading the wire. Of course, there is a thorough instruction booklet that covers not only the tool itself, but general wire-wrapping techniques.

STUDIO SPEC™ MAGNIFIER LAMP

AT \$59.95 YOU CAN'T AFFORD TO BE WITHOUT IT



This quality all-metal construction UL recognized lamp uses a standard 22 W fluorescent circline bulb (the bulb is included!). Features of this great buy include a polished, distortion-free glass magnifier (X3); a 4-way, all metal clamp bracket; a full 45" reach. The lamp is available in two colors: Ivory or chocolate brown.

You must agree, it's a steal at only \$59.95 ea. (plus shipping). If you buy 5 or more, it's only \$54.95 (plus shipping). Order No. MX114.

Shipping is only \$5.00 ea. in the continental USA.

SPECIAL BONUS! If you buy one or more of the magnifier lamps, you can get our LTS103 bench lamp for only \$10.95 ea. (plus \$2.80 ea. shipping). The LTS103 is UL listed to 100 W, utilizes a porcelain socket, and includes mounting brackets.

ORA
ELECTRONICS
A DIVISION OF ALLIANCE RESEARCH CORPORATION

"OUR SERVICE MAKES THE DIFFERENCE"

18215 Parthenia Street, Northridge, CA 91325

To Order Call Toll Free
(800) 423-5336

Calif. Toll Free
(800) 382-3663

Local
(213) 701-5848



QTY	ORDER NO.	COLOR	PRICE	SHIPPING	EXT
_____	85-MX114	_____	\$59.95*	\$5.00	_____
_____	85-LTS103	_____	10.95	2.80	_____
_____	85-MX115-FL	_____	5.95	2.00	_____
*Only \$54.95 for 5 or more				TOTAL	_____
Credit Card # _____			Exp. Date _____		
Name (Please print) _____					
Signature _____					

CIRCLE 37 ON FREE INFORMATION CARD

Altogether, the Vector P184-7 and P180-7, which sell for \$175 each, are well-designed, effective and well-package. Using either or both of these tools will provide increased efficiency and maximum assurance that the wraps are mechanically and electrically sound. The P180-7 and P184-7 are worthy additions to the *Slit-N-Wrap* line. **R-E**

System Saver Protection Device for Apple II Computers



CIRCLE 105 ON FREE INFORMATION CARD

Kensington Microware		System Saver											
OVERALL PRICE													
EASE OF USE													
INSTRUCTION MANUAL													
PRICE/VALUE													
		1	2	3	4	5	6	7	8	9	10		
		Poor		Fair		Good							Excellent

A NUMBER OF TODAY'S SMALL COMPUTERS, such as the members of the *Apple II* family, do not use forced-air cooling. Because of their relatively low component count, and the fact that most of the IC's are the low-power Schottky type, they can get by with convection cooling through ventilation slots in the computer case.

The problem with the *Apples*, though, is that their seven or eight expansion slots encourage the addition of additional boards that contain additional heat-producing components. By the time you've added a disk-controller card, extra RAM, an 80-column display board, and I/O capabilities, it starts to get pretty warm inside the case.

Heat, as you are no doubt aware, is the enemy of electronics components. It shortens their lives and can frequently cause IC's to act erratically. (So *that's* why my disks got garbaged last night!)

Kensington Microware Ltd. (300 E. 54th St., New York, NY 10022) has come up with a solution to the "baked *Apple*" problem; it's called the *System Saver*.

The solution

The *System Saver* is really a very simple device. It attaches to the left side of the computer, over the ventilation slots there, and contains a fan that pulls 15-cubic-feet-per-minute of air through the

computer, across the area where the accessory boards are located. That flow of air carries away the heat generated by the boards and keeps the computer operating comfortably.

In operation, the fan is quiet enough to become completely unobtrusive after a little while, and the air exhausted is only mildly warm to the hand. What really matters is that the computer runs cool, and can be operated for extended periods without fear of overheating something inside and causing the system to crash.

The device offers several convenience features as well. At its rear are two three-prong electrical outlets rated at eight amps (total). They allow you to plug in your monitor and printer and, by throwing the rocker switch—which contains a pilot light, by the way—at the front of the unit, to turn those two pieces of equipment, and the computer, on all at the same time.

The *System Saver* provides another benefit in that it has a surge suppressor built in; voltage spikes that may appear on the power line are clipped off at a level of 130-volts RMS (175-volts DC). That will help keep glitches out of the system. You'll appreciate that, especially if you live in an area where spikes and surges are a way of life.

And, to put the icing on the cake, there is also a "pi"-type RF filter to prevent

continued on page 38

SATELLITE TELEVISION SYSTEMS

VARIETY IS THE NORM, NOT THE EXCEPTION. Placed over the equator, by the U.S. and Canada, are 12 satellites carrying over 80 channels of TV programming. First run and classic movies, sports, specials, childrens shows and night club acts. Super stations from New York, Atlanta and Chicago. Adult films. Network broadcasts from ABC, CBS, NBC and PBS. Channels dedicated to health, medicine, science, religion, news, weather, financial information and live coverage of congress. Even video music in STEREO. There are channels dedicated to Pop/Rock and Country music. Yours with the push of a button and the twist of a knob on your TRITON satellite system.

ANTENNAS AS SMALL AS SIX FEET in diameter will deliver a picture that is quite watchable in most of the U.S. Some areas do require larger antennas to view all channels. TRITON carries complete systems to suit your individual need. Systems are available for ground or roof mounting with antennas constructed of aluminum, fiberglass or plastic. Optional equipment includes programable antenna positioners, wireless remote control and stereo. Prices start as low as \$1395.00

INSTALLATION IS SIMPLE. Most people who purchase our systems do their own installations. You need no special tools or skills. Instructions, aiming coordinates and alignment instruments are provided with each system shipped. Just in case there is any part of the procedure not

perfectly clear, we have a technical staff standing by on our TOLL FREE line to answer any questions that you may have. What a great feeling !!! Watching satellite TV from a system YOU installed.

THE TIME TO ACT IS NOW. TRITON has all systems IN STOCK for immediate delivery. Shipping is done by motor freight and UPS, depending on size and weight. Our shipping staff is alert and efficient, assuring you quick, complete shipments at the lowest possible cost. Many systems can be shipped to you for less than \$100.00

DEALERSHIPS ARE WELCOME. We at TRITON would be pleased to discuss dealership opportunities with the established satellite dealer as well as those who are thinking about selling satellite equipment. National advertising, fast product delivery, lead generation and technical support are only a few reasons to choose TRITON as your satellite equipment distributor.


TO ORDER your TRITON satellite system, just phone. To make purchasing quick and simple we will accept MASTERCARD and VISA on all systems and accessories. Sorry, no charge cards on dealer sales. All systems and components carry a full one year warranty.

TRITON MARKETING Corp.
679 REMSEN AVENUE
BROOKLYN, NY 11236

In NEW YORK
212 345-8000
Outside NY
800 221-6535

CIRCLE 54 ON FREE INFORMATION CARD

You gotta shop around.

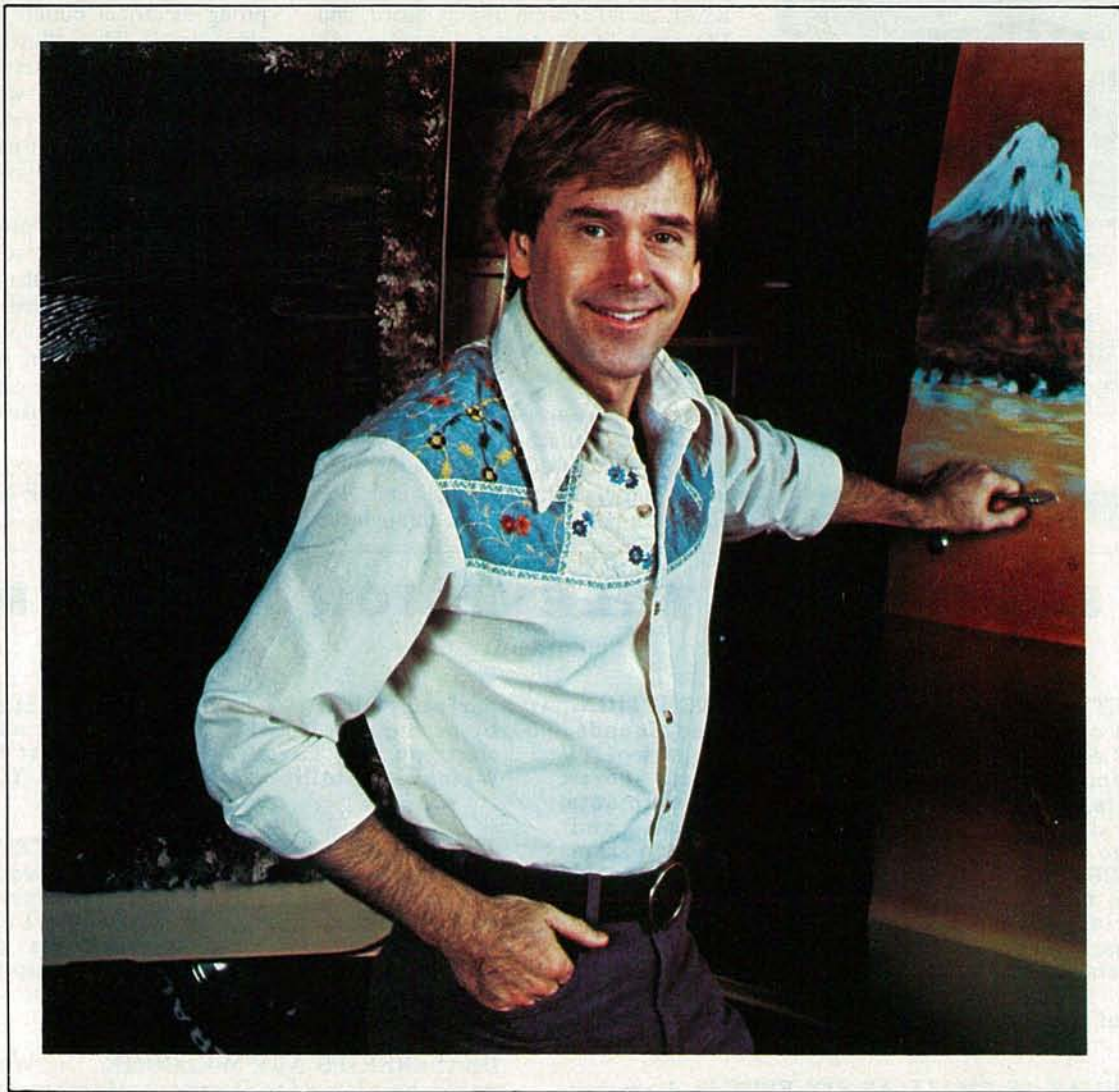

**When you do, you'll probably pick CIE.
You can't afford to settle for
less when it comes to something like
electronics training that could
affect your whole life.**

When you shop around for tires, you look for a bargain. After all, if it's the same brand, better price—why not save money?

Education's different. There's no such thing as "same brand!" No two schools are alike. And, once you've made your choice, the training you get stays with you for the rest of your life.

So, shop around for your training. Not for the bargain. For the best. Thorough, professional training to help give you pride and confidence.

* * *

If you talked to some of our graduates, chances are you'd find a lot of them shopped around for their training. They pretty much knew what was available. And they picked CIE as number one.

Why you should shop around yourself.

We hope you'll shop around. Because, frankly, CIE isn't for everyone.

There are other options for the hobbyist. If you're the ambitious type—with serious career goals in electronics—take a close look at what we've planned for you at CIE.

What you should look for first.

Part of what makes electronics so interesting is it's based on scientific discoveries—on ideas! So the first thing to look for is a program that starts with ideas and builds on them!


That's what happens with CIE's Auto-Programmed® Lessons. Each lesson takes one or two principles and helps you master them—before you start using them!

How practical is the training?

This is the next big important question. After all, your career will be built on what you can do—and on how well you do it.

Here are ways some of CIE's troubleshooting programs help you get your "hands-on" training...

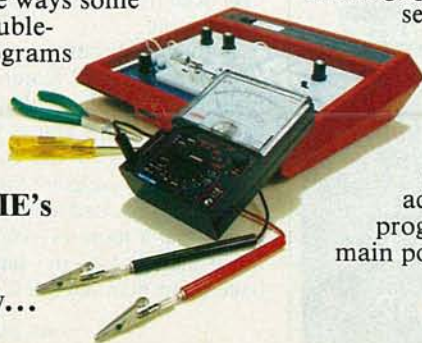With CIE's Personal Training Laboratory...



you learn and review the basics—perform dozens of experiments. Plus, you use a 3-in-1 precision Multimeter to learn testing, checking, analyzing!



When you build your own 5 MHz Triggered-Sweep, Solid-State Oscilloscope you take your first real professional step. You use it as a doctor uses an X-ray machine—to "read" waveform patterns... lock them in...study, understand and interpret them!

When you get your Digital Learning Laboratory you'll be into digital theory—essential training today for anyone



who wants to keep pace with the state of the art of electronics in the eighties. With CIE's Digital Lab, you'll be applying in dozens of fascinating ways the theory you've learned. For example, you'll compare analog and digital devices. You'll learn to make binary to decimal conversions and to work with semiconductor devices and circuits. You'll see how digital equipment is vital in today's exciting, growing fields such as security where digital theory provides the brains for space-age alarm and protective devices.

Of course, CIE offers even more advanced training programs, too. But the main point is simply this:

All this training takes effort. But you'll enjoy it. And it's a real plus for a troubleshooting career!

Do you prepare for your FCC License?

Avoid regrets later. Check this out before you enroll in any program.

More than half of CIE's courses prepare you for the government-administered FCC License exam. In continuing surveys, nearly 4 out of 5 CIE graduates who take the exam get their Licenses!

Associate Degree

Now, CIE offers an Associate in Applied Science Degree in Electronics Engineering Technology. In fact, all or most of every CIE Career Course is directly creditable towards the Associate Degree.

Shop around...but send for CIE's free school catalog first!

Mail the card. If it's gone, cut out and mail the coupon. If you prefer to write, mention the name and date of this magazine. We'll send you a copy of CIE's FREE school catalog—plus a complete package of independent home study information! For your convenience, we'll try to have a representative contact you to answer your questions. Mail the card or coupon—or write:

CIE, 1776 East 17th St.,
Cleveland, OH 44114.

CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114

YES... I'm shopping around for the right kind of career training in electronics troubleshooting — and CIE sounds well worth looking into. Please send me my FREE CIE school catalog — including details about the Associate Degree program — plus my FREE package of home study information!

Print Name _____

Address _____ Apt. _____

City _____

State _____ Zip _____

Age _____ Phone _____ (area code)

Check box for G.I. Bill information:
 Veteran Active Duty

Mail today!

RE-64

EQUIPMENT REPORTS

continued from page 33

electrical noise that may be present on the lines from getting into the computer. The filter is most effective from 600 kHz to 20 MHz, with an attenuation factor varying from 30 dB to 50 dB. Its effect is strongest at 2 MHz, which is close to the fundamental frequency of the computer's crystal clock.

Installation and use

Setting up the *System Saver* is so simple that I'll quote the instructions here in full. My comments appear in parentheses.

1. Attach *System Saver* to your *Apple II* as shown. (A lip on the unit slips over the top of the side of the computer; the unit then just rests there.)
2. Disconnect your *Apple II* power cord. You won't need it any more. (But I'd hold onto it if I were you—you never know when it will come in handy.)
3. Plug the *System Saver*'s short power cord into the back of your *Apple II*. Plug *System Saver*'s long power cord into your wall outlet. IMPORTANT: Leave your *Apple* power switch permanently on. You'll never use it again.
4. Plug your monitor and printer in *System Saver*'s rear outlets.
5. You're all set! *System Saver*'s

front-mounted switch now controls your *System Saver*, *Apple II*, monitor, and printer.

That's all there is to it. The *System Saver* is in place and ready to protect your computer from heat, power surges, and line noise and, as far as I can tell, it does a good job of it. The *System Saver* is color matched to the *Apple II*, and can also be used with the *Apple Stand*, if you use one. \$89.95 buys a lot of protection. **R-E**

CEI

The Technician's Choice

Semiconductors SORRY NO MIXED QUANTITIES

Consolidated Electronics SORRY NO MIXED QUANTITIES

YOUR COMPLETE ELECTRONIC PARTS SOURCE!

MOST ORDERS SHIPPED WITHIN 24 HOURS.
CALL OR WRITE FOR YOUR FREE CATALOGUE.
COMPARE OUR LOW PRICES AND SAVE!



CEI Consolidated Electronics, Incorporated

705 WATERLIET AVE., DAYTON, OHIO 45420. TELEX NO. 288-229
IN DAYTON, (513) 252-5662

CALL TOLL FREE TODAY! **1-800-543-3568** **1-800-762-3412**
NATIONAL WATS OHIO WATS

CIRCLE 48 ON FREE INFORMATION CARD

Soar Corporation 8050 Digital Multimeter



CIRCLE 106 ON FREE INFORMATION CARD

Soar	8050 DMM									
OVERALL PRICE	1	2	3	4	5	6	7	8	9	10
EASE OF USE	1	2	3	4	5	6	7	8	9	10
INSTRUCTION MANUAL	1	2	3	4	5	6	7	8	9	10
PRICE/VALUE	1	2	3	4	5	6	7	8	9	10
	Poor			Fair			Good			Excellent

THE NORTH AMERICAN SOAR CORPORATION (1126 Cornel Avenue, Cherry Hill, NJ 08002) is offering a digital multimeter, their model 8050, that has just about all the ranges and functions you'll ever need for almost any kind of electronic servicing.

Before we discuss its capabilities, let's look at its external features. The case is made of strong plastic that should be able to withstand some abuse. In the center of the front panel of the case is a single, recessed range-selector switch. The power switch is located at the upper left of the case—that's more convenient than having it included on the range selector. (I have more than once left my multimeter

continued on page 98

NEW PRODUCTS

For more details use the free information card inside the back cover

WAVEFORM ANALYZER, model *SC61*, is the first instrument to automate completely every conventional scope measurement for the purpose of obtaining faster, more accurate waveform analysis than is possible with conventional scopes. The unit includes a digital readout on both channels for peak-to-peak



CIRCLE 131 ON FREE INFORMATION CARD


volts, DC volts, frequency, and time.

The automatic readout eliminates the time-consuming graticule counting and calculating for conventional scope measurements. That total automatic readout is an exclusive. All measurements are made through one probe, available on both channels, eliminating any extra time-consuming lead hookup. Peak-to-peak volts, TIME and 1/TIME are also featured for any waveform section using a variable bar called "DELTA MEASUREMENTS."

For a limited time, the model *SC61* is priced at \$2995.00.—**Sencore, Inc.**, 3200 Sencore Dr., Sioux Falls, SD 57107.

MODEM ENHANCER, the *turboMUX*, is designed for owners of 212A modems, and doubles the throughput of a 1200-baud modem. It provides two types of improvements: 2400-baud full-duplex throughput, and the operation of a 2-channel statistical multiplexor.

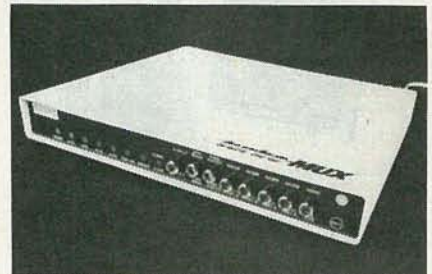The *turboMUX* has 2 channels. It attaches via standard *RS-232-C* interfaces, to the




CIRCLE 132 ON FREE INFORMATION CARD

212A modem on one end, and to the data-terminal equipment on the other. When one channel is used, it accepts data at 2400 bits per second. As a multiplexor, each channel receives data at a minimum of 1200 baud and up to 2400 baud, for a total data throughput of 2400 bits per second. The *turboMUX* unit compacts the data for transmission over dial-up lines.

To double the 212A modem's throughput,

CABLE TV Buy Direct & Save

SUPER SPECIALS

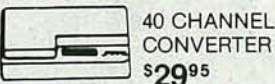

40 CHANNEL
CONVERTER
\$29⁹⁵

Advanced Solid State design and circuitry allows you to receive mid & super band channels. Restores programming to Video Recorders.



36 CHANNEL
REMOTE CONTROL
CABLE CONVERTER
\$69⁹⁵

JERROLD 400
THE ULTIMATE CABLE TV
CONVERTER



60 CHANNEL
INFRARED
REMOTE
CONTROL
\$129⁹⁵

Send \$5 for Complete Catalog

DIRECT VIDEO SALES

P.O. BOX 1329
JEFFERSONVILLE, INDIANA 47130

CALL

1-812-282-4766

CIRCLE 53 ON FREE INFORMATION CARD

NOW!

GET IBM-PC Capacity at a Fraction of IBM'S Price!

New **NETRONICS 16 Bit EXPLORER 88-PC Kit**
Starts at Just \$399.95 - Accepts All IBM Peripherals.

It's true! Now you can enjoy the power of the Intel 8088—the same microprocessor which powers the IBM-PC—and run any program compiled for the IBM-PC...starting at only \$399.95!

Take this easy, low cost way to learn 16-bit technology! Two-board system features:

1. 8088 mother board with 5-slot expansion bus; accepts any hardware designed for IBM-PC; and
2. 64K memory board, expandable to 256K; with IBM compatible RS232 communications port.

Any disk-operating system which works on the IBM will work directly on the EXPLORER 88-PC, and all programs compiled for the IBM will run on it.

The system monitor ROM included in the Starter system features a user-friendly operating system that allows easy program generation and debugging. The commands include display/modify memory...display/modify registers...input/output data to 1/0 ports...block moves...single-step trace mode...go/run with optional breakpoint and register reports...cassette load/save with file labels...plus a complete system test program that tests and reports condition of ROM, RAM, cassette interface, timer, DMA controller, interrupt controller, and the communications port. These test programs not only allow easy debugging of software but they serve as hardware and software learning tools.

The EXPLORER 88-PC STARTER KIT includes a mother board, memory/I/O board, all components needed, sockets for IC's used, one 62-pin bus connector and complete assembly/test instructions. All you need is a soldering iron, solder, a power supply, and a standard RS232 terminal (Netronics has 2 low-cost ones to choose from).
Explorer 88-PC Starter Kit...\$399.95

- + 10.00 p&i
- (wired & tested, add \$100.00)
- Extra 62-pin connectors at \$4.25 ea. + 1.00 p&i.

Use your own terminal with the EXPLORER 88-PC or, if you plan to expand it to be fully IBM compatible, we offer our IBM compatible keyboard and an IBM compatible color graphics board (only available wired and tested).

- IBM compatible keyboard...\$299.95 + 10.00 p&i.
- IBM compatible color board...\$299.95 + 10.00 p&i.
- Additional ROM required...\$35.00.

Set your own pace! Invest and learn, at the rate YOU want! Add to your EXPLORER 88-PC:

Deluxe heavy-duty steel cabinet that houses either two 5 1/4" floppies or a 5 1/4" hard disk with one floppy. This cabinet features a brush-finish front panel and a wood-grained sleeve.

- EXPLORER 88-PC Cabinet...\$199.95 + 18.00 p&i.

A heavy-duty open frame power supply with fan that can be used in your own cabinet or installed into the Netronics cabinet is available as follows:

- 10 amp power supply for system + 2 floppies...\$149.95 + 8.00 p&i.
- As above + extra power for 1 hard disk...\$169.95 + 8.00 p&i.
- IBM compatible disk controller board. Controls four 5 1/4" floppy drives (w/2 drive cable). Available wired and tested only...\$250.00 + 8.00 p&i.
- Monitors and BIOS source listings: available on either disk or hard copy at \$35.00. Please specify format and system required.
- INTEL 8086/8088 user manual...\$15.00 + 1.50 p&i.
- THE 8086 BOOK by RECTOR & ALEX...\$16.00 + 1.50 p&i.



Special IBM compatible system: with keyboard, color graphics board, floppy disk controller, 64K RAM, cabinet, standard power supply and a single 5 1/4" floppy drive... \$1899.95 + 25.00 p&i.

IBM compatible hard disks, built-in modem board, eeprom burner, print buffer system plus more will be available shortly.

Over 100 EXCLUSIVE Products and Kits—including the 'Speak Easy' universal voice synthesizer, a Diagnostic card with built-in logic probe for the IBM-PC, terminals, monitors, the ELF and EXPLORER 85 computers, and much more, are described in our upcoming catalog. It's yours FREE if you check here



"p&i" stands for "postage and insurance".

CALL TOLL FREE 1-800-243-7428 for Charge Card Orders.

In Conn., call 203-354-9375, Conn. res. add sales tax.

TO ORDER BY MAIL, CHECK BOXES FOR PRODUCTS DESIRED AND MAIL ENTIRE AD TO:



NETRONICS R&D LTD.

333 Litchfield Rd., New Milford, CT 06776

Amount enclosed OR Charge my VISA MASTERCARD
Acct. No. Exp. Date

Signature

PRINT NAME

Address City State Zip

Digital Features.



Analog Prices.

Now you can get all the measurement capability you've been looking for in a digital multimeter for the price of an analog.

Priced as low as \$59.95, the Circuitmate™ Series DMMs from Beckman offer a superior combination of standard features including:

- DC + AC Volts
- DC + AC Amps
- Resistance
- Diode Test
- 0.8% or 0.5% DC Accuracy (depending on model)
- Single Rotary Selection Switch

Depending on the model you choose—you can enjoy the added capability and convenience of 10 Amps AC + DC, audible continuity checking, hFE testing, capacitance and conductance capability.


Get your hands on a Circuitmate™ DMM today. For the dealer nearest you, write or call Beckman Instruments, Inc., Instrumentation Products, 2500 Harbor Blvd., Fullerton, CA 92634, (714) 993-8803.

BECKMAN

the *turboMUX* unit uses a data-compaction algorithm. For phone-line inconsistencies, the *turboMUX* unit provides error detection and re-transmission facilities.

The *turboMUX* is priced at \$995.00. (At \$1,275.00, the *turboMUX* unit offers a 20-channel statistical multiplexor that can operate with the 212A modem.)—**Chung Telecommunications, Inc.**, 4046 Ben Lomond Dr., Palo Alto, CA 94306.

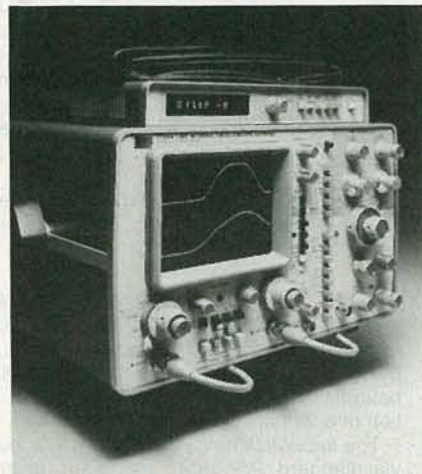TIME-INTERVAL OSCILLOSCOPE, model 1726A, offers 50-picosecond accuracy and 10-picosecond resolution; it combines counter and oscilloscope technologies and has the viewing and measuring capabilities of a 275-MHz oscilloscope, and the ease of use of a time-interval counter.




CIRCLE 133 ON FREE INFORMATION CARD

The model 1726A uses a crystal-reference time base (i.e., the counter measurement technique) in conjunction with a CRT and stable triggering circuits (i.e., the oscilloscope measurement technique). The combination allows the model 1726A to display the signal being tested as well as measure the designated interval with up to 50-picosecond accuracy. The hybrid technology provides new measurement capabilities (e.g., first-pulse measurements) with a repeatability characteristic (± 30 picoseconds) not offered by any other time-interval measurement instrument.

The model 1726A is priced at \$7675.00.—**Hewlett-Packard**, PO Box 2197, Colorado Springs, CO 80901.

DC POWER SUPPLIES, model 7400 (shown), model 7401, model 7402, and model 7403, all feature large, bright, 3-digit LED displays that indicate voltage or current. The output of each model is uniform. Ripple is held below 1 mA, line regulation is less than 5mV and 5mA, and load regulation is better than $\pm 0.3\%$ on voltage and $\pm 0.5\%$ on current. All models have constant voltage and constant current outputs. If the load current exceeds the established setting, the decimal point in the LED readout blinks and the unit stabilizes, i.e., the output current remains constant while the output voltage changes by whatever amount is necessary to accomplish that.

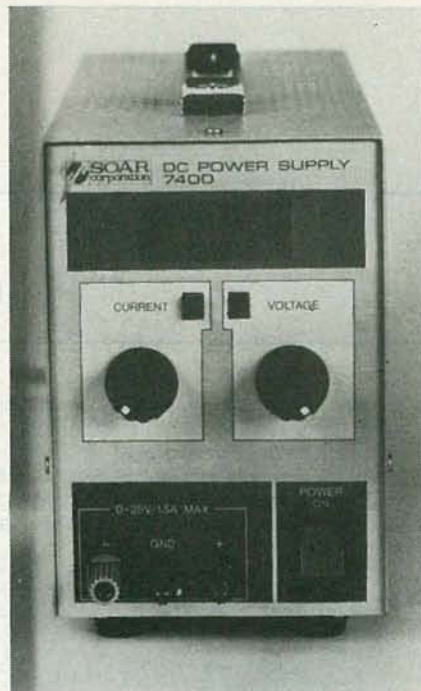
The model 7400 delivers 0 to 25V to 1.5A, and is priced at \$235.00. The model 7401 is 0 to 25V at 0 to 3A, while the model 7402 is 0 to 36V at 0 to 2A; both have the same price: \$275.00 each. The model 7403 is 0 to 36V at



CIRCLE 134 ON FREE INFORMATION CARD

0 to 3A, and is priced at \$325.00.—**North American Soar Corp.**, 1126 Cornell Ave., Cherry Hill, NJ 08002.

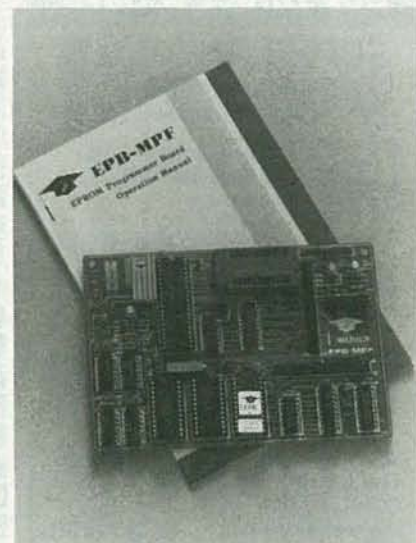BOARD, the EPROM Programming Board, model EPB-MPF allows the user to program all single-supply (+5-volts) 1K/2K/4K EPROMS. Software stored in 2K bytes of on-board ROM gives the model EPB-MPF the capability to read, write, copy, test, and verify desired program code. The software also provides for restart, delete, and insert operations using 4K bytes of on-board static RAM as a buffer memory.



CIRCLE 135 ON FREE INFORMATION CARD


The model EPB-MPF's features include: 2K bytes of ROM, 4K bytes of RAM, 24 parallel I/O lines, 24 pin zero-insertion-force socket, 9-volt 400 MA power adaptor, complete accessories to hook up the model EPB-MPF, and a detailed operations manual.

The model EPB-MPF is priced at \$169.00.—**Etronix**, 14803 N.E. 40th Street, Redmond, WA 98052. **R-E**

2300 MHz VARIABLE DOWNCONVERTER

ANTENNA KIT

\$16.95

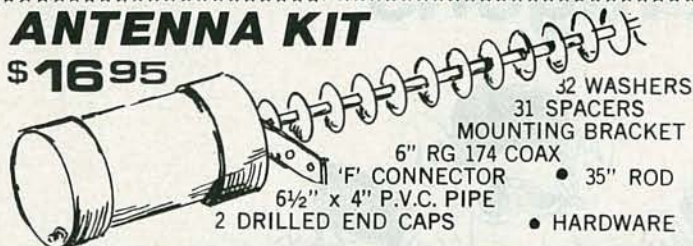


- 32 WASHERS
- 31 SPACERS
- MOUNTING BRACKET
- 6" RG 174 COAX
- 1 'F' CONNECTOR
- 6 1/2" x 4" P.V.C. PIPE
- 2 DRILLED END CAPS
- 35" ROD
- HARDWARE

PARTS

- Converter P.C. Board Plated through holes for stability.....\$4.95
- Power Supply
- P.C. Board2.95
- MRF 9012.00
- NEO21354.95
- 2835 Diodes95
- .001 Chip Caps. 10/3.95
- Choke Set of 4.....1.95
- LM 317 Regulator 1.25
- 'F' Connectors
- Chassis50
- Wall Transformer
- 12 VAC 700 MA....4.95
- 'U' Bolt95
- BALUN
- 75 to 300 ohm.....1.95
- BALUN for rabbit ears...2.95
- *RG 59/U COAX WITH CONNECTORS
- FACTORY MADE
- 100 Ft.\$17.50
- 50 Ft. 9.50
- 25 Ft. 5.75
- 3 Ft. 2.50

CONVERTER KIT

\$16.95

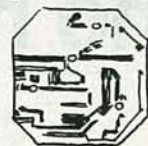

P.C. BOARD PRE-DRILLED SOLDER PLATED WITH PLATED THROUGH HOLES FOR A MORE STABLE PICTURE.


- NEW!!
 ... 2137 HOT TRANS...
 3 MRF 901 TRANSISTOR
 2 HP 2835 Diodes
 6 .001 Chip Caps.
 9 Resistors
 4 Prewound chokes
 1 Electrolytic Cap.
 1 Pre Made Probe



★ WIRED P.C. BOARD TESTED, READY TO CONNECT TO CAN WITH PROBE & CABLE CONNECTOR ATTACHED.
\$24.95

POWER SUPPLY KIT

\$16.95

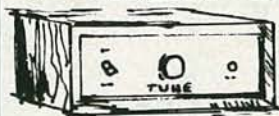

- POWER TRANSFORMER
- COURSE TUNE POT.
- FINE TUNE POT.
- 3 'F' CONNECTORS
- RESISTORS & CAPS
- LED WITH HOLDER
- TERMINAL STRIP
- P.C. BOARD
- RF CHOKE
- KNOB
- WIRE
- 2 SWITCHES
- 4 DIODES
- LM 317 REG.

WOOD GRAIN CABINET WITH SILK SCREENED front and back \$10.95 Extra

BUILT POWER SUPPLY.....\$34.95

Complete Down Converter System
 INCLUDES ANTENNA KIT
 POWER SUPPLY KIT
 CONVERTER KIT
SPECIAL \$49.95

QUANTITY DISCOUNTS
 Any Price in Adv.
 10 pcs. 12% off
 25 pcs. 18% off
 50 pcs. 25% off
 100 pcs. 30% off
 1000 pcs. 35% off
 No Mixing for Quantity Discount

We will tune converter board for \$12.50
 trouble shoot add7.50
 trouble shoot power supply..\$12.50
 plus any parts needed.

We will accept telephone orders for Visa & Mastercard
 No C.O.D. Orders
To Order Call 800-428-3500 317-291-7262
 Complete Kit Weighs 10 pounds. Please add Sufficient Postage
6254 La Pas Trail
Indianapolis, Indiana 46268

ELECTRONIC RAINBOW INC

SATELLITE TELEVISION RECEIVER

KITS



Rainbow makes a top-of-the-line Receiver affordable

The Electronic Rainbow Receiver consists of a receiver with an external down-converter that mounts at the antenna, feeds the voltage to the LNA through the coax cable. The 4GHz signal is down converted to 70 MHz and is fed through the RG59/U coax to the receiver.

Rainbow Kits are supplied with simple step by step instructions. All the circuits that you need expensive test equipment to do are pre wired and tested. All printed circuit boards have the outline of each part printed on them.

RECEIVER FEATURES

- Built in RF modulator • Detent Tuning-3.7 to 4.2 GHz • Variable Audio-5.5 to 7.5 MHz • Invert Video • Channel Scan • Voltage monitoring • Meter output • Remote Tuning

SPECIFICATIONS:

- Single Conversion Image Rejection Downconverter • Threshold 8 db CNR • IF Bandwidth 24MHz • Output IV Audio and Video • IF Frequency 70MHz • Video Bandwidth 4.5MHz • Size 3 1/2" Hx8 1/2" Dx11 1/4" W

Complete Satellite TV Receiver

KIT #1 — Contains:

- Mainboard • Tuning Board • Down-converter Board • Modulator Board
- All parts needed to complete receiver
- Down Converter built in case.
- Cabinet, attractive black brushed anodized metal with silk screened front and back for a professional look
- 70 MHz Filter is pre-wired and tested.
- Complete instruction Manual.

\$395.00

KIT #2 — Board Kit Contains:

- Main Board • Tuning Board • Down-converter board • Modulator Board
- Parts List, assembly and alignment manual
- 4GHz local oscillator and 70MHz filter is pre-wired and tested.

\$129.00

Instruction manual. Contains printed circuit board layouts, parts placement, and alignment instructions. **\$25.00**



Ask about guaranteed to play

We will accept telephone orders for Visa & Mastercard
 No C.O.D. Orders
To Order Call 800-428-3500 317-291-7262
 Complete Kit Weighs 10 pounds. Please add Sufficient Postage
6254 La Pas Trail
Indianapolis, Indiana 46268

ELECTRONIC RAINBOW INC

JULY 1983

A bench full of dragons and no relief?

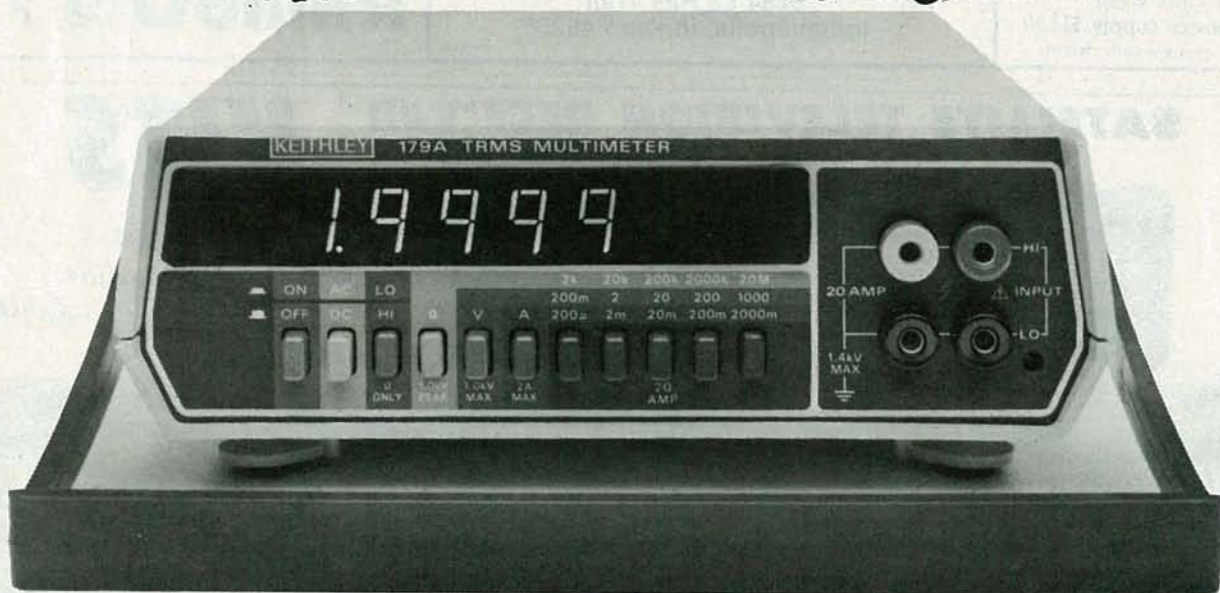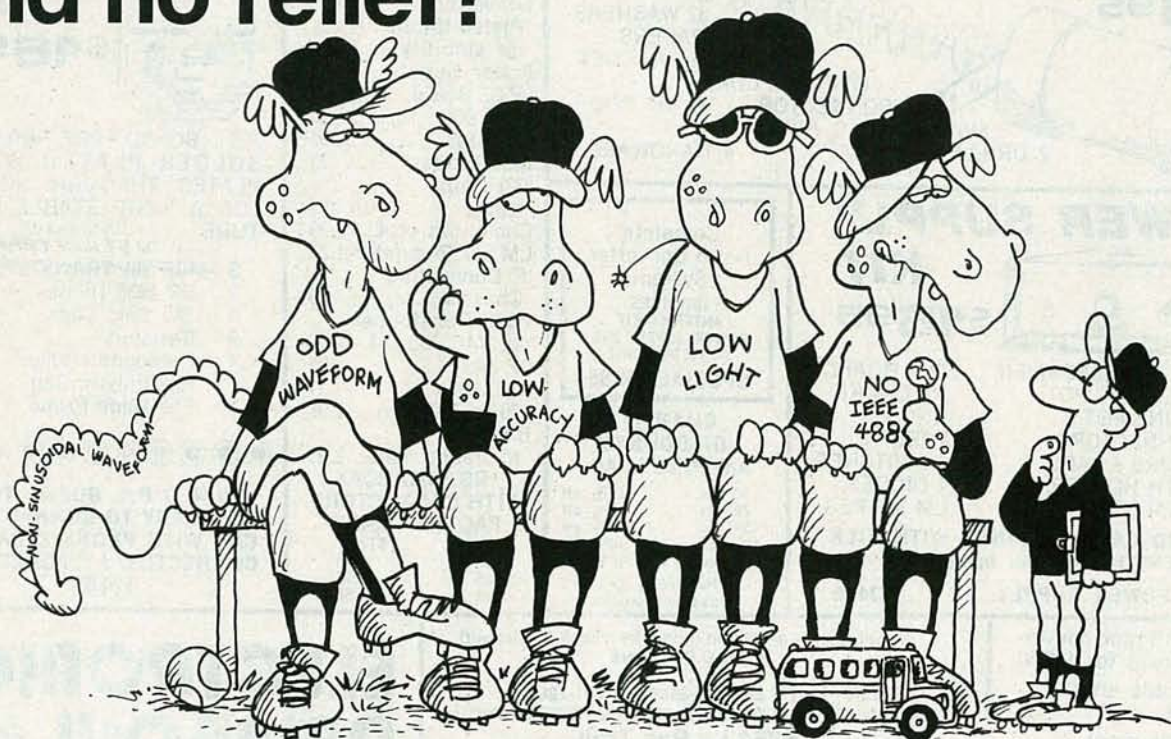

Send in old reliable Keithley 179A. It could help you save the game. Get the high-performance accuracy you need today, and field-installable IEEE-488 compatibility you'll need soon. Our oversize LED is easier to read. And non-sinusoidal waveforms won't throw you a curve with our TRMS. Here's your workhorse Portable/Bench DMM at a price that won't strike out your budget. Keithley DMMs and Thermometers. **The Dragon Slayers.**

179A Features

- Five full functions
- 10 μ V sensitivity
- 20A capability
- 0.04% DCV accuracy
- HI-LO Ω
- Field-installable battery pack
- Field-installable IEEE-488 Interface
- \$379

Price U.S.A. only.

KEITHLEY

ALL ABOUT

AUTOMOTIVE

NAVIGATION

SYSTEMS

IF YOU WATCH ANY "SCIENCE FICTION," EITHER ON TV or at the movies, you have a pretty good idea of what's Hollywood's concept of the car of the future—a sleek sports model with enough computer screens and controls to make even a Boeing 767 cockpit look like a child's toy.

But researchers are hard at work trying to separate the science from the fiction. A Sunnyvale, California inventor and a major Japanese automobile-manufacturer—in independent efforts—are bringing us closer to the day when you can equip your car with an automotive navigation-computer to guide you

Computers are finding more and more applications in the car, and soon one will even be able to tell you where you are and where you are going. Here's a look at the automobile navigation-systems of the not-too-distant future.

DANNY GOODMAN



through unfamiliar territory. We are not talking about the Mercedes-Benz system that you might have read about; that system relies on communication between your car and central traffic computers and requires roadbed cables and sensors. The navigation systems we'll be looking at consist of self-contained computers and sophisticated optics systems that will, among other things, eliminate the folded mess of roadmaps in your glove compartment.

Ready applications

If you frequently travel on business, you've probably arrived in a new or unfamiliar city armed with little knowledge about it other than the address of the company you're there to visit. Arriving at the car rental counter, you first ask for an area map that, to your dismay, features only a sketch of the main roads. Asking the agent behind the counter draws a blank as to the location of the company or the small industrial-park street on which it is located.

With a navigation system designed into every car in the agency's fleet, however, the agent could preprogram a small film pack that will display a map on the car's video screen; that map will show both your present location and the location of your appointment. When you're done with the business call, the computer could show you how to get to your next appointment, or perhaps a local restaurant or your hotel.

Preprogramming routes on a map could save time and money for trucking companies and local delivery services. The most efficient routes for each driver could be defined by the company's loading-dock computer based on the listing of deliveries to be made that day. Then each driver could plug his route module into the truck's computer and follow the directions. The same on-board computer could also be used to determine each driver's fuel efficiency and monitor how closely the driver follows the prescribed schedule. A long-haul trucking company could use the same computer-encoded film pack in an office version of the navigation computer to determine the best route for a potential customer, and then quote a price based on actual operating costs that will be incurred over the route.

The system should also prove quite helpful in your family car. Trouble with one-way streets or tricky expressway entrances would be a thing of the past as the computer could help you pinpoint those easily. And cross-country drives would be much more fun since the computer would be able to call up detailed maps of cities and towns for those impromptu side trips. Moreover, you'll never really be "lost" because the computer keeps constant track of where you are and what direction you're going: just check the screen map for your location in relation to some distant landmark.

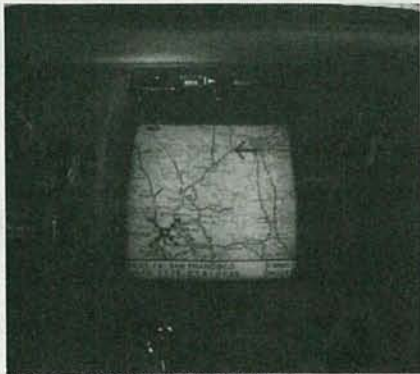


FIG. 1—A TOUCH-SENSITIVE flat-panel screen displays a full-color area map that shows your location and destination

The Navigator

Perhaps the most sophisticated system is being developed by Michael J. Alton and his company, Omni Devices, Inc. (845 Roble Dr., Sunnyvale, CA 94086) Although the system, called *The Navigator*, looks like something out of the 21st century, it is revolutionary only in the sense that it combines existing technologies—fiber optics and computers—in a new application. The result is a touch-sensitive flat-panel screen that displays a full-color area map indicating your location and destination (see Fig. 1). As you move toward the destination, your position on the map changes, and the screen zooms tighter on the map, producing increased detail over a smaller area.

Figure 2 shows how the *The Navigator* works. The light source consists of multiple bulbs, reflectors (to intensify the light in one direction), and color filters (explained later). Using many small bulbs instead of a single, high-intensity bulb helps disperse heat better. A single bulb would probably require space- and power-consuming forced-air cooling. The multiple light-sources are blended into a single projection beam using the coalescing fibers.

Next, the light passes through a condensing lens, followed by an LCD matrix that is under control of the computer. The matrix is where variable images—your location, destination, alphanumeric readouts, etc.—are added. Just as the electronically activated display-segments in an LCD watch block light from traveling to the reflective silver-gray back plate, images created and positioned by the computer in the LCD matrix of picture elements (pixels) will block light from passing any farther—thus making a shadow appear on the display screen. The prototype system uses a 32×32 pixel matrix, but the projected resolution for the production version is 128×128 pixels.

The film contained in the film cartridge plays a multiple role in the system. In addition to its obvious purpose of providing the map images that appear on the dashboard screen, the film is also contains the software that tells the computer

all about the area you're traveling through.

Map images are about the size of a 35-mm negative, and a single cartridge can hold as many as 400 separate map frames—enough to cover quite a large section of the U.S. for long-distance travel. But some frames contain solid "pages" of computer data (we'll see in a moment how the computer reads the data). The data frames hold not only "raw" data like street names and number ranges or hotel and restaurant locations, but also data the computer needs to follow a given street on the map: where the street starts, what color it is on the map, its direction of travel, length, etc. That data is important because in locating a precise address on a map, the computer essentially "walks up" the street. Text-like data (streets, hotels, etc.) would be converted to LCD matrix characters for display on the dashboard screen. Other coded data including data addresses (that is, where on the film other related data can be found) are implanted on the map's "black areas;" those areas include streets, boundaries, and frame edges. A film cartridge reportedly has space for six gigabytes of information.

To achieve the affect of zooming in on an increasingly smaller area as you approach your destination, the system uses motorized lenses in a sliding bellows-type arrangement. Each map will offer between four and eight different levels of magnification.

After it passes through the lenses, the map image passes through a beam splitter. A small portion of the light is passed straight through, via resolution-intensifying fibers, to film-reading sensors capable of handling a minimum resolution of one thousand lines per inch; those sensors are connected to the computer. The computer correlates what its sensors "see" with the previously obtained computer data to further reposition the zoom lens and variable objects on the LCD matrix. The computer "looks" for color images on the map to help it track exact locations. Instead of using expensive color sensors, the computer controls rapid sequencing of the multiple bulbs at the light source through their respective color filters. Thus, simple sensors in sync with the light-source bulbs can detect which color is being passed at any point on the map.

The majority of the map image light is reflected up through projection fibers in such a way that the screen image is divided into small pieces like a checkerboard. The fiber bundles are attached to a lens plate which in turn projects the segments onto a plastic display screen. The prototype 8-inch-square screen consists of 64 one-inch square segments. That flat-screen projection system is much more space efficient and safer in an accident than the traditional, long-necked cathode-ray tube (CRT) display.

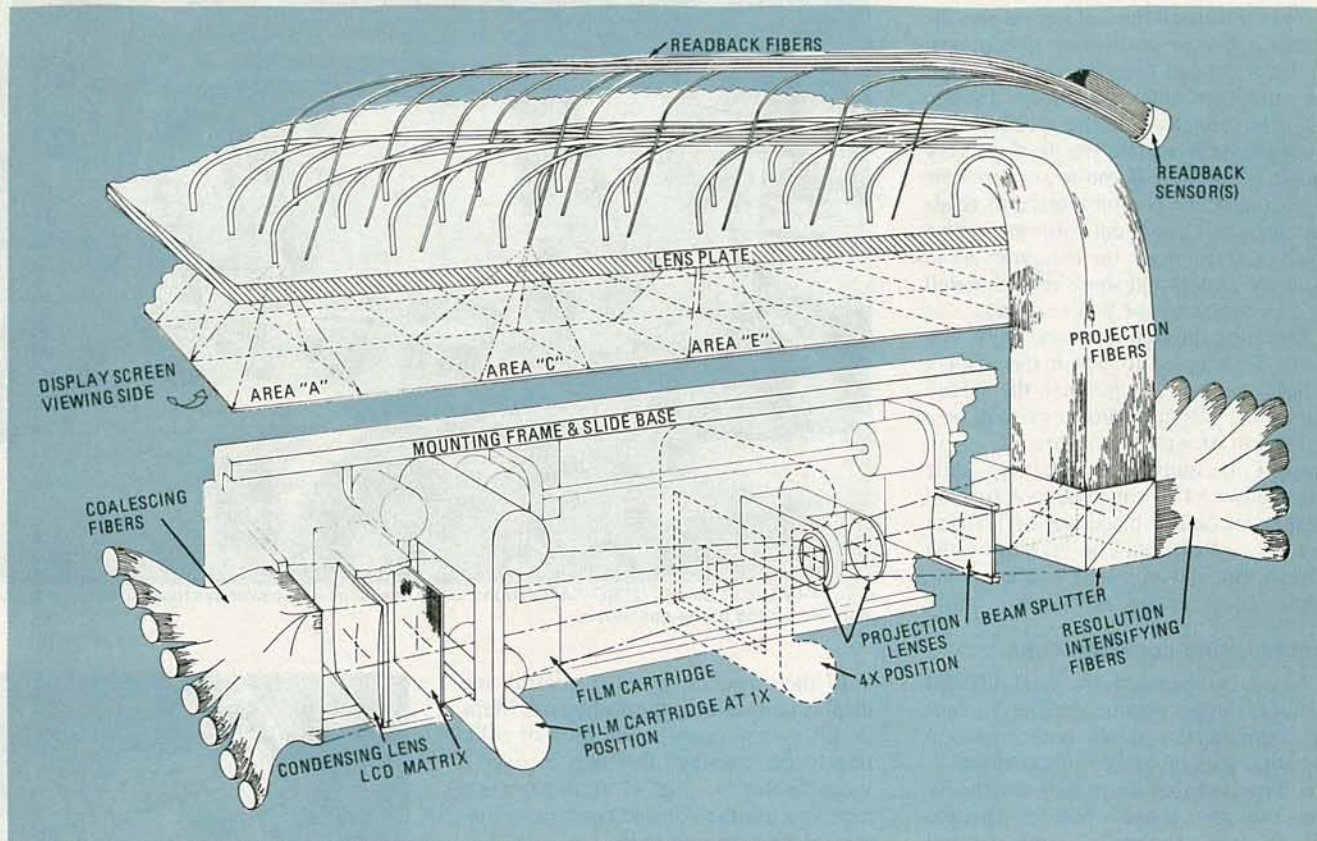


FIG. 2—INNER STRUCTURE of *The Navigator*. In the more recent version, the sliding film-cartridge has been replaced by a sliding bellows-type zoom-lens system.

Another feature of the display assembly is that readback sensors allow the screen to become touch-sensitive. When used in conjunction with screen menus (see Fig. 3), the sensors eliminate the need for a keyboard in an already crowded dashboard.

The prototype computer that controls all of that is currently designed around three Z80 8-bit microprocessors. It is anticipated that before production models become available, the computer will be based on 16-bit microprocessors such as the 8086 or 68000. In any case, multiple microprocessors will be the rule for the sake of redundancy: in case of one's failure, another can step in to keep the system operational.

Intelligent software

Most of the inner workings we've discussed will be completely invisible to the operator. Intelligent software is the key to making *The Navigator* easy to use without any computer knowledge—and perhaps without any knowledge of what *The Navigator* is.

As already mentioned, operator input will be done using screen menus. When it comes to trying to fool the computer by asking for an intersection of two streets that don't meet or an address out of the range of the actual street, the computer will pre-check the commands and alert the operator that those entries are not legitimate and perhaps that a slip of the

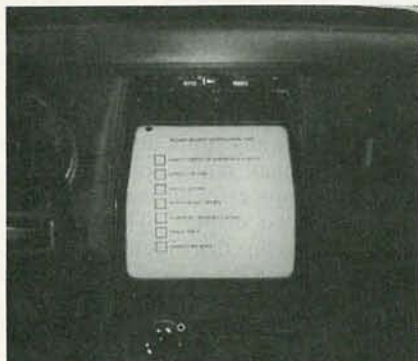


FIG. 3—WITH *THE NAVIGATOR*, no additional controls need be added to an already crowded dashboard. The touch-sensitive screen allows you to select functions, modes, and more by simply touching the display.

finger has occurred. Of course, while the computer can check map data for whether an address falls within a legitimate range, it won't be able to tell you if the location is a clothing store or an empty lot.

A typical trip

To see how intelligent the software is, let's take a hypothetical trip in a rental car that is equipped with *The Navigator* of the future.

You've just picked up the keys and an area-map cartridge from the rental counter and are ready to leave the parking stall. You start the car, plug in the film pack, and the screen lights up and displays a

menu. By placing your finger on the screen, you select the menu item that asks for your destination's address. The screen changes to a scrolling alphabetical list of street names contained on the map. A command line at the bottom of the screen—also touch operated—offers fast, slow, and stop scrolling options. Finding the street name, you stop the scroll and touch the screen beside the street name. Next the screen fills with the numbers zero through nine, which you press to input the address digits. The numbers appear at the bottom command line along with the street name, and stays there throughout the trip.

Since your present location is already preprogrammed, the computer plots the destination on the map and adjusts the amount of lens zoom required to be able to display both the present location and destination. Then the map appears on the screen. Your location is designated by a black arrow pointed in the direction that the car is facing, and the destination appears as a square.

At this point, you'll have a choice of two routing methods. With the aid of the map on the screen, you can determine your route as you would with an ordinary paper map by spotting the major roads or highways to get you across town. Or, with the help of the computer, you can trace a route on the touch-sensitive screen map with your finger. Then, if you deviate from the prescribed route, by taking a wrong turn for example, the computer will alert you to it.

Your estimated time of arrival and the distance to your destination also appear on the command line. As you head out, the computer obtains readings from a magnetic compass and the speedometer; it uses those to update the display every couple of seconds. If you're not sure how to get out of the complex maze of roads that surrounds most major airports, with a touch, you can make the computer zoom in on the airport and show enough detail for you to see where you're going.

Traveling through area roadways, you won't be tempted to watch the display rather than the road because the screen blacks out. Display on/off time will be a function of speed. After all, you shouldn't be studying a video map while racing down a freeway at 60 mph (indeed most states outlaw installing a television in a car so that it can be viewed by the driver). But if you come to a stop, the display automatically reappears.

Programming considerations

As can be imagined, the most difficult part of making a system like *The Navigator* commercially viable is the creation and programming of the film cartridges—it is expected that those will eventually cost consumers roughly \$30 for a metropolitan area. Naturally, sophisticated computers will play a large part in getting the job done.

Two techniques could be used to generate the maps. One would be to simply photograph high-detail conventional maps. The other is to generate the maps using computer graphics. The maps could then be drawn by a graphics plotter and photographed as before. New technology, however, may allow the cost-effective use of high-resolution computer-graphics-to-film conversion. Computers will also be needed to generate the data that is to be implanted in the black areas, as well as to bring together all of the map's detailed information for inclusion on the data-only frames.

Software for the on-board computer may be designed to be compatible with CP/M or other popular operating systems. The advantage to that is that a vehicle owner could preprogram a route into a cartridge on a home or portable computer the night before.

The Navigator's developer predicts that it could be offered as optional equipment on U.S. automobiles in about five years, at an estimated cost of about \$1000. It is likely that the most interest in such a device will be shown by the commercial transportation companies, which will benefit from routing and other economies offered by system.

Honda's system

In Japan, the Honda Motor Company is already offering a simpler navigation device, called the *Electro Gyro-Cator*, on a limited basis.



FIG. 4—IN THE *ELECTRO GYRO-CATOR* from Honda, the maps are on overlays that slip over a display that sits on top of the dashboard.

In their system, a small control and display unit sits atop the dashboard. Maps in this system come in the form of color translucent overlays that slip in over a video display (see Fig. 4). At the start of a trip, you use the console controls to maneuver a screen cursor (a "+" symbol) to the place on the map that corresponds to your position and the direction you're facing.

Then, as your travel, a trip sensor (a magnetic detection system) measures the frequency of tire rotation. At the same time, a directional sensor (shown in Fig. 5) that contains a self-calibrating gyroscope detects any turns off the original course. A small navigational computer (see Fig. 6) processes the data and generates the video display. The computer traces a video line that highlights the path you've taken on the map overlay. Therefore, you'll have a display of where you are on the map and how you got there. If traffic is at a standstill, you can check the detailed map overlay for an alternate route. As with *The Navigator*, the *Electro Gyro-Cator's* 5- x 6-inch display stays off until the car comes to a stop. A passenger, however, can keep the display on at all times if so desired.

Overlays are produced in varying

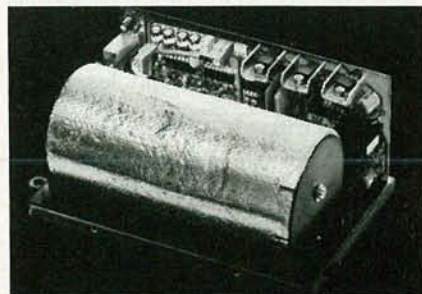


FIG. 5—THE DIRECTIONAL SENSOR contains a self-calibrating gyroscope. Its purpose is to advise the computer of any changes in direction.

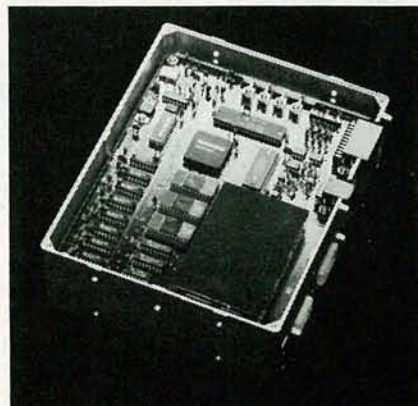


FIG. 6—THE NAVIGATIONAL COMPUTER processes data from the sensors and generates the video display.

scales and are coordinated with adjustable scales on the display screen. You can also map out paths on overlays with a grease pencil to assist in maneuvering through new territory. Cost for the *Electro Gyro-Cator*, including installation by Honda, is around \$1100, but the system is presently not available in the United States.

Compared to *The Navigator's* built-in map-generation technique, Honda's overlays seem cumbersome, especially when they may need to be changed in the middle of a trip. But both systems point toward increased use of computers in automobiles of the future, and even if their introduction here is five years or so away, it is an indication of how far and how fast consumer applications of computer technology have come. Concepts that were considered to be too complex for 20th-century development will likely be realized even before the end of the 1980's. Considering that, one must wonder what the next decade, and the next century will bring. It might even leave those in Hollywood breathless. R-E

BUILD THIS

EXPAND

Your

TIMEX/SINCLAIR Operating System



Build this upgrade for your Timex/Sinclair 1000 and you'll be able to store your own system-software modifications in 8K of nonvolatile RAM.

DESPITE ITS LIMITATIONS, THE TIMEX/Sinclair 1000 microcomputer (previously sold as the Sinclair ZX81) is a remarkable machine. It comes complete with an operating system and BASIC interpreter in 8K of ROM; 2K of RAM (the ZX81 came equipped with only 1K); an RF modulator for black-and-white video output to any TV, and a cassette interface for program and data storage. Perhaps the most remarkable thing about the machine, however, is its \$99.95 price, which is often discounted to as low as \$70, and may drop even lower in the coming months.

If you own a Timex/Sinclair 1000, you have probably wondered whether it can be improved. Well, it can. This article describes one upgrade that you can build for your machine—an 8K CMOS RAM board with battery backup. The board can be used simply to expand the computer's system/user memory, or—a more useful

application—the board can be used to store machine-language subroutines and, in effect, expand the operating system of the computer.

The 8K RAM board is designed to be used with the Timex/Sinclair 1000 computer and a 16K RAM pack to form a 32K system (8K of ROM, 16K of RAM, and 8K of battery-backed-up nonvolatile memory—see the memory map of Fig 1). In that 32K system, the memory board would occupy the 8K block from 8K to 16K. That area of memory is a very convenient location to store your own system-software modifications and machine-language subroutines because it is transparent to the computer's operating system. That means that the memory is not affected by NEW, LOAD, or other such commands that would normally clear the contents of memory. Even resetting the computer (turning it off and then on) will not affect the memory.

PAUL W.W. HUNTER

The CMOS RAM board that we will describe requires very little power, so it can use the computer's +5-volt regulated supply. Also, the board requires very little drive, so it is unnecessary to buffer the Z80's data, address, and control lines.

Possible applications

What can you store in an 8K block of memory that is transparent to the computer's operating system? The list is almost endless, but we'll give you some examples.

The Timex/Sinclair BASIC, although

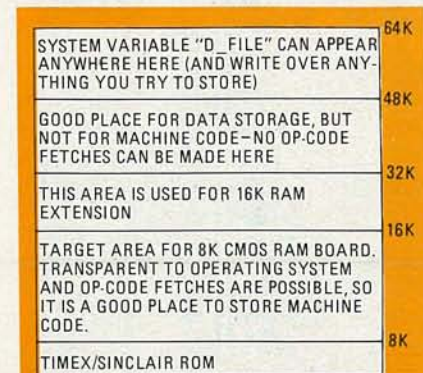


FIG. 1—MEMORY MAP OF the Timex/Sinclair 1000. The RAM board ignores address line A15, so additional decoding is necessary if you want the CMOS RAM to reside at a block of addresses above 32K.

powerful (especially for its 8K size), does not have READ or DATA commands. However, machine-code routines can be written to simulate those commands, and then those routines can be stored in the nonvolatile memory and called (by a user statement) when needed. That procedure thereby expands the operating system of the computer.

Other examples of user-defined system-routines that might be stored in the 8K-16K block are: line renumbering, resequencing, copying, and other editing routines; custom mathematical or statistical functions; routines to enter, examine, and edit machine-language programs; a machine-language disassembly program; a checksum routine; decimal/hex/octal conversion routines; other new BASIC commands; Sinclair code/ASCII conversion-tables, etc.

Once you have your software well established, the memory IC's can be replaced by pin-compatible 2716 or 2732 EPROM's. Thus you can even make up your own "game cartridges" that load almost instantly!

The expansion port

Before we discuss the expansion board any farther, we will take a look at the port to which it will be connected. That port, which is located at the back of the computer, provides access to all of the lines from the computer's Z80 microprocessor. The lines that are available are listed in Table 1, and the port's pinout is shown in Fig. 2.

Peripheral modules like the Timex/Sinclair 16K RAM pack—as well as the

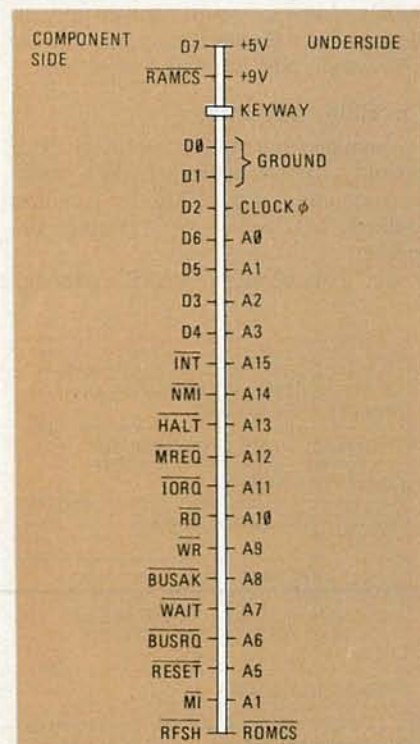


FIG. 2—THE PINOUT of the Timex/Sinclair 1000 card edge that is available at the port at the back of the computer.

TABLE 1

Description	Signal	Function
Address bus	A0 - A15	Outputs memory-and I/O-device addresses
Data bus	D0 - D7	Transmits bidirectional data into/out of CPU
System control	MREQ	Identifies any memory-access in progress
	IORQ	Identifies any I/O operation in progress
	RD	Indicates that the CPU wants to read data
	WR	Indicates that the CPU wants to output (write) data
	MI	Identifies the op-code fetch cycle of instruction Also used with IORQ to acknowledge interrupt
System clock	RFSH	Synchronizes dynamic-memory refresh
	ϕ	3.25 MHz clock (output)
	RESET	Resets CPU when pulled low
CPU control	INT	Interrupt request input
	NMI	Interrupt request input; cannot be disabled
	WAIT	Indicates wait state in machine cycle
	HALT	Indicates CPU has executed a HALT instruction
Bus control	BUSRQ	Request to CPU for control
	BUSAK	Acknowledgement of release of control by CPU
RAM/ROM select	RAMCS	If pulled high will disable computer's on board RAM
	ROMCS	If pulled high will disable computer's ROM
Power	+9V	Unregulated
	+5V	Regulated
	GROUND	

wide variety of other plug-in units that are available from various manufacturers—plug in at the port, as does the CMOS RAM board. A "piggyback" connector is included, which allows you to plug the memory board into the computer, and then plug other peripherals into the computer via the board.

The signals that are available at the expansion port are predominantly the Z80 CPU signals. Two additional signals provided are $\overline{\text{RAMCS}}$ and $\overline{\text{ROMCS}}$ —the chip-select signals for the onboard RAM and the system ROM. Having those lines available allows the user to disable the internal memory by tying the appropriate chip-select signal to +5-volts.

Unfortunately, the connector that is required for connection to the port is a non-standard, 46-position (23 per side) card-edge connector with 0.1-inch spacing. However, that really isn't as bad as it sounds because the connector can be fabricated easily enough by cutting the ends off a standard 50-position card-edge connector with 0.1-inch spacing. (The connector for the computer must have open ends.) A key should be inserted in the third position to prevent anything from being inserted backwards.

The CMOS RAM board

As we said earlier, the board is designed to occupy the 8K block of memory from 8K-16K. However, it can be easily "programmed" to occupy other 8K blocks, simply by changing jumper positions. (We'll get to the particulars of that in a little while.) Of course, you would probably not want the memory to occupy the first 8K block (where the computer's operating system is contained), but it could even do that if you wanted it to. The board could equally well, for example, replace half of the 16K RAM pack.

The schematic of the memory expansion is shown in Fig. 3. The Z80 MREQ control signal is used to enable the first half of the 74LS139 dual 1-of-4 decoder (IC5-a), which is used to divide the 32K of memory into four 8K blocks. The particular 8K block that the memory board will occupy is then selected by a jumper (JU1). (We will discuss how to position JU1 as well as all of the other jumpers in a following section.) The second half of that 74LS139 decoder (IC5-b) is used to provide chip-select signals for the 6116P 2K RAM's. The Z80 RD signal is used to enable the outputs of the memory IC's.

The Hitachi MH6116P (standard or 6116LP-3 low-power version) static CMOS RAM can be left in a standby mode when the computer is not in operation. That is done by backing-up the power supply with a lithium battery as shown in Fig 3. With such a back-up, the data stored in the RAM becomes non-volatile. (There is also a provision on the board for an external battery supply other than the lithium cell.) The 6116P data sheet specifies that for low-power standby, the chip-enable pin should be held at a voltage at least equal to $V_{cc} - 0.2$ volt. Simple NPN-transistor switches (Q2-Q5) allow passage of the $\overline{\text{CS}}$ signal when the power supply is connected, but pull the chip-enable pins to V_{cc} through resistors R2-R5 when the main power supply is not present. Transistor Q1 acts as a voltage-sensitive switch—it switches off when power from the main supply is not present which, in turn, switches off transistors Q2-Q5.

The RAM does not require a full +5-volt supply in standby mode, and a lithium cell (3 volts, 150 mAh) works well. The current drain for a fully populated board is less than one microamp. That means that a single lithium cell

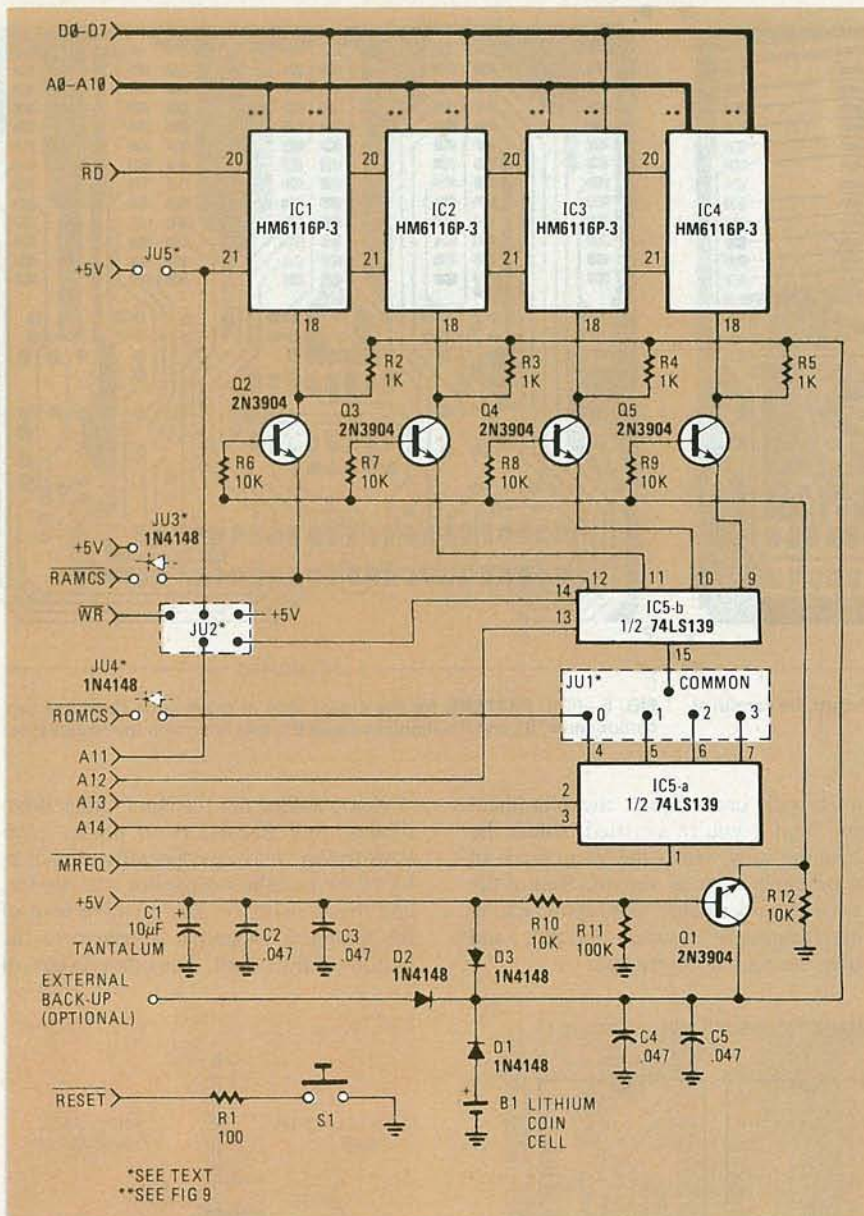


FIG. 3—SCHEMATIC of the 8K CMOS RAM board. Note that the exact pin connections for the data and address busses are not shown here—see Fig. 9.

should last for many years. Be sure to keep the CMOS RAM board plugged into the microcomputer even when you're not using it, and even when the computer is switched off. Doing that prevents the data and address lines from floating high—standby current consumption can increase two orders of magnitude if those lines go high.

A reset switch is located on the board to make it unnecessary to unplug the power supply every time you want to reset the system. It is recommended that you use the switch, because if you reset the computer by pulling the plug and then reinserting it, there is a chance that the filter capacitor in the power supply will not have time to discharge. If that happens, the CPU will not reset when the power is restored, and you may find that it will write over all of your nonvolatile memory.

Construction

We recommend that you use a printed-circuit board for the CMOS 8K RAM extension. (The foil pattern for the piggyback extender board is shown in Fig. 4, and the foil patterns for the double-sided board are shown in Figs. 5 and 6. The parts-placement diagram is shown in Fig. 7). The author, however, did put together a prototype CMOS memory board using wire-wrap techniques, and the circuit worked well. The usual rules apply—

keep the connections as short as possible; lay out the circuit in an orderly way in the smallest possible area without unnecessary overcrowding; include decoupling capacitors at the power-supply pins of the IC's; avoid bundling wires together to prevent crosstalk, etc. With a wire-wrap board you will notice slight additional interference on your TV screen. Using prototype boards with a ground plane, and then shielding the boards in a grounded metal case helps a lot. However, interference is usually less of a problem with a printed-circuit board, and such a board will be more reliable in operation and construction.

If you do use a PC board, solder the sockets to the board first—use a fine-tipped low-power (about 27 watts) iron and take care not to cause solder bridges between the traces. Make sure the iron is hot and use a minimum amount of solder—too much solder may run through and form a solder bridge on the component side of the board.

PARTS LIST

All resistors 1/4 watt, 5%, unless otherwise specified

- R1—100 ohms
- R2-R5—1000 ohms
- R6-R10, R12—10,000 ohms
- R11—100,000 ohms

Capacitors

- C1—10 μ F, 16 volts, tantalum
- C2-C5—0.047 μ F, ceramic disc

Semiconductors

- IC1-IC4—HM6116LP-3 150-nS low-power 2K \times 8 CMOS RAM
- IC5—74LS139 dual 1-of-4 decoder
- Q1-Q5—2N3904
- S1—SPST pushbutton switch (Panasonic EVQ-P1R04K or similar)
- B1—3-volt lithium coin-type battery (Panasonic BR-2325 or similar)

Miscellaneous: PC board or wire-wrap board, IC sockets, card-edge connector, battery holder, etc.

The following are available from Paul Hunter, 1630 Forest Hills Drive, Okemos, MI 48864: complete kit, including a drilled, plated, solder-masked, and silkscreened PC board; edge connector; piggyback connector; IC sockets; battery holder; battery; one HM6116LP-3, and all other components, \$29.95 plus \$1.95 shipping and handling. (Michigan residents add 4% sales tax.) The PC board alone is available for \$15.00 postpaid. An additional three HM6116LP-3 CMOS RAM'S may be purchased with the kit for an additional \$16.


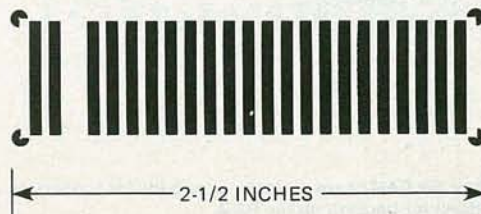
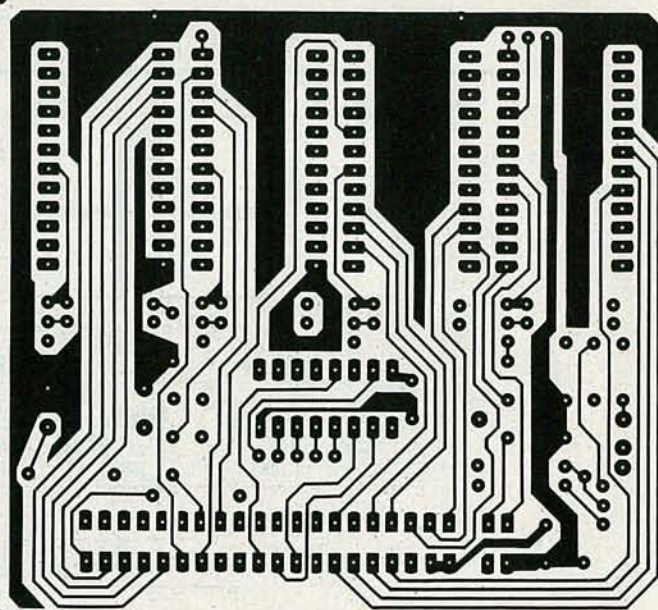


FIG. 4—FOIL PATTERN for the piggyback extender board that lets you use other peripherals with the CMOS RAM extension. Although it is a double-sided board, both sides are the same, so only one pattern is shown. The installation of this board is discussed in the text and is shown in Fig. 8.

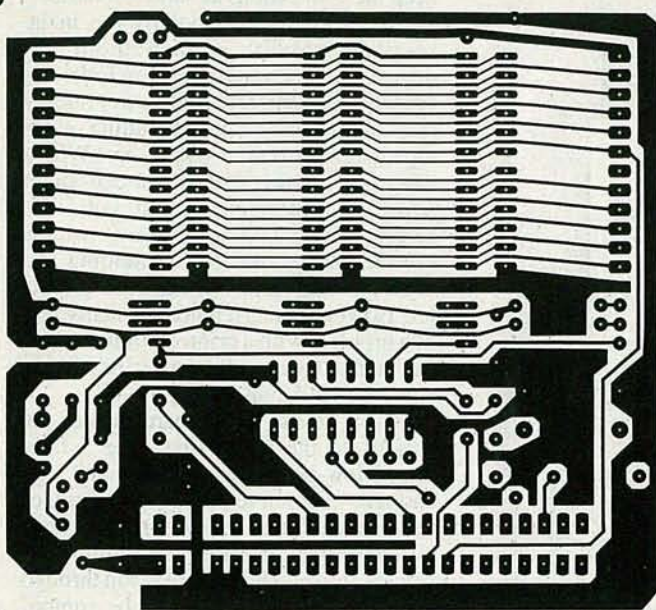

3-5/8 INCHES

FIG. 5—FOIL PATTERN for the component side of the board. Be careful at the tight spots when you are soldering.

3-5/8 INCHES

FIG. 6—FOIL PATTERN for the circuit side of the board. There are two components, S1 and the lithium battery B1, that mount on the circuit side.

Solder the card-edge connector in place as follows: Insert the connector in the appropriate holes and adjust the stand-off distance to at least 1/4 inch as shown in Fig. 8. Make sure the connector is the same distance off the board at both ends, and at right angles to it; then solder one

pin at each end. Check the alignment again, and if you're satisfied, solder the remaining pins. Bend the wrap posts in toward each other as shown. Secure the second extender board (for piggybacking other peripherals) between the pins, and solder the pins to its traces.

Next, solder the resistors, capacitors, diodes, and transistors in place—refer back to Fig. 7. Note especially the polarity of the tantalum capacitor, the diodes, and the transistors. The positive lead of the tantalum capacitor is nearer to the bottom of the board. The curved sides of

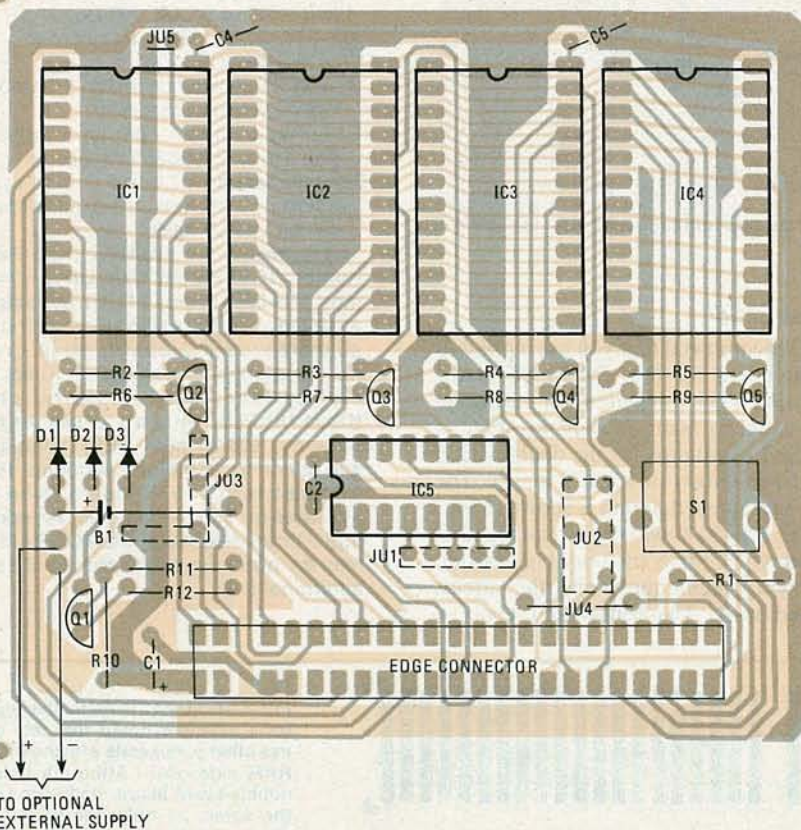


FIG. 7—COMPONENT-PLACEMENT DIAGRAM for the RAM board. Note the extra pads for connecting an external battery (other than the lithium battery) for backing up the RAM.

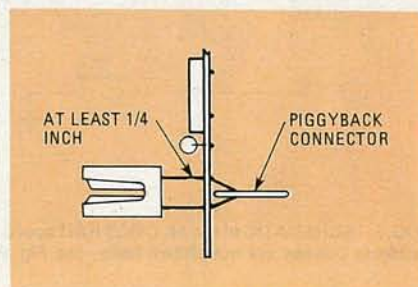


FIG. 8—SIDE VIEW OF THE CARD-EDGE CONNECTOR mounted on the PC board. Note also how the piggyback extender-board is attached.

all the transistors point to the left side of the board. Although we will not discuss the jumpers in great detail at this point, if you plan to vary your use of the board, insert wire-wrap pins at the jumper positions and use wire-wrap wire for the connections.

You should mount the RESET switch on the opposite side (circuit side) of the PC board where there's a little more room for your finger to get at it. Also solder the lithium-cell holder to the that side of the board. Hold the battery-holder firmly against the board when soldering it, and make sure it's oriented correctly.

When we continue we'll finish up the construction, discuss the available options, and look at some software you can store. **R-E**

BUILD THIS

Part 2 WE HAVE ALREADY DISCUSSED the theory behind how this clock talks. (See the May 1983 issue of *Radio-Electronics*.) Now we'll discuss how to build the clock, and how to operate it.

Hardware description

Please refer to the block diagram (Fig. 2), and the schematic diagram (Fig. 3) of the talking clock as we discuss its internal operation.

The entire clock is controlled by a Z80 microprocessor, IC1. It keeps track of the time, reads all the switches, and controls the speech synthesizer. The control software for the processor is stored in a 2516 or 2716 EPROM, IC4, with a capacity of 2K bytes. The microprocessor also uses two $1K \times 4$ 2114 RAM's (IC2 and IC3).


The six mode and set switches, S1-S6, are connected to the microprocessor through a Tri-State buffer IC10.

A 74LS139 address decoder, IC9, connected to the microprocessor's address and control lines, generates the various strobe pulses that control reading and writing from and to the memory, speech synthesizer, and the switch buffer.

The voice-synthesis processor is the TMS5220, IC6, which is connected to the microprocessor bus through a 74LS245 bidirectional octal buffer, IC5. The buffer is needed to isolate the TMS5220 from the microprocessor data bus.

In operation, the TMS5220 and the microprocessor operate at different speeds—the TMS5220 is a very slow device. Therefore, the microprocessor has to be slowed down whenever it does a

TALKING

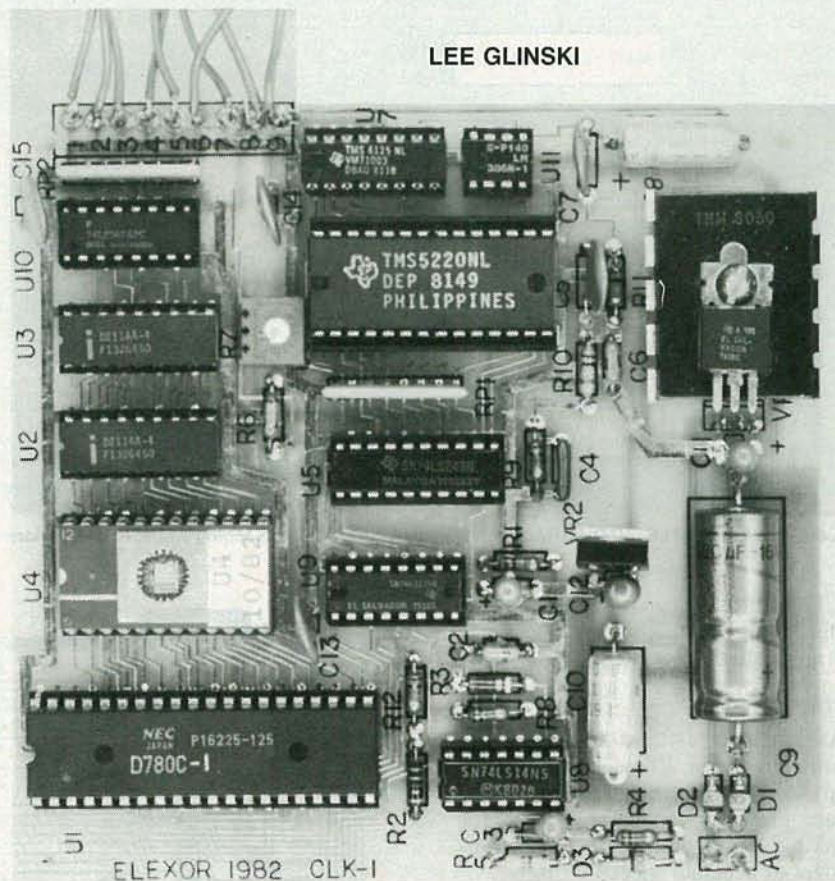

ALARM CLOCK

When you need to know what time it is, this clock tells you—literally.

read or write from or to the VSP. That is accomplished by using a special line coming out of the voice synthesizer—the **READY** line. That line is connected to the microprocessor's **WAIT** line. When the microprocessor reads or writes from or to the VSP, the **READY** line indicates when the TMS5220 has finished its data transfer. The VSP will take the microprocessor's **WAIT** line low to signal the microprocessor to temporarily stop and wait until it (the VSP) has completed its data transfers. As soon as the data transfer is complete, the VSP releases the Z80, and program execution continues.

Speech data for time announcements is contained in ROM IC7, a Texas Instruments VM71003 that is pre-

programmed with a clock vocabulary. It is connected to the TMS5220 by means of a dedicated interface bus.

The audio output of the voice processor IC is fed to a simple, passive, low-pass filter consisting of R9-R11, C5, and C6. The filter is needed because the speech waveform coming from the D/A converter contains some digitizing noise and must be smoothed out to produce a clean analog waveform. The filtered waveform is fed to audio amplifier IC11, an LM386 audio amplifier capable of delivering over 100 mW—more than enough for most purposes.

The power supply uses a wall-plug-type transformer, T1. The nine-volts AC from the transformer is rectified by diodes

D1 and D2. The rectified voltage is filtered by capacitors C9 and C10 and then goes to two 3-terminal regulators, IC12 and IC13, which regulate it to +5 and -5 volts, respectively. The clock draws under 500 mA from the +5-volt supply, and under 50 mA from the -5-volt supply.

The transformer also supplies the 60-Hz reference frequency used for the timekeeping function. A 60-Hz sinewave is taken from the transformer and rectified by diode D3. The signal is then dropped to TTL levels by a voltage divider made up from R4 and R5. That TTL-level signal is buffered by a Schmitt trigger (IC8-c) and applied to the non-maskable-interrupt (NMI) line of the microproces-

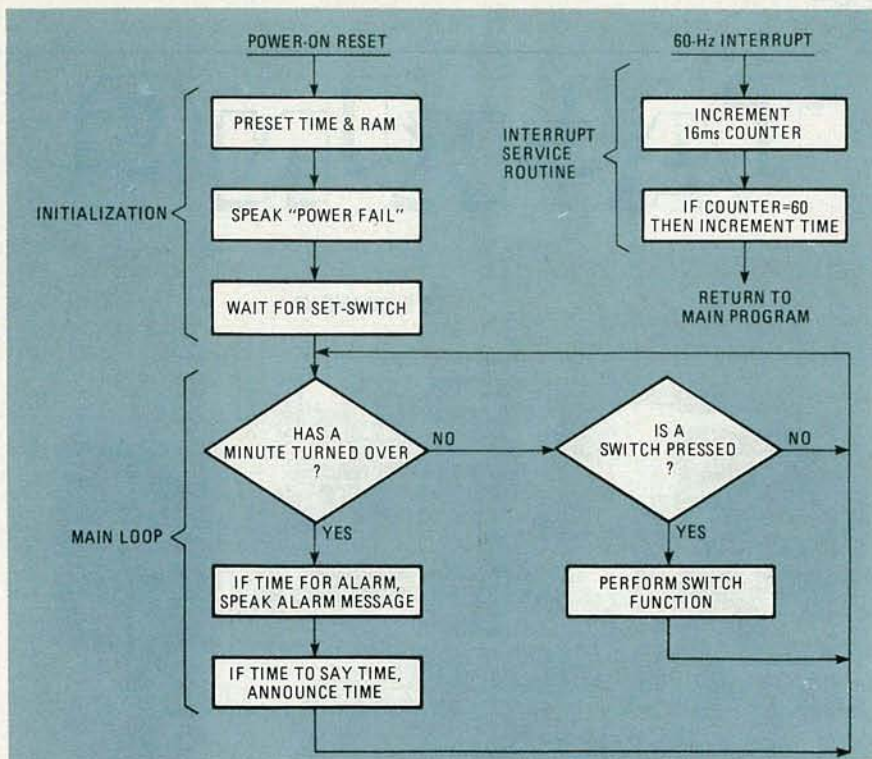


FIG. 4—MAIN LOOP IN LOGIC DIAGRAM handles coordination of timekeeping and speech functions.

sor. Capacitor C3 across the input of the buffer filters out high-frequency noise that might give false interrupts.

Software

As mentioned earlier, the entire clock is software-driven. There are routines to keep track of time, check whether switches are pressed, compose phrases for speaking, and control the voice synthesizer to generate speech.

As indicated in the flowchart, Fig. 4, the microprocessor takes care of all timekeeping functions, as well as causing the speech synthesizer to speak words and phrases.

When power is applied to the clock, the microprocessor RESET line is activated, and the microprocessor performs a power-on initialization routine. That routine presets the time and the alarm to 12:00 AM, as well as initializing some internal registers. It then alerts you to set the time by first beeping and then announcing, "Power fail. Set the time," twice. During initialization the normal time-speaking function is inhibited. That's done to prevent false time-indications. When the TALK button is pressed, instead of announcing the time, the clock will tell you to "set the time." The normal speaking-function is enabled only after the time has been set.

The 60-Hz line frequency provides the time reference for the clock. The 60-Hz power-line signal is applied to the non-maskable-interrupt line of the microprocessor. Every time the interrupt occurs, the microprocessor increments a counter. Since the interrupts come every 16.67 ms

(1/60-second), a count of 60 will indicate precisely one second. So, every time the counter reaches 60, the time of day is incremented by one second. The only action performed at the time the interrupt takes place is the incrementing of the time counters; resetting of the clock functions is done in the main loop of the software.

As shown in the flowchart, the primary function of the main loop is to decide when to perform certain operations.

Whenever the minute-point is reached, the software checks to see whether the alarm is on, and whether the time of day matches the alarm time. If the alarm is on and the two times match, then an alarm message is spoken.

The software also checks to see whether it's time to speak the time in the auto-speak mode. Once it decides that the time is to be spoken, it composes a phrase containing the appropriate "hour" and "minute" words. That phrase is then spoken by the voice processor.

Another function of the program's main loop is to continuously check on whether one of the pushbutton switches is pressed. If it finds one of the SET switches pressed, it increments the time, thus allowing the user to set the time of day. If

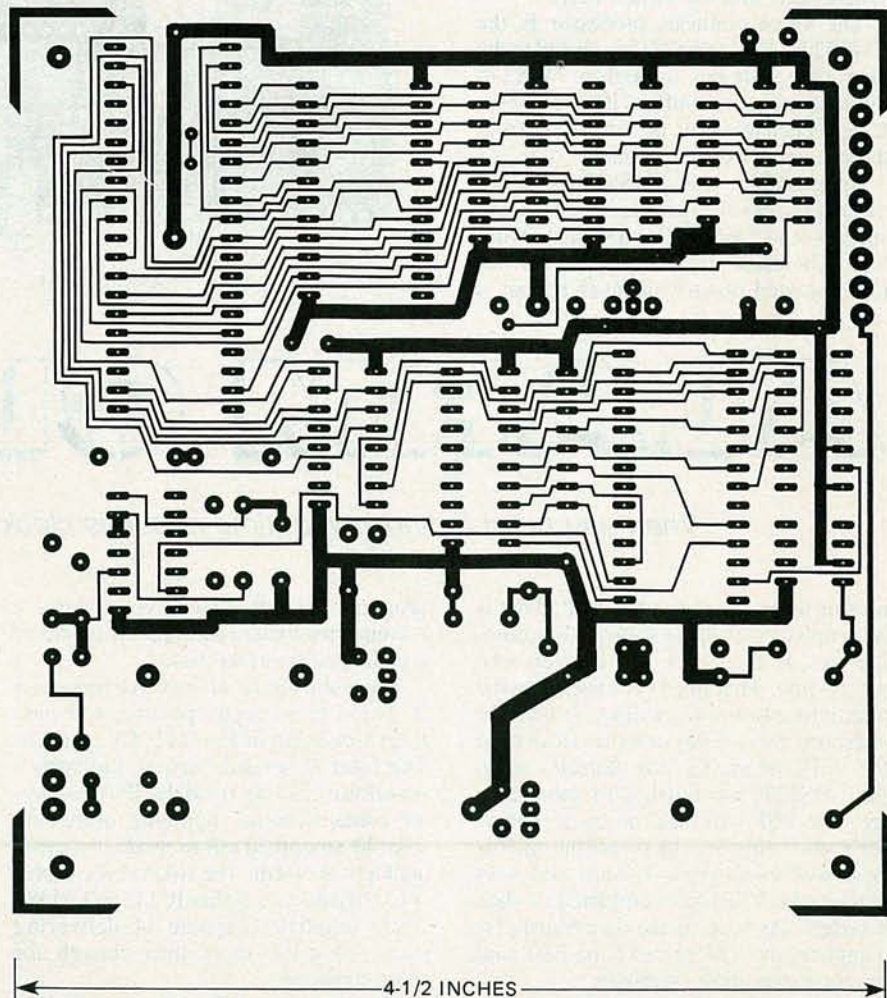


FIG. 5—COMPONENT SIDE of clock board. Large pads at right are for connections to switches and speakers.

the SPEAK TIME switch is found pressed, the software composes a phrase containing the current-time information, and announces it.

Construction

The talking clock should be built using a double-sided printed-circuit board with plated-through holes. A foil pattern for the component side of the board is shown in Fig. 5, and one for the "foil" side in Fig. 6. A professionally made silk-screened board can be obtained from the source shown in the Parts List.

PARTS LIST

All resistors 1/4 watt, 5% unless otherwise noted

R1, R11—10,000 ohms
 R2—330 ohms
 R3—620 ohms
 R4, R8, R9, R12—1000 ohms
 R5—470 ohms
 R5—180,000 ohms
 R7—100,000 ohms, PC-mount trimmer potentiometer
 R10—100,000 ohms
 R13, R14—8 × 1K SIP (Single In-line Package) resistor pack

Capacitors

C1—330 μF, 10 volts, electrolytic or tantalum
 C2—0.001 μF, ceramic disc
 C3, C11, C12—2.2 μF, 10 volts, electrolytic or tantalum
 C4—0.05 μF, ceramic disc
 C5, C7, C13—C15—0.1 μF, ceramic disc
 C6—0.01 μF, ceramic disc
 C8, C10—100 μF, 16 volts, electrolytic
 C9—680 μF, 16 volts, electrolytic

Semiconductors

IC1—Z80 microprocessor
 IC2, IC3—2114 1K × 4 RAM
 IC4—2516 or 2716 2K × 8 EPROM, pre-programmed
 IC5—74LS245 octal bus transceiver
 IC6—TMS5220 voice-synthesis processor
 IC7—VM71003 clock-vocabulary ROM
 IC8—74LS14 hex inverting Schmitt trigger
 IC9—74LS139 dual 2/4 decoder
 IC10—74LS367 hex Tri-State bus driver
 IC11—LM386 audio amplifier
 IC12—7805 5-volt positive regulator
 IC13—7905 5-volt negative regulator
 D1—D3—1N4001
 T1—9 VAC, 600 mA, wall-plug transformer
 S1—S3—SPST slide or toggle switch
 S4—S6—SPST N.O. pushbutton switch

Miscellaneous: PC board, speaker, IC sockets, heat sink for +5-volt regulator, enclosure, wire, solder, etc.

The following are available from ELEXOR, PO Box 246, Morris Plains, NJ 07950: double-sided plated-through PC board, \$12.50; IC4, \$7.50; IC6 and IC7, \$25.00; kit of all parts (less enclosure) \$69.50. Please add \$2.50 for postage and handling as well as applicable state and local sales tax(es).

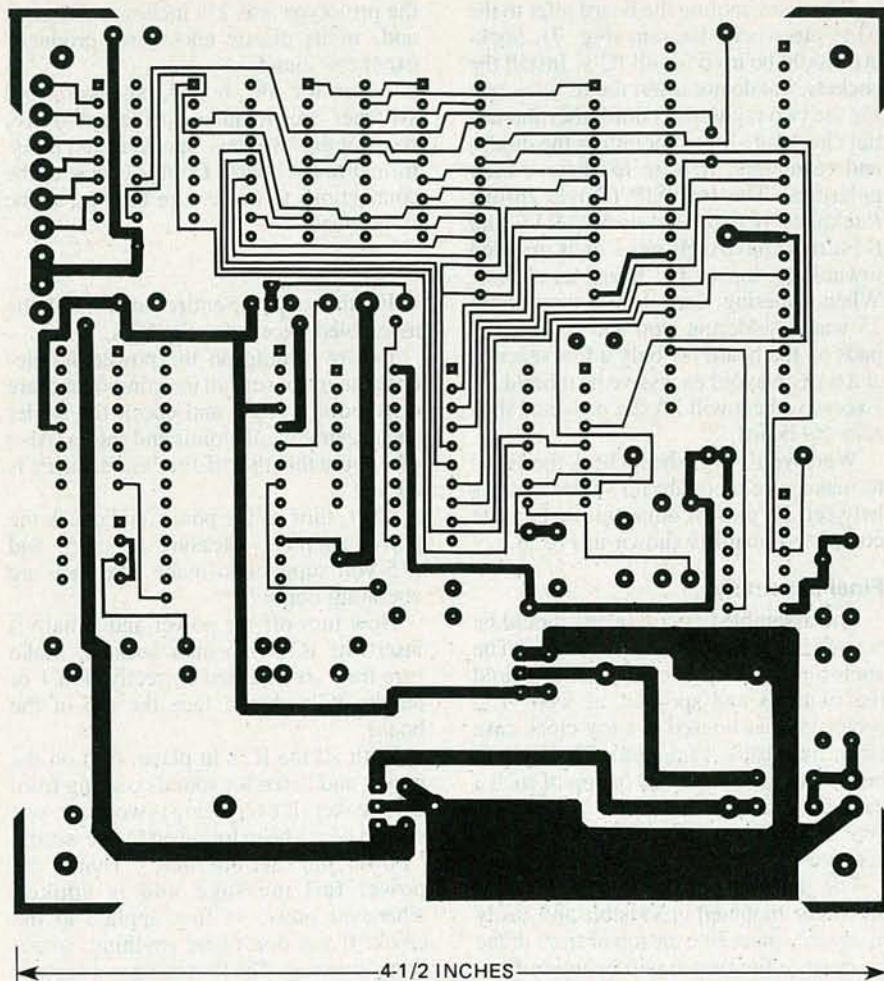


FIG. 6—"FOIL SIDE" of clock board. Double-sided board uses plated-through holes and can be ordered from supplier indicated in Parts List.

Hand-wired breadboard construction can also be used if a great deal of care is taken. The layout should follow the PC-board design. Use heavy wire for the

ground and power lines, and make sure the audio section is away from the other IC's to eliminate noise-pickup by the amplifier.

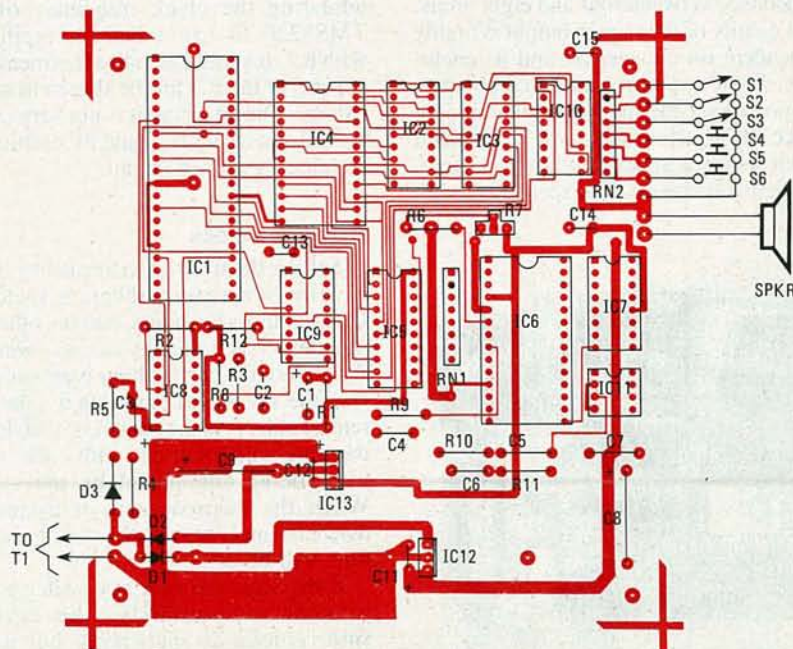


FIG. 7—OFF-THE-BOARD COMPONENTS (with the exception of T1) are mounted on clock case. See Fig. 3 for switch functions.

When assembling the board refer to the parts-placement diagram (Fig. 7). Sockets should be used for all IC's. Install the sockets, but do not insert the IC's (except for the two regulators) until after the initial checkout. When mounting the diodes and capacitors, be sure to observe their polarities. The two SIP (Single In-line Package) resistor-networks, R13 and R14, must have their pin-1 ends oriented toward the top of the board as shown. When soldering, use a low-power (about 25 watts) soldering iron and contact the pads on the board for only a few seconds at a time to avoid excessive heat buildup. Excessive heat will lift the pads and thus ruin the board.

When you've finished, check the board to make sure there are no solder bridges between IC pins or adjacent traces. The completed board is shown in Fig. 8.

Final assembly

The assembled circuit board should be housed in some type of an enclosure. The enclosure should be large enough to hold the switches and speaker, as well. The prototype was housed in a toy-clock case (with the insides removed). The "alarm bells" could be mounted on top of such a case and could contain two pushbutton switches (S6) connected in parallel to activate time speaking.

The SPEAK TIME pushbutton switch should be mounted in a visible and easily accessible place like the top or front of the case, since the switch will be used often. If the alarm is also to be used frequently, then the alarm ON-OFF switch should be mounted in an easily accessible place. The MODE and SET switches should be mounted on the rear of the box to keep curious fingers from disturbing the time setting.

The speaker can be any type with an impedance between four and eight ohms. The quality of the speech output is highly dependent on the speaker and its enclosure. Some experimentation can be performed to get the most natural sounding voice. Best performance will be obtained when using a speaker with good low-frequency response. The speaker used in

the prototype was 2¾ inches in diameter and, in its plastic enclosure, produced excellent sound.

After the PC board, speaker, and switches are mounted in the enclosure, connect the switches, speaker, and transformer to the board. Double check all the connections to make sure they go to the right places.

Checkout

For this step, the entire clock should be assembled except for the IC's.

Before turning on the power double-check to make sure all the components are oriented correctly, and check the solder pads again for cold joints and shorts. Also make sure that the off-the-board wiring is correct.

Next, turn on the power and check the power supplies. Measure the +5- and -5-volt supplies to make sure they are operating correctly.

Now turn off the power and (finally!) insert the IC's into their sockets. Make sure they are oriented correctly. Pin 1 of all the IC's should face the top of the board.

With all the IC's in place, turn on the power and listen for sounds coming from the speaker. If everything is working, you should hear a beep followed by the words, "Power fail. Set the time." That is the power-fail message and is spoken whenever power is first applied to the clock. If you don't hear anything, something is wrong. The first thing to do is turn off power and re-check the board for cold solder joints and shorts. Make sure that all the IC's are inserted correctly, all the parts are the correct values, and that the power supply is working.

Calibration

Calibration of the clock consists of adjusting the clock frequency of the TMS5220 (it has a built-in oscillator) with R7. It should be 640 kHz (measured at pin 3 of the IC) for the speech to sound natural. The adjustment is not very critical, and can easily be made by listening to the clock's speech output.

Using the clock

Setting the time is performed by using the two SET TIME pushbutton switches. One advances the hours, and the other the minutes. When the SET HOURS switch is depressed, the current hour is announced. (For the SET MINUTES switch it's the current minute.) As the switch is held down, the time will count up, with each increment being announced by the clock. When the desired hour or minute is reached simply release the switch and the time will be set.

If the MINUTE/HOUR SET switch is depressed momentarily, the current MINUTE/HOUR is announced, but is not incremented. At the same time, a counter inside the microprocessor is cleared to

S1	S2	Function
Mode 0	Mode 1	
OFF	OFF	Speak time every minute
OFF	ON	Speak time on the hour
ON	OFF	Speak time on the quarter hour
ON	ON	Auto-speak disabled

zero. That counter is used to count time in seconds, and every time it reaches 60 the time-count will increment by a minute. Thus, momentarily depressing the SET switch will synchronize time to the second.

If the clock is just plugged in without the time being set, every time the SPEAK TIME pushbutton is pressed, the clock will say, "Set the time" as a reminder that the time has not yet been set.

The position of the ALARM switch determines whether the time or the alarm is to be set. If the switch is off, the time of day will be set. If it's on, the time the alarm goes off will be set. The alarm is set just like the time, except that the ALARM switch must be in the ON position. Remember that whenever the switch is on, the SET switches will set the alarm time and not the time of day. The current alarm setting can be heard by throwing the ALARM ON/OFF switch from the OFF to the ON position. Every time that's done, the clock will announce the alarm setting.

To use the alarm, first set the time you want it to go off, as described above. Then set the ALARM ON-OFF switch to the ON position; that will enable the alarm circuitry. When the alarm time-setting time matches the time of day, you'll hear the following: "Good morning. The time is seven twenty-six AM. Time to get up." The time announced is the actual time of day, and the "good morning" changes to "good afternoon" or "good evening," depending on the time of day.

After using the alarm several times I found it much more effective and pleasant than the conventional buzzer. If you are a heavy sleeper and don't wake up to turn off the alarm, it will repeat the alarm message every minute until it is turned off. Once the alarm is tripped, it can be shut off either by pressing the SPEAK switch, or by setting the alarm switch to the OFF position.

Switches S1 and S2 are used to select the auto-speak mode of the clock. In that mode the time will be announced automatically at predetermined intervals. The settings are shown in Table 1.

If you choose not to use the auto-speak mode, you can make the clock tell you the time simply by pressing the TALK button. If the button is held down, the time will be announced continuously. **R-E**

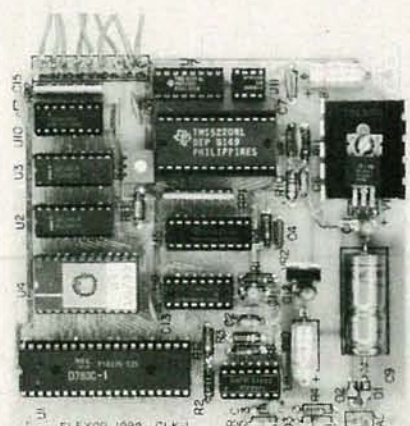


FIG. 8—THE COMPLETED CLOCK BOARD. Note that IC12 requires a heat sink.

CIRCUITS AND COMPONENTS

IT SEEMS HARD TO BELIEVE THAT THE first integrated-circuit operational amplifiers (op-amps) were introduced less than twenty years ago. The extremely low price of IC op-amps, and the almost unlimited number of applications for them, have served to make them one of the mainstays of modern electronic-circuit design. Indeed, it is difficult to flip through the pages of any electronics publication without seeing some reference to those useful IC's.

Actually, the term "op-amp" doesn't describe one integrated-circuit, but rather is a generic term for a whole family of linear circuits. There are compensated and uncompensated types, single-supply types, current-differencing types, BIFET types, and so on. But one breed of op-amp, known as the operational transconductance amplifier (OTA) hasn't received the amount of attention that it deserves. This article details both the theoretical and practical aspects of the OTA. By the time you are done reading it, you should feel confident enough to attempt your own design with this interesting type of IC.


One of the earliest OTA's was the 3080. There are now several others available and, while they offer several additional interesting features, they essentially obey the same rules and operate just like their predecessor. Hence, designing with the 3080 is emphasized in this article, but keep in mind that switching over to other OTA's is easy.

Before considering the internal makeup of the 3080, we should consider in general terms just what it is, and what it can do. In many respects, the 3080 is much like a common op-amp. It has differential inputs. The difference between the voltages at those two inputs is multiplied by a certain gain, and the result is available at an output pin. Also, the gain

Often ignored by beginners, operational transconductance amplifiers are useful and easy to work with. This article will give you a good start toward designing and building your own projects using these versatile devices.

THOMAS HENRY

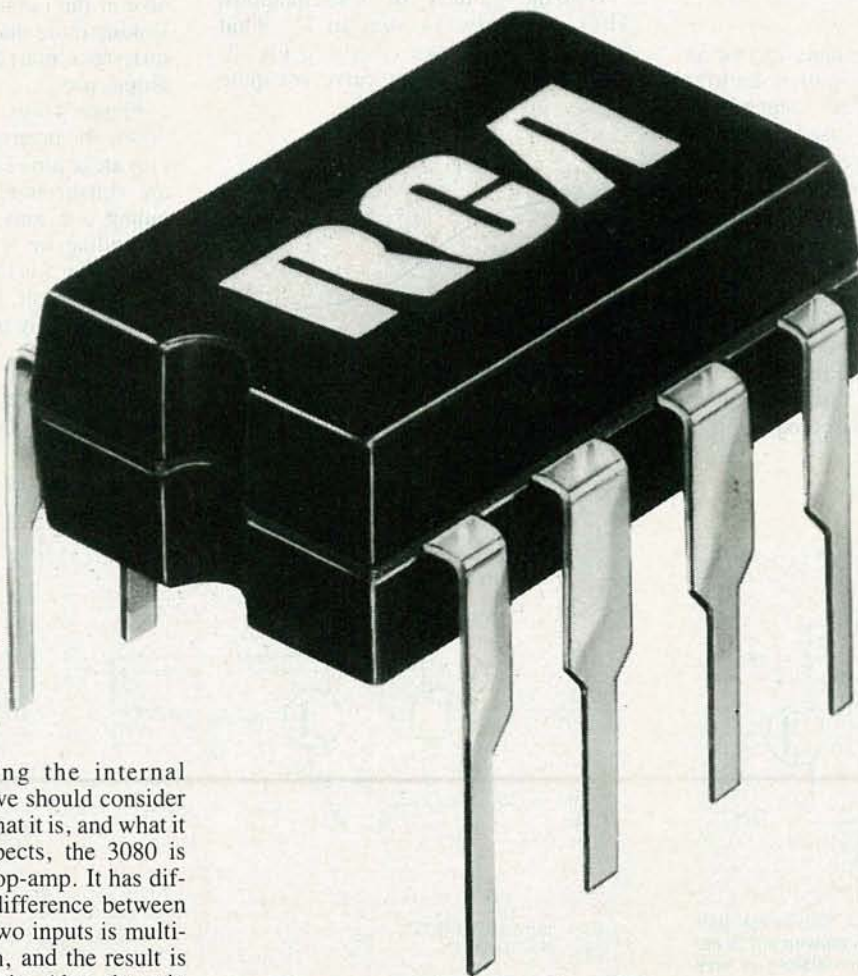How to Use Transconductance Operational Amplifiers



can be altered simply by changing the values of certain resistors. And, finally, the 3080 needs a bipolar power-supply.

What sets it apart from the common op-amp, however, is the inclusion of another pin that allows the user to change the gain (or more properly, the transconductance) of the amplifier. That control pin, pin 5, is a current-type input. The more current, I_{ABC} that flows into the pin, the greater the IC's gain. In other words, that input current varies the transconductance of the device.

In the January, 1983 issue of **Radio-Electronics**, in the series on analog-circuit design, the op-amp was modeled as a voltage source in series with an output resistance. (See Fig. 3 of that article.) The transconductance amplifier, on the other hand, is modeled as a current source in parallel with an output resistance. So, yet another difference between an OTA and other op-amps is that an OTA features a current output. Speaking very generally, then, the 3080 is a current-controlled amplifier. If you consider the input for I_{ABC} (the control current) to be a programming input, then the 3080 is a programmable OTA.

What can such a device be used for? There are countless applications, but some of the more interesting ones are voltage-controlled amplifiers, voltage-controlled oscillators, sample and hold circuits, analog switches, a trianglewave-to-sinewave converter, and so on. Several of those circuits will be discussed later in this article.

Internal structure

Now that we know basically what a 3080 is and what it can do, we can start to consider its internal makeup. Unlike some other integrated circuits,

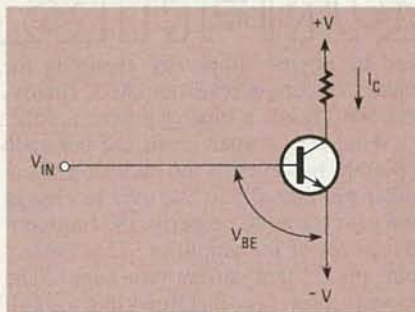


FIG. 1—THE OPERATION of the transistor differential-pair amplifier is based on the relationship of the input voltage to the collector current

where no specific knowledge of the internal circuitry is needed to use them, the unusual nature of the 3080 makes such knowledge very important.

The usual model used to demonstrate the internal structure of the 3080 is the differential-pair amplifier, although there are a few differences between them. Let's take a closer look at such an amplifier.

To understand the operation of the transistor differential-pair amplifier let's first look at the relationship of input voltage to collector current in a single transistor (see Fig. 1). That relationship is exponential and is given by the equation:

$$I_C = I' (e^{qV_{BE}/K_B T} - 1)$$

Several physical constants appear in that equation. The so-called emitter saturation-current, I' , depends on the particular transistor used. Its value will generally be between 1 and 0.01 picoamperes. Other constants that appear include K_B , the Boltzmann constant, and q , the charge of a single electron. The equation can be considerably simplified by letting $V_T = K_B T/q$, where T is the temperature of the transistor in degrees Kelvin. The value of V_T is then about 26 mV at room temperature. Finally, the -1 term can be ignored if the transistor is forward biased. The revised equation is then:

$$I_C = I' e^{V_{BE}/V_T}$$

That revised equation is considerably easier to work with.

Figure 2 shows a transistor differential-pair amplifier. The input of the amplifier is at the base of Q1, while the base of Q2 is grounded. A control current is drawn from the two tied emitters, and it is that control current that is used to alter the gain of the circuit. The output is taken from the two collectors.

In examining the operation of this amplifier, it is convenient to assume that the beta of the transistors is large. In that case, the emitter currents are approximately equal to the collector current. Hence, $I_O = I_1 + I_2$. Using the transistor equation we previously discussed, and Ohm's law, the equations for I_1 and I_2 can be derived. They are:

$$I_1 = \frac{I_O}{(1 + e^{-V_{IN}/V_T})}$$

$$I_2 = \frac{I_O}{(1 + e^{+V_{IN}/V_T})}$$

Note the symmetry of those equations; They must always sum to I_O . That relationship is shown clearly in Fig. 3. The asymptotes of that curve are quite

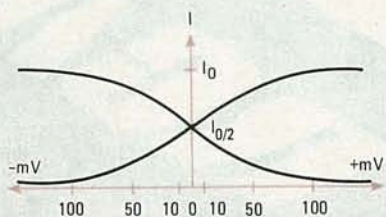


FIG. 3—THIS PLOT of emitter currents I_1 and I_2 shows that their sum is never greater than I_O . In fact, the sum of I_1 and I_2 is a constant and is equal to I_O .

important; neither I_1 or I_2 can be less than zero or greater than I_O . At $V_{IN} = 0$, the currents both equal $I_O/2$.

The curves are, of course, exponential, but for input voltages of less than 10 mV or so, the relationship between I_1 and I_2 , and V_{IN} , is more or less linear. Therefore, to keep distortion to an acceptable level in linear applications, V_{IN} should be held to 10 mV or less. Also, once the input voltage exceeds 100 mV, raising V_{IN} farther has no additional affect. One of the transistors will be cut-off, while the other will be saturated.

A simplified schematic of the 3080 is shown in Fig. 4. The transistor differential-pair is quite apparent, as is the absence of resistors. In their place, current mirrors are used. In a current mirror, the output current "mirrors" the input current, hence the name. Current mirrors CM1 and CM4 are current-sinking types, while CM2 and CM3 are current-sourcing types.

Current mirrors CM3 and CM4 mimic the collector currents of the two transistors of the differential pair. The sum of those currents is thus presented to the output. If the two currents are equal, indicating equal potentials at the inverting and noninverting inputs, the currents balance and there is no current at the output. If, however, CM3 sources more than CM4 can sink, the surplus is made available at the output. Similarly, if CM4 is sinking more than CM3 can provide, the difference must be provided through the output pin.

Figure 4 also shows a pinout of the 3080. The inverting and non-inverting inputs are at pins 2 and 3 respectively; those are voltage inputs. Pin 6 is the current output and may source or sink current depending on the conditions described above. Pin 5 is the input for the amplifier control-current, I_{ABC} . Finally, pin 7 is the positive supply pin and pin 4 is the negative supply pin.

Some practical design-equations

Having described the internal structure

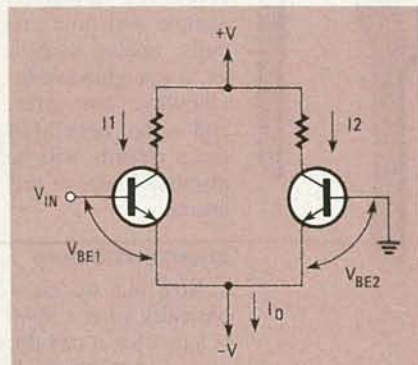


FIG. 2—A SIMPLE transistor differential-pair amplifier. In analyzing it, it is convenient to assume that the beta of the transistors is very large.

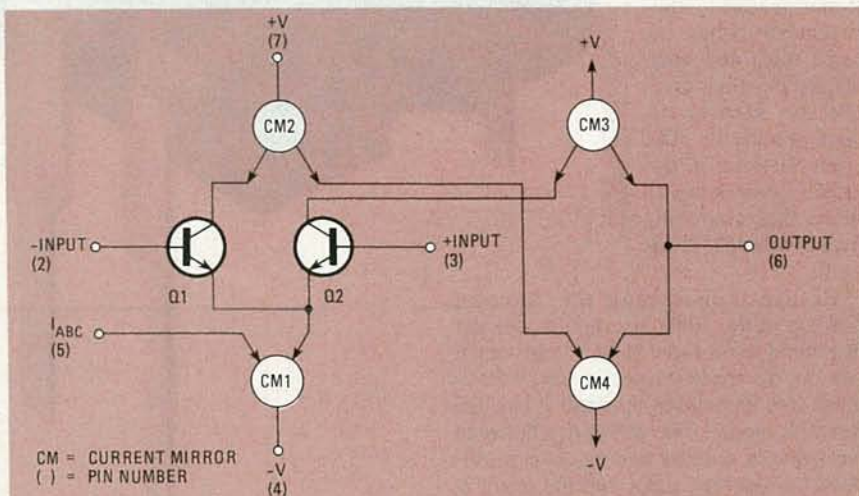


FIG. 4—SIMPLIFIED SCHEMATIC DIAGRAM of the 3080. The pin-out of the device is also shown here.

of the 3080 we can derive some practical design-equations. The most important is the so-called general transconductance equation that relates the output current to the input voltage and control current. It is: $I_{OUT} = 19.2 I_{ABC} V_{IN}$, where I_{OUT} and I_{ABC} are measured in milliamps and V_{IN} is measured in volts.

Eventually, we will want to convert I_{OUT} to a voltage, so that the unit will operate as a voltage amplifier, but for the moment, note that if V_{IN} is some fixed input-signal, we can vary the output amplitude simply by modulating the control current I_{ABC} .

Before the foregoing equation can be put to good use, some practical limits must be specified. In general I_{ABC} should always lie between $0.5 \mu A$ and $0.5 mA$ for best results. While it is possible to increase that upper limit somewhat, it is best not to do so since the 3080 can go into thermal runaway.

The inputs at pins 2 and 3 also have certain limitations that must be respected for good results. As we previously saw, the relationship between the input voltage and the output current is exponential and once the input reaches 100 mV any further increase will have no effect on the output current. Obviously, then, the input must be limited to less than 100 mV (or 200-mV peak-to-peak) for any sort of normal amplifier-response. But for true linear-response, the input voltage must be limited even more—a maximum value of 10 mV (20-mV peak-to-peak) is usually best. There is a trade-off here too, however, as the lower the input voltage, the lower the signal-to-noise ratio. Thus, keeping the inputs at the high end of the linear range—as close to 10 mV as possible—is desirable.

Let's now consider the supply voltage. The 3080 will work well with any power supply between ± 2 volts and ± 18 volts. Those high and low limits are extremes; best results are obtained with voltages that are somewhat between those. In many modern designs, a bipolar 15-volt supply is used, and that seems about right.

Before we move on, let's consider two other points. First of all, pin 5, the control-current input, is usually at a potential that is about one diode drop above the negative supply-voltage. Thus, if a bipolar 15-volt supply is used, the potential at pin 5 is -14.4 volts. When calculating resistor values for that input, be sure to take the negative potential into account.

Secondly, even though the 3080 is an uncompensated-type op-amp, compensation is not usually needed since most applications use an open-loop design. Compensation is only needed when negative feedback is introduced. And simplifying things still farther, the two most common negative-feedback applications for the 3080, the voltage-controlled lowpass filter and the sample-and-hold, already use

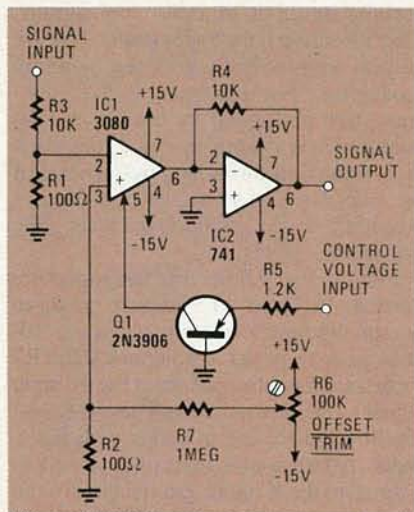


FIG. 5—THIS VOLTAGE-CONTROLLED AMPLIFIER uses just two IC's and a transistor. Though simple, this circuit works surprisingly well.

capacitors in their designs. Thus no additional compensation is needed.

Of course, there is much more to working with the 3080, but that can be picked up with experience. For now, the rules we've presented are all that you need to begin designing. Let's see how to use them in practice.

Some practical circuits

Figure 5 shows a common 3080 application, a voltage-controlled amplifier, (VCA). That circuit is common nowadays, and shows up in everything from noise-reduction units and computerized recording-studio mixing consoles to electronic music-synthesizers. (See the May, 1983 **Radio-Electronics** for a discussion of how VCA's are used in such synthesizers.) We'll examine that circuit first because it involves a very straightforward application of the design formulas and constraints we've discussed.

Suppose that our VCA is going to process a signal with a peak amplitude of ± 1 volt. As we've said, however, the 3080 works best when the input-level is limited to 10 mV. Hence, resistors R1 and R3 are used to drop the voltage to that level. Since R1 is 100 ohms, a similar resistor, R2 is placed at the other input of the 3080. In theory the 3080 should now be properly balanced, and there should be no DC feedthrough. In practice, however, offsets can still occur and when those are modulated by the amplifier severe "thumps" will result. Therefore, trimmer potentiometer R6 is added to the circuit so that any offsets can be nulled out. To adjust that trimmer, modulate the control voltage input rapidly while watching the output on an oscilloscope. Adjust R6 for minimum DC-feedthrough.

It was seen above that I_{ABC} , fed to pin 5, should be no greater than $0.5 mA$ under most circumstances. Resistor R5 and transistor Q1 provide a linear current that

meets that requirement. At the maximum control-voltage of $+15$ volts, Ohm's law shows that R5 will conduct a current of about $0.5 mA$. (Remember, pin 5 is at -14.4 volts).

A 741 op-amp, IC2 is configured as a current-to-voltage converter and will provide a low-impedance output as well. To calculate the value for R4, we apply the general transconductance equation. We know that I_{ABC} is a maximum of $0.5 mA$, and we know that the input voltage is 10 mV (thanks to the attenuator—R1 and R3). Substituting those numbers into the transconductance equation yields an output current of $96 \mu A$. Now using Ohm's law, a value for R4 can be calculated. For unity gain, divide 1 volt (the original peak input-voltage) by $96 \mu A$ and the result is $10.4K$. Pick $10K$ as the nearest standard value.

That VCA, while very simple, works quite well. Perhaps its main fault is the non-linear response of the control input when the control voltage is small. A better circuit can easily be realized with the addition of a few parts. Such a circuit is shown in Fig. 6.

That circuit is actually a linear voltage-to-current converter. It will produce a current that is linearly dependent on the input voltage. In addition, since the transistor is within the feedback loop, a very precise response is guaranteed whether the control voltage is small or large. The design equation is:

$$I_{ABC} = \frac{V_{IN} (R1/R2)}{R2 \parallel R}$$

where $R2 \parallel R3$ is the parallel combination of R2 and R3.

In designing this circuit, you determine

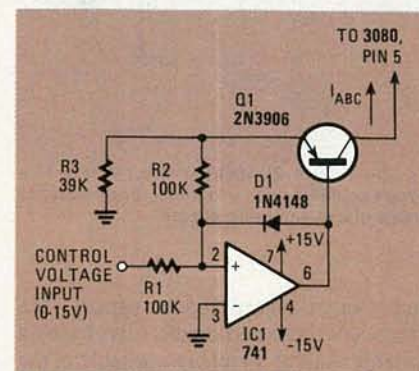


FIG. 6—FOR BEST RESULTS, this high-precision current source can be used with the circuit shown in Fig. 5. Its output is fed to pin 5 of the 3080.

the desired output-current and then select appropriate values for R1 and R2. Those three values are then used in the equation to determine the value of R3. The circuit, using the values shown, is set up to output a maximum current of $0.5 mA$ for a 15-volt input. That current is fed to pin 5 of the 3080. Diode D1 is included to protect the circuit from large negative input-

voltages.

The VCA just described is actually a two-quadrant multiplier. It is a multiplier in the sense that the input signal is multiplied by a certain gain; that gain is determined by the control-voltage input. And it has two-quadrant operation because the signal is allowed to be bipolar; the control voltage, though, can only be positive. For that reason, the graph of the product of the two inputs, which is the output of the circuit, can lie only in one or the other of two quadrants of the four-quadrant Cartesian plane so familiar to most of us from elementary algebra. A four-quadrant multiplier, on the other hand, allows both the control voltage and the signal to be bipolar. Thus the output of that circuit can fall in any of the four quadrants.

Four-quadrant multiplier

Perhaps one of the most interesting circuits to come along in quite a while is a four-quadrant multiplier that uses a single 3080 and a 741 op-amp. Figure 7 shows such a circuit; its simplicity is quite striking. Before describing the circuit in detail, a few things should be said about four-quadrant multiplier applications. As mentioned above, either input of the

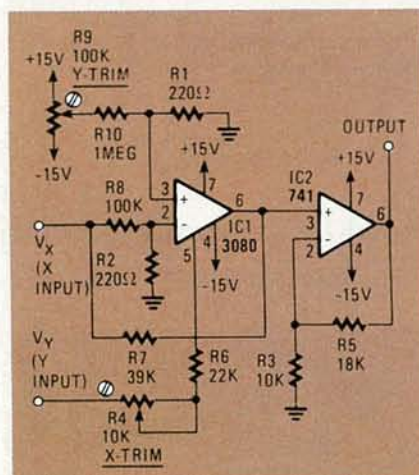


FIG. 7—A FOUR-QUADRANT MULTIPLIER. This circuit could be used in a music synthesizer to create chime and gong effects.

amplifier will accept bipolar signals. The product of those two signals (divided by a suitable scaling factor) is available at the output. But, most important, the polarity of the output will be correct. For example, if two negative signals are multiplied, the output will be positive. That, of course, makes such a circuit quite interesting for, among other things, analog-computer applications. (Actually the circuit given here is inverting; that means that the output will be the opposite of the true product. That can easily be corrected, if needed, by adding an additional inverting-stage).

Another place that the circuit is es-

pecially useful is in audio applications. That's because it produces sounds that are quite similar to those produced by a ring modulator. For example, if two sine-waves are multiplied by the device, the output will be a complex signal composed of the sum and difference frequencies of the two. Such a signal can be used in electronic music-synthesis to create gong and chime effects.

Refer to Fig. 7 now. The two inputs are labeled "X" and "Y" and are set up to accept bipolar 5-volt signals (i.e., 10-volts peak-to-peak). Resistors R8 and R2 form an attenuator and drop the X-input signal to the desired 10-mV level. Resistors R4 and R6 are in series with the Y input. To balance the multiplier you apply a signal to the X input, ground the Y input (0 volts), and then adjust R9 for minimum feedthrough. Then, reverse the procedure—apply a signal to the Y input, ground the X input, and adjust R4 for minimum feedthrough.

The output is converted to a voltage by IC2, a 741 op-amp. For more demanding applications, that IC should be changed to a BiFET-type op-amp, such as the LF351. Note that this stage not only buffers, but also scales the output suitably—since the circuit is set up to accept bipolar 5V signals the output is scaled so that it equals $-V_x V_y / 5$. That puts the output in the same range as the inputs.

One drawback of this circuit is that

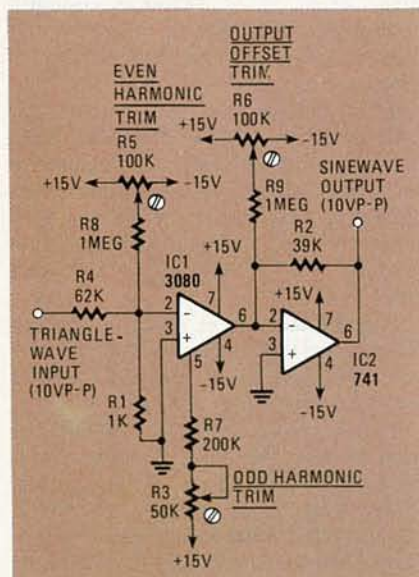


FIG. 8—IF A TRIANGLEWAVE is fed to the input of this circuit, the output will be a sinewave of the same amplitude. The total harmonic distortion will range from 2% to 4%.

only very-low-impedance input sources can be used. That is easy enough to correct, though, by buffering the two inputs. Additionally, the driving sources must be DC coupled. If those limitations are respected, however, the circuit performs very well and is far cheaper to build than any equivalent.

Trianglewave-to-sinewave converter

When we looked at the differential pair, we said that the input signal must always be at or below 10 mV for lowest distortion. A circuit that deliberately violates that rule is shown in Fig. 8.

In that circuit, which is a trianglewave-to-sinewave converter, a triangular wave with a value of 10-volts peak-to-peak is applied to the input at R4. Resistors R4 and R1 drop the voltage to about 160-mV peak-to-peak, which is applied to the 3080. Resistor R5 is used to trim the symmetry, which reduces the even-order harmonics. Resistors R7 and R3 form the current source for the 3080, and adjusting R3 has the effect of rounding or flattening the output; the result is that the odd harmonics are reduced. By adjusting R5 and R3, a very close approximation of a sine-wave can be obtained. The total harmonic distortion of the circuit will typically range from 2% to 4%. Resistor R6 is used to adjust the output offset.


The output of this circuit will be a sine-wave with the same amplitude as the input triangular wave. An important thing to note about the circuit is that it is non-reactive—it uses no capacitors or inductors. Thus it will work over a wide range of frequencies.

As this article has shown, the 3080 operational transconductance amplifier is not only versatile, but quite easy to work with. The equations we've presented, and Ohm's law, are really all it takes to get circuits using that device up and running. Obviously there are many refinements that can be made—correcting for temperature effects, for instance—but they can be tackled later on when you've had more experience with the device. **R-E**



BUILD THIS

DIGITAL VOLTMETER

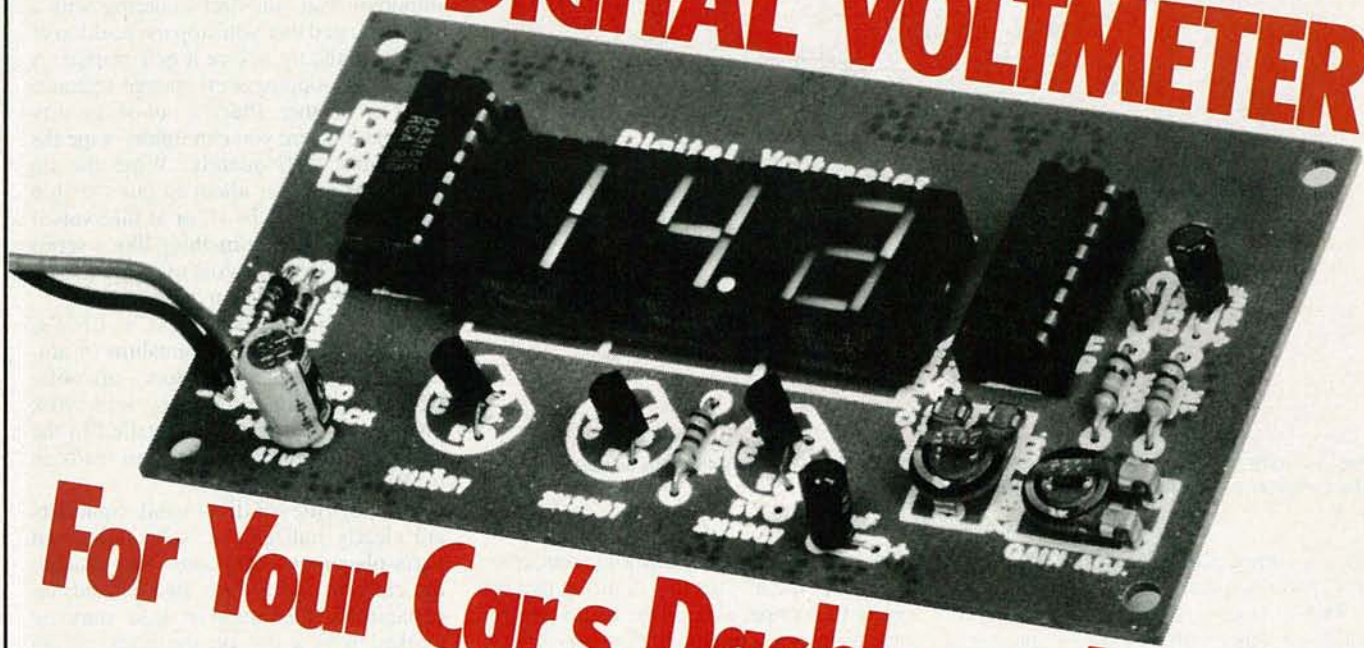

For Your Car's Dashboard

FRED L. YOUNG, SR. and FRED L. YOUNG, JR.

Keep an eye on the condition of your car's electrical system with this 3-digit digital voltmeter. Even if you're just a beginner in electronics, you can easily assemble it.

MOST CARS THESE DAYS DON'T HAVE gauges or meters on their dashboards—they have "idiot lights" instead. They're great for telling you when something has gone wrong, but they do very little to warn you when something is *about to* go wrong. What's more, even if you are one of the lucky ones and your car does have gauges, their accuracy is not the best. A device with a digital readout would be much more satisfactory in many cases and easier to read as well.

The digital voltmeter described here can be installed in your car (or boat, or truck) to give you constant and accurate (to a tenth of a volt) information about the state of your battery. It is equally useful in electrically powered vehicles like golf carts and electric service-trucks (forklifts, baggage carts, etc.). While most of the latter do have meters, this voltmeter will prove to be more accurate.

The meter is very simple to build—it has only three IC's, three capacitors, five resistors, three transistors (and, of course, three LED's)—and for that reason makes an excellent project for the electronics novice who wants to "get his feet wet." Because it may be your first project, we'll go into the details of construction a little more deeply than we usually do in **Radio-Electronics**.

How it works

Figure 1 is a schematic of the entire voltmeter. The LM340T-5 regulator, IC1, has an output of five volts, which is ideal for the other two IC's in the circuit and for the LED displays. The input to the regulator is protected by diodes D1 and D2, and by a 47 μ F capacitor, C1. Those components minimize positive- or negative-going voltage spikes that may be caused by switching inductive devices like the windshield wipers, air conditioning, electric windows, etc., on or off. A 10 μ F capacitor, C2, at IC1's output damps any noise or transients that may appear on the five-volt output line and makes the regulator a very stable voltage source, which is critical for accurate readings.

The heart of the voltmeter circuit is IC2, a CA3162E dual-slope, dual-speed, A/D (Analog-to-Digital) converter that reads the battery voltage and converts it into a BCD (Binary-Coded Decimal) digital number. That number appears at pins 2, 1, 15, and 16 of the IC and is fed to pins 7, 1, 2, and 6, respectively, of IC3, a CA3161E BCD 7-segment decoder/driver that drives the three FND507 seven-segment LED numeric displays (DISP1-DISP3).

The CA3161E deserves a little further

attention. It performs several functions that, in the past, would have required the circuit to contain a number of additional components. For one thing, it limits the current that is drawn by the displays. Without current-limiting, the LED's would tend to overheat and burn out and, in the past, current-limiting resistors would have been required to prevent that from happening; the CA3161E eliminates the need for them. That IC also allows the displays to be multiplexed; that means that only one LED is on at a time—although they're switched on and off so rapidly through driver transistors Q1-Q3 that they all seem to be on simultaneously. Multiplexing the displays saves a lot of power, and the total current needed to operate the voltmeter is 160 mA or less.

The maximum voltage differential allowed between the input pins on IC2—pins 10 and 11—is 999 mV. Therefore, resistors R1 and R2, whose values have the ratio 100:1, are used to form an attenuation network with a factor of 100. If 13.8 volts are applied to the attenuator network, the voltage difference between the pin 10 (which is grounded) and that at pin 11 (the input pin) will be, according to Ohm's law, 136.6 mV. What we want it to be, though, is 138.0 mV. That differ-

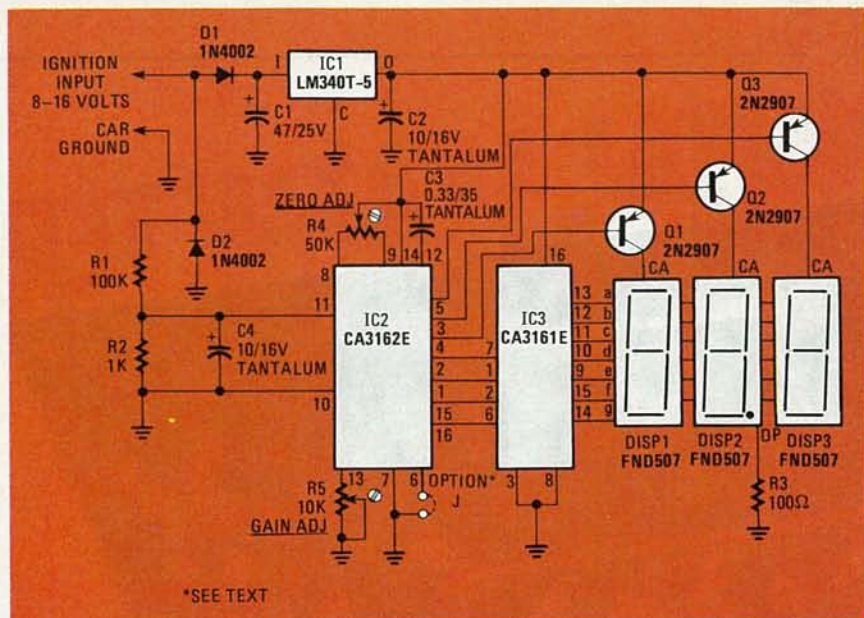


FIG. 1—NOTE THE POINTS MARKED "OPTION" at pins 6 and 7 of IC2; they allow the sampling rate of the converter A/D to be changed. See the text for details.

ence is compensated for by the GAIN ADJUST potentiometer, R5.

The ZERO ADJUST potentiometer, R4, is used—together with a 0.33 µF capacitor, C3—to generate the correct internal ramp-voltage (needed for the dual-slope A/D conversion process) for IC2. We'll discuss the adjustment of both potentiometers later.

Finally, there are two different conversion rates (the rate at which the A/D converter samples the analog input and changes it to digital form) available from IC2. Tying its pin 6 to five volts will produce a conversion rate of 96 (samples) per second. That speed, though, will cause the last digit of the display to become a blur, so we use the other conversion rate—four samples-per-second—by tying pin 6 to ground. The point at which the choice of conversion rates is made is marked "OPTION" in the schematic.

Construction tips

The voltmeter is so easy to build that the process really needs little description. Instead, we'll assume that this is the first circuit you've ever put together, and give you lots of helpful information. Even if you're an experienced constructor, you may find something of interest here, so don't skip this section!

While an etched and drilled circuit board is available from the source indicated in the Parts List, you may decide to go all the way and make your own (the foil pattern is reproduced in Fig. 2). Techniques for making your own PC boards were discussed in detail in the December 1982–February 1983 issues of *Radio-Electronics*. If the board's foil traces are naked copper, there is the possibility that some oxidation may have taken place if the board was not used immediately, and the copper may be difficult to solder to. If

that's the case (or even as a preventative measure) use a clean *dry* scouring pad to wipe the copper side of the board gently and bring it to a relatively high polish. *Do not* try to clean it up using a buffing wheel! Then wipe it off with a soft cloth. It should then be as solderable as a board that's just been produced.

The choice of a soldering iron is very important. It should be low power—about 27 watts—and should be used sparingly. Keep it in contact with the points to be soldered only long enough to do the job; if you apply too much heat to a PC board the foil is apt to separate from the board. Use as fine a tip as you can get—that not only keeps heat-buildup down, but lessens the possibility of your creating solder blobs and bridges between adjacent foil points that were meant to be isolated. A fine (thin) rosin-core solder will also help keep your work neat. Use only as much solder as is needed to "wet" the connection; don't make big

blobs.

A final word about soldering: keep the tip of the iron clean. A clean tip is a requirement for precision soldering. As your work progresses, solder will usually accumulate on the tip of the iron and it is important that you start soldering with a clean tip, and that you stop the buildup of solder on the tip before it gets started. A damp (not sopping wet) sponge makes a good tip cleaner. Place it out of the way on a plate where you can lightly wipe the tip against it frequently. Wipe the tip whenever you are about to put the iron down after using the it, or at intervals if you are soldering something like a series of IC pins. And, of course, wipe the tip well at the end of your work session.

Many components—like IC's, LED's, diodes, transistors, and tantalum or aluminum electrolytic capacitors—are polarized. That means that they will work properly only if they are installed in the circuit so that the correct pins or leads go to the appropriate points.

The polarities of diodes and capacitors are clearly indicated in schematics and parts-placement diagrams. On diodes, the cathode end is indicated a band; on capacitors, the positive lead may be marked with a dot on the body of the capacitor, or in another fashion. The September 1982 and November 1982 issues of *Radio-Electronics* contained a lot of valuable information on the various types of electronic components; you might want to take a look at them.

Integrated circuits like the ones used in the voltmeter come in DIP (Dual In-line Pin) packages. The pin-1 end of the IC may be marked with a notch, a dot (usually placed next to pin 1), or both. Many IC sockets—which you should use, by the way, in case you have to remove an IC for some reason—also have their pin-1 ends marked, even though the sockets themselves are not polarized. Those markings help you to remember which way the IC is to be installed.

Finally, a word of caution about IC's. Many of them—including the CA3161E

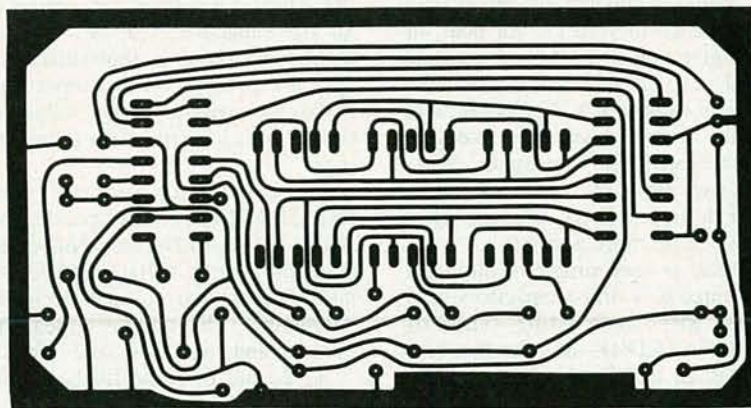


FIG. 2—FOIL PATTERN FOR ETCHING the voltmeter PC-board. A ready-to-use board is available from the supplier indicated in the Parts List.

and CA3162E—can be damaged by static electricity. Do not wear clothing made of synthetic fibers when working with such devices (although, once they've been installed on the PC board, they're relatively safe from harm and you can pretty much wear what you like). If static electricity is a problem for you, handle the IC's under humid conditions. A good solution to the problem is to steam up your bathroom by running the hot water in the shower for a few minutes and then installing the IC's in their sockets in that room while the air is still damp. That trick is especially useful in winter.

Construction

A red plastic filter will make the displays of the voltmeter easier to read under difficult lighting conditions. Use a piece of plastic 1/8-inch thick and a little larger than the PC board. Drill a hole in each corner of the PC board, and drill matching holes in the plastic. To avoid cracking the fragile material, drill small pilot-holes first, and then carefully enlarge them. Be careful not to scratch the plastic. Then set the plastic aside temporarily and, with the advice just given in mind, proceed to "stuff" the PC board.

Use Fig. 3, the parts-placement diagram, to guide you. Install the IC sockets first, and then the resistors, diodes, and capacitors. Don't forget the "OPTION" jumper, which can be a piece of leftover resistor lead. Save the larger parts, like the potentiometers, for last. The 47 μ F capacitor, C1, can be mounted on the foil side of the board if you wish to conserve height between the plastic filter and the voltmeter board.

When you install the LED's, which can be soldered directly to the board, be certain that you mount them with the side with the ridges at the top (if you look closely, you'll be able to see the decimal point of the display at the lower right). Solder only two pins, at opposite corners

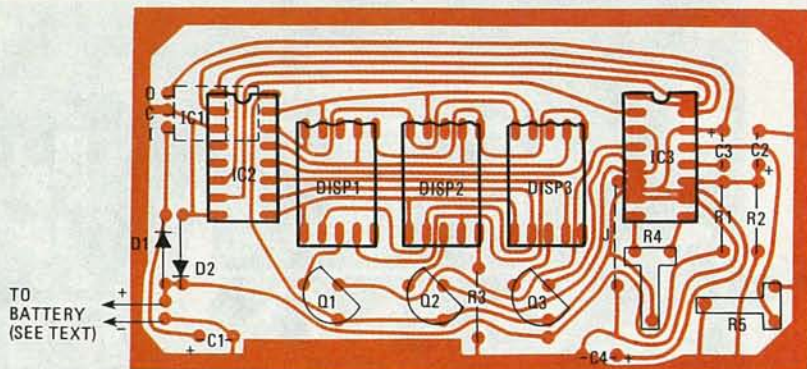


FIG. 3—NOTE THE RIDGES AT THE TOPS of the display LED's. The devices must be installed with the ridges in that position.

of each device, first. That will allow you to reposition the displays easily if you find that they're in at an angle.

The five-volt regulator, IC1, should be mounted on the foil side of the board as shown in Fig. 4. Bend the leads carefully as shown so they arch backwards. The reason for installing the regulator on the back of the board is, again, to conserve height.

Connect about three feet each of red and black 22-gauge wire to the "IGNITION" and "GROUND" pads of the board, respectively. That will prevent confusion later on in connecting the voltmeter to the vehicle.

Finally, *do not* install IC1 and IC2 in their sockets until you have carefully inspected the board for poor solder-connections, solder bridges, proper component-orientation, and anything else that you might conceivably have done wrong (*anyone*—even you—can make a mistake). Then verify that the supply voltages to the IC sockets are correct. If you temporarily connect the red and black wires to a 12-volt-DC source, you should measure five volts at pin 14 of the socket for IC2 and at pin 16 of the socket for IC3. Pins 7 and 8, respectively,

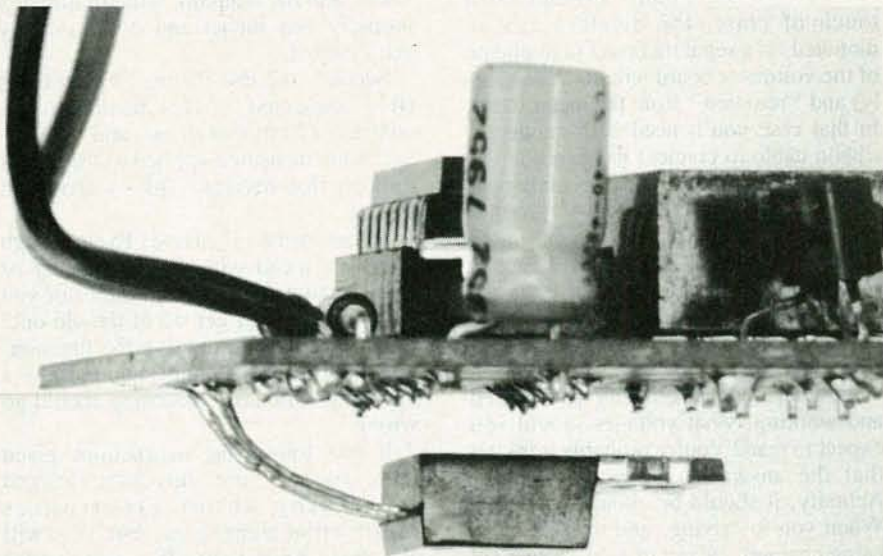


FIG. 4—THE FIVE-VOLT regulator is mounted on the bottom of the PC board, exactly as shown.

PARTS LIST

All resistors 5%, 1/4 watt unless otherwise indicated

- R1—100,000 ohms
- R2—1000 ohms
- R3—100 ohms
- R4—50,000 ohms, trimmer potentiometer
- R5—10,000 ohms, trimmer potentiometer

Capacitors

- C1—47 μ F, 25 volts, electrolytic (axial leads)
- C2, C4—10 μ F, 16 volts, tantalum or electrolytic (axial leads)
- C3—0.33 μ F, 35 volts, tantalum

Semiconductors

- IC1—LM340T-5 (7805) five-volt regulator, tab type
- IC2—CA3162E dual-speed, dual-slope A/D converter
- IC3—CA3161E BCD 7-segment LED decoder/driver
- Q1—Q3—2N2907 or similar PNP transistor
- DISP1—DISP3—FND507 or FND510 7-segment LED
- D1, D2—1N4002

Miscellaneous: PC board, IC sockets, wire, red plastic filter, mounting hardware, etc.

The following are available from Digital World, PO Box 5508, Augusta, GA 30906: PC board only, \$7.50; PC board with schematic, \$8.50; CA3161E and CA3162E, \$12.00; PC board with all three IC's and with IC sockets, \$20.00; kit of all parts (no filter, chassis or solder) \$30.00. The prices of the *first two items only* include postage and handling costs within the continental U.S. and Canada. For all other items add \$2.00 within the continental U.S.; \$3.00 all other U.S., APO, and FPO. Canadians please use U.S. postal money order. Other countries write for prices and shipping costs. Please allow 4-6 weeks for delivery.

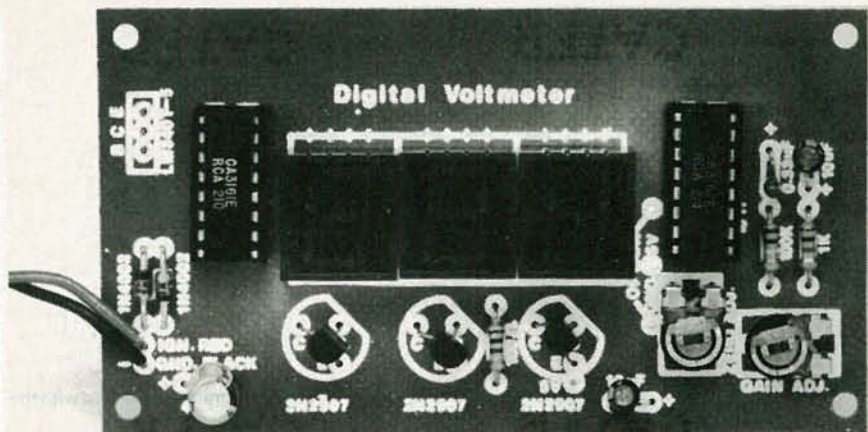


FIG. 5—THIS IS WHAT the completed voltmeter should look like prior to installation.

of those sockets should be at ground potential; you should measure no voltage there.

If your voltage readings are correct, you can disconnect the board from its temporary power supply and install the two remaining IC's. If your measurements differed from those indicated, recheck the board carefully for errors. The completed board should look similar to the one shown in Fig. 5, assuming, of course, that you used the same types of capacitors and other parts.

Calibration

Connect a known, accurate, voltage source to the red and black input wires of the voltmeter. If you already have an accurate meter, connect it in parallel with the one you're calibrating to act as a double check. The calibration voltage should be between 10 and 16 volts; 13.8 volts is recommended. Do not attempt to use a source of less than 10 volts, for it may result in inaccuracies.

To set the ZERO ADJUST trimmer potentiometer, R4, temporarily ground pins 10 and 11 of IC2 to the ground foil of the PC board. Then, very carefully adjust the pot until the display reads "00.0." (You'll need a very fine screwdriver—and some patience—for this.) You can then unground the two IC pins.

Adjust the GAIN ADJUST trimmer potentiometer, R5, until the display indicates the exact value of the calibration voltage being applied. That's all there is to it.

Troubleshooting

If the voltmeter did not light up for the calibration procedure, first make sure that potentiometer R4 is centered. If there is still no response, double check your work once again for solder bridges, unsoldered connections, components installed incorrectly, etc. *Carefully* remove the IC's from their sockets and make sure that none of their pins were bent under.

If the displays are dim, check the emitter and collector leads of transistors Q1-Q3; you might have mistakenly inserted the transistors backwards.

If a digit seems to be trying to display two numbers at the same time, its driver transistor may be defective.

If, after you've installed the meter, it doesn't work, make certain that the red and black wires are properly connected to the "tie in" point and to ground, respectively.

Installation

The first step in installing the meter is to mount the plastic filter in front of it. That can be done using 3/4-inch spacers, or by making spacers using 1 1/2-inch bolts and nuts. If you use the latter method, insert a bolt through the plastic and put a nut on the reverse side. Then put a second nut on the bolt, allowing 3/4-inch of space between it and the first nut. Do that at all four corners of the plastic. Next, insert the bolts through the holes drilled in the PC board, and secure them with four more nuts. Securing the plastic at all four corners gives the assembly greater strength and minimizes the potential for the plastic's cracking from vibration.

The voltmeter does not require a special cabinet or chassis. It can be mounted in a recess in the dashboard of the vehicle and the edges of the mounting hole covered with a frame, or bezel. For a touch of class, the displays can be mounted on a separate board (a duplicate of the voltmeter board will do quite nicely) and "remoted" from the meter itself. In that case you'll need a 14-conductor ribbon cable to connect the two boards.

The black wire should be securely connected to the vehicle's chassis ground. The red wire should go to a point in the vehicle's electrical system that is active only when the ignition switch is turned on; a good place for that connection is at the same fuse terminal to which the radio is connected.

Now that your voltmeter is installed and working, what voltages should you expect to read? You're probably thinking that the answer is 12 volts. Wrong! Actually, it should be about 12.6 volts. When you're driving, and the battery is being charged, expect to read about 13.8 volts. Any readings above 17 volts or

below 11 volts (such as when cranking the starter) indicate trouble!

A possible problem

It is possible that the display-multiplexing circuit will interfere with the operation of an AM radio (especially if the meter and the radio are connected to the same point) by generating some radio-frequency interference that will cause the radio to "whine."

Some radios are more sensitive to that problem than others. There are several solutions to that problem, should it occur.

First, try using a "tie in" point other than the one used by the radio. Just remember that it should be active only when the ignition switch is on.

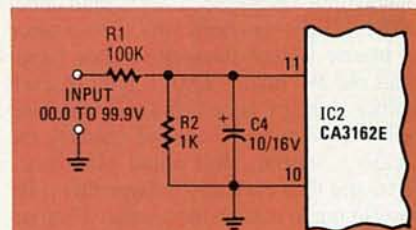


FIG. 6—USING RESISTOR R1 as the input allows you to measure up to 99.9 volts. See the text for precautions.

You can also try moving the meter away from the radio (or vice versa).

Finally, you can try shielding the voltmeter circuit in a metal box. That is usually very effective.

If you decided to "remote" the display from the rest of the meter circuit, wrap the connecting ribbon cable in aluminum foil, and connect the foil to ground. That is almost a "must" in applications where the two units will be separate.

Use with higher voltages

The voltmeter can be used to measure voltages up to 99.9 volts *provided that two conditions are met.*

First, the supply voltage to the board must be between 8 and 16 volts. Any lower, and the regulator will not function properly; any higher and it will quickly self-destruct.

Second, the end of the 100K resistor (R1) connected to D2 should be disconnected from that diode, and the voltage being measured applied to the circuit through that resistor. This is shown in Fig. 6.

A last word of advice: Even though your new meter will almost certainly be more accurate than the old indicator you were using, don't get rid of the old one! Keep it in place to monitor the functioning of the meter you built, and to act as a backup just in case something should go wrong.

If you follow the instructions given here, you will not only have learned something about electronics construction-techniques, but you will also have built yourself a very useful measurement instrument. **R-E**

Using LORAN-C for Time and


THE LORAN NAVIGATION SYSTEM OPERATES on two different frequencies, each with a different set of characteristics. Each frequency has its own Loran designation—Loran-A and Loran-C. Although Loran-C's primary purpose is for long-distance navigation, it has another important use. Because Loran stations have to maintain a high level of precision they can—if used properly—serve as extremely accurate frequency standards. In this article we'll be discussing how we can use Loran-C signals for such applications as calibrating a frequency standard or a frequency-counter timebase.

Before we get into the details of the Loran-C system, let's take a brief look at how Loran-C signals can be used for calibration purposes. The Loran-C signals are observed on an oscilloscope that is externally triggered by a special pulse generator. (The pulse generator is quite simple, and we will provide construction details for it shortly.) The pulse generator is driven by the frequency standard you wish to calibrate. (Details for calibrating a 1-MHz frequency standard will be given, but other frequency-standards can also be calibrated using this technique.) The stability of the frequency standard can be obtained by determining the time it takes the display of the Loran-C signal to drift a given distance across the screen. Using this technique you can calibrate a 1-MHz oscillator to better than 0.001 Hz.

The Loran-C navigation system

Loran-C signals are broadcast on a frequency of 100 kHz with a 20-kHz bandwidth (from 90 to 110 kHz). Because of their low frequency, Loran-C signals tend to be ground waves—they follow the earth's curvature. The signals are usually very stable because they are not affected by the ionosphere. But how are they used for navigation?

Loran signals are sent from a *chain* (usually three to five) of stations. One station in each chain is the *master* and the others are *slaves*. The master station transmits groups of pulses that are received by the slave stations. Each slave station transmits similar groups of pulses, and adds a fixed time-delay between the groups of pulses transmitted by the master and its own pulse groups. A Loran-C receiver receives both pulse groups and

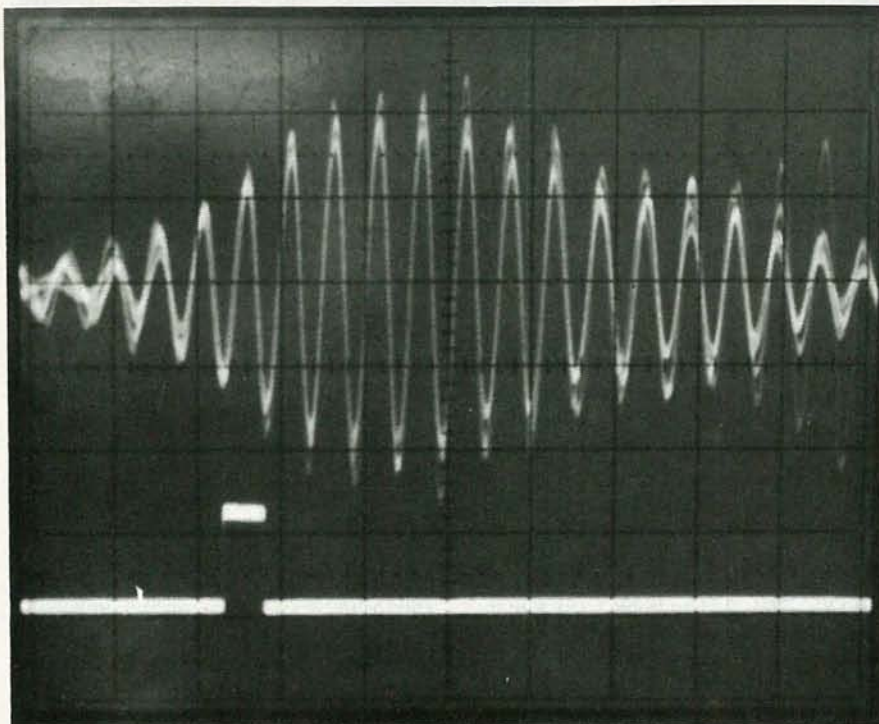

Frequency Calibration

Here's a look at the Loran-C navigation system—what it is and how it works. We will also discover how Loran-C signals can be used as frequency standards for calibrating oscillators.

R.W. BURHANS

calculates the time difference between them. It is that time difference that is used to establish a line of position that is used for navigation.

If (at the receiving end) the time difference between the received signals were to equal the original delay added by the slave station, the receiver would be somewhere along a straight line equidistant from both the slave and the master transmitters. If the time difference were to deviate from that fixed time-delay, the

receiver would be somewhere along a particular hyperbola. (A hyperbola is a curve where the *difference* of the distances from any point on the curve to two fixed points is a constant.)

As shown in Fig. 1., a second pair of transmitters (the same master but a different slave) can be used to construct a second hyperbola. The intersection of the two hyperbolas is the receiving point. To be useful for navigation, at least three Loran stations in a chain must be re-

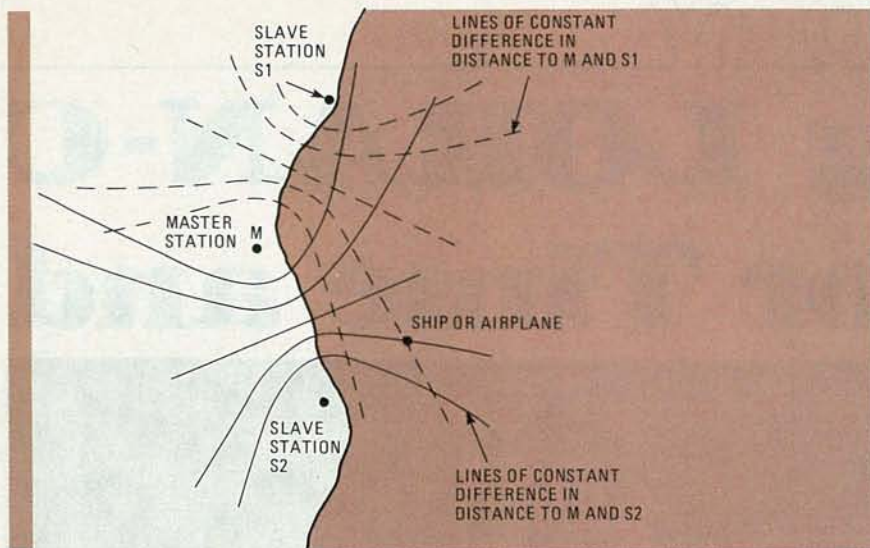


FIG. 1—AT LEAST THREE Loran stations must be received to be useful for navigation. Each master-slave pair is used to establish a particular hyperbola of constant time-differences. The intersection of the hyperbolas gives the receiver location.

ceived. However, for time- and frequency-calibration applications—which is what we are interested in—only one Loran station needs to be received.

One source of more detailed information on the Loran-C navigation system, is the *Loran-C Handbook*. For information on its price and availability, write the Superintendent of Documents, U.S. Government Printing Office, Washington D.C. 20402. The book's stock number is 050-012-00171-5.

Loran-C receivers

The sophistication of modern Loran-C receivers is now very high—some will directly compute your latitude, longitude, range, and bearing. The cost of those receivers is also high, typically \$5000 for marine systems and \$10,000 for airborne receivers. The navigational precision that can be obtained varies with the chain's geometry and distance, but it can be as good as ± 50 feet when differential and propagation corrections are taken into account.

A complete Loran-C navigation receiver usually consists of the main components shown in Fig. 2: an active-antenna coupler, an RF sensor, a sensor processor, a navigation processor, and finally a data-display device. The last three are microprocessor controlled.

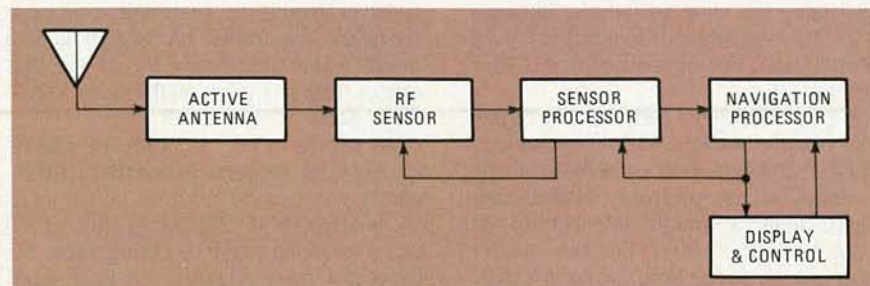


FIG. 2—BLOCK DIAGRAM of a Loran-C navigation receiver.

The Loran-C signal

Before we can understand how a Loran-C signal is used by the receivers, and how we can use it for frequency calibration, we have to look at its characteristics. A Loran-C signal consists of pulses. An ideal pulse is shown in Fig. 3. Each Loran-C transmitter transmits a series of 8-pulse groups with the pulses spaced 1 millisecond apart. An extra (ninth) pulse (sent two milliseconds after the 8-pulse sequence) is used to identify the master station. (The master station is the beginning of the chain's sequence.) The sequence is repeated at a certain GRI (Group Repetition Interval) that identifies the chain. Figure 4 shows the relative amplitudes of the pulse envelopes as received from one Loran-C chain (Northeast US: the repetition period is 99,600 μ s). Each vertical line in the figure represents one pulse. Note that the relative amplitudes as well as the time separations between the groups will vary depending on the receiver location. (Of course if that weren't true, Loran would not be very useful for navigation.)

An additional characteristic that we should point out, although it is not shown in Fig. 4, is that the Loran signals are phase coded. That allows Loran receivers to automatically identify master and secondary stations; to have an automatic

search mode, and to reject multi-hop sky waves.

Sky waves

One problem encountered when using Loran-C is that the ground waves are often contaminated by sky waves. (Remember—one of the reasons that Loran can be used for great accuracy is due to the stability of ground waves.) So that the signal at the receiver will not be contaminated by the arrival of sky waves, a signal with a fast risetime is used. That allows the pulse to build up to its maximum value at the receiver before the sky waves arrive. Also, the tail of one pulse should be low in amplitude when compared to the beginning of the next one so that the trailing sky waves will not contaminate the beginning of the next pulse. The limiting constraint on a signal's risetime is its bandwidth. (For example, a squarewave has a very fast risetime, but its bandwidth would be too large to be used by the Loran system.)

The pulse shape shown in Fig. 3 is used to reduce the problem of one pulse affecting the beginning of the next—the tails of the pulses are greatly attenuated (and the 20-kHz bandwidth constraint is still met.) The third cycle of the pulse (that's the one which is tracked by the receiver) will not be contaminated by sky-wave (or reflected) signals.

Because the transmitted signals have a relatively wide (20-kHz) bandwidth, ordinary communications receivers cannot do a good job of detecting Loran-C pulses, although some receivers with a 12-kHz bandwidth can do a reasonable job for long-term frequency calibration (where the local clock is kept running 24 hours a day).

As we mentioned previously, a Loran-C receiver is designed to detect a point on the signal (the third cycle) before the stronger sky waves have a chance to contaminate the envelope. That task is not easy to perform and there is still argument over the best way to detect the earlier, weak ground wave at long range when it has been contaminated with sky waves (which often have a peak level 20 dB greater than the ground wave). Because

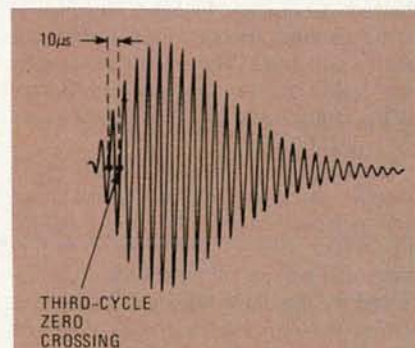


FIG. 3—IDEAL SHAPE of a 100-kHz Loran-C transmitted pulse. Note how the trailing edge is attenuated so that the trailing sky waves will not interfere with the next pulse.

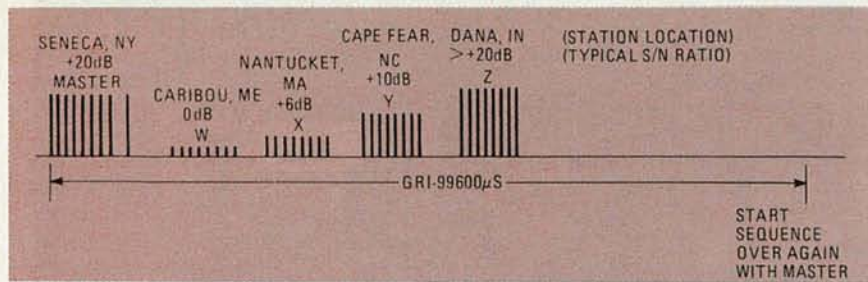


FIG. 4—RELATIVE ENVELOPE AMPLITUDES of a Loran-C chain as received in the midwestern US. Note the "extra" pulse that identifies the master.

the sky-wave signals are not stable—they vary considerably in amplitude and risetime—large errors will be produced if the receiver tracks them.

Another problem with Loran receivers is that any filtering will delay the risetime of the signal so that, with many receivers, a point later than the ideal third cycle is tracked. However, as long as that point is the same for all signals, strong or weak, and is chosen to precede the sky wave's reaching an appreciable amplitude, then the receiver can still operate satisfactorily. Let's look at how the third cycle of the Loran-C pulse is detected.

Third-cycle detection

A theoretical way of detecting a point on the pulse shown in Fig. 3 is to generate the second derivative of the pulse's envelope shape. The resultant envelope has a zero crossing at about $35 \mu\text{s}$. The problem in this case is that the envelope generator (with the differentiators) ends up with an extremely wide bandwidth—that adds a lot of noise to the system.

Another way to detect the third cycle is to produce a delay-and-add circuit. Such a circuit delays the signal $5 \mu\text{s}$ (180°) and then algebraically adds the delayed signal to the original (with a multiplying constant) to produce a phase reversal at about

the $30\text{-}\mu\text{s}$ point. A simple implementation of a delay-and-add network—and the effect it has on the Loran-C signal—is shown in Fig. 5.

If the output *pinched-balloon* shape of the delay-and-add network is fed to a *hard limiter*, then the result, as shown in Fig. 5, is a rectangular waveform where the phase-reversal point (the third-cycle point) has a gap. All the receiver designer then has to do is to devise some machine-language software to track that gap for the stations of a given chain. That is, of course, no easy task. But that's what is done in the sensor processor of many Loran-C receivers.

Another problem with Loran reception and third-cycle detection is that the conductivities of the earth and of seawater are different. That can cause the group velocity and the phase velocity of the signal to differ, producing an envelope-to-cycle difference (ECD) error up to several microseconds (depending on the terrain and the distance). (Some very precise Loran-C receivers can use that to an advantage. Precision measurements of the amplitude and phase of Loran-C signals made while flying at low altitudes can yield information on the ground's contours.)

Still another problem associated with Loran-C receivers is the fact that strong interference on frequencies like 88 kHz or 116 kHz can produce errors in the navigation data. Fixed, tuned traps—that are designed for particular coverage areas where there are interfering signals—are often found in Loran-C receivers.

RF filtering

A signal takes a finite time to pass through a filter. That time, called a delay, is a function of the signal's velocity. The signal's velocity is a function of its frequency. (For instance, the signal's velocity is lowest at the lower band-edge.) Thus, a filter can cause EDD (Envelope Delay Distortion).

The effect that a filter with narrow skirts has on the received signal is shown in Fig. 6. Here we have assumed a worst-case sky wave rising at about $30 \mu\text{s}$ after the start of the ground wave, and we have assumed that the peak amplitude of the sky wave is 20 dB greater than that of the ground wave.

The filter delays the Loran ground-wave signal (the envelope's zero crossing

occurs at a later time), but coincidentally, the strong sky-wave signal is also delayed. Unfortunately, however, the ground wave's third cycle (which we want to detect) is at -60 dB . Fortunately, though, even at the $50\text{-}\mu\text{s}$ point the desired pulse is some 30 dB greater than the sky-wave contamination.

A -30-dB contamination of the tracking point at $50 \mu\text{s}$ would result in a small error in the data. The data will contain additional error because the results are not as precise when the fifth cycle ($50\text{-}\mu\text{s}$ point) is tracked instead of the third cycle. However, as long as the sky-wave contamination is low enough, and the same point is tracked for all signals, then the error can be kept down to perhaps $0.1 \mu\text{s}$, even for a weak signal.

The effect of filtering and AGC in conventional communications receivers destroys most of the information in the Loran-C signal. However with a receiver such as the Yaesu FRG7700 in the WIDEBAND AM (12-kHz) mode, it is just possible to track the fifth cycle (which will be about the start of the pulse envelope as observed at the receiver's line-level output terminal). Noise blankers in communications receivers also destroy the pulse information because they are inherently timed to blank a pulse of the Loran-C shape and duration.

The envelope detector and simple GRI generator that we will discuss next are useful for experimental observations but are not well suited to precision navigation-receiver applications. The minimal equipment required for Loran-C observation is: a triggered-sweep oscilloscope, a frequency standard, a GRI generator (we'll discuss one), and a reasonably wideband AM receiver. If you do not have a suitable receiver available, you can use the Loran-C front end (or envelope detector) that we'll discuss next.

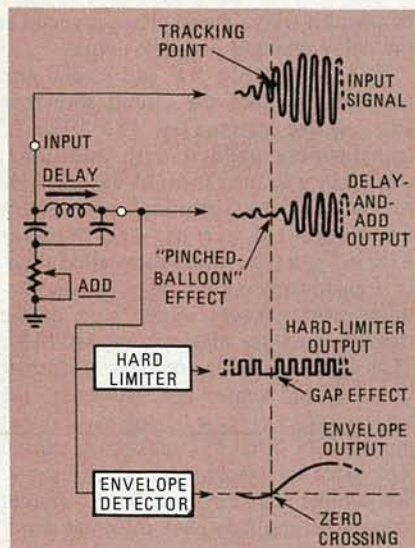


FIG. 5—A DELAY-AND-ADD network can be used to produce a pinched-balloon effect output, which is then used to produce an envelope with a zero crossing at the third cycle.

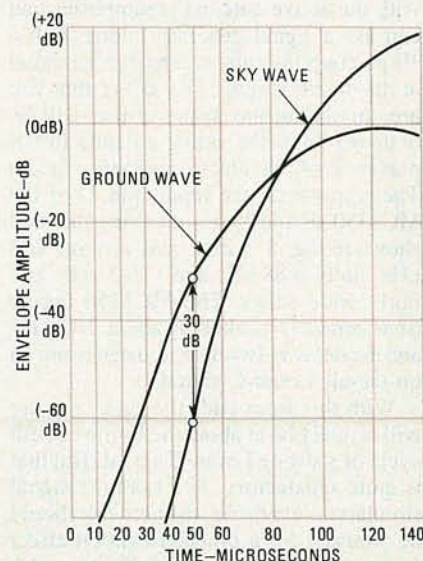


FIG. 6—A FILTER DELAYS both the Loran-C sky-wave and ground-wave signals, resulting in an zero crossing at about the fifth cycle.

RF envelope detector

For the experimenter who wishes only to study Loran-C or to use the signals as a frequency-calibration source, the envelope method (which detects the envelope zero-crossing as shown in Fig. 5) is simple and effective. A schematic of an envelope detector is shown in Fig. 7. The active-antenna preamplifier has been described previously (see the February, March, and April 1983 issues of **Radio-Electronics**). It uses a 1-meter whip with a 150-kHz lowpass filter at the antenna input. The "receiver" coupler is built as part of the Loran-C front end (Fig. 7) and consists of an 80-kHz highpass filter (instead of the 10-kHz filter used with the previous active-antenna circuits). The output of that coupler is fed to a network consisting of a 100-kHz impedance-matching transformer; to series T-notch traps tuned to 88 kHz and 115.3 kHz; and finally to an MC1350 RF amplifier. The sequence of matching and filtering at the input is an impedance step-up to the MC1350 RF stage such that there is a net voltage gain of 10 dB or more between the active antenna and the RF stage, which provides an added 60 dB of gain. The RF stage is operated with a manual control-voltage for the RF gain (or an external AGC system could be devised). The amplifier drives a transformer and a delay-and-add network. The delayed output and the undelayed (RF-amplifier) output are fed to an MC1357 FM detector. There, the hard-limited RF carrier is mixed or multiplied with the delay signal. That results in an envelope with the same amplitude and phase as that from the delay-and-add network. The zero crossing is adjusted for 40 to 50 μ s, and the ADD trimmer potentiometer is adjusted for a good null at the zero-crossing point. The actual pinched-balloon effect can be observed on a scope at pin 11 of the MC1357.

To align the RF transformers and traps with the active antenna preamplifier you can use a signal generator along with a 10-pF coupling capacitor to inject a signal at the antenna input. (By doing that you are simulating the response that will be obtained from the active antenna in the presence of an electromagnetic field.) The response at the input (pin 4) of the MC1350 should look something like that shown in Fig. 8, with a peak at about 103 kHz, nulls at 88 kHz and 115.3 kHz, and fairly wide skirts. The MC1350 output transformer is peaked at about 100 kHz and the delay network is adjusted using an on-the-air Loran-C signal.

With this front end, the zero crossing will actually be at about the fourth or fifth cycle of a strong Loran-C signal. But that is quite satisfactory. If a Loran-C signal simulator is available, the network should be adjusted for a pinched-balloon effect (or zero crossing) at about 40 μ s.

The output from the limiter/detector drives a 3-pole 33-kHz lowpass filter (IC3

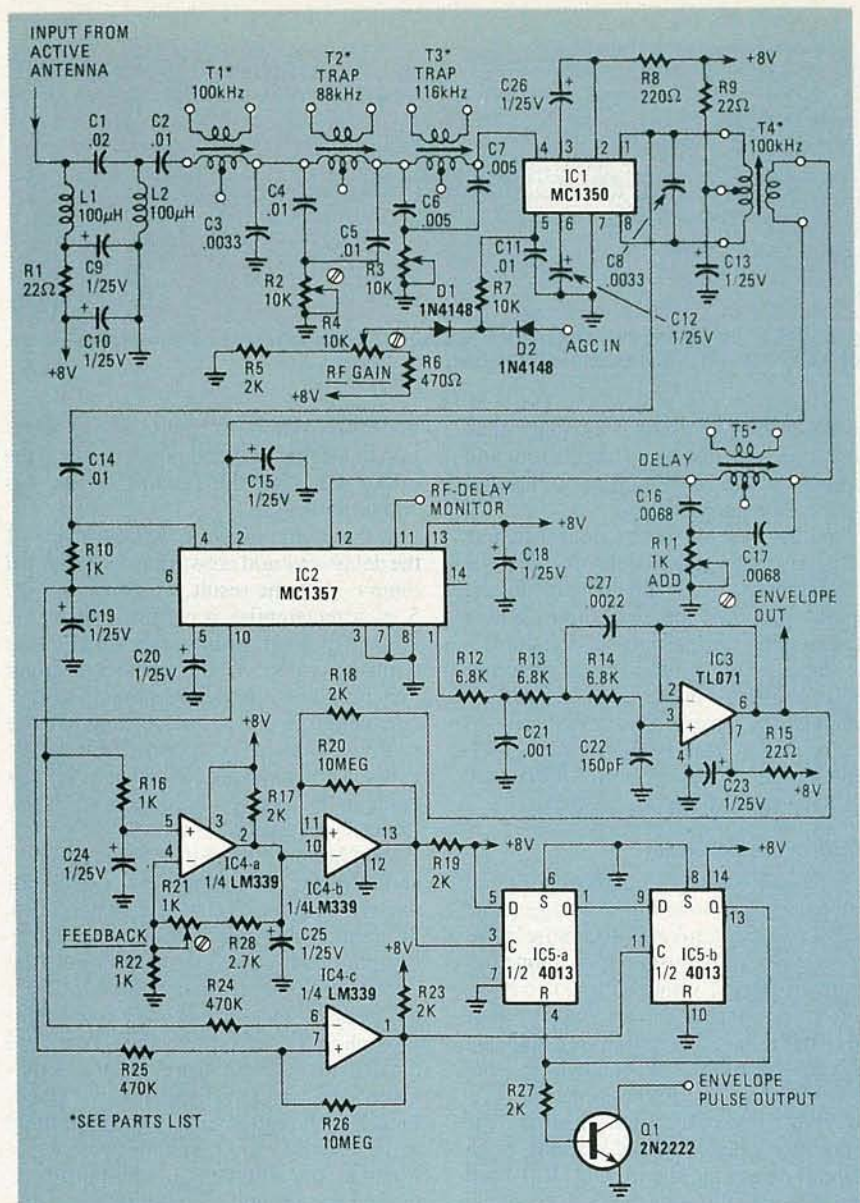


FIG. 7—THE LORAN-C FRONT END can be used to study Loran signals if a receiver with sufficient bandwidth is not available.

and its associated components) to generate a DC envelope that can be observed on an oscilloscope. The comparators and flip-flop provide a synchronized 10- μ s pulse at the envelope's zero-crossing point, but it is fairly noisy compared to observing the envelope at the analog lowpass-filter output. However, this output pulse for each Loran-C envelope is useful for further experimenting with microcomputer tracking-loops (where the bandwidth of the noise can be narrowed with memory-aided numerical techniques in software).

West-coast and foreign experimenters may wish to align the interference traps at some other frequencies. It is a good idea to keep the traps outside the 90 to 110 kHz region because they are not high enough in Q and could attenuate too much of the desired Loran-C signal. A lot of retuning—going back and forth over the adjustments of all of the tuned circuits—pays off in arriving at a reasonably wide

bandwidth with a sharp phase-reversal at the delay-and-add network output.

The adjustable RF inductors and transformers used the circuit shown in Fig. 7 are normally 455-kHz IF transformers padded with additional capacitance to tune them to the 100-kHz region. The particular transformers in this experimental circuit are Mouser 42IF303's, a type sometimes called a 3rd-IF transformer. Other types will sometimes work, except in the case of the transformer at the output of the MC1350. That's because the tap on the transformer is not a true center tap. However, the loading effect of the 0.01-mF capacitor at pin 4 of the MC1357 makes the output look like a balanced load for the RF stage. Some older transformers, from different manufacturers, may have different winding phases, so you may have to reverse the secondary connections to get everything operating properly. The phase of the smaller output-winding has to be such

PARTS LIST— ENVELOPE DETECTOR

All resistors 1/4 watt, 5% unless otherwise specified

R1, R9, R15—22 ohms
R2, R3, R4—10,000 ohms, trimmer potentiometer
R5, R17, R18, R19, R23, R27—2000 ohms
R6—470 ohms
R7—10,000 ohms
R8—220 ohms
R10, R16, R22—1000 ohms
R11, R21—1000 ohms, trimmer potentiometer
R12, R13, R14—6800 ohms
R20, R26—10 megohms
R24, R25—470,000 ohms
R28—2700 ohms

Capacitors

C1—0.02 μ F, polystyrene
C2—0.01 μ F, polystyrene
C3, C8—0.0033 μ F, ceramic disc
C4, C5—0.01 μ F polystyrene
C6, C7—0.005 μ F, polystyrene
C9, C10, C12, C13, C15, C18, C19, C20, C23—C26—1 μ F, 25 volts, tantalum
C11, C14—0.01 μ F, ceramic disc
C16, C17—0.0068 μ F, polystyrene
C21—0.001 μ F, ceramic disc
C22—150 pF, ceramic disc
C27—0.0022 μ F

Semiconductors

IC1—MC1350 video-IF amplifier
IC2—MC1357 sound-IF amplifier and quadrature detector
IC3—TL071 JFET-input op-amp
IC4—LM339 quad comparator
IC5—4013 dual D-type flip-flop
D1, D2—1N4148
Q1—2N2222 or similar NPN-type
T1—T5—455-kHz IF transformer, Mouser 42IF303 or equivalent
L1, L2—100- μ H RF choke

that a positive-going envelope is created at pin 1 of the MC1357 detector IC. The transformers come with a small 150-pF built-in capacitor across the main primary winding, but it can be ignored since it is very small compared to the 3300-pF capacitor required for resonance at 100 kHz.

The LM339 comparator (for the envelope pulse signal) generates a reference voltage from pin 6 of the MC1357. The small FEEDBACK trimmer potentiometer across the LM339 reference source is used to adjust the DC level of the pulse edge that is fed to the flip-flop. The reason for doing that is that the DC level is controlled by the MC1357, so that drift in the lowpass filter DC-level or in the comparator reference DC-level is self-compensating. The envelope 10- μ s-pulse output is intended to drive external logic, usually at a five-volt level. The power source for the whole RF front-end should be from an eight-volt regulated source (using a regulator such as an LM7808).

GRI pulse source

Practically every Loran-C experimenter needs a GRI generator that is capable of producing pulse-repetition intervals of

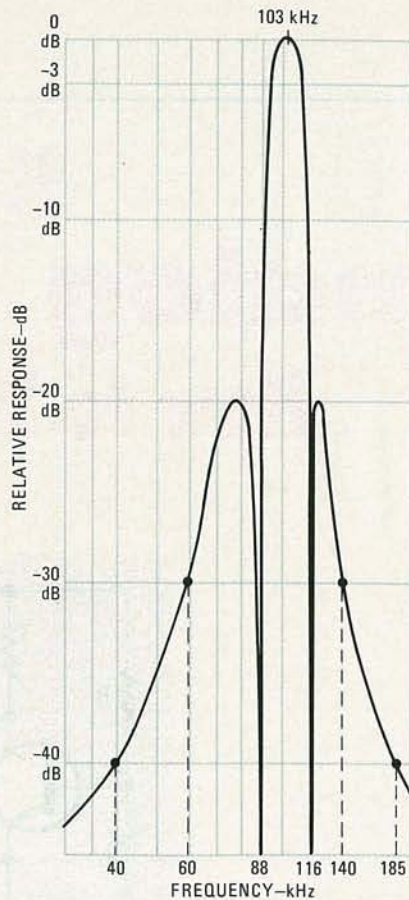


FIG. 8—THE RESPONSE AT THE INPUT to the RF stage (due to the filters) should look like this.

50,000 to 100,000 μ s. We'll discuss a simple generator that consists of a 4040 programmable ripple-counter and a dual decade-divider that is driven from a 1-

PARTS LIST— GRI PULSE SOURCE

All resistors 1/4-watt, 5% unless otherwise specified

R1—47,000 ohms
R2, R3—10,000 ohms

Capacitors

C1, C2—0.001 μ F

Semiconductors

IC1—4518 dual decade divider
IC2—12-stage binary ripple counter
IC3—quad 2-input nor gate
D1—D12—1N4148
S1—S3—Hexadecimal thumbwheel switch, 16 position BCD, Unimax SF-54 or equiv.

MHz crystal-controlled frequency standard. There are other methods for producing GRI pulses, but the three-IC circuit of Fig. 10 is about as simple as they come. (You could, for example, use only programmable decade-dividers. And you could use something other than a 1-MHz standard to drive the GRI generator and obtain the same results.) The circuit is programmed in hexadecimal notation for the GRI intervals as indicated in Table 1. That table lists the common designation for the GRI in 4-digit numbers (μ s/10), as is done on Loran charts and in United States Coast Guard data. The pulse generator that's shown in Fig. 9 produces a 10- μ s pulse that is used to synchronize your oscilloscope for observing Loran-C signals.

The programmable GRI-source allows the experimenter to stop the Loran-C signals on the scope trace and examine them in minute detail. That is also the basic


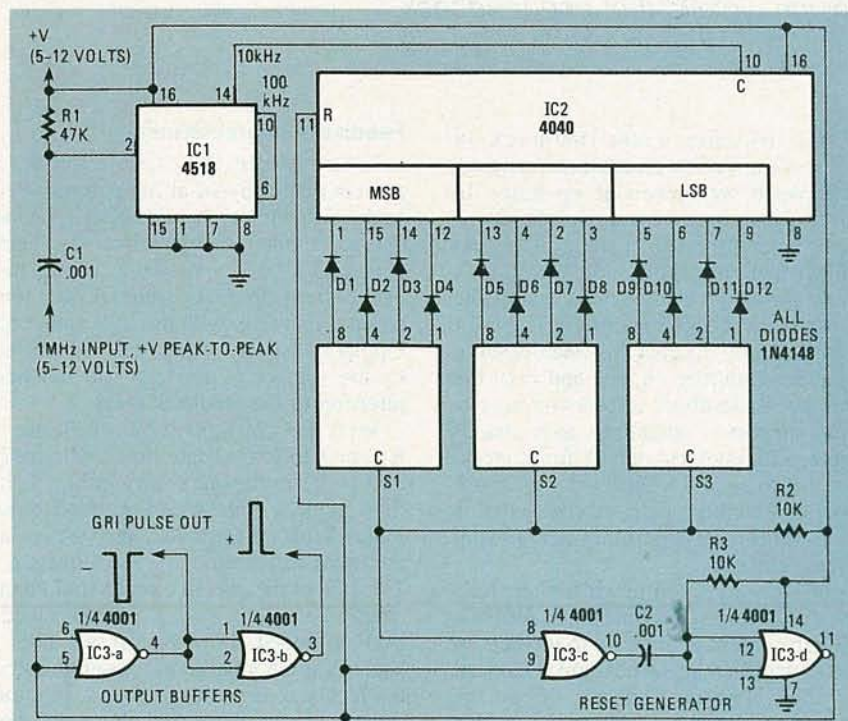


FIG. 9—THE GRI PULSE GENERATOR is used to stop the Loran signals on the scope trace so that they can be examined, and their drift measured. The drift indicates the stability of your frequency standard.


continued on page 92

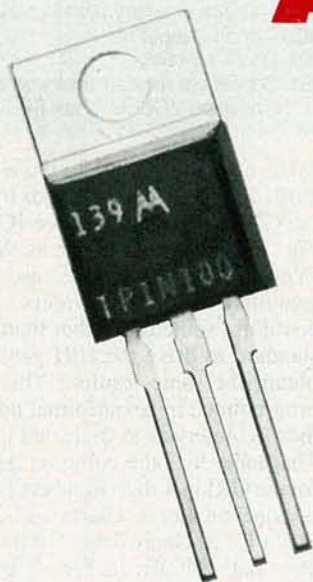How to Design Analog Circuits How to Use Feedback



MANNY HOROWITZ

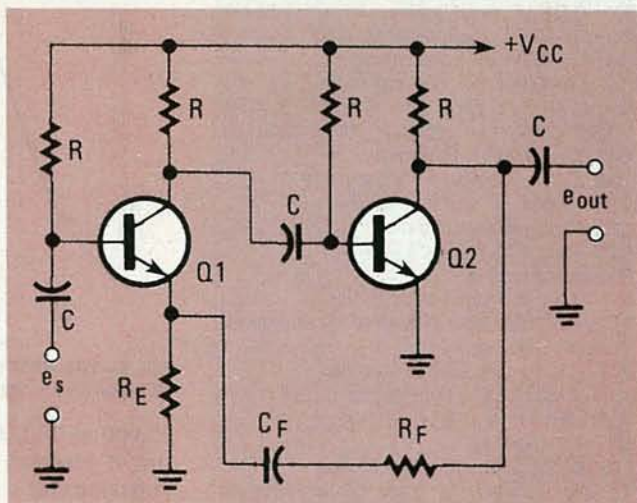This month we turn our attention to an in-depth look at both positive and negative feedback. We will discuss both the advantages and disadvantages of feedback and how to properly design circuits that use feedback.



WE'VE TOUCHED UPON FEEDBACK IN some of our earlier discussions, particularly when we looked at op-amps. In those discussions we saw that feedback was important in establishing many circuit characteristics; this month we'll look more closely at that topic. Among the things we'll see are the different types of feedback, how feedback is established in an audio-amplifier circuit, and how the presence of feedback affects various circuit parameters including gain, bandwidth, and input and output impedances. We'll also see how feedback can cause circuit instability, a characteristic that is undesirable in an audio amplifier but vital in an oscillator.

Before we get too much farther, let's clarify two terms. A signal that is fed back from the output of a circuit to its input in such a way that the overall gain is reduced is called *negative* feedback. If, on the other hand, the signal is fed back in such a way that the overall gain is increased, or so that it causes the circuit to go into oscillation, it is called *positive* feedback.

Feedback characteristics

In any circuit that uses feedback, a portion of the signal at the output is fed back to the input. The ratio e_f/e_{out} , where e_f is the amount of signal that is fed back and e_{out} is the signal at the output, has been called β for many years. So as not to confuse that term with the I_C/I_B ratio of a bipolar transistor, which is also identified by the symbol β , we will use B when referring to the feedback ratio.

With that convention out of the way, let's now look at a basic circuit with feedback, such as the one shown in Fig. 1. In that circuit, a voltage e_s is applied to the input. With no feedback, the voltage at the input to amplifier A , e_{in} , equals e_s . The gain of the overall circuit would then simply be $e_{out}/e_{in} = e_{out}/e_s$. When feedback is added, however, some of e_{out} appears at the input as e_f . Assuming that the feedback is positive, that is, that the signals are in phase and thus add, the input to the amplifier becomes $e_s + e_f$. When feedback is negative, the signals are 180° out-of-phase and the input to the

amplifier equals $e_s - e_f$. Since e_f depends upon e_{out} and B , the gain of the circuit with feedback is:

$$A_F = \frac{A_v}{1 - BA_v} \quad (1)$$

where A_v is the voltage gain of the amplifier without feedback, or e_{out}/e_{in} , and A_F is the gain of the overall circuit with feedback. The denominator of the equation, $1 - BA_v$, is known as the feedback factor. When negative feedback is used, the expression BA_v is negative; when positive feedback is used, that term is positive.

Assuming that the feedback is negative, and BA_v is much larger than 1, the gain of the amplifier is just about equal to $1/B$. Negative feedback makes the gain of an amplifier less sensitive to variations in the circuit's parameters, such as the supply voltage. Positive feedback makes the gain more sensitive to such variations. We will see why that's important when we discuss oscillators.

Because the feedback in this circuit is

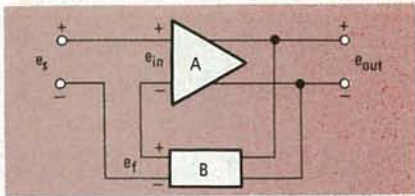


FIG. 1—AN AMPLIFIER with negative voltage feedback is shown in this block diagram.

applied in series with the input signal, the input impedance increases over what it would have been without any feedback; the amount it increases is directly proportional to the feedback factor. The output impedance, on the other hand, is reduced because the feedback signal is taken from across the load; the amount it decreases is indirectly proportional to the feedback factor. We'll see more about how input and output impedances are related to feedback later in this article.

Another effect of negative feedback is that distortion is reduced and the frequency response of an audio amplifier is improved. Distortion with feedback is equal to the distortion without feedback divided by the feedback factor. High-frequency response is extended from f_{OH} , the high-frequency limit without feedback to $f_{OH}(1 - BA_V)$, while the low-frequency response is extended from f_{OL} , the low-frequency limit without feedback, to $f_{OL}/(1 - BA_V)$. Remember here that since the feedback is negative the BA_V terms are negative and $1 - (-BA_V) = 1 + BA_V$.

Designing a circuit

When designing an amplifier with feedback, the first step is to determine the amount of overall gain that will be required. Let us say you need a circuit with a voltage gain of 40 dB, or 100. Assume that in this application about 20 dB of negative feedback is necessary around the circuit to reduce the distortion to about 10% of what it would have been without feedback. Then the gain of the overall circuit must be $100 \times 10 = 1000$ if it is to be adequate after feedback has been applied. The circuit shown in Fig. 2 should

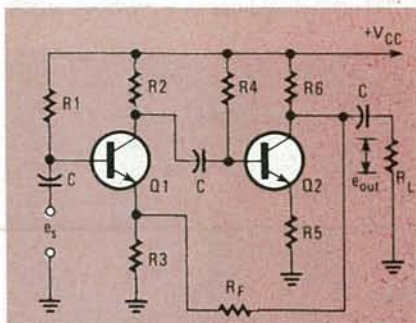


FIG. 2—IF THE FORWARD GAIN of this circuit is to be 100 after 20 dB of negative feedback is applied, the forward gain before the feedback is applied must be 1000. The circuit shown here uses series feedback.

fulfill all the requirements. (That circuit, minus the feedback loop, was first covered in the December 1982 issue of **Radio-Electronics**; please see that issue for a more complete discussion of the circuit). Assume the load, R_L , is 10,000 ohms, $V_{CC} = 9$ volts, and the β of Q1 and Q2 are 100.

Let's start by determining the values needed to get an overall gain of 1000 (before feedback is applied). The signal across the output load should be capable of an output voltage-swing of close to 9 volts, the voltage of the power supply. To accomplish that, the value of R6 should be less than one-fifth of R_L . Resistor R6 is chosen to be 1800 ohms.

The load in the collector circuit is equal to the resistance of R6 in parallel with R_L , or about 1500 ohms. It is actually somewhat less because R_F is in parallel with the 1500 ohms. In this first step of the design, however, R_F can be ignored. For one thing, we have not yet determined what the value of R_F is. Also, it usually has only a minor effect on the load resistance as that of R_F is very small compared to that of R_L in parallel with R6. So we'll ignore R_F until after the feedback circuit has been designed.

The gain of the overall circuit should be divided between Q1 and Q2. If the overall gain without feedback is 1000, we can let the gain of each stage be about 35 so that the total gain will be 35×35 , or 1225, which, of course, is somewhat more than 1000. As the gain around Q2 is just about equal to the ratio of the load in the collector circuit to the load in the emitter circuit (assuming that the load in the emitter circuit is much greater than the AC resistance of the emitter junction itself), by rearranging terms we can see that the value of R5 should equal $1500/35$, or about 43 ohms.

The Q2 circuit presents an impedance of $\beta \times 43$ ohms = $100 \times 43 = 4300$ ohms to the collector of Q1. If a 4300-ohm resistor is used for R2, the impedance in the collector circuit of Q1 is equal to 4300 ohms in parallel with 4300 ohms, or about 2150 ohms. If Q1 is to provide a gain of 35, the value of R3 should equal $2150/35$, or about 61.5 ohms; the closest standard value to that is 56 ohms.

Now, let's add feedback to the circuit. Resistor R_F and the 56-ohm emitter resistor, R3, are the components that determine the B term in the feedback factor. If gain is to be reduced by 20 dB and be equal to 10% of the gain without feedback, the gain with feedback, A_F , must be equal to:

$$A_F = 100 = \frac{A_V}{1 - BA_V}$$

$$A_F = \frac{1000}{1 + \left(\frac{56}{56 + R_F}\right) 1000}$$

so that R_F must be about 6200 ohms. Note that since we are again applying negative feedback, the BA_V term here is also negative and $1 - (-BA_V) = 1 + BA_V$.

When R_F is 6200 ohms, it reduces the load in the collector of Q2 to a substantial degree. It was originally calculated to be at about 1500 ohms. With the additional 6200 ohms across it, the collector load becomes about 1200 ohms. With the 43 ohms in the emitter of Q2, its forward gain is now reduced to about 29. To re-establish a gain of 35 for that circuit, R5 must be changed from 43 ohms to $1200/35 = 34$ ohms. Use a standard 33-ohm resistor.

In the preceding analysis and example, the circuit discussed used series feedback. The next circuit we'll discuss uses parallel feedback; in it, the feedback signal is applied in parallel with the input. That circuit is shown in Fig. 3.

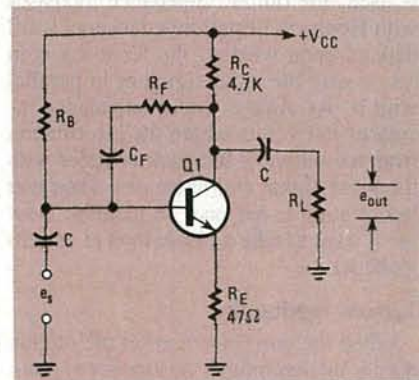


FIG. 3—PARALLEL FEEDBACK is used in this circuit.

Let's assume that we want to use that circuit in an application where the gain must be 10. If the β of the transistor is 100, the impedance at the base of the transistor due to R_E , the 47-ohm emitter resistor, is 4700 ohms. Now assume that all other impedances at the input of the transistor are high when compared to the 4700-ohm input impedance. As for the output impedance, if R_L were 47,000 ohms, the output impedance would be 47,000 ohms in parallel with R_C , the 4700 ohm collector resistor, or about 4200 ohms.

Ignoring feedback resistor R_F , the voltage gain of the circuit is the output impedance divided by the value of R_E ; that is $4200/47$, or about 90. In order to get a gain of 10, the feedback factor, $1 + BA_V$, must equal 9. If $A_V = 90$, B is just about equal to $8/90$. Because B is equal to the input resistance divided by R_F , $8/90 = 4700/R_F$. So R_F must be about 49,000 ohms. Make the impedance of capacitor C_F very small with respect to R_F at the lowest frequency to be reproduced by the circuit so that the capacitor does not affect the feedback.

While the input impedance of a circuit with series feedback is its impedance without feedback multiplied by the feed-

back factor, in parallel-feedback circuits the input impedance without feedback must be divided by the feedback factor to determine the input impedance. The output impedance is likewise reduced by that same feedback factor, just as it was in the series-feedback circuit. That is because the feedback signal in both instances is taken from across the load at the output.

In all of our discussion thus far, the feedback has been a function of the voltage at the output and hence is called voltage feedback. The feedback could, however, be a function of the current at the output instead. In that case, the signal is not fed back from across the load but from across a resistor or other device connected in series with it. That is referred to as current feedback because the the voltage generated across that device depends upon the current flowing through it as well as the load. When that configuration is used, the output impedance increases with feedback. Input impedance will still depend upon whether the feedback is in series with the input signal or in parallel with it. As always, input impedance increases in circuits where the information from the output is fed back in series with the input signal and decreases when that information is fed back in parallel. Now we'll want to take a closer look at current feedback.

Current feedback

When the current sensed at the output of a circuit determines the amount of voltage fed back to its input, the circuit is called a current-feedback amplifier. Such a circuit is shown in Fig. 4. As was the case with the circuit in Fig. 1, the feedback voltage is applied in series with the input signal.

In Fig. 4, voltage e_s is amplified and appears at the + and - output terminals of amplifier A. The total output is applied across the two series-connected resistors, R_L and R_S . The output voltage across R_L , as well as the voltage developed across R_S , varies with the current flowing through the two resistors. Because the signal voltage developed across R_S depends upon the amount of current flowing through it, all or a portion of that voltage can be used to supply the required feedback information. Voltage gain of the

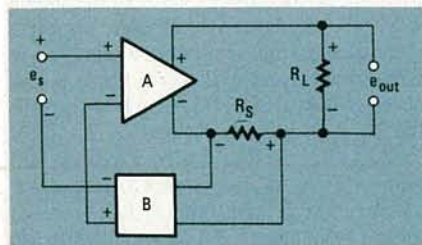


FIG. 4—SINCE FEEDBACK IS GENERATED across a resistor, R_F , that is in series with the load, this amplifier is said to use current feedback. That's because the same current that flows through the load must flow through that resistor

overall circuit, with feedback, is:

$$A_F = \frac{A_v}{1 - BA_v \left(\frac{R_S}{R_L} \right)} \quad (2)$$

The values of resistors R_L and R_S can usually be adjusted so that there will be no need to further reduce the signal fed back through use of additional B networks. If that is done, equation 2 can then be simplified by setting B equal to 1.

Although the circuit in Fig. 3 was treated as if it used voltage feedback, it can also be thought of as an amplifier with current feedback (affecting current rather than voltage gain). To see that more clearly, remove R_B and C1 from the circuit and connect R_F directly from the collector of Q1 to the base. The value of R_F must be larger than was found in our original analysis of that circuit so that it can do the dual job of establishing the feedback and setting the DC bias of the amplifier. As collector current divides between R_F and R_C , the portion of the current fed back to the input is $4700/R_F$. If the current gain of the amplifier without feedback is A_1 , the current gain with feedback, A_{IF} , becomes:

$$A_{IF} = \frac{A_1}{1 + \left(\frac{4700}{R_F} \right) A_1}$$

Note that while one requirement in establishing a substantial amount of voltage feedback was to make R_F small, its magnitude here has been greatly increased. If R_F is large, voltage gain with feedback is affected slightly by its presence while current gain is reduced considerably.

In practical circuits, current feedback can radically affect voltage gain. Consider the circuit shown in Fig. 5. Here, current in the base circuit due to the input signal voltage is amplified by the transistor. The amplified current flows through both R_C and R_E in the transistor's output circuit. Voltage e_f developed across R_E due to the signal current in the emitter circuit is subtracted from e_s (because the voltages are 180° out-of-phase with each other e_f bucks e_s) and applied to the base-emitter circuit of the transistor. Because $e_s - e_f$ is less than e_s , the gain of the overall circuit is less with feedback than without feedback.

Gain may be reduced further by increasing the size of R_E . Now a larger voltage will be developed across that resistor. That larger voltage is subtracted from e_s so that less voltage is applied to the base-emitter circuit, reducing the gain further. Hence the gain of the overall circuit is inversely related to the value of R_E . That was noted earlier when we indicated that voltage gain of a circuit similar to the one in Fig. 5, is equal to about R_C/R_E . That is true because of the presence of current feedback.

It was pointed out that for this circuit,

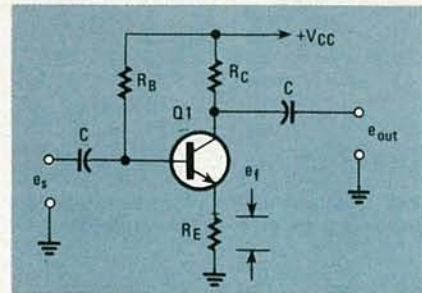


FIG. 5—IN PRACTICAL CIRCUITS such as this one, current feedback can greatly affect the circuit's voltage gain.

the fed-back voltage is in series with the input signal voltage. From our discussion of feedback characteristics, we can conclude that the input impedance of that circuit should increase with the amount of voltage fed back. That amount depends upon the value of R_E . When basic amplifiers were discussed, we noted that the input impedance of that type of circuit is βR_E in parallel with R_B . That effect of R_E on the input impedance also holds in circuits where feedback is used.

In order to minimize the affect of R_B on the input impedance, a bootstrapping circuit may be used. An example of that type of circuit is shown in Fig. 6. Capacitor C1 has a large value and it acts as a short circuit to input signal voltage e_s . Without C1, the input impedance seen by e_s is $\beta R_E + R_{IN}$ in parallel with R_B ; the combination is in parallel with R_X . (As far as the signal is concerned, V_{CC} and ground are at the same potential.) By adding C1 to the circuit, R_X and R_B are, signal-wise, across R_E while R_{IN} is connected from the base to the emitter of Q1. Now the input impedance of the circuit is equal to the parallel combination of R_B , R_X , and R_E , multiplied by beta. Resistor R_{IN} does not come into the picture for it is directly across the low impedance base-emitter junction; it is negligible when compared to that impedance. Because R_B and R_X have been shifted to be across R_E , the input impedance of the circuit is increased many times over what it would have been if C1 were not present.

Feedback in audio circuits

It was pointed out in a previous article

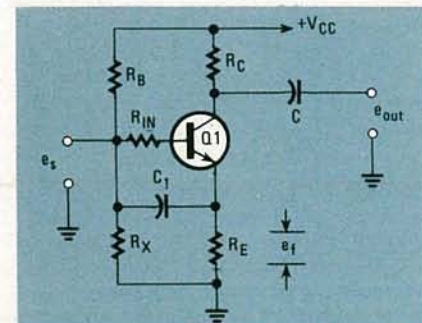


FIG. 6—TO MINIMIZE THE EFFECT OF R_B on input impedance, a bootstrap circuit such as this one can be used.

that negative feedback is used around power amplifiers, small-signal audio amplifiers, op-amps, and so on. Its primary function is to reduce distortion, broaden the bandwidth of the amplifier, and reduce the output impedance. If a resistor-capacitor network is included in a feedback loop, the feedback network can also be designed to alter the frequency-response characteristics of the circuit.

Let's take a look at an audio amplifier. An example of an amplifier that can be used to reproduce the output from a tape player is shown in Fig. 7; an approximate curve that shows the desirable frequency characteristics of such an amplifier is shown in Fig. 8. The curve shows that the amplifier's output should remain at a maximum at frequencies below 50 Hz, should drop at the rate of 6-dB-per-octave from 50 Hz to 3000 Hz, and then become level once again at all frequencies above 3000 Hz. To establish that frequency characteristic, only a series resistor-capacitor circuit is required in the feedback loop. That is shown as C_F and R_F in the circuit.

The circuit to accomplish that goal can be designed through use of an R-C impedance equation and equation 1. The impedance of the series circuit consisting of C_F and R_F is $Z_F = (R_F + j/6.28fC_F) = (j + 6.28fC_FR_F)/6.28fC_F$. (For those unfamiliar with the topic, the impedance of a resistor and a capacitor in series is equal to the resistance of the resistor plus the reactance of the capacitor, where the capacitive reactance, X_C , equals $1/2\pi fC$. However, those two quantities can not simply be summed, as the voltages across the components are out of phase. Hence the introduction of the j operator, where $j = \sqrt{-1}$. That of course is an imaginary number and the reactive portion of the impedance is the imaginary component; the resistive part of the impedance is called the real component.) Plugging the impedance equation into equation 1, the voltage gain with feedback is:

$$A_{VF} = \frac{A_v}{1 + BA_v}$$

$$A_{VF} = \frac{A_v}{1 + A_v \left(\frac{R_E}{R_E + Z_F} \right)}$$

The portion of the output voltage that appears across resistor R_E is $R_E/(R_E + Z_F) = B$. That is the B that should be used in the equation. Should R_F be much larger than R_E , B simplifies to being equal to R_E/Z_F . The entire equation may be simplified farther if the voltage gain is very large. When $A_v(R_E/Z_F)$ is much greater than 1, the equation simplifies to:

$$A_{VF} = \frac{Z_F}{R_E} = \frac{j + 2\pi f C_F R_F}{2\pi f C_F R_F}$$

The above equation is the equation of the curve shown in Fig. 8. From the curve, we see that there are two break

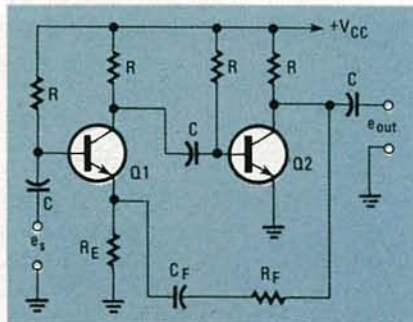


FIG. 7—A TAPE PLAYBACK PREAMPLIFIER is shown here; its simplified frequency-characteristic curve is shown in Fig. 8.

points, or corner frequencies, where rolloff begins and ends. The lower break-point occurs at a frequency such that the denominator of equation 2 is equal to zero. The upper break-point occurs at a frequency such that the numerator of equation 2 is equal to $j + 1$.

Let's first find the frequency where the denominator is equal to zero. That is, of

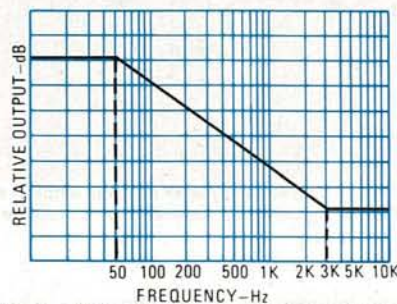


FIG. 8—THE SLOPE between the 50- and 3000-Hz points is 6-dB-per-octave.

course, at $f = 0$. Thus, at $f = 0$ rolloff begins. It will keep rolling off indefinitely unless there is some frequency where gain due to feedback begins to rise to compensate for that initial rolloff. That happens when the numerator in equation 2 is equal to $j + 1$, or when $f = 1/6.28C_FR_F$. Since the curve calls for a corner frequency of 3000 Hz, choose values of R_F and C_F that satisfy that condition.

Getting back to the frequency where rolloff starts, it was determined from our calculations that for this circuit it begins at 0 Hz. Actually, the curve calls for it to start at 50 Hz. That is taken care of by coupling capacitor $C1$. In an actual circuit, the value of the capacitor would be selected so that the corner frequency would fall as close to 50 Hz as possible. In a more accurate circuit, a resistor would be placed across $C1$ so that the corner frequency could be made precisely 50 Hz.

The curve in Fig. 8 is shown with sharp points at the corner frequencies. In the "real world" that never happens—the changes in the curve are never sharp at the corner frequencies and the rolloff and the flat-response sections do not follow the

exact contours shown in the drawing. The curve in Fig. 8 is only an approximation of the actual curve required to satisfy the requirements of the circuit, and is used as shown here to simplify the design problem. When designing an actual circuit, most designers follow that procedure.

Stability

Even when only resistors are used in a feedback circuit, the feedback is not uniform over the entire band. It varies with the overall gain of the circuit as well as with the capacitance, inductance, and resistance inherent in the different sections of the circuit.

To check for stability, plot the frequency response of the circuit before feedback is applied. Note the response at the extreme high and low ends of the band. If a circuit is to be stable, the rolloff, when feedback is applied, should be less than 12-dB-per-octave. That can be shown with the help of Fig. 9.

That figure shows the frequency response of a circuit. Two feedback lines have also been plotted—one at -10 dB and one at -20 dB. At the points where the -10-dB feedback line crosses the frequency-response curve, the rolloff is 6-dB-per-octave. At the points where the -20-dB feedback line crosses the frequency-response curve, the rolloff is 12-dB-per-octave. Thus if 10 dB of feedback is added to the amplifier, the circuit is stable, but if 20 dB of feedback is added, the amplifier will be only marginally stable—it may have a tendency to oscillate because the line indicating the -20-dB feedback level crosses the frequency-response curve at a point where the rolloff is 12-dB-per-octave. At that point, feedback has a tendency to turn positive.

If the rolloff should exceed 12-dB-per-octave at the extreme high or low ends of the band, anything more than 20 dB of negative feedback at mid-frequency will turn the circuit into an oscillator.

Oscillators

Getting back to equation 1, if feedback is positive, the BA_v factor is positive. If BA_v is made equal to +1, the denominator of equation 1 becomes zero and the gain with feedback becomes infinite. A circuit with in-phase positive

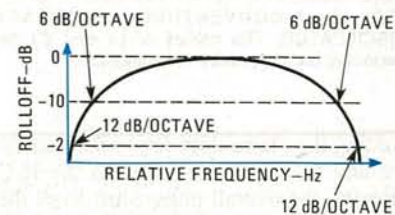


FIG. 9—TO CHECK AN AMPLIFIER FOR STABILITY, first plot its frequency response and then the feedback. At the points where the curves intersect, the rolloff should be less than 12-dB-per-octave to insure stable operation.

feedback and a gain of 1 or more after feedback has been applied will oscillate—there is an output even though no input signal is applied.

A conventional feedback arrangement is shown in Fig. 10. A resonant circuit is formed by L1 and C1. All feedback oscillators are resonant at a frequency of about $1/2\pi\sqrt{LC}$ Hz. Oscillation occurs because of the following sequence of events: When the supply voltage is applied to the oscillator circuit, a pulse reaches the L-C circuit. The L-C circuit turns the pulse into a waveform at its resonant frequency. It is coupled from L1 to L_F and from there to the base-emitter circuit of the transistor. That signal is amplified by the transistor and applied to the resonant circuit. If the signal across L1 and L_F is in the proper relative phase, it keeps on being fed back and amplified until the overall circuit remains in oscillation.

Oscillators have many shapes and forms—three are shown in Fig. 11. The oscillator shown in Fig. 11-a is known as a Colpitts oscillator. When calculating its resonant frequency, use $C1C2/(C1 + C2)$ for the total capacitance of the L-C circuit. Another popular oscillator is the Hartley, shown in Fig. 11-b; its resonant frequency is simply $1/2\pi\sqrt{L/C}$. A feedback oscillator circuit using only resistors and capacitors is shown in Fig. 11-c. It oscillates because the transistor shifts the phase of the signal 180° from the base to the collector. Each of the R-C networks in the circuit is designed to shift the phase 60° at the frequency of oscillation, for a total of 180°. The appropriate values of R and C for each network is found from $f = 1/(2\sqrt{3}\pi RC)$; that equation allows for the 60° phase shift required by the design.

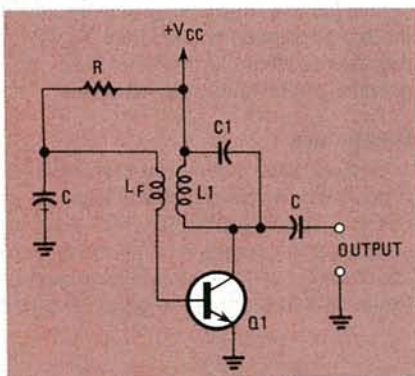


FIG. 10—A CONVENTIONAL FEEDBACK OSCILLATOR. The values of L1 and C1 determines the frequency of oscillation.

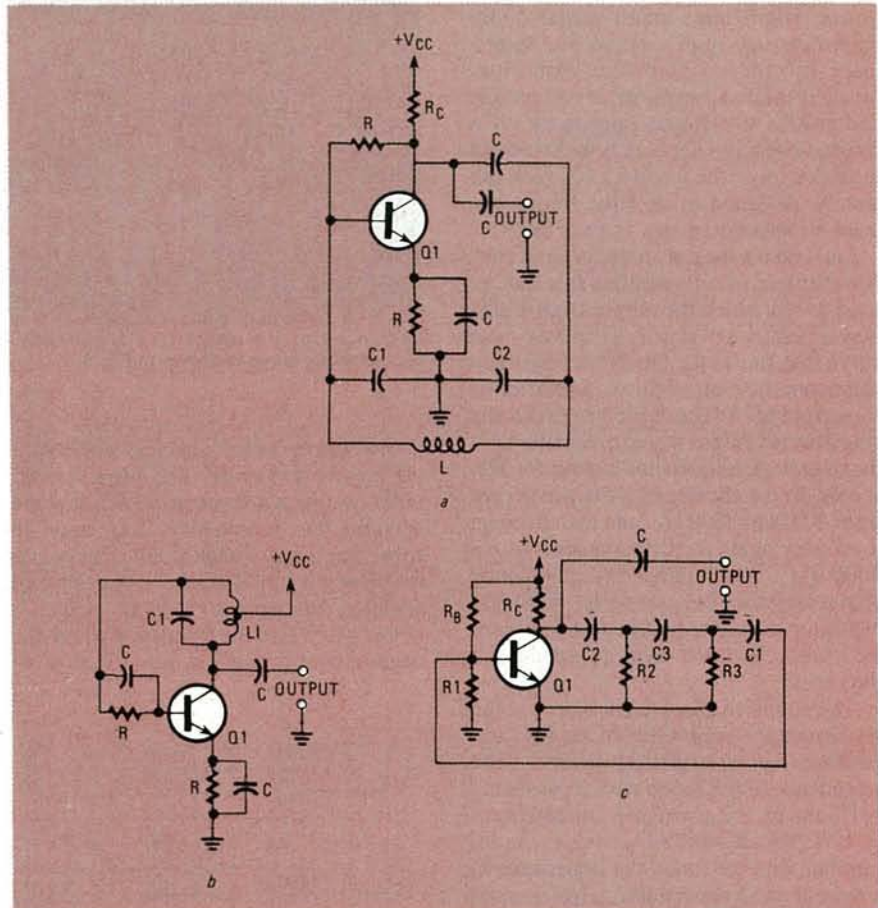


FIG. 11—THERE ARE MANY different kinds of oscillators. A Colpitts oscillator (a), a Hartley oscillator (b), and a phase-shift oscillator (c) are shown here.

was initiated by a random pulse when power was applied to the circuit, it was amplified, the phase shifted 360°, and fed back. The oscillator frequency will be about:

$$f = \frac{1}{2\pi(C1)} \sqrt{4(R1)R_C + 6(R1)^2}$$

if R_B is considerably larger than R₁. Should R₁ be omitted from the base circuit, when combined in parallel with R_B, must be chosen so that the combination is equal to R₂ or R₃ (note that R₁, R₂, and R₃ are all equal).

Oscillators can be built around op-amps. The output of the circuit shown in Fig. 12 is a squarewave; let's see why. Negative feedback is established through R_{F1}, while there is positive feedback through R_{F2}. For that circuit, as well as for circuits described below, assume that the positive saturation voltage at the output of the op-amp is +V_{CC} and that the negative saturation voltage at the output is -V_{CC}. The voltage at the non-inverting input depends upon the voltage at the output. It is positive when the saturation voltage is at +V_{CC}, and negative when it is at -V_{CC}.

Assume the oscillation starts when the output is at +V_{CC}. At that time, C1 gets charged to a positive level through R_{F1}.

When that voltage exceeds the positive voltage at the non-inverting input, voltage at the output drops to -V_{CC}. When that happens, the voltage across C1 begins to drop and become negative because its charging voltage is now being supplied by the negative voltage at the output of the op-amp. Once it drops to below the voltage at the non-inverting input, the voltage at the output returns to +V_{CC}. The process keeps repeating itself. Consequently, the output is a squarewave. The frequency of oscillation is $1/2R_{F1}C$, provided that B = 0.462. Since B = $R1/(R1 + R_{F2})$, that condition will hold true if R_{F2} is made equal to 1.16R₁.

A sawtooth generator is composed of

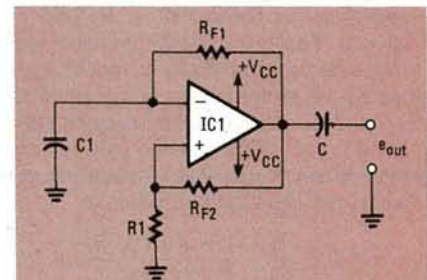


FIG. 12—OP-AMPS are commonly found in oscillator circuits. The output of this circuit is a squarewave.

continued on page 94

SWD-1 VIDEO CONVERTER

FOR CABLE TV



The SWD-1 Video Converter is utilized on cable TV systems to remove the KHz's signal from a distorted video (channel 3 in/out) and also pass thru the normal undistorted/detected audio signal. Rocker switch selects operating mode to remove KHz's distortion from the video or pass all other channels normally. Simple to assemble—less than 30 minutes. Pre-tuned. Input/output Channel 3. Impedance 75 ohms. 117VAC.

SWD-1 Video Converter Kit \$69.95

0-35dB VARIABLE GAIN

RF AMPLIFIER

USES TWO REVOLUTIONARY NEW HYBRID BROADBAND AMPLIFIER ICs

Works on all RF Signals from 40-900MHz



EXCELLENT FOR USE WITH:

- All Antenna Systems
- Voice Communications
- MATV Systems
- CCTV Systems
- Video RF Line Amplifiers
- Frequency Counters
- Oscilloscopes
- FM Broadcasts

Now you can use one TV/FM Antenna to cover all close and distant stations without experiencing overloading problems. Ideal for outdoor and indoor use. I/O impedance is 75 ohms. Power Supply is separate coax feed system which allows amplifier to be located anywhere in cable run. Power Supply has knob to control variable gain, LED power on indicator and on/off switch.


ALL-2VG Wired and Tested..... \$49.95

Our New STVA 14.5dB GAIN, 14 ELEMENT CORNER REFLECTOR YAGI ANTENNA



STVA-3 Yagi Antenna, 14.5dB Gain, Selectable 75 or 300 ohm Channel 60-80..... \$19.95
 STVA-4 Yagi Antenna, 14.5dB Gain, Selectable 75 or 300 ohm Channel 44-52..... \$19.95
 RG-59/U 75 ohm Low Loss Coax Cable... \$12/ft. F-59 Coax Connector... \$.39 ea.
 MT-1 Special UHF 75-300 ohm Matching Transformer..... \$1.45 ea.

AMATEUR — ETV 32 ELEMENT YAGI ANTENNA

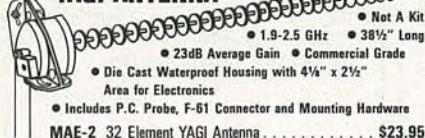

• Not A Kit
 • 1.9-2.5 GHz • 38 1/2" Long
 • 23dB Average Gain • Commercial Grade
 • Die Cast Waterproof Housing with 4 1/4" x 2 1/2" Area for Electronics
 • Includes P.C. Probe, F-61 Connector and Mounting Hardware
 MAE-2 32 Element YAGI Antenna..... \$23.95

Kato Sons' Regulated Variable DC Power Supply
 For use with KSDC-KIT 1.9 - 2.5GHz Down Converter. Completely assembled with Attractive Cabinet, TV/Converter Mode Switch, Frequency Control and LED Indicator.
 Model KSPS-1A Assembled Power Supply..... \$23.95

SPECIAL PACKAGE OFFER
 ORDER ALL THREE ITEMS
 MAE-2, KSDC-KIT and KSPS-1A for Only..... \$74.95
 Regular price if ordered separately \$82.85
 — CO-AX CABLES ARE NOT INCLUDED —

Switch to Bambi™!

Electronically

Bambi Electronic Video Switch ... makes switching of your VCR/VTR, Pay TV Decoders, Cable TV, Video Discs, Video Games, Closed Circuit TV, Antennae and Microcomputer as easy as pushing buttons.

The Bambi Electronic Video Switch is an electronic computerized switching network with memory which can accept up to six different sources of video signals and provide the flexibility of directing the inputs to any or all of the three outputs.

Now you can eliminate ... the drudgery of disconnecting and reconnecting your video equipment each time you use it ... the tangled mess of cables which are impossible to trace out ... not being able to use more than one function at a time.


Bambi lets you enjoy using your video equipment the way it should be ... electronically and on line at the push of a button.

Model BEVS-1 Completely Wired and Assembled. Includes comprehensive Instruction/Operation Manual and Decal Set for customizing your Video Switch installation.

\$129.95



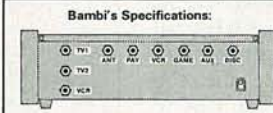Bambi's front panel was designed with the user in mind. Computer styled construction, with soft-touch keyboard (rated for over 10 million operations), arranged in matrix form allows easy input/output selection without referring to charts. Functions selected through the keyboard are immediately displayed on the 18 LED status indicators.



Bambi's Specifications:

- Input/Output Impedance 75 ohm
- Signal Loss 3dB ±1dB
- Noise 40dB ±1dB
- Input Return Loss 12dB min.
- Isolation 65dB min.
- Power Req. 117VAC 60 Hz, 2W
- Dimensions 10 1/4" W x 6 1/4" D x 3 1/4" H
- Weight 4 1/2 lbs

Check the quality of Bambi against that of much higher priced competition. All solid state electronic switching provides low attenuation (3dB), wide frequency response (40-890 MHz), and excellent isolation between signal sources (each I/O section individually shielded for 65dB min. isolation).



FREE Bambi Poster with any purchase

NEW VCR Quality



Assembly Time Approximately 5 Minutes.

MODULATOR

Not a Game Type Modulator

The MPS-1 Kit converts Video/Audio signals to a crystal controlled RF output for TV Channels 3 and 4. The MPS-1 Modulator's adjustable inputs are designed to match all TV Cameras and VCRs and features a voltage regulated power supply, power switch and LED indicator. No Tuning Required. Operates on 117VAC. Ideal for use with our new Debbie CCTV-1 and revised Bambi BEVS-1S.

MPS-1 Modulator Kit..... \$39.95

SEE PACKAGE OFFER BELOW FOR ANTENNA, DOWN CONVERTER, POWER SUPPLY, & RF AMP.

Kato Sons' Down Converter Kit ★1.9 - 2.5GHz★

Designed for Simple Simon by former Japanese CQ Amateur Magazine's UHF Editor/Engineer. Unit utilizes new ingenious Printed Circuit Probe for maximum gain. Circuit board fits inside MAE-2 antenna housing. Requires mechanical assembly only. All electronics are pre-soldered and pre-tested. Usable up to approximately 15 miles.

Model KSDC-KIT 1.9 - 2.5GHz Down Converter Kit..... \$34.95

Kato Sons' RF Amplifier ★22dB Gain★

High quality 2 stage low noise RF Amplifier for 1.9 to 2.5GHz. Unit requires approximately 10 minutes assembly. Fits in same housing with down converter. Covers distances of up to 30 miles.

Model KSRF-2 RF Amplifier..... \$23.95

BE SECURE WITH BAMBI!

Bambi Now Provides Home/Industrial Security With The New ... **Automatic Sequential Scanning BEVS-1S**

That's right! In addition to Bambi's regular features listed above, we have added Autoscaning with a controlled 1-10 second Variable Delay for up to six input security cameras. The BEVS-1S allows simultaneous recording on a VCR while observing activity on the monitor. Manual lock-on of any one of six inputs can be accomplished at any time. The BEVS-1S coupled with our new Debbie CCTV-1 listed below makes an excellent security system for your Home or Business.

BEVS-1S Sequential Scanning Electronic Video Switch... \$199.95

You Should Have Debbie's™ Quality!

Debbie CCTV-1 CLOSED CIRCUIT TELEVISION CAMERA



Excellent For Use In Home or Business Security Systems, Monitoring Production Lines, Childrens Play Areas, Etc.

Features:

- 2/3" Electrostatic Focusing Vidicon Tube
- EIA 525 Line, 60 Fields Per Sec. Scanning System
- 600 Line at Center Horizontal Resolution
- 1 Footcandle Minimum Illumination
- 10,000 to 1 Automatic Light Control Range
- 1.0Vpp Composite, Negative Sync, 75 Ohm Video Output
- 40dB Signal to Noise Ratio
- Standard "C" Lens Mount
- 110V ±10%, 50-60Hz, 9 Watts

Debbie CCTV-1 Requires C-Mount Lens..... \$159.95
 16mm, F1.6 Hi-Resolution Lens w/Cap..... 19.95
 Mounting Bracket Flexible, Locking, 360° Gooseneck for use in ceiling or wall mounting..... 12.95

NOTE: When using the Debbie CCTV-1 with Bambi BEVS-1S, an RF Modulator such as our Model MPS-1 is required.

MODEL IC-1 INFRARED CONVERTER

Adapts to any video camera. Reduces energy costs for night viewing by 60%. Video tape in the dark without being detected. Excellent for • Factory Grounds Security • Home Surveillance. Write for Details.

★ PWD FOR DETAILS SEE OUR PAST ADS

★ SPECIAL \$109.95

WRITE FOR OUR CATALOG OF ADDITIONAL CCTV ACCESSORIES

SIMPLE SIMON ELECTRONIC KITS,™ Inc.
 3871 S. Valley View, Suite 12, Dept. R, Las Vegas, NV 89103

In Nevada Call: 702-871-2892

1-800-782-3716

NEED 6 OR MORE OF AN ITEM? WRITE FOR QUANTITY DISCOUNTS

Outside Nevada Call:

Available by Mail Order Only Send Check* or Money Order. Minimum Order: \$16.95. Add 10% Shipping and Handling on orders under \$40.00. For orders over \$40.00, add 5%. Minimum Shipping and Handling \$2.00. Cat. \$1.00 — VISA and Mastercard Acceptable — *Check orders will be held 30 days before shipping.

NEW IDEAS

Low-distortion audio limiter

SHORTWAVE LISTENING AND DXING IS, without a doubt, an enjoyable hobby. However, it does pose a hazard to your ears—or to your peace of mind—because of the annoying loud-volume pops and blasts you're sure to hear from your communications receiver. Although the AGC (Automatic Gain-Control) circuits in communications receivers are supposed to take care of those sudden changes in volume, they never seem to do the job well enough. Those of you who wear headphones are especially vulnerable to the annoyance. What's especially annoying then is that you're probably wearing the headphones not for your own benefit, but for the benefit of those around you.

I tried several ways to reduce the problem (for example, using FET's as attenuators) but I was unhappy because I was always trading one problem off for another: distortion. But I finally came up with a design that does what I want—it attenuates the blasts from my communications receiver while causing no noticeable distortion.

The circuit of the audio limiter is shown in Fig. 1. The level at which it comes into action can be set with the LIMIT LEVEL trimmer potentiometer. When that level is exceeded, the output from the LIMITER-DETECTOR half of the op-amp (which is used as a comparator) causes the LED to light. The light from the LED causes the resistance of the photoresistor to decrease rapidly. That in turn causes the gain of the LIMITER half of the op-amp to decrease. When the signal drops below the desired limiting level the LED turns off, the resistance of the photoresistor increases, and the gain of the LIMITER op-amp returns to its normal level—that set by the combination of resistors R1 and R2. A dual-polarity power supply (± 12 volts is desirable) is, of course, needed for the op-amp.

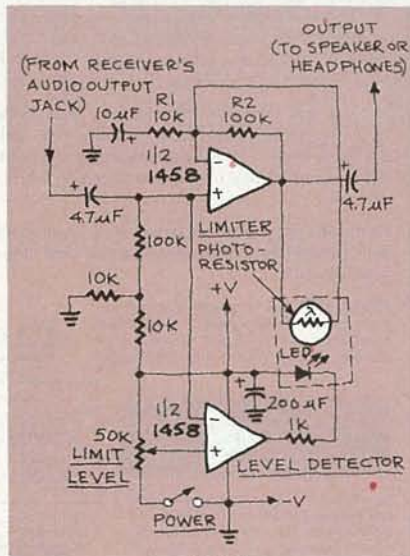


FIG. 1

The circuit is very easy to build, and since the construction method is not critical, use the one you prefer. You might even want to mount the circuit inside your receiver. One important construction note, however, is that the photoresistor and LED should be encased facing each other in a light-tight enclosure.

The parts that you use are not critical either. One note here however is that the (cadmium sulfide, or CdS) photoresistive cell is most sensitive to light with a wavelength of about 5000 angstroms (or, approximately, green light). Therefore, you may want to use a green LED for best response.

Perhaps the best feature of the audio-limiter circuit is that it can be used with any receiver, whether it's a tube-type shortwave receiver or a new solid-state scanner. Your ears will thank you.—
Daniel Ulmer

NEW IDEAS

This column is devoted to new ideas, circuits, device applications, construction techniques, helpful hints, etc.

All published entries, upon publication, will earn \$25. In addition, Panavise will donate their model 333—The Rapid Assembly Circuit Board Holder, having a retail price of \$39.95. It features an eight-position rotating adjustment, indexing at 45-degree increments, and six positive lock positions in the vertical plane, giving you a full ten-inch height adjustment for comfortable working.



I agree to the above terms, and grant **Radio-Electronics Magazine** the right to publish my idea and to subsequently republish my idea in collections or compilations of reprints of similar articles. I declare that the attached idea is my own original material and that its publication does not violate any other copyright. I also declare that this material has not been previously published.

Title of Idea

Signature

Print Name

Date


Street

City

State

Zip

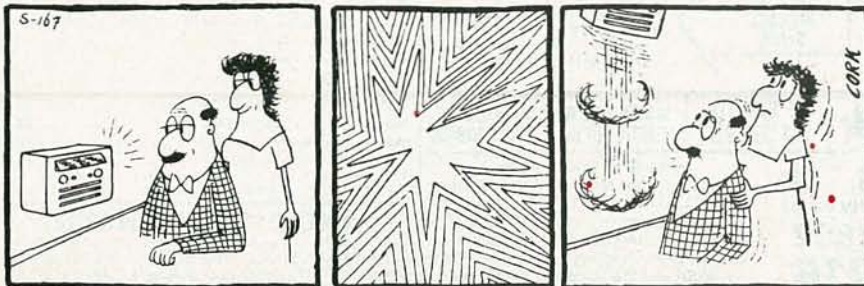Mail your idea along with this coupon to: **New Ideas Radio-Electronics**,
200 Park Ave. South,
New York, NY 10003



4.....3.....2.....1.....0.....LEFT OFF!!

No wonder they call it the SUPERFONE!

At Last—a Cordless Phone with TWICE the Range, Sound Fidelity to Rival Phones with Cords, and a Privacy Code System — All This in a Phone Less Than an Inch Thick!



The Super Fone is less than 1" thick. The base unit has a built-in speaker phone, a fully independent intercom and is 110 volt-220 volt switchable.

Until now, cordless phones have given you wonderful convenience. But they've had two problems:

1. The range is limited to 600 to 700 feet.
2. Some of them sound as though you're talking inside a barrel.

As cordless phones have become enormously popular, another problem has arisen: two people, living near each other, can have the same channel. Not only is there line confusion, but someone else can literally make a long distance call on your phone.

No more. Never again.

Range: 1500 Feet OR MORE!

The SuperFone 650 uses state-of-the-art electronics to bring you the ultimate cordless phone. Sound quality is superb — and it stays superb, 1500 feet or more from the base station. That's more than twice the distance of standard cordless phones.

Only SuperFone 650 has a secret code system to prevent interference and false operation of the phone. You choose from 512 possible "code" combinations. Both the base unit and the phone are locked onto that code, which you can change when you want to.

No other phone can interfere. No other unit can share the signal. No one else can hear or speak on your carrier-wave.

Enormous Range

We say the SuperFone 650 has a range of 1500 feet.

Notice we didn't say "up to" or "as far as" 1500 feet. There's no hedging, because this seems to be the minimum, not the maximum range.

Users report 1800 and 2000 feet. That's nearly half a mile. SuperFone 650 is a radiophone, not a toy, and that's why its signal doesn't break up or start hissing or crackling when you get half a block away.

You can tell when you heft it. It's a Little Giant. You can feel the power inside. What a marvel of electronic engineering it is! And it's tough, too. It fits into your shirt pocket, and you can bounce it around all day without damaging it.

Speakerphone, Intercom — Everything!

SuperFone 650 is The Everything Phone. Anything any phone can do, it can do.

First, the base station is a speaker phone. Touch a button and you can have a hands-free conference conversation in the room in which the base station sits.

Next, it's an intercom. You can page the handset from the base unit and have a private conversation. You have a true wireless intercom, not just a signal.

Third, you have a privacy button. Push that button and you'll still be able to hear anything the other party says, but he or she won't be able to hear you until you take the button off "hold."

Fourth, you have an automatic redial. Touch the key and the SuperFone will redial the last complete number.

What else? A security switch which makes it impossible for anyone to call out on the remote phone, without changing the ability to receive calls. A volume control for the speaker on the base unit. A call button to page the base from the cordless phone. THIS PHONE HAS EVERYTHING!

30-Second Installation

Plug your SuperFone 650 into any wall AC outlet. Push its standard modular terminal into the telephone plug. You're in business.

Every component is heavy-duty, from the built-in condenser microphone (with automatic gain control) to the LED indicator lights. This phone is designed for hard use.

The SuperFone 650 is yours for \$249.95. If you want the SuperAntenna with it, giving you a range of a mile — or even more — you can have both for \$319.95. (Or you can get the SuperAntenna alone for \$79.95.)

We Absolutely Guarantee!

Use the SuperFone 650 (or any electronic instrument you acquire from us) for up to 30 days. If for any reason you decide not to keep it, return it for a 100% refund.

The SuperFone 650 — \$249.95
The SuperAntenna — \$79.95
BOTH Phone and Antenna — \$319.95
Adapter for Multi-Line phone — \$39.95

Add \$4.50 per total order for shipping.

New! MULTILINE ADAPTER FOR BUSINESS PHONES

If you have several lines, you can plug them into your SuperFone with this single adapter.

The adapter costs \$39.95. Nothing else is required to attach multi-line phones to one SuperFone 650.

TRIPLE THE RANGE OF ANY CORDLESS PHONE!

The SuperAntenna will give your cordless phone, regardless of make or model, three times the range it has now.

If the range is 700 feet, it'll leap to over 2,000. If it's 1500 feet, it could be as far as one mile!

Easy to install. Only \$79.95 complete. Add \$4.50 for shipping.



For instant service, if you have a VISA or MasterCard, call toll-free 24 hours a day, seven days a week:

1-800-824-7888

Ask for Operator 551.
(in California: 1-800-852-7777)

The SuperFone 650, SuperAntenna, and Multi-Line Adapter are more electronic marvels from

NEW HORIZONS

Dept. RE-7, 1 Penn Plaza, Suite 100
New York, NY 10119

HOBBY CORNER

Reducing battery drain

EARL "DOC" SAVAGE, K4SDS, HOBBY EDITOR

THE FIRST LETTER THAT WE'LL LOOK AT this month is from Ken Alexander in Tennessee. He built and installed a security alarm system in his car. The alarm doesn't draw any current until it is activated. The problem, though, is that the LED indicator light *does* draw current—typically about 40 mA. When the car is not moved for a long period of time, the battery can be affected, particularly in cold weather. Ken wants a way to run the LED with less current drain.

Suppose there were a way to keep the LED turned off most of the time, and on for only short periods. Then, the "heavy" battery drain would occur only in short bursts as the LED was turned on briefly. That would not only solve the main problem but, in my opinion, provide a better indicator—a flashing light usually attracts more attention than a steady one.

Of course, there are many ways to make an LED flash, but one of the simplest is to use a 3909 LED flasher/oscillator IC. The best thing about it (from Ken's viewpoint) is that the operating current is 1 mA—and usually less, depending on the applied voltage (6.4 volts maximum).

The circuit, in spite of the current peaks on flashes, draws only about $\frac{1}{40}$ the power used by an LED alone. Add to that the reduced average-current as the flash rate is lowered and you have an in-

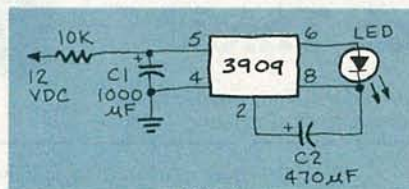


FIG. 1

significant load for a car battery.

Figure 1 shows a schematic of a simple 3909 flasher circuit operated from a 12-volt source. The 10K resistor drops the voltage to the four volts needed to operate the IC. It also restricts the current that flows when the LED does flash. Capacitor C1 is needed to provide that burst of current.

The flashing rate is determined by the value of capacitor C2. I suggest that the rate be made fast enough for the LED to attract attention, but not too fast—the faster it flashes, the more current you'll need. If C2 is 220 μ F the rate is about one Hz. For a rate around four Hz, use a 1000 μ F capacitor.

If there is a voltage source between 1.5 and 6 volts available, just omit C1 and the 10K resistor. I hope this little circuit meets your needs, Ken.

Battery voltages

Peter Poulos in our nation's capital wonders why all batteries of the same size don't have the same output voltage. (I guess he also is wondering why many batteries of different sizes *do* have the same output voltage.) Well, Pete, it all depends upon the materials of which the batteries are made. Different metals separated by different chemicals (called electrolytes) will produce different voltage potentials.

Let's make a few simple batteries to see how it works. Get a couple of paper cups

and put salt water in one and lemon juice in the other. Now find a piece of copper wire, a piece of aluminum wire, and a shiny nail. Clip different pairs of the three metals to the leads of your voltmeter (set on the one- or two-volt scale) and dip them into the two solutions.

You will find that your "batteries" will produce potentials of from 0.15-volt to over a half of a volt. Try some other solutions and other metals (especially an old silver coin if you can find one). What combination can you find to give the highest voltage?

Yes, those really are batteries (actually, wet cells). I wouldn't care to hook them together and carry them around in my flashlight, but they will do real work. Folk who lived out in the country often used similar power sources for early radios. But let's stick with the "dry cells" that we're familiar with. In those batteries, the electrolyte material, which is usually damp, is considered to be "dry."

There you have the basic principles that you need to answer your question, Pete. Of course, sometimes the manufacturers will fool you. They may stack several low-voltage cells together. For example, the common nine-volt "transistor-radio" battery is actually a package of six small 1.5-volt cells. In any event, now you know why all batteries of the same size are not the same voltage. And why some batteries that *are* the same size produce different voltages.

Young entrepreneur

I have a letter from a 12-year-old by the name of Steve Knely. (I don't know where he lives because I misplaced the envelope.) The rest of us had better watch out because this young man is going somewhere. Steve has a videogame ma-

AN INVITATION

To better meet your needs, "Hobby Corner" will undergo a change in direction. It will be changed to a question-and-answer form in the near future. You are invited to send us questions about general electronics and its applications. We'll do what we can to come up with an answer or, at least, suggest where you might find one.

If you need a basic circuit for some purpose, or want to know how or why one works, let us know. We'll print those of greatest interest here in "Hobby Corner." Please keep in mind that we cannot become a circuit-design service for esoteric applications; circuits must be as general and as simple as possible. Please address your correspondence to:

Hobby Corner
Radio-Electronics
200 Park Ave. South
New York, NY 10003

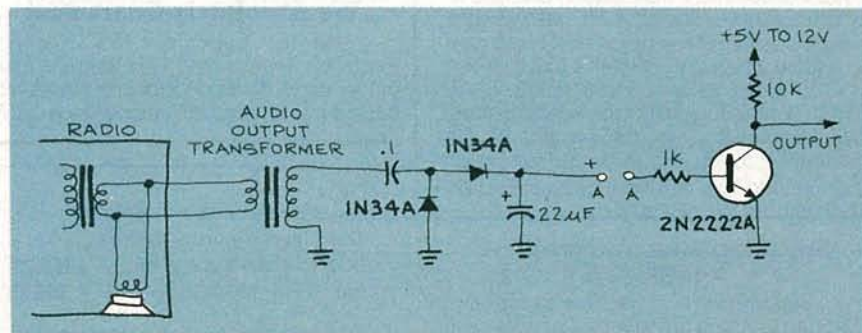


FIG. 2

chine and he is looking for the plans for a coin box similar to the ones used in the arcades. He wants the box to accept dimes, so he must realize he has to beat the competition when he starts out. That boy has a head on his shoulders.

Sorry, Steve, but I can't seem to find plans for a coin box. Perhaps you could figure out a way to use a key-operated switch to turn on a timer that would supply AC to the machine for a preset time-period. Hobby Corner has discussed timer circuits on several occasions in the past. Good luck!

Sound activation

Don Dawson of Ontario, Canada needs help on a circuit to activate some device when sound comes out of his radio. (I'm sure that many of you could use such a circuit to activate something that will wake you up when the clock radio doesn't.) Well, Don, the circuit you wrote me about is on the right track, but I would do it as shown in Fig. 2.

An audio-output transformer is connected "backwards" across the audio output of the radio. This transformer outputs still-higher-level audio, and it goes to the following rectifier. Note that germanium diodes are used instead of silicon ones—the voltage drop across them is lower.

The output at point A is just straight old direct-current created from the audio signal fed into the rectifier. Whenever sound comes from the radio, a positive voltage appears. If that voltage is not great enough for your purposes, an audio amplifier can be added between the transformer and the rectifier.

The DC output (at A) can be used for a variety of purposes. It can turn on a signal light, sound a tone, or do almost anything else. Not knowing what use Don intends for the device, I have shown a 2N2222A transistor switch connected to the output, but almost any NPN transistor can be used. As shown, the switch output varies between ground and the applied voltage. The circuit could as easily activate a relay or other low-voltage device. Of course, if your relay is sensitive enough, it can be operated right from point A without the need for the transistor switch.

Experiment!

Before closing this month's column, I would like to preach a small sermon. Surprisingly often, the mailbag contains a letter that refers to a circuit published here, in another article in **Radio-Electronics**, or even in another magazine. The question usually goes something like this: "Wouldn't it work better if you connected A to C instead of to B?" or "What would happen if you connected a wire from X to Z?"

Well, friends, let me suggest that you get down and dig into the matter for yourselves. Study the circuit as best you can and then try it out. If there are costly

OF ALL THE MICROWAVE DEVICES AVAILABLE ONLY THE ET-1000 . . .

PORTABLE "POCKET" "MICROWAVE"

HAS SO MANY USES

\$169⁰⁰



SETS ON TV!

Versatility — Works indoors, Channels 2 & 3, (or you specify) color or B&W TV. Great for apartments, hotels, office buildings, condominiums, anywhere an outdoor antenna cannot be used. Works best above ground level. (upstairs apts., etc.)

Description — All metal construction, high concentration parabolic reflector with dual element Yagi for center element at focal point for maximum gain. One year in testing and development. One year warranty, parts & labor. Personal check, M.O. — Return address, plus \$4.00 handling. Tex. res. add 5% sales tax. (214) 341-3397.

VIDEO ENG Supply Co.
9794 Forest Ln., Suite 106 • Dallas, Texas 75243

CIRCLE 15 ON FREE INFORMATION CARD


components involved, take whatever measures you can to protect them and *experiment*. Even a failed experiment is of value—you'll learn what not to do the next time!

It's easy to try out different things when you use a solderless breadboard. Just build a circuit on it and then start changing component values or connections until you find the combination that makes the circuit perform best. I learn quite a bit by experimenting—you can do the same. **R-E**



"They demand a franchise fee or they'll knock out our satellites."

The world of electronics gee-wizardry

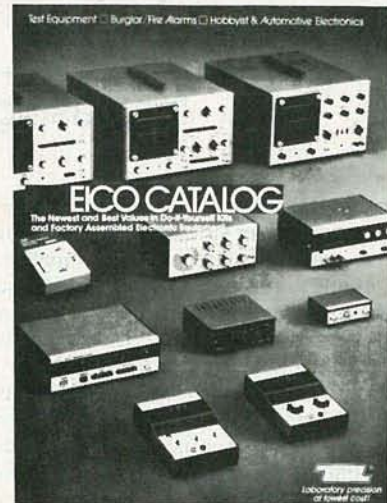

-YOURS FREE.

32-pages of test instruments—from the latest digital multimeters to the famous EICO scopes. Security systems. Automotive and hobbyist products. Kits and assembled. EICO quality. EICO value. For FREE catalog, check reader service card or send 50¢ for first class mail.

EICO® 108 New South Road
Hicksville, N.Y. 11801

CIRCLE 59 ON FREE INFORMATION CARD

ELECTRONIC PROJECTS FOR MUSICIANS

27 ALL NEW PROJECTS

\$14.95

Even if you don't know an ohm from a volt, Craig Anderton's newly revised and expanded book shows you how to build 27 accessories that enhance your sound and broaden your musical horizons.

If you're an old hand at musical electronics, you'll really appreciate that all of these processors, from Tube Sound Fuzz to Phase Shifter are compatible and work together without creating noise, signal loss, bandwidth compression or any of the other problems common to interconnecting effects from different manufacturers. There's even a complete chapter on how to modify and combine effects to produce your own custom pedal board.

Low cost project kits available from PAIA help make even your first exposure to electronics a pleasant, hassle-free experience and thanks to the sound sheet demo record bound into the book you know just how the completed device will sound before you even start.

CHARGE TO VISA OR MC TOLL-FREE
1-800-654-8657 9AM to 5PM CST MON-FRI

DIRECT INQUIRIES TO:

PAIA Electronics, Inc.

1020 W. Wilshire Blvd., Oklahoma City, OK 73116 - (405)843-9626

- | | RUSH MY COPY OF "ELECTRONIC PROJECTS FOR MUSICIANS", \$14.95 plus \$1 postage enclosed.
- | | SEND FREE CATALOG OF OTHER PAIA PRODUCTS.

name _____
address _____
city _____ state _____ zip _____

PAIA Electronics, Inc.

Dept. 5R, 1020 W. Wilshire Blvd., Oklahoma City, OK 73116
CIRCLE 52 ON FREE INFORMATION CARD

JULY 1983

THE DRAWING BOARD

Increasing current-handling capability of regulators

ROBERT GROSSBLATT

THE TREND IN MODERN LOGIC FAMILIES IS to make them operate with smaller and smaller amounts of power. (I suppose the ultimate goal is the family that can run on potential energy!) Lower power-requirements get rid of the necessity for wrist-thick cables and glass insulators, but there's an even more important benefit. Lower power means smaller, and less complicated, regulator circuits. Some IC's even have the regulator circuitry built onto the chip's substrate. Less current-draw means that the layout of the +V run on printed-circuit boards is much simpler. Remember that when heavy amounts of current are running through a trace on a board, a potentially troublesome voltage drop will be generated because of the resistance (however small) of the copper trace. That can lead to inductive oscillation and other nightmares.

That "low power" side benefit, however, can tend to make you a bit forgetful when you're developing a power supply. LED's, relays, and other things can still gobble up current at an alarming rate. A power supply that can deliver half an amp may seem perfectly adequate for, say, a CMOS circuit—and it is. Unfortunately, when we start asking the circuit to turn something on or light something up, the current draw is going to increase dramatically and our half-amp supply is rapidly going to drop dead.

The voltage-regulator circuit that we've been developing over the past few months can so far safely supply about a half amp over its full range, but it's a smart move to design it so that it can provide a lot more. Since the internal circuitry of the 7805 is limited to less than one amp, it's obvious that we're going to need some other device to provide the additional current.

Adding a pass transistor

In Fig. 1, we've added a transistor and a resistor to take care of the additional current. For simplicity's sake I haven't drawn in the rest of the circuit we've developed so far. All the current that goes into the regulator has to pass through R_B since it's in series with the regulator input. Ohm's law tells us that as the current flow through a resistor increases, so does the voltage developed across it. The base-emitter junction of Q1, a PNP transistor, is in parallel with R_B . As long as the current flowing through the resistor is be-

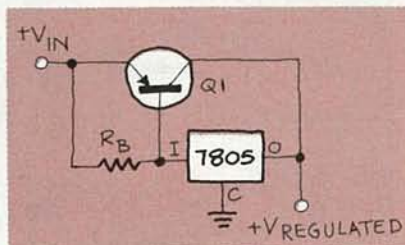


FIG. 1

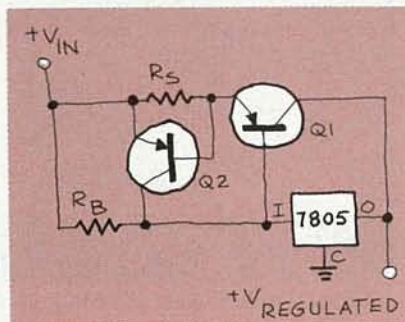


FIG. 2

low a certain level, just about all that's going to happen is that the resistor will get a little warm. At some point, however, the voltage drop across R_B is going to get high enough to turn on the transistor, which will start to pass current through its collector. That current is added to the current supplied by the regulator and allows the draw on our power supply to be increased by the amount that the Q1 can handle without blowing up.

Transistor Q1, then, is used as a switch that senses when the regulator output is near some limit and turns on to provide the extra current that the regulator can't handle. The turn-on point of Q1 is determined by the value of R_B and the base-emitter voltage of Q1. One other thing to be aware of is that the difference between the input and output voltages is going to change. Since Q1 and R_B are in series with the regulator input, the voltage drop across them has to be added to the inherent 2-volt drop of the regulator. That is important to remember when we're figuring out how much voltage we need at the output of the rectifier.

Short-circuit protection

Before we start doing any arithmetic to calculate the value of R_B we have to add some short-circuit protection to the circuit. I know you're thinking that we took care of that earlier, but we've now added

active components to the input. If the output is shorted now, all our earlier protection springs into action—but it only takes care of the regulator. The collector of Q1 is going to be shorted out and the transistor is going to start passing current through the short. It will rapidly exceed its maximum collector-current rating, and all you'll be able to do is administer the last rites.

That is, to say the least, an undesirable state of affairs. In Fig. 2 we've added a safety net for Q1 in the form of Q2 and R_S . Those of you with sharp eyes will recognize that those two new components form a switch in exactly the same manner as R_B and Q1. The same sort of analysis also applies.

All the current that flows through Q1 has to pass through R_S . When a certain point is reached, the emitter-base junction of Q2 is going to conduct and the transistor will turn on. When it does, it will lower the voltage across R_B and turn Q1 off. Since Q2 isn't going to turn on until the power supply is providing really large amounts of current, we need a hefty transistor there. It has to handle pretty close to the sum of the short-circuit currents of both the 7805 and Q1.

Since there are more components connected in the circuit between the base and emitter of Q1, the math needed to calculate the values of the two resistors is going to be more complicated. Rather than going through it however, let's make a few intelligent assumptions and see if we can make life easier.

If we use silicon transistors for Q1 and Q2, we know that the base-emitter voltage is going to be about .65 volts when the transistor is turned on. As long as the voltage is below that, the transistor will be turned off.

Now let's look at Fig. 1 again and assume that Q1 isn't there. The 7805 needs about 8 mA to operate—the rest of the current it passes is available to whatever circuit it's powering. The regulator can handle half an amp without any problem, but let's be on the safe side and arrange for Q1 to turn on when the regulator draw exceeds 250 mA. Since the turn-on voltage for the transistor is 0.65 volts, calculating the value of R_B is a snap: $R_B = E/I = .65/.250 = 2.6$ ohms

Now, it's true that the emitter-base junction of Q1 is in parallel with R_B so that bunch of arithmetic isn't strictly cor-

rect. Remember, though, that the apparent resistance of the junction when the transistor is in cutoff is pretty high. It's not really accurate to talk about the resistance of a transistor (or any semiconductor, for that matter), because they're dynamic devices and we should more properly refer to their "impedance." That's the DC resistance coupled with an AC component. For our "real world" circuit, however, the difference doesn't amount to much and we can ignore it.


If you look at Fig. 2, you'll see that we have to go a little farther in figuring the value of R_B . Since both R_B and R_S are across the emitter-base junction of Q1, both their values have to be taken into account when we figure the trip point of Q1. Once again, the "resistance" of Q2 in cutoff is high enough for us to ignore it and just work with the resistor values.

Since R_S has to pass all the current that flows through Q1, we have to decide what we're going to let the maximum current be. Five amps is a good value for our regulator circuit—more than that will cause design problems we don't want to get involved with. Just as was the case with Q1, Q2 will start conducting when its emitter-base voltage reaches 0.65 volts. If we want that to happen when Q1 is passing 5 amps, R_S has to be on the order of 0.13 ohms. The total resistance we need to turn on Q1 is 2.6 ohms. Since R_S must be .13 ohms, the new value of R_B will be 2.47 ohms.

Now, I'm the first to admit that those are pretty oddball values for resistors. You can't exactly amble down to your local resistor store and buy a 2.47 ohm resistor. There are ways around that, though.

Next month we'll take care of all the unfinished business and complete our regulator. We'll consider choices for Q1, Q2, and the proper wattage for the resistor. Not only all that, but, since we've all been working so hard we'll find ourselves treated to a surprise in the circuit that's not only useful, but that's one we get for free.

R-E

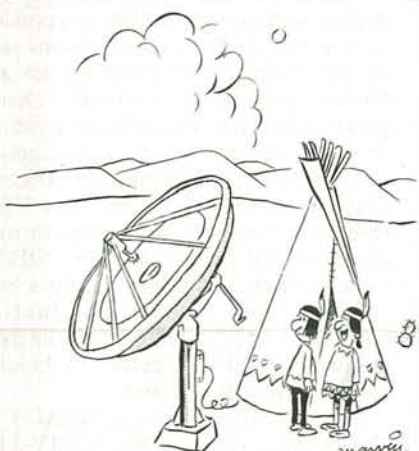


"I'm not too thrilled with its aesthetic value, but I sure dig the variety of channels I can get."

HOBBY MICROWAVE ANTENNAS


"COMPLETE SYSTEMS"




OUR DAISY ONLY \$89.50



OUR SOLID 20" ONLY \$94.50

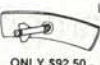


OUR LOW PROFILE ONLY \$92.50




A B \$18.00 TUNER
A B C \$22.00 TUNER

65 COAX 3 COAX TUNER W/SYSTEM "NOT FOR S.T.S."
WE REPAIR ALL MICROWAVE \$17.00




REDIAL PHONE ONLY \$19.50



CORD-FREE UP TO 1 MILE RANGE "PACER" MULTIPLEX \$297.50 TRUE TOUCH TONE

DEALER PROGRAMS AVAILABLE
COMPLETE BOMAN PRODLIN SATELLITE SYSTEM \$2250.00




SPACE AGE
14824 CAMDEN AVE. SAN JOSE, CA 95124
(408) 266-1511


CIRCLE 57 ON FREE INFORMATION CARD

TIMEX/SINCLAIR COMPUTER USERS


We Have The Books You Need



ART OF PROGRAMMING THE 1K ZX81.
How to use the features of the ZX81 in programs that fit into the 1K machine. 96pp. \$5.75 postpaid.



ART OF PROGRAMMING THE 16K ZX81.
How to use your 16K RAM pack and ZX printer to the full. 144 pp. \$6.95 postpaid.



ART OF PROGRAMMING THE ZX SPECTRUM.
Everything you need to know to put the ZX Spectrum to work for you. 144 pp. \$8 postpaid.

ELECTRONIC TECHNOLOGY TODAY, INC.
P.O. BOX 83
MASSAPEQUA PARK, NY 11762

Name: _____
Address: _____
City: _____ State: _____ Zip: _____
 Number of books ordered

POWER LINE PROBLEMS?



SPIKE-SPIKERS™... The Solution!

Minimize equipment damaging spikes and conducted RF noise to or from sensitive equipment. Transient surge protection plus low pass RFI hash filtering. All units 120V 15A.



MINI II \$44.95
Wall Mount
3-stage filter
2 sockets



QUAD II \$59.95
Wall mount. Dual 3-stage filter
4 sockets & light

DELUXE \$79.95
Dual 5-stage filtered ccts. 8 switch sockets main switch, fuse, light





Kalgio Electronics Co., Inc. Order Factory Direct
65 84 Ruch Rd., Dept. RE **215-865-0006**
Bethlehem, PA 18017
Out of State **800-523-9685**

DEALERS INVITED
PA Res. Add 6% • COD add \$3.00 + Shipping

BIG PERFORMANCE

small PACKAGE

Model 240




Video Generator

- Video output for all VCR, CCTV and Monitor Applications \uparrow 1 volt into 75 Ω load
- RF output: CH 2, 3, 4
- Scope trigger output for V or H sync
- 10 step gray-scale staircase signal for video circuit analysis
- 10 bar and 3 bar gated rainbow pattern
- 8 other dot, bar and line patterns
- Operates from 2 std. 9V batteries or 115VAC
- Single slide switch control
- Complete with test leads, protective cover, AC adapter, comprehensive instruction manual

PRICED UNDER \$200.

THE 240 DOES SO MUCH FOR SO LITTLE!!



HICKOK
the value innovator

THE HICKOK ELECTRICAL INSTRUMENT CO.
10514 Dupont Avenue • Cleveland, Ohio 44108
(216) 541-8060 • TWX: 810-421-8286

CIRCLE 46 ON FREE INFORMATION CARD

CIRCLE 85 ON FREE INFORMATION CARD

STATE OF SOLID STATE

Power MOSFET amplifiers

ROBERT F. SCOTT, CONTRIBUTING EDITOR

SOME OF THE NEWER HI-FI AMPLIFIERS are designed around power FET's in the output stage. That's because they offer low harmonic distortion, extended SOA (Safe Operation Area), and infinite current gain. The design, construction, and performance of such an amplifier is covered in a recent Intersil applications note. Its schematic diagram is shown in Fig. 1. The amplifier delivers 50 watts into an 8-ohm load. Its frequency response is ± 3 -dB from 20 Hz to 100 kHz while distortion is less than 0.25% from 20 Hz to 20 kHz.

The amplifier's design is unconventional in several respects: First, there are no rolloff or compensation capacitors. Instead, rolloff is provided by the input capacitance of the power MOSFET's (Q8 and Q9) that are arranged in a quasi-complementary output stage. The driver stage uses bipolar transistors and provides the usual voltage amplification and phase-splitting functions. Finally,

the positive power-supply line is bootstrapped to insure that the positive and negative half-cycles of the output signal are equal and maximized.

The input stage is designed around Q3, a U402 dual N-channel JFET in a differential configuration. A pair of J113 JFET's (Q1 and Q2) provide a constant current for the U402. That current controls the bias current of the output stage and is set by R18, a 10-turn 1K trimmer potentiometer. Bipolar transistor pairs Q4-Q6 and Q5-Q7 turn on in proportion to the input signal and provide drive current for output transistors Q9 and Q8, respectively. The drive current flows through R10 and R11 and develops the necessary gate-source voltage for the output transistors. The power gain of the output stage is quite high because of the comparatively high value of the resistors connected between gate and source.

The boot-strapped positive power-supply line, mentioned earlier, is needed

because if Q8 is to clip at the level of the positive power-supply line, its gate voltage must be driven beyond that point. Thus, a voltage higher than $\frac{1}{2}$ must be supplied to the input and driver stages. Instead of using an external power-supply with an output of more than 35 volts, the designers elected to bootstrap the $\frac{1}{2}$ -volt supply; that bootstrap circuit consists of D7, C4, D6, C9, and R15.

The closed-loop gain is determined by resistors R16 and R17. Capacitor C3 compensates for any offset in the output. In this design, the open-loop gain is set at 20 kHz by the gate capacitance of the power MOSFET's and the values of the gate resistors, R10 and R11. This frequency can be pushed higher by reducing the value of the gate resistor. However, this will increase the power dissipated in the driver stage—particularly in Q6 and Q7.

Data for this section of the column was taken from a pre-published copy of Application Note A0-40 (A Low-Cost Audio Amplifier Using Power MOSFET's by Bruce Rosenthal and Jim Meador) from Intersil, Inc., 10710 N. Tantau Ave., Cupertino, CA 95014.

High-voltage trigger

A series of new semiconductor devices for high-voltage bilateral trigger applications has been introduced by Motorola. Known as SIDAC's, the devices combine the high-voltage bilateral trigger functions of triacs with the simplicity and low cost of two-terminal diac triggers. The devices replace less reliable components such as neon bulbs for applications such as: high-voltage regulators, strobos and flashers, ignitors, line-transient clippers, pulse generators, fluorescent lighting, and high-pressure sodium-vapor lighting.

The devices are designed for direct interface with the AC power line. Upon reaching the breakdown voltage in each direction (104 to 135 volts) the SIDAC switches from a blocking state to a low-voltage "on" state. Conduction continues—as in an SCR—until the main terminal current falls below the holding current, typically 100 mA.

The new MK1V series of SIDAC's includes three devices, the MK1V-115, MK1V-125, and MK1V-135; with the last three numbers indicating the maximum repetitive break-over voltage. Fig-

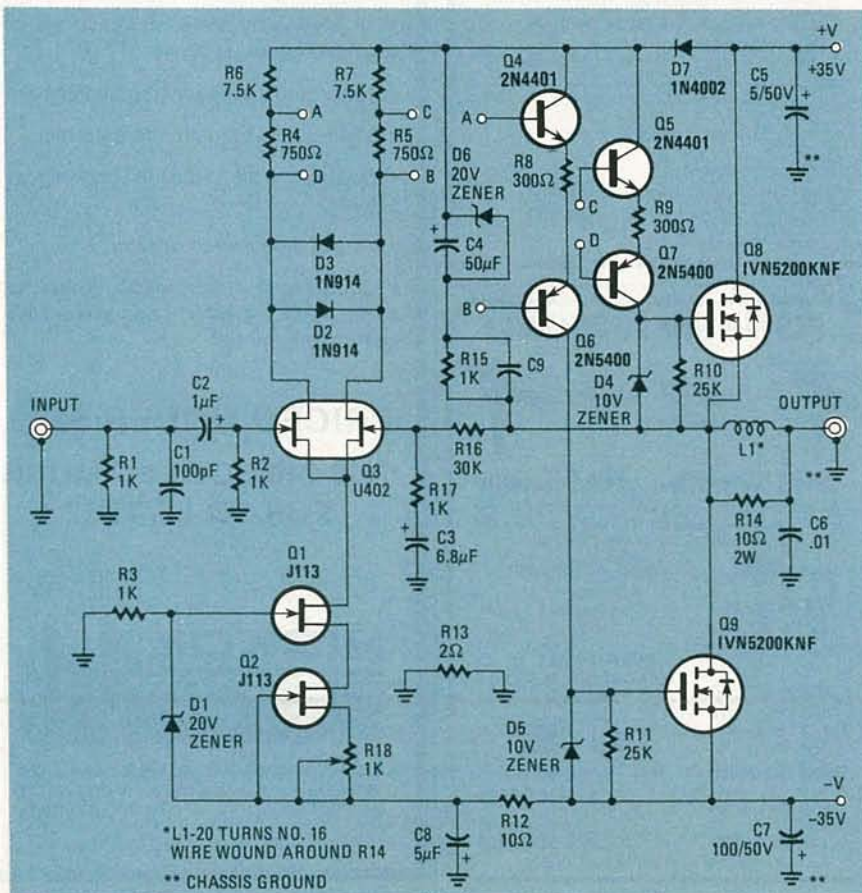


FIG. 1

ure 2 shows two SIDAC circuits; Fig. 2-a shows how electronic equipment can be protected against line-voltage transients and Fig. 2-b shows a SIDAC as a two-terminal trigger for a strobe or flasher application.

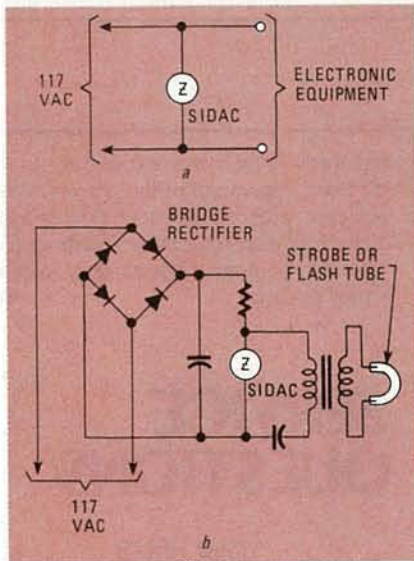


FIG. 2

The minimum breakover (breakdown) voltages are 104, 110, and 120, respectively for the three devices. Off-state repetitive voltage is ± 90 volts and repetitive peak off-state current is $10 \mu\text{A}$. Instantaneous on current is 1.0 amp RMS for each device. Maximum breakdown current (60-Hz sinewave) is $200 \mu\text{A}$. Forward "on" voltage is typically 1.1 while dynamic holding current is 100 mA.

Transistor data book

Field-Effect Transistors—Selector Guide and Cross Reference is a 32-page booklet chock full of valuable information on FET's. It opens with a brief description of all types of field-effect transistors and then comparing FET's to bipolar devices and then JFET's versus MOSFET's. This is followed by many listings of pertinent characteristics of JFET's, single- and dual-gate MOSFET'S, dual-gate DMOS as well as power MOSFET's.

A numerical index lists approximately 70 devices whose characteristics are listed in tables depending on their classification as Switches and Choppers, Power MOS, Low-Frequency Low-Noise Amplifiers, or High-Frequency Amplifiers. A Cross-Reference and Interchangeability Guide matches industry type numbers of approximately 1900 FET's with equivalent types from Motorola. The book concludes with illustrated FET applications that include an ionization-chamber smoke detector and a 500-MHz dual-gate MOSFET amplifier that is suitable for service in the front-end of a communications receiver.—**Motorola Semiconductor Products**, PO Box 20912, Phoenix, AZ 35036.

continued on page 89

Quick charge cordless soldering iron. Up to 125 electronics joints per charge. Total recharge in less than 4 hours. Isolated tip design. One of more than 2 dozen ISO-TIP and ORYX irons available. Write for free catalog and name of nearest distributor.

A Hot Tip on Cordless Soldering

No. 7700
QUICK CHARGE
Cordless
Soldering Iron

ISO-TIP®
ORYX®

WAHL CLIPPER CORPORATION
Sterling, Illinois 61081 • (815) 625-6525

CIRCLE 19 ON FREE INFORMATION CARD

Radio-Electronics REPRINT BOOKSTORE

- | | |
|---|---|
| <input type="checkbox"/> Build Your Own Satellite TV Receiver..... \$7.00 | <input type="checkbox"/> Radio-Electronics back issues (1981)..... \$3.50
(March, December 1981 not available)
Write in issues desired..... |
| <input type="checkbox"/> 8-Ball Satellite TV Antenna..... \$5.00 | <input type="checkbox"/> Special Projects (Winter 1980)..... \$4.00 |
| <input type="checkbox"/> Build Your Own Robot..... \$12.00 | <input type="checkbox"/> Special Projects (Spring 1981)..... \$4.00 |
| <input type="checkbox"/> TV Descrambler (January, February 1981)..... \$3.00 | <input type="checkbox"/> Special Projects #4 (Summer 1982)..... \$4.00 |
| <input type="checkbox"/> Video Entertainment (January 1982)..... \$2.00 | <input type="checkbox"/> Special Projects #5 (Winter 1983)..... \$3.00 |
| <input type="checkbox"/> Your Own Computer (October 1981)..... \$3.00 | <input type="checkbox"/> Special Projects #6 (Spring 1983)..... \$3.00 |
| <input type="checkbox"/> Radio-Electronics back issues (1983)..... \$3.00
(January, February 1983 not available)
Write in issues desired..... | <input type="checkbox"/> Radio-Electronics Annual 1983..... \$2.50 |
| <input type="checkbox"/> Radio-Electronics back issues (1982)..... \$3.00
(January 1982 not available)
Write in issues desired..... | <input type="checkbox"/> How to Make PC Boards..... \$2.00 |
| | <input type="checkbox"/> All About Kits..... \$2.00 |
| | <input type="checkbox"/> Modern Electrics (Vol. 1, #1)..... \$2.25
April 1908) |
| | <input type="checkbox"/> Electro Importing Co. Catalog..... \$4.95
(1918) (176 pp) |

To order any of the items indicated above, check off the ones you want. Complete the order form below, include your payment, check or money order (DO NOT SEND CASH), and mail to Radio-Electronics, Reprint Department, 200 Park Ave. South, New York, NY 10003. Please allow 4-6 weeks for delivery.

If you need a copy of an article that is in an issue we indicate is unavailable you can order it directly from us. We charge 50¢ per page. Indicate the issue (month & year), pages and article desired. Include payment in full, plus shipping and handling charge.

ARTICLE _____

MONTH _____ YEAR _____

PAGES _____

TOTAL PAGES _____ @ 50¢ each _____ TOTAL PRICE _____

MAIL TO: **Radio-Electronics** 7 83
Reprint Department, 200 Park Ave. South, New York, NY 10003 All payments must be in U.S. funds

Total price of order..... \$ _____

Sales Tax (New York State Residents only)..... \$ _____

Shipping & Handling (U.S. & Canada only) (Includes FIRST CLASS POSTAGE) \$1.00 per item..... \$ _____

All other (\$2.00 per item, sea mail)..... \$ _____

(\$4.00 per item, air mail)..... \$ _____

Total Enclosed..... \$ _____

Name..... _____

Address..... _____

City..... State..... Zip.....

SERVICE CLINIC

A dish full of bugs

JACK DARR SERVICE EDITOR

SATELLITE-RECEIVING SYSTEMS HAVE BECOME very popular of late, especially in rural areas where cable TV is pretty certain to remain merely a dream. Such systems, and the large outdoor antennas that they use, have their own peculiar problems, some of which can really "bug" you if you don't recognize the cause. Here are some cases that you may find interesting.

In the first case, the system had been working well, until suddenly the reception started getting worse and worse, and finally went out completely. Checks of the system showed nothing out of order in the electronics—LNA, downconverter, etc. That left only the dish antenna. Nothing was immediately apparent, but close examination finally showed the cause.

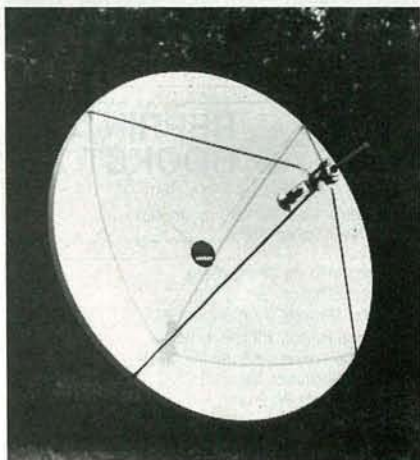


FIG. 1

A parabolic dish reflects the 3–4-GHz satellite signals on to a structure called a feed horn at the focal point of the dish (see Fig. 1). The feed horn directs the signal on to a small pickup device. There are various ways of picking up the signal; some antennas use very tiny dipoles, others use a waveguide, and so on. But one thing is common to all designs—there is a small hole at the end of the feed horn that the signal must pass through. In this case, the hole had been chosen by a female mud-dauber wasp to make her nest in. That busy little bug finds a deposit of wet clay, and carries vast quantities of it, considering her size, to your garage eaves, or anyplace else she can find to build nests, which are long tubes of clay. She loves to use holes in anything she can find—garden hose stored for the winter, a set of

socket wrenches in an open toolbox, a paint spray-gun left on the bench; etc. In this case, she had adopted the end of the feed horn—and it's hard to get a signal through a couple of inches of wet clay. Cleaning the aperture out, and guarding against further problems by tying a small piece of plastic wrap over the end, cleared up the problem.

In the second case the system worked nicely during the day, but at dusk the reception gradually got worse until it quit altogether. Once again a wasp eventually proved to be the source of the problem. That one is called the paper-making wasp; their nests, found under eaves, etc., look like a cone made of paper. Those wasps also like to adopt any kind of hole as their own. They were settling in the horn, and getting ready to build their nest there. During the day, they were all out foraging; at dusk, they came back and crawled into the horn. This is a big wasp, and it didn't take many to fill the feed horn completely.

Here's a word of caution. Those red-bodied wasps have a nasty disposition and when they sting you you'll know it. The best way to deal with them is to spray the feed horn with a strong wasp killer while it's "occupied," and come back later to clean it out. Once again, cover the opening with plastic wrap to prevent any future problems.

A different kind of animal

The last case we'll talk about deals with another kind of animal, one that can do far more damage. The animal I am talking about is man, and in particular the type of man that doesn't think.

One such critter was working as an assistant to a dish installer. The installer wrote me asking for help (incidentally, this is the only case of satellite trouble we've ever fixed—by mail, of course). One of his customers had complained that the system got very noisy in rainy weather. I told him to tighten all the coax fittings and then spray them with a clear acrylic coating to weatherproof them. The installer then sent his assistant out to spray the plugs. Spray them he did—with a penetrating oil (the fellow simply did not read the label before doing the job). Of course, the oil not only penetrated the plugs, but went right down to the coax's center conductor, dissolving the insulation as it went. All the coax had to be

replaced—which was expensive, to say the least. The moral of the story is: When you give someone instructions to do a job, make sure everyone understands exactly what's to be done. Otherwise, you're inviting disaster. **R-E**

SERVICE QUESTIONS

TWO HINTS

Here are a couple you might be interested in. I had a Wollesak 3M tape recorder that would not run in one direction. It had an odd clutch setup; when the direction was reversed, the idler ran up a spiral groove to engage the other drive. After cleaning the grooves, the idler worked, but the clutch facings were so badly worn that they slipped. The fix turned out to be fairly simple. We got some fairly thin gasket material from an auto supply store, and cut two new clutch facings out of it. Those were cemented to the idler and the whole thing works better than new.

The second hint is for those into restoring old radios. A good place to find information about parts and services is *Hemmings Motor News*, Box 380, Bennington, VT 05201. Their classified section includes ads for various components, as well as for such services as reconing speakers and restoring wood veneer.

Thanks to Rodney K. Schrock of Somerset, PA for these.

BURNING RESISTOR

I repaired a Satchell-Carlson 3C66, including installing a new CRT and so on. I noticed that the 22K resistor between the cathode of the 3A3 and the plate of the 6BK4 had burnt up and replaced it with one of equal value, but rated at 2 watts. The set worked and the customer took it home. A while later I got a call—the set had gone out again. When I got it back into the shop, I found that the same 22K resistor was once more charred beyond recognition. I'm puzzled; is it possible that a common carbon resistor won't work there?—L.P., Osceola, IA

I think your guess is right. I've had some embarrassing experiences trying to use common carbon-types in high-voltage circuits. The best bet here would be to use a glass-film or flameproof type. Carbon resistors, when used in high-voltage circuits, have to handle a lot more power than you might suspect at first glance. As a result, they get hot and burn up.

To tell you the truth, I'm not sure what that resistor is doing there anyhow. The only other time I've seen something like that was in an old Zenith. Incidentally, that resistor, which was a 1K unit, also burned up regularly. We eventually replaced it with a short piece of heavy hook-up wire.

WHICH CAPACITORS?

In the February, 1983 issue of Radio-Electronics you had a question about "flag waving" (instability) in older sets when using a VCR. We have a CTC-68 (1973) with that problem. You said to reduce the value of the AFC capacitors; are those the ones that are called out as C2 and C3 in the MAH001A module in that set?—L.K., Newark, CA

I took a look at the Sams Photofact (number 1378-2), and I'm pretty sure that they are; try smaller ones there. You might also try reducing the value of the 100K resistors, although I've never heard of anyone having to do that.

POSSIBLE CURE

A recent letter in your column described a problem with a Zenith 16Z7C19Z that was destroying 6HV5's; I may have a solution. In several of those I have found that the tube's screen resistor, a 1K unit, has either increased in value or opened. If that happens, it may produce the symptoms observed. If the 6HV5 has to be replaced, it is a good practice to check that resistor, especially if the tube's glass is cracked; the resistor can be checked from the top of the chassis. Hope that helps—Robert Cortner Jr., Davison TV, Buffalo, MO

VERTICAL PROBLEM

I have a Sears 528.41670314 with nothing but a bright horizontal line on the screen. The sound is OK. I checked the vertical circuit and found one problem: There was -50 volts on V6A where there should have been +300. I scoped the boost that fed that plate and found a very high ripple-voltage. Replacing C113C in the +300-volt line cleared up that problem. The moral is that you should always scope the B+ lines.

That bad capacitor was evidently allowing feedback that was upsetting everything. Incidentally, when you see mysterious vertical lines at one side of the picture, and the set uses flyback-derived low-voltage sources, always scope those. You may find, as we did in several sets, that the small filter-capacitor on the low-

YOUR EXCITING NEW HOBBY!

- ☛ Enjoy fantastic savings by assembling your own organ or piano.
- ☛ It's easy. No technical knowledge required.
- ☛ Just follow our clear, pictured instructions.
- ☛ Choose from many models from portables to consoles.
- ☛ Ask about our interest-free installment plan.



ORGAN & PIANO KITS



For Free Information Pack M40

Call Toll Free

800-233-3865

In PA 717-299-4327

or send coupon below

WERSI Dept. M40 P.O. Box 5318
Lancaster, PA 17601

- Free Info. Pack: Organ Piano
 Catalog & Demo Record (enclose \$6)

Name _____
Address _____
City _____ State _____ Zip _____
Phone (____) _____

Rep inquiries invited

CIRCLE 95 ON FREE INFORMATION CARD

voltage supply is open and you're getting a ripple voltage at the horizontal frequency!

Thanks to Lesley F. Dahm for this.

REPLACEMENT IC

I need a replacement or substitute for IC-200 in a K-Mart SKC-1940-AM; the part number is 56A49-2 or 56C49-2. I've looked everywhere I can think of.—C.H., Liberty Lake, WN

That set was made by Admiral for the Kresge Co. To my surprise I found a listing for the IC in the Sylvania ECG guide; it's an ECG-854. Incidentally, the letter in most Admiral part numbers doesn't mean much, hence both part numbers you listed are the same. If you need other Admiral parts, and can't get them locally, try their WATS-line number: 1-800-447-8361. Be sure to have the correct Admiral part number handy or they can't do much for you.

CLOCK IC

An Imperial clock radio, model CR-102, made for Superscope, was stuck in the calendar mode. The data sheet for the clock IC, an Electronic Arrays 7317, showed that an internal pull-down resistor at pin 24 enables the clock mode unless V_{SS} (20 volts in this case) is applied to the pin. When I measured, I found the

continued on page 99



GET MICROCONTROL WITH SAMS.

This fascinating book shows how you can turn a low-cost computer into a dedicated microcontroller for a robot, your home's environment, games, instruments, and more! You can even design your own microcontroller from scratch!

No previous design experience is needed. Just your brain, a microchip and Sams MICROCOMPUTER DESIGN AND TROUBLESHOOTING.

Starting with the basic controller functions, it covers sequencing, counting, timing, computation and management. It also answers such questions as, "What is a development system?" and "Can you use a Motorola chip with an Intel processor?" It even discusses how to put together a simple test instrument for locating board faults and other useful troubleshooting techniques.

Also included are detailed chapters on read/write timing, interfacing ROM and RAM, bus schemes, address decoding and other important design and system considerations. MICROCOMPUTER DESIGN AND TROUBLESHOOTING is like having a computer consultant in your pocket, yet it costs only \$17.95!

Get your hands on a copy and get computer control! To order MICROCOMPUTER DESIGN AND TROUBLESHOOTING (No. 21819), call 800-428-3696 or 317-298-5566 and ask for Operator 393.



SAMS BOOKS AND SOFTWARE
HOWARD W. SAMS & CO., INC.
4300 West 62nd Street
P.O. Box 7092
Indianapolis, IN 46206

Offer good in USA only and expires 10/31/83. Prices subject to change without notice. In Canada, contact Lenbrook Electronics, Markham, Ontario L3R 1H2. AD393

CIRCLE 32 ON FREE INFORMATION CARD

EQUIPMENT AND TRAINING NO OTHER SCHOOL CAN MATCH.

**NTS HOME TRAINING INVITES YOU TO EXPLORE MICROCOMPUTERS,
DIGITAL SYSTEMS AND MORE, WITH STATE-OF-THE-ART EQUIPMENT
YOU ASSEMBLE AND KEEP.**

Without question, microcomputers are the state of the art in electronics. And NTS is the only home study school that offers you training for this booming field with a choice of 3 production-model micro computers.

We'll explain the principles of troubleshooting and testing your microcomputer and, best of all, we'll show you how to program it to do what you want.

You'll use a digital multimeter, a digital logic probe and other sophisticated testing gear to learn how to localize problems and solve them.

Send for the full color catalog in the electronics area of your choice—discover *all* the advantages of home study with NTS!

NTS also offers courses in Auto Mechanics, Air Conditioning and Home Appliances. Check card for more information.



We believe that training on production-model equipment, rather than home-made learning devices, makes home study more exciting and relevant. That's why you'll find such gear in most of NTS's electronic programs.

For instance, to learn Color TV Servicing you'll build and keep the 25" (diagonal) NTS/HEATH digital color TV.

In Communications Electronics you'll be able to assemble and keep your own NTS/HEATH 2-meter FM transceiver, plus test equipment.

But no matter which program you choose, NTS's Project Method of instruction helps you quickly acquire practical know-how.



Simulated TV Reception 4.

3. The NTS/Heath HN-89A Microcomputer features floppy disk storage, "smart" video terminal, two Z80 microprocessors, with 32K RAM Memory, expandable to 64K on board. 4. The NTS/Heath GR 2001 Digital Color TV (25" diagonal) features specialized AGC-SYNC muting, filtered color and new solid-state high voltage tripler rectifier.

1. The NTS/Rockwell AIM 65 Dedicated Microcomputer A Single board unit featuring on board printer and display—4K RAM (expandable). Application Functions: Central processor—Controller/Monitor—Development System. 2. "The NTS/SYM-1 Microcomputer" 6502 Based CPU—4K bytes ROM (expandable)—1K RAM (expandable). 51 active I/O lines for versatile interfacing: disk drives, ASCII key boards, cassette tape, etc.

NTS NATIONAL TECHNICAL SCHOOLS

TECHNICAL-TRADE TRAINING SINCE 1905
Resident and Home-Study Schools
4000 SO. FIGUEROA ST., LOS ANGELES, CA. 90037



NATIONAL TECHNICAL SCHOOLS
4000 South Figueroa Street, Dept. 206-073
Los Angeles, California 90037

Please rush FREE color catalog on course checked below

- | | |
|---|---|
| <input type="checkbox"/> MicroComputers/MicroProcessors | <input type="checkbox"/> Auto Mechanics |
| <input type="checkbox"/> Communications Electronics | <input type="checkbox"/> Air Conditioning |
| <input type="checkbox"/> Digital Electronics | <input type="checkbox"/> Home Appliances |
| <input type="checkbox"/> Industrial Technology | <input type="checkbox"/> Color TV Servicing |

Name _____ Age _____
 Address _____
 Apt. _____ City _____
 State _____ Zip _____

- Check if interested in G.I. information.
 Check if interested ONLY in classroom training in Los Angeles.

COMPUTER CORNER

Recently-introduced microcomputers

LES SPINDLE*

NOT WILLING TO BE LEFT BEHIND WHILE well-established computer companies like IBM and DEC moved aggressively into the personal-computer marketplace, veteran personal-microcomputer manufacturers like Tandy/Radio Shack and Apple Computer recently came back with a vengeance.

After months of media speculation about its not-too-well-kept secret, Apple unveiled its new 32/16-bit *Lisa* computer. Both the *Apple IIe* and the simultaneously-announced Radio Shack *Model 12* were upstaged by the attention-grabbing *Lisa*.

If *Lisa* actually lives up to its pre-release promises, it may well give all competitors a run for their money. Priced just below \$10,000, *Lisa* barely fits into the "personal" or "small business" computer categories. Yet, its comprehensive list of features and integrated software may well compensate for its price. And there's plenty of room for expansion as the applications needs grow. But its biggest feature is its user-friendliness. It's aimed at those not well-versed in "computerese." Apple claims that a first-time user can put the *Lisa* to work in less than a half-hour.

The hallmark feature of *Lisa* (Local Integrated Software Architecture) is the extreme ease of use promised by its "mouse" device. The mouse is a palm-sized box connected to the terminal that allows the user to manipulate a cursor just by moving the mouse across the desk top. Pictorial symbols, such as a file folder, a wastebasket, and stationery, provide the user with an immediately-identifiable range of functions—such as filing a document, discarding old data, or writing a letter. By simply moving the cursor to the desired function, the user can perform functions that ordinarily require a good deal of key-punching, several commands—and occasional swearing by newcomers or those not familiar with the particular system—to accomplish.

Meanwhile, a menu at the top of the screen continuously lists the various functions within each application. By simply moving the mouse to point at one item, another detailed menu is displayed on the screen to guide the user step-by-step through that particular function. The



FIG. 1

interactive process continues, allowing even a complete computer novice to move quickly from one transaction to another with a minimum of time and effort.

The range of software that comes standard with the computer is also impressive, and—another important feature of the machine—data from each package is easily integrated with data from the other packages through the use of the versatile mouse. *LisaCalc* is a spreadsheet program for financial planning. The *LisaWrite* word-processing program integrates several text-editing functions for correspondence, reports, short memos, etc. *LisaGraph* integrates spreadsheet data with various graphs—bar, line, bar/line, scatter graph, or pie charts. That program can work in conjunction with the *LisaDraw* program for creating graphic designs. The *LisaList* program performs comprehensive data-base and filing functions, while *LisaProject* handles various critical-path and project-management functions. And that, too, can be integrated with the other programs.

To make the machine even more versatile, it is compatible with either BASIC, Cobol, or Pascal. Two operating systems—CP/M and Xenix—are supported.

The microprocessor for the *Lisa* is the MC68000, which combines a 32-bit internal architecture with a 16-bit external data path. The computer comes with one

megabyte of RAM. Two 5¼-inch floppy-disk drives are standard and a *Profile* hard disk supplies 5 megabytes of storage.

The CRT screen is a 12 inch, black-and-white display. The resolution is 364 × 720 pixels. A typewriter-style keyboard and numeric keypad are standard.

Two serial ports and one parallel port are included and allow for a multitude of additional functions. The *AppleNet* software package (not available as this was written) will enable local-area network communications. Data-base access to The Source, CompuServe, and other such services is possible with the *LisaTerminal* software accessory.

Another new Apple

Somewhat buried under all the hoopla surrounding *Lisa*, the *Apple IIe* (e is for "enhanced") is a successor to Apple's most popular computer—the *Apple II*. The system is priced below the similarly-configured *Apple II +*. The 64K unit offers easy expansion to 128K with a plug-in card. A low-cost 80-column card is also available.

The system is fully compatible with all *Apple II* software on the market. Meanwhile, enhancements to existing programs are rapidly being developed by various companies to add new features that are possible on the *Apple IIe*. Among new programs are the *Apple Writer II* word processor and *Quick File II*.

*Managing Editor, *Interface Age* magazine

The price for a complete system (with 64K memory, floppy-disk drive with controller card, 12-inch monitor with stand, and the 80-column card) is \$1,995.

Not to be outdone

Last, but not least, Tandy/Radio Shack craftily unveiled its latest offering almost the same day as Apple. The TRS-80 *Model 12* (priced at \$3,199 with one disk drive, \$3,999 with two) is Tandy's low-cost alternative to its popular *Model II*. While running all software designed for the *Model II*, the system looks very much like the 16-bit *Model 16* introduced last year.

The system includes a Z80A 8-bit processor, direct memory access, and vectored interrupts. Standard memory capacity is 80K, with either one or two 1.25-megabyte disk drives.

TRSDOS 4.2 is the unit's resident operating system—an enhancement of the TRSDOS 2.0. Double-density disks are supported, as well as double- or single-sided 8-inch floppy disks.

The display is a 12-inch green-phosphor monitor capable of 80 × 24 or 40 × 24 lines. Upper and lower case characters are supported, as well as 32 graphics characters. A detachable keyboard includes 82 keys, with a numeric keypad and eight special-function keys.

An optional card cage provides six slots for expansion. An upgrade card will convert the system to *Model 16* capability. High-resolution graphics and a 64K VisiCalc are other possible expansions.

Meanwhile, further expansion is available with the newly introduced 12-megabyte hard-disk drive, adaptable to the TRS-80 *Model II*, *16*, or *12* systems. The price is \$3,495 for the primary drive and \$2,495 for a secondary drive.

While the *Model 12* unveiling may not have been as exciting as Apple's double announcement, Radio Shack reportedly has more tricks up its sleeve, including a portable computer to rival the *Osborne I* and all of its imitators. In any event, it's clear that the pioneer microcomputer companies are determined not to be undone by the flood of competitors entering the market. As the competition heats up, the coming months should offer a number of surprises.

R-E

STATE OF SOLID STATE

continued from page 81

High-power 900-MHz transistors

Motorola has introduced three new 24-volt DC, 900-MHz power transistors. The line includes the MRF890, a 2-watt, 9.0-dB minimum-gain predriver; the MRF892 14-watt, 8.5-dB driver; and the MRF894 30-watt, 7.0-dB final amplifier. A chain of those three devices is capable of boosting a 100-mW UHF input signal (804 to 960 MHz) to 30 watts output. The

new transistors are intended for large-signal, common-base amplifier applications in industrial and commercial cellular-FM radiotelephone equipment. All three devices have guaranteed gain performance at 900 MHz, collector efficiencies of 55% minimum, and will withstand a 30:1 VSWR load mismatch at their rated voltages and power outputs. The MRF390 is packaged in a 305-1 case; the other two devices in the family in 319-04 packages. Prices in quantities of 100-499 are \$10.00, \$19.55, and \$30.60 for the MRF890, -892 and -894, respectively.—**Motorola Semiconductor Products**, Attention: Tom Bishop, PO Box 20912, Phoenix, AZ 20912.

Voltage regulator design data

Linear Voltage Regulators, (Application Note APN-27) is a 16-page booklet that provides detailed design information on a wide variety of voltage-reference circuits and voltage regulators. The material includes schematics, performance data, and descriptions of 18 circuits. Those circuits include band-gap voltage references, Zener-diode references, series and shunt regulators, and positive and negative voltage regulators. The designs include information on such parameters as temperature stability, noise voltages, and line and load regulation.—**Interdesign, Inc.**, 1255 Reamwood Ave., Sunnyvale, CA 94086.

R-E

DON'T FORGET



USE
YOUR
READER
SERVICE
CARD

64K Applesoft Compatible Micro-Professor II™

\$399.95

Dear Computer Enthusiast:
You can now have a 64K Applesoft-compatible computer for only a fraction of what you might expect. The Micro-Professor II™ is a full 64K computer with expansion capabilities. This great little computer has entry level pricing with professional grade quality. See for yourself. Try out the Micro II today.

Sincerely,
Chris Johnson
Customer Service

P.S. Act now and get a full size keyboard (a \$29.00 VALUE) ABSOLUTELY FREE.



Compatible: *Micro II is 98% compatible to Applesoft and 90% compatible to Machine Language. Most programs written for the Apple can be run directly or with slight modification.

Expandable! Add a printer, game paddles, floppy disk drives, speech and sound synthesizer, and Firmware ROM cartridges to expand the Micro II to cover many applications.

- | | | |
|--|--|---|
| Features: | Options: | Options: |
| <ul style="list-style-type: none"> • 6502 CPU • 16K BYTES of ROM (12K BASIC) • 64 BYTES of RAM • 46 one-key Basic Commands • Joystick Interface • Video Monitor & TV Interface • Printer Interface (Parallel) | <ul style="list-style-type: none"> • Tape Cassette Interface • Video Display Memory Mapped into System RAM • Systems Diagnostic Tape • Instant Color Graphics • Installation/Diagnostic/Basic Programming Manuals | <ul style="list-style-type: none"> • Floppy Disk with Controller (\$395.00) • Joystick Game Controller (\$24.95) • Printer Interface cable and software (\$34.95) • MPE-11 Printer (\$199.95) • Green Screen Monitor (\$99.95) |

MONEY BACK GUARANTEE

Order today and receive a **FREE** Full Size Keyboard for the Micro-Professor II™ — a \$39.95 value.

For Fast Service Call
Toll Free
1-800-426-1044

ETRONIX Dept. RE073
14803 NE 40th
Redmond, WA 98052

CIRCLE 10 ON FREE INFORMATION CARD

A 10 HOUR TAPE RECORDER

WAS \$125.00

NOW only \$95.00*
LONG PLAY

Modified Panasonic Slimline high quality AC-DC Recorder provides 5 continuous hrs. of recording & play back of top quality sound on each side of cassette for a total of 10 hrs. Built-in features include:

- Voice level control
- Digital counter, etc.



TDK DC-180 Cassette included.

PHONE RECORDING ADAPTER

Records calls automatically. All Solid state connects to your telephone jack and tape recorder. Starts recording when phone is lifted. Stops when you hang up.

\$24.50*

FCC APPROVED

VOX VOICE ACTIVATED CONTROL SWITCH

Solid state. Self contained. Adjustable sensitivity. Voices or other sounds automatically activate and control recorder. Uses either recorder or remote mike.

\$24.95*

*Add for ship. & hdg. Phone Call Adapter & VOX Recorder \$4.00. Cal. Res. add tax. Mail order, VISA, M/C, cod's ok. Qty. disc. avail. Money back guar. Free data. Dir. inq. inv.

AMC SALES, Dept. A, 9335 Lubec St., Box 928, Downey, CA (213) 902-4111 Phone 869-8519

CIRCLE 51 ON FREE INFORMATION CARD

JULY 1983

89

COMMUNICATIONS CORNER

Communications for the disabled

HERB FRIEDMAN, COMMUNICATIONS EDITOR

FOR ALMOST ALL MY WORKING LIFE I WAS associated with New York City's High School of the Air for Home Instruction. Using FM radio and sophisticated (for their day) telephone couplers and switching systems, the High School of the Air created real-time classrooms for disabled children who could leave home only infrequently, if at all.

The dial-up telephone system connected the homebound students to the studio console where they were mixed (electronically) with a teacher and his class. We could do straight classroom simulations, or even dramatic programs with music, sound effects, in-studio performers, and dial-up telephone performers. The studio mix was then fed to the transmitter and also out to up to 25 telephone users. (The budget-cutters eliminated the five teachers who serviced 1000 students, and thereby—after 35 successful years—destroyed the program.)

While it was easy for most disabled children to use the service, the blind and deaf had severe communications handicaps, which carried through to adulthood. There is little in the way of low-cost communications equipment for the disabled, and little information on what there is, even from the manufacturers and distributors. (Most of them simply appear concerned with charging as much as the traffic will bear.) Personal computers appeared to be an ideal solution for providing low- or moderate-cost communications for the deaf and blind, but

again, there is no centralized information source.

When several of our readers with disabled children inquired about using personal computers for communications, I ran up against the same problem they did—too little information. By chance, I got to talking with some people at The Source about the problem, and it turned out that they were working toward a similar goal of providing a bulletin board and information database for the disabled. In less than two weeks the system was in place.

Users of The Source can go directly from the command mode to a bulletin board and message center for the disabled by typing "POST R DISABILITY" on the terminal. Manufacturers and users can leave general information or specific details concerning special personal-computer equipment specifically intended for the disabled. Also, through the Texas Instruments *Texnet* tie-in with The Source, the UPI news service is prepared for voice output through a personal computer with a speech synthesizer. (Got the idea of what we're looking for? We want everything in communications for the disabled!)

If you have any specific knowledge about personal-computer or communications equipment that would benefit the disabled—such as a moderately priced Braille printer for the Apple computer, or a store-and-forward with voice output for any personal computer—put it

up on The Source or pass it along to me here.

Saving money by telephone

The way I heard it a few years ago, the telephone was dead. Microprocessors, satellites, and systems that we hadn't even yet conceived were going to make the telephone system as obsolete as the singing telegram. Well, here it is a few years into the computer age and the telephone is livelier than ever thanks to new developments. We're getting more low-cost telephone systems than we could imagine, all thanks to the computer, microwave communications, satellites, and whatever new inventions our engineers will conjure up in the coming years.

Just as soon as I finish typing this column I am going to telephone the editor and explain why it's late. It's a call in the same part of the state, but it will cost a lot less than usual. I will press two keys on the keypad built into the mouthpiece of my phone, and a computer also built into the mouthpiece will dial Sprint. Sprint is one of several communications services that provide short- and long-distance telephone service that is less expensive than the equivalent service from the telephone company (which we'll call Telco). When I hear the Sprint answer-tone, I will press two more keys, and the mouthpiece computer will transmit my identification, travel code (which I can use from coast to coast), and the number that I'm calling. A Sprint computer will recognize who I am and route my call through its facilities to New York City, put it back into the Telco system, and connect my call. I will be billed by Sprint, and pay about 40% less than I would for a telephone call made in the standard way. My only extra charge will be the local one for the connection to Sprint.

As you might guess, the secret to all that is a computer that does the Telco-system interconnects and the monthly billing. There are several ways that such a communications system can be put together, so we'll construct a "basic" model that will help you understand this new wrinkle that's shown up in telephone communications.

First, it's possible to purchase "bulk" telephone service from Ma Bell at lower rates than regular subscribers pay. Then, there are private and public microwave systems through the main business corri-

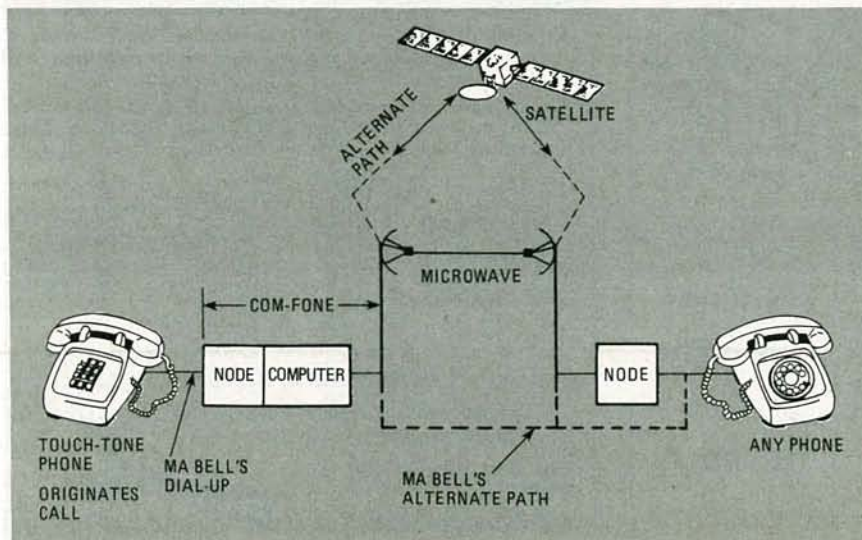


FIG. 1

SAVE!

MONEY • TIME • FREIGHT

- ♪ QUALITY STEREO EQUIPMENT AT LOWEST PRICES.
- ♪ YOUR REQUEST FOR QUOTATION RETURNED SAME DAY.
- ♪ FACTORY SEALED CARTONS—GUARANTEED AND INSURED.
- ♪ SAVE ON NAME BRANDS LIKE:

PIONEER	JVC
KENWOOD	TEAC
MARANTZ	SANSUI
TECHNICS	SONY

**AND MORE THAN 50 OTHERS
BUY THE MODERN WAY
BY MAIL—FROM**

illinois audio

BANK CARDS ACCEPTED
12 East Delaware
Chicago, Illinois 60611
312-664-0020
800-621-8042

CIRCLE 94 ON FREE INFORMATION CARD

For Home or Business
WHAT...WHEN...HOW...

BE A COMPUTER PROGRAMMER

Train at home in spare time! No previous experience needed! Now you can learn it all! Computer programming...computer applications...computer games...everything you ever wanted to know about computer operations! Write your own computer programs or use hundreds of programs already available...budgeting, real estate, bookkeeping, expenses, investments, interest, taxes, shopping lists, vacation planning, addresses, phone numbers, routing...even foreign languages and graphics.

You'll know what really happens when you have a computer problem with a bank, store, loan company, oil company, utility or anyone else. You'll be able to talk their language...understand why and how things happen...to be able to take the offensive when you're the victim of a computer error. Experts explain everything in easy-to-understand language with step-by-step directions.

- TIMEX COMPUTER INCLUDED WITH YOUR TRAINING • Plugs into any TV
- SEND FOR FREE FACTS!

IGS
SINCE 1891

COMPUTER TRAINING, Dept. DE063
Scranton, Pennsylvania 18515

Please rush me free facts and color brochure that tells how I can learn computer applications, programming and operation at home in spare time. No cost. No obligation.

Name _____ Age _____
Address _____
City/State/Zip _____

dors, such as New York to Atlanta, or Los Angeles to Chicago, or Houston to everywhere. Since communications circuits are often kicked upstairs to a satellite (because it's easier to get over a mountain that way), it's a safe bet that part of our budget communications will involve satellite transmission (as is often the case with "regular" telephone service).

Figure 1 shows how a hypothetical system we'll call "Com-Fone" might be used to provide you with low-cost telephone communications. Starting at point "A," you use your standard phone with rotary or *Touch-Tone* dialing to get into the nearest Com-Fone node (switching center). Com-Fone's computer answers, and on hearing the answer tone, you transmit your identification code using *Touch-Tone* frequencies. You cannot use the standard telephone dial pulses because the Com-Fone computer "understands" only the DTMF (Dual-Tone Multi-Frequency) tones used by the *Touch-Tone* system. Still using tones, you dial the area code and number you want. The computer checks your I.D. If it's not valid, the computer does an intercept and a computerized voice informs you that that's the case. If your account is clear, the computer seizes an open communications path that may be part microwave link, part satellite, and part Ma Bell's wiring. At the receiving end, the computer connects back into Ma Bell's system and dials the local telephone number that you are trying to reach.

You pay the telephone charge (to your local telephone company) from your phone to the Com-Fone node. Com-Fone's computer calculates and bills you for the charges for service from the node right up to the party you called. Com-Fone's costs (what Com-Fone must pay Ma Bell) at the receiving end—where your call re-enters Ma Bell's wiring—are calculated and built into your Com-Fone charges. But because Com-Fone purchases bulk telephone-service, your total bill is reduced.

Oh yes! That computer inside the telephone mouthpiece! That's not hypothetical, it's a *Soft-Touch* dialer from Buscom Systems, Inc. (4700 Patrick Henry Drive, Santa Clara, CA 95050) that provides *Touch-Tone* dialing on rotary dial telephones. It substitutes a microphone and miniature keypad for the existing carbon microphone. It has 80 programmable memories that are accessed by pushing two buttons. The memories are maintained by subminiature batteries that last several years. The memories stack automatically, so you can program any series of access numbers and codes; all of them are transmitted by pressing the two buttons representing the initial memory address.

Next month, when we continue, we will look more closely at that *Touch-Tone* autodialer. We'll also be looking at other applications for *Touch-Tones*. R-E

SEE YOUR DEALER TODAY

FROM

'Firestik'®
ANTENNAS
ACCESSORIES

HERE'S A TIP
THAT'S PERFECT!

AM/FM AUTO RADIO
AND CB

'Firestik'® II
GOLDEN SERIES

BARE-HANDS TUNABLE
"NO TOOLS NEEDED"
HIGH PERFORMANCE ANTENNAS

ALSO ANTENNAS FOR
CORDLESS TELEPHONES
MONITOR SCANNERS

Dealer & Distributor Inquiries Invited
SEND FOR FREE CATALOG

'Firestik' Antenna Company
2614 East Adams/Phoenix, AZ 85034

Name _____
Street _____
City _____
State _____ Zip _____

Serving the CB and
Communications Market Since 1962.

5-YEAR REPLACEMENT WARRANTY

CIRCLE 40 ON FREE INFORMATION CARD

NEW
1983 Products

TINKER TRON
MINI POWER SUPPLIES

•5 Models •100mA to 3.0A •1.5 to 20 Volts

MODEL	VOLTAGE	DIGITAL DISPLAY		AMP ADJ.	CURRENT	PRICE
		I	V			
1530A	1.2-15V	Yes	Yes	Yes	3 Amp	\$216.00
2020A	1.2-20V	Yes	Yes	No	2 Amp	179.95
0530A	5V	Yes	No	No	3 Amp	149.95
1230B	12V	Yes	No	No	3 Amp	149.95
1295B	5, 9, 12V	No	No	No	100mA	69.95

The Phaser II (Model P-2280)

Infrared Transmitter and Receiver Switch
* Turn Appliances On/Off
* Range Up to 30'
* Switch Handles 500 Watts
* Directional (Just Point)

\$29.95

Magic Touch Ceiling Fan/Light Control

* Works on any Fan/Light
* No Additional Wiring
* Controls Fan Speed/Light Brightness
* Eliminates Motor Hum (Not Triac)

\$39.95

This new concept totally simplifies ceiling fan installation. Just remove light fixture and switch, and replace with your fan and the Magic Touch control system. With no addition to your existing wiring, you can control fan speed and light brightness.

Encapsulated Modules for PCB Mount

(Application notes included)
Z500 AUDIO AMPLIFIER — 4-12V operation, 4mA quiescent current, output 500mW with 9V supply and 8 ohm speaker. Requires only a speaker and 10K pot. \$6.95 3/\$18.00
Z100 PREAMP — (for additional amplification) \$5.95

DC to DC Polarity Converters

Generate negative output from positive input voltage

MODEL	INPUT VOLTAGE	OUTPUT VOLTAGE	I (max)	PRICE	3 or More
PC100	2.0-6.0	-(2.0-6.0)	15mA	\$7.25	\$6.35
PC200	6.1-10	-(5.0-9.0)	15mA	\$7.25	\$6.35

Solid State Relays

Optically coupled, TTL, CMOS compatible, zero crossing (Resistive or Inductive loads)

MODEL	INPUT DCV	mA	OUTPUT V (max)	I (max)	PRICE	3 or more
SST20AC	4-15	25-1.0	120VAC	5A	\$10.95	\$9.60
SS050DC	4-15	25-1.0	50VDC	1A	9.95	8.85

Send 25c for our 1983 Summer Catalog of electronic parts (free with order) including resistors, capacitors, semiconductors, plastic boxes, motors, etc.

LOWEST PRICES — SAVE UP TO 50% OR MORE!

Add \$2.00 shipping to each order. In Texas add 4% tax. \$10.00 minimum order.

VISA

TINKER TRON
P. O. BOX 53128
LUBBOCK, TEXAS 79453
806/745-2228

MasterCard

All TinkerTron Products Have A Ten Day Money-Back Trial Period.

CIRCLE 30 ON FREE INFORMATION CARD

USING LORAN-C ETC.

continued from page 67

idea of using Loran-C for frequency-standard checking/calibration. The GRI source, driven from a local frequency standard, is used to trigger the scope externally. The Loran-C signal, either from a suitable receiver or from the RF front end (the circuit shown in Fig. 7) is displayed, and the sweep time is adjusted to observe some part of a particular signal. The Loran-C signal at a given GRI can be momentarily speeded up or slowed down by "bumping" the thumbwheel switches of the GRI generator to place the Loran-C trace at some point on the scope so that a very small part of the leading edge of a pulse can be observed. Then, by determining the length of time it takes the Loran-C signal to move a given distance across the screen of the scope, the fractional frequency-stability of the local 1-MHz standard can be determined.

How is that time measurement used to obtain a measurement of the relative frequency stability? The two measurements can be related by calculus; we will only give the result: $\Delta f/f = -\Delta t/T$.

Here, Δt is the change in time (the drift) read over a measurement time, T .

If, for example, the result was 1.5×10^{-6} , it would indicate that the oscillator's actual frequency was its nominal frequency (in this case 1 MHz) multiplied by 1.5×10^{-6} . In this case, the actual frequency of the standard would be 1.0000015 MHz. Typically, with a good (proportional oven controlled) standard, the Loran-C signal will only move to the right or left about 10 $\mu\text{s}/\text{hour}$. That implies an offset of the order of 3×10^{-9} .

The expanded scope-trace (about 10 $\mu\text{s}/\text{division}$) is useful for examining the actual RF-carrier output from the pin-11 test point of the MC1357 detector in Fig.

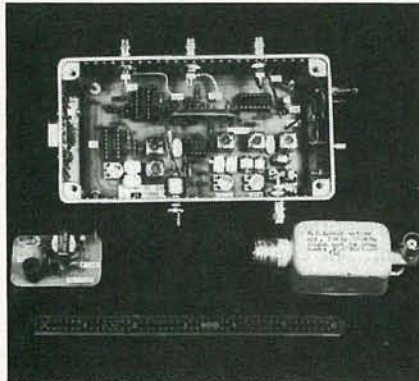


FIG. 10—EXPERIMENTAL MODEL of the Loran-C envelope detector with active antenna preamp and housing.

TABLE 1—GRI RATES

GRI ($\mu\text{s}/10$)	CHAIN	COUNTER CODE
4990	Suez Canal	1F3
4990	Central Pacific	1F3
5930	Canada East	251
5990	Canada West	257
7930	North Atlantic	319
7960	Gulf of Alaska	31C
7970	Norwegian Sea	31D
7980	US Southeast	31E
7990	Mediterranean Sea	31F
8970	US Great Lakes	381
9940	US Westcoast	3E2
9960	US Northeast	3E4
9970	NW Pacific	3E5
9990	North Pacific	3E7
10000	(HF Radar 0.1s)	3E8
8000	(USSR West)	320
5000	(USSR East)	1F4
1000	(0.01s)	064
100	(0.001s)	00A
10	(0.0001s)	001


7. The envelope of that signal at the output of the op-amp-filter can also be observed, and the movement of the inflection point or zero crossing can be recorded at hourly intervals to check the clock-stability.

When using receivers like the FRG7700 for Loran-C, the envelope rise-time is smeared out over 150 μs or so. But by observing the change of that signal at daily time intervals, with the clock and GRI source operating continuously, the frequency stability of the clock can be determined without any special Loran-C front-end hardware.

For Loran-C DX hunting on late winter evenings when the noise level is low and DX is coming in from other stations such as Allouis in France on 164 kHz, the GRI rate can be set to try to find some chain not normally observed in the USA. That is done by examining the whole GRI frame in detail (with the oscilloscope in the expanded-sweep mode) and slowly bumping the GRI rate a few tens of milliseconds at a time to find weaker sky-wave pulses standing still. Loran-C signals from the USSR using GRI rates of 8000 and 5000 can sometimes (although rarely) be observed that way. The main problem in looking for weak signals is the cross-rate interference from other chains drifting by the desired small-amplitude signal on the scope trace.

A photograph of an experimental model of a Loran-C RF-envelope detector is shown in Fig. 10. Circuit-board layouts have been prepared for the Loran-C RF detector and the GRI generator. Contact: R. W. Burhans, 161 Grosvenor St., Athens, Ohio 45701. Include a SASE for information on the availability of these boards for experimental use. **RE**

NOW AVAILABLE: FREE ZX81/TS1000 CATALOG

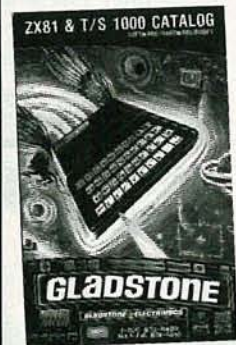

New from Gladstone Electronics! Our ZX81/TS1000 catalog will take you where no one has dared go before! You will view the widest selection of up-to-date software, books and hardware add-ons available to get the most from your personal computer. This exciting new 34 page color catalog lists arcade, fantasy and family games, business and educational programs; books for beginners as well as experienced users; hardware add-ons and other peripherals for use with ZX81/TS1000 Home Computer!

Use the convenient coupon below and send for your FREE catalog TODAY!

Call toll free 1-800-833-8400

N.Y. (716) 874-5510

In Canada call toll free 1-800-268-3640

GLADSTONE Electronics

Please rush me this exciting new ZX81/TS1000 catalog.

Name _____


Address _____

City _____ State _____ Zip _____

Mail to: 1585 Kenmore Ave., Buffalo, N.Y. 14217

In Canada: 1736 Avenue Rd., Toronto, Ont. M5M 3Y7

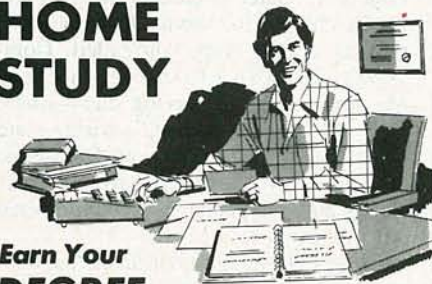Put Professional Knowledge and a COLLEGE DEGREE in your Electronics Career through HOME STUDY



Earn Your DEGREE

No commuting to class. Study at your own pace, while continuing your present job. Learn from easy-to-understand lessons, with help from your home-study instructors whenever you need it.

In the Grantham electronics program, you first earn your A.S.E.T. degree, and then your B.S.E.T. These degrees are *accredited* by the Accrediting Commission of the National Home Study Council.

Our *free* bulletin gives full details of the home-study program, the degrees awarded, and the requirements for each degree. Write for *Bulletin R-83*.

Grantham College of Engineering
2500 So. LaCienega Blvd.
Los Angeles, California 90034

Radio-Electronics #7 \$2.25 SUMMER 1983 45784

Special Projects

The magazine for people who build electronic projects

SYNDLE
The Electronic Candle that flickers like a Wax Taper

MAKE PRO CABINETS
for Home-Brew Projects

Build it for JUN

- 3-Band Shortwave Converter
- Electronic Slot Machine
- Preamplifier for moving coil Phono Cartridge
- Soundbox-80 for Computer Game Sounds
- Prototyping Power Supply

Test Gear Projects

- Ribbon-Cable Tester
- Meg-O-Dapter for DVM
- Mini-Audio Generator
- Scope Calibrator
- Single Sweeper One Blanker

PLUS....

JBL Sound System
for the musician!

Special Projects #7

■ IF YOU'RE THE KIND OF READER that doesn't want to wait, you can get your copy of **Special Projects #7** now. This 100-page magazine is crammed full of electronic projects that you won't be able to wait to build for yourself. There's a Digital Prototyping System, a Soundbox to add sound to TRS-80 games, a Code-Practice Oscillator, Electronic Flasher for your car, plus all the other articles listed on the cover above. You get a total of 21 fun-filled build-it stories.

■ TO HELP YOU TO BE SURE that you don't miss any future issues—SUBSCRIPTIONS ARE NOW AVAILABLE!

■ YOU CAN HAVE THE NEXT FOUR ISSUES of **Special Projects** delivered directly to your home for only \$9.00. We pay the postage. If you want the next eight issues, you can even save a dollar off the newsstand price. Get eight issues for \$17.00.

ON SALE

AT YOUR LOCAL NEWSSTAND

JUNE 2

Reserve your copy now!

Get every issue SUBSCRIBE TODAY!

Use the order form below

■ EVERY ISSUE OF SPECIAL PROJECTS will continue to contain a variety of construction articles to suit every taste. In addition, feature articles on electronics fundamentals, test equipment and tools will round out each issue. Of course, we will continue to provide new product and literature listings to keep you up to date on the latest developments in electronic technology.

■ GET IN ON THE ACTION! Order your next issue of **Special Projects** today. Use the convenient order coupon below.

Special Projects #7

DETACH AND MAIL TODAY TO:
SPECIAL PROJECTS
SUBSCRIPTION DEPT.
200 PARK AVE. SOUTH
NEW YORK, N.Y. 10003

CASH WITH ORDER ONLY RE-7
Allow 6-8 weeks for the first issue to arrive.

Send me _____ copies of **Special Projects #7** at \$2.25 plus \$1.00 postage and handling for U.S., Canada and Mexico. U.S. funds only. All others add \$2.00.

I want to be sure I don't miss any issues. Send me the next four issues of **Special Projects** for \$9.00: starting with #7. Postage is free in U.S. For Canada add \$3.00. Foreign add \$7.00.

I want to be sure I don't miss any issues and want to save \$1.00 too. Send me the next eight issues of **Special Projects** for \$17.00: Starting with #7. Postage is free in U.S. For Canada add \$6.00. Foreign add \$14.00.

Please print

(Name)

(Street Address)

(City)

(State)

(Zip)

DRE

ANALOG CIRCUITS

continued from page 72

complex passive- and active-circuits around an op-amp. A triangular wave can be formed by adding the op-amp integrator shown in Fig. 13 to the output terminals of a squarewave generator like the one shown in Fig. 12.

Among the most popular oscillator circuits is the Wien bridge. A basic transistor circuit using the Wien bridge is shown in Fig. 14. Here, the Wien bridge circuit is placed around a single-ended differential amplifier; it consists of the series and parallel-connected R-C networks. Current is fed back through that filter network from the output to the input. Oscillation

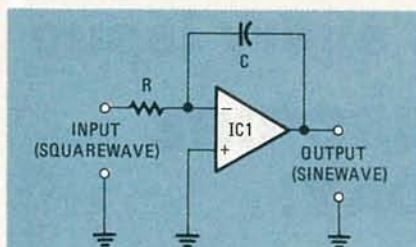


FIG. 13—AN INTEGRATOR, such as the one shown here, can be used to change a square-wave into a triangular wave.

occurs if the forward gain of the amplifier is greater than 3 because the output at the junction of the series and parallel R-C circuits is $\frac{1}{3}$ of that at the collector of Q2. The frequency of oscillation is $1/2\pi R_1 C_1$, assuming that $R_1 = R_2$ and $C_1 = C_2$.

A similar circuit can be built around an op-amp, as shown in Fig. 15. Positive feedback is applied through the R-C Wien bridge to the non-inverting input of the op-amp. Negative feedback is applied through a resistor divider to the inverting input. The frequency of oscillation is found exactly as it was in the previous example. Two Zener diodes are included

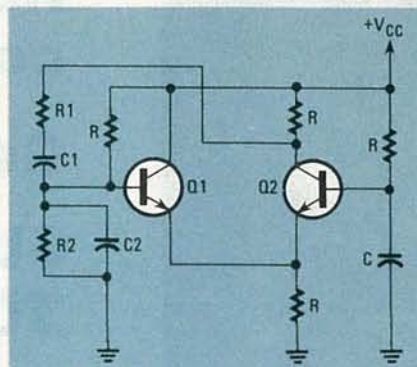


FIG. 14—ONE OF THE MOST POPULAR sine-wave generators, the Wien-bridge circuit has been around since the days of vacuum tubes.

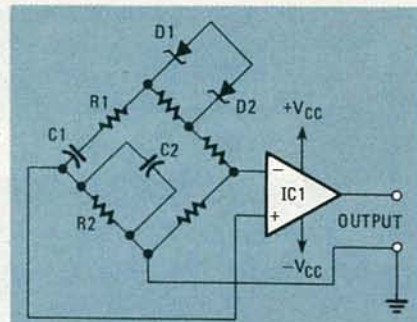


FIG. 15—ANOTHER EXAMPLE of the Wien bridge, this one is built around an op-amp.

in the circuit to keep the output voltage, when at a peak, from putting the op-amp circuit into saturation. If it did go into saturation, the circuit would remain in that state and oscillation would no longer take place.

High frequency

Unwanted feedback is quite likely to occur in high-frequency circuits. It has many causes: To give just one example, signal at an output can be coupled back to the input through adjacent wiring or through stray capacitances in a circuit. In the next article in this series, we will explore and determine just what its effects are and how to handle them in transistor circuits. **R-E**

TAFT

ELECTRONIC SALES

HAS IT ALL FOR LESS

NORTH AMERICAN SOAR CORPORATION



- MS-3015-15MHZ DUAL TRACE PORTABLE
- MS-6020-20MHZ DUAL TRACE
- MS-6035-35MHZ DUAL TRACE
- MS-6050-50MHZ DUAL TRACE
- MS-6100-100MHZ QUAD TRACE

CALL FOR LOW, LOW PRICES

DIGITAL MULTIMETERS

FLUKE

- 8060A \$345
- 8062A \$275
- 8022B \$143
- 8020B \$193
- 8024B \$247

BECKMAN

- 300 \$109
- 310 \$129
- 330 \$199

Xcelite®



- TC-100ST XCELITE'S BEST CONTAINS 53 TOOLS \$329
- TC-150ST SMALLER UNIT CONTAINS 23 TOOLS \$279

BK PRECISION



- 1476P-10MHZ DUAL TRACE \$439
- 1477P-15MHZ DUAL TRACE \$495
- 1479BP-30MHZ DUAL TRACE \$609
- 1570P-70MHZ QUAD TRACE \$1079

PRICES INCLUDE PROBES

6.5MHZ OSCILLOSCOPE AT ONLY \$188.00



- 6.5MHZ
- 75MM ROUND SCREEN
- 10mV/DIV. SENSITIVITY
- INTERNAL OR EXTERNAL SYNC
- XY VECTORSCOPE CAPABILITIES
- 8½ LBS. LIGHT & COMPACT
- OUTPERFORMS UNITS COSTING MUCH MORE

ONE-YEAR WARRANTY

20,000 OHM/VDC V-O-M



- DC/AC VOLT TO 1 KV
- FUSE & DIODE PROTECTION
- 17 RANGES ON MIRROR SCALE
- LEVER SELECTOR RANGE SWITCH

\$19.88 ONE-YEAR WARRANTY

VIDEO CONTROL CENTER



\$16.88

REMOTE CONTROL ACCESS OF ALL VIDEO, TV OR CABLE INPUTS TO TV SET. 4 INPUTS TO ONE OUTPUT

46 CHANNEL VCR CONVERTER WITH FINE TUNING \$27.88



WATCH ONE CHANNEL AND RECORD ANOTHER

STABILIZER/VIDEO FADER/ ENHANCER/RF CONVERTER



\$99.88

ONE UNIT DOES IT ALL

TAFT ELECTRONIC SALES

68 W. 45th Street
N.Y.C., N.Y. 10036

CALL
212-575-8632

- MASTER CHARGE
- VISA
- MONEY ORDER
- CHECK
- 25% DEPOSIT ON C.O.D.'s

ADD FOR SHIPPING
UP TO \$300.00 - \$5.50
OVER \$300.00 - \$8.00
N.Y.S. ADD SALES TAX

NEW BOOKS

For more details use the free information card inside the back cover

MY INVENTIONS, The Autobiography of Nikola Tesla (Introduction by Ben Johnston); Hart Brothers, Publishing, PO Box 205, Williston, VT 05495; 112 pp., illustrated; 5½ × 8½ inches; softcover; \$7.95; hardcover \$12.95.

This material by the great Yugoslav-American inventor (1856-1943) has been virtually unavailable since 1919 when it was published serially in Hugo Gernsback's *Electrical Experimenter*. The editor's note tells us that Tesla's "idiosyncratic phonetic spellings" have not been changed in this edition, but some of the picture captions have been revised. All the original illustrations are here, and six new ones have been added. There are two excellent wash illustrations by Frank R. Paul, who later became world-famous as the principal illustrator for the Gernsback science fiction magazines.

Tesla was 63 when these articles were published; they reveal his youthful struggle to harness his runaway imagination; after the chapters "My Early Life," and "My First Efforts in Invention", we proceed to the discovery of the rotating magnetic field, the Tesla coil and transformer, the magnifying transmitter, and the art of teleautomatics. Much of what the reader may have seen in various biographies is a mixture of fact and fiction; here the inventor himself sets the record straight.

Although he lived and worked in the United States for nearly 60 years, by the time he died he was virtually forgotten. The present volume is needed to bring Nikola Tesla into proper perspective.

CIRCLE 121 ON FREE INFORMATION CARD

MICROCOMPUTER EXPERIMENTATION WITH THE MOS TECHNOLOGY KIM-1, by Lance A. Leventhal; Prentice-Hall, Inc., Englewood Cliffs, NJ 07632; 467 pp., including appendices and index; 6¾ × 9¼ inches; softcover; \$16.95.

This practical easy-to-follow and self-contained guide to MOS Technology KIM-1 experiments represents diverse disciplines and a wide variety of applications. The emphasis throughout is on approaches that are fundamental to the design of controllers for external systems; at the same time, it illustrates its points through examples that use nothing more complex than switches, single displays, and the on-board peripherals.

The inexpensive and widely available KIM-1 microcomputer and 6502 microprocessor were selected to provide realistic experience with popular devices for those involved in a wide range of control-operation applications: instrumentation, communications equipment, test equipment, computer peripherals, industrial processes, signal processing, business equipment, consumer products, and many more.

There are two major groupings of experiments. Those in the first group focus on writing and running simple programs, simple input and output, processing of inputs and outputs, forming and processing data arrays, designing and debugging programs, and arithmetical operations. Those in the second group deal with subroutines and the stack, input/output using handshakes, interrupts, timing methods, serial input/output, and microcomputer timing and control.

CIRCLE 122 ON FREE INFORMATION CARD

70 YEARS OF RADIO TUBES AND VALVES, by John W. Stokes; The Vestal Press, Ltd., PO Box 97, Vestal, New York 13850. 256 pp., including glossary and index; 8½ × 11 inches; hardcover; \$21.95 through bookstores—add \$2.00 shipping when ordering from publisher, and New York residents add 7% sales tax.

Here is the history of the radio tube from its invention in 1904 to its gradual eclipse, beginning in the 1960's when it was replaced by solid-state devices. The emphasis, however, is on developments occurring between 1927 and 1937—the period when the "all electric" receiver evolved to become a familiar part of our daily lives.

All the giants of the industry—Westinghouse, General Electric, Sylvania, RCA, Raytheon, and others their size, as well as many smaller firms now forgotten—are covered in this story of how our technical know-how progressed in the period. It ranges from Edison's discovery that electrons would flow in a vacuum (the "Edison effect") to Lee deForest's invention of the "grid", to RCA's "Nuvistor" that closed the era.

CIRCLE 123 ON FREE INFORMATION CARD

A MANAGER'S GUIDE TO INDUSTRIAL ROBOTS, by Ken Susnjara; Corinthian Press, publishing division of EDR Corporation, Shaker Heights, OH; 181 pp., including appendices, but no index; 6½ × 8¼ inches; hardcover; \$24.95.

The robot industry is one of the fastest-growing industries. The capability of those machines, the number of units available, the number of manufacturers, and the number of installations, are all growing at an astounding pace.

This book discusses the new technology in a simple, straightforward manner. It is designed for the non-technical manager who must deal with robots, and assumes no previous knowledge or experience in the area on the reader's part. The author addresses such questions as: "What is an industrial robot?"; "How do industrial robots work?"; "What can they do and what can they not do?"; "How much do they cost?"; "How do I find applications in my plant?"; and "How do I handle labor and community relations?"

This illustrated, comprehensive guide includes a reference manual covering the details of installing and using an industrial robot. It also provides a glossary of robotic and technical terms explained in simple, non-technical language.

CIRCLE 124 ON FREE INFORMATION CARD

THE ILLUSTRATED DICTIONARY OF ELECTRONICS (2nd Edition), by Rufus P. Turner; TAB Books, Inc., Blue Ridge Summit, PA 17214; 893 pp.; 5½ × 8¼ inches; softcover; \$16.95.

Anyone in any way associated with the electronics field, whether beginning hobbyist, experienced, amateur, or professional will find this book valuable. From "A" to "zymurgy", the more than 25,000 definitions provide needed information to anyone who wants to look up an electronics term in a hurry. The new 2nd edition has not only been completely updated, but contains over 600 new entries, covering electronics, radio, audio, computers, and related studies.

In addition to the alphabetically-arranged definitions, there is a "Tables and Data" appendix that includes the resistor color code, electronics symbols, wire gauge, abbreviations, and a variety of conversion tables.

CIRCLE 125 ON FREE INFORMATION CARD

THE BASIC HANDBOOK (2nd edition), Encyclopedia of the BASIC Computer Language, by David A. Lien; Compuser Publishing, San Diego, CA 92119; 480 pp., 7 × 9 inches; softcover; \$19.95.

The BASIC language has changed in many ways since 1978, when the first edition of this book appeared. With each new computer came new words, and with each new word the need to update. Drawing upon his extensive BASIC language library, and with the assistance of many manufacturers, the author has attempted to document and explain virtually every BASIC feature of every type of computer in the world.

Special attention has been given to documenting the diverse BASICs implemented on the many new computers introduced (and about to be introduced) from Europe and Asia. In addition to filling gaps in the 1st edition, a strong effort has been made to continue documenting "disk BASIC", which many users find frustrating. Although there are as yet no standards for "disk BASIC's," only common concepts, the documentation follows those trends that can be identified.

This new second edition introduces 238 additional words, bringing the total of BASIC words to almost 500. Nearly every significant BASIC word, used by virtually every BASIC-speaking computer in the world is explained.

CIRCLE 126 ON FREE INFORMATION CARD

\$1590



Full size smart terminal with detachable keyboard

4Mhz Z80A CPU
64K RAM Main Memory
200Kbyte 5 1/4" floppy disk
(Osborn, Xerox, IBM, CP/M-86 formats)
Two serial ports

Complete software package includes:
WordStar word processing
Correct-It spelling checker
LogiCalc electronic spreadsheet
Microsoft BASIC
NorthStar compatible BAZIC
CP/M 2.2 Operating System

At \$1790, this computer was selling like hotcakes. So we dropped the price.

Crazy? No, not really. You see in order to meet the demand for the Micro Decision™ we increased our production. When we did that, our costs dropped. We're passing our savings on to you, because that's our philosophy.

More for less.

So now it only takes \$1590 to buy a Micro Decision with 64K of memory, a 200K double-density floppy drive and a full-size Morrow smart terminal with detachable keyboard. Not bad. But there's more.

The Micro Decision also includes a package of business and professional software worth well over \$2000. The WordStar® word processor. A 36,000 word spelling checker. The LogiCalc™ electronic spreadsheet. And both Microsoft BASIC-80® and NorthStar-compatible BAZIC®. Plus, the CP/M® 2.2 Operating System that gives you access to thousands of other software programs. And, we take the mystery out of CP/M with plain English commands and single-key operation.


If you have your own terminal, you can buy the complete computer and software package for \$995. That's the Micro Decision MD1™. The MD2™ includes another double-density disk drive, plus Personal PEARL™ the relational data base manager. Price? Only \$1395.

More memory? No problem. The Micro Decision MD3™ gives you two double-sided, double-density disk drives with 768K of storage and Personal PEARL for only \$2490. Without the terminal, \$1895.

Come in for a complete demonstration at your nearest Morrow dealer. If you don't know who that is, call us toll-free at (800) 521-3493. In California, call (415) 430-1970. At \$1790, the Micro Decision sold like hotcakes. At \$1590, we've just sweetened the deal.

MORROW

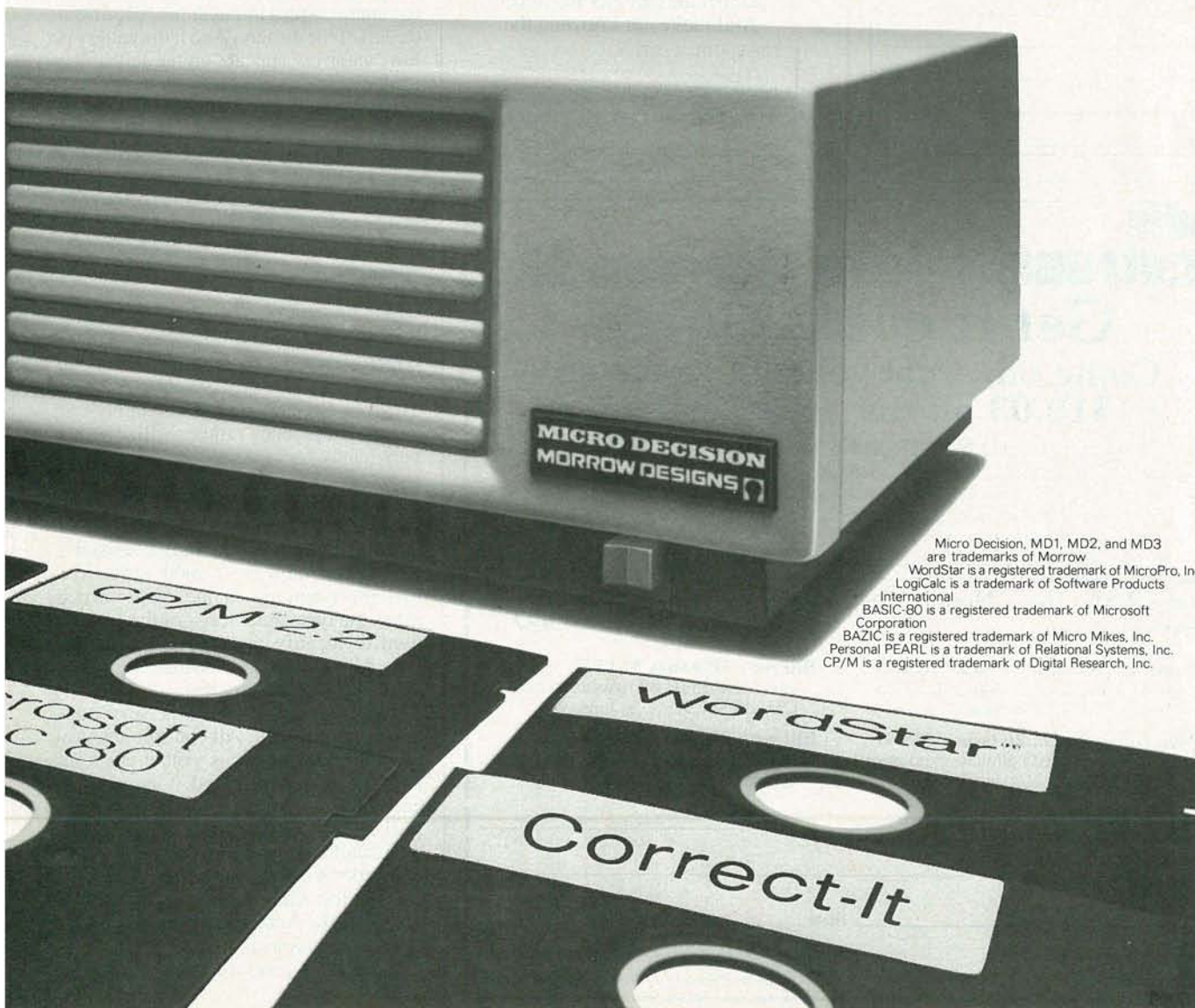MORROW, 600 McCormick Street, San Leandro, CA 94577
(800) 521-3493, (415) 430-1970 In California




Micro Decision, MD1, MD2, and MD3 are trademarks of Morrow.
WordStar is a registered trademark of MicroPro, Inc.
LogiCalc is a trademark of Software Products International.
BASIC-80 is a registered trademark of Microsoft Corporation.
BAZIC is a registered trademark of Micro Mikes, Inc.
Personal PEARL is a trademark of Relational Systems, Inc.
CP/M is a registered trademark of Digital Research, Inc.

CIRCLE 77 ON FREE INFORMATION CARD

JULY 1983

97

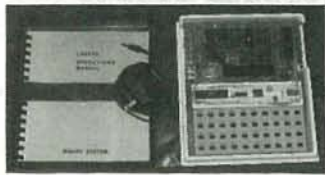MASTERING MICROPROCESSORS BEGIN WITH LS6802



LS6802 is a complete learning system to master microprocessor hardware and software. It is based on the 6802 CPU, an improved version of the renowned 6800 and is a good starting point to master the varieties of 6800 family microprocessors so widely used in industry.

Its features include: 2K monitor program with 20 editing, debugging functions; 2K RAM; spare socket for 2K RAM or 4K EPROM; built-in breadboarding system for hardware experiments; speaker; cassette tape interface; 16 programmable I/O lines (6821 PIA); 3 user keys; the full capabilities of 6802 CPU and an AC/DC adaptor to power the LS. An ideal tool for learning, teaching, experimenting and prototyping at only \$159.00. 90 days warranty.

Binary System, Maxwell Road, P.O. Box 1583, Singapore 9031, Republic of Singapore.

Send me ___ unit(s) of LS6802 at \$159.00 each, a total amount of _____. I am paying by ___ Money order, ___ Visa, ___ Mastercard ___ American Express.

Name _____

Signature _____

Address _____

Card No. _____ Expires _____

CANCER. NOT KNOWING THE RISKS IS YOUR GREATEST RISK.

A lot of people think cancer is unbeatable.

That simply isn't true. In fact, over two million people have had cancer and survived to lead happy, normal lives.

And not only can cancer be beaten, it can also be prevented.

There are definite precautions that have been proven to decrease your risk of getting certain cancers.

Ask your local American Cancer Society to send you a free booklet about cancer risks.

Learn the facts about cancer. And make not knowing the risks, one less risk.

AMERICAN CANCER SOCIETY®
How you live may save your life.

This space contributed as a public service.

EQUIPMENT REPORTS

continued from page 38

in the OHMS range and have come back to it only to find a dead battery. Of course my multimeter didn't have a separate power switch.) Across from the POWER switch is a transistor test socket. Four input-jacks (V-Ω, COM, MA, and 10A) are in a row across the bottom, below the range selector. The readout is a "bright," easy-to-read, 3½-digit LCD display that includes a low-battery indicator.

The 8050 has thirty ranges that cover eight functions. It can measure DC voltages to 1000 volts over five ranges (200 mV, 2 volts, 20 volts, 200 volts, and 1000 volts), and AC voltages to 750 volts over similar ranges (except for the upper limit). The input impedance is 10 megohms on all voltage ranges. AC and DC current can be measured to 10 amperes over five ranges: 200 μA, 2 mA, 20 mA, 200 mA, and 10 amperes. (The 10-amp range requires that a separate input jack be used.) Polarity indication is automatic, with a minus sign appearing at the left of the display. And if the battery is low, an arrow appears on the left of the readout.

Resistance measurements (with automatic zeroing) can be made to 20 megohms over six ranges: 200 ohms, 2K, 20K, 200K, 2 megohms, and 20 megohms. Those resistance measurements are accurate to within 1% of the reading on all but the 20-megohm range, where the accuracy 2%.

Other features

A separate position on the range-selector switch, marked with a diode symbol, lets you quickly check diodes. There is also an audible continuity-test position. It sounds rather shrill, but it's very handy for making quick continuity checks.

One unusual feature that is included on the 8050 is a test socket at the upper right of the panel that lets you find a transistor's hFE (Beta) on a 0 to 1000 scale. The NPN-PNP positions on the range switch select the type under test—or they can be used to identify an unknown transistor type. Maximum collector-to-emitter voltage is 2.8 volts under test.

This little instrument is very convenient easy to use. All controls are easy to get at, the readout is visible under all practical conditions, and it is compact enough to fit into the average work-shirt pocket. It's also magnetically shielded; the manufacturer claims that even strong magnetic fields will not affect its accuracy. The test leads that come with it have nice sharply pointed tips that can make some measurements much easier. All in all, the 8050 is a lot of meter for its \$89.95 price.

R-E

Radio-Electronics® You deserve it!

Get it every month

Come on, treat yourself...save up to \$10.03 off the newsstand price.

Subscribe to RADIO-ELECTRONICS and have the best electronics magazine delivered to your home—check off the money-saving offer you prefer on the handy coupon, and start enjoying RADIO-ELECTRONICS every month. Enclose your payment and get ONE EXTRA ISSUE per year.

Get the Best—Every Month! Mail Today!

YES! please send me

7HG33

Payment enclosed, 13 issues \$14.97
(You save \$4.53 off newsstand price.)
Canada \$17.97 - U.S. funds only

Bill me - 12 issues \$14.97
(You save \$3.03 off newsstand price.)
Canada \$17.97 - U.S. funds only

Payment enclosed, 26 issues \$28.97
(Save More! \$10.03 off newsstand price.)
Canada \$34.97 - U.S. funds only

Bill me - 24 issues \$28.97
(Save More! \$7.03 off newsstand price.)
Canada \$34.97 - U.S. funds only

Name _____ (please print)

Address _____

City _____ State _____ Zip Code _____

Mail to: RADIO-ELECTRONICS
P.O. Box 2520
Boulder, Colorado 80322

Offer valid in U.S. and Canada only

Allow 6-8 weeks for delivery of first issue.

SERVICE QUESTIONS

continued from page 83

voltage at the pin to be 18 volts. Installing a 14.2K resistor between pin 24 and pin 29 (ground) pulled that voltage down to 14.5, and restored proper clock operation in all modes. The value of the resistor was found experimentally. Incidentally, if you need a new clock IC, they can be bought from SSI Components Ltd., Suite 201, Austin Centre, 21 Austin Ave., Kowloon, Hong Kong. They cost \$11.00 each (in U.S. funds) when bought in quantities of 1 to 24.—V.M., Bronx, NY

BURNING CAPACITOR

After fixing some other problems in this Zenith 23EC15, I noticed a burning smell, but no smoke, coming from the set during testing. When I investigated I found that fuse F204 had blown, and that capacitor C267 had burned to a crisp. Replacing the fuse and capacitor got the set working, but after an hour the capacitor began getting hot again. What's going on here?—B.M., S. Portsmouth, KY

What you're describing is fairly common in solid-state sets, although this is the first time I've ever heard about it in a tube set. In any event, the cure should be the same. Capacitor C267 is in a circuit with horizontal-frequency pulses; an ordinary capacitor won't work there. You need one of the special "RF" types, one with dielectrics rated to handle the high frequency. Either get an exact Zenith replacement, or one rated for high-frequency service.

UNUSUAL VERTICAL PROBLEM

I had a vertical problem in a Zenith 13A16Z. You made several suggestions including checking the resistance of the vertical-output transformer's primary. After following all of your other hints, and replacing several bad components that I had found, the problem was still there. When I did get around to checking that transformer, the primary's resistance was indeed lower than it should have been. Replacing the transformer solved the problem.—A.S., Middletown, NJ

Glad to hear that you found it. Failure in those transformers is really quite rare, but, as you discovered, it can happen.

PEGGING METER

The meter needle on this tube-type VTVM pegs to the right side. I've heard about pegging to the left, but never this. What's going on?—A.M., Darlington, MD

If the meter pegs in either direction, it means that there is a bad unbalance in the circuit. Most often, the cause is a defective VTVM bridge tube, usually a 12AT7 or similar twin triode. Note that you may need to try several tubes, especially in the older models, before you'll

find one that will balance the circuit.

Feedback—That was the problem; only needed to try one tube before the trouble cleared up.

COLLAPSING RASTER

I've run into a problem that seems to be common in the Zenith System-3 sets that use the 9-153 high-voltage module. The symptom is an intermittent collapse of the raster and horizontal foldover. The cause is poor solder-connections on two components: the horizontal-output transformer and T3301. It helps to take those components out, scrape the connections clean, and then reinstall them. I've seen that problem in six sets over the past few months, including my own.—George Yarbrough, West Yellowstone, MT

CREEPING HIGH VOLTAGE

The high voltage in this Sears 528.41681941 can be varied between 22 and 27 kilovolts when the set is first turned on. After it has been on for a while, however, the high voltage creeps up until it can be varied only between 28 and 30 kilovolts. The B+ voltages are all close to what they should be and stable, but the boost voltage rises from +800 volts at turn-on to +870 volts. Any ideas on this?—J.O., Winthrop, ME

I ran into this some time ago in an RCA that used a 31JS6 output tube. Here's what to do: Check the grid waveform on your 40KD6 tube with an oscilloscope. If it is normal at turn on, but the peaks flatten as the tube warms up, you've got it. The problem is grid emission in the 40KD6. If the peaks flatten enough, it will make a normal waveform look almost like a squarewave. The flattened peaks keep the tube turned on too long, raising the boost, high voltage, etc. The only cure is to replace the tube, and check to make sure the replacement is good; I've gone through 4 or 5 new tubes at times before I've found a good one.

MORE HINTS

Here are a couple more hints from Mike Danish of Aberdeen Proving Ground, MD:

The first involves bad colors and low brightness in an RCA CTC59XD. Resistor RT201 was burnt up. Replacing it, however, did not help. Looking farther, I found that I had no control over the CRT screens. The only thing common to all of the screens was that they got 600 volts from the flyback through a 1K resistor and the boost rectifier. When I looked at the 1K resistor, I found that it, too, had burned up. I tried replacing the resistor, but the replacement also burned out in short order. The problem turned out to be in the boost rectifier. Once it was replaced, and a new 1K resistor was installed, everything returned to normal.

The second one involves a Packard-

Bell 1C620WL; that set is actually a GE C2 chassis. The set had no raster but the audio was fine. The trouble was traced to R189 and R191 in the video-output circuit. Those two resistors had burned up. When they were replaced, the set ran fine.

HORIZONTAL FOLDOVER

This Zenith HT2382P came in with intermittent horizontal-foldover in the center of the screen; the left side of the screen was perfect but the raster pulled away from the right side and folded in the center with a vertical white line about 1/2 inch wide. Replacing the horizontal module had no effect. When I checked the driver transformer I found that the resistance was off—it was 40-45 ohms instead of 96 ohms. A new transformer fixed the problem, for about three weeks. When I got it back in the shop I finally found the true culprit; C227, a 50µF electrolytic was intermittently opening. Replacing that capacitor fixed things permanently.—Danny Joe Davis, Moundsville, AL

BAD TRACKING

I asked you about an old RCA AM-FM portable that wouldn't track at the low end of the dial. You suggested spraying contact cleaner on the tuning capacitor, and running the dial back and forth several times. I did that, and it worked. It also cleared up a bad drift problem on FM at the same time. Thanks—Bill Suhy, Stratford, CT

Old-radio restorers take note! The cause of that problem is a very poor or corroded contact between the rotor of the capacitor and the frame. As the rotor turns, the resistance varies, which of course changes the capacitance. That used to be quite common in the old sets, but I haven't seen it lately, till now.


OSCILLOSCOPE HINT

We had some Dumont 208 oscilloscopes in our lab with problems in the vertical positioning of the trace. Your column in **Radio-Electronics** about bad contacts rang a bell. We simply pulled the 6V6 vertical amplifier tubes and then put them back in. That fixed everything up. Dumont used the DC plate current of those tubes to provide the positioning voltage for the trace, and the humid summers here had caused some corrosion in the wafer sockets.—J.R., Ocala, FL

ION BURN

I saw a question in **Radio-Electronics** some time ago about what seemed to be ion burn in a modern CRT. I ran into a similar problem a while back with a Zenith 14B36Z. After checking several things, I read the high voltage and, lo and behold, it was only 5 kilovolts. The cause of the problem was a bad flyback. Replacing it cleared everything up.—Bert Balt, Rochester, NY


R-E

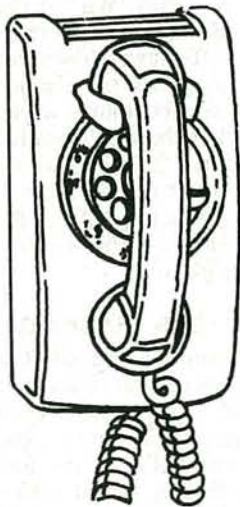

**CALL NOW
AND
RESERVE
YOUR SPACE**

- 6 x rate \$550 per each insertion.
- Reaches 220,500 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads.
- We typeset and layout the ad at no additional charge.

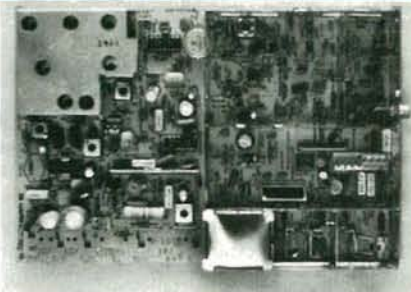Call 212-777-6400 to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: mini-ADS, RADIO-ELECTRONICS, 200 Park Ave. South, New York, NY 10003.



TELEVISION MODULE includes VHF, UHF, and CABLE-TV TUNERS, IF AMPLIFIER, VIDEO DETECTOR, SOUND DETECTOR and AMPLIFIER, and SYNC PROCESSOR: **\$85.00**. TELEVISION SIGNAL PROCESSING MANUAL explores standard and non-standard television: **\$15.95**. Add 5% handling and shipping. Catalog \$2.00. Visa and MC accepted. ORDER DESK (415) 439-7470. ABEX, P.O. BOX 26601-RZ, SAN FRANCISCO, CA 94126.

CIRCLE 62 ON FREE INFORMATION CARD




SOLDERING STATION FOR LESS Front display of tip temperature, adjustable temperature 200°F to 900°F. UL listed, low current leakage, high insulation. Complete as shown. 7 tips available, also takes standard tips. **ORDER MODEL 81-XY 168. \$79.95** plus shipping. To order call toll free: (800) 423-5336. In California (800) 382-3663. Or send **\$79.95** (California residents add sales tax) plus **\$5.00**, shipping to **ORA ELECTRONICS DEPT. RE, 18215 Parthenia St., Northridge, CA 91325 (213) 701-5848.**

CIRCLE 92 ON FREE INFORMATION CARD



**CONVERTERS
DESCRAMBLERS-MICROWAVE**-Not C and D grade. Only grade A new, genuine Oak, Jerrold, Zenith, Hamlin, Pico, Bogner, Pioneer! Name it! Sine-wave, gated-sync, vari-sync, in-band, out-band. We sell 'em all! No order too big or small. Dealers-we can beat any price. Send \$3.00 for catalog to: **TV PRODUCTS CO., 635 Park Avenue, Suite 222, Idaho Falls, ID 83402.**

CIRCLE 61 ON FREE INFORMATION CARD

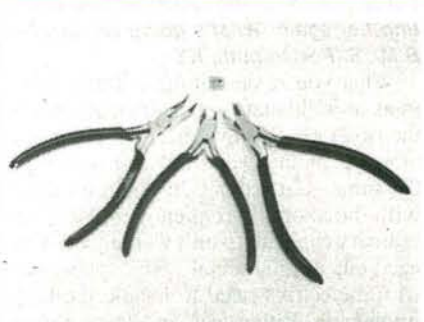


QUALITY TOOLS AT HALF PRICE! Sunnex manufactures a wide range of high precision, box joint cutters and pliers for the electronics industry. Sunnex only sells direct and can offer you quality tools at the most competitive prices. **A HALF PRICE INTRODUCTORY OFFER** will be enclosed with the catalog **SUNNEX INC., 87 Crescent Rd., Needham, MA 02194. Phone 1-800-225-8480 (in MA 617-444-4730).**

CIRCLE 98 ON FREE INFORMATION CARD



FREE CATALOG OF HARD-TO-FIND TOOLS is packed with more than 2000 quality items. Your single source for precision tools used by electronic technicians, engineers, instrument mechanics, schools, laboratories and government agencies. Also contains Jensen's line of more than 40 tool kits. Send for your free copy today! **JENSEN TOOLS INC., 7815 46th St., Phoenix, AZ 85040. (602) 968-6231.**

CIRCLE 97 ON FREE INFORMATION CARD

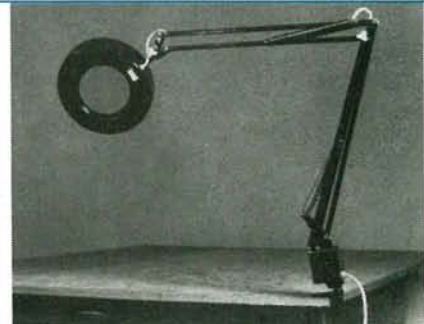

MAGNIFIER LAMP FOR LESS All metal construction, UL approved 5", 3x magnifier, 22 watt fluorescent circline lamp. 45" arm reach, heavy duty clamp mount. **Only \$59.95** plus shipping. (California residents add sales tax.) To order call (800) 423-5336. In California, (800) 382-3663 or send **\$59.95** plus **\$5.00** shipping to **ORA ELECTRONICS, 18215 Parthenia St., Northridge, CA 91325 (213) 701-5848.**

CIRCLE 96 ON FREE INFORMATION CARD




SHEET METAL WORKER - The 24" TRIOK is a Press Brake, Shear and Slip-roll machine-perfect for research and development or maintenance shops. Over a thousand machines world wide in little to the largest companies. For free literature on this and our other sheet metal working machines contact: **PACIFIC ONE CORPORATION**, 513 Superior Ave. Suite K201, Newport Beach, CA 92663, (714) 645-5962.



ELECTRO IMPORTING CO. CATALOG. This reprint of the historic 176-page catalog No. 20 gives you an accurate look at the state of electronics in 1918. Contains everything from a Zinc Spark Gap to a 1000-Mile Receiving Outfit. You can get your own copy of this modern antique, profusely illustrated, for only \$4.95 plus \$1.00 P&H. Order yours from **R-E BOOKSTORE**, Radio-Electronics, 200 Park Avenue South, New York, NY 10003.



CLOSE OUT - BLOW OUT - LIQUIDATION SALE - AMATEUR MICROWAVE RECEIVER - REGULARLY \$99.50. NOW LIQUIDATING AT ONLY \$59.95 EACH! (Dealer "eight-pack" for just \$399.00) Complete system includes dish, probe/downconverter, co-ax cables, power supply, hardware and instructions. Top quality units with genuine #2137 transistors for hi-gain, lo-noise. **ORDER TODAY!** Supply limited. Money order, VISA or Mastercard only. (No C.O.D. at this price.) **T.V. PRODUCTS CO., 635 Park Ave., Dept. 222, Idaho Falls, Idaho 83402.** DESCRABLERS?? We stock all types. Send \$3.00 for catalog!

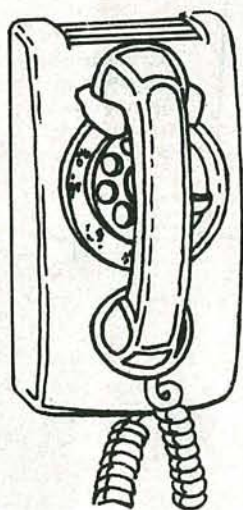


**CALL NOW
AND
RESERVE
YOUR SPACE**

- 6 x rate \$550 per each insertion.
- Reaches 220,500 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads.
- We typeset and layout the ad at no additional charge.

Call **212-777-6400** to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: mini-ADS, RADIO-ELECTRONICS, 200 Park Ave. South, New York, NY 10003.



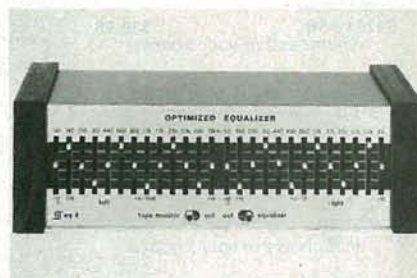3S-WICK STARTS AT 450°F.....3S-Wick is the best and most economical wick. Give it a try. The special 80¢ a spool price for a minimum order of 30 spools can be lowered to as little as 59¢ a spool when purchased in 1000+ piece lots. **Call our toll free number 1-800-628-8862** for free sample, and to place an order (Distributor inquiries welcomed.) **CIRCLE 100 ON FREE INFORMATION CARD**



OPTIMIZED Graphic Equalizer—NEW Our latest EQ has been optimized for room equalization, emphasizing the critical mid-range. Construction article: **Computers & Electronics** 12/82. Near 20-band capability, but...Kit only \$100 ppd; M/C, Visa add shpg. Kit instructions \$3.50 (refundable). **SYMMETRIC SOUND SYSTEMS**, 856K Lynn Rose Ct., Santa Rosa, CA 95404, (707) 546-3895.

CIRCLE 72 ON FREE INFORMATION CARD



MODERN ELECTRICS. Miniature souvenir of the first publication ever produced by Gernsback Publications. This issue appeared in April 1908—just 75 years ago. You can own your own reprint of this unique first edition for just \$2.50 plus 75¢ P&H. It's available from **R-E BOOKSTORE**, Radio-Electronics, 200 Park Avenue South, New York, NY 10003



APPLIANCE REPAIR HANDBOOKS—13 volumes by service experts; easy-to-understand diagrams, illustrations. For major appliances (air conditioners, refrigerators, washers, dryers, microwaves, etc.), elec. housewares, personal-care appliances. Basics of solid state, setting up shop, test instruments. \$2.65 to \$5.90 each. Free brochure. **APPLIANCE SERVICE**, PO Box 789, Lombard, IL 60148. 1-(312) 932-9550. **CIRCLE 64 ON FREE INFORMATION CARD**

Go with McGraw-Hill's EXPERIENCE!

TAKE ANY 3 BOOKS FOR ONLY \$100 EACH when you join McGraw-Hill's Electronics and Control Engineers' Book Club (Values up to \$87.00)*

INTUITIVE IC ELECTRONICS: A Sophisticated Primer for Engineers and Technicians. By T. M. Frederiksen. 208 pp., illus. Covering both the simplest and the most complicated IC designs, this lively, easy-to-read volume provides a sophisticated, nonmathematical explanation of the basic internal mechanisms common to all semiconductor devices. 219/230 \$19.95

RADIO HANDBOOK, 22/e. By W. Orr. 1,136 pp., more than 1,300 illus. Here's the latest edition of what is universally regarded as the most useful reference in the industry. It's a "course" in communications, a fact-packed reference, and a how-to guide—all in a single book! 582442-6B \$39.95 (Counts as 2 of your 3 books)

VLSI TECHNOLOGY By S. M. Sze. 672 pp., 400 illus., 50 tables. An anthology from more than 3,000 technical papers, by 14 leading experts, covering everything from crystal growth to special packaging considerations. 626/863B \$32.50 (Counts as 2 of your 3 books)

ANTENNA THEORY: Analysis and Design. By C. A. Balanis. 816 pp., illus. Packed with equations, design procedures, and plenty of nuts-and-bolts know-how, this is the first place to turn for answers to all your antenna design questions. 582493-0B \$39.50 (Counts as 2 of your 3 books)


MICROPROCESSOR DATA BOOK. By S. A. Money. 350 pp., 220 illus. Easily the most comprehensive collection of data on microprocessors and their support chips available anywhere! Provides important facts on a wide range of popular devices from American, European, and Japanese manufacturers. 427/062B \$35.00 (Counts as 2 of your 3 books)

HANDBOOK OF SEMICONDUCTOR AND BUBBLE MEMORIES. By W. A. Triebel and A. D. Chu. 416 pp., illus., over 50 worked-out problems. This detailed, comprehensive guide brings you right up to the minute on such newly developed devices as the PLA, FIFO, CAM, CCD, and magnetic bubble memory—as well as all the standard storage devices from ROMs and RAMs to shift registers. 582376-4 \$24.95

INTRODUCTION TO RADAR SYSTEMS, 2/e. By M. I. Skolnik. 698 pp., 244 illus. This new edition of a widely used text on radar from the systems engineer's point of view brings you full discussions of the many major changes that have occurred in the field recently. 579/091B \$39.95 (Counts as 2 of your 3 books)

McGraw-Hill's long-established club that saves you BIG money on the important new books of all publishers!

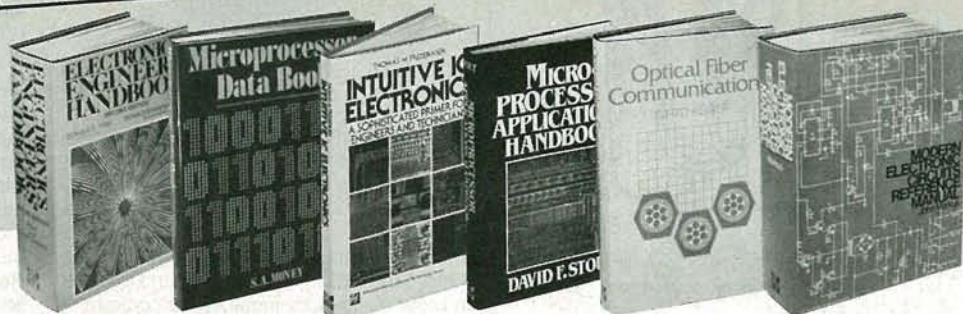*If you join now for a trial period and agree to purchase three more books—at handsome discounts—over the next year. (Publishers' prices shown)



ELECTRONICS ENGINEERS' HANDBOOK, 2/e. Edited by D. G. Fink & D. Christiansen. 2,272 pp., 2,189 illus. This updated and enlarged edition covers the latest knowledge in the field, including new advances in integrated circuits, pulsed and logic circuits, laser technology, telecommunications, and much more. 209/812A \$75.00 (Counts as 3 of your 3 books)

ELECTRONIC COMMUNICATION, 4/e. By R. L. Shrader. 801 pp., 870 illus. This thoroughly updated edition offers all the theory and fundamentals you need to prepare yourself for the FCC commercial and amateur grade license examinations—and pass them the first time! 571/503 \$26.95

DIGITAL HARDWARE DESIGN. By J. B. Peatman. 428 pp., over 400 illus. Taking you beyond the microcomputer, this guide reexamines traditional techniques and focuses on the design of circuitry too fast for the microcomputer alone. 491/321B \$35.50 (Counts as 2 of your 3 books)

MICROPROCESSOR APPLICATIONS HANDBOOK. Editor-in-Chief, D. F. Stout. 472 pp., 284 illus. At last—a reference guide to microprocessor applications to help you make your systems timely, versatile, and cost-effective. 617/988B \$35.00 (Counts as 2 of your 3 books)

SIGNALS AND SYSTEMS. By A. Oppenheim, A. Willsky, and I. Young. 869 pp., more than 350 illus. This unique volume presents a comprehensive discussion of methods for analyzing discrete-time systems. Includes a look at feedback, convolution, and other concepts not treated in depth elsewhere. 582674-7B \$32.50 (Counts as 2 of your 3 books)

MODERN ELECTRONIC CIRCUITS REFERENCE MANUAL. By J. Markus. 1,264 pp., 3,666 circuit diagrams. Complete with values of components and suggestions for revisions, plus the original source of each circuit in case you want additional performance or construction details. 404/461A \$67.95 (Counts as 3 of your 3 books)

OPTICAL FIBER COMMUNICATIONS. By G. Keiser. 416 pp., illus. For those with little or no prior experience with optical fibers, the perfect book to walk you through a typical system. 334/676B \$35.95 (Counts as 2 of your 3 books)

PCM AND DIGITAL TRANSMISSION SYSTEMS. By R. Owen. 320 pp., 186 illus. This useful volume allows newcomers to the field to familiarize themselves with its problems and equipment in two weeks, instead of the three months it would ordinarily take. 479/542B \$30.00 (Counts as 2 of your 3 books)

MANUAL OF ACTIVE FILTER DESIGN, 2/e. By J. L. Hilburn and D. E. Johnson. 225 pp., 157 easy-to-use design graphs. This ingenious manual enables you to design filter circuits for virtually any application in minutes—without making a single computation! Covers all the latest designs. 287/694B \$37.50 (Counts as 2 of your 3 books)

DIGITAL CIRCUITS AND MICRO-PROCESSORS. By H. Taub. 608 pp., heavily illus. This fast-paced, carefully written guide gives you thorough explanations of all the basic principles of digital systems and logic design—plus a solid introduction to microprocessors and micro-processor-based designs.

629/455B \$32.95
(Counts as 2 of your 3 books)

DIGITAL COMMUNICATIONS. By J. G. Proakis. 624 pp., illus. A wealth of new material, information about spread spectrum signals, requiring a minimum of math to get through it.

509/271B \$37.50
(Counts as 2 of your 3 books)

ELECTRONICS ENGINEERING FOR PROFESSIONAL ENGINEERS' EXAMINATIONS. By C. R. Hafer. 336 pp., more than 200 illus. Actually two books in one—a quick preparation manual to help you pass your P.E. exams on the first try and a rich source of practical electronics engineering information and know-how.

254/303 \$27.50

MICROPROCESSOR SUPPORT CHIPS Theory, Design and Application. By J. J. Byers. 228 pp., 170 illus. Everything from pinouts to operating characteristics is spelled out for telecommunications, power supplies, interfaces, control, video and A/D and D/A converters.

095/183B \$38.00
(Counts as 2 of your 3 books)

INTEGRATED CIRCUIT FABRICATION TECHNOLOGY. By D. J. Elliott. 480 pp., 220 illus. Covering every step in the transformation of a silicon chip to an integrated circuit, this is the first book to combine, in a single volume, a cohesive examination of the equipment, materials, and techniques of IC fabrication.

192/383 \$29.75

STANDARD HANDBOOK FOR ELECTRICAL ENGINEERS, 11/e. By D. G. Fink and H. Beaty. 2,448 pp., 1,414 illus. Today's most widely used source of electrical engineering information and data serves you as no other single work when you need detailed, timely, and reliable facts

209/74XA \$65.95
(Counts as 3 of your 3 books)

McGraw-Hill's NATIONAL ELECTRICAL CODE® HANDBOOK, 17/e. By J. F. McPartland. 1,162 pp., 1,096 illus. Bigger and better than ever! This mammoth reference explains and clarifies the many complex provisions of the current (1981) Code® to help you meet rules exactly and pass inspections the very first time.

456/933 \$26.50

HANDBOOK OF ELECTRONIC PACKAGING DESIGN AND ENGINEERING. By B. Matisoff. 480 pp., 312 illus. This handy volume examines the broad array of packaging techniques available today, providing the data you need to select the best one for a given application. Stresses the interplay between design criteria.

582515-5B \$32.50
(Counts as 2 of your 3 books)

ANALYSIS AND DESIGN OF DIGITAL INTEGRATED CIRCUITS. By D. A. Hodges & H. G. Jackson. 448 pp., illus. The only book available written from a quantitative point of view for those who design as well as use ICs.

291/535 \$27.50

Be sure to consider these important titles as well!

RADAR TRANSMITTERS. By G. W. Ewell. 198/438 \$26.95

16-BIT MICROPROCESSOR SYSTEMS. By Texas Instruments, Inc. 637/601B \$45.00
(Counts as 2 of your 3 books)

ELECTRONIC CIRCUITS NOTEBOOK: Proven Designs for Systems Applications. Edited by S. Weber. 192/448B \$35.50
(Counts as 2 of your 3 books)

OPTICAL FIBER SYSTEMS: Technology, Design, and Applications. By C. K. Kao. 332/770 \$26.00

INTRODUCTION TO THE THEORY AND DESIGN OF ACTIVE FILTERS. By L. P. Huelsman & P. E. Allen. 308/543B \$34.50
(Counts as 2 of your 3 books)

MICROELECTRONICS. By J. Millman. 423/27XB \$35.95
(Counts as 2 of your 3 books)


HANDBOOK OF OPERATIONAL AMPLIFIER CIRCUIT DESIGN. By D. E. Stout & M. Kaufman. 617/97XB \$38.00
(Counts as 2 of your 3 books)

MICROCOMPUTER-BASED DESIGN. By J. Peatman. 491/380B \$35.95
(Counts as 2 of your 3 books)

BIT-SLICE MICROPROCESSOR DESIGN. By J. Mick & J. Brick. 417/814 \$29.50

NETWORK SYSTEMS. By R. Sharma & P. DeSousa. 582557-0 \$29.95

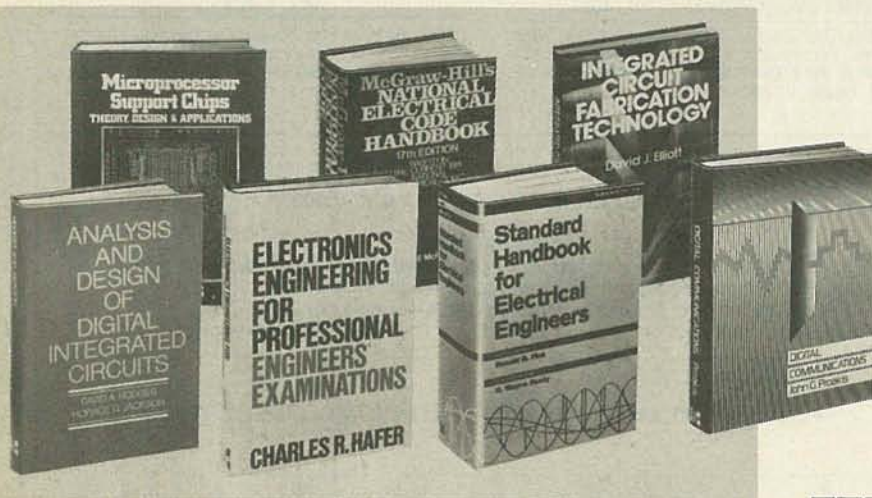ENGINEERING MATHEMATICS HANDBOOK, 2/e. By J. J. Tuma. 654/298B \$31.25
(Counts as 2 of your 3 books)



Why YOU should join now!

■ **BEST AND NEWEST BOOKS IN YOUR FIELD!** Books are selected from a wide range of publishers by expert editors and consultants to give you continuing access to the best and latest books in your field.

■ **BIG SAVINGS!** Build your library and save money too! Savings ranging up to 30% or more off publishers' list prices—usually 20% to 25%.

BONUS BOOKS! You will immediately begin to participate in our Bonus Book Plan that allows you savings up to 80% off the publisher's prices of many professional and general interest books!

■ **CONVENIENCE!** 12-14 times a year [about once every 3-4 weeks] you receive the Club Bulletin FREE. It fully describes the Main Selection and alternate selections. A dated Reply Card is included. If you want the Main Selection, you simply do nothing—it will be shipped automatically. If you want an alternate selection—or no book at all—you simply indicate it on the Reply Card and return it by the date specified. You will have at least 10 days to decide. If, because of late delivery of the Bulletin you receive a Main Selection you do not want you may return it for credit at the Club's expense.

As a Club Member you agree only to the purchase of three additional books during your first year of membership. Membership may be discontinued by either you or the Club at any time after you have purchased the three additional books.

Other McGraw-Hill Book Clubs: Accountants' and Controllers' Book Club • Architects' Book Club • Byte Book Club • Chemical Engineers' Book Club • Civil Engineers' Book Club • Mechanical Engineers' Book Club

For more information, write to:

McGraw-Hill Book Clubs • P.O. Box 582, Hightstown, NJ 08520

MAIL THIS COUPON TODAY

McGraw-Hill Book Clubs Electronics and Control Engineers' Book Club

P.O. Box 582, Hightstown, New Jersey 08520

Please enroll me as a member and send me the three choices I have listed below. Bill me only \$3.00 plus local tax, postage, and handling. If not satisfied, I may return the books within 10 days and my membership will be canceled. I agree to purchase a minimum of three additional books during my first year of membership as outlined under the Club plan described in this ad. A shipping and handling charge is added to all shipments. Indicate below by number the books you want. A few expensive books (noted in the descriptions) count as more than one choice.

Name _____

Address/Apt. _____

City/State/Zip _____

This order subject to acceptance by McGraw-Hill. All prices subject to change without notice. Offer good only to new members. Orders from outside the U.S. cannot be accepted.

E33606

MARKET CENTER

SATELLITE TELEVISION

SATELLITE antennas build 10' wood under \$160 metal \$93 plans \$40. **PROTOTYPE ENGINEERS**, Box 1812 Deming, NM 88030.

SATELLITE TV receiver breakthrough! Build your own commercial quality receiver now! Instruction manuals, schematics, circuit boards! Send stamped envelope: **XANDI**, Box 25647, Dept. 21L, Tempe, AZ 85282.

SATELLITE Television. Free wholesale price list! Save big! **COMMUNICATIONS CONSULTANTS**, PO Box 5099, Fort Smith, AR 72913.

INTERESTED in home satellite television? Don't buy anything until you've read **Homesat Handbook & Buyers Guide**. Our book tells everything about home satellite TV and may save you **hundreds, even thousands of dollars** in your selection and installation of a system! \$10.00: **H & G HOMESAT SERVICES**, Box 422, Seaford, N.Y. 11783.

SATELLITE TV WEEK

The most complete weekly listings.
Send \$1 for sample copy.

Satellite TV Week

P.O. Box 308, Fortuna, California 95540

Call (800) 358-9997 • California (707) 725-2476

CB EQUIPMENT

CB radio books, kits, modifications, free catalog. **APS**, POB 263RE, Newport, RI 02840.

VIC-20

CAPACITOR tester/meter. Connects to userport. Displays values 10-PFD through 650-MFD. Indicates shorts and opens. Needs no extra memory. Guaranteed. Wired tester and cassette program. \$39.95. **SANDI ELECTRONICS**, 203 Cambridge Belton, MO 64012.


WIRELESS MICROPHONES

BIG savings on **Cony** transmitters— up to 30% off! Send two stamps for catalog. **S.E. CORP.**, Box 1132-RC, Yorba Linda, CA 92686.

SECURITY-MONITORING DEVICES

ULTRA-miniature, super-range wireless FM transmitters as small as 7/8" long! Micro wireless telephone transmitter, voice activators, telephone voice changers, six-channel crystal communication systems, and more! Professional, high-tech microelectronics now available to you. Free brochures. **EXTENDO-TAPE SYSTEMS**, Dept. R-E, Box LC, Temple Terrace, FL 33687 (813) 985-3014.

XENON FLASH LAMPS

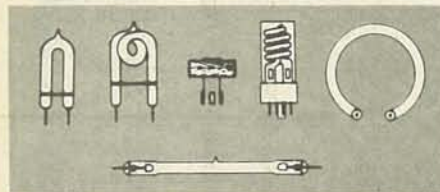

ASK FOR OUR NEW CATALOG.
CALL OR WRITE FOR INFORMATION.

TEC/WEST (USA) INC.

10889 WILSHIRE BLVD., SUITE 740

LOS ANGELES, CA 90024-4299

CA: 213/208-5529 • OUTSIDE CA: 1-800-421-7215

BUSINESS OPPORTUNITIES

PROJECTION TV... Make \$\$\$ assembling projectors... Easy... Results comparable to \$2500.00 projectors... Your total cost less than \$17.00. ... **Plans, lens & dealers** information \$15.50. ... Illustrated information **free** ... **MACROCOMGKX**, Washington Crossing, PA 18977. Credit card orders 24 hours. (215) 736-2880.

HIGHLY PROFITABLE

ONE-MAN ELECTRONIC FACTORY

Investment unnecessary, knowledge not required, sales handled by professionals. Ideal home business. Write today for facts!

Postcard will do, Barta-RE-X, Box 248, Walnut Creek, CA 94597.

WIND power an investment in the future. The right decision is essential. Information \$2.00. **WINDESIGN**, Box 138, Boston, NY 14025.

HOME burglar alarms. Career opportunities. **High income.** Information \$2.00. **SECURITY ELECTRONICS INTERNATIONAL**, PO Box 1456-XE, Grand Rapids, MI 49501.

MECHANICALLY inclined individuals desiring ownership of small electronics manufacturing business — without investment. Write: **BUSINESSES**, 92-R, Brighton 11th, Brooklyn, NY 11235.

WHOLESALE MATV/CATV/VCR equipment, antennas, audio cables, adapters, original/replacement cartridges & styli, telephone accessories, radios, cassette recorders, speakers, etc. Send letterhead for free catalog (212) 897-0509. **D&WR**, 69-19 Booth, Flushing, NY 11374.

COMPUTERS

\$44,000 first year in computers. Get in now! Free details. **DIGATEK CORPORATION**, Suite T2, 2723 West Butler Drive, Phoenix, AZ 85021.

FREE high technology semiconductors catalog 32bit microprocessor, 64KDRAM, speech synthesizer kits, 128KEPROM, no minimum or piece order, toll free number, etc., etc., **H.T.S.**, Box 213 Tustin, CA 9268L (714) 731-8859.

AT LAST!!

CABLE devices for 'beeping' or 'buzzing' channels. Details \$4.00. **Money back guarantee.** **CATV INFORMATION CENTER**, PO Box 17621, Ft. Laud., FL 33318.

To run your own classified ad, put one word on each of the lines below and send this form along with your check for \$1.90 per word (minimum 15 words) to:

Radio-Electronics, 200 Park Avenue South, N.Y., N.Y. 10003

ORDER FORM

PLEASE INDICATE in which category of classified advertising you wish your ad to appear. For special headings, there is a surcharge of \$15.00.

() Plans/Kits () Business Opportunities () For Sale
() Education/Instruction () Wanted () Satellite Television

Special Category: \$15.00

PLEASE PRINT EACH WORD SEPARATELY, IN BLOCK LETTERS.)

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

PLEASE INCLUDE FOR OUR FILES YOUR PERMANENT ADDRESS AND PHONE NUMBER.

CLASSIFIED COMMERCIAL RATE for firms or individuals offering commercial products or services). \$1.90 per word prepaid (no charge for zip code)...**MINIMUM 15 WORDS**. 5% discount for 6 issues, 10% for 12 issues within one year, if prepaid.

NON-COMMERCIAL RATE (for individuals who want to buy or sell a personal item) \$1.25 per word prepaid...no minimum.

ONLY FIRST WORD AND NAME set in bold caps. Additional bold face (not available as all caps) at 15¢ per word. All copy subject to publisher's approval. **ADVERTISEMENTS USING P.O. BOX ADDRESS WILL NOT BE ACCEPTED UNTIL ADVERTISER SUPPLIES PUBLISHER WITH PERMANENT ADDRESS AND PHONE NUMBER.** Copy to be in our hands on the 20th of the third month preceding the date of the issue (i.e., August issue closes May 20th). When normal closing date falls on Saturday Sunday, or a holiday, issue closes on preceding working day.

EDUCATION & INSTRUCTION

EARN your university degree through evaluation assessment, of existing education, experience, achievements. Call, (614) 863-1791, or write, **ASSESSMENT**, Box 13130 R, Columbus, OH 43213.

YOUR own radio station! AM, FM, cable, licensed, unlicensed. Low cost transmitter kits, free info. **BROADCASTING**, Box 130-F7, CA 95969.

ELECTRONICS computer books. International publishers. Lowest rates. Ask list. **BUSINESS PROMOTION**, Lajpat Rai Market, Delhi, India.

REEL TO REEL TAPES

TRUCKLOAD sale Ampex high quality open reel tape, 1800- or 2400-feet on 7-inch reels, used once. Case of 40, \$45.00. Cassettes available. **VALTECH ELECTRONICS**, Box 6-RE, Richboro, PA 18954.

CABLE TV

CHANNEL 3—60dB notch filter. 63.5MHz. \$32. **CROSLLEY**, Dept 606, Box 840, Champlain, NY 12919.

CB RADIO

GET more CB channels and range! Frequency expanders, boosters, speech processors, FM converters, PLL/slider tricks, how-to books, plans, modifications. Catalog \$2.00. **CB CITY**, Box 31500 RE, Phoenix, AZ 85046.

CONVERTERS

GATED pulse wave UHF (speaker box type), has true AGC, parts \$125.00. The following have sound out of the TV like normal with only an antenna connection to the TV or VCR. Deluxe IIB sine wave UHF, has true AGC, parts \$150.00. Digital sync suppression/active video inversion VHF/UHF FV-4, has true AGC, parts \$225. Mitsumi tuner module with AGC, AFT, 504KHZ, etc., \$60.00. Quantity discounts. Plans: large SASE (54 cents postage). Free shipping/handling. 1-312/267-3455. **LSR ENGINEERING**, Dept. RE, PO Box 6075, Chicago, IL 60680.

LONG-PLAY RECORDER

FOUR unique models, allowing up to 20 recording hours on a single ordinary cassette! Models as small as 1½ pounds! Fidelity, features, and quality unavailable elsewhere. Free brochures. **EXTEND-TAPE SYSTEMS**, Dept. R-E, Box LC, Temple Terrace, FL 33687 (813) 985-3014.

SAVE CABLE TV \$\$

CABLE TV Consumer Buyers Guide. Guaranteed lowest prices on cable TV devices and converters. We are an independent consumer service. Manual includes info on which equipment works on your cable system. \$8.00. **CATV INFORMATION CENTER**, PO Box 17621, Ft. Laud., FL 33318.

TI-99/4A SOFTWARE

TI-99/4A owners. Games and application software on cassettes as low as \$5.95. Write: **TI-99/4A CASSETTE SOFTWARE**, 4129 Abercorn Rd., Knoxville, TN 37921.

TIMEX/SINCLAIR SOFTWARE

T/S 1000 programs finance aid (barcharts, interest, record keeping), math quiz (20 levels), electro solve (solves most electronics circuit problems), \$6.95 each. **BILL KEMP**, Box 26086, Bluff Park, AL 35226.

UPGRADE YOUR TELEPHONES

ADD THESE EASY-TO-INSTALL SPECIAL FEATURES

Hold Busy Silencer Circuit

Allows you to put calls on hold. Also lets you silence bell or put phone on "busy". Plans: \$4.00. Kit: \$4.00 - \$2.00 phone.

Intercom Circuit

Lets you use phones as an intercom. No extra wiring required. Less costly than wireless models. Plans: \$7.00. Kit: \$15.00 + \$5.00 phone.

* Kits include plans, parts and board. When ordering kits add \$2.00 for postage. Send SASE for more information.

88 Enterprises, Box 8, Oradell, NJ 07649

TRS-80 COLOR COMPUTER

COLOR COMPUTER OWNERS—12 different programs on cassette for only \$15.00! Games, quizzes, etc. Send check or money order to: **QJN ENTERPRISES**, PO Box 983, Sarasota, FL 33578. Fla. residents add 5% sales tax.

A SINGER'S DREAM!

REMOVES VOCAL FROM MOST STEREO DISCS
The Thompson Vocal Eliminator can actually remove most or virtually all of a solo vocalist from a standard stereo record and yet leave most of the background music untouched! Not an equalizer! We can prove it works over the phone. Write or call for a 24 page brochure and demo record.
Write to: **LT Sound**, Dept. R, P.O. Box 338, Stone Mountain, GA 30086. Phone (404) 493-1258. COST: \$295.00

REVERBERATION FOR ORGANS

Solid state with controls for reverberation and room size.

EVERY ORGAN SHOULD OWN ONE. Send for free flyer—

DEVTRONIX ORGANS, INC.

6101 WAREHOUSE WAY

SACRAMENTO, CALIFORNIA 95826 Dept. B

PLANS & KITS

SUBSCRIPTION TV manual, covers both sine wave and gated sync system, only \$12.95. Includes theory, circuits, waveforms, and trouble-shooting hints. Video game cartridges are easy and inexpensive to duplicate. Plans \$9.95. Information \$2.00, refundable. **RANDOM ACCESS** (Formerly D & S Enterprises), Box 41770R, Phoenix, AZ 85080.

CATALOG! 40 pages of neat electronics parts and kits. Send 50 cents, refundable first order. **BEC ELECTRONICS**, Box 401244R, Garland, TX 75046.

UHF over the air all types, cable systems. Coming soon 2 new complicated UHF units (compatible with satellite owners). Now brand new Deluxe III gated pulse unit, sound through TV. Call for information 301-882-9362, or send \$2.00 (refundable) for catalog. **SATELLITE ELECTRONICS**, PO Box 9534, Baltimore, MD 21237.

FREE KIT Catalog

FUNCTION GENERATOR KIT \$59.95

Auto-Ranging Cap-meter kit \$79.95

Phone 209-772-2076

Write or Phone for FREE CATALOG

DAGE SCIENTIFIC INSTRUMENTS
BOX 144 VALLEY SPRINGS CA 95252

INCREDIBLE price and quality for amplifier, power supply, and many many new electronics kits. Write now for your absolutely free catalog. **INTERNATIONAL POLYTECHNIQUES**, PO Box 862R, New York, NY 10002.

BREADBOARD using spirafit lead kit. Pretinned, spiral leads stretch to desired lengths. No cutting, stripping, wrapping required. Send 50 cents for sample, details, prices free. **CALDER TRADING**, 720 Smithtown Ave., Bohemia, NY 11716.

FUN kits — low cost. Easy to build educational electronics projects. Handbook/catalog \$1.00. **TRIANGLE ELECTRONICS**, 89 Arkay Drive, Hauppauge, NY 11788.



MINI FM MIC

Compact size, only 2" x 1" x 3/4". Transmits to FM radio 88-108 MHz. Exceptional audio quality. Transmits stable signal up to 900 ft. Complete kit incl. case, battery & instructions. Only \$15.95. Assembled \$20.95. Add \$1.55 S&H ea. CA. RES. ADD TAX. Send 20c stamp for brochure.

S.E. Corp., Box 1132-RE
Yorba Linda, CA. 92686

TIMEX/SINCLAIR 1000/ZX81 How-To hardware upgrade book. Covering: buffered expansion interface, serial interface, standard printer interface, and more. \$6.95 ppd 10-day money back guaranteed. **INNER KNOWLEDGE COMPUTERS & PERIPHERALS**, 5944 N.E. Sandy Blvd., Portland, OR 97213.

SUBSCRIPTION TV KITS

UHF Gated Pulse Kit.....\$39.00
UHF Sinewave Kit.....\$37.00
Special Both Kits.....\$69.00
Informative Catalog.....\$ 2.00

Kits include all parts, manual and an etched & drilled PC board. Send for our "Informative Catalog" and find out what type you need.

J & W ELECTRONICS, INC.

P. O. BOX 61-B

CUMBERLAND, RI. 02864

OWN a tone remote retrieve telephone answering device? Throw your tone device away. Retrieve messages with any standard Touch-Tone® telephone. Plans \$10.95 — kit including PC board \$39.95 — check or M.O.— **APP-COM**, PO Box 1031, New Castle, IN 47362.

CATALOG—transmitters, linears, MDS downconverters, scramblers, broadcasting, CB, hobby plans & kits. \$1.00. **PANAXIS**, Box 130-F7, Paradise, CA 95969.

NEW FM transmitter kit. Great for experimenters. Instructions and parts only \$19.95. Buy now. **TUCKER ENTERPRISES**, PO Box 10120, Alexandria, VA 22310-0120.

CONTROL and read up to 256 devices. Plugs into Radio Shack model III. Simple construction, software included. Plans \$15.00. **SPECIALTY ENGINEERING & MFG.**, Inc. PO Box 120, Gonzales, TX 78629.

ELECTRONIC combination lock, patented. Plans available for \$3.00 and SASE from **JINN**, Box 764, Herndon, VA 22070.

TIMEX/Sinclair kits: 2parallel and 2RS232C/O ports \$69.95. **Color graphics** and sound w/16K RAM \$179.95. 32K RAM \$88.95. All kits furnished with high quality PC boards, and plug into the **ST-50**, fully buffered, 8slot motherboard \$149.95. **CW/TTY** interface available soon. Brochure \$1.00 (refundable). **SIGMA-TECHNOLOGY**, Dept. K, Box 971, Va. Beach, VA 23451.

CUSTOM PC boards and photo masks from sketches, schematics, or artwork. Free brochure on services, products, and kits: TTL logic probe, \$13.35. **AIE**, Box 2287, Arcadia, FL 33821.

PRINTED circuit boards. Quick prototypes, production, design, reflow solder. Send print or description for quote to **KIT CIRCUITS**, Box 235 Clawson, MI 48017.

LIGHT display sequencer kits. Send stamp for flyer. **DESIGN SPECIALTY**, P.O. Box 1995, Huntington Beach, CA 92647.

PROJECTION TV ... Convert your TV to project 7 foot picture. Results comparable to \$2,500 projector... Total cost less than \$20.00 ... Plans and lens \$17.50... Illustrated information free... Credit card orders 24 hours. (215) 736-3979. **MACROCO-MAGK**, Washington Crossing, PA 18977

ELECTRONIC touch light control pad five modes dim, medium, bright, delay, and off. Two kits available. Write for free brochure. **EXOTIC ELECTRONIC IDEAS**, PO Box 446, Lake Bluff, IL 60044.

SINE wave decoder problems? Manual includes trouble shooting, alignment, antenna hookup, improvements, theory. \$15.00. **SIGNAL**, Box 2512-R, Culver City, CA 90230.

PROFESSIONAL electronics devices plans, kits, P.C. circuitry, famous drop-in microphone cartridge, debugging equipment, more items available. For information send \$3.00. **MOUNTAIN ELECTRONICS**, R.2, Box 30, Charlotte, TN 37036.

FREE phone calls made by users. Electronics device report, plans sold for information, education only. \$7.50. **DISTRIBUTORS MART**, Dept. RE73, Box 333, Modena, NY 12548.

SAVE energy! Build a computerized thermostat. Schematic and software \$5.00. **GLOVATRON**, PO Box 559, East Detroit, MI 48021.

MICROWAVE television "downconverters." Exclusive new five stage design. Easily assembled. Catalog: \$2.00 (refundable). **NDS**, Box 12652R, Dallas, 75225.

FOR SALE

NEW Repair any TV ... Easy. Anyone can do it. Write **RESEARCH**, Box 517C, Brea, CA 92621.

CABLE TV products: Wireless, corded, & settop converters. Send \$3.00 for catalog. **ADDITIONAL OUTLET CORP.**, 231 E. Commercial Blvd., Ft. Lauderdale, FL 33334.

CABLE TV SECRETS—the outlaw publication the cable companies tried to ban. HBO, Movie Channel, Showtime, descramblers, converters, etc. Suppliers list included. Send \$7.95 to **CABLE FACTS**, Box 711-R Pataskala, OH 43062.

PCB 15 cents sq-in. Free drilling. Quantity discount. **INTERNATIONAL ENTERPRISE**, 6452 Hazel Circle, Simi Valley, CA 91363.

RESISTORS 1/4W & 1/2W 5% C.F. 3 cents. 1% M.F. All values. **No minimums** Volume discounts. Write **JR INDUSTRIES**, 5834-B Swancreek, Toledo, OH 43614.

RELIABLE MICROWAVE TV ANTENNAS

**2.1 to 2.6 GHz
Frequency Range**

34db System Gain (or Greater)
Complete System (pictured) \$119.95
Down Converter Probe Style
(Assembled & Tested) \$49.95
Power Supply (12V to 16V DC+)
(Assembled & Tested) \$39.95

PETERSON ELECTRONICS

4558 Auburn Blvd.
Sacramento, CA 95841
(916) 486-9071

SPECIAL QUANTITY PRICING
Dealers Wanted - COD'S



**1 YEAR WARRANTY
PARTS & LABOR**

COLOR computer VIC-20 programs hardware Rtty code EPROM Programmer RS-232. **FRANK LYMAN**, Box 3091, Nashua, NH 03061.

THE Intelligence Library. Restricted technical secrets—books on **electronic surveillance, lock-picking, demolitions, investigation, etc.** Free brochures: **MENTOR**, Dept. Z, 135-53 No. Blvd., Flushing, NY 11354.

SURVEILLANCE device schematics, books on electronic surveillance methods & equipment, locksmithing, covert technologies, etc. Catalog, \$1.00. **MENTOR**, Dept. Z, 135-53 N. Blvd., Flushing, NY 11354.

.125 aluminum—make your own chassis! Cut to size, squares, rectangles only. 6 cents sq. in., \$10.00 minimum, \$2.00 handling. Shipped UPS collect. Send dimension(s) of piece(s) to: **O'DAY**, PO Box 248, Lansing, IL 60438.

QUALITY MICROWAVE TV SYSTEMS

Complete Systems From \$69⁹⁵

**1.9 to 2.5
GHz
Antennas**

**Galaxy
Electronics**
6007 N. 61st Ave.
Glendale, Az.
85301

1-602-247-1151
1-800-247-1151

COO's / Dealers Wanted



WIRELESS THERMOSTAT

TELESTAT - a portable, wireless thermostat that moves with you. From room to room. To the TV room after dinner. To the bedroom at night. To the kitchen early in the morning. Your furnace works to keep the room where you and Telestat are, at a comfortable level. Telestat saves you money because your furnace works only when needed, instead of running continuously. Use with forced air furnaces and air conditioners. That's double the savings. Year in and year out. **\$94.95***

***SPECIAL THROUGH AUG. 31, 1983**

CALL 1-800-426-8075 or write

COMMUNICATIONS RESEARCH CORPORATION
1720 - 130th Ave. N.E. Bellevue, WA 98005

UNUSUAL UHF subscription TV kits. Also microwave downconverters. Catalog 50 cents. **TROJAN**, 2920 Shelby, Indianapolis, IN 46203.

TELEPHONES—extensive selection—parts, accessories, systems. Free catalog. **NDS**, Box 35444, Los Angeles, CA 90035-0444 (213) 935-9900.

PRINTED circuit boards: quotes free. **SASE** to **JAHMAAL ELECTRONIC SUPPORT**, PO Box 397, Troy, NY 12181.

ELECTRONICS catalog: Scanners, CB, video. All kinds of electronics goodies. Send \$1.00 refundable. **CLEM ELECTRONICS**, 1520 N. Pacific, Fresno, CA 93728.

Full Size Keyboard Conversion

10 3/4 x 7 1/4 x 2 1/8

For
Your
**ZX81/
TS1000**

SUN KD-81

\$69⁹⁵



Easy To Install

No Soldering - No Modifications

41 Keys with Full Size Space Bar - Allows Touch Typing Same Key Layouts as Sinclair - Two Color Keypops Keyboard Case Holds Both Keyboard and Computer Commands and Graphics Spelled Out on Keypops Rear Cutout for Any RAM or Expansion Modules

16K Piggyback RAM Module ... P/N MX-16 \$49.95

SUNTRONICS CO., INC.

In Calif Call **213-644-1149**

Outside Calif Call **1-800-421-5775**

Or send Check or M.O. to:

P.O. Box 1957 Hawthorne CA 90250

California residents add 8 1/2% sales tax.

Add \$4.00 ship/handling. VISA/Mastercard include expiration date.

TUBES — all types, discount prices. Many oldies and hard-to-find types. **SASE** for list. **ANTIQUÉ RADIO & TUBE CO.**, Dept. 701, 1725 W. University, Tempe, AZ 85281.

XFORTH — Forth-79 standard sub-set plus extra utilities. 10K + available for user code. Or cassette for 16K ZX-81. \$25.00 + \$1.00 P&H. Arkansas residents add \$1.00. **HAWG WILD SOFTWARE** Box 7668-R, Little Rock, AR 72207.

TRANSPOSERS digital rhythm displays super cymbal, many more inexpensive accessories, all organs. Send for free brochure. **SACHA INTERNATIONAL**, 943 Archer Street, San Diego, CA 92109.

"Bare Power Supply Boards"

(FOR ALL TO-220 3 TERMINAL REGULATORS)

"Four Styles In Stock" All Boards 2"x3" - 610
 • 7800 Positive Fixed Silk Screened - Soldermasked
 • 7900 Negative Fixed Make Projects A Snag!
 • 3177 Positive Adjustable Includes: Detailed Instructions
 • 3377 Negative Adjustable Parts Lists-Schematics-Design Tips

\$2.50 ea. - 4 for \$8.00 add \$1.00 postage & handling

MIDWEST TECHNICAL
P.O. BOX 272, AURORA, IL 60507


HI-REL mil-spec metal film resistors. RN55's, RNC60's, etc. at super low prices. Contact us for free inventory listing and price list. **INTERMOUNTAIN ELECTRONICS**, Box 531, Boise, ID 83701 (208) 384-9755.

PRINTED-circuit boards: single side, prototype, and quantity, quick delivery. Send positive, free quotes. **FABTRON**, Box 925, Dept. C, Columbia, TN 38401 (615) 381-1143.

SUPER summertime surplus savings! Free flyer. **ELECTRONIX LTD.**, Dept. R-7, 3214 S. Norton, Sioux Falls, SD 57105.

RADIO West — still the best for SW/MW DX receivers and receiver modifications! Catalog 50 cents. **RADIO WEST**, 3417 Purer Road, Dept RE, Escondido, CA 92025 (619) 741-2891.

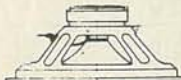SPECIAL sale —40-channel TV converter, built-in fine tuning. Only \$28.95, add \$2.50 postage and handling. Free bargain catalog. **IN-X-SALES**, Box 222, Medford, MA 02155.



WRITE FOR

McGEE'S

SPEAKER & ELECTRONICS CATALOG

1001 BARGAINS IN SPEAKERS

Tel.: 1 (816) 842 5092

1901 MCGEE STREET KANSAS CITY, MO. 64108

SCANNER accessories and crystals. Free catalog — best prices anywhere. **SCANNER PLUS**, Box 45, Tilton, NH 03276 (603) 286-3082.

SCANNER/monitor accessories—kits and factory assembled. Free catalog. **CAPRI ELECTRONICS**, Route 1R, Canon, GA 30520.

ZX81/TS1000: 25 Family Fun Programs for 16K! You type and save! Send \$7.50 to **H. DAILY**, Box 553, Valley Center, CA 92082.

MICROWAVE antenna 38 dB gain, slotted dish, probe, power supply, 60' cable, warranty. **AMA SYSTEMS**, PO Box 1354, Sandy, UT 84091. Only \$79.95.

THE BEST PLACE to BUY, SELL or TRADE NEW and USED EQUIPMENT

NUTS & VOLTS MAGAZINE

BOX 1111-E • PLACENTIA, CA 92670

(714) 632-7721

Join Thousands of Readers Nationwide

Every Month

ONE YEAR U.S. SUBSCRIPTIONS

\$7.00 - 3rd Class • \$12.50 - 1st Class

☐ \$25.00 - Lifetime - 3rd Class

NUTS & VOLTS

HIGH GEAR COMPUTERS

SOFTWARE

SCANNERS • OPTICS

TEST EQUIPMENT

MICROWAVE

SATELLITES

ALSO VISUAL

NEW PRODUCTS

COMPONENTS • KITS

ANTIQUÉ ELECT.

PUBLICATIONS

PLANS • SERVICES

Many Happy Returns



Take stock in America.



NEW ITEMS, SUPER VALUES AT THE PARTS PLACE™

No Minimum Order! Friendly Service! See Before You Buy!

Telephone Ringer IC



NEW! 3.99

- Phone Line Powered
- Ideal for Remote Ringers

TCM1512A. Detects ring and drives an external piezo element (not incl.). 800 to 2 kHz output with 10 Hz warble, determined by external resistor. On-chip static protection and anti-tap circuitry. 276-1302 3.99

Enclose Your Project!



NEW!
Low As **4.99**

Aluminum. Eggshell white with black top. Complete with hardware and rubber feet.

Size	Cat. No.	Price
1 1/8" x 4 1/4" x 4 1/8"	270-271	4.99
1 1/8" x 5 1/4" x 6 1/8"	270-272	5.99
3 1/8" x 4 1/4" x 4 1/8"	270-273	6.99
3 1/8" x 6 1/4" x 6 1/8"	270-274	7.99

Sale! 25-Range Multitester

Save \$12

Reg. 27.95

15.95

- 20,000 Ohms Per Volt DC Sensitivity
- With Leads And Manual



Buy now and get this accurate Micronta® multitester at 43% off! Features a big 4" mirrored scale, "output" jack to measure AC signals present in DC circuits. Measures 0 to 1200 volts DC in seven ranges, 0 to 1200 volts AC in five ranges, 0 to 300 milliamps DC current in four ranges, resistance in four ranges, and -20 to +63 dB in five ranges. 5 1/2" x 3 7/8" x 1 1/2". Requires "AA" battery. 22-202 **Sale 15.95**

IF, FM & Video ICs



179

MC1330 Video Detector. 3rd IF, detector, video and AFC buffers. High linearity. 10-24VDC. 8-pin w/specs. 276-1757 2.29
MC1350 Universal IF Amp With AGC. For radio and TV circuits. Usable to beyond 60 MHz. 8-pin w/specs. 276-1758 1.99
MC1358/CA3065 FM Detector. IF amp, limiter, FM detector, electronic volume attenuator and audio driver. For 100 kHz-5.5 MHz IFs. 14-pin w/specs. 276-1759 1.79

Ceramic TV-Sound Filters



NEW!

Low As **69¢**

- Replace Costly Transformers
- Pretuned—No Peaking or Tweaking!

SFE4.5MB. Use in place of 4.5 MHz sound take-off transformer. 3 db bandwidth: 105 kHz, typ. 272-1304 69¢
CDA4.5MD3 Discriminator. This differential peak detector works great with our FM detector IC #276-1759, above. 274-1305 79¢

10% IRD Capacitors



NEW!
Low As **59¢**

IC pin spacing. 63WVDC

.01 µF. 272-110 59¢
 .1 µF. 272-111 69¢
 .47 µF. 272-112 89¢

Horizontal Output



7.95
TO-3 Case

2SC1308. Rugged NPN transistor is exact replacement in many 19" color TVs. Servicemen—keep several on hand! 276-2055 7.95

3PDT Toggle Switch



3.49 Mini Size

Contacts rated 6 amps at 125VAC. 1/4" mounting hole. With hardware. 275-661 3.49

Tri-Color LED



1.39 Ideal Status Indicator

XC-5491. Glows red on DC, green on reverse DC, yellow on AC! 2.2V at 25 milliamps, typical. 276-035 1.39

Micro 5VDC Relay

2.49 ACTUAL SIZE



Ideal for crowded PC boards. SPDT contacts: 1 amp at 125VAC. 55-ohm coil, .100" pin spacing. 275-240 2.49

Sale! Program Books for Your TRS-80



39% Off!
Your Choice Only

Reg. 7.95

4.88



Computer Games. Contains listings for over 25 fun-filled game programs for TRS-80 Level II BASIC. Selections include Blackjack, Poker, Tennis, Tic-Tac-Toe, Escape, Golf, Basketball, Psycho, Star Trek, Biorhythm, Poem and more. 151 pages. 62-2068 **Sale 4.88**
Using the TRS-80 in Your Home. Listings for over 75 practical programs in Level II BASIC including finance, analysis, games, scheduling, lists and much more. 330 pages. 62-2069 **Sale 4.88**


Electret Element



99¢
Hi-Fi Response

Omnidirectional, PC mountable. 20 to 15 kHz ± 4 dB. 2-10VDC, only 1 milliamp current drain. 270-090 **New Low Price 99¢**

Portable Solar Panel

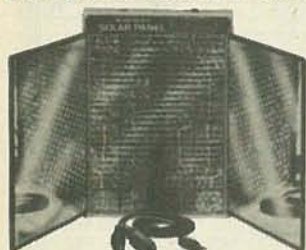

24.95

Radio Shack Exclusive!

Switchable 6 or 12VDC output. 32 full-spec cells produce approximately 1/2 watt of "free" power. 277-1250 24.95

Resistor Networks



NEW!
89¢ Each
IC Lead Spacing

Five 1/4-watt resistors in one package. Ideal for digital pull up, LED current limiting. 470-Ohm, 271-095. 1000-Ohm, 271-096. 10k-Ohm, 271-097.


Fun Sounds Made Easy!



Only **2.49**
16-Pin DIP With Data

SN94281. Just add a speaker and a few parts to make amazing sounds. Heart of a rewarding project—try it! 276-1767 2.49

D-Sub 25 Connectors

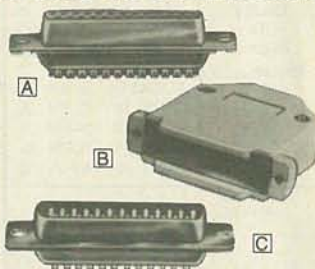

Solder type. Perfect for computer interfacing and making your own RS-232 cables and extension cords.

- A Male.** 276-1547 2.99
- B Optional Hood.** 276-1549 1.99
- C Female.** 276-1548 3.99

CPU's & SUPPORT CHIPS	8251 4.50 8253 5.95 8256 6.95 8279-5 6.95 8255 4.50	
8039 6.95 8080A 2.75 8085A 5.75 8088 29.95 AMD 2901 8.95 8202 19.95 8212 1.90 8214 3.00 8216 1.75 8224 2.25 8226 1.80 8228 3.50 8156 5.00 8159 8.95 8257 14.50 8748 19.95 8755 19.95	8257 (AM9517) 7.95 8259 5.95 8355 12.95 8502 5.75 290A CPU 4.75 290B CPU 12.95 290A S10 10.95 290A P10 4.95 290CTCA 6.75 TMS 9927 NL 9.95 8275 16.95 893L 12.95 6810 13.95 6815 2.50 6821 2.95 6850 2.95 68000L8 39.50	
SHIFT REGISTERS	74102 2.00	
DISC CONTROLLERS	MM1402 1.75 MM1403 1.75 MM1404 1.75 MM5013 2.50 MM5055 2.50 MM5057 2.00 MM5058 2.00 MM5060 2.50	1793 35.00 1795 45.00 1797 45.00 D76C 16.95
ROM's	2708 2.95 2716 + 5V 3.50 2732 5.95 2732A-2 15.95 2532 7.95 2764 9.95 82S23 1.95 82S115 4.00 (6381) 1.95 82S129 1.95 82S130 1.95 9628A-3 3.00 AM524C 2.95 82S5-5 1.25 74S387 1.75 74S474 3.95	21L02-3 .70 211AL 1.95 214L-3 1.65 2147-3 4.95 TMS3408 1.75 MK4069 1.35 MK4027-3 1.75 TMS4050NL 2.95 MK4096-11 1.25 4116-3 1.10 4116-15 1.50 5101E 2.95 29104-4 2.50 6115-5 5.50 6264 (4184-2) 5.75 5875 6.95
RAM's	2708 2.95 2716 + 5V 3.50 2732 5.95 2732A-2 15.95 2532 7.95 2764 9.95 82S23 1.95 82S115 4.00 (6381) 1.95 82S129 1.95 82S130 1.95 9628A-3 3.00 AM524C 2.95 82S5-5 1.25 74S387 1.75 74S474 3.95	21L02-3 .70 211AL 1.95 214L-3 1.65 2147-3 4.95 TMS3408 1.75 MK4069 1.35 MK4027-3 1.75 TMS4050NL 2.95 MK4096-11 1.25 4116-3 1.10 4116-15 1.50 5101E 2.95 29104-4 2.50 6115-5 5.50 6264 (4184-2) 5.75 5875 6.95

SCR's	1.5A 6A 35A 110A	TRIAC's	PRV 1A 10A 25A	
100 .35 .40 1.40		100 .35 .50 1.40		
200 .40 .50 1.80 9.00		200 .50 .80 1.90		
400 .60 .70 2.40 12.00		400 .70 1.00 2.60		
600 1.00 3.60 15.00		600 1.00 1.20 3.00		
INTER FACE & DRIVERS	4001 - .25 4006 - .85 4007 - .27 4009 - .39 4010 - .46 4011 - .22 4012 - .22 4013 - .35 4015 - .39 4016 - .30 4017 - .60 4018 - .30 4019 - .39 4020 - .35 4021 - .70 4022 - .76 4023 - .76 4024 - .85 4025 - .25 4026 - .85 4027 - .40 4028 - .75 4029 - .35 4034 - 1.75 4035 - .75 4036 - .85 4042 - .56	4043 - .85 4044 - .85 4046 - .85 4047 - .85 4048 - .35 4049 - .35 4051 - .75 4052 - .75 4053 - .75 4054 - .39 4055 - .39 4056 - .75 4057 - .75 4058 - .35 4059 - .35 4060 - .35 4061 - .35 4062 - .75 4063 - .75 4064 - .35 4065 - .35 4066 - .39 4067 - .39 4068 - .75 4069 - .75 4070 - .35 4071 - .35 4072 - .20 4073 - .85 4074 - .85 4075 - .75 4076 - .85 4077 - .35 4078 - .35 4079 - .25 4080 - .15 4081 - .49 4082 - .49 4083 - .49 4084 - .15 4085 - .85 4086 - .85 4087 - .15 4088 - .15 4089 - .15 4090 - .15 4091 - .15 4092 - .15 4093 - .15 4094 - .15 4095 - .15 4096 - .15 4097 - .15 4098 - .15 4099 - .15 4100 - .15	4583 - .90 4584 - .75 74C00 - .77 74C02 - .27 74C04 - .35 74C08 - .30 74C10 - .27 74C14 - .85 74C20 - .27 74C32 - .39 74C42 - 1.00 74C43 - .50 74C76 - .70 74C85 - 1.40 74C86 - .35 74C90 - .90 74C92 - .90 74C164 - .85 74C167 - 1.75 74C180 - 1.20 74C181 - 1.15 74C183 - 1.15 74C173 - .75 74C174 - 1.93 74C175 - 1.19 74C81 - .39 74C92 - .70 74C94 - 1.75 74C95 - 1.00 74C83 - 1.25	
C/MOS	4001 - .25 4006 - .85 4007 - .27 4009 - .39 4010 - .46 4011 - .22 4012 - .22 4013 - .35 4015 - .39 4016 - .30 4017 - .60 4018 - .30 4019 - .39 4020 - .35 4021 - .70 4022 - .76 4023 - .76 4024 - .85 4025 - .25 4026 - .85 4027 - .40 4028 - .75 4029 - .35 4034 - 1.75 4035 - .75 4036 - .85 4042 - .56	4043 - .85 4044 - .85 4046 - .85 4047 - .85 4048 - .35 4049 - .35 4051 - .75 4052 - .75 4053 - .75 4054 - .39 4055 - .39 4056 - .75 4057 - .75 4058 - .35 4059 - .35 4060 - .35 4061 - .35 4062 - .75 4063 - .75 4064 - .35 4065 - .35 4066 - .39 4067 - .39 4068 - .75 4069 - .75 4070 - .35 4071 - .35 4072 - .20 4073 - .85 4074 - .85 4075 - .75 4076 - .85 4077 - .35 4078 - .35 4079 - .25 4080 - .15 4081 - .49 4082 - .49 4083 - .49 4084 - .15 4085 - .85 4086 - .85 4087 - .15 4088 - .15 4089 - .15 4090 - .15 4091 - .15 4092 - .15 4093 - .15 4094 - .15 4095 - .15 4096 - .15 4097 - .15 4098 - .15 4099 - .15 4100 - .15	4583 - .90 4584 - .75 74C00 - .77 74C02 - .27 74C04 - .35 74C08 - .30 74C10 - .27 74C14 - .85 74C20 - .27 74C32 - .39 74C42 - 1.00 74C43 - .50 74C76 - .70 74C85 - 1.40 74C86 - .35 74C90 - .90 74C92 - .90 74C164 - .85 74C167 - 1.75 74C180 - 1.20 74C181 - 1.15 74C183 - 1.15 74C173 - .75 74C174 - 1.93 74C175 - 1.19 74C81 - .39 74C92 - .70 74C94 - 1.75 74C95 - 1.00 74C83 - 1.25	
NO. 30 WIRE WRAP WIRE SINGLE STRAND	100' \$1.40	CRYSTALS	2.95 ea.	

EPOXY GLASS VECTOR BOARD	1/16" thick with 1/10" spacing 4 1/2" x 6 1/2" \$1.95
TRANSISTOR SPECIALS	2N1307 PNP GET-O-5 .40 2N4004 PNP GET-O-5 \$11.00 HEP 68014 - PNP GET-O-3 .85 TIP 111 - .50 TIP 145 .11.35 2N3833 NPN SWITCHING POWER .40 MRF-8004 CM RF TRANSISTOR NPN .75 2N3772 NPN SI TO-3 .11.00 2N4908 PNP SI TO-3 .11.00 TIP 2662 PNP SI .70 2N2222 NPN SI TO-18 .71/1.00 2N2907 PNP SI TO-18 .61/1.00 2N3055 NPN SI TO-3 .50 2N3804 NPN SI TO-92 .71/1.00 2N3808 PNP SI TO-92 .71/1.00 2N1078 NPN SI TO-220 .11.55 TIP 318 NPN SI TO-220 .40 TIP 328 PNP SI TO-220 .40 TIP 34 PNP SI .95 TIP 121 PNP SI U87 .60 BU205 .81.75 DPS2000 - DUAL POWER DIARL .93.95 MJE3057 .50
TTL SERIES	7400 .17 7472 .30 74612 .60 7401 .17 7473 .35 74163 .60 7402 .17 7474 .32 74164 .60 7403 .17 7475 .35 74165 .60 7404 .24 7476 .35 74166 .60 7405 .24 7480 .45 74170 1.60 7406 .28 7483 .50 74173 .75 7407 .28 7485 .55 74174 .65 7408 .24 7486 .35 74175 .60 7409 .18 7488 1.60 74176 .75 7410 .17 7490 .35 74180 1.50 7411 .22 7491 .45 74182 .60 7412 .30 7492 .45 74190 .70 7413 .35 7493 .35 74191 .75 7414 .45 7494 .60 74193 .79 7415 .25 7495 .55 74194 .85 7416 .25 7496 .60 74195 .45 7417 .25 74107 .30 74196 .75 7425 .25 74116 1.50 74221 1.00 7426 .25 74121 .29 74273 .85 7427 .25 74122 .39 74279 .60 7430 .17 74123 .42 74298 .65 7432 .27 74126 .45 74305 .65 7437 .27 74145 .60 74367 .65 7438 .27 74148 1.10 74390 .90 7440 .17 74150 1.10 75324 1.75 7441 .27 7491 .45 75325 1.50 7442 .45 74153 .40 75492 1.05 7445 .65 75154 1.10 9601 .75 7446 .65 74155 .50 9602 .75 7447 .65 74157 .50 8726 1.00 7448 .65 74160 .85 8797 .90 7450 .17 74161 .65 8798 .90
74LS SERIES	74LS00 .28 74LS109 .45 74LS240 1.10 74LS01 .28 74LS112 .50 74LS241 1.10 74LS02 .33 74LS113 .60 74LS242 1.10 74LS03 .33 74LS114 .65 74LS243 1.10 74LS04 .35 74LS123 .85 74LS244 1.30 74LS06 .38 74LS125 .60 74LS245 1.75 74LS08 .35 74LS126 .60 74LS246 .95 74LS09 .35 74LS132 .75 74LS247 .90 74LS10 .35 74LS136 .95 74LS248 1.10 74LS11 .35 74LS137 .95 74LS249 .90 74LS12 .35 74LS138 .70 74LS250 .70 74LS13 .45 74LS139 .70 74LS257 .70 74LS14 .50 74LS147 1.95 74LS258 .80 74LS15 .50 74LS151 .70 74LS259 1.00 74LS20 .35 74LS153 .70 74LS260 .70 74LS21 .35 74LS154 2.40 74LS273 1.15 74LS22 .35 74LS157 .95 74LS279 .90 74LS23 .45 74LS158 .80 74LS280 1.80 74LS27 .40 74LS159 .80 74LS283 .80 74LS28 .50 74LS167 .80 74LS283 .80 74LS30 .35 74LS168 .90 74LS290 .90 74LS32 .40 74LS169 .90 74LS291 .90 74LS37 .40 74LS169 .90 74LS291 .90 74LS38 .40 74LS169 .90 74LS291 .90 74LS42 .35 74LS169 .90 74LS291 .90 74LS43 .35 74LS169 .90 74LS291 .90 74LS44 .35 74LS169 .90 74LS291 .90 74LS45 .35 74LS169 .90 74LS291 .90 74LS46 .35 74LS169 .90 74LS291 .90 74LS47 .35 74LS169 .90 74LS291 .90 74LS48 .35 74LS169 .90 74LS291 .90 74LS49 .35 74LS169 .90 74LS291 .90 74LS50 .35 74LS169 .90 74LS291 .90

ACTIVE RECEIVING ANTENNA

Gives excellent reception, 50 KHz to 30 MHz.

New MFJ-1024 Active Receiving Antenna mounts outdoors away from electrical noise for maximum signal. Gives excellent reception of 50 KHz to 30 MHz signals. Equivalent to wire hundreds of feet long. Use any SWL, MW, BCB, VLF or Ham receiver. High dynamic range RF amplifier. 54 in. whip. 50 foot coax. 20 dB attenuator prevents receiver overload. Switch between two receivers. Select auxiliary or active antenna. Gain control. "ON" LED. Remote unit, 3x2x4 in. Control, 6x2x5 in. 12 VDC or 110 VAC with optional adapter, MFJ-1312, \$9.95.

\$129.95 (+\$4.00 shipping)

Order from MFJ and try it. If not delighted, return within 30 days for refund (less shipping). One year unconditional guarantee. Order today. Call TOLL FREE 800-647-1800. Charge VISA, MC, or mail check, money order. Write for free catalog. Over 100 products.

CALL TOLL FREE 800-647-1800

Call 601-323-5869 in Miss., outside continental USA, tech/order/repair info. TELEX 53-4590.

MFJ ENTERPRISES, INCORPORATED

Box 494, Mississippi State, MS 39762

CIRCLE 66 ON FREE INFORMATION CARD

50 PIN RIBBON CONNECTORS . . . \$2.25	34 PIN RIBBON CABLE CONN . . . \$2.00
26 PIN RIBBON CABLE CONN . . . \$1.75	20 PIN RIBBON CABLE CONN . . . \$1.50
10 PIN RIBBON CABLE CONN . . . \$1.00	
2N3820 P FET . . . \$.45	2N5457 N FET . . . \$.45
2N2646 UJT . . . \$.45	ER 900 TRIGGER DIODES . . . 4/\$1.00
2N 6028 PROG. UJT . . . \$.65	
DISC CAPACITORS	1UF 16V . . . 10/\$1.00 100/\$8.00
01UF 35V . . . 16/\$1.00 100/\$5.00	
PRINTED CIRCUIT BOARD	4" x 6" DOUBLE SIDED EPOXY BOARDED 1/16" THICK \$4.00 ea.
5" x 12" . . . \$42.60	
TOGGLE SWITCHES	1080 - SPDT80
3060 - DPDT1.20	209P - DPDT - CENTER OFF \$1.40
IN4148 (IN914) 15/1.00	
L1411-IR DETECTOR . . . 3/\$1.00	FP 100 PHOTO TRANS . . . \$.50
RED LED's 2" 8/\$1.00	YEL. GREEN or AMBER LARGE LED's 2" . . . 6/\$1.00
RED-GREEN BIPOLAR LED . . . \$.90	RED-YELLOW BIPOLAR LED . . . \$.90
MLED92 IR LED \$.40	MRD148 PHOTO DARL. XTOR . . . \$.50
MCT2 OPTO ISOLATORS . . . \$.40	4N25 OPTO ISOLATOR . . . \$.40
1 WATT ZENERS: 3.3, 4.7, 5.1, 5.6, 6.8, 8.2, 9.1, 10, 12, 15, 18, or 22V . . . 6/\$1.00	

74S SERIES	74S85 1.25 74S163 1.40 74S00 .30 74S86 .60 74S169 1.75 74S02 .30 74S89 .90 74S174 1.40 74S03 .30 74S112 .85 74S175 1.40 74S04 .40 74S133 .50 74S182 1.75 74S05 .45 74S135 1.10 74S194 1.10 74S08 .40 74S138 1.25 74S240 1.00 74S10 .30 74S139 1.10 74S241 1.50 74S11 .35 74S140 1.70 74S257 1.30 74S15 .40 74S151 1.25 74S258 1.30 74S20 .40 74S152 .95 74S260 1.50 74S30 .40 74S157 1.25 74S280 1.75 74S32 .40 74S158 1.25 74S273 2.25 74S74 .70 74S161 1.75 74S374 1.75	
LINEAR CIRCUITS	DA4085EQ - 3.75 LF356 - 1.00 747 - .50 TL062 CP - .85 LM358 - 1.00 CA758 - 1.75 TL064 CN - 1.50 LM361 - 1.75 LM310 - 1.60 TL064 - 1.50 LM370 - 1.60 4558 - .80 LM201 - .75 LM377 - 1.60 4558 - .50 LM301/748 - .30 LM380 - .85 LM2008 - 1.75 LM307 - .30 LM383 - 1.90 LM2191 - .95 LM308 - .60 LM386 - .85 CA3018 - 1.95 LM310 - 1.10 LM387 - 1.25 CA3078AT - 1.50 LM311 .50 LM390 - .75 CA3095 - .75 LM318 - .75 LM555 - .34 AD270LD - 4.95 LM319 - .95 LM556 - .65 CA3140 - 1.00 LM324 - .55 565 - .95 3900 - .45 LM339 - .65 566 - 1.25 4138 - .85 LM348 - .90 567 - .85 NS5698A - 1.50 LF361 - .55 709 - .25 DE630B - 1.75 LM310 .50 710 - .45 8038CC - 3.90 LF355 - .90 711CH - .40 LM1300 - .95 741CV - .40 CA3089E - 1.75	
FULL WAVE BRIDGE	PRV 2A 6A 25A 100 1.40 200 80 1.30 2.20 400 1.00 1.65 3.30 600 1.30 1.90 4.40	12V DC RELAYS TTL SIZE S.P. 1200 ohm coil .75 D.P. 400 ohm coil .95
SILICON POWER RECTIFIERS	PRV 1A 3A 12A 50A 125A 240A 100 .05 1.4 35 90 4.25 6.00 200 .06 1.7 50 1.30 5.25 9.00 400 .09 2.5 65 1.50 6.50 12.00 600 .11 3.0 80 2.00 8.50 15.00 800 1.3 35 1.00 2.50 10.00 18.00 1000 20 45 1.25 3.00 12.50 26.00	
REGULATORS	LM338K \$5.75 223K (LA1406) . . . \$1.75 LM317T \$1.00 LM3095 \$.75 78L05, 78L12 . . . \$.40 240T-5, 6, 8, 9, 12 7207, 5, 12, 15 or 24 \$.85 LAS1412 + 12V . . . \$.75 LM 337T \$1.95 3A \$3.95	
TANTALUM CAPACITORS	22UF 35V 5/\$1.00 15UF 16V 3/\$1.00 47UF 35V 5/\$1.00 30UF 6V 5/\$1.00 68UF 35V 5/\$1.00 33UF 15V \$.50 1UF 20V 5/\$1.00 47UF 20V \$.85 2.2UF 20V 5/\$1.00 68UF 16V \$1.00 3.3UF 20V 4/\$1.00 120UF 6V \$.75 4.7UF 35V 4/\$1.00 200UF 20V \$1.75 6.8UF 20V 4/\$1.00 150UF 16V \$1.30 10UF 20V - \$.40 330UF 10V \$1.75 22UF 10V - \$.30	

FLAT RIBBON CABLE GRAY 28 gauge	26 conductor .60/ft 40 conductor .90/ft 50 conductor 1.00
WIREWRAP SOCKETS	14 PIN .45 18 PIN .50 18 PIN .65 20 PIN .90 24 PIN 1.10 28 PIN 1.25 40 PIN 1.50
DIP SWITCHES	CTS 206-4 4 POSITION .75 CTS 206-7 7 POSITION .95 CTS 206-8 8 POSITION .95 CTS 206-10 10 POSITION 1.25
DIP SOCKETS 20 PIN .25	8 PIN .10 22 PIN .25 14 PIN .12 24 PIN .25 16 PIN .15 28 PIN .35 18 PIN .20 40 PIN .40
DB CONNECTORS	DB9P - \$2.00 DB25P - \$2.40 DB9S - 3.00 DB25S - 3.20 HOODS - 1.10 HOODS - 1.10

SCR

Free Buyers Guide

pages of the latest in components, tools and instruments - a must for DESIGNERS, instructors and maintenance engineers.

NEW ZENITH ZXM 121

High legibility 12" green phosphor monitor. 15 Mhz bandwidth, 40 or 80 character selectable full compatibility. **\$99.95**

PARTS	PRICES	ITEM	PRICES
7808	1.59	2200 40VDC UF	1.89
7815	1.59	1000 UF 16VDC	1.69
1330	1.89	470 35 V	1.09
1350	1.65	220 MFD 25V	.89
1358	2.50	100 MFD 16V	.79
38B-3	2.50	10 MFD 50V	.36
4558	2.00	4.7 MFD 35V	.36
1458	1.25	1 MFD 50V	.36

RESISTOR BUYOUT

MOST STANDARD VALUES
1/4 WATT 5% RESISTORS 1 OHM TO 10 MEG. OHM
2 K MIN. BUY 1 K MIN. PER VALUE

\$6.50 Per 1,000

UHF/VHF Conversion Kit - with Genuine Mitsumi Tuner. **\$119.95**

CALL OUR HOT LINES

IN CALIF. (714) 527-2554
OUTSIDE CAL. (800) 854-8660

SCR ELECTRONICS CENTER

5303 Lincoln Ave., Cypress, CA 90630

POSTAGE RATES	ADD 10% FOR ORDERS UNDER \$25.00 ADD 5% FOR ORDERS BETWEEN \$25.00 & \$50.00 ADD 3% FOR ORDERS ABOVE \$50.00
TERMS: FOB CAMBRIDGE, MASS. SEND CHECK OR MONEY ORDER. MINIMUM TELEPHONE. C.O.D. PURCHASE ORDER OR CHARGE \$20.00. MINIMUM MAIL ORDER \$5.00.	SEND \$25 FOR OUR CATALOG FEATURING TRANSISTORS & RECTIFIERS. 145 HAMPSHIRE ST., CAMBRIDGE, MASS. 02138

SOLID STATE SALES	P.O. BOX 74 D SOMERVILLE, MASS. 02143
--------------------------	--

TEL (617) 472-7053	WE SHIP OVER 95% OF OUR ORDERS WITHIN 24 HOURS OF RECEIPT
TOLL FREE 1-800-343-5230	FOR ORDERS ONLY

WE HAVE QUALITY PARTS, DISCOUNT PRICES AND FAST SHIPPING!

TRANSFORMERS

120 volt primaries

5.6 VOLTS at 750 MA	\$3.00
8 VOLTS at 150 MA	\$1.25
16.5 V. at 3 AMPS	\$6.50
18 V. at 850 MA	\$3.60
18 VOLTS at 1 AMP	\$4.50
18 V.C.T. at 2 AMP	\$5.50
24 VOLTS at 250 MA	\$2.50
24 VCT at 1 AMP	\$4.50
42 V.C.T. at 1.2 AMP	\$4.50

DC WALL TRANSFORMER

ALL ARE 115 VAC PLUG IN

4 VDC at 70 MA	\$2.50
9 VDC at 225 MA	\$3.00
16.5 VAC at 10 VA	\$3.50
17 VAC at 500 MA	\$4.00
22 VDC at 60 MA	\$2.50

VARACTOR DIODE

MV2205 3 FOR \$1.00
16 PF 100 FOR \$30.00

BB-103 3 for \$1.00
33 PF 100 FOR \$30.00

2 CHANNEL LIGHT ORGAN

EASILY HOOKS INTO STEREO SPEAKERS AND ALLOWS 110 VAC LIGHTS TO DANCE WITH MUSIC. TWO SEPARATE 110 VAC OUTPUTS FOR HIGH AND LOW FREQUENCY AUDIO SIGNALS. USE TWO ORGANS FOR STEREO...

\$6.50 PER UNIT

COLOR LIGHT STRING AVAILABLE \$1.75 EA

BLACK PLASTIC CASE

PAC-TEC SERIES C

BLACK PLASTIC ENCLOSURE ADJUSTABLE HEIGHT FROM 1.63" TO 2.93"; WIDTH 6.85"; DEPTH 8"; BUILT-IN STAND OFFS FOR P.C. BOARDS... FRONT AND BACK PANELS NOT INCLUDED...

\$5.25 PER CASE

2K 10 TURN MULTI-TURN POT

SPECTROL #MOD 534-7161
\$5.00 EACH

MIKE CONNECTOR

5 CONDUCTOR IN-LINE PLUG AND CHASSIS MOUNT JACK. TWIST LOCK STYLE. SAME AS SWITCHCRAFT 12CL5M.
\$2.50 PER SET

CRYSTALS

CASE STYLE HC33/U

2 MHZ	COLORBURST
	3579.545 KC

\$3.50 EACH \$1.00 EACH

T.V. GAME SWITCH

RCA PLUG or 300 OHM IN

300 ohms OUT

\$2.75 EACH

S.C.R.

0.8 AMPS 30 VOLTS 5 for \$1.00

4 AMPS 200 VOLTS 65¢ EACH

4 AMPS 500 VOLTS 85¢ EACH

TRIAC

6 AMPS 400 VOLTS 75¢ EACH

TRANSISTORS

2N706	5 for \$1.00
2N2222A	4 for \$1.00
PN2222	8 for \$1.00
2N2904	4 for \$1.00
2N2905	4 for \$1.00
2N2907	4 for \$1.00
MJ3030	\$2.50
2N3055	\$1.00
2N3585	\$1.00
2N3904	5 for \$1.00
2N3906	5 for \$1.00
2N4401	5 for \$1.00
2N4403	5 for \$1.00
2N4898	\$1.50
D43C	2 for \$1.00
D44C2	.75
TIP 31	.75
TIP 32	.75
TIP 121	.75
TIP 126	.75

MICROWAVE TRANSISTOR

MRF 901 REDUCED TO N.P.N. SILICON **\$2.00 EACH**

LIGHTS

GRAIN OF WHEAT T1 SIZE

.125" DIA. (3.15mm)

3 to 6 VOLTS 3 for \$1.00
Rated: 55ma @ 5 VOLTS

6 to 12 VOLTS 3 for \$1.00
Rated: 55ma @ 8 VOLTS

12 to 24 VOLTS 3 for \$1.00
Rated: 45ma @ 14 VOLTS

T1 SIZE WITH WIRE LEADS

3 to 6 VOLTS 2 for \$1.00
Rated: 55ma @ 5 VOLTS

6 to 12 VOLTS 2 for \$1.00
Rated: 55ma @ 8 VOLTS

12 to 24 VOLTS 2 for \$1.00
Rated: 45ma @ 14 VOLTS

T1- 3/4 SIZE WITH WIRE LEADS

.163" DIA. (4.14mm)

3 to 6 VOLTS 2 for \$1.00
Rated: 45ma @ 6 VOLTS

6 to 12 VOLTS 2 for \$1.00
Rated: 55ma @ 8 VOLTS

12 to 24 VOLTS 2 for \$1.00
Rated: 45ma @ 14 VOLTS

NEON W/ RESISTOR

DIRECT OPERATION

7 for \$1.00 FROM 120 VOLT

120V INDICATOR

NEON INDICATOR. RATED 120 V 1/3 W. MOUNTS IN 5/16" HOLE... RED LENS. 75¢ EACH
10 FOR \$7.00
100 FOR \$65.00

12 VOLT A.C. POWER UNIT

THIS UNIT CONSISTS OF A 12 VOLT 2 AMP TRANSFORMER, 1 AMP CIRCUIT BREAKER, 4 PRONG CINCH JONES SOCKET AND A 3 WIRE A.C. CORD ALL MOUNTED IN AN ATTRACTIVE 4 1/2" x 5 1/2" x 3" CHASSIS BOX. GOOD FOR PARTS OR A NICE START FOR D.C. POWER SUPPLY. **\$8.50 PER UNIT**

CO-AX SWITCH (A/B SWITCH)

75 ohms IN TWO

75 ohms OUT

\$3.50 EACH

LINE CORDS

TWO WIRE

6' 18ga TWO WIRE 3 FOR \$1.00

THREE WIRE

18 INCH 18ga THREE WIRE 2 for \$1.00

8 FOOT 18ga THREE WIRE **\$2.00 EACH**

METERS 0 - 20 V.D.C.

0-20 VDC FULL SCALE FACEPLATE BATTERY TEST SET-UP AS INDICATOR **\$5.50 EACH**

1 MA

2 5/16" SQUARE PANEL METER MOUNTS IN 2 1/8" HOLE **\$5.50 EACH**

0 - 15 V.D.C.

THIS 2-1/4" SQUARE METER MEASURES 0-15 VDC. **\$4.50 EACH**

METAL OXIDE VARISTOR

2 FOR \$1.50

G.E. # V82ZA12 50 VOLTS, NOMINAL D.C. VOLTAGE. 5/8" DIAMETER.

SWITCHES

MINI-PUSH BUTTON

S.P.S.T. MOMENTARY NORMALLY OPEN 1/4" BUSHING **35¢ EACH**

10 FOR \$3.25
100 FOR \$30.00

SPECIFY COLOR: RED, BLACK, WHITE, GREEN, YELLOW.

KEY SWITCH

S.P.S.T. 4 AMPS @ 125 VAC KEY REMOVES BOTH POSITIONS **\$3.50 EA**

LIGHTED PUSH BUTTON

RED LIGHTED 120 VAC 10 AMP. S.P.S.T. "POWER" PRINTED ON FACE. MOUNTS IN 7/8" SQUARE HOLE. **\$1.50 EA 10 FOR \$13.50**

FREE! FREE! free! SEND FOR OUR NEW 40 PAGE CATALOG free! FREE! FREE!

2-WAY CAR STEREO SPEAKER SYSTEM

THESE SPEAKERS COME IN HEAT RESISTANT ABS PLASTIC CABINETS. IDEAL FOR CAR INTERIORS WHERE HEAT CHANGING OCCURS... POWER RATING: 15 WATT NOM. 45 WATT MAX.

EACH SYSTEM CONTAINS A 4 INCH 10 OZ. WOOFER AND 2 INCH TWEETER

SPECIAL PRICE \$36.00 PER PAIR

KEY ASSEMBLY 5 KEY

CONTAINS 5 SINGLE-POLE NORMALLY OPEN SWITCHES. MEASURES 3 3/4" LONG

\$1.00 EACH

6 KEY

CONTAINS 6 SINGLE-POLE NORMALLY OPEN SWITCHES. MEASURES 4 1/4" LONG.

\$1.25 EACH

SLIDE POTS

100K linear tape

2" LONG 1 5/8" TRAVEL **75¢ EACH**

500K linear taper

2 7/8" LONG 1 3/4" TRAVEL **75¢ EACH**

DUAL 100K audio taper

3 1/2" LONG 2 1/2" TRAVEL **\$1.50 EACH**

POWER SUPPLY W/ PRE-AMP

THIS SUPPLY WAS USED TO POWER AN 8 TRACK/CASSETTE UNIT. IT WILL SUPPLY APPROX. 18 VDC AND INCLUDES A SMALL PRE-AMP TO BOOST SIGNAL LEVEL. RCA PLUGS FOR LINE IN/OUT.

\$4.50 EACH

RELAYS

6 VDC RELAY

MINIATURE D.P.D.T. 3 AMP CONTACTS FUJITSU # FBR321D006 **\$1.75 EA 10 / 16.00**

MINIATURE 6 VDC RELAY

SUPER SMALL SPDT RELAY; GOLD COBALT CONTACTS.

RATED 1 AMP AT 30 VDC; HIGHLY SENSITIVE, TTL DIRECT DRIVE POSSIBLE, OPERATES FROM 4.3 TO 6 V. COIL RES. 220 OHM.

1 3/16" x 13/32" x 7/16" AROMAT # RSD-6V **\$1.50 EACH 10 FOR \$13.50**

13 VDC RELAY

CONTACT: S.P.N.C. 10 AMP @ 120 VAC ENERGIZE COIL TO OPEN CONTACT... COIL: 13 VDC 650 OHMS **\$1.00 EACH**

4 PDT RELAY

• 14 pin style
• 3 amp contacts
• 24 volt d.c. or 120 volt a.c. coil
• Used but fully tested **\$1.70 EACH**
specify coil voltage
LARGE QUANTITIES AVAILABLE
SOCKETS FOR RELAY 50¢ each

COMPUTER GRADE CAPACITORS

1700 mfd. 150 VDC **\$2.00**

2 1/2" DIA. x 4 3/4" HIGH

3,600 mfd. 40VDC \$1.00

1 3/8" DIA. x 3" HIGH

6,400 mfd. 60 VDC \$2.50

1 3/8" DIA. x 4 1/4" HIGH

18,000 mfd. 75 VDC \$4.00

2 1/2" DIA. x 4 1/2" HIGH

22,000 mfd. 15 VDC 2" DIA. x 2 1/2" HIGH **\$2.00**

22,000 mfd. 40 VDC 2" DIA. x 5" HIGH **\$3.00**

24,000 mfd. 30 VDC 1 3/4" DIA. x 4" HIGH **\$3.50**

31,000 mfd. 15 VDC 1 3/4" DIA. x 4" HIGH **\$2.50**

72,000 mfd. 15 VDC 2" DIA. x 4" HIGH **\$3.50**

180,000 mfd. at 6V 2 1/2" DIA. x 4 1/2" HIGH **\$1.50**

CLAMPS TO FIT CAPACITORS 50¢ ea.

MINIATURE TOGGLE SWITCHES

ALL ARE RATED 5 AMPS @ 125 VAC

S.P.D.T. (on-on) P.C. STYLE, NON-THREADED BUSHING. **75¢ EACH 10 FOR \$7.00**

S.P.D.T. (on-on) SOLDER LUG TERMINALS. **\$1.00 EACH 10 FOR \$9.00 100 FOR \$80.00**

S.P.D.T. (on-off-on) P.C. LUGS, THREADED BUSHING. **\$1.00 EACH 10 FOR \$9.00 100 FOR \$80.00**

D.P.D.T. (on-on) SOLDER LUG TERMINALS. **\$2.00 EACH 10 FOR \$19.00 100 FOR \$180.00**

EDGE CONNECTORS

ALL ARE .156" SPACING

15 PIN GOLD SOLDER EYELET **\$1.75 EACH**

15/30 GOLD SOLDER EYELET **\$2.00 EACH**

18/36 GOLD SOLDER EYELET **\$2.00 EACH**

22/44 GOLD SOLDER TAIL (P.C. STYLE) **\$2.50 EA 10 FOR \$22.50**

SOLID STATE RELAY

CONTROL: 3-32VDC

LOAD: 10 AMP 140 VAC **\$9.50 EACH**

L.E.D.'S STANDARD JUMBO DIFFUSED

RED 10 FOR \$1.50

GREEN 10 FOR \$2.00

YELLOW 10 FOR \$2.00

FLASHER LED 5 VOLT OPERATION RED JUMBO SIZE **\$1.00 EACH**

BI POLAR LED 2 FOR \$1.70

SUB-MINI LED

.079" x .098" .20 MA AT 1.75V

RED 10 FOR \$1.00

200 FOR \$18.00

GREEN 10 FOR \$1.50

PHOTO-FLASH CAPACITORS

35 MFD 330 VOLT

1" x 5/8" DIA. 45¢ EACH... 10 FOR \$4.00

170 MFD 330 VOLT

1 1/8" x 7/8" 2 FOR \$1.50 10 FOR \$7.00

750 MFD 330 VOLT

2" HIGH x 1 1/4" DIA. **\$1.25 EACH 10 FOR \$11.00**

ALL ELECTRONICS CORP.

905 S. Vermont Ave. P.O. BOX 20406 Los Angeles, Calif. 90006

QUANTITIES LIMITED
MINIMUM ORDER \$10.00
USA: \$2.50 SHIPPING
FOREIGN ORDERS:
INCLUDE SUFFICIENT SHIPPING
CALIF. RES. ADD 6%
NO C.O.D.!

7400

**Number of Pins of each I.C. for easy checkout purposes

Part No.	**Pins	Price	Part No.	**Pins	Price	Part No.	**Pins	Price
SN7400N	14	19	SN7472N	14	29	SN74150N	16	59
SN7401N	14	19	SN7473N	14	35	SN74151N	16	59
SN7402N	14	25	SN7474N	14	35	SN74152N	16	59
SN7403N	14	25	SN7475N	14	45	SN74153N	16	59
SN7404N	14	25	SN7476N	14	45	SN74154N	16	59
SN7405N	14	25	SN7477N	14	45	SN74155N	16	59
SN7406N	14	25	SN7478N	14	45	SN74156N	16	59
SN7407N	14	29	SN7479N	14	45	SN74157N	16	59
SN7408N	14	25	SN7480N	14	45	SN74158N	16	59
SN7409N	14	25	SN7481N	14	45	SN74159N	16	59
SN7410N	14	25	SN7482N	14	45	SN74160N	16	59
SN7411N	14	25	SN7483N	14	45	SN74161N	16	59
SN7412N	14	35	SN7484N	14	45	SN74162N	16	59
SN7413N	14	35	SN7485N	14	45	SN74163N	16	59
SN7414N	14	49	SN7486N	14	45	SN74164N	16	59
SN7415N	14	25	SN7487N	14	45	SN74165N	16	59
SN7416N	14	25	SN7488N	14	45	SN74166N	16	59
SN7417N	14	25	SN7489N	14	45	SN74167N	16	59
SN7420N	14	19	SN7490N	14	49	SN74168N	16	59
SN7421N	14	35	SN7491N	14	49	SN74169N	16	59
SN7422N	14	45	SN7492N	14	49	SN74170N	16	59
SN7423N	16	59	SN7493N	14	49	SN74171N	16	59
SN7424N	16	59	SN7494N	14	49	SN74172N	16	59
SN7425N	16	59	SN7495N	14	49	SN74173N	16	59
SN7426N	16	59	SN7496N	14	49	SN74174N	16	59
SN7427N	16	59	SN7497N	14	49	SN74175N	16	59
SN7428N	14	49	SN7498N	14	49	SN74176N	14	49
SN7429N	14	49	SN7499N	14	49	SN74177N	14	49
SN7430N	14	25	SN7500N	14	49	SN74178N	14	49
SN7431N	14	25	SN7501N	14	49	SN74179N	14	49
SN7432N	14	25	SN7502N	14	49	SN74180N	14	49
SN7433N	14	25	SN7503N	14	49	SN74181N	14	49
SN7434N	14	25	SN7504N	14	49	SN74182N	14	49
SN7435N	14	25	SN7505N	14	49	SN74183N	14	49
SN7436N	14	25	SN7506N	14	49	SN74184N	14	49
SN7437N	14	25	SN7507N	14	49	SN74185N	14	49
SN7438N	14	25	SN7508N	14	49	SN74186N	14	49
SN7439N	14	25	SN7509N	14	49	SN74187N	14	49
SN7440N	14	25	SN7510N	14	49	SN74188N	14	49
SN7441N	14	25	SN7511N	14	49	SN74189N	14	49
SN7442N	14	25	SN7512N	14	49	SN74190N	14	49
SN7443N	14	25	SN7513N	14	49	SN74191N	14	49
SN7444N	14	25	SN7514N	14	49	SN74192N	14	49
SN7445N	14	25	SN7515N	14	49	SN74193N	14	49
SN7446N	14	25	SN7516N	14	49	SN74194N	14	49
SN7447N	14	25	SN7517N	14	49	SN74195N	14	49
SN7448N	14	25	SN7518N	14	49	SN74196N	14	49
SN7449N	14	25	SN7519N	14	49	SN74197N	14	49
SN7450N	14	25	SN7520N	14	49	SN74198N	14	49
SN7451N	14	25	SN7521N	14	49	SN74199N	14	49
SN7452N	14	25	SN7522N	14	49	SN74200N	14	49
SN7453N	14	25	SN7523N	14	49	SN74201N	14	49
SN7454N	14	25	SN7524N	14	49	SN74202N	14	49
SN7455N	14	25	SN7525N	14	49	SN74203N	14	49
SN7456N	14	25	SN7526N	14	49	SN74204N	14	49
SN7457N	14	25	SN7527N	14	49	SN74205N	14	49
SN7458N	14	25	SN7528N	14	49	SN74206N	14	49
SN7459N	14	25	SN7529N	14	49	SN74207N	14	49
SN7460N	14	25	SN7530N	14	49	SN74208N	14	49
SN7461N	14	25	SN7531N	14	49	SN74209N	14	49
SN7462N	14	25	SN7532N	14	49	SN74210N	14	49
SN7463N	14	25	SN7533N	14	49	SN74211N	14	49
SN7464N	14	25	SN7534N	14	49	SN74212N	14	49
SN7465N	14	25	SN7535N	14	49	SN74213N	14	49
SN7466N	14	25	SN7536N	14	49	SN74214N	14	49
SN7467N	14	25	SN7537N	14	49	SN74215N	14	49
SN7468N	14	25	SN7538N	14	49	SN74216N	14	49
SN7469N	14	25	SN7539N	14	49	SN74217N	14	49
SN7470N	14	25	SN7540N	14	49	SN74218N	14	49

MICROPROCESSOR COMPONENTS

MICROPROCESSOR CHIPS			DYNAMIC RAMS			
Part No.	**Pins	Price	Part No.	**Pins	Price	
80C80	40	39	1103	16	1024x1 (300ns)	2.49
80C81	40	39	4027	16	4096x1 (250ns)	2.49
80C82	40	39	4118N-2	16	16384x1 (150ns)	1.89
80C83	40	39	4118N-3	16	32768x1 (200ns)	1.89
80C84	40	39	4118N-4	16	65536x1 (250ns)	1.49
80C85	40	39	4118N-5	16	131072x1 (300ns)	1.49
80C86	40	39	4118N-6	16	262144x1 (350ns)	1.49
80C87	40	39	4118N-7	16	524288x1 (400ns)	1.49
80C88	40	39	4118N-8	16	1048576x1 (450ns)	1.49
80C89	40	39	4118N-9	16	2097152x1 (500ns)	1.49
80C90	40	39	4118N-10	16	4194304x1 (550ns)	1.49
80C91	40	39	4118N-11	16	8388608x1 (600ns)	1.49
80C92	40	39	4118N-12	16	16777216x1 (650ns)	1.49
80C93	40	39	4118N-13	16	33554432x1 (700ns)	1.49
80C94	40	39	4118N-14	16	67108864x1 (750ns)	1.49
80C95	40	39	4118N-15	16	134217728x1 (800ns)	1.49
80C96	40	39	4118N-16	16	268435456x1 (850ns)	1.49
80C97	40	39	4118N-17	16	536870912x1 (900ns)	1.49
80C98	40	39	4118N-18	16	1073741824x1 (950ns)	1.49
80C99	40	39	4118N-19	16	2147483648x1 (1000ns)	1.49
80C100	40	39	4118N-20	16	4294967296x1 (1050ns)	1.49
80C101	40	39	4118N-21	16	8589934592x1 (1100ns)	1.49
80C102	40	39	4118N-22	16	17179869184x1 (1150ns)	1.49
80C103	40	39	4118N-23	16	34359738368x1 (1200ns)	1.49
80C104	40	39	4118N-24	16	68719476736x1 (1250ns)	1.49
80C105	40	39	4118N-25	16	137438953472x1 (1300ns)	1.49
80C106	40	39	4118N-26	16	274877906944x1 (1350ns)	1.49
80C107	40	39	4118N-27	16	549755813888x1 (1400ns)	1.49
80C108	40	39	4118N-28	16	1099511627776x1 (1450ns)	1.49
80C109	40	39	4118N-29	16	2199023255552x1 (1500ns)	1.49
80C110	40	39	4118N-30	16	4398046511104x1 (1550ns)	1.49
80C111	40	39	4118N-31	16	8796093022208x1 (1600ns)	1.49
80C112	40	39	4118N-32	16	17592186444416x1 (1650ns)	1.49
80C113	40	39	4118N-33	16	35184372888832x1 (1700ns)	1.49
80C114	40	39	4118N-34	16	70368745777664x1 (1750ns)	1.49
80C115	40	39	4118N-35	16	14073749155328x1 (1800ns)	1.49
80C116	40	39	4118N-36	16	28147498310656x1 (1850ns)	1.49
80C117	40	39	4118N-37	16	56294996621312x1 (1900ns)	1.49
80C118	40	39	4118N-38	16	112589993242624x1 (1950ns)	1.49
80C119	40	39	4118N-39	16	225179986485248x1 (2000ns)	1.49
80C120	40	39	4118N-40	16	450359972970496x1 (2050ns)	1.49
80C121	40	39	4118N-41	16	900719945940992x1 (2100ns)	1.49
80C122	40	39	4118N-42	16	1801439891881984x1 (2150ns)	1.49
80C123	40	39	4118N-43	16	3602879783763968x1 (2200ns)	1.49
80C124	40	39	4118N-44	16	7205759567527936x1 (2250ns)	1.49
80C125	40	39	4118N-45	16	14411519130558688x1 (2300ns)	1.49
80C126	40	39	4118N-46	16	28823038261117376x1 (2350ns)	1.49
80C127	40	39	4118N-47	16	57646076522234752x1 (2400ns)	1.49
80C128	40	39	4118N-48	16	115292153044469504x1 (2450ns)	1.49
80C129	40	39	4118N-49	16	230584306088939008x1 (2500ns)	1.49
80C130	40	39	4118N-50	16	461168612177878016x1 (2550ns)	1.49
80C131	40	39	4118N-51	16	922337224355756032x1 (2600ns)	1.49
80C132	40	39	4118N-52	16	1844674488711520064x1 (2650ns)	1.49
80C133	40	39	4118N-53	16	3689348977423040128x1 (2700ns)	1.49
80C134	40	39	4118N-54	16	7378697954846080256x1 (2750ns)	1.49
80C135	40	39	4118N-55	16	14757395116972160512x1 (2800ns)	1.49
80C136	40	39	4118N-56	16	29514790233944321024x1 (2850ns)	1.49
80C137	40	39	4118N-57	16	59029580467888642048x1 (2900ns)	1.49
80C138	40	39	4118N-58	16	118059160935777284096x1 (2950ns)	1.49
80C139	40	39	4118N-59	16	236118321871554568192x1 (3000ns)	1.49
80C140	40	39	4118N-60	16	472236643743109136384x1 (3050ns)	1.49
80C141	40	39	4118N-61	16	944473287486218272768x1 (3100ns)	1.49
80C142	40	39	4118N-62	16	1888946554732576545536x1 (3150ns)	1.49
80C143	40	39	4118N-63	16	3777893109465153091072x1 (3200ns)	1.49
80C144	40	39	4118N-64	16	7555786218930306182144x1 (3250ns)	1.49
80C145	40	39	4118N-65	16	15111572437860613642288x1 (3300ns)	1.49
80C146	40	39	4118N-66	16	30223144875721227284576x1 (3350ns)	1.49
80C147	40	39	4118N-67	16	60446289751442454569152x1 (3400ns)	1.49
80C148	40	39	4118N-68	16	120892579502884891118304x1 (3450ns)	1.49
80C149	40	39	4118N-69	16	241785159005769782236608x1 (3500ns)	1.49
80C150	40	39	4118N-70	16	483570318011539564473216x1 (3550ns)	1.49
80C151	40	39	4118N-71	16	967140636023079128946432x1 (3600ns)	1.49
80C152	40	39	4118N-72	16	193428127204615825792864x1 (3650ns)	1.49
80C153	40	39	4118N-73	16	386856254409231651585728x1 (3700ns)	1.49
80C154	40	39	4118N-74	16		

Wall Transformers AC and DC Types

Part No.	Input	Output	Price
AC 250 (Picture)			
AC 500	117V/60Hz	12VAC 250mA	\$3.95
AC 1000	117V/60Hz	12VAC 500mA	\$4.95
AC2004	117V/60Hz	12VAC 2.5 amp	\$5.95
DC 800	120V/60Hz	8VDC 400mA	\$1.95
DC5812	120V/60Hz	8.5VDC 300mA	\$2.95
DC5480	117V/60Hz	9.5VDC 275mA	\$2.95
DC900	120V/60Hz	9VDC 500mA	\$3.95
DC1200	120V/60Hz	9.5VDC 500mA	\$2.95
DV9200	117V/60Hz	9VDC 200mA	\$3.95

PCB-3 Makes Circuit Assembly A Breeze!

Let's you work with both hands. Sturdy aluminum construction.

Clamp "3rd Hand" on edge of bench table or workboard. Insert circuit board, position components. Notice convenient working angle. Flip circuit board to flat position for soldering and clipping. Reverse procedure for double-sided boards.

PCB-3 \$13.95

Extension to hold PCB-3 2" from bench and 6" from front edge. PCB-X \$6.95

Mostek DC/DC Converter +5 VOLTS TO (regulated) 30V

Input: +5V. Output: -9V (regulated) @ 30mA. Printed circuit mounting. Specifications incl. DC10 \$2.95 ea. or 2/\$4.95

Jameco Digital Thermometer Kit

Dual sensors - switch control for indoor/outdoor or dual monitoring - can be extended to 500 feet. Continuous LED .8" ht. display. Range: -40°F to 199°F, -40°C to 100°C. Accuracy ±1° nominal. Calibrate for Fahrenheit/Celsius. Simulated walnut case. AC wall adapter included. Size: 6 1/2" x 3 1/2" x 1 1/2".

JE300 \$39.95

RADIO CONTROL CIRCUITS

Ideal to use for:

- Toys, hobby crafts, robots, trains
- Burglar alarms + IR data link
- Remote slide projector control
- Consumer remote data links
- Energy-saving, remotely switched lighting systems

A complete RF channel digital encoder and RF transmitter; low power, at frequency of 27MHz or 40MHz, a field strength of 10,000V/meter at 3 meters. 9V operation on chip RF oscillator/transmitter, on chip 4.8 regulator. Up to 80MHz carrier frequency operation.

LM1871N RC Encoder/Transmitter Chip \$1.95

A complete RF receiver/decoder, used at either 27MHz, 40MHz or 72MHz. It provides 4 independent channels when used with LM1871 (2 analog, 2 dig.) operates from four 1.5V cells. Crystal controlled.

LM1872N RC Receiver/Decoder Chip \$2.49

SRX1504 49.435MHz Crystal (LM1872N) \$3.95

SRX1505 49.890MHz Crystal (LM1871N) \$3.95

ATARI

ATARI PADDLES

JSP (2) \$4.95 pair

ATARI DRIVER

JSD (1) \$2.95 ea.

TV GAME SWITCH

Used on Atari. Cosmetically blemished. 100% functional.

TGS-1 \$2.95 ea.

BOOKS

NATIONAL SEMICONDUCTOR - INTERSIL - INTEL

30003	National Linear Data Book (1982) (1376 pages) LM, LF, ADC, DAC, LH Series	\$11.95
30008	National Memory Data Book (1980) (484 pages) RAMs, ROMs, PROMs, EPROMs Series	\$6.95
30009	Intersil Data Book (1983) (1356 pages) Complete line.	\$9.95
30010	National Audio/Radio Handbook (1980) (240 pages) Pre-Amps, AM, FM & FM Stereo, Power Amps	\$5.95
30011	National Linear Application Handbook (1980) (736 pages) Application Notes, Linear Briefs, etc.	\$15.95
30012	National PAL Data Book (1982) (176 pages) Application Notes, Linear Briefs, etc.	\$5.95
30013	Zilog Data Book (1983) (641 pages) Microprocessors and Support Chips	\$7.95
210630	Intel Memory Components Handbook (1983) (798 pages) Contents: Application Notes, Article Reprints, Data Sheets, and other design information on Intel's RAMs, EPROMs, EPROMs & Bubble Memories.	\$14.95
210844	Intel Microprocessor & Peripheral Handbook (1983) (1027 pages) Contains Data Sheets on all of Intel's Microprocessors and Peripherals.	\$14.95

Universal Computer Keyboard Enclosures

"OTE" Blank Desk-Top Enclosures are designed for easy modification. High strength epoxy molded and pieces in mottled brown finish. Sliding rear/bottom panel for service/component access. Top/Left panels .080" thick slum, sliding type 1200 finish (gold tint color) for best paint adhesion after modification. Vented top & bottom panels for cooling efficiency. Rigid construction provides unlimited applications. Assembly instructions included.

DTE-8	Panel Width 7.5"	\$24.95
DTE-11	Panel Width 10.13"	\$27.95
DTE-14	Panel Width 13.5"	\$29.95
DTE-20	Panel Width 19.25"	\$34.95

TIMEX Sinclair 1000

• Powerful - fully programmable 2K memory • Portable - 6 1/2" x 6 1/2" x 1 1/2" - 12 oz. • Expandable - Optional 16K RAM module • Single-key entry commands • Educational • Unique syntax-check report codes for error finding • Accurate to 9 1/2% decimal places for full range math and scientific functions • Graph drawing and animated display • Advanced 4-chip design combining power, portability and affordable price.

TS1000 \$69.95

ACCESSORIES FOR TIMEX Sinclair 1000 and ZX81

TIMEX Sinclair 1016 Expansion from 2K to 16K, size: 3" x 3" x 1.5" (5 oz) TS1016 \$49.95

TIMEX Sinclair 2040 32 column thermal printer (4 lbs) TS2040 \$99.95

Keyboard Mask for Your ZX81/1000* Computer

JES81 KEYBOARD MASK provides users of the ZX81/1000 series computer the individual feel of each keypad on the keyboard. The mask has a raised outline around each keypad allowing the user to feel and correctly position their fingers onto the keypad.

JES81 KEYBOARD MASK \$9.95 each

JES82 KEYBOARD Conversion Kit

JES82 KEYBOARD Conversion Kit \$89.95 ea. (WITH DTEAK CASE - AS PICTURED)

JES83 KEYBOARD Conversion Kit

JES83 KEYBOARD Conversion Kit \$59.95 ea. (WITHOUT DTEAK CASE)

CONTROL DATA KEYBOARDS

- ★ Parallel ASCII
- ★ SPST Switching
- ★ FTZ Shielded Base
- ★ N-Key Rollover
- ★ 128 Character ASCII
- ★ Non-Slip, Non-Glare Keycaps
- ★ CDC752 Terminal Keyboards
- ★ Attractive Case

These Control Data Keyboards consist of a base, cover, the keyboard assembly, and an interface cable. Color (case): Harvest gold and black. Color (keycaps): Black, blue, and red. Electrical requirements: +5V @ 600mA, -12V @ 50mA. Weight: 8 lbs. All units brand new in original boxes, specifications included.

80-Key Keyboard	
CA150C	\$69.95
84-Key Keyboard	
CA153A	\$69.95
95-Key Keyboard	
CA154A	\$79.95

Keytronics 90-Key Soft-Programmable Keyboard

WITH SECURITY KEYLOCK SWITCH

- RFI shielded
- Cursor controls
- Numeric keyboard
- 8-bit Parallel
- Capacitance keys
- 10 user-programmable keys
- Positive TTL Logic
- Size: 17" L x 8 1/4" W x 2 1/4" H

Made for Visual Technology, this keyboard features: a security keylock (includes two keys) to guard against unauthorized use; an 11-key numeric keypad; cursor control; and 10 user-programmable keys. Electrical requirements: +5VDC. Color (case): White. Color (keycaps): Black. Complete with case, keyboard assembly, 40-inch interface cable, and schematics. Weight: 7 lbs.

Part No. KB270 \$109.95 each

MICRO SWITCH 85-KEY KEYBOARD Word Processing Keyboard, 28 Pin Edge Card Connection. Supply Voltage +5VDC. Main Keyboard in QUERTY. Additional Key Pads for Cursor and word processing functions. Part No. 85SD18-1 \$29.95 each	HI-TEK 14-KEY NUMERIC KEYPAD SPST switching, Charcoal grey keycaps. Mounted on printed circuit board. Part No. K-14 \$9.95 each
ALPS 29-KEY CALCULATOR KEYBOARD Features one 8-position decimal select switch, one 3-position switch, and two 2-position switches, mechanical SPST switching, 22-pin edge card connection. Pin-out included. Part No. KB2970AD (Fits DTE-11 Enclosure) \$4.95 each	POWER SUPPLY +5VDC @ 1 AMP REGULATED Transaction Tech Input: +5VDC @ 1A (also +30VDC) reg. Input 115VAC 60Hz. 2-tone (black/brown) self-enclosed case. 3 in. x 3 in. black power cord. 8 1/2" W x 7 1/2" H x 2 1/2" D. Data sheet incl. Part No. PS51194S \$14.95 each
POWER SUPPLY +5VDC @ 3 AMP REGULATED Dalltron Input: 115VAC 47-440Hz. Output: 5VDC Adjustable @ 3 amp. 5VDC @ 2.5 amp. Adjustable current limit. Ripple & Noise: 1mV rms. 50mV p-p. 2 mounting ampers. UL recognized. Size: 4" W x 4 1/2" L x 2 1/2" H. Wt. 2 lbs. Data sheet included. Part No. QPS-1 \$29.95 each	POWER SUPPLY +5VDC @ 7.5 AMP, 12VDC @ 1.5 AMP SWITCHING Input: 115VAC 50-60Hz @ 3 amp/230VAC 50Hz @ 1.5 amp. Fan vol. 8 amp. Fan power cord. 11 1/2" W x 13 1/2" D x 3 1/2" H. Wt. 6 lbs. Part No. PS34VDS \$39.95 each
POWER SUPPLY 4-Channel Switching - Apple Compatible Microprocessor, mini-computer, terminal, medical equipment and process control applications. Input: 90-120VAC 47-440Hz. Output: +5VDC @ 5A, -5VDC @ 1A, +12VDC @ 1A, -12VDC @ 1A. Line reg. ±0.2%. Ripple: 30mV p-p. Load reg. ±1%. Overcurrent protection. Adj. SW main output: ±10%. 6 1/2" L x 1 7/8" W x 4-15/16" H. Wt. 1 1/2 lbs. Part No. FCS-604A \$69.95 each	

\$10.00 Minimum Order - U.S. Funds Only
California Residents Add 6 1/2% Sales Tax
Shipping - Add 5% plus \$1.50 Insurance
Send S.A.S.E. for Monthly Sales Flyer!

Spec Sheets - 30c each
Send \$1.00 Postage for your
FREE 1983 JAMECO CATALOG
Prices Subject to Change

Mail Order Electronics - Worldwide

Jameco ELECTRONICS

1355 SHOREWAY ROAD, BELMONT, CA 94002
7183 PHONE ORDERS WELCOME - (415) 592-8097 Telex: 176043

MasterCard VISA

2708, 2716, 2732 & 2764 EPROM Programmer

JE664 EPROM PROGRAMMER

8K TO 64K EPROMS - 24 AND 28 PIN PACKAGES
- PROGRAMS 2716'S IN 16 SECONDS -

- Programs, validates, and checks for properly erased EPROMs • Emulates PROMs or EPROMs • RS232C Computer Interface for editing/program loading • Loads data into RAM by keyboard • Changes data to RAM by keyboard • Loads RAM from an EPROM • Compares EPROMs for content differences • Copies EPROMs • Power Input: 115VAC, 60Hz, ±10% power consumption • Enclosure: Color-coordinated, light tan panels w/rotated mottled brown and beige • Size: 15-5/8" L x 8 1/2" W x 2 1/4" H • Wt.: 3 1/2 lbs.

JE664-A EPROM Programmer Assembled & Tested (Includes JM16A Module) \$995.00

JE665 - RS232C INTERFACE OPTION

The JE665 RS232C Interface Option implements computer access to the JE664's RAM. Sample software written in BASIC provided for TRS-80 Model I, Level II Computer. Baud rate: 9600. Word length: 8 bits - odd parity. Stop bits: 2. Option may be adapted to other computers.

JE664-ARS EPROM Prog. w/ JE665 Option Assembled and Tested (Includes JM16A Module) \$1195.00

EPROM JUMPER MODULES

The JE664 JUMPER MODULE (Personality Module) is a plug-in Module that pre-sets JE664 for proper programming pulses to the EPROM & configures EPROM socket connections for that particular EPROM.

Part No.	EPROM	EPROM MANUFACTURER	PRICE
JM08A	2708	AMD, Motorola, National, Intel, TI	\$14.95
JM16A	2716, TMS2516	Intel, Motorola, National, NEC, TI	\$14.95
JM16B	TMS2716	Motorola, TI (+5, -12, +12)	\$14.95
JM32A	TMS2532	Motorola, TI	\$14.95
JM32B	2732	AMD, Fujitsu, NEC, Hitachi, Intel	\$14.95
JM32C	2732A (21V)	Fujitsu, Intel	\$14.95
JM4A	MCM58764, MCM58L764	Motorola	\$14.95
JM4B	2764	Intel	\$14.95
JM4C	TMS2564	TI	\$14.95
JM4D	HM482764G-4	Hitachi (21V)	\$14.95

EXPAND YOUR MEMORY

TRS-80 to 16K, 32K, or 48K

**Model 1 = From 4K to 16K Requires (1) One Kit
Model 3 = From 4K to 48K Requires (3) Three Kits
Color = From 4K to 16K Requires (1) One Kit

**Model 1 equipped with Expansion Board up to 48K Two Kits Required - One Kit Required for each 16K of Expansion -

TRS-16K3 *200ns for Color & Model III \$12.95
TRS-16K4 *200ns for Model I \$10.95

TRS-80 Color 32K or 64K Conversion Kit

Kit comes complete with 8 each 4164-2 (200ns) 64K dynamic RAMs and conversion documentation. Converts TRS-80 color computers with D and E circuit boards, and all new color computers to 32K. Minor modifications of 32K memory will allow the use of all 64K of the dynamic RAM providing you have a FLEX DOS operating system.

TRS-64K2 \$54.95

IBM MEMORY EXPANSION KIT

SAVE HUNDREDS OF \$\$\$ BY UPGRADING MEMORY BOARDS YOURSELF!

Most of the popular memory boards allow you to add an additional 64K, 128K, 192K, or 256K. The IBM4K Kit will populate these boards in 64K byte increments. The kit is simple to install - just insert the nine 64K RAM chips in the provided sockets and set the two groups of switches. Directions are included.

IBM4K (Nine 200ns 64K RAMs) \$59.95

5 1/4" Mini-Floppy Disk Drive

FOR TRS-80 MODEL I (Industry Standard)
Features single or double density. Recording mode: FM single, MFM double density. Power: +5VDC (±0.2V) 1.6A max., +5VDC (±0.25V) 0.8A max. Unit as pic. at right (does not include power supply, cables). 30-pg. data book incl. Wt. 3 1/2 lbs. Size: 5 1/4" W x 8" D x 3 1/4" H. Part No. Limited Quantity! Price

FD200 \$179.95
Single-sided, 40 tracks, 250K bytes capacity

FD250 \$199.95
Double-sided, 35 tracks, 438K bytes capacity

8" FLOPPY DISK DRIVE

Shugart 801R compatible
Single-Sided
77 Tracks
400/800K Bytes Capacity
Factory
Industry Standard

The FDD100-8 8" Floppy Disk Drive (Industry Standard) features single or double density. Recording mode: FM single, MFM double density. Transfer rate: 250K bits/sec. single density; 500K bits/sec. double density. The FDD100-8 is designed to work with the single-sided soft sector IBM Diskette I, or sq. disk cartridge. Power: +5VDC @ 50-60Hz; +24VDC @ 1.7 amps max., +5VDC @ 1.2 amps max. Unit as pictured above (does not include case, power supply, or cables). Size: 8.55" W x 14" L x 4.5" H. Weighs 12 lbs. Incl. 90-pg. manual. Part No.

FDD100-8 \$169.95 ea.

UV-EPROM Eraser

8 Chips - 51 Minutes
1 Chip - 37 Minutes

Erases 2708, 2716, 2732, 2764, 2516, 2532, 2564. Erases up to 8 chips within 51 minutes (1 chip in 37 minutes). Maintains constant exposure distance of one inch. Special conductive foam liner eliminates static build-up. Built-in safety lock to prevent UV exposure. Compact - only 9.00" x 2.70" x 2.60". Complete with holding tray for 8 chips.

DE-4 UV-EPROM Eraser \$79.95
UVS-11EL Replacement Bulb \$16.95



FORMULA INTERNATIONAL INC.

12603 Crenshaw Blvd., Dept. B, Hawthorne, CA 90250

For information (213) 973-1921 • Orders Only (outside Calif.) (800) 672-8758



pinecom™

The Alternative! The Compatible! The Affordable! 64K Color Computer Kit!

Copyright Problem Free!



\$645⁰⁰ EACH

(please add 5% shipping and handling)
DEALERS INQUIRIES INVITED!

FEATURES:


- ★ Fully compatible with Apple® II+
- ★ Singleboard for easy assembly
- ★ Popular 6502 MPU for large amount of software
- ★ Game paddle connector on both sides of case
- ★ Upper/lower case
- ★ Built in 2-watt amplifier for realistic sound effect with volume control
- ★ 8 on board peripheral connectors for expansion
- ★ 14 key numeric key pad
- ★ 5-amp switching power supply
- ★ Auto repeat

Easy to assemble! All components are clearly silk-screened on the high quality double-sided mother board. All integrated circuits, IC sockets, peripheral connectors, keyboard, switching power supply and the professional high impact plastic case are included.

*Pinecom is a trade mark of Pineapple Computer Products (HK) Ltd.

5 1/4" DISC DRIVE FROM QUENTIN RESEARCH INC.

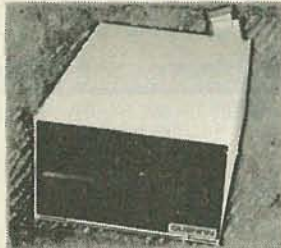100% Made in USA 100% Apple and Pincom Compatible
50% Faster Seeking Time Than Apple Disk II Drive!



- 1 Year Full Warranty
- 40 Tracks
- One of the Most Quiet Drives
- Color and Shape same as the Disk II Drive


Disk Drive **\$285.00**
Controller Card **\$ 75.00**
Controller Card with 13 Sector, 16 Sector Auto Select **\$ 85.00**

The APPLE II LOOKALIKE COMPUTER CASE

Made with high impact plastic.
Color and shape are compatible with the APPLE II

Special
\$99.95


Keyboard not included with this price!

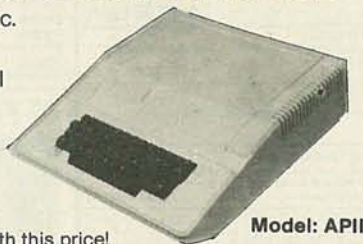

Model: APII

6502 CPU MOTHER BOARD

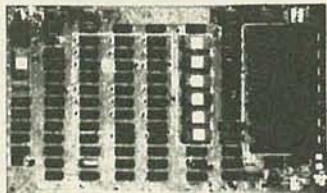- 48K on board RAM (4116)
- 12K on board ROM (2716)
- Upper/lower case
- Composite-video output
- Apple II alternative
- Size: 14 1/4" x 8 1/2"



P.C. Board Only **\$99.00 ea.**
Complete Component Pack (No ROMs) **\$175.00**

GUARANTEED TO WORK! BUILD IT IN 2 HOURS!

Big Savings On Peripheral Cards

Buy them in kit form.

All cards APPLE II and PINEAPPLE compatible.

80 column card kit	\$120.00	EPROM writer card assembled (For 2708,2716,2732,2764,2532)	\$89.50
Z80 CP/M card kit	\$110.00	Printer interface card kit (For Epson or Oki)	\$69.50
16K RAM card kit	\$49.50	New disk controller card kit (3.2, 3.3 auto select)	\$69.50
RS232 Interface card kit	\$95.00		
16K RAM card (cable-less) kit	\$59.50		

HEAVY DUTY SWITCHING POWER SUPPLY for Apple II, AP-II™ and Pinecom Computers

- +5V at 5.0 Amp
- +12V at 2.5 Amp
- 5V at 0.5 Amp
- 12V at 0.5 Amp



Model: THB-43H

Size and mounting holes are same as the ones used in the Apple II

\$145.00 ea.

APPLE II+ COMPATIBLE KEYBOARD

- LSI keyboard decoder
- Upper/lower case function
- Full ASCII code output
- N-key rollover function
- LED ON/OFF indicator



LKB-3600-N



Keyboard Case

Keyboard Only **\$99.00 EA.** Plastic Case **\$35.00 EA.**



MICRO-II CASE

Made with ABS Plastic
Same size as the Apple II, with Numeric
Key-Pad and Upper/Lower Case.



\$250.00 ea.

Keyboard Included

SEND ONE DOLLAR
FOR OUR DETAIL CATALOG

Inside California
Outside Calif. (incl. Mexico & Canada)
Overseas

Shipping & Handling Charges	
Under \$50.00 Purchase	Under \$50.00 Purchase
10%	5%
15%	10%
25%	20%

Minimum Order \$10.00/Calif. Residents add 6.5% Sales Tax. Phone Orders Accepted on VISA or MC ONLY. NO C.O.D.'s. Prices subject to change without notice.



STORE HOURS
MON-FRI-10-7
SAT-10-6

*Apple and Apple II are the trademark of APPLE COMPUTERS, INC.

CIRCLE 76 ON FREE INFORMATION CARD

QUALITY
SERVICE
AVAILABILITY



ACTIVE, YOUR
NUMBER ONE
CHOICE

Active Electronics

WE ARE THE LARGEST BECAUSE WE ARE THE BEST.
Over \$40 million in stock. The world's most complete hobbyist inventory.

Active Electronics is your one stop source for the widest variety of top quality semiconductors, microprocessors, memories, microcomputer systems, peripherals and electronic components.

NEW — 1983 IC MASTER

The FIRST and ONLY complete guide to IC's, Microcomputer Boards and Development Systems. Deluxe 2-volume set 3300 pages Regular Price: \$95.00



Call or write for our FREE comprehensive catalogue. If you work with electronics you shouldn't be without it!

ACTIVE'S PRICE
ONLY \$79.95

Circle No. 3 on free information card or write:
P.O. Box 8000, Westboro, Mass. 01581
CALL TOLL FREE: 1-800-343-0874
MASS. customers call (617) 366-0500

CIRCLE 3 ON FREE INFORMATION CARD

POPULAR CHIPS


LM 301	.39
LM 380	1.25
LM 386	.79
NE 564	2.50
LM 565	.89
MC 1330	1.10
MC 1350	1.00
MC 1358	1.10
MC 1458	.49
MC 1496	1.50
LM 1889	1.95
7808	.75
7812	.75
7815	.75
7818	.75
MV 2109	.69
2N2222A	.30
MC1349	1.39



MITSUMI
UES A55F
VARACTOR TUNER
CHAN. 14-83
300 ohm INPUT \$17.95

DELUXE PARTS ASSORTMENTS

#1 Resistors & Trimpots 68 1/4 watt, 5% resistors & 5 PT-15 10K trimpots. 1 each - 51, 75, 100, 470, 1.5K, 3.6K, 51K, 470K, 13-1.2K, 2-220, 3-100K, 6-330, 6-12K, 7-910, 9-3.3K, & 14-4.7K. \$5.25 each	#4 Coll & Chokes 1 each of 15, 33, and 100 (uh) micro henries chokes. 1-variable RF coll (same as #49A537MPC) \$3.25 each
#2 Capacitor "A" Monolythics - 1-560pf, 7-.1 mfd, & 1-.22 mfd, Silver Micas - 2-10pf, & 1 each of 43pf, 110pf, 560pf, 1200pf, 3300pf or 3300pf. \$5.45 each	#5 IC's, Sockets, & Semi's 1 each of: NE564, LM565, MC1330, MC1350, MC1496, LM1889, 7812, 7818, 2N2222A, MV2109, heat sink 2-MC1458, 4-1N4002, 4-8 pin, 2-14 pin, 1-18, & 1-18 pin socket. \$13.25 each
#3 Capacitor "B" Mylars 4-.001, 2-.047, 29-.01. Radial lytics 3-10 mfd 16V, 1-1000 mfd 50V, 1-2200 mfd 35V. Disc Caps 1 each of 5, 12, 27, 36, 110, 330pf, 2-120pf, 3-39pf, 3-220pf, and 1 Vari Cap 5-35pf. \$7.50 each	#6 Misc. Hardware LED & holder, fuse & holder, line cord, grommet, SPST switch, DPDT switch, 2-F61 conn. & lugs, knob, 4-spacers, 6-screws & nuts, 2-RG-174, matching transformer w/nut. \$5.95 each

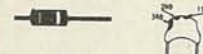

CHOKES

.33 uh	33 uh
.47 uh	100 uh
15 uh	10 mh
18 uh	69c each

VARI CAPS

10 - 60 pf	69c each
30 - 90 pf	69c each

UHF AMP KIT
25 db gain stripline PC board using (2) BFR-90's \$9.95 power supply for above \$3.49

METAL BOX—PRE-DRILLED
DIM: 10"W x 4 1/2" x 3" High
HOLES: (4) 1/8" in back, (1) 1/8" in front, (2) 1/4" in front, 6 #6 on bottom
PAINTED \$10.95 ea., 10/\$99.50 25/\$223.75

NETWORK SALES, INC.
2343 W. BELMONT AVE.
CHICAGO, IL. 60618
312-248-3202

TERMS: Visa, M.C., Check, Money Order or COD (add 3.00). Min. Order \$10.00. Add \$2.50 S&H for USA Ill. add 7% Tax. MAIL ORDER ONLY. Phone Orders Welcome. WRITE FOR OUR MONTHLY UN-ADVERTISED SPECIALS

CIRCLE 90 ON FREE INFORMATION CARD

CIRCUIT SPECIALISTS

YOUR SEMICONDUCTOR SUPERMARKET

74LS00 SALE

74LS00	.20	74LS123	.50	74LS249	1.25
74LS01	.24	74LS125A	.50	74LS251	.60
74LS02	.24	74LS126A	.50	74LS253	.60
74LS03	.24	74LS132	.80	74LS256	1.50
74LS05	.24	74LS133	.80	74LS257A	.60
74LS08	.24	74LS136	.40	74LS258A	.60
74LS09	.24	74LS137	1.00	74LS259	1.25
74LS10	.24	74LS138	.80	74LS260	.55
74LS11	.24	74LS139	.80	74LS266	.55
74LS12	.24	74LS145	1.30	74LS273	1.25
74LS13	.45	74LS147	1.65	74LS279	.55
74LS14	.60	74LS148	1.65	74LS280	2.25
74LS15	.32	74LS151	.55	74LS283	.90
74LS20	.29	74LS153	.55	74LS290	.80
74LS21	.32	74LS155	.85	74LS293	.90
74LS22	.32	74LS156	.80	74LS295A	.95
74LS26	.32	74LS157	.80	74LS298	.90
74LS27	.32	74LS158	.80	74LS299	2.60
74LS28	.32	74LS160A	.85	74LS322A	4.60
74LS30	.32	74LS161	.85	74LS323	4.60
74LS32	.32	74LS162	.80	74LS348	1.75
74LS33	.32	74LS163A	.80	74LS352	1.25
74LS36	.40	74LS164	.80	74LS353	1.25
74LS40	.35	74LS165	1.25	74LS365A	.55
74LS42	.60	74LS166	1.25	74LS366A	.55
74LS47	.89	74LS168	1.25	74LS367A	.55
74LS48	1.00	74LS169	1.25	74LS368A	.55
74LS49	1.00	74LS170	1.75	74LS373	1.35
74LS51	.29	74LS173	.80	74LS374	1.25
74LS54	.29	74LS174	.55	74LS375	.55
74LS55	.42	74LS175	.60	74LS377	1.25
74LS73A	.42	74LS181	2.25	74LS378	1.25
74LS74A	.42	74LS182	1.25	74LS379	1.25
74LS75	.45	74LS183	2.75	74LS385	3.50
74LS76A	.45	74LS190	.85	74LS386	.55
74LS77	.70	74LS191	.85	74LS390	1.25
74LS78A	.45	74LS192	.85	74LS393	1.25
74LS83A	.75	74LS193	.85	74LS395	1.25
74LS86	.45	74LS194A	.80	74LS398	2.25
74LS90	.90	74LS195A	.80	74LS399	1.25
74LS91	1.10	74LS196	1.00	74LS490	2.10
74LS92	.55	74LS197	1.00	74LS540	2.10
74LS93	.55	74LS221	1.25	74LS541	2.10
74LS95B	.65	74LS240	1.25	74LS568	3.99
74LS107A	.45	74LS242	1.25	74LS569	3.99
74LS109A	.45	74LS243	1.25	74LS620	2.00
74LS112A	.45	74LS244	1.25	74LS621	2.00
74LS113A	.45	74LS245	1.75	74LS622	2.00
74LS114A	.60	74LS247	1.25	74LS623	2.00
74LS122	.80	74LS248	1.25	74LS640	2.00

7400

7400	.20	7475	.50
7401	.29	7476	.38
7402	.29	7485	1.10
7403	.29	7486	.35
7404	.31	7489	2.40
7405	.32	7490	.52
7406	.38	7492	.52
7408	.31	7493	.52
7410	.30	7495	.67
7411	.31	7496	.73
7413	.46	74107	.35
7414	.59	74121	.40
7417	.32	74123	.58
7420	.29	74125	.52
7425	.31	74145	.75
7427	.32	74147	1.67
7430	.30	74151	.75
7432	.31	74153	.75
7437	.31	74154	1.17
7438	.31	74157	.75
7440	.29	74164	1.05
7441	1.00	74165	1.05
7442	.60	74174	1.00
7446	.83	74175	.83
7447	.83	74176	.80
7448	.83	74177	.80
7450	.29	74190	1.08
7472	.35	74192	.99
7473	.35	74193	.99
7474	.35	74196	.80

VOLT-REGS

7805	.80	LM317T	1.00
7806	.80	LM317K	3.75
7808	.80	LM323K	6.95
7812	.80	LM350T	3.25
7815	.80	LM350K	5.50
7818	.80	LM338K	7.60
7824	.80	LM337T	1.90
7905	1.30	78L05	.40
7906	1.30	78L12	.40
7908	1.30	78L15	.40
7912	1.30	79L05	.80
7915	1.30	79L12	.80
7918	1.30	79L15	.80
7924	1.30	78H05KC	9.25
		78H12KC	9.25

LINEAR IC'S

LM301AN	.48	LM3900	.75	MC1489P	1.10
LM307N	.56	LM3909	1.00	MC1496P	1.48
LM308N	.71	LM3911	1.50	MC1723P	.62
LM310N	2.40	LF347	2.35	MC1741CP1	.56
LM311N	.69	LF351	.60	MC3301	.90
LM318N	2.50	LF353	.99	MC3302	.80
LM319N	2.40	LF357	1.10	MC3401	.90
LM324N	.71	NE555	.42	MC3403P	1.30
LM325N	3.30	MC1306P	1.10	MC1648P	3.80
LM326N	3.30	MC1310	4.29	MC1658P	4.50
LM556N	.93	MC1330A1P	1.50	MC4024P	4.49
LM339N	.69	MC1349P	1.17	MC4044P	4.49
LM383T	2.30	MC1350P	.98	ICM7208	15.95
LM377N	2.40	MC1351P	1.70	ICM7207A	6.00
LM378N	3.15	MC1357P	1.49	ICM7217A	9.95
LM379N	4.60	MC1358P	1.30	ICM7205	12.95
LM380N	.90	MC1372P	4.42	ICM7045	15.50
LM381N	2.25	MC1373P	3.54	ICL8038	3.40
LM381AN	3.60	MC1403U	2.71	ICM7555	1.20
LM384AN	2.00	MC1405L	9.70	MWA110	7.45
LM386N	.99	MC1413P	1.20	MWA120	7.80
LM565N	1.35	MC1374P	2.61	MWA130	8.25
LM566N	2.30	MC1376P	2.08	MWA310	8.25
LM567N	1.35	MC1458CP1	.77	MWA320	8.65
LM1889	3.20	MC1488P	1.10	ZN414	2.00

CMOS

CD4001	.30	CD4046	1.50	MC14000	.40	MC14023	1.22
CD4007	.32	CD4047	1.40	MC14001	.40	MC14024	1.06
CD4010	.55	CD4049	.45	MC14002	.40	MC14024	1.47
CD4011	.32	CD4050	.45	MC14006	1.42	MC14027	.72
CD4013	.45	CD4051	1.00	MC14007	.40	MC14028	1.02
CD4016	.50	CD4066	.65	MC14008	1.25	MC14032	1.93
CD4017	1.00	CD4069	.32	MC14012	.40	MC14034	3.50
CD4020	1.17	CD4070	.45	MC14013	.72	MC14035	1.86
CD4023	.32	CD4071	.32	MC14014	1.25	MC14038	2.19
CD4024	.83	CD4081	.32	MC14015	1.47	MC14040	1.47
CD4025	.32	CD4093	.60	MC14016	.72	MC14042	1.06
CD4027	.55	CD4510	1.17	MC14017	1.25	MC14043	.99
CD4029	1.42	CD4511	2.20	MC14018	1.15	MC14044	.99
CD4040	1.17	CD4515	2.80	MC14020	1.47	MC14046	1.57
CD4044	.80	CD4518	1.17	MC14021	1.25	MC14049	.72

MOST MOTOROLA CMOS IN STOCK

CIRCUIT SPECIALISTS INC.
BOX 3047, SCOTTSDALE, AZ 85257
(602) 966-0764

INCLUDE \$1.25 SHIPPING


CIRCLE 44 ON FREE INFORMATION CARD

"The Deluxe II"

Is The Ultimate In UHF Sine Wave Converter Technology

PC BOARD & PLANS \$20.00

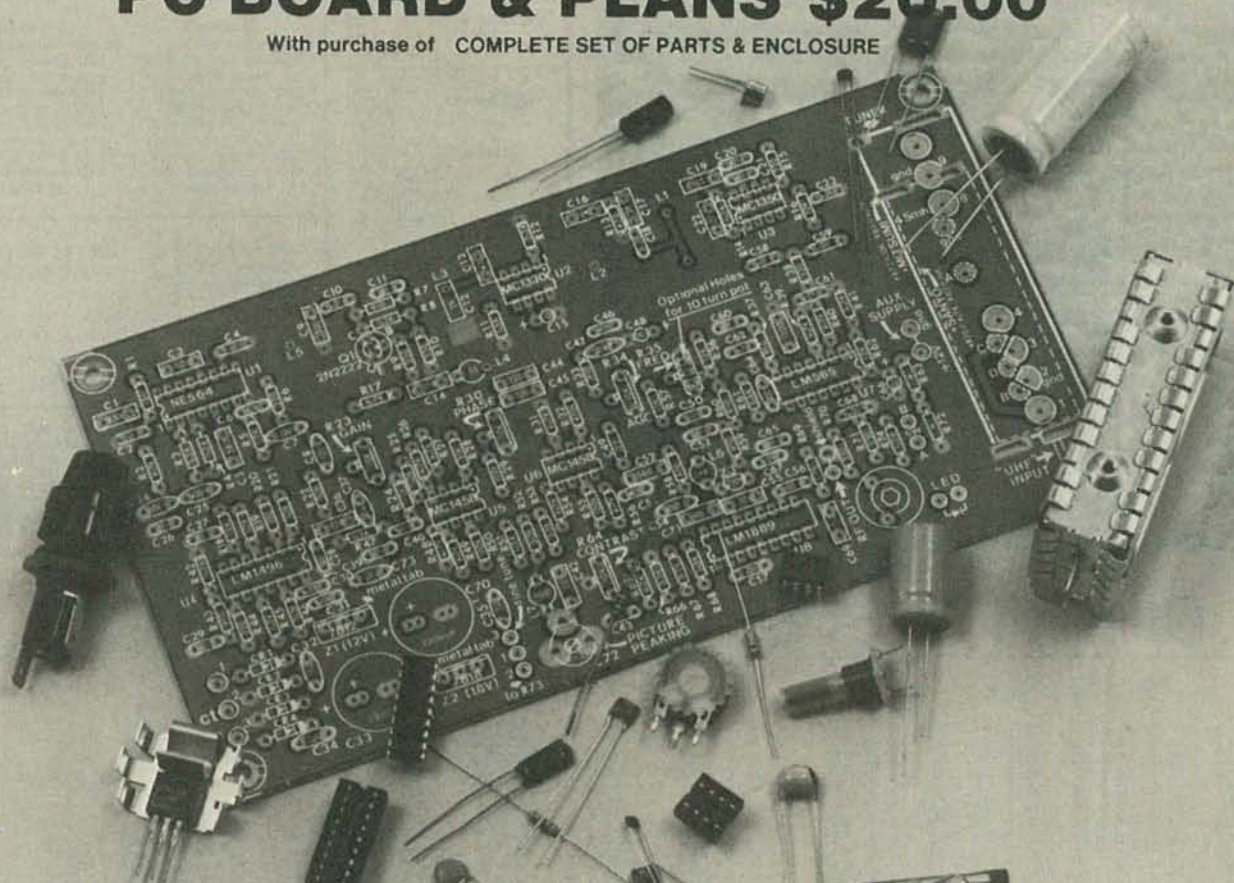With purchase of COMPLETE SET OF PARTS & ENCLOSURE



The latest state of the art electronics combined with the excellence in printed circuit manufacturing creates this high performance UHF Sine Wave Converter kit that outperforms the imitations by a long shot. Engineered for reliable stability and outstanding reception clarity, uninterrupted modulated audio and fully illustrated instructions with the amateur in mind.

TOLL FREE

BETA ELECTRONICS, 1700 E. DESERT INN ROAD, SUITE 222, LAS VEGAS, NEVADA, 89109 **1-800-782-2701**

QTY	DESCRIPTION OF ITEM	COST EACH	SHIPPING EACH	TOTAL
	PC BOARD, PLANS, PARTS & ENCLOSURE	\$152.99	\$4.95	
	PARTS & ENCLOSURE ONLY	\$132.99	\$4.95	
	PC BOARD & PLANS ONLY	\$30.00	\$1.50	
GRAND TOTAL				\$

PLEASE PRINT CLEARLY

SEND THIS ORDER FORM

NAME _____

ADDRESS _____

CITY/STATE/ZIP _____

VISA MST. CARD CARD NO. _____

ORDER DATE _____

EXP. DATE _____

QUANTITY DISCOUNTS AVAILABLE

MO. DAY YR.

FOR IMMEDIATE DELIVERY MONEY ORDERS OR CERTIFIED CHECKS PREFERRED PERSONAL CHECKS ALLOW 4 WEEKS FOR DELIVERY

DoKay Computer Products, Inc.

VISIT OUR RETAIL STORE

3250 KELLER STREET, #9 • SANTA CLARA, CA 95050

8000			
8035	4.95	8251	4.39
8039	5.95	8253	6.89
8080A	3.89	8253-5	7.89
8085A	5.89	8255	4.39
8086	24.95	8255-5	5.19
8088	34.95	8257	7.89
8155	7.75	8259	6.85
8156	8.75	8272	39.00
8185	29.00	8275	29.00
8202	27.95	8279	8.89
8205	3.45	8279-5	9.89
8212	1.79	8282	6.49
8214	3.75	8283	6.49
8216	1.69	8284	5.49
8224	2.19	8286	6.49
8226	1.79	8287	6.49
8228	3.34	8288	24.95
8237	19.00	8289	39.00
8238	4.39	8741	34.95
8243	4.39	8748	34.95
8250	10.49	8755	29.95

16K APPLE RAM CARD
 Upgrade your 48K Apple II to full 64K
BARE BOARD 14.00
ASSEMBLED & TESTED 42.50

EPROM ERASERS
 HOLDS 15 EPROMS
 ERASES IN 20 MINUTES
59.95

CONNECTORS

RS232 Male	3.00
RS232 Female	3.50
RS232 Female RA	4.95
RS232 Hood	1.20

6500 1 MHz	
6502	5.25
6504	6.85
6505	7.60
6507	9.85
6520	3.95
6522	4.95
6532	5.95
6545	16.95
6551	10.95

UPGRADE YOUR APPLE or TRS-80 4116 200ns 8/10.00

Z80 4.0 MHz
 Z80A-CPU 4.90
 Z80A-PIO 4.90
 Z80A-CTC 4.90
 Call for Complete List

MICROPROCESSOR REAL-TIME CLOCK
 MSM 5832 6.90

WE WILL BEAT ANY COMPETITOR'S PRICES!
 Call before you buy

CRYSTALS			
32.768 KHz	1.90	6.144	2.69
1.00 Hz	4.50	6.5536	2.69
1.8432	4.50	8.0	2.69
2.0	3.90	10.0	2.69
2.097152	3.90	12.0	2.69
2.4576	2.69	14.31818	2.69
3.2768	2.69	15.0	2.69
3.579545	2.69	16.0	2.69
4.0	2.69	17.430	2.69
5.0	2.69	18.0	2.69
5.0688	2.69	18.432	2.69
5.185	2.69	20.0	2.69
5.7143	2.69	22.1184	2.69
6.0	2.69		

74LS00 SERIES

74LS00	.23	74LS123	.49	74LS253	.58
74LS01	.23	74LS124	1.24	74LS257	.58
74LS02	.23	74LS125	.44	74LS258	.58
74LS03	.23	74LS126	.44	74LS259	1.19
74LS04	.23	74LS132	.54	74LS260	.58
74LS05	.23	74LS136	.89	74LS266	.58
74LS08	.23	74LS137	.49	74LS273	1.48
74LS10	.23	74LS138	.49	74LS275	3.20
74LS11	.25	74LS139	.49	74LS279	.48
74LS12	.25	74LS145	1.19	74LS280	1.79
74LS13	.39	74LS147	2.39	74LS283	.74
74LS14	.39	74LS148	1.29	74LS290	.68
74LS15	.29	74LS151	.39	74LS293	.78
74LS20	.23	74LS153	.39	74LS296	.98
74LS21	.23	74LS154	1.89	74LS298	.88
74LS22	.23	74LS155	.59	74LS324	1.74
74LS26	.29	74LS156	.69	74LS352	1.28
74LS27	.23	74LS157	.44	74LS353	1.28
74LS28	.29	74LS158	.49	74LS363	1.34
74LS30	.23	74LS160	.68	74LS364	1.89
74LS32	.25	74LS161	.64	74LS365	.48
74LS33	.49	74LS162	.68	74LS366	.48
74LS37	.29	74LS163	.64	74LS367	.44
74LS38	.29	74LS164	.68	74LS368	.44
74LS40	.23	74LS165	.79	74LS373	.98
74LS42	.43	74LS166	1.69	74LS374	.98
74LS47	.49	74LS168	1.69	74LS377	1.24
74LS48	.74	74LS169	1.74	74LS378	1.15
74LS49	.74	74LS170	1.45	74LS379	1.34
74LS51	.23	74LS173	.68	74LS385	1.89
74LS54	.23	74LS174	.44	74LS386	.44
74LS55	.28	74LS175	.39	74LS390	1.15
74LS63	1.19	74LS181	1.89	74LS393	1.15
74LS73	.34	74LS189	8.79	74LS395	1.15
74LS74	.34	74LS190	.79	74LS399	1.48
74LS75	.34	74LS191	.79	74LS424	.37
74LS76	.34	74LS192	.64	74LS447	.37
74LS78	.45	74LS193	.64	74LS490	1.94
74LS83	.59	74LS194	.68	74LS668	1.69
74LS85	.65	74LS195	.68	74LS669	1.89
74LS86	.35	74LS196	.78	74LS670	1.48
74LS90	.35	74LS197	.78	74LS674	9.45
74LS91	.79	74LS221	.74	74LS682	2.99
74LS92	.54	74LS240	.89	74LS683	2.99
74LS93	.54	74LS251	.89	74LS684	2.99
74LS95	.74	74LS242	.98	74LS685	2.99
74LS96	.69	74LS243	.98	74LS688	2.39
74LS107	.35	74LS244	.79	74LS689	2.99
74LS109	.35	74LS245	1.48		
74LS112	.35	74LS247	.74	81LS95	1.48
74LS113	.35	74LS248	.89	81LS96	1.48
74LS114	.35	74LS249	.89	81LS97	1.48
74LS122	.39	74LS251	.58	81LS98	1.48

DISC CONTROLLERS

1771	15.95
1791	27.95
1793	29.95
1795	49.95
1797	49.95
6843	32.95
8272	39.00
UPD765	34.95
1691	17.95

INTERFACE

8T26	1.65
8T28	1.95
8T95	.95
8T96	.95
8T97	.95
8T98	.95
DM8131	2.90
DP8304	2.25
DS8835	1.89
DS8836	.99

IC SOCKETS

ST	W/W
8 PIN	.10 .49
14 PIN	.12 .50
16 PIN	.15 .57
18 PIN	.20 .85
20 PIN	.25 .99
22 PIN	.25 1.30
24 PIN	.25 1.40
28 PIN	.35 1.50
40 PIN	.40 1.80

ST = Solder tail
W/W = Wirewrap

ORDER TOLL FREE

(800) 538-8800
(800) 848-8008

(CALIFORNIA RESIDENTS)
 ALL MERCHANDISE IS 100% GUARANTEED

APPLE SUPER COOLING FANS
49.95
 WITH SURG PROTECH
69.95

APPLE PADDLES
9.95

APPLE* II COMPATIBLE DISK DRIVE
225.95
CONTROLLER CARD
79.95

LINEAR

LM301	.32	LM741	.29
LM308	.75	LM747	.75
LM309K	1.25	LM748	.49
LM311	.64	LM1310	2.45
M317T	1.65	MC1330	1.69
LM317K	1.70	MC1350	1.25
LM318	1.49	MC1358	1.69
LM323K	3.75	LM1414	1.49
LM324	.59	LM1458	.55
LM337K	3.90	LM1488	.65
LM339	.79	LM1489	.65
LM377	2.25	LM1800	2.45
LM380	1.25	LM1889	2.45
LM386	1.00	LM3900	.59
LM555	.38	LM3909	.95
LM556	.65	LM3914	3.70
LM555	.95	LM3915	3.70
LM566	1.45	LM3916	3.70
LM567	.99	75451	.35
LM723	.49	75452	.35
LM733	.95	75453	.35

DoKay Computer Products, Inc.
 3250 Keller Street, #9
 Santa Clara, CA 95050
 (800) 538-8800
 Calif. Residents (800) 848-8008

STORE HOURS:
 MON-FRI 8:30 A.M.-5:30 P.M.
 SAT 10:00 A.M.-3:00 P.M.



TERMS: For shipping include \$2.00 for UPS Ground. \$3.00 for UPS Blue Label Air. \$10.00 minimum order. Bay Area residents add 6 1/2% Sales Tax. California residents add 6% Sales Tax. We reserve the right to limit quantities and substitute manufacturer. Prices subject to change without notice. Send SASE for complete list.

• Minimum Order \$9.00
• Please include \$1.50 for shipping (UPS)
• We accept VISA and MASTERCHARGE
• EXTRA FAST SERVICE

P.O. BOX 27038, DENVER, CO. 80227
PHONE ORDERS: 303-781-5750

120VAC VARIABLE STROBE LIGHT KIT

Complete variable rate strobe light kit produces brilliant flashes of light. Operates from standard 120VAC. Reliable design—thousands of these are in use throughout the world. Overall size of completed board: 3"L x 2"W x 3"H.

C3071 \$9.99



3VDC ELECTRONIC WARNING FLASHER KIT

This portable battery operated device continuously emits bursts of intense light at a fixed repetition rate. Can be seen for great distances making it a great safety device. Features xenon flashtube. Operates on 3VDC (two 1.5V Batteries). Size of board: 2 1/2"L x 2"W.


C3207 \$7.95



FASCINATION STAR KIT

Produces an "exploding star" visual effect using 25 LEDs and IC circuitry. The center LED lights first then the next group of LEDs light and then another set of lights until the outer edge of the star lights up. The process then reverses itself. Operates from 9V battery.


C4432 \$10.95

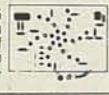

SEQUENTIAL LED FLASHER KIT

This kit combines IC circuitry and 10 jumbo red LEDs to produce a unique visual display. LEDs continuously light sequentially from right to left. Easy to build kit. Operates from 9V battery. Size of board: 5.25" x 1.5".

C4431 \$6.75

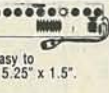

MICRO-MINIATURE SPEAKER

Only 3/16" dia. mounted on a 1" square PC board.

C4832 \$1.49 ea.



SOLID CARBIDE PC DRILL BIT

#65 .035 Standard size for PC boards.

C4800 \$1.49 ea.
10 for \$12.00



KESTER PC TYPE SOLDER

6 foot coil of ultra thin diameter low melting temperature 60/40 rosin core.

C4456



\$1.00

Kits!!!

We offer over 70 complete electronic kits. Send for our free catalog.


CIRCLE 34 ON FREE INFORMATION CARD

FINEST QUALITY
Government Approved QQ-S-571e
SOLDER

SPECIAL FOR THE MONTH

Good until June 30, 1983

SN 60/40 Rosin Core (RA)

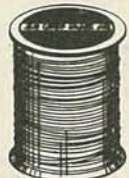

One lb. Reels
16 swg. (.064) \$8.50
18 swg. (.048) \$8.95
19 swg. (.040) \$9.50
21 swg. (.032) \$10.50
1/2 lb. Reels
22 swg. (.028) \$6.95
24 swg. (.022) \$8.95

Plus FREE Desoldering Wick
with each pound of solder

FREE Freight On All Orders Over \$25

Under \$25 add \$2.50 per order. Minimum order \$10

■ Check ■ Money Order ■ Master Charge ■ Visa

N.Y. State residents add appropriate sales tax.
To place your order call:
TOLL FREE 800-645-4808

In NYS (516) 334-2660 No COD's accepted

SolderCraft™
P.O. Box 668 Jericho, N.Y. 11753

CIRCLE 69 ON FREE INFORMATION CARD

FUJITECH AUDIO KITS

LATEST AUDIO TECHNOLOGY FROM JAPAN

Model A501 Power Amp

- Pure Class A 25W + 25W
- Switchable to Class AB 100W + 100W
- Switchable to Bridge Class A 100W mono
- Switchable to Bridge Class AB 300W mono
- Frequency Response 5-200KHz (-1dB)
- Signal-to-Noise Ratio 120dB
- Non-magnetic Chassis
- "Out-board" comprehensive protection circuitry
- DC circuitry with limited use of NFB
- High Efficiency Fluid Convection Cooling
- THD under 0.007%

KIT ONLY \$299.00



\$299.00

Model A502 DC Stereo Control Center

- Direct DC coupling from Input to Output
- DC servo circuitry
- Cascade FET input in all stages
- Separate Moving Coil RIAA amplifier
- Distortion below 0.005% (3V)
- Max Output 15V
- Frequency Response 20Hz-20KHz ±0.2 dB
- Maximum Phono Input
MC = 16mv RMS (1KHz)
MM = 270mv RMS (1KHz)
- Built-in Headphone amplifier
- Relay Output Muting

KIT ONLY \$349.00




\$349.00

Model A1033 Integrated Tube Amplifier

- Latest Japanese Design
- Distortionless Output Transformer using special winding techniques
- Most circuitry on PCB for easy assembly and humfree performance
- Output 30W x 2 Ultra Linear (Switchable to Triode)
15W x 2 Triode Output (near class A performance)
- THD under 0.4%
- Frequency Response 30~30,000 Hz (-1dB)
- Separate Pre-Out and Main-in

KIT ONLY \$499.00

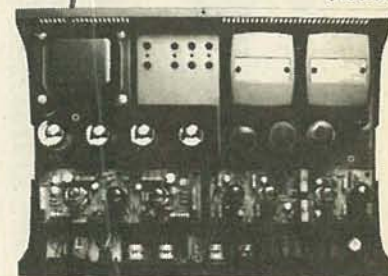

\$499.00

Send \$5.00 for each assembly manual, refundable with order.

Monarchy Engineering, Inc.
380 Swift Avenue, Unit 21
South San Francisco, CA 94080

Visa or Mastercharge acceptable.

Graymark Electronic Kits

Quality Products for 18 Years



Digital Dice

Roll-em electronically. Handy, portable set of electronic dice for your favorite games. 14 LEDs for realistic dice count, Battery operated. PCB, instructions, and all parts included.

Order Model 146F

Only \$15.90 each



Variable Strobe Light



Great for parties and photography. Variable flash rate of long life xenon tube assures hours of fun. AC operated. Comes complete with parts, PCB, and instructions.

Order Model 104F

Only \$14.70 each

5 Volt Power Supply



Perfect for digital circuits. Provides 1.5 amps at 5V under full load. IC voltage regulator. Ripple less than 0.5%. AC operated. Includes all necessary parts, PCB, and instructions.

Order Model 135F

Only \$18.20 each

Warbling Siren



Two-tone oscillating siren for automobile or other 12V system. Loud, penetrating sound driven by 2 ICs. Parts, PCB, and instructions are all included.

Order Model 124F

Only \$8.60 each

1-IC Radio



Private earphone listening to your favorite stations. AM broadcast band with high selectivity. No alignment necessary. Battery operated. Comes complete with parts, PCB, and instructions.

Order Model 141F

Only \$12.00 each



MC & VISA orders only call Toll Free

800-854-7393

(In CA 714-540-5480)

Send \$1.00 for Catalog [over 60 Kits]

(Refundable with 1st Order)

Graymark

Box 17359 • Irvine, CA 92713

SATISFACTION GUARANTEED

(602) 971-0990 (602) 971 0996

ARIZONA ELECTRONIC

SURPLUS
Wholesale - Retail - Surplus
Electronic Parts

12627 N. Cave Creek Rd. • Phoenix, AZ 85022

The Most Unbelievable Electrolytic Sale In The USA!

AXIAL		RADIAL	
33/6.3	12/1.00	1000/10	12/1.00
220/6.3	20/1.00*	10/16	30/1.00*
470/6.3	10/1.00	47/16	30/1.00*
220/10	15/1.00	220/16	25/1.00*
47/35	12/1.00	470/16	20/1.00*
220/35	10/1.00	47/25	20/1.00*
15/50	20/1.00*	47/100	5/1.00
22/50	20/1.00*	100/100	4/1.00
47/50	20/1.00*	4.7/160	10/1.00
150/50	8/1.00	10/160	10/1.00
220/50	8/1.00	22/250	5/1.00
10/75	12/1.00	BI-POLAR	
47/100	5/1.00*	4/50	10/1.00
1500/100	2/1.00*	10/50	10/1.00
2.2/150	12/1.00	4.7/75	4/1.00
3.3/150	12/1.00	10/75	4/1.00
47/200	5/1.00	Carbide Drill Bits *1.00 ea.	

* Yes All Prices Are Correct! • \$10.00 Minimum Order on All Above Capacitors • Some Quantity Pricing Available •

MORE \$1.00 SPECIALS

1N4001	15/1.00	Horz P.C. Trimpots, 250Ω
2N3905	5/1.00	500Ω, 5kΩ, 10Ω
2SC828	5/1.00	MC3420P
2SC644	5/1.00	SN75150
MINI D.P.D.T. Slide	4/1.00	Transformer
D.P.D.T. Rocker Sw		12 V.C.T. 250 MA
4A. 120 VAC	3/1.00	7805
1N4152	25/1.00	7812
Similar to 1N914		1N5239
4 Pos DIP switch	3/1.00	9 V. ZENER
LED's	8/1.00	

12V 6 A.H. Re-chargeable
GEL CELL BATTERY
\$9.95



NOT A KIT

Regulated Supply 5V, 2A
w/Transformer & 4" x 2.3" Heat Sink
\$5.50 ea. or 2/\$10.00

1 1/2 WATT AMPLIFIER
w/DC Bridge

\$2.75 ea. or 2/\$5

Contains: Volume Control, (1) LM 386N, (1) NPN Pre-amp, (4) 4001 Diodes, (2) Coupling Caps
100% Functional! NOT A KIT

LIMITED QUANTITY!

\$3.29 ea. or 2/\$6

4 Scales

- (1) R.F. Power 0-6
 - (2) SWR 1-10
 - (3) Modulation 0-100%
 - (4) Signal Strength 1-40
- Ext. Shunt 2.3" x 2.3"

ITEMS MC, VISA, COD VIA UPS
(Plus Shipping/Handling)



CIRCLE 89 ON FREE INFORMATION CARD

MICROWAVE TRANSISTORS

42¢ ea.

M 2369

- f_T 4.5 GHz
- NF 1.5 dB @ 1GHz
- MAG 14 dB @ 1GHz
- V_{CB0} 25V
- Replaces NE021-37, MFR-901

42¢ ea. in lots of 1,000 (larger quantity pricing is available)

1SS98 MIXER DIODE

- Glass Package (type DO-35)
- $V_F = 0.34 V$ Max @ 1mA
- Replaces MBD-101

15¢ ea. in lots of 1,000 (larger quantity pricing is available)

Just call Jeff or Linda TOLL FREE at 1-800-543-4330 or 1-800-762-4315 (in Ohio).

EMCM ELECTRONICS

CIRCLE 35 ON FREE INFORMATION CARD

CABLE TV

CONVERTERS DESCRAMBLERS

Largest Selection
of Equipment Available
Buy Warehouse Direct & Save \$



36 channel
converter
\$45.95

36 channel
wired remote
converter
only
\$89.95



Send \$2 for complete catalog
of converters and unscramblers

Quantity Discounts • Visa • Master Charge
Add 5% shipping—Mich. residents add 4% sales tax

C&D Electronics, Inc.
P.O. Box 21, Jenison, MI 49428
(616) 669-2440

<p>TUSA A WHOLE NEW WORLD OF TV VIEWING WITH TUSA'S NEW MODEL CVU-40, 40 CHANNEL CABLE TV CONVERTER Receive all the EXTRA CABLE TV "MIDBAND" & SUPERBAND CHANNELS on your UHF DIAL. Eliminates the need for renting or leasing. This system takes the "midband" and "superband" channels your TV, VCR or projector can't receive and converts them to standard UHF channels that any set can tune in.</p> <p>A MUST FOR VIDEO-TAPING FROM CABLE TV! The system allows you to program both pay (pay TV decoder required) and standard cable channels for taping on any VCR — while you are watching a different channel on your TV. Now \$28.95 ea. Simple to install and operate on any make of TV with UHF. PLUS POSTAGE</p> <p>NOW AVAILABLE NEW TUNEABLE DELUXE MODEL CVU-1000 \$34.95 ea.</p>	<p>UHF TUNERS Continuous Tune Model 45MHz Output</p> <p>While They Last</p> <p>\$3.50 ea. 5 or more \$2.25 ea.</p>	<p>POPULAR IC's TOP QUALITY NO SECONDS</p> <table border="1"> <thead> <tr> <th>TYPE</th> <th>DESCRIPTION</th> <th>1-8</th> <th>10-UP</th> </tr> </thead> <tbody> <tr> <td>LM-580N</td> <td>2 watt Audio Power Amp</td> <td>\$1.49</td> <td>\$1.12</td> </tr> <tr> <td>LM-380N-3</td> <td>500mWV Low Voltage Audio Amp</td> <td>1.59</td> <td>1.19</td> </tr> <tr> <td>NE-554N</td> <td>Digital Phase Locked Loop</td> <td>3.50</td> <td>2.89</td> </tr> <tr> <td>LM-555N</td> <td>Phase Locked Loop</td> <td>1.49</td> <td>1.12</td> </tr> <tr> <td>LM-733N</td> <td>Video Amp</td> <td>1.89</td> <td>1.27</td> </tr> <tr> <td>MC-1300</td> <td>Video Detector</td> <td>2.49</td> <td>1.87</td> </tr> <tr> <td>MC-1348</td> <td>Video If Amp</td> <td>2.06</td> <td>1.55</td> </tr> <tr> <td>MC-1300</td> <td>Video If Amp</td> <td>1.75</td> <td>1.31</td> </tr> <tr> <td>MC-1302</td> <td>Video If Amp AGC</td> <td>2.89</td> <td>2.09</td> </tr> <tr> <td>MC-1300</td> <td>Audio If Amp</td> <td>1.95</td> <td>1.48</td> </tr> <tr> <td>MC-1374P</td> <td>R.F. Modulator</td> <td>3.19</td> <td>2.29</td> </tr> <tr> <td>MC-1456</td> <td>Dual Comp. Op Amp</td> <td>.85</td> <td>.65</td> </tr> <tr> <td>MC-1496N</td> <td>Balanced Mod/Demodulator</td> <td>1.79</td> <td>1.34</td> </tr> <tr> <td>LM-1900</td> <td>PLL Stereo Decoder</td> <td>2.29</td> <td>1.90</td> </tr> <tr> <td>LM-1889</td> <td>Video Modulator</td> <td>2.79</td> <td>2.19</td> </tr> </tbody> </table> <p>LINEAR VOLTAGE REGULATORS</p> <table border="1"> <tbody> <tr> <td>LM-7805</td> <td>5 Volt Positive Volt. Reg.</td> <td>1.19</td> <td>.89</td> </tr> <tr> <td>LM-7808</td> <td>8 Volt Positive Volt. Reg.</td> <td>1.19</td> <td>.89</td> </tr> <tr> <td>LM-7812</td> <td>12 Volt Positive Volt. Reg.</td> <td>1.19</td> <td>.89</td> </tr> <tr> <td>LM-7815</td> <td>15 Volt Positive Volt. Reg.</td> <td>1.19</td> <td>.89</td> </tr> <tr> <td>LM-7818</td> <td>18 Volt Positive Volt. Reg.</td> <td>1.19</td> <td>.89</td> </tr> <tr> <td>LM-7824</td> <td>24 Volt Positive Volt. Reg.</td> <td>1.19</td> <td>.89</td> </tr> </tbody> </table>	TYPE	DESCRIPTION	1-8	10-UP	LM-580N	2 watt Audio Power Amp	\$1.49	\$1.12	LM-380N-3	500mWV Low Voltage Audio Amp	1.59	1.19	NE-554N	Digital Phase Locked Loop	3.50	2.89	LM-555N	Phase Locked Loop	1.49	1.12	LM-733N	Video Amp	1.89	1.27	MC-1300	Video Detector	2.49	1.87	MC-1348	Video If Amp	2.06	1.55	MC-1300	Video If Amp	1.75	1.31	MC-1302	Video If Amp AGC	2.89	2.09	MC-1300	Audio If Amp	1.95	1.48	MC-1374P	R.F. Modulator	3.19	2.29	MC-1456	Dual Comp. Op Amp	.85	.65	MC-1496N	Balanced Mod/Demodulator	1.79	1.34	LM-1900	PLL Stereo Decoder	2.29	1.90	LM-1889	Video Modulator	2.79	2.19	LM-7805	5 Volt Positive Volt. Reg.	1.19	.89	LM-7808	8 Volt Positive Volt. Reg.	1.19	.89	LM-7812	12 Volt Positive Volt. Reg.	1.19	.89	LM-7815	15 Volt Positive Volt. Reg.	1.19	.89	LM-7818	18 Volt Positive Volt. Reg.	1.19	.89	LM-7824	24 Volt Positive Volt. Reg.	1.19	.89
TYPE	DESCRIPTION	1-8	10-UP																																																																																							
LM-580N	2 watt Audio Power Amp	\$1.49	\$1.12																																																																																							
LM-380N-3	500mWV Low Voltage Audio Amp	1.59	1.19																																																																																							
NE-554N	Digital Phase Locked Loop	3.50	2.89																																																																																							
LM-555N	Phase Locked Loop	1.49	1.12																																																																																							
LM-733N	Video Amp	1.89	1.27																																																																																							
MC-1300	Video Detector	2.49	1.87																																																																																							
MC-1348	Video If Amp	2.06	1.55																																																																																							
MC-1300	Video If Amp	1.75	1.31																																																																																							
MC-1302	Video If Amp AGC	2.89	2.09																																																																																							
MC-1300	Audio If Amp	1.95	1.48																																																																																							
MC-1374P	R.F. Modulator	3.19	2.29																																																																																							
MC-1456	Dual Comp. Op Amp	.85	.65																																																																																							
MC-1496N	Balanced Mod/Demodulator	1.79	1.34																																																																																							
LM-1900	PLL Stereo Decoder	2.29	1.90																																																																																							
LM-1889	Video Modulator	2.79	2.19																																																																																							
LM-7805	5 Volt Positive Volt. Reg.	1.19	.89																																																																																							
LM-7808	8 Volt Positive Volt. Reg.	1.19	.89																																																																																							
LM-7812	12 Volt Positive Volt. Reg.	1.19	.89																																																																																							
LM-7815	15 Volt Positive Volt. Reg.	1.19	.89																																																																																							
LM-7818	18 Volt Positive Volt. Reg.	1.19	.89																																																																																							
LM-7824	24 Volt Positive Volt. Reg.	1.19	.89																																																																																							
<p>WINEBARD 75 OHM UHF YAGI ANTENNAS</p> <p>12 db GAIN SPECIFY CHANNEL \$8.95 ea. 8 OR MORE \$6.95 ea.</p> <p>OPTIONAL Winegard UHF Antenna Preamp 18db Gain \$39.95 ea.</p>	<p>BRAND NEW UHF VARACTOR TUNERS</p> <p>Sanyo YOUR CHOICE Mitsumi 45 MHz Output \$24.95 ea. 45 MHz Output</p> <p>Call for Quantity Prices</p>	<p>AC LINE CORDS</p> <p>18 gauge wire 6 ft. long cable Prestriped and tinned ends for easy installation.</p> <p>AC-6G 12-Up 49¢ ea. 39¢ ea.</p>																																																																																								
<p>SPEAKER CABINET Popular speaker cabinets for those famous homebrew TV circuits. Speakers included. Dimensions: 7 1/2" wide x 5 1/2" high x 5 1/2" deep. Removable 1/8" thick back cover.</p> <p>SC001 \$10.95 ea. 2 or more \$8.95 ea.</p>	<p>VCR-TV 10db VHF/CABLE/FM SIGNAL AMPLIFIER</p> <p>#401 50-400 MHz. This one really works! Boosting those weak VHF/FM, midband & superband cable channels. Standard F connectors for 75 ohm input/output.</p> <p>SC001 \$9.95 ea. 4 or more \$8.95 ea.</p>	<p>Special Purchase MV-2109 33pf Tuning Slide 1-9 \$1.11 25 ea. 12 or more 16¢ ea. 10-Up .39 ea.</p> <p>5% MICA CAPS 5%</p> <table border="1"> <tbody> <tr> <td>10pf .42¢ ea.</td> <td>500pf .60¢ ea.</td> </tr> <tr> <td>43pf .35¢ ea.</td> <td>1200pf .89¢ ea.</td> </tr> <tr> <td>110pf .35¢ ea.</td> <td>5000pf 1.39 ea.</td> </tr> </tbody> </table> <p>Call for Quantity Discount</p>	10pf .42¢ ea.	500pf .60¢ ea.	43pf .35¢ ea.	1200pf .89¢ ea.	110pf .35¢ ea.	5000pf 1.39 ea.																																																																																		
10pf .42¢ ea.	500pf .60¢ ea.																																																																																									
43pf .35¢ ea.	1200pf .89¢ ea.																																																																																									
110pf .35¢ ea.	5000pf 1.39 ea.																																																																																									
<p>QUALITY POWER TRANSFORMERS 24V CT, 400 mA \$3.69 ea. 10-49 \$2.75 ea. 50 or more \$2.25 ea.</p>	<p>75 OHM CHASSIS MOUNT CONNECTOR</p> <p>F-61 Female connector. Rear chassis mount with nut. Mates with male "F" connector. While they last! 4 for \$1.00</p>	<p>POPULAR MICROWAVE PARTS</p> <table border="1"> <tbody> <tr> <td>MNF-001</td> <td>.....</td> <td>\$2.75</td> </tr> <tr> <td>9-Up</td> <td>.....</td> <td>2.19</td> </tr> <tr> <td>MNF-011</td> <td>.....</td> <td>3.49</td> </tr> <tr> <td>9-Up</td> <td>.....</td> <td>3.12</td> </tr> <tr> <td>MBD-101</td> <td>.....</td> <td>.99</td> </tr> <tr> <td>CHIP CAPS .001 mfd</td> <td>.....</td> <td>.20</td> </tr> <tr> <td>25-Up</td> <td>.....</td> <td>.30</td> </tr> <tr> <td>2N6903 (formerly MRF 902)</td> <td>.....</td> <td>11.99</td> </tr> </tbody> </table>	MNF-001	\$2.75	9-Up	2.19	MNF-011	3.49	9-Up	3.12	MBD-10199	CHIP CAPS .001 mfd20	25-Up30	2N6903 (formerly MRF 902)	11.99																																																																
MNF-001	\$2.75																																																																																								
9-Up	2.19																																																																																								
MNF-011	3.49																																																																																								
9-Up	3.12																																																																																								
MBD-10199																																																																																								
CHIP CAPS .001 mfd20																																																																																								
25-Up30																																																																																								
2N6903 (formerly MRF 902)	11.99																																																																																								
<p>DELUXE A-B SWITCHES Specify Pushbutton or lever type For CATV - MATV - VCR 75 ohm - 90 db Isolation While They Last \$6.95 ea.</p>	<p>PROJECT BOXES Woodgrain This box is 11 1/4" W - 4 1/4" H - 6 1/2" D with a removable aluminum U-shaped chassis 11" W - 3 1/4" H - 6" D inside. \$12.50 ea. 4 or more \$10.95 ea. For Larger Quantities - CALL</p>	<p>WINEBARD UHF - VHF - FM SPLITTER</p> <p>40-900 MHz Model PM-1030 Low Loss 3.5-4 db. Low VSWR Waterproof 1-9 \$2.49 ea. Housing 10-Up \$1.89 ea.</p>																																																																																								

ORDER NOW TOLL FREE
800-854-4655
OUTSIDE CALIFORNIA
714-835-5090
INSIDE CALIFORNIA

R.F. ELECTRONICS

1056 N. STATE COLLEGE BLVD., DEPT. R
ANAHEIM, CALIFORNIA 92806

PERSONAL CHECKS HELD FOR CLEARANCE — NO MINIMUM ORDER

ALL PREPAID ORDERS 2 LBS OR LESS MUST INCLUDE \$2.50 SHIPPING & HANDLING — SHIPPED SAME DAY RECEIVED

OPEN TUES - FRI
10-6
SAT 10-5
CLOSED SUN & MON

CALL TO ORDER
TOLL FREE
Order Catalog


CIRCLE 27 ON FREE INFORMATION CARD

JULY 1983

119

"THE NEW DELUXE II"

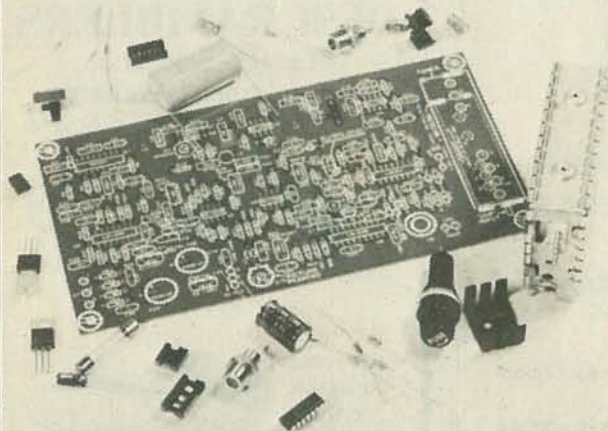The new leader in sinewave technology is now available at industry shattering prices. We also have the new and improved plusewave kit.



New Deluxe II Board with free complete assembly plans **20.00**
 New Deluxe II complete kit and enclosure **119.95**
 Pulse Wave AD-1 board with free complete assembly plans **20.00**
 Pulse Wave AD-1 complete kit and enclosure **119.95**
 Add 5% shipping and handling for Continental U.S. Add 10% shipping and handling for outside Continental U.S.

GAMMA ELECTRONICS

455 Massachusetts Avenue
 Arlington, Mass. 02174

To Order Call:
1-617-641-0778



DEALERS WANTED

CIRCLE 21 ON FREE INFORMATION CARD

Special Take 2 Sale!



Take 2 12" CRT MONITOR 2 for 1 Special

THIS MONTH ONLY

Untested 12" CRT Monitors, no broken tubes, all are whole, but untested. 12" P-31 phosphor, transformer AC, 120/220 VAC. Includes schematic.

Buy 1 Get 1 FREE \$39⁰⁰ each
 Add \$5 Packaging Plus Shipping



Take 2 MPI/CDC 9404

- Single sided single density
- Removed from equipment to install DSSD drives
- Includes data & schematics
- Untested, complete

Plus Shipping **2/\$199⁰⁰**

Take 2

2 BAND PRINTER TERMINALS FOR THE PRICE OF 1



Features:

- RS32 ASCII Input • Fully Formed Type • Up to 1200 Baud (120 cps) for almost 60 lpm • 120 Columns at 10 pitch • Changeable Print Band • Ultra Reliable • 94 Characters (Upper & Lower Case) • 115 VAC 60 Hz • MFG R's PRICE OVER \$5K

One unit is fully tested and operational, cleaned and ready to use. The other is clean and whole but UNTESTED (use as a spare or as parts machine). Line Cord & Forms Tractor NOT included (available from GE direct!) Tractor GE Part No. 44C414730-G02.

2 FOR 1 SALE PRICE **Only \$295⁰⁰ Pair**

(Add \$30 for Pkg.-Pay Shpg. on Delivery)

"SELECTRIC" 745 I/O Printers



- No time to test 'em
- Complete w/TTL driver inputs
- IBM model 745 I/O printer
- Use as a typewriter or printer

JUST **\$279⁰⁰**

Cleaned & Adjusted Fully Operational **\$399⁰⁰**
 Plus Shipping (\$20.00 Ea. Pkg.)

We Stock New "Selectric" Parts For The Above

Write or Call Now For Our NEW BARGAIN-PACKED FLYER

Computer Products & Peripherals Unlimited

WAREHOUSE: 18 Granite St. Haverhill, Mass. 01830
 MAIL ORDERS: Box 204, Newton, New Hampshire 03858

617/372-8637

Sorry No Collect Calls
 MasterCard & VISA Accepted

CIRCLE 68 ON FREE INFORMATION CARD

Components is Our First Name Call Us with Your Requirements



NEW 12" Green Monitor

Easy on the Eyes. Connects to most popular computers w/o interface or modifications

\$85⁰⁰

APPLE IIe 64K RAM CARD
 80 x 24, 64K RAM
 Compatible with Apple IIe Software

\$149⁰⁰

for APPLE

16K RAM CARD
 Language Transparent
 COEX FACTORY WARRANTY

\$69⁹⁵

5 1/4" Floppy DISKETTES

All Certified-100% Guaranteed

BOX of 100 ... **\$149⁰⁰**
 Above with Hub Rings **\$169.00**

FLOPPY DISK DRIVE

Apple IIe Compatible
 with • Track Zero Micro Switch
 • DOS 3.2.1 & DOS 3.3
 • CP/M and PASCAL

DESIGNED FOR YOUR APPLE™ **\$235⁰⁰**

Controller Card for above **\$75.00**

COEX 80-Ft DOT MATRIX PRINTER

- 9x7 Dot Matrix, 80 CPS, Bi-Directional Printing
- 2K Buffered Memory
- 80, 96, 132 Columns, Graphics and Block Printing
- Selectable Char Pitch, Line Spacing and Feed



COEX Interface Card to Apple .. **\$49.95**
 Commodore Interface Card to VIC, 64, PET **\$79.95**

\$275⁰⁰

VISION-80® \$229⁰⁰

80x24 Video Display Card
 Vista Computer Company's new Vision-80 board is a sophisticated yet easy to use video display card for the Apple™ computer.

EXTENDER CARDS

for APPLE... **\$16.95**
 for I.B.M.... **\$19.95**

DO YOU HAVE A COMMODORE?

NEW ROM for COEX 80 & DP8480
 Allows Full Graphics Compatibility with All Commodore Computers **\$29⁹⁵**

PARALLEL INTERFACE EPSON TO APPLE

New From COEX **\$49⁹⁵** CABLE INCLUDED

"Have You Kissed Your Computer Lately?"

Components Express, Inc.

1380 E. Edinger • Santa Ana, Calif. 92705 • 714/558-3972

Terms of Sale: Cash, Checks, Credit Cards, M.O., C.O.D. FOB Santa Ana. Calif. residents add 6% sales tax.



ramsey the first name in Counters!



9 DIGITS 600 MHz \$129⁹⁵ WIRED

PRICES:

CT-90 wired, 1 year warranty	\$129.95
CT-90 Kit, 90 day parts warranty	
AC-1 AC adapter	109.95
BP-1 Nicad pack + AC Adapter/Charger	3.95
OV-1, Micro-power Oven time base	12.95
External time base input	49.95
	14.95

The CT-90 is the most versatile, feature packed counter available for less than \$300.00! Advanced design features include: three selectable gate times, nine digits, gate indicator and a unique display hold function which holds the displayed count after the input signal is removed! Also, a 10MHz TCXO time base is used which enables easy zero beat calibration checks against WWV. Optionally, an internal nicad battery pack, external time base input and Micro-power high stability crystal oven time base are available. The CT-90, performance you can count on!

SPECIFICATIONS:

Range:	20 Hz to 600 MHz
Sensitivity:	Less than 10 MV to 150 MHz Less than 50 MV to 500 MHz
Resolution:	0.1 Hz (10 MHz range) 1.0 Hz (60 MHz range) 10.0 Hz (600 MHz range)
Display:	9 digits 0.4" LED
Time base:	Standard-10.000 mHz, 1.0 ppm 20-40°C. Optional Micro-power oven-0.1 ppm 20-40°C
Power:	8-15 VAC @ 250 ma

7 DIGITS 525 MHz \$99⁹⁵ WIRED



SPECIFICATIONS:

Range:	20 Hz to 525 MHz
Sensitivity:	Less than 50 MV to 150 MHz Less than 150 MV to 500 MHz
Resolution:	1.0 Hz (5 MHz range) 10.0 Hz (50 MHz range) 100.0 Hz (500 MHz range)
Display:	7 digits 0.4" LED
Time base:	1.0 ppm TCXO 20-40°C
Power:	12 VAC @ 250 ma

The CT-70 breaks the price barrier on lab quality frequency counters. Deluxe features such as; three frequency ranges - each with pre-amplification, dual selectable gate times, and gate activity indication make measurements a snap. The wide frequency range enables you to accurately measure signals from audio thru UHF with 1.0 ppm accuracy - that's .0001%! The CT-70 is the answer to all your measurement needs, in the field, lab or ham shack.

PRICES:

CT-70 wired, 1 year warranty	\$99.95
CT-70 Kit, 90 day parts warranty	
AC-1 AC adapter	84.95
BP-1 Nicad pack + AC adapter/charger	3.95
	12.95

7 DIGITS 500 MHz \$79⁹⁵ WIRED



PRICES:

MINI-100 wired, 1 year warranty	\$79.95
AC-Z Ac adapter for MINI-100	3.95
BP-Z Nicad pack and AC adapter/charger	12.95

Here's a handy, general purpose counter that provides most counter functions at an unbelievable price. The MINI-100 doesn't have the full frequency range or input impedance qualities found in higher price units, but for basic RF signal measurements, it can't be beat! Accurate measurements can be made from 1 MHz all the way up to 500 MHz with excellent sensitivity throughout the range, and the two gate times let you select the resolution desired. Add the nicad pack option and the MINI-100 makes an ideal addition to your tool box for "in-the-field" frequency checks and repairs.

SPECIFICATIONS:

Range:	1 MHz to 500 MHz
Sensitivity:	Less than 25 MV
Resolution:	100 Hz (slow gate) 1.0 KHz (fast gate)
Display:	7 digits, 0.4" LED
Time base:	2.0 ppm 20-40°C
Power:	5 VDC @ 200 ma

8 DIGITS 600 MHz \$159⁹⁵ WIRED



**NEW
RECEIVER
FREQUENCY**

SPECIFICATIONS:

Range:	20 Hz to 600 MHz
Sensitivity:	Less than 25 mv to 150 MHz Less than 150 mv to 600 MHz
Resolution:	1.0 Hz (60 MHz range) 10.0 Hz (600 MHz range)
Display:	8 digits 0.4" LED
Time base:	2.0 ppm 20-40°C
Power:	110 VAC or 12 VDC

The CT-50 is a versatile lab bench counter that will measure up to 600 MHz with 8 digit precision. And, one of its best features is the Receive Frequency Adapter, which turns the CT-50 into a digital readout for any receiver. The adapter is easily programmed for any receiver and a simple connection to the receiver's VFO is all that is required for use. Adding the receiver adapter in no way limits the operation of the CT-50, the adapter can be conveniently switched on or off. The CT-50, a counter that can work double-duty!

PRICES:

CT-50 wired, 1 year warranty	\$159.95
CT-50 Kit, 90 day parts warranty	
RA-1, receiver adapter kit	119.95
RA-1 wired and pre-programmed (send copy of receiver schematic)	14.95
	29.95



DIGITAL MULTIMETER \$99⁹⁵ WIRED

PRICES:

DM-700 wired, 1 year warranty	\$99.95
DM-700 Kit, 90 day parts warranty	79.95
AC-1, AC adapter	3.95
BP-3, Nicad pack + AC adapter/charger	19.95
MP-1, Probe kit	2.95

The DM-700 offers professional quality performance at a hobbyist price. Features include: 26 different ranges and 5 functions, all arranged in a convenient, easy to use format. Measurements are displayed on a large 3½ digit, ½ inch LED readout with automatic decimal placement, automatic polarity, overrange indication and overload protection up to 1250 volts on all ranges, making it virtually goof-proof! The DM-700 looks great, a handsome, jet black, rugged ABS case with convenient retractable tilt bail makes it an ideal addition to any shop.

SPECIFICATIONS:

DC/AC volts:	100uV to 1 KV, 5 ranges
DC/AC current:	0.1uA to 2.0 Amps, 5 ranges
Resistance:	0.1 ohms to 20 Megohms, 6 ranges
Input impedance:	10 Megohms, DC/AC volts
Accuracy:	0.1% basic DC volts
Power:	4 °C cells

AUDIO SCALER

For high resolution audio measurements, multiplies UP in frequency.

- Great for PL tones
- Multiplies by 10 or 100
- 0.01 Hz resolution!

\$29.95 Kit \$39.95 Wired

ACCESSORIES

Telescopic whip antenna - BNC plug	\$ 7.95
High impedance probe, light loading	15.95
Low pass probe, for audio measurements	15.95
Direct probe, general purpose usage	12.95
Tilt bail, for CT 70, 90, MINI-100	3.95
Color burst calibration unit, calibrates counter against color TV signal	14.95

COUNTER PREAMP

For measuring extremely weak signals from 10 to 1,000 MHz. Small size, powered by plug transformer-included.

- Flat 25 db gain
 - BNC Connectors
 - Great for sniffing RF with pick-up loop
- \$34.95 Kit \$44.95 Wired

ramsey electronics, inc.

2575 BAIRD RD. • PENFIELD, NY 14526



PHONE ORDERS
CALL 716-586-3950

TERMS:

Satisfaction guaranteed - examine for 10 days, if not pleased, return in original form for refund. Add 5% for shipping - insurance to a maximum of \$10. Overseas add 15%. COD add \$2. Orders under \$10, add \$1.50. NY residents, add 7% tax.

CIRCLE 79 ON FREE INFORMATION CARD

DIGI-KEY 800-346-5144

In Mn., Ak., HI, Call 218-681-6674

NATIONAL SEMICONDUCTOR • PANASONIC • QUALITY - Name brand products from nationally recognized manufacturers. CHEMICALS • ARIES • PLESSEY • MOLEX • E. WACHNE • DIAMOND TOOL • UNICAR • GC CH AS INSTRUMENTS • ITT • A.P. PRODUCTS • DIA ND TOOL • UNICAR • GC CHEMICALS • ARIES • PLESSEY • MOLEX • E. WACHNE • DIAMOND TOOL • UNICAR • GC CH

SAVINGS - Volume Discounts • OEM Quantity Pricing • Toll Free 800 Number
 SERVICE - Computerized order processing and inventory control.
 The DIGI-KEY Discount makes a Big Price Difference

master charge
 DISC CAPACITORS
 PANASONIC RESIN DIPPED TANTALUM CAPACITORS

INTEGRATED CIRCUITS

7400 TTL	74ALS00 TTL	74ALS00 TTL	74ALS00 TTL
7400	7400	7400	7400
7401	7401	7401	7401
7402	7402	7402	7402
7500	7500	7500	7500

TEXAS INSTRUMENTS I.C. SOCKETS

Body - 94 V-0 polypropylene with Copper Alloy contacts. Accommodates standard IC leads up to 0.04" diameter and 0.025" wide. Contact is designed and oriented to the socket to give the best "break" of the IC leads, allowing for low insertion and high retention forces. Socket is constructed of stainless steel and is available in standard or custom lead configurations.

SOLDER TAIL DIP SOCKETS
 • Single lead
 • Low profile
 • YOUR CHOICE: TIN OR GOLD
 • Standard 18 pin
 • 24 pin
 • 28 pin
 • 32 pin
 • 36 pin
 • 40 pin
 • 44 pin
 • 48 pin
 • 52 pin
 • 56 pin
 • 60 pin
 • 64 pin
 • 68 pin
 • 72 pin
 • 76 pin
 • 80 pin
 • 84 pin
 • 88 pin
 • 92 pin
 • 96 pin
 • 100 pin

GOLD PLATED SOLDER TAIL
 Part No. Description Price
 CS18 18 pin solder tail, tin 1.15 10 180
 CS24 24 pin solder tail, tin 1.15 10 240
 CS28 28 pin solder tail, tin 1.15 10 280
 CS32 32 pin solder tail, tin 1.15 10 320
 CS36 36 pin solder tail, tin 1.15 10 360
 CS40 40 pin solder tail, tin 1.15 10 400
 CS44 44 pin solder tail, tin 1.15 10 440
 CS48 48 pin solder tail, tin 1.15 10 480
 CS52 52 pin solder tail, tin 1.15 10 520
 CS56 56 pin solder tail, tin 1.15 10 560
 CS60 60 pin solder tail, tin 1.15 10 600
 CS64 64 pin solder tail, tin 1.15 10 640
 CS68 68 pin solder tail, tin 1.15 10 680
 CS72 72 pin solder tail, tin 1.15 10 720
 CS76 76 pin solder tail, tin 1.15 10 760
 CS80 80 pin solder tail, tin 1.15 10 800
 CS84 84 pin solder tail, tin 1.15 10 840
 CS88 88 pin solder tail, tin 1.15 10 880
 CS92 92 pin solder tail, tin 1.15 10 920
 CS96 96 pin solder tail, tin 1.15 10 960
 CS100 100 pin solder tail, tin 1.15 10 1000

WIRE WRAP DIP SOCKETS
 • Standard profile
 • Universal mounting and packaging applications
 • Concrete construction, 95% through hole
 • or round shell top leads
 • Wire wrap leads are positioned at 90° providing a true position of 80° on boards for efficient automatic wire wrapping.
 • YOUR CHOICE: TIN OR GOLD
 • Standard 18 pin
 • 24 pin
 • 28 pin
 • 32 pin
 • 36 pin
 • 40 pin
 • 44 pin
 • 48 pin
 • 52 pin
 • 56 pin
 • 60 pin
 • 64 pin
 • 68 pin
 • 72 pin
 • 76 pin
 • 80 pin
 • 84 pin
 • 88 pin
 • 92 pin
 • 96 pin
 • 100 pin

TEXAS INSTRUMENTS GOLD EDGEBOARD CONNECTORS
 Part No. Description Price
 CE18 18 pin edge board, tin 3.00 3 180
 CE24 24 pin edge board, tin 3.00 3 240
 CE28 28 pin edge board, tin 3.00 3 280
 CE32 32 pin edge board, tin 3.00 3 320
 CE36 36 pin edge board, tin 3.00 3 360
 CE40 40 pin edge board, tin 3.00 3 400
 CE44 44 pin edge board, tin 3.00 3 440
 CE48 48 pin edge board, tin 3.00 3 480
 CE52 52 pin edge board, tin 3.00 3 520
 CE56 56 pin edge board, tin 3.00 3 560
 CE60 60 pin edge board, tin 3.00 3 600
 CE64 64 pin edge board, tin 3.00 3 640
 CE68 68 pin edge board, tin 3.00 3 680
 CE72 72 pin edge board, tin 3.00 3 720
 CE76 76 pin edge board, tin 3.00 3 760
 CE80 80 pin edge board, tin 3.00 3 800
 CE84 84 pin edge board, tin 3.00 3 840
 CE88 88 pin edge board, tin 3.00 3 880
 CE92 92 pin edge board, tin 3.00 3 920
 CE96 96 pin edge board, tin 3.00 3 960
 CE100 100 pin edge board, tin 3.00 3 1000

DISC CAPACITORS

NEW! KIT
 28 DISC CAPACITORS
 Price includes container, gold plated leads with tin and solder, and a 100 ohm resistor.
 ASSORTMENT OF 18 POPULAR VALUES
 CAT. NO. P2000-KIT
 ONLY \$3.95

NEW! KIT
 28 DISC CAPACITORS
 Price includes container, gold plated leads with tin and solder, and a 100 ohm resistor.
 ASSORTMENT OF 18 POPULAR VALUES
 CAT. NO. P2000-KIT
 ONLY \$3.95

NEW! KIT
 28 DISC CAPACITORS
 Price includes container, gold plated leads with tin and solder, and a 100 ohm resistor.
 ASSORTMENT OF 18 POPULAR VALUES
 CAT. NO. P2000-KIT
 ONLY \$3.95

NEW! KIT
 28 DISC CAPACITORS
 Price includes container, gold plated leads with tin and solder, and a 100 ohm resistor.
 ASSORTMENT OF 18 POPULAR VALUES
 CAT. NO. P2000-KIT
 ONLY \$3.95

WIRE WRAP DIP SOCKETS

• Standard profile
 • Universal mounting and packaging applications
 • Concrete construction, 95% through hole
 • or round shell top leads
 • Wire wrap leads are positioned at 90° providing a true position of 80° on boards for efficient automatic wire wrapping.
 • YOUR CHOICE: TIN OR GOLD
 • Standard 18 pin
 • 24 pin
 • 28 pin
 • 32 pin
 • 36 pin
 • 40 pin
 • 44 pin
 • 48 pin
 • 52 pin
 • 56 pin
 • 60 pin
 • 64 pin
 • 68 pin
 • 72 pin
 • 76 pin
 • 80 pin
 • 84 pin
 • 88 pin
 • 92 pin
 • 96 pin
 • 100 pin

TEXAS INSTRUMENTS GOLD EDGEBOARD CONNECTORS
 Part No. Description Price
 CE18 18 pin edge board, tin 3.00 3 180
 CE24 24 pin edge board, tin 3.00 3 240
 CE28 28 pin edge board, tin 3.00 3 280
 CE32 32 pin edge board, tin 3.00 3 320
 CE36 36 pin edge board, tin 3.00 3 360
 CE40 40 pin edge board, tin 3.00 3 400
 CE44 44 pin edge board, tin 3.00 3 440
 CE48 48 pin edge board, tin 3.00 3 480
 CE52 52 pin edge board, tin 3.00 3 520
 CE56 56 pin edge board, tin 3.00 3 560
 CE60 60 pin edge board, tin 3.00 3 600
 CE64 64 pin edge board, tin 3.00 3 640
 CE68 68 pin edge board, tin 3.00 3 680
 CE72 72 pin edge board, tin 3.00 3 720
 CE76 76 pin edge board, tin 3.00 3 760
 CE80 80 pin edge board, tin 3.00 3 800
 CE84 84 pin edge board, tin 3.00 3 840
 CE88 88 pin edge board, tin 3.00 3 880
 CE92 92 pin edge board, tin 3.00 3 920
 CE96 96 pin edge board, tin 3.00 3 960
 CE100 100 pin edge board, tin 3.00 3 1000

TEXAS INSTRUMENTS GOLD EDGEBOARD CONNECTORS
 Part No. Description Price
 CE18 18 pin edge board, tin 3.00 3 180
 CE24 24 pin edge board, tin 3.00 3 240
 CE28 28 pin edge board, tin 3.00 3 280
 CE32 32 pin edge board, tin 3.00 3 320
 CE36 36 pin edge board, tin 3.00 3 360
 CE40 40 pin edge board, tin 3.00 3 400
 CE44 44 pin edge board, tin 3.00 3 440
 CE48 48 pin edge board, tin 3.00 3 480
 CE52 52 pin edge board, tin 3.00 3 520
 CE56 56 pin edge board, tin 3.00 3 560
 CE60 60 pin edge board, tin 3.00 3 600
 CE64 64 pin edge board, tin 3.00 3 640
 CE68 68 pin edge board, tin 3.00 3 680
 CE72 72 pin edge board, tin 3.00 3 720
 CE76 76 pin edge board, tin 3.00 3 760
 CE80 80 pin edge board, tin 3.00 3 800
 CE84 84 pin edge board, tin 3.00 3 840
 CE88 88 pin edge board, tin 3.00 3 880
 CE92 92 pin edge board, tin 3.00 3 920
 CE96 96 pin edge board, tin 3.00 3 960
 CE100 100 pin edge board, tin 3.00 3 1000

TEXAS INSTRUMENTS GOLD EDGEBOARD CONNECTORS
 Part No. Description Price
 CE18 18 pin edge board, tin 3.00 3 180
 CE24 24 pin edge board, tin 3.00 3 240
 CE28 28 pin edge board, tin 3.00 3 280
 CE32 32 pin edge board, tin 3.00 3 320
 CE36 36 pin edge board, tin 3.00 3 360
 CE40 40 pin edge board, tin 3.00 3 400
 CE44 44 pin edge board, tin 3.00 3 440
 CE48 48 pin edge board, tin 3.00 3 480
 CE52 52 pin edge board, tin 3.00 3 520
 CE56 56 pin edge board, tin 3.00 3 560
 CE60 60 pin edge board, tin 3.00 3 600
 CE64 64 pin edge board, tin 3.00 3 640
 CE68 68 pin edge board, tin 3.00 3 680
 CE72 72 pin edge board, tin 3.00 3 720
 CE76 76 pin edge board, tin 3.00 3 760
 CE80 80 pin edge board, tin 3.00 3 800
 CE84 84 pin edge board, tin 3.00 3 840
 CE88 88 pin edge board, tin 3.00 3 880
 CE92 92 pin edge board, tin 3.00 3 920
 CE96 96 pin edge board, tin 3.00 3 960
 CE100 100 pin edge board, tin 3.00 3 1000

TEXAS INSTRUMENTS GOLD EDGEBOARD CONNECTORS
 Part No. Description Price
 CE18 18 pin edge board, tin 3.00 3 180
 CE24 24 pin edge board, tin 3.00 3 240
 CE28 28 pin edge board, tin 3.00 3 280
 CE32 32 pin edge board, tin 3.00 3 320
 CE36 36 pin edge board, tin 3.00 3 360
 CE40 40 pin edge board, tin 3.00 3 400
 CE44 44 pin edge board, tin 3.00 3 440
 CE48 48 pin edge board, tin 3.00 3 480
 CE52 52 pin edge board, tin 3.00 3 520
 CE56 56 pin edge board, tin 3.00 3 560
 CE60 60 pin edge board, tin 3.00 3 600
 CE64 64 pin edge board, tin 3.00 3 640
 CE68 68 pin edge board, tin 3.00 3 680
 CE72 72 pin edge board, tin 3.00 3 720
 CE76 76 pin edge board, tin 3.00 3 760
 CE80 80 pin edge board, tin 3.00 3 800
 CE84 84 pin edge board, tin 3.00 3 840
 CE88 88 pin edge board, tin 3.00 3 880
 CE92 92 pin edge board, tin 3.00 3 920
 CE96 96 pin edge board, tin 3.00 3 960
 CE100 100 pin edge board, tin 3.00 3 1000

TEXAS INSTRUMENTS GOLD EDGEBOARD CONNECTORS
 Part No. Description Price
 CE18 18 pin edge board, tin 3.00 3 180
 CE24 24 pin edge board, tin 3.00 3 240
 CE28 28 pin edge board, tin 3.00 3 280
 CE32 32 pin edge board, tin 3.00 3 320
 CE36 36 pin edge board, tin 3.00 3 360
 CE40 40 pin edge board, tin 3.00 3 400
 CE44 44 pin edge board, tin 3.00 3 440
 CE48 48 pin edge board, tin 3.00 3 480
 CE52 52 pin edge board, tin 3.00 3 520


DI-GI-KEY CORPORATION

In Mn., Ak., Hi. Call 218-681-6674

NATIONAL SEMICONDUCTOR • PANASONIC • QUALITY — Name brand products from nationally recognized manufacturers.
ASIMOV • CHEMVAL • BISHOP GRAPHICS • N. MEXICO • MOLEX • PLESSEY • MOLEX • E. MACHINE • LANGAR • GC CHEMICALS • A. NATIONAL SEMICONDUCTOR • PANASONIC • SAVINGS — Volume Discounts • OEM Quantity Pricing • Toll Free 800 Number
SERVICE — Computerized order processing and inventory control.
THE DIGI-KEY DISCOUNT MAKES THE PRICE DIFFERENCE

TERMINATION JUMPERS
 B-SOCKET CONNECTOR TERMINATION
 P-PCB CONNECTOR TERMINATION
 X-CARD EDGE CONNECTOR TERMINATION

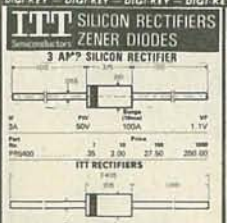alpha cable tubing
 Monohy Wire, Stranded, PVC Insulated
 4 Core MIL-1787 Type B, 500 Volt, 50° to 100° C
 Monohy Wire, Solid, PVC Insulated
 4 Core MIL-1787 Type B, 1000 Volt, 50° to 80° C



SIUCON RECTIFIERS
ZENER DIODES
3 AMP ZENER RECTIFIER

IT RECEIVERS

IT SILICON ZENER DIODES

Part No.	Description	10	100	1000
MA1001	1 Amp 100V Zener Diode	80	100	800
MA1002	1 Amp 200V Zener Diode	80	100	800
MA1003	1 Amp 300V Zener Diode	80	100	800
MA1004	1 Amp 400V Zener Diode	80	100	800
MA1005	1 Amp 500V Zener Diode	80	100	800
MA1006	1 Amp 600V Zener Diode	80	100	800
MA1007	1 Amp 700V Zener Diode	80	100	800
MA1008	1 Amp 800V Zener Diode	80	100	800
MA1009	1 Amp 900V Zener Diode	80	100	800
MA1010	1 Amp 1000V Zener Diode	80	100	800

National Semiconductor
MA1024 7 Inch 4-Digit LED Clock Module
 12 or 24 Hour display
 • P and/or I/O and usually any number of sensors.
 • 50-60V line frequency operation.
 • 12 or 24 Hour display.

Typical Applications Include:
 Clock, Clock, Clock, Clock, Clock, TV and Stereo Tuner, Instrument Panel Clock, Digital Thermometer and more.

Part No. Description Price

MA1024A	12 hr. 4 digit module only	\$27.79
MA1024B	Digi-Key switch panel kit (P.C. Board, 12 hour display, 1000V 100mA fuse, temp. sensor, fuse MA1024P)	\$11.99
MA1024C	12 hr. 4 digit module with 1000V 100mA fuse	\$39.78
MA1024D	12 hr. 4 digit module with 1000V 100mA fuse and temp. sensor	\$41.77
MA1024E	12 hr. 4 digit module with 1000V 100mA fuse and temp. sensor and I/O	\$43.76

Silicon Transistors

Part No.	10	100	1000
2N2001	1.41	1.20	1.00
2N2002	30	17.9	16.25
2N2003	20	17.9	16.25
2N2004	21	18.0	16.25
2N2005	22	20.1	18.25
2N2006	21	18.0	16.25
2N2007	34	23.0	20.25
2N2008	31	18.0	16.25
2N2009	34	23.0	20.25
2N2010	34	23.0	20.25
2N2011	34	23.0	20.25
2N2012	34	23.0	20.25
2N2013	34	23.0	20.25
2N2014	34	23.0	20.25
2N2015	34	23.0	20.25
2N2016	34	23.0	20.25
2N2017	34	23.0	20.25
2N2018	34	23.0	20.25
2N2019	34	23.0	20.25
2N2020	34	23.0	20.25
2N2021	34	23.0	20.25
2N2022	34	23.0	20.25
2N2023	34	23.0	20.25
2N2024	34	23.0	20.25
2N2025	34	23.0	20.25
2N2026	34	23.0	20.25
2N2027	34	23.0	20.25
2N2028	34	23.0	20.25
2N2029	34	23.0	20.25
2N2030	34	23.0	20.25
2N2031	34	23.0	20.25
2N2032	34	23.0	20.25
2N2033	34	23.0	20.25
2N2034	34	23.0	20.25
2N2035	34	23.0	20.25
2N2036	34	23.0	20.25
2N2037	34	23.0	20.25
2N2038	34	23.0	20.25
2N2039	34	23.0	20.25
2N2040	34	23.0	20.25
2N2041	34	23.0	20.25
2N2042	34	23.0	20.25
2N2043	34	23.0	20.25
2N2044	34	23.0	20.25
2N2045	34	23.0	20.25
2N2046	34	23.0	20.25
2N2047	34	23.0	20.25
2N2048	34	23.0	20.25
2N2049	34	23.0	20.25
2N2050	34	23.0	20.25

TERMINATION JUMPERS

B-SOCKET CONNECTOR TERMINATION

P-PCB CONNECTOR TERMINATION

X-CARD EDGE CONNECTOR TERMINATION

Number After Dash is Cable Length in Inches

Part No.	10	100	1000
1001-0001	1.15	1.20	1.40
1001-0002	1.15	1.20	1.40
1001-0003	1.15	1.20	1.40
1001-0004	1.15	1.20	1.40
1001-0005	1.15	1.20	1.40
1001-0006	1.15	1.20	1.40
1001-0007	1.15	1.20	1.40
1001-0008	1.15	1.20	1.40
1001-0009	1.15	1.20	1.40
1001-0010	1.15	1.20	1.40
1001-0011	1.15	1.20	1.40
1001-0012	1.15	1.20	1.40
1001-0013	1.15	1.20	1.40
1001-0014	1.15	1.20	1.40
1001-0015	1.15	1.20	1.40
1001-0016	1.15	1.20	1.40
1001-0017	1.15	1.20	1.40
1001-0018	1.15	1.20	1.40
1001-0019	1.15	1.20	1.40
1001-0020	1.15	1.20	1.40
1001-0021	1.15	1.20	1.40
1001-0022	1.15	1.20	1.40
1001-0023	1.15	1.20	1.40
1001-0024	1.15	1.20	1.40
1001-0025	1.15	1.20	1.40
1001-0026	1.15	1.20	1.40
1001-0027	1.15	1.20	1.40
1001-0028	1.15	1.20	1.40
1001-0029	1.15	1.20	1.40
1001-0030	1.15	1.20	1.40
1001-0031	1.15	1.20	1.40
1001-0032	1.15	1.20	1.40
1001-0033	1.15	1.20	1.40
1001-0034	1.15	1.20	1.40
1001-0035	1.15	1.20	1.40
1001-0036	1.15	1.20	1.40
1001-0037	1.15	1.20	1.40
1001-0038	1.15	1.20	1.40
1001-0039	1.15	1.20	1.40
1001-0040	1.15	1.20	1.40
1001-0041	1.15	1.20	1.40
1001-0042	1.15	1.20	1.40
1001-0043	1.15	1.20	1.40
1001-0044	1.15	1.20	1.40
1001-0045	1.15	1.20	1.40
1001-0046	1.15	1.20	1.40
1001-0047	1.15	1.20	1.40
1001-0048	1.15	1.20	1.40
1001-0049	1.15	1.20	1.40
1001-0050	1.15	1.20	1.40

alpha cable tubing
 Monohy Wire, Stranded, PVC Insulated
 4 Core MIL-1787 Type B, 500 Volt, 50° to 100° C
 Monohy Wire, Solid, PVC Insulated
 4 Core MIL-1787 Type B, 1000 Volt, 50° to 80° C

DIP Jumper Cable Assembly
 Standard Assembly Styles

Number After Dash is Cable Length in Inches

Part No.	10	100	1000
1001-0001	1.15	1.20	1.40
1001-0002	1.15	1.20	1.40
1001-0003	1.15	1.20	1.40
1001-0004	1.15	1.20	1.40
1001-0005	1.15	1.20	1.40
1001-0006	1.15	1.20	1.40
1001-0007	1.15	1.20	1.40
1001-0008	1.15	1.20	1.40
1001-0009	1.15	1.20	1.40
1001-0010	1.15	1.20	1.40
1001-0011	1.15	1.20	1.40
1001-0012	1.15	1.20	1.40
1001-0013	1.15	1.20	1.40
1001-0014	1.15	1.20	1.40
1001-0015	1.15	1.20	1.40
1001-0016	1.15	1.20	1.40
1001-0017	1.15	1.20	1.40
1001-0018	1.15	1.20	1.40
1001-0019	1.15	1.20	1.40
1001-0020	1.15	1.20	1.40
1001-0021	1.15	1.20	1.40
1001-0022	1.15	1.20	1.40
1001-0023	1.15	1.20	1.40
1001-0024	1.15	1.20	1.40
1001-0025	1.15	1.20	1.40
1001-0026	1.15	1.20	1.40
1001-0027	1.15	1.20	1.40
1001-0028	1.15	1.20	1.40
1001-0029	1.15	1.20	1.40
1001-0030	1.15	1.20	1.40
1001-0031	1.15	1.20	1.40
1001-0032	1.15	1.20	1.40
1001-0033	1.15	1.20	1.40
1001-0034	1.15	1.20	1.40
1001-0035	1.15	1.20	1.40
1001-0036	1.15	1.20	1.40
1001-0037	1.15	1.20	1.40
1001-0038	1.15	1.20	1.40
1001-0039	1.15	1.20	1.40
1001-0040	1.15	1.20	1.40
1001-0041	1.15	1.20	1.40
1001-0042	1.15	1.20	1.40
1001-0043	1.15	1.20	1.40
1001-0044	1.15	1.20	1.40
1001-0045	1.15	1.20	1.40
1001-0046	1.15	1.20	1.40
1001-0047	1.15	1.20	1.40
1001-0048	1.15	1.20	1.40
1001-0049	1.15	1.20	1.40
1001-0050	1.15	1.20	1.40

LED's
 3mm, 4mm, 5mm, Round, Rectangular Array

DIGI-CLOCK KIT
 12:38
 12:48
 Part No. 5011 ONLY \$7.95


LED's
 3mm, 4mm, 5mm, Round, Rectangular Array

Part No.	10	100	1000
1001-0001	1.15	1.20	1.40
1001-0002	1.15	1.20	1.40
1001-0003	1.15	1.20	1.40
1001-0004	1.15	1.20	1.40
1001-0005	1.15	1.20	1.40
1001-0006	1.15	1.20	1.40
1001-0007	1.15	1.20	1.40
1001-0008	1.15	1.20	1.40
1001-0009	1.15	1.20	1.40
1001-0010	1.15	1.20	1.40
1001-0011	1.15	1.20	1.40
1001-0012	1.15	1.20	1.40
1001-0013	1.15	1.20	1.40
1001-0014	1.15	1.20	1.40
1001-0015	1.15	1.20	1.40
1001-0016	1.15	1.20	1.40
1001-0017	1.15	1.20	1.40
1001-0018	1.15	1.20	1.40
1001-0019	1.15	1.20	1.40
1001-0020	1.15	1.20	1.40
1001-0021	1.15	1.20	1.40
1001-0022	1.15	1.20	1.40
1001-0023	1.15	1.20	1.40
1001-0024	1.15	1.20	1.40
1001-0025	1.15	1.20	1.40
1001-0026	1.15	1.20	1.40
1001-0027	1.15	1.20	1.40
1001-0028	1.15	1.20	1.40
1001-0029	1.15	1.20	1.40
1001-0030	1.15	1.20	1.40
1001-0031	1.15	1.20	1.40
1001-0032	1.15	1.20	1.40
1001-0033	1.15	1.20	1.40
1001-0034	1.15	1.20	1.40
1001-003			

ADVANCED COMPUTER PRODUCTS

SEND \$2.00 for 1983 CATALOG

16K Apple™ Ramcard

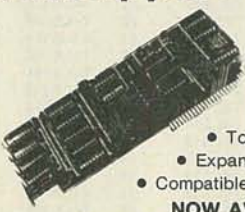

LIST 195
ACP

\$59.95

- Full 1 year warranty
- Top quality — gold fingers
- Expand Apple II 48K to 64K
- Compatible with Z-80 Softcard™

NOW AVAILABLE

Apple IIe 64K Add-in Memory with 80 Columns **\$149.95**

32K STATIC RAM

2 or 4 MHz Expandable Uses 2114L's

- 16K 4 MHz Kit \$159.95
- 16K 4 MHz A&T \$217.95
- 32K 4 MHz Kit **\$129.95**
- 32K 4 MHz A&T **\$269.95**
- 32K 4 MHz A&T \$339.00
- BAFE BOARD 39.95
- Barcode w/all parts less mem. 99.95

REPEAT OF SELL-OUT

58 Key Unencoded Keyboard **\$19.95 ea.**

This is a new 58 key terminal Keyboard manufactured by a major manufacturer. It is unencoded with SPST keys unattached to any PC board. Solid molded plastic 11" x 4" base.

Unencoded Key Pad

15 key Keypad with 1-10 keys and tab, return, (-), and (.) **\$9.95 ea.**

UV "EPROM" ERASER

Model DE-4 **\$89.95**

Holds 4 EPROM's at a time. **\$325.00**

16K Memory Expansion Kits

for Apple/TRS-80 8 pcs 4116 16K 200/250ns **\$12.95**

Specify computer CALL FOR VOLUME PRICING

CORCOM FILTER

Popular CORCOM Filter **\$4.95**

6 amps Compatible Line Cord Add. **\$3.50**

Astec RF Modulator

for COLOR & B/W P/N 1082 Channel 3 or 4 **\$6.95**

AMD MODEM IC

P/N AM7910 1200Baud 5 Volts **\$9.90**

PARALLEL ALPHA NUMERIC PRINTER

19 Column Printer prints 16 numerical columns plus 3 columns which have math, alpha and other notations. Each wheel has 12 positions with position 12 blank. Position 11 on numerical columns have decimal point or =. Utilizes 2.75" wide adding machine tape and a dual color ink ribbon. Input data parallel with four bit BCD comparator circuit (schematic provided). Print rate, 3 lines per second. Operating voltage 22-28VDC with typical cycle time of 340ms. Size 6 1/2" W x 3 1/4" H x 5 3/4" Dp. New. **\$8.95 ea. 3/\$25**

MICROPROCESSORS

Z8001	899.00	8008-1	\$14.95	6802P	14.95
Z8002	68.00	2801	9.90	8035	12.85
Z8003	9.95	2801A	14.95	8039	12.85
Z8004	11.95	9000L	49.95	8073N	34.95
F-8 (3800)	16.95	6502	9.95	8755	49.95
8050A	16.95	6502A	16.95	8756	49.95
1802	9.75	IM6100	29.95	6609	30.00
8080A	4.75	6800	11.75	8086	49.95
8085	14.95	69008	19.95	69000	129.95

RAMS

6116/2016	\$7.95	2147	\$5.99	5290	\$1.99
8264-64K	5.95	411	5.99	5298	1.49
4116-2	1.99	414	4.69	6508	4.50
4116-2	8/12.95	1101	3.99	6516	6.79
2101	3.99	1103	3.99	6851	3.79
2102	.79	4027	4.69	6804	3.59
21L02-2	1.49	4044	3.99	6606	7.79
21L02-4	1.29	4050	4.69	9130	8.99
2111	3.49	4090	4.69	9140	8.99
3212	3.49	4096	3.99	93415	6.99
2114	1.99	4115	1.49	93425	6.99
2114L-2	3.25	4200	7.95		
2114L-4	2.29	4402	1.99		
2125	6.99	5280	4.80		

CALL FOR QTY PRICING

8155	\$9.95	8259	\$8.95	68047	\$22.95
8156	9.95	8275	19.95	68488	19.95
8202	29.95	8279	9.60	46506	22.95
8205	2.69	6810	4.75	6520	6.95
8212	2.75	6820	6.50	6522	9.95
8214	4.95	6821	6.50	6530-X	24.95
8216	2.75	6828	10.50	6532	17.95
8224	2.95	6834	16.95	6551	19.95
8228	2.95	6845	22.95	Z80-PIO	6.50
8228	3.95	6847	27.95	Z80A-PIO	9.50
8243	9.50	6850	5.25	Z80-CTC	5.25
8250	14.95	6852	5.25	Z80A-CTC	9.50
8251	6.50	6860	10.95	Z80-DMA	19.95
8253	11.95	6862	10.95	Z80A-DMA	27.95
8255	4.50	6875	5.95	Z80-SIO	24.95
8257	9.50	6880	2.49	Z80A-SIO	29.95

MOS PROMS

2764 (8Kx8) TS	\$69.95	2708 (450nS)	\$5.75
2732 (4Kx8) TS	12.95	2708 (600nS)	5.25
2716/2516, 5V		1702A	6.75
(2Kx8) TS	7.95	MM5203AQ	1.50
TM52716, 5V, 12V	17.95	MM5204Q	9.95
2758, 5V, (450nS)	3.50		

HI-TECH

2513-001 (5V) Upper	99.50	DA208	99.95
2513-002 (5V) Lower	10.95	DA210	9.95
2513-ADM3 (5V) Lower	14.95	8038 Function Generator	4.50
MCMB6710 ASCII Shifted 12.95		MC4024 VCO	2.85
MCMB6740 Math Symbol 13.95		LM566 VCO	1.95
MCMB6750 Alpha Control 13.45		XR2206 Function Generator 5.25	
1771-01 8" & Miniploxy 24.95		TR1602B (5V, 12V)	3.95
1781 Dual Floppy 29.95		AY5101 (5V, 12V)	4.95
1791-01 Dual Floppy 36.95		AY5101A (1612 (5-14V))	6.95
1791-02 Dual Floppy 44.95		AY5101A (1613 (5V))	6.95
1793-01 DS Floppy 44.95		IM6403	7.95
1797 DS DS Floppy 54.95		IM6403	8.95
1691 Data Separator 18.95		1355 USBT	18.95
2143 Clock Generator 18.95		16718 Address	24.95
8700 8 bit Binary 13.50		MC14411	11.95
8703 10 bit Binary 22.00		4702	14.95
8703 8 bit TS 13.50		WD1941	16.95
9400 Volt to Freq Conv 7.25		COM5016	16.95
8750 3 1/2 Digi BCD 13.95		WS3255	13.95
1408L 8 bit 3.95		AY5-2376	13.75
1408L 8 bit 5.95		AY5-3000	13.75
DA031 D to A 5.95		MM5740AAC	8.95

SOCKETS

8 pin LP	.16	.15	.14
14 pin LP	.22	.21	.20
16 pin LP	.22	.21	.20
18 pin LP	.29	.28	.27
20 pin LP	.34	.32	.30
22 pin LP	.29	.27	.24
24 pin LP	.32	.31	.30
28 pin LP	.45	.44	.43
40 pin LP	.60	.59	.58

LOW PROFILE SOCKETS (TIN)

1-24	25-49	50-100	
8 pin WW	.55	.54	.49
10 pin WW (Tin)	.65	.63	.58
14 pin WW	.75	.73	.67
16 pin WW	.80	.77	.70
18 pin WW	.95	.90	.81
20 pin WW	1.15	1.08	.99
22 pin WW	1.45	1.35	1.23
24 pin WW	1.25	1.20	1.11
28 pin WW	1.60	1.53	1.38
40 pin WW	2.20	2.09	1.89

3L WIREWRAP SOCKETS (GOLD)

8 pin WW	.55	.54	.49
10 pin WW (Tin)	.65	.63	.58
14 pin WW	.75	.73	.67
16 pin WW	.80	.77	.70
18 pin WW	.95	.90	.81
20 pin WW	1.15	1.08	.99
22 pin WW	1.45	1.35	1.23
24 pin WW	1.25	1.20	1.11
28 pin WW	1.60	1.53	1.38
40 pin WW	2.20	2.09	1.89

CONNECTORS

DB25P (RS232)	\$3.25
DB25S Female Hood	3.75
Set with Hood, Sale	7.50
22/44 S/T, KIM	2.95
43/86 S/T, MOT	6.95
50/100 S-100 Connector W/W	4.50
50/100 S-100 Connector S/T	3.95

SUPER IC CLOSEOUT SPECIALS

14411	\$7.95	6571A	\$6.95	8080A CPU	\$2.95	5027 CRT	\$9.95	
74LS688	3/1.99	SIG 2B52	3.95	2102 RAM	.75	2901	3.95	
74LS377	2/1.99	8253	6.95	4080 RAM	1.40	8039	3.95	
74LS241	2/1.99	2758 EPROM	2.95	2732	.72	6.95	MM6320	5.99
8259	6.95	1800	6.95	UPD411	2.75	2.91	RAM	1.99
6561 RAM	2.95	Z80A CPU	4.95	UPD411	2.98	EMMA402	1.99	
LM733CN	3/1.99	6522	6.95	2708 EPROM	8/29.95	10415	4.95	
LM323K	3.95	6502 CPU	5.95	2114	8/14.50	8700 A/D	2/16.95	

TOLL FREE 800-854-8230

Mail Order: P.O. Box 17329 Irvine, CA 92713
Retail: 1310B E. Edinger, Santa Ana CA 92705 (714) 558-8813
542 W. Trimbale, San Jose, CA 95131 (408) 946-7010

LINEAR

78H06K	\$5.95	LM1414N	\$1.90
78M06	1.49	LM1458CN	.49
78L06	1.49	LM1458N	.49
LM108AH	2.95	MC1489N	.99
LM300H	.99	LM1496N	.89
LM301CN	.35	LM1558N	1.50
LM304H	1.98	LM1820N	.95
LM305H	1.99	LM1820N	.95
LM306H	3.29	LM1889N	3.10
LM307CN	.29	LM2111N	.75
LM308CN	.98	LM2900N	.99
LM309K	1.49	LM2901N	2.50
LM310CN	1.25	LM2917N	2.95
LM312H	.89	PC5014T	2.19
LM317T	1.70	CA3018T	1.99
LM318CN	1.49	CA3021T	3.49
LM318H	1.25	CA3023T	2.99
LM320K-XX*	1.35	CA3035T	2.75
LM320T-XX*	1.35	CA3039T	1.29
LM320H-XX*	1.25	CA3046N	1.29
LM323K	4.95	LM3053N	1.49
LM324N	.95	CA3069N	3.19
LM337K	5.95	CA3069N	3.19
LM337N	6.95	CA3062N	4.95
LM339N	.95	CA3065N	4.95
LM340K-XX*	1.75	CA3080T	1.29
LM340H-XX*	1.25	CA3081N	1.69
LM340H-XX*	1.25	CA3082N	1.69
LM348N	1.95	CA3083N	1.55
LM350K	5.60	CA3089N	2.99
LM358CN	.98	CA3096N	3.49
LM360N	1.49	CA3097N	1.99
LM372N	1.95	CA3130T	1.19
LM373N	3.75	CA3140T	1.19
LM377N	2.75	CA3160T	1.19
LM380CN/N	1.25	CA3190N	1.95
LM381N	1.79	CA3410N	.59
LM383T	1.95	MC3423N	1.49
LM386N	1.25	MC3460N	3.95
LM392N	1.40	MC3524N	3.95
LM396N	1.95	CA3800N	3.99
NE513V/T	3.75	LM3900N	.59
NE555V	.39	LM3905N	1.19
NE555N	.98	LM3909N	.98
NE568V	19.95	LM3914N	3.75
NE568H/V	1.25	LM3915N	3.95
NE568V/V	1.75	LM3916N	3.75
NE567V/H	1.50	RC4131N	2.95
NE592N	2.75	RC4138N	1.10
LM702H	1.99	RC4151N	3.70
LM703H	.29	RC4154T	4.45
LM710H/V	.75	RC4195T	5.40
LM711H/V	.39	ULN2001	1.25
LM716N	1.95	ULN2003	1.50
LM723H/V	.98	SN75450N	.59
LM733H/V	.98	SN75451N	.49
LM739N	1.15	SN75452N	.49
LM741CN/H	.33	SN75453N	.49
LM741CN-14	.19	SN75454N	.49
LM747H/V	.39	SN75491N	.89
LM748H/V	.75	SN75492N	.89
LM753H/V	2.95	SN75493N	.89
LM1310N	1.90	SN75494N	.89
MC1330	1.95	TL494CN	4.20
MC1350	1.95	TL496CP	1.65
MC1358	1.75		

74S00

74S00	\$.39	74S124	3.69	74S244	\$2.99
74S02	.43	74S133	5.14	74S251	1.35
74S03	.45	74S134	.66	74S263	1.35
74S05	.52	74S135	1.15	74S267	1.29
74S06	.52	74S137	4.65	74S275	1.29
74S08	.49	74S138	1.29	74S280	.75
74S09	.49	74S139	1.29	74S280	.75
74S10	.42	74S140	.73	74S287	2.99
74S11	.42	74S151	1.29	74S288	2.55
74S12	.4				

4164

64K DYNAMIC
200 NS

\$595

TMM2016

2KX8 STATIC
200 NS

\$415

STATIC RAMS

2101	256 x 4 (450ns)	1.95
5101	256 x 4 (450ns) (cmos)	3.95
2102-1	1024 x 1 (450ns)	.89
2102L-4	1024 x 1 (450ns) (LP)	.99
2102L-2	1024 x 1 (250ns) (LP)	1.49
2111	256 x 4 (450ns)	2.49
2112	256 x 4 (450ns)	2.99
2114	1024 x 4 (450ns)	8/9.95
2114L-4	1024 x 4 (450ns) (LP)	8/12.95
2114L-3	1024 x 4 (300ns) (LP)	8/13.45
2114L-2	1024 x 4 (200ns) (LP)	8/13.95
2147	4096 x 1 (55ns)	4.95
TMS4044-4	4096 x 1 (450ns)	3.49
TMS4044-3	4096 x 1 (300ns)	3.99
TMS4044-2	4096 x 1 (200ns)	4.49
MK4118	1024 x 8 (250ns)	9.95
TMM2016-200	2048 x 8 (200ns)	4.15
TMM2016-150	2048 x 8 (150ns)	4.95
TMM2016-100	2048 x 8 (100ns)	6.15
HM6116-4	2048 x 8 (200ns) (cmos)	4.75
HM6116-3	2048 x 8 (150ns) (cmos)	4.95
HM6116-2	2048 x 8 (120ns) (cmos)	8.95
HM6116LP-4	2048 x 8 (200ns) (cmos)(LP)	5.95
HM6116LP-3	2048 x 8 (150ns) (cmos)(LP)	6.95
HM6116LP-2	2048 x 8 (120ns) (cmos)(LP)	10.95
Z-6132	4096 x 8 (300ns) (Qstat)	34.95

LP - Low Power Qstat - Quasi-Static

DYNAMIC RAMS

TMS4027	4096 x 1 (250ns)	1.99
UPD411	4096 x 1 (300ns)	3.00
MMS280	4096 x 1 (300ns)	3.00
MK4108	8192 x 1 (200ns)	1.95
MMS298	8192 x 1 (250ns)	1.85
4116-300	16384 x 1 (300ns)	8/11.75
4116-250	16384 x 1 (250ns)	8/11.95
4116-200	16384 x 1 (200ns)	8/12.95
4116-150	16384 x 1 (150ns)	8/14.95
4116-120	16384 x 1 (120ns)	8/29.95
2118	16384 x 1 (150ns) (5v)	4.95
4164-200	65536 x 1 (200ns) (5v)	5.95
4164-150	65536 x 1 (150ns) (5v)	6.95

5V - single 5 volt supply

EPROMS

1702	256 x 8 (1us)	4.50
2708	1024 x 8 (450ns)	3.95
2758	1024 x 8 (450ns) (5v)	5.95
2716	2048 x 8 (450ns) (5v)	3.95
2716-1	2048 x 8 (350ns) (5v)	5.95
TMS2516	2048 x 8 (450ns) (5v)	5.50
TMS2716	2048 x 8 (450ns)	7.95
TMS2532	4096 x 8 (450ns) (5v)	5.95
2732	4096 x 8 (450ns) (5v)	4.95
2732-250	4096 x 8 (250ns) (5v)	8.95
2732-200	4096 x 8 (200ns) (5v)	11.95
2764	8192 x 8 (450ns) (5v)	9.95
2764-250	8192 x 8 (250ns) (5v)	14.95
2764-200	8192 x 8 (200ns) (5v)	24.95
TMS2564	8192 x 8 (450ns) (5v)	17.95
MC68764	8192 x 8 (450ns) (5v) (24 pin)	39.95

5v Single 5 Volt Supply

EPROM ERASERS

	Timer	Capacity Chip	Intensity (uW/Cm ²)	
PE-14		6	5,200	83.00
PE-14T	X	6	5,200	119.00
PE-24T	X	9	6,700	175.00
PL-265T	X	20	6,700	255.00
PR-125T	X	16	15,000	349.00
PR-320	X	32	15,000	595.00

Z-80

2.5 Mhz

Z80-CPU	3.95
Z80-CTC	4.49
Z80-DART	10.95
Z80-DMA	14.95
Z80-PIO	4.49
Z80-SIO/0	16.95
Z80-SIO/1	16.95
Z80-SIO/2	16.95
Z80-SIO/9	16.95

4.0 Mhz

Z80A-CPU	4.95
Z80A-CTC	4.95
Z80A-DART	11.95
Z80A-DMA	16.95
Z80A-PIO	4.95
Z80A-SIO/0	16.95
Z80A-SIO/1	16.95
Z80A-SIO/2	16.95
Z80A-SIO/9	16.95

6.0 Mhz

Z80B-CPU	11.95
Z80B-CTC	13.95
Z80B-PIO	13.95
Z80B-DART	19.95

ZILOG

Z6132	34.95
Z8671	39.95

CRYSTALS

32.768 khz	1.95
1.0 mhz	4.95
1.8432	4.95
2.0	3.95
2.097152	3.95
2.4576	3.95
3.2768	3.95
3.579535	3.95
4.0	3.95
5.0	3.95
5.0688	3.95
5.185	3.95
5.7143	3.95
6.0	3.95
6.144	3.95
6.5536	3.95
8.0	3.95
10.0	3.95
10.738635	3.95
14.31818	3.95
15.0	3.95
16.0	3.95
17.430	3.95
18.0	3.95
18.432	3.95
20.0	3.95
22.1184	3.95
32.0	3.95

CRT CONTROLLERS

6845	14.95
68B45	19.95
HD46505SP	15.95
6847	11.95
MC1372	6.95
68047	24.95
8275	29.95
7220	99.95
CRT5027	39.95
CRT5037	49.95
TMS9918A	39.95
DP8350	49.95

KEYBOARD CHIPS

AY5-2376	11.95
AY5-3600	11.95

8000

8035	5.95
8039	6.95
INS-8060	17.95
INS-8073	24.95
8080	3.95
8085	5.95
8085A-2	11.95
8086	29.95
8087	CALL
8088	39.95
8089	89.95
8155	6.95
8155-2	7.95
8156	6.95
8185	29.95
8185-2	39.95
8741	39.95
8748	24.95
8755	24.95

8200

8202	24.95
8203	39.95
8205	3.50
8212	1.80
8214	3.85
8216	1.75
8224	2.25
8226	1.80
8228	3.49
8231	call
8237	19.95
8237-5	21.95
8238	4.49
8243	4.45
8250	10.95
8251	4.49
8253	6.95
8253-5	7.95
8255	4.49
8255-5	5.25
8257	7.95
8257-5	8.95
8259	6.90
8259-5	7.50
8271	39.95
8272	39.95
8275	29.95
8279	8.95
8279-5	10.00
8282	6.50
8283	6.50
8284	5.50
8286	6.50
8287	6.50
8288	25.00
8289	49.95

DISC CONTROLLERS

1771	16.95
1791	24.95
1793	26.95
1795	49.95
1797	49.95
2791	54.95
2793	54.95
2795	59.95
2797	59.95
6843	34.95
8272	39.95
UPD765	39.95
1691	17.95
2143	18.95

CONNECTORS

RS232 MALE	2.50
RS232 FEMALE	3.25
RS232 HOOD	1.25
S-100 ST	3.95

6800

68000	59.95
6800	3.95
6802	7.95
6808	13.90
6809E	19.95
6809	11.95
6810	2.95
6820	4.35
6821	3.25
6828	14.95
6840	12.95
6843	34.95
6844	25.95
6845	14.95
6847	11.95
6850	3.25
6852	5.75
6860	9.95
6862	11.95
6875	6.95
6880	2.25
6883	22.95
68047	24.95
68488	19.95

6500

1 MHZ	
6502	4.95
6504	6.95
6505	8.95
6507	9.95
6520	4.35
6522	7.95
6532	9.95
6545	22.50
6551	11.85
2 MHZ	
6502A	6.95
6522A	9.95
6532A	11.95
6545A	27.95
6551A	11.95
3 MHZ	
6502B	14.95

UARTS

AY3-1014	6.95
AY5-1013	3.95
AY3-1015	6.95
PT1472	9.95
TR1602	3.95
2350	9.95
2651	8.95
TMS6011	5.95
IM6402	7.95
IM6403	8.95
INS8250	10.95

GENERATORS BIT-RATE

MC14411	11.95
BR1941	11.95
4702	12.95
COM5016	16.95
COM8116	10.95
MM5307	10.95

FUNCTION

MC4024	3.95
LM566	1.49
XR2206	3.75
8038	3.95

74LS00

74LS00	.24	74LS173	.69
74LS01	.25	74LS174	.55
74LS02	.25	74LS175	.55
74LS03	.25	74LS181	2.15
74LS04	.24	74LS189	8.95
74LS05	.25	74LS190	.89
74LS08	.28	74LS191	.89
74LS09	.29	74LS192	.79
74LS10	.25	74LS193	.79
74LS11	.35	74LS194	.69
74LS12	.35	74LS195	.69
74LS13	.45	74LS196	.79
74LS14	.59	74LS197	.79
74LS15	.35	74LS221	.89
74LS20	.25	74LS240	.95
74LS21	.29	74LS241	.99
74LS22	.25	74LS242	.99
74LS26	.29	74LS243	.99
74LS27	.29	74LS244	.99
74LS28	.35	74LS245	1.49
74LS30	.25	74LS247	.75
74LS32	.29	74LS248	.99
74LS33	.55	74LS249	.99
74LS37	.35	74LS251	.59
74LS38	.35	74LS253	.59
74LS40	.25	74LS257	.59
74LS42	.49	74LS258	.59
74LS47	.75	74LS259	2.75
74LS48	.75	74LS260	.59
74LS49	.75	74LS266	.55
74LS51	.25	74LS273	1.49
74LS54	.29	74LS275	3.35
74LS55	.29	74LS279	.49
74LS63	1.25	74LS280	1.98
74LS73	.39	74LS283	.69
74LS74	.35	74LS290	.89
74LS75	.39	74LS293	.89
74LS76	.39	74LS295	.99
74LS78	.49	74LS298	.89
74LS83	.60	74LS299	1.75
74LS85	.69	74LS323	3.50
74LS86	.39	74LS324	1.75
74LS90	.55	74LS352	1.29
74LS91	.89	74LS353	1.29
74LS92	.55	74LS363	1.35
74LS93	.55	74LS364	1.95
74LS95	.75	74LS365	.49
74LS96	.89	74LS366	.49
74LS107	.39	74LS367	.45
74LS109	.39	74LS368	.45
74LS112	.39	74LS373	.99
74LS113	.39	74LS374	.99
74LS114	.39	74LS377	1.39
74LS122	.45	74LS378	1.18
74LS123	.79	74LS379	1.35
74LS124	2.90	74LS385	1.90
74LS125	.49	74LS386	.45
74LS126	.49	74LS390	1.19
74LS132	.59	74LS393	1.19
74LS133	.59	74LS395	1.19
74LS136	.39	74LS399	1.49
74LS137	.99	74LS424	2.95
74LS138	.55	74LS447	

2114

450 NS

8/\$995

2114

250 NS

8/\$1095

7400

7400	.19	74132	.45
7401	.19	74136	.50
7402	.19	74141	.65
7403	.19	74142	2.95
7404	.19	74143	2.95
7405	.25	74145	.60
7406	.29	74147	1.75
7407	.29	74148	1.20
7408	.24	74150	1.35
7409	.19	74151	.55
7410	.19	74152	.65
7411	.25	74153	.55
7412	.30	74154	1.25
7413	.35	74155	.75
7414	.49	74156	.65
7416	.25	74157	.55
7417	.25	74159	1.65
7420	.19	74160	.85
7421	.35	74161	.69
7422	.35	74162	.85
7423	.29	74163	.69
7425	.29	74164	.85
7426	.29	74165	.85
7427	.29	74166	1.00
7428	.45	74167	2.95
7430	.19	74170	1.65
7432	.29	74172	5.95
7433	.45	74173	.75
7437	.29	74174	.89
7438	.29	74175	.89
7440	.19	74176	.89
7442	.49	74177	.75
7443	.65	74178	1.15
7444	.69	74179	1.75
7445	.69	74180	.75
7446	.69	74181	2.25
7447	.69	74182	.75
7448	.69	74184	2.00
7450	.19	74185	2.00
7451	.23	74190	1.15
7453	.23	74191	1.15
7454	.23	74192	.79
7460	.23	74193	.79
7470	.35	74194	.85
7472	.29	74195	.85
7473	.34	74196	.79
7474	.33	74197	.75
7475	.45	74198	1.35
7476	.35	74199	1.35
7480	.59	74221	1.35
7481	1.10	74246	1.35
7482	.95	74247	1.25
7483	.50	74248	1.85
7485	.59	74249	1.95
7486	.35	74251	.75
7489	2.15	74259	2.25
7490	.35	74265	1.35
7491	.40	74273	1.95
7492	.50	74276	1.25
7493	.35	74279	.75
7494	.65	74283	2.00
7495	.55	74284	3.75
7496	.70	74285	3.75
7497	2.75	74290	.95
74100	1.75	74293	.75
74107	.30	74298	.85
74109	.45	74351	2.25
74110	.45	74365	.65
74111	.55	74366	.65
74116	1.55	74367	.85
74120	1.20	74368	.85
74121	.29	74376	2.20
74122	.45	74390	1.75
74123	.49	74393	1.35
74125	.45	74425	3.15
74126	.45	74426	.85
74128	.55	74490	2.55

LINEAR

LM301	.34	LM340 (see 7800)	
LM301H	.79	LM348	.99
LM307	.45	LM350K	4.95
LM308	.69	LM350T	4.60
LM308H	1.15	LM358	.69
LM309H	1.95	LM359	1.79
LM309K	1.25	LM376	3.75
LM310	1.75	LM377	1.95
LM311	.64	LM378	2.50
LM311H	.89	LM379	4.50
LM312H	1.75	LM380	.89
LM317K	3.95	LM380N-8	1.10
LM317T	1.19	LM381	1.60
LM318	1.49	LM382	1.60
LM318H	1.59	LM383	1.95
LM319H	1.90	LM384	1.95
LM319	1.25	LM386	.89
LM320 (see 7900)		LM387	1.40
LM322	1.65	LM389	1.35
LM323K	4.95	LM390	1.95
LM324	.59	LM392	.69
LM329	.65	LM394H	4.60
LM331	3.95	LM399H	5.00
LM334	1.19	NE531	2.95
LM335	1.40	NE555	.34
LM336	1.75	NE556	.65
LM337K	3.95	NE558	1.50
LM337T	1.95	NE561	24.95
LM338K	6.95	NE564	2.95
LM339	.99	LM565	.99

H = TO-5 CAN

T = TO-220

K = TO-3

LM566

LM566	1.49	LM1800	2.37
LM567	.89	LM1812	8.25
NE570	3.95	LM1830	3.50
NE571	2.95	LM1871	5.49
NE592	2.75	LM1872	5.49
LM709	.59	LM1877	3.25
LM710	.75	LM1889	1.95
LM711	.79	LM1896	1.75
LM723	.49	LM2003	2.49
LM723H	.55	LM2877	2.05
LM733	.98	LM2878	2.25
LM741	.35	LM2900	.85
LM741N-14	.35	LM2901	1.00
LM741H	.40	LM3900	.59
LM747	.69	LM3905	1.25
LM748	.59	LM3909	.98
LM1014	1.19	LM3911	2.25
LM1303	1.95	LM3914	3.95
LM1310	1.49	LM3915	3.95
MC1330	1.69	LM3916	3.95
MC1349	1.89	MC4024	3.95
MC1350	1.19	MC4044	4.50
MC1358	1.69	RC4136	1.25
MC1372	6.95	RC4151	3.95
LM1414	1.59	LM4250	1.75
LM1458	.59	LM4500	3.25
LM1488	.69	RC4558	.69
LM1489	.69	LM13080	1.29
LM1496	.85	LM13600	1.49
LM1558H	3.10	LM13700	1.49

RCA

CA 3023	2.75	CA 3082	1.65
CA 3039	1.29	CA 3083	1.55
CA 3046	1.25	CA 3086	.80
CA 3059	2.90	CA 3089	2.99
CA 3060	2.90	CA 3096	3.49
CA 3065	1.75	CA 3130	1.30
CA 3080	1.10	CA 3140	1.15
CA 3081	1.65	CA 3146	1.85
CA 3160	1.19		

TI

TL494	4.20	75365	1.95
TL496	1.65	75450	.59
TL497	3.25	75451	.39
75107	1.49	75452	.39
75110	1.95	75453	.39
75150	1.95	75454	.39
75154	1.95	75491	.79
75188	1.25	75492	.79
75189	1.25	75493	.89
75494	.89		

BI FET

TL071	.79	TL084	2.19
TL072	1.19	LF347	2.19
TL074	2.19	LF351	.60
TL081	.79	LF353	1.00
TL082	1.19	LF355	1.10
TL083	1.19	LF356	1.10
LF357	1.40		

CMOS

4000	.29	4527	1.95
4001	.25	4528	1.19
4002	.25	4531	.95
4006	.89	4532	1.95
4007	.29	4538	1.95
4008	.95	4539	1.95
4009	.39	4541	2.64
4010	.45	4543	1.19
4011	.25	4553	5.79
4012	.25	4555	.95
4013	.38	4556	.95
4014	.79	4581	1.95
4015	.39	4582	1.95
4016	.39	4584	.75
4017	.69	4585	.75
4018	.79	4702	12.95
4019	.39	74C00	.35
4020	.75	74C02	.35
4021	.79	74C04	.35
4022	.79	74C08	.35
4023	.29	74C10	.35
4024	.65	74C14	.59
4025	.29	74C20	.35
4026	1.65	74C30	.35
4027	.45	74C32	.39
4028	.69	74C42	1.29
4029	.79	74C48	1.99
4030	.39	74C73	.65
4034	1.95	74C74	.65
4035	.85	74C76	.80
4040	.75	74C83	1.95
4041	.75	74C85	1.95
4042	.69	74C86	.39
4043	.85	74C89	4.50
4044	.79	74C90	1.19
4046	.85	74C93	1.75
4047	.95	74C95	.99
4049	.35	74C107	.89
4050	.35	74C150	5.75
4051	.79	74C151	2.25
4053	.79	74C154	3.25
4060	.89	74C157	1.75
4066	.39	74C160	1.19
4068	.39	74C161	1.19
4069	.29	74C162	1.19
4070	.35	74C163	1.19
4071	.29	74C164	1.39
4072	.29	74C165	2.00
4073	.29	74C173	.79
4075	.29	74C174	1.19
4076	.79	74C175	1.19
4078	.29	74C192	1.49
4081	.29	74C193	1.49
4082	.29	74C195	1.39
4085	.95	74C200	5.75
4086	.95	74C221	1.75
4093	.49	74C373	2.45
4098	2.49	74C374	2.45
4099	1.95	74C901	.85
14409	12.95	74C902	.85
14410	12.95	74C903	.85
14411	11.95	74C905	10.95
14412	12.95	74C906	.95
14419	7.95	74C907	1.00
14433	4.18	74C908	2.00
4502	.95	74C909	2.75
4503	.65	74C910	9.95
4508	1.95	74C911	8.95
4510	.85	74C912	8.95
4511	.85	74C914	1.95
4512	.85	74C915	1.19
4514	1.25	74C918	2.75
4515	1.79	74C920	17.95
4516	1.55	74C921	15.95
4518	.89	74C922	4.49
4519	.39	74C923	4.95
4520	.79	74C925	5.95
4522	1.25	74C926	7.95
4526	1.25	74C928	7.95
		74C929	19.95

74S00

74S00	.32	74S163	1.95
74S02	.35	74S168	3.95
74S03	.35	74S169	3.95
74S04	.35	74S174	.95
74S05	.35	74S175	.95
74S08	.35	74S181	3.95
74S09	.40	74S182	2.95
74S10	.35	74S188	1.95
74S11	.35	74S189	6.95
74S15	.35	74S194	1.49
74S20	.35	74S195	1.49
74S22	.35	74S196	1.49
74S30	.35	74S197	1.49
74S32	.40	74S201	6.95
74S37	.88	74S225	7.95
74S38	.85	74S240	2.20
74S40	.35	74S241	2.20
74S51	.35	74S244	2.20
74S64	.40	74S251	.95
74S65	.40	74S253	.95
74S74	.50	74S257	.95
74S85	1.99	74S258	.95
74S86	.50	74S260	.79
74S112	.50	74S274	19.95
74S113	.50	74S275	19.95
74S114	.55	74S280	1.95
74S124	2.75	74S287	1.90
74S132	1.24	74S288	1.90
74S133	.45	74S289	6.89
74S134	.50	74S301	6.95
74S135	.89	74S373	2.45
74S138	.85	74S374	2.45
74S139	.85	74S381	7.95
74S140	.55	74S387	1.95
74S151	.95	74S412	2.98
74S153	.95	74S471	4.95
74S157	.95	74S472	4.95
74S158	.95	74S474	4.95
74S161	1.95		

CABINETS FOR 5 1/4" DISK DRIVES

CABINET #1 \$29.95

- * DIMENSIONS 8 1/2" x 5 1/4" x 3 1/4"
- * COLOR MATCHES APPLE
- * FITS STANDARD 5 1/4" DRIVES, INCL. SHUGART
- * INCLUDES MOUNTING HARDWARE AND FEET

CABINET #2 \$79.00

- * COMPLETE WITH POWER SUPPLY, SWITCH, LINE CORD, FUSE & STANDARD POWER CONNECTOR
 - * DIMENSIONS: 11 1/2" x 5 1/4" x 3 1/4"
 - * +5V @ 1 AMP, +12V @ 1.5 AMP
 - * FITS STANDARD 5 1/4" DRIVES
 - * PLEASE SPECIFY GRAY OR TAN
- NOTE: Please include sufficient amount for shipping on above items.

CONNECTORS

RS232 MALE	2.50
RS232 FEMALE	3.25
RIGHT ANGLE	5.25
RS232 HOOD	1.25
S-100 ST	3.95
S-100 WW	4.95
44 pin ST	2.95
44 pin WW	4.95
72 pin ST	6.95
72 pin WW	7.95

SWITCHES

SPDT mini-toggle	1.25
DPDT mini-toggle	1.50
SPDT push-button	1.49

OPTO-ISOLATORS

MCA-7	1.50
MCA-255	1.75
IL-1	1.25
ILA-30	1.25
ILQ-74	2.75
H11C5	1.25
TIL-111	1.00
TIL-113	1.75
4N26	1.00
4N27	1.10
4N28	.69
4N33	1.75
4N35	1.25
4N37	1.25
MCT-2	1.00
MCT-6	1.50

TRANSISTORS

2N918	.50	2N3772	1.85
MPS918	.25	2N3903	.25
2N2102	.50	2N3904	.10
2N2218	.50	2N3906	.10
2N2218A	.50	2N4122	.25
2N2219	.50	2N4123	.25
2N2219A	.50	2N4249	.25
2N2222	.25	2N4304	.75
PN2222	.10	2N4401	.25
MPS2369	.25	2N4402	.25
2N2484	.25	2N4403	.25
2N2905	.50	2N4857	1.00
2N2907	.25	PN4916	.25
PN2907	.125	2N5086	.25
2N3055	.79	PN5129	.25
3055T	.69	PN5139	.25
2N3393	.30	2N5209	.25
2N3414	.25	2N6028	.35
2N3563	.40	2N6043	1.75
2N3565	.40	2N6045	1.75
PN3565	.25	MPS-A05	.25
MPS3638	.25	MPS-A06	.25
MPS3640	.25	MPS-A55	.25
PN3643	.25	TIP29	.65
PN3644	.25	TIP31	.75
MPS3704	.15	TIP32	.79
MPS3706	.15		

MICROCOMPUTER HARDWARE HANDBOOK FROM ELCOMP — \$14.95

Over 800 pages of manufacturers data sheets on most commonly used IC's.

- Includes:
- * TTL — 74/74LS and 74F
 - * CMOS
 - * Voltage Regulators
 - * Memory — RAM, ROM, EPROM
 - * CPU's — 6800, 6500, Z80, 8080, 8085, 8086/8
 - * MPU support & interface — 6800, 6500, Z80, 8200, etc.

HEAT SINKS

TO-3 style	.95
TO-220 style	.35

DISK DRIVES

TANDON

TM100-1 5 1/4" (FOR IBM) SS/DD 229.00

TM100-2 5 1/4" (FOR IBM) DS/DD 295.00

SHUGART

SA 400L 5 1/4" (40 TRACK) SS/DD 199.95

SA 400 5 1/4" (35 TRACK) SS/DD 189.95

SIEMENS

FD100-8 8" SS/DD (801 REPLACEMENT) 259.00

PERTEC

FD-200 5 1/4" SS/DD 179.95

FD-250 5 1/4" DS/DD 199.95

MPI

MP-52 5 1/4" (FOR IBM) DS/DD 295.00

RESISTORS

1/4 WATT 5% CARBON FILM ALL STANDARD VALUES FROM 1 OHM TO 10 MEG OHM

50 PCS. SAME VALUE	.025
100 PCS. SAME VALUE	.02
1000 PCS. SAME VALUE	.015

BYPASS CAPS

.01 UF DISC	100/6.00
.1 UF DISC	100/8.00
.1 UF MONOLITHIC	100/15.00

WE HAVE THE COMPLETE LINE OF DISC, TANTALUM AND ELECTROLYTIC CAPACITORS IN STOCK!

POWER SUPPLY

MODEL 2 \$39⁹⁵

MOUNTED ON PC BOARD MANUFACTURED BY CONVER

+5 VOLT 4 AMP

±12 VOLT 1 AMP

NOTE: Please include sufficient amount for shipping on above items.

DIODES

1N751	5.1 volt zener	.25
1N759	12.0 volt zener	.25
1N4148	(1N914) switching	25/1.00
1N4004	400PIV rectifier	10/1.00
KBP02	200PIV 1.5amp bridge	.45
KBP04	400PIV 1.5amp bridge	.55

D-SUBMINIATURE

DESCRIPTION	SOLDER		RIGHT ANGLE SOLDER		RIBBON CABLE		HOODS	
	MALE	FEMALE	MALE	FEMALE	MALE	FEMALE	BLACK HOOD-B	GREY HOOD
ORDER BY	DBxxP	DBxxS	DBxxPR	DBxxSR	IDBxxP	IDBxxS		
CONTACTS 9	2.08	2.66	1.65	2.18	3.37	3.69	---	1.60
15	2.69	3.63	2.20	3.03	4.70	5.13	---	1.60
25	2.50	3.25	3.00	4.42	6.23	6.84	1.25	1.25
37	4.80	7.11	4.83	6.19	9.22	10.08	---	2.95
50	6.06	9.24	---	---	---	---	---	3.50

For order instructions see "IDC Connectors" below.

RIBBON CABLE

CONTACTS	SINGLE COLOR		COLOR CODED	
	1'	10'	1'	10'
10	.50	4.40	.83	7.30
20	.65	5.70	1.25	11.00
26	.75	6.60	1.32	11.60
34	.98	8.60	1.65	14.50
40	1.32	11.60	1.92	16.80
50	1.38	12.10	2.50	22.00

IDC CONNECTORS


DESCRIPTION	SOLDER HEADER	RIGHT ANGLE SOLDER HEADER	WW HEADER	RIGHT ANGLE WW HEADER	RIBBON HEADER SOCKET	RIBBON HEADER	RIBBON EDGE CARD
ORDER BY	IDHxxS	IDHxxSR	IDHxxW	IDHxxWR	IDSxx	IDMxx	IDExx
CONTACTS 10	.82	.85	1.86	2.05	1.15	---	2.25
20	1.29	1.35	2.98	3.28	1.86	5.50	2.36
26	1.68	1.76	3.84	4.22	2.43	6.25	2.65
34	2.20	2.31	4.50	4.45	3.15	7.00	3.25
40	2.58	2.72	5.28	4.80	3.73	7.50	3.80
50	3.24	3.39	6.63	7.30	4.65	8.50	4.74

ORDERING INSTRUCTIONS: Insert the number of contacts in the position marked "xx" of the "order by" part number listed. Example: A 10 pin right angle solder style header would be IDH10SR.

VISIT OUR RETAIL STORE

HOURS: M-W-F, 9-5 T-Th., 9-9 Sat. 11-3

PLEASE USE YOUR CUSTOMER NUMBER WHEN ORDERING
 TERMS: For shipping include \$2 for UPS Ground or \$3 for UPS Blue Label Air. Items over 5 pounds require additional shipping charges. Foreign orders, include sufficient amount for shipping. There is a \$10 minimum order. Bay Area and Los Angeles Counties add 6 1/2% Sales Tax. Other California residents add 6% Sales Tax. We reserve the right to substitute manufacturer. Not responsible for typographical errors. Prices are subject to change without notice. We will match or beat any competitor's price provided it is not below our cost.

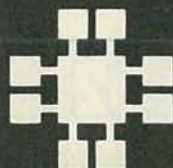

JDR Microdevices

1224 S. Bascom Ave. • San Jose, CA 95128

(408) 995-5430 • Telex 171-110

© 1983 JDR MICRODEVICES, INC.

CIRCLE 49 ON FREE INFORMATION CARD

SPRING APPLE SALE!

FD-35 DISK DRIVE

By MA Systems

- ★ Direct Replacement for Apple Disk II
- ★ Compatible with Apple Controller or other Apple compatible controllers
- ★ Specially designed electronics with **low power consumption**
- ★ DOS 3.3 and 3.2 compatible
- ★ Owner's Manual and Warranty Card included
- ★ 90-day Warranty

NEW INTRODUCTORY OFFER **\$229⁹⁵**
CONTROLLER CARD \$89.95

NEW IMPROVED JDR COOLING FAN FOR YOUR APPLE II

- ★ Easy modification — no modification of Apple required
- ★ Eliminates overheating problems
- ★ Switch on front controls fan, Apple, and extra outlet
- ★ Rotron whisper fan is the quietest, most reliable on the market

NOW WITH SURGE SUPPRESSION
\$69.95

WITHOUT SURGE SUPPRESSION \$59.95

JDR 16K RAMCARD

For Apple II*

- ★ Expand your 48K Apple to 64K
- ★ Fully compatible with Apple Language System — Use in place of Apple Language card
- ★ Provides extra memory for Visicalc™
- ★ Run PASCAL, FORTRAN, Integer Basic with appropriate software
- ★ Highest quality card features: gold edge connector, sockets for all IC's

NOW WITH 2 YEAR WARRANTY

ASSEMBLED & TESTED WITH WARRANTY **\$44⁹⁵**
KIT — INCLUDES ALL PARTS & INSTRUCTIONS... **\$40⁹⁵**
BARE PC CARD WITH INSTRUCTIONS **\$14⁹⁵**

APPLE II KEYBOARD \$99.95

From the Keyboard Co.

- ★ Brand New Rev. 7 keyboard — NOT an imitation
- ★ Special Purchase — Supply very limited
- ★ Includes Encoder Board and Cable

APPLE COMPATIBLE POWER SUPPLY \$99.95

- ★ Compact Switching Design
- ★ All Outputs regulated
- ★ Short Circuit and Overload Protection
- ★ Complete with Apple-type plug-in power cord
- ★ Apple Compatible — Yet higher output allows more disk drives and cards without overheating
- ★ +5V @ 5A, +12V @ 3A, -5V @ .5A, -12V @ .5A
- ★ Shielded enclosure: 10 3/4" x 3 1/2" x 2 3/8"

INTERFACE CARDS

By Perisoft

PRINTERLINK \$79.00

- ★ Centronics Standard Parallel Interface for Apple II
 - ★ Simple to use — Yet supports custom driver applications from ROM or Disk
 - ★ Includes card, cable and user's manual
 - ★ 1 Year Warranty
- ### MESSENGER \$119.00
- ★ Serial I/O for Apple II
 - ★ Connects virtually any RS-232 serial device
 - ★ 6 switch selectable drivers:
 - 4 printer drivers
 - Terminal Driver — 40 or 80 driver
 - ★ Includes card, cable and user's manual
 - ★ 1 Year Warranty

MONITORS

GREEN PHOSPHOR

NEC JB1201M **\$169⁰⁰**
ZENITH ZVM-121 **\$119⁰⁰**
COLOR
AMDEK COLOR 1 **\$335⁰⁰**

IF YOU CAN FIND A PRICE LOWER ELSEWHERE, LET US KNOW AND WE WILL MEET OR BEAT THEIR PRICE! (SEE TERMS BELOW)

VIEWMAX 80

A Full Function 80 column card for Apple II*

2 YEAR WARRANTY

\$199⁹⁵

OKIDATA PRINTERS

- ★ 120 cps, 9x9 Dot Matrix
- ★ 50% faster than EPSON
- ★ Parallel and Serial interfaces are standard

ML-82A **\$479⁵⁰**

ML-83A **\$699⁹⁵**

ML-84 PARALLEL . . . **\$1059⁰⁰**

CALL FOR PRICES ON 82A TRACTOR OPTION AND 82A, 83A GRAPHICS OPTION. CABLES AND INTERFACE CARDS AVAILABLE

5 1/4" DISKETTES

ATHANA SS SD SOFT . . . **24.95**
MEMOREX SS SD SOFT **26.95**
VERBATIM SS DD SOFT **29.95**
VERBATIM 10 SECT. HARD **29.95**

NASHUA

TOP QUALITY — LOW PRICE!

Single Sided, Single Density
Soft Sected with Hub Ring

\$19.95 BOX OF 10

**ORDER TOLL FREE
ALL MERCHANDISE
100% GUARANTEED**

800-538-5000



**800-662-6279
(CALIFORNIA RESIDENTS)**

CALL US FOR VOLUME QUOTES

© 1983 JDR MICRODEVICES, INC.

* APPLE IS A TRADEMARK OF APPLE COMPUTER CO.

WHY SPEND A FORTUNE ON A DIGITAL CAPACITANCE METER?

As a matter of fact you don't have to pay \$180 to \$500 and up anymore for a Digital Capacitance Meter that is both dependable and rugged with good accuracy. The MC100A comes completely assembled and calibrated and at \$79.95 is an outstanding value. The extensive range of 30 pF to 9,999 uF (no external meters required) and true hand held portable size (only 4 1/4" x 2 1/2" x 1 1/2") make the MC100A an extremely practical and easy to use instrument for the hobbyist technician or engineer.

CHECK THESE OTHER FEATURES

- * Basic accuracy 2% (± one count) on pF, nF ranges, 5% (± one count) on uF range.
- * Uses single 9V battery (not included).
- * Decimal points light up when battery is low or when capacitor is overrange.
- * Full 4 digit high efficiency LED display uses special circuitry to save on batteries.
- * Maximum conversion time for 9,999 uF is less than 6 seconds.
- * Constructed with a tough impact resistant plastic case.
- * 90 day parts and labour warranty.



\$79.95



DAETRON
935 THE QUEENSWAY, BOX 641
TORONTO, ONTARIO M8Z 5Y9
(416) 499-7221
DEALER ENQUIRIES INVITED


PLEASE SEND ME

(Quantity) MC100A(s) @ \$79.95 U.S. (Canadian residents send \$89.95 CDN.) \$ _____
 Ontario residents add 7% PST \$ _____
 Postage — \$2.25 for U.S. \$1.85 for Canada (per instrument) \$ _____
 I ENCLOSE CHECK MONEY ORDER BILL MY VISA TOTAL \$ _____
 VISA CARD NO. _____ EXPIRY DATE _____ SIGNATURE _____
 Immediate shipping on orders with money orders or VISA.
 Personal checks please allow 2 to 3 weeks for clearance.
 NAME _____
 ADDRESS _____
 CITY _____ STATE _____ ZIP CODE _____

MAIL TO DAETRON 935 THE QUEENSWAY BOX 641
TORONTO ONTARIO M8Z 5Y9

MICROWAVE TV ANTENNA SYSTEMS

Freq. 2.1 to 2.6 GHz • 34 db Gain +

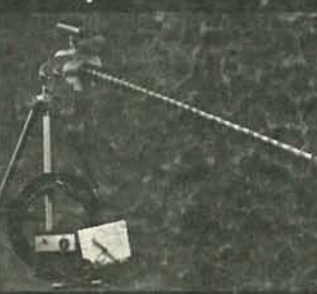


- COMPLETE SYSTEMS**
(as Pictured)
- Commercial 40" Rod Style \$109.95
 - Parabolic 20" Dish Style \$ 99.95

- COMPONENTS**
- Down Converters (both types) \$ 34.95
 - Power Supplies (12V to 16V) \$ 24.95
 - Data Info (Plans) \$ 9.95

CALL OR WRITE FOR KITS, PARTS, INDIVIDUAL COMPONENTS
 We Repair All Types Down Converters & Power Supplies

Phillips-Tech Electronics
P.O. Box 34772
Phoenix, AZ 85067
(602) 265-8255

Special Quantity Pricing Dealers Wanted

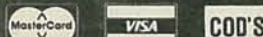

TWO YEAR WARRANTY PARTS & LABOR



RADIO-ELECTRONICS

CIRCLE 9 ON FREE INFORMATION CARD

MICRO MART

508 Central Ave.
Westfield, N.J. 07090
(201) 654-6008

UHF-TV PREAMP

(As featured in Radio Electronics March/May articles, 1982)

This inexpensive antenna mounted preamp can add more than 25 dB of gain to your system. Lots of satisfied customers and repeat orders for this high quality kit, which includes all component parts, PC Board, Case, Power Supply and Balun \$34.50 Assembled Version..... \$57.50

APPLE Heart Rate Monitor KIT-\$39.95

- 2N3055 (PRIME).....2/81
- 2N3791 (PRIME).....2/81
- 2055'S (TELETYPE 355).....3/81
- 2716 EPROM (450ns).....\$3.85
- MPS 4571 (NPN SILICON TRANS).....10/81
- "BOOT" SOLDERING IRON (20w).....\$9
- "BOOT" SOLDER SUCKER (works great).....\$12
- LM1310.....3/82
- CD4047.....2/83
- RF CHOKE 10uH 1/2W FIXED.....3/82
- LM1889.....2/84
- BNC "T" CONNECTOR.....\$1
- 20V 1W EPOXY ZENERS.....20/81
- 78L08 (5V REGULATOR).....5/81
- NOTION DETECTOR BOARDS-62 EACH.....7/81
- NOTION DETECTOR (IC ONLY) 3/82.....20/81
- CONDENSER MICROPHONE.....3/82
- 9V BATTERIES.....2/81
- 1000 PIECE RESISTOR ASSY 1/2W.....\$5
- CRYSTALS-1MHz.....\$2-3; 5MHz.....\$1/4MHz.....\$2
- 2560.0 KC.....\$1
- .22uF 50V SUB MINI EPOXY DISC.....20/81
- .33uF 100V DIP MYLAR.....8/81
- 47uF 25V MINI RADIAL.....5/81
- 4.7uF 40V MINI RADIAL.....10/81
- 6.8uF 35V SOLID TANTALUM.....2/81
- 10uF 50V DIP TANTALUM.....3/82
- 3200uF 50V TANTUM LOCK.....3/82
- 11000uF 50V (COND GRAD MALLORY).....\$2
- 1000uF 16V TWIST LOCK.....2/81
- VINYL COATED (FIBERGLASS REINFORCED) SLEEVEING-1" LENGTHS, 10 DIAMETERS.....\$3
- LED (HIGH INTENS. RED EMITTER, WATER CLEAR LENS) 10/81, 100/87.50, 1000/869
- BATTERY SNAPS.....5/81
- HEAVY DUTY ALLIGATOR CLIPS.....10/83
- LIGHTER WEIGHT CLIPS.....10/82
- 74LS174 (PRIME TEXAS INST).....2/81
- VERY LOUD BUZZER.....2/81
- SN75324 IC.....3/81

Have Some Fun...Fun...Fun! PROGRAMMABLE MESSAGES IN SPACE, with SPACE WRITER Kit \$39.50

Signalman Mark I Modem-\$99

Direct connect modem/RS-232C; Built in interface cable and connector; Light, compact, Bell 103 compatible Data/Voice switch

BMC-12A, 12" Green Phosphor Monitor \$99

- LM1391 (PRIME, HOUSE #D).....3/81
- ULN 2001 (UNTESTED).....10/81
- RS232 CONNECTOR (DB-25P-A123).....\$3
- 100K TRIMPOT.....4/81
- 10K TRIMPOT.....4/81
- SN7447.....2/81
- SN7492.....3/81
- SN95B 2-P (DTL).....5/81
- 8P 85 UHF HIGH GAIN AMPS.....2/83
- WINGARD HU420 UHF ANT, 4WAY BOWTIE#25 CONNECTOR FOR RIBBON CABLE 34 PIN.....\$2
- 9243 16 LINE I/O EXTENDER CHIP.....\$5
- 7805, 7812, 7905, 7912 MIX/MATCH.....4/85
- AM/FM RADIO IC (UNTESTED) W/SPECS 10/83
- POTS-LIN TRAP/BAND-10K, 100K, 1M.....3/82
- IC BOX (STORES 8 LABELS IC'S).....\$2
- DIP SWITCHES-4, 6, 8, 10 POB.....2/83
- TV 7 INDS.....10/81
- *****AMBEK COLORI MONITOR.....\$305*****
- Voltage-Mate (switching regulator) kit with adjustable DC/DC voltage conversion. Output voltages:-24 to +30VDC, 3 op. modes (step-up, down, inversion) -\$19
- CHIP CAPS (SET OF 4, 2EACH 2.7nF, 3pF) \$3
- FPA104 INFR-RED EMITTER/SENSOR.....\$9
- MINIATURE SPEAKER (1 1/2").....2/81
- OKIDATA, EPSON, CENTRONICS PRINTERS/TEL CONVENIENCE PAPER PAKS, CONT. ROLL TEAR AWAY RAZOR EDGE, 1K SHEETS.....\$16
- LOWEST PRICES VERBATIM DISKETTES/CALLE TEX/700L ZERO INSERTION IC TEST SOCKS-EIS- 14 PIN-\$9.....16 PIN-\$10
- 47pF 470pF 1KV DISCS (NICE SIZE) 20/81
- LM380 (ULN2280).....3/81
- UDN7180 GAS DISCHARGE DISP/DRVR.....3/85

MICRO-CONTROLLER BOARD (KIT/\$99.50)

Terms: MICRO-MART accepts Visa, MC and telephone COD's. Minimum order \$10.00. Shipping—U.S. orders, \$2.00. Canada and other countries \$3.50 (includes ins.). Shipping rate adjusted where applicable. NJ residents add 5% sales tax.

MICRO-MART • 508 CENTRAL AVE., WESTFIELD, NJ 07090 • (201) 654-6008

CIRCLE 12 ON FREE INFORMATION CARD



KCS

ELECTRONICS CORPORATION

SEMICONDUCTOR PARTS & PRODUCTS

FACTORY PRIME DEVICES INCLUDE:


- Capacitors
- all types & styles
- Chokes & Coils
- Connectors
- Digital & Linear IC's
- Hardware & Accessories
- IC Sockets
- Memory
- Microwave Semiconductors
- Resistors
- fixed & variable
- Transformers
- Transistors & MORE!

MANUFACTURERS SUCH AS: Motorola, National, NEC, J.W. Miller, Texas Instruments and more!

WE STOCK & SUPPLY DEVICES FOR: OEM's, Distributors, Hobbyists, Magazine Projects, Engineers, Schools, Technicians & You!

Call or Write for Quantity Pricing and FREE Catalog.

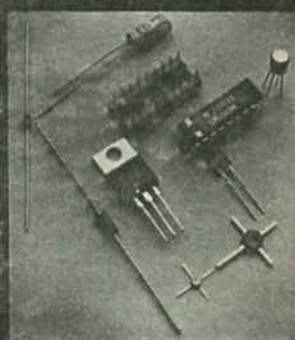P.O. Box 33205
Phoenix, AZ 85067 **(602) 274-2885**




CIRCLE 83 ON FREE INFORMATION CARD



POPULAR TELEVISION CIRCUITS

SINE WAVE SUPER BOARD

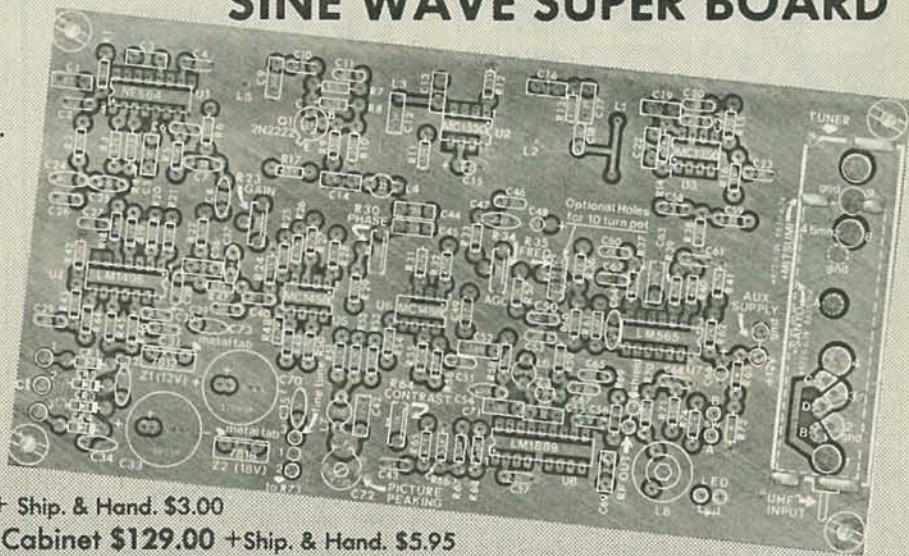- * NO Internal Connection to T.V.
- * Continuous Audio/Video Modulation
- * AGC FOR STABILITY
- * Quality Circuit Board
- * Silk Screened Parts Layout
- * Fully Illustrated Instructions
- * Quantity Discounts Available



- P.C. Board and Plans \$30.00 + Ship. & Hand. \$3.00
- All Parts, and Wood Grained Cabinet \$129.00 + Ship. & Hand. \$5.95
- P.C. Board, Plans, All Parts and Wood Grained Cabinet \$149.00 + Ship. & Hand. \$5.95

ZENITH M1

09-151-03




- * No Internal Connection to T.V.
- * Continuous Audio/Video Modulation
- * AGC FOR STABILITY
- * Quality Circuit Board
- * Fully Illustrated Instructions
- * Quantity Discounts Available

- FV-5 Board and Plans \$30.00 + Shipping and Handling \$3.00
- All Parts, Wood Grain Cabinet \$149.95 + Shipping & Handling \$6.95
- P.C. Board, Plans, All Parts, Wood Grain Cabinet \$169.95 + Shipping & Handling \$6.85

FV-5

Phase Video/Sync. Suppression

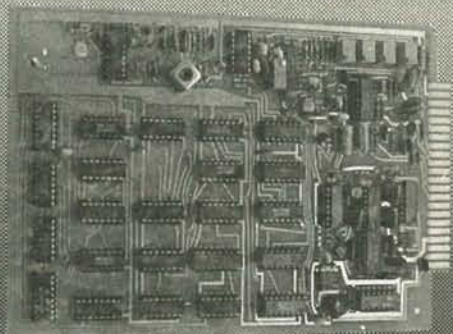

MICROWAVE PROBE KIT

P.C. Board, Microwave Transistors, All Parts and Plastic Housing

Complete \$24.95 + Shipping & Handling \$3.00

Power Supply Complete Kit \$19.95 + Shipping & Handling \$3.00

- * COMPLETE REPAIR SERVICE ON ALL ITEMS
- * AVAILABLE BY MAIL ORDER ONLY
- * SEND FOR INFORMATION ON OTHER KITS
- * HOBBY USE ONLY, NOT FOR UNAUTHORIZED RECEPTION OF T.V. SIGNALS



CERTIFIED FUNDS AND MONEY ORDERS SHIPPED IMMEDIATELY. PERSONAL CHECKS HELD FOR 3 WEEKS FOR CLEARANCE. MASTERCARD/VISA/UPS/C.O.D.



4242 South 48th Street
Phoenix, Arizona 85040

INFO PHONE: (602) 829-6700

ORDERS ONLY: (800) 243-6700

CIRCLE 13 ON FREE INFORMATION CARD

FREE THE WORLD FAMOUS **ETCO** CATALOG OF ELECTRONICS

• VIDEO
• TELEPHONE
• CABLE TV
• PARTS
• AUDIO
• ELECTRONICS
• and much more!

1000's OF FASCINATING FACTORY CLEAROUTS, SURPLUS SPECIALS AND BARGAIN OFFERS NOT FOUND IN STORES OR CATALOGS ANYWHERE!

ETCO ELECTRONICS
DEPT. 591
Mailing List Control Center
Box 840
Champlain, N.Y. 12919

I Enclose _____ (cash OK);
Please rush postpaid

\$1 for 1 year subscription to the world famous ETCO catalog.
 \$3 Canadian & Foreign 1 year subscription to the ETCO catalog.
 304 page handbook "BUILD YOUR OWN EARTH STATION". (TA025) \$10.00
 360 pages MASTER HANDBOOK OF TELEPHONES. (TA001) \$11.00
 FREE - sample copy of the bargain packed ETCO catalog. (USA only)

Name _____
Address _____
City _____
State _____ Zip _____

NOW 112 PAGES

CIRCLE 50 ON FREE INFORMATION CARD

HIGH QUALITY 55 dB GAIN

MICROWAVE TV SYSTEM

Variable from 1.9 to 2.5 GHz



The latest advance in microwave technology with a **SNOW-FREE PICTURE.**

Introductory **SPECIAL**

\$124⁹⁵

Includes Tax and Shipping

THIS UNIT COMES COMPLETE WITH:

- 20" Fiberglass Parabolic Dish
- Pre-Assembled Probe with Down Converter
- Power Supply and Coax Switch
- 60' of RG-59/U Coax with Connector
- Transformer for 75 to 300 Ohms
- All Mounting Hardware for Fast and Easy Installation

Send Cashiers Check or Money Order to: (Personal Checks, allow 2-5 weeks to clear)

PROFESSIONAL VIDEO, Inc.
4670 Hollywood Blvd., Hollywood, Calif. 90027
219-0227
For C.O.D. Orders Call (213) 352-9681

CIRCLE 43 ON FREE INFORMATION CARD

AMAZING DEVICES

PHASORS

PHASOR PAIN FIELD — Patented and recently developed in our labs is being tested by Gov't for riot control. Soon to come under weapons restrictions as an infernal machine. Easily hand-held. Hazardous IF NOT USED WITH DISCRETION.
PPF-1 PLANS (sold for animal control) \$15.00

INVISIBLE PAIN FIELD GENERATOR — Produces a directional field of moderately intense pain to back of head up to 50'. Cigarette pack size enclosure is easily hidden.
IPG-3 PLANS \$7.00 IPG-3K KIT & PLANS \$44.50
IPG-30 (assembled for animal control) \$59.50

PHASOR STUN/BURNING WAND — Produces sufficient electrical energy capable of burning flesh. Intended as a personal defense device.
PSW-3 PLANS \$8.00 PSW-3K KIT & PLANS \$59.50

LASERS

RUBY LASER RAY PISTOL — Intense visible red, burns, hazardous, with parts sources \$15.00

RUBY PLANS (includes all part sources) \$15.00

CARBON DIOXIDE LASER — Generates 20-40 watts of continuous power capable of burning, cutting, hazardous. (with all part sources) \$15.00

LASER RIFLE — Produces 200-3000 pulses of 30 watt optical energy. Portable and easily hand-held.
LRG-3 PLANS \$10.00
LRG-3K KIT PLANS (minus diode) \$129.50

POCKET LASER — For the beginner, visible red "optical version", non-hazardous.
LHC-2 \$5.00 LHC-2K KIT & PLANS \$24.50

HIGH POWERED PORTABLE ENERGY SOURCE FOR LASERS AND MAGNETIC WEAPONS — Exploding wires, shockwave, etc. Miniature size.
HPS-1 PLANS \$8.00 HPS-1K KIT & PLANS \$49.50

PARTICLE BEAM WEAPON — PLANS \$15.00

SECURITY

INFINITY XMTR — Uses telephone lines for selective home or office listening while away on business or vacation.
INF-1 PLANS \$15.00

SEE IN DARK — Long range, total darkness.
SD-4 PLANS \$10.00

LONG RANGE WIRELESS MIKE — Crystal clear quality — miniature
FBT-7 PLANS \$7.00 FBT-7K PLANS & KIT \$34.50

WIRELESS TELEPHONE TRANSMITTER — Long range, automatic
VWPM-5 PLANS \$10.00 VWPM-5K PLANS & KIT \$34.50

Send for **FREE** catalog description of above plus hundreds more plans, kits and completed items. We accept MC or Visa or when ordering, send check or money order. We pay shipping charges on orders over \$50.00, otherwise include 10% with remittance.

SEND TO: **SCIENTIFIC SYSTEMS**
DEPT. R8, BOX 716, AMHERST, N.H. 03031

OVER 70,000 ITEMS IN STOCK

DISCOUNT PRICES

ON ALL MAJOR INDUSTRIAL AND PERSONAL ELECTRONICS

VISA MasterCard

PANASONIC

KX-T3820 CORDLESS
700' Cordless Range • Auto Redial • Auto Dial Lock Switch • 2-Band Frequency And Tone/Pulse Selector • Built-In Recharger • 2-Way Paging • Standby/Talk • Pause • Base And Handset LED Indicators
\$141.25

KX-T3830 CORDLESS WITH INTERCOM
\$180.00

LINEAR TELEPHONE UNIVERSAL DIALING KEYS
Unique Linear Keypad Arrangement • UDK Provides Pushbutton Operation On Most Private Lines • Auto Redial • Call Hold • 3 Position Electronic Tone Ringer • Fully Modular
\$46.00

LINEAR TELEPHONE TOUCH CALL KEYS
\$53.00

REVERE RTR-1 VHF TRANSMITTER/RECEIVER
2 Required • 2 Way Hands Free Radio Communication • Rugged • Lightweight • 400-800 Meters Range
\$39.95

KEITHLEY

132C
Temp. Gauge -20°C To 1370°C • 1°C Resolution • DCV • TRMS AC Volts • DC Amps • Resistance And Diode Test • Drop Proof • \$177

132F
Temp Gauge 0°F To 2000°F • 1°F Resolution • All Features Of 132C • \$185.70

8024B
3½ Digit • 11 Functions • 0.1% DC Accuracy • Safety Designed Test Leads • \$217

8062A
4½ Digit • Full Functions And Ranges • True RMS To 30 KHz • 0.05% DC Accuracy • \$244

FLUKE

LX-306
3½ Digit • New VARI-PITCH Full Function, Variable Audible Tone • ±0.25% Accuracy • AC/DC Volts • AC/DC Current • Resistance And Diode Test • Low Battery Indicator • Sustains 4' Drop • \$139

HICKOCK
WITH CARRYING CASE BATTERY • \$139

WELLER SOLDERING TOOLS

WTCPN Soldering Station
Closed Loop • Auto Temp • Lightweight • Pencil Iron • \$72.95

7200 Soldering Iron
Lightweight • Fingertip Trigger • Self Support Back • \$10.99

7200 Standard Soldering Gun

XCELITE TOOL CASES

TC Series With Wide Range Of Tools • Sturdy-Spacious • Professional • Solid Wood Frame • Classic Cover

TC-100 \$346.95
TC-150 279.99
TC-200 178.75

PANAVISE ELECTRONIC WORK CENTER 324
Keeps Everything At Hand • Holds Up To 10" Board • 6 Compartment Tray Base • Solder Iron Holder • Stable • \$38.00

PERSONAL COMMUNICATIONS **TEST EQUIPMENT** **TOOLS & ACCESSORIES**

TOTAL ELECTRONICS CENTER • LOWER PRICES • IMMEDIATE DELIVERY

WM. B. ALLEN SUPPLY COMPANY, INC.

800 535-9593 1601 BASIN STREET, NEW ORLEANS, LA 70116 LOUISIANA TOLL FREE 800 462-9520 800 535-9593

CIRCLE 26 ON FREE INFORMATION CARD

SJB DISTRIBUTORS. THE MOST COMPETITIVE PRICES ON COMMODORE.

commodore

NEW COMMODORE PRODUCTS

CBM 128-40	\$ 695
CBM C128-80	795
CBM B700	2990
CBM 1520 Plotter	169
CBM 1701 Color Monitor	269
B Series Software	Call
CBM 4023 Printer	399

SOFTWARE FOR CBM 64

Word Processing (WordPro 3+)	\$ 69
M File Database (merge with Word Pro)	89
Quick Brown Fox	56
Writer's Assistant (easy and flexible)	99
File Assistant (database with merge)	99
Spreadsheet Assistant	99
Pers. Finance Assist. (great reports)	45
Busicalc (Spreadsheet)	55
Coco II (build your own games easily)	45
Calc Result	125
General Ledger, A/R, A/P (with check writing)	ea. 139
CBM EasyFinance	50
CBM EasyScript	80
CBM EasyFile	80
Data Manager	70
Stock (investment analysis)	80
Pet Emulator (emulates 4.0 basic)	30
Sprite-Master	29
Assembler Package (cassette or disk, compiled, includes editor, loader, disassembler)	39
Spacebelt	20
Retrobball	34
ZWARK	25

INTERFACES & ACCESSORIES

80 Column Expander	\$159
VIC 1600 Modem	95
VIC 1650 (auto answer, auto dial)	150
VIC 1525 Graphic Printer	329
VIC 1530 Datasette Recorder	65
VIC 1541 Disk Drive	329
VIC Switch (connect 8 64's or Vics to printer, dd)	149
PET-IEEE cable	33
IEEE-IEEE cable (2m)	43
Parallel Interface (Epson, Okidata, IDS, NEC)	80
RS-232 Printer Interface (Okidata, Diablo, etc.)	60
Programmers Reference Guide	18
Verbatim Diskettes (10 per box)	26
Victree (Programmers Utility)	75

VIC PRODUCTS & ACCESSORIES

8K RAM Memory Expansion Cartridge	\$ 40
16K RAM	70
24K RAM	105

VIC 3 Slot Expander	27
VIC 6 Slot Expander	70
RS-232 Printer Interface	65
Cassette Interface	30
Gorf (64 also)	30
Omega Race	30
Arcade Joystick - Heavy duty w/2 firing buttons! Great for the VIC or 64	25

MONITORS - GREAT RESOLUTION (64 OR VIC)

Amdek Color I.	\$ 299
Amdek II or III	call
Panasonic CT160	279
Comrex 6500 - 13" Color	299
Transtar 20 (High Resolution Green Phosphor)	129
Video/Audio Cable	15

PRINTERS - LETTER QUALITY

CBM 8300, 40 cps	\$1450
Diablo 620, 25 cps	949
ComRiter, 17 cps	819
Transtar 130, 16 cps (auto load, wp features!)	769
NEC 7700 series	2350
NEC 3500 series	1600

PRINTERS - DOT MATRIX

CBM 8023, 150 cps/graphics	589
Epson FX Printer, 160 cps	549
Epson MX-80FT	459
Epson MX-80 w/ Graftrax	349
CBM Graphics for Epson	65
Okidata 82A, 120 cps (serial and parallel)	429
NEC 8023A (parallel)	429
Okidata 92	559
Star Gemini, 10	329
Star Gemini, 15	499

COMMODORE BUSINESS SERIES

SuperPet (5 languages, 2 processors)	\$1409
CBM 8032 Computer, 80 Column	1029
CBM Memory Expansion, 64K	359
CBM 8050, 1 mg. Dual Drive	1259
CBM 8250, 2 mg. Dual Drive	1395
CBM D9060, 5 mg. Hard Disk	1995
CBM D9090, 7.5 mg. Hard Disk	2295
CBM 2031, 170K Single Drive (New)	489
DC Hayes Smart Modem	220

BUSINESS SOFTWARE

WordPro 4+ or 5+	\$ 309
Administrator	489
VisiCalc (expanded)	199
The Manager (database)	199
BPI A/R, G/L, Job Cost, Inventory, Payroll	ea. 325

MasterCard, Visa, Money Order, Bank Check

COD (add \$5) accepted.
Add 3% surcharge for credit cards.
In stock items shipped within 48 hours,
F.O.B. Dallas, Texas
All products shipped with manufacturer's
warranty.

Prices are subject to change without notice.

**TO ORDER
CALL TOLL FREE
800-527-4893
800-442-1048
(Within Texas)**

Business Hours
Mon.- Fri. 8 to 6, Sat. 10-2

Write for free catalog.

GAME OF THE MONTH

Adventu-Writer (make your
own adventure game)
 39 |

PRODUCT OF THE MONTH

INTERPOD (intelligent IEEE
RS232, serial interface
for VIC or C64)
 \$ 179 |



SJB DISTRIBUTORS INC.


10520 Plano Road, Suite 206
Dallas, Texas 75238
(214) 343-1328

Electronics Paperback Books


Quality Paperbacks at Affordable Prices



- 30 SOLDERLESS BREADBOARD PROJECTS BOOK-1.** \$5.75. Whenever possible the same parts are used in several projects. Even a first-time builder can complete these circuits.
- MODERN OP-AMP PROJECTS.** \$5.00. Wide range of specialized op-amp circuits including hi-noise, hi-distortion, ultra-hi input impedance, etc.
- HOW TO GET YOUR ELECTRONIC PROJECTS WORKING.** \$5.00. Helps you troubleshoot and repair home-built projects of every description.
- MINI-MATRIX BOARD PROJECTS.** \$5.00. A variety of projects that can all be built upon a mini-matrix board that has 10 strips and is 24 holes long.
- MULTI-CIRCUIT BOARD PROJECTS.** \$5.00. 21 fairly simple projects that can all be built on a single printed-circuit board. All are powered by a 9V battery.
- IC PROJECTS FOR BEGINNERS.** \$5.00. Inexpensive digital and linear IC's are used to assemble this selection of circuits intended for the beginner.

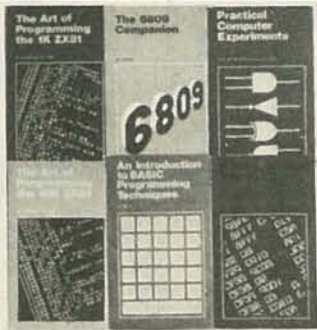

- ART OF PROGRAMMING THE 1K ZX81.** \$6.25. Topics include full screen, scrolling, PEEK & POKE, plus actual working programs.
- ART OF PROGRAMMING THE 1K ZX81.** \$5.00. How to use the features of the ZX81 in programs that fit the 1K machine and are still fun to use.
- THE 6809 COMPANION.** \$5.00. Written for the average assembly language programmer. A discussion of 6809 features & reference work for the 6809 programmer.
- INTRODUCTION TO BASIC PROGRAMMING TECHNIQUES.** \$5.00. Based on author's own experience in learning BASIC and helping others to learn to program.
- PRACTICAL COMPUTER EXPERIMENTS.** \$4.50. Fills in background to microprocessor by constructing typical computer circuits using discrete logic components.
- A MICROPROCESSOR PRIMER.** \$4.50. Painless approach to computing for the beginner. Step-by-step explains computer operations and assembly.

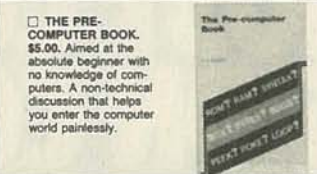

- THE PRE-COMPUTER BOOK.** \$5.00. Aimed at the absolute beginner with no knowledge of computers. A non-technical discussion that helps you enter the computer world painlessly.
- AN INTRODUCTION TO VIDEO.** \$5.00. Perfect for the person just about to buy a VCR. Discusses pros & cons of the various formats; video discs; videotext; tape copying and more.
- PRACTICAL ELECTRONIC BUILDING BLOCKS-Book 1.** \$5.00. All electronics circuits consist of simple building blocks. When you know how to make the blocks you can easily create your own projects.



- POWER SUPPLY PROJECTS.** \$4.50. Contains designs and construction details for almost any power supply the experimenter is likely to need.
- REMOTE CONTROL PROJECTS.** \$5.00. Radio-control infra-red, visible light, & ultrasonic systems are all included, along with methods of applying them.
- ELECTRONIC TEST EQUIPMENT CONSTRUCTION.** \$4.50. Construction details of a wide range of test equipment the experimenter can build at home.
- ELECTRONIC PROJECTS USING SOLAR CELLS.** \$5.00. Simple circuits that have numerous applications around the home.
- ELECTRONIC TIMER PROJECTS.** \$5.00. Timing circuits for almost any application the experimenter might need. A most valuable reference.
- COUNTER DRIVER & NUMERICAL-DISPLAY PROJECTS.** \$4.50. Features applications & projects using various types of numerical-display devices.




- PRACTICAL ELECTRONICS CALCULATIONS AND FORMULAE.** \$7.50. A basic reference work that bridges the gap between complicated technical theory & cut and tried methods.
- INTERNATIONAL DIODE EQUIVALENTS GUIDE.** \$5.75. Helps you find substitutes for the many different types of semiconductor diodes in use today.
- INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE.** \$7.50. Products of more than 100 manufacturers are listed & cross-referenced with possible replacements.
- HOW TO MAKE WIKIE TALKIES.** \$5.00. Describes equipment for low-power handheld operation. 112 pages of must reading for the dedicated experimenter.
- ELECTRONIC CALCULATOR USERS HANDBOOK.** \$3.95. Presents formulae data, methods of calculation, conversion factors & more from the view of the calculator user.
- LINEAR IC EQUIVALENTS AND PIN CONNECTIONS.** \$8.25. Shows equivalents & pin connections of a popular user-oriented selection of linear IC's.



- ELECTRONIC SYNTHESIZER PROJECTS.** \$4.50.
- 50 CIRCUITS USING GERMANIUM, SILICON & ZENER DIODES.** \$3.75.
- 50 PROJECTS USING RELAYS, SCRS & TRIACS.** \$5.00.
- 50 (FET) FIELD-EFFECT TRANSISTOR PROJECTS.** \$4.50.
- 50 SIMPLE LED CIRCUITS.** \$4.25.
- 50 CIRCUITS USING 7400 SERIES IC'S.** \$4.50.
- 50 SIMPLE LED CIRCUITS BOOK 2.** \$3.95.
- PROJECTS USING 555 IC'S.** \$5.00.
- PROJECTS USING LM3900 IC'S.** \$4.75.
- RADIO CONTROL FOR BEGINNERS.** \$4.50.
- ELECTRONIC GAMES.** \$4.50.
- SINGLE IC PROJECTS.** \$4.25.
- RADIO CIRCUITS USING IC'S.** \$4.50.
- ELECTRONIC PROJECTS FOR BEGINNERS.** \$5.00.
- ELECTRONIC MUSIC & CREATIVE TAPE RECORDING.** \$5.00.
- ELECTRONIC SECURITY DEVICES.** \$5.00.
- HOW TO BUILD YOUR OWN SOLID-STATE OSCILLOSCOPE.** \$5.00.
- SECOND BOOK OF CMOS IC PROJECTS.** \$4.25.
- PRACTICAL CONSTRUCTION OF PRE-AMPS, TONE CONTROLS, FILTERS AND ATTENUATORS.** \$3.75.
- BEGINNERS GUIDE TO DIGITAL TECHNIQUES.** \$3.75.
- ELECTRONIC HOUSEHOLD PROJECTS.** \$4.50.
- ELECTRONIC MUSIC PROJECTS.** \$4.50.
- POPULAR ELECTRONIC PROJECTS.** \$3.75.
- PROJECTS IN OPTO-ELECTRONICS.** \$5.00.



- ANTENNA PROJECTS.** \$5.00. Covers practical antenna designs including active, loop & ferrite types that are easy & inexpensive to build.
- RADIO STATIONS GUIDE.** \$4.75. Comprehensive listing of transmitters around the world. Presents location, frequency, power.
- LONG DISTANCE TV RECEPTION (TVDX) FOR THE ENTHUSIAST.** \$5.00. Practical & authoritative introduction to this unusual aspect of electronics.
- CB PROJECTS.** \$5.00. A number of useful and interesting designs for CB accessories. Speech processor, interference filter & more.
- CRYSTAL SET CONSTRUCTION.** \$4.50. Packed full of easy to duplicate designs for crystal radio receivers.
- AN INTRODUCTION TO RADIO DXING.** \$5.00. Listen, in your home, to broadcasts originating thousands of miles away. Tells how you can do it.

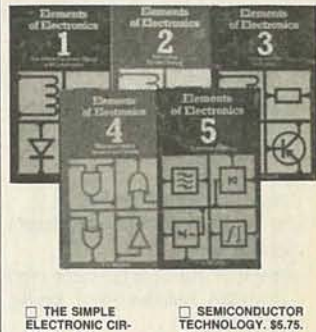

- THE SIMPLE ELECTRONIC CIRCUIT & COMPONENTS.** \$5.75. All the fundamental theory needed to lead to a full understanding of the simple electronic circuit and its components.
- ALTERNATING CURRENT THEORY.** \$5.75. Alternating current theory without which there can be no comprehension of speech, music, radio, or television.
- MICROPROCESSING SYSTEM & CIRCUITS.** \$7.50. A truly comprehensive guide to all of the elements of a microprocessing system.
- SEMICONDUCTOR TECHNOLOGY.** \$5.75. Everything you always needed to know about solid-state devices in one volume.
- COMMUNICATIONS.** \$7.50. Covers most modern communication systems. Line, microwave, submarine, satellite, digital multiplex, radio & telegraphy.
- FIRST BOOK OF HI-FI SPEAKER ENCLOSURES.** \$4.50.
- SOLID STATE NOVELTY CIRCUITS.** \$3.50.
- 28 TESTED TRANSISTOR PROJECTS.** \$4.25.

ELECTRONIC TECHNOLOGY TODAY INC.
P.O. Box 83, Massapequa Park, NY 11762

Number of books ordered

Total Price of Books\$

Sales Tax (NY State Residents)

Shipping (75¢ 1st two books, 30¢ ea additional)

TOTAL ENCLOSED\$

Name _____

Address _____

City _____ State _____ ZIP _____

Prices good until August 30, 1983

AMATEUR MICROWAVE TV ANTENNA'S

1.9 to 2.5 GHz Frequency Range
50 db System Gain

Complete System (Rod Style as pictured, 25 db Gain)

PS-3 assembled, tested \$79.95
PS-3 kit form \$64.95

Complete System (Dish Style as pictured, 50 db Gain)

PS-5 assembled, tested \$109.95
PS-5 kit form \$79.95

All systems come complete with accessory package of

- Control Box
- 60' Coax Cable
- Mounting Hardware
- Matching Transformer
- Instructions
- 90 Day Warranty



S.E.I., Inc.

912 West Touhy Ave. • Park Ridge, IL 60068

To Order Call: 1-800-323-1327 Out of State

1-312-564-0104 In Illinois

For Information Call: 1-312-564-0104

C.O.D.'s Accepted • Special Quantity Pricing

Dealers Wanted

5% shipping and handling. 10% for out of Continental U.S.



CIRCLE 55 ON FREE INFORMATION CARD

OUR ISOLATORS FOR YOUR PROTECTION

Prevents:

disk drive woes,
printer interaction,
memory loss and damage due to lightning
or AC power line disturbances.



Commercial Grade Isolator
ISO-1 3 Isolated Sockets... \$76.95

Industrial Grade Isolator
ISO-3 3 Double Isolated Sockets... 115.95

Laboratory Grade Isolator
ISO-17 4 Quad Isolated Sockets... 200.95

Circuit Breaker
any model (Add-CB)... Add 10.00
Remote Switch
any model (Add-RS)... Add 18.00

ESF Electronic Specialists, Inc.
171 S. Main St., Box 389, Natick, MA 01760

Toll Free Order Desk 1-800-225-4876
MasterCard, VISA, American Express

CIRCLE 6 ON FREE INFORMATION CARD

ELECTRONIC KITS FROM HAL-TRONIX

2304 MHZ DOWN CONVERTERS. TUNES IN ON CHANNELS 2 TO 7 ON YOUR OWN HOME T.V. HAS FREQUENCY RANGE FROM 2000 MHZ TO 2500 MHZ. EASY TO CONSTRUCT AND COMES COMPLETE WITH ALL PARTS INCLUDING A DIE-CAST ALUM CASE AND COAX FITTINGS. REQUIRE A VARIABLE POWER SUPPLY AND ANTENNA (Antenna can be a dish type or coffee can type depending on the signal strength in your area.)

2304 MOD 1 (Basic Kit) \$19.95
(Less case & fittings)

2304 MOD 2 (Basic/Pre-amp) \$29.95
(Less case & fittings)

2304 MOD 3 (Hi-Gain Pre-amp) \$39.95
(Includes case & fittings)

POWER SUPPLY FOR EITHER MODEL ABOVE IS AVAILABLE. COMES COMPLETE WITH ALL PARTS, CASE, TRANSFORMER, ANTENNA SWITCH AND CONNECTORS (Kit) \$24.95

Assembled..... \$34.95
Slotted Microwave Antenna For Above Downverters..... \$39.95

PREAMPLIFIERS

HAL PA-19—1.5 mhz to 150 mhz. 19db gain operates on 8 to 18 volts at 10ma. Complete unit \$8.95.

HAL PA-14—3 mhz to 1.4 ghz. 10 to 12 db gain operates on 8 to 18 volts at 10 ma. Complete unit \$12.95.

(The above units are ideal for receivers, counters, etc.)

16 LINE TOUCH TONE DECODE KIT WITH P.C. BOARD AND PARTS..... \$69.95

12 LINE TOUCH TONE DECODE KIT WITH P.C. BOARD AND PARTS..... \$39.95

16 LINE ENCODER KIT, COMPLETE WITH CASE, PAD AND COMPONENTS..... \$39.95

12 LINE ENCODER KIT, COMPLETE WITH CASE, PAD AND COMPONENTS..... \$29.95

Complete Sets of P.C. Boards Available For: Unicorn Robot Project and Heart-A-Matic Project.
MANY, MANY OTHER KITS AVAILABLE

Send 20 cents stamp or S.A.S.E. for information and flyer on other HAL-TRONIX products. To order by phone: 1-313-585-1782.



HAL-TRONIX
P.O. Box 1101
Southgate, MI 48195

SHIPPING INFORMATION: ORDERS OVER \$25.00 WILL BE SHIPPED POSTPAID EXCEPT ON ITEMS WHERE ADDITIONAL CHARGES ARE REQUIRED. ON ORDERS LESS THAN \$25.00 PLEASE INCLUDE ADDITIONAL \$2.00 FOR HANDLING AND MAILING CHARGES.

CIRCLE 75 ON FREE INFORMATION CARD

Order Line
800-435-0907
(outside Calif.)
Please use for
orders only

RANA Systems
Apple Drives
\$395.00 w/controller
\$295.00 w/o controller

SUPER 3.5amp POWER SUPPLY
for APPLE → \$82.00 ☆

Diskette Storage BOX
5 1/4 in. > 5/8" : 8 in. > 5/8"
\$2.50 ea. \$10.00 : \$3.50 : \$15.00

Bare Bones APPLE II
EURO

w/o Keyboard = 48K RAM
\$399.
w/o Pwr. Supply

Microswitch: \$75.00
Power Supply: \$79.00
Apple Reference Manl.: \$18.00

CONCORD COMPUTER PRODUCTS

2910 B E LA PALMA
ANAHEIM CA 92806
(714) 632-6790 CHECK - M - O

10 MIN ORDER C.A.R.Y. ADD \$1.00
Freight \$10 - 49 \$2.00 \$250 - 499 \$3.00
50 - 99 \$4.00 500 - 999 \$5.00
100 - 240 \$6.00 1000 - UP \$7.00
PRIME TIME \$1.00
send \$100 for catalog

MONITORS ☆ ☆
ZENITH # ZVM-121
12in. 15MHz./GREEN Phos.

→ \$94.00 ☆

BMC # BM-12EUN
12in 20 MHz./GREEN Phos.
Non-Glare Screen
→ \$134.00 ☆

BMC # BM1401RGB
13in. "RGB" COLOR
with Apple interface!!
→ \$425.00 ☆

74LS

74LS00	21	74LS95	25	74LS139	50	74LS194	85	74LS299	195	LM300H	35
74LS02	24	74LS173	36	74LS145	115	74LS195	85	74LS323	455	LM301H	45
74LS03	24	74LS174	35	74LS147	176	74LS196	75	74LS352	105	LM307H	45
74LS04	23	74LS175	38	74LS148	135	74LS197	75	74LS353	105	LM308AN	225
74LS05	20	74LS176	38	74LS151	55	74LS221	95	74LS385	45	LM309K	125
74LS06	24	74LS178	42	74LS153	50	74LS240	95	74LS386	45	LM310	145
74LS08	24	74LS183	48	74LS154	175	74LS241	95	74LS387	75	LM311	50
74LS10	23	74LS185	60	74LS155	75	74LS242	85	74LS388	45	LM317K	385
74LS11	30	74LS186	30	74LS156	75	74LS243	125	74LS373	90	LM318H	145
74LS12	29	74LS190	50	74LS157	95	74LS244	85	74LS374	95	LM322	155
74LS13	40	74LS191	85	74LS158	85	74LS245	165	74LS375	95	LM323K	495
74LS14	45	74LS192	50	74LS160	89	74LS247	110	74LS377	95	LM324	55
74LS15	29	74LS193	50	74LS161	85	74LS248	110	74LS378	95	LM339	99
74LS20	24	74LS195	85	74LS162	89	74LS249	110	74LS379	110	LM348	125
74LS21	20	74LS196	89	74LS163	85	74LS251	55	74LS386	45	LM358	65
74LS22	24	74LS197	38	74LS164	85	74LS253	55	74LS390	115	LM390	110
74LS26	26	74LS199	38	74LS165	85	74LS257	50	74LS393	115	LM381	185
74LS27	28	74LS199	38	74LS166	175	74LS258	55	74LS395	115	LM386	140
74LS28	28	74LS199	38	74LS168	155	74LS259	125	74LS399	125	LM501	195
74LS30	24	74LS199	38	74LS169	155	74LS260	55	74LS400	175	LM555	27
74LS32	27	74LS199	38	74LS170	135	74LS266	55	74LS623	175	LM558	110
74LS33	35	74LS199	38	74LS173	85	74LS273	145	74LS668	125	LM558	245
74LS37	30	74LS199	38	74LS174	55	74LS279	45	74LS669	125	LM565	95
74LS38	32	74LS199	38	74LS175	85	74LS280	185	74LS670	145	LM568	145
74LS42	45	74LS199	38	74LS181	195	74LS283	65	74LS683	275	LM703	75
74LS48	75	74LS199	38	74LS180	89	74LS290	95	74LS685	275	LM709	40
74LS49	75	74LS199	38	74LS191	89	74LS293	85	74LS687	350	LM710	75
74LS51	24	74LS199	38	74LS192	75	74LS295	95	74LS783	1695	LM711	49
74LS54	25	74LS199	38	74LS193	75	74LS298	85	LM720	175	LM723	55
								LM733	95	LM741-B	35
								LM741H-14	35	LM741H-35	35
								LM747	65	LM751	25
								LM753	25	LM755	160
								LM757	175	LM758	115
								LM759	135	LM761	135
								LM762	137	LM763	145
								LM764	145	LM765	145
								LM766	145	LM767	145
								LM768	145	LM769	145
								LM770	145	LM771	145
								LM772	145	LM773	145
								LM774	145	LM775	145
								LM776	145	LM777	145
								LM778	145	LM779	145
								LM780	145	LM781	145
								LM782	145	LM783	145
								LM784	145	LM785	145
								LM786	145	LM787	145
								LM788	145	LM789	145
								LM790	145	LM791	145
								LM792	145	LM793	145
								LM794	145	LM795	145
								LM796	145	LM797	145
								LM798	145	LM799	145
								LM800	145	LM801	145
								LM802	145	LM803	145
								LM804	145	LM805	145
								LM806	145	LM807	145
								LM808	145	LM809	145
								LM810	145	LM811	145
								LM812	145	LM813	145
								LM814	145	LM815	145
								LM816	145	LM817	145
								LM818	145	LM819	145
								LM820	145	LM821	145
								LM822	145	LM823	145
								LM824	145	LM825	145
								LM826	145	LM827	145
								LM828	145	LM829	145
								LM830	145	LM831	145
								LM832	145	LM833	145
								LM834	145	LM835	145
								LM836	145	LM837	145
								LM838	145	LM839	145
								LM840	145	LM841	145
								LM842	145	LM843	145
								LM844	145	LM845	145
								LM846	145	LM847	145
								LM848	145	LM849	145
								LM850	145	LM851	145
								LM852	145	LM853	145
								LM854	145	LM855	145
								LM856	145	LM857	145
								LM858	145	LM859	145
								LM860	145	LM861	145
								LM862	145	LM863	145
								LM864	145	LM865	145
								LM866	145	LM867	145
								LM868	145	LM869	145
								LM870	145	LM871	145
								LM872	145	LM873	145
								LM874	145	LM875	145
								LM876	145	LM877	145
								LM878	145	LM879	145
								LM880	145	LM881	145
								LM882	145	LM883	145
								LM884	145	LM885	145
								LM886	145	LM887	145
</											

SPARTAN Electronics Inc.



CALL
(516) 499-9500
MAIL
6094 Jericho Tpke.
Commack, N.Y. 11725

CTC9R

Philips Remote Cable Converter



\$139.95

• Micro computer technology • Quartz controlled IC's lock in picture & prevent drift • 68 channel selections • Programmable time on & off • 24 hour LED digital clock • Favorite channel memory & recall plus scan • Wireless hand held remote - transmitter system • Automatic fine tune • Adaptable to any brand television • One year warranty service

CABLE TV ACCESSORIES

2 set coupler	2.95
3 set coupler	3.95
4 set coupler	4.50
F Connectors	.25
Matching transformer	.99
TV Game Switch	3.95
VHF-UHF AMP-28DB	29.95

2-WAY SWITCH for

printers, modems,
& computers
(RS232)



\$119.95

SGL WABER

Protect your computer and electronic equipment from voltage spikes

\$35.95
DG115P



DG115S
(6 Outlet)
\$45.95

SCOTCH DISKETTES



5 1/4 SSDD Soft Box 10 \$29.95
5 1/4 DSDD Soft Box 10 \$39.95

REFURBISHED MONITORS

9", 12", Commercial Grade
as low as \$49.95



1500 Feet Cordless Phone \$229.95



10 KM (6 miles) Cordless
Phone for Export Use Only
\$325.00

BECKMAN CIRCUITMATE 20

8 functions and 30 ranges - Diode/transistor test function - auto-polarity, auto-zero, and auto-decimal - 10 Amps AC and DC Current Capability - Transistor Gain Test (hFE) - Conductance



\$64.95

Jerrold 36 Channel Remote CATV Converter

w/on/off Fine Tuning \$94.95
58 Channel Wireless \$109.95



40 Channel VHF to UHF Block Converter



28.95 Ea.
24.95 4 & up

Deluxe Version - Features fine tuning knob, matching X former & 2 cables \$38.95

Volume Discounts

Dealers Welcome
Visa, MC, BAC, Amex, 4% AdB
C.O.D. money order, check
Add for Shipping

Min Order \$25.00	to 75.00	\$2.50
International shipping Add'l.	76.00 to 250.00	\$4.50
Prices subject to change without notice.	251.00 to 500.00	\$6.00
COD 2.00 Extra	501.00 to 750.00	\$8.50
*Add'l. shipping for monitors	751.00 to 1000.00	\$12.00
	Over 1000.00	\$12.50

(516) Mon Th Tu W F Sa
499-9500 9-8 9-6 9:30-5

CIRCLE 47 ON FREE INFORMATION CARD

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

Free Information Number	Page		Page
62	Abex.....	100	PAIA Electronics Inc.....77
3	Active Electronic Sales Corp.....	115	93 Paladin.....28
—	Advance Electronics.....	31	9 Phillips-Tech Electronics.....130
80	Advanced Computer Products.....	125	— Radio-Electronics Bookstore.....81
73	All Electronics Corp.....	111	86 Radio Shack.....109
51	AMC Sales.....	102	79 Ramsey Electronics Inc.....121
56	AP Products.....	11	27 R. F. Electronics.....119
14	Appliance Service News.....	101	32 Sams Books.....83
89	Arizona Electronic Surplus.....	119	25 SCR Electronics Center.....110
60	ABC Metrawatt.....	Cover II	55 SEI.....135
41, 78	Beckman Instruments.....	Cover III, 40	70, 71 Sencore.....1
67	Beta Electronics.....	116	— Simple Simon Electronic Kits Inc.....73
—	Binary System.....	98	91 Simpson Electric Company.....24
42	BK Precision Dynascan Corp.....	9	82 Sintec Company.....30
17	Bondhus Corp.....	28	24 SJB Distributors Inc.....133
—	CD Electronics Inc.....	119	— Solder Absorbing Technology Inc.....100
34	Chaney Electronics Inc.....	118	69 Solder Craft.....118
—	CIE, Cleveland Institute of Electronics Inc.....	34-37	23 Solid State Sales.....110
44	Circuit Specialists Inc.....	115	28 Sony.....20
2, 21	Communications Electronics.....	2, 21	57 Space Age Video Dist Inc.....79
88	Components Express Inc.....	120	47 Spartan Electronics Inc.....136
68	Computer Products Peripherals Unltd.....	120	72 Symmetric Sound Systems.....101
7	Concord Computer Products.....	135	98 Sunnex Inc.....100
48	Consolidated Electronics Inc.....	38	38 Taft Electronics.....94
—	Daetron.....	130	8 Technical Electronics.....136
39	Digi-Key Corp.....	122, 123	74 Tektronix.....7
—	Digitron Electronic.....	124	30 Tinker Tron.....91
53	Direct Video Sales.....	39	43 Triton Mkt Corp.....33
99	Dokay Computer Products Inc.....	117	18 Ungar.....Cover IV
59	EICO.....	77	15 Video Engineering Supply Co.....77
5	Electra Company.....	29	19 Wahl Clipper.....81
45	Electronic Rainbow.....	41	13 Westech.....131
6	Electronic Specialists Inc.....	135	95 Wersi.....83
—	Electronic Technology Today Inc.....	79, 134	26 Wm B Allen Supply.....132
33	Electronics Book Club.....	25	
10	Etronix.....	89	
40	Firestick Antenna Company.....	91	
—	Fordham Radio.....	13, 15, 22	
76	Formula International Inc.....	114	
21	Gamma Electronics.....	120	
84	Gilco International Inc.....	124	
—	Gladstone.....	92	
31	Global Specialties Corp.....	23	
—	Grantham College of Engineering.....	92	
—	Graymark Inc.....	118	
75	Hal-tronix.....	135	
16	Heath Company.....	5	
85	Hickok.....	79	
—	ICS Computer Training.....	91	
94	Illinois Audio.....	91	
20	Jameco Electronics.....	112, 113	
29	Javanco.....	124	
49	JDR Microdevices Inc.....	126-129	
97	Jensen Tools Inc.....	100	
11	Jim-Pac Electronic Components.....	26, 27	
46	Kalgl Electronics Company Inc.....	79	
83	KCS Electronics Corp.....	130	
36	Keithly Instruments Inc.....	42	
—	McGraw-Hill Book Clubs.....	102-105	
35	MCM.....	119	
66	MFJ Enterprises Inc.....	110	
12	Micro-Mart.....	130	
—	Monarchy Engineering Inc.....	118	
77	Morrow.....	96, 97	
—	Netronics R D Ltd.....	39	
90	Network Sales Inc.....	115	
—	New Horizons.....	75	
—	NRI Schools.....	16-19	
—	NTS Schools.....	84-87	
61	OEM Distributing Company.....	100, 101	
37, 100	Ora Electronics.....	32, 100, 101	
58	Pacific 1.....	100	

TEK-EL

TECHNICAL ELECTRONICS,
YOUR SUPPLY SOURCE
WITH BARGAINS LIKE THESE:

RECHARGEABLE AA CELL



Standard AA nickel cadmium rechargeable battery.
Stock No. 16-2379 \$.95 ea.



AUDIO AMP

Complete audio amp
includes volume/on-
off and tone controls.

Requires 6-9 VDC. Just the thing for PA systems,
record players, or intercoms!


Stock No. 36-3023

\$4.95 ea.

4" SOLAR CELL

1 amp at .5 volts at
an unbelievably low price!

Stock No. 47-3029 \$5.95 ea.

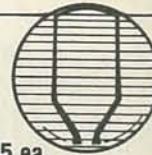

ORDER TODAY! VISA, MASTERCARD & COD
accepted for phone orders. Please add \$3.00
for UPS ground. Satisfaction guaranteed.
Call or write for your FREE CATALOG!

TECHNICAL ELECTRONICS

Dept. J P.O. Box 2361
Woburn, MA 01888 (617) 935-1717

CIRCLE 8 ON FREE INFORMATION CARD



The Workaholics.

Beckman DMMs stay on the job when others call it quits. They're a hard-nosed breed of 3½ digit hand-held multimeters you can always count on for outstanding performance.

Staying power

Beckman DMMs work up to 2000 hours on a common 9V battery. That's ten times longer than other DMMs. And to prevent burnout on the job, Beckman DMMs can withstand 1500 Vdc loads and 6kV transients. Current ranges are protected with a 2A/250V fuse, and resistance ranges are protected up to 500 Vdc.

Easy to work with

No matter how hard they work, they're never hard to work with. Their single rotary switch makes function and range selection simple and sure. For your added convenience, most Beckman DMMs have built-in 10-Amp capability and Insta-ohms® continuity indication. That means you never have to carry an accessory shunt or wait for a continuity check.

SELECTION CHART

MODEL	SPECIAL FEATURES	BASIC DC ACCURACY	INSTA-OHMS®	10 AMPS	SUGGESTED RETAIL PRICE (U.S.)
Tech 300	Basic six functions	0.5%			\$120
Tech 310	Added features	0.25%	✓	✓	145
Tech 310UL	UL-listed	0.25%	✓	✓	155
Tech 320B	Audible continuity beeper	0.1%	✓	✓	189
Tech 330	High accuracy & true RMS (AC & DC)	0.1%	✓	✓	219
HD-100	Heavy duty (drop-proof, contamination-proof)	0.25%	✓		169
HD-110	Heavy duty, plus 10 Amps	0.25%	✓	✓	189

And to make sure that the job is done right the first time, Beckman DMMs have superior RF shielding, and an impressive 22 Meg-ohm input impedance that reduces circuit loading to ensure accurate readings.

No matter how much the job demands, you can count on Beckman DMMs to see you through.

There's a Beckman DMM just right for every application. Use the selection chart to find the model best for you.


For a closer look at the workaholics, see your local Beckman distributor today. To locate the one nearest you, call or write Beckman Instruments, Inc., Instrumentation Operations, 210 S. Ranger Street, Brea, CA 92621. (714) 993-8803.

BECKMAN

UNGAR®

The Professionals' Choice.

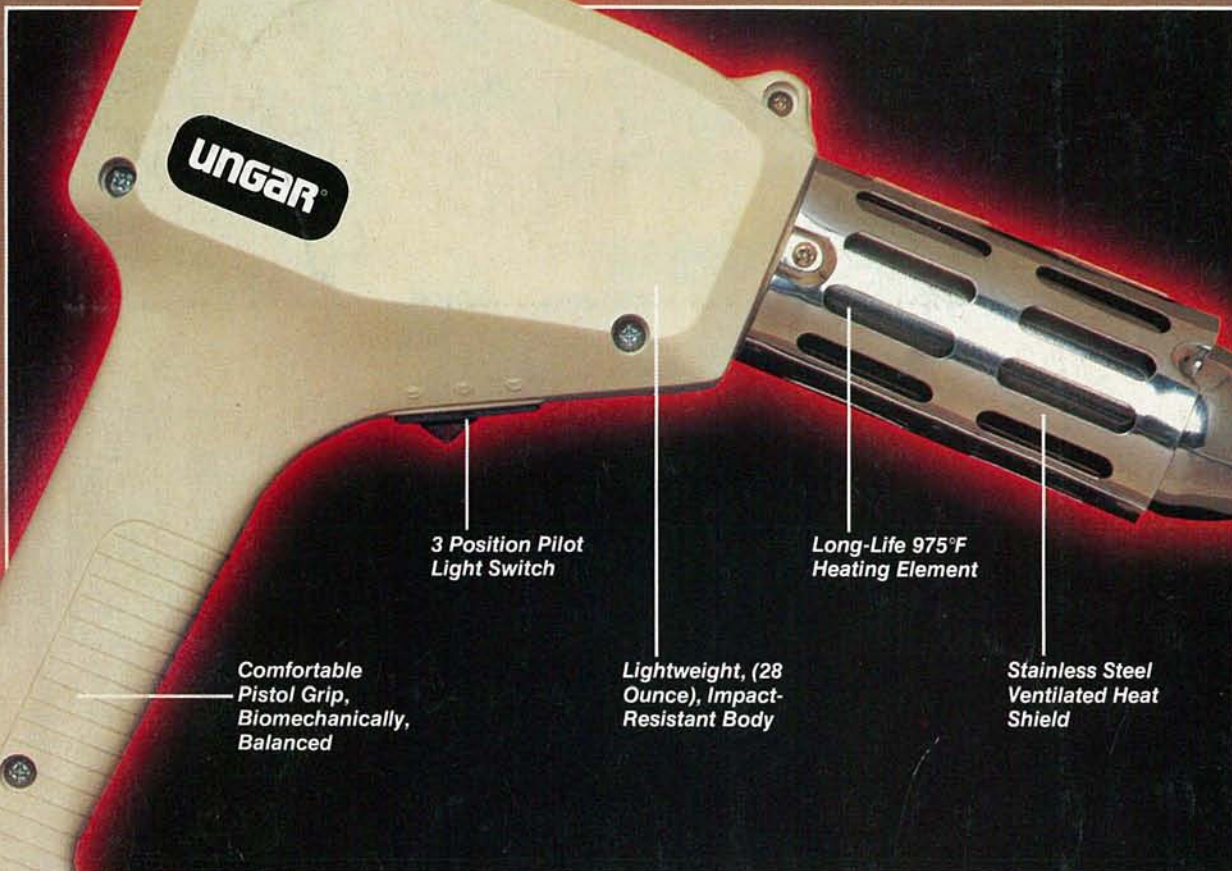Introducing Ungar's New Lightweight Heat Gun For Heavyweight Jobs.



Comfortable Pistol Grip, Biomechanically, Balanced

3 Position Pilot Light Switch

Lightweight, (28 Ounce), Impact-Resistant Body

Long-Life 975°F Heating Element

Stainless Steel Ventilated Heat Shield



Cure Thermoset Adhesives



Shrink Tubing



Heat Liquids



Form Plastics



Peel Paint

At Ungar, we've designed the ultimate heat gun for the hard-working pro. Feature for feature, no other heat gun can make your job quicker, easier or safer.

To begin with, our new 6977 is the lightest heat gun of its kind (28 ounces). You can use it for hours on end with maximum control and minimum fatigue. The contoured handle provides a firm grip and remains cool at all times.

The 6977 is a high-temp, high air volume heat gun with power

for the heaviest jobs. It delivers 975°F to the nozzle in seconds and is perfect for curing adhesives, forming plastics, shrinking tubing, peeling paint and just about any other tough job you'll ever run across.

And the 6977 can take it in the real world. The body is made of rugged, impact-resistant Valox® 855. It features a proven, reliable high-rpm motor, low noise operation, long-life heating element and a 6-foot, 3-conductor ground cord.

A wide range of optional attachments can provide additional versatility. The new Ungar 6977 heat gun... light years ahead of the competition, is Underwriter's Laboratory, Inc. listed. For more information, contact your local Ungar distributor or call Ungar in California 1-213-774-5950.

UNGAR®

Division of Eldon Industries, Inc.
Compton, California 90220

CIRCLE 18 ON FREE INFORMATION CARD