

Radio - PHONE-SYSTEM PRIMER

\$1.95 OCT. 86
IN CANADA \$2.50

Electronics®

TECHNOLOGY - VIDEO - STEREO - COMPUTERS - SERVICE

A
GERNSBACK
PUBLICATION

BUILD THIS SATELLITE-TV DESCRAMBLER

For the Telease-Maast scrambling system

SATELLITE JAMMING
How Captain Midnight took on HBO

OSCILLATORS
Circuits you can breadboard

DELAY LINES
A circuit cookbook

**BUILD AN OLD TIME
CRYSTAL RADIO**
Vintage circuitry and vintage looks

BURN YOUR OWN EPROM's
With R-E's easy-to-build programmer

ALL ABOUT TELEPHONES
A phone-system primer



PLUS:

- ★ Ask R-E
- ★ PC Service
- ★ Antique Radios
- ★ Robotics
- ★ **COMPUTERDIGEST**
- ★ Video News

New GPS Series: Tek sets the pace with SmartCursors™ and push-button ease.

Work faster, smarter, with two new general purpose scopes from Tektronix. The four-channel, 100 MHz 2246 and 2245 set the new, fast pace for measurements at the bench or in the field. They're easy to use and afford, by design.

On top: the 2246 with exclusive integrated push-button measurements. Measurements are accessed through easy, pop-up menus and implemented at the touch of a button. Measure peak volts, peak-to-peak, \pm peak, dc volts and gated volts with new hands-off convenience and on-screen readout of values.

SmartCursors™ track voltmeter measurements in the 2246 and visually indicate where ground and trigger levels are located. Or use cursors in the manual mode for immediate, effortless measurement of waveform parameters.

Both scopes build on performance you haven't seen at the bandwidth or prices. Lab grade features include sweep speeds to 2 ns/div. Vertical sensitivity of 2 mV/div at full bandwidth for

Features	2246	2245
Bandwidth	100 MHz	100 MHz
No. of Channels	4	4
Scale Factor Readout	Yes	Yes
SmartCursors™	Yes	No
Volts Cursors	Yes	No
Time Cursors	Yes	No
Voltmeter	Yes	No
Vertical Sensitivity	2 mV/div	2 mV/div
Max. Sweep Speed	2 ns/div	2 ns/div
Vert/Hor Accuracy	2%	2%
Trigger Modes	Auto Level, Auto, Norm, TV Field, TV Line, Single Sweep	
Trigger Level Readout	Yes	No
Weight	6.1 kg	6.1 kg
Warranty	3-year on parts and labor including CRT	

low-level signal capture. Plus trigger sensitivity to 0.25 div at 50 MHz, to 0.5 div at 150 MHz.

Accuracy is excellent: 2% at vertical, 2% at horizontal. And four-channel capability includes two channels optimized for logic signals.

Best of all, high performance comes with unmatched convenience. You can see it and feel it — in the

responsive controls and simple front-panel design, in extensive on-screen scale factor readouts, and in simplified trigger operation that includes Tek's Auto Level mode for automatic triggering on any signal.

Contact the Tektronix office or sales representative nearest you for complete details. Each scope is backed by Tek's three-year warranty, plus excellent documentation, training programs and outstanding service support — worldwide.



Featuring four channels, flexible triggering, extensive CRT readouts and push-button ease of use, the new Tek 2246 (left) and 2245 (above) bring high-quality, low-cost analysis to diverse applications in digital design, field service and manufacturing.

Tektronix®
COMMITTED TO EXCELLENCE

BUILD THIS

- 50 SATELLITE-TV DESCRAMBLER**
With this easy-to-build device, you can watch satellite-TV broadcasts that are scrambled using the Telease-Maast encoding system. **Victor J. Terrio, Jr. and James Perodi**
- 54 OLD-TIME CRYSTAL RADIO**
Bring back the early days of radio with this vintage receiver. **Pat O'Brian**
- 61 EPROM PROGRAMMER**
Here's a low-cost programmer that let's you get started with EPROM projects. It programs all popular devices. **Lubomir B. Sawkiw**
- 75 PC SERVICE**
use our exclusive direct-etch foil patterns to make circuit boards for the satellite-TV descrambler. One side of the EPROM programmer board is shown this month.

RADIO

- 92 COMMUNICATIONS CORNER**
Closed captioning. **Herb Friedman**
- 94 ANTIQUE RADIOS**
Cabinets and speaker baffles. **Richard D. Fitch**

COMPUTERS

- Following page 88 **COMPUTER DIGEST**
Biofeedback, Dish positioning, and more.

TECHNOLOGY

- 12 VIDEO NEWS**
Inside the fast-changing video scene. **David Lachenbruch**
- 47 THE RAID ON HBO**
A look at how deliberate satellite interference can be accomplished and how Captain Midnight might have done it. **William Sheets and Rudolf Graf**
- 56 INSIDE THE TELEPHONE**
The phone is so commonplace, we don't think of the technology involved. It's worth a look. **Rudolf Graf and Calvin Graf**
- 86 SATELLITE TV**
What's happening on the Ku band. **Bob Cooper, Jr.**
- 82 ROBOTICS**
A look at a rover called Ernie. **Mark J. Robillard**

EQUIPMENT REPORTS

- 27 Heathkit Model GR-4500 Projection-TV Kit**
- 32 Dioconix 150 Portable Printer**

CIRCUITS AND COMPONENTS

- 67 ANALOG DELAY LINES**
Perfect circuits for audio experimenters. **Ray Marston**
- 85 SERVICE CLINIC**
Some thoughts on screwdrivers. **Jack Darr**
- 85 SERVICE QUESTIONS**
Solutions to servicing problems.
- 89 STATE OF SOLID STATE**
Condition sensing. **Robert F. Scott**

DEPARTMENTS

- 120 Advertising and Sales Offices**
- 120 Advertising Index**
- 14 Ask R-E**
- 4 Editorial**
- 4 Free Information Card**
- 22 Letters**
- 98 Market Center**
- 42 New Products**
- 6 What's News**

COVER 1



Our cover story this month is part of our continuing coverage of one of the most important issues in the field of satellite TV: signal scrambling and descrambling. The descrambler shown on the cover will decode programming encrypted using the Telease-Maast system. The theory behind the encoding is discussed and, of course, we describe how to restore the video to its proper form.

Before you build the descrambler, you should be aware that it may be unlawful to decode some scrambled satellite transmissions. But it's certainly not unlawful to learn as much as you can about descrambling! To learn more, turn to page 50.

NEXT MONTH

THE NOVEMBER ISSUE IS
ON SALE OCTOBER 2

BUILD A CLOSED-CAPTION DECODER

It decodes closed-captioning and Line 21 Teletext

BUILD AN EPROM PROGRAMMER

Part 2 shows you how to add a hex display and gang-programming capability. The solder side of the main board appears in PC Service.

BUILD A LATCHING CONTINUITY TESTER

Find those intermittent shorts and opens.

SATELLITE-TV SIGNAL DESCRAMBLING

Part 5 looks at the SSAVI scrambling technique.

TELEPHONE INSTALLATION ACCESSORIES

This month, you learned how the telephone system works. Next month, you'll learn how to make it work best for you.

THE EARLY DAYS OF RADIO

Another installment in our series of occasional articles on electronics nostalgia.

As a service to readers, RADIO-ELECTRONICS publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, RADIO-ELECTRONICS disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

Since some of the equipment and circuitry described in RADIO-ELECTRONICS may relate to or be covered by U.S. patents, RADIO-ELECTRONICS disclaims any liability for the infringement of such patents by the making, using, or selling of any such equipment or circuitry, and suggests that anyone interested in such projects consult a patent attorney.

Radio-Electronics

Hugo Gernsback (1884-1967) founder
M. Harvey Gernsback,
editor-in-chief, emeritus

Larry Steckler, EHF, CET, editor-in-chief
and publisher

EDITORIAL DEPARTMENT

Art Kleiman, editorial director
Brian C. Fenton, managing editor
Carl Laron, WB2SLR, associate editor
Jeffrey K. Holtzman,
assistant technical editor
Robert A. Young, assistant editor
Julian S. Martin, editorial associate
Byron G. Wels, editorial associate
M. Harvey Gernsback,
contributing editor
Jack Darr, CET, service editor
Robert F. Scott,
semiconductor editor
Herb Friedman,
communications editor
Bob Cooper, Jr. satellite-TV editor
Robert Grossblatt, circuits editor
David Lachenbruch,
contributing editor
Richard D. Fitch,
contributing editor
Mark J. Robillard, robotics editor
Teri Scaduto Wilson, editorial assistant

PRODUCTION DEPARTMENT

Ruby M. Yee, production director
Robert A. W. Lowndes,
editorial production
Andre Duzant, technical illustrator
Karen Tucker, advertising production
Geoffrey S. Weil, production traffic

CIRCULATION DEPARTMENT

Jacqueline P. Cheeseboro,
circulation director
Wendy Alanko,
circulation analyst
Theresa Lombardo,
circulation assistant

Cover photo by Robert Lewis

Typography by Mates Graphics

Radio-Electronics, Gernsback Publications, Inc., Executive Offices, 500-B Bi-County Blvd., Farmingdale, NY 11735, 516-293-3000

Radio-Electronics is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature*. Microfilm & Microfiche editions are available. Contact circulation department for details.

Advertising Sales Offices listed on page 120.



NEW! Lower Price Scanners

Communications Electronics,[™] the world's largest distributor of radio scanners, introduces new lower prices to celebrate our 15th anniversary.

Regency[®] MX7000-GR

List price \$699.95/CE price \$469.95
10-Band, 20 Channel • Crystalless • AC/DC
Frequency range: 25-550 MHz. continuous coverage and 800 MHz. to 1.3 GHz. continuous coverage. The Regency MX7000 scanner lets you monitor Military, Space Satellites, Government, Railroad, Justice Department, State Department, Fish & Game, Immigration, Marine, Police and Fire Departments, Broadcast Studio Transmitter Links, Aeronautical AM band, Aero Navigation, Paramedics, Amateur Radio, plus thousands of other radio frequencies most scanners can't pick up. The Regency MX7000 is the perfect scanner to receive the exciting 1.2 GHz. amateur radio band.

Regency[®] Z60-GR

List price \$299.95/CE price \$179.95/SPECIAL
8-Band, 60 Channel • No-crystal scanner
Bands: 30-50, 88-108, 118-136, 144-174, 440-512 MHz. The Regency Z60 covers all the public service bands plus aircraft and FM music for a total of eight bands. The Z60 also features an alarm clock and priority control as well as AC/DC operation. Order today.

Regency[®] Z45-GR

List price \$259.95/CE price \$159.95/SPECIAL
7-Band, 45 Channel • No-crystal scanner
Bands: 30-50, 118-136, 144-174, 440-512 MHz. The Regency Z45 is very similar to the Z60 model listed above however it does not have the commercial FM broadcast band. The Z45, now at a special price from Communications Electronics.

Regency[®] RH250B-GR

List price \$659.00/CE price \$329.95/SPECIAL
10 Channel • 25 Watt Transceiver • Priority
The Regency RH250B is a ten-channel VHF land mobile transceiver designed to cover any frequency between 150 to 162 MHz. Since this radio is synthesized, no expensive crystals are needed to store up to ten frequencies without battery backup. All radios come with CTCSS tone and scanning capabilities. A monitor and night/day switch is also standard. This transceiver even has a priority function. The RH250 makes an ideal radio for any police or fire department volunteer because of its low cost and high performance. A 60 Watt VHF 150-162 MHz. version called the RH600B is available for \$454.95. A UHF 15 watt version of this radio called the RU150B is also available and covers 450-482 MHz. but the cost is \$449.95.

NEW! Bearcat[®] 50XL-GR

List price \$199.95/CE price \$114.95/SPECIAL
10-Band, 10 Channel • Handheld scanner
Bands: 29.7-54, 136-174, 406-512 MHz. The Uniden Bearcat 50XL is an economical, hand-held scanner with 10 channels covering ten frequency bands. It features a keyboard lock switch to prevent accidental entry and more. Also order part # BP50 which is a rechargeable battery pack for \$14.95, a plug-in wall charger, part # AD100 for \$14.95, a carrying case part # VC001 for \$14.95 and also order optional cigarette lighter cable part # PS001 for \$14.95.

NEW! Scanner Frequency Listings

The new Fox scanner frequency directories will help you find all the action your scanner can listen to. These new listings include police, fire, ambulances & rescue squads, local government, private police agencies, hospitals, emergency medical channels, news media, forestry radio service, railroads, weather stations, radio common carriers, AT&T mobile telephone, utility companies, general mobile radio service, marine radio service, taxi cab companies, tow truck companies, trucking companies, business repeaters, business radio (simplex) federal government, funeral directors, veterinarians, buses, aircraft, space satellites, amateur radio, broadcasters and more. Fox frequency listings feature call letter cross reference as well as alphabetical listing by licensee name, police codes and signals. All Fox directories are \$14.95 each plus \$3.00 shipping. State of Alaska-RL019-1; State of Arizona-RL025-1; Baltimore, MD/Washington, DC-RL024-1; Buffalo, NY/Erie, PA-RL009-2; Chicago, IL-RL014-1; Cincinnati/Dayton, OH-RL006-2; Cleveland, OH-RL017-1; Columbus, OH-RL003-2; Dallas/Ft. Worth, TX-RL013-1; Denver/Colorado Springs, CO-RL027-1; Detroit, MI/Windsor, ON-RL008-3; Fort Wayne, IN/Lima, OH-RL001-1; Hawaii/Guam-RL015-1; Houston, TX-RL023-1; Indianapolis, IN-RL022-1; Kansas City, MO/KS-RL011-2; Long Island, NY-RL026-1; Los Angeles, CA-RL016-1; Louisville/Lexington, KY-RL007-1; Milwaukee, WI/Waukegan, IL-RL021-1; Minneapolis/St. Paul, MN-RL010-2; Nevada/E. Central CA-RL028-1; Oklahoma City/Lawton, OK-RL005-2; Orlando/Daytona Beach, FL-RL012-1; Pittsburgh, PA/Wheeling, WV-RL029-1; Rochester/Syracuse, NY-RL020-1; San Diego, CA-RL018-1; Tampa/St. Petersburg, FL-RL004-2; Toledo, OH-RL002-3. New editions are being added monthly. For an area not shown above call Fox at 800-543-7892. In Ohio call 800-621-2513.

NEW! Regency[®] HX1500-GR

List price \$369.95/CE price \$239.95
11-Band, 55 Channel • Handheld/Portable
Search • Lockout • Priority • Bank Select
Sidelit liquid crystal display • EAROM Memory
Direct Channel Access Feature • Scan delay
Bands: 29-54, 118-136, 144-174, 406-420, 440-512 MHz. The new handheld Regency HX1500 scanner is fully keyboard programmable for the ultimate in versatility. You can scan up to 55 channels at the same time including the AM aircraft band. The LCD display is even sidelit for night use. Includes belt clip, flexible antenna and earphone. Operates on 8 1.2 Volt rechargeable Ni-cad batteries (not included). Be sure to order batteries and battery charger from accessory list in this ad.

Bearcat[®] 100XL-GR

List price \$349.95/CE price \$203.95/SPECIAL
9-Band, 16 Channel • Priority • Scan Delay
Search • Limit • Hold • Lockout • AC/DC
Frequency range: 30-50, 118-174, 406-512 MHz. The world's first no-crystal handheld scanner now has a LCD channel display with backlight for low light use and aircraft band coverage at the same low price. Size is 1 3/4" x 7 1/2" x 2 1/4". The Bearcat 100XL has wide frequency coverage that includes all public service bands (Low, High, UHF and "T" bands), the AM aircraft band, the 2-meter and 70 cm. amateur bands, plus military and federal government frequencies. Wow...what a scanner! Included in our low CE price is a sturdy carrying case, earphone, battery charger/AC adapter, six AA Ni-cad batteries and flexible antenna. Order your scanner now.

Bearcat[®] 210XW-GR

List price \$339.95/CE price \$209.95/SPECIAL
8-Band, 20 Channel • No-crystal scanner
Automatic Weather • Search/Scan • AC/DC
Frequency range: 30-50, 136-174, 406-512 MHz. The new Bearcat 210XW is an advanced third generation scanner with great performance at a low CE price.

NEW! Bearcat[®] 145XL-GR

List price \$179.95/CE price \$102.95/SPECIAL
10 Band, 16 channel • AC/DC • Instant Weather
Frequency range: 29-54, 136-174, 420-512 MHz. The Bearcat 145XL makes a great first scanner. Its low cost and high performance lets you hear all the action with the touch of a key. Order your scanner from CE today.

TEST ANY SCANNER

Test any scanner purchased from Communications Electronics[™] for 31 days before you decide to keep it. If for any reason you are not completely satisfied, return it in original condition with all parts in 31 days, for a prompt refund (less shipping/handling charges and rebate credits).

NEW! Bearcat[®] 800XLT-GR

List price \$499.95/CE price \$317.95
12-Band, 40 Channel • No-crystal scanner
Priority control • Search/Scan • AC/DC
Bands: 29-54, 118-174, 406-512, 806-912 MHz. The Uniden 800XLT receives 40 channels in two banks. Scans 15 channels per second. Size 9 1/4" x 4 1/2" x 1 1/2."

OTHER RADIOS AND ACCESSORIES

Panasonic RF-2600-GR Shortwave receiver \$179.95
RD95-GR Uniden Remote mount Radar Detector..... \$128.95
RD55-GR Uniden Visor mount Radar Detector..... \$98.95
RD9-GR Uniden "Passport" size Radar Detector..... \$199.95
BC-WA-GR Bearcat Weather Alert" \$49.95
DX1000-GR Bearcat shortwave receiver SALE..... \$349.95
PC22-GR Uniden remote mount CB transceiver..... \$99.95
PC55-GR Uniden mobile mount CB transceiver..... \$59.95
R1060-GR Regency 10 channel scanner SALE..... \$92.95
MX3000-GR Regency 30 channel scanner..... \$229.95
XL156-GR Regency 10 channel scanner..... \$139.95
UC102-GR Regency VHF 2 ch. 1 Watt transceiver..... \$124.95
P1405-GR Regency 5 amp regulated power supply..... \$69.95
P1412-GR Regency 12 amp reg. power supply..... \$164.95
MA256-GR Drop-in charger for HX1200 & HX1500..... \$84.95
MA518-GR Wall charger for HX1500 scanner..... \$14.95
MA516-GR Carrying case for HX1500 scanner..... \$14.95
MA257-GR Cigarette lighter cord for HX12/1500..... \$19.95
MA917-GR Ni-Cad battery pack for HX1200..... \$34.95
SMMX7000-GR Svc. man. for MX7000 & MX5000..... \$19.95
SMMX3000-GR Service man. for Regency MX3000..... \$19.95
B-4-GR 1.2 V AAA Ni-Cad batteries (set of four)..... \$9.95
B-8-GR 1.2 V AA Ni-Cad batteries (set of eight)..... \$17.95
FB-E-GR Frequency Directory for Eastern U.S.A..... \$14.95
FB-W-GR Frequency Directory for Western U.S.A..... \$14.95
ASD-GR Air Scan Directory..... \$14.95
SRF-GR Survival Radio Frequency Directory..... \$14.95
TSG-GR "Top Secret" Registry of U.S. Govt. Freq..... \$14.95
TIC-GR Techniques for Intercepting Comm..... \$14.95
RRF-GR Railroad frequency directory..... \$14.95
CIE-GR Covert Intelligent, Elect. Eavesdropping..... \$14.95
A60-GR Magnet mount mobile scanner antenna..... \$35.95
A70-GR Base station scanner antenna..... \$35.95
USAMM-GR Mag mount VHF/UHF ant. w/ 12' cable..... \$39.95
USAK-GR 3/4" hole mount VHF/UHF ant. w/ 17' cable..... \$35.95
USATLM-GR Trunk lip mount VHF/UHF antenna..... \$35.95
Add \$3.00 shipping for all accessories ordered at the same time.
Add \$12.00 shipping per shortwave receiver.
Add \$7.00 shipping per scanner and \$3.00 per antenna.

BUY WITH CONFIDENCE

To get the fastest delivery from CE of any scanner, send or phone your order directly to our Scanner Distribution Center. Michigan residents please add 4% sales tax or supply your tax I.D. number. Written purchase orders are accepted from approved government agencies and most well rated firms at a 10% surcharge for net 10 billing. All sales are subject to availability, acceptance and verification. All sales on accessories are final. Prices, terms and specifications are subject to change without notice. All prices are in U.S. dollars. Out of stock items will be placed on backorder automatically unless CE is instructed differently. A \$5.00 additional handling fee will be charged for all orders with a merchandise total under \$50.00. Shipments are F.O.B. Ann Arbor, Michigan. No COD's. Most products that we sell have a manufacturer's warranty. Free copies of warranties on these products are available prior to purchase by writing to CE. Non-certified checks require bank clearance. Not responsible for typographical errors.

Mail orders to: Communications Electronics, Box 1045, Ann Arbor, Michigan 48106 U.S.A. Add \$7.00 per scanner for R.P.S./U.P.S. ground shipping and handling in the continental U.S.A. For Canada, Puerto Rico, Hawaii, Alaska, or APO/FPO delivery, shipping charges are three times continental U.S. rates. If you have a Discover, Visa or Master Card, you may call and place a credit card order. Order toll-free in the U.S. Dial 800-USA-SCAN. In Canada, order toll-free by calling 800-221-3475. WUI Telex anytime, dial 671-0155. If you are outside the U.S. or in Michigan dial 313-973-8888. Order today.

Scanner Distribution Center[™] and CE logos are trademarks of Communications Electronics Inc.
† Bearcat is a registered trademark of Uniden Corporation.
‡ Regency is a registered trademark of Regency Electronics Inc. AD #070286-GR

Copyright © 1986 Communications Electronics Inc.

For credit card orders call
1-800-USA-SCAN

**COMMUNICATIONS
ELECTRONICS INC.**

Consumer Products Division
P.O. Box 1045 □ Ann Arbor, Michigan 48106-1045 U.S.A.
Call 800-USA-SCAN or outside U.S.A. 313-973-8888
CIRCLE 79 ON FREE INFORMATION CARD



EDITORIAL

I just received a letter insisting that the editorial content of **Radio-Electronics** is being bought by our advertisers. The letter mentioned Dick Smith Electronics specifically and said: "Isn't it funny that one month you get this new advertiser out of nowhere, and then feature their kits in numerous articles?"

That's a very easy question to answer, because **Radio-Electronics** has a strict policy that separates our Editorial and Advertising departments. Even if Dick Smith Electronics buys twenty pages of advertising per issue, we'll never give one of their kits any coverage if we don't think that kit deserves it. On the other hand, if they never bought one single page of advertising, our January 1986 issue would still have featured their \$99 satellite-TV receiver, and it would still have been our cover story.

Take a look at the projects that we've featured over the last few months. Our July cover displayed a 1.2-GHz frequency counter that was designed and sold by a small company in Florida that has never (as far as I know) advertised with us. Our August cover featured a radar speed-gun calibrator that is available in kit form from another company that has never advertised in this magazine. Last month's cover shows a stun gun that is available as a kit from a company that usually runs a 1/6-page ad, and this month's cover story is available as a kit from a company that has run a one-inch classified ad a few times.

What has me a little confused is that I don't really understand what some readers are complaining about. Are they saying that we

shouldn't cover a great construction project because it's commercially available as a kit? Just because a circuit is available as a kit doesn't mean we shouldn't cover it in **Radio-Electronics**. When we run a story based on a kit, we treat it as we do every other construction project—with complete schematics, circuit descriptions, and printed-circuit patterns. Remember: We're not just covering a kit; we're covering circuits and technology.

We do our best to ensure that you don't have to buy the kit or specific parts from a specific supplier. The circuit is there for you to build whether you buy parts or pull them out of your junkbox. But don't forget that, for many of our readers, having a supplier of parts and complete kits can make the difference between building or not building a project.

Now that I've re-affirmed our long-standing policy, it seems like a good time to offer an invitation to all individuals, companies, and corporations, whether or not you advertise in **Radio-Electronics**: If you have an electronics project that you think will interest our readers, let me know about it.



Brian C. Fenton
Managing Editor



ELECTRONICS, INC.

TEST EQUIPMENT BONANZA

POWER SUPPLIES

B&K		
1601	0-50V/2A	\$345.00
1650	2 @ 0-25V/5A, 5V5A	350.00

TOPWARD

2202	0-20v/2a	150.00
2203	0-20v/3a	165.00
2301	0-30v/1a	150.00
2302	0-30v/2a	165.00
2303	0-30v/3a	180.00
2306	0-30v/6a	270.00
2310	0-30v/10a	450.00
2601	0-60v/1a	165.00
2603	0-60v/3a	280.00
2606	0-60v/6a	490.00

TOPWARD TRIPLES

4302	2 @ 0-30v/2a, 5v3a	270.00
4303	2 @ 0-30v/3a, 5v3a	325.00

TOWARD WITH DIGITAL MTR

2302D	0-30v/2a	195.00
2303D	0-30v/3a	215.00
4302D	2 @ 0-30v/2a, 5v3a	340.00
4303D	2 @ 0-30v/3a, 5v3a	395.00

VIZ DIGITAL METERS

WP-705A	0-50v/2a	330.00
WP-706A	0-25v/2a	327.00
WP-707A	2 @ 0-25v/2a	419.00
WP-708A	2 @ 20v/2a, 5v4a	453.00
WP-709	5or13v/7.5a	329.00
WP-711A	0-40v/1a	254.00
WP-712A	0-20v/2a	266.00
WP-713A	2 @ 0-20v/1a	349.00
WP-714A	2 @ 0-20v/7.5a, 5v4a	372.00
WP-715A	0-36v/3a	319.00
WP-716A	2 @ 0-24v/0.5a, 5v4a	369.00
		349.00
WP-717A	0-20v/5a	349.00

GLOBAL

1300	2 @ 5-18v/25a, 5v1a	109.00
1301	2 @ 5-18v/5a, 5v1a	199.00
1302	2 @ 30v/1a, 5v5a	299.00

POWER DESIGN 5YR WRNTY

5015V	0-50v/1.5a	450.00
4050	0-40v/5a	595.00

COUNTERS/FREQUENCY ONLY



TOPWARD

TFC-1201	100MHZ	195.00
TFC-1204	650MHZ	305.00
TFC-1207	1000MHZ	380.00

SIMPSON

710	80MHZ	199.00
-----	-------	--------

VIZ

4WD-754	100MHZ	219.00
WD-756	1GHZ	399.00

B&K DYNASCAN

1803	100MHZ	149.00
------	--------	--------

LEADER

LDC-831	150MHZ	188.00
GLOBAL		
MAX-100A	100MHZ	99.00
6000	650MHZ	379.00

COUNTERS/UNIVERSAL

TOWARD

TFC-1211	100MHZ	270.00
TFC-1214	650MHZ	395.00
TFC-1217	1GHZ	490.00

VIZ

WD-755	125MHZ	255.00
WD-757	1GHZ	489.00

LEADER

LDC-822	80MHZ	319.00
LDC-823S	250MHZ	424.00
LDC-824S	520MHZ	520.00
LDC-825	1GHZ	1,197.00

B&K DYNASCAN

1805	80MHZ	259.00
1822	175MHZ	399.00
1851	520MHZ	509.00

FLUKE

1900A	80MHZ	369.00
1910A	125MHZ	513.00

GLOBAL

5001	10MHZ	359.00
------	-------	--------

FUNCTION GENERATORS

TOPWARD

TFG-8101	2MHZ	185.00
TFG-8104	2MHZ	

AM/FM MOD.

TFG-8111	2MHZ	240.00
+6 DIG 100MHZ COUNTER		275.00
TFG-8114	5MHZ SWEEP	
+5 DIG 100MHZ COUNTER		495.00

SIMPSON

420A	1MHZ	189.00
420D	1MHZ+BAT	219.00

B&K DYNASCAN

3010	1MHZ	175.00
3011	2MHZ+COUNTER	175.00
3020	2MHZ+SWEEP	349.00
3025	5MHZ+SWEEP	420.00

GLOBAL

2001	100KHZ	149.00
2002	2MHZ	199.00

LEADER

LFG-1300S	2MHZ+SWEEP	439.00
LFG-1310	10MHZ+SWEEP	989.00

HANDHELD DIGITAL METERS

FLUKE

73	.7% 3 1/2	71.00
75	.5% 3 1/2	89.00
8060A	.04% 4 1/2 TRMS	319.00
8062A	.05% 4 1/2 TRMS	265.00
8026B	.1% 3 1/2 TRMS	179.00
8020B	.1% 3 1/2	179.00

HITACHI

3525	.25% 3 1/2 AUTO	64.00
QTY 3EA.+	SPECIAL	54.00
3510	.1 3 1/2 AUTO	79.00
QTY 3EA.+	SPECIAL	67.00

B&K DYNASCAN

2802	.7% 3 1/2 PROBE	69.00
2820	.4% 4 1/2 TRMS	297.00

SIMPSON

470	.15% 3 1/2	123.00
474	.03% 4 1/2	197.00

KEITHLEY (TEGAM)

130A	.25% 3 1/2	125.00
132F	.25%+TEMP. 3 1/2	235.00
132C	.25%+TEMP. 3 1/2	235.00
135A	.05% 4 1/2	245.00

BENCH DIGITAL METERS

FLUKE

8010A	.1% 3 1/2	249.00
8012A	.1% 3 1/2	329.00
8050A	.03% 4 1/2	359.00

B&K DYNASCAN

2834	.04% 4 1/2 TRMS	440.00
------	-----------------	--------

KEITHLEY (TEGAM)

169	.25% 3 1/2	179.00
179A	.04% 4 1/2 TRMS	399.00

DATA PRECISION

248R	.03% 4 1/2 TRMS	339.00
2590R	.004% 5 1/2 TRMS	789.00
248	.05% 4 1/2 TRMS	379.00

SIMPSON

461-2	.1% 3 1/2 TRMS	220.00
463	.1% 3 1/2 BAT.	189.00

HITACHI CCTV

VIDICON CAMERAS

HV-720/721	175.00
HV-730/731	225.00

NEWICON CAMERAS

HV-725/726	510.00
HV-735/736	599.00

SOLID STATE CAMERAS

KP-120	775.00
KP-130A	HIGH RESOLUTION
KPC-100	COLOR
	1,249.00
	1,575.00

MONITORS B&W

VM-900	9"/500LINE	135.00
VM-910	9"/500LINE/RM	176.00
VM-906A	9"/700LINE	220.00
VM-129	12"/700LINE	289.00
VM-173	17"/700LINE	329.00

LENS COSMICAR C MOUNT

B1214DEX-2	12MM	225.00
C1614EX-2	16MM	189.00
C5018ES-3	50MM	135.00
C7518ES-3	75MM	275.00

OSCILLOSCOPES



STANDARD BENCH HITACHI

V212	2CH20MHZ	489.00
V222	2CH20MHZ	579.00
V223	2CH20MHZDLYT.B.	649.00
V422	2CH40MHZ	759.00
V423	2CH40MHZDLYT.B.	809.00
V650	3CH60MHZDLYT.B.	1,019.00
V1050	4CH100MHZDLYT.B.	1,359.00

HAMEG W/COMPONENT TESTER

203-6	2CH20MHZ	489.00
204-2	2CH20MHZDLYT.B.	629.00
605	2CH60MHZDLYT.B.	899.00

LEADER

LBO-524L	2CH40MHZDLYT.B.	789.00
LBO-516	3CH100MHZDLYT.B.	1,195.00

IWATSU

SS-5705	3CH40MHZDLYT.B.	849.00
SS-5710	4CH60MHZDLYT.B.	1,179.00
SS-5710D	+DVM,COUNTER	1,895.00
SS-5711	4CH100MHZDLYT.B.	1,599.00
SS-5711D	+DVM,COUNTER	2,370.00
SS-5712	4CH200MHZDLYT.B.	2,850.00

B&K

1524	2CH20MHZ	649.00
1541	2CH40MHZ	715.00
1564	3CH60MHZDLYT.B.	1,075.00

MINI PORTABLES

HITACHI

V209	2CH20MHZ	875.00
V509	2CH50MHZDLYT.B.	1,295.00

LEADER

LBO-323	2CH20MHZ	1,079.00
LBO-325	2CH60MHZDLYT.B.	1,359.00

IWATSU

SS-3510	2CH50MHZ	1,600.00
---------	----------	----------

B&K

1420	2CH15MHZ	698.00
------	----------	--------

CRT READOUT

HITACHI

V680	3CH60MHZDLYT.B.	1,395.00
V1070A	2CH100MHZDLYT.B.	1,695.00
V1100A	4CH100MHZDLYT.B.	2,250.00
V1150	4CH150MHZDLYT.B.	2,750.00

STORAGE ANALOG

HITACHI

V134	2CH10MHZ 50DIV/MS	1,495.00
------	-------------------	----------

STORAGE DIGITAL

HAMEG

205	2CH20MHZ100KHZ	799.00
208	2CHMHZ20MHZ	2,380.00
208-1	WITH I FEE	2,860.00

B&K


2520	2CH20MHZ2Ms/S	1,600.00
------	---------------	----------

LEADER

LBO-5825	2CH35MHZ5Ms/S	2,690.00
----------	---------------	----------

WHAT'S NEWS

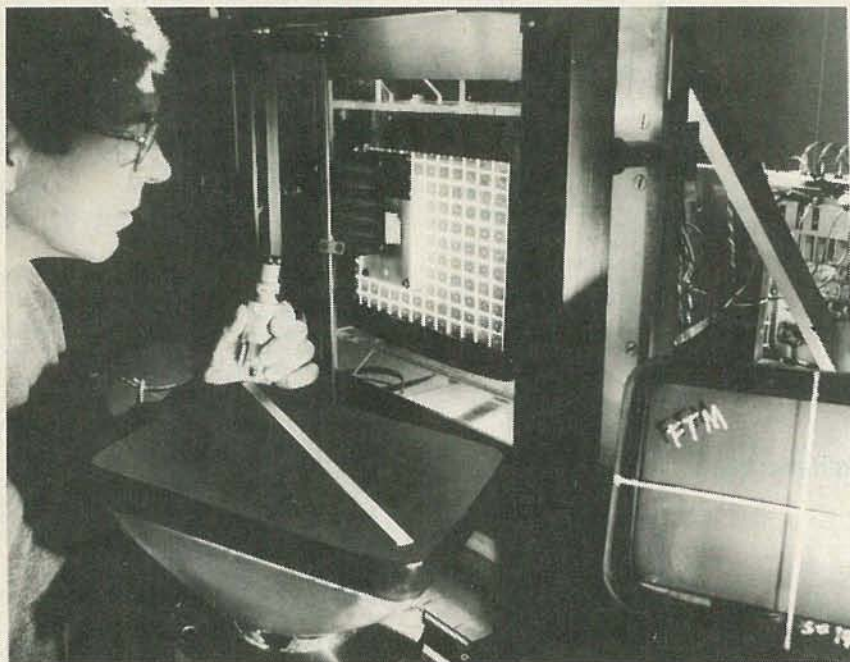New CR display tube has flat tension mask



ZENITH'S NEW FTM COLOR PICTURE TUBE has a perfectly flat face and truly square corners, so straight lines appear straight, rather than curved, as on a conventional picture tube.

A new cathode-ray display tube with a perfectly flat and almost reflection-free faceplate was announced by Zenith at the recent annual symposium of the Society for Information Display. The new Flat Tension Mask (FTM) tube is 80 percent brighter than a conventional tube at equivalent levels of resolution and contrast, and has a 70 percent increased contrast ratio, as well as greater resolution and color fidelity than conventional tubes. It is freer from glare and reflection because it doesn't reflect light like a convex tube, and because its flat surface can be economically treated with both anti-glare and anti-reflection coatings.

In a conventional color CRT, a curved shadow mask is supported by a frame and suspended by springs inside the tube. As elec-

tron beams strike the mask, it heats up and moves. In the new Zenith FTM, the shadow mask is held under tension directly behind the tube's flat glass faceplate. It does not move even at brightness levels that cause discolored images in conventional tubes.

The new mask is sealed to the tube with melted ground glass (frit-sealed). Heated by that process, the mask goes into tension upon cooling to room temperature. Stretched tight, the mask is virtually immune to the deformation that plagues conventional shadow masks.

The flatness of the tube also simplifies the problem of a protective faceplate. Ordinary flat glass can be used for the plate, resulting in lower cost and facilitating both anti-reflection and anti-glare surface treatments.

Electrical measurements may be made with light

The National Bureau of Standards is reviewing the economic and technical advantages that may result from using new optical technologies for measuring voltages and current. Those advantages may be particularly great in power systems, where such measurements are traditionally made with bulky but accurate transformer systems.

The advantages are: isolation from electrical circuits (important at some of the extremely high voltages used in power transmission); high speed (optical methods have been used to measure nanosecond pulses), and economy (optical fibers are much cheaper than transformers).


Optical measurements depend on three opto-electric phenomena: the Faraday effect, in which the application of a magnetic field to a suitable material produces a change in the material's index of refraction; the Pockels effect, in which the application of an electric field produces the same kind of change, and the Kerr effect, also one in which the index of refraction is changed by an electric field. In the Pockels effect, the change is proportional to the change in the field; in the Kerr effect it is proportional to the square of the change.

Various methods may be used to apply those effects to electrical measurement. For example, a number of turns of optical fiber may be coiled around a conductor. Light from a laser is beamed through the fiber. Changes in refraction due to the current result in changes in the intensity of the light transmitted by the fiber. The output of the optical fiber is focused on a photodiode that detects those changes in output and transforms them into changes in electrical current.

R-E



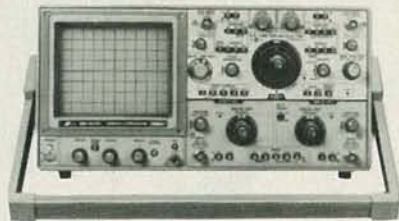IWATSU OSCILLOSCOPES...QUALITY BY DESIGN!



**DC-60 MHz
4 Input, 8 Trace, Portable**

- Typical Frequency Of From DC To 70 MHz, -3 dB (10 MHz margin over the specified frequency response)
- Reliable Time Difference Between Channels
- Built-In TV Sync Separator
- 3 Year Warranty

SS-5710 — \$1245
 SS-5710C — With Counter \$1799
 SS-5710D — With Counter/DMM \$1995
 CIRCLE 64 ON FREE INFORMATION CARD



**DC-100 MHz
4 Input, 8 Trace, Portable**

- Typical Frequency Of From DC To 120 MHz, -3 dB (20 MHz margin over the specified frequency response)
- Reliable Time Difference Between Channels
- Jitterless Circuitry For Stable Triggering
- 3 Year Warranty

SS-5711 — \$1695
 SS-5711C — With Counter \$2295
 SS-5711D — With Counter/DMM \$2495
 CIRCLE 198 ON FREE INFORMATION CARD



DC-40 MHz

SS-5705—DC-40 MHz SS-5706—DC-30 MHz

- 3 Input, 6 Trace (SS5705); 3 Input, 3 Trace (SS5706)
- Versatile Trigger Capability With TV-SYNC
- Jitter-Free Circuitry And Variable Hold-Off
- High Accuracy For V And H ($\pm 2\%$)
- Accurate Calibrator (Amplitude $\pm 1\%$ And Frequency $\pm 1\%$)

SS-5705 — \$899
 SS-5706 — \$749
 CIRCLE 201 ON FREE INFORMATION CARD



**DC-100 MHz
Digital Storagecope**

- 100 MHz Analog And Digital Bandwidth
- 40 Ms/s Sampling Rate
- Cursor Measurement (Analog And Digital)
- 4 Waveform & 7 Set-Up Memories
- GO/NO GO Judgement

DS-6121 — \$5550
 DS-6121A — With Envelope Mode \$5950
 CIRCLE 202 ON FREE INFORMATION CARD



**DC-200 MHz
4 Input, 8 Trace, Portable**

- Reliable Time Difference Between Channels
- Freerunning Ground Facility
- High-Grade 6 Inch Quadrupole-Lens, Dome Mesh CRT
- Combination Trigger Probe (SS-0071) Optional
- 3 Year Warranty

SS-5712 — \$2999
 CIRCLE 203 ON FREE INFORMATION CARD



**DC-10 MHz
Digital Storagecope**

- Built-in GP-IB (General-Purpose Interface Bus)
- High-Brightness CRT
- 3-Channel 10 MHz Oscilloscope Function
- 8-bit x 2048 Word/Channel, 1 μ s/word Digital Storage
- Both Real-Time And Digital Storage Waveforms Can Be Displayed On The CRT Simultaneously

SS-5802 — \$2750
 CIRCLE 204 ON FREE INFORMATION CARD




OSCILLOSCOPES

Instruments For Your Success



IWATSU INSTRUMENTS, INC.

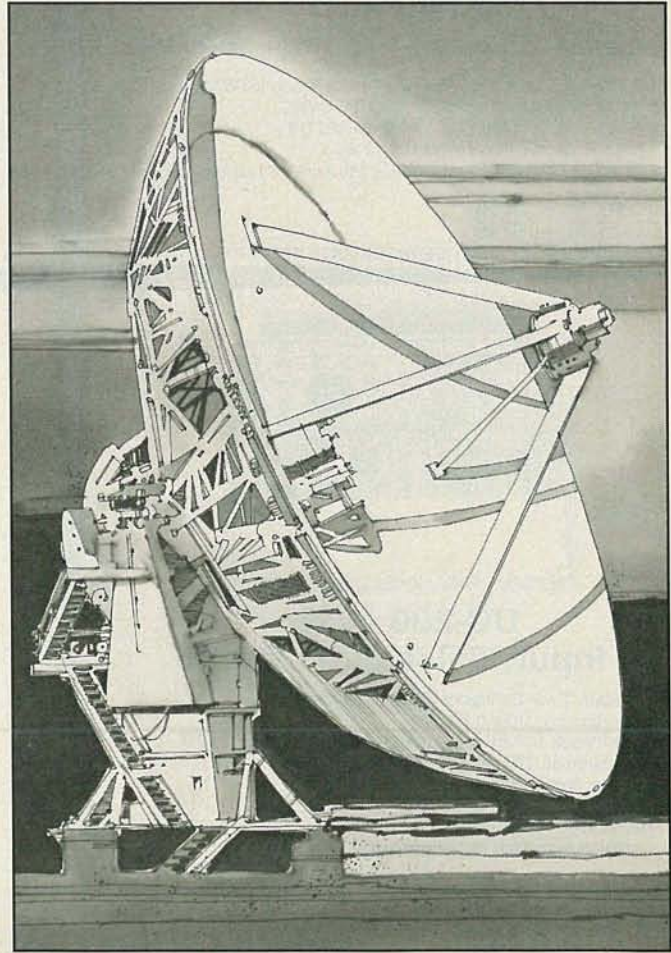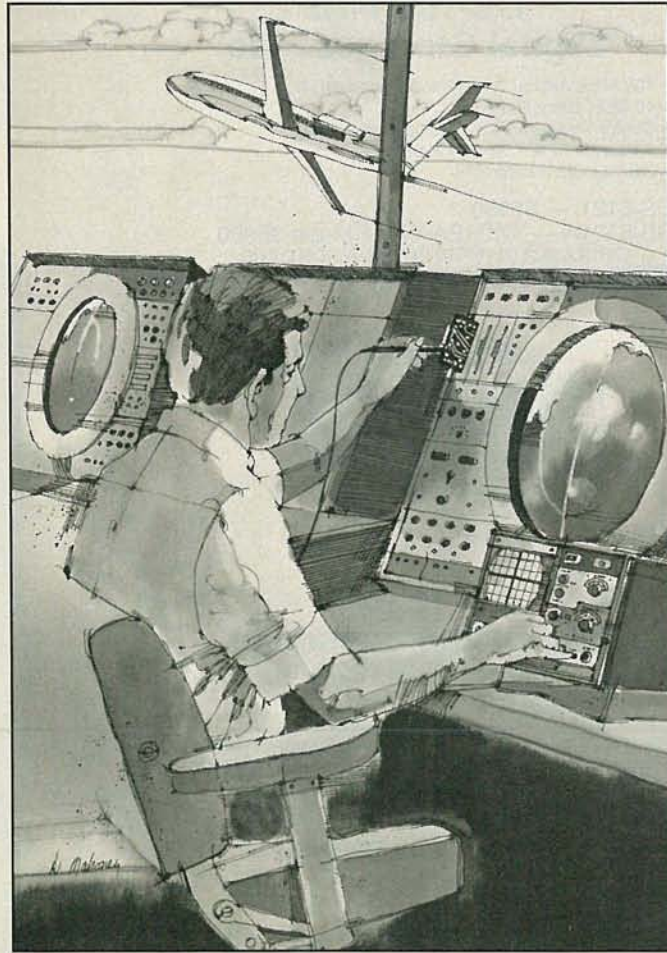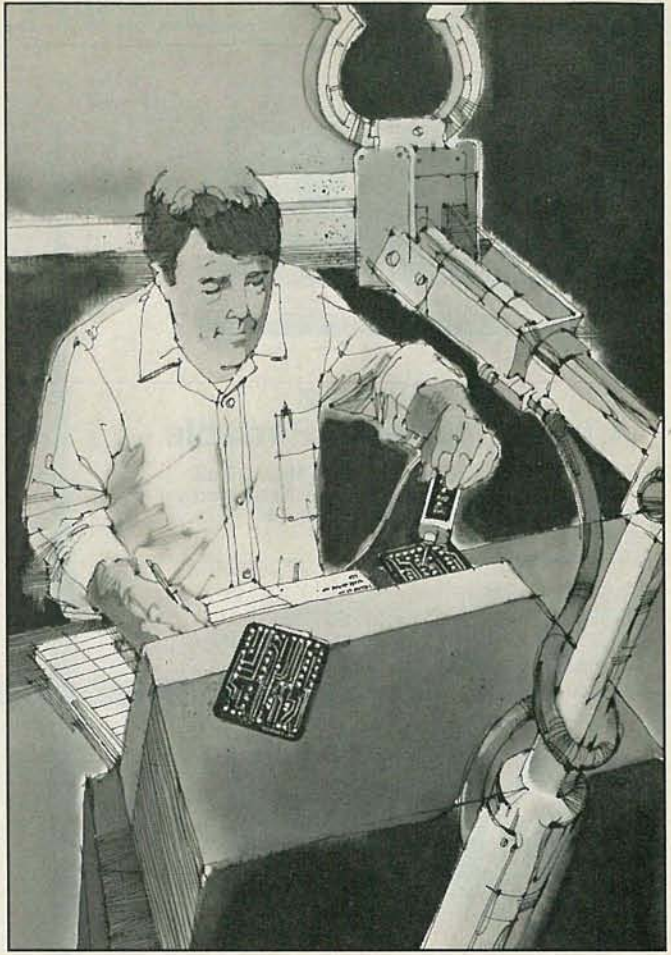430 Commerce Boulevard, Carlstadt, NJ 07072 PHONE: (201) 935-5220; TLX. 710-989-0255



CIE MAKES THE WORLD OF ELECTRONICS YOURS.

Today's world is the world of electronics. To be part of it, you need the right kind of training, the kind you get from Cleveland Institute of Electronics, the kind that can take you to a fast growing career in business, aerospace, medicine, science, government, communications, and more.

Specialized training.

You learn best from a specialist, and that's CIE. We're the leader in teaching electronics through independent study, we teach only electronics and we've been doing it for over 50 years. You can put that experience to work for you just like more than 25,000 CIE students are currently doing all around the world.

Practical training.

You learn best with practical training, so CIE's Auto-Programmed® lessons are designed to take you step-by-step, principle-by-principle. You also get valuable hands-on experience at every stage with sophisticated electronics tools CIE-designed for teaching. Our 4K RAM Microprocessor Training Laboratory, for example, trains you to work with a broad range of computers in a way that working with a single, stock computer simply can't.

Personalized training.

You learn best with flexible training, so we let you choose from a broad range of courses. You start

with what you know, a little or a lot, and you go wherever you want, as far as you want. With CIE, you can even earn your Associate in Applied Science Degree in Electronics Engineering Technology. Of course, you set your own pace, and, if you ever have questions or problems, our instructors are only a toll-free phone call away.

The first step is yours.

To find out more, mail in the coupon below. Or, if you prefer, call toll-free **1-800-321-2155 (in Ohio, 1-800-523-9109)**. We'll send a copy of CIE's school catalog and a complete package of enrollment information. For your convenience, we'll try to have a representative contact you to answer your questions.

CIE Cleveland Institute of Electronics

1776 East 17th St., Cleveland, Ohio 44114

YES! I want to get started. Send me my CIE school catalog including details about the Associate Degree Program. I am most interested in:

- | | |
|----------------------------------------------|-----------------------------------------------------------|
| <input type="checkbox"/> computer repair | <input type="checkbox"/> television/high fidelity service |
| <input type="checkbox"/> telecommunications | <input type="checkbox"/> medical electronics |
| <input type="checkbox"/> robotics/automation | <input type="checkbox"/> broadcast engineering |
| <input type="checkbox"/> other _____ | |

Print Name _____

Address _____ Apt. _____

City _____ State _____ Zip _____

Age _____ Area Code/Phone No. _____

Check box for G.I. Bulletin on Educational Benefits

- Veteran Active Duty

MAIL TODAY!

OR CALL TOLL FREE
1-800-321-2155
(In Ohio, 1-800-523-9109)

RE-46

VIDEO NEWS



DAVID LACHENBRUCH
CONTRIBUTING EDITOR

• **Beta I returns.** In the beginning there was Beta I, which delivered excellent picture quality, but only about one hour of recording time. Then came VHS, which initially delivered two hours of recording time, but later could allow tapes as long as eight hours to be made. Of course, the longer tapes came at the expense of picture quality. The Beta camp responded with Beta II and later Beta III, which also offered longer recording times at the expense of video quality.

Much to the dismay of some Betaphiles, in the rush to offer longer playing time, the Beta group ceased to offer the Beta I recording speed, although some recorders that could playback Beta I tapes were still available. Those Betaphiles will be pleased to learn that Beta I has made a comeback. Sony's latest top-of-the-line SuperBeta VCR will record and play back in the Beta I speed as well as in all the others. In addition it has a wireless remote control containing a professional-type jog-and-shuttle dial, which can operate two VCR's and control editing functions previously possible only with professional-type VCR's. The combination of the Beta I speed and the SuperBeta highband recording-technology provides what probably is the best picture available from a consumer VCR.

Tubeless TV. Trying to estimate the size of the market for TV-sets that use LCD's (*Liquid Crystal Displays*) instead of picture tubes is an exercise in futility. There are now four major brands offering those pocket TV's—Casio, Citizen, Epson, and Seiko—and their estimates of sales this year vary from 350,000–400,000 (Casio) to more than 2,000,000 (Citizen). The fact remains that those little sets are coming into the U.S. in increasing numbers, in both color and monochrome models, and that their picture quality is constantly improving. Some proponents estimate that the LCD TV's—after large-screen versions are developed—will represent 40-50% of all TV sets sold by 1995. No matter what, one thing is certain—most major TV-set manufacturers are seriously considering moving into the LCD-TV field, now occupied almost exclusively by Japanese watch and calculator makers.

Swansong for Beta? Although the Beta VCR-format is still preferred by many videophiles—particularly those who pioneered in the field—it seems to be fading from the mass-market scene. In this space we've enumerated the defections from the Beta camp in the past, as major Beta manufacturers have added VHS units to their lines. More recently, NEC, which was an original member of the Beta group and later added VHS, said it was phasing out of Beta in the U.S. because of low demand. Toshiba, whose VHS sales now eclipse those of its Beta line, is adding no new Beta models for the U.S. and says it will continue to supply Beta units upon demand. The only home VCR manufacturers in the Beta camp that do not now offer VHS models are Beta's inventor, Sony, and its affiliate, Aiwa. Sony is now pushing 8mm for both camcorders and home decks, while continuing to offer Beta in the SuperBeta models, which produce pictures demonstrably better than the original Beta units.

• **HDTV on UHF band?** High-definition TV may be coming down to earth. Many of the proposals for the new super service (more than 1,000 lines, widescreen aspect ratio) have centered on inaugurating it via direct satellite transmission, or possibly over special cable channels. An industrywide working group, Advanced Television Systems Committee (ATSC), has been looking into the entire subject. Now, for the first time, there are strong hints that HDTV could actually start on the standard broadcast frequencies—in the UHF band—as a compatible service. Here's how it would work: A UHF channel would transmit a standard 525-line picture, receivable by any conventional TV set. An adjacent channel would simultaneously transmit the additional information needed to provide a 1,050-line widescreen picture to special advanced HDTV receivers. (UHF probably would have to be used because there's no room in the VHF band for such adjacent-channel broadcasts.) CBS and others have already outlined basic parameters for such compatible systems, and there are indications that the FCC would look with favor on proposals for testing. **R-E**

BP Video Processor gives you precision picture control.



You'll get 5 units in one! The BP Video Processor functions as a **Stabilizer** to end video guard distortion...as an **Enhancer** to provide peak sharpness...as an **RF Converter** to feed signals from video cameras, computer or VCR in your TV...as a **Video Fader** for professional fade-in and fade-out effects...and as a **Dual Output Distribution Amplifier** to send TV signals to other sets.

\$79⁹⁵

Model V-1880

Preserve your memories on videotape



Macro Lens Attachment
Model V-14 **\$14⁹⁵**

The video-cine converts your slides and home movies to VCR tape with any video camera. This easy to use model features precision optics and rear projection. Macro lens attachment available for cameras without close-up capability.

Model V-1701
\$34⁹⁵

Increase the life of your VCR head and tape with BP VHS or Beta Tape Rewinders.



Don't risk worn-down heads and tape damage by rewinding on your VCR. BP Tape Rewinders feature counter, soft button action, controlled speed and automatic shutoff.

Model V-7779
VHS **\$59⁹⁵**

Model V-7780
BETA **\$59⁹⁵**

A small investment...buys
BIG VIDEO
PERFORMANCE!
Get the most out of your video and stereo equipment

Add Stereo to your Video



The mini speaker with maxi sound. 3" long throw woofer; 1" soft dome tweeter; 2" extended midrange speaker. Max power 50 watts.

\$29⁹⁵
per pair

Model HF-9

FM Antenna fine-tunes your fm/stereo reception.



You'll get clear, crisp, undistorted sound from this high quality, directional FM antenna. Mounts instantly indoors, comes complete with coaxial cable and transformer.

\$34⁹⁵

Model FM-9700

Get true-to-life color...and reduce noise...with Audio Video Color Processor.



This versatile color processor corrects off color tape, eliminates single color dominance and restores sharpness in detail. Plus, it stabilizes copy guarded tapes and filters audio noise.

\$149⁹⁵

Model V-1895

Send for **FREE** catalog of hundreds of items. Money orders, checks accepted. C.O.D.'s require 25% deposit.

Fordham

260 Motor Parkway, Hauppauge, NY 11788



Toll Free
800-645-9518
In NY State **800-832-1446**


Service & Shipping Charge Schedule
Continental U.S.A.

FOR ORDERS	ADD
\$25-\$100	\$4.50
\$101-\$250	\$6.00
\$251-500	\$8.00
\$501-750	\$10.50
\$751-1,000	\$12.50
\$1,001-1,500	\$16.50
\$1,501-2,000	\$20.00
\$2,001 and up	\$25.00

ASK R-E

WRITE TO:

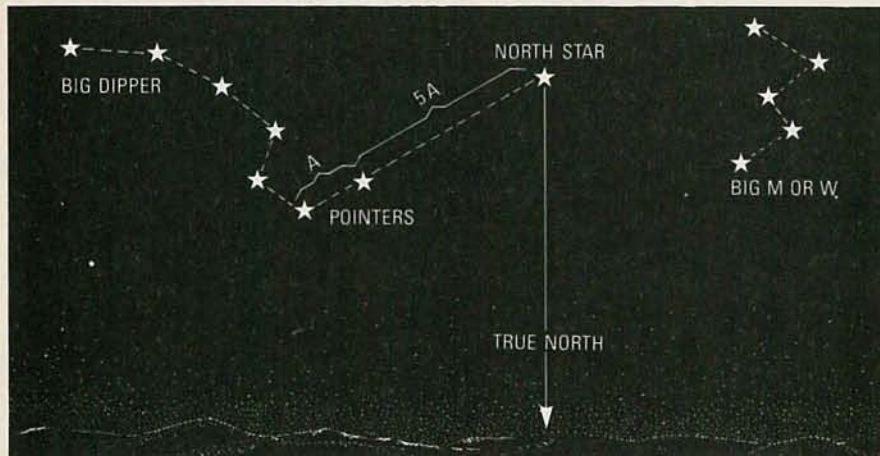ASK R-E
Radio-Electronics
500-B Bi-County Blvd.
Farmingdale, NY 11735



WHERE IS TRUE NORTH?

I have all the components for a TVRO system and I'm ready to install the dish. I plan to use my old magnetic army compass to orient the dish. But some "experts," including my son, say that I can't use the compass until I correct its readings for "True North," whatever that is. The compass seems to work OK and points north as far as I can tell. What are my friends talking about? How can I fix the compass?—H. W. McD., Orlando, FL.

Barring outside influences that might be exerted on the compass needle by large steel structures, nearby power lines, or magnetic ore deposits, a magnetic compass points to the *magnetic* North Pole, which is not located at exactly the same place as the Earth's *geographic* North Pole. It is some distance away in a location that is constantly and slowly changing with respect to the geographic or true North Pole.

From most points on the globe, there will be an angle between true north and the magnetic north indicated by the compass needle.

The angle of separation between these two poles is called variation and is measured in degrees east or west of true north. Variation varies with locality and time. In some areas, magnetic north is west of true north; that is called variation west or westerly variation. On the other hand, when magnetic north is east of true north, we have easterly variation.

At a number of points through the southeastern and central United States there is no (zero degrees of) variation, and the directions for true north and magnetic north coincide. An imaginary line passing through the points of zero-variation is called the *agonic* line. As a rule, magnetic variation ranges from about 25 east in the Washington State/British Columbia area to about 15 west in the Maine/Nova Scotia area.

So, to correct your compass to get a heading for true north, you must first determine the amount and direction of variation. You can get this from marine or aviation navigation charts. Check with the operators of a local airport or mari-

na. If there are none in your area, check with a local surveyor.

When variation is westerly add the amount of variation to the compass reading to get the true bearing. And, when variation is easterly, subtract the amount of variation from the compass reading. For example, suppose variation is 15 west in your area. True north will be 15° east of magnetic north.

If you are really out in the boon-docks and can't get help, you can use the stars. The North Star, or Polaris, appears directly over the geographic North Pole and its position is accurate to within 1 degree. The Big Dipper can help you locate the North Star.

The two stars (called pointers) forming the side of the dipper farthest from the handle are in a line pointing directly to the North Star, as shown in Fig. 1. The distance (A) from the pointer star at the dipper's lip is about five times the distance (5A) between the two pointer stars. The Big Dipper constellation (among others) rotates around the North Star during the night and may not be aligned as shown in the drawing on your first attempt to locate the North Star. If you're not sure that you've identified the Big Dipper or located the North Star, look to the east for a five-star grouping that forms the letter "W" or "M," depending on how you view it. In any case, the bottom of the "M" or top of the "W" points to the North Star.

When you've pin-pointed the North Star, drive a stake at the point where you're standing and then, sight along the line toward True North and drive a second stake 100 yards or so from the starting point. With this line indicating

Make your home into something special!

That's exactly what your home will be when you fill it with Heathkit electronic products – products that make your life easier and more enjoyable. Within our diverse line are kit and assembled products sure to enhance each room in your home.



1. Make your entryway more secure and easy to use with the Keyless Doorlock. You'll never again be locked out because of lost or forgotten keys. All it takes is a simple fingertip entry of a four-digit code, and the Keyless Doorlock unlocks your door.

2. Add a new dimension to your living room with your own Computerized Weather Station. This Digital Weather Station displays up-to-the-minute temperature, wind, and barometric pressure readings, along with time and date.



3. Give your kitchen a unique blend of style and efficiency with our Digital Wall Clock. This easy-to-build kit keeps time with quartz-crystal accuracy. And with its simulated oak wood-grain finish cabinet, you'll have a timepiece that fits into almost any decor.



4. Put your den to greater use with this IBM PC AT Compatible Computer. Do word processing, personal accounting and more when you run exciting IBM-compatible software on your fast and powerful HS-241. And you can build it yourself in just a few hours.



5. Bring the latest in digital technology to your bathroom. This Digital Scale lets you closely monitor your weight with electronic precision. And, it's battery operated so it's safe to use right out of the shower.



6. Add a video entertainment center to your bedroom. Our 19"-diagonal stereo TV kit gives you an extra-sharp color-corrected picture with full stereo sound, and convenient viewing that you can control from your bed. Comes in a simulated walnut cabinet that complements your room.



7. Transform your rec room into a haven for hobby fun. Put our Deluxe QRP CW Transceiver in this room and enjoy superb HAM radio operation that excels in performance and features. It offers expandable transmission and reception capabilities.



8. Give your workbench a touch of professionalism with this oscilloscope. Whether you're a service technician or a hobbyist, you'll love the wide range of measurement capability our laboratory-grade Dual Trace 10 MHz Oscilloscope gives you.



9. Add practicality to the utility room and save money, too. Avoid expensive food spoilage with our Freezer Alarm that




warns you when the inside temperature of your freezer rises too high. Prevent water damage with our Food Alarm that warns you of water that's where it shouldn't be.



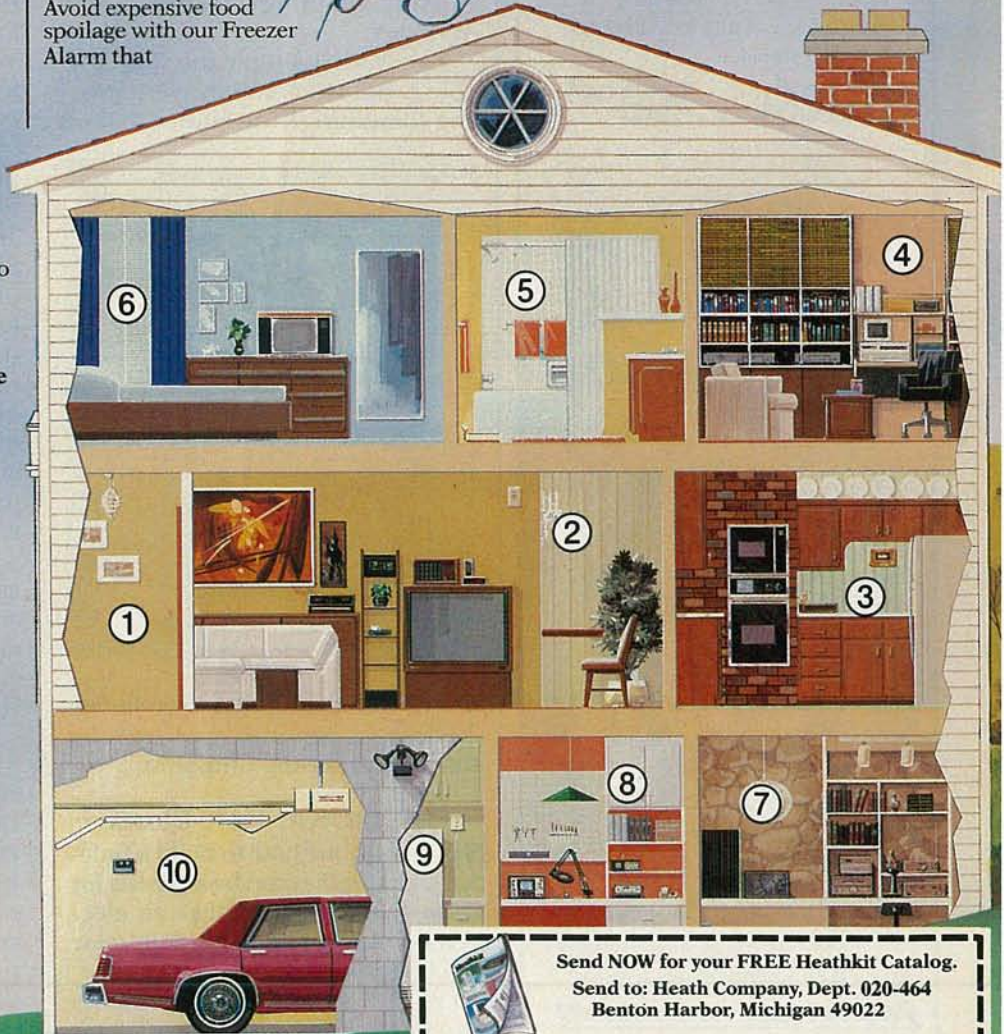10. Make your coming and going easier than ever. Your garage door will open with incredible

ease and dependability with our Deluxe Garage Door Opener. Easy to install, this opener is durable and includes a handy security light.

You'll find fun and excitement with every Heathkit product. Whether they're in kit form or already assembled, our products will help you enjoy your home more than you ever dreamed possible.



Heathkit
Heath
Company

CIRCLE 86 ON FREE INFORMATION CARD



Send NOW for your FREE Heathkit Catalog.
Send to: Heath Company, Dept. 020-464
Benton Harbor, Michigan 49022

Name _____

Address _____

City _____ State _____ Zip _____

A subsidiary of Zenith Electronics Corporation CL-789A

Capacitance, logic and more. For less.

Now, a fully-loaded DMM combines a capacitance meter, logic probe, and an hFE meter, all for the price of a DMM.

- TTL Logic Probe: 20 MHz
- Hi/lo/off indications
- Detects 25ns pulse width
- Capacitance: 5 ranges (2nF to 20μF)
- hFE (NPN or PNP): 1 range (1000)
- DMM: DCV-5 ranges (.2V to 1kV)
- ACV-5 ranges (.2V to 750V)
- DCA-4 ranges (200μA to 10A)
- ACA-3 ranges (20mA to 10A)
- Ohms-7 ranges (200 Ohms to 2000 Megohms)
- Continuity beeper
- Diode check
- Built-in bail
- Anti-skid pads

See one now at your local Beckman Industrial distributor.

DM25L... \$89.95*



*Suggested list price (\$US) with battery, test leads and manual.

Beckman Industrial™

Beckman Industrial Corporation
A Subsidiary of Emerson Electric Company
630 Puente Street, Brea, CA 92621
(714) 671-4800

© Copyright 1985 Beckman Industrial Corporation

True North, use it to calibrate your compass. Take your compass and sight along the line. Record the angle of variation between the line and magnetic north, as indicated on the compass.

Remember that if variation is west, add the deviation to the compass reading, and subtract deviation when it is east. If you want to point the dish toward the west (270°) and variation is 12° west, simply aim the dish on a compass heading of 282 degrees (270 + 12). If variation is 8 degrees east then aim for 262 degrees.

BALUN FOR TV RHOMBIC WHERE'S THE FIGURE?

You answered a question in your August issue regarding a balun for a rhombic antenna. You referenced a figure, but I couldn't find any. Am I missing anything?—G.S.W., New York, NY.

No. Your weren't missing anything, but we certainly were missing something! The figures that we

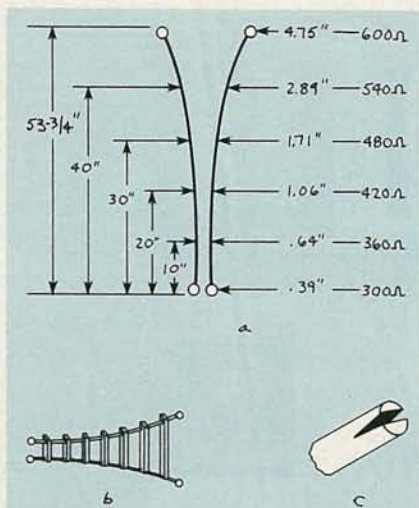


FIG. 2

referred to are shown here in Fig. 2. Please accept our apologies for that embarrassing omission.

ELECTRONIC TIME DELAY

Please show me how to build a time-delay circuit that can be adjusted for up to five minutes. Either an electromechanical or a solid-state relay will be OK.—C. C. S., Holiday, FL.

Figure 3 shows the circuit of an inexpensive general-purpose timer based on a 555 IC. The time delay T in seconds is:

$$T = 1.1 \cdot C_1 \cdot (R_1 + R_2)$$

Resistances should be specified in

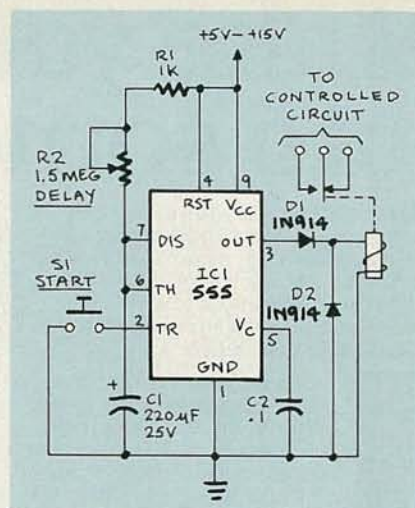


FIG. 3

megohms and capacitance in microfarads. The sum of R1 and R2 should not be less than 1000 ohms nor higher than 20 megohms. Pressing S1 starts the timing cycle. You could use a low-going pulse, instead of S1, to initiate the timing cycle.

Suppose that you have a good 5-megohm linear pot that you want to use as the adjustable control. Then $C_1 = 300 / (1.1 \cdot 5) = 55 \mu\text{F}$. Since that's not a standard value, use the next highest standard value, 75 μF . The actual value of a device with 20% tolerance can range from 60 to 90 μF . So the maximum time delay (with R2 at 5 megohms) will be 5 minutes and 30 seconds if the value of C1 is 60 μF , or 8 minutes and 15 seconds if C1 is 90 μF .

With the values shown in the diagram, and allowing for the tolerances of the 200- μF capacitor, the delay will range from 4 minutes and 50 seconds to 7 minutes and 26 seconds.

The output terminal, pin 3, of a 555 is normally low and switches high during the timing cycle. The output can either sink or source currents up to 200 mA. Therefore a load such as a relay coil can be connected between pin 3 and V_{CC} or between pin 3 and ground, depending on circuit requirements. When the relay is connected between pin 3 and ground, as in Fig. 3, it is normally de-energized, so it is energized only during the timing cycle. Connecting the relay to ground will save power and allow the IC to run cool.

R-E

PERFORMANCE

THAT IS OUT OF THIS WORLD...



\$389⁰⁰
MODEL 2000 20MHz
DUAL TRACE

\$549⁰⁰
MODEL 3500 35MHz
DUAL TRACE DELAYED SWEEP

...AT A DOWN TO EARTH PRICE

At last! Truly affordable test equipment with no compromise in design, and features you would expect to find only on oscilloscopes costing hundreds of dollars more! JDR Instruments presents two, new, high-performance models backed by a two year warranty and technical support which is only a phone call away. Perfect for the technician or advanced hobbyist, both models feature Dual Trace capability and a variety of operating and triggering modes, including CH-B Subtract and X-Y operation.


MODEL 2000 has a 20 MHz bandwidth and 20 calibrated sweeps ranging from .2s to .2 μ s. A convenient built-in component tester provides additional diagnostic power.



MODEL 3500 features a 35 MHz bandwidth and exceptional 1mV/DIV sensitivity. Delayed sweep and variable holdoff allow stable viewing of complex waveforms.

CIRCLE 59 ON FREE INFORMATION CARD

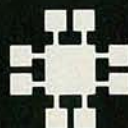ORDER TOLL FREE
800-538-5000
800-662-6279 (CA)



JDR INSTRUMENTS

1224 South Bascom Avenue
San Jose, California 95128 (408) 995-5430

Train for the Fastest Growing Job Skill in America

Only NRI teaches you to service all computers as you build your own 16-bit IBM-compatible micro

Now that computers are firmly established in offices by the millions—and in homes, too—the demand for trained computer service technicians surges forward. The Department of Labor estimates that computer service jobs will actually *double* in the next ten years—a faster growth than any other occupation.

Total systems training

No computer stands alone... it's part of a total system. And if you want to learn to service and repair computers, you have to understand computer *systems*. Only NRI includes a powerful

computer system as part of your training, centered around the IBM-PC compatible Sanyo 550 Series computer.

As part of your training, you'll build this highly rated 16-bit IBM-compatible computer system, assemble Sanyo's "intelligent" keyboard, install the power supply and disk drive, interface the high-resolution monitor and dot matrix printer, even expand the memory from 128K to 256K RAM. It's confidence-building, real-world experience that includes training in programming, circuit design, and peripheral maintenance.

Even if you've never had any previous training in electronics, you can succeed with NRI at-home training.

No experience necessary, NRI builds it in

You'll start with the basics, then rapidly build on them to master such concepts as digital logic, microprocessor design, and computer memory. You'll build and test advanced electronic circuits using the exclusive NRI Discovery Lab, professional digital multimeter, and logic probe. Like your computer system, they're all yours to keep as part of your hands-on

Learn Computer Servicing Skills with NRI's "Hands-On" Training . . .



You'll set up and perform electronics experiments and demonstrations using your NRI Discovery Lab. You'll even interface the lab with your computer to "see" keyboard-generated data.



After you build this digital logic probe, you'll explore the operation of the Sanyo detached "intelligent" keyboard and its dedicated microprocessor.



The power supply is assembled in the main unit of the computer. You check out keyboard connections and circuits with the digital multimeter included for training and field use.



NRI's total systems training includes:
 • NRI Discovery Lab, Digital multimeter, Digital logic probe for visual examination of computer circuits • Sanyo 550 Series computer with "intelligent" keyboard and 360K double-density, double-sided disk drive • High-resolution monochrome monitor • RAM expansion module gives you 256K memory • Dot matrix printer • EasyWriter I, WordStar, CalcStar bundled software

training. You even get over \$1,000 worth of software, including the popular WordStar and CalcStar.

Send for 100-page free catalog

See all the training equipment you get in this exciting, state-of-the-art computer course, including the educator-acclaimed NRI Discovery Lab, digital multimeter, and logic probe. Read

detailed descriptions of each lesson, each experiment you perform. And check out other NRI high-tech training like Robotics, Digital Electronics Servicing, Data Communications, TV/Audio/Video Servicing, and more.

Mail the postage-paid card today, and see how NRI can prepare you for advancement, a new career—even a business of

your own in the exciting world of electronics. If the card has been used, write to NRI at the address below.

NRI SCHOOLS
 McGraw-Hill Continuing Education Center
 3939 Wisconsin Avenue
 Washington, DC 20016
 We'll give you tomorrow



as You Build Your Own Sanyo Computer System.



Next, you install the disk drive. You learn disk drive operation and adjustment, make a copy of MS-DOS operating disk and begin your exploration of the 8088 CPU.



Using the monitor, you focus on machine language programming, an indispensable troubleshooting tool for the technician. You continue by learning BASIC language programming.



Finally, you install your dot matrix printer and perform experiments showing operating principles and maintenance and adjustment techniques, including changing the print head.

LETTERS

LASER TECHNOLOGY

Thanks for Josef Bernard's report on laser technology in the June 1986 *Radio-Electronics*. I agree with his view that the laser is one of the most significant inventions of this century.

Regarding the brief description of semiconductor lasers, I would like to add that such lasers can produce high-power outputs. For example, pulsed gallium arsenide and aluminum arsenide laser diodes can emit pulses having a peak power of 100 watts or more. If

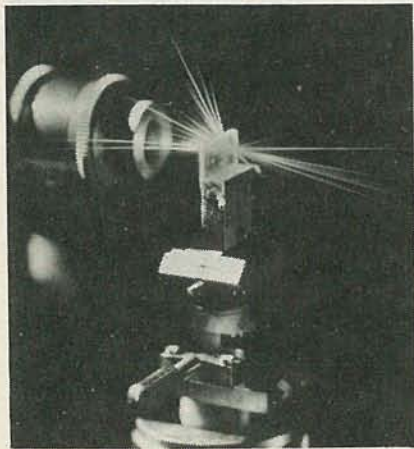


FIG. 1

the light-emitting region of the front facet of one of those lasers could be enlarged to a square centimeter, the device would emit a million watts of optical power. That coincides nicely with the power available from crystal- and glass-host lasers. Large area, non-junction, electron-beam pumped semiconductor lasers have been developed by several laboratories, and at least one was made commercially available.

The family of cw laser diodes used in compact-disc players, laser printers, and lightwave communications emit from 1 to 50 milli-

watts continuously when driven by a forward current of from 25 to a few hundred milliamperes. Experimental laser diodes with lasing thresholds on only a few mA have been fabricated.

FORREST M. MIMS, III
Seguin, TX

KIRLIAN PHOTOGRAPHY

John Iovine's article on Kirlian Photography (*Radio-Electronics*, May 1986) is an extremely interesting project. I hope that many of you carry out some of his interesting experiments and add your own observations to the phenomena, while observing all of the safety precautions—particularly the one about not grounding a live subject!

If, however, any of you are encouraged to experiment with Kirlian Photography, please let me recommend an article that appeared in *The Skeptical Inquirer*: "A Study of the Kirlian Effect," by Arleen J. Watkins and William S. Bickel (Spring 1986). The article describes the numerous experimental parameters and controls that must be considered before any Kirlian photographs can be considered as evidence of paranormal phenomena.

To receive a copy of the article, please send me a self-addressed, 22-cent stamped envelope. (Permission to copy the article has been obtained). I believe that it is extremely important to carry out your experiments with adequate controls and an understanding of the many parameters that are involved. If that is not done, erroneous conclusions will be drawn.

ERNEST L. LIPPERT, JR.
2228 Barrington Drive
Toledo, OH 43606-3149.

COMPLEX CONSTRUCTION PROJECTS

I was scanning the "Letters" column in the May 1986 issue, and noticed Troy Laminack's letter. I have been a *Radio-Electronics* reader for some time now (+25 years), and have watched your magazine's direction change with the times...from vacuum tubes, to transistors, to integrated circuits. I have also watched the demise of a few other electronics magazines at the same time.

Reader Laminack bemoans the inclusion of some of your more complex electronics construction projects in lieu of more simpler (and perhaps more practical) beginner's projects. To quote: "While the \$2500 IBM look-alike (*PC Compatible Computer*, July, 1985) would be great to build, and was fun to read, and while a \$200 see-in-the-dark-doo-hickey (*See-In-The-Dark Viewer*, August, 1985) would be fun for a few weeks, how practical is it really, and how many of your thousands of readers have hundreds of bucks to spend on that type of tinkering?"

I'd like to answer his question. To begin with, I don't have hundreds of bucks to spend on that type of tinkering. I almost never build the more complex construction projects featured in *Radio-Electronics*, or in any of the other magazines, either. What I do with those articles is to learn about how such devices work, and to extract any circuit ideas from them that may be useful to me at a later date. Many of the projects that I build result from fragments of circuits that I have seen elsewhere.

While I haven't built many of the projects, I have learned a great deal about how things work, circuitry in general, and various fac-



ets of electronics design. I owe a great deal to the knowledge that I have gained over the years from magazines such as **Radio-Electronics**.

In closing, please enter my vote to keep the content of the magazine substantially the same. The balance you now present is good as it stands. Anything else would narrow your focus.

RICK CHINN
Redmond, WA

OPPORTUNITIES FOR HANDICAPPED

We are a non-profit organization founded to help the handicapped and disabled to acquire job skills and jobs with the assistance of personal computers. Our staff helps coordinate the efforts of rehabilitation agencies and educational institutions; whenever possible, we supply the needed PC equipment at no cost, and provide training in use of the equipment.

To disseminate information, reach, and encourage the handicapped and disabled, we publish a bi-monthly newsletter, *Personal Computer Opportunities for the Handicapped*. Anyone wishing to subscribe, please send your name and address. We ask that you make a contribution of at least \$10.00. That contribution is fully tax deductible. If you are handicapped, or prefer not to make a contribution, drop us a note and we will give you a subscription at no charge.

JAMES R. NICHOLS, Chairman
Personal Opportunities for the Handicapped,
P.O. Box 374
Spicer, MN 562888

PHOTON BUSTER

We read your review of the Melville Technologies Phot-On-Off CD Cleaner with great interest.

The argument that photons may collect underneath the clear plastic surface of a CD sheds some light on the subject of telecommunication via fiber-optics cables. A problem very similar to the one you described in the April, 1986 issue of **Radio-Electronics** exists with the fiber-optic telephone lines.

Everyone has, at one time or an-

Analyze defective waveforms faster, more accurately, and more confidently — every time or your money back



with the SC61 Waveform Analyzer
Patented \$2,995

If you value your precious time, you will really want to check out what the exclusively patented SC61 Waveform Analyzer can do for you. 10 times faster, 10 times more accurate, with zero chance of error.

End frustrating fiddling with confusing controls. Exclusive ultra solid ECL balanced noise cancelling sync amplifiers, simplified controls, and bright blue dual trace CRT help you measure signals to 100 MHz easier than ever.

Accurately and confidently measure waveforms from a tiny 5 mV all the way to a whopping 3,000 V without hesitation with patented 3,000 VPP input protection — eliminates expensive "front end" repairs and costly equipment downtime.

Make only one circuit connection and push one button for each circuit parameter test: You can instantly read out DC volts, peak-to-peak volts and frequency 100% automatically with digital speed and accuracy. It's a real troubleshooting confidence builder.

Confidently analyze complex waveforms fast and easily. Exclusive Delta measurements let you intensify any waveform portion. Analyze glitches, interference signals, rise or fall times or voltage equivalents between levels; direct in frequency or microseconds.

Speed your digital logic circuit testing. Analyzing troublesome divide and multiply stages is quicker and error free — no time-consuming graticule counting or calculations. Simply connect one test lead to any test point, push a button, for test of your choice, for ERROR FREE results.

To see what the SC61 can do for your troubleshooting personal productivity and analyzing confidence, CALL TODAY, WATS FREE, 1-800-843-3338, for a FREE 15 day Self Demo.



Call Today Wats Free 1-800-843-3338

SENCORE

3200 Sencore Drive
Sioux Falls, SD 57107
605-339-0100 In SD Only

*innovatively designed
with your time in mind.*

CIRCLE 179 ON FREE INFORMATION CARD

OCTOBER 1986

other, had the unfortunate experience of using a "bad link." That bad link is usually a fiber-optic cable which has a large photon accumulation. It manifests itself as a "static"-like sound or a reduced received-voice level.

The solution to the problem is gamma radiation, as in the case with CD's. We are in the process of developing such a device for a major long-distance carrier. It will be introduced next April (1987). It will be called "Photon-buster," and

will allow the user to efficiently rid fiber-optic cable of excess photon buildup.

For further information, please telephone us at 1-800-PHO-TONS. ART COPPER and HARRY STEEL, Engineers
Photon Technologies
 6006 West John Street
 Hicksville, NY 11802

MUSIC MAKERS

Congratulations on the greatest magazine ever! I look forward to

every single issue; even if the constructional projects don't interest me, I always enjoy all the other sections—especially "Letters."

A new interest is developing at an incredible rate in projects devoted to music-makers. I'm one of those musicians who struggle to hunt down a high-quality music peripheral (i.e. sequencer). As you know, computers and synthesizers are all one and inseparable in these days of the MIDI link. Please consider running a series on dedicated music-assisting tools that are on par with the overpriced ready-built units.

I'd like to describe my setup briefly: KORG MS-20 Modular Mono Synthesizer, which I'd love to accompany with a sequencer. How about a micro-interfaceable DAC, which is run off the Timex/Sinclair 1000, with 16K RAM (very fair, don't you think?) I'm sure you'd have no problem in starting the design. I'll leave the rest of the design up to you, as I'm sure that you know the necessary requirements of such a versatile musical instrument.

I'm hoping to spark an interest amongst your readers to support my request. Please consider it seriously; many of us just can't afford the commercial units, and using a cheap micro (such as a ZX81) as a dedicated controller is a rock-bottom start for many struggling music experimenters.

TONY KALOMIRIS
 Quebec, Canada

VOICE-SWITCHED SPEAKERPHONE

I would like to thank you for mentioning Motorola's Voice-Switched Speakerphone IC, the MC34018, in your April issue (page 6). We have received almost two dozen inquiries from hobbyists around the country since that issue's distribution. In order to speed up our response to those who write to Motorola for data sheets and applications information, I would like to provide a more direct mailing address for the department responsible for the MC34018. Please send inquiries to: Dennis Morgan (PR340), Motorola Semiconductor Products, 7402 S. Price Rd., Tempe, AZ 85283. All inquiries will be an-



THE ONE SCANNER THAT'S REALLY GOING PLACES.

The Fox BMP 10/60™ is the only scanner that goes everywhere. You can use it at home, on the road, even as a battery-operated portable.* Police, fire, mobile phone and weather are just a few of the action-packed frequencies you can listen in on. The BMP 10/60 is easy to program and it's ideal for both personal and professional use. For

more information about the scanner that's going places, call 1-800-543-8000, Dept. M-779. Fox Marketing.



FOX® BMP 10/60 BASE/MOBILE/PORTABLE SCANNER

* with optional Porta-Pac

swered with the latest available information.

DENNIS MORGAN
Applications Engineering,
Motorola, Inc.

IC PACKAGING

I am writing in response to your article entitled "A Revolution in IC Packaging," *Radio-Electronics*, May 1986.

The author, T. J. Byers, gave an excellent overall picture of the various packages and the handling of them. There is one very important feature that I think was glossed over. The SMD's (Surface Mounted Device) offer a substantially lesser amount of parasitic impedance than the DIP packages. At higher frequencies, that is of extreme importance. Above 100 MHz, although that figure may be argued, lead inductance (in series) and stray capacitance (in parallel) must be taken into account, and compensated for, to ensure a "clean" signal. SOIC's, PLCC's and LCCC's have a 12 to 15% better rise/falltime than DIP packages. Also V_{CC} noise, pin-to-pin crosstalk, and noise-margin problems are less of a problem.

An excellent article on the subject appeared in the December 1985 issue of *Design Technology*, entitled "SMD's Make Bipolar Quick and Quiet." The authors are Charles Hefner and Rich Moore, from Texas Instruments.

DANA C. GLEN
San Leandro, CA


MORE ON IC PACKAGING

I would like to comment on the article, "A Revolution in IC Packaging," that appeared in the May 1986 issue of *Radio-Electronics*. It seems that our world is getting more complicated and changing at rapid pace, as well as being more "global" in nature.

For example: There was a time when you could say "TO-92, TO-3, or TO-5" and people would know what kind of package you were talking about. Now, some use a number—TO-236; some use a name—"super-mini type," and some another name—"small outline transistor." Isn't that confusing?

We at JEDEC recognize TO-236 because it's our standard; the Jap-

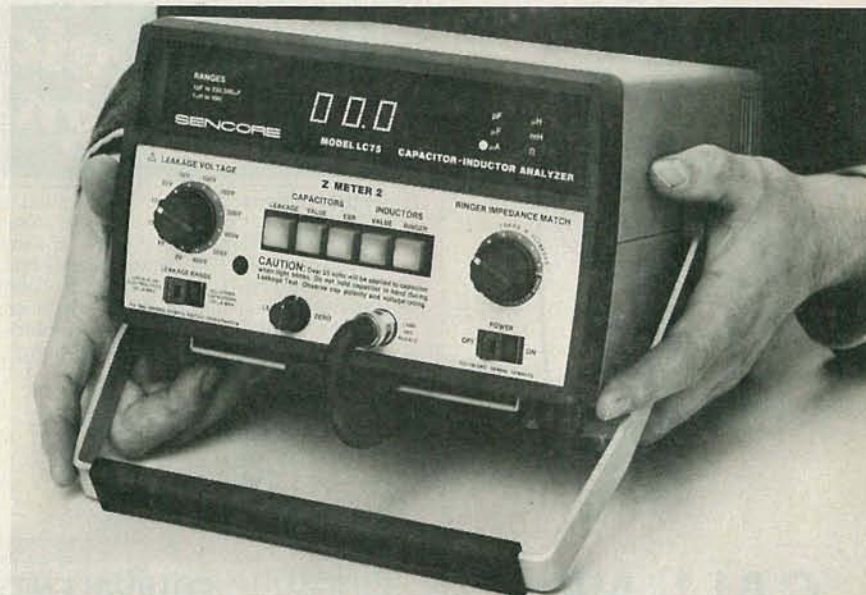Exclusive, triple patented dynamic cap and coil analyzing . . . guaranteed to pinpoint your problem every time or your money back



with the all new LC75 "Z METER 2"
Capacitor Inductor Analyzer
Patented \$995

The "Z METER" is the only LC tester that enables you to test all capacitors and coils dynamically — plus, it's now faster, more accurate, and checks Equivalent Series Resistance (ESR) plus small wire high resistance coils.

Eliminate expensive part substitution and time-consuming shotgunning with patented tests that give you results you can trust every time. Test capacitor value, leakage, dielectric absorption, and ESR dynamically; with up to 600 volts applied for guaranteed 100% reliable results — it's exclusive — it's triple patented.

Save time and money with the only 100% reliable, in- or out-of-circuit inductor tester available. Dynamically test inductors for value, shorts, and opens, automatically under "dynamic" circuit conditions.

Reduce costly parts inventory with patented tests you can trust. No more need to stock a large inventory of caps, coils, flybacks, and IHVTs. The "Z METER" eliminates time-consuming and expensive parts substituting with 100% reliable LC analyzing.

Turn chaos into cash by quickly locating transmission line distance to opens and shorts to within feet, in any transmission line.

Test troublesome SCRs & TRIACs easily and automatically without investing in an expensive second tester. The patented "Z METER 2" even tests SCRs, TRIACs, and High-Voltage Diodes dynamically with up to 600 volts applied by adding the new SCR250 SCR and TRIAC Test Accessory for only \$148 or FREE OF CHARGE on Kick Off promotion.

To try the world's only Dynamic LC Tester for yourself, CALL TODAY, WATS FREE, 1-800-843-3338, for a FREE 15 day Self Demo.



Call Today Wats Free 1-800-843-3338

SENCORE


3200 Sencore Drive
Sioux Falls, SD 57107
605-339-0100 In SD Only

*innovatively designed
with your time in mind.*

CIRCLE 180 ON FREE INFORMATION CARD

R-E Engineering Admart

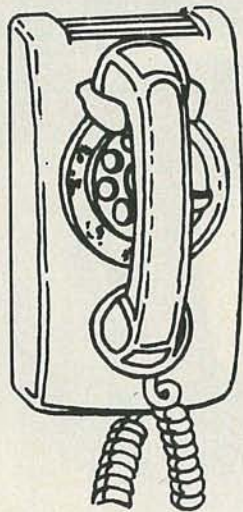Rates: Ads are 2 1/4" x 2 7/8". One insertion \$825. Six insertions \$800 each. Twelve insertions \$775 each. Closing date same as regular rate card. Send order with remittance to Engineering Admart, Radio Electronics Magazine, 500-B Bi-County Blvd., Farmingdale, NY 11735. Direct telephone inquiries to Arline Fishman, area code 516-293-3000. Only 100% Engineering ads are accepted for this Admart.



CALL NOW AND RESERVE YOUR SPACE

- 6 x rate \$800.00 per each insertion.
- Reaches 239,312 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads.

Call 516-293-3000 to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: Engineering Admart, RADIO-ELECTRONICS, 500-B Bi-County Blvd., Farmingdale, NY 11735.

IBM-PC Schematic Design

A professional package enabling you to design, edit, print & plot electronic schematics. Supports "A" — "E" size sheets, over 2000 Unique Library Parts, Auto Panning, Part Rotation, 5 Zoom Levels, Rubberbanding, Powerful Macros, Hi-Res Color & Monochrome Graphics, Much More! \$495 Includes Everything.


Call to Receive Free Demo Disk.

OrCAD Systems Corporation 
1049 S.W. Baseline St.
Hillsboro, OR 97123
(503) 640-5007


CIRCLE 195 ON FREE INFORMATION CARD

LINEAR IC EQUIVALENTS & PIN CONNECTIONS

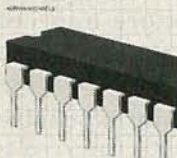Linear IC
Equivalents
and Pin
Connections



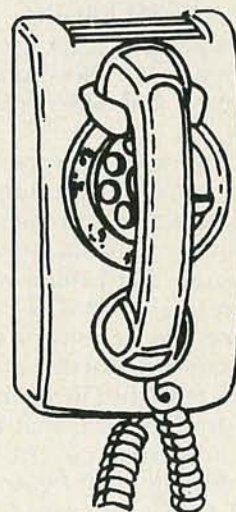BP141—Shows equivalents & pin connections of a popular user-oriented selection of European, American and Japanese linear IC's 320 pages, 8 x 10 inches. \$12.50 Plus \$2.75 shipping. **ELECTRONIC TECHNOLOGY TODAY INC., PO Box 240, Massapequa Park, New York 11762-0240.**



CALL NOW AND RESERVE YOUR SPACE

- 6 x rate \$800.00 per each insertion.
- Reaches 239,312 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads.

Call 516-293-3000 to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: Engineering Admart, RADIO-ELECTRONICS, 500-B Bi-County Blvd., Farmingdale, NY 11735.

anese recognize SC-59, and others recognize Philips's designation SOT-23. Your article uses TO-236/SOT-23, and then quickly drops the TO-236 part, saying that SOT-23 is popularly accepted. I don't see why we need to use three numbers if the parts are the same; and if they are different, we should not say that they are the same.

But there *are* differences. And for the popular SOT-23, we get disagreement on how you make it, even to the extent of putting j-bend leads on it.

What furthers the confusion is that people want to use the JEDEC

2N numbers on surface-mount parts. For example, the popular 2N3904 transistor is registered in a TO-92 (we know what it is) package. Now people want the 2N3904 in an SOT-23 package—but the package cannot handle the heat generated by the part. Is it still a 2N3904? It can't meet the JEDEC specification.

The SO-8 SOIC package that your article referred to is also a Philips design. JEDEC has a standard width on SOIC's both in the .150" width (MS-012) and the .300" width (MS-013). We prefer to use the JEDEC numbers because they

have had the review of the entire semiconductor industry, and because JEDEC controls the drawing.

The PLCC's that your article refers to are also JEDEC standards. The square version is the MO-047, and the rectangular is the MO-052 with 50-mil leadspacing. If people would like to see the US-approved packaging standards, JEDEC sells Publication 95. Copies can be obtained from our address below.

KEN McGHEE
JEDEC Solid State Products Engineering Council,
2001 Eye Street NW
Washington, DC 20006

R-E

EQUIPMENT REPORTS

Heathkit Model GR-4500 Projection-TV Kit

*The first build-it-yourself
projection TV.*



CIRCLE 9 ON FREE INFORMATION CARD

MANY YEARS BACK, HEATHKIT (THE Heath company, Benton Harbor, MI 49022) developed and marketed the first color TV-set in kit form that was sold to the general public. Easy to build, thanks to the meticulous instructions that accompanied the unit, that TV-set, as well as many of the ones that followed, became favorites among electronics enthusiasts.

Now, Heath has a new first: It's the GR-4500, the first projection TV-set to be offered in kit form. As you might expect from Heath, the

WM. B. ALLEN has unbelievable prices on LEADER!

LEADER
Instruments Corporation




LBO5825 TWO CHANNEL DIGITAL STORAGE OSCILLOSCOPE
5MHz sampling rate, 35MHz analog bandwidth, A/D converter each channel, 1k word per channel, two channels, Memory protect, X-Y recorder, Roll function, 5MHz storage.

REGULARLY \$2850.00
NOW ONLY \$2565.00

LPS151 TRIPLE OUTPUT POWER SUPPLY
0 to +6V, 0 to +25V
0 to -25V all adjustable,
0 to 6V output-3.0A max.,
+25V-0.5A max.

REGULARLY \$425.00
NOW ONLY \$392.00

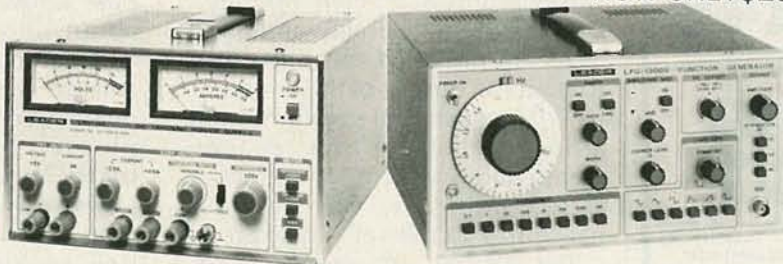


LFG1300S FUNCTION/SWEEP GENERATOR
Sine, square, triangle, ramp
and pulse output, Adjustable
pulse width, Linear or log
sweep, 1000:1 range.

REGULARLY \$495.00
NOW ONLY \$426.00

LAG-27 SINE/SQUARE WAVE GENERATOR 1 MHz
10MHz -1MHz range, 600 Ohm output impedance
approx., Square wave frequency range 10Hz-100KHz,
Output voltage 5V p-p or more (unloaded).

REGULARLY \$225.00
NOW ONLY \$207.00

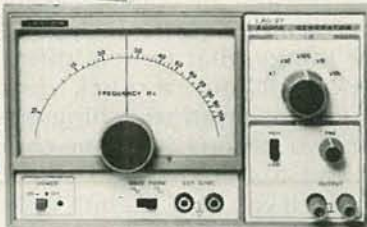

FOR PRICES ON
OTHER LEADER
PRODUCTS, CALL
WM. B. ALLEN
TOLL FREE!

WM. B. ALLEN SUPPLY COMPANY, INC.

NATIONWIDE 800-535-9593
NEW ORLEANS 504-525-8222
LOUISIANA 800-462-9520

ALLEN SQUARE
300 BLOCK, N. RAMPART STREET
NEW ORLEANS, LA 70112



CIRCLE 103 ON FREE INFORMATION CARD

OCTOBER 1986

COMB

Authorized Liquidator



Amazing Hearoid™ talks and serves you!

19" tall

Remote Control Unit (Batteries not incl.)

He Obeys Your Commands!

REMOTE CONTROLLED HEAROID™ ROBOT Great Fun For Everyone!

Liquidation due to famous Japanese manufacturer discontinuing this model.

- Loads of fun as Hearoid™ delights the family by serving them, carrying objects in hand or on a removable tray.
- Amaze and impress friends as Hearoid™ serves them and guides them on a talk tour of home (built-in cassette recorder).
- Remote microphone lets you converse with guests through robot.
- Hearoid™ obeys 12 voice commands. Performs programmed routines up to 45 minutes long.
- Switch from voice-activated to push-button control on remote unit.
- Programmable digital alarm clock lets you schedule daily tasks at a set time.
- Rechargeable battery (included) runs up to 3 hours at a time. Recharger incl.
- Factory new, first quality product.

90-Day Limited Factory Warranty.

Mfr. List: \$399.95 **\$149**

Liquidation Price . . . Item H-1520-7000-862 Ship, handling: \$8.00

Credit card customers can order by phone.

24 hours a day.

7 days a week.



Toll-Free: 1-800-328-0609

Sales outside the 48 contiguous states are subject to special conditions. Please call or write to inquire.

C.O.M.B. Direct Marketing Corp. Item H-1520
1405 Xenium Lane No./ Minneapolis, MN 55441-4494

Send Hearoid™ Robot(s) Item H-1520-7000-862 at \$149 each plus \$8 each for ship, handling. (Minnesota residents add 6% sales tax. Sorry, no C.O.D. orders.)

My check or money order is enclosed. (No delays in processing orders paid by check, thanks to TeleCheck.)

Charge: VISA® MasterCard® American Express®

Acct. No. _____ Exp. / _____

PLEASE PRINT CLEARLY

Name _____

Address _____

City _____

State _____ ZIP _____

Phone (____) _____

Sign Here _____

COMB Direct Marketing Corp.
Authorized Liquidator
1405 Xenium Lane North
Minneapolis, Minnesota 55441-4494

projection TV is not a stripped-down, bare-bones model. Instead it offers an array of features that will satisfy even the most ardent videophile, and at a price of only \$1695.00

Heathkit		GR-4500												
OVERALL PRICE														
EASE OF USE														
INSTRUCTION MANUAL														
PRICE/VALUE														
		1	2	3	4	5	6	7	8	9	10			
		Poor		Fair			Good			Excellent				

Features

The GR-4500 is a 45-inch (diagonal measure) rear-projection television receiver. It uses liquid-cooled, high-definition projection tubes, with optically-coupled projection optics, and a black matrix projection screen to yield a picture with superior contrast. Further, the screen acts to absorb ambient light, thus reducing glare and room reflections.

The top-notch optics are complemented by a stereo-audio system complete with MTS decoder for stereo-TV or SAP audio. The amplifier has an output of 5-watts-rms-per-channel into an 8-ohm load with less than 2% THD (Total Harmonic Distortion). The built-in speakers include 2 6½-inch woofers and 2 2½-inch tweeters. For maximum flexibility, audio I/O jacks are provided that allow you to feed the output of the amplifier to a pair of external speakers, feed a line-level signal to a separate stereo-audio system, or to feed a stereo-audio signal from an external source to the set's speakers.

The set has, of course, an infrared remote control. Among other things, that remote offers parental lockout, a quick view function for rapid switching between two stations, a volume control, and a stereo-sound select function. If you own a Zenith VCR, it is likely that the remote can also be used to operate that unit.

Other features that one would expect to find on a high-end piece of video equipment are all present. Those include PLL tuning, on-

screen time and channel display, and a comb-filter for the highest possible resolution. The tuner is "cable-ready" and can receive 178-channels of programming if available. The set can be used with the newer HRC cable systems.

The set does not include a resolution control. Instead that function is handled by a preset filter. When switched out, resolution is at its greatest, but so is the video-noise level. If you live in a fringe area, or otherwise suffer from low signal levels, the filter can be used to remove some of the video noise (static, sparkles, etc.), but it will also reduce the set's resolution somewhat.

One item you won't find in any other projection TV is a built-in cross-hatch generator. That is used in aligning the set and eliminates the need to buy additional test equipment. Therefore it is possible to build the unit using just common tools.

Building the set

That brings us to building the unit. In the past, when we've reviewed other kits in this space we've used the "Heathkit" test: That is, how good are the instructions, etc., compared to those found in Heath products. The highest compliment we could pay a kit is to say that it is just as good as a Heathkit. This is a Heathkit.

Those of you that have dealt with that company's products in the past know what we are talking about. Illustrations are detailed and complete. Every step in the set-up, construction, and alignment process is painstakingly explained. As a result, if the instructions are carefully followed, the odds of obtaining a correctly working product the first time are high.

To top it off, in keeping with Heath's policy, all stages that are difficult to build or align are pre-assembled. In a kit of the complexity of a projection TV-set, that means that just about the entire unit is contained within a series of pre-assembled modules. The electronic construction is pretty much limited to a single small board. Even the wire harness comes pre-assembled. The result is that the kit can be built in just a few eve-

Discover—Explore—Experience
Today's Electronics With ...

McGraw-Hill's Contemporary Electronics Series

Now you can meet the challenges of today's electronics quickly and easily. This professional level learning series is as innovative as the circuitry it explains and as fascinating as the experiments you build and explore! And it's for anyone who has an interest in electronics... from the hobbyist to the professional.

Thousands Have Already Experienced the Excitement!

Today's high-tech world demands an entirely new and innovative approach to understanding electronics. That's why McGraw-Hill has developed this unique "hands-on" learning method that brings to life the dynamics of the new electronics. It's a unique combination of interactive materials that gets you involved as you build and experiment with today's latest electronic circuitry.

Just how well this innovative learning approach meets the challenge of the new electronics is confirmed by those who have already completed the Series... "You have put me right into the middle of an extraordinary learning experience. With each lab exercise I have gained a new understanding of the intricacies of today's electronics." Or... "For me, the Series was just the answer. I felt confident within my specialty, but my grasp of other areas of electronics was slipping away. Your Series helped me upgrade my knowledge of the latest electronics concepts." Or this from a company director of training... "We manufacture sophisticated electronic products, with a lot of people in sales, assembly and purchasing. McGraw-Hill has answered a real need in helping our employees see the total picture. They now communicate with customers and each other more effectively."

Your Involvement in the New Electronics Begins Immediately.

You master one subject at a time with 15 McGraw-Hill *Concept Modules*, sent to you one

every 4 to 6 weeks. You waste no time on extraneous materials or outdated history. It's an entertaining, lively, nontraditional approach to the most modern of subject matter.

Your very first module takes you right to the heart of basic circuit concepts and gets you ready to use integrated circuits to build a digital oscillator. Then, you'll verify the operation of different electronic circuits using a light emitting diode (LED).

And each successive module brings you up to speed quickly, clarifying the latest advances in today's electronics... from digital logic and micro-processors to data communications, robotics, lasers, fiber optics, and more.

Unique Combination of Interactive Instruction Materials Makes Learning Easy.

Laboratory experiments, vividly illustrated text and interactive cassette tapes all blend together to give you a clear, simplified understanding of contemporary electronics.

With each module, you receive a McGraw-Hill *Action-Audio Cassette* that brings to life the facts and makes you feel as if you're participating in a lively dialogue with experts.

Your ability to quickly make this knowledge your own is further aided by strikingly *illustrated* texts that use diagrams, explanations, illustrations, and schematics to drive home and rein-

force the meaning of each important point. Carefully indexed binders conveniently house all this material, as well as the instructions that will guide you through your "hands-on" lab experiments.

Throughout your Series, *laboratory experiments* reinforce every significant concept. With this essential "hands-on" experience using actual electronic components, you master principles that apply all the way up to tomorrow's VLSI (Very Large Scale Integrated) circuitry.

Discover, Explore, Experience for Yourself—15-Day Trial.

In all ways, the Contemporary Electronics Series is an exciting learning experience that offers you the quickest and least expensive method available to master today's electronics... and the only one with "hands-on" experience.

To order your first module for a 15-day

trial examination, simply complete the card and send today! If the card is missing, write to us for ordering information.



McGraw-Hill
Continuing
Education Center

3939 Wisconsin Avenue, NW
Washington, DC 20016

OCTOBER 1986

nings Heath's estimate is 23 hours and we agree that it is accurate.

There was one problem that bears mention. Those of you who are familiar with convergence adjustments know how tricky they are to make, even for someone who does those adjustments on a daily basis. The dynamic adjustments on our completed GR-4500 seemed particularly difficult to perform, even with Heath's detailed manual.

We eventually were able to obtain acceptable convergence, but we are still not completely satisfied, so we plan to keep after it until it's perfect.

For those of you who run into that or other problems, Heath provides direct technical-assistance telephone numbers. By calling the appropriate number listed in the manual, you can reach directly a specialist in the type of product (computer, TV, ham, etc.) you are building. Even if you never need it, knowing that help is just a telephone call away can be very reassuring. **R-E**

Diconix 150 Portable Printer

This battery-powered printer is IBM and Epson compatible.



CIRCLE 10 ON FREE INFORMATION CARD

TAKE A CMOS MICROPROCESSOR IN AN SMT package, five Ni-Cd C cells, a couple of stepper motors, and a bladder of ink. What do you come up with? How about a versatile portable printer? Diconix, Inc., (3100 Research Blvd., Dayton, OH 45420), a division of Kodak, came up with their model 150, an under-\$500 printer that deserves attention from those needing a portable printer with Epson FX and IBM-PC compatibility.

The model 150 is an ink-jet printer. A disposable printhead contains a bladder of ink; the ink is forced electrostatically through a vertical series of 12 nozzles to form characters and graphic images. The printheads (which bear the Hewlett-Packard logo) cost about \$10 apiece, and are good for about 500 standard sheets of double-spaced text.

The model 150 can print on just about any kind of paper, but best results are obtained on special ink-jet paper, which is available from the manufacturer. The maximum page width is 8-1/2 inches; both sprocket-fed paper and single sheet (such as letterhead stationery) can be accommodated.

In addition to the power switch, the model 150 has three pushbutton switches that control operation. Each has several functions, depending on whether the printer is on- or off-line when it is pushed. The ON LINE switch selects and de-selects the printer. The FORM FEED switch advances the paper to the top of the next page if it is pressed when the printer is off-line; if it is

The Best Now Costs Less

Introducing lower pricing on 3M's A P Products™ brand Super-Strip® and Circuit-Strip®

3M's A P Products brand Super-Strip and Circuit-Strip are the world's best solderless breadboard units. No others can compare on quality and reliability. Now the best costs less.

Design, prototype and test electronic circuits, faster and easier, with A P Products brand Super-Strip and Circuit-Strip.

A P Products brand solderless breadboards, laid out on a 0.1" x 0.1" matrix, accept all DIP sizes and a wide variety of discrete components with lead diameters of up to .032".

Super-strip features 840 plug-in tie points and Circuit-Strip has 610 tie points. Both have separate distribution buses for power, ground and signal lines.

Call your A P Products Prototype & Test Devices distributor today. For immediate response call 800-321-9668, or (216) 354-2101 in Ohio to find the name and location of your nearest distributor.

We Solve Problems.

**Super-Strip – WAS \$20.95
NOW \$16.95**

**Circuit-Strip – WAS \$13.00
NOW \$10.95**

Suggested retail prices in U.S. currency.

Associated Electronics/3M

A P Prototype & Test Devices
9325 Progress Parkway
P.O. Box 540
Mentor, Ohio 44060


CIRCLE 76 ON FREE INFORMATION CARD

RAG

ELECTRONICS, INC.

New and Used Electronic Test Equipment
Sales • Service • Rental • Leasing

HAMEG Oscilloscopes with Component Tester 2-year warranty

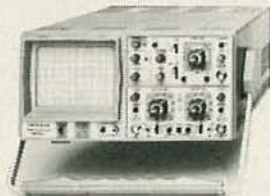


HM 203-6 DC to 20MHz **\$489.00**

- Rectangular screen, internal graticule 8x10cm.
- Deflection: 5mV/cm to 20V/cm
- Timebase: 0.5 μ s/cm to 0.2s/cm X-Magnification x 10
- Component Tester
Test voltage: max. 8.5Vrms (open circuit)
Test current: max. 24mA rms (shorted)




HM 204-2 DC to 20MHz **\$629.00**

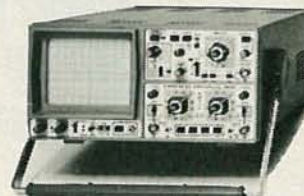- Component Tester
- Deflection: 5mV/cm to 20V/cm Y-Magnification x 5
- Timebase: 0.1 μ s/cm to 0.5s/cm X-Magnification x 10
- Sweep delay: 100 ns to 0.1 s.
- Calibrator: square-wave generator, \approx 1 kHz/1MHz switchable, risetime < 5ns, for probe compensation, output voltages: 0.2V and 2V \pm 1%.



HM 605 DC to 60 MHz **\$899.00**

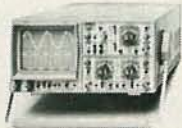- Component Tester
- Deflection: 5mV/cm to 20V/cm Y-Magnification x 5
- Y-Output from Ch. I or Ch. II: \approx 45 mV/cm into 50 Ω .
- Timebase: 50ns/cm to 1 s/cm X-Magnification x 10
- Sweep delay: 100ns to 0.1s.



HM 205 **\$799.00**

Real-time - See 203-6 Specifications

Digital Storage

- Operating modes: Refresh and Single with Reset (incl. LED indication for Ready), Hold Ch.I, Hold Ch.II. 1024x8 bit for each chan. Sample rate: max. 100kHz. Resolution: vertical 28 pts/cm, horiz. 100 pts/cm.
- Option: Interface for plotter.
- Component Tester



Modular System 8000



HM 208 **\$2,380.00**

HM 208-1 **\$2,860.00**

(with IEEE Interface)

Real-time - See 203-6 Specifications

Digital Storage

- Operating modes: XY, Roll, Refresh, Single (LED ind.), Hold Ch.I, Hold Ch.II, Plot I and Plot II with read-out check on screen, backing storage, Dot Joining button. 2 x 1024 x 8bit for each ch. Sample rate: max. 20MHz. Resolution: vert. 28 pts/cm, horiz. 200 or 100 pts/cm.
- Plotter output: vertical 0.1V/cm, horizontal 0.1V/cm. Output imped.: 100 Ω each. Penlift: TTL/CMOS compat. Output speed rate: 5-10-20/10-20-40 s/cm.
- Option: Lithium battery for memory backup.

ATTACHES TO ALL HAMEG SCOPES ON THIS PAGE!

HM 8001	2 BAY Mainframe	\$228.00
HM 8002	4 BAY Mainframe	call \$00N
HM 8011-2	Digital Multimeter 4½ digits	298.00
HM 8014	Milli Ohm Meter	298.00
HM 8021-2	Counter, 0.1Hz-1GHz	324.00
HM 8027	Distortion Meter	248.00
HM 8030-2	Function Gen. 0.1Hz-1MHz	288.00
HM 8032	Sine Wave Gen. 20Hz-20MHz	288.00
HM 8035	Pulse Generator, 2Hz-20MHz	455.00
HM 8037	Low Dist. Sine Gen. 5Hz-50kHz	248.00
HM 8040	Triple Power Supply	278.00
HM 8045	Oscilloscope Calibrator	378.00

CIRCLE 126 ON FREE INFORMATION CARD
CALL US TOLL FREE

1-800-732-3457
IN CALIFORNIA TOLL FREE
1-800-272-4225

- Master Charge
- VISA ■ COD
- Money Order
- Check



ADD FOR SHIPPING AND INSURANCE

\$0 to \$250.00	\$4.50
\$251.00 to 500.00	\$6.50
\$501.00 to \$750.00	\$8.50
\$751.00 to \$1000.	\$12.50
over \$1000.00	\$15.00/1000


Prices subject to change without notice.

RAG ELECTRONICS, INC. / 21418 Parthenia Street / Canoga Park, CA 91304 / 1-818-998-6500

SUPER LONG PLAY TAPE RECORDERS

10 Hour Model — \$95.00*
14 Hour Model — \$159.00*

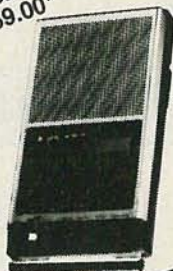Modified Panasonic Slimline, high quality, AC-DC Recorders provide 5 or 7 continuous hours of quality recording & playback on each side of cassette for a total of 10 or 14 hours depending on model. Built-in features include • Voice level control • Digital counter, etc. TDK DC 180 Cassette Furnished.



PHONE RECORDING ADAPTER

Records calls automatically. All Solid state connects to your telephone jack and tape recorder. Starts recording when phone is lifted. Stops when you hang up.

\$24.50*
FCC APPROVED



VOX VOICE ACTIVATED CONTROL SWITCH

Solid state. Self contained. Adjustable sensitivity. Voices or other sounds automatically activate and control recorder. Uses either recorder or remote mike.

\$24.95*



*Add for ship & hdlg. Phone Adapter & Vox \$1.50 ea. Recorders \$4.00 ea. Cal. Res. add tax. Mail order. VISA, MIC, COD's OK. Money Back Guarantee. Qty. disc. avail... Dealer inquiries invited. Free data. ©

AMC SALES, Dept. A 9335 Lubec St., Box 928, Downey, CA (213) 90241 Phone 869-8519

CIRCLE 108 ON FREE INFORMATION CARD

A Time to Remember

Remember family or friends with Special Occasion, Get Well or Memorial cards.

WE'RE FIGHTING FOR YOUR LIFE

American Heart Association




pressed when the printer is on-line, the printer's correspondence mode (called Vintage-12 by Diconix) is selected. Similarly, the LINE FEED switch advances the paper one line or selects the draft quality mode. Print quality may also be chosen through software.

Several other options are available through the switches; some, but not all, are also available through software. One innovative and useful feature is the envelope mode. The printer enters the envelope mode when you press the LINE FEED key while powering the printer up. Then you insert a #10 business envelope into the model 150 sideways. Last, you send the

Diconix		150											
OVERALL PRICE													
EASE OF USE													
INSTRUCTION MANUAL													
PRICE/VALUE													
		1	2	3	4	5	6	7	8	9	10		
		Poor			Fair			Good			Excellent		

35mm Color

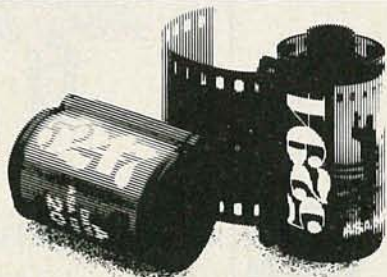

Prints and Slides from the same roll

Seattle FilmWorks has adapted Kodak's professional Motion Picture film for use in your 35mm camera. Now you can use the same film—with the same microfine grain and rich color saturation—Hollywood's top studios demand. Its wide exposure latitude is perfect for everyday shots. You can capture special effects, too. Shoot it in bright or low light—at up to 1200 ASA. What's more, it's economical. And remember, Seattle FilmWorks lets you choose prints or slides, or both, from the same roll. Try this remarkable film today!

\$2 INTRODUCTORY SPECIAL

1986 SEW

RUSH me two 20-exposure rolls of Kodak MP film for my 35mm camera. Enclosed is \$2 for a 2-roll starter pack including Eastman 5247® and 5294®

100% Satisfaction Guaranteed
Ideal for use in Canon, Nikon, Minolta, Olympus, Pentax... any 35mm camera.

NAME _____

ADDRESS _____

CITY _____

STATE _____

ZIP _____

Mail to: Seattle FilmWorks
500 Third Ave. W., P.O. Box 34056
Seattle, WA 98124

4110

Kodak, 5247 and 5294 are trademarks of Eastman Kodak Co. Seattle FilmWorks is wholly separate from the manufacturer. Process ECN-11.

data to be printed (as many as 20 lines of 100 characters each). Upon receipt of a form feed [CHR\$(12)], the model 150 will then print the envelope with all characters rotated 90° clockwise. Multiple copies of an envelope can be printed without resending the same data.

Another special mode is enabled by pressing all three push-button switches simultaneously. At that point, the ON LINE and PAPER EMPTY LED's begin flashing alternately. The flashing indicates that the model 150 is recharging the five Ni-Cd cells. You cannot print while recharging.

To save space, Diconix has cleverly chosen to use the platen to store the Ni-Cd's. They must be purchased separately at extra cost. A fully-charged set of batteries will power the model 150 for about 50 minutes of continuous printing, in which time about 150 pages may be printed in draft mode.

The printer measures about 2 × 10½ × 6½ inches and weighs about four pounds—that's less than most portable computers! It comes with a parallel interface; a

What Pomona knows about Grabbers™ would fill a book.


The Pomona Electronics line of Grabber test clips is a perfect example of our commitment to stay on the leading edge of electronic test technology. A quality product designed to fill a specific need, and to do it well.

Design engineers have made their professional lives a little easier by using our Grabbers to reach and test discrete components and terminals in tight places. They like the ease of operation and positive connection.

In our 1986 General Catalog you'll find more than 50 different Grabber versions to simplify your exacting test requirements. We have even added seven new models to test surface mounted devices.

Here's how to get your copy of our 1986 General Catalog: Just circle the reader service number below; call us at (714) 623-3463; write us at ITT Pomona Electronics, a division of ITT Corporation, 1500 East Ninth Street, P.O. Box 2767, Pomona, California 91769.

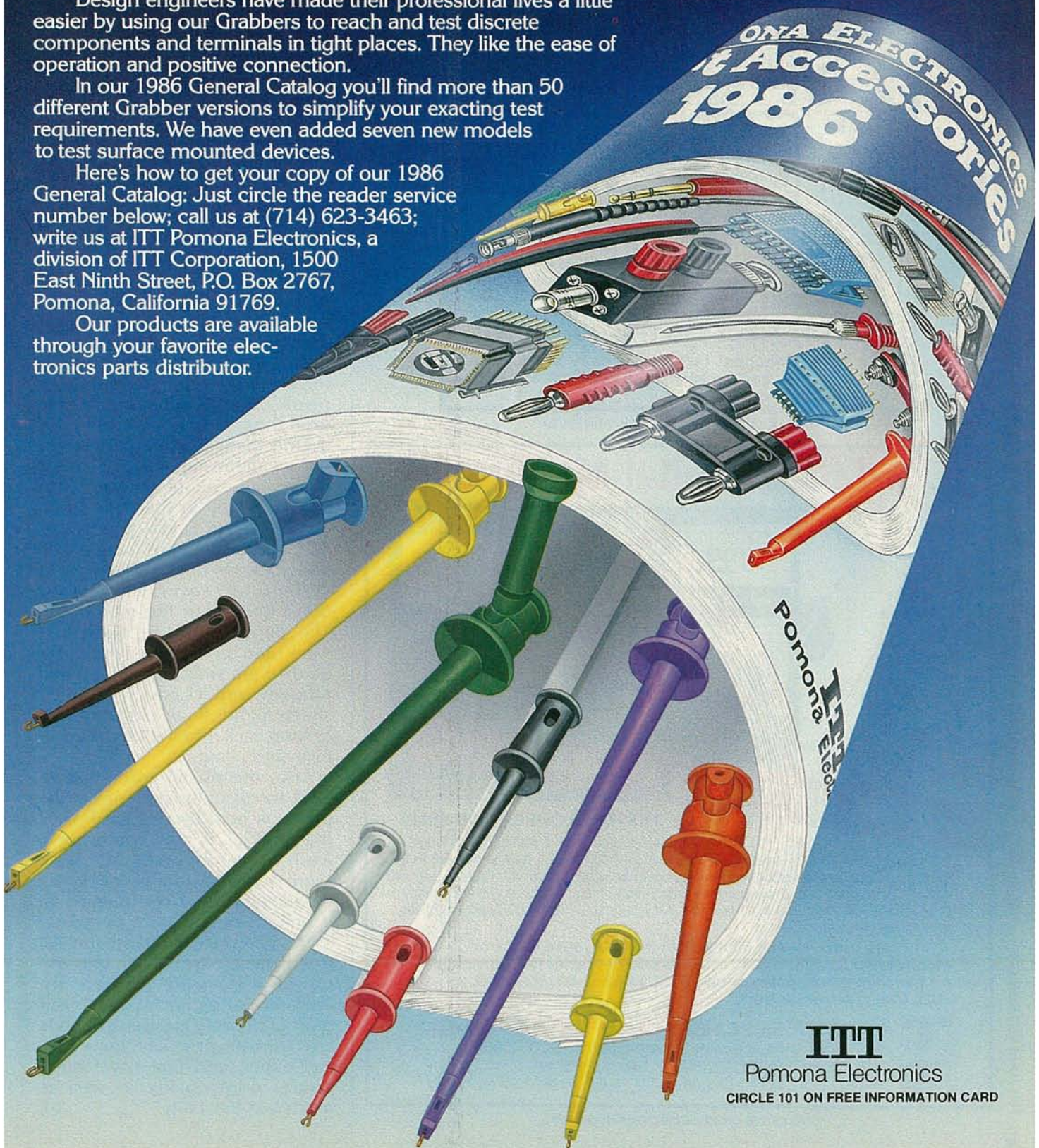Our products are available through your favorite electronics parts distributor.



ITT
Pomona Electronics
CIRCLE 101 ON FREE INFORMATION CARD

Call us FREE **1-800-626-6343**

or write for FREE Flyer.

COPPER ELECTRONICS

4200 PRODUCE ROAD - LOUISVILLE, KY 40217

 <p>RAEBIT VCR Multiplying System</p> <p>WATCH YOUR VCR FROM ANY TV IN THE HOUSE!</p> <p>6 LOT 64.95</p> <p>Retail 139.95 69.95</p>	 <p>WHISTLER</p> <p>Q2500 Superhet Quadradyne Radar Detector</p> <p>Retail 239.95 119.95</p>
 <p>Snake Charmer</p> <p>Retail 119.95 59.95</p> <p>QUANTITY PRICING AVAILABLE</p> <ol style="list-style-type: none">1. FORWARD WATTAGE AND REFLECTED WATTAGE2. CALIBRATE FOR SWR (VSWR) STANDING WAVE3. POWER WATTAGE RANGE SETTING4. SEALED METER MOVEMENT	 <p>uniden Beacon</p> <p>800XLT AIR/POLICE/800 MHz SCANNING RADIO</p> <p>Retail 449.95 289.95</p>

LOWEST PRICES IN THE COUNTRY!

We have a national factory warranty service on many brands, and we service All CB, Amateur, and Commercial Equipment.

CIRCLE 125 ON FREE INFORMATION CARD

Card Size Digital Multimeter



puts an ace in your pocket.

TESTON'S CHECKMAN MINI

fits any shirt pocket. Carry it with you at all times to test and measure AC/DC volts, ohms, and even do diode checks. **Self-contained in a vinyl case, with probes attached, this compact 3 1/2" digit multimeter folds to approx. 4.5" H x 3" W x 0.5" D and weighs only 3 oz.** Always ready for action, the high quality CHECKMAN MINI offers built-in autoranging, easy-to-read 0.4" high LCD, continuity/diode testing, and low cost.

To order, for shipment within the USA, send check or money order for \$29.95 (CT residents add 7 1/2% sales tax) plus \$1.50 for handling and shipping or call TOLL FREE: 1-800/221-5749. **FULL ONE YEAR WARRANTY.**



SIBER HEGNER NORTH AMERICA INC.

5 Landmark Square, Stamford, CT 06901

Call TOLL FREE: 1-800/221-5749

In CT: 203/967-4441 Telex: 279653 SANDH UR

CIRCLE 188 ON FREE INFORMATION CARD

unit with a serial interface should be available by the time you read this. No cable is included.

Our impressions

The model 150 is certainly compact enough to be stowed in a briefcase along with a portable computer such as the Radio Shack model 100. And its ability to operate from batteries makes it very handy for field use.

The model 150's print quality is not bad. It's definitely not good enough for business correspondence, but it is good enough for program listings, student papers, and the like. And its Epson/IBM compatibility should make it compatible with 90% of the software on the market, for personal computers ranging from Apples to CP/M machines to IBM PC's.

Print quality is very dependent on the paper that you use. Rough bond paper that is highly absorbent gives smeared characters; polished tractor-fed paper we use for everyday printouts produced results almost indistinguishable from the special ink-jet paper.

One thing that we particularly like about the model 150 is that it is quiet—quiet enough to use with a sleeping baby in the next room. The printhead is easy to change, and configuring the single DIP switch for set-up is also easy.

There are several things we don't like about the model 150. The paper feed mechanism is weak and poorly designed. It's hard to get single sheets aligned properly, and it's easy for printed sheets (either single or tractor-fed) to loop back into the feed mechanism and jam it.

Also, the plastic cover that allows access to the batteries in the platen is held by two weak clips that look as if they could break easily. If one (or both) did break, there would be no way of keeping the batteries in place. The manual is only so-so and lacks an index.

The \$479 price of the Diconix 150 is a little steep; other battery-powered portable printers are available for as little as \$100. But most of the very inexpensive units are thermal types that require special paper, and that have much poorer print quality, as well as much less flexibility.

R-E

Now electronics technicians can get into VCR Servicing quickly and easily

Learn professional VCR servicing at home or in your shop with exclusive videotaped demonstrations

Today, there are more than 10 million VCRs in use, with people standing in line to have them serviced. You can bring this profitable business into your shop with NRI professional training in VCR servicing. This top-level training supports the industry's claim that the best technicians today are those who service VCRs.

Integrated Three-Way Self-Teaching Program

In one integrated program, NRI gives you a study guide, 9 instructional units, 2 hours of video training tapes accompanied by a 32-page workbook that pulls it all together. At home or in your shop, you'll cover all the basic concepts of video recording, mechanical and electronic systems analyses, and the latest troubleshooting techniques. Your workbook and instructional units also contain an abundance of diagrams, data, and supplementary material that makes them valuable additions to your servicing library.

The "How-To" Videotape

Your NRI Action Videocassette uses every modern communications technique to make learning fast and easy. You'll enjoy expert lectures and see animation and video graphics that make every point crystal-clear. You'll follow the camera eye into the heart of the VCR as step-by-step servicing techniques are shown. Both electronic and mechanical troubleshooting are covered . . . including everything from complete replacement and adjustment of the recording heads to diagnosing micro-processor control faults.

Plus Training On All The New Video Systems

Although your course concentrates on VCRs covering Beta, VHS, and 3/4" U-Matic commercial VCRs, NRI also brings you up to speed in other key areas. You'll get training in capacitance and optical video disc players, projection TV, and video cameras. All are included to make you the complete video technician. There's even an optional final examination for NRI's VCR Professional Certificate.



Covers Beta *and* VHS systems with actual instruction on videotape.

The Best Professional Training

This exclusive self-study course has been developed by the professionals at NRI. NRI has trained more television technicians than any other electronics school! In fact, NRI has consistently led the way in developing troubleshooting techniques for servicing virtually every piece of home entertainment equipment as it appears in the marketplace.

Satisfaction Guaranteed . . . 15-Day No-Risk Examination

Send today for the new NRI Self-Study Course in VCR Servicing for

Professionals. Examine it for 15 full days, look over the lessons, sample the videotape. If you're not fully satisfied that this is the kind of training you and your people need to get into the profitable VCR servicing business, return it for a prompt and full refund, including postage. Act now, and start adding new business to your business.

Special Introductory Offer

This complete VCR training course with two hour videotape is being offered for a limited time only, on orders received from this ad, at our low introductory price of \$179.95. Save \$20 by acting now!

NRI Training For Professionals
McGraw-Hill Continuing Education Center
3939 Wisconsin Avenue Washington, DC 20016

YES! Get me started in profitable VCR servicing. Rush me my NRI self-study course in VCR Servicing for Professionals. I understand I may return it for a full refund within 15 days if not completely satisfied.



NRI Training For Professionals
McGraw-Hill Continuing
Education Center
3939 Wisconsin Avenue
Washington, DC 20016

PLEASE SPECIFY TAPE FORMAT DESIRED VHS BETA

Name (please print) _____

Company _____

Street _____

City/State/Zip _____

Enclosed is my check money order for \$179.95 (D.C. residents add 6% tax) Make check payable to NRI

Charge to VISA MasterCard _____

Interbank Number

Card Number _____ Expiration Date _____

Signature _____

(required for credit card sales)

2600-106

Join the Electronics and Control Engineers' Book Club®



DESIGNING ELECTRONIC CIRCUITS. By R. G. Middleton. 351 pp., 192 illus. Covers virtually every category of circuits commonly used. This practical manual provides the basic design procedures, tables and formulas vital to effective electronic circuit design. Plus over 60 start-to-finish procedures are featured along with scores of computer programs to help you design and analyze electronic circuits. 583673-4 Pub. Pr., \$36.95 Club Pr., \$27.50

POWER INTEGRATED CIRCUITS: Physics, Design, and Applications. Edited by P. Antognetti. 544 pp., 410 illus. This comprehensive book offers an exceptionally thorough overview of the state of the art in design and technology—including the latest design advances in voltage regulators, audio amplifiers, power MOS devices, BiMOS power ICs, and improved transistor structures. 021/295 Pub. Pr., \$42.50 Club Pr., \$31.95

TROUBLESHOOTING ELECTRONIC EQUIPMENT WITHOUT SERVICE DATA By R. G. Middleton. 303 pp., 162 illus. and tables. Packed with charts, diagrams, and case histories, this practical handbook shows you how to pinpoint defective electronic circuitry when no service data is available. 583134-1 Pub. Pr., \$27.95 Club Pr., \$19.95

STANDARD HANDBOOK OF ENGINEERING CALCULATIONS T. G. Hicks, Editor in Chief. 2nd Ed., 1,468 pp., 1,292 illus. and tables. Now revised, updated, and considerably expanded, this huge handbook provides more than 5,100 step-by-step procedures for solving the kinds of engineering problems you encounter most frequently in your work. 287/35X Pub. Pr., \$59.50 Club Pr., \$44.50

POWER CONTROL WITH SOLID-STATE DEVICES By Irving M. Gottlieb. 372 pages, 218 illustrations. This comprehensive book discusses every type of solid-state device and circuitry now available for power electronics. It covers both the proven-in-practice power control systems and the avant garde—as well as some promising combinations of the older and newer devices and circuitries. 583240-2 Pub. Pr., \$28.95 Club Pr., \$21.95

DIGITAL LOGIC DESIGN. By B. Holdsworth. 338 pp., 192 illus. All of the recent advances in digital design techniques are presented here in depth. It's both a text covering basic concepts and a practical guide to design techniques for combinational, clock-driven, and event-driven circuits. 582852-9 Pub. Pr., \$39.95 Club Pr., \$27.50

INTRODUCTION TO RADAR SYSTEMS. By M. I. Skolnik. 2nd Ed., 698 pp., 244 illus. Covering every radar fundamental and all important changes, this EE text exposes you fully to the systems themselves—and to their applications! Topics include radar equation, CW and frequency-modulated radar, MTI, pulse-doppler, tracking radar, receivers, displays, duplexers, noise, and more. 579/091 Pub. Pr., \$49.95 Club Pr., \$35.75

Get the competitive edge with the *newest* and the *best* information in your field . . . with books from all the leading publishers

New members!
Any one of these great professional books for only **\$2⁸⁹** as a premium with your 1st selection!

Spectacular values up to **\$105.00**

ANTENNA ENGINEERING HANDBOOK, 2/e. Edited by R. C. Johnson and H. Jasik, with contributions by 57 recognized authorities. 1,408 pp., 946 illus. This widely acclaimed Handbook gives you the guidance you need to solve problems in antenna design and application. 322/910 Pub. Pr., \$105.00 Club Pr., \$62.50

HANDBOOK OF PRACTICAL ELECTRICAL DESIGN. By J. F. McPartland. 416 pp., 300 illus. This volume provides a step-by-step explanation of designing electrical systems for industrial, commercial, and residential applications. 456/95X Pub. Pr., \$44.50 Club Pr., \$33.50

ELECTRONICS ENGINEERS' HANDBOOK, 2/e. Edited by D. G. Fink & D. Christiansen. 2,272 pp., 2,189 illus. This updated and enlarged edition covers all the latest knowledge in the field, including new advances in integrated circuits, pulsed and logic circuits, laser technology, telecommunications, and much more. 209/812 Pub. Pr., \$89.00 Club Pr., \$50.00

CONTROL SYSTEM DESIGN: An Introduction to State-Space Methods. By B. Friedland. 513 pp., illus. Covers feedback control, dynamics of linear systems, frequency-domain analysis, linear observers, linear, quadratic optimum control, random processes, and many other topics. 224/412 Pub. Pr., \$41.95 Club Pr., \$31.50

FUNDAMENTALS OF LOGIC DESIGN AND SWITCHING THEORY. By A. D. Friedman and P. R. Menon. 261 pp., 233 illus. Covering both theory and design techniques, this is an easy-to-understand introduction to the analysis and synthesis of digital circuits and their interconnection to create digital systems. 583601-7 Pub. Pr., \$26.95 Club Pr., \$21.50

CHOOSING AND USING CMOS. By M. J. Walsh. 304 pp., 155 illus. Offers a comprehensive overview of the semiconductor technology used . . . gives practical advice on circuit techniques to make your job easier. Specifications, characteristics and applications are included. 679/576 Pub. Pr., \$35.50 Club Pr., \$24.95

THE ENCYCLOPEDIA OF ELECTRONIC CIRCUITS. By R. Graf. 760 pp., 1,256 illus. This large volume provides circuits for virtually every type of application in 98 different categories. Each has a clear and concise explanatory text accompanying it. 583265-8 Pub. Pr., \$50.00 Club Pr., \$39.95

TELEVISION ENGINEERING HANDBOOK.—By K. B. Benson. 1,478 pp., 1,091 illus. Packed with the technical information and know-how you need to design, operate and maintain every type of TV equipment in current use. 047/790 Pub. Pr., \$89.50 Club Pr., \$62.50

68000 MICROPROCESSOR. By W. A. Triebel and A. Singh. 335 pp., 129 illus. This guide to Motorola's 68000 microprocessor uses a systems approach that includes extensive coverage of the 68000, its architecture, assembly language programming, and hardware interfacing techniques. 583613-0 Pub. Pr., \$34.95 Club Pr., \$26.95

MICROPROCESSOR HANDBOOK. Edited by J. D. Greenfield. 656 pp., 222 illus. This first-ever handbook helps you select the best microprocessor, enables you to understand the operation of a microprocessor you are now using and provides easily accessed coverage of the most popular 8 and 16-bit microprocessors currently available. 583636-X Pub. Pr., \$44.95 Club Pr., \$33.50

MCGRAW-HILL CONCISE ENCYCLOPEDIA OF SCIENCE AND TECHNOLOGY. Editor-in-Chief S. P. Parker and the Staff of the McGraw-Hill Encyclopedia of Science and Technology. 2,065 pp., 1,600 illus. This volume serves every need for understanding today's science and technology. Written by over 3,000 of the world's topmost experts, including 19 Nobel Prize winners, it covers 75 disciplines from Acoustics to Zoology. 454/825 Pub. Pr., \$95.00 Club Pr., \$66.50

CONTEMPORARY ELECTRONICS CIRCUITS DESKBOOK Compiled By H. Helms. 272 pp., 442 circuit diagrams. Packed with clearly reproduced circuit diagrams, all proven-in-action, covering the entire spectrum of electronics technology. Each diagram includes a title, a brief description, type numbers or values for significant components and a citation of the original source.

279/802 Pub. Pr., \$29.95 Club Pr., \$23.50

INTRODUCTION TO RADIO FREQUENCY DESIGN. By W. H. Hayward. 383 pp., illus. This comprehensive volume prepares you to actually design HF, VHF, and UHF equipment and enables you to follow much of the current literature. Structured equation sets make it easy to write programs for small computers or calculators.

582748-4 Pub. Pr., \$27.95 Club Pr., \$22.95

McGRAW-HILL ENCYCLOPEDIA OF ELECTRONICS AND COMPUTERS. By S. P. Parker, Editor-in-Chief. 960 pp., 1,266 illus., outsized 8 1/2 x 11 format. It's a single-volume library that covers the entire world of electronics from Edison's pioneering work in electricity right up to optical fiber communications, control systems, lasers, radar, TV receivers, artificial intelligence, and computer storage technology.

454/876 Pub. Pr., \$67.50 Club Pr., \$41.50

ELECTRONICS ENGINEERING FOR PROFESSIONAL ENGINEERS' EXAMINATIONS. By C. R. Hafer. 336 pp., more than 200 illus. Actually two books in one—a quick preparation manual to help you pass your P.E. exams on the first try and a rich source of practical electronics engineering information and know-how.

254/303 Pub. Pr., \$32.50 Club Pr., \$25.50

COMPUTER METHODS FOR CIRCUIT ANALYSIS AND DESIGN. By J. Vlach and K. Singhal. 656 pp., 148 illus. Computational methods have become an integral part of circuit analysis and design. And a solid understanding of the basics of computer-aided design is a must for engineers who want to achieve their career objectives.

582855-3 Pub. Pr., \$46.95 Club Pr., \$35.95

MODERN ELECTRONIC CIRCUITS REFERENCE MANUAL. By J. Markus. 1,264 pp., 3,666 circuit diagrams. Complete with values of components and suggestions for revisions—plus the original source of each circuit in case you want additional performance or construction details.

404/461 Pub. Pr., \$79.50 Club Pr., \$57.95

STANDARD HANDBOOK FOR ELECTRICAL ENGINEERS, 11/e. By D. G. Fink and H. Beaty. 2,448 pp., 1,414 illus. Today's most widely used source of electrical engineering information and data serves you as no other single work when you need detailed, timely, and reliable facts.

209/74X Pub. Pr., \$85.00 Club Pr., \$51.00

Be sure to consider these important titles as well!

DESIGN OF FEEDBACK CONTROL SYSTEMS. By G. H. Hostetter, C. J. Savant, and R. T. Stefani. 583206-2 Pub. Pr., \$41.95 Club Pr., \$31.45

MODERN COMMUNICATION CIRCUITS. By J. Smith. 587/302 Pub. Pr., \$43.95 Club Pr., \$32.50

MICROPROCESSOR SUPPORT CHIPS: Theory, Design, and Applications. By T. J. Byers. 095/183 Pub. Pr., \$43.50 Club Pr., \$35.25

DATA COMPRESSION: Techniques and Applications. By T. J. Lynch. 583267-4 Pub. Pr., \$44.50 Club Pr., \$31.25

DESIGNING DIGITAL FILTERS By C. Williams. 583627-0 Pub. Pr., \$36.95 Club Pr., \$27.95

ANALYSIS AND DESIGN OF DIGITAL INTEGRATED CIRCUITS. By D. A. Hodges and H. G. Jackson. 291/535 Pub. Pr., \$44.95 Club Pr., \$35.95


HANDBOOK OF OPERATIONAL AMPLIFIER CIRCUIT DESIGN. By D. E. Stout & M. Kaufman. 617/97X Pub. Pr., \$48.50 Club Pr., \$34.95

ENGINEERING MATHEMATICS HANDBOOK, 2/e. By J. J. Tuma. 654/298 Pub. Pr., \$41.50 Club Pr., \$31.00

DIGITAL COMMUNICATIONS. By J. Proakis. 509/271 Pub. Pr., \$45.95 Club Pr., \$32.95

CRYSTAL OSCILLATOR CIRCUITS. By R. J. Matthys. 583251-8 Pub. Pr., \$37.95 Club Pr., \$26.95

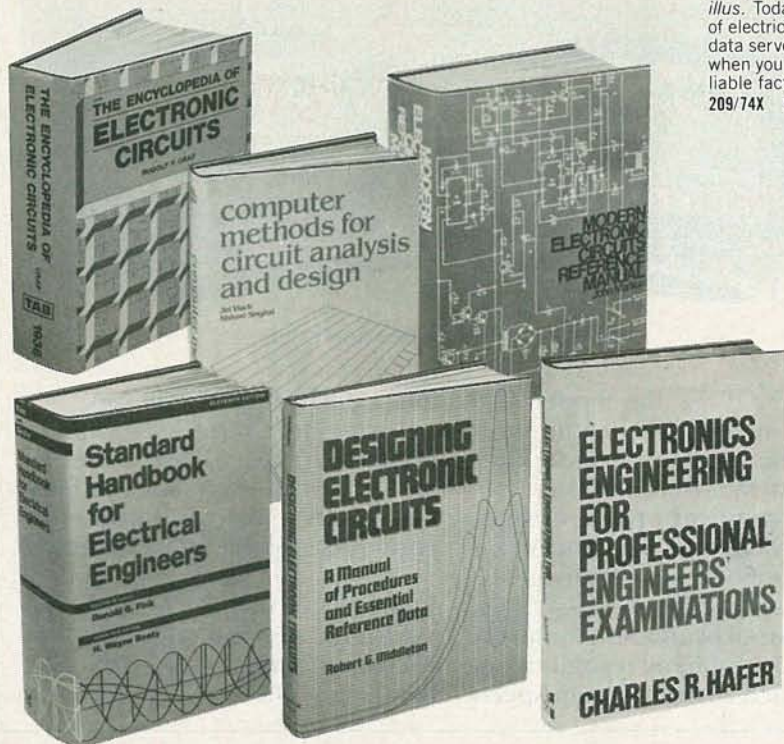NEW DIGITAL TROUBLESHOOTING TECHNIQUES: A Complete, Illustrated Guide. By R. G. Middleton. 583351-4 Pub. Pr., \$24.95 Club Pr., \$18.75



Why YOU should join now!

■ **BEST AND NEWEST BOOKS IN YOUR FIELD**—Books are selected from a wide range of publishers by expert editors and consultants to give you continuing access to the best and latest books in your field.

■ **BIG SAVINGS**—Build your library and save money too! Savings ranging up to 40% or more off publishers' list prices—usually 20% to 30%.

BONUS BOOKS—You will immediately begin to participate in our Bonus Book Plan that allows you savings up to 70% off the publishers' prices of many professional and general interest books!

■ **CONVENIENCE**—12-14 times a year (about once every 3-4 weeks) you receive the Club Bulletin FREE. It fully describes the Main Selection and Alternate Selections. A dated Reply Card is included. If you want the Main Selection, you simply do nothing—it will be shipped automatically. If you want an Alternate Selection—or no book at all—you simply indicate it on the Reply Card and return it by the date specified. You will have at least 10 days to decide. If, because of late delivery of the Bulletin you receive a Main Selection you do not want, you may return it for credit at the Club's expense.

As a Club member you agree only to the purchase of three books (including your first selection) during your first year of membership. Membership may be discontinued by either you or the Club at any time after you have purchased the first selection plus two additional books.

Other McGraw-Hill Book Clubs:

Architects' Book Club • Byte Book Club • Chemical Engineers' Book Club
• Civil Engineers' Book Club • Mechanical Engineers' Book Club

For more information, write to:

McGraw-Hill Book Clubs, P.O. Box 582, Hightstown, New Jersey 08520-9959

MAIL THIS COUPON TODAY

McGraw-Hill Book Clubs
Electronics and Control Engineers'
Book Club®
P.O. Box 582, Hightstown, New Jersey, 08520-9959

Please enroll me as a member and send me the two books indicated, billing me for the \$2.89 premium and my first selection at the discounted member's price, plus local tax, shipping, and handling charges. I agree to purchase a minimum of two additional books during my first year of membership as outlined under the Club plan described in this ad. A shipping and handling charge is added to all shipments.

Write Code No. of
\$2.89 selection here

Write Code No. of
first selection here

Signature _____

Name _____

Address/Apt. # _____

City _____

State _____ Zip _____

This order subject to acceptance by McGraw-Hill. All prices subject to change without notice. Offer good only to new members.

E33823

Power to the Product!

Low cost
B&K-PRECISION
DC power supplies
with high cost
features

NEW



Model 1630 (3 amp) \$225
Model 1610 (1 amp) \$150

Now you can have the power you need, wherever you need it, at a surprisingly low cost.

These new B&K-PRECISION power sources each give you control up to 30 volts DC with fully adjustable current limiting. Other features include:

- Excellent regulation and low-ripple characteristics
- Dual meters monitor voltage and current simultaneously
- Two current ranges
- Fine and coarse voltage controls
- Isolated output
- Protected against reverse polarity external voltages
- Two identical supplies can be connected in series or parallel
- Can be used as a constant voltage or constant current source

Compare prices, features and performance, and you'll agree that the 1610 and 1630 power supplies are revolutionary.

Available for immediate delivery at your local B&K-PRECISION distributor. For additional information or the name of your local distributor contact B&K-PRECISION.


BK PRECISION
DYNASCAN
CORPORATION

6460 West Cortland Street
Chicago, Illinois 60635 • 312/889-9087

International Sales: 6460 W. Cortland St., Chicago, IL 60635
Canadian Sales: Atlas Electronics, Ontario

South and Central American Sales,
Empire Exporters, Plainview, NY 11803

NEW PRODUCTS

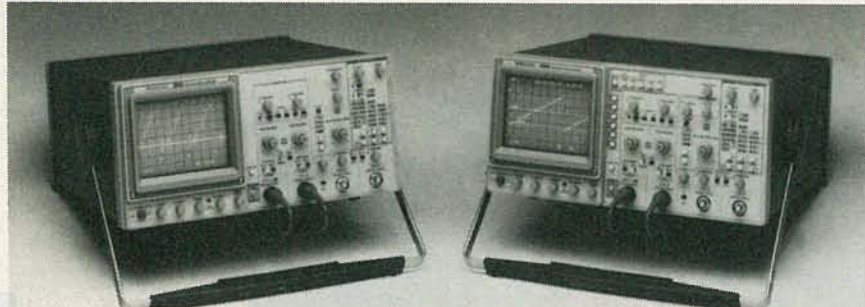

CIRCLE 30 ON FREE INFORMATION CARD

OSCILLOSCOPES, the model 2245 and the model 2246, feature four channels, 100-MHz bandwidth, and lend themselves to a multitude of applications in design, field service, and manufacturing.

Each model has a sensitivity of 2 mV to capture low-level signals, and 2% vertical and horizontal accuracy. Good timing resolution results from a 2 nS/div sweep speed

and a delay jitter of 1:20,000.

The model 2246 offers additional accuracy in DC voltage measurements and in delta voltage measurements via pushbutton measurement capability and cursors.

The model 2245 is priced at \$1800.00; the model 2246 oscilloscope is priced at \$2500.00.—**Tektronix, Inc.**, P. O. Box 500, Beaverton, OR 97007.

FIBER OPTIC CABLE TESTERS, the model 6800, (850 nm) and the model 6810, (1300 nm) fiber optic cable testers feature transmit and receive fiber testing, plus a six-



CIRCLE 31 ON FREE INFORMATION CARD

function digital multimeter (with K-type thermocouple) capability in one compact tester. The tester is designed for making on-site, optical attenuation measurements in communication cables, for testing electrical characteristics of optical devices, and for measuring temperature when finishing the end surface of plastic cables.

Both power input in nW and light input in dBm measurements at the light-receiving connector are provided. A relative value may be established by setting the current input value to "zero" by enabling a reference switch. That permits direct reading of input value changes without the necessity for calculations. Light output is achieved with an integral LED with -30 dBm or greater output power.

Accessories included are: 1300

nm sensor for the model 6810 and 850 nm sensor for the model 6800, (2) FC-type connector adapters, wavelength-sensitivity response chart, 4 AA batteries, AC adapter, carrying case, and comprehensive instruction manual.

The model 6800 (shown in photo) is priced at \$500.00; the model 6810 costs \$2995.00.—**Triplet Corporation**, One Triplet Drive, Bluffton, OH 45817.

HANDHELD COMPUTER, the model PC-1600, is the first to feature random-access floppy-disk storage. It has an optional 2½" micro floppy-disk drive with 128K mass storage, and also includes the first fiber-optic interface to be offered on a handheld unit.

The new model is software compatible with the model PC-1500A, with many peripherals fitting both units. That is because the ROM-resident BASIC interpreter and 60-pin I/O bus are the same in both models. The model PC-1600's Z80-like processor is about 2.5 times



CIRCLE 32 ON FREE INFORMATION CARD

faster than the PC-1500A's, making it a complement to the unit's increased memory capacity.

Measuring 3½ by 8 inches, and weighing less than a pound, the model PC-1600 features an easy-to-read, four-line, 26-character display. The standard configuration includes 16K RAM, expandable to 80K. The unit also has an analog input and an RS-232C serial port.

Suggested retail prices for the model PC-1600 and options are as follows: PC-1600 pocket computer: \$345.00; CE-1600F micro floppy drive: \$210.00; CE-1600; CE-1600P 4-color pen plotter/cassette interface: \$315.00; CE-1600M 32K RAM module: \$155.00.—**Sharp Electronics Corporation**, Sharp Plaza, Mahwah, NJ 07430.

DMM, the model 7061, provides up to 7½ digits of resolution for DC measurements and 6½ digits for all others. It can capture 1500 readings per second in an internal memory of 8000 readings, and it can output 300 readings per second on the IEEE bus. Response to an external trigger is less than 3 ms and an alarm condition is signaled in 1 ms.

Using a capture feature, the model 7061 will track results against a preset input level and record measurements before and after the desired event. An extensive math and statistics package



CIRCLE 33 ON FREE INFORMATION CARD

**DESOLDER-IT,
CLEAN-IT, COAT-IT,
FREEZ-IT...SEND FOR IT!**
Our new electronic problem solving catalog!

Chemtronics
681 Old Willets Path
Hauppauge, N.Y. 11788
800-645-5244
In NY 516-582-3322
Telex 968567

CIRCLE 54 ON FREE INFORMATION CARD

FLUKE

70 Series Digital Multimeters

3½ digit multimeters combine a 3200 count LCD display with an analog bar graph for quick visual checks of continuity, peaking, nulling and trends. The unparalleled operating ease, instant autoranging and 2,000+ hour battery life make this a lot of meter for the price. 3 year warranty.

<p>FLUKE 73 •0.7% basic DC accuracy •Autoranging only Reg.\$79.00 SALE \$76.50</p>	<p>FLUKE 75 •0.5% basic DC accuracy •Autoranging w/range hold •10 amp + autoranged mA ranges •Continuity & diode •Test beeper Reg.\$99.00 SALE \$89.00</p>	<p>FLUKE 77 •0.3% basic DC accuracy •Autoranging w/range hold •10 amp + autoranged mA ranges •Continuity & diode •Test beeper •Touch-Hold Reg.\$139.00 SALE \$125.00</p>
---------------------------------------------------------------------------------------------------------------------	-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------

Send now for your **FREE** catalog of electronic tools & test equipment

Call TOLL-FREE **1-800-638-6405**

W.S. JENKS & Son

1933 Montana Ave. NE Washington DC 20002

CIRCLE 66 ON FREE INFORMATION CARD

Radio-Electronics mini-ADS

can format results exactly as required. A ratio function is also available for comparison of any one measurement to any other measurement.

Using Solatron's exclusive pulse-width conversion technique, DC voltages from 100 nV to 1000 V are measured to an accuracy of 0.0005%. A true RMS AC function provides readings from 1 volt to 750 volts over a 10 Hz to 500 kHz bandwidth with a 10:1 crest-factor capability. Additional functions include AC and DC current, high-accuracy ohms, and temperature.

The model 7061 is priced at \$2795.00. A lower-cost version, the model 7062 provides identical performance with simplified front-panel controls, and costs \$2595.00.—**Solartron Instruments**, 2 Westchester Plaza, Elmsford, NY 10523.



CIRCLE 34 ON FREE INFORMATION CARD

VOICE-RECOGNITION SYSTEM, the *VOTAN TeleCenter*, is a full-featured interactive messaging system for companies or departments with 20 to 400 employees. Acting as a centralized message system, *VOTAN TeleCenter* will record, playback, and distribute messages for all callers; it can work with a company's PBX or function as a stand-alone voice mail system.

The system enhances a company's telephone-message operation by allowing callers to leave confidential messages in a user's voice mailbox—messages that might be too long or too complicated to leave with a receptionist.

Prices range from \$10,950.00 for a 2-channel system with 30 megabytes of memory to \$19,450.00 for a 4-channel system with 60 megabytes of memory.—**VOTAN**, 4487 Technology Drive, Fremont, CA 94538. R-E




THE MODEL WTT-20 IS ONLY THE SIZE OF A DIME, yet transmits both sides of a telephone conversation to any FM radio with crystal clarity. Telephone line powered - never needs a battery! Up to ¼ mile range. Adjustable from 70-130 MHz. Complete kit **\$29.95 + \$1.50 S+H**. Free Shipping on 2 or more! COD add \$4. Call or send VISA, MC, MO. **DECO INDUSTRIES**, Box 607, Bedford Hills, NY 10507. (914) 232-3878. CIRCLE 127 ON FREE INFORMATION CARD



THIS CHRISTMAS GIVE THE GIFT OF MTS Stereo with the Reconton V622 Entertainment Decoder. The V622 adds a new dimension to your TV viewing - cinema-like audio reproduction that was never before possible. Features include • dbx/NDR Noise Reduction • Stereo Synthesizer • MPX input **\$109.75 ea.** plus **\$3.50 shipping** (In NY add Tax.) 15 day money back guarantee. **DEL-PHONE INDUSTRIES INC.**, Box 150, Elmont, NY 11003, (718) 468-7367. CIRCLE 56 ON FREE INFORMATION CARD



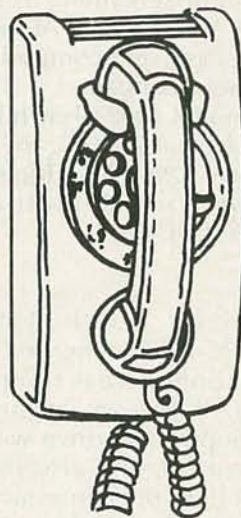MODULAR PROBE FITS ALL SCOPES • Save up to fifty percent • Instant repair - no soldering • Satisfaction guaranteed • 250 MHz 10X Attenuation • Model M12X10 ... **\$62 with readout ... \$68** Free accessories catalog. For immediate service call: 800-368-5719 outside Calif. 800-643-8382 in Calif. **TEST PROBES, INC.**, P.O. Box 2113, La Jolla, California 92038. CIRCLE 123 ON FREE INFORMATION CARD



CALL NOW AND RESERVE YOUR SPACE

- 6 x rate \$745.00 per each insertion.
- Reaches 239,312 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads.
- We typeset and layout the ad at no additional charge.

Call **516-293-3000** to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: mini-ADS, RADIO-ELECTRONICS, 500-B Bi-County Blvd., Farmingdale, NY 11735.




SCIENTIFIC ATLANTA superFall sale. Now available Scientific Atlanta 8500 and 8550 cable converters. It's the real thing! Perfect reception on all channels. Sale price 8500 or 8550 **\$239.95**. Hand remotes **\$20.00**. Call now to insure your order. (Limited supply!) Sale ends Oct. 31, 1986. C.O.D. orders accepted. **V.I.P. ELECTRONICS**, P.O. Box 628, Forestdale, R.I. 02824, (617) 755-9778. CIRCLE 192 ON FREE INFORMATION CARD

Radio-Electronics mini-ADS



60 dB SIGNAL ELIMINATOR—for removal of undesirable TV/FM/VHF signals. Can be tuned precisely to ANY signal within these ranges: *Model 26 - Ch's. 2-6 plus FM (54-108 Mhz) *Model 1422 - Ch's. 14(A) - 22(1) (120-174Mhz) *Model 713 - Ch's. 7-13 (174-216 Mhz). Highly selective notch/adjustable strength. Singles \$30. Quantity discounts to 60%. **STAR CIRCUITS - P.O. Box 8332 - Pembroke Pines, FL. 33084**
CIRCLE 94 ON FREE INFORMATION CARD

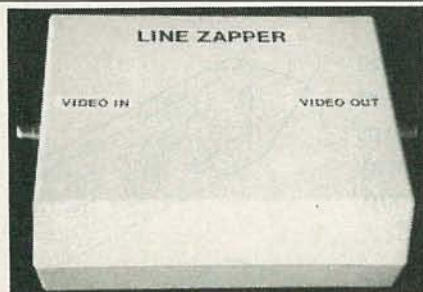


DESCRAMBLE THE NEW VIDEO TAPE COPY PROTECTION SCHEME. When you rent or buy a recent movie release, stop the vertical jumping and jittering in your TV picture with the LINE ZAPPER. This project detects and removes selected lines of video that have been modified and often interfere with normal television operation. Get your kit today only \$49.95 plus \$2.00 for shipping and handling. **ELEPHANT ELECTRONICS, Box 41865-L, Phoenix, AZ 85080. (602) 581-1973.** MasterCard and Visa accepted.
CIRCLE 120 ON FREE INFORMATION CARD



NEW JERROLD CS 68 CHANNEL CABLE TV CONVERTER with volume control & descrambler loop (Port). Programmable clock turns TV on/off & changes channel. Audio mute kills commercials. Programmable channel scan. Instant channel recall. Automatic fine tuning with manual override. Video & audio outputs. Friendly to all descramblers. Specify output. 1 year warranty. \$139. (Introductory offer) Free delivery. (Dealer Inquiries Invited) 514-739-9328. **CROSLY ELECTRONICS, Box 840, Champlain, N.Y. 12919.**
CIRCLE 196 ON FREE INFORMATION CARD




NEW SATELLITE DECODER. Parts, kits, assembled units. **BASIC KIT** with PC board, all parts, manual—\$69.95. **COMPLETE KIT**, including RF modulator & cabinet—\$109.95. **COMPLETE UNIT** (no RF modulator, but ready to run)—\$169.95. **COMPLETE UNIT w/ RF MODULATOR**—\$189.95. **PC BOARD & assembly manual**—\$24.95. **TWO BASIC KITS...Get the third free**—\$139.90. **PILGRIM VIDEO PRODUCTS, P.O. Box 3325, Plymouth Center, MA 02361.**
CIRCLE 197 ON FREE INFORMATION CARD

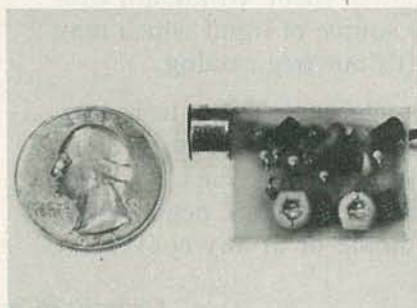

SIMPLY SNAP THE WAT-50 MINIATURE FM TRANSMITTER on top of a 9v battery and hear every sound in an entire house up to 1 mile away! Adjustable from 70-130 MHz. Use with any FM radio. Complete kit \$29.95 + \$1.50 S + H. Free shipping on 2 or more! COD add \$4. Call or send VISA, MC, MO. **DECO INDUSTRIES, Box 607, Bedford Hills, NY 10507. (914) 232-3878.**
CIRCLE 127 ON FREE INFORMATION CARD



"SODDER" WITH THE NEW BUTANE POWERED PORTASOL. No matter how you spell it Portasol is the handiest soldering iron around. Seven inches long. Variable power: 10 to 60 watts. 60 minutes use per refill. Only 29.95 + 2.00 P&H. Replacement tips: 1.2, 2.4 (standard), 3.2, 4.8mm, 7.50 + .50. Butane: 3.50 + .50. VA add 4% tax. Quantity discounts/dealers invited. Visa/MC orders: (703) 323-8000. Mail Ck/Money-order to: **PORTASOL, 4358 Harvester Farm Lane, Fairfax, VA 22032.**
CIRCLE 193 ON FREE INFORMATION CARD

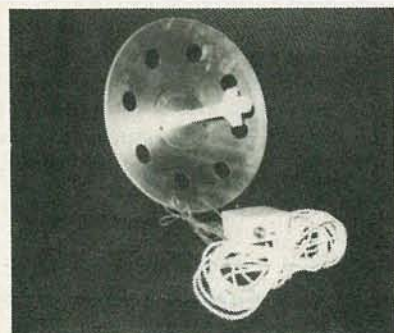

MICROWAVE ANTENNAS \$69.95. Now including shipping and Lifetime warranty. We Repair all types of Downconverters. Cable Converters and equipment available! Jerrold 400 wireless Converter \$72.95 plus shipping. Coax cable, T.V. parts, accessories, connectors, T.V. amplifiers. Write for free catalog or call for prices. **BLUE STAR IND., Dept. 105-RE10-86, 4712 Ave. N, Brooklyn, N.Y. 11234 (718) 338-8318 Ext. 105.**
CIRCLE 85 ON FREE INFORMATION CARD



ZENITH SSAVI \$169 EACH, beat the price increase. UHF gated pulse \$199. Reconditioned original equipment for UHF chs. 27, 48, 51, 60, etc. Quantity discounts. Satellite equipment. Surplus TV equipment: N-12, SB-3, Hamlin 1200, converters, amplifiers, etc. Catalog \$1. SSAVI modification/troubleshooting handbook \$6.50 ppd. **AIS SATELLITE, INC., P.O. BOX 1226-E Dublin, PA, 18917. 215-249-9411.**
CIRCLE 81 ON FREE INFORMATION CARD



PRICE BREAKTHROUGH... on the full-featured AR-140K 3½ digital multimeter KIT from the manufacturer. • 0.5% accuracy guaranteed • DCV range 0-1000V, 5 ranges • ACV range 0-750V, 2 ranges • DCA range 0-10A, 6 ranges • Resistance measurement up to 20M ohm, 6 ranges • Plus diode check. Includes test probe and manual. \$44.95 plus \$3, plus postage and handling. Use MC or Visa. **AMERICAN RELIANCE, INC. 9241 E. Valley Blvd., Suite 201, Rosemead, CA 91770, (818) 287-8400, 1-800-654-9838 (outside CA).**
CIRCLE 187 ON FREE INFORMATION CARD

Which Way To YOUR Future?

Are you at a crossroads in your career? Have you really thought about it? Are you *planning* for your future, or perhaps refusing to face the subject? Which way will you go — down the same old road? Or are you ready for something else?

In electronics you can't stand still. If you are not moving ahead, then you're falling behind. At the crossroads of your career, various choices are available — and, yes, *decisions* have to be made.


Which road will you take — one that doesn't go where you want to be, or one that leads to hard work *but also* to the better life? Ah, decisions, decisions!

Career decisions are so important that you need all the *input* you can get before locking-in on one of them. Grantham College of Engineering offers you *one* source of input which may help you in making that decision. It's our free catalog.

Ask for our free catalog and you may be surprised to learn how it is easily possible to earn a B.S. degree in electronics without attending traditional classes. Since you are already in electronics (you are, aren't you?), you can complete your B.S. degree work with Grantham while studying at home or at any convenient place.

But don't expect to earn that degree without hard work. Any degree that's worth your effort can't be had without giving effort to the task. And of course it is what you learn in the process, as much as the degree itself, that makes you stand out above the crowd — that places you in an enviable position, prestige-wise and financially.

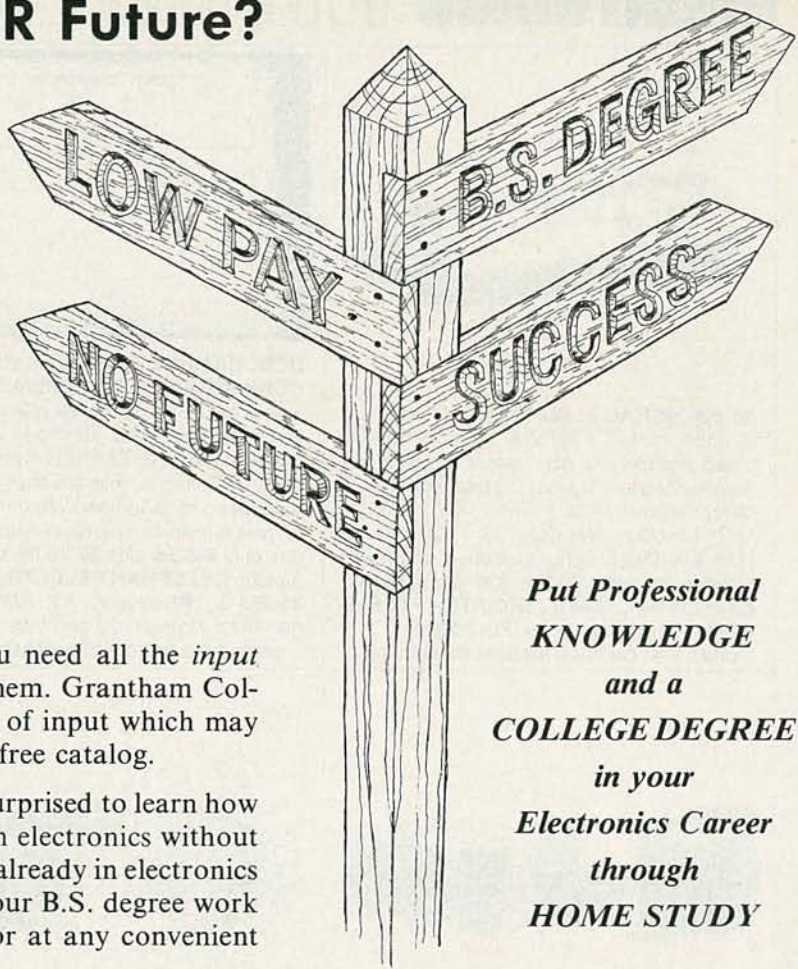Grantham College of Engineering
10570 Humbolt Street
Los Alamitos, California, 90720



*Put Professional
KNOWLEDGE
and a
COLLEGE DEGREE
in your
Electronics Career
through
HOME STUDY*

Grantham offers this program, complete but without laboratory, to electronics technicians whose objectives are to upgrade their level of technical employment.

Recognition and Quality Assurance

Grantham College of Engineering is accredited by the Accrediting Commission of the National Home Study Council, as a degree-granting institution.

All lessons and other study materials, as well as communications between the college and students, are in the English language. However, we have students in many foreign countries; about 80% of our students live in the United States of America.

**This booklet
FREE!**

This free booklet explains the Grantham B.S. Degree Program, offered by independent study to those who work in electronics.



for
**FREE
Booklet
CLIP
COUPON**
and mail in
envelope or
paste on
postal
card.


Grantham College of Engineering R10-86
10570 Humbolt Street, Los Alamitos, CA 90720

Please mail me your free catalog which explains your B.S. Degree independent-study program.

Name _____ Age _____

Address _____

City _____ State _____ Zip _____

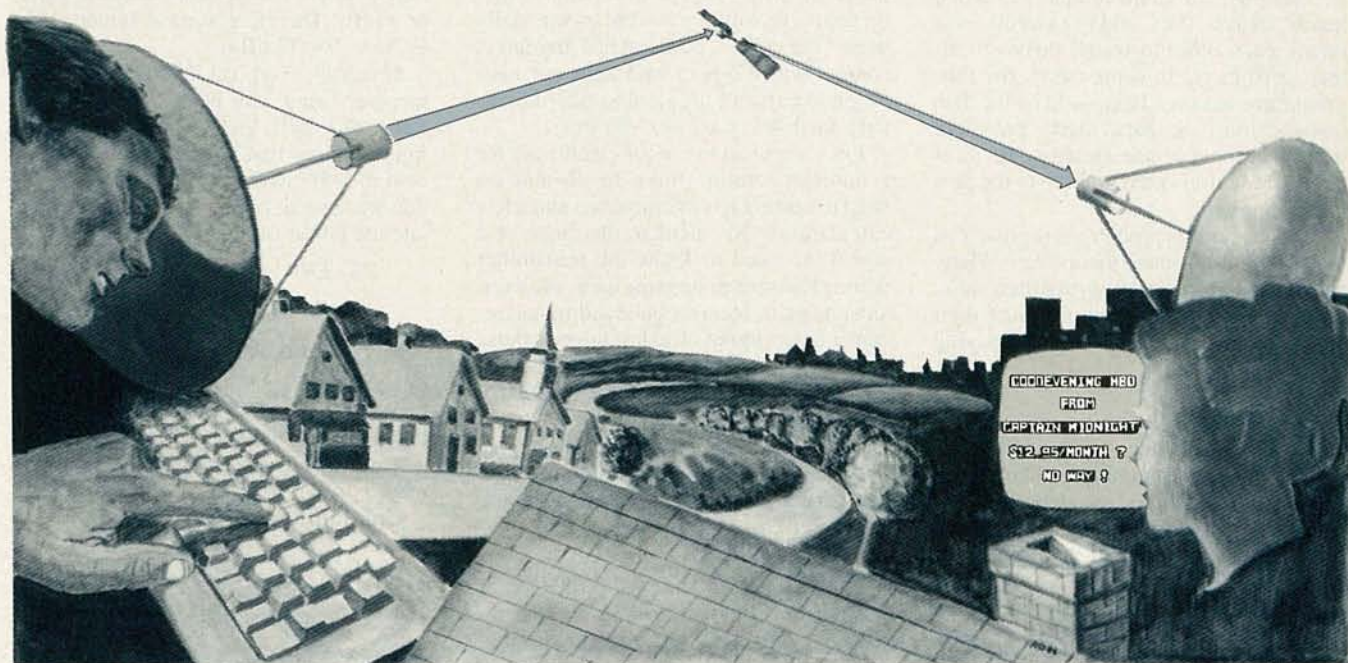

The Raid on HBO

Here's one way Captain Midnight might have engineered his daring raid on HBO.

WILLIAM SHEETS and RUDOLF GRAF

IN THE EARLY MORNING HOURS OF APRIL 27, 1986 the satellite-communications industry received a jolt that it's not likely to forget. For roughly four to five minutes, a satellite "pirate" commandeered HBO's east-coast feed, located on Galaxy 1, transponder 23. Viewers of a movie entitled "The Falcon and the Snowman" were suddenly treated to a color-bar display. Superimposed on the display was the following message:

"Goodevening HBO
From Captain Midnight
\$12.95/month
No way!
(Showtime/Movie Channel beware)"

Public reaction to the incident ranged from joy to outrage. But no matter what the reaction to the event, almost everyone asked the same question: How did Captain Midnight engineer his stunning "heist?"

HBO and other satellite-industry sources were in no hurry to reveal all that they knew about the incident; as you read on you'll come to realize why. As a result there was much misinformation in the media. One report stated that the feat required a great deal of technical expertise and about \$60,000 worth of equipment.

TVRO "hackers" must have had a few chuckles over that one. The truth of the matter is that taking over a private communications satellite is so terribly simple that the surprise is that no one had done it before.

And that fact, so clearly illustrated by Captain Midnight's escapade, has HBO and the rest of the satellite-communications industry scared silly.

A little background

In the beginning, satellite TV was the province of the professionals. The broadcast- or cable-network program producers used satellite to distribute their products to local TV stations or cable companies.

If you happened to live in a city or town serviced by one or more TV stations or cable companies, that arrangement sufficed because you had access to that programming either for free or for a monthly fee. But if you lived in one of the many areas of the country that had no such service, you were out of luck.

The early TVRO pioneers had no desire to "rip off" the cable companies. Their only aim was to obtain TV programming the only way possible—directly from satellites.

Early experimenters were faced with incomplete information and expensive equipment. Later on, savings were made possible by using salvaged radar gear and other surplus equipment. Eventually, the market grew large enough to encourage some companies to mass-produce TVRO gear.

All the while, a shadow of legality hung over the infant industry. The major producers all considered TVRO users a nuisance. Their position was that any unauthorized reception of their signals was against the law. But, partially due to pressure from their cable affiliates and partially due to the headache of having to track hundreds if not thousands of individual accounts, the cable networks refused to give authorization to TVRO owners, even if those owners offered to pay a fee.

Legislation passed in 1984 allowed everyone to receive satellite signals in their own homes as long as that reception was for personal use. The satellite industry took off. Prices fell as more and more manufacturers jumped into the TVRO field. For instance, the price of a good (85°K) LNA was once greater than \$500; today it is less than \$100.

By now, the original aims of the TVRO pioneers were largely forgotten. Many new TVRO buyers were mainly interested in "beating" the cable companies. Small hotels, motels, bars, and restaurants were racing each other to install dishes to attract customers. In some cases, the programming was even being sold by the dish owners; that was particularly prevalent with apartment-house systems. In most cases, those users paid nothing to the program suppliers.

A more serious problem was presented by the cable affiliates themselves. Many were habitually late in paying their bills. Others understated the numbers of their subscribers. Some didn't bother paying their bills at all.

Enter scrambling

The cable networks, led by HBO, answered back by scrambling their feeds. That one act achieved two goals: It enabled the programmers to control who could receive their signal, and it brought the cable affiliates into line.

Scrambling, though recognized by many as a necessary evil, did not come without bitterness. Used to receiving their programming for free, TVRO users were now required to shell out just under \$400 for a decoder, providing one could be located. Further, most services charged a monthly fee for their programming.

No one realized how much bitterness there was until that fateful night in April.

The raid

It is generally assumed that the raid was carried out by using a remote uplink to overpower HBO's signal and commandeer its transponder on Galaxy 1. See Fig. 1. Let's spend some time and see what the technical requirements are to conduct

such a raid. Particularly, we will see what dish sizes and power levels are needed. Note that the information provided is illustrative only. We will show what is theoretically possible, not what was actually done. The authors have not had any direct contact with Captain Midnight nor have they had a chance to examine that individual's facilities. (See box—Editor)

Let's see what the requirements are for a minimal satellite link. To do that we need to make a few assumptions and a few calculations. To calculate the range of a signal we need to know the transmitter power, transmitter-antenna gain, receiver-antenna gain, receiver bandwidth, and receiver noise-figure. The last three of those factors can be found by examining the technical details of the satellite we wish to transmit to. Determining the first two factors is the point of the following exercise.

Let's start off by determining the path loss between the transmitter and receiver.

That is found from:

$$PL = 37 + 20 \text{ LOG}(f) + 20 \text{ LOG}(D)$$

where PL is the path loss in dB, f is the frequency in MHz, and D is the distance between two points in miles. Assuming an uplink frequency of 6000 MHz (6 GHz) and a distance of 22,500 miles, the resulting path loss is:

$$PL = 37 + 20 \text{ LOG}(6000) + 20 \text{ LOG}(22,500)$$

$$PL = 37 + 75.56 + 87.04$$

$$PL = 199.6$$

At a downlink frequency of 4 GHz it is slightly less. Sparing you the mathematics, it is about 196.1 dB.

Next, let's do the calculations for a typical satellite downlink. A typical Effective Radiated Power (ERP) level for a transponder is 36 dBw (dB's referenced to one

watt). That means that the effective transmitter power is 3981 watts (or approximately 4000 watts). Actual transponder output levels are typically about 8 watts, or 9 dBw. Therefore, typical antenna gain is $36 - 9 = 27$ dBw.

On earth, a typical TVRO will have a receiver bandwidth of 30 MHz, a noise figure of 1.5 dB, and a 10-foot dish. From Fig. 2 we see that the gain of a 10-foot dish at 4000 MHz is about 40 dB. Now that we have all of the facts, we can calculate the power of a received signal.

$$P_R = \text{ERP} - \text{PL} + \text{antenna gain}$$

$$P_R = 36 - 196.1 + 40$$

$$P_R = -120.1 \text{ dBw}$$

or, converting to dBm (decibels referenced to a milliwatt), -90.1 dBm. Note that assuming a 50-ohm input, $0 \text{ dBm} = 223 \text{ mV}$; we'll need that figure in a moment.

Continuing with our calculations, since:

$$\text{dB} = 10 \text{ LOG}(P_2/P_1) = 20 \text{ LOG}(V_2/V_1)$$

$$90.1 = 20 \text{ LOG}(0.223/V_R)$$

where V_R is the received signal. Continuing:

$$4.505 = \text{LOG}(0.223/V_R)$$

$$V_R = 6.97 \mu\text{V}$$

Receiver sensitivity can be found from:

$$S_R = \text{NP} + \text{LOG}(\text{BW}) + \text{NF}$$

where S_R is the receiver sensitivity in dBm, NP is the noise power in dBm per Hz at 25°C, BW is receiver bandwidth in Hz, and NF is the noise figure. A typical noise power value would be -174 . Solving:

$$S_R = -174 + \text{LOG}(30 \times 10^6) + 1.5$$

$$S_R = -97.72 \text{ dBm}$$

The resulting S/N ratio can be found from:

$$S/N = P_R - S_R$$

Since our received signal is -90.1 dBm and our receiver sensitivity is -97.7 dBm, the resulting signal-to-noise ratio is 7.6 dB.

Incidentally, that is a marginal signal. Generally a TVRO receiver requires an 8-dB or greater S/N ratio for good performance. To improve signal performance, a larger dish (say 12-foot) would be called for. Many transponders output signal levels higher than our illustration; those could be viewed with satisfactory results.

We are getting off the track here a bit, so let's push on. Our point thus far was to lay the groundwork so that we could supply the missing data. The parameters required for a successful downlink do not differ greatly from those required for a successful uplink. Let's assume that we want to supply to our satellite-borne receiver an S/N of at least 10 dB, and prefer-

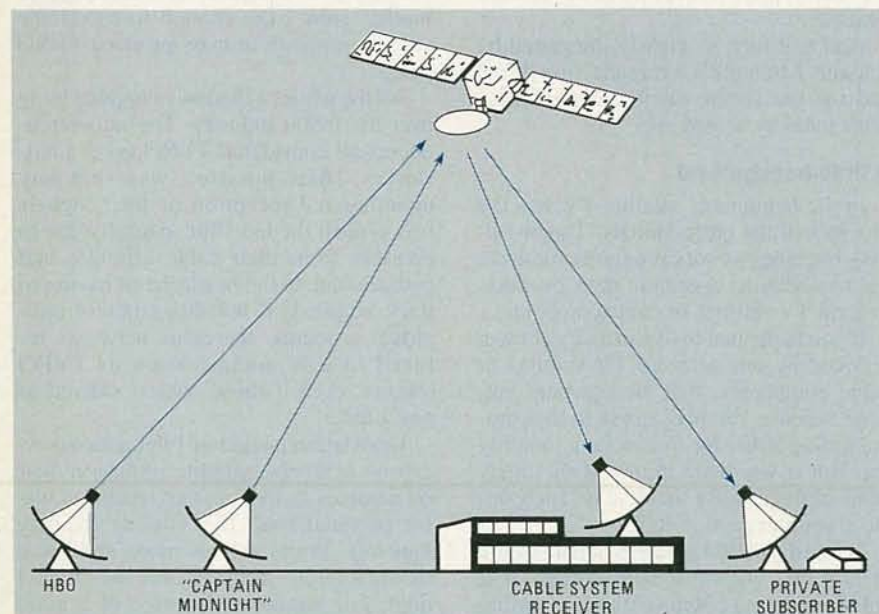


FIG. 1—IN THE MOST LIKELY SCENARIO, Captain Midnight commandeered HBO's transponder on Galaxy 1 by transmitting to the satellite from a secret uplink sight.

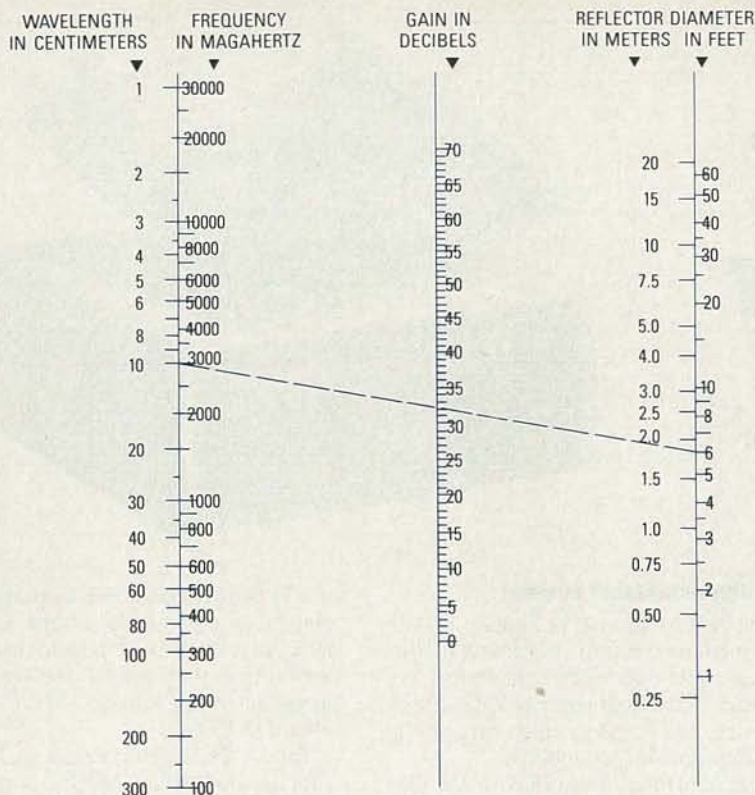


FIG. 2—IN THIS NOMOGRAPH, dish gain as a function of frequency and reflector diameter can be found.

ably one of 16 dB. Also, assume that the receiving antenna on the satellite has the same gain as the transmitting one. Finally, assume a satellite receiver NF of 1.5 dB and a receiver bandwidth of 36 MHz. We can plug those values into our equation for signal-to-noise ratio and solve for the required power level:

$$S/N = P_R - S_R$$

$$S/N = P_R - 174 + \text{LOG}(BW) + \text{NF}$$

$$P_R = -174 + 75.56 + 1.5 + 16 = -80.94$$

Let's round that off to -81 dBm. With an antenna gain of $+27$ as previously calculated, the effective received-power-level required would be $-81 - 27 = -108$ dBm. We earlier saw that at 6 GHz, path loss is 199.6 dB. Therefore, the effective transmitted power required would be $199.6 - 108 = +91.6$ dBm, or $+61.6$ dBw.

Assuming a modest 10-foot dish diameter with a gain of about 42 dB, the transmitted power would be $61.6 - 42 = 19.6$ dBw. That translates to a transmitter power level of 91.2 watts.

In other words, all that is needed to uplink to a satellite is about 91 watts into a 10-foot dish. Smaller dish sizes could also be used. For instance, with a 6-foot dish the job could be done with 280 watts. With larger dish sizes, less power would be needed.

Granted it is not cheap to generate those types of power levels at 6 GHz, but it does not really pose much of a technical

obstacle. It's even easier to generate pulse power at those levels. Intelligence could not be conveyed, but a prospective jammer could achieve his aim of knocking a transponder out of service. Further, an encoded signal presents even an easier target. All that a would-be pirate needs to do is to disrupt the signal enough that the system's decoders cannot do their jobs.

As you can now see, large dish sizes and high power levels are not needed to establish satellite communications. With a moderate-sized dish, a few tens of watts are all that are needed at microwave frequencies. It is feasible, in fact, to mount a satisfactory uplink system in a small truck or van.

Other considerations

So far we have seen what is needed to establish satellite communications. But what is needed to snatch control of a transponder that is already in use? A characteristic of FM systems is the so-called "capture effect," which allows the system to receive only the strongest of two or more competing signals. Usually the weaker signal is suppressed by between 20 and 30 dB. The difference between signal levels, called the capture ratio, need not be great for the capture effect to take place. In high-quality receivers, capture ratios of less than 2 dB are common.

Of course, FM is used for both video and audio satellite communications. That means that to take over a transponder, a pirate need only have a signal that is a few

Captain Midnight Unmasked!

On July 22, an Ocala Florida man surrendered to Federal authorities and admitted to being Captain Midnight.

As part of a plea-bargain agreement, John R. MacDougall was to be fined \$5000 and sentenced to a year's probation in exchange for a guilty plea to one count of interfering with an FCC authorized transmission, a misdemeanor. That offense normally carries a maximum penalty of one year in jail and/or a \$100,000 fine.

MacDougall, 25, owns a TVRO dealership and also worked part-time as an operator for Central Florida Teleport, a satellite-TV uplink facility. He used that facility's equipment when he interrupted HBO's Galaxy 1 uplink from Hauppauge, NY on April 27.

The FCC used information provided by HBO and Hughes Communications, owner of the Galaxy bird, as well as analysis of several videotape recordings of the interfering signal to track down MacDougall. Further, the investigators also learned that another transmission, consisting of a color-bar pattern only, had over-ridden HBO's signal nearly a week before the celebrated message from Captain Midnight.

Using the supplied data, the FCC was able to determine approximate dish size (seven meters) and the model of character generator used. Examining the nearly 2,000 professional uplink sites in this country, those factors, and others such as transmitter power, allowed the investigators to narrow their search to less than a dozen sites.

Further, the Central Florida Teleport was the only one of those facilities that was not otherwise in use at the time of the April, 27 incident. Sealing the case was the fact that both interfering transmissions occurred just after scheduled programming from the Florida facility had ended and the operator on duty both times was MacDougall.

Asked to speculate as to why the Captain turned himself in, investigators revealed that several of MacDougall's associates at the Central Florida Teleport had been questioned and that he himself had been subpoenaed. No other individuals or organizations have been implicated in the jamming incident. **R-E**

dB stronger than that of the legitimate user.

Repelling the raiders

Now that we have a little insight into how a pirate might take over a transponder, what can the programmers do to stop or catch him? Unfortunately, the answer is not much. Let's see why.

HBO has stated that it will simply increase power to override any future would-be pirate. But that approach presents its own problems. Some satellite-

continued on page 80

Satellite-TV Descrambler

VICTOR J. TERRIO, JR. and JAMES PERODI

Learn about one of the more popular satellite-TV scrambling systems, and how it can be decoded.



IF YOU HAVE BEEN WAITING FOR AN EASY-to-build satellite decoder, your wait is over. Here is a relatively simple unit that can be built in just a few evenings. In the process, it can teach you about some of the technology behind satellite-TV scrambling.

Before you get too excited, we should tell you that the unit will *not* decode HBO, Showtime, or any of the other services that use the *VideoCipher II* system. Instead, it decodes the *Telease-Maast* system. That medium-security system is used by two adult-oriented direct-broadcast systems, as well as by a few sports-programming services.

Next, heed this important warning: **The use of an unauthorized descrambler may constitute a violation of federal or local laws. It is up to the user to determine what the requirements for use are, and to meet them fully before using the unit.** The details presented in this article are for informational purposes only.

Design philosophy

The decoder represents the latest version of a series of decoders that have been developed over the last five years. We took the best features of previous designs and combined them with the latest technical advancements to achieve the unit described here. The unit offers a number of convenience features, including front-panel-mount phase-control adjustments and crystal socket.

The unit is designed to accept baseband audio and video inputs; outputs of that type are available from just about any satellite-TV receiver. The unit as described in this article features an RF modulator. It is an easy matter to eliminate that modulator and bring out baseband audio and video outputs for connection to a VCR, etc. If applicable, that modification is recommended. It will be fully described later on.

The *Telease-Maast* system

The *Telease-Maast*, or *Telease* system is a medium security system that uses analog audio and video scrambling. By contrast, to the high-security *VideoCipher II* system uses analog video scrambling and digital audio scrambling.

That's not to say that a *Telease*-encoded signal is simple to descramble. In the *Telease* system the video is inverted, its level is reduced to one half of normal, and it is modulated by a 94-kHz sine wave. The audio is modulated by a 15.67 kHz sine wave before being placed on the usual 6.8-MHz subcarrier. To further complicate matters, no attempt is made to precisely control the frequency of the scrambling oscillator at the uplink and no reference signal is transmitted with the scrambled signal. Finally, 94 kHz is nearly 6 times the TV horizontal-scan frequency (15.734 kHz), but not exactly. If the scrambling sine wave is not completely cancelled, the 6th harmonic of the horizontal frequency (94.4 kHz) can beat with the sine wave to generate an annoying 400-Hz interference signal.

Descrambling *Telease*

A block diagram of the descrambler circuit is shown in Fig. 1. Circuit details for that unit are shown in the schematic of Fig. 2. Refer to both of those figures as we describe the operation of the circuit.

Transistors Q1 through Q4 form a balanced differential video amplifier. The baseband video input jack, J1, is connected to the inputs of Q1 and Q2. The signals at the collector of Q3 and the emitter of Q4 are inverted with respect to each other, and are also 180° out of phase. Those signals are fed to the inputs (pins 1 and 4) of IC3, an MC1496 balanced demodulator. That IC removes the 94-kHz carrier from the video signal. The outputs of IC3 appear at pins 6 and 12; the outputs differ in phase by 180°.

The outputs of IC3 are fed to IC1-a, ¼

of a TL084CN quad biFET op-amp. That amp takes the outputs of the balanced demodulator and uses them to develop an error voltage that in turn is used to control operation of the Voltage Controlled Oscillator (VCO).

The VCO, which consists of XTAL1, varactor diode D2, and Q9, is part of a Phase-Locked Loop (PLL). The other stages of the PLL consist of a divide-by-16 counter, a divide-by-4 counter, and a 94-kHz bandpass filter. The PLL accurately tracks the scrambling sine wave frequency and allows the decoder to generate the reference signal needed for descrambling. The output of the VCO, taken from Q9, is fed to Q8 and then Q7 for amplification and buffering. It is then fed to pin 1 of IC5, a 4024 7-stage binary ripple counter that is set up as a divide-by-16 counter. The output of that stage (pin 6) is then fed to IC4, a 4027 dual J-K flip-flop that is set up as a divide-by-4 counter. Three outputs are taken from IC4. One, taken from pins 6 and 15 and labeled CLOCK1 in Fig. 1, is fed to a 94-kHz bandpass filter built around IC1-b. The output of that filter serves as a reference signal for IC3.

The second output, taken from pins 1 and 11 and labeled CLOCK2, is fed to another 94-kHz bandpass filter, which is built around IC1-c. The output of that filter is the correction signal used to remove the scrambling sine wave. It is fed to the cancel- and phase-adjust stage, which consists of R70, R65, R39, R47, R49, C10, and C11. That stage is used to adjust the phase of the correction signal for proper cancellation of the scrambling signal.

The actual cancellation of the scrambling signal takes place in the clamper-amp and adder stage. In that stage, which consists of transistors Q5 and Q6 the scrambled video, which is taken from the output of the differential amp, is summed with the correcting sine wave to yield an unscrambled video signal.

The third output of IC4, taken from

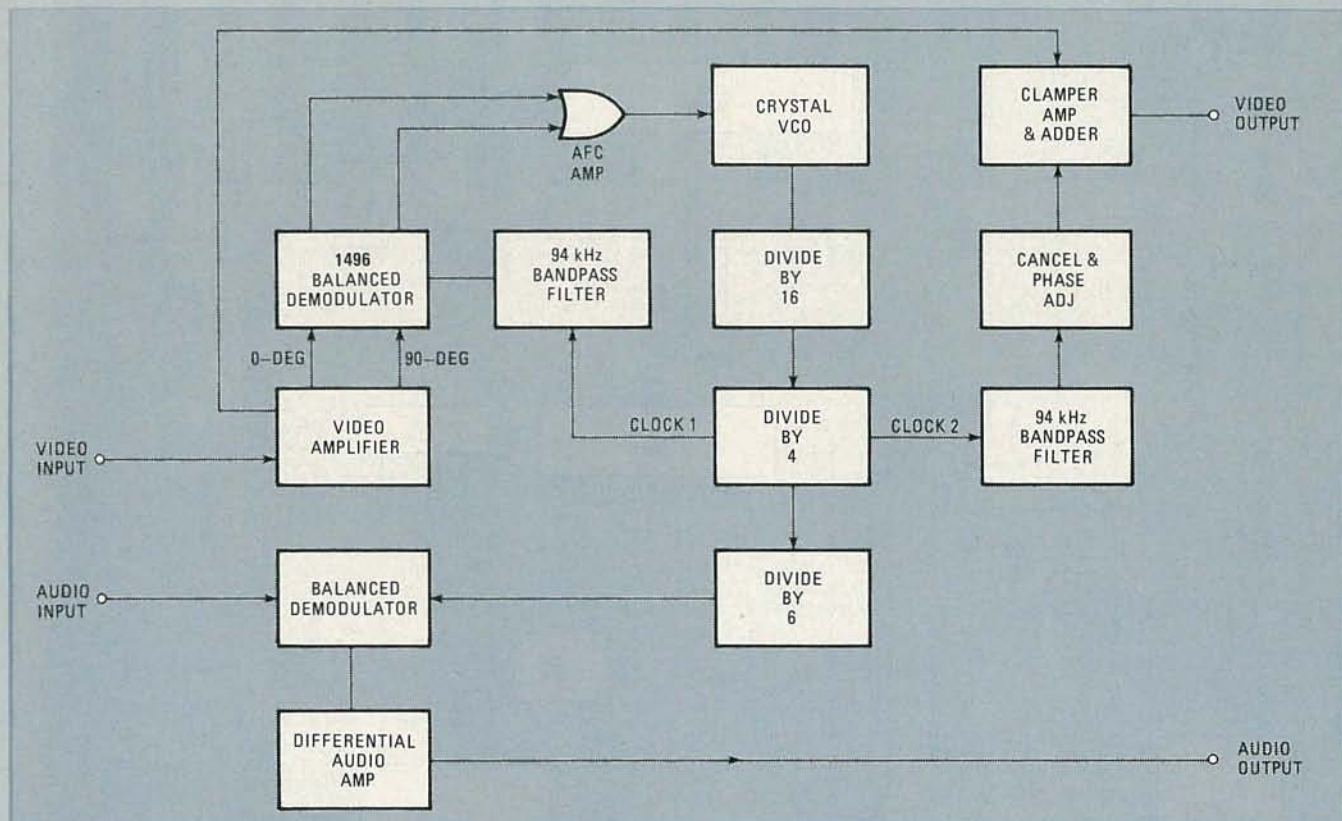


FIG. 1—DESCRAMBLING TELEVISION. This block diagram shows the steps that a descrambler must take to decode that medium-security system.

pins 2 and 10, is fed to IC6, a divide-by-2-through-10 synchronous counter configured as a divide-by-6 counter. The output of that IC is used as a reference signal by IC2, a second MC1496 balanced demodulator. That demodulator removes the 15.67-kHz scrambling sinewave from the audio and passes the audio to a differential audio amplifier, which is the last of the four op-amps of IC1-d. The output of that amp is fed either to an audio output or to the RF modulator, if it is used.

Building the unit

The first step in building the descrambler is to obtain the board. An appropriate double-sided PC pattern is shown in PC Service, found elsewhere in this issue. Otherwise, a board can be purchased from the supplier mentioned in the Parts List.

A parts-placement diagram for the board is shown in Fig. 3. Note that the version shown includes an RF modulator. If you have a VCR, TV, etc. that can accept direct audio and video inputs, the RF modulator and its associated components (D1, C1, and R46) can be deleted. If that is done, the audio and video inputs to the modulator can be brought out to the rear panel of the case and terminated with standard phono plugs. If your TV, VCR, or other equipment can accept direct au-

dio and video inputs that is the recommended approach as it will yield superior picture and sound.

Building the unit is a fairly straightforward procedure, although a few things bear special mention. Before mounting S1, trim the lead nearest the outer edge of the board so that it does not make contact with the board when the switch is mounted. Connect the lead stub to the appropriate pad in the center of the PC board with a jumper as indicated in Fig. 3. The unused pad beneath the switch becomes the ground connection for the external power supply (more on that in a moment).

The crystal socket should be accessible from the front panel so that you can switch between services easily. There are a number of ways to accomplish that. One is to use a panel-mounted socket and to make the connections to the PC board with short jumpers. Another is to mount a PC-mounted socket on Y-shaped PC-mount tie points, creating a 90° crystal socket.

As mentioned, the PC board is double-sided. If you buy the board from the supplier mentioned in the Parts List, it will be provided with plated-through holes. Otherwise, you should solder all component leads on both sides of the board and you must also install feedthroughs at all un-

used pads. Use short, uninsulated pieces of wire for that and be sure to solder them on both sides of the board. Clipped resistor, capacitor, etc. leads are ideal for use as feedthroughs.

Three components, C17, R74, and R75, are installed on the solder side of the board. One end of R74 shares a mounting hole with the base of Q5; one end of R75 shares a mounting hole with Q6. The other end of both resistors is tack-soldered to the ground plane. One end of C17 connects to the junction of C8/R43; it shares its mounting hole with either of those components. The other end of the capacitor is connected to the ground plane. You likely will need to extend the lead length of the capacitor with a jumper to make that connection.

The unit requires ± 5 volts, and +12 volts if the optional RF modulator is used. Most aftermarket computer power supplies are capable of supplying the needed voltages and current levels.

Note that the components are tightly spaced in some regions of the board. Because of that, some of the resistors must be mounted vertically.

For easiest construction, if used, mount the RF modulator last. Otherwise you might run into difficulty when mounting the surrounding components. Note that the output channel is selected by the

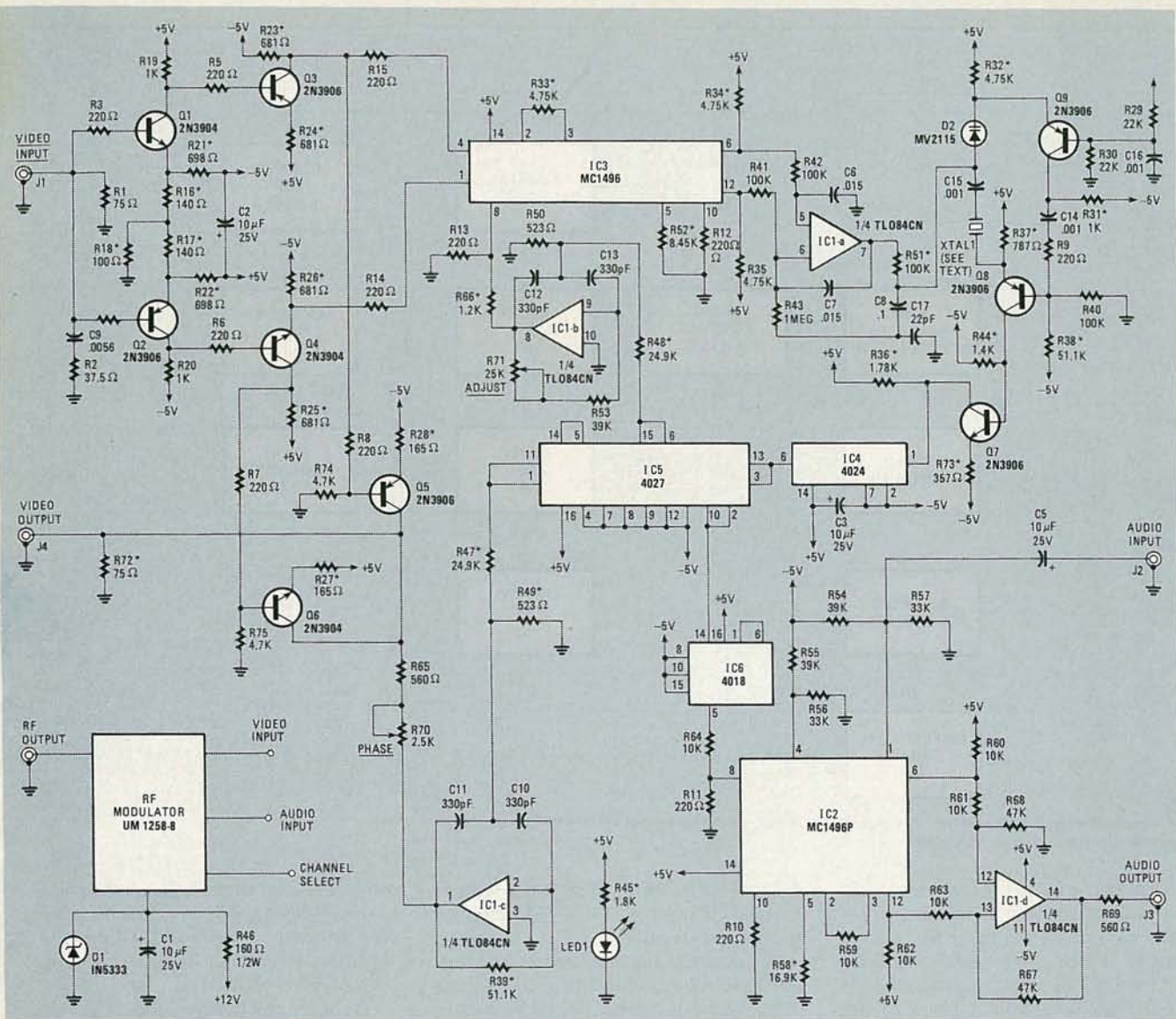


FIG. 2—THE DESCRAMBLER CIRCUIT uses just a handful of IC's and transistors to restore a Telease-encoded signal to normal.

CHANNEL SELECT lead. For a Channel 3 output, that lead should be grounded; otherwise, clip the lead. Finally, be sure to solder all four of the modulator's mounting lugs to the ground plane.

Note that many of the resistors are 1% precision types. Do not substitute 5% units for them.

Checkout

Before you test or use the unit, read the following notice:

It may be unlawful to operate a descrambler to decode certain satellite transmissions without authorization. It is up to the user to determine what the requirements are for legal use of the decoder and to meet them.

Once you have obtained the needed authorizations, if any, you may proceed with the testing.

Plug in the power pack and switch S1 to the on position. LED1 should light up.

Check the power-supply voltages at the following locations: B, +5; Y, -5; R, +12, and cathode side of D3 (if RF modulator is used), +6. All voltages should be within 5% of the given values. Assuming that all voltages are correct, plug an appropriate crystal into the socket and monitor the unit for signs of overheating. If none of the transistors or IC's become hot, you can proceed.

Actually, we've gotten a little ahead of ourselves. Let's backtrack and say a few words about selecting and obtaining the crystal.

Table 1 lists the required crystal frequencies to decode some of the satellite services that use the Telease system. Note that the crystal's resonant frequency must be within 150 Hz of the listed center frequency for acceptable picture locking.

Crystals can be obtained from several sources. Among those are JAN Crystals (2400 Crystal, Fort Myers, FL 06017) and

B&D Crystal Company (1727 West Galbraith Rd., Cincinnati, OH 45239). Further, crystals are available from a source mentioned in the Parts List. However, due to Federal law, it is illegal to supply a descrambler in assembled or kit form with a crystal. Thus, the kit supplier will not honor orders for crystals.

Once you have selected and obtained the proper crystal, and obtained any required authorization, it is time to do the final checkout.

Connect the baseband-video and the audio outputs of your satellite receiver to the appropriate inputs on the descrambler. If using the RF modulator, connect the modulator's output to the VHF terminals on your TV set. Be sure to use only the highest grade shielded cable and to terminate that cable with a 75-ohm-to-300-ohm matching transformer. If using direct video outputs, connect the video and audio outputs of the descrambler to the ap-

PARTS LIST

All resistors 1/4 watt, 5% unless otherwise noted

R1—75 ohms
 R2—37.5 ohms
 R3—R15—220 ohms
 R16, R17—140 ohms, 1%
 R18—100 ohms, 1%
 R19, R20—1000 ohms
 R21, R22—698 ohms, 1%
 R23—26—681 ohms, 1%
 R27, R28—165 ohms, 1%
 R29, R30—22,000 ohms
 R31—1000 ohms 1%
 R32—R35—4750 ohms, 1%
 R36—1780 ohms, 1%
 R37—787 ohms, 1%
 R38, R39—51,100 ohms, 1%
 R40—R42—100,000 ohms
 R43—1 megohm
 R44—1400 ohms, 1%
 R45—1800 ohms, 1%
 R46—160 ohms, 1/2 watt
 R47, R48—24,900 ohms, 1%
 R49, R50—523 ohms, 1%
 R51—100,000 ohms, 1%
 R52—8450 ohms, 1%
 R53—R55—39,000 ohms
 R56, R57—33,000 ohms
 R58—16,900 ohms, 1%
 R59—R64—10,000 ohms
 R65, R69—560 ohms
 R66—1200 ohms, 1%
 R67, R68—47,000 ohms

R70—2500 ohms, potentiometer, PC mount
 R71—25,000 ohms, potentiometer, PC mount
 R72—75 ohms, 1%
 R73—357 ohms, 1%
 R74, R75—4700 ohms

Capacitors

C1—C5—10 μ F, 25 volts
 C6, C7—.015 μ F
 C8—0.1 μ F
 C9—.0056 μ F
 C10—C13—330 pF
 C14—C16—.001 μ F
 C17—22pF

Semiconductors

IC1—TL084CN quad BIFET op-amp (Texas Instruments)
 IC2, IC3—MC1496P balanced modulator (Motorola)
 IC4—4024B CMOS 7-stage binary ripple counter
 IC5—4027B CMOS dual J-K flip-flop
 IC6—4018B CMOS divide-by-2-through-10 counter
 Q1, Q4, Q6, Q7—2N3904 NPN transistor
 Q2, Q3, Q5, Q8, Q9—2N3906 PNP transistor

D1—1N5333 6-volt Zener diode
 D2—MV2115 Varactor diode
 LED1—green LED

Other components

S1—SPDT toggle switch

J1, J2—phono jacks, PC mount
Miscellaneous: PC board, regulated power supply (+5 volts, 0.9 amps, -5 volts, 0.1 amps, +12 volts, 0.3 amps), RF modulator (optional, Astec UM-1285-8 or equivalent), crystal socket (see text), additional phono jacks (optional, for direct video/audio version), cabinet, wire, solder, hardware, etc.

Note: The following are available from Pilgrim Video Products, 33 Grasshopper La, Marshfield MA 02050: Complete kit including PC board, RF modulator, case, power supply, and all parts except the crystal, \$109.95; basic kit, including PC board, power supply, and all components except the crystal, but minus the modulator and case, \$69.95; PC board alone, \$24.95; Assembled and tested unit, minus the crystal, \$189.95. Other components and kit configurations are available; contact the supplier for more information. Please add \$2.50 for postage and handling. All MA residents must add 5% for sales tax.

Crystals are available from Blackbeard, P.O. Box 737, Prudential Center Station, Boston, MA 02199 for \$22.00 each. Be sure to specify frequencies desired. All MA residents must add 5% for sales tax.


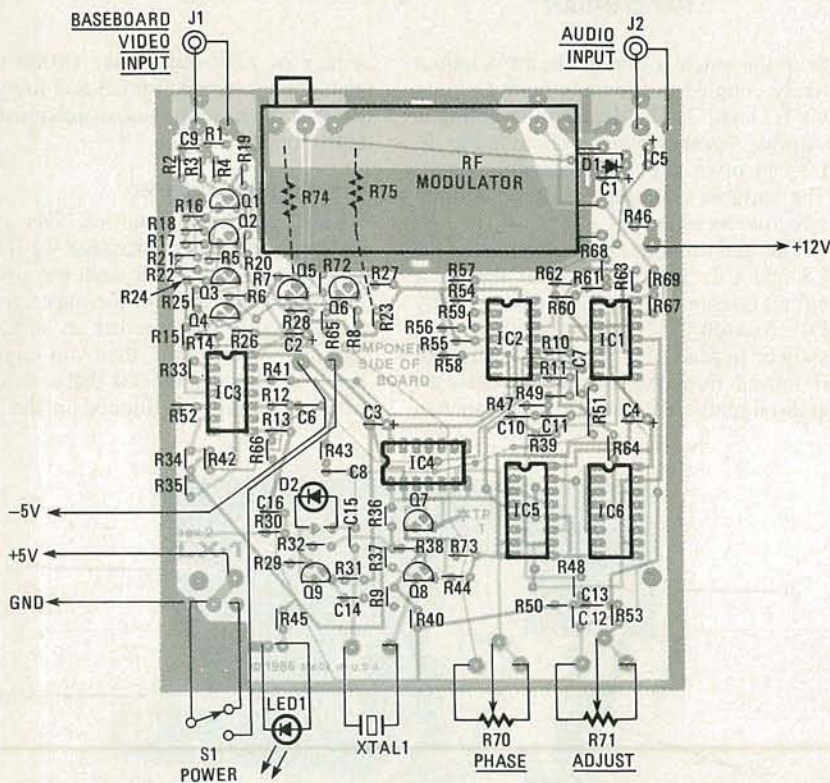


FIG. 3—FOLLOW THIS PARTS-PLACEMENT DIAGRAM when building the decoder. The patterns for the double-sided PC board are provided in PC Service.

appropriate inputs on your TV-set, monitor, or VCR.

Turn the unit on, using S1. You should

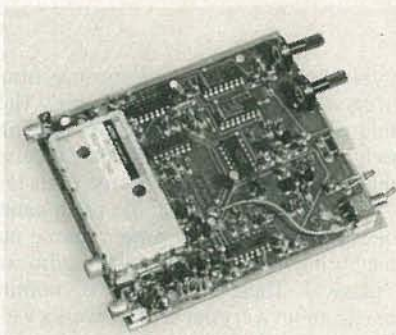now be receiving clear audio. Adjust potentiometers R70 and R71 until the picture locks in. That's all there is to it. If you run



THE COMPLETED DESCRAMBLER board is shown here.


TABLE 1—
CRYSTAL FREQUENCIES

Service	Frequency (MHz)
Italian Soccer	6.052167
Portuguese Soccer	6.056800
Fantasy Channel	6.020412
American Triple Ecstasy	6.028440
Wrestle/Mania	6.025140

into trouble, go back over your work looking for things like cold solder joints, solder bridges, or out-of-place components. If you've satisfied yourself that all is as it should be, your crystal may be off frequency. Remember, one that is off by as little as 150 Hz will cause the unit to fail to function. Obtain a different one and try again.

R-E

BUILD THIS

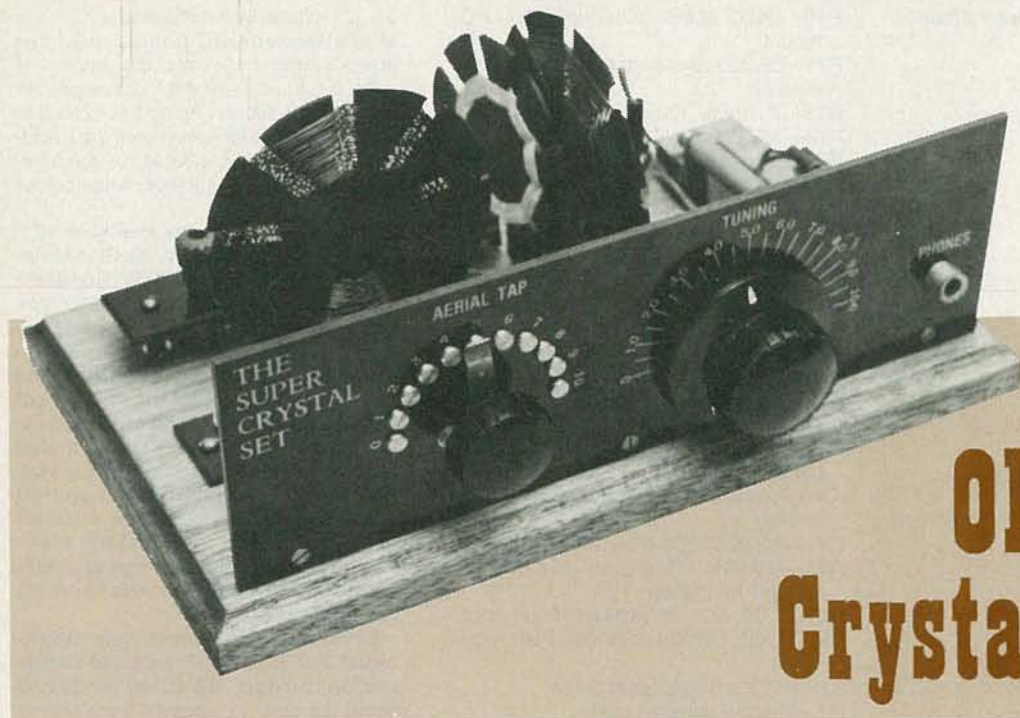

Old-Time Crystal Radio

Here's how to build a vintage-style crystal radio receiver with performance that might surprise you.

PAT O'BRIAN

EVERY ELECTRONICS HOBBYIST HAS BUILT a crystal set. What? *You* haven't? Then this vintage-style crystal radio is the one to build! It's a high-performance receiver that tries its best to remain true to its era.

Crystal radios capture the imagination because they need no power source and they bring back the days when radio was "magic." There is, of course, nothing magic about a crystal set that works well. But careful design can make a receiver something special. This design uses the signals captured by the antenna very efficiently. Of course, the attractive polished wood base helps make the receiver special, too—even to those who aren't usually fascinated by the "magic" of crystal radios.

A high-performance circuit

The schematic of the receiver is shown in Fig. 1. One of the features of the design is that the antenna-tuning circuit is separate from the main frequency-selection circuit. The antenna-tuning circuit is made up of an 80-turn, 10-tap coil (L1), a coupling coil (L2), and an optional fixed capacitor (C1). It acts as a pre-selector for the main tuning circuit. In other words, it maximizes the strength of the signals received by the antenna at a particular frequency or frequency band.

The inductance of L1 is varied by selecting one of the coil's taps. The energy

from the antenna-tuning circuit is inductively coupled to the main tuning circuit via L2 and L3. The degree of coupling is variable. As shown in the photo in Fig. 2, L2 can pivot about its mounting point. The variable coupling results in a more selective receiver.

The main tuning circuit is made up of L3 and C2. RF energy from that tank circuit is tapped off by S2 and detected by D1. Switch S2 isn't a conventional switch. Instead, it is an alligator clip that is moved from tap to tap. The detected audio signals are fed to jack J1, and then to

a pair of high-impedance (4000 ohm) headphones. Capacitor C3 acts to bypass RF past the headphones, which must be a high-impedance type.

Building the receiver

How you build your receiver is, of course, a personal choice. But we'll show you what we think is the right way to do it. If you lack the skills or the materials that are needed to put together an authentic-looking crystal radio, then you might be better off buying the kit that's available from the source mentioned in the Parts

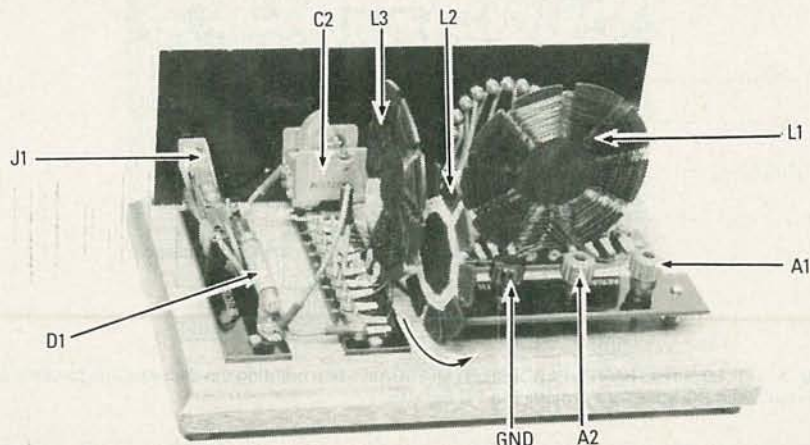


FIG. 1—THE CRYSTAL RADIO SCHEMATIC. The coils are hand-wound. Their starting points are indicated by bold dots. Note that switch S2 is not a standard switch—it is an alligator clip at the end of a "flying lead."

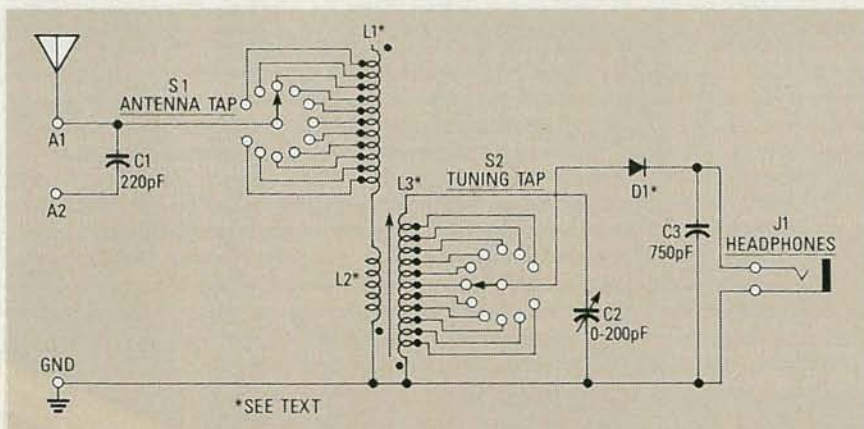


FIG 2—REAR VIEW of the crystal set shows how the components are mounted on bakelite panels, which are in turn mounted to the hardwood base. Note that the coupling coil, L2, pivots around its mounting point so that its degree of coupling to L3 can be adjusted. Also note the case in which D1, the crystal detector, is mounted.

List. (The receiver shown in the photos was built from a kit.) If you choose to put yours together from scratch, don't hesitate to change our layout to suit the components you find. Just try to keep the flavor of the past by following our prototype and by using things like brass screws, DCC (Double Cotton Coated) wire, bakelite mounting panels, etc.

Before we can build the receiver, we have to get all the components together. It will take some scrounging but it can be done. The best place to start is with the

components you'll have to make yourself: the three "spider-web" coils.

Winding the spiderweb coils is perhaps the most difficult part of building the receiver. It's actually not that difficult if you follow our directions carefully. Two of the coils, L1 and L3, are wound identically. They consist of 80 turns of 26-gauge enamel-coated wire wound on a 9-spoke spiderweb coil form with a diameter of 4 1/4 inches.

The coil is wound as ten separate 8-turn coils. After they are wound, they are con-

PARTS LIST

D1—1N34A germanium. See text
 C1—220 pF, mica
 C2—0-200 pF, variable
 C3—750 pF, mica
 L1, L3—80 turns of 26-gauge wire on spider-web form. See text.
 L2—16 turns of 26-gauge wire on spider-web form. See text.
 J1—phone jack, 1/4 inch
 Miscellaneous: Hardwood base, coil forms, 26-gauge wire, binding posts, rubber mounting feet, high-impedance headphones, etc.

NOTE: A complete kit for the crystal receiver (order No. K-9002) is available from Dick Smith Electronics, Inc., P.O. Box 8021, Redwood City, CA 94063, 800-332-5373 (orders) 415-368-8844 (inquiries) for \$79.95 plus \$5.50 handling. High-impedance vintage (1940) headphones (order No. C-4001) are available for \$19.95 plus \$2.50 shipping. California residents must add 6.5% sales tax.

nected together—the connections become the taps. Figure 3 shows what your coil form should look like, and indicates some of the winding specifics.

The coils are wound from the "front" of the coil forms, which is the side where the "L" mounting brackets are attached. Start at the inside of the coil and work outward. To start each 8-turn coil, feed about 10 inches of wire through the appropriate hole from the front of the form, taking it around the right side of the mounting spoke (which we'll call the anchor spoke), and feeding it again through the same hole and pulling it tight. That anchors the start of each coil in place. Now wind the wire around the coil form, under the first spoke, over the second, under the third, and so on.

The "finish" end of the coil is pushed through the next hole toward the outside of the form, and it is anchored to the spoke by bringing the wire around the left side of the mounting spoke and through the hole and pulling it tight.

The start of the next coil is anchored at the hole where the preceding coil ended. Be sure to wind the coils tightly so that a total of 80 turns will fit on the coil form, and so that you don't cover holes on the anchor spoke.

When all ten 8-turn coils are wound correctly on the coil form, you should be left with 9 pairs of wire, and two single wires (the start and end). Twist each pair together tightly, and cut to an appropriate length. Solder the 9 pairs together, and tin the start and finish leads. You'll have to apply a good amount of heat from the soldering iron because you need to melt the enamel coating. If you do it right, you won't have to scrape the leads bare. You can check your work by measuring con-

continued on page 101

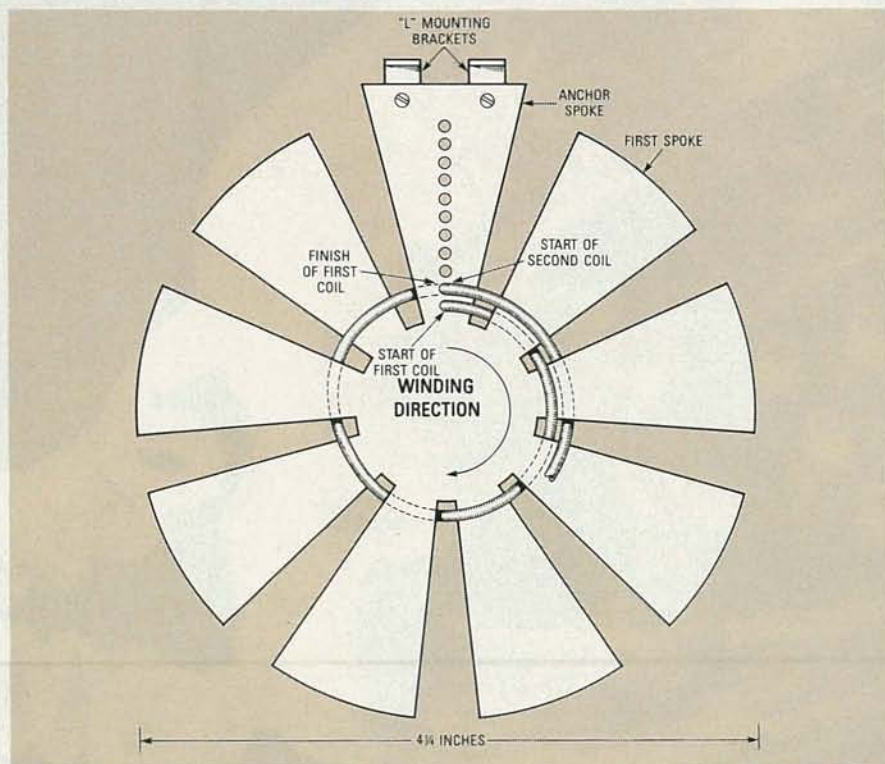


FIG 3—THE SPIDER-WEB COILS must be hand wound. Here, shown half size, is the coil form for L1 and L3. Each coil consists of 80 turns of 26-gauge enamel-coated wire, tapped every 8 turns. However, as explained in the text, they are wound as ten separate 8-turn coils. Coil L2 is wound as 16 turns of 26-gauge cotton-coated wire on a 3 1/4-inch form. Use stiff, black cardboard to make the forms.

DEFINED BY WEBSTER AS AN INSTRUMENT FOR CONVERTING sound into electrical impulses for transmission by wire, the telephone has become much more than that in the over 100 years since its invention. The modern telephone is among the more sophisticated appliances in your home or office. Despite that, it is often taken for granted, even by those that are technically inclined. Let's correct that by taking a look inside that electronic marvel.

Inside the telephone

In any communications system, the basic goal is to transmit intelligence from one point to another with a minimum of distortion. To transmit intelligence using the telephone sys-

tem we must convert sound into an electrical signal, send the electrical signals over the wires to a distant point, and then convert the electrical signals back into sound energy.

It is important that all of that occur with a minimum of distortion. In face-to-face communications much information is exchanged by facial expression, gestures, etc. With a telephone, all of that information must be exchanged by sound only. Feelings, emphasis, and the like are therefore conveyed by voice tones and, as a result, the recreated voice at the receiving side of the link must be as accurate as possible.

Because of that, the key link in the telephone system is the

In this look inside the telephone, we'll learn how one of man's most important inventions does its job so reliably.



Inside The TELEPHONE

RUDOLF GRAF and CALVIN GRAF

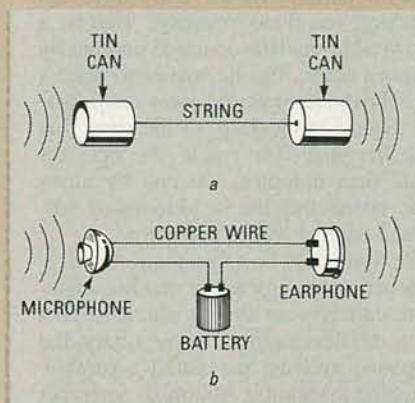


FIG. 1—TWO COMMUNICATIONS SYSTEMS. A mechanical system that is often experimented with by children is shown in *a*. The electrical system shown in *b* is the basis of our modern telephone system.

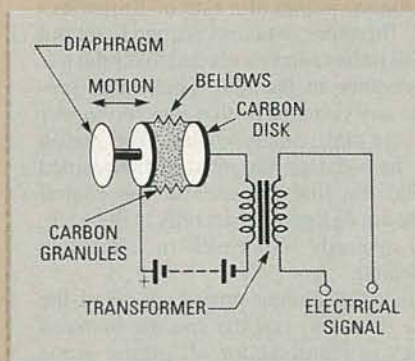


FIG. 2—IN A CARBON MICROPHONE, the vibration of a disc causes the compression of carbon granules inside a bellows to vary. That in turn varies the load across a battery.

transducer, a device for converting one type of signal into another type. The telephone "system" shown in Fig. 1-*a* uses a transducer that converts sound into mechanical energy. When you speak into one of the cans, sound waves cause the end of the can to vibrate. The vibrations from the can are carried to the receiver can a tightly stretched string. The end of the receiving can follows the in-and-out motions of the transmitting can and causes the air around it to vibrate to reproduce, albeit poorly, the transmitted sound.

A far superior system is shown in Fig. 1-*b*. There we see a circuit consisting of a microphone, earphone, battery, and wires. The microphone is a transducer that converts sound energy to electrical energy. The earphone is its complement; it converts electrical energy into sound energy. Power for the system is supplied by the battery. If two such circuits were combined, a simple telephone system would be formed.

Let's take a closer look at the transducers. In Fig. 2 we see a diagram of a simple carbon microphone. Such microphones have been used in telephones almost since the beginning.

The microphone contains a flat, round, metal diaphragm. When sound strikes that diaphragm it vibrates. The diaphragm is connected by a rod to a bellows that is filled with carbon granules. The vibration of the diaphragm causes the bellows to expand and contract, varying the compression of the carbon granules. That varying compression presents a varying load to the battery, causing a time-varying current to be created. That current is passed through a coupling transformer and sent down the telephone line to the earphone.

The earphone converts the varying current back into sound. A diagram of an earphone is shown in Fig. 3. The current passes through the coupling transformer and then through a coil that is wound on a permanent magnet. That generates a time-varying magnetic field. That field causes a rigid metal diaphragm to vibrate, re-

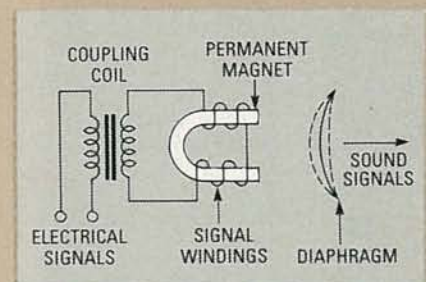


FIG. 3—IN A TELEPHONE EARPHONE, current passing through coils wound on a permanent magnet causes variations in the field of that magnet. That causes a metal diaphragm to vibrate, which generates sound.

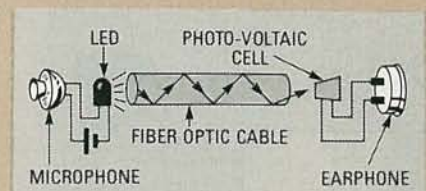


FIG. 4—COMMUNICATING WITH LIGHT. A basic fiber-optic communications system is shown here.

producing the original sound.

The principles behind the communications loop we have described have remained essentially unchanged since the invention of the telephone. However, technology does evolve. Currently, the telephone system is in the midst of one of its most significant changes. It is changing from a system based on wires and electric current to one that is based on optical fibers and light.

Figure 4 shows how a light-based communications loop works. At the transmitter end, a microphone is used to modulate the output of an LED. The light from the LED is conducted to the receiver by an optical fiber. At the receiver, the varying

light levels are translated to a varying current by a photocell and fed to an earphone. The earphone turns the current into sound as previously described.

A modern telephone

As we've seen, the telephone started out as a relatively simple instrument. But it evolved quickly into a complex piece of electronic equipment as shown in Fig. 5. In addition to performing its basic task of communications, a telephone is required to perform a number of functions that help the telephone switching system make the proper connections. It also performs some basic signal-processing functions. For instance, it automatically compensates for variations in speech amplitude.

The simple telephone system that we've described thus far is of limited usefulness. That's because it can only be used to communicate between two established points. If an individual wanted to communicate with a number of people, he would need a separate telephone "system" for each of those. To overcome that limitation, we need a way to connect one telephone to a number of other telephones. That capability is provided by a system of local, exchange-area, and long-distance switching networks.

On the local level, switching functions are handled by a *central office*. That facility contains the switching and signaling equipment for a local area or *exchange*, as well as the batteries for the local system.

Each *subscriber telephone*, or individual telephone number (extension telephones are merely extensions of the subscriber telephone) is connected to the central office via a *local loop*. The loop consists of a color-coded wire pair. The positive wire is always green, while the negative wire is always red. Those wires are also designated as *ring* (negative) and *tip* (positive). That corresponds to the tip and ring connections of the plugs used in manual switchboards.

The central office and all of the local loops that it serves make up the *local exchange* or *local network*. A block diagram of a typical local exchange is shown in Fig. 6. The geographical area served by a local exchange can vary greatly. In urban areas, it might cover less than 12 square miles, while in rural areas a local exchange might serve a region as large as 130 square miles.

Central offices in a region are linked together into what is known as an *exchange-area* network. An exchange-area network might cover several cities and towns over a wide geographical area or just a single city or part of a city. Its coverage area is of course determined by the number of subscribers it must serve. Figure 7 shows a simplified diagram of an exchange-area network.

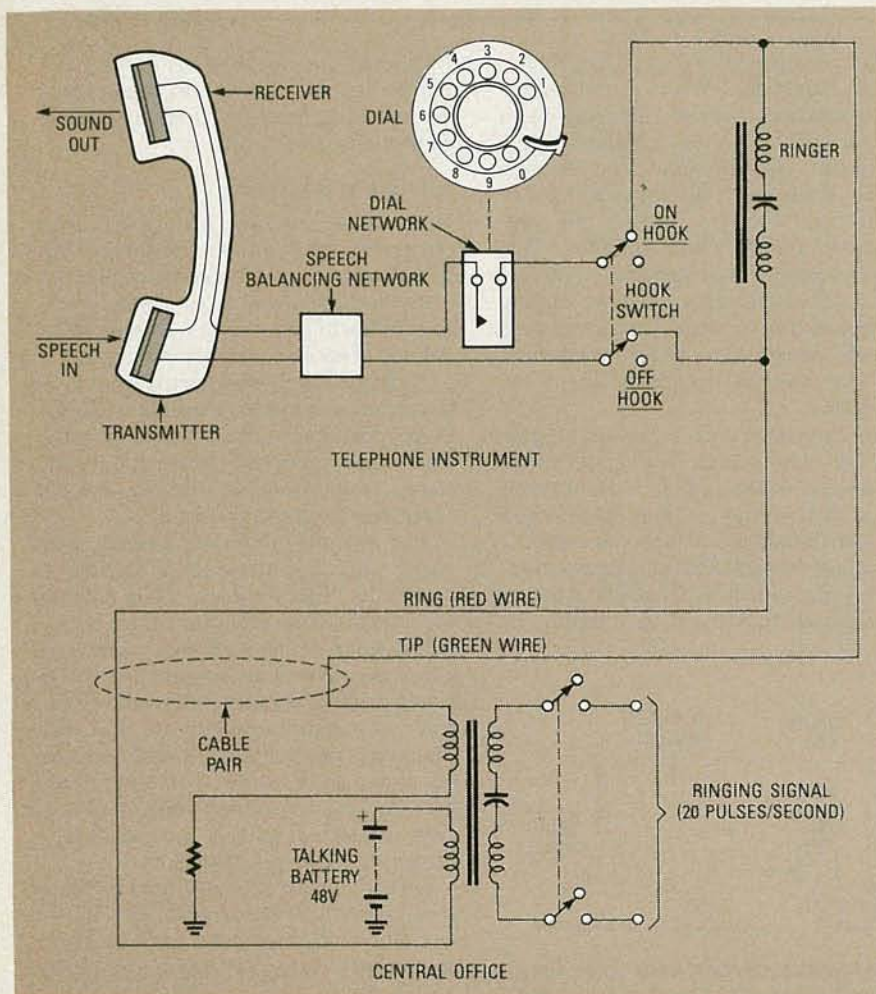


FIG. 5—A TELEPHONE is connected via the local loop to a central office. The central office supplies power for the phone and handles switching functions.

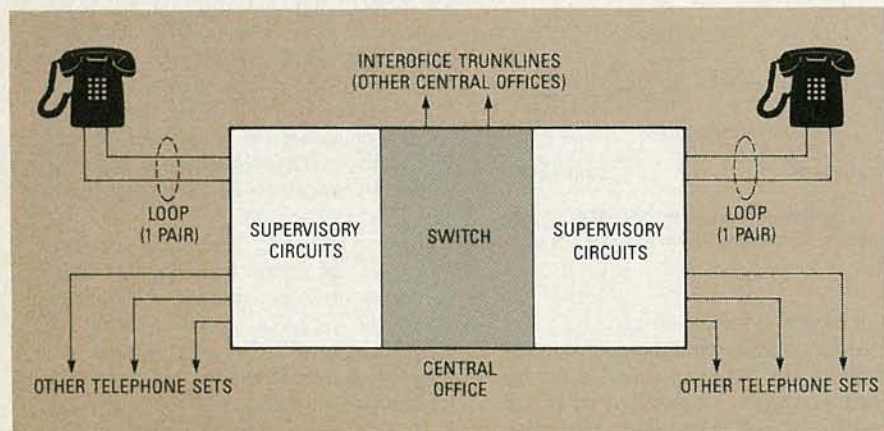


FIG. 6—CENTRAL OFFICE block diagram. Such an office is responsible for thousands of telephone subscribers.

Calls to points outside of your exchange area require use of the long-distance or *long-haul* network. In that network, exchange-area networks are interconnected. Figure 8 shows a portion of the long-haul network. That portion covers the busy West Coast of the United States.

Because of the high amount of volume

it must carry, the links in that network have become highly sophisticated. Overhead cable has largely been abandoned in favor of microwave, satellite, and fiber-optic technologies.

Making connections

As we previously stated, a telephone would be of limited use if it could not be

used to communicate with a number of different parties. In the early days, all switching was done manually. That is, a user would signal the operator, perhaps by turning a crank, that he wished to place a call. The operator would come on the line and request the identity of the party that the caller wished to reach. The operator would then complete the call by physically connecting the local loops of calling and desired with a patch cord.

While manual switching adds a pleasant touch to the process of making a telephone call, it is not terribly efficient. That led to the development of the rotary-dial telephone and its associated automatic switching system by Almon B. Strowger in 1892. That type of equipment is still in widespread use, so let's spend a few moments and examine its characteristics.

The signaling mechanism in a rotary-dial phone is spring loaded and designed to produce pulses at a rate of 10-per-second. Therefore, it takes 1 second to output a 0 (10 pulses) and $\frac{1}{10}$ second to output a 1. A governor in the dial mechanism prevents any changes in that rate, no matter how the dial is manipulated. The reason that the constant rate must be maintained is that the line switches at the central office are designed to act only at that rate. Any disparity will result in inaccurate switching.

Since the dialing pulses are all of the same duration, and the spacing between pulses is identical for all digits, some small time interval is required between digits. That interval is called the *interdigit time*.

The *switching time* or pulse duty cycle is also constant. It is specified as 39%; that is, the pulse waveform is high 39% of the time for each digit. That low duty cycle is used to conserve battery power.

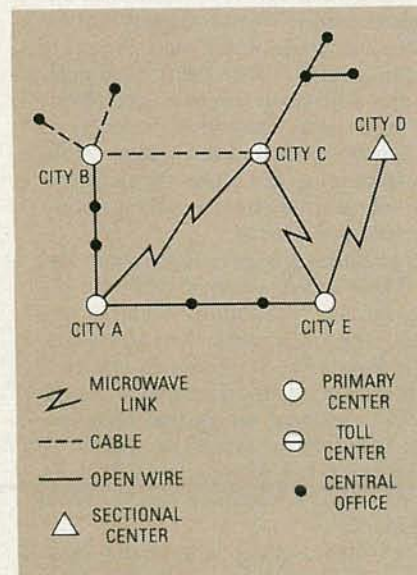


FIG. 7—A SIMPLIFIED EXCHANGE AREA network. Links between the various central offices and centers are handled by buried cable, overhead wire, and occasionally by microwave.

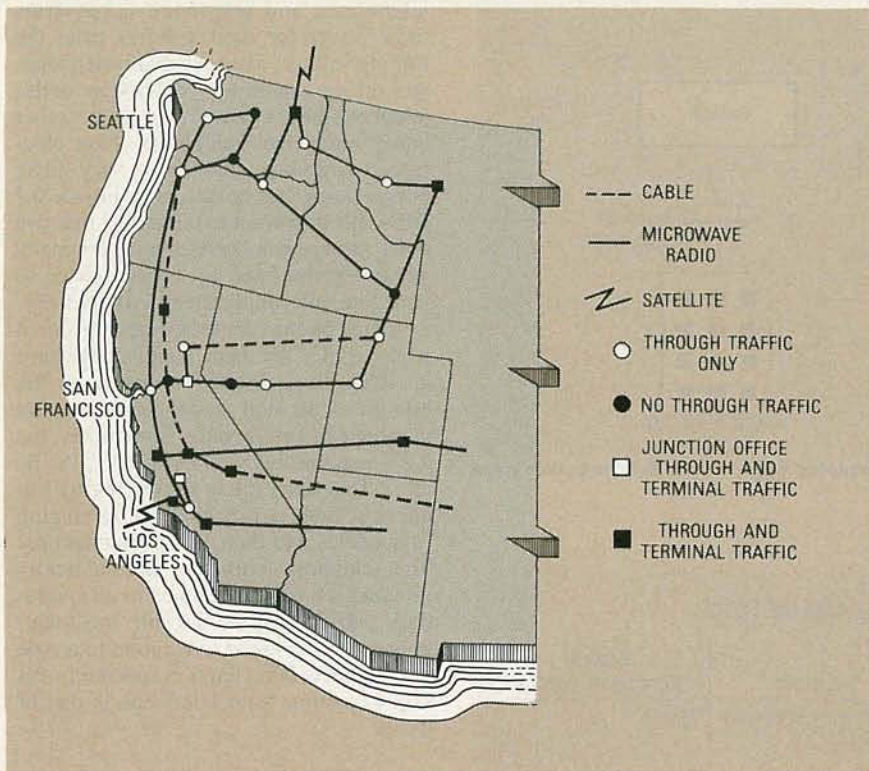


FIG. 8—THE LONG-HAUL NETWORK handles telephone calls to points beyond an exchange area. Here, a simplified diagram of the west-coast portion of that network is shown.

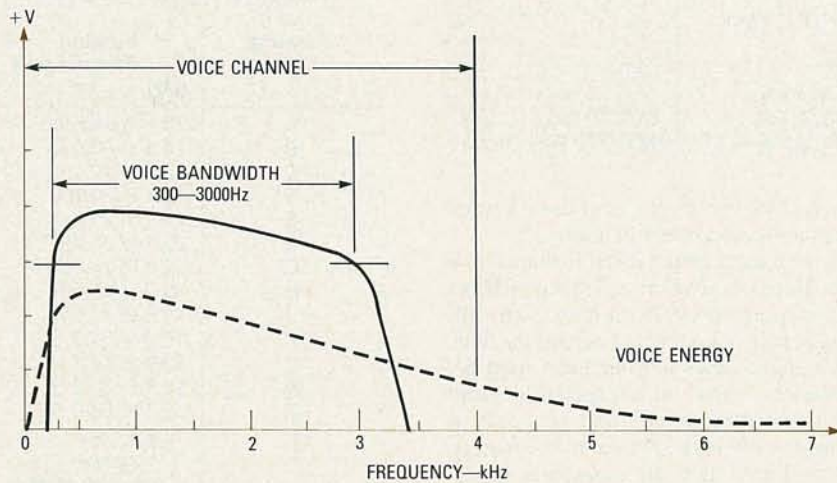


FIG. 9—ELECTRONIC TELEPHONE block diagram. Such a phone uses tone dialing. All circuitry is contained on just a few IC's.

TABLE 1—CALL PROGRESS TONES

Tone Type	Frequency (Hz)	Off Time	
		On Time	
Dial	350 and 440	continuous	
Ringback, normal	440 and 480	2 sec	4 sec
Ringback, PBX	440 and 480	1	3
Busy	480 and 620	0.5	0.5
Congestion (toll)	480 and 620	0.2	0.3
Reorder (local)	480 and 620	0.3	0.2
Receiver off-hook	1400, 2060, 2450, 2600	0.1	0.1
No such number	200 to 400	continuous	
		(Frequency modulated at 1 pulse per second rate.)	

The first tone-dialed telephones appeared in 1964. Those units were extremely sophisticated for their time but still relied on electromechanical bells, a carbon microphone, and a pushbutton pad that consisted of 120 separate components. In modern versions of that device, the circuitry is contained in IC's, the bells have given way to piezoelectric ringers, and the carbon mike has been replaced by a dynamic unit. A block diagram of a tone-dial phone is shown in Fig. 9.

While tone dialing is a relatively recent development, tones have been used for various system-signaling functions for a very long time. Among the tones that should be familiar to you are the dial tone, ringback tones (normal and busy), receiver off-hook tone, and circuits-busy or congestion tone. Most of the signals are actually made up of tone pairs, though some use a single tone while others use multiple tones. A summary of the most common tones, their frequencies, and their duty cycles (on time vs. off time) is provided in Table 1.

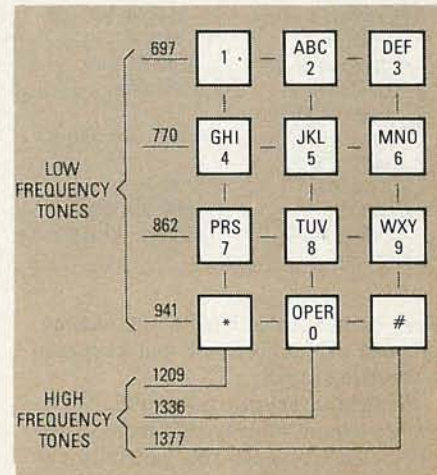


FIG. 10—IN TONE DIALING, each digit is represented by a frequency pair as shown here.

In tone or Dual Tone MultiFrequency (DTMF) dialing, each press of a key generates a duplex tone. (That type of dialing is also called *Touch-Tone*, which is a trade mark of AT&T.) Figure 10 shows the frequencies for each digit. Note that the frequencies can be classified as low or high. There are four frequencies in the low range (697-, 770-, 862-, and 941-Hz) and three frequencies in the high range (1209-, 1336-, and 1377-Hz). Also note that none of the frequencies are harmonically related. That ensures that a signal harmonic will not confuse the telephone company's switching equipment.

The presence of a keypad does not in itself indicate whether a telephone uses tone or pulse dialing. Many keypad-equipped telephones have pulse-dial capability that allows them to be used with any telephone system. Remember that not

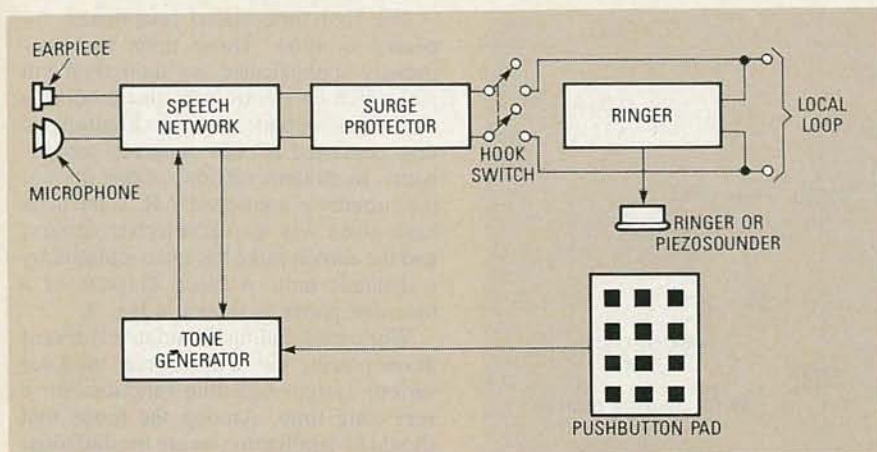


FIG. 11—ALTHOUGH THE HUMAN voice spans a wide frequency range, in the telephone system voice bandwidth is limited to just 300 Hz to 3 kHz.

TABLE 2—OPERATING PARAMETERS

Parameter	Typical U.S. values	Limits	Typical European values
Common battery voltage	-48-volts DC (on-hook)	-47 to -105 volts DC	Same
Common battery voltage	-6-volts DC (off-hook)		
Operating current	20 to 80 mA	20 to 120 mA	Same
Resistance of telephone set	300 ohms	100-400 ohms	
Subscriber loop resistance	0 to 1,300 ohms	0 to 3,600 ohms	
Loop loss	8 dB	17 dB	Same
Distortion	-50 dB total	not applicable	
Ringing signal	20 pps, 90-volts rms	16 to 60 pps 40 to 130 volts rms	15 to 50 pps 40 to 130 volts rms

every exchange can handle tone dialing, although the number with that limitation is shrinking rapidly.

Incidentally, keypad pulse-dialed telephones require some type of memory device. That's because you generally can key in a number faster than the telephone can output its pulses. The pulse-duration requirements that we mentioned earlier hold whether the phone is equipped with a rotary dial or a keypad.

Odds and ends

Figure 11 shows the frequency response of the telephone system. While the human voice can generate sounds over the range of 100 Hz to 6 kHz and beyond, that entire range is not needed for communications. In the telephone system, a voice "channel" of 4 kHz is used. Within that channel, frequencies between 300 Hz and 3 kHz are passed. While the conversations such a system allows are not "Hi-Fi," they are certainly intelligible enough for satisfactory communications.

That voice channel and voice bandwidth are just two of the operating standards adopted many years ago. Others cover such things as handset dimensions, sound-pressure levels, and ringing volt-

age and frequency. Some of those parameters are summarized in Table 2.

One parameter not listed in that table is the *Ringer Equivalence Number (REN)*. When your phone is on-hook, only the ringer bell is connected across the line. No current flows in your local loop because of a capacitor connected in series with the ringer circuit and no power is consumed from the central office battery. As we know, there are thousands of telephones to be rung from each central office, but since we are dealing with battery power, only a finite amount of power is available to ring all of those telephones. As a result, the telephone company only guarantees to supply enough power to each subscriber to sound five standard electromagnetic ringers. That amount of power is referred to as 5 REN.

The importance of that to a subscriber is that it limits the number of devices that can be connected to a line. For instance, if five standard telephones are connected to a line, each must have an REN no greater than one. Otherwise, there's no guarantee that any of the ringers will sound for an incoming call.

These days, the REN has taken on greater importance because a number of

telephones and telephone accessories draw power for their features from the ringing voltage. Those include telephone-answering machines, extension bells, telephone-hold circuits, etc. On the other hand, many new telephones have electronic sounders that draw very little power. Some may be rated at as little as 0.1 REN. It's important to remember that you must notify your local phone company whenever you hook up a new device to your line and supply them with its REN.

All telephones that have been registered with the FCC by their manufacturer have an REN. It is usually stamped on the bottom of the unit along with the serial number and similar data. Sometimes, the REN may be followed by a letter (A, B, etc.). That letter refers to the ringing frequency. Table 3 lists the various ringing frequencies and their letter designations. The telephone company automatically provides a type A frequency to all single-party subscribers. As a result, most telephones are designed to respond to a type A frequency. If no letter is specified, it is safe to assume your telephone is one of those.


TABLE 3—RINGING FREQUENCIES

Ringing Type	Ringing Frequencies (Hz)
A	20 ± 3 and 30 ± 3
B	15.3 to 68.0
C	15.3 to 17.4
D	19.3 to 20.7*
E	24.3 to 25.7
F	29.3 to 30.7*
G	32.6 to 34.0
H	39.2 to 40.9
J	41.0 to 43.0
K	49.0 to 51.0
L	52.9 to 55.1
M	53.8 to 61.2
N	65.4 to 68.0
P	15.3 to 34.0

*Frequency-selective ringing (party line use)

Next time

In the past, customers were prohibited from tampering with their telephone equipment in any way. If you wanted a telephone installed or moved, telephone company personnel did the job, for a fee. That all has changed since the break-up of AT&T. Now, you pretty much can do what you want—as long as you know what you are doing! A service call to correct an error, or for any work for that matter, can be extremely expensive. Next time, we will provide you with a crash course in telephone installation that can help you save time, money, and aggravation. **R-E**

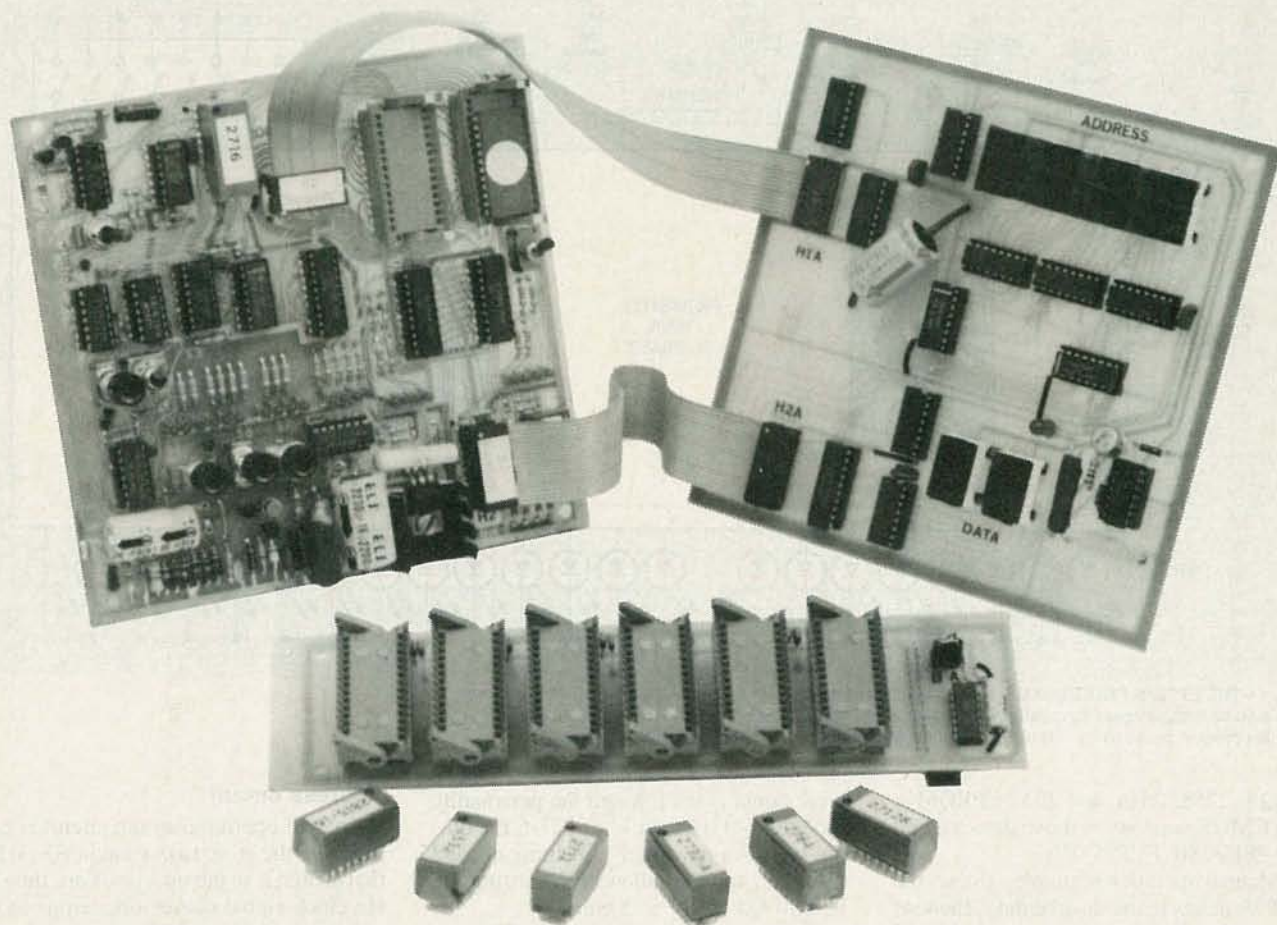

EPROM PROGRAMMER

Our low-cost EPROM programmer can burn all the popular types, including EEPROM's!

LUBOMIR B. SAWKIW

THE MICROPROCESSOR IS TURNING UP in some very unlikely places these days. You might find one in a TV remote control, an automotive ignition and timing circuit, a video game, or even a microwave oven. But a microprocessor can't do the work all by itself: It requires permanent memory that stores the data and instructions that allows it to do its job. And that's where the EPROM comes in. It can provide a low-cost way of developing, testing, and even distributing data and programs for many types of computer systems.

EPROM's aren't used solely with computers, of course. Often a complex logic problem that would require numerous individual gates can be solved with a small EPROM.

So, sooner or later, whatever your involvement with digital electronics, you'll find it necessary to burn (program) an

EPROM. And we've got an inexpensive way of doing so. Our EPROM programmer can be built for about \$60 (less PC board) in its basic form, and it can burn all of the popular five-volt EPROM's in both 24- and 28-pin packages, as well as several popular types of EEPROM's. The unit allows you to burn single locations one by one, burn one value into a number of consecutive locations, or copy one entire EPROM to another. An optional multi-EPROM board allows you to program up to six EPROM's simultaneously.

Features

The programmer is a stand-alone unit; no computer or ASCII display terminal is required to operate it. But it has input/output lines (labeled A-G in Fig. 1) that you can use to automate control of all functions.

In the basic programmer, data input is provided by an eight-position DIP switch (S8), and addresses are selected by means of FAST (S5) and STEP (S6) switches. Address and data lines are displayed in binary by 22 discrete LED's (LED1-LED22). An optional display board allows you to view the address and data lines in hexadecimal.

The programmer has a verification feature that allows you to view the contents of each EPROM location after that location has been programmed.

Personality modules are used to accommodate a variety of EPROM's. The personality module matches the operating requirements and pin assignments of each EPROM to the address, data, programming and timing signals developed on the programmer board. By using the appropriate personality module, you can program the 2716, 2732, 2732A, 2764,

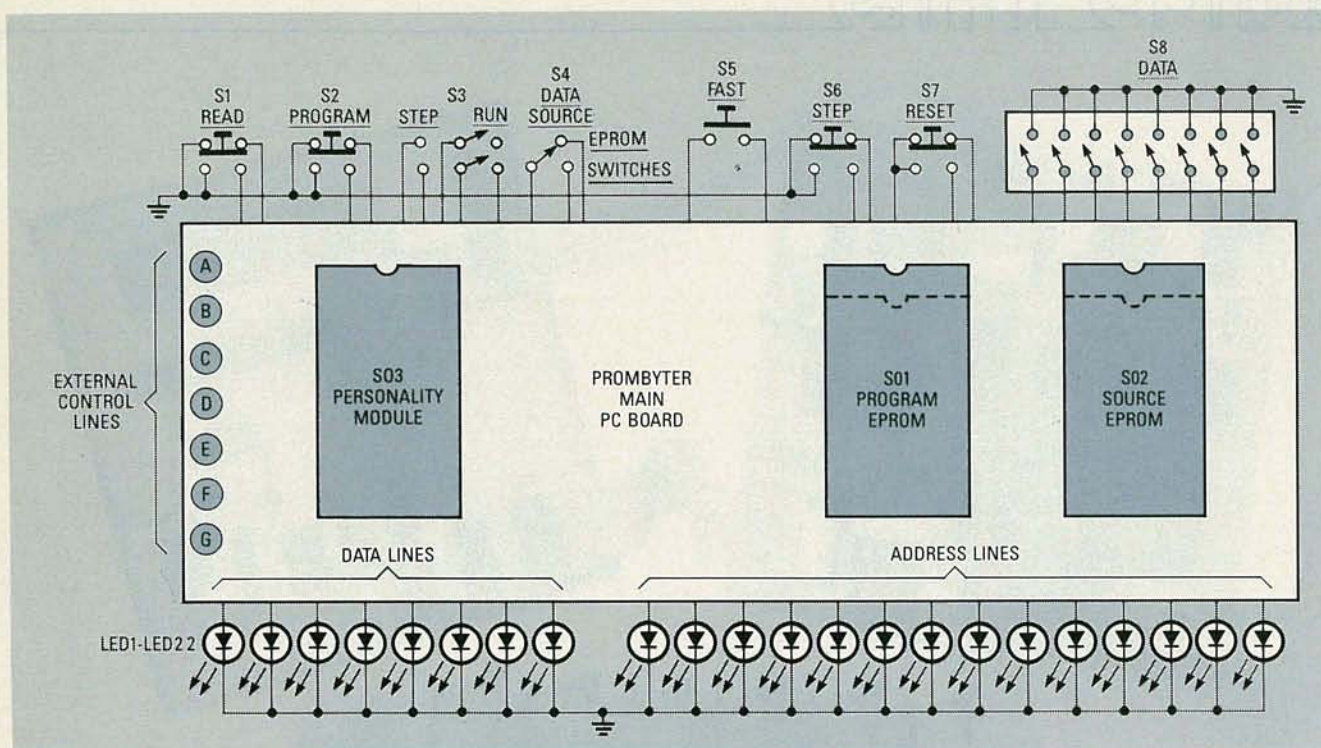


FIG. 1—THE EPROM PROGRAMMER can copy an entire EPROM or single locations; single locations can also be programmed manually. Separate sockets are provided for source and program EPROM's, and for plug-in personality modules that feed each type of EPROM the proper signals.

27128, 2758, 2516, and 2532 EPROM's; the CMOS versions of those devices; and the 2815/2816 EEPROM's.

Manual operation is simple. You set the DIP switches to the desired data, then set the FAST and STEP switches to the desired address, and last press the PROGRAM switch (S2). When that location has been programmed, the programmer automatically moves to the next location.

Circuit description

Except for the AC transformer, the entire power supply is contained on the main PC board. As you can see in Fig. 2, the regulated five-volt supply is derived from an eight-volt AC input. That AC is rectified by bridge BR1, filtered by capacitor C7, and then regulated by IC14, a 7805 regulator. Output capacitor C6 and bypass capacitors C10 through C17 further filter the +5-volt line. Optional resistor R57 provides extra power for the optional display board.

The 25-volt AC input is rectified and filtered for two purposes: to provide the +35-volt programming voltage (V_{PP}), and to provide the 120-Hz clock signal that is the core of the circuit's timing chain. Diodes D4 and D9 isolate the clock circuit from the V_{PP} output. Zener diode D10 clips the positive half-cycles of the unfiltered output at about 9 volts. Then IC7-b and IC7-c square up those pulses.

The programming voltage, V_{PP} , is what "burns" each bit into an erased EPROM. Digital control of V_{PP} is provided by IC7-f and IC7-a. When a high

level signal is fed through the personality module (SO3) to pin 13 of IC7-f, the output of IC7-a goes high, Q1 turns on, Q2 turns off, and that allows D2 to bring the base of Q3 up to +25 volts.

At that point Q4 turns on and allows approximately +25 volts to appear at its emitter. That voltage is fed back to pin 8 of SO3. Capacitors C2 and C3 prevent a transient overshoot of the +25-volt line during switching. An overshoot of more than one volt could ruin the EPROM you are programming. Components in some personality modules reduce the +25- to +21-volts, for EPROM's that need +21 volts.

Transistor Q5 is used to prevent V_{PP} pulses from damaging an EPROM when power is removed from or applied to the circuit. As stated previously, Q2 normally conducts and shorts out Zener diode D2. However, Q2 is biased from the +5-volt supply line. If for any reason during power up the +35-volt line receives power an instant before the +5-volt line, Q3's base would shoot up to about +26-volts, and a +25-volt program pulse would appear on the V_{PP} line.

To prevent that surge, Q5's emitter is connected to the +5-volt supply, and its base is biased at +4.7 volts from the voltage at Q3's base by means of Zener diode D3. So, if the base of Q3 were trying to go up to +26-volts, and the +5-volt supply were not quite up yet, Q5 would be forward biased, so it would conduct through R52, and thereby reduce the voltage at the base of Q3.

Address circuit

Overall operation of the circuit is governed by the FUNCTION switch, S3. When that switch is in the RUN position, the 120-Hz clock signal causes operations to occur sequentially every 1/20th of a second. When S3 is in the STEP position, addresses must be set manually, and PROGRAM switch S2 must be pressed for each location that is to be programmed by the EPROM programmer.

Addresses are selected by pressing switches S5 and S6. When switch S6 is pressed, it is debounced by IC5-a, which delivers one pulse through IC6-b and IC6-d to IC8, a 4040 12-stage binary counter. That pulse increments the address held in IC8 by one. On the other hand, when switch S5 is pressed, it connects the 120-Hz clock signal to IC6-b and IC6-d, and then to IC8, which then increments at a rate of 120 Hz.

Since larger EPROM's have as many as 14 address lines, and the 4040 has only 12 outputs, IC3-b is also used as an address counter. When pin 1 of IC8 goes low, IC3-b increments. Its A, B, and C outputs provide the A12, A13, and A14 address lines. Two IC's buffer the current address for display on LED1-LED14: IC9 and IC10.

Reset

Switch S7 forces the system to reset. When that switch is pressed, a reset pulse is fed to all counters and flip-flops. Also, a reset pulse occurs at power up by means of C1's charging up through R8.

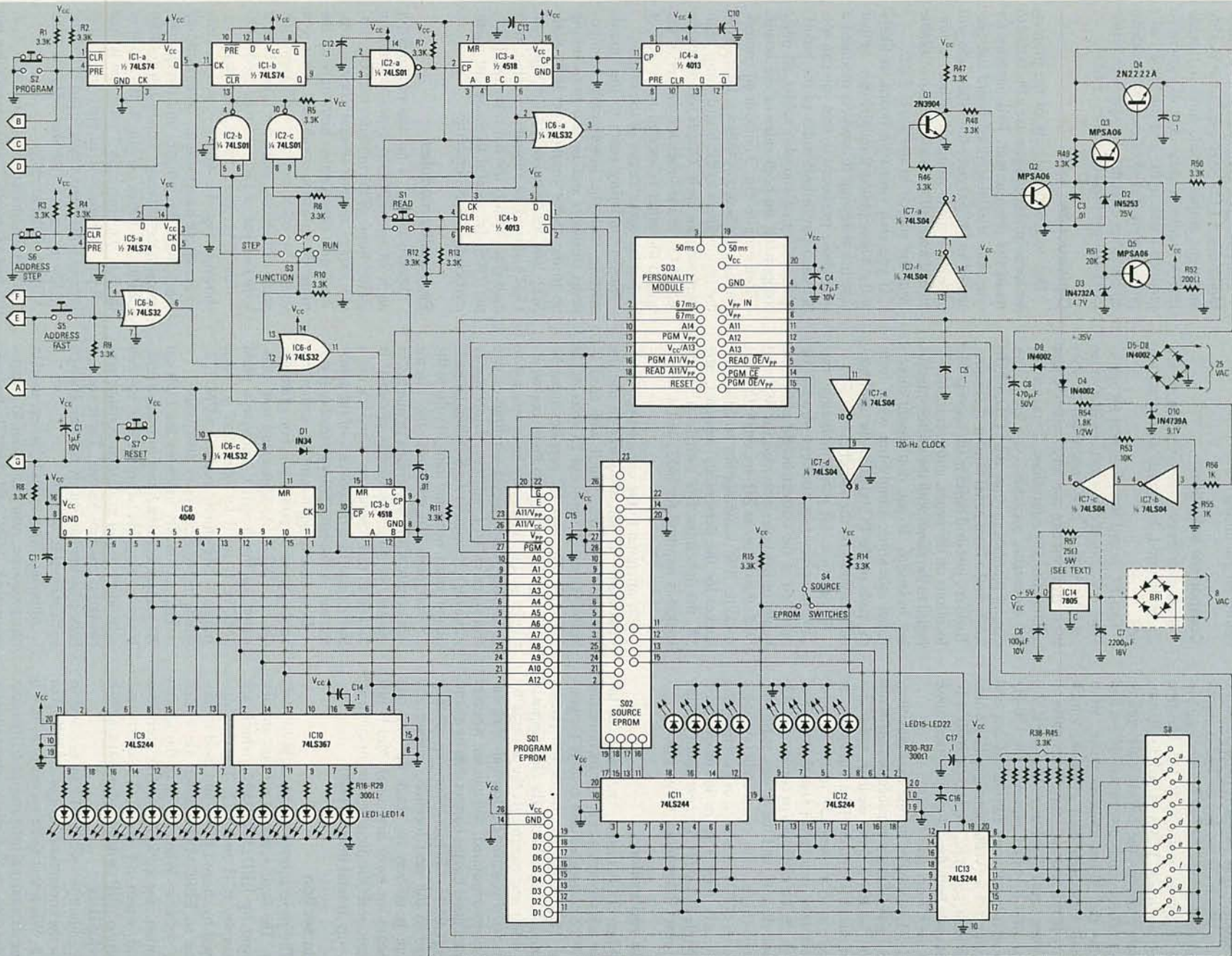


FIG. 2—THE EPROM PROGRAMMER IS DRIVEN BY A 120-Hz clock circuit that is generated by IC7-c and IC7-d; LED's indicate addresses and data in binary.

Programming circuitry

Assume that S3 is in the STEP position. Then, when S2 is pressed, a program cycle begins. That switch is debounced by IC1-a, which clocks IC1-b. The Q output of IC1-b allows the 120-Hz clock (at pin 2 of IC2-a) to be fed to IC3-a. The first count to reach IC3-a is fed to IC4-b, which provides the 67-ms data gating pulse. The second pulse presets IC4-a and begins the 50-ms program pulse. Both signals stay high until count 8, which clears IC4-a and ends the 50-ms pulse.

When count 9 arrives NAND gate IC2-c clears IC1-b, which prevents the 120-Hz signal from passing through IC2-a and counter IC3-a. At that time \bar{Q} of IC1-b also goes high, resets IC3-a, and clears IC4-b. That ends both the 50-ms program-pulse and the 67-ms gating pulse.

If S3 is toggled to the RUN position, NAND gate IC2-c never receives the ninth count, so IC1-b is not cleared, and IC3-a continues to count until the tenth pulse, at which time it internally resets to zero. Since there is no reset signal from \bar{Q} of IC1-b, IC3-a continues to count, so IC4-b is not cleared, and the 67-ms pulse line remains high. Also, count eight (available at pin 6 of IC3-a) is used to increment the address counter (IC8) in this mode. If S3 is toggled to STEP, the next count of nine will reset the programming cycle.

Data verification

When S3 is in the STEP position, the 4040 address counter is not incremented until S2 is released and Q of IC1-a goes low. That low-going transition passes through S3 and IC6-d to the clock input of the 4040 and increments the address by one. So, if you hold S2 down after a location is programmed, you can see whether that location has the correct data by examining LED15-LED22. When you're ready to go to the next location, release S2. There is no way to "back up" by one location (or more than one). You'll just have to reset the prom burner, or cycle all the way around through 0000.

Data section

The programmer has an eight-bit data bus. The logic levels of all bits are displayed by LED15-LED22, which are driven by IC11 and IC12. The data displayed by those LED's (and used to program an EPROM) is chosen via switch S4, SOURCE. When S4 is in the EPROM position, the EPROM in SO2 provides data; when S4 is in the SWITCHES position, DIP switches S8-a through S8-h provide data.

Pushbutton switch S1 can be used to view the contents of the source EPROM in SO2. When that switch is pressed, IC4-b is preset, and that activates the 67-ms data gating line, which places the program EPROM in a standby mode. In addition, that signal places the source EPROM in a

read mode, and connects its data input pins to the data bus. That allows you to view the contents of the source EPROM before programming.

Component selection

With that basic understanding of the circuit in mind, let's build a programmer now.

Our PC board was designed for miniature, PC-mountable switches like those sold by Alco, C & K, and other companies. But you can use any switches that are functionally equivalent. If you use the PC-mountable switches, you can, with careful planning, secure the PC board directly to the front panel of your enclosure. To do so, just drill holes in the appropriate locations on the panel, and secure the PC board to the panel with the switch-mounting hardware. If you don't want direct-panel mounting, simply run wires from the pads on the PC board to the appropriate terminals on the switches.

In addition, for panel mounting, two 28-pin wirewrap sockets should be mounted at the correct height above the board in the holes provided for SO1 and SO2; then plug the ZIF sockets into those sockets. The same applies to SO3, the socket for the personality modules, and S8, the data input DIP switch. A 20-pin socket is required for SO3, and a 16-pin socket for S8.

Pay attention to the circuit's power requirements. If you are going to use the two option boards, you'll will need 8-volts AC at 1.2 amps and 25-volts AC at 280 mA. The two AC supplies must be separate; they cannot be taps on one winding or in any other way be connected to each other. Two separate windings on one transformer will suffice. Don't apply more than 10 volts to the 8-volt input pads on the board, nor more than 30 volts to the 25-volt pads. In addition, the circuit works only with a power-line frequency of 60 Hz, because the timing circuitry is locked to that frequency. Also, it's not a bad idea to fuse the primary of the transformer. A ¼-amp, 250-volt fuse will do.

Don't use bargain transistors; they can be destroyed at power up. For example, Q4 is a 2N2222A. Make sure your transistor has the A suffix, because a plain 2N2222 is rated for operation at lower voltages. Nor should you use a PN2222, which has limited power dissipation.

The personality modules are built on 20-pin headers which may be hard to find. If you have trouble locating them, you can substitute 20-pin machined-contact, solder-tail IC sockets instead. Those sockets have pins that are sturdy but thin enough to fit into an IC socket.

Although 74LS series IC's were used in our prototype, you may want to experiment with 74HC and 74HCT devices. They are CMOS versions of the 74LS series, and they feature speed and drive

capacity comparable to those of the 74LS series, but with the advantage of CMOS's low power consumption.

Last, use good quality LED's. We have found that LED's vary greatly in quality and light output. Some hobbyist-grade LED's require a great deal of current to produce much light, and the 7805 can't provide a great deal of current and drive all the other circuitry. So stay with prime LED's or get high-brightness LED's.

Construction

Due to the complexity of the project, we recommend that you use a PC board to build the programmer. Foil patterns for one side of double-sided board are presented in PC Service; the other side will appear in next month's issue. A pre-etched and drilled board is also available from the source in the Parts List.

If you etch your own board, it likely will not have plated-through holes. In that case use wirewrap IC sockets mounted a little above the board so that you can solder each pin to both sides of the board. Make sure that you also solder all other components on both sides of the board.

Referring to Fig. 3, mount all components on the board as follows. First solder the two jumpers to the board using insulated wire for each. One is located to the left of Q3 in the lower left corner of the board; the other is located to the left of IC8 in the upper center of the board.

Begin soldering parts to the board, starting with the lower-profile components (resistors and diodes) and working up to the larger components (C8, SO1, SO2, and all switches). All the discrete LED's should be mounted so that their cathodes (usually the flat side) face IC14, the 7805. Be careful to mount all polarized components correctly.

Personality modules

Shown in Fig. 4 are the modules for each of the EPROM types mentioned above. Some of the modules are very simple; others require several components. We'll give construction hints only for the more complicated modules. After you verify that each module works correctly, pot it with epoxy, mark pin 1, and label it with the type of EPROM it is used with.

The 2532, 2732, and 2372A modules, shown in Fig. 4-c-Fig. 4-e, are the only ones that are hard to build. When building them, wire the jumpers and the discrete components first, and then install the 4001 CMOS IC. Break off pins 4, 10, and 11 of the IC. Then bend pin 3 under the IC and solder an insulated jumper to it; that jumper will connect later to pin 15 (for the 2532) or pin 14 (for the 2732 and the 2372A) of the module.

Short the unused input pins (5, 6, 8, 9, 12, and 13) to pin 7, and connect that pin to pin 4 (ground) of the module. Finally, bend IC pins 1, 2, and 14 so that they can

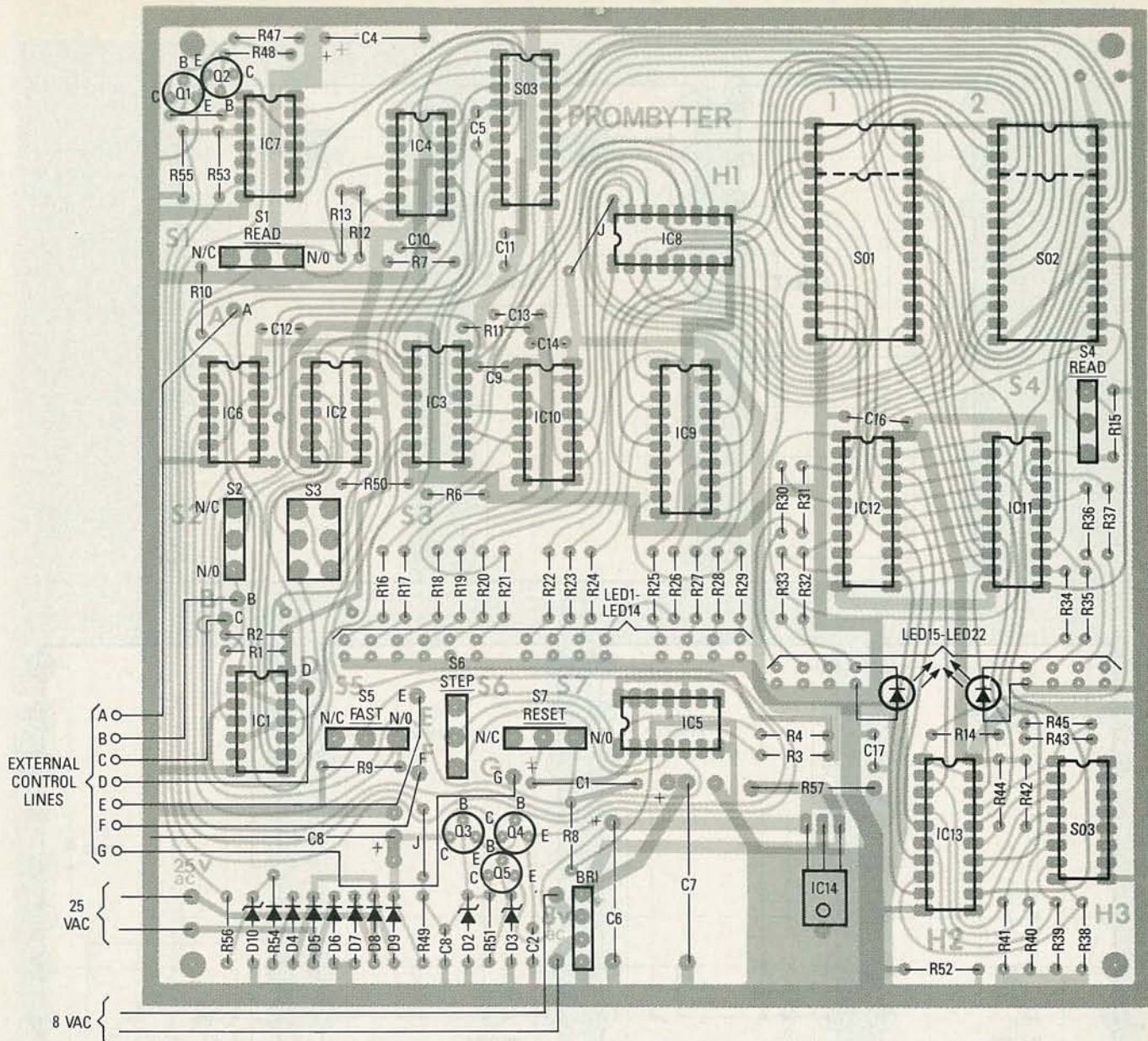


FIG. 3—THE EPROM PROGRAMMER'S PC BOARD is double-sided; all components mount as shown here. Since a home-made board's holes are not plated through, the IC sockets must be mounted slightly above the board so that the socket pins can be soldered to the top side of the board.

PARTS LIST

All resistors are 1/4-watt, 5% unless otherwise noted.

- R1-R15, R38-R50—3300 ohms
- R16-R37—300 ohms
- R51—20,000 ohms
- R52—200 ohms
- R53—10,000 ohms
- R54—1800 ohms, 1/2 watt
- R55, R56—1000 ohms
- R57—25 ohms, 5 watts (see text)

Capacitors

- C1—1 μ F, 10 volts, electrolytic
- C2, C5, C10-C17—0.1 μ F, disk
- C3, C9—0.01 μ F, disk
- C4—4.7 μ F, 10 volts, electrolytic
- C6—100 μ F, 10 volts, electrolytic
- C7—2200 μ F, 16 volts, electrolytic
- C8—470 μ F, 50 volts, electrolytic

Semiconductors

- IC1, IC5—74LS74 dual flip-flop
- IC2—74LS01 quad 2-input NAND gate

- IC3—4518 CMOS dual BCD counter
- IC4—4013 CMOS dual flip-flop
- IC6—74LS32 quad 2-input OR gate
- IC7—74LS04 hex inverter
- IC8—4040 12-stage binary counter
- IC9, IC11-IC13—74LS244 octal 3-state buffer
- IC10—74LS367 hex 3-state buffer
- IC15—7805 5-volt regulator
- BR1—1-amp 50-PIV bridge rectifier
- D1—1N34A germanium signal diode
- D2—1N5253 25 volts, 1 watt, Zener diode
- D3—1N4732A 4.7 volts, 1 watt, Zener diode
- D4-D9—1N4002 rectifier
- D10—1N4739A 9.1 volts, 1 watt, Zener diode
- LED1-LED22—miniature, high-brightness LED

Other components

- Q1—2N3904 NPN transistor
- Q2, Q3, Q5—MPSA06 NPN transistor
- Q4—2N2222A NPN transistor
- S1—SPDT, toggle, momentary
- S2, S6—SPDT, pushbutton, momentary
- S3—DPDT, toggle
- S4—SPDT, toggle
- S5, S7—SPST, pushbutton, momentary
- S8—8-position DIP switch

Miscellaneous: Dual-secondary transformer: 8-volts at 1.2 amps, and 25-volts at 280 mA; heatsink for IC14; two 28-pin ZIF sockets; IC sockets, wire solder, case, etc.

Note: The following are available from Lubomir Sawkiw, P.O. Box 555, Rensselaer, NY 12144: A transformer with 25 and 10 volt AC secondaries, \$8.00 plus \$3.00 shipping and handling; 9368 Fairchild IC's, \$4.25 each postpaid. New York residents must add 7% sales tax.

The following are available from E²VSI, P.O. Box 72100, Roselle, IL 60172: main circuit board, \$25.00; hex display board: \$15.00; gang board, \$10.00; set of three boards, \$45.00.

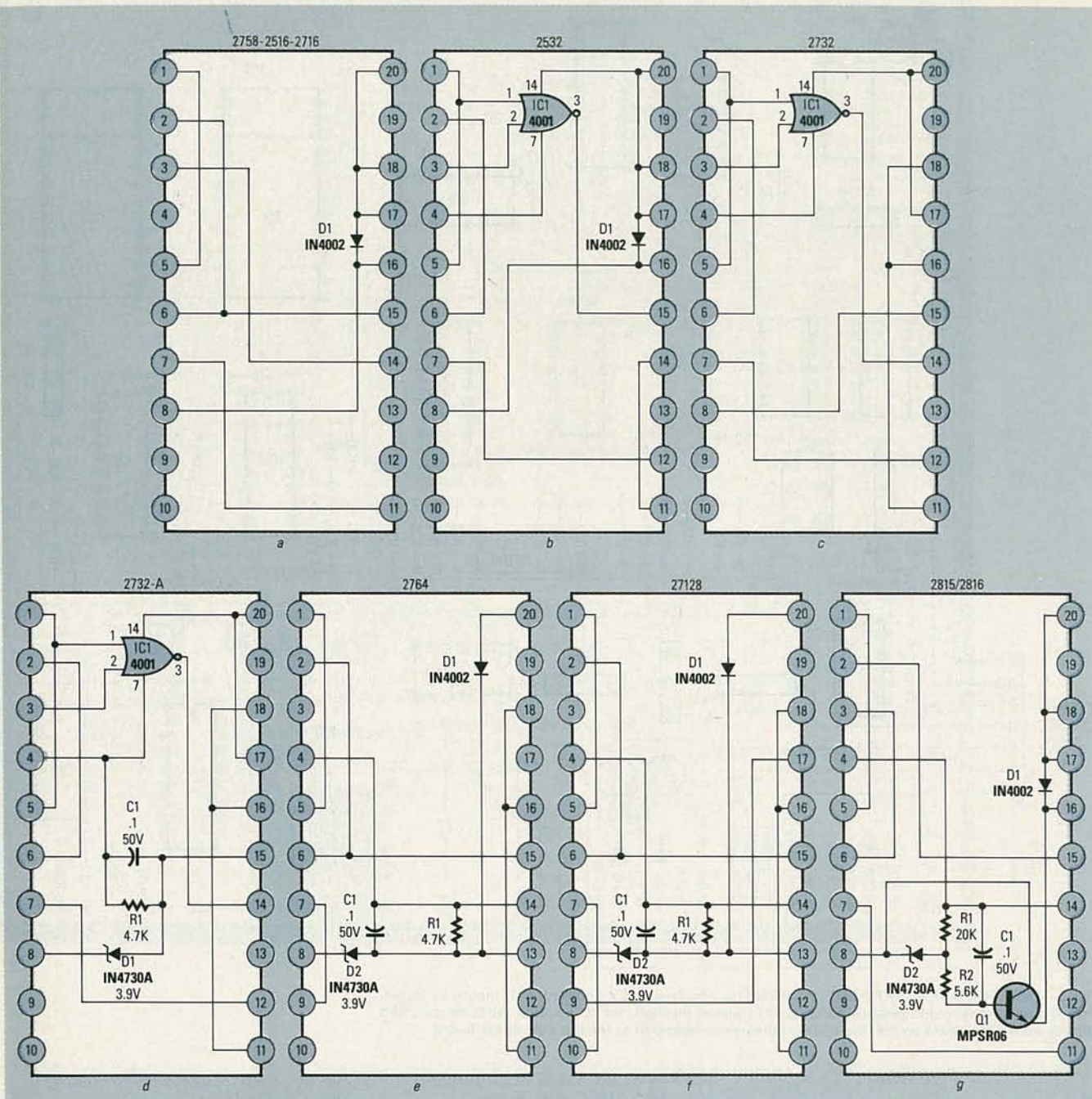


FIG. 4—EACH PERSONALITY MODULE is built on a 20-pin header; see the text for information on building the 2532, 2732, and 2732A modules.

attach directly to module pins 1, 3, and 20, respectively. When soldered in place correctly, the IC should sit firmly above the carrier wiring and components.

Initial check-out


Install all IC's and a personality module in the proper sockets, but don't install an EPROM yet. Measure the +5-volt DC output of the regulator IC as you power the board. To measure that (or any other) voltage on the board, do not clip the negative lead of your meter to the edge of the board; you would short out the power supply. Rather, connect your negative test lead to the negative side of C6, C7, or C8.

After checking the +5-volt supply, measure V_{PP} across C8. The voltage there shouldn't exceed 40 volts. You need only about 27 volts to do the job; a higher voltage could destroy one of the transistors.

Now remove power and install an erased EPROM into SO1. Whether you use a 24-pin device (such as a 2716) or a 28-pin device (such as a 2764), the EPROM should be "bottom justified." In other words, pin 12 of a 24-pin device, or pin 14 of a 28-pin device should be plugged into pin 14 of the socket. After the EPROM is oriented properly, move the socket's locking lever to the closed position.

With power still off, insert the eight-position DIP switch in its socket. Mount it so that switch 1 is closest to the EPROM sockets. That places data bit 0, on switch one and data bit 7 on switch 8. A closed DIP switch puts a low (logic 0) on that line. An open switch puts a high (logic 1) on that line. At this point you should have an erased EPROM, the corresponding personality module, and the DIP switch inserted in the correct sockets. Place S3 in the STEP position, apply power, and press RESET (S7).

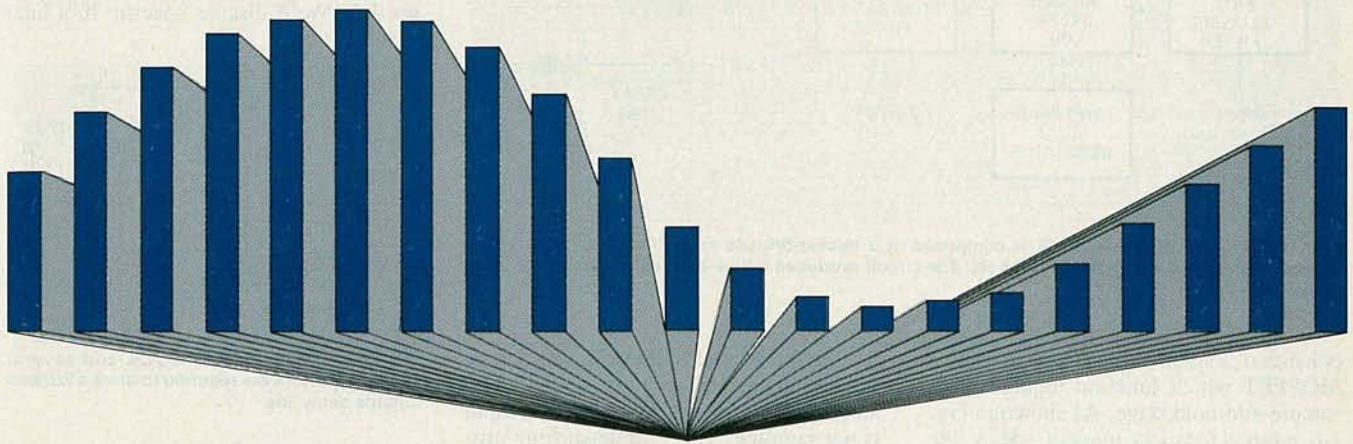Next time we'll present more testing details, as well as plans for the optional display and gang-programming boards.



Analog Delay Lines

You can use analog delay lines to produce special audio effects such as echo, reverb, room expansion, and many others. Find out how here.

RAY MARSTON

SOLID-STATE DELAY LINES ARE WIDELY used in modern music and audio systems. They can be used to produce effects such as echo, reverb, chorus, phasing, and flanging (sweepable filtering) for performing artists. In addition, delay lines can produce ambience synthesis and room expansion for home hi-fi systems. Further, a delay line can be used as the heart of a click/scratch filter for a record player, and as a sound-activated switch.

There are two basic types of solid-state delay systems: analog and digital. Digital delay systems tend to be more expensive and more complex than analog types, except when delay times exceed 250 ms, so we'll confine this discussion to analog systems only. But before we get into the hardware, let's talk about psycho-acoustics. In that way we'll learn why the effects produced by delay lines work.

Psycho-acoustics

Many of the special effects obtainable with delay lines depend heavily on how the human brain interprets sounds. The brain does not always perceive sounds as they truly are, but it interprets those sounds so that they conform to a preconceived pattern. Therefore, sometimes the brain can be tricked into misinterpreting those sounds. Scientists have discovered several psycho-acoustic laws that explain how the brain interprets various sounds.

1. If the ears perceive two sounds that are identical in form (wavelength and amplitude) and time-displaced by less than 10 ms, the brain integrates them and perceives them as a single sound.

2. If the ears perceive two sounds that are identical in form but time-displaced by 10–50 ms, the brain perceives them as two independent sounds, but integrates their information content into a single easily recognizable pattern, with no loss of information fidelity.

3. If the ears perceive two sounds that are identical in form but time-displaced by more than 50 ms, the brain perceives them as two independent sounds, but may be unable to integrate them into a recognizable pattern.

4. If the ears perceive two sounds that are identical in shape but not in magnitude, and which are time-displaced by more than 10 ms, the brain interprets them as two sound sources (primary and secondary), and draws conclusions concerning both the location of the primary sound source and the distance between the two sources.

Regarding location identification, the brain identifies the first perceived signal as the primary sound source, even if its magnitude is substantially lower than that of the second perceived signal. That is known as the Hass effect. So a delay line can be used to trick the brain into wrongly identifying the location of a sound source.

Regarding distance identification, the brain correlates distance and time-delay at roughly 0.3 meters (about 13 inches) per millisecond of delay. So a delay line can be used to trick the brain about how far apart two sound sources are.

5. The brain uses echo and reverberation (repeating echoes of diminishing amplitude) information to construct an

image of environmental conditions. For example, if a sound reverberates for a total of two seconds, and an echo occurs every 50 ms, the brain may interpret its environment as being a 50-foot cave or a similar hard-faced structure. But if the reverberation time is only 150 ms, the brain may interpret the environment as being a softly-furnished 50-foot room. Those sorts of facts can be used to trick the brain into drawing false conclusions concerning its environment; in fact, it is those tricks that are used in ambience synthesizers and room expanders.

6. The brain is highly sensitive to sudden increases in sound intensity, such as clicks and scratches on record albums, but it is insensitive to sudden decreases in intensity. We're speaking now of transients that last only a few milliseconds. Those facts are what make click/scratch filters possible. We'll discuss how to do that later, but first let's discuss some of the basics of how delay lines work.

Delay-line basics

Modern analog delay lines come in integrated-circuit form and are commonly known as CTD (Charge Transfer Device) or bucket-brigade delay lines. Those devices contain a number of analog memory cells (buckets). Each cell is actually a sample-and-hold circuit and, usually, 512, 1024, or 4096 cells are wired in series. Analog input signals are applied at the first cell and the delayed output is taken from the last cell.

Figure 1-a illustrates the basic components of an analog delay line. Each bucket

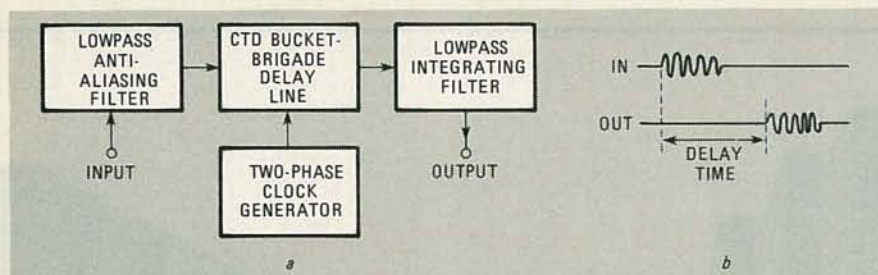


FIG. 1—AN ANALOG DELAY LINE is composed of a bucket-brigade delay line, input and output lowpass filters, and a two-phase clock (a). The circuit produces a time-delayed replica of the input signal (b).

consists of a small-valued capacitor and a MOSFET which function together as a sample-and-hold stage. As shown in Fig. 1-b, a signal fed to the input of a delay line will appear at the output at a later time; as we'll see below, that time depends on both the clock frequency and the number of buckets.

The input signal is applied to the delay line via a lowpass filter that has a cutoff frequency one third (or less) of the clock frequency. The lowpass filter is used to overcome aliasing (intermodulation) problems. The output of the delay line is passed through a second lowpass filter, which also has a cutoff frequency one third (or less) of that of the clock. That filter also rejects clock-breakthrough signals and integrates the output of the delay line into a faithful (but time-delayed) replica of the original input signal.

As shown in Fig. 2, an electronic switch is placed at the input of the delay line; that switch is externally biased to a pre-set voltage. Charges can then be shifted from cell to cell, one cell at a time, at a rate determined by an external two-phase clock. One phase of the clock controls shifting, and the other phase drives the input-sampling switch. The operating sequence is as follows.

On the first half of the clock cycle, the contents of each bucket are shifted to the next bucket in line and a sample of the input signal is fed to the first bucket via

S1. On the second half-cycle, all charges (including the most recently sampled one) are shifted to the next bucket, but the input is not sampled. That double-shifting process repeats on each clock cycle, and input samples are repeatedly taken and then shifted.

Near the end of the delay line two sections of buckets are wired in parallel. Those sections differ in that one section has an extra bucket. There is also a phase difference between the clock signals applied to the parallel sections. So the circuit has two outputs which, when added together, effectively fill in the "gaps" in the main delay line. The outputs can be summed either by shorting them together or, preferably, by connecting them to a BALANCE potentiometer, as shown in Fig. 2. The final output of the delay line is thus a time-delayed replica of the original input signal.

Figure 3 shows the essential components of an analog delay circuit. The delay-line MOSFET's have a tetrode structure, so the IC needs two supply voltages (V_{DD} and V_B), plus a ground connection. The input terminal must be biased into the linear mode by resistors R1 and R2. The two outputs of the device are added together, as discussed earlier. Last, the IC must be provided with a two-phase clock signal; usually that signal is a pair of out-of-phase squarewaves that switch fully between V_{DD} and ground. Some

analog delay lines have clock dividers so that only a single-phase clock input is needed. We'll discuss specific IC's later in this article.

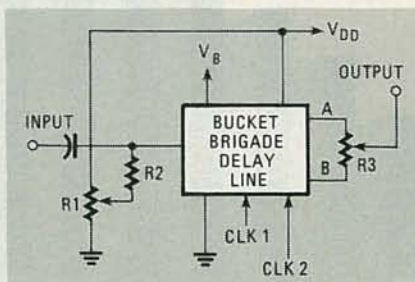


FIG. 3—A TWO-PHASE CLOCK and several biasing resistors are required to drive a bucket-brigade delay line.

How much delay?

The cells of an analog delay line are alternately empty and charged. Each complete clock cycle shifts a charge two stages along the delay line. Therefore the maximum number of samples that a line can take is equal to half the number of stages. For example, a 1024-stage line can take only 512 samples. The actual time delay available from a line is given by $t = ST/2$, where t is the time in seconds, S is the number of stages, and T is the period of the clock. In terms of clock frequency, that equation is $t = S/2f$.

For example, a 1024-stage delay line using a 10-kHz (100 μ s) clock gives a delay of $1024 / (2 \cdot 10,000) = 51.2$ ms. A 4096-stage line gives a 204.8-ms delay at the same clock frequency.

It's worth pointing out that the bandwidth of an analog delay line is limited to about one third of the clock frequency. Hence a delay line clocked at 10 kHz has a useful bandwidth of only about 3.3 kHz.

Simple effects

Figures 4-15 illustrate a variety of applications for analog delay lines. In these block diagrams we will, for the sake of simplicity, not show the usual input and output lowpass filters. An actual circuit

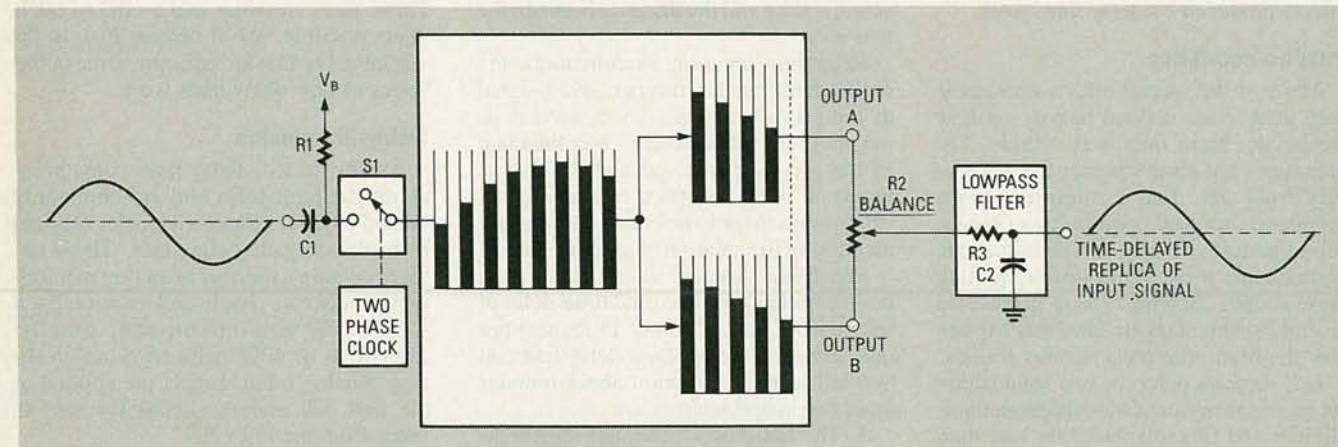


FIG. 2—THE BUCKET-BRIGADE DELAY LINE operates by sequentially shifting charges through alternate cells. The two outputs are summed and filtered for further processing.

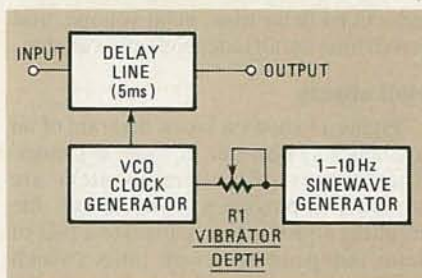


FIG. 4—THE VIBRATO CIRCUIT frequency modulates the input signal with a low-frequency oscillator.

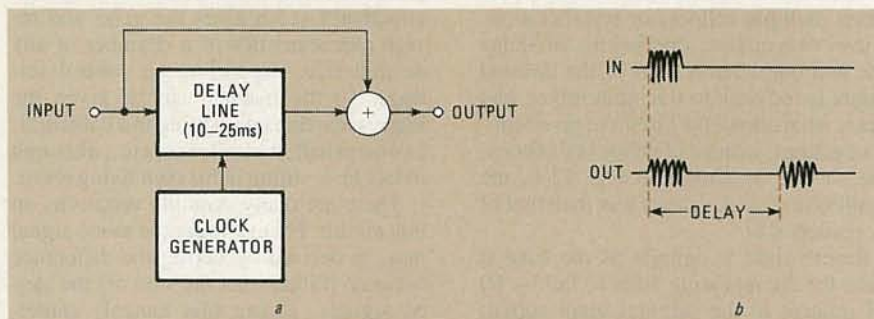


FIG. 5—THE DOUBLE-TRACKING CIRCUIT, or micro chorus, mixes the input signal with a delayed replica of the input signal (a). Input and output waveforms are shown in b.

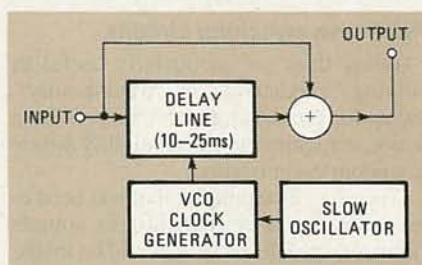


FIG. 6—THE AUTOMATIC DOUBLE-TRACKING, or mini-chorus, frequency modulates the delayed signal.

would have to include filters with the appropriate cutoff frequencies.

Figure 4 shows how the delay line can be used to apply *vibrato* (frequency modulation) to a signal. The low-frequency sine wave generator modulates the clock generator's signal and thereby causes the output signal of the delay line to be time-delay modulated.

Figure 5-a shows a delay line used to give a double-tracking effect. The delay is in the perceptible range (10–25 ms), and the delayed and direct signals are added in an audio mixer to give the composite output. Figure 5-b illustrates the circuit's input and output signals. One use for a double-tracking circuit is to feed a solo singer's voice through the unit. The output sounds as if two performers were singing in very close harmony. The double-tracking circuit is also called a mini-echo and a micro-chorus.

Figure 6 shows how the circuit shown in Fig. 5 can be modified to act as an Auto Double Tracking (ADT) circuit. Such a circuit is also called a mini-chorus. Clock

signals are derived from a VCO that is modulated by a slow oscillator, so that the delay times slowly vary. The effect that results is that a solo singer's voice sounds like a pair of singers in loose or natural harmony.

Figure 7 shows how three ADT circuits can be wired together to form a "chorus" machine. Each delay line has a slightly different delay time. The original input and the three delay signals are summed; the net effect is that a solo singer sounds like a quartet, or a duet sounds like an octet, etc.

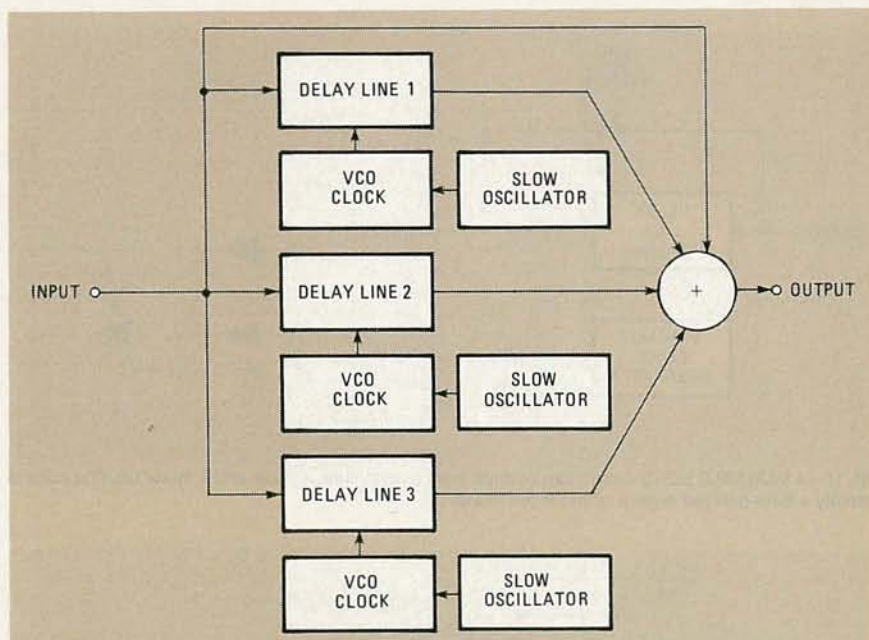


FIG. 7—A CHORUS GENERATOR is composed of several double-tracking circuits.

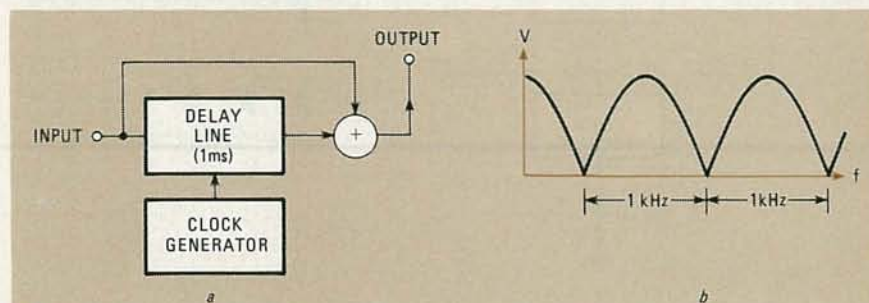


FIG. 8—A COMB FILTER can be built from a delay line, a clock, and a mixer (a). With a 1-ms delay, the notches are about 20–30 dB deep, and 1 kHz apart (b).

Comb filters

Figure 8 shows a delay line configured as a comb filter. In that circuit, the direct and the delayed signals are added together. In-phase components of both signals increase output amplitude, and those that are out of phase cancel each other and reduce output level. Consequently, as shown in Fig. 8-b, the frequency response shows a series of notches; the spacing between notches is the reciprocal of the delay-line time. In the example circuit, the 1-ms delay gives a 1-kHz (1/0.001) notch spacing. Those phase-induced notches are typically about 20–30 dB deep.

The two most popular musical applications of the comb filter are in phasers and flangers. In the phaser (shown in Fig. 9) the notches are swept slowly up and down the audio band via a slow-scan oscillator. Selected components of the input signal are then effectively deleted from the output signal.

The flanger circuit (shown in Fig. 10) differs from the phaser in that the mixer is placed ahead of the delay line, and part of the delayed signal is fed back to one input of the mixer, so that the in-phase signals

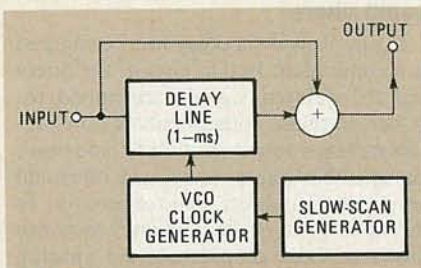


FIG. 9—THE PHASER is a variable comb filter in which the notches are slowly swept up and down the audio band.

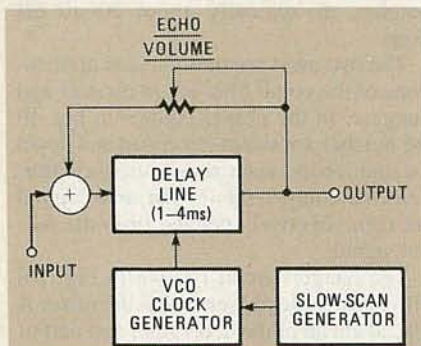


FIG. 10—THE FLANGER is a phaser with accentuated and variable notch depth.

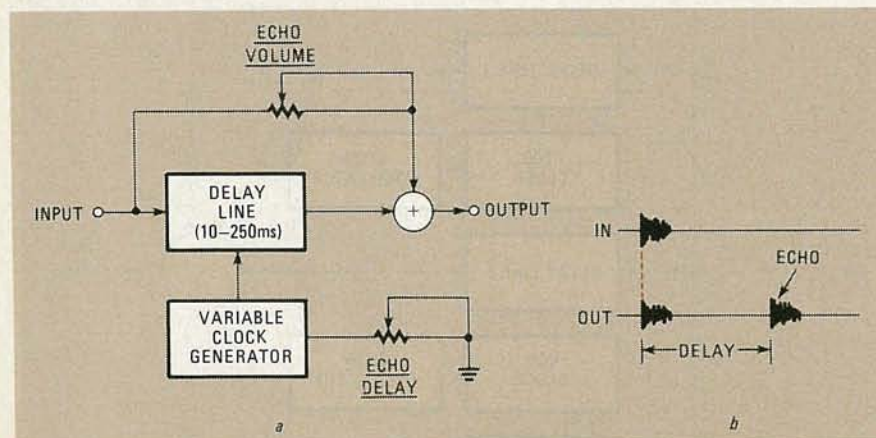


FIG. 11—A VARIABLE ECHO circuit can be built from a delay line, a clock and a mixer (a). The echo is actually a time-delayed replica of the input signal (b).

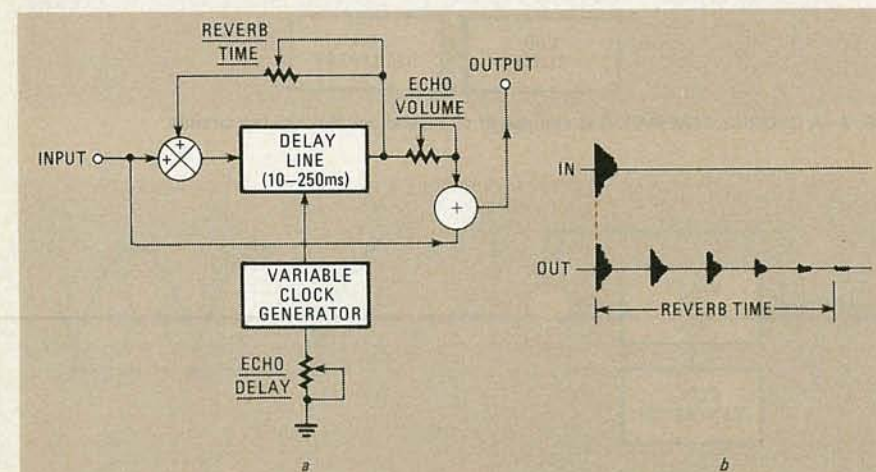


FIG. 12—ADDING REVERB to the echo circuit requires an additional mixer (a) to provide progressively diminishing echoes (b).

add together regeneratively. Peak amplitudes depend on the amount of feedback, and they can be made very steep. Those phase-induced peaks introduce very powerful acoustic effects as they are swept up and down the audio band.

Echo and reverb circuits

Figure 11 shows how to build an echo circuit with a delay line. The delay (echo) may vary from 10 to 250 ms, and it is adjustable, as is the amplitude of the echo. Note that this circuit produces only a single echo, as shown in Fig. 11-b.

The echo/reverb circuit of Fig 12 produces multiple echoes, or reverberation. It uses two mixers, one before the delay line and one after it. Part of the delayed output is fed back to the input mixer, and that is what allows the circuit to give echoes of echoes, echoes of echoes of echoes, and so on. As shown in Fig. 12-b, the amplitude of each echo is less than that of its predecessor.

Reverb time is defined as the time it takes for the repeating echo to fall by 60 dB relative to the original input signal; reverb time depends on the delay time and the overall attenuation of the feedback sig-

nals. Echo delay time, echo volume, and reverb time are all independently variable.

Hi-fi effects

Figure 13 shows a block diagram of an ambience synthesizer or room expander. The outputs of a stereo system are summed to provide a mono image; the resulting signal is then passed to a pair of semi-independent reverb units (which produce repeating echoes, but not the original signal). The reverb outputs are then summed and passed to a mono amplifier and speaker; the latter is usually placed behind the listener. The system effectively synthesizes the echo and reverb characteristics of a chamber of any desired size, depending on control settings, so the listener can be given the impression that he is sitting in a cathedral, a concert hall, a small club, etc., although in fact he is sitting in his own living room.

There are many possible variations on that circuit. For example, the mono signal may be derived by taking the difference between (rather than the sum of) the stereo signals. Doing that cancels center-stage signals and overcomes a rather disconcerting "announcer-in-a-cave" effect that occurs in "summing" systems.

Predictive switching circuits

Delay lines are particularly useful in solving "predictive" or "anticipatory" switching problems, in which a switching action is required to occur slightly *before* a random event occurs.

Suppose, for example, that you need to record random or intermittent sounds (thunder, speech, etc.). It would be inefficient and expensive to run a tape recorder continuously, but it would be impractical to try to activate the recorder via a sound switch, because part of the sound will already have passed by the time the recorder's motors get up to speed.

Figure 14 shows a delay-line solution to that problem. The sound input activates a switch that (because of mechanical inertia) turns the recorder's motor on in about 20 ms. In the meantime, the sound travels through the 50-ms delay line towards the recorder's audio input. When the sound arrives, the motors have already been turning for 30 ms, so no sound is lost. When the original sound ceases, the sound switch turns off, but the switch extender keeps the motor running for another 100 ms or so, and that enables the entire delayed signal to be recorded.

Click/scratch filter

To conclude our discussion of applications, Fig. 15 shows how predictive switching can be used to help eliminate the sounds of clicks and scratches from an audio system. Sounds of that sort can be detected easily by using stereo phase-comparison techniques.

In Fig. 15, signals from a record album

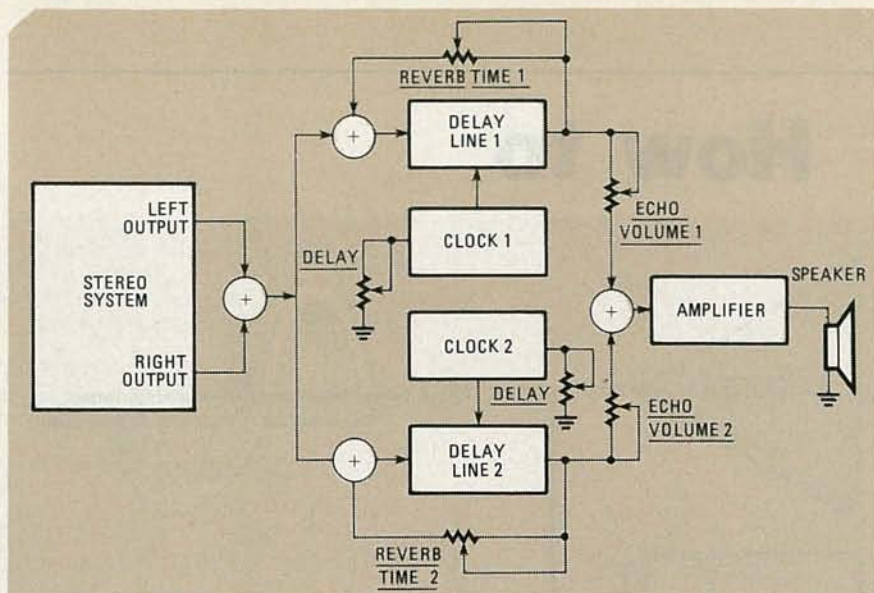


FIG. 13—THE ROOM EXPANDER produces a monophonic delayed output of the sum of the stereo outputs.

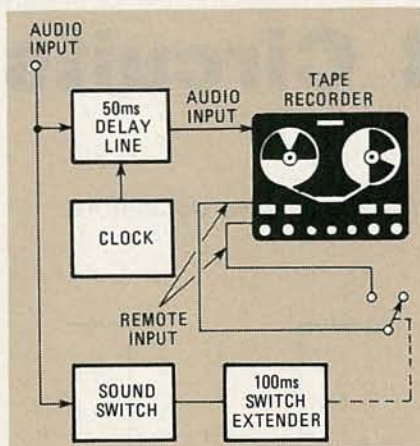


FIG. 14—A SOUND-ACTIVATED RECORDER that does not miss sound input can be built using an analog delay line.

are fed to the audio amplifier via a 3-ms delay line, an analog switch, and a sample-and-hold circuit. Normally the switch is closed, so the signal reaching the audio amplifier is a delayed but otherwise unmodified replica of the input signal. However, when a click or a scratch occurs, the detector/extender circuit opens the switch for 3 ms, and that momentarily blanks the audio signal. Since the ear is relatively insensitive to dropouts, the deletion is not noticed. As you can see in Fig. 15-b, when the click in the upper waveform is deleted, the signal is much smoother, as shown in the lower waveform.

Delay-line circuits

Figure 16 shows a practical delay line using an RD5106 (512 stages), RD5107 (1024 stages), or RD5108 (4096 stages) delay line. Those IC's are manufactured by Reticon, Inc. (345 Potrero Avenue,

Sunnyvale, CA 94086-9930); Radio Shack should have them in distribution by the time you read this.

Potentiometer R2 should be adjusted so

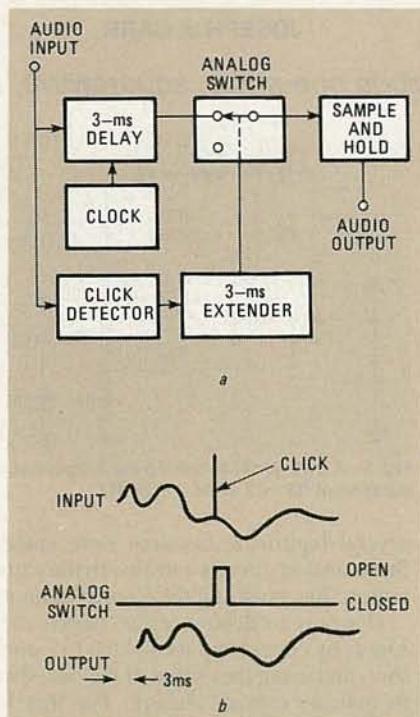


FIG. 15—AN AUDIO CLICK/SCRATCH FILTER can be built with an analog delay line and other components (a). The Click Detector opens the Analog Switch for 3 ms to delete a click (b).

that symmetrical clipping occurs under over-drive conditions. The maximum clock frequency is 1.6 MHz; the clock should be a fairly sharp squarewave with a risetime of less than 50 ns. The input signal should be limited to 1.5-volts rms to keep distortion less than 1%.

Clock circuits

The clock signal that is fed to a CTD delay line should be reasonably symmetrical, should have fairly fast rise and fall times, and should switch fully between the supply-rail voltages. CMOS devices make good clock generators

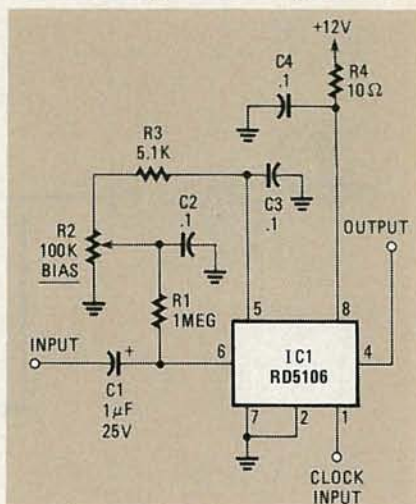


FIG. 16—AN ANALOG DELAY LINE can be built from just a few discrete components. Limit the input signal to less than 1.5-volt rms to keep harmonic distortion less than 1%.

because they are capable of generating waveforms that meet those requirements.

The general-purpose two-phase clock circuit shown in Fig. 17 is inexpensive and can be used in many applications where a fixed or a manually-variable frequency is needed. The frequency can be swept over a 100:1 range via R3; the center frequency can be altered by changing the value of C1.

A high-performance two-phase clock generator based on the VCO section of a 4046 phase-locked loop is shown in Fig. 18. That circuit is useful in applications where the frequency needs to be swept over a very wide range, or needs to be voltage-controlled. The frequency is controlled by the voltage at pin 9. Higher voltages correspond to higher frequencies. Maximum frequency is set by the values of C2 and R1, and minimum frequency is set by the value of C2 and the series values of R3 and R4.


The preceding clock circuits can be used to clock many delay lines. Some, however, have high-capacitance (0.001 μF) inputs and therefore require a low-impedance clock driver. One way of providing a low-impedance clock driver is by connecting two 4013 "D" flip-flops in parallel, as shown in Fig. 19. That circuit is driven by a single-phase clock signal, which can be obtained from either of the preceding circuits.

Filter circuits

As we mentioned previously, in most applications a lowpass filter must be inserted

continued on page 80

How to

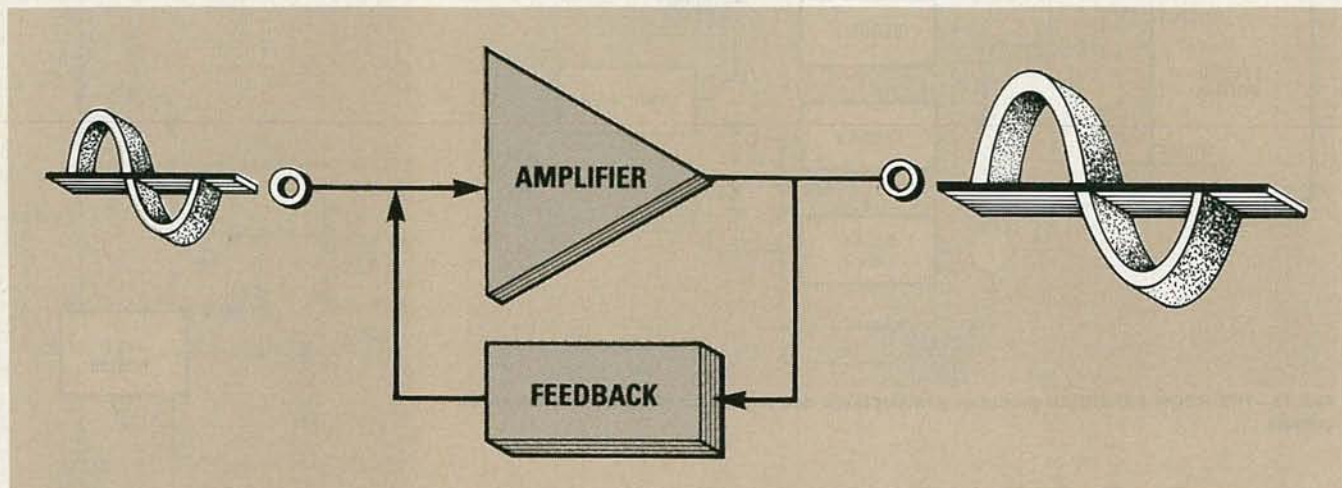

Design OSCILLATOR Circuits

JOSEPH J. CARR

Our subjects this month include one-shots, squarewave, and triangle wave oscillators.

Part 4 LAST TIME WE DISCUSSED several types of sinewave oscillators. This time we'll investigate three different types of signal generators: one-shots, squarewave oscillators, and triangle-wave oscillators. All our circuits this month are based on op-amps, and they're easy to build and to customize.

The one-shot

The monostable multivibrator, or one-shot, is so called because it has one stable state, high or low, depending on the circuit configuration. A monostable produces one output pulse for each input pulse. Each pulse has the same duration and amplitude. Monostables are used in a variety of applications: pulse stretching, switch debouncing, and others.

The concept of pulse stretching may be somewhat confusing because a pulse is not really stretched. Instead, a pulse with a short duration is used to trigger one with a longer duration.

Switch debouncing is a common application for one-shots; it is actually a form of pulse stretching. The mechanical contacts in most switches don't make and break cleanly; they literally bounce. That means that the contacts open and close several times in quick succession. The multiple makes and breaks can fool the circuitry that follows into thinking that

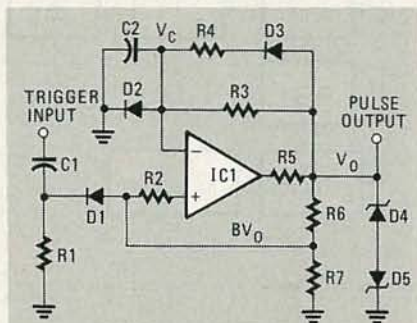


FIG. 1—A ONE-SHOT circuit's pulse output has a duration of $R3 \times C2$, if $R6 = 0.58 R7$.

several legitimate closures were made. Some analog circuits can absorb the extra pulses, but most digital circuits cannot.

One way to debounce the switch closure is by connecting the switch to a one-shot, and using the output of the one-shot to indicate contact closure. For that to work, the duration of the output pulse must exceed the time during which the contacts are bouncing.

An op-amp based one-shot is shown in Fig. 1; waveforms present at the output of the circuit (V_O) and across $C2$ (V_C) are shown in Fig. 2. The one-shot has only one stable output state, which in this case is $+V_Z$. The one-shot is triggered at time t_1 so the output snaps to the unstable state, $-V_Z$. It will remain in that state for time T , which is defined as $t_2 - t_1$.

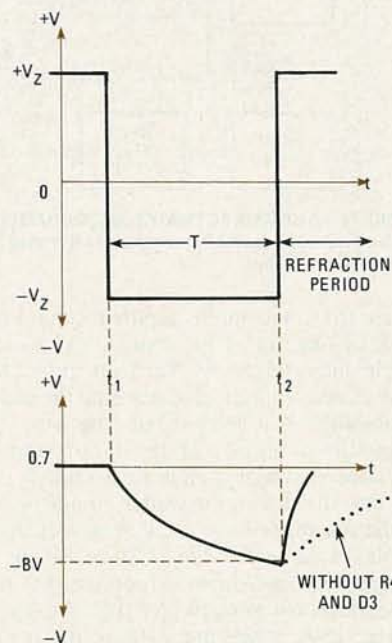


FIG. 2—DURING THE REFRACTORY PERIOD, the one-shot circuit will not respond to a trigger input. Adding a diode and a resistor can shorten the refractory period.

Normally the output of the op-amp is high ($+V_Z$), but when a pulse is applied to the trigger input, the output snaps low ($-V_Z$). At that instant capacitor $C2$ will still be charged to a positive voltage (not

+ V_Z because D2 clamps the voltage to about 0.7 volts).

However, the output voltage is $-V_Z$, so the charge across C2 will begin to approach that potential. It will never reach it, however, because the noninverting input of the op-amp is biased to a fraction of the output voltage, B, as determined by the voltage divider composed of R6 and R7. When the voltage across C2 exceeds BV_O , the output of the op-amp will snap back to the stable (high) state.

The refractory period

The period immediately after the output returns to the stable state is called the refractory period. The circuit will not respond to trigger inputs during that period. To understand why that is the case, first assume that R4 and D3 are not present. Then C2 can discharge only through R3, and that takes a long time. However, by including R4 and D3, we can shorten the refractory period. If the resistance of R4 is much less than that of R3, then the circuit will discharge much faster than it will charge. Diode D3 ensures that current flows through R4 only during discharge. The lower curve in Fig. 2 indicates the different discharge times with and without those components.

The duration T of the output pulse is given approximately by this equation:

$$T = R3 \cdot C2 \cdot \ln [1/(1 - B)]$$

In that equation, T is given in seconds, R3 is in ohms, C2 is in farads, \ln denotes the use of the natural logarithm, and B is the feedback factor. B is determined from the voltage-divider equation: $B = R6/(R6 + R7)$.

That timing equation is derived from the time it takes C2 to charge from +0.7 volts to voltage BV_O . We can simplify the equation by making B a constant. For example, if the values of the resistors are equal, then $B = R/(R + R) = 0.500$, so the equation can be simplified as follows:

$$T = R3 \cdot C2 \cdot \ln [1/(1 - B)]$$

$$T = R3 \cdot C2 \cdot \ln [1/(0.500)]$$

$$T = R3 \cdot C2 \cdot \ln [2]$$

Therefore,

$$T = R3 \cdot C2 \cdot 0.693$$

If $R6 = 2R7$, then $B = R/(R + 2R) = R/3R = 0.333$. In that case we can simplify the timing equation as follows:

$$T = R3 \cdot C2 \cdot \ln [1/(1 - 0.333)]$$

$$T = R3 \cdot C2 \cdot \ln [1.500]$$

$$T = R3 \cdot C2 \cdot 0.406$$

B is often given a value of 0.632. Doing so allows us to reduce the timing equation to

$$T = R3 \cdot C2$$

Since $R7/(R6 + R7) = 0.632$, we can do a little algebra and find that $R6 = 0.582 R7$.

In practical terms, we usually select a capacitor and then calculate resistor values, since there are fewer standard values of capacitance.

Automatic calculations

Listing 1 contains a BASIC program that will calculate component values for the one-shot multivibrator. The program is written for the dialect of BASIC used in the IBM-PC (and compatibles), but it should run on many other machines as-is, and it should be easy to translate into other dialects of BASIC, if necessary.

When you run the program it asks you for the duration of the pulse (in milliseconds) and a value of capacitance (in μF). The program then calculates the required resistance, and reports it. At that point you can either run the program again, or exit.

Squarewave oscillators

As you can see in Fig. 3, an op-amp-based squarewave generator is relatively

LISTING 1— ONE-SHOT CALCULATIONS

```

100 REM Monostable Multivibrator
110 FOR I=1 TO 30
120 PRINT
130 NEXT
140 PRINT " Monostable
150 PRINT "Multivibrator
160 PRINT " Circuit
170 PRINT " Design
180 PRINT
190 PRINT
200 PRINT
210 INPUT "Pulse duration in ms: ",T
220 T = T/1000
230 INPUT " Capacitor in uF: ",C
240 PRINT
250 C = C/10^6
260 R = T/(.693*C)
270 R = INT(R)
280 C = C*10^6
290 T = T*1000
300 PRINT "For a pulse duration of:"
310 PRINT
320 PRINT T;"milliseconds"
330 PRINT " use a
340 PRINT R;"ohm resistor"
350 PRINT " and a
360 PRINT C;"uF capacitor."
370 PRINT
380 PRINT
390 PRINT "What Now?"
400 PRINT
410 PRINT "1. Do another"
420 PRINT "2. Quit
430 PRINT
440 INPUT "Choose one: ",D
450 IF D = 1 THEN GOTO 200
460 END

```

simple. The timing diagram of that circuit is shown in Fig. 4. Refer to both during the discussion that follows.

In contrast to the one-shot, the squarewave oscillator is called an astable oscillator, because it has no stable output

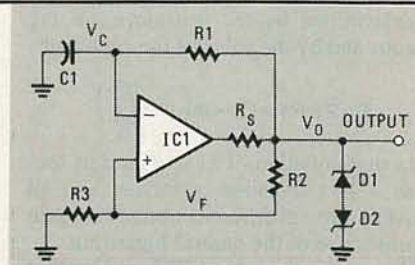


FIG. 3—THIS SQUAREWAVE OSCILLATOR'S frequency of oscillation is given by $f = 1/(3.2 R C1)$.

state. In other words, its output snaps back and forth between the high ($+V_Z$) and low ($-V_Z$) states.

The noninverting input of the op-amp is biased by a fraction of the output voltage, as determined by the R2/R3 network; the inverting input is biased by the voltage (V_C) across capacitor C1. That voltage is determined by V_O and by the R1C1 time constant.

When the circuit is initially turned on, the capacitor has no charge, so the inverting input has no potential with respect to ground. Therefore the output will be high. The capacitor will begin to charge toward $+V_O$ at a rate that is determined by the product of the values of R1 and C1.

When that voltage reaches the bias

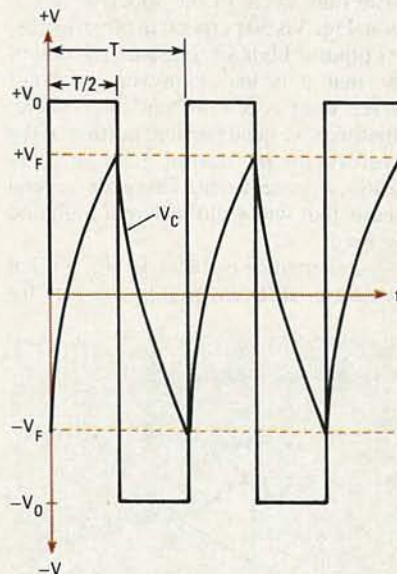


FIG. 4—THE VOLTAGE ACROSS C1 (in Fig. 3) varies between $+V_F$ and $-V_F$.

point of the noninverting input ($+V_F$), the output will snap low. At that point the charging of the capacitor reverses, and the voltage will discharge from $+V_F$ toward zero, and then toward $-V_F$. When it reaches that negative voltage, the output again snaps high, the capacitor begins to discharge toward zero and then toward $+V_F$. That oscillating cycle will continue

for as long as power is applied to the circuit.

The time T that is required for one cycle is determined by the resistances in the circuit, and by the value of the capacitor:

$$T = 2 \times R_1 \times C_1 \times \ln\left(1 + \frac{2R_2}{R_3}\right)$$

In that equation, T is specified in seconds, C1 is specified in farads, and all resistors are specified in ohms; ln again signifies use of the natural logarithm.

By making the value of R2 equal to that of R3, we can simplify the equation to:

$$T = 3.2 \cdot R_1 \cdot C_1$$

Solving for the resistance,

$$R_1 = T / (3.2 C_1)$$

To work in frequency rather than period, recall that $T = 1/f$. Then we can substitute:

$$1/f = 3.2 \cdot R_1 \cdot C_1$$

or

$$f = 1/(3.2 \cdot R_1 \cdot C_1)$$

Now let's work a practical example. Calculate the values of the components needed to build a 1500-Hz oscillator. Assume we'll use a 0.001- μ F capacitor.

$$R_1 = T / (3.2 C_1)$$

$$R_1 = (0.00067) / (3.2 \times 10^{-9})$$

$$R_1 = 209,375 \text{ ohms}$$

The duty cycle of the squarewave circuit in Fig. 3 is 50 percent; in other words, the output is high for the same amount of time that it is low. However, we don't always want a 50 percent duty cycle; sometimes we need the high portion of the waveform to be shorter than the low portion, or vice versa. There are several circuits that will yield different high and low times.

One alternative is shown in Fig. 5. That circuit uses different timing resistors for

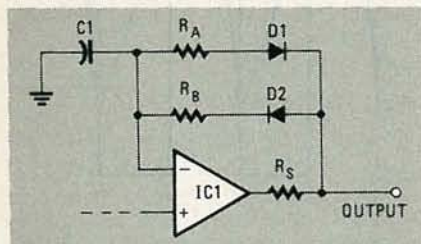


FIG. 5—TO OBTAIN UNEQUAL DUTY CYCLE in the squarewave oscillator, use two different timing resistors. Resistor R_B controls the positive half-cycle, and R_A controls the negative half-cycle.

the high and the low portions of the cycle; the diodes switch R_A or R_B into the circuit at the appropriate time. When the output is high, D2 is forward-biased, so R_B controls timing. Similarly, when the output is low, D1 is forward-biased, so R_A controls timing.

LISTING 2—TRIANGLE-WAVE CALCULATIONS

```

100 REM Triangle wave generator
110 FOR I=1 TO 30
120 PRINT
130 NEXT I
140 PRINT "Fixed or Variable?"
150 PRINT
160 PRINT "1. Fixed
170 PRINT "2. Variable
180 PRINT
190 INPUT "Choice: ",A
200 IF A > 2 THEN GOTO 140
210 GOSUB 1100
220 ON A GOTO 230, 480
230 PRINT
240 PRINT "Fixed Frequency"
250 PRINT
260 INPUT "Frequency in Hz: ",F
270 PRINT
280 PRINT
290 INPUT "Capacitor in uF: ",C
300 C = C/(10^6)
310 IF K = 1 THEN R = .25/(F*C)
320 IF K = 2 THEN GOSUB 940
330 R = INT(R)
340 C = C*10^6
350 PRINT
360 PRINT "Fixed frequency "
370 PRINT "component values:"
380 PRINT
390 PRINT "Frequency=";F;" Hz"
400 PRINT "Capacitor=";C;" uF"
410 PRINT "Resistor =" ;R;" Ohms"
420 IF K<>2 THEN 450
430 PRINT "R1 =" ;R1;" Ohms "
440 PRINT "R2 =" ;R2;" Ohms"
450 PRINT
460 PRINT
470 GOTO 820
480 PRINT "Variable Frequency
490 PRINT
500 PRINT "Enter upper and lower"
510 PRINT "frequency limits in Hz"
520 PRINT
530 INPUT "Lower Limit: ",FL
540 PRINT
550 INPUT "Upper Limit: ",FH
560 PRINT
570 INPUT "Capacitor in uF: ",C
580 C = C/10^6
590 IF K = 2 THEN GOSUB 1020
600 IF K = 1 THEN RL = .25/(FL*C)
610 IF K = 1 THEN RH = .25/(FH*C)
620 C = C*10^6
630 RL = INT(RL)
640 RH = INT(RH)
650 PRINT "Variable frequency
660 PRINT "component values
670 PRINT
680 PRINT "Frequency range:";
690 PRINT FL;" to ";FH;" Hz"
700 PRINT "Capacitor=";C;" uF"
710 PRINT "Resistor =" ;RH;"
720 PRINT " to ";RL;" Ohms"
730 PRINT
740 IF K <> 2 THEN 770
750 PRINT "R1 =" ;R1;" Ohms, "
760 PRINT "R2 =" ;R2;" Ohms"
770 GOTO 820
780 INPUT "Choice: ",W
790 IF W > 2, THEN GOTO 780
800 ON W GOTO 810,240
810 RETURN
820 PRINT
830 PRINT "What's next?"
840 PRINT
850 PRINT "1. The same again"
860 PRINT "2. Options menu"
870 PRINT "3. Quit"
880 PRINT
890 INPUT L
900 IF L > 3, THEN GOTO 820
910 ON L GOTO 220,140,920
920 PRINT "PROGRAM ENDED"
930 GOTO 1210
940 PRINT
950 INPUT "Value of R1: ",R1
960 PRINT
970 INPUT "Value of R2: ",R2
980 PRINT
990 R = R1/(4*R2*C*F)
1000 R = INT(R)
1010 RETURN
1020 PRINT
1030 INPUT "Value of R1: ",R1
1040 PRINT
1050 INPUT "Value of R2: ",R2
1060 PRINT
1070 RH = R1/(4*R2*C*FH)
1080 RL = R1/(4*R2*C*FL)
1090 RETURN
1100 PRINT
1110 PRINT "Select One:"
1120 PRINT
1130 PRINT "1. Standard Version ";
1140 PRINT "(R1=R2)"
1150 PRINT "2. Custom Values ";
1160 PRINT "(you enter R1 and R2)"
1170 PRINT
1180 INPUT "Select One: ",K
1190 IF K > 2, THEN GOTO 1110
1200 RETURN
1210 END

```

Another method of obtaining a non-symmetrical waveform is shown in Fig. 6. In that circuit we bias the timing capacitor

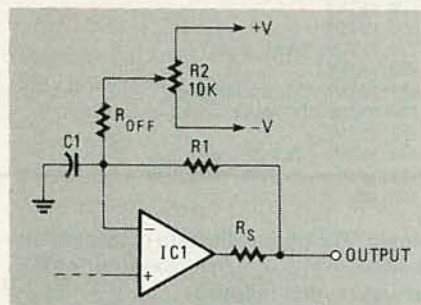


FIG. 6—UNEQUAL DUTY CYCLE may also be obtained by biasing the timing capacitor (C1) positive or negative through R_{OFF} and R2.

either positive or negative by the actions of potentiometer R2 and R_{OFF} . The polarity of the bias voltage is determined by the setting of R2; that voltage can vary anywhere from $-V$ through zero to $+V$.

Triangle-wave oscillators

There are numerous ways of designing a triangle-wave oscillator, but few have the simplicity of a squarewave oscillator followed by a Miller integrator. The latter is shown in Fig. 7; its timing diagram is shown in Fig. 8.

The slope of the waveform in the lower trace depends on the RIC_1 time constant. When that time constant is long compared with the period of the squarewave input, a

continued on page 79

PC SERVICE

One of the most difficult tasks in building any construction project featured in **Radio-Electronics** is making the PC board using just the foil pattern provided with the article. Well, we're doing something about it.

We've moved all the foil patterns to this new section where they're printed by themselves, full sized, with nothing on the back side of the page. What that means


for you is that the printed page can be used directly to produce PC boards!

Note: The patterns provided can be used directly only for *direct positive photoresist methods*.

In order to produce a board directly from the magazine page, remove the page and carefully inspect it under a strong light and/or on a light table. Look for breaks in the traces, bridges between traces, and in

general, all the kinds of things you look for in the final etched board. You can clean up the published artwork the same way you clean up your own artwork. Drafting tape and graphic aids can fix incomplete traces and doughnuts, and you can use a hobby knife to get rid of bridges and dirt.

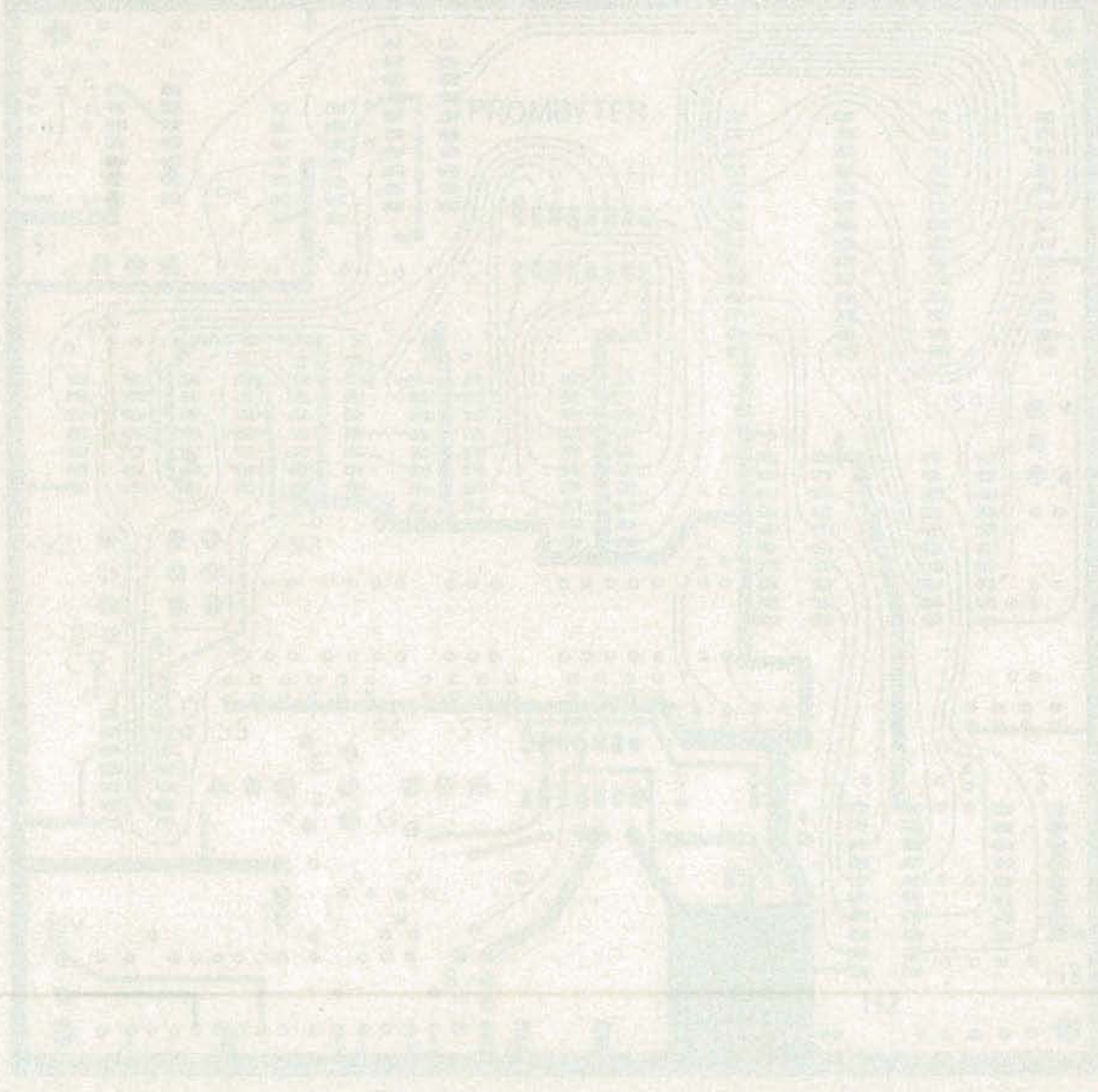An optional step, once you're satisfied that the artwork is clean, is to take a little bit of mineral oil and carefully wipe it



PC SERVICE


across the back of the artwork. That helps make the paper translucent. Don't get any on the front side of the paper (the side with the pattern) because you'll contaminate the sensitized surface of the copper blank. After the oil has "dried" a bit—patting with a paper towel will help speed up the process—place the pattern front side down on the sensitized copper blank, and make the exposure. You'll

probably have to use a longer exposure time than you are used to.

We can't tell you exactly how long an exposure time you will need as it depends on many factors but, as a starting point, figure that there's a 50 percent increase in exposure time over lithographic film. But you'll have to experiment to find the best method for you. And once you find it, stick with it.


Finally, we would like to hear how you make out using our method. Write and tell us of your successes, and failures, and what techniques work best for you. Address your letters to:

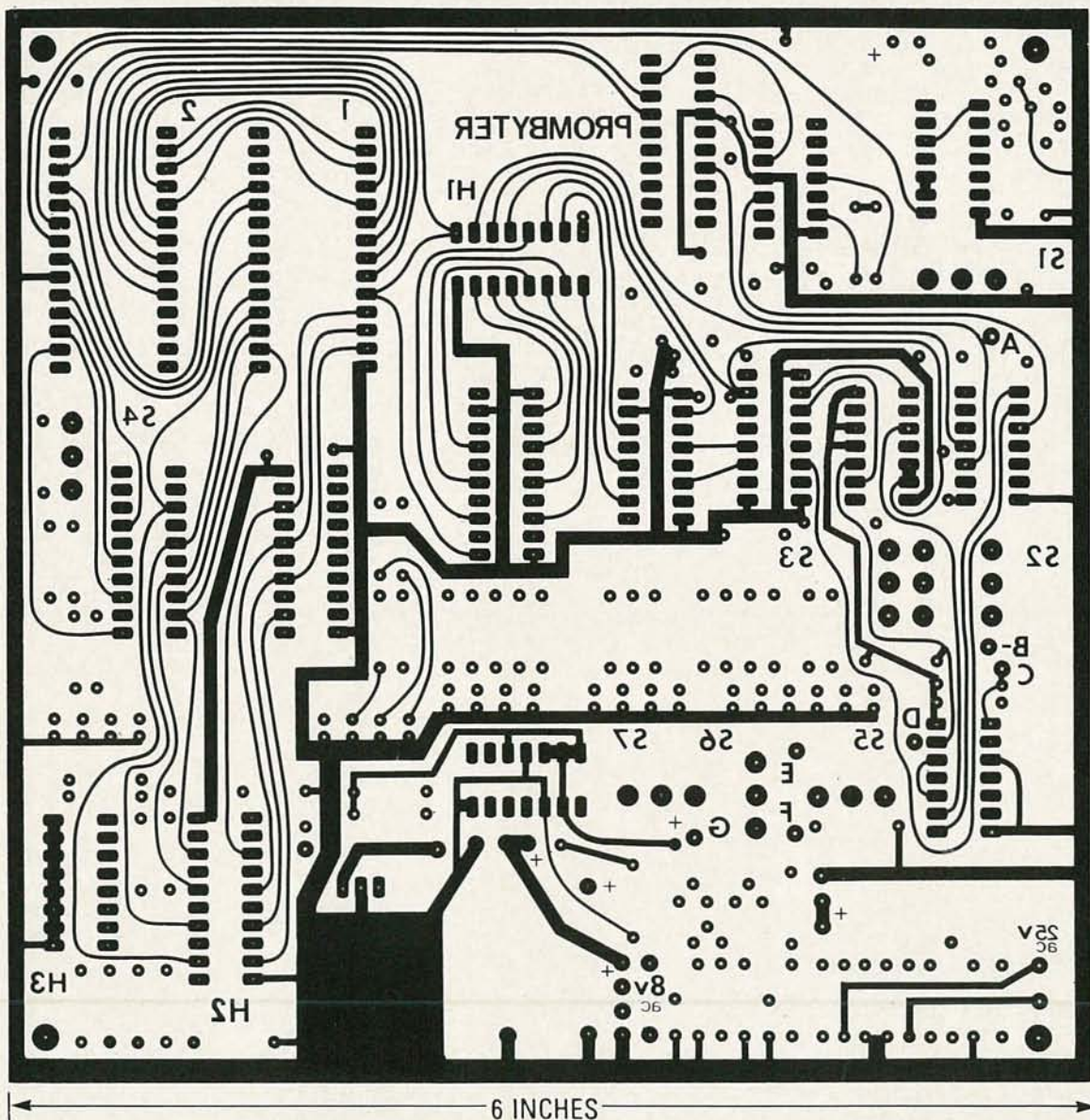Radio-Electronics
Department PCB
500-B Bi-County Blvd.
Farmingdale, NY 11735





THE COMPONENT SIDE of the EPROM programmer PC board is shown here. Due to space limitations, the solder side will be shown next time.

PC SERVICE

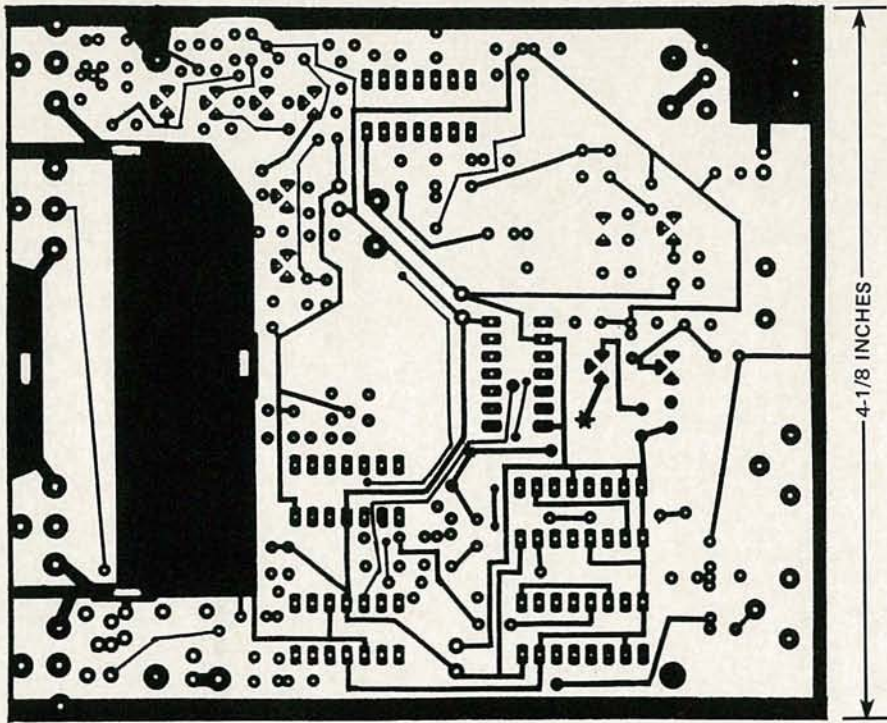

SINCE THE PC BOARD for the Telease-Maast decoder is double sided, feedthroughs should be installed at all unused pads. Also, be sure to solder all component leads on both sides of the board. The component side is shown here.

PC SERVICE

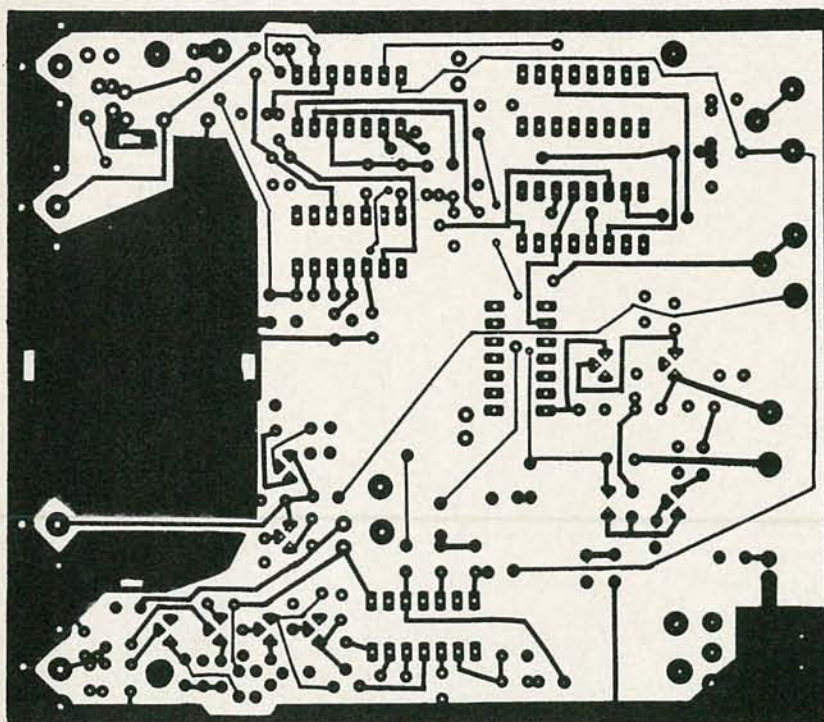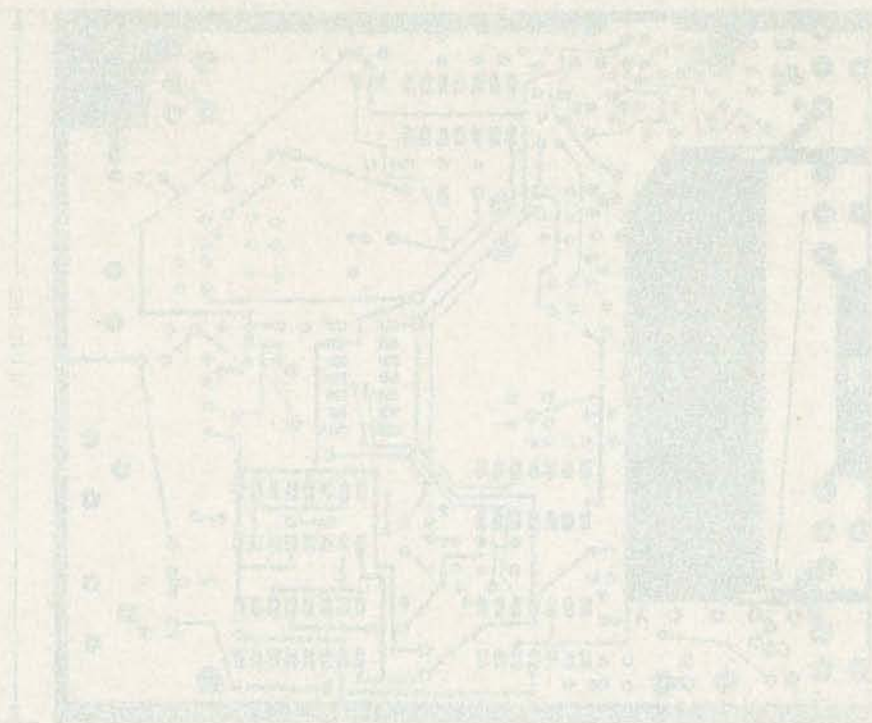

4-1/8 INCHES

HERE'S THE SOLDER SIDE of our double-sided Telease-Maast decoder PC board. For more on the decoder, turn to page 50.

OSCILLATORS

continued from page 74

fairly linear output will result, because the capacitor is never allowed to fully charge or discharge. You can think of that graphically as restricting charging and discharging to a small portion of the curve shown in Fig. 4.

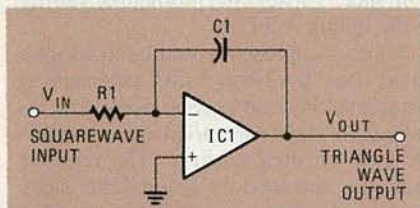


FIG. 7—A MILLER INTEGRATOR may be used to create triangle waves from squarewaves.

The schematic of a complete triangle-wave generator based on the Miller integrator is shown in Fig. 9. In that circuit a Miller integrator is connected to a square-wave generator. That circuit's frequency of oscillation is given by the following equation:

$$f = R2 / (4 \cdot R1 \cdot R3 \cdot C1)$$

In Listing 2 is another program (also in IBM-PC BASIC); that program will cal-

culate the resistor and capacitor values of the triangle-wave circuit in Fig. 9. The program is very similar to the one for calculating the circuit requirements for a

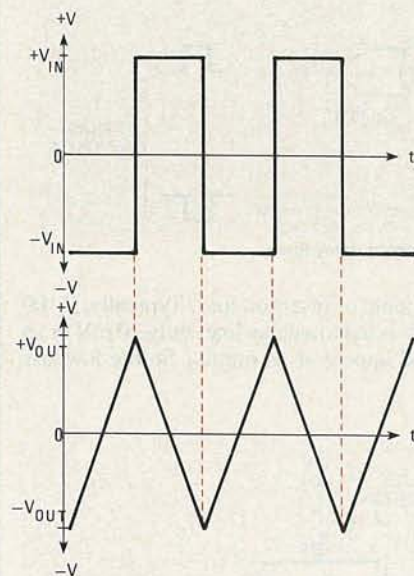


FIG. 8—LINEARITY OF A MILLER integrator is maintained by making the R1C1 time constant long compared with that of the incoming squarewave.

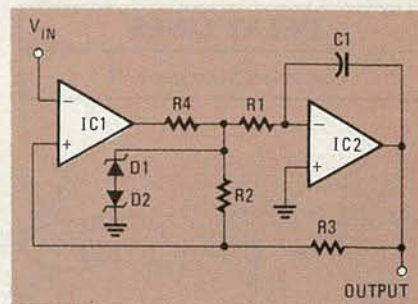


FIG. 9—A COMPLETE TRIANGLE-WAVE GENERATOR may be built from a Miller integrator and a squarewave generator.

one-shot that is shown in Listing 1. The triangle-wave program, however, will calculate resistance values for both fixed- and variable-frequency oscillators. For the latter, a variable resistor (or a series combination of a fixed and a variable resistor) should be substituted for R2.

Next time

In the next installment in this series we'll discuss the crystal-based sinewave oscillator. Future installments will also deal with crystal-based squarewave oscillators; among other things, those circuits are used in computers and in other digital circuits for clocks and other sequence controllers. **R-E**

Send Purchase Order
Check, Money Order, or C.O.D.
or Call Toll Free
800-223-0826
In N.Y. State (212) 865-5580

CABLE BOXES JERROLD CORDLESS CABLE TV CONVERTERS

MODEL DRX3-105/400

- 60 channels
- Remote channel changing
- Remote ON/OFF switch
- Remote fine tuning

\$69⁹⁵

EXTRA HAND REMOTES
REM 400 - \$29⁹⁵



JERROLD CORDLESS
CABLE TV CONVERTER
Model STARCOM CS-V

\$129

- Volume control
- 68 channels
- Mute control
- Instant channel recall
- Automatic fine tuning



JERROLD CORDLESS
CABLE TV CONVERTER
Model DRZ/450

\$69⁹⁵
\$79⁹⁵ ea.

- 66 CHANNELS
- AUTOMATIC FINE TUNING
- A/B SWITCH OPTION



TEKNICA CORDLESS
CABLE TV CONVERTER
Model 6510

\$139⁹⁵

- VOLUME CONTROL
- 140 CHANNEL CAPABILITY



JERROLD CORDLESS
CABLE TV CONVERTER
Model JRX3-105

\$49⁹⁵

- 36 channels



HITACHI SCOPES

V-212-20 MHz- \$460
V-222-20 MHz- \$535
V-422-40 MHz- \$689
V-223-20 MHz- \$599
DELAYED SWEEP



PROBES INCLUDED

B&K DUAL TRACE SCOPES

1476-10MHz- \$375
1477-15MHz- \$425
1479-30MHz- \$550
DELAYED SWEEP

■ MASTER CARD ■ VISA

OMNITRON ELECTRONICS

770 Amsterdam Ave., New York, NY 10025

Write for
**FREE
CATALOG**
136 page

SHIPPING CHARGES

For Orders	Add
\$25-100	\$6.50
\$100-500	\$8.50
\$500-750	\$10.50
\$750 and up	\$20.00

CIRCLE 110 ON FREE INFORMATION CARD

OCTOBER 1986

DELAY LINES

continued from page 71

frequency can be reduced to 12.5 kHz by giving C2 and C3 values of 0.001 and 0.006 μF , respectively. All delay lines suffer from a certain

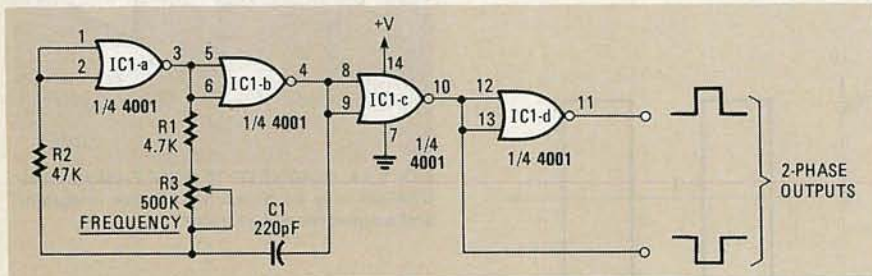


FIG. 17—A TWO-PHASE CLOCK is required by most analog delay lines.

amount of insertion loss. Typically, if 100 mV is fed to a delay line, only 70 mV or so will appear at its output. So the lowpass

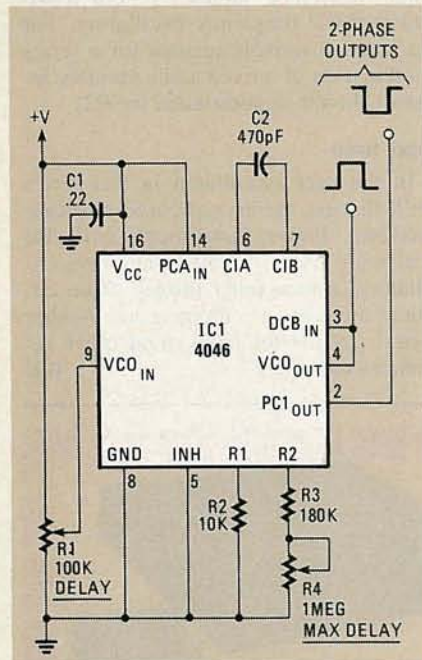


FIG. 18—A VCO CLOCK provides wider range and more precise control over clock frequency.

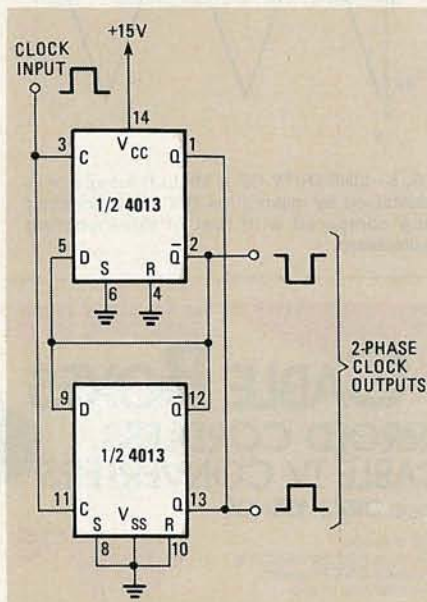


FIG. 19—A LOW-IMPEDANCE single- to two-phase clock converter is used with delay lines having high input capacitance.

ted between the actual input signal and the input of the delay line to prevent aliasing problems. In addition, another delay line must be connected in series with the output of the delay line to provide clock-signal rejection and integration of the sample signals. For maximum bandwidth, both filters should have cutoff frequencies that are one third (or less) of the maximum clock frequency. The input filter usually has at least a 1st-order (6-dB per octave) response, and the output filter usually has at least a 2nd-order (12-dB per octave) response.

Figure 20 shows the schematic of a 25-kHz 2nd-order lowpass filter with AC-coupled input and output. The non-inverting terminal of the op-amp (pin 3) is biased at $V_{CC}/2$, usually by a simple resistor network. The cutoff frequency can be varied by giving C2 and C3 alternative values, but they should be maintained in a 1:6 ratio. For example, cutoff

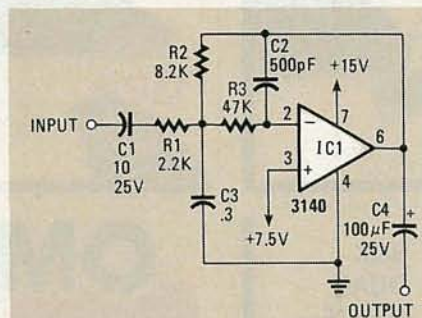


FIG. 20—THIS LOW-PASS FILTER has a cutoff frequency of 25 kHz and 2nd-order response.

filter on the output should be given some gain, in order to provide an overall circuit gain of one. That is done by designing the filter around an active element, such as an op-amp.

R-E

RAID ON HBO

continued from page 49

receiver systems require that the RF level at the uplink receiver be kept within certain limits. HBO could, of course, increase power by a factor of 100, and place a 20-dB attenuator at the input to the receiver. But aside from being a crude solution, there's always the problem of getting to the uplink receiver.

Another approach would be to adopt a tactic used by 2-way radio repeaters to avoid unauthorized access. That is to require authorized users to place a subaudible tone on their carriers. The repeater cannot be activated by a signal that lacks the tone. Even more security is provided by using a digital access code.

However, once the transponder has been accessed, there is nothing to stop another signal from taking over the transponder, even if it is not encoded. That signal will control the transponder until the appropriate security circuitry detects an improper or absent access tone or code, causing the transponder to shut down. Therefore, even with such a system a pirate would be able to wreak havoc with the authorized user's signal. And, of course, the problem of reaching existing satellite equipment to make the required modifications remains.


What about the possibility of catching a video pirate? Typical dish beamwidths are 2° to 3°. Because of that, it is virtually impossible to detect a transmission from the ground using conventional means.

How about finding the signal from the air? Assuming that the pirate is using a really lousy dish, that is, one with a 3° beamwidth, sidelobes should be detectable out to about 10°. Sparing you the geometry, that translates to a detection area of about 3.14 square miles. (With a better dish, which is likely, the detection area would be even smaller.) Consider for a moment the number of aircraft that would be required to cover the continental United States. And what if the signal originated off shore? Further, those aircraft would have to be in place constantly because no one aside from the pirate knows when he will strike next.

In summary, unless someone turns the pirate in, or unless his ego gets the better of him, the chances of finding Captain Midnight are just slightly higher than zero.

The possibility of deliberate interference to a satellite is a weak link in the satellite-communications chain. That fact has been obvious to the military since the dawn of the satellite age. But the military has the methods, and the money, to make their communications links secure. HBO and other programmers do not. It is little wonder that the industry is terrified. R-E


ELENCO PRODUCTS AT DISCOUNT PRICES!

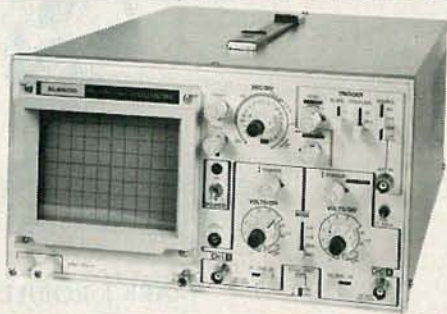

20 MHz DUAL TRACE OSCILLOSCOPE

\$369 MO-1251

FREE
DIGITAL
METER
WITH
SCOPE
PURCHASE

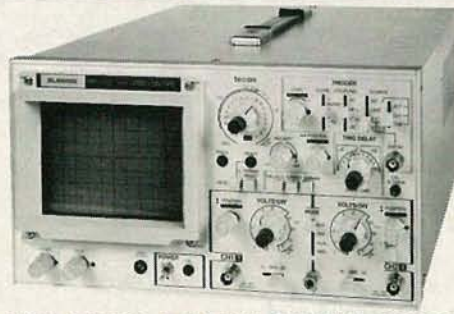

35 MHz DUAL TRACE OSCILLOSCOPE

\$545 MO-1252

Top quality scopes at a very reasonable price. Contains all the desirable features. Elenco's 2 year guarantee assures you of continuous service. Two 1x, 10x probes, diagrams and manual included. Write for specifications.



MULTI METER with CAPACITANCE and transistor tester

\$65 Model CM-1500

Reads Volts, Ohms, Current, Capacitors Transistors & Diodes



TRUE RMS 4 1/2 DIGIT MULTIMETER

\$135 Model M-7000

.05% DC Accuracy
.1 % Resistance with Freq. Counter & Deluxe Case



AUTO RANGING plus MANUAL RANGING 3 1/2 DIGIT METER 28 FUNCTIONS FULLY PROTECTED

M-1180 .7% ACY \$36.95
M-1182 .25% ACY \$39.95
M-1181 .1% ACY \$42.95

GF-8016 Function Generator with Freq. Counter

\$219

- Sine, Square, Triangle,
- Pulse, Ramp, .2 to 2 MHz
- Frequency .1 thru 10 MHz

GF 8015 without Freq. Meter \$169

10 MHz OSCILLOSCOPE

\$190

S-3000

10 MHz DC or AC Triggered Sweep
Calibrated Vert & Hor
Reads Volts & Freq

BREARDBORD

Shown 9434

9430 1,100 pins \$15
9434 2,170 pins \$25
9436 2,860 pins \$35

Triple Power Supply XP-660


\$14950

0-20V @ 1A
0-20V @ 1A
5V @ 5A

Fully Regulated, Short Circuit Protected with 2 Limit Cont. 3 Separate Supplies.

50 MHz LOGIC PROBE

\$23

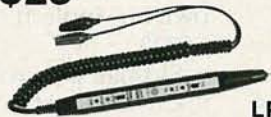

LP-700

20 nec with memory

LOGIC PULSER

\$25



LP-600

2 us pulse @ 1A

3 Amp Power Supply XP-650

\$11950

0-40V @ 1.5A
0-20V @ 3A

Fully regulated, short circuit protected current limit control



DIGITAL LCR METER

Model LC-1800
Measures: Inductors
Capacitors, Resistors

\$148

Inductors .1μH to 200 H
Capacitor .1Pf to 200μf
Resistor .01Ω to 20M Ω
Ranges 6 Ind, 7 cap, 7 res

C&S SALES, 8744 W. North Ter. Niles, IL 60648
800-292-7711 (312) 459-9040



15 DAY MONEY BACK GUARANTEE ASK FOR CATALOG

2 Year Limited Guarantee! Add 5% for Postage (\$10 max.), IL Res., 7% Tax

CIRCLE 109 ON FREE INFORMATION CARD

ROBOTICS



MARK J. ROBILLARD,
ROBOTICS EDITOR

Rovers revisited

THOSE OF YOU WHO HAVE FOLLOWED this column since its inception will remember the simple two-wheeled mobile platform we presented in the September 1985 issue. That platform consists of a wooden base, two small wheels, and a surplus motor from a Milton Bradley *Big Trak*. No, there wasn't much to it, but apparently several readers thought that it was just right to start experimenting with robotics.

Then in the October issue we reviewed the *Scorpion* robot kit that is available from Rhino Robots (3402 N. Mattis, P. O. Box 4010, Champaign, IL 61820). Once again, based on the letters we've received, quite a few of you thought that was just the right way to get started in robotics.

This month we'll visit the subject of rovers again, for two reasons. One, a product has come to our attention that we feel warrants further investigation, and two, we've been revitalizing the simple platform robot.

Meet Ernie

Recently we received a large packet of information from a Canadian company called Micromega (#6 918 16th Ave N. W., Calgary, Alberta, Canada T2M 0K3). The package contained the technical manual for their robot rover, who is named *Ernie*, and is shown in Fig. 1. My first impression was of *Ernie* was, "Oh no. Not another turtle." In fact, I was quite skeptical because of the Darth Vader sunglasses.

However, a day or so later I picked up the manual and began to read it. The image of a trivial toy robot slowly disappeared; as I read, it became clear that *Ernie* has



FIG. 1

designed-in features that I had not previously encountered in a product of his class. Let's look at *Ernie* in terms of both hardware and software.

Ernie's hardware

Figure 2 shows a block diagram of the *Ernie* system. Keep in mind that *Ernie* is not *Hero 2000*, but, basically, a turtle. The CPU is a CMOS version of the popular 6502. That makes it easy to design custom programs for *Ernie* if you own an Apple II or a Commodore 64/128.

Storage is provided by 2K of static CMOS RAM. It is there that the programs you write and send to *Ernie* will be stored. The operating system that interprets your commands is contained in a 4K EPROM. I'll explain what's in the EPROM in the discussion of software later.

Motion is provided by two servo drive wheels. The servo mechanism is based on a small DC motor, and feedback to the controller (the microprocessor) is through an optical encoder wheel much like the ones described here in the September 1986 column. You can actually tell the microprocessor how

far to move each motor, and it will take care of everything.

A rover needs more than a brain and some muscle to move around in our rather unpredictable world, so *Ernie* comes with a built-in sonar rangefinder. The sunglasses function as a bezel for the ultrasonic transducers. After discovering why the sunglasses are necessary, I never again winced at *Ernie's* style of dressing.

Micromega has not neglected to include some entertainment value with *Ernie*. Whereas the Rhino *Scorpion* has a built-in tone generator and LED "eyes," *Ernie* is much more sophisticated. He sports an allophone-based speech

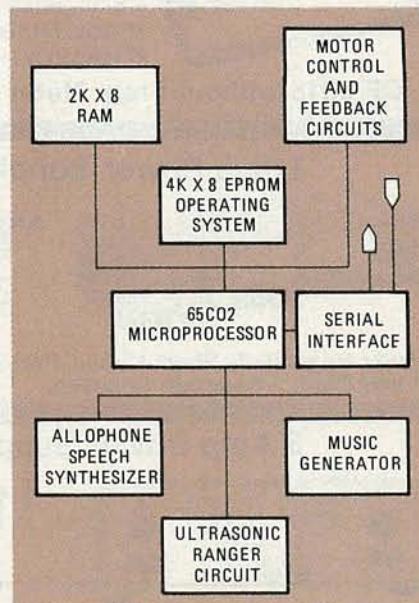


FIG. 2

synthesizer. (An allophone is a short sound segment that when combined with other allophones can be used to pronounce words in any language.) Although no

provision has been made for a text-to-speech algorithm (which would convert ASCII-encoded text data into recognizable sounds), the manual does an excellent job of introducing the reader to the use of the synthesizer. A music synthesizer is also included.

Now for the important part. Sure, the CPU, memory, and the extra goodies are nice, but there is one aspect of *Ernie I* haven't seen in a rover before. *Ernie* has a built-in rechargeable battery pack. The machine comes with a portable charger that allows you to charge *Ernie's* batteries as simply as charging a calculator. No power-supply wires need be connected during operation (which can last for about two hours on a full charge).

Ernie depends on you for ideas. You write a program in his native language and download it to him. That is done over a simple TTL-level serial interface. If you have a computer with a ± 12 -volt RS-232 interface, use a pair of 1488 and 1489 IC's to convert those voltages to *Ernie*-compatible levels.

As you can see from our brief description, *Ernie* has the hardware to do some serious experiments. If you're a beginner and

Ernie's software

Built-in software includes a random roam program, a demo program, and a language interpreter. Upon power-up *Ernie* awaits a command. An action is initiated by pressing either of two microswitches located on his base. Pressing the left switch puts him into a "receive file" mode wherein a user-written program can be downloaded from another source.

The language interpreter, of


course is what you use to write control programs for *Ernie*. Programs consist of sentences and paragraphs. Each sentence is composed of special command words that *Ernie* interprets and acts on. Table 1 lists *Ernie's* vocabulary. The language itself is called *Ernie's Mother*. Programs are written on your PC, compiled there, and then transmitted to the robot in special codes. *Ernie* comes with a special disk that aids the compiling and transmission process. The ability

TABLE 1—ERNIE COMMANDS

COMMANDS

Forward	Exit
Reverse	Again
Turnleft	Stop
Turnright	Look
Lookleft	Monitor
Lookright	Original
Wait	Sonaroff
Jump To	Sonaron
If Sonar	AvoidB
If Random	AvoidL
Else	AvoidR
Endif	AvoidS
Loop	Spk
Endloop	Auto
Do	M
	M2

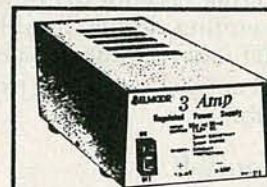feel that your lack of experience would hamper your use of *Ernie*, I've got a pleasant surprise for you. The *Ernie* technical manual not only describes the robot from top to bottom, but it acts as a tutorial introduction to the field of robotics. Each subsystem—from the motors to the speech synthesizer—is described in detail from a beginner's point of view.



3 Amp Regulated Power Supply BM-510


Specification: input voltage: 115 Vac. Output voltage: 13.8 VDC. Current: 3 amp constant. 5 amp surge, short circuit protection.

Special Sale **\$14.95**
Reg Price \$23.40



VOM Multitester
20,000 Ohms per volt DC

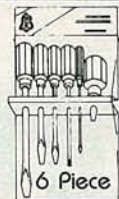Special Sale **\$15.95** Reg. \$22.70
BM-313



6 Piece
Cushion Grip
Screwdriver Set
Reg. Price \$4.50

Super Special **\$1.70** EA. SET
MIN. 5 PA-109



21 PC. PRECISION
SCREW DRIVER SET

COMPLETE w/5 SIZES
PRECISION WRENCHES, 2 CROSSPOINT
SCREWDRIVERS 3 HEX KEY WRENCHES,
5 HEX NUT DRIVERS, 6 SLOT
SCREWDRIVERS, & TORX KEY

Reg. \$9.38

SALE **\$5.95** BM-353



MINI
STEREO
HEADPHONE

\$4.99

BM-73

TRIPLERS:

T-184 equivalent to ECG-523 1-9 10 up
T-53 equivalent to ECG 526 **\$9.95** **\$8.99**
T-45 equivalent to ECG 500A

GE, Magnavox,
Sony, Sears
CALL FOR NUMBERS

ALL SAFETY CAPACITORS

10 FOR \$35.00

TRANSISTORS

A-41.....SANYO 1308K.....1-49 **1.79** 50-99 **1.59** 100-up **1.45**
A-15.....TOSHIBA 1172B.....1-25 **2.65** 26-49 **2.25** 50-up **2.00**

COAXIAL CABLE

Copper Braid Shield

Add \$5.00 per roll shipping

RG 59U.....1000'.....Reg. \$82.00 **SALE \$44.00**
RG 6U.....500'.....Reg. \$55.10.....**SALE \$35.95**

ESI

Electronic Parts & Accessories

3820 14th Avenue, Brooklyn, NY 11218

a division of ALPHA-KENCO INC.
SYSTEMS & ELECTRONICS

ORDER BY PHONE:

800-645-4720

(718)436-9700



call for
our free
104 Page
CATALOG

CIRCLE 199 ON FREE INFORMATION CARD

OCTOBER 1986

83

Learn micro-processing with the new
MICRO-PROFESSOR 1P



Students, engineers or technicians—
upgrade your micro-processing skills
with the new Micro-Professor 1P.

The MPF-1P features:

- extensive software support
- more built-in memory
- improved keyboard
- larger display

Three tutorial guides help cover all
capabilities. The ideal training tool!
MPF-1P will deliver you into the growing
world of micro-processing. Invest now!

Plus—FREE GIFT Only **\$199.95**

Check this box for FREE
Z-80 Microprocessor
Programming and
Interfacing textbook when
you order within 7 days.
\$16.95 value. (Include
\$7.50 postage &
handling)

ETRONIX

Dept. RE 1086
5326 9th Ave. N.E.
Seattle, WA 98105-3617

For immediate action call TOLL FREE:

1-800-426-1044

Full money back guarantee.
Pictured with optional printer.



CIRCLE 111 ON FREE INFORMATION CARD

to write programs in *Ernie's* high-level language makes it easier to understand and modify those programs later.

As you can see in Table 1, *Ernie* has many typical commands for motion. In addition, there are conditional statements that check the sensors and act according to the presence or absence of a signal.

Ernie has much to offer the experimenter. The robot comes completely assembled and ready to go. The host software supports several popular personal computers, and more are on the way. The price for *Ernie* had not been fixed as of this writing, but it should be in the \$500 range. Contact Micro-mega directly for current price and availability.

Build it yourself

For those die-hards in the group, let's now revisit the motion platform mentioned earlier. Outside of the base and the motor controls, no electronic control circuits were presented. Since that discussion I've been busy adding to the system.

Figure 3 is a block diagram of the

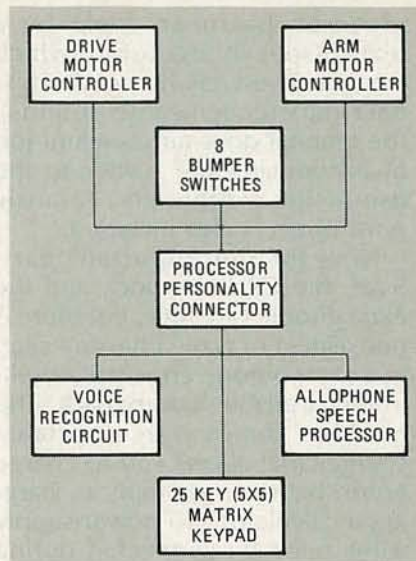


FIG. 3

platform and the mechanical configuration as it now exists. The control circuitry is mounted on perfboard and the assembly is mounted on a second platform. After much investigation, I decided not to design the robot using any particular microprocessor. Instead, a "personality pack" plugs
continued on page 91

HAMEG
Instruments

Scope and new
Modular System 8000
to make a compact test set-up

HAMEG's range of oscilloscopes is complemented by a growing number of measuring and generator modules, fitting in a matching mainframe with power supply.

2-year
warranty



HAMEG Inc.
88-90 Harbor Road · Port Washington N.Y. 11050
Phone (516) 883.3837 · TWX (510) 223.0889

SERVICE CLINIC



JACK DARR,
SERVICE EDITOR

The screwdriver serviceman

THERE ARE SO MANY DIFFERENT TYPES of screws and other fasteners in use today that you can never find the right screwdriver, nutdriver, etc., when you need it. So you have to maintain a collection of fancy expensive tools, like those shown in Fig. 1, that are seldom used, but indispensable when you need them.

However, as bad as things are now, they're much better than they used to be. In the (not necessarily good) old days, there were Phillips, Reed, and Prince screw heads, and several other types that showed up mostly on European sets. When you took the cover off a foreign set, you never knew what kind of arcane fasteners you would find. The Prince type has a crosspoint like the Phillips, but with smaller lands.

Fortunately, things are better today because parts of all kinds are much more standardized than they used to be. So we can often get by with only a few standard straight blade screwdrivers, a few Phillips cross-point screwdrivers, and a 1/4-inch nutdriver.

Loose screws

I used to bring a bottle of screws on every service call. Then, if I ran into a set with oddball heads, I replaced all the non-standard screws with standard ones. (You can see that I was planning on being the next serviceman to work on that set!)

I'll never forget the TV that had four bolts in the bottom. After taking them out, the set remained as firmly fixed as before! I couldn't figure out what was going on until finally I woke up and found two

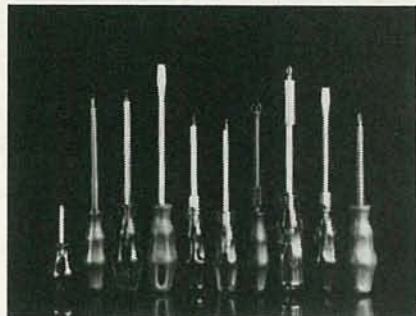


FIG. 1

more bolts that I hadn't seen! They were shipping bolts that were used to hold the chassis firmly in place during transit, and they should have been removed when the set was installed. I removed them and the chassis slid right out.

The good old days are gone, and it's all right with me if they never come back! I remember the days when my tube caddy was full of wrench sets and assorted thingamajigs for removing oddball fasteners. And I'm happy now that my toolbox is not so full of tools I hardly ever use. R-E

SERVICE QUESTIONS

CAN'T TUNE LOWER CHANNELS

I've been working on a Toshiba TV, model C998, that has a scanning tuner and a memory. The problem is that the higher channels—7 and up—can be tuned, but not the lower ones. Any help you can give would be deeply appreciated.—F.K., Port Hope, MI

It's times like these that make

me understand why technicians are leaving the repair field by the droves. As television technology becomes more and more complex, the information that we have to work with becomes less and less helpful.

According to *Sams Photofact* for your set, the tuner has two input terminals (VHF high and VHF low). But the tuner schematic doesn't take us any further than that, so that we can see how the two inputs are used. However, we must conclude that each terminal is turned on by a voltage being applied to it at the right time.

If that is taking place, it's safe to assume that some other event is failing to occur in the tuner. But if it's not, you'll have to work your way back to the band-select switch and the control unit (IC101) to find what's happening in an earlier stage.

READER INPUT

Perhaps your readers might be interested in hearing about an experience we had at our Magnavox service center. We've had a number of sets come in recently that had repeated failures in various sweep-circuit components of several E34018 chassis.

On one set, we noticed that the flyback was running hot. After plenty of "hair pulling," we discovered that the picture tube required a higher G2 setting on our CRT tester. When we installed a new tube, the chassis ran much cooler.

We've spoken to the factory technicians who said that it was a new one to them, but that they would look into it.—Thanks to Chris Milda, Kirksville, MO

SATELLITE TV



BOB COOPER, JR.,
SATELLITE-TV EDITOR

The Ku change

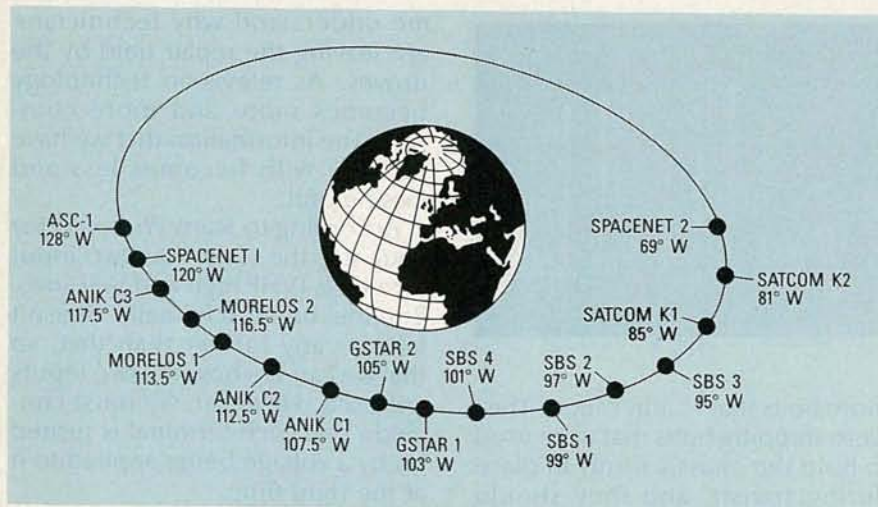


FIG. 1

THE NEW 11/12-GHZ OR KU-BAND SATELLITES have had marginal impact on the video field to date. However, some people firmly believe that, as the Clarke Orbit Belt fills up, the next satellite revolution will take place on the higher frequencies. And the revolution has already begun; as you can see in Fig. 1, there are at least 15 satellites offering Ku-band service. But the Ku revolution is not going as smoothly as originally hoped; let's see why that is so.

The original C-band (3.7–4.2-GHz) satellites were launched in spite of the protests of AT&T and other terrestrial users of the C band. The Bell system's point-to-point microwave network covers the entire North American continent and is concentrated around major metropolitan areas. So there are many locations, in and around big cities, where you cannot install a C-band dish system without experiencing interference from signals originating from the

Bell system's terrestrial communications network on C-band satellite channels.

Special filters and traps are available to reduce or eliminate that type of interference, but currently-available traps and filters leave much to be desired. The point is that the C band is not the ideal part of the spectrum to transmit weak signals back to Earth.

The Ku-band frequencies were reserved from the start for satellite-to-earth transmissions. There are actually two separate bands, both residing in the 11- to 12-GHz range. One is for something called "fixed service," which we won't discuss here; the other has been slated by the FCC for DBS (Direct Broadcast Satellite) service, which is the service we're interested in. Without interference from AT&T's terrestrial microwave sources in those two 500-MHz-wide bands, it is unlikely that there will be problems with those bands in and around metropolitan areas.

Currently there are only a few terrestrial users of those bands. They have been given a few years to move to a new band, but even today they operate in only a few locations, such as the Los Angeles basin.

Interested in TVRO?

For nearly two years Bob Cooper has provided a no-charge kit of printed materials that describes the challenges of and opportunities in selling TVRO systems today. With the present intense interest in scrambling systems, Coop's CSD has made available a new no-charge service.

The SCRAMBLE FAX hotline is a 24-hour-per-day telephone service that provides accurate, detailed, and hard-to-find facts concerning the changeover to scrambling in the satellite communications industry. Information describing satellite receivers tested for scrambling compatibility, sources for authorized descramblers, wholesale rates of scrambling equipment and services—all are provided on the SCRAMBLE FAX hotline. There is no charge for that service, other than your long-distance telephone expenses. Simply dial (305) 771-0575 for a concise and timely three-minute capsule report that covers the latest in scrambling news.

The FCC's original plan, which was formulated in 1979, called for satellite transmitter powers of about 230 watts per channel. Had that been technically feasible, dish antennas (on Earth) in the two- to three-foot range would have provided wideband video service. Since the plan was formulated, however, several technological changes have occurred:

- Receivers have become more sensitive, making it possible to receive weaker signals with smaller antennas.
- Attempts to produce satellite

satelliteTVweek

Try us once and you'll know why
we're the best satellite
TV program guide you can buy ...



Request a **free** sample today!

Let us be your guide to better accuracy of weekly listings for
over 100 channels, better movie information, more sports
coverage, financial advice, world news, arts and entertainment.
Let us be your guide to world-wide entertainment.

Fill out this coupon to receive your free copy of Satellite TV Week.

satelliteTVweek

Please enter my subscription order today.

2 years (104 issues) \$89 1 year (52 issues) \$48

1 year Alaska, Hawaii, Puerto Rico, Mexico, Canada \$100 US

Payment enclosed Please advise foreign rates

Visa MasterCard Exp. Date _____

Card No. _____

Signature _____

Send my free sample today!

NAME _____

ADDRESS _____

CITY _____

STATE _____ ZIP _____

TELEPHONE (_____) _____

Mail this coupon to **SATELLITE TV WEEK**, P.O. Box 308, Fortuna, CA 95540, or
for immediate service, call **TOLL FREE 800:358-9997 (US)/800:556-8787 (CA)/707:725-2476 (Others)**.

H2502

CIRCLE 186 ON FREE INFORMATION CARD

transmitters at the 230-watt power level have failed.

Currently the only time-tested Ku-band transmitters operating on satellites can generate output powers of only 20 to 50 watts. That works out to be 6 to 8 dB less power than had been suggested for Ku-band service. Some of that shortfall can be compensated for by the improved receivers that are available today—they're much better than those that were available in 1979. The rest can only be

made up with larger antennas that offer greater gain.

RCA and Ku

RCA, which pioneered the explosion of C-band services in the mid 1970's by launching a pair of 24-channel satellites for domestic use, has now launched a pair of 50-watt Ku-band satellites (Ku-1 and Ku-2). They are presently the most powerful satellites in orbit that offer commercial transponders for lease on the Ku band. Many of the

transponders on the RCA birds have already been spoken for by the established cable programmers. And HBO is planning a partnership arrangement with RCA for the third satellite in this series, Ku-3.

So there is clearly much interest in the Ku band and the supposed advantages of shorter wavelengths. But, for all of the apparent advantages (mainly, smaller antennas and greater utility in metropolitan areas), there are some serious disadvantages as well. Rain is one. Moisture in the air, at either the uplink site or at any downlink site, can cause significant degradation of any passing signal. In a two-inch-per-hour rainstorm, losses of as much as 10 dB are possible for receiving sites with low "look" angles.

In 1978 Holiday Inn was a C-band pioneer; they installed terminals at hundreds of motels coast to coast. Now they are replacing the C-band terminals with 4.5-meter (that's about 14-3/4 feet!) Ku-band terminals, and are broadcasting a new five-channel TV service into their franchised and wholly-owned motels. Many of the 4.5-meter Ku-band dishes are actually larger than the C-band dishes they are replacing. Why is that the case, since Ku band is supposed to allow smaller antennas?

First of all, Holiday Inn is using a 20-watt (per channel) satellite; that's an automatic penalty of 4 dB, (compared with RCA's 50-watt satellites). Next, Holiday Inn's engineers are convinced that losses due to rain and heavy fogs will be severe, so they want as much reserve gain in their systems as possible to prevent loss of signal at any motel.

Years ago the careful planner of a small dish system always gave consideration to something called margin, extra gain simply tucked away in the closet to be used in the event of a rainy day (pun intended). A typical margin was 3 dB. You could build in margin by selecting a larger antenna than what was required for normal, clear-sky reception. The problem is that, on the Ku band, 3 dB will doubtless prove inadequate for many locations; especially those where heavy rains are possible.

R-E

SCRAMBLE-FAX SCRAMBLE-FAX

from Bob Cooper

IF satellite scrambling is important to you, here is a single source of timely, confidential information of great value; SCRAMBLE-FAX. Bob Cooper is routinely gathering all of the important scrambling information (who, what, when, where and how) and compiling it in printed form in an important newsletter called *SCRAMBLE-FAX tm*. Sources for pirate decoders, reports on attempts to 'beat the system', full lists of who is scrambling, how and when. Each issue of **SCRAMBLE-FAX** is timely and new; but, each issue is a detailed encyclopedia of scrambling information and totally complete.

REPORTS on M/A-Com efforts to shut down pirate units, exporting of bootleg descramblers outside of the USA, complete listings of all (37+) channels now scrambling and those planning to scramble. The activities of DESug, the DES Users Group, and their progress on 'breaking' the Videocipher 'code', modifying receivers to accept Videocipher and much-much more.



WESTAR Communications/Westcom, the Toronto area alleged manufacturer of 'pirate decoders' for HBO/Showtime and other Videocipher type scrambled services reportedly has been sold to a new group of investors; all Canadian. The firm has been offering their pirate-type decoder unit for \$500 (US) for several weeks claiming it decodes all Videocipher scrambled video plus audio signals. Attempts to locate the firm other than through their 800 telephone number (1-800/265-5675) typically meet with failure and the firm is quick to explain that it would be inappropriate for them to identify their actual street address location (SCRAMBLE-FAX suggests you try 504 Troquois Shore, Oakville, Ontario; and 416/842-2877 as their non-800 telco).

EACH issue of SCRAMBLE-FAX is sent to you via AIR-mail the very day your order is entered. Simply call 305/771-0505 to order your copy (have VISA or Mastercharge card handy) or write for your copy enclosing payment for \$10 (US funds) to the address shown below. PLUS — each issue is 'supported' by a SCRAMBLE-FAX 'Hotline' telephone updating service.

DIAL 305/771-0575 anytime for a complete update on the status of scrambling. 'Hotline' recorded reports are provided by Bob Cooper as an 'instant update' to SCRAMBLE-FAX and carry fast-breaking news items of interest to the scrambling scene. But have your notebook and pen handy; each 'Hotline' report contains many telephone numbers and addresses you will want to retain!

SCRAMBLE-FAX by Bob Cooper

305/771-0505 or for free 'Hotline' service, 305/771-0575. To order by mail, send check/money order or enclose VISA/Mastercharge number and expiration date: CSD Magazine, P.O. Box 100858, Ft. Lauderdale, Fl. 33310

COMPUTER DIGEST

VOL. 3 NO. 10 October 1986

A NEW KIND OF MAGAZINE FOR ELECTRONICS PROFESSIONALS

OKIDATA UPGRADE

Breathing New Life Into An Old Workhorse

A
GERNSBACK
PUBLICATION



GRAPHIC BIOFEEDBACK MONITOR

Using Your Computer to Control Emotions

TVRO ANTENNA POINTER

Taking Out The Guesswork

CONTENTS

Vol. 3 No. 10

October 1986

6 Graphic Biofeedback Monitor

You can actually train yourself to be more composed and at peace. Using your computer, a color monitor and this device, it's easy.

Ronald A. Peterson

10 TVRO Antenna Pointer

Here's how to use your computer to pinpoint your dish to bring in those satellites. It saves a lot of arithmetic!

Elery C. Smith, Jr.

12 Okidata Upgrade

Got an Okidata printer? Wish you had a bigger, better one? Here's how you can quickly, easily, and at low cost, get more performance.


Elliott S. Kanter

3 Editorial

4 Letters

4 Computer Products

5 Software Review

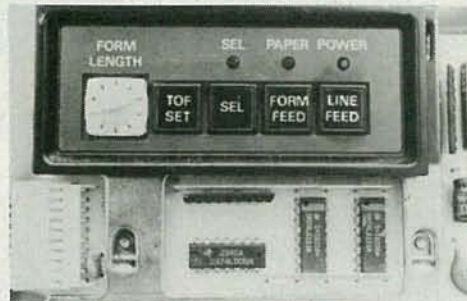

See Page 6



See Page 12

ON THE COVER

That big, beautiful OKDATA® printer you see on our cover may be little more than a gleam in your eye, but until you can afford to replace the one you have, you can upgrade to get more and better performance. See page 12.

COMING NEXT MONTH

We've got an absolutely dynamite issue coming up in November! We're kicking off with a story on streaming tape for computer backup, and following that with an easy-to-build protocol converter. Then we've got a handy-dandy program for helping design Schmitt triggers, and another program that gives you all the TV channel frequencies plus a lot more. And as a wrap-up, you'll find an excellent piece on retrofitting printers. Of course, we'll still have our Editorial, our Letters, and our Computer Products. It's going to be a winner, so don't miss it!



EDITORIAL

The changing face of computing

■At one time, a "memory" unit consisted of tiny ferrite beads strung on three wires. Today, things have advanced radically. And the room-sized computer that required a controlled temperature and raised floorboards has gone the way of the Reo, the Franklin, the Cord and the Tucker. Today's personal computer would appear to have reached a zenith, and the small "z" is intended.

But recently, we've seen advances in our own state-of-the-art technology that predict even greater things yet to come. Surface Acoustic Wave technology, optical disks, and advanced levels of miniaturization are aborning. If we could pull aside the veil, we'd see wonders as yet hidden and we can but speculate on what those might be.

Tomorrow's computer miracles are already here. We've already got fluorescent flat screens, we've got bi-directional high-speed printers, and scientifically-designed keyboards that allow you to almost think with your fingers. And our computers operate faster than the human mind, and accept your input at a faster rate than you can type it in.

Which reveals almost instantly what the weakest link in computing is... It's us, the human element that slows computing from what it could be to what it is. Our next great advance in computing is to design a new type of human. We should have *four* eyes instead of just two. In that way, those of us that have to look at the keyboard while inputting would be able to keep two eyes on the keys and two eyes on the screen. And since the typical computer keyboard has 83 keys, we should develop hands with at least 42 fingers on each one. In that way, one finger could rest on a separate key and the need to move the fingers while typing would be obviated. Imagine how that would increase your speed!

While I'm on the subject, we should have an RS-232 jack at the backs of our skulls so we could do away with the monitor entirely. When you're plugged into your computer, all you'd be able to see would be the screen, and you'd be able to do it without using a separate monitor.

And finally, I want to build an illuminated sign for the top of my monitor, that when it hears the words "DINNER'S READY" it automatically lights up and says "IN A MINUTE!"

Yes, some great, new advances are coming in the world of computers. I just don't believe that I've outlined any of them.



Byron G. Wels
Editor

ComputerDigest is published monthly as an insert in Radio-Electronics magazine by Gernsback Publications, Inc., 500-B Bi-County Blvd., Farmingdale, N.Y. 11735. Second-Class Postage Paid at New York, N.Y. and additional mailing offices. Copyright © 1986 Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

COMPUTER DIGEST

M. Harvey Gernsback,
editor-in-chief, emeritus

Larry Steckler,
EHF, CET: publisher & editor in chief

Art Kleiman,
editorial director
Byron G. Wels,
editor

Brian C. Fenton,
managing editor

Carl Laron,
associate editor

Robert A. Young,
assistant editor

Ruby M. Yee,
production director

Karen Tucker,
production advertising

Robert A. W. Lowndes,
production associate

Geoffrey S. Weil,
production assistant

Andre Duzant,
technical illustrator

Jacqueline P. Cheeseboro
circulation director

Arline R. Fishman,
advertising director

Computer Digest
Gernsback Publications, Inc.

Executive offices
500-B Bi-County Blvd.,
Farmingdale, NY 11735
516-293-3000

President: Larry Steckler
Vice President: Cathy Steckler

ADVERTISING SALES 516-293-3000

Larry Steckler
Publisher

NATIONAL SALES

Joe Shere
1507 Bonnie Doone Terrace
Corona Del Mar, CA 92625
714-760-8967

LETTERS

The Cost of Change

I bought a new computer and find that my old serial printer won't work with it. An interface would cost almost as much as a used parallel printer. Could any of your readers use my old printer? It's letter quality, and I'd like to get a hundred bucks plus shipping costs.—P.T., Trenton, NJ.

We never meant the Letters Column to be "swap shop," but we're willing to help out.

Errors

Whenever I want to build a project in a magazine, I always wait a couple of months to see if there are going to be any corrections. Considering the number of projects you publish, there are relatively few mistakes! —R. S., Sioux Falls, SD.

Thank you! We thought we

made a mistake once, but we were wrong!

Help!

I'm desperately looking for a program called "Computer Novel Construction Set" from Hayden Software. It's no longer being produced, and I'm willing to pay for it, or a copy of it. Can anybody help me?—L.S., Massapequa, NY.

If you can help, write to ComputerDigest.

Caveat Emptor!

If I buy a piece of computer equipment am I better off to buy something expensive or something far-less costly and upgrade it by putting in add-ons? I am a capable electronics technician but was wondering about the economics.—F.L., Ft. Lauderdale, FL.

It's hard to say. Usually we advise people to buy the best they can afford, thereby making their first expense their last. But if you construct your own, work carefully and install with equal care, you have the advantage of choosing your own times and costs.

Wants A Book

I read in a recent editorial that **ComputerDigest** is now three years old. Are you planning a book of "The Best Articles?"—R.S., Atlanta, GA.

Not yet.

Goof-Off


I'm trying to stall a science project for school and told the teacher I had written to you for information. So what's the value of a resistor with three red bands?—M.P., Portland, RI.

2.2K. Now get to work.

COMPUTER PRODUCTS

For more details use the free information card inside the back cover

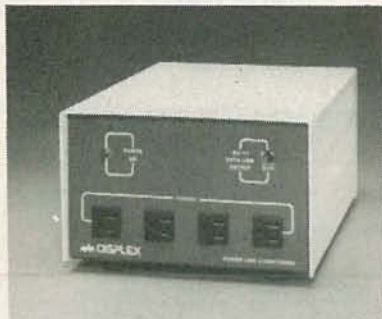LINE CONDITIONER, features a surge-protected RJ-11 data link, in addition to a plug-in AC power-surge suppressor, protecting sensitive electronics equipment against voltage spikes and surges, as well as virtually eliminating common-and-normal-



CIRCLE 18 ON FREE INFORMATION CARD

mode noise. There is a noise rejection of 130 dB common-mode and 80 dB normal-mode.

A field-replaceable power-line surge arrester is plugged into the unit and isolates itself if damaged by high-energy strikes. An LED status light continuously monitors its condition. The unit features better than 95% efficiency, potential to handle inrush current up to 10x rating, and multiple service outlets.

Line-conditioner units are available in 500VA, 1, 2, 3k VA power ratings, with end-user prices ranging from \$395.00 to \$935.00.—**Displex, Inc.**, 1 Alexander Place, Glen Cove, NY 11542.

GRAPHIC TABLET, the model *GT 1510*, is compatible with every personal computer available today; it interfaces easily with PC's when it is used in conjunction with CAD software.

Included with the model *GT 1510* are a pen and puck. It is the only tablet to offer the following as standard features: a relegendable menu-strip area with strips for AUOTCAD and

blank for customized CAD instructions. In addition, it comes with a power supply and all cable connections.



CIRCLE 19 ON FREE INFORMATION CARD

The model *GT 1510* Graphic Tablet, complete with cursor puck and pen, is priced at \$795.00.—**Cherry Electrical Products Corporation**, 3600 Sunset Avenue, Waukegan, IL 60087.

SOFTWARE REVIEW

How to back up a protected disk...

■As long as there were newcomers to personal computing the distributors of the most popular programs justified the prices for their software by the myth of *software pirates*, who made millions of unpaid for and unauthorized copies. Although it was the best of times for software sales—creating multimillionaires overnight—the distributors went to great lengths to prevent unauthorized backups, “unauthorized” meaning a backup for the user who might have just plunked down \$300 to \$500 for the program. Now, software sales are tough to come by. There are at least five decent versions of every kind of program, and with competition much of the top-selling software is now available in unprotected versions. Meanwhile, thousands of users are stuck with unbackable software, dreading the day when the “original” disk actually wears out (yes, oxide wears), while those who have converted to hard disk find the protected software won’t run on a hard disk at all, or requires a “key” disk to be in drive A: (Requiring a key disk eliminates the advantage of a hard disk, as well as wearing the unbackable original.) Either way, the protected programs provide limited use, and the distributors won’t swap the protected software for the unprotected version.

A low-cost solution to the problem of older, protected software is a program called COPYIIPC, which can back up either protected disks or protected working disks, or it can bypass hard disk restrictions. A *protected working disk* is an uncopiable working disk that was created from the distribution (original) program disk by an *install* program. Either the working copy contains the DOS and is self-booting (but cannot be backed up), or it does not contain the DOS and must be used in Drive B: while the original distribution disk in Drive A: functions as a *key*. Often, the install program permits an extra backup working disk to be made from the original, but the original disk cannot be run by itself.

There are two kinds of hard disk restrictions. One precludes the program running from a hard disk even if the user can copy it to the hard disk. The other requires the distribution disk to be in Drive A: as the “key.” If your computer has the usual one floppy and hard disk configuration, it’s obvious that you can’t write to a floppy data disk.

COPYIIPC which resolves the problems, consists of six utilities. Only four are used for making backups and by-passing hard disk restrictions. One of the others is a

SETUP program which installs DOS on the disk so it can be made self-booting. (But the DOS must be an unmodified version.) The other is BULKERAS which electronically wipes a disk by destroying all data, leaving only the track formatting.

The backup utilities consist of the main COPYIIPC program itself, a special version for the IBM-PC-Jr, NOGARD, which backs up software that resists the normal COPYIIPC backup procedure, and NOKEY, which is loaded into RAM prior to a program from a hard disk and eliminates the need for a “key” disk in Drive A:.

COPYIIPC needs a minimum of 64K RAM but it will use all available memory to speed things. It will back up either single or double sided disks as written. It’s equal to the DOS’s DISCOPY and DISCOMP utilities combined. The COPYIIPC program also tests the speed of the disk drives used for making backups because even with the drives running at the normal tolerance of 200 rpm backups should be made from the faster drive to the slower (you can run out of disk space if copying from a slower to a faster drive). While the easiest procedure uses two drives, backups can be made using one drive by following the screen prompts on when to swap disks.

COPYIIPC cannot make a functional backup of certain programs, although it might appear the backup is successful the program won’t run from the copy. However, it will usually indicate this problem and prompt for the user to run the NOGUARD utility, which uses both the original distribution disk and the non-functional backup to create a functional unprotected copy that can even be installed on a hard disk.

Users of hard disks having several hundred dollars invested in software that won’t run unless the original distribution disk is installed in drive A: as a “key” will find the most valuable feature of COPYIIPC to be the NOKEY utility, which is loaded into RAM just before the main program. NOKEY “tricks” the restricted program into believing the key disk really is in drive A: Drive A: cycles once and as far as the hard disk is concerned the key disk really is in drive A: However, drive A: is empty and available for a data disk, a disk file source, or whatever.

Although COPYIIPC backs up the distribution disk and frees the hard disk restrictions of many commonly-used programs, it doesn’t work for everything; at least that’s what’s implied in the documentation. (Since our collection of software is more or less conventional, everything we tried could be backed up or used on a hard disk.) Central Point Software supplies a long list of some 150 popular programs with which users have reported success using COPYIIPC. If you have software that isn’t on the list the best thing to do is phone the distributor direct at (503) 244-5782.

COPYIIPC is available for \$39.95 (plus \$3.00 shipping and handling) direct from Central Point Software, Inc., 9700 SW Capitol Highway, #100, Portland, OR 97219. It runs on the IBM PC, XT, AT and PCjr, the Compaq, the Columbia, the Corona, and some other very compatible compatibles. If you’re not certain it will run on your computer, call the distributor before you buy.



CIRCLE 17 ON FREE INFORMATION CARD

GRAPHIC BIOFEEDBACK MONITOR

Here's a simple and interesting experiment...

Ronald A. Peterson

■Biofeedback is a fascinating area of exploration in that it allows you to mechanically produce a physical reaction that is associated with a change in your thoughts. Perhaps some of the fascination comes from the possibility that with a subtle enough device one could draw a line on a computer screen or direct a robot to move an object. Such an advance would give us the ultimate in remote control and would provide an end to many excuses for not doing things, since the

thought would be sufficient to trigger the action.

This article describes the interfacing of a simple biofeedback device to a Commodore 64 computer to provide a graphic display of your state of mental relaxation. The most easily measured property of your body which can be linked to changes in state of mind

```
1 REM---BIOFEEDBACK ROUTINES
2 REM---RE DECEMBER 5,1985
3 REM--- RONALD PETERSON
10 REM---LOAD MACHINE ROUTINES
20 FOR I=4096 TO 4165
30 READ A:POKEI,A:CK=CK+A
40 NEXT I
50 FOR I=12288 TO 12386
60 READ A:POKEI,A:CK=CK+A
70 NEXT I
80 FOR I=12544 TO 12557
90 READ A:POKEI,A:CK=CK+A
100 NEXT I
110 IF CK=22442 THEN 120
115 PRINT"ERROR IN DATA STATEMENTS"
116 STOP
120 REM---SET FREQUENCY
130 SYS4096
140 PRINTPEEK(8192)+256*PEEK(8193)
150 FORI=1TO100:NEXT
160 PRINT "SET TO 50-->";
170 GETA#:IFA#<>" THEN 200
180 GOTO130
190 REM---CLEAR SCREEN
200 POKE53280,0:POKE53281,0
210 FOR I=1024 TO 2023
215 POKEI,160:NEXT I
220 FOR I=55296 TO 56295
225 POKEI,0:NEXT I
230 REM---UPDATE GRAPHICS
240 SYS4096
250 Q=PEEK(8192)+256*PEEK(8193)
260 CL=CL+1:CL=CLAND15:POKE12434,CL
270 FOR J=1 TO 3*Q:NEXT
280 SYS12288
290 GOTO 240
295 REM---READ JOYSTICK PORT
300 DATA 120, 169, 0, 141
310 DATA 0, 32, 141, 1
320 DATA 32, 173, 0, 220
330 DATA 41, 1, 240, 249
340 DATA 173, 0, 220, 41
350 DATA 1, 208, 249, 32
360 DATA 64, 16, 173, 0
370 DATA 220, 41, 1, 240
380 DATA 246, 32, 64, 16
390 DATA 173, 0, 220, 41
400 DATA 1, 208, 246, 88
410 DATA 96, 173, 0, 32
420 DATA 24, 105, 1, 141
430 DATA 0, 32, 173, 1
440 DATA 32, 105, 0, 141
450 DATA 1, 32, 173, 0
460 DATA 220, 41, 1, 240
470 DATA 232, 96
480 REM---DISPLAY ROUTINES
490 DATA 169, 0, 133, 251
500 DATA 169, 216, 133, 252
510 DATA 169, 0, 141, 144
520 DATA 48, 169, 40, 141
530 DATA 145, 48, 162, 12
540 DATA 173, 146, 48, 172
550 DATA 144, 48, 234, 234
560 DATA 145, 251, 234, 200
570 DATA 204, 145, 48, 208
580 DATA 247, 32, 0, 49
590 DATA 238, 146, 48, 238
600 DATA 144, 48, 206, 145
610 DATA 48, 202, 16, 224
620 DATA 234, 234, 234, 206
630 DATA 144, 48, 206, 144
640 DATA 48, 238, 145, 48
650 DATA 238, 145, 48, 162
660 DATA 12, 173, 146, 48
670 DATA 172, 144, 48, 145
680 DATA 251, 200, 204, 145
690 DATA 48, 208, 248, 32
700 DATA 0, 49, 238, 146
710 DATA 48, 206, 144, 48
720 DATA 238, 145, 48, 202
730 DATA 16, 227, 96
740 REM---SUBROUTINE
750 DATA 165, 251, 24, 105
760 DATA 40, 133, 251, 165
770 DATA 252, 105, 0, 133
780 DATA 252, 96
```

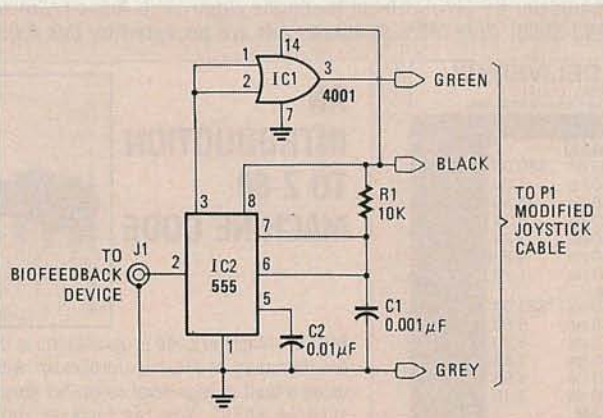



Fig. 1—SCHEMATIC DIAGRAM of interface device between joystick port and the biofeedback monitoring device.

is the resistance of your skin. To measure skin resistance we will use a biofeedback device made by Radio Shack (catalog #63-675, \$12.95) The output of this device will be connected through a simple interface circuit to the joystick port on the computer and used to control the speed at which a graphic pattern changes.

To begin, build the circuit shown in figure 1. Since circuit speed is not a problem and there are no dangerous voltages, the construction technique is not critical. Building the circuit on perfboard or an experimenters socket is fine. A 1/8-inch miniature phone plug is used to connect the earplug output from the biofeedback device to the circuit. A joystick extension cable is modified by cutting off the end that goes to the joystick in order to connect the circuit to the computer's joystick port. Pay attention to the color coding of the modified cable. (See figure 2.) Improper wiring could short out the five volt power supply in your computer, destroying it!

Next type the program into the computer and Save It BEFORE running it. Since the program uses machine code routines, any error in typing it in could cause the computer to hang up, thus making it necessary to type the program in again. When you run the program the machine code will be loaded into memory and

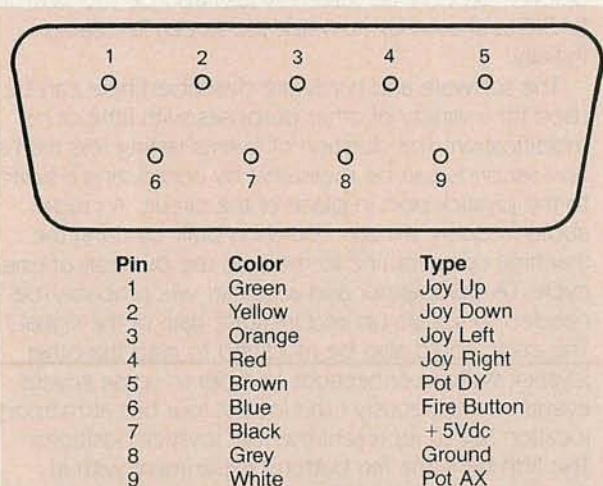


Fig. 2—JOYSTICK PORT pinout diagram for the Commodore. Refer to the text for further clarification.

automatically checked. Examine the DATA statements if an error occurs when it is run. The program can be tested by connecting a joystick to port 2 and running the program while moving the joystick up and down. A message will appear with a number next to it while you move the joystick. Keep moving the stick and hit the space bar on the computer. After a few moments the screen will clear and a graphic pattern will appear. If you do not get the pattern then something is wrong and you should check the program for typing errors.

To make it all work together, first load the program and run it. Then plug the biofeedback device into the circuit and connect the circuit to joystick port 2 on the computer. Next you need to set the frequency of the oscillator in the biofeedback device. It will not oscillate unless it is connected to something so attach it to your fingers and then turn it on and adjust its pitch control until the number next to the message on the computer screen begins to change. When you have a reading in the 50 to 200 range, hold down the space bar to activate the display. The screen will clear and a moving pattern will appear. Then sit back and relax! The speed with which the pattern changes should now alter depending on how relaxed you are. Since the device is sensitive to changes in skin resistance be careful not to move the hand with the electrodes attached to it or you will alter the pattern speed.

How it works


When you are relaxed your breathing slows, your heart slows down and your muscles loosen up. In this state your body doesn't need to burn as much fuel to keep going, and so with the furnaces damped down there is less oil, water and other wastes expelled through your skin. This causes a change in the resistance of your skin and it is this change that can be measured and fed back to your senses with the proper device.

Radio Shack's biofeedback device is essentially a variable frequency pulse generator where the frequency is controlled by resistance. A small current is fed through your skin, amplified, and then used to control the oscillator. The pulse output from the oscillator is fairly sloppy however so it has to be cleaned up before being sent to the computer. The 555 timer is configured as a monostable multivibrator (one-shot flip-flop) to extend the duration of the pulses which are then fed to an inverter made from a NOR gate to further square them up. Power for the circuit is provided by a +5Vdc line from the joystick port. The output of the inverter is fed to a pin on this port which is usually connected to the UP switch on a joystick. Thus each pulse from the biofeedback device is made to look to the computer like a joystick switch opening and closing.

The software contains three fundamental parts. The first is a BASIC routine which provides master control. The second is a machine language subroutine that reads the joystick port and counts the time between pulses. Lines 140 and 250 in the BASIC program read this count from where it is stored in RAM. The third is another machine language routine that draws the colored pattern on the screen. Line 260 in the BASIC

R-E Computer Admart

Rates: Ads are 2 1/4" x 2 7/8". One insertion \$825. Six insertions \$800 each. Twelve insertions \$775. each. Closing date same as regular rate card. Send order with remittance to **Computer Admart**, Radio Electronics Magazine, 500-B Bi-County Blvd., Farmingdale, NY 11735. Direct telephone inquiries to Arline Fishman, area code-516-293-3000. **Only 100% Computer ads are accepted for this Admart.**

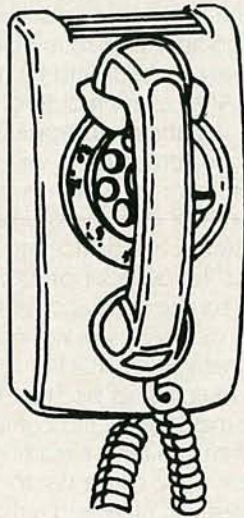

CALL NOW AND RESERVE YOUR SPACE

- 6 x rate \$800.00 per each insertion.
- Reaches 239,312 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads.

Call 516-293-3000 to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: Computer Admart, RADIO-ELECTRONICS, 500-B Bi-County Blvd., Farmingdale, NY 11735.

ICs PROMPT DELIVERY!!!

SAME DAY SHIPPING (USUALLY)
QUANTITY ONE PRICES SHOWN FOR JULY 28, 1986

OUTSIDE OKLAHOMA		NO SALES TAX	
DYNAMIC RAM			
1M	1000Kx1	100 ns	\$70.00
256K	64Kx4	150 ns	4.00
256K	256Kx1	100 ns	5.50
256K	256Kx1	120 ns	3.74
256K	256Kx1	150 ns	2.74
128K	128Kx1	150 ns	4.25
64K	64Kx1	150 ns	1.29
EPROM			
27512	64Kx8	250 ns	\$23.00
27C256	32Kx8	250 ns	6.65
27256	32Kx8	250 ns	5.20
27128	16Kx8	250 ns	3.65
27C64	8Kx8	200 ns	4.55
2764	8Kx8	250 ns	3.40
STATIC RAM			
43256L-12	32Kx8	120 ns	\$35.00
6264LP-15	8Kx8	150 ns	2.94

OPEN 6 1/2 DAYS WE CAN SHIP VIA FED-EX ON SAT


SUNDAYS & HOLIDAYS: SHIPMENT OR DELIVERY, VIA U.S. EXPRESS MAIL

SAT DELIVERY INCLUDED ON FED-EX ORDERS RECEIVED BY: Th: 5:00 AM, Sa: 4:00 AM, Fr: 7:00 AM \$13.2 lbs. MasterCard/VISA or UPS CASH COD **Factory New, Prime Parts** MICROPROCESSORS UNLIMITED, INC. BEGGGS, OK. 74421 (918) 267-4961

Please call for current prices because prices are subject to change. Shipping & insurance extra. Cash discount prices shown. Orders received by 5 PM CST can usually be delivered to you the next morning, via Federal Express Standard Air @ \$6.00, or Priority One @ \$13.00!

CIRCLE 61 ON FREE INFORMATION CARD

COMPUTER MUSIC PROJECTS

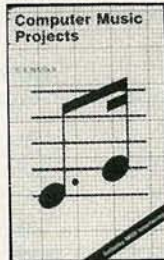

BP173—Computer Music Projects shows how to use your home computer to produce electronic music. Many circuits. Mostly jargon free. Send \$6.95 plus \$1.75 shipping to **ELECTRONIC TECHNOLOGY TODAY INC., PO Box 240, Massapequa Park, New York 11762-0240.**

AN INTRODUCTION TO Z-80 MACHINE CODE



BP152—Machine code programming is direct programming of the microprocessor without using a built-in high-level computer language such as BASIC. You can increase running speeds dramatically by using machine code. Learn how to write your own machine code programs. Some simple demo programs are included. Get your copy by sending \$5.95 plus \$1.00 shipping in the U.S. to **Electronic Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240.**


MICRO INTERFACING CIRCUITS — BOOK 2



BP131—This book is about real-world interfacing including topics such as sound and speech generators, temperature and optical sensors, motor controllers and more. Includes circuit descriptions and background info to aid in using or adapting the circuits to your applications. To order your copy send \$5.75 plus \$1.00 shipping in the U.S. to **Electronic Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240**

program sets the starting color for the pattern every time it is redrawn. Machine language is used here for speed. The pulses from the biofeedback device are at audio frequencies and BASIC is far too slow to count the length of time between pulses. Changing all the

colored bars on the screen would also be too slow in BASIC as shown by how fast the screen is cleared initially.

The software and hardware described here can be used for a variety of other purposes with little or no modification. The duration of events lasting less than a few seconds can be measured by connecting a switch to the joystick port in place of the circuit. A crude audio frequency meter could be built by using the machine code routine to measure the duration of one cycle. (A comparator and amplifier will probably be needed to square up and increase gain of the signal.) The code could also be modified to read the other joystick switch connections in order to sense several events simultaneously. (The lowest four bits at memory location 56320 represent the four joystick positions. The fifth bit is the fire button.) Experiment with it! Maybe you'll be the first to build a thought-controlled robot! 

PARTS LIST

Semiconductors

IC1—4001 quad NOR gate

IC2—555 timer

Resistor

R1—10,000 ohms, 1/4 watt, 5%

Capacitors

C1—.001µF., ceramic

C2—.01µF., ceramic

Miscellaneous

J1—Miniature phone plug

P1—Modified joystick extension cable (see text)

BF1—Biofeedback monitor (Radio Shack #63-675)

Wire, perfboard, solder, etc.


Electronics Paperback Books

EVERY BOOK IN THIS AD \$6 OR LESS!



- BP125—25 SIMPLE AMATEUR BAND ANTENNAS.....\$5.00.** All are inexpensive to build, yet perform well. Diodes, beams, triangle and even a mini rhombic.
- BP128-20 PROGRAMS FOR THE ZX SPECTRUM & 16K ZX81.....\$5.75.** Programs to run. Programs to have fun with. Even programs that will help you learn to write programs.
- 160—COIL DESIGN & CONSTRUCTION MANUAL.....\$5.95.** How the hobbyist can build RF, IF, audio and power coils, chokes and transformers. Covers AM, FM and TV applications.
- 208—PRACTICAL STEREO & QUADROPHONY HANDBOOK.....\$3.00.** A reference book for all interested in stereo and multichannel sound reproduction.
- BP99—MINI-MATRIX BOARD PROJECTS.....\$5.00.** Here are 20 useful circuits that can be built on a mini-matrix board that is just 24 holes in length copper-foil strips.
- BP157—HOW TO WRITE ZX SPECTRUM AND SPECTRUM + GAMES PROGRAMS.....\$5.95.** A crystal-clear step-by-step guide to writing your own graphics games programs.
- BP117—PRACTICAL ELECTRONIC BUILDING BLOCKS—Book 1.....\$5.75.** Oscillators, Timers, Noise Generators, Rectifiers, Comparators, Triggers and more.
- 219—SOLID-STATE NOVELTY PROJECTS.....\$4.95.** Fun projects include the Optomin, a musical instrument that is played by reflecting a light beam with your hand, and many more.
- 222—SOLID STATE SHORT WAVE RECEIVERS FOR BEGINNERS.....\$5.00.** Modern solid-state circuits that will deliver a fairly high level of performance.
- BP126—BASIC & PASCAL IN PARALLEL.....\$4.95.** Takes these two programming languages and develops programs in both languages simultaneously.
- 224—50 CMOS IC PROJECTS.....\$5.25.** Includes sections on multivibrators, amplifiers and oscillators, trigger devices, and special devices.
- 225—A PRACTICAL INTRODUCTION TO DIGITAL IC'S.....\$4.95.** Mainly concerned with TTL devices. Includes several simple projects plus a logic circuit test set and a digital counter timer.
- 226—HOW TO BUILD ADVANCED SHORT WAVE RECEIVERS.....\$5.50.** Full practical construction details of a number of receivers are presented.
- 227—BEGINNERS GUIDE TO BUILDING ELECTRONIC PROJECTS.....\$5.00.** How to tackle the practical side of electronics so you can successfully build electronic projects.
- BP6—ENGINEERS AND MACHINISTS REFERENCE TABLES.....\$2.25.** Screw thread data, drill sizes, circle division, angles, tapers and more.
- 123—FIRST BOOK OF PRACTICAL ELECTRONIC PROJECTS.....\$3.75.** Projects include audio distortion meter, super FET receiver, guitar amplifier, metronome and more.
- BP24—52 PROJECTS USING IC 741.....\$5.25.** Lots of projects built around this one available IC.
- BP32—HOW TO BUILD YOUR OWN METAL & TREASURE LOCATORS.....\$5.00.** Electronic and practical details on the simple and inexpensive construction of hetrodyne metal locators.

- BP33—ELECTRONIC CALCULATOR USERS HANDBOOK.....\$5.75.** Invaluable book for all calculator owners. Tells how to get the most out of your calculator.
- BP36—50 CIRCUITS USING GERMANIUM, SILICON & ZENER DIODES.....\$5.00.** A collection of useful circuits you'll want in your library.
- BP37—50 PROJECTS USING RELAYS, SCR'S & TRIACS.....\$5.00.** Build priority indicators, light modulators, warning devices, light dimmers and more.
- BP39—50 FET TRANSISTOR PROJECTS.....\$5.50.** RF amplifiers, test equipment, tuners, receivers, tone controls, etc.
- BP42—SIMPLE LED CIRCUITS.....\$5.00.** A large selection of simple applications for this simple electronic component.
- BP127—HOW TO DESIGN ELECTRONIC PROJECTS.....\$5.75.** Helps the reader to put projects together from standard circuit blocks with a minimum of trial and error.
- BP122—AUDIO AMPLIFIER CONSTRUCTION.....\$5.75.** Construction details for preamps and power amplifiers up through a 100-watt DC-coupled FED amplifier.
- BP43—HOW TO MAKE WALKIE TALKIES.....\$5.00.** Equipment for low-power hand-held or portable operation.
- BP45—PROJECTS IN OPTOELECTRONICS.....\$5.00.** Includes infra-red detectors, transmitters, modulated light transmission and photographic applications.
- BP48—ELECTRONIC PROJECTS FOR BEGINNERS.....\$5.00.** A wide range of easily completed projects for the beginner. Includes some no-soldering projects.
- BP49—POPULAR ELECTRONIC PROJECTS.....\$5.50.** Radio, audio, household and test equipment projects are all included.
- BP51—ELECTRONIC MUSIC AND CREATIVE TAPE RECORDING.....\$5.50.** Shows how you can make electronic music at home with the simplest and most inexpensive equipment.
- BP56—ELECTRONIC SECURITY DEVICES.....\$5.00.** Includes both simple and more sophisticated burglar alarm circuits using light, infra-red, and ultrasonics.
- BP59—SECOND BOOK OF CMOS IC PROJECTS.....\$5.00.** More circuits showing CMOS applications. Most are of a fairly simple design.
- BP72—A MICROPROCESSOR PRIMER.....\$5.00.** We start by designing a small computer and show how we can overcome its shortcomings.
- BP78—PRACTICAL COMPUTER EXPERIMENTS.....\$5.00.** Construct typical computer circuits using discreet logic to form a basic understanding of how computers function.
- BP91—AN INTRODUCTION TO RADIO DXING.....\$5.00.** How you can tune in on those amateur and commercial broadcasts from around the world in the comfort of your home.
- BP94—ELECTRONIC PROJECTS FOR CARS AND BOATS.....\$5.00.** Fifteen simple projects that you can use with your car or boat. All are designed to operate from 12-volt DC supplies.

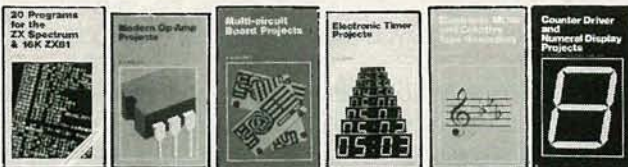

ELECTRONIC TECHNOLOGY TODAY INC.
P.O. Box 240, Massapequa Park, NY 11762-0240

SHIPPING CHARGES IN USA & CANADA

\$0.01 to \$5.00	... \$1.00
\$5.01 to \$10.00	... \$1.75
\$10.01 to 20.00	... \$2.75
\$20.01 to 30.00	... \$3.75
\$30.01 to 40.00	... \$4.75
\$40.01 to 50.00	... \$5.75
\$50.01 and above	... \$7.00

OUTSIDE USA & CANADA
Multiply Shipping by 2 for sea mail
Multiply Shipping by 4 for air mail

Number of books ordered

Name _____
Address _____
City _____ State _____ Zip _____

Total price of merchandise \$ _____
Sales Tax (New York State Residents only) \$ _____
Shipping (see chart) \$ _____

All payments must be in U.S. funds Total Enclosed ... \$ _____

RE10-86

TVRO ANTENNA POINTER

Let your computer nail those satellites!

Elery C. Smith, Jr.

■ Okay, you've got a computer and you're into Satellite reception for your TV. The program offered here will help you in aiming your dish right on the money, and we're even going to give you a way to check and make sure that everything's working right.

The TVRO Antenna Pointing program is written in BASIC and can easily be programmed into almost any computer. All your entries must be in decimal. If your

```
10 PRINT"TV CHANNEL FREQUENCY DIRECTORY"
20 PRINT"*****"
30 INPUT"TV CHANNEL ";A$
40 A=ASC(A$):IFA>64THEN300
50 C=VAL(A$)
100 IFC<2THEN600
110 IFC<5THEN200
120 IFC<7THEN190
130 IFC<14THEN180
140 INPUT"UHF OR CABLE ";B$
150 IF LEFT$(B$,1)="C"THEN320
160 IFC>83THEN600
170 BC=14:BF=470:GOTO400
180 BC=7:BF=174:GOTO4
190 BC=2:BF=54:GOTO400
200 IFA>90THEN600
310 C=A-51:PRINTA$;" =CABLE CH# ";C
320 IFC>65THEN600
330 IFC<23THENPRINT"MID BAND CHANNEL":GOTO360
340 PRINT"SUPER BAND CHANNEL"
350 BC=23:BF=216:GOTO400
360 BC=14:BF=120
400 LB=BF+(C-BC)*6
410 UB=LB+6
420 FV=LB+1.25:FC=FV+3.58:FA=FV+4.5
430 FL=LB+47
440 IL=UB+41*2:IU=LB+47*2
450 PRINT"FREQUENCY RANGE=";LB;"TO";UB;"MHZ."
460 PRINT"PIX CARRIER=";FV;"MHZ."
470 PRINT"COLOR CARRIER=";FC;"MHZ."
480 PRINT"SOUND CARRIER=";FA;"MHZ."
490 PRINT"NOTE: THE FOLLOWING"
500 PRINT"ASSUMES A RECEIVER"
510 PRINT"WITH A 41-47MHZ I.F."
515 PRINT"<41.25MHZ SOUND, 45.75MHZ PIX.>"
520 PRINT"LOCAL OSCILLATOR=";FL;"MHZ."
540 PRINT"IMAGE RANGE=";IL;"TO";IU;"MHZ."
550 PRINT"MORE?"
560 GETC$:IFC$=""THEN560
570 PRINTC$:IFC$="Y"THEN20
580 END
600 PRINT"NON-EXISTENT CHANNEL":GOTO20
```

PROGRAM LISTING ABOVE is written in BASIC and lets you use almost any computer to help aim your satellite antenna.

```
TV CHANNEL?
36
UHF OR CABLE?
CABLE
SUPER BAND CHANNEL
FREQUENCY RANGE= 294 TO 300 MHZ.
PIX CARRIER= 295.25 MHZ.
COLOR CARRIER= 298.83 MHZ.
SOUND CARRIER= 299.75 MHZ.
NOTE: THE FOLLOWING
ASSUMES A RECEIVER
WITH A 41-47MHZ I.F.
<41.25MHZ SOUND, 45.75MHZ PIX. >
LOCAL OSCILLATOR= 341 MHZ.
IMAGE RANGE= 382 TO 388 MHZ.
MORE?
Y
*****
TV CHANNEL?
W
W =CABLE CH# 36
SUPER BAND CHANNEL
FREQUENCY RANGE= 294 TO 300 MHZ.
PIX CARRIER= 295.25 MHZ.
COLOR CARRIER= 298.83 MHZ.
SOUND CARRIER= 299.75 MHZ.
NOTE: THE FOLLOWING
ASSUMES A RECEIVER
WITH A 41-47MHZ I.F.
<41.25MHZ SOUND, 45.75MHZ PIX. >
LOCAL OSCILLATOR= 341 MHZ.
IMAGE RANGE= 382 TO 388 MHZ.
MORE?
N
```

SAMPLE PRINTOUTS are for Orlando, Florida, and Huntsville, Texas. Enter our numbers after the program is installed and see if you come up with the same answers.

longitude is 95 degrees, 30 minutes, it must be entered as 95.5. And of course, you must not reverse longitude and latitude.

Included here are two typical samples of entries, one for Orlando, Florida, the other for Huntsville, Texas. To check your program once it's installed, simply enter my numbers and see if you come up with the same answers. It's that easy.

There's one other thing. Most computers calculate angles using radians. The .01745329 changes your "degrees" entry to radians and back to degrees again. If your computer compensates for a direct entry, simply leave the .01745329 out of the program. ◀▶

R-E Books Admart

Rates: Ads are 2 1/4" x 2 7/8". **One** insertion \$825. **Six** insertions \$800 each. Twelve insertions \$775 each. Closing date same as regular rate card. Send order with remittance to **Books Admart**, Radio Electronics Magazine, 500-B Bi-County Blvd., Farmingdale, NY 11735. Direct telephone inquiries to Arline Fishman, area code-516-293-3000. *Only 100% Book ads are accepted for this Admart.*

SILICON-CONTROLLED RECTIFIER PROJECTS

1586T—From TAB Books. A treasure trove of exciting projects using SCR's and other low-cost thyristor devices for power-control applications. Includes a sophisticated burglar-alarm system, an SCR-based smoke-alarm system, a remote-control garage-door opener, and a high-tech light dimmer that uses the output from your stereo to modulate the intensity of your lights. And then there are 20 more. To order—ask for book **1586T**, include your check for **\$9.95 plus \$1.75 shipping** in the US, and order from—**Electronic Technology Today Inc.**, P.O. Box 240, Massapequa Park, NY 11762-0240.




THE TRANSDUCER PROJECT BOOK

1992T—From TAB Books. A unique collection of practical transducer devices that you can put together simply and inexpensively. You can build a seismic sensor, a temperature survey meter, an open-door annunciator, a moisture detector, an automatic night light, and more. To order—ask for book **1992T**, and include your check for **\$8.95 plus \$1.75 shipping** in the US, and order from—**Electronic Technology Today Inc.**, P.O. Box 240, Massapequa Park, NY 11762-0240.



THE COLLECTED WORKS OF MOHAMMED ULLUYSES FIPS

166—By HUGO GERNS-BACK. Here is a collection of 21 April Fools Articles, reprinted from the pages of the magazines they appeared in, as a 74-page, 8 1/2 x 11-inch book. The stories were written between 1933 and 1964. Some of the devices actually exist today. Others are just around the corner. All are fun and almost possible. Stories include the Cordless Radio Iron, The Visie-Talkie, Electronic Razor, 30-Day LP Record, Teleyeglasses and even Electronic Brain Servicing. Get your copy today. Ask for book **166** and include **\$12.00 plus \$2.75 shipping** in the US, and order from **Radio-Electronics Bookstore**, 500-B Bi-County Blvd., Farmingdale, NY 11735.

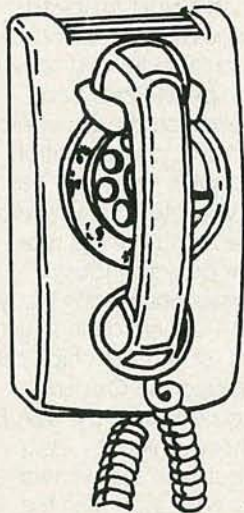

CALL NOW AND RESERVE YOUR SPACE

- 6 x rate \$800.00 per each insertion.
- Reaches 239,312 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads.

Call **516-293-3000** to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: Books Admart, RADIO-ELECTRONICS, 500-B Bi-County Blvd., Farmingdale, NY 11735.

ELECTRONIC CALCULATOR HANDBOOK USERS

BP33—Presents formulae, data, methods of calculation, conversion factors, etc., with the calculator user especially in mind; often illustrated with simple examples. An invaluable book for all calculator users, whatever their age or occupation. **\$5.00 plus \$1.00 shipping** in the US and Canada gets you your copy. Ask for **BP33** and order from **Electronic Technology Today Inc.**, P.O. Box 240, Massapequa Park, NY 11762-0240.



INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE

BP85—Designed to help the user find possible substitutes for a popular user-oriented selection of modern transistors. Includes devices produced by more than 100 manufacturers. Wherever possible, equivalents are sub-divided into European, American and Japanese types. Material type, polarity and manufacturer are also shown. To order **BP85** send **\$7.50 plus \$1.75 for shipping** in the US and Canada to **Electronic Technology Today Inc.**, P.O. Box 240, Massapequa Park NY 11762-0240.




PRACTICAL ELECTRONICS CALCULATIONS AND FORMULAE

BP53—A workshop manual for the electronics enthusiast. It bridges the gap between complicated technical theory, which sometimes seems to have little relevance to practical work, and 'cut and try' methods that may bring success in design, but leave the experimenter unfulfilled. To get your copy send **\$6.95 plus \$1.75 for shipping** in the US and Canada to **Electronic Technology Today Inc.**, P.O. Box 240, Massapequa, NY 11762-0240.



ELECTRONIC GAMES

BP69—A number of interesting electronic game projects using IC's are presented. Includes 19 different projects ranging from a simple coin flipper, to a competitive reaction game, to electronic roulette, a combination lock game, a game timer and more. To order **B69** send **\$5.00 plus \$1.00 shipping** in the US and Canada to **Electronic Technology Today Inc.**, P.O. Box 240, Massapequa Park, NY 11762-0240.

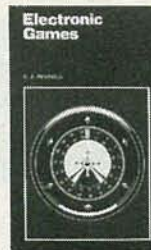

OKIDATA UPGRADE

How to get more out of your Okidata— Without putting a lot more into it...

Elliott S. Kanter

■The Okidata Models 82 and 83A have for years been a part of many home and business computer systems. Their reasonable cost and good reliability and speed have made them a staple for the medium- or small-volume printer user who was willing to put up with inconvenience in exchange for the durability and reliability usually associated with an army tank.

One of the minor inconveniences present with both printers, which only vary in column width capability (82A-80 col., 83A-132 Col.) is clearly shown in Table 1, an actual print sample of the rather limited selection of (4) type sizes. However, to further complicate this limitation, there was no easy way other than writing a simple BASIC program with an appropriate "LPRINT" command to change these type sizes, unless you went to the trouble of customizing your wordprocessing program and convert these command codes to others which a program such as WordStar™ could recognize. As if to placate those users of the Okidata line, the company included some values/benefits which were not present on other printers. Okidata 82A and 83A

supported your choice of either serial or parallel ports, to a degree. The serial port had a built-in speed limitation of 1200 baud and could only support certain protocols without the addition (at extra cost) of what Okidata referred to as a High-Speed Serial Card. Essentially, the parallel port followed the Centronics conventions, but the printer codes, those control sequences which determined what type size was selected, *i.e.* 10 CPI (normal type), 16.5 CPI (condensed type), 8.3 CPI (expanded type) or CPI (wide type) were not compatible with the defacto industry standard Epson codes. This made interfacing many of the features available to IBM™ PC users difficult unless you purchased a replacement set of ROM chips called the "Plug 'N Play" option or added the Okidata OKIGRAPH option. You had to really love the 82A/83A to put up with these minor inconveniences—but considering the fact that it would run forever with a change or two of ribbon, and was faster than the Epson competition, the printers found their way into many computer applications.

While offering two options to enhance the ability of the Okidata Printers to respond (much in the same fashion) as the IBM Graphics or Epson MX-80/MX-100 printers, not much else was done to improve upon the printing quality except perhaps by some diehards with the expertise to write custom programs and make the printers do other and somewhat better printing jobs. Yet at the same time there were aftermarket products available for the Epson products which permitted alternative type styles, sizes and even near letter-quality at fairly reasonable cost adding in the neighborhood of about \$130.00 to the basic cost of the printer. When the Okidata owners called or wrote these companies whose ads said "...enhances dot-matrix printers...offers near letter quality...etc." they found out, sorry, but we only support the Epson and true-Epson compatible printers, we have no plans to support the Okidata



Fig. 1—Front view and orientation of the Okidata ML 82A Printer.

products. This remained true until a Costa Mesa and now Irvine, California Company called Rainbow Technologies Inc., introduced the first in a series of enhancements for the Okidata printers. The original or parent product, OK-Writer™ added near letter quality, dot addressable graphics and other features to the printer via a PC card which replaced the existing three ROM chips, it also expanded the speed of the built-in serial port from its 1200 baud limitation to 2400 baud and provided some other goodies which were front panel selectable and didn't require any skills in computer programming.

Progress, like time, stands still for no person, company or computer and Rainbow Technologies built its second generation product, the PC-writer™, incorporating many of the features of the OK-Writer and adding just a few more enhancements like:

- * Pica, elite or compressed type styles
- * Double width characters in any type style
- * Draft (DQ 120CPS) or Near Letter Quality (LQ 30 CPS)
- * Ability to print all IBM printer symbols
- * Ability to print double line box drawing symbols
- * Backspace for easy overstriking

The items listed above can't really do the PC-Writer as much justice as the print sample of the self-test. This actual print sample is the result of the built in self-test activated from the front panel in much the same manner (pressing and holding the LINE FEED button while turning the power ON) as the conventional and unmodified self-test runs on the 82A/83A. However the results and printout are outstanding.

In order to gain some things you sacrifice others. In the case of near letter quality, the PC-Writer, like its competition, the super-enhanced Epsoms will not operate at the nominal 120 CPS, but will slow to around 30 CPS, however, because near letter quality requires multiple passes, there's always a chance of a higher noise level due to vibration. In the case of the PC-Writer, this problem is minimized by converting the horizontal emphasis commands into vertical emphasis or double strike commands.

To make any dot-matrix printer's output more closely resemble near letter or letter-quality, the dots formed by the print head must be made to form a denser pattern. This is accomplished by multiple-passes and

Sample Printouts for Unmodified Okidata 82A

THIS IS A SAMPLE OF CONDENSED 16.5 CPI TEXT

THIS LINE RETURNS YOU TO NORMAL

EXPANDED 8.3CPI TEXT

RETURN TO NORMAL 10 CPI

WIDE 5CPI SAMPLE TEXT

RETURN TO NORMAL

Sample print out unmodified Okidata ML 82A printer. All print styles were accessed via "LPRINT" commands.

results in a decrease in speed. However, these usual techniques do not allow for all of the type fonts available with PC-Writer, and are the result of creative approaches to command code programming in order to make a printer whose average retail price (my area) was about \$239.00 plus the PC-Writer (at a suggested list price of \$112.95) perform like a letter quality printer selling for double its price! One catch, you have to be handy enough to install the small circuit board yourself.

For those of you who read and followed my articles in the July and August issues of Radio Electronics and built your own compatible PC/XT's what comes next will be a piece of cake. If you haven't worked on any electronics devices, the instructions and illustrations that follow will make the conversion seem easy enough to follow. A note of caution to either group of installer/builders, once the cover of your printer has been removed, there is a potential for accidental electric shock. Before proceeding any further, unplug your printer from the AC wall outlet and disconnect the cable leading to your computer.

You will need the following hand tools to accomplish the modification: Phillips Head screwdriver with at least a 4-inch shaft, IC Puller (Radio Shack) or small flat-bladed screwdriver.

These items are desirable, but not essential to the modification: Anti-static wrist bracelet, Diagonal Cutters, or A length of hookup wire, a 25K ohm (or greater) resistor and two alligator clips.

Warning

The PC-Writer circuit board module can be damaged by static electricity. Do not remove it from its protective packaging until you are ready to install it in your printer.

INSTALLATION

After you unplug your printer from the wall and computer, position it as shown in Figure 1. As you view the printer from the front, you will see to your right, a large black plastic knob coming out of the right side of the case. This knob is the platen knob and must be removed before we can proceed. Remove this knob by gently pulling it off and set it aside.

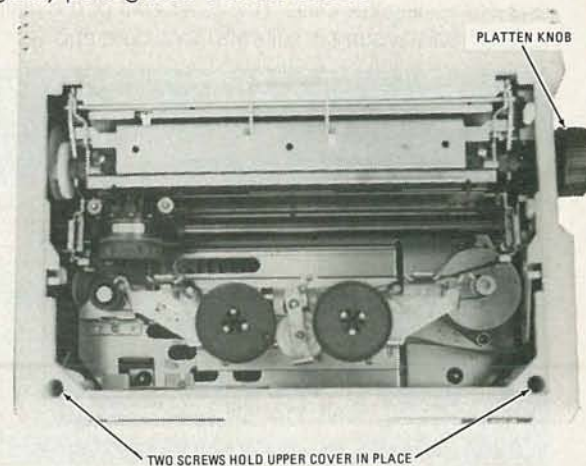


Fig. 2—Detail view with call outs of the upper cover showing the two screws which must be removed as well as the platten knob.

Remove the access cover by gently lifting it up and set it aside.

Refer to Figure 2 and loosen the two recessed phillips head screws which hold the front upper cover in place. Remove the cover by lifting it up and pushing it back to release the hooks located on the back panel of the printer. Carefully set the cover aside, taking the necessary precautions to avoid losing the two screws.

Turn your printer around as shown in Figure 3 and locate the control circuit board. It is normally located in the first slot from the rear unless you have the optional high speed serial card. If you have the high speed serial card installed, you will have to remove this card before going any further. If you have the high speed serial card, locate the two hold-down screws one at each side of the circuit board and carefully remove the board to enable you to access the control circuit board.

If you do not have the high speed serial card installed, loosen the two hold-down screws at either end of the control circuit board and carefully lift it up until you can identify the three large ICs located at the top right hand corner (as viewed from the rear) and shown in Figures 4. Using either the small flat bladed screw driver or the IC puller, remove these three 24-pin ICs by gently prying them loose from their sockets. The ICs are numbered 004, 005 and 006. You may have to remove cable CN5 from its socket on the control board in order to access these 3 ICs. Once you have removed the ICs you may put them aside, they will not be required when you install the PC-Writer module. Before proceeding with the installation, check that capacitors C27, C28 and C29 are at approximately a 60 degree angle relative to the control circuit board, if they are not, bend them as required. Check to see that capacitor C28 is at approximately a 90-degree angle and correct if need by bending. This will facilitate the installation of the PC-Writer Module.

If you have the anti-static bracelet, place it around your wrist and connect the alligator clip at the end of the wire to a suitable ground connection. If you are wearing a metal watch band, you can use the wire, resistor and two alligator clips to form a similar protective device. Connect one end of the resistor to one of the alligator clips. The other end of the resistor is fastened (twisting is suitable) to a bare end (either

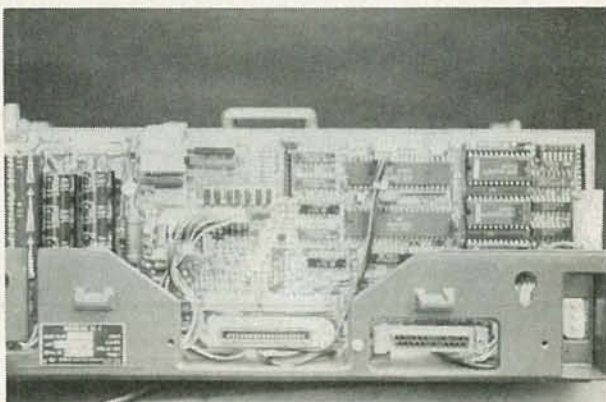


Fig. 3—Rear view of the printer's control circuit board visible when the upper cover has been removed.

end of the wire), the remaining alligator clip should be attached to the end of the wire and connected to a suitable ground connection. The reason for these anti-static precautions is to eliminate the chance that static electric discharges could damage the PC-Writer module. Now you may open the PC-Writer container and carefully remove the module. Refer to Figure 5, the PC-Writer and locate it with the arrows pointing upwards and the circuit components facing you. If you are installing the PC-Writer in an Okidata 83A, locate resistor B labeled "CUT FOR ML83A." Using a diagonal cutter, carefully cut the wires attaching this resistor to the circuit board and discard the resistor. Carefully remove the protective foam from the underside of the circuit board, and observe the pins extending from the non-component side.

Align these pins with the corresponding locations of sockets 004 and 006 on the circuit control card. Gently press the module into these two sockets and continue the pressure until all pins have been seated in the sockets. Your PC-Writer does not use socket 005. Check your work and ensure that all pins are firmly seated as shown in Figure 6. If you had to remove cable CN5, reconnect it at this time. Carefully slide the circuit board down and refasten the two hold down screws located at either end of the circuit board. Be careful not to pinch any wires under the circuit board during this step.

Turn your printer around so that it is facing you and set the front operator control DIP switch as follows:

Position	ON	OFF
1		X
2	X	
3		X
4		X
5		X
6		X
7		X

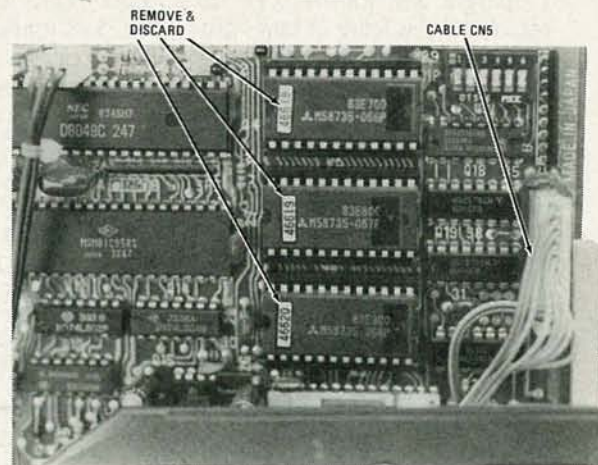


Fig. 4—Detail view of the ROM's (3) and the cable CN5. The 3 ROM ICs are removed and discarded, the cable CN5 may require disconnection.

If you wish, you may refer to Section 4 or Appendix C of the manual which comes with your PC-Writer to select other conditions, however, the conditions selected as shown above (2 on, all others off) are the recommended power-on conditions.

Replace the upper cover by reversing the process used to remove it. Hook the cover at the rear panel and seat it, ensuring that the wire paper guide is flipped forward. Using the Phillips screwdriver tighten the two recessed hold down screws. Replace the access cover and replace the platen knob previously removed. You have now completed the installation of the PC-Writer. The protective foam may be used to store the 3 ROMs removed from the printer. Proceed to the following section and test your installation.

Testing

Load your printer with paper. Plug the printer into the AC wall outlet. Press and hold the line feed button while you turn the power switch on. Release the LINE FEED button and your printer will begin to print the one page document/type sample. This one page will be repeated until you depress the SEL button or turn the printer OFF.

In case of problems

If the printer does not operate immediately and begin the self-test printout, turn the power off, disconnect the AC power cord and recheck all of the installation steps.

Exploring your new PC-Writer

Now that you have installed the module, the normal control functions of the Okidata Printer (See Figure 7) have been enhanced and have additional functions which will be described at this time.

LINE FEED BUTTON-With the printer deselected (RED LED SEL is OFF), pressing the button for more than one second causes the line feeding paper motion to repeat until the button is released. This can make it easier to move the paper over a short distance to the next top-of-form. It can also be used in conjunction with the TOF (top-of-form) button to advance the paper

upwards by small amounts. Holding the TOF SET button down and gently pressing the LINE FEED button continuously will advance the paper, when you reach the desired position, relax the LINE FEED button and the new top of form will be set.

SEL (Select) BUTTON-Each time this button is pressed the print head will move to a new position. When the printer is first selected the print head will move to the left margin to recalibrate for proper printing. When you deselect the printer by pressing the button and the RED LED is off, the print head will move to the center to permit you to install the paper without the need to manually move the print head. It is also possible to put the printer ON-LINE after starting a form feed action even though the paper is still moving. Briefly press and release the SEL button and the SEL LED will come on as soon as the paper has stopped moving.

FORM LENGTH ROTARY SWITCH-This switch now has several new functions. If you are using the 132 col. 83A, switch setting 6 now selects a page length of 8½ inches rather than the 8 inch page length shown in the printer manual and repeated on the 83A's access cover. This will allow you to use paper 11 inches wide by 8½ inches high. The other uses of this rotary switch will be covered under the "Feature Selection" category.

Now that you have installed your PC-Writer, your Okidata Printer will provide full emulation of the IBM Graphics printer and more. How much more will depend on what you elect to set by using escape sequences described in detail in the PC-Writer manual (Section 6.2), how you make use of the front panel Features Selection which will be described in detail and your own specific requirements.

The default setting you made earlier on the DIP switch located on the form of the operator control panel enables the selection of all of the enhanced functions. If you desire to use only those functions used or supported by the IBM graphics printer, and no more, you would set switch 5 to ON and 1 and 8 to OFF, and not use any of the unique escape sequences for the PC-Writer. A description of some of the possible settings can be found in Section 4 and 6 of your PC-Writer's manual. For the present, let's leave the switch as

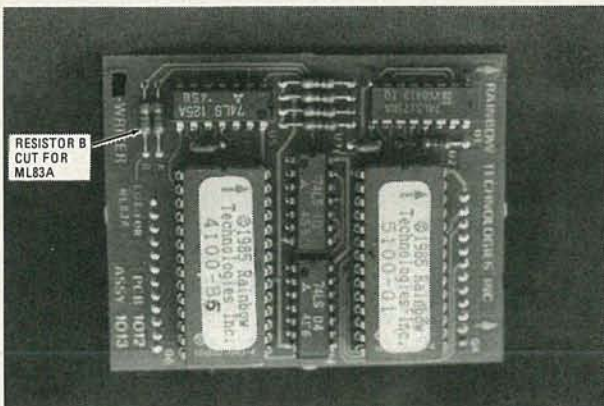


Fig. 5—The PC WRITER Module with call out for location of Resistor B. This resistor is not used with the wide carriage ML 83A printer.

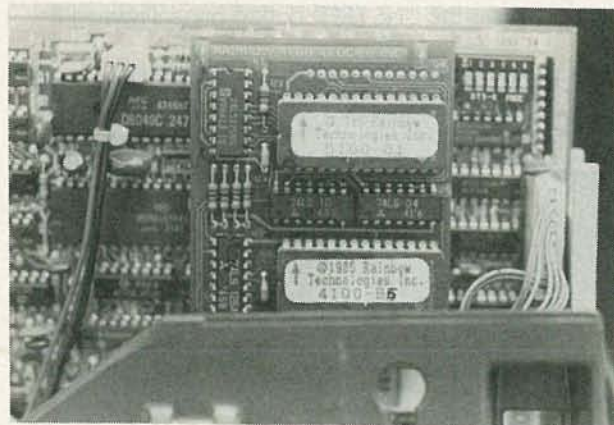


Fig. 6—The PC WRITER Module installed on the control circuit board.

set previously, and enjoy as much of the ease-of selection and feature as possible.

Feature selection

The PC-Writer's features can be accessed in two ways. The first is via traditional computer control mode, this will require that you use the escape sequences unique to your PC-Writer and for the present, we suggest that you confine yourself to the second mode, the user of the now enhanced Front Panel Selection Mode which will allow you access to the most desirable features without the need to program or refer to charts or tables.

FRONT PANEL SELECTION MODE-In this mode, you will use the SEL button, the LINE FEED button and the FORM FEED button and the FORM LENGTH rotary switch. Each of these controls and their function will be explained separately.

Selecting a feature

To convert the front panel control to feature selection, depress the SEL button for one or more seconds to activate the front panel selection mode. This is indicated by an audible tone and the SEL LED flashing at a rate of about 2 or 3 times per second.

To select a feature rotate the FORM LENGTH switch from its normal forms length setting to the desired setting as listed below:

Setting#	Feature Selected
0	Print HELP Menu
1	Letter quality
2	Elite character pitch
3	Compressed character mode
4	Wide characters
5	Shortened characters at 12 lines per inch (1pi)
6	Emphasized printing (bold faced)
7	Double Strike printing
8	Dumb terminal mode
9	Print shifting alphabet test

If position 1 through 8 is selected the SEL LED will indicate if that feature is ON (selected) or OFF. If the feature is ON the SEL LED will be ON more than it is off, if the feature selected is OFF, the LED will be OFF more than it is on. To change the setting or state of the selection, press the LINE FEED button once. Pressing it

again will change the selected feature to its opposite setting (off becomes ON, or on becomes OFF). If the FORM LENGTH switch is at the 0 position, pressing the line feed button will print a list (menu) of the features available from PC-Writer and their status (ON or OFF). Position 9 if selected will immediately begin to print a shifting alphabet test as shown in Table 3. To stop this test, press the SEL button.

Draft quality is selected whenever letter quality is not selected. The compressed mode has no effect while the Elite character pitch is selected. Pica character pitch of 10 cpi is selected whenever neither elite or compressed mode is selected. Turning off the shortened character mode (Position 5) will also select 6 LPI spacing. In the dumb terminal mode, all control codes except Carriage Return (CR), Line Feed (LF) and Form Feed (FF) are ignored.

You can also print out the part numbers of the PROMs installed in the module. This information could be helpful whenever you need to discuss either a problem or performance with a factory representative. To print these parts numbers, press the TOF SET and FORM FEED buttons simultaneously.

Once you have selected the desired features, briefly press the SEL button. The LED lamp will go off and an audible tone will sound to indicate that the normal off line (deselected) mode is in effect. Return the FORMS LENGTH switch to its normal forms length setting and press the SEL button again to place the printer ON-LINE. The printer will now be ready to print using the selected PC-Writer Feature.

While the normal functions of the operator front panel controls are well described and documented in your printer manual, using PC-Writer you can also make power-on selections of these features by pressing and holding the button while turning the printer power on. The buttons and their Power-On features are as follows:
Operator Button Feature Activated TOP SET
Compressed character pitch in draft mode FORM FEED
Pica character pitch in letter quality mode SEL
Electronically reverses the operator DIP SW Pos 8 for ON/OFF or OFF/ON, allows both a serial and parallel cable to be connected to the printer (DO NOT USE WITH HI-SPEED SERIAL CARD!) LINE FEED
Self-test and demonstration mode. FROM & LINE FEED
Diagnostic Hex dump mode

All features can be deactivated by depressing (deselecting) the SEL button once or when you turn off the printer.

There are many more things you can do with PC-Writer, but if they were all described here, Rainbow Technologies wouldn't have to print a manual. The manual that comes with PC-Writer has sections on code information which is well structured and complete enough to enable you to really take charge of your new printer and exploit it to the limit, after all that's one of the best reasons for buying an enhancement in the first place.

For more information about PC-Writer and any of Rainbow Technologies other products write to them at: Rainbow Technologies Inc., 17971-E Skypark Circle, Irvine, CA 92714. (714) 261-0228. ◀▶

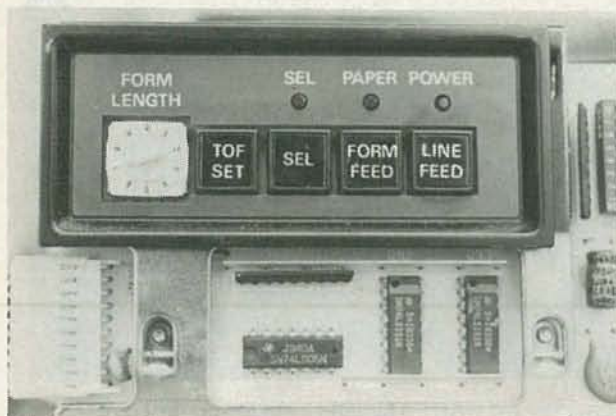


Fig. 7—Detail view of the front panel controls. All controls now have enhanced functions under the PC WRITER.

STATE OF SOLID STATE

Dual-condition sensing



ROBERT F. SCOTT,
SEMICONDUCTOR EDITOR

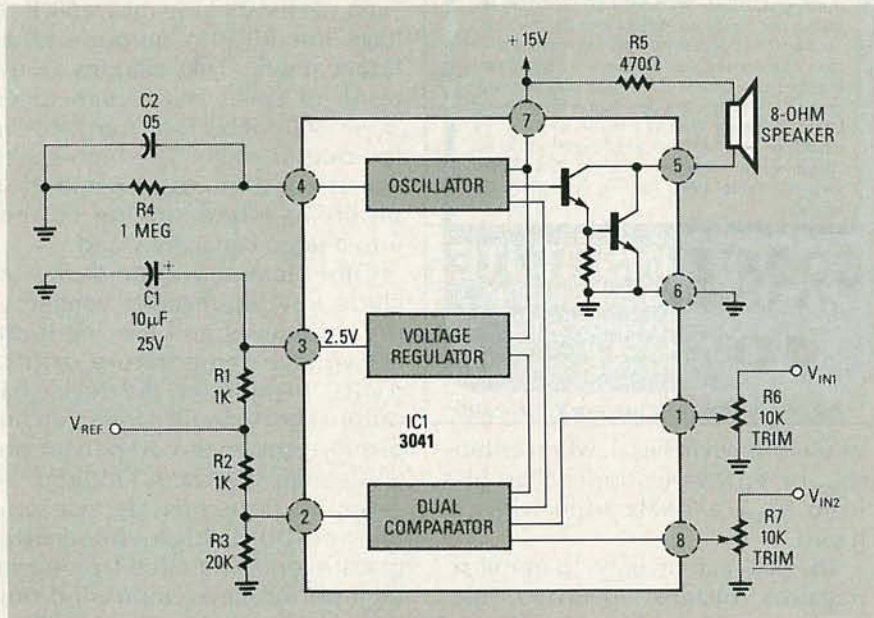


FIG. 1

OFTEN WE NEED TO MONITOR TWO DIFFERENT conditions and raise an alarm when either condition falls above or below a normal value. Those conditions might be, for example, the outputs of a dual-voltage power supply, indoor and outdoor temperatures, or the high and low levels of the contents of a tank.

The electronics of such a two-input monitoring circuit has been greatly simplified by the introduction of the 3041 Monitor/Alarm IC by the Microcircuits Division of Intech. The 3041 is a dual-input circuit designed to monitor two different voltages and give an indication if either varies from the preset level by more than a user-settable predetermined percentage. The IC can provide a steady or an oscillating output, depending on the state of pin 4. The

steady-state output is suitable for driving an LED, a lamp, or a TTL gate; the oscillating output is suitable for driving a speaker or a lightbulb.

The 3041 is packaged in an eight-pin mini-DIP. As shown in Fig. 1, it consists of a dual-input voltage comparator, a voltage regulator, and an oscillator. The 2.5-volt reference that is supplied by the regulator may vary between 2.2- and 2.7-volts DC. The reference voltage is available at pin 3. Maximum current drain (with the alarm on) is 13 mA from a 5-volt supply, and 25 mA from a 15-volt supply. Temperature stability is typically +50 ppm/°C.

The dual-input comparator monitors the voltages applied to pins 1 and 8, and compares them with reference voltage V_{REF} , which is present at the junction of exter-

nal resistors R1 and R2. Actually, the voltage at pin 2 of the IC is used as the reference voltage, but the voltage at the junction of R1 and R2 is a more accurate representation of the voltage to which the comparator inputs are compared.

Only six discrete components are needed to build a basic monitor/alarm circuit. External resistors R1 and R2 are typically 1000 ohms each. Resistor R3 is determined by the desired "trip" tolerance, the percentage deviation from normal that will cause the alarm to trip. The resistor's value can be calculated as follows:

$$R3 = (100,000 \div \% \text{ Tolerance}) - 1000$$

The accuracies of resistors R1, R2, and R3 affect the tolerance of the comparator outputs by a factor of 10:1. For example, if the value of R3 is off by 5%, the comparator output will be off by 0.5%.

Capacitor C1 filters the voltage regulator's output, reduces noise to the comparator, and ensures a high-resolution trip point.

The internal oscillator can be disabled by grounding pin 4. For an AC output, connect an RC network to that pin as shown in Fig. 1. The values shown there will produce an output of about 1000 Hz; other frequencies are easily obtainable by using other components. Intech's data sheet contains a nomograph that aids component selection for various frequencies.

The 3041's open collector output (pin 1) can supply as much as 30 mA of current. The output is off (high) when both comparator inputs are within tolerance, and on (low) when either input is out of tolerance. With the component

Get A Complete Course In

ELECTRONIC ENGINEERING

8 volumes, over 2000 pages, including all necessary math and physics. 29 examinations to help you gauge your personal progress. A truly great learning experience.

Prepare now to take advantage of the growing demand for people able to work at the engineering level.

Ask for our brochure giving complete details of content. Use your free information card number, or write us directly. **\$89.95**, Postage Included. Satisfaction guaranteed or money refunded.



**Banner
Technical
Books, Inc.**

1203 Grant Ave.
Rockford, IL 61103

CIRCLE 176 ON FREE INFORMATION CARD

ATTENTION! ELECTRONICS TECHNICIANS

EARN YOUR
**B.S.E.E.
DEGREE**



THROUGH HOME STUDY

Our New and Highly Effective Advanced-Placement Program for experienced Electronic Technicians grants credit for previous Schooling and Professional Experience, and can greatly reduce the time required to complete Program and reach graduation. No residence schooling required for qualified Electronic Technicians. Through this Special Program you can pull all of the loose ends of your electronics background together and earn your B.S.E.E. Degree. Upgrade your status and pay to the Engineering Level. Advance Rapidly! Many finish in 12 months or less. Students and graduates in all 50 States and throughout the World. Established Over 40 Years! Write for free Descriptive Literature.

COOK'S INSTITUTE OF ELECTRONICS ENGINEERING

CI 347 RAYMOND ROAD
P.O. BOX 20345
JACKSON, MISSISSIPPI 39209

CIRCLE 191 ON FREE INFORMATION CARD

Power Supplies Discount Prices!

VERSATILE LAB POWER SUPPLY



ELECTRO INDUSTRIES MODEL 3002A

Reg. \$125.00 Sale Price **\$99⁹⁵**

• 0-30 VDC at 0-2A • Fully adjustable current limiting • Constant voltage/constant current modes — automatic crossover • Excellent regulation with low ripple • Floating output • Built-in short-circuit and overload protection. Options: 10-Turn Voltage & Current Controls, **\$25 each**. Both for **\$45**.

EPSCO MODEL EC-2 POWER SUPPLY

• 0-16 VDC at 5A • Comb. V/A meter • Benchtop • 1.8 volt/amp load change • 0.5% ripple @ 5A

Reg. \$169.50 Sale Price **\$130⁰⁰**

Check, Money Order or C.O.D. Add \$4.50 per unit for shipping & insurance. Outside U.S. \$9.00. IL residents add 7% tax. 15-Day Money Back Guarantee.

Salen Enterprises

P.O. Box 915, Morton Grove, IL
60053 Area 312-465-1424

CIRCLE 178 ON FREE INFORMATION CARD

sistance between the arm and the high end. Select a capacitor whose reactance at the lowest frequency is small compared with the resistance it will be shunting.

For a data sheet and additional information on the 3041, write to **Intech, Inc.** Microcircuits Div., 2270 Martin Ave., Santa Clara, CA 95050-2781.

New dual JFET op-amp

NEC Electronics has introduced the μ PC812, a new low-offset-voltage dual-JFET-input op-amp designed for stable operation when driving high-capacitance loads. Even when working into a 6800-pF load, the μ PC812's output is absolutely stable. That stability is the result of using NEC's high-speed ($f_T = 300$ MHz) PNP transistor in the output stage. The high-speed transistor eliminates oscillation problems when sinking current into a large capacitive load.

Other features of the device include low input-offset voltage (3 mV maximum) and low input-offset voltage temperature drift (7 μ V/ $^{\circ}$ C). In addition, the device has output short-circuit protection, internal frequency compensation, and a high slew rate (13 V/ μ s).

Applications include fast sample-and-hold, high-speed integrators, and any circuit requiring high-performance input and output characteristics. The μ PC812 is available in standard 8-pin plastic DIP and surface mount packages. Pricing for the DIP package is \$0.66 for 100+ lots. **NEC Electronics, Inc.**, P. O. Box 7241, Mountain View, CA 94039.

Quad multiplying D/A

Precision Monolithics' DAC-8408 quad 8-bit, multiplying CMOS D/A converter with memory is designed for applications that require data-path verification, self diagnostics, and PC-board space savings.

The IC contains four identical 8-bit DAC's on a single CMOS chip. Each DAC has its own reference input, feedback resistor, data latches, and internal 3-state buffers. The IC uses an 8-bit TTL/CMOS-compatible data port that is bus-compatible with most 8-bit microprocessors, including the 6800, the 8080, the 8085, and the

Z80. The port is common to all DAC's in the IC; doing so reduces pin count and allows the device to be packaged in a 28-pin, 0.6" DIP.

The DAC-8408 features a read/write capability that allows each DAC's data word to be read from an addressable memory location. By reading the latched register contents back, the controlling computer can execute data-path verification, self-checks, and analog output updating.

The device is available in two grades in both military/industrial and commercial temperature ranges. Prices in 100-piece lots range from \$8.03 for the lower-grade commercial devices to \$35.82 for the top military grade. **Precision Monolithics**, P. O. Box 58020, Santa Clara, CA 95052.

New P-channel JFET's

The 2N5460-2N5465 from Siliconix are low-cost P-channel JFET devices designed for a broad range of applications, including servo amplifiers, analog switches, level shifters, and control loops. Featured are high breakdown voltages of 40 to 60 volts, low operating currents of 1 to 9 mA, and high gain (1000 to 6000 μ mhos, minimum). Fast switching is made possible by the devices' low inter-electrode capacitance (typically 1 to 5 pF). The JFET's come in TO-92 packages. In 1000 piece lots the 40-volt 2N5460, 2N5461, and 2N5462 are \$0.40 each. The 60-volt 2N5463, 2N5464, and 2N5465 are \$0.60 each. **Siliconix, Inc.**, 2201 Laurelwood Rd., Santa Clara, CA 95054.

High-power Darlingtons

The ZTX600 is the latest addition to Ferranti's family of E-Line (TO-92) NPN Darlington transistors. The new series of high-performance, medium-power devices handle collector currents of as much as 1 amp, and that makes them ideal for automotive and industrial applications. Pulsed currents (I_{CM}) of up to 4 amps, and gains (h_{FE}) up to 100,000 at continuous currents ranging from 500-1000 mA are attainable.

The ZTX600 series offers V_{CEO} ratings of 140 to 160 volts. The construction of the E-Line package permits high junction temperature operation (200°C) that is usually as-

ROBOTICS

continued from page 84

into the control board; the personality pack provides the CPU and any memory it requires.

The arm used for the robot is an adaptation of the Milton Bradley *Robotix* series we discussed in the July 1986 issue. Optical encoders are placed on all joints; feedback from them is routed to the control circuitry. Motor control is by means of subminiature mechanical rather than solid-state relays.

The mobile platform also includes an allophone speech synthesizer. The IC set is available through Radio Shack.

Because of the complexity of the construction details, it is not feasible to present them here. If you are interested in obtaining a full packet of information on the robot (schematic, theory, programming, and mechanical details) drop me a note and include a self-addressed stamped business envelope. **R-E**

sociated with metal-can devices, which can dissipate up to 1.5 watts.

The ZTX600 series is available with several lead configurations and on radial or surface-mount tape for auto-placement. Unit prices are below \$0.18 in quantities of 50,000. **Ferranti Semiconductor**, 87 Modular Ave., Commack, NY 11725.

Four new MOSFET's

Four ITT-type MOSFET transistors that complement its line of N- and P-channel devices have been announced by Ferranti Semiconductors. The devices, BS170P, BS107P and BS107PT (N-channel), and BS250P (P-channel) are numbered according to the Pro-Electron or European system. They provide low threshold, low leakage and fast switching at breakdown voltages between 60 and 200 volts. The BS107P and BS107PT can withstand lightning surges of 1500 volts.

The BS107P costs \$0.31 in lots of 1000. The BS107P and BS107PT cost \$0.41 and \$0.42, respectively, in similar quantities.—**Ferranti Semiconductors**, 87 Modular Ave., Commack, NY 11725. **R-E**

30 Ways to Help You Qualify for the Job You Want

Free Facts about Career Diplomas and Degrees

Now at home in your spare time, without any previous experience, you can train for a money-making career...even get a Specialized Associate Degree. Call or send for free information on the career field that interests you most and how to train for it.



CALL TOLL FREE

1-800-228-5300 / Dept. DES96

CALL ANYTIME—24 hours a day, 7 days a week. No cost. No obligation. No salesman will visit.

OR MAIL COUPON TODAY

ICS International Correspondence Schools
SINCE 1891 Dept. DES96, Scranton, PA 18515

Send free facts on how I can study at home for the career I have chosen. No obligation. No salesman will visit. **CHECK ONE CAREER ONLY.**

ASSOCIATE IN SPECIALIZED BUSINESS DEGREE PROGRAMS

- Business Management
- Accounting
- Business Management with option in Marketing
- Business Management with option in Finance

ASSOCIATE IN SPECIALIZED TECHNOLOGY DEGREE PROGRAMS

- Mechanical Engineering Technology
- Civil Engineering Technology
- Electrical Engineering Technology
- Electronics Technology

CAREER DIPLOMA PROGRAMS

- Computer Programming
- High School
- Catering/Gourmet Cooking
- Microcomputer Repair
- Auto Mechanics
- Bookkeeping
- Hotel/Restaurant Management
- Drafting
- Air Conditioning & Refrigeration
- Electronics
- Electrician
- Police Science
- Art
- Small Business Management
- Wildlife Forestry Conservation
- Diesel Mechanics
- Gun Repair
- Motorcycle Repair
- Surveying & Mapping
- TV/VCR Repair
- Veterinary Assistant
- Travel Agent

These courses are offered by ICS and North American Correspondence Schools.

NAME _____ AGE _____

ADDRESS _____

CITY/STATE/ZIP _____

PHONE NO. () _____

STUNGUN



EQUALIZER

- The ultimate non-lethal defense weapon.
- In five seconds can immobilize your attacker, even through heavy clothing.
- Discharges over forty thousand volts of electricity from a nine volt nickel-cadmium battery.
- \$39.95, Mass 5% sales tax, \$3.00 shipping and handling.

1-800-522-2636

FOR ORDERS ONLY

617-871-5611

FOR INFORMATION

Cameo Enterprises, Inc.
P.O. Box 63, Accord, MA 02018

CIRCLE 89 ON FREE INFORMATION CARD

COMMUNICATIONS CORNER



HERB FRIEDMAN,
COMMUNICATIONS EDITOR

Closed-captioning

IN THE OLD DAYS, WHEN TECHNICIANS showed up for a remote broadcast in black tie, a remote broadcast generally required a separate cue and chit-chat circuit that was independent of the primary signal path. But just about any sort of communications circuit costs big bucks, whether it's a private radio or telephone system, or someone with a pocketful of change ducking into the nearest phone booth. So, as soon as it became technically feasible, broadcasters began to piggyback subsidiary communications on the main TV and FM broadcast channels.

The FM SCA (Subsidiary Communications Authorization) subcarrier channel was legal as far back as 1945, but until recent times the FM subcarriers were used almost exclusively for telemetering the transmitter, or as a second broadcast channel for background music and "storecasts." FM subcarriers were not used as a substitute for a conventional communications system.

But thanks to modern technology it is now relatively easy and convenient to integrate independent cue and control signals with the main broadcast signal. And it's also possible to piggyback special programming with the main broadcast signal.

Piggyback channels

Two examples of commonly used piggyback communications are the television professional subcarrier channel and closed-captioning for the hearing-impaired. The professional channel is an audio subcarrier that is displaced 102.3 kHz from a TV station's main

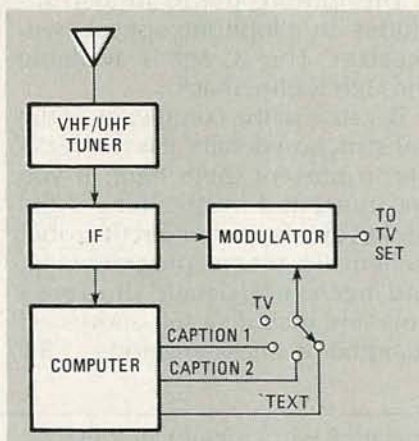


FIG. 1

audio carrier. It can have a maximum power output no more than 10% of the main audio carrier. Unlike the TV SAP (Second Audio Program) channel, which is locked to the horizontal sync, the professional subcarrier is crystal controlled and limited to ± 3 kHz deviation. It is intended specifically for station business such as the control tones that are used for electronic news gathering, and for cuing and coordinating remote broadcasts. Pro subcarrier signals might also be used to aim the antenna that is used to receive microwave signals from a remote pickup truck, or it might simply turn on a light that means "You're on the air."

Closed-captioning is a means whereby titles and "balloons" are superimposed on a TV picture so the hearing-impaired can understand TV programs and commercials (yes, commercials). Titles are similar to the subtitles used in foreign films, in that they run across the bottom of the picture. Balloons are shorter subtitles that re-

semble the "speech balloons" used in comic strips. The words are positioned adjacent to the person speaking, and that helps convey the flow of conversation when several persons are in the picture.

Closed-caption reception requires a special adapter which is nothing more than a special-purpose microcomputer combined with a VHF/UHF tuner and an RF modulator that can deliver a signal to TV channel 2 or 3. As shown in Fig. 1, the adapter connects to a standard TV set just like a VCR or a cable converter. The major difference is that the computer decodes the captions and inserts them into the conventional TV picture. (We'll present plans for a closed-caption decoder in the next month's issue.—Editor)

Closed-captions do not interfere with normal video because the ASCII captioning codes are inserted into the TV signal during line 21 of Field 1, which occurs during the vertical blanking interval. The microprocessor in the closed-caption adapter extracts the data from line 21, converts it into displayable form, and applies it to the modulator for output. (Line 21 of Field 2 is generally not used for other than perhaps a control signal because only half the line is available for ASCII encoding.)

The ASCII data in line 21 represents a single character which may be preceded by a "preamble" that contains information needed to position the inserted text: the line on which it is located, and its indentation from the left edge of the picture. The preamble permits the title or balloon to be located any-

continued on page 97

KENWOOD

...pacesetter in Amateur radio

Scan the World



R-2000

All-mode receiver

Superior engineering, quality, and performance describe Kenwood's multi-mode communications receiver.

The R-2000 receiver has the most often-needed features for the serious or casual shortwave broadcast listener. Listen in on overseas news, music, and commentary. "Listen up" on the VHF public service and Amateur radio frequencies, as well as aircraft and business band communications with the R-2000 and VC-10 option. The R-2000 has a muting circuit so you can monitor your Amateur radio station's signal quality.

- Covers 150 kHz—30 MHz in 30 bands.
- All mode: USB, LSB, CW, AM, FM.
- Digital VFO's. 50-Hz, 500-Hz or 5-kHz steps. F. LOCK switch.

- Ten memories store frequency, band, and mode data. Each memory may be tuned as a VFO.
- Lithium batt. memory back-up.
- Memory scan.
- Programmable band scan.
- Fluorescent tube digital display of frequency (100 Hz resolution) or time.
- Dual 24-hour quartz clocks, with timer.
- Three built-in IF filters with NARROW/WIDE selector switch. (CW filter optional.)
- Squelch circuit, all mode, built-in.
- Noise blanker built-in.
- Large front mounted speaker.
- RF step attenuator. (0-10-20-30 dB.)
- AGC switch. (Slow-Fast.)
- "S" meter, with SINPO scale.
- High and low impedance antenna terminals.
- 100/120/220/240 VAC operation.
- RECORD output jack.
- Timer REMOTE output (not for AC power).
- Muting terminals.

Optional accessories:

- VC-10 VHF converter for R-2000 covers 118-174 MHz
- YG-455C 500 Hz CW filter for R-2000
- HS-4 Headphones
- HS-5 Deluxe headphones
- HS-6 Lightweight headphones
- HS-7 Micro headphones
- DCK-1 DC cable kit for 13.8 VDC operation

Additional information on Kenwood all-band receivers is available from authorized dealers.

25th
Anniversary

KENWOOD

TRIO-KENWOOD COMMUNICATIONS
1111 West Walnut Street
Compton, California 90220

CIRCLE 102 ON FREE INFORMATION CARD

Service manuals are available for all receivers and most accessories.
Specifications and prices subject to change without notice or obligation.

ANTIQUE RADIOS

Antique radio cabinets

IT'S HARD TO TALK ABOUT ANTIQUE RADIOS without also talking about the cabinets of antique radios. Those cabinets are as collectible as the chassis they contain. In the early days of radio, it was not unusual to have an elaborate cabinet for the speaker and none at all for the chassis. Some early speaker cabinets were so large that there was room inside to mount the chassis, which many listeners did. And many chassis were mounted in cabinets made for purposes totally unrelated to radio.

The antique of the month

Speaking of large cabinets, the massive 1940 Philco Model 41-616 combination radio/phono shown in Fig. 1 has the largest cabinet in my collection. Measuring 40 inches across and about 48 inches high, it completely dominates my "shack." Usually the shack is used only for quarantine and preliminary inspection. However, that console was too large to carry down to my "museum" (the cellar).

I received the Philco just for removing it from a location where it was unwanted. Not being one to turn down anything free, I planned to restore that monster and then sell it (or trade it) for some older (and smaller) collectibles. But, after repairing the chassis and hearing the big-band sounds emanating from the grille cloth, I decided to keep it. Now I listen to it whenever I work in the shack. My only problem is getting in and out of the shack, because the Philco almost completely blocks the door.

Its 15-tube chassis has a broadcast band and three shortwave

bands; and a 14-inch dynamic speaker is located under the record changer.

Antique cabinets

Over the years, the radio cabinet took the form of everything from a simple box to a huge elaborately scrolled cabinet. When the chassis was no longer repairable, a nice cabinet might be converted into a bookcase, a grandfather clock, a lamp, a bird house, a phonograph, a secretary, or any of a number of other things.

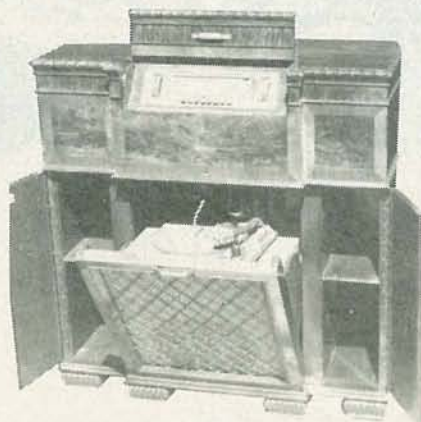


FIG. 1

On the other hand, many clocks, etc., had more than enough space to mount a radio chassis and a speaker. These days many collectors come into possession of an unidentifiable radio built into a clock or some other device by an early radio hobbyist. In fact, the only identifying information may be the tube numbers. Many readers have indicated that that lack of identification is a common problem.

For many years radio cabinets followed (and sometimes led)

fashions in furniture design. Of course, being beautiful was not the only function of a radio cabinet. In addition to protecting the internal circuitry, the cabinet also provided a baffle arrangement for the loudspeaker.

Both the magnetic loudspeaker and the dynamic cone loudspeaker (both of which were discussed here in the September 1986 issue) sound better when mounted in a cabinet. Because it has trouble reproducing low notes, the magnetic loudspeaker greatly benefits from a baffle.

Enclosure design

Speaker cabinets weren't used just for looks and to house the chassis; they were designed to improve the sound produced by speakers. So designers spent a great deal of effort trying to match enclosure and loudspeaker to get the best looks and the best sound. Some designers went to fantastic lengths to come up with better-sounding speaker enclosures. In fact, collectors who dismantle the cabinets of some 1930-era consoles may well be baffled by the baffle arrangement (pun intended). You may not be able to find the speaker because of all of the internal parts! Another area of much engineering effort was the fabric design of the loosely-woven grille cloth. It was hoped that the grille cloth wouldn't interfere with the sound waves.

Through the 1930's the ability to reproduce bass notes was the most desirable feature, and one of the hottest selling points, of many console radios. Bass response was improved by using a large re-



RICHARD D. FITCH,
CONTRIBUTING EDITOR

producer, by adding bass and treble controls, and by using a well-designed enclosure.

In the developing days of radio, not just the type of speaker, but its location were items of contention among designers. In an effort to improve reproduction, shelves were installed, removed, installed in another location, and so on, in early cabinet designs. Information on that type of alteration, and others, could be obtained from the early radio magazines.

For some unknown reason, cabinets for radio chassis were not very popular. Buying radios in bits and pieces was the beginning of "component" sets, which younger readers may think began with hi-fi in the 1950's. Actually, component sets are as old as radio itself.

Many speaker cabinets were large enough to use as closets. Enterprising experimenters knew that an oversized speaker cabinet and a cabinet-less chassis could be combined. Even then, as little as 25% of the grille area might be taken up by the speaker.

Of course, it would have been a crime to destroy the front of a beautiful speaker cabinet to mount a chassis with tuning dials, volume controls, etc., protruding through the front. But there were ways around that. To maintain the integrity of the front panel of the cabinet, one place to put the tuning knob, volume control, and power switch was on the side. Of course, the chassis had to have provision for appropriate shaft extenders, as well as for other mechanical fixes.

Converting a console speaker cabinet to a complete self-contained radio was a very popular activity in the late 1920's. There were thousands of builders, and that explains why many collectors have attractive, professional-looking radios that they can't seem to be able to identify.

The cabinets themselves were made by hundreds of different cabinet makers; many of them didn't bother to label their work. All it took was a few simple alterations, such as adding a shelf, to be able to mount the chassis in the cabinet.

A homemade tuning knob (with a painted dial) that is mounted on

the side of a cabinet is a good clue that a radio wasn't originally a console radio. Converting those speaker cabinets to console radios surely didn't please the cabinet manufacturers, because the added shelves and other components did little for the cabinet's sound quality. If a back panel was present, it had to be removed to allow heat dissipation, and heat was something there was plenty of in early chassis with big tubes. Also, an AC-powered amplifier located close to a speaker often created hum that didn't exist when the speaker was mounted in the cabinet alone.

Baffle design

Sound waves emanating from the front of the speaker cone must be separated from the out-of-phase sound waves emanating from the rear. One fairly successful attempt to separate those sound waves looks like a speaker mounted on a paddle. The "paddle" is called a baffle board, and the assembly was designed to

Learn the IBM PC's secrets with the MICROPROFESSOR 1/88



Students, engineers, or technicians—
Now you can learn micro-processing and understand the technology which made the IBM PC famous.

The MPF-1/88 features:

- extensive documentation
- 16-bit central processor
- full-size keyboard
- special options

Three tutorial guides cover all capabilities. The ideal training tool! If the IBM PC or micro-processing are in your future, you owe yourself an MPF-1/88. Invest now!

Only \$349.95

Plus—

- Check this box for a FREE MPF 1-88 tutorial textbook when you order within 7 days. \$24.95 value



Dept. RE1086
5326 9th Ave. NE
Seattle, WA 98105-3617

For immediate action call TOLL FREE:

1-800-426-1044

Full money back guarantee.



CIRCLE 181 ON FREE INFORMATION CARD

Be an FCC LICENSED ELECTRONIC TECHNICIAN!



Learn at home in spare time. No previous experience needed.

No costly school. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radiotelephone License". This valuable license is your "ticket" to thousands of exciting jobs in Communications, Radio-TV, Microwave, Computers, Radar, Avionics and more! You don't need a college degree to qualify, but you do need an FCC License.

No Need to Quit Your Job or Go To School
This proven course is easy, fast and low cost! **GUARANTEED PASS** — You get your FCC License or money refunded. **Send for FREE facts now. MAIL COUPON TODAY!**

COMMAND PRODUCTIONS

FCC LICENSE TRAINING, Dept. 90
P.O. Box 2223, San Francisco, CA 94126
Please rush FREE details immediately!

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

SEE YOUR DEALER TODAY

FROM



HERE'S A TIP THAT'S PERFECT!

AM/FM AUTO RADIO AND CB

'Firestik' II

GOLDEN SERIES

BARE-HANDS TUNABLE "NO TOOLS NEEDED" HIGH PERFORMANCE ANTENNAS

ALSO ANTENNAS FOR CORDLESS TELEPHONES MONITOR SCANNERS

Dealer & Distributor Inquiries Invited
SEND FOR FREE CATALOG

'Firestik' Antenna Company
2614 East Adams/Phoenix, AZ 85034

Name _____
Street _____
City _____
State _____ Zip _____

Serving the CB and Communications Market Since 1962.

5-YEAR REPLACEMENT WARRANTY

CIRCLE 100 ON FREE INFORMATION CARD

OCTOBER 1986

complement the furniture that was in style at that time (the late 1920's).

One baffle board, the 1928-ish *Musicone*, was made by Crosley. When first introduced, the *Musicone* sold for under \$40.00 complete. That was quite a buy, when you consider that a magnetic speaker was included. The *Musicone* is an attractive piece of furniture with an ornate, scalloped, solid mahogany baffle, and a three-legged stand. Standing about 40 inches tall, the baffle of

the *Musicone* can be adjusted from side to side to accommodate the listener's pleasure.

As with other components of developing radio, there was much controversy over which type of cabinet was best, and how components should be mounted inside it. Some designers thought that the speaker should be mounted in the top of the cabinet so that sound would be directed at the ears of the listeners in the room. Many readers have sent in photos

of that type of antique radio, such as the Grigsby Grunow *Majestic*; some RCA models with a phono mounted over the speaker (from about 1933); some RCA Radiolas; the Stromberg-Carlson *Highboy*, and several Philco models, such as the nine-tube model *90B* shown in Fig. 2.



FIG. 2

It may have been a good idea to mount the speakers at ear height, but tuning some of those sets was difficult. You might have to get down on your knees to see the tuning dial, which sometimes was mounted a scant 14 inches above the floor.

So some people used the bottom part of the speaker cabinet as a baffle. The speaker faced downward, so sound came out of the bottom of the cabinet. That type of cabinet could be used only in rooms with heavily carpeted floors, because the echoes that result could degrade the sound quality.

The speaker-design wars ended in a compromise: Speakers were mounted in the bottom of the front panel facing forward. The difference in sound (from the upper position) wasn't noticeable, and the radio was much easier to tune when the dial was mounted above the speaker.

Early speaker cabinets often had thin supporting legs, but later the legged cabinets gave way to models that were enclosed almost all the way to the floor. The extra cabinet, besides conforming to more modern ideas about furniture design, gave the engineers new ways of reinforcing the bass notes. The extra length of the cabinet made it

★ CABLE TV SPECIALS ★

CONVERTERS

JERROLD:	DRZ-3DIC105—66 Channel Wireless	\$199.⁹⁵
	JRX-3 DIC—36 Channel Corded Remote	\$149.⁹⁵
	JSX-3 DIC—36 Channel Set Top	\$129.⁹⁵
	SB-3—'The Real Thing'	\$119.⁹⁵

MAGNAVOX:	6400—60 Channel Wireless w/Parental Lockout for Jerrold systems	\$199.⁹⁵
------------------	------------------------------------------------------------------------------	----------------------------

ZENITH:	Z-TAC Cable Add-On	\$225.⁰⁰
----------------	---------------------------------	----------------------------

VIEW STAR:	EVSC-2000—60 Channel Wireless— with Parental Lockout	\$ 99.⁹⁵
-------------------	-------------------------------------------------------------------	----------------------------

	EVSC-2000A-B—Same as above with A-B Switch	\$109.⁹⁵
--	---------------------------------------------------------	----------------------------

	View Star 1000—60 Channel Wireless— with Volume	\$119.⁹⁵
--	--------------------------------------------------------------	----------------------------

MISCELLANEOUS

OAK:	N-12 Mini-Code	\$ 89.⁹⁵
	N-12 Mini-Code Vari-Sync	\$109.⁹⁵
	N-12 Mini-Code Vari-Sync Plus Auto On-Off ..	\$165.⁰⁰

JERROLD:	400 & 450 Handheld Transmitters	\$ 29.⁹⁵
-----------------	--------------------------------------------------	----------------------------

HAMLIN:	MLD-1200	\$ 99.⁹⁵
----------------	-----------------------	----------------------------

NEW ITEMS:	Standard Components—66 Channel Wireless— with Parental Lockout \$	99.⁹⁵
-------------------	--------------------------------------------------------------------------	-------------------------

Scientific Atlanta **Call for Price**

	Power Zapper Stun Gun, 46, 000V	\$ 59.⁹⁵
--	----------------------------------------------	----------------------------

	K-40 Radar Detector—Dash Model	\$199.⁹⁵
--	---------------------------------------------	----------------------------

	K-40 Radar Detector—Remote	\$229.⁹⁵
--	-----------------------------------------	----------------------------

ALL UNITS GUARANTEED. QUANTITY PRICES AVAILABLE.

UNITED ELECTRONIC SUPPLY

P.O. BOX 1206 • ELGIN, ILLINOIS 60121 • 312-697-0600

possible to delay the sound waves (by bouncing them around inside the cabinet) until they were in phase with the waves coming from the front of the cone.

Troubleshooting hints

If you have a cabinet with a "Labyrinth," you must remove a felt hood to get at the speaker. Be sure to replace the hood (behind the speaker) and all cabinet parts, or the sound will not be reproduced as the manufacturer intended. Also, speaker cabinets without backs should stand about six inches from a wall, or in a corner for best sound.

Most early cabinets were made of extremely heavy wood. The "Sonic Arc" baffle made by RCA required a heavy cabinet. So did their model that pumped bass tones through pipes and emitted them in phase through the bottom of the baseboard.

When you dismantle those cabinets to service the loudspeaker, don't destroy all the early engineers' hard work. Be sure to replace everything just as it was when you finish. Remember: that includes any sound-deadening material, and especially the heavy flat or curved backboards.

Have and needs

We have one "have" this month, and a couple of "needs."

Tony Peterson (800 12th Ave. NE, Blaine, MN 55434) needs a 1939 Stromberg Carlson, 12-tube remote control unit.

John Kendall (301-877-3593) has a Jackson model 648 tube tester for antique tubes. George E. Kemmet (60-05 70th Ave., Ridgewood, NY 11385) needs someone to repair a Majestic Model 90.

Help needed

I am compiling a list of useful reading material for inclusion in a future column. If you have a book, magazine, newsletter, catalog, reprint, or other source of information that you consider particularly useful, I'd appreciate it if you would let me know about it. Please include a sample issue, or complete publication data, including a source where it can be purchased by our readers. R-E

OVER 2,000 TUBE TYPES IN-STOCK

78% - 90% off list

Plus thousands of
electronic parts
including

- VCR/Cable Accessories
- Telephone Accessories
- Audio Accessories
- Computer Accessories
- Capacitors, Resistors, Diodes, etc.
- Speakers
- Many other items

Send for FREE
Catalog

Steven



MAIL ORDER ELECTRONICS CORP.
P.O. Box 698 Melville, New York 11747
(516) 752-0060

CIRCLE 189 ON FREE INFORMATION CARD

COMMUNICATIONS CORNER

continued from page 92

where on the screen.

If you think that a single character per line may not provide much information, bear in mind the fact that there are 30 usable fields per second. So in two seconds the system can transmit almost two complete lines of subtitles, which the microprocessor then integrates into a single display. Characters don't come up on the screen one at a time unless the captioning is being done in real time.

You might wonder whether the adapter can simply strip off the video information and display only text (in the manner of Teletext). A Teletext bulletin-board is, in fact, one of the options provided by the adapter's function selector. For example, the Teletext mode is used to piggyback news bulletins from the ABC network onto broadcasts, and real-time school news and notices on educational stations. R-E

Get in on...
ELECTRONICS!



TRAIN TODAY for an exciting money-making career in:

- Electronics Engineering Technology
- Computer Programming • Data Processing
- Information Systems • Drafting with C.A.D.

NATIONAL EDUCATION CENTERS has 50 campuses nationwide, so there's a Center near you. In as little as 9 months, you can train for a high-tech career, in a state-of-the-art environment.

ASK ABOUT OUR BENEFITS! Day and Evening classes, Financial Aid to those who qualify, and Job Placement Assistance! Many of our schools are Approved for Veterans Training, and all are accredited members of either N.A.T.T.S. or A.I.C.S.

SO DON'T DELAY! For information send in the handy coupon today. Or call 7 days a week —

TOLL-FREE:



**National
Education
Centers**

1-800-722-7337
Ext. 210

National Education Centers — Headquarters
1732 Reynolds - Irvine, CA 92714

The program I am interested in is: _____
Year of High School Graduation or G.E.D. _____

NAME: _____

ADDRESS: _____

CITY/STATE/ZIP: _____

PHONE: _____

RE108



- General Communication
- Industry
- Marine VHF
- Scanners
- Amateur Bands
- CB Standard
- CB Special
- Microprocessor

Call or Write
JAN CRYSTALS
P.O. Box 06017
Fort Myers
FL 33906-6017
(813) 936-2397

CIRCLE 104 ON FREE INFORMATION CARD 97

OCTOBER 1986

MARKET CENTER

PLANS AND KITS

CATALOG: Hobby/broadcasting/1750 meters/ham/CB: transmitters, amplifiers, antennas, scramblers, bugging devices, more! **PANAXIS**, Box 130-F10, Paradise, CA 95969.

STEREO TV adapter kit Easily converts any TV/VCR to receive the new stereo TV sound. Contains all parts PCB and instructions to build a quality stereo decoder. For additional information send SASE to **SOKOLOWSKI**, Box 150, Elmont, NY 11003.

CRYSTAL radio sets, plans, parts, kits, catalog \$1.00. **MIDCO**, 660 North Dixie Highway, Hollywood, FL 33020.

BUILD this five digit panel meter and square wave generator including an ohms, capacitance and frequency meter. Detailed instructions \$2.50. **BAGNALL ELECTRONICS**, 179 May, Fairfield, CT 06430.

VOICE disguisers! Telephone bugs! FM bugs! Other kits! Send stamped envelope: **XANDI**, Box 25647, Dept. 60C, Tempe, AZ 85282.

EPROM, EEPROM zapper kit. Stand alone, RS232, parallel. \$5.00 plans, \$99.00 kit, free literature. **MICRO KIT**, 6910 Patterson, Caledonia, MI 49316 (616) 791-9333.

CLASSIFIED AD ORDER FORM

To run your own classified ad, put one word on each of the lines below and send this form along with your check to:

Radio-Electronics Classified Ads, 500-B Bi-County Boulevard, Farmingdale, NY 11735

PLEASE INDICATE in which category of classified advertising you wish your ad to appear. For special headings, there is a surcharge of **\$23.00**.

Plans/Kits Business Opportunities For Sale
 Education/Instruction Wanted Satellite Television

Special Category: \$23.00

PLEASE PRINT EACH WORD SEPARATELY, IN BLOCK LETTERS.

(No refunds or credits for typesetting errors can be made unless you clearly print or type your copy.) Rates indicated are for standard style classified ads only. See below for additional charges for special ads. **Minimum: 15 words.**

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15 (\$42.75)
16 (\$45.60)	17 (\$48.45)	18 (\$51.30)	19 (\$54.15)	20 (\$57.00)
21 (\$59.85)	22 (\$62.70)	23 (\$65.55)	24 (\$68.40)	25 (\$71.25)
26 (\$74.10)	27 (\$76.95)	28 (\$79.80)	29 (\$82.65)	30 (\$85.50)
31 (\$88.35)	32 (\$91.10)	33 (\$94.05)	34 (\$96.90)	35 (\$99.75)

We accept MasterCard and Visa for payment of orders. If you wish to use your credit card to pay for your ad fill in the following additional information (Sorry, no telephone orders can be accepted.):

Card Number

Expiration Date

Please Print Name

Signature

IF YOU USE A BOX NUMBER YOU MUST INCLUDE YOUR PERMANENT ADDRESS AND PHONE NUMBER FOR OUR FILES. ADS SUBMITTED WITHOUT THIS INFORMATION WILL NOT BE ACCEPTED.

CLASSIFIED COMMERCIAL RATE: (for firms or individuals offering commercial products or services) \$2.85 per word prepaid (no charge for zip code)...**MINIMUM 15 WORDS.** 5% discount for same ad in 6 issues; 10% discount for same ad in 12 issues within one year; if prepaid. **NON-COMMERCIAL RATE:** (for individuals who want to buy or sell a personal item) \$2.30 per word, prepaid....no minimum. **ONLY FIRST WORD AND NAME** set in bold caps at no extra charge. Additional bold face (not available as all caps) **50¢ per word additional (20% premium).** Entire ad in boldface, **add 20% premium** to total price. **TINT SCREEN BEHIND ENTIRE AD:** add 25% premium to total price. **TINT SCREEN BEHIND ENTIRE AD PLUS ALL BOLD FACE AD:** add 45% premium to total price. **EXPANDED TYPE AD:** \$4.30 per word prepaid. All other items same as for STANDARD COMMERCIAL RATE. **TINT SCREEN BEHIND ENTIRE EXPANDED TYPE AD:** add 25% premium to total price. **TINT SCREEN BEHIND ENTIRE EXPANDED TYPE AD PLUS ALL BOLD FACE AD:** add 45% premium to total price. **DISPLAY ADS:** 1" x 2 1/4"—\$310.00; 2" x 2 1/4"—\$620.00; 3" x 2 1/4"—\$930.00. **General Information:** Frequency rates and prepayment discounts are available. **ALL COPY SUBJECT TO PUBLISHERS APPROVAL. ADVERTISEMENTS USING P.O. BOX ADDRESS WILL NOT BE ACCEPTED UNTIL ADVERTISER SUPPLIES PUBLISHER WITH PERMANENT ADDRESS AND PHONE NUMBER.** Copy to be in our hands on the 12th of the third month preceding the date of the issue. (i.e., August issue copy must be received by May 12th). When normal closing date falls on Saturday, Sunday or Holiday, issue closes on preceding working day.

BUILD THIS ELECTRONIC DIGITAL LOCK

- thousands of combinations
- wrong No. alarm
- use 9-12VDC • led indicator
- control up to 200W
- good for home and auto security
- satisfaction guaranteed

every order please add \$2.00 for shipping assembled only **\$16.50**
 only **\$12.50** M.T.F. Box 810391, Houston, TX. 77281

CABLE and Subscription TV secret manual. New expanded edition. Build your own descramblers, converters. Instructions, schematics for: sinewave, inband/outband gated sync pulse, SSAVI—(HBO, Showtime, Cinemax, UHF, Etc. Send \$8.95 to **CABLETRONICS**, Box 30502R, Bethesda, MD 20814.

CABLE TV Converters: Jerrold Products include "New Jerrold Tri-Mode." SB-3, Hamlin, Oak VN-12, M-35-B, Zenith, Magnavox, Scientific Atlanta, and more. (Quantity discounts) **60 day warranty. Service converters sold here. For fast service C.O.D. orders accepted. Send SASE (60 cents postage) or call for info (312) 637-4408. HIGGINS ELECTRONICS, 5143-R, W. Diversey, Chicago, IL 60639. No Illinois orders accepted.**

PROJECTION TV... Convert your TV to project 7 foot picture. Results comparable to \$2,500 projectors. Total cost less than \$30. Plans and 8" lens \$21.95. Illustrated information free. **MACROCOMAGB**, Washington Crossing, PA 18977. Credit card orders 24 hours (215) 736-3979.

MOBILE telephone using your 2-way radio, plans \$9.95, with Pc/brds \$24.95. Parts available. **CURRENT DEVELOPMENT CORP**, Box 384, Westmoreland, NY 13490.

TELEPHONE bug, FM room bug schematics with detailed construction procedures using Radio Shack's numbered parts. Both, \$6.00. Receivers available. **SCHEFFIELD ELECTRONICS**, 7223 Stony Island, Chicago, IL 60649.

FLASH 6 bright LED's, random pattern. Round etched board plus schematics, \$2.79 post-paid. **PARAWING**, PO Box 65, Menlo Park, CA 94026.

STRANGE stuff. Plans, kits, new items. Build satellite dish \$69.00. Descramblers, bugs, adult toys. Informational photo package \$3.00 refundable. **DIRIJO CORPORATION**, Box 212, Lowell, NC 28098.

FOR SALE

TUBES new, unused. Send self-addressed, stamped envelope for list. **FALA ELECTRONICS**, Box 1376-2, Milwaukee, WI 53201.

LINEAR parts, tubes, transistors —MRF454 \$16.00, MRF455 \$12.00, MRF477 \$11.00, MRF492 \$18.00. Catalog. **RFPC**, Box 700, San Marcos, CA 92069 (619)744-0728.

OLDTIME radio programs on high quality tapes. Comedy! Adventure! Music! Free catalog. **CARL F. FROELICH**, Heritage Farm, New Freedom, PA 17349.

TV tunable notch filters, free brochure. **D.K. VIDEO**, Box 63/6025, Margate, FL 33063 (305)752-9202.

TEST equipment, reconditioned. For sale. \$1.25 for catalog. **WALTER'S**, 2697 Nickel, San Pablo, CA 94806 (415)724-0587.

LASERS and nightvision surplus components. Free catalog. **M.J. NEAL COMPANY**, 6672 Mallard Ct., Orient, OH 43146.

CABLE-TV converters and descramblers. Low prices, quality merchandise, we ship C.O.D. Send \$2.00 for catalog. **CABLETRONICS UNLIMITED**, P.O. Box 266 South Weymouth, MA 02190. (617) 871-6500.

DESCRAMBLER plans for Jerrold. Theory, schematic, parts list, waveforms. For speedy delivery send \$10.00 cash or money order. **BAY STATE ELECTRONICS**, P.O. Box 63, Accord, MA 02018.

FREE Adapter (limited offer) with **Assortment #103**—consisting of **Toko Coils** 144LY-120K, 520 HN-3000023, BKAN-K555AXX (2); **PCB; Transistors** 2N3904 (2), BFQ85 (sub); **IC's** 7812, 74123, MC1330A1P; **Diodes** 1N914, 1N5231B. Only \$25.00. 10% discount for 5 or more. Shipping \$3.00/order MC/Visa/COD. **Toll free 1-800-821-5226 Ext. 426** (orders). **JIM RHODES, INC.**, 1025 Ransome Lane, Kingsport, TN 37660.

TUBES, name brands, new, 80% off list. **KIRBY**, 298 West Carmel Drive, Carmel, IN 46032.

INDIVIDUAL Photofact-folders #1 to #1400. \$3.00 postpaid. **LOEB**, 414 Chestnut Lane, East Meadow, NY 11554.

ELECTRON tubes—radio, TV & industrial types—huge inventory. Call toll free (800) 221-5802 or write Box **ESC TRANSLETORNIC, INC.**, 1365 39th St., Brooklyn, NY 11218, (718) 633-2800.

WHOLESALE catalog of unusual money making electronic items. Dealers wanted. Rush \$1. **CROSLEY (A)**, Box 840, Champlain, NY 12919.

FREE transistors: Sample of PN2222 and 2N3904 with our **Catalog of Budget Priced Electronic Components** for hobbyists and industry. Send \$2.00 P&H (refundable) **BUDGET ELECTRONICS**, Box 1477, Moreno Valley, CA 92388 (714) 653-1663.

BUGGED? Wiretapped? Find out fast. Countermeasures equipment catalog \$1.00. **CAPRI ELECTRONICS**, Route 1R, Canon, GA 30520.

WHOLESALE car-radio computer telephone audio video accessories antenna catalog (718) 897-0509 **D&WR**, 68-12 110th St., Flushing, NY 11375.

SB3 descrambler parts to construct project in Feb/84 Radio-Electronics. \$49.95 (Dealer inquires invited). **CROSLEY**, Box 840, Champlain, NY 12919.

WORLDS best channel 3 notch filter. \$39.95. (Dealer inquires invited). **CROSLEY (A)**, Box 840, Champlain, NY 12919.

SPECTACULAR strobe light chasers, stroboscopic devices, **Helium-Neon Laser components**, scientific items, more! Free catalog. **ALLEGRO ELECTRONIC SYSTEMS**, #3R Mine Mountain, Cornwall Bridge, CT 06754.

TUBES: "oldest," "latest". Parts, components, schematics. SASE for list. **STEINMETZ**, 7519 Maplewood Ave., R.E., Hammond, IN 46324.

ELECTRONICS. \$1.50 brings flyer, grab bag. **LYNN JOHNSON**, 2221 The Alameda #176, Santa Clara, CA 95050.

ANTIQUE radio hobbyists—20 page catalog of tubes, parts, and literature for radio restoration. Send \$2.00 to **ANTIQUE ELECTRONIC SUPPLY**, 688 W. First St., Tempe, AZ 85281.

CABLE-TV converters and equipment. Plans and parts. Build or buy. Free information. **C&D ELECTRONICS**, PO Box 1402, Dept. RE, Hope, AR 71801.

CABLE-TV

WE'LL MATCH OR BEAT ANYONE'S
ADVERTISED RETAIL OR WHOLESALE PRICES!

BONANZA!

ITEM	SINGLE UNIT PRICE	DEALER 10-UNIT PRICE
RCA 36 CHANNEL CONVERTER (CH. 3 OUTPUT ONLY)	29.95	18.00 ea.
PIONEER WIRELESS CONVERTER (OUR BEST BUY)	88.95	72.00 ea.
LCC-58 WIRELESS CONVERTER	92.95	76.00 ea.
JERROLD 450 WIRELESS CONVERTER (CH. 3 OUTPUT ONLY)	105.95	90.00 ea.
SB ADD-ON UNIT	109.95	58.00 ea.
BRAND NEW — UNIT FOR SCIENTIFIC ATLANTA	Call for specifics	
MINICODE (N-12)	109.95	58.00 ea.
MINICODE (N-12) VARISYNC	119.95	62.00 ea.
MINICODE VARISYNC W/AUTO ON-OFF	179.95	115.00 ea.
M-35 B (CH. 3 OUTPUT ONLY)	139.95	70.00 ea.
M-35 B W/AUTO ON-OFF (CALL FOR AVAILABILITY)	199.95	125.00 ea.
MLD-1200-3 (CALL IF CH. 2 OUTPUT)	109.95	58.00 ea.
INTERFERENCE FILTERS — CH. 3	24.95	14.00 ea.
JERROLD 400 OR 450 REMOTE CONTROLLER	29.95	18.00 ea.
ZENITH SSAVI CABLE READY (DEALER PRICE BASED ON 5 UNITS)	225.00	185.00 ea.

SPECIFY CHANNEL 2 or 3 OUTPUT Other products available — Please Call

Quantity	Item	Output Channel	Price Each	TOTAL PRICE
California Penal Code #593-D forbids us from shipping any cable descrambling unit to anyone residing in the state of California.			SUBTOTAL	
Prices subject to change without notice.			Shipping Add \$3.00 per unit	
			COD & Credit Cards — Add 5%	
			TOTAL	

PLEASE PRINT

Name _____
 Address _____ City _____
 State _____ Zip _____ Phone Number () _____
 Cashier's Check Money Order COD Visa Mastercard
 Acct # _____ Exp. Date _____
 Signature _____

FOR OUR RECORDS:

DECLARATION OF AUTHORIZED USE — I, the undersigned, do hereby declare under penalty of perjury that all products purchased, now and in the future, will only be used on cable TV systems with proper authorization from local officials or cable company officials in accordance with all applicable federal and state laws.

Dated: _____ Signed: _____

Pacific Cable Company, Inc.

7325 1/2 RESEDA BLVD., DEPT. R-10 • RESEDA, CA 91335
 (818) 716-5914 • No Collect Calls • (818) 716-5140

IMPORTANT: WHEN CALLING FOR INFORMATION
 Please have the make and model # of the equipment used in your area. Thank You

Quality Microwave TV Antennas

Multi-Channel 1.9 to 2.7 GHz
40dB Gain True Parabolic 20 Inch Dish
Complete System \$99.95 (plus shipping)
Dealerships, Qty. Pricing, Replacement Parts

Phillips-Tech Electronics

P.O. Box 8533 • Scottsdale, AZ 85252
(602) 947-7700 (\$3.00 Credit all phone orders!)

MasterCard • Visa • C.O.D.s

RESTRICTED technical information: Electronic surveillance, schematics, locksmithing, covert sciences, hacking, etc. **Huge selection. Free brochure: MENTOR-Z**, 135-53 No. Blvd., Flushing, NY 11354.

TURBO circuit analysis Generates matrix equations for AC, DC and transient analysis. Source code for worst case, plots. Requires MS-DOS and Turbo Pascal or FORTRAN. VISA/MC. \$149.00.
CLIFFORD VANDER YACHT, Computer Consultant, 3778 Hitching Post Road, Jackson, MI 49201, (517)782-2297.

HIGH gain descramblers, CRT automatic dimmer, SCR Tester, plus other unusual electronic devices. Send \$3.00 for info. **RB ELECTRONICS ENGINEERING**, PO Box 643, Kalamazoo, MI 49005.

CABLE TV converters manual and wireless Jerrold DRZ DRX Philips volume converters. **REDCOAT ELECTRONICS**, PO Box 504, Jamaica, NY 11475. (718) 459-5088.

SCIENTIFIC Atlanta stand alone—8500 series (Original units), remote control. Fully guaranteed. \$250.00. **N.A.S.**, (213) 631-3552.

FREE electronics parts. All sorts, for inventors, designers, experimenters. How and where to get them. No exaggeration. Send single fee \$6.95 to **AMERICAN TRANS-GLOBAL**, Box 7033, Huntington, WV 25775.

CABLE TV equipment, Scientific Atlanta, Zenith, Jerrold, Oak, send \$2.00 for catalog. **K.D. VIDEO**, P.O. Box 29538 Mpls., MN 55429.

SURPLUS software, hardware, audio kits, solar cells, lots of bargains. Free catalog. GIL ELECTRONICS, Box 1628-H, Soquel, CA 95073.

DISK drives repaired. Stop data errors, loss of valuable information. Driveteck will tune up your disk drive \$35. IBM type \$30. Apple C64 type. Call for others. **DRIVETECH**, (617) 924-2122. P. O. 234, Boston MA 02258.

SPECIAL purchase sprague capacitors, 20,000 MUF 25V \$2.50 ea. 2 for \$4.00 postpaid. Unused surplus. **CHARLES BARRETT**, 5312 Bruckner, Lewisville, TX 75028.

I-4 GHZ equipment VCO's, signal sweep generators, LNAs, detectors. Send SASE. **ROENSCH MICROWAVE**, RR 1, Brookfield, MO 64628. (816) 895-5431.

SELL blank video cassettes. Super high grade Olympia VHS T-120. Fully guaranteed. Only \$3.49 your cost. Add \$5.00 shipping and handling for any quantity. **STRANDBERG**, 1001 S. Elm Street, Greensboro, NC 27406. Telephone (919) 274-3775. Check, M.O., VISA or MasterCard account number & expiration date.

TUBES! 59 cents. Year Guarantee. Free catalog. Tube tester \$8.95. **CORNELL**, 4215 University, San Diego, CA 92105.

DESCRAMBLER manuals, sinewave, gated pulse, SSAVI, \$4.00 each, all three \$10.00. **DMF**, 6690 7 Mile, S. Lyon, MI 48178.

CORDLESS—phone interference? We've got the answer. Have a radar speeding ticket? We can help. Home phone extension in your car? You can have it. 50-page color catalog airmailed \$3. **DBE**, P.O. Drawer G, Waikiki, HI 96830.

TI-99/4A software/hardware bargains. Hard to find items. Huge selection. Fast service. Free catalog. **DYNA**, Box 690, Hicksville, NY 11801.

CLONE kits, modems, hard drive kits, disk drives, diskettes and printers, memory, and IC's. Distributor pricing to end users and dealers. For catalog call **1-800-833-2600**. In Ohio call 513-531-8866. Free shipping.

TUBES, \$2.49. TV, audio, special, 2000 types, SASE brings lists. **ADNF**, 6690 7 Mile, S. Lyon, MI 48178.

CATALOG: cable converters, both kits and assembled units. Built N12 mini-code \$98.00, Jerrold 400 \$99.00. Pulse descrambler kit (assembles in half hour) \$79.00, built \$120.00. Satellite descrambler kit \$120.00, built \$190.00. Surplus components, hobby kits. Send \$1.00. **MJ INDUSTRY**, Box 531, Bronx, NY 10461.

\$ \$ WIN with thoroughbred/harness, Greyhound handicapping software...\$29.95, enhanced...\$49.95. Professional football handicapping system...\$39.95. For most computers. Free information. **SOFTWARE EXCHANGE**, Box 5382RE, W. Bloomfield, MI 48033. (313) 626-7208.

PICTURE flyer lists quality electronics surplus at low prices. Since 1970. Send for the last 3 issues. **STAR-TRONICS**, Box 683, McMinnville, OR 97128.

WRITE FOR McGEE'S

SPEAKER & ELECTRONICS CATALOG

1001 BARGAINS IN SPEAKERS
toll free 1-800-346-2433 for ordering only.

1901 MCGEE STREET KANSAS CITY, MO. 64108

ATTENTION are you looking for surplus test equipment signal generator voltmeters oscilloscope. **J.B. ELECTRONICS**, 9518 Grand, Franklin Park, IL 60131.

PROGRAMMABLE telephone restrictor lets you selectively restrict outgoing calls from the keypad of any phone. Changeable code overrides system. Fully modular. \$89.95. Free brochure. **ARUS ELECTRONICS**, P. O. Box 662, Chappaqua, NY 10514.

ANTIQUE radio schematics send SASE make model number. **A. TORRES**, 604 South 11th, Las Vegas, NV 89101.

SQUEEZING additional status lights onto any cramped control panel is no problem using fiber-optics with remotely located light sources. No need to dismantle anything with our "Front-Feed" technique! Kit with detailed instructions. LED's and optical fiber sufficient for many applications: \$5.00 ppd. **HAND-IKITS**, Box 143, Hatboro, PA 19040.

MICROWAVE Antenna tuning and repair service. All makes and models. 90 day warranty. (612) 483-3037.

DECODERS converters new best prices N-1200 channel 2 & 3 \$75.00, varisync \$85.00, S.B.'s \$78.00, quantity discounts. COD's send SASE catalog. **M.D. ELECTRONICS**, 5732 South 98 Plaza #1B, Omaha, NE 68134 (402) 331-4957.

SURPLUS military/commercial test and communications equipment—1986 catalog. Send \$1. **MIL-COM EXCHANGE ELECTRONICS**, Box 982-RE, Orange Park, FL 32067-0982.



REMOVES VOCALS FROM RECORDS!

Now You can sing with the world's best bands! The Thompson Vocal Eliminator can remove most or virtually all of a lead vocal from a standard stereo record and leave the background!
Write or call for a free brochure and demo record.

LT Sound, Dept. R-1, P.O. Box 338,
Stone Mountain, GA 30086 (404) 493-1258

DO IT YOURSELF TV REPAIR

NEW...repair any TV...easy. retired serviceman reveals secrets. Write, **RESEARCH**, Rt 3, Box 601BR, Colville, WA 99114.

PRINTED-CIRCUIT BOARDS

PCB 15 cents sq-in. Free drilling. Quantity discounts. Professional work. **INTERNATIONAL ENTERPRISE**, 6452 Hazelcircle, Simivalley, CA 93063.

GUARANTEED lowest quotes. Quick service. Highest quality. Avg. \$0.12/inch **FR-4**. Prototypes through production quantities. Single, double sided and multilayered boards. Plated through holes. Call or write for quotes. **T.O.R.C.C.C.**, Box 47148, Chicago, IL 60647. (312) 342-9171. Electronic projects and components catalog available, send SASE.

INVENTORS

INVENTORS! Can you patent and profit from your idea? Call **AMERICAN INVENTORS CORPORATION** for free information. Over a decade of service. 1-800-338-5656. In Massachusetts or Canada call (413) 568-3753.

CABLE-TV DESCRAMBLERS

ALL brands available. "We won't be undersold." Dealer inquiries welcome. We ship C.O.D.'s. For catalog send \$3.00 to **CONSUMER VIDEO CORP.** (518) 783-5636 M-F 9AM-5PM E.S.T.

SPEAKER REPAIR

SPEAKER reconing-radio, hi-fi, musical instrument. All work guaranteed. **SSI**, 725 Archer St., Ft. Wayne, IN 46808 219-42-MUSIC.

THE BEST PLACE to BUY, SELL or TRADE NEW and USED EQUIPMENT

NUTS & VOLTS MAGAZINE
BOX 1111-E • PLACENTIA, CA 92670
(714) 632-7721

Join Thousands of Readers Nationwide
Every Month

ONE YEAR U.S. SUBSCRIPTIONS

\$10.00 - 3rd Class • \$15.00 - 1st Class

\$35.00 - Lifetime - 3rd Class

NUTS & VOLTS

HAM GEAR
COMPUTERS
SOFTWARE
SCANNERS • OPTICS
TEST EQUIPMENT
MICROWAVE
SATELLITE
AUDIO VISUAL
NEW PRODUCTS
COMPONENTS • KITS
ANTIQUE ELECT.
PUBLICATIONS
PLANS • SERVICES

EDUCATION & INSTRUCTION

F.C.C. Commercial General Radiotelephone License. Electronics home study. Fast, inexpensive! "Free" details. **COMMAND**, D-176, Box 2223, San Francisco, CA 94126.

COMPUTER repair career training in 5 months by accredited Florida electronics school. Lifetime placement. Financial assistance if qualified. Call **SYSTEMS TECHNOLOGY INSTITUTE**. (305) 331-2840.

FCC Commercial general radiotelephone license correspondence course. 60 individual lessons for \$89.50. Payment plan. Results guaranteed! Details free. **AMERICAN TECHNICAL INSTITUTE**, Box 201, Cedar Mountain, NC 28718.

COMPREHENSIVE EVALUATION and ADVISORY SERVICE

For professional electronic technicians by prestigious **NON-PROFIT** organization. Earn University Degree (Bachelors or Masters) through Home Study! Credit given for previous schooling and professional experience. Upgrade your status and life-style.

CONTINENTAL EDUCATION ASSOCIATES
P.O. Box 1197 • Champlain, NY 12919-1197

EPROM PROGRAMMING

HOBBYISTS; Pretested EPROMS sold with your programming installed. Program listing provided. Fast service. Write or call: **ROMULUS MICRO-CONTROL**, Box 8669, Rockville, MD 20856; (301) 540-8863.

BUY BONDS

CRYSTAL RADIO

continued from page 55

tinuity from the beginning of the coil to the end.

The coupling coil, L2, is wound in the same manner as the larger coils, but it's wound on a smaller (3/4-inch diameter) form, and is made up of 16 turns of 26-gauge DCC wire. The anchor spoke has a single mounting point, so that the coupling to L3 can be adjusting by pivoting L2 around that point.

Diode D1 can be just about any germanium diode. But if you want to keep your crystal radio authentic-looking, you should mount it in a case like the one shown in Fig 2. Such cases were commonly used to mount fixed-contact cat-whisker detectors.

The variable capacitor is a 200-pF device. It won't be easy to find, so feel free to experiment with its value. Capacitors C1 and C3 are fixed-mica types.

Perhaps the most important part of building the receiver is putting up the antenna system. For good results, your antenna should be as long and as high as possible. If you can manage to put up a 75-foot long-wire antenna, great! Just remember: your ground system is also very important. A four-foot copper pipe or rod hammered into the earth can make a good ground. If you can't manage that, try your cold-water pipe.

The wooden base shown in the photographs is about 11 by 7 inches (it's 3/4 inch thick). The edges are routed for a smooth appearance. Choose some type of hardwood, such as oak or maple for the base, and sand it well. Stain it according to taste, and then give it a couple of coats of satin-finish polyurethane. (*Sand very lightly*) between coats.

If you want to finish both sides of the breadboard base at the same time, then use four woodscrews as temporary feet. (Install them where you will be installing the rubber feet.) Finish the bottom of the breadboard first, and then turn it over and finish the top and the sides. The screws will keep the bottom of the board from touching anything else. Before you give the breadboard a second coat (which we do recommend), just be sure to let the first coat dry thoroughly. Then sand very lightly with super-fine-grit paper, and apply the second coat.

When your base is finished, it's time to start mounting parts. The parts on the prototype (and the available kit), including the coil taps, are mounted on small bakelite panels which are, in turn, mounted to the base. The main tuning capacitor, the headphone jack, and the antenna tap switch are mounted to the front panel, which is, in turn, mounted to the base using small "L" brackets.

Operating the receiver

Tuning your crystal set can be tricky business until you get used to it. The first step is to set the detector tap to the midway point, and to set the antenna tap switch, S1, to 0 (minimum inductance) and adjust L2 for maximum coupling to L3. When you plug in your high-impedance headphones, you'll hear one or more stations.

Tune to a station at the lower-frequency end of the band by adjusting the main tuning capacitor, C2, so that its plates are about 2/3 in mesh. Then reduce the coupling between L2 and L3, until you can

barely hear the station. Advance the antenna tap switch until you reach the peak volume for that station. When that station is tuned, you can reduce the coupling further between L2 and L3. While that will reduce the volume, it will increase the receiver's selectivity, so you can tune in other stations on nearby frequencies.

Once you get used to tuning the radio, you can experiment with the detector tap. If you are in a strong-signal area, you can probably get by with decreased inductance of L3. That will increase the receiver's selectivity also. **R-E**

Radio-Electronics REPRINT BOOKSTORE

- | | |
|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------|---------------------------------------------------------------------------------------------------------------------------------|
| <input type="checkbox"/> 150 TV Descrambler \$3.00
(Jan., Feb. 1981) | <input type="checkbox"/> SP10 Special Projects #10 (Spring 1984) .. \$5.50 |
| <input type="checkbox"/> 151 Build Your Own Robot \$12.00 | <input type="checkbox"/> 111 Hands-On Electronics #1 \$4.50 |
| <input type="checkbox"/> 152 8-Ball Satellite TV
Antenna \$5.00 | <input type="checkbox"/> 112 Hands-On Electronics #2 \$4.50 |
| <input type="checkbox"/> 106 Radio-Electronics back issues (1986) .. \$3.00
Write in issues desired..... | <input type="checkbox"/> 113 Hands-On Electronics #3 \$4.00 |
| <input type="checkbox"/> 105 Radio-Electronics back issues (1985) .. \$3.50
Write in issues desired..... | <input type="checkbox"/> 114 Hands-On Electronics #4 \$4.00 |
| <input type="checkbox"/> 104 Radio-Electronics back issues (1984) .. \$4.50
(December 1984 issue is not available)
Write in issues desired..... | <input type="checkbox"/> 115 Hands-On Electronics #5 \$4.00 |
| <input type="checkbox"/> 103 Radio-Electronics back issues (1983).... \$4.50
(Jan., Feb., May are not available)
Write in issues desired..... | <input type="checkbox"/> 115A Hands-On Electronics #6 \$3.50 |
| <input type="checkbox"/> 102 Radio-Electronics back
issues (1982) \$5.00
(January 1982 is not available)
Write in issues desired..... | <input type="checkbox"/> 116A Hands-On Electronics (Jan-Feb '86) .. \$3.50 |
| <input type="checkbox"/> 101 Radio-Electronics back issues (1981) .. \$6.00
(Jan., Feb., Mar., May, Dec. are not available)
Write in issues desired..... | <input type="checkbox"/> 116B Hands-On Electronics (Mar/Apr '86) .. \$3.50 |
| <input type="checkbox"/> 153 Etch your own PC boards \$3.00 | <input type="checkbox"/> 116C Hands-On Electronics (May/Jun '86) .. \$3.50 |
| <input type="checkbox"/> SP4 Special Projects #4 (Summer 1982) .. \$5.50 | <input type="checkbox"/> 116D Hands-On Electronics (Jul/Aug '86) .. \$3.50 |
| <input type="checkbox"/> SP5 Special Projects #5 (Winter 1983) .. \$5.50 | <input type="checkbox"/> 116E Hands-On Electronics (Sep/Oct '86) .. \$3.50 |
| <input type="checkbox"/> SP6 Special Projects #6 (Spring 1983) .. \$5.50 | <input type="checkbox"/> 154 How to Repair VCR's \$3.50 |
| <input type="checkbox"/> SP7 Special Projects #7 (Summer 1983) .. \$5.50 | <input type="checkbox"/> 155 IBM Typewriter to Computer \$3.00 |
| <input type="checkbox"/> SP8 Special Projects #8 (Fall 1983) \$5.50 | <input type="checkbox"/> 125 Radio-Electronics Annual 1985 \$3.50 |
| <input type="checkbox"/> SP9 Special Projects #9 (Winter 1984) \$5.50 | <input type="checkbox"/> 126 Radio-Electronics Annual 1986 \$2.50 |
| | <input type="checkbox"/> 156 How to Make PC Boards \$2.00 |
| | <input type="checkbox"/> 157 All About Kits \$2.00 |
| | <input type="checkbox"/> 158 Electro Importing Co. Catalog (1918) .. \$5.95 |
| | <input type="checkbox"/> 159 Low Frequency Receiving Techniques
Building and using VLF Antennas \$6.00 |
| | <input type="checkbox"/> 160 New Ideas - 42 circuits \$3.50 |
| | <input type="checkbox"/> 161 Descrambling (Feb., 1984) \$2.00 |
| | <input type="checkbox"/> 162 Build Your Own Satellite TV Receiver \$7.00 |
| | <input type="checkbox"/> 163 Receiving Satellite TV \$7.00 |
| | <input type="checkbox"/> 164 Modern Electronics (April 1908) \$3.00 |
| | <input type="checkbox"/> 165 How to Repair CD Disc Players \$5.00 |
| | <input type="checkbox"/> 166 Collected Works of Mohamic Ulyssis Fips
(62 pages, April Fools Collection) \$10.00 |

To order any of the items indicated above, check off the ones you want. Complete the order form below, include your payment, check or money order (DO NOT SEND CASH), and mail to Radio-Electronics, Reprint Department, 500-B Bi-County Boulevard, Farmingdale, NY 11735. Please allow 4-6 weeks for delivery.

If you need a copy of an article that is in an issue we indicate is unavailable you can order it directly from us. We charge 50¢ per page. Indicate the issue (month & year), pages and article desired. Include payment in full, plus shipping and handling charge. Make checks payable to Gernsback Publications, Inc.

ARTICLE _____

PAGES _____

MONTH _____

YEAR _____

TOTAL PAGES _____

(@ 50¢ each)

TOTAL PRICE _____

MAIL TO: Radio-Electronics

Reprint Bookstore, 500-B Bi-County Boulevard, Farmingdale, NY 11735

All payments must be in U.S. funds

SHIPPING CHARGES IN USA & CANADA

\$0.01 to \$5.00 \$1.00

\$30.01 to 40.00 \$4.75

OUTSIDE USA & CANADA

\$5.01 to \$10.00 \$1.75

\$40.01 to 50.00 \$5.75

Multiply Shipping by 2 for sea mail

\$10.01 to 20.00 \$2.75

\$50.01 and above \$7.00

Multiply Shipping by 4 for air mail

\$20.01 to 30.00 \$3.75

Total price of merchandise

\$ _____

Sales Tax (New York State Residents only)

\$ _____

Shipping (see chart)

\$ _____

Name _____

Total Enclosed \$ _____

Address _____

City _____ State _____ Zip _____

RB06

BLACK BOX DE-SI-FURING THE SOLUTION TO SATELLITE SCRAMBLING VOL. II

AMERICAN AND CANADIAN

Latest Satellite Technology available. Over 100 pages of how to build. Comes with complete schematics. Parts lists and suppliers of parts & kits.

\$29.95

BLACK BOX
DE-SI-FURING
THE SOLUTION
TO SATELLITE
SCRAMBLING

CONTENTS OF MANUAL

- 4 different types of satellite scrambling
- Modes of operation
- How to build a De-Si-Fur
- Digital audio & CRT controllers
- Digital audio processors
- Schematic dia.

To order Vol. II send postal money order only for \$29.95 plus \$3.00 shipping & handling. CALL ORDER LINE (401) 333-8775. BELLRAE DIST. CO., P.O. Box 41, Warren, RI 02885.

SATELLITE TV

CABLE TV Secrets—the outlaw publication the cable companies tried to ban. HBO, Movie Channel, Showtime, descramblers, converters, etc. Suppliers list included \$8.95. **CABLE FACTS**, Box 711-R, Pataskala, OH 43062.

CABLE TV Source Book—a complete listing of suppliers for hard-to-find converters, descramblers, technical information, schematics and much more. Full refund if not satisfied. Send \$4.95 to **CABLE**, Box 12505-R, Columbus, OH 43212.

PATENTED optical process satellite sound system. For information send \$3.00 to: **BEDINI ELECTRONICS**, PO Box 769, San Fernando, CA 91341.

SATELLITE systems \$349.00, catalog \$2.00. Also: KU band, exports. **STARLINK, INC.**, 2603-16R Artie, Huntsville, AL 35805.

DECODER true! Broadcast stereo TV-VCR complete kit PCB/parts \$29.95. **BILL'S SAT**, 451-D, Whitehouse Station, NJ 08889.

"TRIPLE-X" Satellite TV descramblers (Non Addressable). XXX—Adult Movies, Fully assembled. \$225.00. **NAS-SAT**, Box 5261, Long Beach, CA 90805, (213) 631-3552.

BUILD your own satellite system and save! Instructions, schematics, parts! Send stamped envelope: **XANDI**, Box 25647, Dept. 21F, Tempe, AZ 85282.

QUALITY products—low prices—no gimmicks—send for free brochure and 800 number to **S.S.E.**, POB 3833, Ocala, FL 32678.

Pay TV and Satellite Descrambling All New 6th Edition!

Now over 100 pages of working schematics, theory and "hard" information on all the major cable and over the air scrambling systems. Schematics and theory for all 4 satellite descrambling systems used currently. HBO, Anik-D, Fantasy, Extasy etc. New sections on digital audio coding and bypassing. Insider information included. Still the most complete source of descrambling info available \$14.95. Satellite Systems Under \$600, \$11.95. MDS Handbook \$10. Stun gun schematics \$5. Enlarged product catalog of PC's, kits and low cost satellite equipment \$2.

**Shojiki Electronics Corp., 1327R
Niagara St., Niagara Falls, NY
14303. COD's 716-284-2163**

NEW satellite descrambler manual—Decode HBO, Showtime, Cinemax, Anik-D, Fantasy, Extasy. Theory, schematics, thorough explanation of digital audio encoding. \$10.95. **CABLETRONICS**, Box 30502RE, Bethesda, MD 20814.

MULTICHANNEL microwave TV antennas high quality low prices 20 inch dish system \$45.00. High gain rod system \$55.00. **DTC DISTRIBUTORS**, Box 42010 Phoenix, AZ 85080. (602) 863-2208.

CB MODIFICATIONS

Increase channels, range, privacy! We specialize in frequency expanders, speech processors, FM converters, PLL & slider tricks, how-to books, plans, kits. Expert mail-in repairs & conversions. 16-page catalog \$2. Our 11th year!


**CBC INTERNATIONAL, P.O. BOX 31500RE,
PHOENIX, AZ 85046**

WANTED

INVENTORS! AIM wants—ideas, inventions, new products, improvements on existing products. We present ideas to manufacturers. Confidentiality guaranteed. Call toll free 1-(800) 225-5800 for information kit.

INVENTIONS, ideas, new products wanted! Industry presentation/national exposition. Call free 1-800-528-6050. Canada, 1-800-528-6060. X831.

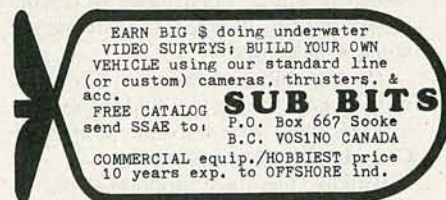INFARED remote control to work with Oak RTC-56 converter. **JAGCO DIST.**, 1323 N. 95th Ave., Omaha, NE 68114.



BUSINESS OPPORTUNITIES

MECHANICALLY inclined individuals desiring ownership of small electronics manufacturing business—without investment. Write: **BUSINESSES**, 92-R, Brighton 11th, Brooklyn, NY 11235.

YOUR own radio station! AM, FM, TV, Cable. Licensed/unlicensed. **BROADCASTING**, Box 130-F10, Paradise, CA 95969.

PROJECTION TV... Make \$\$\$'s assembling projectors... easy... results comparable to \$2500.00 projectors... Your total cost less than \$30.00... plans, 8" lens and dealers information \$20.50... illustrated information free... **MACROCOMA-GBX**, Washington Crossing, PA 18977. Creditcard orders 24 hours (215) 736-2880.

\$10.00—\$360.00 weekly! Become circular mailer. No quotas. Sincerely interested, rush stamped envelope: **NATIONAL MAILING**, Box 19759-RA10, San Diego, CA 92119.

BIG PROFITS ELECTRONIC ASSEMBLY BUSINESS

Start home. spare time. Investment knowledge or experience unnecessary. **BIG DEMAND** assembling electronic devices. Sales handled by professionals. Unusual business opportunity.

FREE: Complete illustrated literature
BARTA, RE-O Box 248
Walnut Creek, Calif. 94597

DEALERS Wanted! DMM's, solderless breadboards, soldering tools. Individuals welcome. **CENTURY INTERNATIONAL COMPANY**, Box 29762, Dallas, TX 75229.

I have over 100 sure fire businesses you can start with little or no investment. Now you can start a part-time business in over 100 different fields including mail order and real estate. Send \$1.00 to **RICHARD WILSON**, 6215 S. Wabash, #304, Chicago, IL 60637 for shipping.

ATTENTION—income opportunities! Need money in a hurry? See amazing profits the first month. Learn a trade technique, secretly in real estate. Results guaranteed! A proven realtor's secret. Limited offer! Rush \$15.00 or write for details to: **RICHARD WILSON**, 6215 S. Wabash St., #304, Chicago, IL 60637.

RECOVER pure gold from old circuit boards, computers, electronic junk. Easy method. Send \$5.00 **RECYCLING**, Box 11216R, Reno, NV 89510-1216.

ALL SALES SUBJECT TO THE TERMS OF OUR 90 DAY LIMITED WARRANTY. FREE COPY UPON REQUEST.

THE NEW 65/9028 VT ANSI VIDEO TERMINAL BOARD!


* FROM LINGER ENTERPRISES *

A second generation, low cost, high performance, mini sized, single board for making your own RS232 Video Terminal. Use as a computer console or with a MODEM for hook up to any of the telephone-line computer services.

FEATURES:

- * Uses the new SMC 9028 Video Controller Chip coupled with a 6502A CPU.
- * RS-232 at 16 Baud Rates from 50 to 19,200
- * On board printer port!
- * 24 X 80 format (50/60 Hz).
- * For 15,750 Hz (Horiz.) monitors.
- * 3 Terminal Modes: H-19, ADM3A, and ANSI X 3.64-1979
- * Wide and thin-line graphics.
- * White characters on black background or reversed.
- * Character Attributes: De-Inten, Inverse or Underline.
- * Low Power: 5VDC @ .7A, ± 12VDC @ 20MA.
- * Mini size: 6.5 X 5 inches.
- * Composite or split video.
- * 5 X 8 Dot Matrix characters (U/L case).
- * Answer back capability.
- * Battery backed up status memory.
- * For ASCII parallel keyboard.

MICRO SIZE!

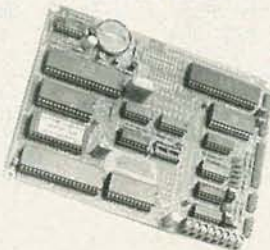

\$99.95
(Full Kit)

**SOURCE DISKETTE:
PC/XT FORMAT
5 1/4 IN. \$15**

ADD \$40 FOR A&T

Digital Research Computers

(OF TEXAS)

P.O. BOX 381450 • DUNCANVILLE TX 75138 • (214) 225-2309

Call or write for a free catalog on Z-80 or 6809 Single Board Computers, SS-50 Boards, and other S-100 products.

TERMS: Add \$3.00 postage. We pay balance. Orders under \$15 add 75c handling. No C.O.D. We accept Visa and MasterCard. Texas Res. add 5-1/8% Tax. Foreign orders (except Canada) add 20% P & H. Orders over \$50 add 85c for insurance.

One tree can make
3,000,000 matches.



One match can burn
3,000,000 trees.



A Public Service of This Magazine
& The Advertising Council


TENMA

TENMA Combination Function Generator and Frequency Counter

■ Six digit display ■ Output range: .2Hz-2MHz: seven ranges ■ Counter range: .1Hz-10MHz ■ 5-15V TTL and CMOS output ■ Wave forms: sine, triangle, square, pulse, and ramp. For detailed specifications call for a complete Tenma catalog.

#72-380

\$21990
(ea.)

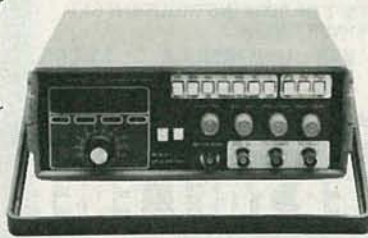

THE NAME YOU CAN TRUST IN ELECTRONIC TEST EQUIPMENT

TENMA 120MHz Frequency Counter

■ Eight digit LED display ■ Measurement range: .1Hz-120MHz ■ High input sensitivity of 20mV RMS. For detailed specifications call for a complete Tenma catalog.

#72-375

\$18995
(ea.)



TENMA 0-18V 3A Power Supply

■ Regulated outputs — constant volt or constant current, both are continuously variable ■ Can be connected in series or parallel for more voltage or current output ■ Reverse polarity and overload protected ■ Isolated output. For detailed specifications call for a complete Tenma catalog.

#72-420

\$9950
(ea.)



TENMA 3 1/2 Digit LCD Multimeter

■ Measures resistance, AC-DC voltage and current ■ Diode and hFe transistor tests ■ Overload protection ■ 10Mohm input impedance ■ Carrying case included. For detailed specifications call for a complete Tenma catalog.

#72-050

\$3980
(ea.)



TENMA Digital LCR Meter

■ Measures inductance, capacitance and resistance ■ L = 1μH-200H, C = .1pF-200μF, R = .01ohm-20Mohm ■ Carrying case included. For detailed specifications call for a complete Tenma catalog.

#72-370

\$14995
(ea.)




TENMA Clamp-On/DMM

■ Measures AC current via clamp ■ High quality built-in DMM measures DC volts, AC volts, resistance, AC current ■ Peak hold ■ Data hold ■ Audible continuity buzzer ■ Test leads and carrying case included. For detailed specifications call for a complete Tenma catalog.

#72-395

\$7995
(ea.)

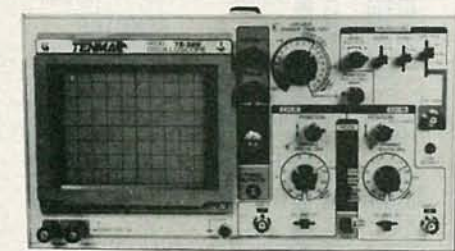

TENMA 20MHz Dual Trace Oscilloscope

■ Two high quality 10:1 probes included. For detailed specifications call for a complete Tenma catalog.



#72-320

~~\$38995~~

SPECIAL!
\$34995
(ea.)

Terms:

- \$10 minimum order. \$1.00 charge for orders under \$10.
- \$20 minimum charge card order.
- Orders shipped UPS C.O.D.
- Most orders shipped within 24 hours.
- Sales office open 8:30 am to 7:00 pm Saturdays 10:00 am to 3 pm EST.
- For prepaid orders add \$2.75 for shipping and handling.
- Should shipping and handling charges exceed \$2.75, the balance due will be sent C.O.D.



TENMA 30A Power Supply

■ Output voltage: 1-15VDC ■ Lighted cross needle meter. Displays voltage, current and power simultaneously ■ Output current: 30A, 22A continuous ■ Fan cooled. For detailed specifications call for a complete Tenma catalog.

#72-035

\$19900
(ea.)

Be Sure To Call For Your FREE Catalog! Over 6,000 Items!



We also have ... a full line of test equipment, computer accessories, telephone accessories, speakers, television parts, flybacks, yokes, switches, fuses, lamps, capacitors, resistors, cartridges, styli, wire, CATV equipment, the largest selection of original Japanese semiconductors in the country and more.



MCM ELECTRONICS

858 E. Congress Park Dr.
Centerville, Ohio 45459-4072
(513) 434-0031

SOURCE NO. RE-25

CALL TOLL FREE 1-800-543-4330
In Ohio 1-800-762-4315 • In Alaska and Hawaii 1-800-858-1849

CIRCLE 87 ON FREE INFORMATION CARD

20MB HARD DISK SYSTEM ONLY \$389⁹⁵!

DISK DRIVES FOR APPLE COMPUTERS

AP-150
\$99.95



- 1/2" HT. DIRECT DRIVE
- 100% APPLE COMPATIBLE
- SIX MONTH WARRANTY

BAL-500
\$129.95



- TEAC MECHANISM-DIRECT DRIVE
- 100% APPLE COMPATIBLE
- FULL ONE YEAR WARRANTY

AP-135
\$129.95



- FULL HT SHUGART MECHANISM
- DIRECT REPLACEMENT FOR APPLE DISK II
- SIX MONTH WARRANTY

DOUBLE SIDED!
MAC535
\$249.95



- 3.5" ADD-ON DISK DRIVE
- 100% MACINTOSH COMPATIBLE
- DOUBLE SIDED 800K BYTE STORAGE
- HIGH RELIABILITY DRIVE
- HAS AUTO-EJECT MECHANISM
- FULL ONE YEAR WARRANTY

AD-3C
\$139.95




- 100% APPLE IIc COMPATIBLE.
- READY TO PLUG IN, W/ SHIELDED CABLE & MOLDED 19 PIN CONNECTOR
- FAST, RELIABLE SLIMLINE DIRECT DRIVE
- SIX MONTH WARRANTY

DISK DRIVE ACCESSORIES
FDD CONTROLLER CARD \$49.95
IIc ADAPTOR CABLE \$19.95
ADAPTS STANDARD APPLE DRIVES FOR USE WITH APPLE IIc

KB-1000
\$79.95


CASE WITH KEYBOARD FOR APPLE TYPE MOTHERBOARD

- USER DEFINED FUNCTION KEYS
- NUMERIC KEYPAD WITH CURSOR CONTROL
- CAPS LOCK
- AUTO-REPEAT



KEYBOARD-AP
\$49.95

- REPLACEMENT FOR APPLE II KEYBOARD
- CAPS LOCK KEY, AUTO-REPEAT
- ONE KEY ENTRY OF BASIC OR CP/M COMMANDS



EXTENDER CARDS

IBM-PC	\$45.00
IBM-AT	\$68.00
APPLE II	\$45.00
APPLE IIe	\$45.00
MULTIBUS	\$86.00

APPLE COMPATIBLE INTERFACE CARDS

EPROM PROGRAMMER \$59.95



MODEL RP525

- DUPLICATE OR BURN ANY STANDARD 27xx SERIES EPROM
- EASY TO USE MENU-DRIVEN SOFTWARE IS INCLUDED
- MENU SELECTION FOR 2716, 2732, 2732A, 2764 AND 27128
- HIGH SPEED WRITE ALGORITHM
- LED INDICATORS FOR ACTIVITY
- NO EXTERNAL POWER SUPPLY NEEDED
- ONE YEAR WARRANTY

16K RAMCARD \$39.95



- FULL TWO YEAR WARRANTY
- EXPAND YOUR 48K APPLE TO 64K
- USE IN PLACE OF APPLE LANGUAGE CARD

BARE PC CARD W/ INSTRUCTIONS \$9.95

IC TEST CARD \$99.95



- QUICKLY TESTS MANY COMMON ICs
- DISPLAYS PASS OR FAIL
- ONE YEAR WARRANTY
- TESTS: 4000 SERIES CMOS, 74HC SERIES CMOS, 7400, 74LS, 74L, 74H & 74S

300B MODEM \$49.95
FOR APPLE OR IBM
INCLUDES ASCII PRO-EZ SOFTWARE



- FCC APPROVED
- BELL SYSTEMS 103 COMPATIBLE
- INCLUDES AC ADAPTOR
- AUTO-DIAL
- DIRECT CONNECT

CABLE FOR APPLE IIc \$14.95

JOYSTICK CR-401 \$7.95
FOR ATARI 400, 800, 2600, VIC 20/64 AND APPLE IIe

DISKFILE
HOLDS 70 5 1/4" DISKETTES

\$895



3.5" DISKFILE HOLDS 40 \$995

POWER STRIP

- UL APPROVED
- 15A CIRCUIT BREAKER

\$12.95



BAL 3-WAY SWITCH BOXES

- SERIAL OR PARALLEL
- CONNECTS 3 PRINTERS TO ONE COMPUTER OR VICE VERSA
- ALL LINES SWITCHES
- HIGH QUALITY ROTARY SWITCH MOUNTED ON PCB
- GOLD CONTACTS
- STURDY METAL ENCLOSURE



SWITCH-3P CENTRONICS PARALLEL \$99.95
SWITCH-3S RS232 SERIAL \$99.95

BAL PRINTER BUFFERS

- FREES COMPUTER FOR OTHER TASKS WHILE PRINTING LONG DOCUMENTS
- STAND-ALONE DESIGN, WORKS WITH ANY COMPUTER OR PRINTER
- ALL MODELS FEATURE PRINT PAUSE MEMORY CHECK, GRAPHICS CAPABILITY

SP120P PARALLEL \$139.95
• 64K UPGRADABLE TO 256K
• LED INDICATOR SHOWS VOLUME OF DATA IN BUFFER

SP120S RS232 SERIAL \$159.95
• 64K UPGRADABLE TO 256K
• 6 SELECTABLE BAUD RATES, FROM 600B-19,200B

SP110P PARALLEL \$249.95
• 64K UPGRADABLE TO 512K
• SPOOLS OUTPUT OF UP TO 3 COMPUTERS
• LED BARGRAPH DISPLAYS AMOUNT OF DATA IN BUFFER
• RESET FUNCTION CLEARS DATA IN BUFFER
• REPEAT FUNCTION CAN PRODUCE MULTIPLE COPIES OF A DOCUMENT



NASHUA DISKETTES DEALS

5 1/4" SOFT SECTOR DS/DD WITH HUB RINGS

\$990 BOX OF 10
69C^{ea} BULK QTY 50
59C^{ea} BULK QTY 250

NASHUA DISKETTES WERE JUDGED TO HAVE THE HIGHEST POLISH AND RECORDED AMPLITUDE OF ANY DISKETTES TESTED ACCORDING TO "COMPARING FLOPPY DISKS", BYTE 9/84

DISKETTES NASHUA 5 1/4"

N-MD2D	DS /DD SOFT	\$9.90
N-MD2F	DS /QUAD SOFT	\$34.95
N-MD2H	DS /HD FOR AT	\$49.95

NASHUA 8"

N-FD1	SS /DD SOFT	\$27.95
N-FD2D	DS /DD SOFT	\$34.95

NASHUA 3.5"

N-3.5SS	3.5" SS/DD FOR MAC	\$32.95
---------	--------------------	---------

VERBATIM 5 1/4"

V-MD1D	SS /DD SOFT	\$23.95
V-MD2D	DS /DD SOFT	\$29.95
V-MD110D	SS /DD 10 SECTOR HARD	\$23.95

TEST EQUIPMENT FROM JDR INSTRUMENTS

DIGITAL MULTIMETER PEN DPM-1000
AUTO RANGING, POLARITY AND DECIMAL!
\$54.95



20MHZ DUAL TRACE OSCILLOSCOPE	MODEL 2000	\$389.00
35MHZ DUAL TRACE OSCILLOSCOPE	MODEL 3500	\$549.00

FOR MORE INFORMATION ON THE OSCILLOSCOPES, CALL US FOR FREE PRODUCT BRIEFS.

Sakata 120 CPS DOT MATRIX PRINTER



MODEL SP-1200 \$169.95

- EPSON / IBM COMPATIBLE
- 9-WIRE PRINthead
- 120 CPS-BIDIRECTIONAL, 80 COL
- FRICTION AND TRACTOR FEED
- PROPORTIONAL SPACING
- CENTRONICS PARALLEL INTERFACE
- 8 CHARACTER SETS AND GRAPHICS

6 FOOT IBM PRINTER CABLE \$9.95
REPLACEMENT RIBBON CARTRIDGE \$11.95

5 1/4" FLOPPY DISK DRIVES

- | | |
|------------------------------------------|----------|
| TEAC FD-55B 1/2" HT DS/DD (FOR IBM) | \$109.95 |
| TEAC FD-55F 1/2" HT DS/QUAD (FOR IBM) | \$124.95 |
| TEAC FD-55GFV 1/2" HT DS/HD (FOR IBM AT) | \$154.95 |
| TANDON TM100-2 DS/DD (FOR IBM) | \$119.00 |
| TANDON TM50-2 1/2" HT DS/DD (FOR IBM) | \$79.95 |
| MPI-B52 DS/DD (FOR IBM) | \$79.95 |
| QUME QT-142 1/2" HT DS/DD (FOR IBM) | \$79.95 |

8" FLOPPY DISK DRIVES

- | | |
|--------------------------------|----------|
| FD 100-8 SS/DD (SA/801 EQUIV) | \$119.00 |
| FD 200-8 DS/DD (SA/851R EQUIV) | \$159.00 |


DISK DRIVE ACCESSORIES

- | | |
|---------------------------------|---------|
| TEAC SPECIFICATION MANUAL | \$5.00 |
| TEAC MAINTENANCE MANUAL | \$25.00 |
| 1/2" HT MOUNTING HARDWARE | \$2.95 |
| MOUNTING RAILS FOR IBM AT | \$4.95 |
| "Y" POWER CABLE FOR 5 1/4" FDDs | \$2.95 |
| 5 1/4" FDD POWER CONNECTORS | \$1.19 |



DISK DRIVE ENCLOSURES

- | | |
|----------------------------------------------------|-----------------|
| CAB-APPLE | \$24.95 |
| APPLE TYPE CABINET W/ OUT POWER SUPPLY | |
| CAB-1FH5 | \$69.95 |
| FULL HT 5 1/4" BEIGE CABINET W/ POWER SUPPLY | |
| CAB-2SV5 | \$49.95 |
| DUAL SLIMLINE 5 1/4" CABINET W/ POWER SUPPLY | |
| CAB-2SV8 | \$209.95 |
| DUAL SLIMLINE 8" CABINET W/ POWER SUPPLY | |
| CAB-2FH8 | \$219.95 |
| HORIZONTAL DUAL FULL HT 8" CABINET W/ POWER SUPPLY | |

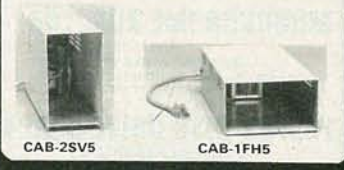

CALL FOR VOLUME QUOTES © COPYRIGHT 1986 JDR MICRODEVICES

CIRCLE 184 ON FREE INFORMATION CARD

20 MEGA BYTE HARD DISK SYSTEM ONLY \$389.95!

SEAGATE ST-225 20 MB HARD DISK SYSTEM


INCLUDES HARD DISK CONTROLLER, CABLES AND INSTRUCTIONS. ALL DRIVES ARE PRE-TESTED AND COME WITH A ONE YEAR WARRANTY.

\$389.95

XT COMPATIBLE MOTHERBOARD

\$129.95

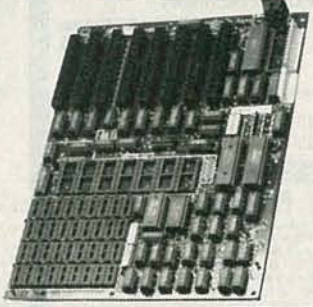- 4.77 MHz 8088 CPU, OPTIONAL 8087 CO-PROCESSOR
- 8 EXPANSION SLOTS
- 0K RAM INSTALLED, EXPANDABLE TO 640K ON-BOARD MEMORY
- ALL ICs SOCKETED-HIGHEST QUALITY PC BOARD
- ACCEPTS 2764 OR 27128 ROMS



PRO-BIOS \$19.95

IBM COMPATIBLE INTERFACE CARDS

ALL WITH A ONE YEAR WARRANTY

MULTI I/O FLOPPY CARD \$89.95

PERFECT FOR THE 640K MOTHERBOARD



- 2 DRIVE FLOPPY DISK CONTROLLER
- 1 RS232 SERIAL PORT; OPTIONAL 2nd SERIAL PORT
- PARALLEL PRINTER PORT
- GAME PORT
- CLOCK/CALENDAR
- SOFTWARE: CLOCK UTILITIES, RAMDISK, SPOOLER
- OPTIONAL SERIAL PORT \$15.95

MULTIFUNCTION CARD \$84.95

ALL THE FEATURES OF AST'S 6 PACK PLUS AT HALF THE PRICE



- CLOCK/CALENDAR
- 0-384K RAM
- SERIAL PORT
- PARALLEL PORT
- GAME PORT
- SOFTWARE INCLUDED
- PRINTER CABLE \$9.95
- 64K RAM UPGRADE \$11.61

COLOR GRAPHICS ADAPTOR \$69.95

FULLY COMPATIBLE WITH IBM COLOR CARD



- 4 VIDEO INTERFACES: RGB, COMPOSITE COLOR, HI-RES, COMPOSITE MONOCHROME, CONNECTOR FOR RF MODULATOR
- COLOR GRAPHICS MODE: 320 x 200
- MONO GRAPHICS MODE: 640 x 200
- LIGHT PEN INTERFACE

MONOCHROME GRAPHICS CARD \$89.95

FULLY COMPATIBLE W/IBM MONOCHROME ADAPTOR & HERCULES GRAPHICS



- LOTUS COMPATIBLE
- TEXT MODE: 80 x 25
- GRAPHICS MODE: 720 x 348
- PARALLEL PRINTER INTERFACE
- OPTIONAL SERIAL PORT \$19.95

MONOCHROME ADAPTOR \$49.95

ANOTHER FANTASTIC VALUE FROM JDR!

- IBM COMPATIBLE TTL OUTPUT
 - 720 x 350 PIXEL DISPLAY
- PLEASE NOTE: THIS CARD WILL NOT RUN LOTUS GRAPHICS AND DOES NOT INCLUDE A PARALLEL PORT

FLOPPY DISK DRIVE ADAPTOR \$34.95



- INTERFACES UP TO 4 STANDARD FDDs TO IBM PC OR COMPATIBLES
- INCLUDES CABLE FOR TWO INTERNAL DRIVES
- STANDARD DB37 FOR EXTERNAL DRIVES
- RUNS QUAD DENSITY DRIVES WHEN USED WITH JFORMAT

1200 BAUD MODEMS

HAYES COMPATIBLE, AUTO-DIAL, AUTO-ANSWER, AUTO RE-DIAL ON BUSY, POWER-UP SELF TEST, FULL ONE YEAR WARRANTY

MODEL 1200B*

- INTERNAL DESIGN
- 10 INCH CARD
- SERIAL PORT INCLUDED

\$169.95

MODEL 1200H*

- INTERNAL DESIGN
- HALF LENGTH (5") CARD
- INCLUDES SPEAKER

\$149.95

SMARTTEAM

- EXTERNAL DESIGN
- WITH POWER SUPPLY
- LED STATUS INDICATORS

\$169.95

*FOR IBM, INCLUDES PC TALK III COMMUNICATIONS SOFTWARE

CRT MONITORS FOR ALL APPLICATIONS



LUXOR HI-RES RGB MONITOR

MODEL 190-9528

- DIGITAL RGB-IBM COMPATIBLE
- 14" SCREEN
- 16 TRUE COLORS
- 25 MHz BANDWIDTH
- RESOLUTION > 640 x 262
- 31mm DOT PITCH
- CABLE FOR IBM PC INCLUDED

\$299.95



SAKATA COMPOSITE COLOR

MODEL SC-100

- TOP RATED FOR APPLE
- 13" COMPOSITE VIDEO
- RESOLUTION 280H x 300V
- INTERNAL AUDIO AMP
- ONE YEAR WARRANTY

\$169.95



CENTER SYSTEMS MONOCHROME

MODEL KLM-1211

- IBM COMPATIBLE TTL INPUT
- 13" NON-GLARE SCREEN
- P39 GREEN PHOSPHORUS
- VERY HIGH RESOLUTION: 25 MHz BANDWIDTH 1100 LINES (CENTER)

AMBER VERSION \$109.95

\$99.95

BUILD YOUR OWN 256K XT COMPATIBLE SYSTEM

- XT MOTHERBOARD \$129.95
- PRO-BIOS \$19.95
- 256K RAM \$26.55
- 130 WATT POWER SUPPLY \$89.95
- FLIP-TOP CASE \$39.95
- DKM-2000 KEYBOARD \$59.95
- 1/2 HEIGHT QUME DRIVE \$79.95
- FLOPPY DISK CONTROLLER \$34.95
- MONOCHROME ADAPTOR \$49.95
- MONOCHROME MONITOR \$89.95

TOTAL: \$611.10

MONITOR STAND



TILTS AND SWIVELS

ONLY \$12.95

IBM PRINTER CABLE



- DB25 TO CENTRONICS
- SHIELDED CABLE

\$9.95

IBM STYLE COMPUTER CASE

AN ATTRACTIVE STEEL CASE WITH A HINGED LID FITS THE POPULAR PC/XT COMPATIBLE MOTHERBOARDS

- SWITCH CUT-OUT ON SIDE FOR PC/XT STYLE POWER SUPPLY
- CUT-OUT FOR 8 EXPANSION SLOTS
- ALL HARDWARE INCLUDED

\$39.95



IBM COMPATIBLE KEYBOARDS

DKM-2000 \$59.95



- "5150" STYLE KEYBOARD
- FULLY IBM COMPATIBLE
- LED STATUS INDICATORS FOR CAPS & NUMBER LOCK
- 83 KEY - SAME LAYOUT AS IBM PC/XT KEYBOARD

IBM-5151 \$79.95



- REPLACEMENT FOR KEYTRONICS KB-5151™
- SEPARATE CURSOR & NUMERIC KEYPAD
- CAPS LOCK & NUMBER LOCK INDICATORS
- IMPROVED KEYBOARD LAYOUT

POWER SUPPLY



NOW ONLY \$69.95

- FOR IBM PC-XT COMPATIBLE
- 135 WATTS
- +5V @ 15A, +12V @ 4.2A
- -5V @ .5A, -12V @ .5A

150 WATT MODEL \$79.95

DISK DRIVES TANDON TM50-2

\$79.95

- 1/2 HT DS/DD
- IBM COMPATIBLE
- EXTREMELY QUIET!

- TEAC FD-55B DS/DD \$109.95
- TEAC FD-55F DS/QUAD \$124.95
- TEAC FD-558 DS/HD \$154.95
- QUME QT-142 DS/DD \$79.95
- MOUNTING HARDWARE \$2.95
- AT/RAILS \$4.95

JDR Microdevices

1224 S. Bascom Avenue, San Jose, CA 95128
Toll Free 800-538-5000 • (408) 995-5430 • FAX (408) 275-8415 • Telex 171-110

Worldwide • Since 1974

• QUALITY COMPONENTS • COMPETITIVE PRICING • PROMPT DELIVERY

Mail Order Electronics • Worldwide
Jameco
ELECTRONICS

COMMODORE COMPATIBLE ACCESSORIES

Now Compatible With C-128!
RS232 Adapter for VIC-20, C-64 and C-128

The JE232CM allows connection of standard serial RS232 printers, modems, etc. to your VIC-20, C-64 (excluding the IX-64 Portable), and C-128. A 4-pole switch allows the inversion of the 4 control lines. Complete installation and operation instructions included.

Plugs into User Port • Provides Standard RS232 signal levels Uses 6 signals (Transmit, Receive, Clear to Send, Request to Send, Data Terminal Ready, Data Set Ready).

JE232CM. \$39.95

Voice Synthesizer VIC-20 & C-64
Plug-In - Talking in Minutes!

JE520CM. \$99.95

300 Baud Auto Modem
Mitey-Mo (For C-64). \$54.95

Parallel Printer Interface
2K Buffer, Expandable to 10K!
MW350 (For VIC-20, C-64 & C-128). \$54.95

TRS-80 COMPATIBLE ACCESSORIES

E-X-P-A-N-D TRS-80 MEMORY
All kits come complete with documentation

TRS-80 MODEL I, III

TRS-16K3 200ns (Model III). \$5.95
TRS-16K4 250ns (Model I). \$5.49

TRS-80 COLOR AND COLOR II

TRS-64K-2. \$11.95
New models only -
TRS-CoCo-Incl. 2-50464's (41464's). \$13.49

TRS-80 MODEL 4, 4P

TRS-64K-2. \$11.95
Expands Model 4 from 16K-64K or Model 4P from 64K-128K

TRS-64K-2PAL. \$29.95
Expands Model 4 from 64K to 128K

TRS-80 Model 100 • NEC • Olivetti
M1008K. \$24.95 ea. or 3 for \$59.95
TRS-80 Model 100 Expansion

NEC8KR. \$24.95 ea. or 3 for \$59.95
NEC Model PC-8201A Expansion

OM108K. \$24.95 ea. or 3 for \$59.95
Olivetti Model M10 Expansion

TANDY 200

M200R. \$74.95 ea. or 2 for \$129.95
Tandy Model 200 Expansion

UV-EPROM ERASER



Erases all EPROMs. Erases up to 8 chips within 21 minutes (1 chip in 15 minutes). Maintains constant exposure distance of 1". Special conductive foam liner eliminates static build-up. Built-in safety lock to prevent UV exposure. Compact - 9.00" L x 3.70" W x 2.60" H. Complete with holding tray for 8 chips.

DE-4 UV-EPROM Eraser. \$74.95
UVS-11EL Replacement Bulb. \$17.95

DATA BOOKS

30003 National Linear Data Book (82). \$14.95
30009 Intersil Data Book (85). \$ 9.95
30013 Zilog Data Book (85). \$14.95
30032 National Linear Supplement (84). \$ 6.95
210830 Intel Memory Handbook (86). \$17.95
230843 Intel Microsystem Hndbk. Set (86). \$24.95

MUFFIN/SPRITE-STYLE FANS

MUF60 (SPN3-15-2462) \$9.95
Howard Industries (4.68" sq., 60 cfm)
SU2C7. \$9.95
EG&G Rotron (3.125" square, 20 cfm)

NEW!



13" Color Composite Monitor
for VIC-20 and C-64

Also compatible with other computers with composite output (i.e. Apple II, II+, IIe*)
Ideal for color graphics and games
• Resolution: 260H x 300V - Recommended Display Character Number: 960 Characters (40 Characters x 24 Rows on 5x7 Dot Matrix)
• CRT: 13" diagonal - Size: 14.6"W x 13.5"H x 15.5"D - Weight: 25.3 lbs.

2 for
CMON. \$129.95 each or \$219.95
RCA-3-DIN (Universal Computer to Monitor Cables for Atari, Commodore & TI). \$3.49


NEW PRODUCTS!

ZUCKERBOARD Expansion Memory Half Card and Clock/Calendar for the Tandy 1000

The Zuckerboard Expansion Memory Board allows you to expand the memory of your Tandy 1000 (128K Model) as much as 640K! 256K DRAM chips increase your computer's memory by either 256K or 512K, bringing your total system memory up to either 384K or 640K. The memory board also includes a DMA controller chip. Optional clock/calendar plugs directly onto the memory board. Manual included.

TAN-Clock Clock/Calendar Option (only). \$ 39.95
TAN-EM256K Includes 256K RAM. \$ 99.95
TAN-EM512K Includes 512K RAM. \$139.95

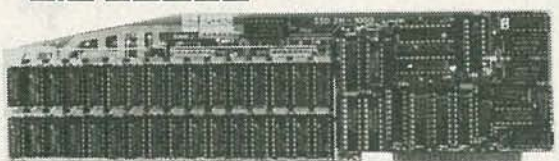BIG BOARD 1MBYTE RAM CARD for Apple II, II+ and IIe*



Introducing a third generation memory card that gives you both great expandability and great versatility at an extraordinary price. Versatility to users means that BIG BOARD is compatible with software written for the Synetix SSD (Flashcard) as well as for Jameco's JE868 128K RAM Card. Big Board makes available 426K of worksheet space, using the program THE Spreadsheet Version 2.0. It is compatible with PLUSWORKS XM for running Applesworks on the Apple II. Versatility also means that BIG BOARD comes complete with RAMDISK software for DOS 3.3, ProDOS, Pascal 1.2, and CP/M for Microsoft's Softcard. A separate driver is available for the AppliCard (StarCard).

BIG BOARD-256K 256K RAM. \$199.95
BIG BOARD-512K 512K RAM. \$249.95
BIG BOARD-1M 1Meg RAM. \$299.95

1 Yr. Warranty! cytes



External Power Supply for the Commodore 64

• Input: 117VAC @ 60Hz • Output: 5VDC @ 3 Amps, 10VAC @ 250mA • Short circuit protected and current limited • Transient spike suppression on 2 auxiliary 110VAC sockets
• Switch on front serves as power switch for the computer and other peripherals
• RFI/EMI filtered • Adjustable linear regulator • Has less than 50mV ripple rms at full load • 5 Amp primary fuse • Two conductor with ground line • Color: brown • Size: 7 1/2" D x 5 1/2" W x 2 1/2" H • Weight: 5 lbs.

CPS-10. \$39.95

IBM COMPATIBLE ACCESSORIES



Identical layout as original IBM PC Keyboard • Highly desirable case with palm rest • Complete with cable and data
JUST PLUG IN!

KB83. SALE \$29.95

Build an IBM PC/XT™ Compatible!
IBM-64K(2) 64K RAM Chips (18). \$ 24.98
KB-83 83-Key Keyboard. \$ 29.95
IBM-FCC Floppy Controller Card. \$ 49.95
IBM-Case Case. \$ 49.95
IBM-MCC Monochrome Card. \$ 79.95
IBM-PS Power Supply. \$ 79.95
FD55B Disk Drive. \$119.95
IBM-MON Monochrome Monitor. \$ 99.95
IBM-MB Motherboard. \$139.95

Regular List \$674.58

IBM™-Special (Incl. 9 items above) . . . \$599.95

Additional Add-Ons Available!
IBM-KB 83-Key Keyboard. \$ 69.95
IBM-ENH Enhanced Keyboard. \$ 99.95
IBM-ICB Integrated Color Board. \$ 99.95
IBM-EGA Enhd. Graphics 256K RAM . . . \$299.95
IBM-20MBK 20MB Hard Disk Drive. . . . \$499.95
IBM is a registered trademark of IBM Computers

NEW! Universal 64K/256K NEW! Printer Buffer



The UBUFFER Universal Printer Buffer is a hi-speed data buffer that accepts data at a high rate, and then outputs this data to your printer. You save valuable computer time. The UBUFFER can be connected to practically any computer or printer. There are four possible combinations: 1) Serial to Serial, 2) Serial to Parallel, 3) Parallel to Parallel, 4) Parallel to Serial. Manual included. Size: 9-1/3" L x 4 1/4" W x 1 1/2" H

UBUFFER-64K . . . \$199.95
UBUFFER-256K . . \$229.95

IBM Compatible! DISK DRIVES

Documentation Included
FD55B Teac 5 1/4" DS 1/2-Height. \$119.95
SA455 Shugart 5 1/4" DS 1/2-Height. . . . \$119.95
TM100-2 Tandon 5 1/4" DS Full-Height. . . \$109.95
JMR 5 1/4" DISK DRIVE ENCLOSURES
Complete with power supply, switch, power cord, fuseholder and connectors.
DDE-1FH. \$69.95
Houses 1 Full-Height 5 1/4" Floppy Drive.
DDE-2HH. \$79.95
Houses 2 Half-Height 5 1/4" Floppy Drives - Vertical
HDDE-1FH. \$199.95
Houses 1 Hard Disk Drive

\$20 Minimum Order - U.S. Funds Only
Shipping: Add 5% plus \$1.50 Insurance

California Residents: Add 6% or 6 1/2% Sales Tax

Spec. Sheets - 30¢ each
Prices Subject to Change

Send stamped, self-addressed envelope to receive a Quarterly Sales Flyer - FREE!
10/86



Mail Order Electronics • Worldwide
Jameco
ELECTRONICS




Send \$1.00 Postage for a FREE 1986 JAMECO CATALOG
© 1986 Jameco Electronics

1355 SHOREWAY ROAD, BELMONT, CA 94002 • PHONE ORDERS WELCOME 415-592-8097 Telex: 176043

Radio Shack Parts Place™

Hurry in for Exciting NEW Items and NEW '87 Catalog!

Computer Connectors

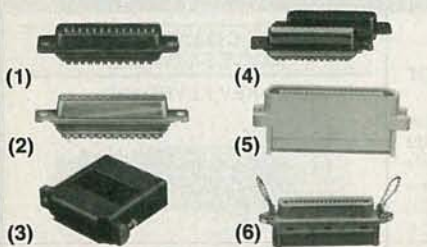


25-Position Solder-Type D-Subs.

Fig.	Type	Cat. No.	Each
1	Male	276-1547	1.99
2	Female	276-1548	2.99
3	Hood	276-1549	1.99

- (4) **NEW!** Multipurpose Hood. Use as standard hood or build a custom gender-changer. #276-1520 1.79
 (5) **36-Position Male Printer Connector.** For fast repairs or extension cables. #276-1533 5.99
 (6) **NEW!** 36-Position Female Printer Connector. Great for printer cable extensions. #276-1523 5.99

Hookup to Value!

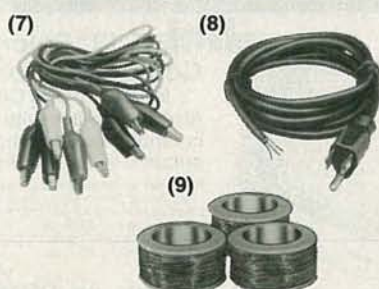

- (7) **Set of 4 Test Cables.** 30" long. With insulated clip at each end. #278-001 3.49
 (8) **6-Ft. AC Line Cord With Three-Prong Plug.** 18-gauge conductors handle up to 10 amps at 125 VAC. SVT jacket. UL listed. #278-1258 ... 2.99
 (9) **Magnet Wire.** 3-spool set is ideal for winding coils. Includes 40-ft. of 22-gauge, 75-ft. of 26-ga., 200-ft. of 30-ga. #278-1345 4.49

Voice Synthesizer Team



- Add Voice to Your Computer**
 (10) **SPO256-AL2 Speech Synthesizer.** MOS/LSI device with a built-in program is easy to interface with most micros. 28-pin DIP and complete data. #276-1784 12.95
 (11) **CTS256-AL2 Text-to-Speech IC.** 8-bit processor translates ASCII into control data for the chip above. 40-pin DIP and data. #276-1786 16.95

Touch-Tone Decoder IC

NEW!




- DTMF Receiver in One 18-Pin DIP**
SSI202. Ideal for ham radio autopatching, repeater, link and remote-station control. Features single analog input and eight built-in switched-capacitor filters—no input filtering is required. Provides selectable hexadecimal or binary coded 2 of 8 output. Clocked by low-cost colorburst crystal (RS #272-1310, not incl.). 5 VDC, single supply. With data and circuit examples. #276-1303 12.95

Biggest & Brightest LEDs



- (12) **Super-Bright Red LED.** Breakthrough! Outputs 300 mcd at 20 mA yet runs cool. #276-066,99¢
 (13) **NEW!** Jumbo Red LED. Two LED elements connected cathode-to-cathode in a huge 10 mm housing. Three-lead pinout lets you use separate current limiting resistors. Really big! #276-065,1.19

Top-Quality Memory

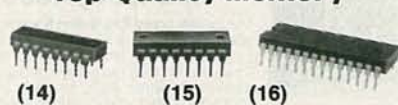

- Manufacturer's Best—Why Settle for Less?**
 (14) **4164 64K Dynamic RAM.** 150 ns access. Add reliable memory today. #276-2506 3.95
 (15) **NEW!** TMS 4256 256K Dynamic RAM. 150 ns access. #276-1252 6.95
 (16) **NEW!** MSM 2764RS 64K EPROM. UV erasable, 250 ns access. #276-1251 6.95


Melody Synthesizer

NEW!



- Preprogrammed With 12 Popular Tunes**
UMC 3482. Ideal for musical doorbells, telephone music-on-hold, game and novelty applications. Tunes include Happy Birthday, Oh My Darling Clementine, London Bridge is Falling Down, Home Sweet Home, Row-Row-Row Your Boat. 16-pin DIP with data and circuit examples. #276-1797 ... 2.99

Hi-Q Ceramic Capacitors

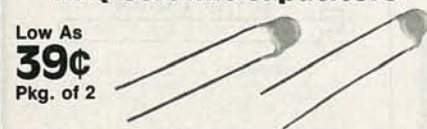

Low As **39¢** Pkg. of 2

pF	VVDC	Cat. No.	2-Pack	µF	VVDC	Cat. No.	2-Pack
5	50	272-120	.39	.001	500	272-126	.49
47	50	272-121	.39	.0047	500	272-130	.49
100	50	272-123	.39	.01	500	272-131	.49
220	50	272-124	.39	.047	50	272-134	.49
470	50	272-125	.39	.1	50	272-135	.49


Unusual Buzzers



- (17) **Electronic Chime.** Melody-synthesizing IC and speaker combo produce a pleasant "ding-dong" sound. Operates 6 to 18 VDC. 5" leads. #273-071 6.95
 (18) **NEW!** Tri-Sound Siren. You've never heard a buzzer like this! Contains an IC, driver circuit and 8-ohm speaker in a compact 1 1/4 x 1 1/16" case. Three distinctive sounds. 3 VDC. #273-072 5.95

Battery Guidebook

1.99
Helps You Select The Right Battery

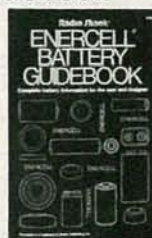

Learn how batteries work, how to recharge and test them, and how to choose the best values. Includes complete technical data on every type of Radio Shack ENERCELL® batteries. 160 pages. #62-1396

Shack® Can Supply Popular Tubes and Almost Any IC



"Hotline" Service From Our Warehouse

Your nearby Radio Shack store can special-order a wide variety of components for projects and repairs. Vacuum tubes, linear and digital ICs, microprocessor and support chips, quartz crystals, transistors, diodes, TV/audio modules, phono styli, cartridges and more. Delivery time for most items is approximately one week. Come in today—we're ready to serve you!

Digital Logic Probe

NEW!



The fast way to test TTL, LS and CMOS digital circuits. Color-coded LEDs indicate high, low or pulsed logic states (up to 10 MHz). Simultaneous tone output frees your eyes for faster testing. 36" leads with clips provide power from circuit under test. With instructions. #22-303 16.95

Digital Logic Pulser

NEW!



Together, the pulser and probe make an effective diagnostic team for testing today's digital circuits. Produces single 5 µs pulse or a continuous 5 Hz pulse train at the push of a button. Overload protected. With instructions. #22-304 ... 17.95

Pocket Multitester

SALE!
Save \$3

Reg. 10.95

7.95

Includes Probes and Owner's Manual



Rugged, easy to use, and 27% off if you hurry! Perfect for beginners and a great second meter for car or toolbox. Features "off" position to protect movement during transit, 8 ranges. Measures to 1000 volts AC/DC. DC current to 150 mA. Resistance to 100,000 ohms. 2000 ohms per volt. Requires "AA" battery. #22-212

Radio Shack®
 A DIVISION OF TANDY CORPORATION

Prices apply at participating Radio Shack stores and dealers

RAMSEY

THE FIRST NAME IN ELECTRONIC TEST GEAR



\$30⁰⁰ OFF

Save \$30 on the RAMSEY 20MHz Dual Trace Oscilloscope

Unsurpassed quality at an unbeatable price, the Ramsey oscilloscope compares to others costing hundreds more. Features include a component testing circuit for resistor,

capacitor, digital circuit and diode testing • TV video sync filter • wide bandwidth & high sensitivity • internal graticule • front panel trace rotator • Z axis • high sensitivity x-y mode • regulated power supply • built-in calibrator • rock solid triggering

Was \$399.95 NOW ONLY **\$369⁹⁵** high quality hook on probes included



NEW RAMSEY 1200 VOM MULTITESTER

Check transistors, diodes and LEDs with this professional quality meter. Other features include, decibel scale • 20K volt metering system • 3 1/2" mirrored scale • polarity switch • 20 measuring ranges • safety probes • high impact plastic case

\$19⁹⁵ test leads and battery included



NEW RAMSEY D-4100 COMPACT DIGITAL MULTITESTER

Compact sized reliability and accuracy. This LCD digital multimeter easily fits in your pocket, you can take it anywhere. It features full overload protection • 3 1/2 digit LCD readout • recessed input jacks • safety probes • diode check function • 2000 hours battery life

\$22⁹⁵ test leads and battery included

NEW 35 MHz DUAL TRACE OSCILLOSCOPE



A heavy duty and accurate scope for service as well as production use. Features include • wide frequency bandwidth • optimal sensitivity • extremely bright display • delayed triggering sweep • hold off • ALT trigger • single sweep • TV sync • 5X magnification • XY or XYZ operation • HF/LF noise reduction

3500 Dual Trace Oscilloscope \$499⁹⁵ includes 2 high quality probes

ALL OSCILLOSCOPES INCLUDE 2 PROBES

NEW 15 MHz DUAL TRACE PORTABLE OSCILLOSCOPE



Ideal for field/bench applications, this scope can display up to 15 MHz signals. Internal battery pack allows up to 2 hours operation on a single charge. Features include • built-in battery charger • 5X horizontal magnification • high brightness CRT • front panel trace rotator • internal rechargeable battery pack

2500 Portable Oscilloscope \$449⁹⁵ includes 2 high quality probes

MINI KITS—EASY TO ASSEMBLE, FUN TO USE BEGINNERS & PROS WILL HAVE A GREAT TIME WITH THESE KITS

FM MINI MIKE

A super high performance FM wireless mike kit! Transmits a stable signal up to 300 yards with exceptional audio quality by means of its built-in electret mike. Kit includes case, mike, on-off switch, antenna, battery and super instructions. This is the finest unit available.

FM-3 Kit **\$14.95**
FM-3 Wired and Tested **19.95**

Color Organ

See music come alive! 3 different lights flicker with music. One light each for, high, mid-range and lows. Each individually adjustable and drives up to 300 W, runs on 110VAC.

Complete kit, ML-1 **\$8.95**

Video Modulator Kit
Converts any TV to video monitor. Super stable, tunable over ch 4-6. Runs on 5-15V accepts std. video signal. Best unit on the market! Complete kit, VD-1 **\$7.95**

Led Blinky Kit
A great attention getter which alternately flashes 2 jumbo LEDs. Use for name badges, buttons, warning panel lights, anything! Runs on 3 to 15 volts. Complete kit, BL-1 **\$2.95**

Super Sleuth
A super sensitive amplifier which will pick up a pin drop at 15 feet! Great for monitoring baby's room or as general purpose amplifier. Full 2W rms output, runs on 6 to 15 volts, uses 8-45 ohm speaker. Complete kit, BN-9 **\$5.95**

CPO-1
Runs on 3-12 Vdc 1 wall out, 1 KHZ good for CPO, Alarm, Audio Oscillator. Complete kit **\$2.95**

FM Wireless Mike Kit

Transmits up to 300' to any FM broadcast radio, uses any type of mike. Runs on 3 to 9V. Type FM-2 has added sensitive mike preamp stage.

FM-1 Kit **\$3.95** FM-2 Kit **\$4.95**

Whisper Light Kit

An interesting kit, small mike picks up sounds and converts them to light. The louder the sound, the brighter the light. Includes mike, controls up to 300 W, runs on 110 VAC.

Complete kit, WL-1 **\$6.95**

Tone Decoder
A complete tone decoder on a single PC board. Features: 400-5000 Hz adjustable range via 20 turn pot, voltage regulation, 567 IC. Useful for touch-tone burst detection, FSK, etc. Can also be used as a stable tone encoder. Runs on 5 to 12 volts. Complete kit, TD-1 **\$5.95**

Siren Kit
Produces upward and downward wail characteristic of a police siren. 5 W peak audio output, runs on 3-15 volts, uses 3-45 ohm speaker. Complete kit, SM-3 **\$2.95**

60 Hz Time Base
Runs on 5-15 VDC. Low current (25ma) 1 min/month accuracy TB-7 Kit **\$5.50**
TB-7 Assy. **\$9.95**

Universal Timer Kit

Provides the basic parts and PC board required to provide a source of precision timing and pulse generation. Uses 555 timer IC and includes a range of parts for most timing needs.

UT-5 Kit **\$5.95**

Mad Blaster Kit

Produces LOUD ear shattering and attention getting siren like sound. Can supply up to 15 watts of obnoxious audio. Runs on 6-15 VDC

Complete kit, MB-1 **\$4.95**

30 Watt 2 mtr PWR AMP

Simple Class C power amp features 8 times power gain. 1 W in for 8 out, 2 W in for 15 out, 4 W in for 30 out. Max output of 35 W, incredible value, complete with all parts, less case and T-R relay.

PA-1, 30 W pwr amp kit **\$22⁹⁵**
TR-1, RF sensed T-R relay kit **6⁹⁵**

Power Supply Kit

Complete triple regulated power supply provides variable 6 to 18 volts at 200 ma and +5 at 1 Amp. Excellent load regulation, good filtering and small size. Less transformers, requires 6 3V (a 1 A and 24 VCT). Complete kit, PS-3LT **\$6⁹⁵**

CT-70 7 DIGIT 525 MHz COUNTER

Lab quality at a breakthrough price. Features • 3 frequency ranges each with pre amp • dual selectable gate times • gate activity indicator • 50mV @ 150 MHz typical sensitivity • wide frequency range • 1 ppm accuracy

\$119⁹⁵ wired includes AC adapter
CT-70 kit **\$99.95**
BP-4 nicad pack **8.95**

CT-50 8 DIGIT 600 MHz COUNTER

\$169⁹⁵ wired
CT-50 kit **\$139.95**
RA-1 receiver adapter kit **14.95**

CT-90 9 DIGIT 600 MHz COUNTER

The most versatile for less than \$300. Features 3 selectable gate times • 9 digits • gate indicator • display hold • 25mV @ 150 MHz typical sensitivity • 10 MHz timebase for WWW calibration • 1 ppm accuracy

\$149⁹⁵ wired includes AC adapter
CT-90 kit **\$129.95**
OV-1 0.1 PPM oven timebase **\$9.95**
BP-4 nicad pack **8.95**

CT-125 9 DIGIT 1.2 GHz COUNTER

\$169⁹⁵ wired includes AC adapter
BP-4 nicad **\$8.95**

DM-700 DIGITAL MULTIMETER

Professional quality at a hobbyist price. Features include 26 different ranges and 5 functions • 3 1/2 digit, 1/2 inch LED display • automatic decimal placement • automatic polarity

\$119⁹⁵ wired includes AC adapter
DM-700 kit **\$99.95**
MP-1 probe set **4.95**

PR-2 COUNTER PREAMP

The PR-2 is ideal for measuring weak signals from 10 to 1,000 MHz • flat 25 db gain • BNC connectors • great for shifting RF • ideal receiver/TV preamp

\$44⁹⁵ wired includes AC adapter
PR-2 kit **\$34.95**

PS-2 AUDIO MULTIPLIER

The PS-2 is handy for high resolution audio resolution measurements, multiplies up in frequency • great for PL tone measurements • multiplies by 10 or 100 • 0.01 Hz resolution & built-in signal preamp/conditioner

\$49⁹⁵ wired
PS-2 kit **\$39.95**

PS-10B 1.5 GHz PRESCALER

Extends the range of your present counter to 1.5 GHz • 2 stage preamp • divide by 1000 circuitry • super sensitive (50 mV typical) • BNC connectors • 1 GHz in, 1 MHz out • drive any counter

\$79⁹⁵ wired includes AC adapter

ACCESSORIES FOR RAMSEY COUNTERS

- Telescopic whip antenna—BNC plug **\$ 8.95**
- High impedance probe, light loading **16.95**
- Low pass probe, audio use **16.95**
- Direct probe, general purpose use **13.95**
- Tilt bail, for CT-70, 90, 125 **3.95**

PHONE ORDERS CALL 716-586-3950

TELEX 466735 RAMSEY CI

TERMS: • satisfaction guaranteed • examine for 10 days, if not pleased, return in original form for refund • add 6% for shipping and insurance to a maximum of \$10.00 • overseas add 15% for surface mail • COD add \$2.50 (COD in USA only) • orders under \$15.00 add \$1.50 • NY residents add 7% sales tax • 90 day parts warranty on all kits • 1 year parts & labor warranty on all wired units.

RAMSEY

RAMSEY ELECTRONICS, INC.
2575 Baird Rd.
Penfield, N.Y. 14526

CIRCLE 70 ON FREE INFORMATION CARD

**Featured
In this
Issue!**



**Limited
Edition!**

**Varometer
Super Crystal Radio Kit** **\$79⁹⁵**
Cat K-9002

Return with us now
to those thrilling
days of yesteryear!
Build a vintage radio
with this unique kit!



From his hideaway home high in Australia's Blue Mountains, vintage radio enthusiast David Whitby has painstakingly hand-crafted these kits from original designs. Using authentic components (a limited supply discovered recently in an old warehouse), Mr. Whitby has created a kit that is not only entertaining & educational, but, as a genuine piece of radio history, can actually appreciate in value! This model, the Varometer Super Crystal Set, is based upon circuitry first used over 60 years ago in naval & other applications where maximum performance was necessary. It uses no power source other than received RF energy from the antenna/earth system which powers the headphones. The design is enhanced by its dove-routed wooden baseboard and gold-type lettered bakelite panel which carries the aerial tap switch (also vintage), dial, & headphone jack socket. But remember, due to the limited stock of components, production of these kits is strictly limited, so order now!

1940 Vintage Headphones

These rugged, yet sensitive phones are the perfect mate for your antique radio. Manufactured in 1940 by the Standard Telephone Company. **\$19⁹⁵**
Cat C-4001

Short Wave Antenna Kit

Expert design, complete with instruction & ready to assemble. No soldering required. **\$11⁹⁵**
Cat K-3490

Fabulous Foxhunting with the DSE RDF kit!

Locate the source of any transmission with this sophisticated radio direction finder from DSE. Similar commercial units may cost hundreds of dollars, but you can build this one yourself and spend the difference on antennas (not included). Complete with detailed construction manual & all hardware for both fixed & mobile installation. Requires only an alligator clip lead & screwdriver to adjust for operation.

Features: 32 unit LED compass • Electronic Antenna Switching Unit (ASU) • Stable digital circuitry • Adjustable internal monitor speaker • Internal alignment reference • Self-aligning commutating filters • 170° calibration
Specifications: 12V operation • 50-500 MHz Freq. range • Accurate ± 5.6°



\$99⁹⁵
Cat K-6345

**Build it better
with DSE!**

**SAVE
35%**

CLOSEOUT!

**Enjoy your home
electronics in
total comfort!**

Build a matchbox-sized transmitter and its matching receiver (capable of switching a 10 amp load) to control lights, appliances, etc. at distances up to 40 feet.



**Receiver
WITH CASE** **\$32**
Cat K-3428



Transmitter \$7⁹⁵
WITH CASE
Cat K-3429



VK Powermaster

This power supply for RF linear amplifiers features a completely discrete design - no IC's are used! The ingenious design by Rex Callaghan also boasts instantaneous short circuit protection with no loss of power or performance!

Specifications:
• 18V, 14A continuous, 25A intermittent (with M-2010 transformer) • Aluminum case
Transformer (Cat M-2010) \$39.95



was \$79.95
\$49⁹⁵
Cat K-3448

**Hurry!
Only 83
kits left!**

Make life a little easier

with TYRÖN

Remote Control Power Booster

Now you can control your home electronics from anywhere in the room - without line of sight or aiming! This unique device (developed by ex-Apple ace Steve Wozniak) attaches quickly & easily to your existing infra-red remote (without tools!). Operates a year or more on a 9V alkaline battery (included).

**NEW
from the
WOZ**

\$29⁹⁵
Cat Y-6002




**Get the Audio Quality
you deserve without
breaking your budget!**

**PLAYMASTER®
200W Mosfet Stereo Amp**

Feature for feature, dollar for dollar, this kit outperforms the big name competition! Electronic input circuitry handles moving magnet, big coil, CD, hi-fi, VCR, cassette, tuner, & more. Soft-touch controls, de-thump, and toroidal transformers are only a few of its many features. Step-by-step instructions make it easy to build (but if, after examination, you decide it's beyond your abilities, just return the kit intact for full refund!).

\$299
Cat K-3516

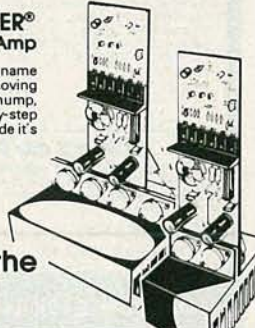- 100W RMS, 200W peak into 8 ohms
- Full frequency response: 20Hz - 20KHz (±3dB), 20Hz - 50KHz (±1dB)
- 100% duty cycle
- Input sensitivity: 1.2V RMS
- Noise: 100dB below full output
- Internal distortion: 0.003%
- 100W (80Hz & 70Hz) @ 4Ω
- 50W (100Hz) @ 2Ω
- 25W (100Hz) @ 1Ω
- Stability: Unconditionally Stable



Build a Mosfet at a fraction of the cost of a commercial module!

High performance, general purpose units with a wide variety of applications. Use with 2 or 4 output devices. Fits standard low-cost chassis.

**THAT'S
VALUE!**

50W RMS max. 100W RMS max.
\$29⁹⁵ \$39⁹⁵
Cat K-3441 Cat K-3443

Units powered by DC POWER SUPPLY consisting of 35V C.T. Transformer, 4 x 8000 V.F. 75V Capacitors and a BP-40 Rectifier Diode.
BP-40 Rect. Diode 8000 Mfd. 75V Electro
Cat Z-3334 **\$4⁵⁰** Cat R-4590 **\$9⁹⁵**

Have you seen the many marvelous DSE kits featured in recent issues of R-E?

- | | | | |
|---------------|------------------------------------------------------------------|--------------------------|-----------------------------------------------------|
| January 1986 | Australis I Satellite Receiver
<i>(No modulator included)</i> | Cat K-6316 | \$89⁹⁵ |
| February 1986 | Build a Music Synthesizer | Cat K-2669 | \$19⁹⁵ |
| March 1986 | Build a Walkman Amplifier | Cat K-2667 | \$14⁹⁵ |
| April 1986 | Build a Teletext Decoder
<i>(Cover Story)</i> | Cat K-6315 | \$199⁰⁰ |
| May 1986 | Teletext Decoder (Part 2) | | |
| June 1986 | Hi-Performance Stereo Amp | Cat K-3516 | \$299⁰⁰ |
| July 1986 | Hi-Performance Amp (Part 2) | | |
| August 1986 | Hi-Performance Amp (Part 3) | | |
| | Build a Remote Power Switch
& Matching Transmitter | Cat K-3428
Cat K-3429 | \$32⁰⁰
\$7⁹⁵ |
| October 1986 | Build an Antique Crystal Radio | Cat K-9002 | \$79⁹⁵ |

Dear Enthusiast: We also carry parts for many of the other fine build-it-yourself projects in *Radio-Electronics*. Try us!

RADIO-ELECTRONICS

Reader's Special

Mini Rotary Fan



Perfect for small devices that require forced air cooling, this little beauty measures 3 1/4" x 3 1/4" x 1 1/2" deep. Mounting holes on 2" radius. The 110V AC motor draws only 60mA. At this special price, it will keep your budget cool, too!

Regularly \$12.95 **\$3.95 ONLY** Cat Y-8505

Offer valid thru 10/31/86
Limit 12 per customer


Note: Fan guard not included!

Matching Fan Guard (Cat Y-8506) \$1.65

ADE U.S.A.

Don't be embarrassed to admit you don't know how to type - learn!

It's not only easy - it's FUN! Type-right™ is dedicated to the task of teaching touch typing. With its full size 47-key color-coded keyboard, 16-page course manual, and instantaneous feedback, Type-right allows students to proceed from basic finger positions to 45 w.p.m. proficiency at their own pace. When a student completes the final lesson with the required speed & accuracy, the LCD screen will display a secret code which can be sent to the manufacturer for an official graduation certificate. For added convenience, Type-right also includes an audio-cassette version of the instruction course. Requires 4 "C" batteries.

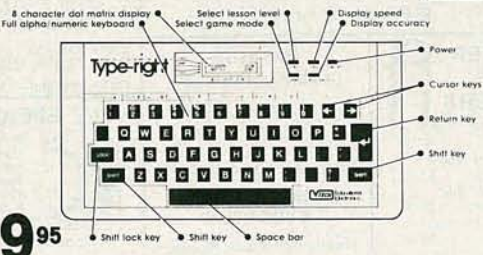

Type-right \$39.95
Typing Tutor Cat Y-1021


Are you tired of buying fancy blister packaging?

Did you know that DICK SMITH ELECTRONICS carries a huge range of components?

Yes! DSE is one of the world's leading component retailers/wholesalers. Whether you're buying one or one million, make us your one-stop shop for polyester capacitors, ceramics, polystyrene, high voltage polycarbonate, variable caps, ceramics feed throughs, trimmer caps, electrolytics, bi-polar electros, tag tantalums, metal film 1% resistors, carbon film & wire wound resistor, slider pots, 10 turn trimpots, joystick pots, single & dual gang pots, horizontal & vertical trimpots, RF chokes, ferrites, toroids, coil formers, transistors, FET's, zeners, thyristors, diodes, LCD displays, bridges, power mosfets, TTL 74LS, 74HZ, 74C/4000 CMOS, voltage regulators, linear IC's, and many hundreds more!

Buy only what you need! At Dick Smith Electronics you don't pay for fancy blister packaging!

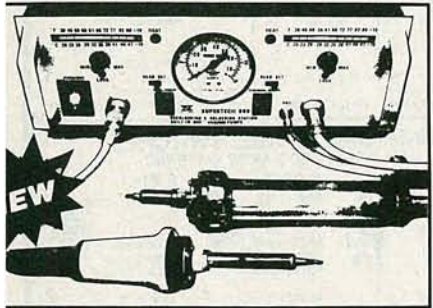ATTENTION BULK BUYERS!
Schools! Colleges! Companies!
Call 415-368-8844
for special quantity pricing!



DSE Soldering De-Soldering Station

This is a professional rack-mount station with excellent facilities - no other piece of equipment we've seen can match its value!
Soldering features: Light weight, adjustable temperature-controlled iron with grounded tip for safe soldering of MOS devices; LED bar graph readout of temperature at tip; tip retainer threaded away from heat zone.
Desoldering features: Rapid, damage-free desoldering of any size joint; adjustable temperature with LED bar graph readout; grounded tip; vacuum gauge for monitoring; easy-to-clean reservoir in handle; filtered vacuum line for trouble-free pump operations.

\$349
Cat T-2200

Accessories

De-Soldering Tip 1/16"	Cat T-2201	\$4.95
De-Soldering Tip 3/22"	Cat T-2202	\$4.95
De-Soldering Tip 1/8"	Cat T-2203	\$4.95
Solder Tip Fine Wedge 1/32"	Cat T-2204	\$2.50
Solder Tip Med. Conical 1/32"	Cat T-2205	\$2.50
Solder Tip Fine Conical 1/4"	Cat T-2206	\$2.50
Solder Tip Med. Wedge 1/16"	Cat T-2207	\$2.50
Solder Tip 1/8"	Cat T-2208	\$2.50
Solder Tip Long Nose Wedge 3/64"	Cat T-2209	\$2.50
Solder Tip Short Wedge 3/64"	Cat T-2210	\$2.50

DSE 3.5 Digit LCD Voltmeter Module

Incorporates a dualscope analog-to-digital converter, a 100mV reference & full scale input in a compact package. Excellent for volt meters, current meters, thermometers, capacitance & P.H. meters.

Features: 3.5 digit LCD with 1/2" digit height; 9V battery operation with LO BAT indicator; auto-zeroing; true differential or single-ended input & automatic polarity indication; surface mountable with optional bezel.

\$29.95
Cat Q-2200
Specifications: Input sensitivity 200mV; input impedance <100M ohms; power dissipation <20mW (typ.); 15V (max.) operating voltage; 0-50°C operating temperature; -10-80°C storage temperature.

4.5 Digit Module (Cat Q-2202) \$59.95

We won't be undersold!
XT COMPATIBLE!

XT Motherboard	X-1001	\$149.00
80486 Motherboard	X-1002	\$249.95
80486 80486	X-1181	\$149.95
80486 80486	X-1012	\$149.95
Manufacturing Graphics Card	X-1009	\$89.95
Flange Disk Controller	X-1110	\$89.95
130 Watt Power Supply	X-1120	\$99.95
IBM Style Case	X-1008	\$99.95
1/2 height Disk Drive	X-1122	\$129.95
IBM compatible Mono Monitor	X-1122	\$129.95
83 Keyboard		
INDIVIDUAL COMPONENTS TOTAL \$158.55		

ONLY \$599
Save \$189

Visit our Retail Centers!

BERKELEY 2474 Shattuck Ave. (415) 486-0755
REDWOOD CITY 330 Conventon Way (415) 338-8844
SAN JOSE 4980 Stevens Creek Blvd. (408) 241-7266
LOS ANGELES 1830 Westwood Blvd. (213) 474-0026
HEAD OFFICE 390 Conventon Way Redwood City CA 94063

Protect your Home & Family with LITE GUARD

\$69.95
Cat L-5020

Light Control System

Lite Guard is a passive infra-red (PIR) sensor that detects movement across the protected areas & turns on floodlight(s) to deter prowlers. Includes hardware & accessories. (Floodlights not included).

Features: All weather operation; photocell deactivates sensor in daylight; multi-zone wide angle Fresnel lens; precise aiming; Auto. Test. Manual & Off modes.

Specifications: Dual element pyroelectric PIR sensor; operating voltage 120V AC, 60Hz; sensitivity adjustable 20-50'; 30 beams; operation time adjustable 1-20 min.; switching capability 500W max. incandescent.

MAIL ORDERS
P.O. Box 8021, Redwood City, CA 94063
14-Day Money-Back Guarantee



CIRCLE 95 ON FREE INFORMATION CARD

Did you get your FREE CATALOG?
The new 1986/7 DICK SMITH ELECTRONICS catalog is 148 colorful pages packed with thousands of fantastic products, incredible values, and an exclusive 15 page data section. We ship our catalogs first class mail, so you'll get yours with no delay!
Send \$1 for postage & handling to DSE, P.O. Box 2249, Redwood City, CA 94064

Name _____ 611 E

Address _____

City _____ State _____ Zip _____

Order Toll Free 1-800-332-5373
Call Monday - Friday 7a.m. - 6p.m. Pacific Time. In California call 415-368-1066

We ship UPS Ground unless otherwise requested. Add 5% of order total (\$1.50 Min.) for shipping. Outside U.S.A. add 20% (\$4 min). There is an additional \$1.50 handling fee. California residents please add sales tax. VISA & MASTERCARD ACCEPTED.

***QUALITY PARTS *DISCOUNT PRICES *FAST SHIPPING!**

SEND FOR FREE 1986 CATALOG... 48 PAGES!

ALL ELECTRONICS CORP.

EDGE CONNECTORS
ALL ARE 1.56" SPACING.

- 22 EDGE CONNECTOR \$1.25 ea solder lug style 10 for \$11.00
- 22/44 EDGE CONNECTOR \$2.00 ea PC style 10 for \$18.00
- 22/44 EDGE CONNECTOR solder lug style \$2.50 each
- 28/56 EDGE CONNECTOR \$2.50 ea PC style 10 for \$22.00
- 36/72 EDGE CONNECTOR PC style \$3.00 each
- 43/86 EDGE CONNECTOR PC style \$4.50 each

- TRANSISTORS**
- 2N706 4 for \$1.00
 - 2N2222A 3 for \$1.00
 - PN2222A 4 for \$1.00
 - 2N2904 3 for \$1.00
 - 2N2905 3 for \$1.00
 - KA2955 \$1.50
 - 2N3055 \$1.00
 - PMD 10K40 \$1.00
 - TIP 121 75¢
 - TIP 125 75¢

- TRANSFORMERS**
- 120 volt primaries
 - 5.5 volts @ 750 ma. \$3.00
 - 6 volts @ 150 ma. \$1.25
 - 6.3 volt @ 600 ma. \$3.00
 - 12 V.C.T. @ 200 ma. \$2.00
 - 12 V.C.T. @ 400 ma. \$3.00
 - 12 V.C.T. @ 1 amp \$4.00
 - 12 V.C.T. @ 2 amp \$4.85
 - 12 V.C.T. @ 4 amp \$7.00
 - 18 volts @ 650 ma. \$3.50
 - 24 V.C.T. @ 200 ma. \$2.50
 - 24 V.C.T. @ 1 amp \$4.85
 - 24 V.C.T. @ 2 amp \$6.75
 - 24 V.C.T. @ 3 amp \$9.50
 - 24 V.C.T. @ 4 amp \$11.00
 - 36 V.C.T. @ 135 ma. \$3.00


- WALL TRANSFORMERS**
- all plug directly into 120 vac outlet
- 4 VDC @ 70 ma. \$2.00
 - 6 VDC @ 500 ma. \$3.50
 - 6 VDC @ 750 ma. \$4.50
 - 9 VDC @ 500 ma. \$5.00
 - 12.5 VDC @ 265 ma. \$3.00
 - 18 VDC @ 18 VA and 8.5 VDC @ 1.28 VA \$3.50
 - 24 VDC @ 250 ma. \$3.00
 - MULTI-VOLTAGE @ 500 ma. 3, 4, 5, 6, 7, 8, 9 or 12 VDC \$7.50

- MINI-BOX**
Pomona #2104. \$1.00 each
- Heavy-duty black phenolic project box with cover and screws. 2 1/8" x 1 1/2" x 1 1/2"

- FUSES**
- 3AG (AGC) SIZE 1 1/2, 2, 2 1/2, 3, 4, 5, 6 AMP
 - GMA SIZE 1, 2, 3, 4, 5 AMP
 - 5 of any ONE amperage 75¢

COMMODORE PRINTER/PLOTTER

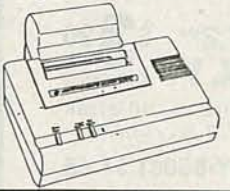Commodore Model # 1520
Four color X-Y plotter. Standard VIC serial interface allows easy connection to Commodore 64 computers. Up to 80 characters per line (upper and lower case) in four sizes.
CAT # COM-1520 \$49.95 each
EXTRA pen sets \$1.50 per set.



SPECIAL PURCHASE

- SPECIALS**
- 1 AMP 50 VOLT DIODES**
IN4001 TAPE AND REEL
100 for \$4.50
1000 for \$30.00
- SOLDER TAIL I.C. SOCKETS**
24 PIN 10 for \$2.50
100 for \$22.00
1000 for \$200.00

- *SPECIAL PRICE* TRANSISTOR**
plastic transistor
PN3569 TO-92 N.P.N.
100 for \$8.00
1000 for \$60.00
LARGE QUANTITIES AVAILABLE

48 KEY ASSEMBLY FOR COMPUTER OR HOBBYIST



NEW T.I. KEYBOARDS. Originally used on computers, these keyboards contain 48 S.P.S.T. mechanical switches. Terminates to 15 pin connector. Frame 4" x 9"
CAT # KP-48 \$6.50 each
2 for \$11.00

- MICRO-CASSETTE MECHANISM**
- Micro-cassette tape transport for standard MC60 or MC45 micro-cassettes. 3 Vdc operation. Contains: drive motor, belt, head, capstan, pinch wheel and other components. 3 1/2" x 2 1/4" x 5/8"
CAT# MCMC \$3.00 each 10 for \$27.50

- COMPUTER GRADE CAPACITORS**
- 2,000 mfd. 200 Vdc 1 3/4" x 5" high \$2.00
 - 6,400 mfd. 60 Vdc 1 3/8" x 3 3/4" high \$2.50
 - 9,700 mfd. 50 Vdc 1 3/8" x 4 1/2" high \$3.00
 - 31,000 mfd. 15 Vdc 1 3/4" x 4" high \$2.50
 - 50,000 mfd. 40 Vdc 3" x 5 3/4" high \$4.50
 - 60,000 mfd. 40 Vdc 3" x 5" high \$3.50
 - 66,000 mfd. 15 Vdc 3" x 3" high \$3.00
 - 86,000 mfd. 30 Vdc 3" x 5 1/4" high \$3.50

- \$1.00 SPECIALS**
- 5,500 mfd. 30 Vdc 1 3/8" x 3 1/2" high \$1.00
 - 5,900 mfd. 30 Vdc 1 3/8" x 2 1/4" high \$1.00
 - 9,300 mfd. 50 Vdc 2" x 4 1/2" high \$1.00
 - 18,000 mfd. 10 Vdc 1 3/8" x 2 5/8" high \$1.00
 - 48,000 mfd. 10 Vdc 2 1/2" x 3 1/4" high \$1.00
 - 100,000 mfd. 10 Vdc 2 1/2" x 6" high \$1.00
 - 185,000 mfd. 6 Vdc 2 1/2" x 4 1/2" high \$1.00

- TI SWITCHING POWER SUPPLY**
- Compact, well-regulated switching power supply designed to power Texas Instruments computer equipment.
- INPUT: 14 - 25 vac @ 1 amp
 - OUTPUT: - 12 vdc @ 350 ma.
 - 5 vdc @ 1.2 amp
 - 5 vdc @ 200 ma.
- SIZE: 4 1/4" x 4 1/4" x 1 1/4" high \$3.50 each

- 13.8 VDC REGULATED POWER SUPPLY**
- These are solid state, fully regulated 13.8 vdc power supplies. Both feature 100% solid state construction, fuse protection, and L.E.D. power indicator. U.L. listed.
- 2 amp constant, 4 amp surge \$20.00 each
 - 3 amp constant, 5 amp surge \$27.50 each

- AUTOMOTIVE CASSETTE PLAYER**
- Ultra Spec #DAT-80-CD
NEW stereo cassette player with auto reverse. 12 Vdc. neg. ground with pre-amp output. Designed for underdash use in 1980 Datsuns.
\$15.00 each
CAT # ACP-80 case of 6 - \$75.00

- 2K 10 TURN**
MULTI-TURN POT
SPECTROL #MOD 534-7161
\$5.00 EACH

- SOLID STATE BUZZER**
- Star # SMB-06L
6 vdc
TTL compatible.
\$1.00 each
10 for \$9.00

- ± 12 Vdc or 24Vdc POWER SUPPLY**
- DELTRON MODEL QD12/15-1.7
Dual plus and minus 12Vdc open frame power supply. Can be used as 24Vdc @ 1.5 amp. INPUT: either 115 Vac or 230 Vac
Fully regulated computer grade supply. 7" x 4 3/4" x 2 3/4"
\$12.50 each 10 for \$110.00

- PHOTO-FLASH CAPACITORS**
- 170 mf 330v 75¢ ea. CAT# PPC-170
 - 400 mf 330v CAT# PPC-400 1.00 ea.
 - 800 mf 330v CAT# PPC-800 1.35 ea.

- LINE CORDS**
- TWO WIRE**
- 6 18/2 SPT-1 flat 3 for \$1.00
 - 6 18/2 SPT-2 flat 2 for \$1.00
 - 6 16/2 SJT round \$1.25 each
- THREE WIRE**
- 6 18/3 flat \$1.50 each
 - 8 18/3 round \$2.00 each

- 3 1/2" SPEAKER**
- 8 ohm impedance. Full range speaker. 8 oz magnet 4" diagonal mounting centers.
\$2.50 each 10 for \$20.00

- TELEPHONE COUPLING TRANSFORMER**
- Stancor # TTPC-8 or Triad # TY-304 P
600 ohms c.t. to 600 ohms c.t.
P.C. board mount 3/4" x 5/8" x 3/4"
CAT - TGTX \$2.50 each

- SPRING LEVER TERMINALS**
- Two color coded terminals on a sturdy 2 1/4" x 3 1/4" bakelite plate.
Great for speaker enclosures or power supplies.
75¢ EACH 10 for \$6.00

- XENON FLASH TUBE**
- 3/4" long X 1/8" dia. Flash tube designed for use in compact camera flash units. Ideal for experimenters.
CAT# FLT-1 2 for \$1.00

- MINIATURE TOGGLE SWITCHES**
ALL ARE RATED 5 AMPS @ 125 VAC
- S.P.D.T. (on-on)** PC style non-threaded bushing. 75¢ each 10 for \$7.00
 - S.P.D.T. (on-on)** Solder lug terminals. \$1.00 each 10 for \$9.00
 - S.P.D.T. (on-off-on)** Solder lug terminals. \$1.00 each 10 for \$9.00
 - S.P.D.T. (on-off-on)** PC style non-threaded bushing. 75¢ each 10 for \$7.00
 - S.P.D.T. (on-on)** PC lugs threaded bushing. \$1.00 each 10 for \$9.00
 - D.P.D.T. (on-on)** Solder lug terminals. \$2.00 each 10 for \$19.00
 - D.P.D.T. (on-on)** Solder lug terminals. \$2.00 each 10 for \$19.00

- STANDARD JUMBO DIFFUSED T 1-3/4**
- RED 10 for \$1.50 100 for \$13.00
 - GREEN 10 for \$2.00 100 for \$17.00
 - YELLOW 10 for \$2.00 100 for \$17.00

- D.P.S.T. LIGHTED ROCKER SWITCH**
- 115 vac lighted rocker. snap mounts in 1 1/2" x 1 1/2" hole. Orange lens. 16 amp contact.
\$1.50

- FLASHER LED**
- 5 volt operation red jumbo T 1 1/4 size \$1.00 each
- NEW GREEN FLASHER**
CAT # LED-4G \$1.00

- MINI-PUSH BUTTON**
- S.P.S.T. momentary normally open 1/8" bushing. Red button.
35¢ each 10 for \$3.00

- BI-POLAR LED HOLDERS**
- Two piece holder for jumbo LED
10 for 65¢ 100 for \$5.00
- CLEAR CLIPLITE LED HOLDER**
- Make LED a fancy indicator. Clear.
4 for \$1.00

- SNAP ACTION SWITCH**
- Cherry elect. #E-21 N.O. or N.C. 0.1A contacts. Suitable for alarms and other low energy circuits. 1 1/2" lever.
45¢ EACH 10 FOR \$4.20

- 220 Vac COOLING FAN**
- ROTRON # MX77A3
Muffin XL
220 Vac
4 1/8" square metal frame fan.
CAT# CF-220 \$6.50 ea
10 for \$60.00 100 for \$500.00
QUANTITIES AVAILABLE

ALL ELECTRONICS CORP.
LOS ANGELES, CA STORE
905 S. Vermont Ave.
213 380-8000

VAN NUYS, CA STORE
6228 Sepulveda Blvd.
818 997-1806

MAIL ORDERS TO:
P.O. BOX 20406
Los Angeles, CA 90006

TWX - 5101010163 ALL ELECTRONIC
EASYLINK MBX - 62887748

TOLL FREE ORDERS ONLY
1-800-826-5432
(ORDER ONLY)
(IN CALIFORNIA: 1-800-258-6666)
ALASKA, HAWAII, OR INFORMATION
(213) 380-8000 NO C.O.D.!

QUANTITIES LIMITED
MINIMUM ORDER \$10.00
USA: \$3.00 SHIPPING
FOREIGN ORDERS:
INCLUDING SUFFICIENT SHIPPING
CALIF. RES. ADD 6 1/2%

RADIO-ELECTRONICS

What's New at AMERICAN DESIGN COMPONENTS?

"The Source" of the
electro-mechanical components
for the hobbyist.

We warehouse 60,000 items at American Design Components — expensive, often hard-to-find components for sale at a fraction of their original cost!

You'll find every part you need — either brand new, or removed from equipment (RFE) in excellent condition. But quantities are limited. Order from this ad, or visit our retail showroom and find exactly what you need from the thousands of items on display.

Open Mon. — Sat., 9–5

THERE'S NO RISK.

With our full 90-day warranty, any purchase can be returned for any reason for full credit or refund.

19" X-Y COLOR DISPLAY



Originally designed for use in Atari coin-operated games. Contains 3-gun color tube, focus and brightness controls. Requires external X-Y inputs, 250-0-24V transformer for power. May be used for oscilloscopes, reprogrammed for game use, or modified with the use of external vertical and horizontal oscillators to a raster scan display or TV monitor for computer use. (IBM compatible.) Transformer supplied.

Item #5449 \$99.00 New

ADAM COMPUTER KIT! (Less printer & w/o cabinet)



Build it yourself from subassemblies. No wiring necessary (just plugs together). Hook-up diagram included. Includes: Keyboard, 1 cassette digital data drive, 2 game controllers, power supply, all memory boards, and one cassette. Is capable of running CP/M, has built-in word processor.

Item #7410 \$99.00 (complete)

500 VA MICRO-COMPUTER REGULATOR (Protect Your Equipment)



Output: 120V/60Hz.
Input range: 95–130V ± 3% Sinusoidal wave output contains less than 3% harmonic distortion. Maintains output additionally +5%–10% down to 78V input. 6 ft. line cord. Input with dual 3-conductor "U" ground output.

Dim.: 16 1/4" L x 8 1/2" W x 7 1/2" H.
Mfr. — Sola #63-13-150.
Item #8007 \$199.00 New

DUAL 3 1/4" DISK DRIVE EXPANSION MODULES



IBM PC Jr.

Side-by-side mounting (PC Jr. mounts on top). With floppy disk drive controller board. Contains: 2 Tabor TC-500 3 1/4" disk drives. Total cap. 500K bytes unformatted*
Item #8825 \$199.00



APPLE

Side-by-side mounting with disk storage space in front. Floppy disk controller board capable of handling four disk drives. Contains: 2 Tabor TC-500 3 1/4" disk drives. Total cap. 500K bytes unformatted*
Item #8826 \$199.00



IBM PC/XT

Stacked mounting, replaces old-fashioned 5 1/4" disk drives. Contains: 2 Tabor TC-500 3 1/4" disk drives. Total cap. 500K bytes unformatted. * Plugs right into your controller.
Item #8827 \$169.00

IBM FORMAT COMPATIBLE 3 1/4" DISK DRIVE

Tabor
TC-500
drivette.

Single-sided, quad density. Capacity: Unformatted—250/500K bytes* Formatted—164K bytes. 80 track/140 TPI, based on 16 sectors. Will work with any 5 1/4" disk controller.
Item #8824 \$79.95

* Total cap. 500K bytes with special software.

5 1/4" DISK DRIVES 96 TPI, DS/QUAD DENSITY



1/2 HT
Tandon #TM55-4
Item #1904 \$79.50 ea.
or 2 for \$150.00



FULL HT
Tandon #TM101-4
Item #1901 \$129.00 ea.

MPI 52S (IBM® Compatible) 5 1/4" FULL HEIGHT DISK DRIVE



Double sided/double density, full height drive. 48 T.P.I., 80 tracks.
Item #7928 \$79.95
2 for \$150.00


115 CFM MUFFIN® FAN



SPECIAL!

115 VAC/60 Hz., 21W., 28A., 3100 RPM; 5-blade model, aluminum housing. Can be mounted for blowing or exhaust. Dim.: 4 1/8" sq. x 1 1/2" deep.
Item #5345 \$5.95 RFE

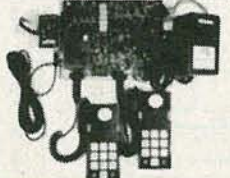COLECO VISION KIT (Assemble yourself, diagram incl.)



Complete unit, without housing. Can be easily mounted on any base. Contains: game board, 2 controllers, power supply, TV game switch & connecting coaxial cable.
Item #7411 \$19.95

ADAM CASSETTES (Assorted)



Buck Rogers, BASIC—plus others! Can be easily erased.
Item #7786 — Bakers Dozen
13 for \$19.95 New

STEP UP-DOWN AUTO-TRANSFORMER 3.5 KVA



3.5 KVA with taps at: 100-115-120/200-208-220-230 & 240V. Ideal for boosting low line voltage, or for use in converting 115 to 230V and 230 to 115V. Dim.: 7"H x 6"W x 5 1/2" deep. Mfr. — Hyde #3575
Item #8006 \$69.00 New

12/24 VDC 1" THIN MUFFIN- TYPE FAN



55/100 CFM, 8W. Can be mounted for blowing or exhaust. 5 plastic blades with feathered edges, aluminum housing. Brushless, ball-bearing type. Dimen.: 4 1/8" sq. x 1" deep
Mfr — Cbntaur CUDC24K4-601
Item #8541 \$19.95

PUMPS—COMPRESSORS—BLOWERS—MOTORS—POTENTIOMETERS—COUNTERS TIMERS—RELAYS—VOLTAGE REGULATORS—POWER SUPPLIES

ADAM PRINTER



Complete, less top cover plate. Friction feed. Takes standard paper 8 1/2" x 11". (Customer returns; tested — operational.)
Item #8839 \$69.50

ADAM COMPUTER TAPE DRIVE



Serial format. Search 80IPS — Read/Write 20IPS. 12V motor, 5V logic, 8 & 9 pin connector cables. Originally designed for the Adam.
Dim: 5"W x 3 1/4"H x 4" deep
Item #6641 \$9.95 New

48-KEY KEYBOARD



Replace the membrane keyboard on your Timex/Sinclair Z-81/1000 with this brand new "big computer" keyboard from Texas Instruments. Simple to install — complete instructions and schematic included.
Item #6712 \$5.95 New

HI-POWER COMPUTER POWER SUPPLY



+5V @ 20A
–12V @ .5A
+12V @ 4A
Input: 115/230V
Dimensions: 9 3/4" L x 4 3/4" deep
Mfr — Power Systems PS1554
Item #8543 \$19.95

AMERICAN DESIGN COMPONENTS, 62 JOSEPH STREET, MOONACHIE, N.J. 07074

YES! Please send me the following items:

Item No.	How Many?	Description	Price	Total

FREE CATALOG of
electro-mechanical
devices sent with
every order.

Shipping & handling, we ship UPS unless otherwise specified. Add \$3 plus 10% total.
Canadian: \$3 plus P.O. cost. Charge only.
Sales Tax (N.J. residents only, please add 6% of total)
ORDER TOTAL

- My check or money order is enclosed. \$15.
- Charge my credit card.
- Visa Master Card Amex

Card No. _____
Exp. Date _____
Signature _____
Telephone: Area Code _____ Number _____
Name _____
Address _____
City _____
State _____ Zip _____

All inquiries and free catalog requests call 201-939-2710.

For all phone orders, call TOLL-FREE 800-524-0809. In New Jersey, 201-939-2710.

cable tv

DESCRAMBLER PARTS!

We stock the exact parts, PC board and AC adaptor for Radio Electronics February 1984 article on building your own **Cable TV Descrambler**.

- #701 PARTS PACKAGE**.....\$29.95
Includes all the original resistors, capacitors, diodes, transistors, integrated circuits, coils, IF transformers (toko BKAN-K5552AXX).
- #702 PC BOARD**.....\$12.95
Original etched & drilled silk-screened PC board used in the article.
- #704 AC ADAPTOR**.....\$12.95
Original (14 volts DC @ 285ma) ac adaptor used in the article.

S □ P □ E □ C □ I □ A □ L □ S

- BOTH #701 & #702..... NOW \$39
- ALL THREE #701, #702 & #704 NOW \$49

Add \$2.50 shipping and handling — \$4.50 for Canadian orders
We also offer quantity Discounts on 5 or more units

FREE Reprint of Radio Electronics article (February 1984) on Building Your Own **CABLE TV DESCRAMBLER** with any purchase of above.

60-CHANNEL CABLE CONVERTER WITH INFRARED REMOTE CONTROL



SC-60R CONVERTER.....\$69.95

Thousands of these converters sold nationally for \$119.95
We offer you this same type of converter for only \$69.95
All converters are NEW, with Full manufacturer's WARRANTY.

FEATURES:

- Full 60 Channel Capability
- Cordless Infrared remote control
- Ultra-Stable Synthesized tuning
- Microprocessor controlled PLL
- Works on all TV models, channel 3 output
- Standard/HRC Switch for compatibility with all Cable Systems
- Will work with all types of external descramblers

Add \$3.50 Shipping and Handling
\$4.50 on Canadian Orders

**ORDER
TOLL FREE
1-800-227-8529**



inside MA 617-695-8699
VISA, MASTERCARD or C.O.D.



**J & W
ELECTRONICS, INC.**

P.O. BOX 800R • MANSFIELD, MA 02048

2001

COMING IN MAY



electronics revolution is in the making, but you don't have to wait until 2001 to find out how it will change your life in the 21st century. Radio-Electronics will forecast the coming changes and how they will affect you in the May 1987 issue!

Created by a special editorial task force—two years in preparation—this unique issue, 2001, takes you into the research laboratories of Westinghouse, Texas Instruments, Ford and Bell Labs where the future is being invented today!

You'll get an advance look at what's coming in artificial intelligence... new cars and highways (cleaner, quieter and more efficient)... futuristic energy sources like magneto-hydrodynamic and particle-beam generators... personal communications systems that will give you instant access to anyone anywhere... super computers and teaching breakthroughs that will multiply your capacity to learn!

Arthur Clarke introduces 2001. Isaac Asimov explores the marvels of robotics. But it is not science fiction. Rather it is

emerging technology with a solid foundation in current research and development.

And its impact will be enormous. It will change the way you work... the way you think... the way you live!

2001 is the kind of special publishing event that can only happen once in any magazine's lifetime and it will happen to Radio-Electronics in May, 1987.

With extra features and extra pages, 2001 will bear a premium cover cost, but you can reserve your copy now at less than the regular cover cost by mailing any one of the subscription orders in this issue.

2001 is coming in May. Make sure now that you don't miss it!

Radio-Electronics[®]

Fluke breaks the old mold.



The Fluke 37. A bold new shape emerges with more features for the money than any other bench DMM. Period.

Dollar for dollar, the new Fluke 37 is unbeatable. In addition to its breakthrough design — with built-in handle and storage compartment — it has all the high-performance features of the world's best, most reliable 3½ digit DMMs.

Autorangeing, to eliminate guesswork. Audible Continuity, so you don't have to look at the display. An exclusive analog and digital display, for the best view of the signal being measured. Superior EMI shielding. And user-friendly features like auto self-test, auto battery test and auto-polarity. All this, *plus* a two-year warranty.

And, how many other \$229 bench meters give you these features? Min-Max recording, for monitoring signals. 38 components dedicated exclusively to input protection. Relative mode, to help you calculate changes in readings. And Fluke's patented Touch Hold, to give you an extra set of hands when you're taking critical measurements.

None. Not at \$229. Not at *any* price.

For your nearest distributor or a free brochure, call toll-free *anytime* **1-800-227-3800, Ext. 229.** (Outside the U.S., call 1-402-496-1350, Ext. 229.)

**FROM THE WORLD LEADER
IN DIGITAL MULTIMETERS.**



FLUKE 37

- \$229*
- 0.1% basic dc accuracy
- Analog/Digital Display
- Volts, Ohms, Amps, Diode Test
- 30 kHz AC bandwidth
- Fused 10A Range
- Integral handle, storage compartment
- 2-year warranty

* Suggested U.S. list price, effective June 1, 1986.

