

Radio - **HOW TO SELECT THE RIGHT SHORTWAVE ANTENNA**

Electronics

JULY 1989

TECHNOLOGY - VIDEO - STEREO - COMPUTERS - SERVICE

TALK ON A LIGHT BEAM

Build R-E's light beam communicator and use the light from an LED to communicate more than 1/2 mile!

BUILD A TV TRANSMITTER

Transmit professional-quality video with our amateur transmitter

BUILD A CAPACITOR TESTER

An easy-to-build way to test and identify capacitors

CIRCUIT COOKBOOK

More than 20 practical oscillators you can build

HOW TO SERVICE DIGITALLY TUNED RADIOS

Practical servicing hints and tips

COMPUTERDIGEST
Build a 80386SX motherboard

Plus: ★ Hardware Hacker
★ Video News
★ Antique Radios
★ And lots more!




\$2.25 U.S.
\$2.75 CAN



FLUKE



PHILIPS

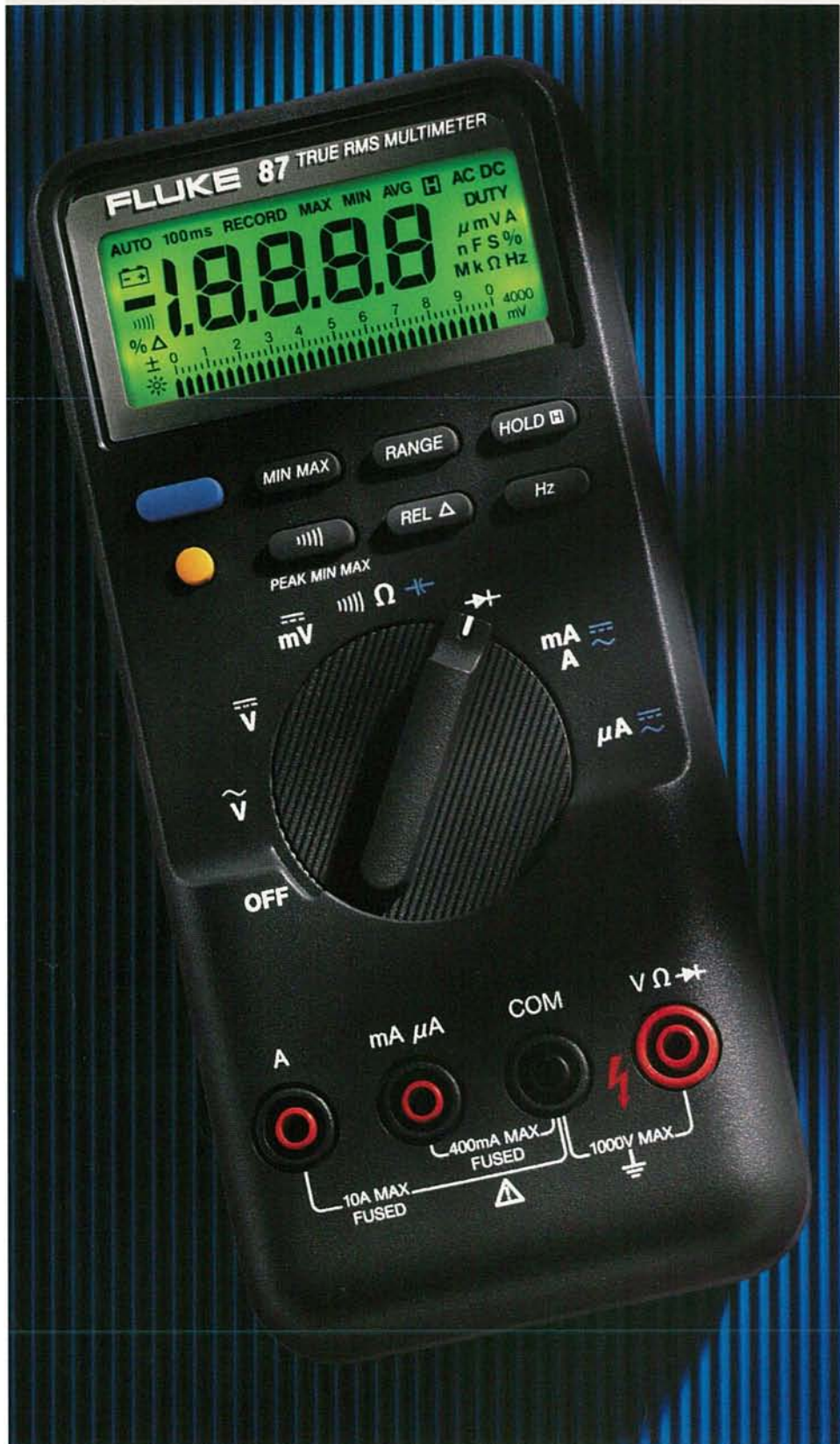

The new 80 Series is a digital meter, an analog meter, a frequency counter, a recorder, a capacitance tester, and a lot more.

It's the first multimeter that can truly be called "multi" ... not only standard features, but special functions usually limited to dedicated instruments.

Plus, innovations only Fluke can bring you. Like duty cycle measurements. Or recording the minimum, maximum and average value of a signal. Or the audible MIN MAX Alert™ that beeps for new highs or lows.

There's even Fluke's exclusive Input Alert™, that warns you of incorrect input connections. And a unique Flex-Stand™ and protective holster, so you can use the 80 Series almost anywhere.

Make sure your next multimeter is truly multi. Call today at **1-800-44-FLUKE, ext 33.**

FROM THE WORLD LEADER IN DIGITAL MULTIMETERS.



FLUKE 83	FLUKE 85	FLUKE 87
Volts, ohms, amps, diode test, audible continuity, frequency and duty cycle, capacitance, Touch Hold™, relative, protective holster with Flex-Stand™.		
\$189*	\$219*	\$259*
0.3% basic dc accuracy	0.1% basic dc accuracy	0.1% basic dc accuracy
5 kHz acV	20 kHz acV	20 kHz acV
Analog bargraph & zoom	Analog bargraph & zoom	High resolution analog pointer
Three year warranty	Three year warranty	True rms ac
		1 ms PEAK MIN MAX
		4½ digit mode
		Back lit display
		Three year warranty

*Suggested U.S. list price

The new Fluke 80 Series shown actual size

John Fluke Mfg. Co., Inc., P.O. Box C9090 M/S 250C, Everett, WA 98206
 U.S.: 206-356-5400 CANADA: 416-890-7600 OTHER COUNTRIES: 206-356-5500
 © Copyright 1988 John Fluke Mfg. Co., Inc. All rights reserved. Ad No. 0581-F80

CIRCLE 121 ON FREE INFORMATION CARD

FLUKE

BUILD THIS

- 31 LIGHT BEAM COMMUNICATOR**
Talk from up to 1/2-mile away using an LED and simple optics.
Roger Sonntag
- 38 DIGITAL CAPACITANCE METER**
A welcome—and easy-to-build—addition to any test bench.
Michael Lashansky
- 45 AMATEUR TV TRANSMITTER**
Get on the air with our transmitter and a video camera!
William Sheets and Rudolf F. Graf

TECHNOLOGY

- 51 OP-AMP OSCILLATORS**
How to design your own op-amp oscillator circuits.
Ray Marston
- 57 NEW RADIOS, NEW PROBLEMS, NEW SOLUTIONS**
Tips for getting digitally-tuned radios back in working order.
Gary McClellan
- 61 CHOOSING THE RIGHT SHORTWAVE ANTENNA**
Learn about antennas for a big improvement in reception.
Joseph J. Carr

COMPUTERS

- 73 OMNIVIEW AND A 386**
Unleash the power of your 386.
Mike Toutonghi
- 81 BUILD AN 80386SX MOTHERBOARD**
Part II provides complete construction details.
Bernard A. McIlhany

DEPARTMENTS

- | | |
|----------------------------------------------------------------------------|------------------------------------------------------------------------------------|
| 6 VIDEO NEWS
The latest happenings.
David Lachenbruch | 28 DRAWING BOARD
A complete circuit.
Robert Grossblatt |
| 8 AUDIO UPDATE
How loud is real?
Larry Klein | 66 HARDWARE HACKER
Get an oscilloscope!
Don Lancaster |
| 20 EQUIPMENT REPORTS
Tektronix 222 digital storage oscilloscope. | 75 EDITOR'S WORKBENCH
Software reviews and more.
Jeff Holtzman |

COMPUTER DIGEST

OMNIVIEW AND A 386 **CeBIT**

OMNIVIEW AND A 386
This article discusses the features and capabilities of the Omniview and A 386 computer system. It covers the hardware components, software options, and performance characteristics. The system is designed for high-speed data processing and is suitable for a wide range of applications, from scientific research to business data management.

CeBIT
This section provides an overview of the CeBIT (Computer Electronics Business Terminals) trade show. It highlights the latest products and technologies on display, including new computer hardware, software, and networking solutions. The show is a key event for the computer industry, offering attendees the opportunity to see and interact with cutting-edge technology.

PAGE 73

TECHNOLOGY

CHOOSING THE RIGHT SHORTWAVE ANTENNA



SA ANTENNAS & ANTENNAS

This article discusses the importance of selecting the right shortwave antenna for improved reception. It covers various types of antennas, their characteristics, and how to choose the best one for your specific needs and budget. The author provides practical advice on installation and maintenance to ensure optimal performance.

PAGE 61

AND MORE

- 100 Advertising and Sales Offices**
- 100 Advertising Index**
- 10 Ask R-E**
- 101 Free Information Card**
- 12 Letters**
- 86 Market Center**
- 22 New Products**
- 56 PC Service**
- 4 What's News**

ON THE COVER



Once in a while we get to present a project that's so much fun to build and use that you hardly realize you're learning while you build. Our Light Beam Communicator is a good example. Built using a high-intensity LED, a sensitive photodiode, and some basic optics, it can be used to communicate over distances that you wouldn't believe possible using an LED! With a range of more than 1/2 mile, it becomes much more than a toy. To get the full story, turn to page 31.

COMING NEXT MONTH

THE AUGUST ISSUE GOES ON SALE JULY 6.

BUILD A SOLAR POWER SUPPLY

Power devices from the sun even at night, using solar cells and nickel-cadmium batteries!

MUSIC-ON-HOLD ADAPTER

An easy-to-build circuit that works with your touch-tone phone.

INSTRUMENT AMPLIFIERS

How they work, and how you can put them to use.

SERVICING DIGITAL RADIOS

Some servicing case histories.

As a service to readers, RADIO-ELECTRONICS publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, RADIO-ELECTRONICS disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

Since some of the equipment and circuitry described in RADIO-ELECTRONICS may relate to or be covered by U.S. patents, RADIO-ELECTRONICS disclaims any liability for the infringement of such patents by the making, using, or selling of any such equipment or circuitry, and suggests that anyone interested in such projects consult a patent attorney.

RADIO-ELECTRONICS, (ISSN 0033-7862) July 1989. Published monthly by Gernsback Publications, Inc., 500-B Bi-County Boulevard, Farmingdale, NY 11735 Second-Class Postage paid at Farmingdale, NY and additional mailing offices. Second-Class mail registration No. 9242 authorized at Toronto, Canada. One-year subscription rate U.S.A. and possessions \$17.97, Canada \$23.97, all other countries \$26.97. All subscription orders payable in U.S.A. funds only, via international postal money order or check drawn on a U.S.A. bank. Single copies \$2.25. © 1989 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

POSTMASTER: Please send address changes to RADIO-ELECTRONICS, Subscription Dept., Box 55115, Boulder, CO 80321-5115.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

Radio Electronics

Hugo Gernsback (1884-1967) founder
M. Harvey Gernsback,
editor-in-chief, emeritus

Larry Steckler, EHF, CET,
editor-in-chief and publisher

EDITORIAL DEPARTMENT

Art Kleiman, editorial director
Brian C. Fenton, editor
Marc Spiwak, associate editor
Daniel Goodman, technical editor
Jonathan A. Gordon,
assistant technical editor
Teri Scaduto, assistant editor
Jeffrey K. Holtzman,
computer editor

Robert A. Young, assistant editor
Byron G. Wels, editorial associate
Jack Darr, CET, service editor
Robert Grossblatt, circuits editor
Larry Klein, audio editor
David Lachenbruch,
contributing editor

Don Lancaster,
contributing editor

Richard D. Fitch,
contributing editor

Kathy Campbell, editorial assistant
Andre Duzant, technical illustrator
Injae Lee, assistant illustrator

PRODUCTION DEPARTMENT

Ruby M. Yee, production director
Robert A. W. Lowndes,
editorial production
Karen Tucker, advertising production
Marcella Amoroso, production traffic

CIRCULATION DEPARTMENT

Jacqueline P. Cheeseboro,
circulation director
Wendy Alanko,
circulation analyst
Theresa Lombardo,
circulation assistant

Typography by Mates Graphics

Cover photo by Diversified Photo Services

Radio-Electronics is indexed in
Applied Science & Technology Index
and *Readers Guide to Periodical Literature*.



Microfilm & Microfiche editions are available. Contact circulation department for details.

Advertising Sales Offices listed on page 100.



GoldStar

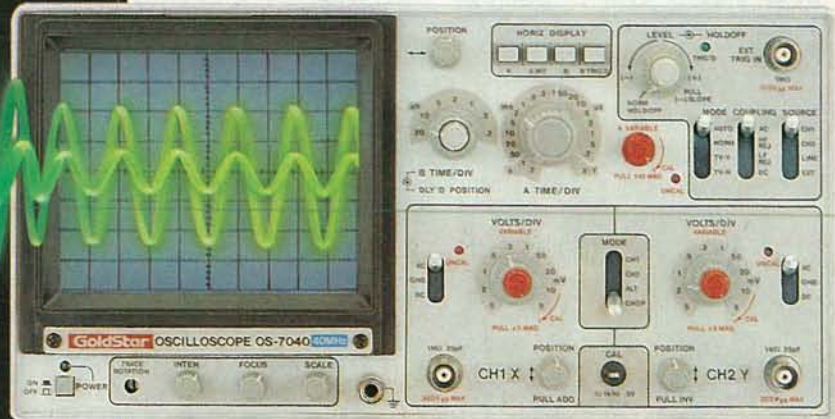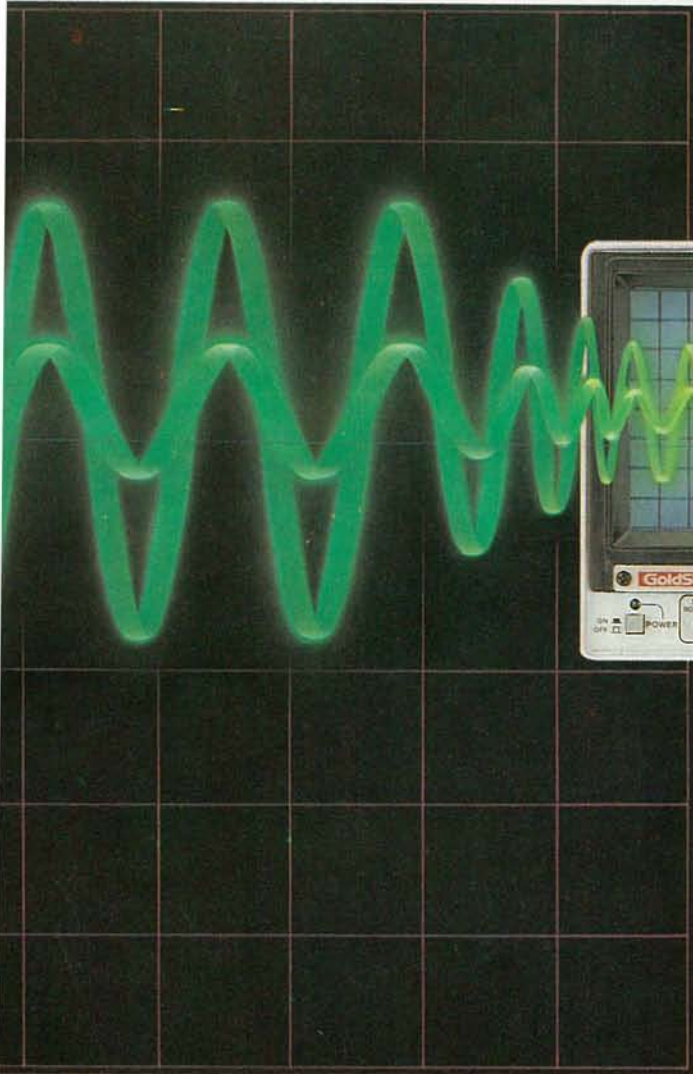THE GOLD STANDARD IN PRECISION ELECTRONICS



Model OS-7040

- 40MHz Dual Trace.
- Delayed Sweep.
- TV Sync. Separation circuit.
- High Sensitivity X-Y mode, Z-axis (intensity modulation)

Precision. The essential quality for all measuring and testing instruments. Goldstar. The name that has come to mean value in over 80 countries around the world.

Goldstar Precision manufactures a complete line of reliable measuring and testing instruments, including:

- oscilloscopes
- function generators
- analog multimeters
- power supplies
- signal generators
- digital multimeters
- frequency counters

In the field or at the bench, these instruments offer the precision technology you need. And the value you've come to expect from Goldstar.

Goldstar measuring and testing instruments. Precision at the right price.

Model OS-7020

- 20MHz Dual Trace.
- TV Sync. Separation circuit.
- High Sensitivity X-Y mode, Z-axis (intensity modulation)



LUCKY-GOLDSTAR

GoldStar Precision

13013 East 166th Street, Cerritos, Ca. 9071
Tel.: (213) 404-0101 Tlx.: (910) 583-5719 LGILA
Fax.: (213) 926-0849, 404-0132


GoldStar Precision Co., Ltd.

19th Fl., East Tower, Lucky-Goldstar Twin Towers
#20, Yoido-dong, Yongdungpo-gu, Seoul 150-721, Korea
Tel.: 787-6835-6, 787-6844, Tlx.: GSRADAR K22838
Fax.: (02) 784-1646 Cable: GOLDRADAR

CIRCLE 180 ON FREE INFORMATION CARD

WHAT'S NEWS

New range opens for spectroscopy

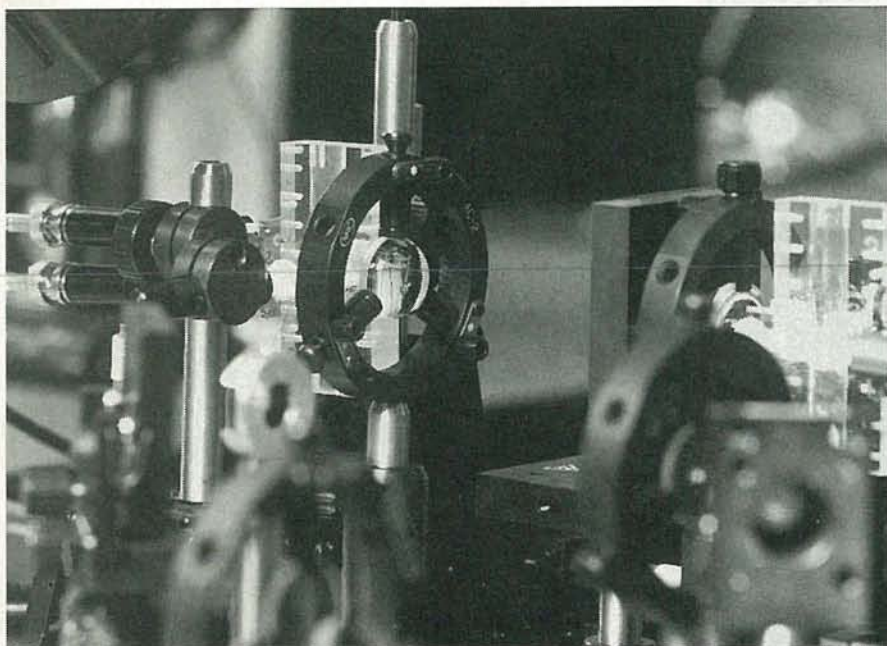

NEW MICROWAVE SPECTROSCOPY TECHNIQUE, developed by IBM scientists, uses picosecond optoelectronic antennas to measure a material's delay and loss characteristics over the microwave spectrum.

Scientists at IBM's Thomas J. Watson Research Institute (Yorktown, NY) report a new spectroscopy technique able to measure the electrical properties of materials over the 10- to 125-gigahertz range. Up to now, information in that area—the microwave spectrum—could be gained only by individual measurements, and only at frequencies for which the required measuring equipment was available. The new system developed by IBM scientists determines the delay and loss characteristics of a material at all points over that wide frequency band, including the electrical connections between high speed computer components.

Circuits in today's computers can generate signals at about 1 GHz. But signals over 100 times as fast are technically feasible. The broad frequency range generated

by such signals interacts with surrounding materials, causing delay and distortion. Knowledge of the delay and loss characteristics of those materials is essential to success in designing future, ultra-fast computers.

In operation, two optoelectronic antennas—fairly new devices in which both electronics and optical components are integrated on a single IC—are positioned 4 centimeters apart. They act as transmitter and receiver, with the material to be examined placed between them. A short laser-pulse photoconductively produces a broad-spectrum microwave pulse in the transmitter. The microwave pulse is transmitted through the sample to the receiver, where a laser pulse samples the signal and produces a record of the delay and loss as it passes through the sample.

New imaging sensor doubles resolution

Scientists at Eastman Kodak Labs have produced an ultra-high-resolution electronic image sensor with more than four million picture elements (pixels). The new development has more than twice the resolving power of sensors now on the market.


The four million pixels, each a tiny square measuring 9×9 microns (millionths of a meter), are in a square of 2,048 vertical columns and 2,048 horizontal rows. Each pixel senses incoming light and converts it into electronic current, which is processed by the device to produce video signals.

Efficient generators use hot gas instead of wires.

A new method of generating electricity, using a generator with conductors of hot gas instead of copper, was announced some years ago. The new method—called magnetohydrodynamics, or MHD—was stated to be 50% more efficient than conventional systems. Nothing further was heard about the method, and it was generally supposed to have been another brilliant but impractical idea.

Now a report comes of a prototype plant in Israel. It appears that the problem had been that the walls of the channel holding the hot gas would corrode and break down. Coating the vulnerable parts with a thin layer of platinum prevents the corrosion.



The plant is said to burn hot coal at 5,000°F. The hot gas is treated chemically to increase its conductivity. It is then injected through a channel in a magnet, generating current. Next, the gas—now cooler—spins a turbine to power a conventional generator, producing more current. That dual generation is said to convert 50% of the coal's energy into electricity, as compared with 34% achieved conventionally. **R-E**

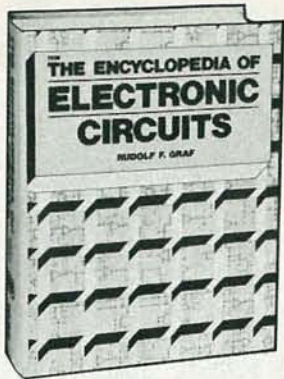

1938 \$60.00
Counts as 3

SELECT 5 BOOKS for only \$3⁹⁵

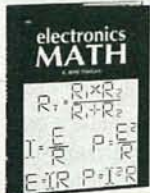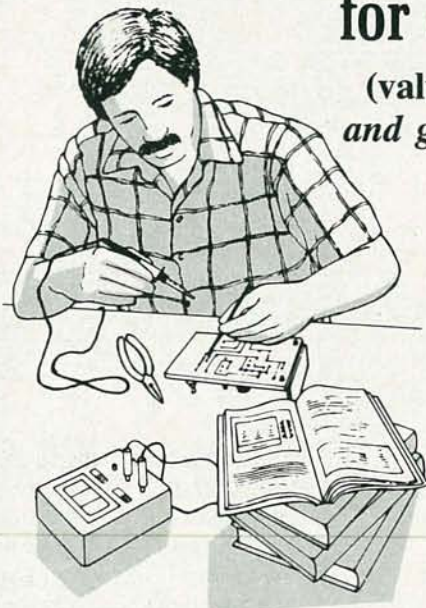(values to \$131.70)
and get a **FREE Gift!**



1962 \$22.95



1964P \$12.95



2753 \$23.95



2898 \$23.95



1536P \$9.95



2867P \$17.95



3054 \$19.95



2707 \$26.95
Counts as 2




3133 \$15.95




1367P \$18.95



2900 \$36.95
Counts as 2

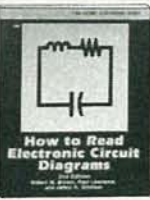

2880 \$20.95

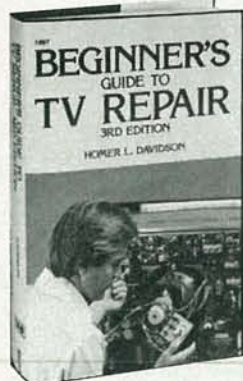

1897P \$14.95



2975 \$24.95



1599P \$17.95



2922P \$15.95



2865 \$21.95



3034 \$19.95



3038 \$22.95

**Electronics projects . . . ideas . . . the latest technology
all at up to 50% off publishers' prices!**

Membership Benefits • Big Savings. In addition to this introductory offer, you keep saving substantially with members' prices of up to 50% off the publishers' prices. • **Bonus Books.** Starting immediately, you will be eligible for our Bonus Book Plan, with savings of up to 80% off publishers' prices. • **Club News Bulletins.** 14 times per year you will receive the Book Club News, describing all the current selections—mains, alternates, extras—plus bonus offers and special sales, with scores of titles to choose from. • **Automatic Order.** If you want the Main Selection, do nothing and it will be sent to you automatically. If you prefer another selection, or no book at all, simply indicate your choice on the reply form provided. As a member, you agree to purchase at least 3 books within the next 12 months and may resign at any time thereafter. • **Ironclad No-Risk Guarantee.** If not satisfied with your books, return them within 10 days without obligation! • **Exceptional Quality.** All books are quality publishers' editions especially selected by our Editorial Board.

All books are hardcover unless numbers are followed by a "P" for paperback. (Publishers' Prices Shown)
© 1989 ELECTRONICS BOOK CLUB®, Blue Ridge Summit, PA 17294-0810

FREE when you join!

15 Easy Electronic Projects From Delton T. Horn
Projects you can build—some unique, some old favorites—from the author's vast treasury of electronics know-how.



Delton T. Horn's
All-Time Favorite
Electronic Projects




ELECTRONICS BOOK CLUB®
Blue Ridge Summit, PA 17294-0810

Please accept my membership in the Electronics Book Club® and send the 5 volumes listed below, plus my FREE copy of *Delton T. Horn's All-Time Favorite Electronic Projects* (3105P), billing me \$3.95 plus shipping and handling charges. If not satisfied, I may return the books within ten days without obligation and have my membership cancelled. I agree to purchase at least 3 books at regular Club prices (plus shipping and handling) during the next 12 months and may resign any time thereafter.

Name _____
Address _____
City _____
State _____ Zip _____ Phone _____
Signature _____

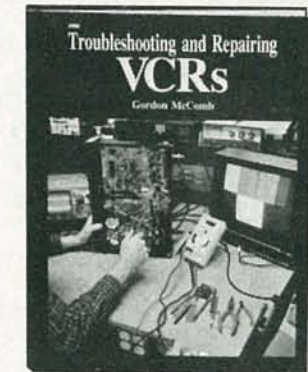Valid for new members only. Foreign applicants will receive special ordering instructions.
Canada must remit in U.S. currency. This order subject to acceptance by the Electronics Book Club® RE769



2960 \$26.95
Counts as 2



2995 \$25.95



2790 \$19.95




2985 \$24.95



2831P \$14.95



1532P \$14.95

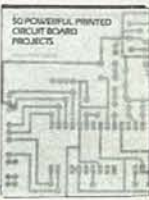

2972 \$23.95

CIRCLE 185 ON FREE INFORMATION CARD

VIDEO NEWS



DAVID LACHENBRUCH,
CONTRIBUTING EDITOR

• **What next for VHS?** Japan's VHS group hopes to continue the evolution of that format, and to keep it ahead of any competition. The next order of business is to try to cope with the problems of the small VHS-C cassette, which is currently being bested in the camcorder battle by the 8mm format. On the theory that the need for an adaptor to play VHS-C cassettes in standard machines is one of the basic problems, the VHS producers are studying the idea of a machine that will play both standard VHS cassettes and VHS-C tapes without requiring an adaptor. Currently, the best thinking is that the machine will be a standard VHS-type with a *built-in* adaptor, which would be pushed to the rear of the recorder when a full-sized cassette is inserted.

The second priority is a digital stereo soundtrack. While the 8mm format has an optional digital-audio system, most 8mm camcorders use a mono AFM analog track that is recorded helically along with the video. The VHS group is working on a helical PCM digital track, but an official of JVC was careful to explain that the aim is compact-disc quality and a substantial improvement on the already excellent AFM.

A longer-term goal is a digital-standards converter built into VHS recorders to eliminate the barriers imposed by different national television signal standards—PAL, SECAM, and NTSC—to make VHS a true worldwide medium. Such a converter would make it possible to play any tape on any TV set in the world, or to dub a recording from one standard to another. Although Matsushita has shown a prototype, it's considered a product for future years.

• **Digital still video.** Although the high-priced analog still-video cameras haven't exactly set the consumer market on fire, there's already discussion in Japan of a standard for a digital still system—which could become the world's first consumer product to employ digital video. The current electronic cameras use a 2-inch "mini-floppy" to record and store analog picture information. Toshiba and Fuji now have proposed an "IC card" camera with virtually no moving

parts. The credit-card-sized IC card currently can store up to 13 exposures, but the two companies are working on signal-compression technology to store at least 50 exposures on one erasable card, and to develop a card that doesn't require a battery backup to keep the picture in storage. The companies say that they're aiming at pictures with at least 400 lines of horizontal resolution, as compared with about 300 in the current video-floppy system. They say that digital images stored on an IC card would allow easy processing of color and the addition or deletion of images, and that their system would bring simpler, more compact and more reliable cameras. The first professional digital cameras could be on the market next year, with a consumer version coming two or three years later.

• **The latest in Videodisc players.** Now available in the U.S. under the Philips brand is a laser-disc player that will play six kinds of discs—including audio CD's and a new type of 8-inch one-sided videodisc "single." It has separate color and luminance outputs, digital special effects, a remote controller with a jog-shuttle dial, and an LCD screen to identify different remote functions. The remote controller is capable of transmitting 750 different commands to TV's, VCR's, and audio equipment in addition to the laser-disc player.

• **A PAL-NTSC VCR.** but Panasonic's latest high-end VCR for the European market helps to eliminate national-standards boundaries. It will play back NTSC tapes through most PAL TV's. It can't convert NTSC's 525 lines into PAL's 625-line picture, nor can it change NTSC's 30 frames per second to PAL's 25. However, it does take advantage of the fact that many PAL sets use the same chips as NTSC sets and adapt themselves to the type of signals they receive. This new set will give many Europeans access to the vast amount of NTSC prerecorded tapes and let them play home movies taped by American friends and relatives. Panasonic is selling the VCR with the warning that it can't play back NTSC tapes on all PAL sets.

R-E

Cable Checklist

ENJOY CABLE TV MORE THAN EVER



SNOOPER STOPPER/DATA BLOCKER \$39⁹⁵



- Prevent cable companies from spying on you to see how many cable converters you have
 - Removes beeping sound from your FM when radio is connected to cable TV
 - Cable TV descramblers are being sold by the thousands, but few people know descramblers can be detected on most addressable systems
- Maintain your privacy with a Snooper Stopper. For more detailed information, send \$2.00 for our "Cable TV Snooper Stopper" article.



MACROVISION... NOW YOU SEE IT, NOW YOU DON'T

MS1-KIT \$29⁹⁵

Includes all the parts, pc board, AC adaptor, and instructions from a published construction article in *Radio Electronics* magazine.



- Remove copy-protection from video cassettes
- Digital filter type; removes only Macrovision pulses

JMAK-4 BLACK BOX \$14⁹⁵

Original box as shown in ad with two feet and four holes to mount pc board.

- No adjustments; crystal controlled
- Compatible with all VCRs
- Uses automatic vertical blanking level
- Assembles in less than three hours



SIGNAL ELIMINATOR \$29⁹⁵




- Works on cable or broadcast TV
- External adjustments allow precise tuning to any frequency
- #23 H-Tuneable to ch. 2 & 3 (50-66 Mhz) also 6 meter HAM TVI interference filter
- #46 FM-Tuneable to ch. 4-6 (66-108 Mhz & FM Band)
- #713-Tuneable to ch. 7-13 (174-216 Mhz)
- #1417-Tuneable to ch. 14-17 (A-D) (120-144 Mhz)
- #1822-Tuneable to ch. 18-22 (E-J) (144-174 Mhz)

ELIMINATE a Channel

that you find unsuitable for family viewing, but is poorly scrambled by your cable company. **OR**

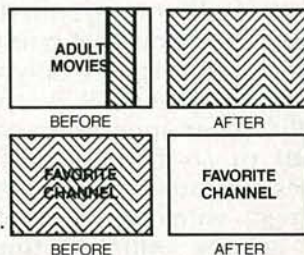
CLEAR UP a Channel that presently contains severe interference by **ELIMINATING** whatever signal is causing this.



Note: If picture and sound are equally affected, this IS interference and CAN be removed by our product. If only picture is affected, this usually IS NOT interference and CANNOT be removed by our product.



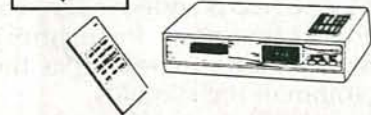72 Channel CABLE CONVERTER with Infra-Red Remote \$79⁹⁵



- Microprocessor controlled PLL operation
- Skip channel memory eliminates unused channels
- Parental control for all channels
- Compatible with all external descramblers
- Last channel recall
- Fine tune memory
- UL listed/FCC approved
- Simple installation with any TV
- Includes battery and 3 foot coax
- Channel output 2 or 3 switchable

Add \$3.50 shipping & handling
\$9.50 Canadian orders

ORDER TOLL FREE ANYTIME 1-800-227-8529

Inside MA: 508-695-8699 Fax: 508-695-9694
Ask for additional free information
Add \$3.00 shipping & handling on all orders unless otherwise noted. \$6.00 Canadian orders.
Visa, MasterCard, or C.O.D.



J & W ELECTRONICS, INC.

P.O. BOX 800 • MANSFIELD, MA 02048

CIRCLE 65 ON FREE INFORMATION CARD

JULY 1989

AUDIO UPDATE

How loud is real?



LARRY KLEIN,
AUDIO EDITOR

DURING THE WILD AND CAREFREE DAYS of my youth, I once participated in a small psychoacoustic experiment. The object was to determine if there was a specific or minimum playback level necessary to achieve a reasonable simulation of "live" sound. After listening to a variety of selections from the best recordings of the day, the participants agreed that there did, indeed, seem to be a specific volume level (that varied somewhat with the recording) at which the music suddenly sounded more "natural." Below that point there was nothing specifically wrong with the sound—it just wasn't *right*. After spending about an hour or so sampling different discs, we found that we generally agreed—within several decibels or so—on the volume setting that sounded best. I don't mean to suggest that the sound was perfect at any level, only that there was a specific volume level at which, for obscure reasons, the reproduced music seemed more realistic.

Calibrating loudness

In the past several decades, I've learned something about the way that the human ear/brain responds to sound levels. Psychoacousticians make a clear and necessary distinction between *loudness* and *sound intensity*. Loudness is the ear/brain's *subjective* auditory reaction to *objective* sound-pressure-level stimuli. It's necessary to distinguish between the subjective and the objective simply because our perception of loudness

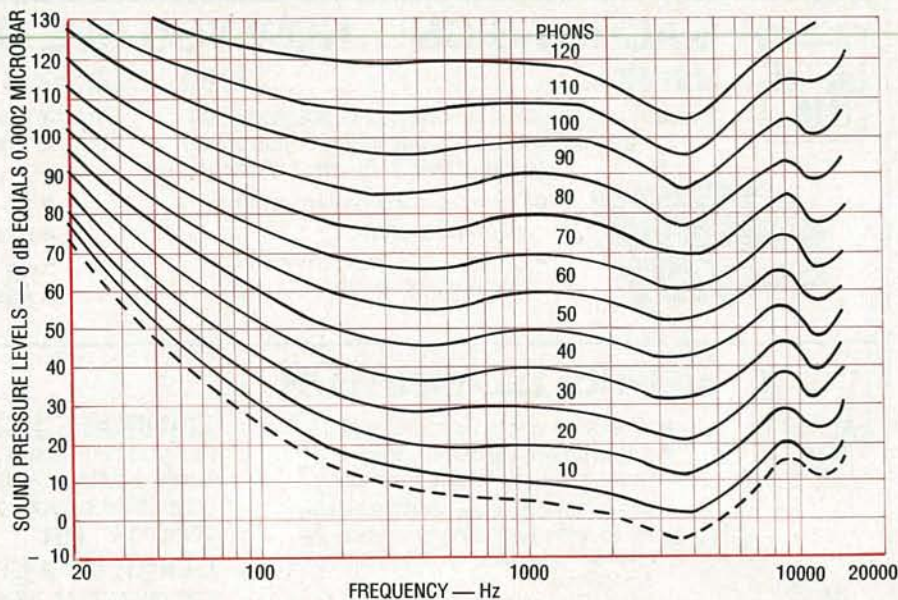


FIG. 1

lacks a one-to-one correspondence with the objective world.

There are good evolutionary reasons why that is so. In respect to volume, for example, the noise created by a jet plane at take-off is about ten-thousand-billion times as powerful as the quietest sound that we can hear. If, on a linear scale, a quiet whisper was assigned one intensity unit, a jet engine would have an intensity of ten-trillion units!

The ability to compress that enormous dynamic range into something that can be handled and evaluated by the human ear/brain was originally investigated by a 19th-century physicist and philosopher, Gustave Theodor Fechner. In 1860, he published a ground-breaking work, *Elements*

of Psychophysics, that attempted to establish a specific relationship between the outer objective world and the inner subjective one in *all* areas of sensation. Fechner's law states, for example, that each time the intensity of a sound is doubled, one step is added to the sensation of loudness. In Fechner's view, sensation increased as the logarithm of the stimulus.

The decibel, which measures sound energy in logarithmic units, would seem to fit nicely into Fechner's law. But it soon became apparent to anyone who listened carefully, that a noise level of, say, 50 dB, was *not* half as loud as 100 dB. (Fifty dB is the background noise in a library reading room; the perceived loudness of 100 dB—equivalent to a jet plane heard

about 1,000 feet overhead—is about 30 times greater than 50 dB.) After much research effort, starting in the 1930's at the Psycho-acoustic Laboratory at Harvard University, Fechner's logarithmic approach to auditory perception was ultimately replaced by a true scale of loudness: the *sones*. The sone scale has a rather straightforward rule: Each intensity increase of 10 decibels doubles the sensation of loudness. Today, it's generally accepted that sound levels have to be raised by 10 dB before they sound twice as loud.

Loudness contours

The names Fletcher and Munson are commonly invoked when amplifier-loudness controls are discussed. In 1933, they were among the first researchers to demonstrate the very non-linear relationships among the objective sound-pressure level of a sound, its frequency, and its subjective loudness. Aside from the fact that the research had conceptual and practical flaws, it also—at least in the audio-equipment area—was misunderstood and misapplied. Let's see where things went wrong.

In the original experiment, listeners in an anechoic chamber were asked to match test tones of different frequencies and intensities with calibrated, 1,000-Hz test tones produced at a variety of specific levels. The general results are familiar to most of us; it was found that the ear loses sensitivity to low frequencies as the sound level is reduced. Later work, by Robinson and Dadson in the mid-1950's, used superior instrumentation and produced a somewhat modified set of loudness contours (Fig. 1). Their results were subsequently adopted by the International Standards Organization and are now known officially as the *ISO equal-loudness contour curves*. Despite the international acceptance of the R-D curves, keep in mind that the techniques used to derive them (pure tones in an anechoic chamber) do not correspond exactly to music listened to in a living room.

Achieving reality

Anyone who has been following my columns with any regularity

should, by now, be convinced that realistic reproduction of music is no easy task. The basic problem is the need to present to the listener's ears a *three-dimensional* acoustic simulation of the live musical event. It has become obvious that the problem can't be solved by conventional, two-channel stereo, and digital "dimension synthesizers" are now becoming commonplace. Although adding the extra channels is a necessary step, it's not a sufficient one; the original playback level at the listener's ears still has to be accurately reproduced.

Why should that be so? Although the question may seem dauntingly complex and laden with philosophical booby-traps, some simple—if incomplete—answers are available. Setting aside the question of the absolute accuracy of the loudness curves discussed earlier, we do know that the ear's frequency response changes in accord with the level of the impinging signal. For example, suppose that you were to make a good recording of a live dance band playing at an average level of 70 dB. If you were to subsequently play back the recording at a 50-dB level, the bass frequencies would automatically suffer a 13-dB loss relative to the mid frequencies, as per Fig. 1. Obviously, not only would the bass line be attenuated, but the entire sound of the orchestra would be thinned out.

Other problems

The ear has other loudness-dependent peculiarities. As a transducer, it is both asymmetrical and non-linear and, therefore, regularly creates (and hears) frequencies that are not in the original material. Known as *aural harmonics* and *combination tones*, they correspond to harmonic- and intermodulation-distortion products in non-biological audio equipment. Since the amounts of those acoustic artifacts generated by the ear depend on signal level, any level differences between the recording and playback are going to cause different reactions in the listener's ears.

To complicate matters further, low-frequency sounds appear to


continued on page 11

When performance & price really count...

CRYSTEK
CRYSTALS
The pulse of dependable communications



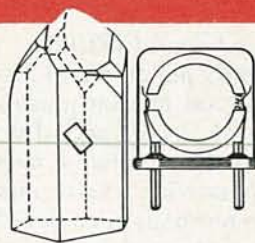Reliability & Quality
From Start To Finished Product



QUARTZ CRYSTALS/OSCILLATORS FOR ELECTRONIC — INDUSTRIAL

- Micro-Processor Control
- Computers/Modems
- Test/Measurement
- Medical

COMMUNICATIONS — REPLACEMENT

- Mobile/2-way/Channel Elements
- Pagers
- Marine
- Aircraft
- Telemetry
- Monitors/Scanners

AMATEURS

- CB
- Hobbies
- Experimenter

COST EFFECTIVE
MODERATE PRICING
FAST DELIVERY



Replacement Crystals Catalog

The Pulse of Dependable Communications

Crystek Crystals offers their new 16 page **FREE** catalog of crystals and oscillators. Offering state-of-the-art crystal components manufactured by the latest automated technology. Custom designed or "off the shelf," Crystek meets the need, worldwide. Write or call today!

CRYSTEK CORPORATION DIVISION OF WHITEHALL CORPORATION

2351/2371 Crystal Dr. • Ft. Myers, FL 33907
P.O. Box 06135 • Ft. Myers, FL 33906-6135
TOLL FREE 1-800-237-3061
(813) 936-2109 — TWX 510-951-7448



CIRCLE 69 ON FREE INFORMATION CARD

ASK R-E

DELAY CIRCUIT

I recently put an alarm system in my house and, to avoid making holes in the walls, I used digital switches inside the door. I'd like some simple circuit to provide a 15-second delay from the normally open switches, so that I can get out of the house before the system is armed.—L. Holmquist, Whitman, MA.

Whenever you need any simple time-delay circuits, the first thing to consider is the 555. Although there are lots of ways to generate a time delay, if your requirements aren't in the nanosecond range, the 555 is the way to go.

Since the 555 was designed for general-purpose timing applications, it can be configured to perform a wide variety of different jobs. The schematic in Fig. 1 is the basic circuit arrangement for setting up the 555 to operate as a pulse generator. You haven't included enough details about your application for me to be sure about the values of the components to use, but the time-delay formula is simple enough for you to fill in the blanks yourself.

The time delay is almost exclusively dependent on the values of R and C, and won't be affected

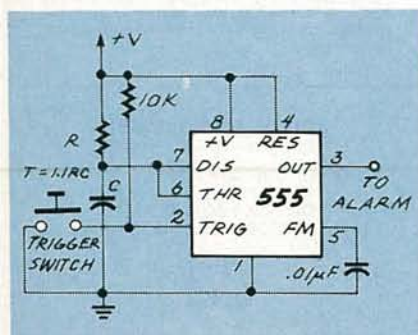


FIG. 1

much at all by temperature or reasonable variations in the supply voltage. All those good things are inherent characteristics of the 555. The trigger input is normally high and the 555 output will be normally low. When the trigger is brought low momentarily, the 555 will start the RC delay and the output will go high. When the 555 times out, the output will go low again and stay there until it's retrigged by your digital switch.

The two important things to remember are that the 555 wants a low trigger and that it will put a high on the output for the delay time that's set by the resistor and the capacitor. You'll have to adapt that to your needs, because I don't know exactly what your setup is; but the 555 is so easy to use that you shouldn't have any trouble at all.

LINEAR TO LOG

Can you show me a simple IC-based circuit which would convert a linear-voltage input into a logarithmic output that could drive a meter? It would be very useful for extending the range of VU and S meters.—J. Cable, Lehigh Acres, FL.

Once upon a time, logarithmic amps were common circuit elements, but as digital stuff started to take over, analog log amps were used less and less. That's really a shame because an analog log amp is a simple one-IC solution to a lot of circuit problems. You're quite right that it's a perfect addition to metering circuitry and, if you get into it, you'll also find that it's great in audio-signal processing as well. It used to be that every compressor and limiter on the market

WRITE TO:

ASK R-E
Radio-Electronics
500-B Bi-County Blvd.
Farmingdale, NY 11735

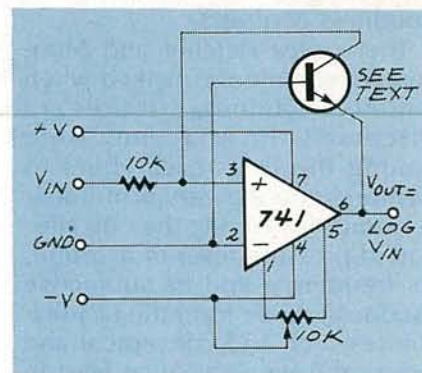


FIG. 2

was built around a log amp, but digital signal processing has shown up in that area as well. But enough nostalgia.

The circuit in Fig. 2 is a basic log amp built around a single op-amp. The configuration is often referred to as a "transdiode" circuit, since the output of the op-amp is equal to the base-emitter voltage of the transistor. The current in the feedback loop of the op-amp is equal to the current flow at the input of the op-amp. Since the input current is proportional to the voltage across the input resistor, it's also proportional to the collector current in the transistor. The base-emitter voltage of the transistor is related logarithmically to the collector current so the output of the op-amp will vary logarithmically with the op-amp's input voltage.

The circuit is built around a 741 but you can use any op-amp you want. The transistor, however, should be a high-gain type, capable of handling the power; since you're only using it to drive a meter, you can probably get by with something like a 2N3391.

I'm sure you know that whenever you build a meter amp, get-

ting the circuit working is only half the battle—you also have to calibrate it. In a straightforward linear amp that isn't much of a problem, but log amps make it a bit more difficult. You can use the brute-force approach of putting known signals at the input and then padding the output, but regardless of the method you use, you have to take into account the offset introduced by the op-amp. That's the purpose of the potentiometer across the offset adjustment pins of the op-amp.

Since the log of one is zero, you should feed the amp with one unit

of positive signal and tweak the potentiometer to get zero out of the op-amp. The amount of accuracy you get depends on the gain, the temperature, and the level of the input.

If you really want to get into this, you'll find that there's a lot of math involved in calculating the circuit parameters and there's just not enough room here to go through all the gory details. It's safe to say, therefore, that the success you're going to have with log amps in general is directly proportional to the number of hours you spend doing research. Good luck. R-E

AUDIO UPDATE

continued from page 9

decrease in pitch when intensity is raised, while highs subjectively increase in pitch. Psychoacousticians know enough about that effect to chart it on what they call the *mel* scale.

Those, and other, reasons help

explain why music sounds correct only when played at the level (the *original* level, that is) that properly relates to the ear's peculiar internal processing. I doubt that it's possible to design a loudness control that really works. So for the present at least, we will just have to do the best that we possibly can, loudness-wise—neighbors and spouses permitting. R-E

DIGITAL VIDEO STABILIZER ELIMINATES ALL VIDEO COPY PROTECTIONS



While watching rental movies, you will notice annoying periodic color darkening, color shift, unwanted lines, flashing or jagged edges. This is caused by the copy protection jamming signals embedded in the video tape, such as Macrovision copy protection. Digital Video Stabilizer: RXII completely eliminates all copy protections and jamming signals and brings you crystal clear pictures.

- FEATURES:**
- Easy to use and a snap to install
 - State-of-the-art integrated circuit technology
 - 100% automatic - no need for any troublesome adjustments
 - Compatible to all types of VCRs and TVs
 - The best and most exciting Video Stabilizer in the market
 - Light weight (8 ounces) and Compact (1x3.5x5")
 - Beautiful deluxe gift box
 - Uses a standard 9 Volt battery which will last 1-2 years.

WARNING :
SCO Electronics and RXII dealers do not encourage people to use the Digital Video Stabilizer to duplicate rental movies or copyrighted video tapes. RXII is intended to stabilize and restore crystal clear picture quality for private home use only.

(Dealers Welcome)

To Order: \$49.95 ea + \$4 for FAST UPS SHIPPING
1-800-445-9285 or **516-694-1240**
 Visa, M/C, COD M-F: 9-6 (battery not included)
 SCO ELECTRONICS INC.
 Dept. CL6 581 W. Merrick Rd. Valley Stream NY 11580
 Unconditional 30 days Money Back Guarantee


CIRCLE 193 ON FREE INFORMATION CARD

Master the skies with the RC Flight Simulator

Learn the ups and downs of RC aircraft and helicopter flight right on your computer screen. Exciting new software designed expressly for Heath Co. by Dave Brown Products lets you take the time you need to become a master pilot. You'll save on heartache and save on dollars when you perfect your skills *before* you ever put your plane in the air.

Menu-driven software gives you a constant read-out of plane distance, true air speed, throttle setting and altitude. Even a dollar estimate of damage flashes on screen each time you crash.

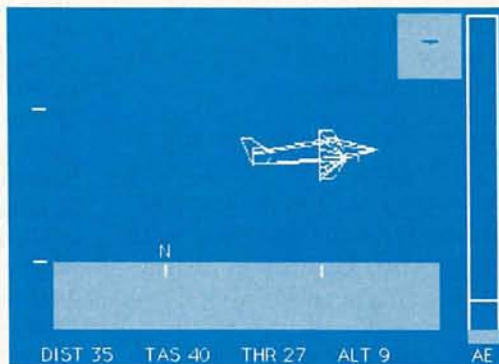Use with Heath/Zenith and IBM PC, XT, AT and compatibles.



Comes with dual joystick controller. Order required gameport adapter separately.

To order your Flight Simulator for only \$129.95 call **1-800-253-0570** 24 hours a day.



Includes flight simulation for helicopters, too!

Heath Company

Benton Harbor, MI 49022

A subsidiary of Zenith Electronics Corporation.

Prices, product availability and specifications are subject to change without notice. © 1989, Heath Company.

CIRCLE 86 ON FREE INFORMATION CARD

ATTENTION! ELECTRONICS TECHNICIANS



EARN YOUR **B.S.E.E. DEGREE**

THROUGH HOME STUDY

Our New and Highly Effective Advanced-Placement Program for experienced Electronic Technicians grants credit for previous Schooling and Professional Experience, and can greatly reduce the time required to complete Program and reach graduation. No residence schooling required for qualified Electronic Technicians. Through this Special Program you can pull all of the loose ends of your electronics background together and earn your B.S.E.E. Degree. Upgrade your status and pay to the Engineering Level. Advance Rapidly! Many finish in 12 months or less. Students and graduates in all 50 States and throughout the World. Established Over 40 Years! Write for free Descriptive Literature.

COOK'S INSTITUTE
OF ELECTRONICS ENGINEERING




4251 CYPRESS DRIVE
JACKSON, MISSISSIPPI 39212

CIRCLE 58 ON FREE INFORMATION CARD

Put Professional Knowledge and a
COLLEGE DEGREE
in your Technical Career through

HOME STUDY

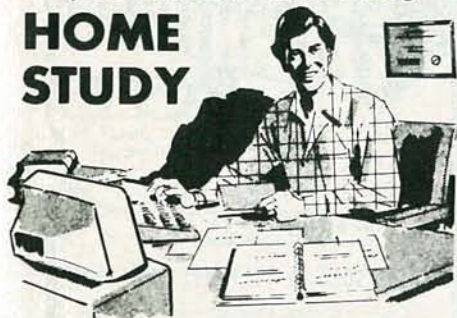

Add prestige and earning power to your technical career by earning your Associate or Bachelor degree through directed home study.

Grantham College of Engineering awards accredited degrees in
electronics and computers.

An important part of being prepared to *move up* is holding the right college degree, and the absolutely necessary part is knowing your field. Grantham can help you both ways—to learn more and to earn your degree in the process.

Grantham offers two degree programs—one with major emphasis in **electronics**, the other with major emphasis in **computers**. Associate and bachelor degrees are awarded in each program, and both programs are available completely by correspondence.

No commuting to class. Study at your own pace, while continuing on your present job. Learn from easy-to-understand lessons, with help from your Grantham instructors when you need it.

Write for our free catalog (see address below) or telephone us at (213) 493-4421 (no collect calls) and ask for our "degree catalog."

Accredited by
the Accrediting Commission of the
National Home Study Council

GRANTHAM
College of Engineering
10570 Humbolt Street
Los Alamitos, CA 90720

LETTERS

HDTV: A POPULIST'S VIEWPOINT

Day of wonders, time of HDTV miracles! The California Cowboys—who gave us Ronald Reagan, Paul Gann, and the shirking of all public responsibility—snuff up to the Federal trough in their BMW's for HDTV grants.

We ought to let the Japanese pay for one of those boondoggles for a change: 99% of the national network/cable-show library is a trashy waste of time, and most of the remainder would gain little from being shown in HDTV format. When I can get an HDTV set for 120% of the price of a regular one then, maybe, I will buy one.

The comparison to compact discs is way off base. Most people buy CD's because LP's are so sickeningly easy to damage. Most likely, the recording will be dubbed onto cassette and played in a car, which is crawling on the freeway at 20 mph because the local government followed Don Lancaster's advice and tore up all those streetcar tracks. The headroom between background noise and gross ear damage will be maybe 40 dB, so who cares about fidelity? And, with today's longer work hours and slower commutes, who has time to listen at home?

I might be willing to fund the California Cowboys' toy development—in proportion to their willingness to fund items that are actually needed. (Even then, as a condition, I would require them to desist permanently from lecturing about "free enterprise," "bootstraps," and so on.) The public and semi-public services of this country—schools, housing, transportation, etc.—are disgraceful, and for the most part, cannot hold a candle to European and Japanese services. Until that is remedied, toys,



LETTERS
RADIO-ELECTRONICS
500-B BI-COUNTY BOULEVARD
FARMINGDALE, NY 11735

however fashionable, deserve no public funding at all.

PAUL SCHICK
Madison, WI

HDTV: ANOTHER OPINION

Thank you for your clear summary of HDTV proposals (**Radio-Electronics**, January 1989). Don Lancaster's view in "Hardware Hacker" was well done, except that he suggested junking existing equipment.

Leave channels 2 through 13 alone, forever, so that folks with ordinary TV sets can tune in as always. Meanwhile, we can open up a brand new set of HDTV channels for the new sets—analogue to AM and FM radio.

No bandwidth available? Painfully untrue. 470–890 MHz is vacant, allocated for 69 little-used UHF channels—a massive piece of RF real estate, waiting for some decent usage. We'd only need half of it for HDTV; the rest could go to cellular and other uses.


Why doesn't the FCC share my opinion? I think that they are too spineless to tell channel 22 to take their re-runs and get off the air, and that they gave in to the political dreamers who think that American companies might manufacture VCR's, TV's, and camcorders. The Japanese did their homework and have their products ready; we didn't. We should just cooperate with their world standard, and enjoy their equipment.

Even if the FCC won't allocate broadcast space, Japan will prevail. Their widescreen TV's and VCR's will sell for pre-recorded

HIGH PLACES



TIGHT SPACES

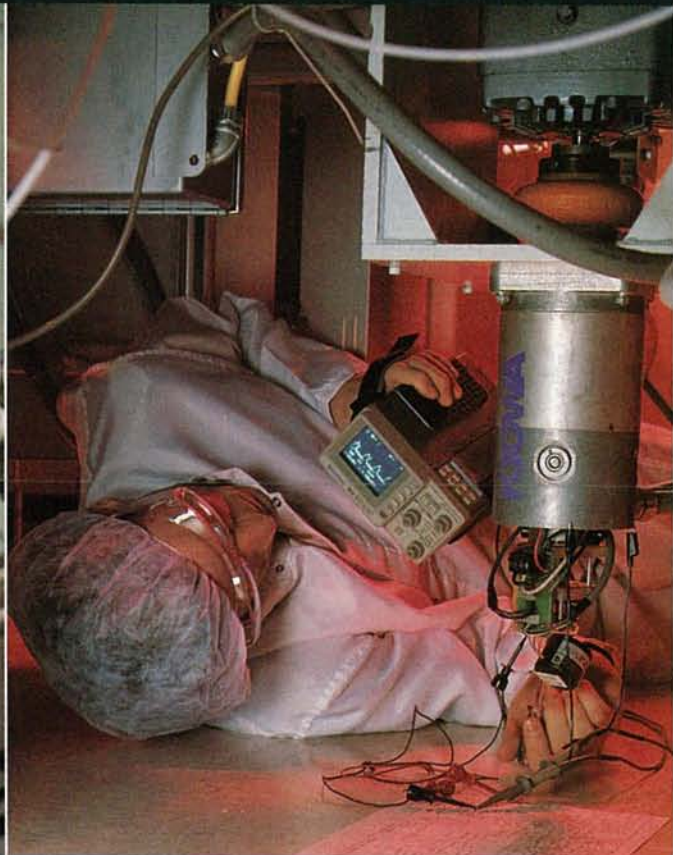

No matter where you go, Tek's new 222 is a perfect fit.

Introducing Tek's new 222 Digital Oscilloscope. Weighing in at under 4.5 pounds, the new Tek 222 is an ultra-portable, 10-MHz digital storage scope that's perfect for service applications. So tough, rugged, and totally self-contained, it can go just about anywhere. And it's incredibly easy to use—even in extreme conditions.

Extraordinary capability and reliability at a great price. The 222 is a dual-channel scope that can measure a wide variety of electronic instrumentation and circuitry. It has rechargeable on-board batteries with a floating ground to 400 volts, and meets tough environmental standards.

Plus, the 222 lets you pre-define front-panel setups, and call them up with a single button in the field. You can also save waveforms in the scope's memory, then transfer them to a PC for analysis and hard-copy output when you get back to the shop.

Best of all, the 222 is yours for only \$2350. And that includes Tek's remarkable three-year warranty on parts, labor, and CRT.

Get one to go! Pack a handful of power with you wherever you go. To order your 222, or for a free brochure, contact your local Tek representative or authorized distributor.

In a hurry? Call
1-800-426-2200.



movies and camcorder use. The cable networks can ignore the FCC. I'll be an early buyer, because I have no need for network-broadcast garbage anyway. I rent video movies.

NORMAN M. HILL
Bellevue, WA

AMPLIFIED SPEAKER MODIFICATIONS

I enjoyed Gary McClellan's "Amplified Speaker" article, which ap-

peared in the September 1988 issue of **Radio-Electronics**. I built two of the speakers, using the exact parts that were specified in the Parts List. Both units performed as suggested in the check-out remarks at the end of the article. However, there's a problem present in both units that I'm hoping you can help me out with.

After turning the power switch on, it is necessary to turn the loudness potentiometer (R2) one-third

to one-half a rotation before getting any volume. When the volume control is turned fully up, I get a moderate amount of sound—approximately half the audio that I get from a 5-watt amplifier that I've had for some time. Is there some slight change I can make that would put more audio into the circuit that would influence the volume potentiometer during the first one-third rotation? Could R1, or R12, or even R10 be reduced for more input to Pin 2 of IC1? Or, perhaps the one-third turn is normal? Not having experience with IC amps, I hesitate to make changes on my own.

T.E. DEWEY
Caney, KS



Shown here:
Model SP100
Switchable 1X-10X **\$43.**

TPI Probes Last Longer, Cost Less

Unique flexible cable and superior strain relief give longer life and easier, more comfortable handling

Order from these distributors:

- | | |
|-------------------------|----------------------------|
| • ACTIVE | • JENSEN TOOLS |
| • ALLAN CRAWFORD ASSOC. | • JOSEPH ELECTRONICS |
| • ALLIED ELECTRONICS | • MARSHALL |
| • BCS ELECTRONICS | • MC MASTER-CARR |
| • CALCOTRON | • OLIVE ELECTRONICS |
| • CHELSEA ELECTRONICS | • RADAR ELECTRIC CO. |
| • CMI METERMASTER | • RS ELECTRONICS |
| • CONTACT EAST | • SOUTHEASTERN ELECTRONICS |
| • EIL INSTRUMENTS | • SPECIALIZED PRODUCTS CO. |
| • ELECTRA TEST | • TECHNI-TOOL |
| • ELECTRONIC PARTS CO. | • WESTCON INC. |
| • ELECTROTEX | • WM. B. ALLEN |
| • FAIRMONT | |

**TEST
PROBES, INC.**



9178 Brown Deer Road, San Diego, CA 92121
Call Toll Free for information and free catalog:
1-800-368-5719
1-800-643-0382 in CA

CIRCLE NO. 123 ON INQUIRY CARD

There are a few things that you can do to improve the sound level. If you think there is a low-volume problem, check the audio-input level, speaker system, and amplifier circuitry.

This unit is intended for input levels above 150 mV, as provided by tuners, tape decks, etc. If your level is less, there are two things you can do. First, connect a 22- μ F electrolytic capacitor across R5. That boosts preamp gain a bit. For more gain, build an amplifier and connect it between the line and the amplifier's volume control. Duplicate the Q1 circuitry from C3 through R4, as shown on the schematic drawing, and power it from D1. With that setup, a dynamic microphone should drive the amplifier to full volume.

The speaker system itself is as important as the amplifier. If you use a low-efficiency unit, the volume will be low. I use a KLH model 23 (8-inch woofer, 2½-inch tweeter), and the volume is enough to drive most reasonable-minded people from my workshop. The sound quality is also quite excellent.

As for the amplifier, your volume-control action is characteristic for the modified log-taper potentiometer specified. If you don't like it, substitute a 100K linear-taper pot, leaving out C2-R1. I guarantee you will be startled by the difference!

Before modifying the circuitry, make sure that all voltages are present and that there is about 5

Radio-Electronics mini-ADS

volts on the collector of Q1. Also, turn up the volume and measure the voltage across C23. If it sags below 11 volts on the audio peaks, get a transformer with more current capacity. Understand that a small transformer cuts power output drastically!

And, finally, to answer your questions on the power-amp IC, gain is set internally and can't be changed by varying parts values.—
GARY McCLELLAN

PC DIS-SERVICE

As a long time subscriber/reader of **Radio-Electronics** and many other Gernsback publications, I would like to comment/complain about a practice that you have taken up recently. I'm an avid experimenter and builder, and I like to make my own printed circuit boards. However, I am not set up on a large scale, and do not own real photographic equipment or have access to any. When I make a board, it is a one-to-one layout with positive artwork transferred by contact exposure to a positive sensitized board.

When your magazine started printing the actual positive artwork for the articles printed in the issue—on a page all alone and with nothing behind them to mess things up—I was delighted. That was the best thing that could have happened for me, because I could directly transfer the layout from the magazine, and didn't have to have a transparency done.

I would like to complain very bitterly about your recent practice of putting a second layout or printing behind the artwork. I thought that the entire idea of putting the artwork on its own page, with nothing behind it, was for people like me who like to make their own boards, but don't have a regular board factory to do it.

Please, please go back to arranging the pages so that the layouts are free of anything behind them.

JIM PRUITT
Richland, WA

If we go back to the practice of leaving the back of PC Service pages blank, that's one less page of information we can print. Well, readers, let's take a vote. Send us your comments.—Editor R-E




CABLE TV CONVERTERS AND DE-SCRAMBLERS SB-3 \$79.00 TRI-BI \$95.00 MLD-\$85.00 M35B \$89.00 JRX-DIC \$129.00 Special combos available. We ship COD. Quantity discounts. Call for pricing on other products. Dealers wanted. FREE CATALOG. We stand behind our products where others fail. One year warranty. **ACE PRODUCTS, P.O. Box 582, Saco, ME 04072 (207) 967-0726.**

CIRCLE 75 ON FREE INFORMATION CARD



THE MODEL WTT-20 IS ONLY THE SIZE OF A DIME, yet transmits both sides of a telephone conversation to any FM radio with crystal clarity. Telephone line powered - never needs a battery! Up to 1/4 mile range. Adjustable from 70-130 MHZ. Complete kit \$29.95 + \$1.50 S+H. Free Shipping on 2 or more! COD add \$4. Call or send VISA, MC, MO. **DECO INDUSTRIES, Box 607, Bedford Hills, NY 10507. (914) 232-3878.**

CIRCLE 127 ON FREE INFORMATION CARD

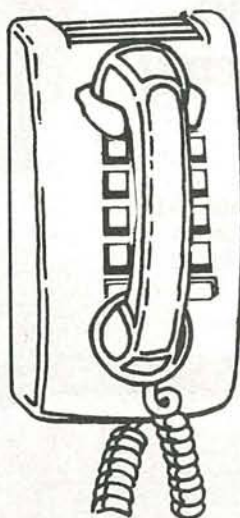

CALL NOW AND RESERVE YOUR SPACE

- 6 x rate \$890.00 per each insertion.
- Fast reader service cycle.
- Short lead time for the placement of ads.
- We typeset and layout the ad at no additional charge.

Call 516-293-3000 to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: mini-ADS, RADIO-ELECTRONICS, 500-B Bi-County Blvd., Farmingdale, NY 11735. FAX: 516-293-3115.



SM-333 Surround Sound Processor for ultimate realism. Features VCR, Video Disc and CD selectable inputs. Can be used with tuners, tape desks and LP discs. Has front panel controlled DYNAMIC NOISE REDUCTION, level, effect and delay. Outputs for front and rear stereo speaker amplifiers. COMPLETE KIT \$62.00 Assembled & Tested \$83.00 + 10% S+H. Call or send VISA, MC, AMEX, MO, CK. **MARK V ELECTRONICS, NC, 8019 E. Slauson Ave., Montebello, CA 90640. (213) 888-8988 FAX (213) 888-6868.**

CIRCLE 190 ON FREE INFORMATION CARD



APPLIANCE REPAIR HANDBOOKS—13 volumes by service experts; easy-to-understand diagrams, illustrations. For major appliances (air conditioners, refrigerators, washers, dryers, microwaves, etc.), elec. housewares, personal-care appliances. Basics of solid state, setting up shop, test instruments. \$2.65 to \$7.90 each. Free brochure. **APPLIANCE SERVICE, P.O. Box 789, Lombard, IL 60148. (312) 932-9550.**

CIRCLE 84 ON FREE INFORMATION CARD

Learn to troubleshoot and service today's computer systems as you build a fully XT-compatible micro, complete with 512K RAM and powerful 20 meg hard drive

Train the NRI Way— and Earn Good Money Servicing Any Brand of Computer

Jobs for computer service technicians will almost double in the next 10 years according to Department of Labor statistics, making computer service one of the top 10 growth fields in the nation.

Now you can cash in on this exciting opportunity— either as a full-time industry technician or in a computer service business of your own—once you've mastered electronics and computers the NRI way.

NRI's practical combination of "reason-why" theory and hands-on building skills starts you with the fundamentals of electronics, then guides you through more sophisticated circuitry all the way up to the latest advances in computer technology. You even learn to program in BASIC and machine language, the essential language for troubleshooting and repair.

Train With a Powerful XT-Compatible — Now With 20 Meg Hard Drive!

To give you hands-on training with the absolute in state-of-the-art computer



You build this powerful Packard Bell VX88 computer, all the while gaining a true mastery of computer electronics. Best of all, it's yours to keep for all your professional and personal computing needs.



technology, NRI includes the powerful new Packard Bell VX88 computer as the centerpiece of your training. As you assemble this fully IBM XT-compatible micro from the keyboard up, you actually see for yourself how every section of your computer works.

You assemble and test your computer's "intelligent" keyboard, install the power supply and 5¼" disk drive, then interface the high-resolution monitor. But that's not all.

Your hands-on training continues as you install a powerful 20 megabyte hard disk drive—today's most-wanted computer peripheral—now included in your course to dramatically increase

Your NRI computer training includes all this:

- NRI's unique Discovery Lab® for circuit design and diagnosis
- NRI's hand-held digital multimeter featuring "talk-you-through" instructions on audio cassette
- A digital logic probe that lets you visually examine computer circuits
- The new Packard Bell VX88 computer with "intelligent" keyboard, 360K double-sided, double-density disk drive, 512K RAM, 16K ROM • 20 megabyte hard disk drive
- Bundled software including MS-DOS, GW-BASIC, word processing, spreadsheet, and database programs
- Packard Bell reference manuals with programming guidelines and schematics.



NEW!
Includes 20 meg
Hard Drive

throughout your training, you've got the full support of your personal NRI instructor and the NRI technical staff, always ready to answer your questions and help you whenever you need it.

FREE 100-Page Catalog Tells More

Send today for NRI's big, 100-page, full-color catalog that describes every aspect of NRI's innovative computer training, as well as hands-on training in robotics, video/audio servicing, electronic music technology, security electronics, data communications, and other growing high-tech career fields. If the coupon is missing, write to: NRI School of Electronics, McGraw-Hill Continuing Education Center, 4401 Connecticut Avenue, NW, Washington, DC 20008.

the data storage capacity of your computer while giving you lightning-quick data access. Plus you work with exclusive word processing, database, and spreadsheet software, yours to use for your own professional and personal applications.

As you build your computer, performing key demonstrations and experiments at each stage of assembly, you get the confidence-building, real-world experience you need to work with, troubleshoot, and service today's most widely used computer systems.

service. You learn at your own convenience in your own home.

No classroom pressures, no night school, no need to quit your present job until you're ready to make your move. And all

NRI School of Electronics

McGraw-Hill Continuing Education Center
4401 Connecticut Avenue, NW
Washington, DC 20008

IBM is a registered trademark of International Business Machines Corporation



No Experience Needed, NRI Builds It In

This is the kind of practical, hands-on experience that makes you uniquely prepared to take advantage of today's opportunities in computer

SEND TODAY FOR FREE CATALOG!



McGraw-Hill Continuing Education Center
4401 Connecticut Avenue, NW, Washington, DC 20008

For Career courses approved under GI Bill
 check for details.



- CHECK ONE FREE CATALOG ONLY**
- Computer Electronics
 - TV/Video/Audio Servicing
 - Robotics
 - Electronic Music Technology
 - Security Electronics
 - Digital Electronics Servicing
 - Electronic Design Technology
 - Industrial Electronics
 - Communications Electronics
 - Basic Electronics
 - Bookkeeping and Accounting
 - Building Construction
 - Automotive Servicing
 - Air Conditioning, Heating & Refrigeration
 - Small Engine Repair
 - Electrician
 - Locksmithing & Electronic Security
 - Travel Careers
 - Computer Programming
 - Paralegal

Name (Please print) _____ Age _____
 Street _____
 City/State/Zip _____ We'll give you tomorrow. _____ Accredited by the National Home Study Council _____ 3-079

JULY 1988

EQUIPMENT REPORTS

Tektronix 222 Handheld Digital Storage Oscilloscope

10-MHz performance in a compact package.

CIRCLE 40 ON FREE INFORMATION CARD



THE IDEA OF A HANDHELD OSCILLOSCOPE has always been attractive. Unfortunately, the idea for the product has been, more often than not, more attractive than the final result. But we recently examined a handheld, dual-channel, 10-MHz scope that we could live with: the model 222 digital storage oscilloscope from Tektronix (P.O. Box 500, Beaverton, OR 97077).

First off, let's define what we mean by "handheld." The 222 measures about $3\frac{1}{2} \times 6 \times 10$ inches. It has a side-mounted strap and rubber-coated grip, so it is indeed designed for handheld operation. However, the scope weighs in at $4\frac{1}{2}$ pounds, so you're not likely to hold it very long without tiring. Fortunately, Tektronix supplies a great carrying case with a shoulder strap that makes portable operation almost comfortable.

We can imagine many applications where the 222 could help the technician on the go. But if you're a field-service engineer, you can undoubtedly come up with dozens of your own applications that would be made easier with a handheld scope. Will the 222 fit your needs?

Specifications

The vertical sensitivity of the 222 is adjustable from 5 millivolts to 50 volts per division, and the timebase is adjustable from 50 nanoseconds to 20 seconds per division.

The scope's 8×10 -division graticule measures about 2.5 inches diagonally.

The 222 has a bandwidth from DC to 10 MHz and a digitizing rate of 10 megasamples per second. Its single-shot storage bandwidth is 1 MHz, while its repetitive storage bandwidth is 10 MHz. For those who are not familiar with digital scopes, some explanation is in order. Digital storage scopes use two digitizing techniques: real-time and equivalent-time sampling. In real-time sampling, all samples for a signal are acquired in a single acquisition period. In equivalent-time sampling, the samples from a repetitive signal are stored; the final display is built up by taking samples of the repetitive signal over multiple sampling periods. Equivalent time sampling serves to extend the useful range of a digital scope.

Digital scopes like the 222 can do lot of things that an analog scope cannot. For example, you can easily freeze any waveform on the screen so that you can examine it closely. For field service, the ability to store up to four waveforms for examination—even hours or days later—can be a godsend. Conversely, you can arrive at the sight with four stored waveforms with which you can compare your field results.

Another example of where a digital scope offers advantages over a

similar analog model is in finding glitches. The 222's envelope acquisition mode accumulates positive and negative peaks on the display. Any peaks that fall outside of the envelope can be easily spotted. If you use a glitch as a trigger event, only a digital scope like the 222 will let you see events that occurred before the trigger.

Using the 222

As you might expect, every effort was made to keep the 222 as small as possible. One of the ways Tektronix accomplished their goal was to use a menu system for selecting many functions. Four *soft keys* are used to select functions from a menu that is displayed alongside the keys on the CRT. For example, when the TRIGGER SOURCE key is pressed, the four soft keys are used to choose between internal and external trigger sources.


The top panel of the scope has a set of 8 frequently-used controls that are used to call up waveform-storage, mode, setup, auxiliary, and trigger-position menus. The rear panel includes such infrequently used controls as intensity, focus, and trace rotation.

The 222's *auto setup* function makes it easy to get a meaningful display on the CRT. When that function is selected, the scope autoranges the vertical sensitivity, timebase, and trigger level. Another time-saving feature is the ability to store and recall up to four front-panel setups.

An RS-232 serial port is available on the rear panel of the 222. A computer can upload front-panel setups and waveforms to the scope and vice-versa. That feature is attractive because, among other things, it lets you do troubleshooting from a remote location.

The Tektronix 222 is priced at \$2350. It would be tough to find more scope for less money in a package this small. **R-E**

OPTOELECTRONICS

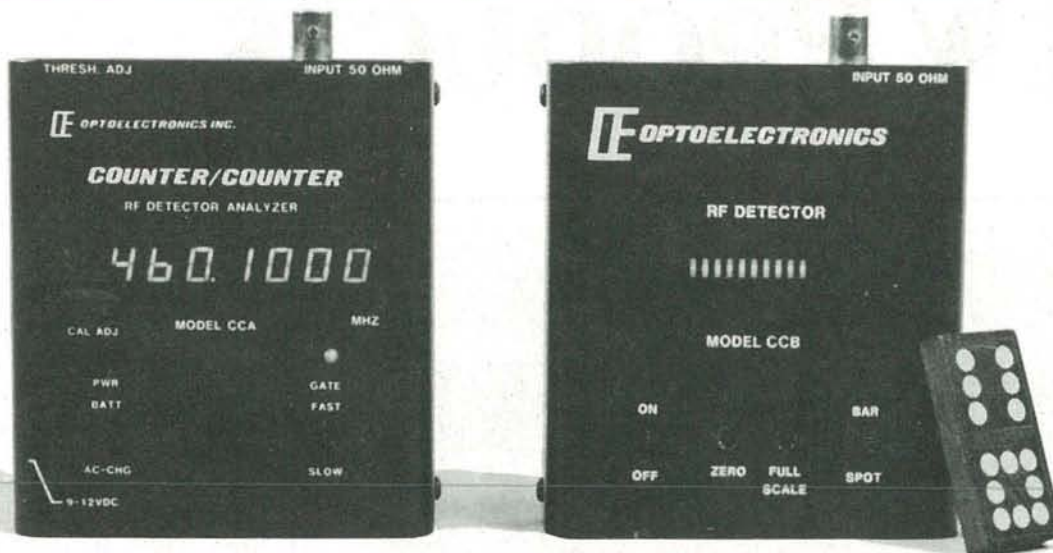

COUNTERING THE RF THREAT COUNTER/COUNTER SERIES FREQUENCY COUNTERS AND RF DETECTORS

Affordable, compact, and ultra-sensitive. More and more people are using CC Series Instruments than ever before for RF detection. Now widely used for personal security, safety and peace of mind, these instruments can locate, identify, isolate, and counter low power radio frequency transmitters that may be concealed in offices, automobiles, conference rooms or are being carried inside clothing, pocket books, etc.

	Range From:	To:	Price:	Sensitivity @ 150 MHz
CCA	10 MHz	550 MHz	\$299	0.1 mV
CCB	10 MHz	2.5 GHz	\$99	1 mV

Model CCA Frequency Counter/RF Detector—Ultra sensitive frequency counter optimized for picking up low power RF transmitters. Features include an RF Indicator LED to confirm presence of RF source nearby. RF Indicator has variable threshold sensitivity control that is adjustable from top of instrument. CCA has 8 digit red .28" LED displays. Internal Ni-Cad batteries provide 2-5 hour portable operation with continuous operation from AC line charger/power supply supplied.

Model CCB RF Detector—Useful for locating exact position of RF source. Will indicate presence of a 1 milli watt transmitter within a twenty foot distance. Ten segment LED display will successively illuminate segments as the distance to transmitter decreases. Powered by 9v alkaline battery for up to 4 hours continuous operation. Front panel switch selects between bar graph and power saving moving spot display. Front panel zero and full scale adjustment pots are provided.

Both instruments require an antenna. Order the model TA-100S Telescoping RF pick up antenna, \$12, for maximum sensitivity. The flexible model RD-100 Rubber Duck is \$20. Model CC12 vinyl zipper carrying case is \$10. Aluminum cabinet is 3.9" H x 3.5" W x 1.1". One year parts and labor guarantee. Add 5% shipping (minimum \$2) all orders.

ORDER FACTORY DIRECT
1-800-327-5912

OPTOELECTRONICS INC.

5821 N.E. 14th Avenue
Fort Lauderdale, Florida 33334

FLA (305) 771-2050
FAX (305) 771-2052




Orders to U.S. and Canada add 5% to total (\$2 min, \$10 max)
Florida residents add 6% sales tax. COD fee \$3.
Foreign orders add 15%

CIRCLE 187 ON FREE INFORMATION CARD

JULY 1989

NEW PRODUCTS

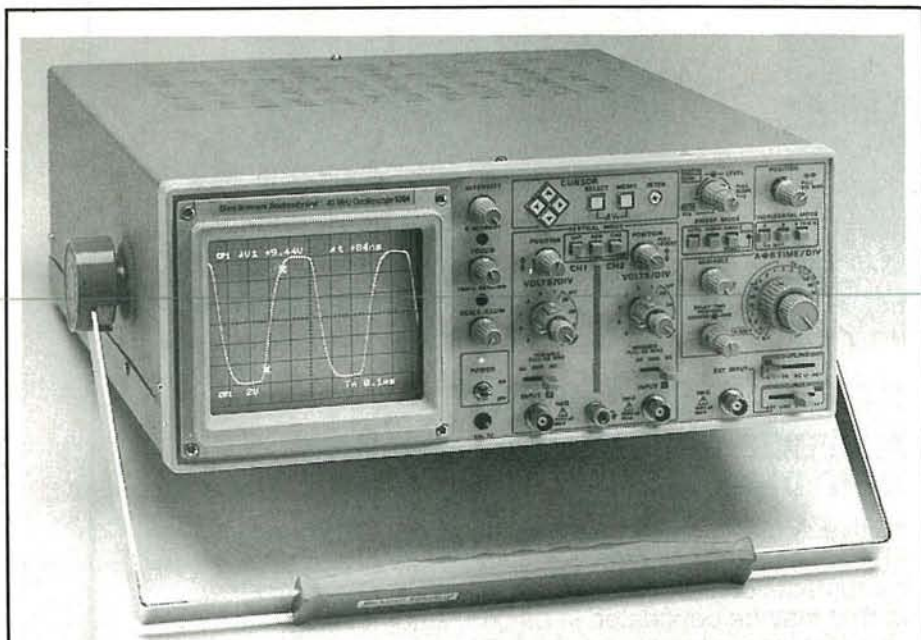

CIRCLE 10 ON FREE INFORMATION CARD

OSCILLOSCOPES. Beckman's 20-MHz model 9202 and 40-MHz model 9204 (pictured) oscilloscopes feature on-screen readouts of cursor positions and scale settings. The "Numeric Readout Display" has two special sets of cursor pairs. Each set has a reference and a delta cursor, both of which can be moved individually or as a pair in eight different directions. The cursors measure amplitude, time, frequency, duty cycle, and phase shift. Voltage and frequency readings can be taken simultaneously.

The scopes are recommended for general electronics- and video-service applications, as well as production tests, quality control,

and engineering research and development. Both models feature "A" and "B" sweeps, with delayed sweep and segment magnification; TV-sync coupling for easy video service; and camera-mount CRT bezel, variable-scale illumination, and single-step operation for waveform photography. A variable hold-off control ensures proper triggering on complex signals. Two switchable $\times 1/\text{REF}/\times 10$ probes are included along with each scope.

The 9202 and 9204 oscilloscopes cost \$865.00 and \$1095.00 respectively.—**Beckman Industrial Corporation**, Instrumentation Products Division, 3883 Ruffin Road, San Diego, CA 92123-1898.

PORTABLE CD SOUND SYSTEM. Soundesign's model 4955 offers on-the-go music lovers a choice of listening to CD's, cassette tapes, or AM/FM radio, through 2-way stereo speakers with "Extra Bass Sound (XBS)" or, more privately,

via a headphone jack. The lightweight unit measures $2\frac{1}{2} \times 8 \times 6$ inches, and has a black, granite-like finish. It runs on AC power or D-size batteries, and has a fold-away carrying handle.

The front-loading CD player

uses 3-beam, 1-laser pick-up, and features a 16-item, random-access memory for standard-size discs. The smaller CD singles can be played with the use of an adapter. Track number, total time, time remaining, program number, pause, and repeat are displayed on a 6-digit LCD.

The 4955's dual tape deck, with high-speed or normal dubbing, allows users to record from the other cassette deck, the CD player, the radio, or live (microphone not included). The cassette deck plays continuously from tape to tape. The AM/FM radio's sound is adjustable with slide controls on the 3-band graphic equalizer. The radio has automatic frequency control for improved reception, and PLL-MPX circuitry for better stereo separation.





CIRCLE 11 ON FREE INFORMATION CARD

The model 4955 portable CD sound system has a suggested retail price of \$229.95.—**Soundesign Corporation**, Harborside Financial Center, 400 Plaza Two, Jersey City, NJ 07311.

CAR CD SYSTEM. Pioneer's DEH-55 is a high-power, one-piece combination CD player, amplifier, and AM/FM tuner that provides the convenience of direct in-dash replacement. The audio package can be installed as either a front- or rear-mount DIN-sized replace-

SELECT 5 BOOKS for only \$395

(values to \$134.75)

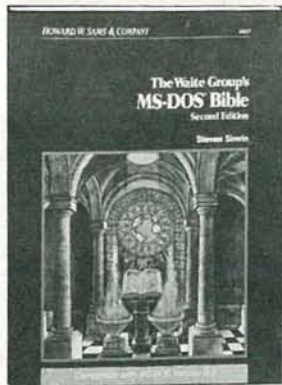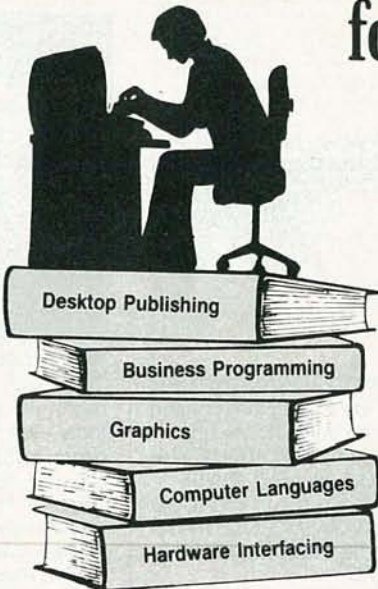

9168P \$22.95
Counts as 2



3068P \$22.95



2870 \$24.95



2852P \$17.95



2807P \$14.95



2913P \$14.95



3032P \$12.95



2838 \$19.95



3119P \$21.95



2943P \$18.95



2654 \$19.95



3030P \$17.95



3122 \$27.95
Counts as 2



8226 \$29.95



3146P \$17.95



2809 \$27.95
Counts as 2



2959 \$29.95
Counts as 2



3031P \$16.95



3016P \$17.95



2856P \$18.95



3127P \$16.95



2890 \$34.95
Counts as 2



2841P \$15.95



2968P \$19.95

When it's new and important in business or personal computing, The Computer Book Club® has the information you need . . . at savings of up to 50% off publishers' prices!



3101 \$29.95
Counts as 2



3128P \$22.95



3109 \$28.95
Counts as 2



3026 \$22.95

Membership Benefits • Big Savings. In addition to this introductory offer, you keep saving substantially with members' prices of up to 50% off the publishers' prices. • **Bonus Books.** Starting immediately, you will be eligible for our Bonus Book Plan, with savings of up to 80% off publishers' prices. • **Club News Bulletins.** 14 times per year you will receive the Book Club News, describing all the current selections—mains, alternates, extras—plus bonus offers and special sales, with scores of titles to choose from. • **Automatic Order.** If you want the Main Selection, do nothing and it will be sent to you automatically. If you prefer another selection, or no book at all, simply indicate your choice on the reply form provided. As a member, you agree to purchase at least 3 books within the next 12 months and may resign at any time thereafter. • **Ironclad No-Risk Guarantee.** If not satisfied with your books, return them within 10 days without obligation! • **Exceptional Quality.** All books are quality publishers' editions especially selected by our Editorial Board.

All books are hardcover unless numbers are followed by a "P" for paperback. (Publishers' Prices Shown)
©1989 THE COMPUTER BOOK CLUB®, Blue Ridge Summit, PA 17294-0820

 **The Computer Book Club®**
Blue Ridge Summit, PA 17294-0820

Please accept my membership in The Computer Book Club® and send the 5 volumes listed below, billing me \$3.95 plus shipping and handling charges. If not satisfied, I may return the books within ten days without obligation and have my membership canceled. I agree to purchase at least 3 books at regular Club prices (plus shipping/handling) during the next 12 months and may resign any time thereafter.

Name _____
Address _____
City _____
State _____ Zip _____ Phone _____
Signature _____

Valid for new members only. Foreign applicants will receive special ordering instructions. Canada must remit in U.S. currency. This order subject to acceptance by The Computer Book Club®. RPIC789



3116 \$27.95
Counts as 2



9811 \$28.95



3049 \$36.95
Counts as 2



2812 \$24.95



2997 \$25.95



9762P \$21.95



9810 \$24.95


CIRCLE 192 ON FREE INFORMATION CARD

Radio-Electronics mini-ADS



CABLE TV CONVERTERS IN STOCK. Stocking all types of converters: Panasonic, Jerrold, Tocom, Pioneer, Scientific Atlanta, Zenith, Oak, Hamlin, Eagle, and others. **Call or write for FREE CATALOG** Mon - Fri 10 to 6 Eastern Time. **VIDEO-LINK Enterprises, Inc., 165 W. Putnam Ave., Greenwich, CT 06830, (203) 622-4386.**

CIRCLE 64 ON FREE INFORMATION CARD

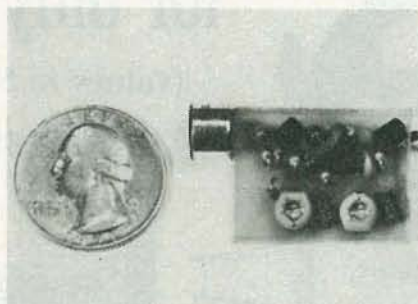


SIMPLY SNAP THE WAT-50 MINIATURE FM TRANSMITTER on top of a 9v battery and hear every sound in an entire house up to 1 mile away! Adjustable from 70-130 MHZ. Use with any FM radio. Complete kit **\$29.95 + \$1.50 S + H.** Free shipping on 2 or more! COD add \$4. Call or send VISA, MC, MO. **DECO INDUSTRIES, Box 607, Bedford Hills, NY 10507. (914) 232-3878.**

CIRCLE 127 ON FREE INFORMATION CARD




FREE CATALOG OF HARD-TO-FIND TOOLS is packed with more than 2000 quality items. Your single source for precision tools used by electronic technicians, engineers, instrument mechanics, schools, laboratories and government agencies. Also contains Jensen's line of more than 40 tool kits. Send for your free copy today! **JENSEN TOOLS INC., 7815 46th St., Phoenix, AZ 85044. (602) 968-6231.**

CIRCLE 115 ON FREE INFORMATION CARD

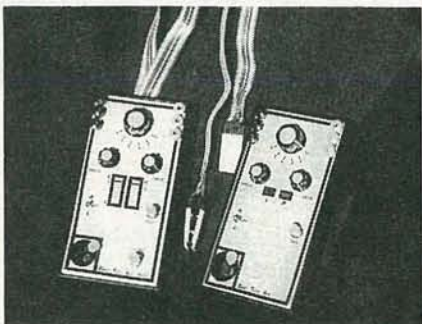


THE E.T.A. VIRTUALLY TESTS ALL COMPONENTS IN OR OUT OF THE PC-BOARD by allowing the user to compare impedance sweeps. It tests: ICs analog and digital, resistors, capacitors, transistors, S.C.R., and diodes. **USE THE AUDIO BY ITSELF** or with the X-Y mode of your oscilloscope. E.T.A. **\$245.** with DIP pin sequencer **\$425.** M.O. VISA MC to **STAR TEST CO., P.O. Box 50067 Denton, TX. 76206 (817) 387-8847.**

CIRCLE 186 ON FREE INFORMATION CARD

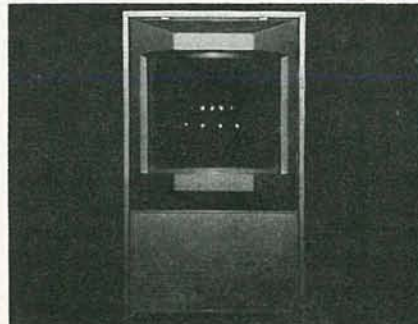

PASSIVE INFRARED DETECTOR • Used in alarm system, moving detection • Super sensitive • Exchangeable lens • Very reliable • Analog Pulse Count • **RK4000PCA \$59.—**
DIGITAL VOICE MODULE • Low cost • Super quality • Selectable banks • 1 W amp • 4 sampling rates • DRAM operation • **DVM-1 \$49—**(without RAM). **MING ENGINEERING, 515 S. Palm Ave., #5 Alhambra, CA 91803. (818) 570-0058.**


CIRCLE 188 ON FREE INFORMATION CARD

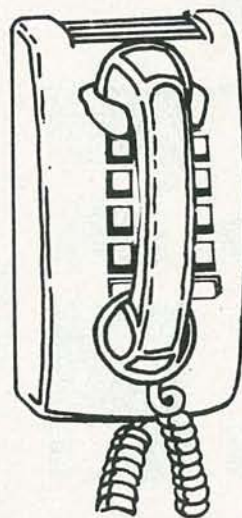

CALL NOW AND RESERVE YOUR SPACE

- 6 x rate \$890.00 per each insertion.
- Fast reader service cycle.
- Short lead time for the placement of ads.
- We typeset and layout the ad at no additional charge.

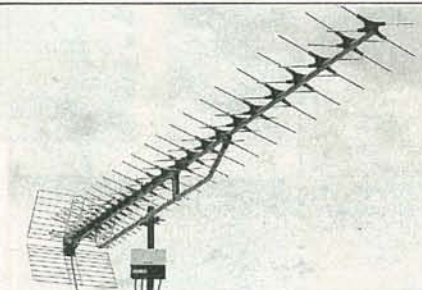Call **516-293-3000** to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: mini-ADS, RADIO-ELECTRONICS, 500-B Bi-County Blvd., Farmingdale, NY 11735.



ULTIMATE UHF FRINGE AREA RECEPTION, receive snow free Uhf/Vhf/Fm signals. Uhf system includes 144 element antenna, 37db low noise pre amp (booster) for **\$219.95.** Complete documentation and one year limited warranty. Tunnel-Vision pre amps for use in interference areas **\$159.95.** Vhf/Fm long yagis and pre amps. STL pre amps **\$209.95.** Visa- Master card and approved CODs. Dealer inquiries accepted. **DX-TELELABS, 6601 E. Clinton St., Scottsdale, AZ 85254 (602) 998-3966.**

CIRCLE 189 ON FREE INFORMATION CARD



GET YOUR RECHARGE CATALOG FREE...EARN BIG \$\$ IN YOUR SPARE TIME—All supplies and Do-It-Yourself kits with complete instructions available. Supplies cost from **\$9.95** in qty and you can sell recharged toner cartridges for **\$40.00** to **\$55.00** each. Printers include HP LaserJet and Series II, Apple LaserWriter, QMS, etc. Canon PC-25 Copier also. **CHENESKO PRODUCTS, 62 N Coleman Rd., Centereach, NY 11720, 516-736-7977, 800-221-3516, Fax: 516-732-4650**

CIRCLE 191 ON FREE INFORMATION CARD



CIRCLE 12 ON FREE INFORMATION CARD

ment unit; all it requires are a pair of digital-ready speakers and a dashboard opening.

The CD player offers a variety of playback modes, including track search, track scan, music repeat, and random play. The two-times oversampling unit with three-beam laser pick-up also offers fast-forward and reverse functions with sound; and power-disk-load, power-eject, and auto-play features included.

The AM/FM tuner uses PLL-quartz electronic digital tuning, with Pioneer's "Supertuner III." It has 24 station presets (18 FM and 6 AM), preset scan for finding local stations, and "best stations memory" that accesses and stores the 6

strongest stations in a designated area. A built-in pulse-noise suppressor eliminates ignition and static noise received through the antenna.


The unit's amplifier delivers 20-watts per channel, and has electronic volume/balance controls, separate bass and treble controls, and an electronic preamp fader control.

The "euro-style" unit has a digital multi-function level display that shows volume, bass, treble, balance, and fader settings in numeric values, rather than bar-graph level indicators. A large LCD with a clock readout is easy to read.

The DEH-55 car-audio package has a suggested retail price of \$600.00.—**Pioneer Electronics (USA) Inc.**, 2265 E. 220th St., P.O. Box 1720, Long Beach, CA 90801-1720.

PORTABLE SPECTRUM ANALYZER.

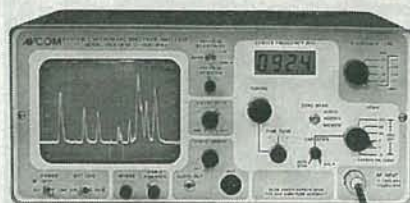The Model PSA-65A from Avcom is a portable microwave spectrum analyzer that covers frequencies through 1,000 MHz in one sweep,



CIRCLE 13 ON FREE INFORMATION CARD


with greater than -90 -dBm sensitivity at narrow spans. The lightweight instrument can be used for 2-way radio, cellular, cable, LAN, surveillance, production, and R&D work.

The PSA-65A measures $11\frac{1}{2} \times 5\frac{1}{2} \times 13\frac{1}{2}$ inches, and weighs 18 pounds. It runs on batteries or AC power. Options include audio demodulators for monitoring, log-periodic antennas, a carrying case, and frequency extenders that enable the instrument to be used at Satcom and higher frequencies.

The PSA-65A portable spectrum analyzer costs \$2,675.00.—**Avcom of VA, Inc.**, 500 Southlake Blvd., Richmond, VA 23236.

With Just One Probe Connection, You Can Confidently Analyze Any Waveform To 100 MHz, 10 Times Faster, 10 Times More Accurately, Absolutely Error Free, Guaranteed — Or Your Money Back!

SC61 Waveform Analyzer™
Patented
\$3295

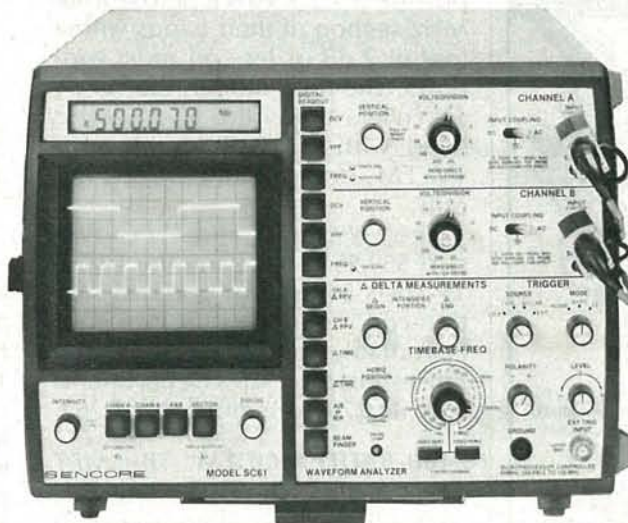

There are other digital readout oscilloscopes, but none of them completely eliminate graticule counting and calculations like the SC61 Waveform Analyzer. The innovative, time-saving AUTO-TRACKING™ digital readout automatically gives you every waveform parameter you need for fast troubleshooting.

The SC61 Waveform Analyzer is a triple patented high performance scope that provides you with a digital LCD read-out of all key waveform parameters (DC volts, peak-to-peak volts, and frequency) at the push of a button, and all with one probe connection.

Other time-saving features include exclusive ECL sync circuits that allow you to lock quickly onto waveforms up to 100 MHz. Plus, with 3000 volts of input protection, you never have to worry about an expensive front end repair job.

Call **1-800-843-3338** to find out more about what the SC61 can do for your service business. In Canada call **1-800-851-8866**.

SENCORE

3200 Sencore Drive, Sioux Falls, SD 57107

100% American Made

CIRCLE 177 ON FREE INFORMATION CARD

Be an FCC LICENSED ELECTRONIC TECHNICIAN!



No costly School. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radio-telephone License". This valuable license is your "ticket" to thousands of exciting jobs in Communications, Radio-TV, Microwave, Computers, Radar, Avionics and more! You don't need a college degree to qualify, but you do need an FCC License.

No Need to Quit Your Job or Go To School
This proven course is easy, fast and low cost! **GUARANTEED PASS**— You get your FCC License or money refunded. **Send for FREE facts now. MAIL COUPON TODAY!**

COMMAND PRODUCTIONS

FCC LICENSE TRAINING, Dept. 90
P.O. Box 2824, San Francisco, CA 94126

Please rush FREE details immediately!

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

New Scanner by AOR

100 Channels
800 MHz



- Includes antenna, rechargeable battery, charger/adaptor & belt clip. Full range of optional accessories available.

- Covers 27-54 MHz, 108-174 MHz, 406-512 MHz, and 830-950 MHz.
- 5 Scan Banks and 5 Search Banks.

AR900

Total Price, Freight Prepaid
(Express Shipping Optional)

\$299.00

- 25 Day Satisfaction Guarantee, Full Refund if not Satisfied.
- No Frequencies cut out.
- Size: 2" x 5 3/4" x 1 1/2" wt: 12 oz.

ACE

COMMUNICATIONS

10707 E. 106th St. Indpls., IN 46256


Toll Free 800-445-7717

Visa and MasterCard
(COD slightly higher)

In Indiana 317-849-2570 Collect FAX (317) 849-8794

CIRCLE 178 ON FREE INFORMATION CARD

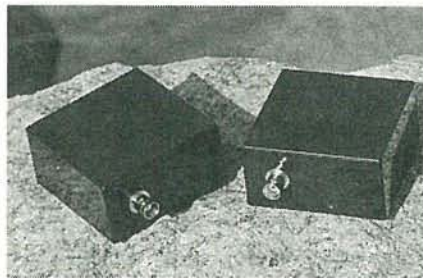OUTSIDE CONNECTOR. The *WPO Window Coupler* from *Electron Processing* provides a novel way to connect an outside antenna to an indoor television, scanner, or UHF/VHF transceiver. The coupler,



CIRCLE 14 ON FREE INFORMATION CARD

which consists of two boxes, mounts on a window using double-faced tape, and completely eliminates the need to drill holes in the window frame to route the antenna line—even coaxial cable. Each 3- x 3- x 1 1/2-inch, weatherproof box contains either a BNC, UHF (PL-259 mate), or type-F connector for antenna and receiver (or transmitter) hookups.

The *Window Coupler* is available in three models. The *WPO-VHF* is for use in the 140-160-MHz range, and the *WPO-UHF* is for the 440-460-MHz range. Both of those models are rated for 25 watts and provide a 1.5:1 VSWR across a 10-MHz section of their bands with a loss of 2 dB or less on most windows. The third model, the *WPO-TV* covers the entire 60-800-MHz band, with only 8-dB loss. It is for TV, FM, and scanner receiving only.

The *WPO-UHF* and *WPO-VHF* cost \$59.95 apiece, and the *WPO-TV* costs \$49.95. An optional suction-cup mounting bracket (*SC-4*) is available for \$20.00.—**Electron Processing, Inc.**, Sales Department, P.O. Box 708, Medford, NY 11763.

2400-BAUD MODEM. The *MET 2400X "Smart Modem"* eliminates




CIRCLE 15 ON FREE INFORMATION CARD

the need to purchase an additional serial port. Because the modem incorporates two RS-232 ports, a printer, mouse, or other peripheral can be linked to the computer through the modem. The modem's "Pass Thru" feature automatically connects the peripheral and the computer when the modem is turned off.

Designed for high-speed synchronous and asynchronous communications, the *MET 2400X* works with all microcomputers that have a serial RS-232 port, and is Bell-103 and 212A compatible. It automatically detects and adjusts to a 2400, 1200, or 300 baud.

The *MET 2400X* costs \$295.00. Volume discounts are available, as are packages including specially priced *Mirror III* (for IBM compatibles) and *Microphone* (for Apple Macintosh PC's) communications software.—**Micro Electronic Technologies Inc.**, Computer Products Division, 35 South Street, Hopkinton, MA 01748.

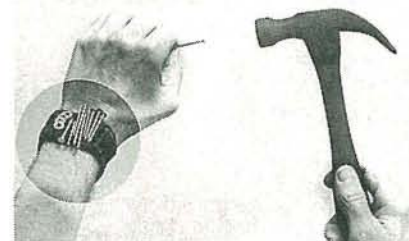MAGNETIC WRIST BAND. If you've ever had to watch a tiny screw roll out of reach under your



CIRCLE 16 ON FREE INFORMATION CARD

workbench while assembling a project, you'll appreciate the *Handy-Dandy Wrist Magnet* from *Yale Audio*. Presenting a simple, convenient solution to such dilemmas, the product resembles a wristwatch—but where you'd expect the face to be, there's a thin, square, flat-surfaced magnet fitted in a durable polymer mounting. Wearing the wrist magnet allows you to keep nails, screws, or tiny metal parts close at hand, leaving both hands free for working.

The *Handy-Dandy Wrist Magnet* costs \$5.49, plus \$1.25 shipping (in U.S.).—**Yale Audio of Florida Corp.**, 2702 Azelee St., Tampa, FL 33609; 813-876-6789.

NEW

LITERATURE

TOOL & TEST CATALOG. Contact East's sourcebook of instrument products for testing, repairing, and assembling electronics equipment features new products in such categories as analog/digital oscilloscopes, static-protection devices, soldering supplies and solder stations, test equipment, precision hand tools, and tool kits.

contact east



CIRCLE 17 ON FREE INFORMATION CARD

Other expanded lines include voice/data-communications test instruments, wire and cable aids, electronic adhesives, and inspection equipment. All products are described in detail, guaranteed, and mailed via the company's "Same-Day Shipment" policy. The 1989 General Catalog, which includes one year of technical supplements, is free upon request.—**Contact East**, 335 Willow Street South, P.O. Box 786, No. Andover, MA 01845.

TEST/MEASUREMENT CATALOG. The third edition of Grainger's catalog contains more than 2,000 products from 45 leading manufacturers, including B&K Precision, Simpson, Pomona, Fluke, Beckman, Hitachi, and A.W. Sperry. Nine product categories—General Testing, Precision Measuring, Electronics, Electrical, Temperature/Humidity Measuring, HVAC/Refrigeration, Environmental, Auto Diagnostics, and Ac-




CIRCLE 18 ON FREE INFORMATION CARD

cessories/Reference—are included in the 156-page manual. The catalog is free upon request.—**W.W. Grainger, Inc.**, 1250 Busch Parkway, Buffalo Grove, IL 60089.

CONFIGURATION PLANNER. The Heath/Zenith planner is a fully-illustrated flow chart that proceeds, step by step, through logical choices in planning individualized data-acquisition and process-control systems.

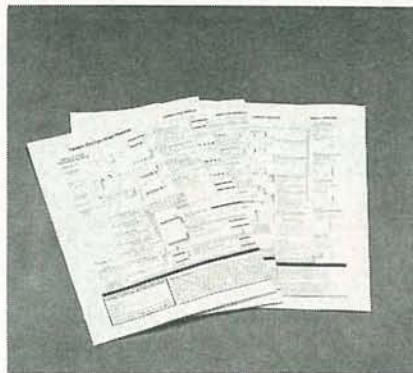The planner, designed for manufacturing and processing personnel, is a "guided tour" of digital or analog input, output, and I/O systems. It highlights the main fea-



CIRCLE 19 ON FREE INFORMATION CARD

tures of Heath/Zenith's modular-instrument products, helping designers to quickly identify the correct components to convert a manual data-gathering or system-control operation into an interactive management-information system, or to make adjustments in an existing system when operations change. The *System Configuration Planner* is free upon request.—**Heath/Zenith Computer Based Instruments**, P.O. Box 21, St. Joseph, MI 49085. **R-E**

If You Fix VCR's, Ask Yourself These Questions

Q Are Most VCR Problems Mechanical?

A Yes, most agree more than 3 out of 4 VCR problems are due to a mechanical malfunction.

Q Are There Universal Test Tools Available Or Do You Have To Buy All The Different Tools Shown In Service Manuals?

A TENTEI provides easier to use, universal, more powerful gauges than all factory tools combined.

Q What Mechanical Measurements Should Be Made To Properly Check Out A VCR?

A Hold back tape tension, tension servo check, reel table heights, carriage alignment, tape guide height, take up torque, restoring torque, brake torque, FF/REW torques & video head wear.

NEW - Just released 68 minute Video Training Tape covering over 28 mechanical VCR tests and measurements **\$24⁹⁵** INTRODUCTORY PRICE Shipping Included

TENTEI® Corporation
1506 Dell Avenue Campbell, CA 95008
(800) 538-6894 / (408)379-1881
(In California)

CIRCLE 184 ON FREE INFORMATION CARD

LEARN VCR CLEANING/MAINTENANCE/REPAIR

EARN UP TO \$1000 A WEEK, WORKING PART TIME FROM YOUR OWN HOME!



THE MONEY MAKING OPPORTUNITY OF THE 1990'S

IF you are able to work with common small hand tools, and are familiar with basic electronics (i.e. able to use voltmeter, understand DC electronics) . . . IF you possess average mechanical ability, and have a VCR on which to practice and learn . . . then we can teach **YOU** VCR maintenance and repair!

FACT: up to 90% of ALL VCR malfunctions are due to simple MECHANICAL or ELECTRO-MECHANICAL breakdowns!

FACT: over 77 million VCRs in use today nationwide! Average VCR needs service or repair every 12 to 18 months!

Viejo's **400 PAGE TRAINING MANUAL** (over 500 photos and illustrations) and **AWARD-WINNING VIDEO TRAINING TAPE** reveals the **SECRETS** of VCR maintenance and repair—"real world" information that is **NOT** available elsewhere!

Also includes all the info you'll need regarding the **BUSINESS-SIDE** of running a successful service operation!

FREE INFORMATION
CALL TOLL-FREE 1-800-537-0589
Or write to: Viejo Publications
3540 Wilshire BL. STE 310
Los Angeles, CA 90010 Dept RE

CIRCLE 181 ON FREE INFORMATION CARD

JULY 1989

DRAWING BOARD



ROBERT GROSSBLATT,
CIRCUITS EDITOR

A complete circuit

OVER THE LAST COUPLE OF MONTHS we've gone through the steps needed to design custom-character generators and looked at some simple ways to use them.

Now let's turn all the pieces into a useful circuit.

The handiest thing to come up with is a way to use one character generator to drive several digits.

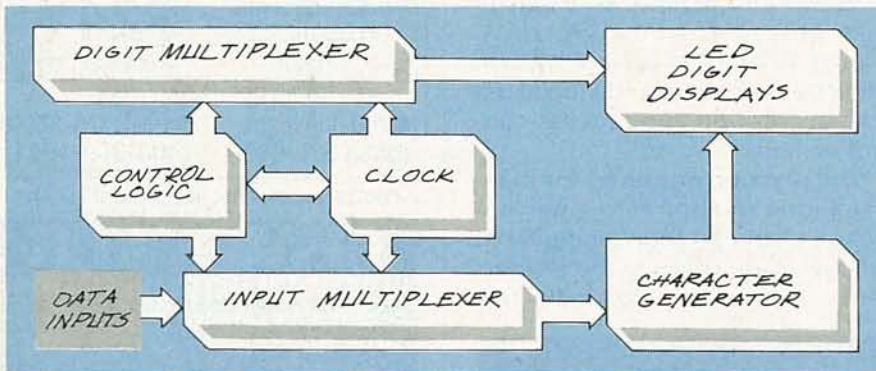


FIG. 1

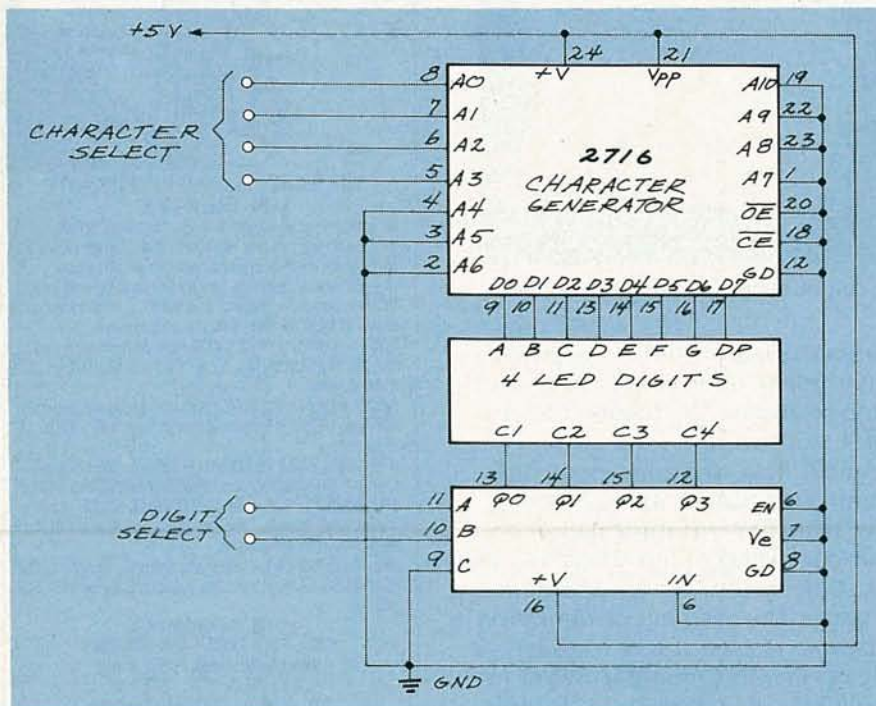


FIG. 2

257#1 OE SEL	257#2 OE SEL	DISPLAYED DIGIT		
L	L	H	X	INPUT 1
L	H	H	X	INPUT 2
H	X	L	L	INPUT 3
H	X	L	H	INPUT 4

FIG. 3

OE	SEL#1	SEL#2	DISPLAY
L	L	X	INPUT 1
L	H	X	INPUT 2
H	X	L	INPUT 3
H	X	H	INPUT 4

FIG. 4

The basic idea here is to build a general-purpose display circuit.

Let's lay down some criteria:

1. The circuit will drive four digits.
2. Each digit will have its own set of inputs.
3. Only one character generator will be used.
4. The circuit will display all the hex digits from 0000h to FFFFh.

Even though we've been designing a character generator that can handle a lot of the ASCII characters, limiting our display to hex will keep the circuit simpler. If you absolutely must display ASCII characters, the circuit will be basically the same, but you'll need more bits assigned to each of the digits. A hex display only cares about the lower four bits while a full ASCII display has to deal with seven bits.

When you come right down to

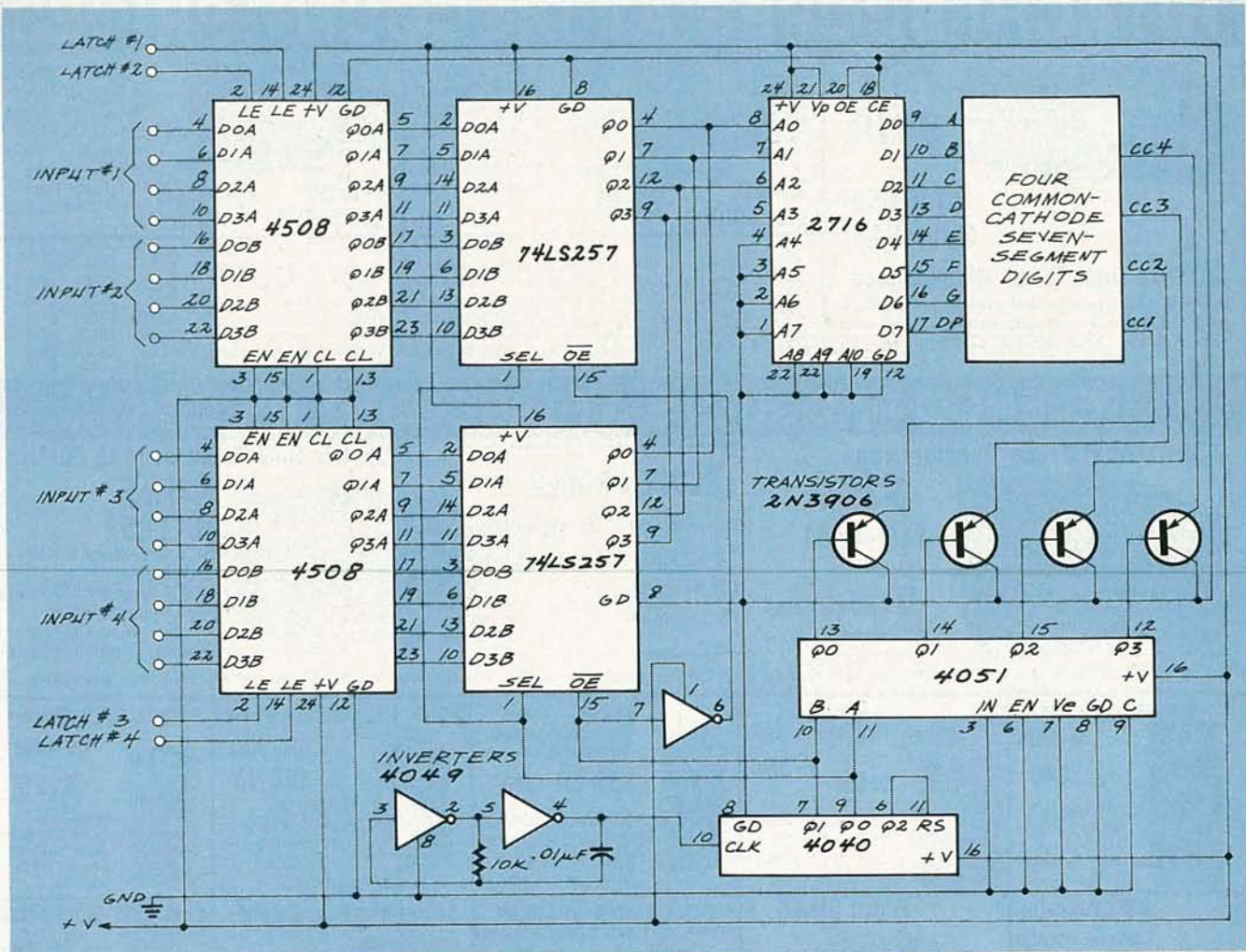


FIG. 5

it, we want the display circuit to be your basic black box with sixteen inputs—four for each of the four digits we'll be driving. Since we're actually building something that can be used elsewhere, we can eliminate some of the parameters we put into the EPROM. We're already disregarding the ASCII stuff and now we'll make the decision to use common-cathode displays.

That last decision is no big deal because it's a relatively trivial thing to convert the circuit to work with a common-anode digit...but we're getting ahead of ourselves.

The block diagram of the circuit we'll be designing is shown in Fig. 1. The heart of the circuit is really the control logic because it has the job of keeping everything in sync. We have to be sure that when we're sending character number 1 to the input multiplexer, that we're also turning on seven-segment LED number 1. If things get out of sync you might have something up on the display but it's not going to

be anything useful.

The starting point of the circuit is shown in Fig. 2. It's similar to the circuit that we looked at in May, but there are two main differences. The first is that we're only using A0-A3 on the EPROM and the second is that the 4051 is going to drive only four digits so the "C" input (pin 9) is tied low. The same thing is done with all of the unused EPROM address lines.

We've already decided on the 4051 as the digit multiplexer so let's take a look at the input multiplexer as well before getting to the control logic. After all, you can't design control logic until you know what you have to control.

Just as the 4051 will sequentially turn on one digit after another, the input multiplexer has to select the corresponding digit data to be displayed. What we need is the electronic equivalent of a four-pole, four-position rotary switch, and one way to do that is to use a pair of 74LS257's. You can use the TTL

version of the chip or the 74HC257 or 74HCT257 pin-equivalent CMOS parts.

The inputs that will appear at the outputs depend on the state of the SEL input. Making that pin low will select the first set of inputs and making it high will select the others. What makes the 257 a good IC for our application is that it also has an OUTPUT-ENABLE pin so that our output can have three states.

Now that we know what multiplexers we'll be using, we can work out what we need for control logic. Designing this kind of circuitry can be a really brain-bending exercise but one way to cut it down to size is to use a truth table like the one shown in Fig. 3.

It may seem a bit confusing at first glance, but one thing it tells us right away is that the OUTPUT-ENABLE pins of the 257's are always opposite each other. When one is high, the other is low, and vice versa. That means we can tie them

continued on page 85

HITACHI SCOPES AT DISCOUNT PRICES



V-212
\$419

List \$560
Save \$141

20MHz Dual Trace Oscilloscope

All Hitachi scopes include probes, schematics and Hitachi's 3 year warranty on parts and labor. Many accessories available for all scopes.



V-425
List \$995 **\$835**

- DC to 40MHz
- Dual Channel
- CRT Readout
- Cursor Meas
- DC Offset
- Alt Magnifier
- Compact Size



V-1060
List \$1595 **\$1,325**

- DC to 100MHz
- Dual Channel
- Delayed Sweep
- CRT Readout
- Sweep Time
- Autoranging
- Trigger Lock
- 2mV Sensitivity

	LIST	PRICE	SAVE
V-223 20MHz	\$770	\$695	\$75
V-422 40MHz	\$875	\$725	\$150
V-423 40MHz	\$955	\$825	\$130
V-660 60MHz	\$1,195	\$1,025	\$170
V-1065 100MHz	\$1,895	\$1,670	\$225
V-1100A 100MHz	\$2,295	\$2,045	\$250
V-1150 150MHz	\$3,100	\$2,565	\$535

ELENCO PRODUCTS AT DISCOUNT PRICES

20MHz Dual Trace Oscilloscope



\$359
MO-1251

- 6" CRT
- Built in component tester
- TV Sync
- X-Y Operation

SCOPE PROBES

P-1 65MHz, 1x, 10x **\$19.95**
P-2 100MHz, 1x, 10x **\$23.95**
Fits all scopes with
BNC connector

35MHz Dual Trace Good to 50MHz



\$495
MO-1252

- High luminance 6" CRT
- 1mV Sensitivity
- 6KV Acceleration Voltage
- 10ns Rise Time
- X-Y Operation • Z Axis
- Delayed Triggering Sweep

Top quality scopes at a very reasonable price. Contains all desired features. Two 1x, 10x probes, diagrams and manual. Two year guarantee.

Autoranging DMM



M-5000
\$45

9 Functions
Memory and
Data hold
1/2 basic acc
3 1/2 digit LCD



True RMS 4 1/2
Digit Multimeter
\$135 **M-7000**


.05% DC Accuracy
.1% Resistance
with Freq. Counter
and deluxe case



Multimeter with
Capacitance and
Transistor Tester
\$55 **CM-1500**

Reads Volts, Ohms,
Current, Capacitors,
Transistors and
Diodes with case

Digital Capacitance Meter

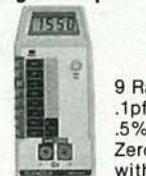

CM-1550
\$58.95

9 Ranges
.1pf-20,000ufd
.5% basic acc
Zero control
with case

Digital LCR Meter



LC-1801
\$125

Measures
Coils 1uH-200H
Caps .1pf-200uf
Res .01-20M

AC Clamp-On Current Adapter



ST-265
\$22

0-1000A AC
Works with
most DMM

Bench DMMS



M-3500 **\$125** **M-4500** **\$175**
3 1/2 digit .1% accy
4 1/2 digit .05% accy

SOLDERING STATION TEMPERATURE CONTROLLED



SL-30
\$135

Digital display
Temp range:
300F-900F
Grounded tip
Overheat prot

Solderless Breadboards



9430
1,100 pins **\$15**
9434
2,170 pins **\$25**
9436
2,860 pins **\$35**
All have color
coded posts

9436 SHOWN

Low Cost Multimeter



M-1600
\$25

3 1/2 digit LCD
1% DC Accy
10A Scale
Auto zero
/polarity


Wide Band Signal Generators



SG-9000 **\$129**
RF Freq 100K-450MHz
AM Modulation of 1KHz
Variable RF output

**SG-9500 with Digital Display
and 150MHz built-in Freq Ctr \$249**


3 1/2 Digit Probe Type DMM

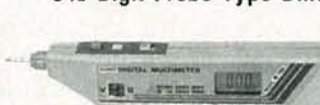

M-1900
\$39

Convenient one hand operation
Measures DCV, ACV, Ohms
Audible continuity check, Data hold
with batteries
and case

Function Generator Blox

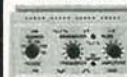

#9600
\$28.95

Provides sine, tri, squ wave
From 1Hz to 1MHz
AM or FM capability

Decade Blox



9610 or
9620
\$18.95

#9610 Resistor Blox
47 ohm to 1M & 100K pot
#9620 Capacitor Blox
47pf to 10MFD

Digital Triple Power Supply



XP-765
\$249

0-20V at 1A
0-20V at 1A
5V at 5A

Fully Regulated, Short circuit protected with
2 Limit Cont., 3 Separate supplies
XP-660 with Analog Meters \$175

Quad Power Supply



XP-580
\$59.95

2-20V at 2A
12V at 1A
5V at 3A
-5V at 5A

Fully regulated and
short circuit protected
XP-575 without meters \$39.95

10MHz XT 100% IBM® Compatible

**5 Year
Warranty**



\$595
**MODEL
PC-1000**

- 5/10MHz Motherboard
- 8 Expansion Slots
- Math Compressor Slots
- 360K Floppy Drive
- AT Style Keyboard
- 150W Power Supply
- 256K RAM
- Expandable to 640K
- Monochrome Monitor
- Monographic Video Card
- Parallel Printer Port

FREE spreadsheet and word processor
3.XXMS DOS and GW Basic add \$75


Four-Function Frequency Counters



F-1000 1.2GH
\$259
F-100 120MH
\$179

Frequency, Period, Totalize,
Self Check with High Stabilized Crystal Oven
Oscillator, 8 digit LED display

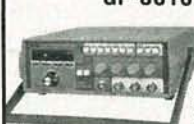GF-8016 Function Generator with Freq. Counter



\$239

Sine, Square, Triangle
Pulse, Ramp, .2 to 2MHz
Freq Counter .1 - 10MHz

GF-8015 without Freq. Meter \$179

WE WILL NOT BE UNDERSOLD!

UPS Shipping: US 5%
(\$10 Max) IL Res., 7% Tax



C & S SALES INC.
1245 Rosewood, Deerfield, IL 60015
(800) 292-7711 (312) 541-0710

15 Day Money Back Guarantee
2 Year Warranty

WRITE FOR FREE CATALOG

LIGHT BEAM COMMUNICATOR

Now, using our top-secret device, you and a partner can communicate across a void at the speed of light—on a beam of light!

ROGER SONNTAG

IF YOU'RE LOOKING FOR A purely *fun* project, then this light beam communciator is for you. It not only contains the usual electronics, it also has an ingenious mechanical assembly whose operation is interesting in its own right. You're sure to find it a refreshing change from the usual board-in-a-box project. But don't think that this light-beam communciator is just for fun. The powerful transmitter and extremely sensitive receiver take this project out of the realm of toys—you can do some pretty serious work with our device!

A complete *Light-Beam Communicator* (LBC) consists of a transmitter and a receiver, installed inside 2 tube-like assemblies, along with various optical components. Two complete LBC's are required for two-way communication, but you will need only one transmitter and one receiver for one-way communication. Full-duplex operation is provided, meaning that you can talk and

listen at the same time—there is no transmit/receive switch.

Figure 1 shows the block diagram of the transmitter. The transmitter houses a high-intensity LED, powered from a constant-current source, as well as the circuitry necessary to modulate an audio signal from a microphone onto the LED's light output. Using the optics, the modulated light from the LED is focused into an intense, narrow beam.

That narrow light beam travels a surprisingly long distance. The standard unit has about a ¼-mile range. The high-power unit has an amazing range of better than ½-mile! (When testing the range of the units, we used small "toy" 100-mW walkie talkies to assist with setup and aiming—the walkie talkies "ran out of gas" long before the LBC did!) At the end of its travel, the beam is received by another identical LBC that turns the modulated

light beam back into the original audio signal. The receiver's block diagram is shown in Fig. 2. Let's examine the individual sections more closely.

The difference between the standard LBC and the high-power LBC is the LED that is used. The standard unit has a high-intensity 3-candela-power (3,000 milli-candela or mcd) LED manufactured by Hewlett Packard (a *candela*, formerly candle, is a measure of luminous intensity). The high-power unit has a very-high-intensity 12-candela (12,000 mcd) LED, also manufactured by Hewlett Packard. Both of those LED's are much brighter than a normal LED, and they have a focusing rather than a diffusing lens. However, *any* LED will work but the useful range of the LBC will be greatly reduced if a high intensity LED is not used.



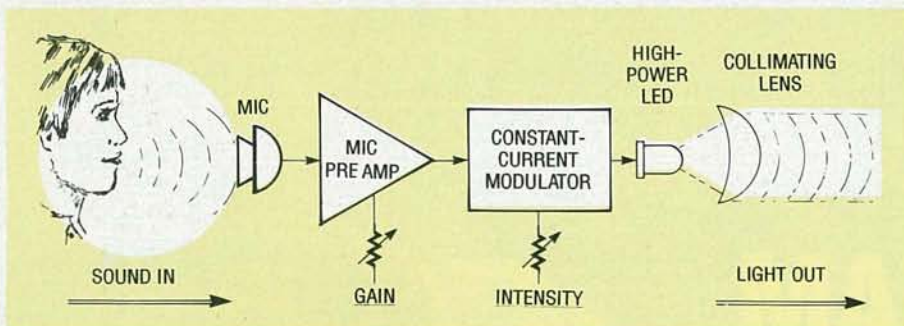


FIG. 1—BLOCK DIAGRAM OF THE TRANSMITTER. This circuit contains a high-intensity LED, powered from a constant-current source, and the circuitry necessary to modulate an audio signal onto the LED's light output.

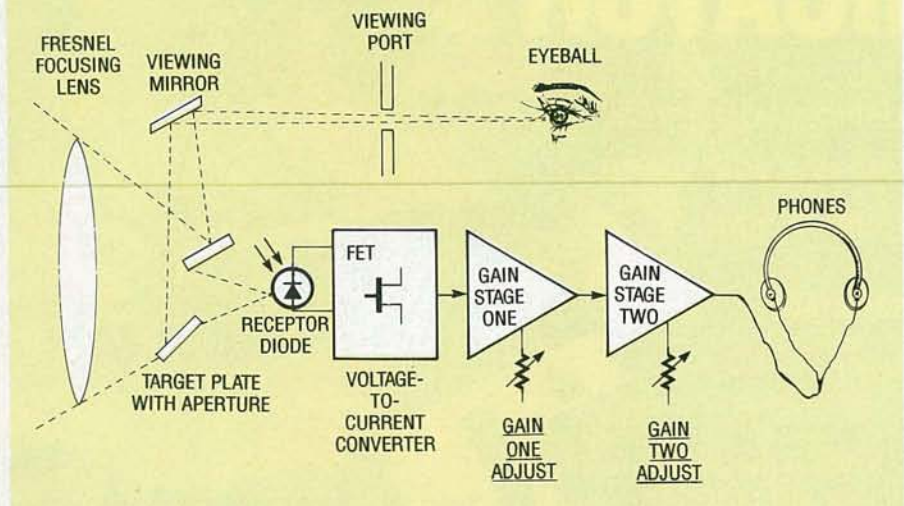


FIG. 2—RECEIVER BLOCK DIAGRAM. This circuit turns the modulated light beam back into the original audio signal.

The transmitter

There are two stages in the transmitter: a microphone preamplifier and a constant-current modulator (see Fig. 3). Each stage uses half of a 5532, which is an internally compensated, dual low-noise op-amp. After the microphone output is pre-amplified by IC1-a, the output signal from pin 1 is fed through C6 to pin 5 of IC1 where it is further amplified.

An adjustable constant-current source is fed to Q1, an NPN transistor capable of handling at least 3 amps. The audio signal at pin 7 of IC1 drives the base of Q1, modulating the signal onto the LED's light output. (An infrared LED can be used for this project, and will, in fact, increase the range. Unfortunately IR light is invisible, so it is not easy to work with. However, among the interesting things you can "hear" with the LBC are IR remote controls and IR burglar-alarm sensors.) Basically, the AC signal either adds or subtracts from the average DC level. Transistor Q1 and LED1 are in the feedback loop of the op-amp, and the DC current flowing

through the LED remains constant due to the setting of R9. The DC current can be adjusted via R9 through a range from 1 to 50 mA.

The transmitter assembly, shown in Fig. 4, is fitted inside one end of a

rugged cardboard tube that has a collimating lens at the other end. That lens focuses the light beam into a very narrow, intense beam, giving the light from an LED such an unusually long range.

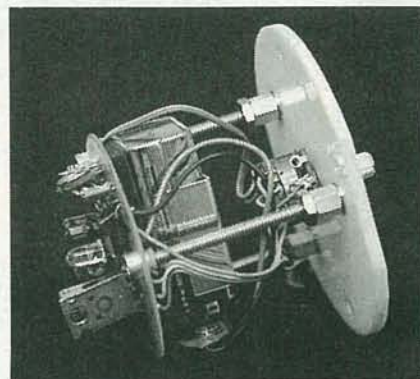


FIG. 4—THE TRANSMITTER ASSEMBLY. It is fitted inside one end of a rugged cardboard tube that has a collimating lens at the other end.

The receiver

The schematic for the receiver section of the LBC is shown in Fig. 5, and the receiver assembly is shown in Fig. 6. The receiver assembly is mounted inside one end of a large tube, which has a fresnel lens at the other end. The fresnel lens concentrates the light beam, and directs it to the photodiode, D1. The photodiode provided in the kit is actually a Kodak part, and not available to the general public. That part is well suited for this application, and it is more sensitive to infrared light than most photodiodes; but if you don't buy the kit, any silicon photodiode or phototransistor

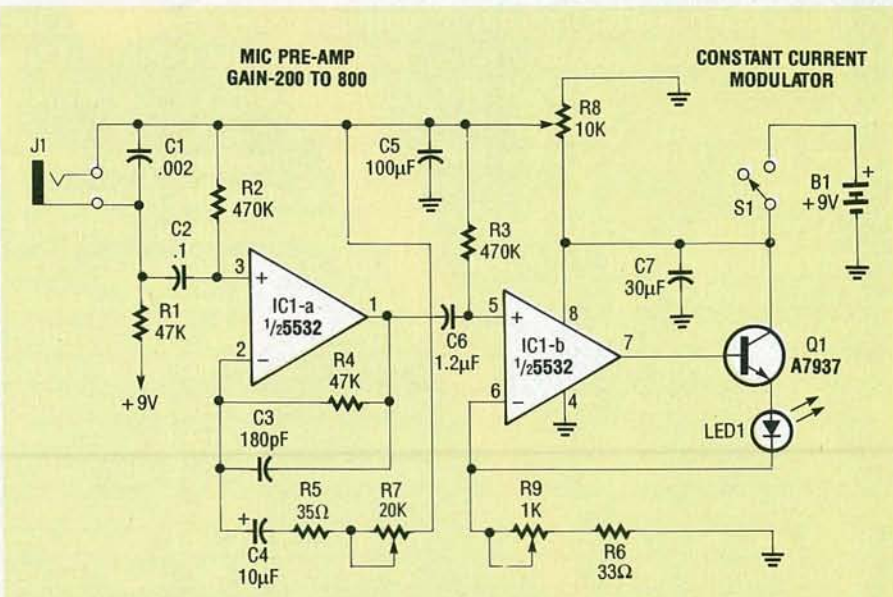


FIG. 3—THE TRANSMITTER CONTAINS TWO STAGES: a microphone preamplifier and a constant-current modulator. Each stage uses half of a 5532 op-amp.

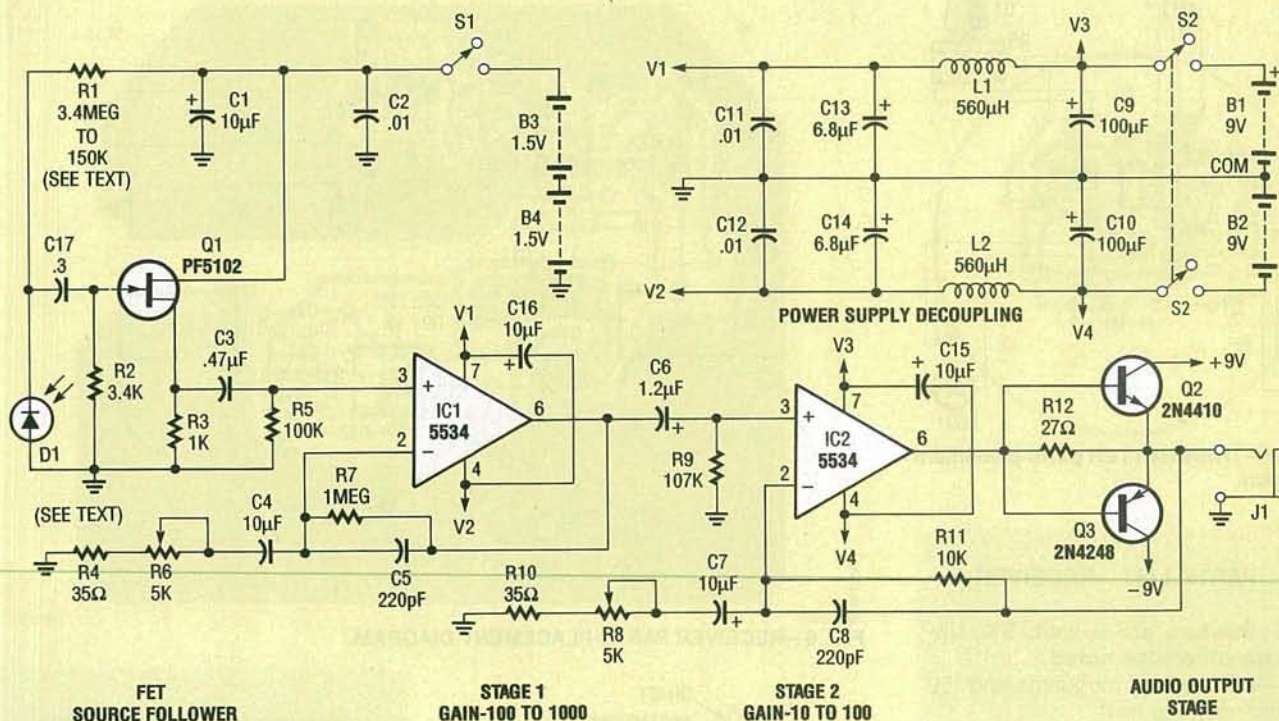


FIG. 5—THE RECEIVER SCHEMATIC.

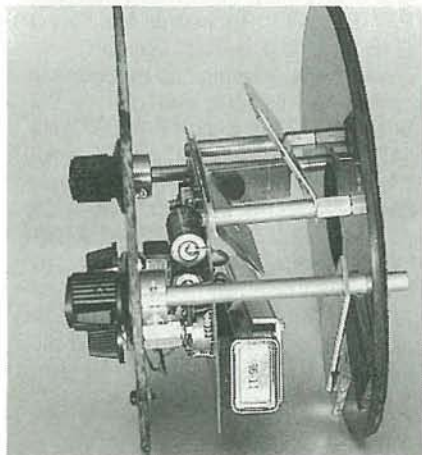


FIG. 6—THE RECEIVER ASSEMBLY. It is mounted inside one end of a large tube, which has a fresnel lens at the other end.

should do. The small signal that is generated by D1 is fed to pin 3 of IC1 via FET Q1.

Op-amp IC1 is the first gain stage in the receiver, and it amplifies the signal from Q1 100 to 1000 times, depending on the setting of gain-control potentiometer R6. The signal from pin 6 of IC1 is then fed through C6 to pin 3 of IC2, which is the second gain stage; the gain of the second stage is variable from approximately 10 to 100 via gain-control potentiometer R8. Two gain-control potentiometers are used to help improve stability, because stray oscillation is hard to avoid

in a circuit with so much gain.

The signal at pin 6 of IC2 is then fed to R12, which is connected across the base-emitter junction of both Q2 and Q3. The voltage across R12 turns Q2 and Q3 on and off; those transistors are capable of driving a pair of low-impedance headphones.

Note that R1 is listed as being 3.4 megohms or 150 kilohms. That's because, if you use a value near 3.4 megohms, the receiver will be extremely sensitive, resulting in the greatest possible range. On the other hand, a value near 150K will decrease the sensitivity while providing a wide bandwidth, giving the unit higher fidelity. You can use any value between 3.4 megohms and 150 kilohms, but do not use a potentiometer, as it will be a source of noise in the circuit.

Construction

Let's start by building the transmitter board. Foil patterns for both boards are provided in PC Service. Figure 7 is the Parts-Placement diagram for the transmitter. First install the resistors, then the capacitors (bend the leads, solder, and then trim), and then the potentiometers. Cut some ribbon cable into 6 2-conductor pieces (3 for now and 3 for later), 1½-inches long, and then separate and strip the ends. (Any thin,

PARTS LIST—TRANSMITTER

All resistors are ¼-watt, 5%, unless otherwise noted.

- R1, R4—47,000 ohms
- R2, R3—470,000 ohms
- R5—35 ohms
- R6—33 ohms
- R7—20,000 ohms, PC-mount potentiometer
- R8—10,000 ohms, PC-mount potentiometer
- R9—1000 ohms, combination potentiometer/switch (incorporates S1)

Capacitors

- C1—0.002 μF, 50 volts, ceramic
- C2—0.1 μF, 50 volts, ceramic
- C3—180 pF, 100 volts, ceramic
- C4—10 μF, 10 volts, electrolytic
- C5—100 μF, 10–25 volts, electrolytic
- C6—1.2 μF, 20 volts, electrolytic
- C7—30 μF, 20 volts, electrolytic

Semiconductors

- IC1—NE5532 dual low-noise op-amp
- Q1—7937 3-amp NPN transistor
- LED1—high-intensity light-emitting diode, can be Hewlett Packard HLMP-8103 (3000 mcd) or HLMP-8150 (12,000 mcd), or any other high-intensity LED.

Other components

- B1—9-volt battery
- S1—SPST switch (part of R9)
- J1—mono phone jack
- Miscellaneous: 9-volt-battery clip, 8-pin DIP socket, wire, solder, etc.

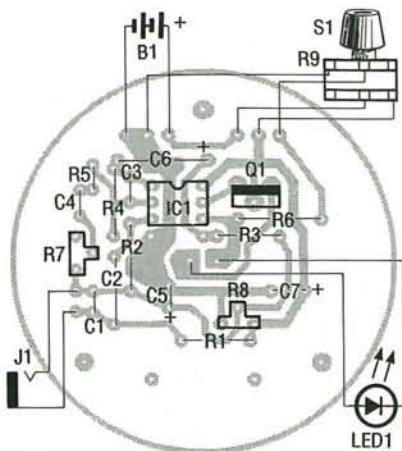


FIG. 7—TRANSMITTER parts-placement diagram.

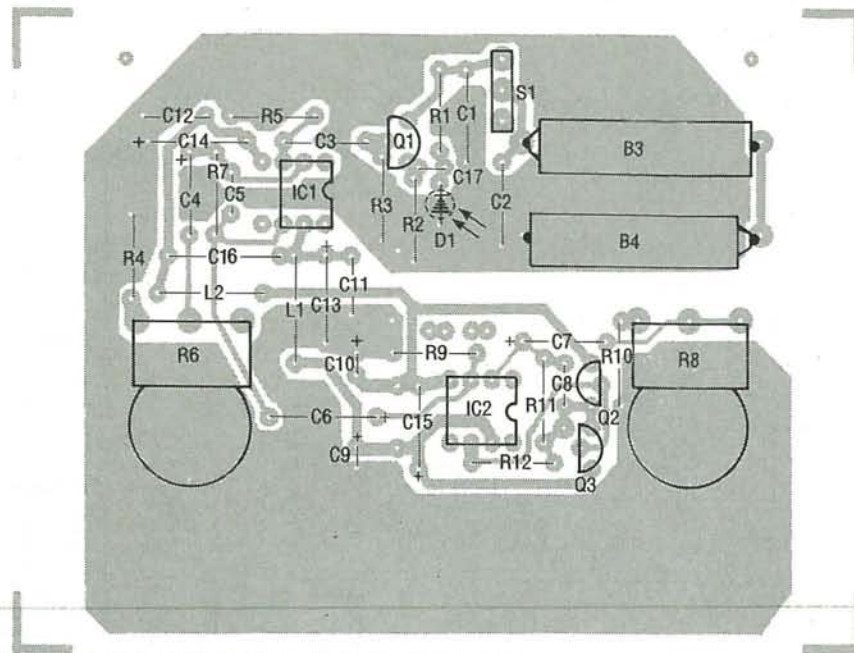


FIG. 8—RECEIVER PARTS-PLACEMENT DIAGRAM.

PARTS LIST—RECEIVER

All resistors are 1/4-watt, 5%, unless otherwise noted.

- R1—between 3.4 megohms and 150 kilohms (see text)
- R2—3.4 ohms
- R3—1000 ohms
- R4—35 ohms
- R5—100,000 ohms
- R6, R8—5000 ohms, potentiometer
- R7—1 megohm
- R9—107,000 ohms
- R10—35 ohms
- R11—10,000 ohms
- R12—27 ohms

Capacitors

- C1—10 μ F, 50 volts electrolytic
- C2, C11, C12—0.01 μ F, 10 volts, ceramic
- C3—0.47 μ F, 20 volts, ceramic
- C4, C7—10 μ F, 10 volts, electrolytic
- C5, C8—220 pF, 100 volts, ceramic
- C6—1.2 μ F, 20 volts, electrolytic
- C9, C10—100 μ F, 15 volts, electrolytic
- C13, C14—6.8 μ F, 20 volts, electrolytic
- C15, C16—10 μ F, 25 volts, electrolytic
- C17—0.3 μ F, 50 volts, ceramic

Semiconductors

- IC1, IC2—NE5534 single low-noise op-amp
- D1—Siemens BPW-33 silicon photodiode (see text)
- Q1—PF5102 field-effect transistor
- Q2—2N4410 NPN transistor
- Q3—2N4248 PNP transistor

Other components

- L1, L2—560 μ H
- S1—SPST switch
- S2—DPDT switch
- B1, B2—9-volt battery
- B3, B4—1.5-volt N-size battery
- Miscellaneous: 2 9-volt-battery clips, DIP sockets, wire, solder, etc.

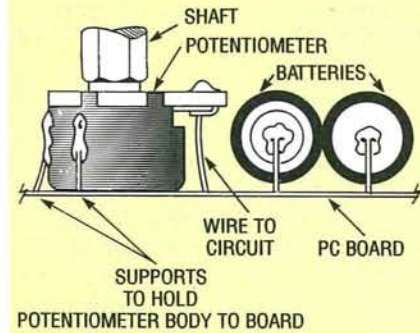


FIG. 9—YOU MUST USE PIECES of bus wire to attach potentiometers R4 and R6 securely to the PC board.

stranded wire will do if you don't have ribbon cable.) Then use one piece to connect the microphone jack, J1, to the pads indicated in Fig. 7, and two more to connect R8/S1.

Connect a 9-volt battery clip to the appropriate pads on the board, and then install IC1. (It's a good idea to use a socket for IC1.) Last, position LED1 (observe its polarity) so that it is standing perfectly straight off the PC board, then solder it in place.

For the assembly of the receiver board, see Fig. 8. First install resistors R1–R12, and then install the capacitors observing polarity where indicated. Then install L1 and L2, and sockets for IC1 and IC2. Using pieces of bus wire, attach potentiometers R4 and R6 securely to the PC board as shown in Fig. 9. Prepare B3 and B4 by soldering a short length of bus wire to each terminal (see Fig. 9) so that each battery can be PC mounted. PC-mount S2 and solder it in place. Now

ORDERING INFORMATION


The following are available from General Science and Engineering, P.O. Box 447, Rochester, NY 14603 (716-338-7001): Kit of all parts, including all electronic and mechanical components, \$98; Set of two PC boards, \$12.00; 6-inch Fresnel lens, \$15.00; A headset with built-in microphone, \$12.00; Telephone-type handset, \$5.00; Siemens BPW-33 photodiode, \$3.50; HLMP-8150 12-cd LED price to be determined (call GSE for information); Assembled and tested communicator, \$198. Note: the spotting scope is not available from GSE.

turn the board over, and solder D1 (the photodiode) in place observing its polarity indicated by a painted dot on its anode.

Take two 9-volt-battery clips and, on one of them, clip the red lead down to 1 inch and the black one to 2 1/2 inches; on the other battery clip, cut the black lead down to 1 inch and the red to 2 1/2 inches. Solder the leads to the PC board as shown. Using three more pairs of leads (as was shown in Fig. 8), connect J1, the headset jack, and S2.

Well, the boards are finished, but that's all we have room for this month. Next month we'll finish the project by detailing the mechanical assemblies. We'll also present a list of the necessary mechanical components. R-E

EXPAND YOUR CAREER HORIZONS...

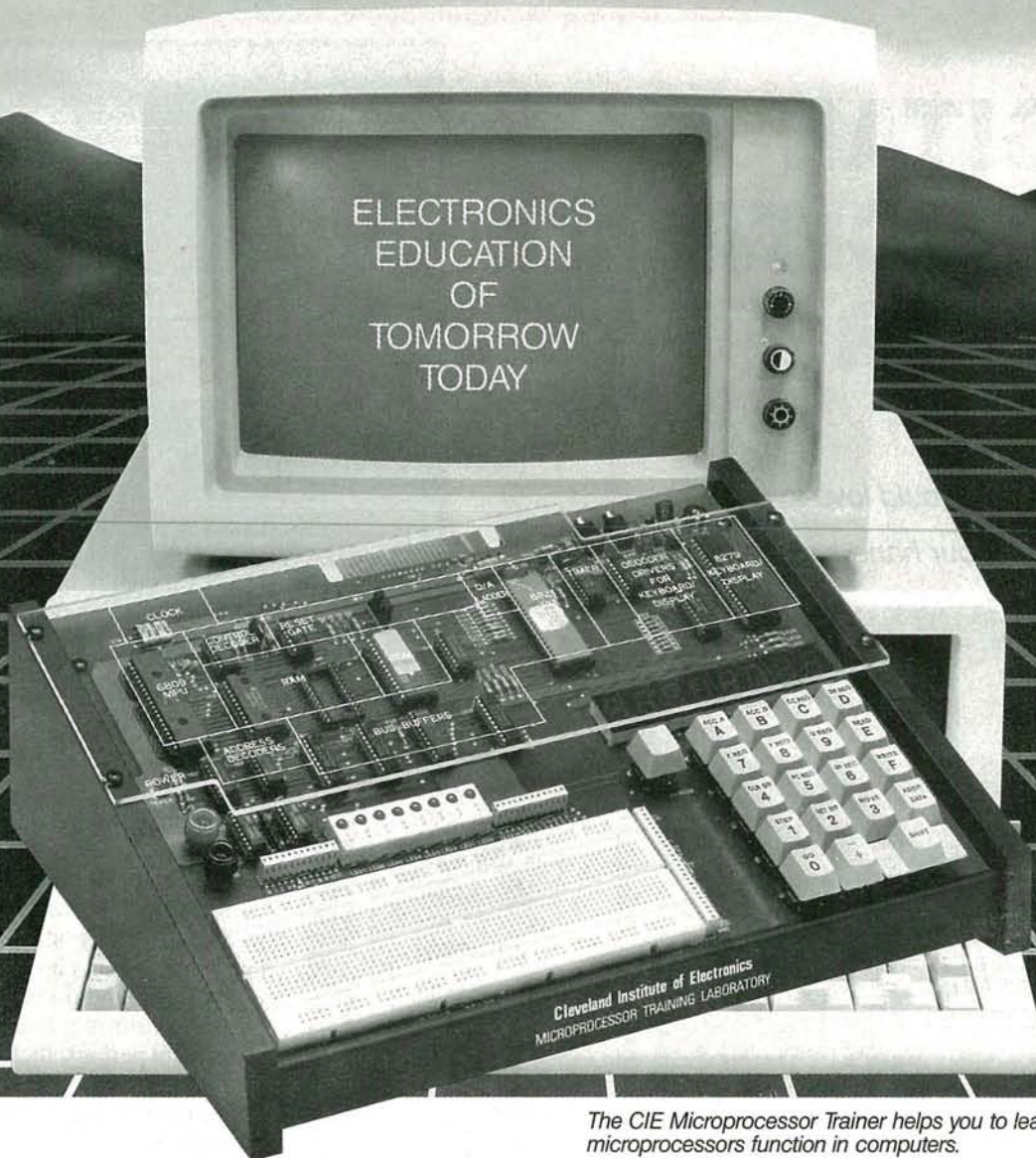

The CIE Microprocessor Trainer helps you to learn how circuits with microprocessors function in computers.

START WITH CIE.

Microprocessor Technology. Satellite Communications. Robotics. Wherever you want to go in electronics... start first with CIE.

Why CIE? Because we're the leader in teaching electronics through independent study. Consider this. We teach over 25,000 students from all over the United States and in over 70 foreign countries. And we've been doing it for over 50 years, helping thousands of men and women get started in electronics careers.

We offer flexible training to meet your needs. You can start at the beginner level or, if you already know something about electronics, you may want to start at a higher level. But wherever you start, you can go as far as you like. You can even earn your Associate in Applied Science Degree in Electronics.

Let us get you started today. Just call toll-free 1-800-321-2155 (in Ohio, 1-800-362-2105) or mail in

CIRCLE 60 ON FREE INFORMATION CARD

the handy reply coupon or card below to:
Cleveland Institute of Electronics,
1776 East 17th Street, Cleveland, Ohio 44114.

CIE World Headquarters

ARE-132

Cleveland Institute of Electronics, Inc.
1776 East 17th Street • Cleveland, Ohio 44114

Please send your independent study catalog.
For your convenience, CIE will try to have a representative contact you — there is no obligation.

Print Name _____

Address _____ Apt. _____

City _____ State _____ Zip _____

Age _____ Area Code/Phone No. _____

Check box for G.I. Bill bulletin on Educational Benefits

Veteran Active Duty **MAIL TODAY!**

Just call toll-free 1-800-321-2155 (in Ohio, 1-800-362-2105)

BUILD THIS

DIGITAL CAPACITANCE METER

Any test bench would love to have
our hand-held capacitance meter!

MICHAEL LASHANSKY

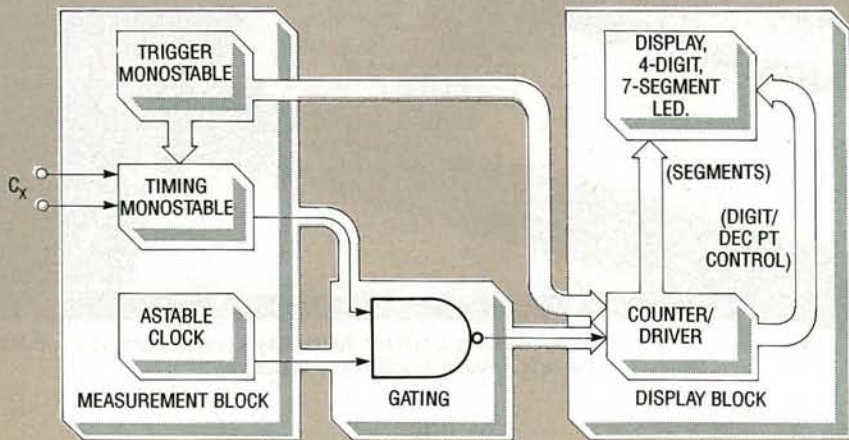
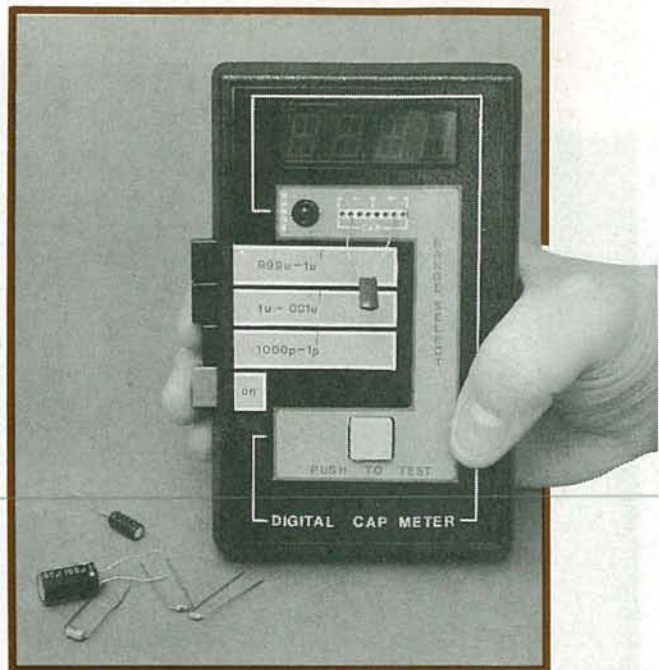


FIG. 1—BLOCK DIAGRAM of the capacitance meter.

HOW MANY TIMES HAVE YOU RUMMAGED through your parts box for a capacitor with a particular value, only to find a handful with confusing color codes or numerical markings that look like weird hieroglyphics? If you're lucky, you might find one you can decipher. Otherwise, you'll have to guess its value, and decide if you can stand a mistake. That's not too professional, but we all do it from time to time.

The problem is that most manufacturers have separate marking nomenclature for capacitors, causing total chaos for hobbyists. The military got smart and standardized their nomenclature requirements a long time ago,

but consumer capacitor values are still almost impossible to read. There's been a push toward total standardization of capacitor values, but don't hold your breath.

So what do you do while the industry bickers over nomenclature? If you can't read your capacitors, you can either throw them out, or buy an expensive commercial capacitance meter. But perhaps the best solution is to build our inexpensive hand-held capacitance meter. It's accurate enough for hobbyists, uses readily available components, and can be powered from either a common 9-volt battery or 7.2-volt Ni-Cd.

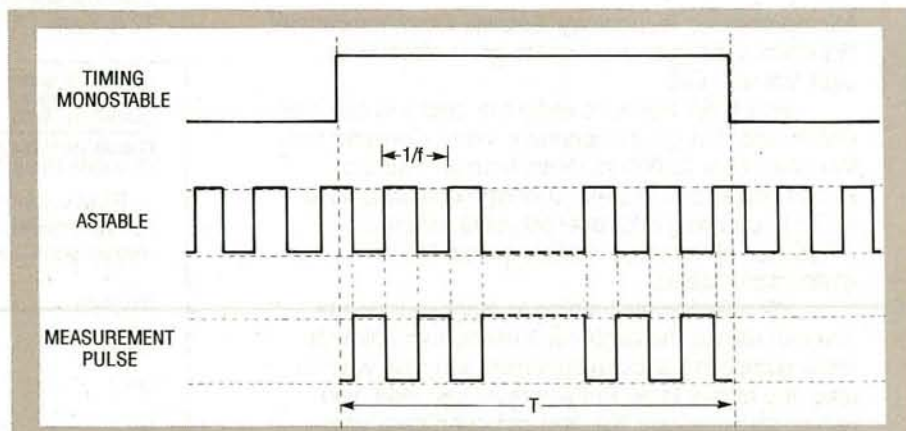


FIG. 2—TIMING WAVEFORMS of the capacitance meter. The number of astable pulses in the measurement pulse is proportional to the value of the unknown capacitor within a factor of 10.

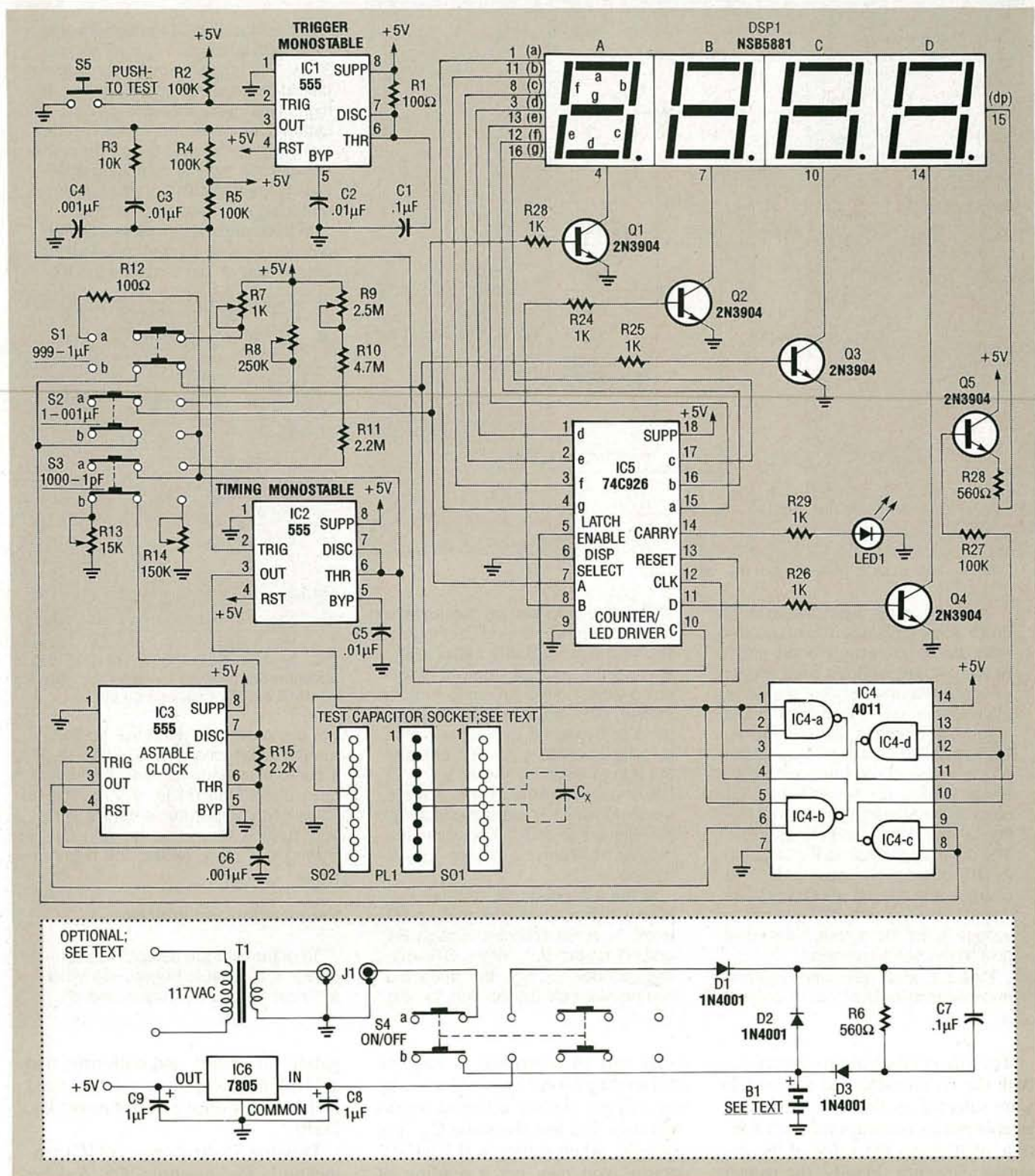


FIG. 3—COMPLETE SCHEMATIC of the capacitance meter.

Circuit theory

To determine the value of an unknown capacitor, C_x , the technique shown in the block diagram of Fig. 1 is used. The unknown capacitor controls the width of the output pulse

from the timing monostable. And since the pulse width is proportional to C_x , its value can be determined by measuring the duration of the pulse.

An independent astable multi-vibrator generates a clock waveform

that is NAND-gated with the timing monostable's pulse to yield a measurement pulse (see Fig. 2). The number of astable pulses fitting within the "window" of the measurement pulse is counted and scaled to C_x .

THE 555

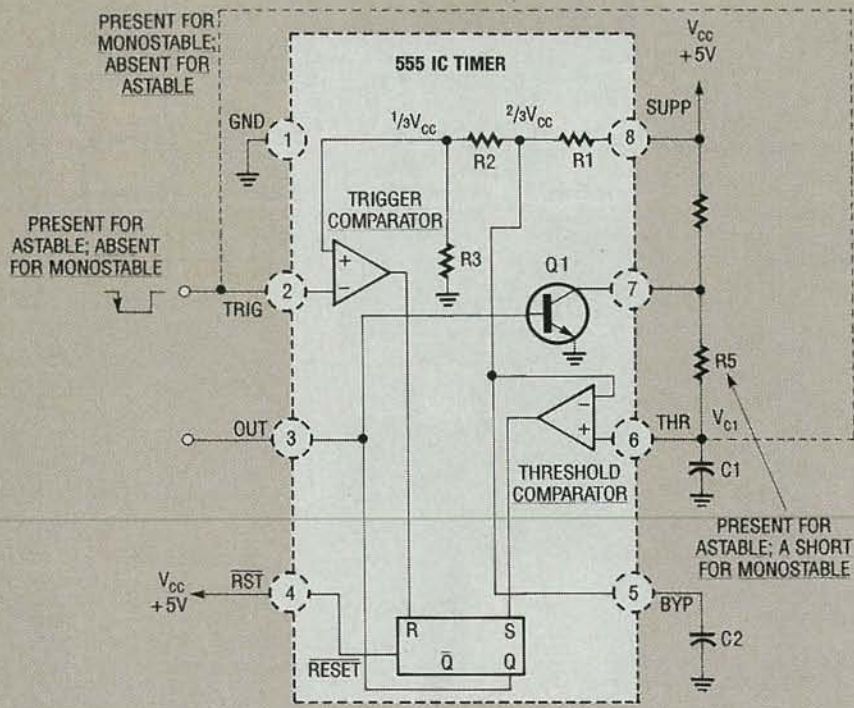


FIG. 1—THE BLOCK DIAGRAM of the 555 timer.

The 555 is the most versatile IC timer ever developed for astable/monostable operating modes, and it needs very few external components to use it. Figure 1 shows the 555's block diagram, with its threshold and trigger comparators, set-reset (S-R) flip-flop, NPN discharging transistor (Q), a noninverting buffer, and an internal voltage divider R1/R2/R3 for comparator reference levels. The flip-flop is "set" if high, and "reset" if low. The comparators sense the variation in C1's voltage in either mode, and charges and discharges C1 between $\frac{1}{3}$ and $\frac{2}{3}$ of V_{CC} , or about 5 volts. C1's voltage is not the output, but it does govern the 555's operation.

Pins 2, 6, and 7 determine astable/monostable operation. Figure 2

shows the 555 set up for astable mode, using R4, R5, and C1. Figure 3 shows the monostable setup, using R4 and C1, and an external down-going trigger pulse on pin 2. In both modes, pin 4 normally goes to V_{CC} ; pin 5 is bypassed by C2 for added stability. In either mode, C1 charges through at least R4 toward V_{CC} , but R5 is present only in the astable mode, for which it varies the duty cycle. Figures 2 and 3 also show the outputs from pin 3 in relation to C1's voltage.

In the astable mode, assume that pin 3 is high, C1 is discharged, and Q is off. Now, C1 charges through R4 and R5 toward V_{CC} . When C1's voltage reaches $\frac{2}{3}$ V_{CC} , the threshold comparator sets the flip-flop, turning

Q on, discharging C1 through R5 until its voltage reaches $\frac{1}{3}$ V_{CC} , driving pin 3 low. The trigger comparator resets the flip-flop, turning Q off, driving pin 3 high. This cycle repeats, yielding a rectangular waveform. If R4 is 0 ohm, charging/discharging is only through R5, giving a symmetric square wave. If R4 is greater than 0 ohm, an asymmetric square wave is generated.

In the monostable mode, an external down-going trigger (needed for each cycle) on pin 2 causes the trig-

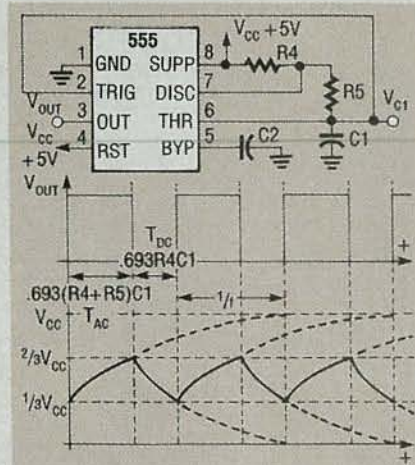


FIG. 2—ASTABLE MODE OF THE 555, showing the relation between the output on pin 3 and C1's voltage on pin 6.

ger comparator to reset the flip-flop, turning Q off, charging C1 from the saturation voltage of Q (effectively ground) through R4 to $\frac{2}{3}$ V_{CC} . The threshold comparator sets the flip-flop, turning Q on, discharging C1, driving pin 3 low, ending the timing pulse.

Frequencies and periods

To determine the astable frequency and monostable period, you have to know how C1 charges and dis-

The value of the timing resistors for both the monostable and the astable were selected so that the number of astable pulses is always an exact multiple of 10 times the value of the unknown capacitor. Finally, the trigger monostable is used to start a measurement, latch the count, and reset the meter.

The time constants for the monostables and astable are exact. However, each time an unknown capacitor is tested, variations in battery voltage, temperature, and comparator trigger

levels will all contribute to vary the final reading for each trial. That's why you will get slightly different results each time you test the same C_x . For example, when testing a 0.1 μ F capacitor, you may get a reading of 0.094 μ F the first time and 0.103 μ F the second.

The schematic

Looking at Fig. 3, 555 timers are used for the monostables (IC1 and IC2) as well as for the astable (IC3). A 4011 quad NAND gate (IC4) provides

gating, inversion, and buffering, and a 74C926 display driver (IC5) is used to drive the 4-digit 7-segment display, DSP1.

Pressing S5 drives pin 3 of IC1 momentarily low, resetting IC5. A delay line (R3-R5 and C3 and C4) increases the rise time of IC1's output pulse, so that the triggering of IC2 is delayed until IC5 is reset. The switch array S1-S3 determines the capacitance range by adjusting the timing parameters of IC2 and IC3. Only one of the three switches in the array can be

charges. Let R_{EFF} be the effective charging/discharging resistance in either mode. In astable mode, R_{EFF} is equal to $R4 + R5$ when charging, and R_{EFF} is equal to $R5$ when discharging. The duty cycle in the astable mode must be the ratio of those, or the duty cycle is equal to $[(R4 + R5)/R5] \times 100\%$, or equal to $[1 + (R4/R5)] \times 100\%$.

In monostable mode, R_{EFF} equals $R4$ when charging; there is no discharge path. If $C1$ is discharged and in series with R_{EFF} with both connected to V_{CC} , $C1$ charges "exponentially" from ground toward V_{CC} . That basically means that $C1$'s voltage never reaches V_{CC} , but gets very close.

The "time constant" is always: $\tau = R_{EFF} \times C1$, in seconds. When speaking of a capacitor charging/discharging, one refers to the number of time constants that have elapsed. A capacitor charges to 63.2% of the dif-

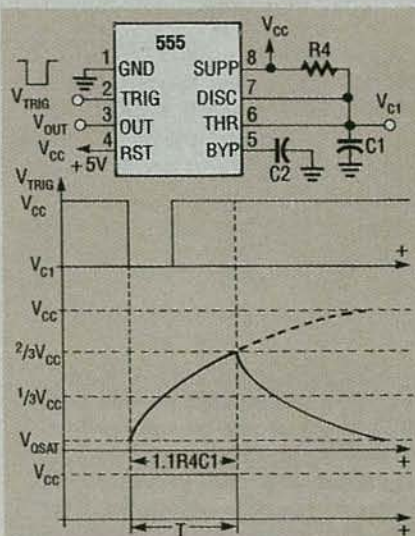


FIG. 3—MONOSTABLE MODE OF THE 555, showing the relation between the output on pin 3 and $C1$'s voltage on pin 6.

pressed "in" at any given time, although all three can be "out" at the same time.

Each DPDT switch in the array (S1-S3) has two sets of contacts. To simplify our discussion, we will call the "upper" set of contacts (the set closest to the top of the figure) "a," and the lower set "b" (see Fig. 3). Note that S3 doesn't have to be pushed "in" to serve a function; because of the way in which it is wired, it does affect the circuit in the "out" position.

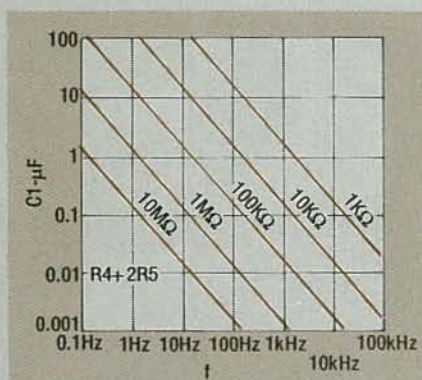


FIG. 4—NOMOGRAPHS FOR SELECTING component values for the 555 timer in the astable mode.

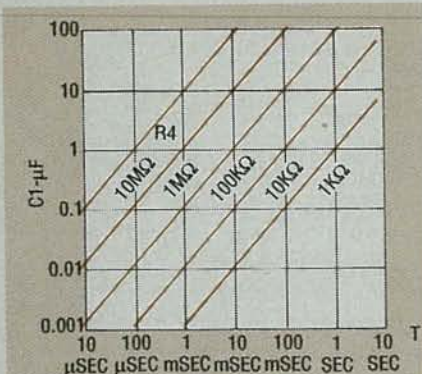


FIG. 5—NOMOGRAPHS FOR SELECTING component values for the 555 timer in the monostable mode.

ference between its initial and target voltages in one τ , and essentially fully charges/discharges to a target voltage within 5τ (99.33%).

The voltage divider partitions the charge/discharge cycle so that there are two sets of target voltages; those created by the divider, and those of V_{CC} and ground. The $C1$ voltage stays between $1/3$ and $2/3$ of V_{CC} in the astable mode. Since $C1$ either charges toward V_{CC} or discharges toward ground, the V_{CC} /ground target

voltages are never reached in the astable mode, being outside the charging/discharging bounds created by the voltage divider.

The intervals required to reach the voltages due to the voltage divider, both charging and discharging, can be determined exactly. This eliminates the problem that $C1$ can only charge/discharge arbitrarily close to a target voltage.

In the astable mode, $C1$ cycles between $1/3$ and $2/3$ of V_{CC} , always charging/discharging to halfway between an initial and target voltage. When charging, the initial voltage is $1/3$ V_{CC} and the target voltage is V_{CC} . When discharging, the initial voltage is $2/3$ V_{CC} , and the target voltage is ground.

For $C1$ to charge/discharge through R_{EFF} from one divider voltage to the other, it always takes:

$$T = 0.693 \times \tau = 0.693 \times R_{EFF} \times C1.$$

In the astable, the charging interval is:

$$T_{AC} = 0.693 \times (R4 + R5) \times C1.$$

The discharge interval is:

$$T_{AD} = 0.693 \times R5 \times C1.$$

The total period is:

$$T_A = T_{AC} + T_{AD} = 0.693 \times [R4 + (2 \times R5)] \times C1$$

And the frequency is:

$$f_A = 1/T_A = 1.44/[R4 + (2 \times R5)]C1.$$

In the monostable mode, Q holds $C1$ at ground. After triggering, $C1$ charges through $R4$ to $2/3$ V_{CC} . Both the charging cycle and the pulse are now ended by the threshold comparator, as mentioned earlier. For reasons too lengthy to discuss in the space we have, pulse duration will be:

$$T_M = 1.1 \times R4 \times C1.$$

Figure 4 is a nomograph of $C1$ vs. f_A in the astable mode for different values of $R4 + (2 \times R5)$. Figure 5 is a nomograph of $C1$ vs. timing-pulse width T_M in the monostable mode for different values of $R4$. R-E

Switches S1-a, S2-a, and S3-a control the capacitance-measurement range by switching in the appropriate potentiometer—R7, R8, or R9. The potentiometers control the duration of the pulse from IC2, with the ranges as shown in Fig. 3. Switches S1-b and S2-b control which decimal point is selected, and S3-b controls the frequency of the astable 555, IC3. There are two potentiometers used to determine the astable frequencies: R13 and R14. Pressing either S1 or S2 switches R13 into the circuit for both the

999-1- μ F and 1-0.001- μ F ranges, for an astable frequency of 100 kHz. However, when S3 is pressed, R13 is removed from the circuit, and R14 is switched in for the 1000-1-pF range, for an astable frequency of 10 kHz.

Counter/driver IC5, a 74C926, contains a 4-digit negative-edge-triggered counter, a 4-digit internal output latch, drivers for a 4-digit 7-segment LED display, an internal multiplexer with four outputs, and its own free-running oscillator. A high on pin 13 resets the counter to zero

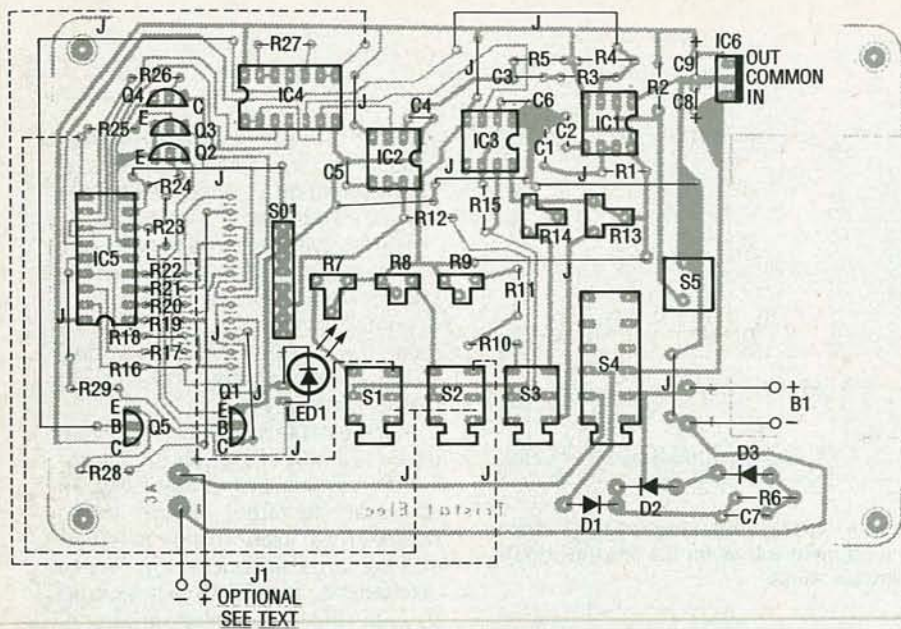


FIG. 4—PARTS PLACEMENT DIAGRAM. The jumpers shown in dashed lines are soldered to the solder lugs on top of the switches.

and drives pin 14 (CARRY OUT) low. A low on pin 5 (LATCH ENABLE) latches the number in the counter using the internal output latches, whereas a high on pin 5 permits a flow-through condition in which the internal latches ignore future counts. A high on pin 6 (DISPLAY SELECT) displays the number in the counter, while a low displays the number in the output latch. In this application, pin 6 is grounded, permanently displaying the contents of the latch, and never the output of the counter.

The pulse from IC2 is positive, and

after being NAND'ed (by IC4-b) with the output from IC3, the resulting output in inverted. The down-going pulse from IC4-a enables IC5 to latch the count of the astable pulses within the measurement pulse. Because pin 5 of IC5 goes low during the timing pulse, the new value in the counter is automatically latched each time a count occurs.

The latched count is then converted into the value of the unknown capacitor by shifting the decimal point on DSP1 via transistors Q1-Q5. IC4-c and IC4-d buffer the outputs from the

A and C digit drivers of counter/driver IC5, to provide sufficient logic swing for the display. When the counter in IC5 exceeds 9999, pin 14 goes high, lighting the range-overflow indicator, LED1.

Pin 7 of IC5 controls digit A, pin 8 controls B, pin 10 controls C, and pin 11 controls D. Pins 1-4 and 15-17 drive each individual segment of each digit. IC5's internal clock scans the digit-control lines fast enough to avoid display flicker. The decimal point is selected by feeding pin 7 of IC5 (which controls digit A) back to S1-a for the 1-.001 μ F range, or pin 10 (which controls digit C) back to S1-b for the 999-1 μ F range. The other two decimal points are not used. The display format has no leading-zero blanking or external scaling. Therefore, 100 pF is displayed as 0100, 0.001 μ F is displayed as 0.001, and 4.7 μ F as 004.7.

Switch S4 supplies power to the 7805 voltage regulator, which provides a steady 5-volts DC to the circuit. If you use a 9-volt battery, you can ignore the optional charger/adaptor jack, J1. (Two pads labeled "AC" are provided on the PC board for J1.) A Ni-Cd battery can only be recharged when the meter is on; that's because S4 connects J1 to D1 and the battery to IC6. Charging the Ni-Cd battery pack normally draws about 300 mA, so be sure that whatever you're using can handle that.

PARTS LIST

All resistors are 1/4-watt, 5%, unless otherwise indicated.

R1, R8, R12, R16-R22—100 ohms
 R2, R4, R5, R27—100,000 ohms
 R3—10,000 ohms
 R6, R28—560 ohms
 R7—1000 ohms, PC-mount potentiometer
 R8—250,000 ohms, PC-mount potentiometer
 R9—2.5 megohms, PC-mount potentiometer
 R10—4.7 megohms
 R11—2.2 megohms
 R12—7.1 megohms
 R13—15,000 ohms, PC-mount potentiometer
 R14—150,000 ohms, PC-mount potentiometer
 R15—2200 ohms
 R23-R26, R29—1000 ohms

Capacitors

C1, C7—0.1 μ F, ceramic disc
 C2, C3, C5—0.01 μ F, ceramic disc
 C4, C6—0.001 μ F, ceramic disc
 C9—1 μ F, tantalum electrolytic

Semiconductors

D1-D3—1N4001 rectifier diode
 Q1-Q5—2N3904 NPN transistor
 IC1-IC3—555 timer IC
 IC4—4011 CMOS quad 2-input NAND gate
 IC5—74C926 CMOS counter/LED display driver
 IC6—7805 5-volt regulator
 DSP1—NSB5881 4-digit 7-segment LED display
 LED1—red light-emitting diode

Other components

SO1, SO2—8-pin SIP wirewrap socket
 PL1—8-pin SIP plug
 S1-S3—board-mounted 3-pushbutton DPDT switch array, 3/16-inch lead spacing, with PC-contact pins and solder lugs for wires
 S4—board-mounted pushbutton 4P2T switch, 3/16-inch lead spacing, with PC-contact pins and solder lugs for wires
 S5—board-mounted momentary pushbutton, 3/16-inch lead spacing

B1—9-volt alkaline battery or optional 7.2-volt rechargeable Ni-Cd (see text)

J1—subminiature jack matching the plug of the charger/adaptor (optional, see text)

T1—optional charger/adaptor, 117/12-volts AC, 300 mA

Miscellaneous: Pacifitec Model HPL-000 project case, 9-volt battery clip, LED bezel, solder, wire, etc.

NOTE: The switches for the prototype were obtained from Active Surplus Annex, 347 Queen Street West, Toronto, Ont., Canada, (416) 593-0967. A kit of all parts except resistors, capacitors, and PC board is available for \$39.95, plus \$5.00 shipping and handling. A PC board is available for \$12.00. Contact Tristat Electronics, 66A Brockington Crescent, NEPEAN, Ont., Canada K2C 5L1.

Construction

The Parts-Placement diagram is shown in Fig. 4, and a foil pattern is provided in PC Service. Before soldering, it's a good idea to clean the foil side of the board with steel wool to remove oxides; that ensures a smooth solder flow. Use sockets for the IC's and various transistors.

Figure 5 shows how to make the test socket, SO1, and its corresponding plug, PL1. SO1 is made from an 8-pin SIP wirewrap socket, and PL1 from an 8-pin SIP plug; the two are connected by a twisted pair. SO1 is epoxied into its opening in the case, and PL1 fits into SO2.

The display is connected to the PC board using 2 inches of No. 12 ribbon cable. Solder one side to the display and the other side to the PC board. (Be certain that pin 1 of the display goes to pad 1 on the PC board.) Only solder pins 1, 3, 4, 7, 8, and 10-16 of the display—the others are not used.

Solder LED1 approximately $\frac{3}{4}$ of an inch above the PC board, so that its top is flush with the case. You can use a mounting bezel for LED1.

Figure 6 is a photograph of the prototype meter. Study Figs. 3, 5, and 7 for the relationship of all components to one another, as well as the position of all components. Note that the 7805 is bent flat for case clearance, with its metallic side facing upward.

If you decide to use Ni-Cd batteries, the most convenient way to install the charging jack (J1) is to drill a hole in the meter case near the "AC" pads on the PC board. (Drill slowly to prevent damaging the plastic.) It's up to you to choose the type of jack for J1; it must, however, match the plug of the charger/adaptor, and be small enough to fit in the case.

Before installing the IC's or transistors in their sockets, apply power to the board and check for correct voltages. Then, shut off the power, insert the IC's and transistors, and turn the meter on again; the display should now show a random 4-digit number. If not, turn the meter off and check the wiring, looking particularly for a short in the display foils.

Exact calibration

To calibrate the meter, you should use an oscilloscope or frequency counter, and one precision unknown capacitor for each range. Connect the oscilloscope or frequency counter between pin 3 of IC3 and ground. Then

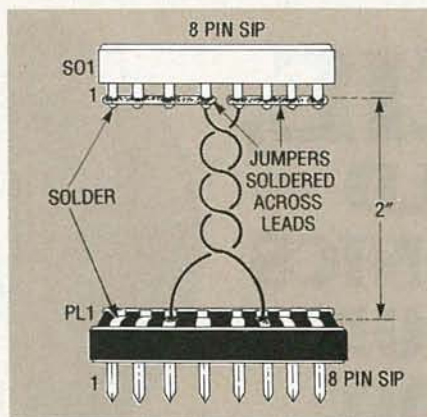


FIG. 5—TEST SOCKET CONNECTORS. This assembly connects the capacitor under test to the PC board's test socket.

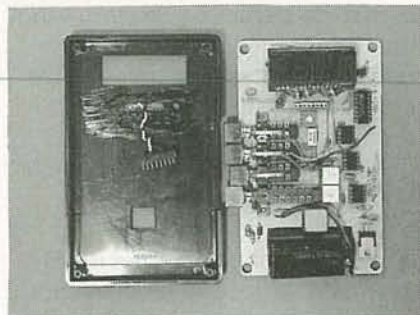


FIG. 6—THE CAPACITANCE METER. Notice how the various parts are oriented.

press either S1 or S2 and adjust R13 for 10 kHz. Now press S3 and adjust R14 for a reading of 100 kHz. If you've got precision capacitors, insert a suitable one for the 999-1 μ F range, press S5, and adjust R7 until the display reads the nominal value.

Without precision unknown capacitors, use an iterative (repetitive) approach. Use three or four non-precision capacitors for each range, of the same nominal value. For the 999-1 μ F range, test an unknown capacitor at random, adjusting R7 until C_X 's nominal value appears on the display, and then set the capacitor aside. Next, without adjusting R7, test and record the other unknowns for that range, and average the results.

Now, using the first unknown capacitor tested (the one set aside), adjust R7 so that the meter shows your average value, rather than the nominal value. Without adjusting R7, test the other unknowns and average the new values. Now, let the first unknown in the new average have the first average value that you came up with. Repeat until the average value no longer changes much. The accuracy of the meter will increase with the number of unknowns tested per range, and the number of iterations. Repeat the pro-

cedures for the other two ranges, adjusting R9 for the 1-0.001- μ F range, and R11 for the 1000-1-pF range.

Approximate calibration

Without proper gear, you can get good but not perfect calibration. Use a nominal value of capacitor suitable for each range as an unknown, and set all potentiometers to mid-point. Select a range, and insert a suitable unknown capacitor. Don't vary R7 or R9; adjust R11, R13, or R14 until the nominal value of the capacitor being tested appears on the display. Set the first unknown aside, and repeat the procedure, sampling the other identical nominal value capacitors for this range without varying any of the potentiometers at this point, and average the display values. Using the first nominal-value capacitor tested, readjust R11, R13, or R14 for the first average value. Repeat the procedures for the other ranges.

Using the meter


Once calibrated, plug PL1 into SO2 on the PC board, and put the meter in its case. A polyethylene faceplate was epoxied to the prototype's case, but the front-panel design for your meter is up to you.

The meter's stray capacitance is about 30 pF, and can't be zeroed on the pF range. If you press S5 with no capacitor attached, while in the pF range, the meter should read about 30 pF. The stray capacitance is in parallel with the unknown, so it must be subtracted from any pF-range reading.

When testing a capacitor, watch LED1 to get higher precision on the two lower ranges. For a nominal value of 0.01 μ F, the meter might read 0.010467 μ F, in which case the pF range would overflow; the number of LED1 flashes gives the overflow digit. On the 1-0.001- μ F scale, the nominal 0.01- μ F capacitor might read 0.011. On the pF range, LED1 should flash once since the counter passed 9999 once; the display should read 0467. However, LED1 flashes rapidly, and is hard to count.

If LED1 flashes once, that means an overflow digit of one; then, C_X is 10,467 pF or 0.010467 μ F. If LED1 flashes twice, the reading would be 20467 pF, etc. Note that holding S5 down doesn't increase accuracy. It just wastes current by repetitively testing a capacitor, and will prevent a reading from being displayed. R-E

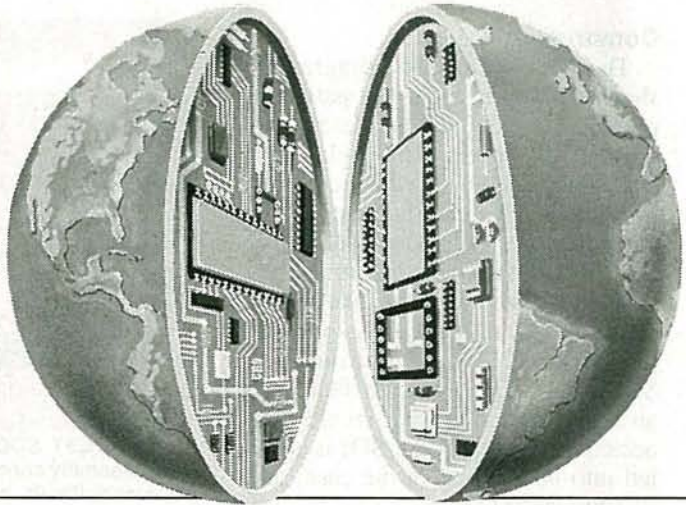WITH CIE, THE WORLD OF ELECTRONICS CAN BE YOUR WORLD, TOO.



Look at the world as it was 20 years ago and as it is today. Now, try to name another field that's grown faster in those 20 years than electronics. Everywhere you look, you'll find electronics in action. In industry, aerospace, business, medicine, science, government, communications—you name it. And as high technology grows, electronics will grow. Which means few other fields, if any, offer more career opportunities, more job security, more room for advancement—if you have the right skills.

SPECIALISTS NEED SPECIALIZED TRAINING.

It stands to reason that you learn anything best from a specialist, and CIE is the largest independent home study school specializing exclusively in electronics, with a record that speaks for itself. According to a recent survey, 92% of CIE graduates are employed in electronics or a closely related field. When you're investing your time and money, you deserve results like that.

INDEPENDENT STUDY BACKED BY PERSONAL ATTENTION.

We believe in independent study because it puts you in a classroom of one. So you can study where and when you want. At your pace, no somebody else's. And with over 50 years of experience, we've developed proven programs to give you the support

such study demands. Programs that give you the theory you need backed with practical experience using some of the most sophisticated electronics tools available anywhere, including our Microprocessor Training Laboratory with 4K of random access memory. Of course, if you ever have a question or problem, our instructors are only a phone call away.



START WHERE YOU WANT, GO AS FAR AS YOU WANT.

CIE's broad range of entry, intermediate, and advanced level courses in a variety of career areas gives you many options. Start with the Career Course that best suits your talents and interests and go as far as you want—all the way, if you wish, to your Associate in Applied Science Degree in Electronics Engineering Technology. But wherever you start, the time to start is **now**. Simply use the coupon below to send for your FREE CIE catalog and complete package of career information. Or phone us, toll-free, at **1-800-321-2155** (in Ohio, 1-800-523-9109). Don't wait, ask for your free catalog now. After all, there's a whole world of electronics out there waiting for you.

CIE

Cleveland Institute of Electronics, Inc.
1776 East 17th Street, Cleveland, Ohio 44114

Member NHSC
Accredited Member National Home Study Council

CIE **Cleveland Institute of Electronics, Inc.**
1776 East 17th Street, Cleveland, Ohio 44114

ARE-133

YES... I want to learn from the specialists in electronics—CIE. Please send me my FREE CIE school catalog, including details about CIE's Associate Degree program, plus my FREE package of home study information.

Name (print): _____

Address: _____

City: _____ State: _____ Zip: _____

Age: _____ Area Code/Phone No.: _____ / _____

Check box for G.I. Bill bulletin on educational benefits:

Veteran Active Duty

**MAIL
TODAY!**

BUILD THIS

AMATEUR TV TRANSMITTER

Get in the picture with our television transmitter.

WILLIAM SHEETS and RUDOLF F. GRAF

LAST MONTH WE ANALYZED THE TV transmitter circuitry in great detail, describing the function of virtually every transistor, capacitor, inductor, and resistor. Now we'll present the construction techniques in the same detail. They should pose no special problems, but your best bet is to duplicate the author's prototype as closely as possible. That's because when working with ultra-high-frequency RF, such things as PC-board layout, component placement, and especially lead lengths become critical.

Assembly hints

As long as the author's design is exactly duplicated, you shouldn't encounter any *off the wall* UHF problems, so follow these suggestions without compromise:

1. As you assemble this project, use only the parts specified in the Parts List because ultra-high frequency circuits are sensitive to changes in component type and value. Also follow the author's parts placement as closely as possible.
2. Lead lengths should be kept short. Handle the surface-mount components and ferrite beads with extra care. The $\frac{1}{10}$ -watt resistors and miniature NPO ceramics should have short leads, and close component spacing.
3. Wind your own slug-tuned coils with available materials, rather than using commercial, hard-to-get factory-made types. That gets rid of the coil headaches. If the dimensions are followed, no problems should result.

As shown in Fig 1, you'll find that the coils are easy to wind, and the largest ones have only eight or nine turns of wire. In fact, several are only loops or pieces of wire because the inductors required at 420–500 MHz are usually in the 0.01 to 0.1-microhenry range. Complete technical data is compiled in Table 1.

4. Pay particular attention to supply bypassing. We have incorporated a tantalum chip capacitor to guarantee good bypassing. By keeping everything compact, and by using a shielded, double-sided PC board with good RF bypassing, all the possible "horrors" associated with VHF and UHF circuitry can be done away with.
5. The PC board is compact and parts are small, so a small iron with a pointed tip is recommended, especially for soldering the chip capacitors.
6. Use only 0.062-inch thick epoxy-fiberglass PC-board materials. Other materials and thicknesses could be used, but may result in different tuning conditions, and stray capacitances. Don't use paper-base phenolic materials; they're too lossy at UHF frequencies.
7. Transistor Q12 must be heat-sinked because it must dissipate up to 3 watts. The method shown in Fig. 2 has proven adequate if at least 1-ounce copper is used. On the other hand, Q7 is adequately heat-sinked if the metal case is soldered to the PC-board ground plane.
8. Solder as many component leads as possible (that pass through the ground



BUILD THIS AMATEUR TV TRANSMITTER

Add TV transmitter to your radio shack.

RUDOLF F. GRAF and
WILLIAM SHEETS

With the new 100-watt transmitter, you can broadcast your own TV program with accompanying audio, color, through coaxial cable, or to a nearby receiver. Build your best, because it's all possible with our video transmitter. An impedance will be provided in all the following applications:

1. Amateur TV transmitter.
2. Video transmitter when cable linkage is impossible, like video.
3. Secure and industrial work.
4. Simultaneous viewing of several video TV screens.
5. Remote viewing application, like mobile viewing.
6. Cable transmission.
7. Wireless camera TV system, or VCR link.

The video-link transmitter is available in two levels of 100 watts. For the power version, build the inductor in a tube or other where simultaneous monitoring of program material is done also without counter-clock linkage. 1. 30 inch in outside, 1/2 inch larger inside up to several inches, or an amateur class TV antenna, and ventilated properly. 2 with wire 1/16 inch lead is available.

The video-link transmitter will accept color and B/W video, and audio signals from VCR's, camcorders, small TV cameras, and microphones. The unit runs on a standard 115 volt, 60 Hz power supply at the impedance shown, or 100 ohm at the 2.4 megohm.

The PC board is only 1 1/2 inch x 4 inches and contains everything needed except a power supply and connectors. We used both

plane) to the top and bottom of the board. In particular, the ground lugs on all trimmer capacitors should be soldered on both sides, and also the resistors that have one side connected to ground. The idea is to ground as much of the ground plane to the ground foil on the component side, in as many places as possible; that's especially important around Q4–Q7.

9. Use chip capacitors where specified. Do not substitute ordinary leaded capacitors.
10. Keep all component leads as short as possible, and as close to the board as possible.
11. Take care to make coils as accurately as possible. While some errors can be tolerated, accurate work will make tuneup easier.

Parts installation

Figure 3 shows the Parts-Placement diagram for the TV transmitter. First install all resistors and then diodes D1 and D3. Don't forget the ferrite beads on R15, R17, R19, and R21. Next install all disc ceramics (0.01 μ F and 470 pF), and then the NPO capacitors. Now install potentiometers R22, R32, and R33, soldering the grounded side of R22 and R33 to both sides of the PC board. Install all trimmer capacitors. Note that C18 and C40 are different from the rest. Solder ground tabs of all trimmers to both top and bottom of the PC board. Install transistors Q1 through Q5, and Q8 through Q11, but don't install Q6, Q7, or Q12 yet.

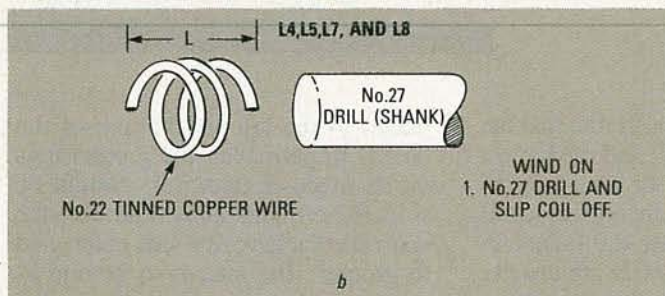
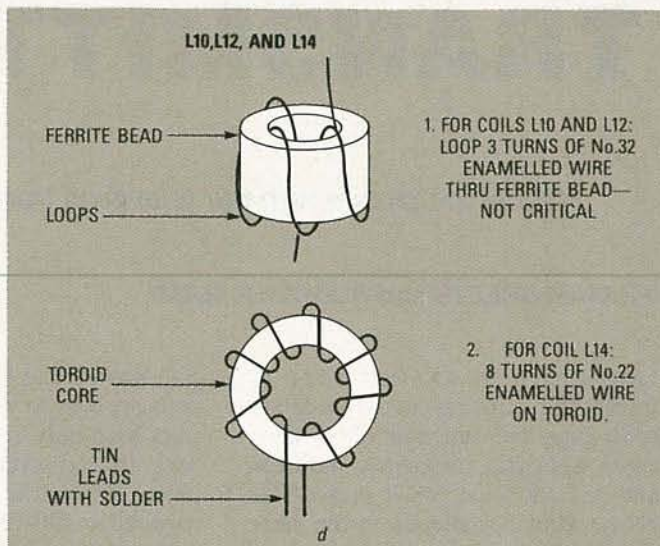
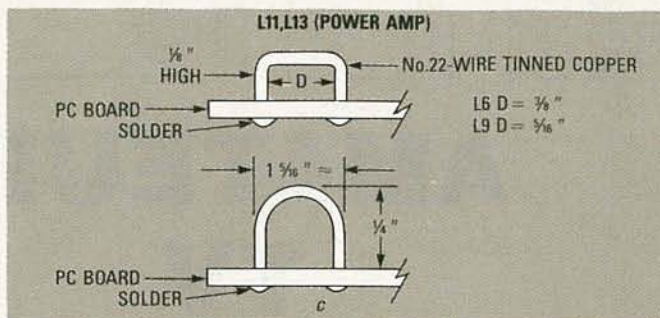
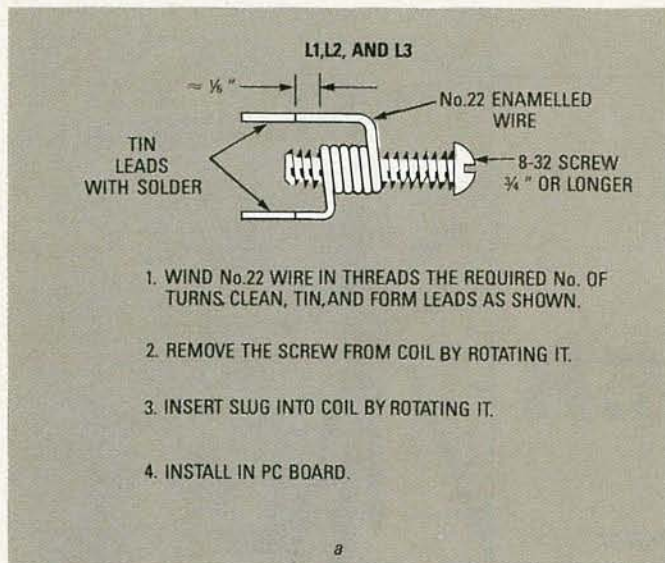


FIG. 1—IF YOU WANT TO CONSTRUCT THE COILS BY HAND, you have to wind them on the threads of a screw (a), the shank of a drill bit (b), using measured bends (c), or around a ferrite bead (d).

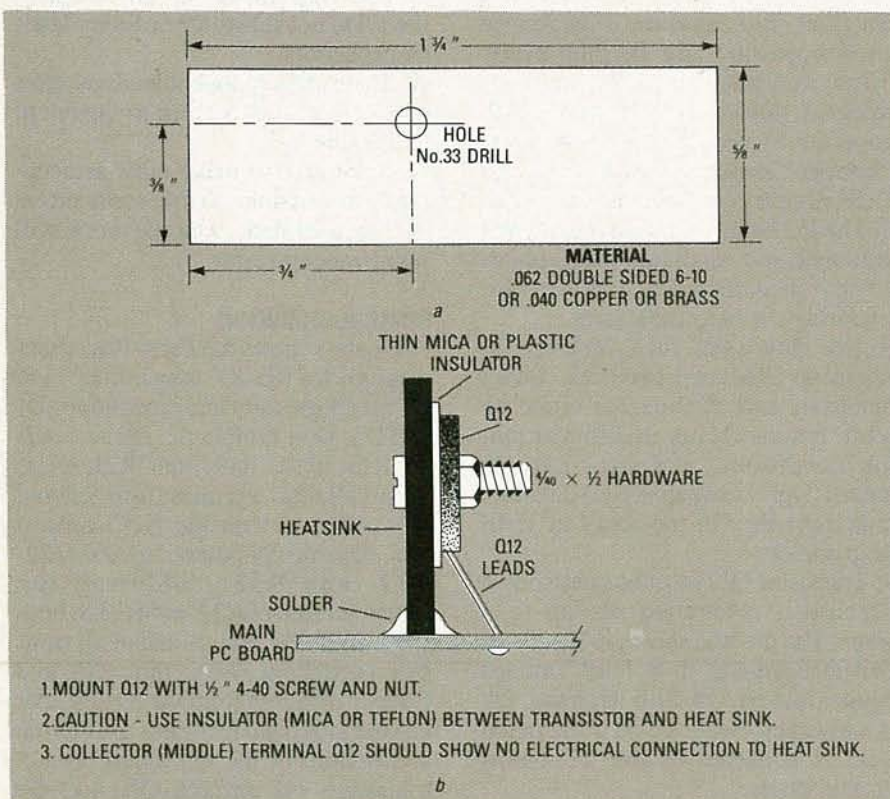


FIG. 2—THE ALUMINUM PLATE THAT IS USED AS A HEAT SINK FOR Q12 also functions as an RF shield for transistors Q6 and Q7.

Wind and install L1 through L9, and L14. If you're building the low-power version, leave out any components associated with Q6 and Q7, except L9; go ahead with the modification shown in Fig. 4, and be sure to omit C22. Install chip capacitors C22, C24, C44, and C20.

Check the PC board for shorts, solder bridges, and trim away any excess foil with a sharp knife (*X-acto* type or equal). Make sure that excess foil on the top side is not touching any component leads that are not intended to be grounded. Slight mis-registration of the top foil during PC fabrication may cause that.

Now install Q12 and its heat sink. Note that the heat sink also serves as an RF shield for Q6 and Q7 (if used). Be sure to solder the heat sink where it butts against the PC board. Note that Q12's case should be insulated from the heat sink. Use a TO-220 insulator (cut to size), or a scrap of mica, mylar, polyethylene, or teflon tape used in plumbing work.

You are now ready to test the main part of the board. If you're construct-

ing the 2-watt version, Q6, Q7, and any associated components will be installed only after the rest of the PC board is tested.

Testing

After checking your work, measure the DC resistance between V_{CC} and ground; it should be greater than 200 ohms. If it's lower than that, check your work again for the cause before proceeding any further.

Next, install the slugs in L1, L2, and L3 if you haven't already done so. The slugs should be initially set fully inside the coils. Set R22, R32, and R33 about halfway between extremes of rotation. Set trimmer C40 and all other trimmer capacitors to half mesh. Final settings will depend on the operating frequency, coil-construction technique, and application.

Apply +12 volts after connecting the negative-supply lead to the PC-board ground plane. Immediately observe power-supply current; if it's over 130 mA, there may be a problem. If anything smokes or gets too hot, immediately remove the power and find the problem before proceeding.

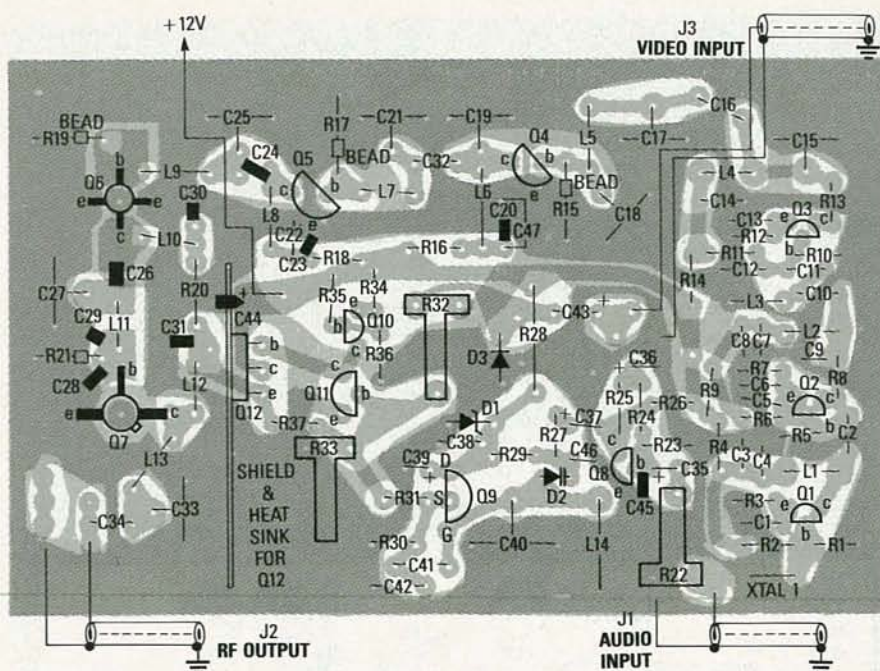


FIG. 3—PARTS PLACEMENT DIAGRAM shows capacitor chips (C20, C23, C24, C26, C28, C29, C30, C31, C45) mounted on the solder side, as is Q6.

If all seems OK, connect a VOM (preferably an analog meter) across R3, and then R7. You should read between 1.5 and 3-volts DC. Next

connect the VOM across resistor R12 Q3; you should read 1 volt or less. Now connect the VOM between point A (emitter of Q12) and ground. Verify

TABLE 1—COIL DESCRIPTIONS L1-L14

COIL	FREQ. RANGE MHz	NO. TURNS & LENGTH	WINDING FORM	NOTES
L1	420-450 (HAM TV) 450-500 (VIDEO LINK)	9½ 8½	8-32 SCREW THREAD	NO. 22 ENAMEL WIRE
L2	420-450 450-500	4½ 3⅓		
L3	420-450 450-500	5½ 3½		
L4	ALL	3 TURNS ¼" LONG	NO. 27 DRILL (0.144" DIA) SPACE TURNS	MADE WITH NO. 22 TINNED COPPER
L5	ALL	4 TURNS ¼" LONG		
L7	ALL	1½ TURNS ⅛" LONG		
L8	ALL	2½ TURNS ⅛" LONG		
L6, L9, L11, L13	ALL	PER FIG. 1	NONE (PC BOARD)	
L10, L12	ALL	PER FIG. 1	FERRITE BEAD	NO. 32 ENAMEL WIRE
L14	4.5 MHz (NTSC SOUND SUBCARRIER)	8 TURNS NO. 22 ENAMEL	TOROID	NO. 22 ENAMEL WIRE

NOTE: Due to individual winding technique and normal circuit tolerances, L1, L2, L3 and L14 may require one turn more or less than shown in Table 1. L4, L5, L7 and L8 may have to be squeezed or spread lengthwise. All dimensions are taken from average of several working units. Individual units vary somewhat from given dimensions due to tolerances, winding techniques, and installation.

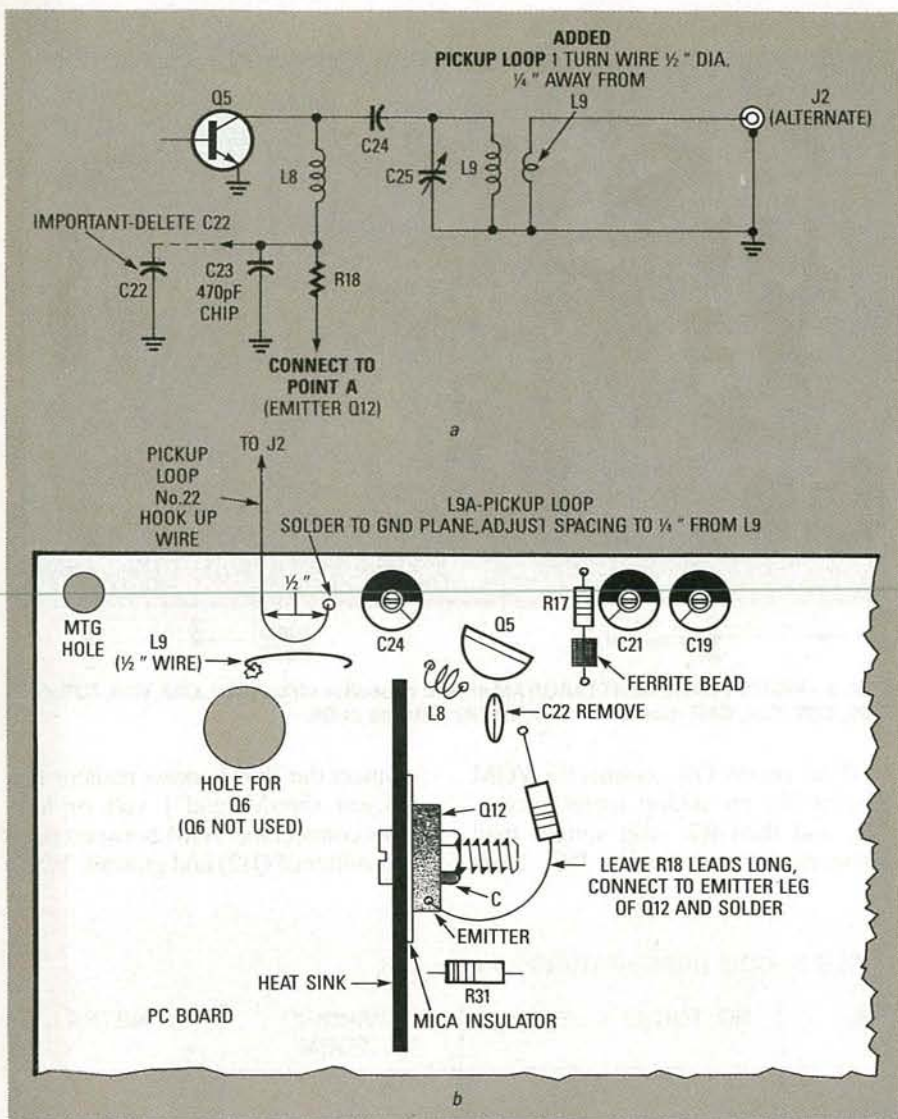


FIG. 4—TO OPERATE THE UNIT AT LOW POWER you should follow schematic (a) and assembly modification (b).

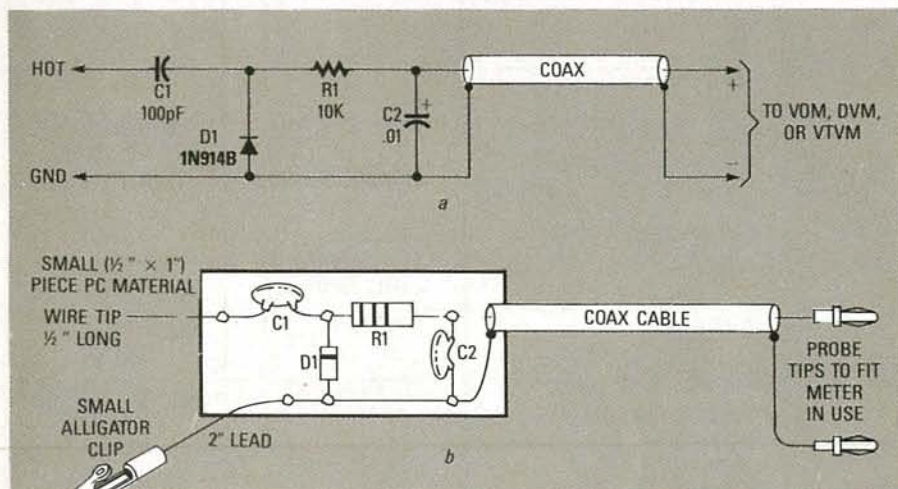


FIG. 5—HERE'S AN RF PROBE YOU CAN BUILD for your DMM, VOM, or scope. It's helpful in adjusting the transmitter for peak power.

that adjusting R33 through its full range will vary the voltage at point-A

between less than 5 volts to greater than 11 volts. Set R3 for full voltage

PARTS LIST

All resistors are 1/8 or 1/10-watt, 5%.

- R1, R5—3900 ohms
- R2, R6, R11, R31—15,000 ohms
- R3, R7, R15—330 ohms
- R4, R9, R12, R14, R16–R19, R35—100 ohms
- R8, R13—10 ohms
- R10—680 ohms
- R20—10 ohms, 1/4-watt
- R21—22 ohms
- R22—100,000-ohms potentiometer
- R23—22,000 ohms
- R24, R29—100,000 ohms
- R25—33,000 ohms
- R26—4700 ohms
- R28—470 ohms, 1/4-watt
- R30—2200 ohms
- R32, R33—1000-ohm potentiometer
- R34—15 ohm
- R36—1000 ohms
- R37—3300 ohms

Capacitors

- C1—56 pF, NPO, ceramic disc
- C2, C12—33 pF, NPO, ceramic disc
- C3, C7, C19, C22, C38, C47—0.01μF, ceramic disc
- C4, C6, C8, C13, C14—470 pF, NPO, ceramic disc
- C5—82 pF, NPO, ceramic disc
- C9, C11—15 pF, NPO, ceramic disc
- C10—2.2 pF, NPO, ceramic disc
- C15, C17, C19, C21, C25, C27, C33—2–10-pF, trimmer
- C16, C32—1 pF, NPO, ceramic disc
- C18—2–18 pF, or 2–20-pF trimmer
- C20, C23, C24, C45—470 pF, ceramic chip
- C26, C30, C31—100 pF, ceramic chip
- C28, C29—22 pF, ceramic chip
- C34—5 pF, silver mica
- C35–C37—1 μF, 50 volt, electrolytic
- C39—10 μF, 16 volt, electrolytic
- C40—3–40 pF, trimmer
- C41—220 pF, NPO, ceramic disc

(greater than 11 volts) at point A for now.

Measure the voltage at Q8's collector; about 4 to 7 volts is OK. Next measure the voltage across D1; it should be between 8- and 10-volts DC. If it is more or less, that indicates a problem in Q8, Q9, or the associated circuitry. Check for 8- to 10-volts across D2. If it reads 1 volt, D2 is installed backwards or is shorted.

If all is good up to this point, install crystal XTAL1, connect a VOM across R7, and apply power. Tuning the oscillator is done as follows: Slowly back L1's slug out of the winding. You'll find that the voltage across R7 will suddenly increase, then slowly decrease as the slug is tuned. Adjust

C42—470 pF, NPO, ceramic disc
 C43—220 μ F, 16 volt, electrolytic
 C44—10 μ F, 16 volt, chip tantalum
 C46—100 pF, NPO, ceramic disc
 C47—0.01 μ F, ceramic chip

Semiconductors

Q1, Q2—2N3563, transistor
 Q3—Q5—MPS3866, transistor
 Q6—MRF559 or MRF627 transistor
 Q7—MRF630, transistor
 Q8—2N3565, transistor
 Q9—MPF102, transistor
 Q10—2N3906, transistor
 Q11—2N3904, transistor
 Q12—MJE180, transistor
 D1—1N757A, diode
 D2—MV2112, varactor diode
 D3—1N914, diode
 D4—1N4007, diode

Inductors

L1—L14—See table 1

Other components

XTAL1—52.5-62.5 MHz

Notes: The following kits are available from North Country Radio, PO Box 53, Wykagyl Station, New Rochelle, NY 10804: Low-Power Kit w/ATV crystal for operation on 439.25 MHz, \$79.95 plus \$2.50 shipping and handling; 2-Watt Kit w/ATV crystal for operation on 439.25 MHz, \$104.95 plus \$2.50 S/H; extra crystals for CH14, CH15 operation, \$6.50 plus \$1.50 S/H; PC board only plus Cores, chip capacitors, and D2, (partial kit), \$49.95 plus \$2.50 S/H; Crystals can be purchased separately from Crystek Corporation, PO Box 06135, Fort Myers, FL 33906. Kits do not include jacks, connectors, batteries, power-supply components, or case.

the slug for maximum voltage (3 to 5 volts), then back out the slug for about a 10% drop to ensure stable oscillation. As a check, a frequency counter connected to the junction of C2 and C5 should indicate the crystal frequency. An unstable reading indicates that the crystal is not controlling the frequency. If that's the case, try re-adjusting L1.

Here's how to tune the 1st doubler. Connect the VOM across R12, and adjust L2 and L3 for maximum voltage (about 1 to 2 volts). If adjusting the L1 and L2 slugs doesn't peak the voltage, then add or subtract a turn from the coil as required, after first checking C9, C10, C11, and C12 for correct values.

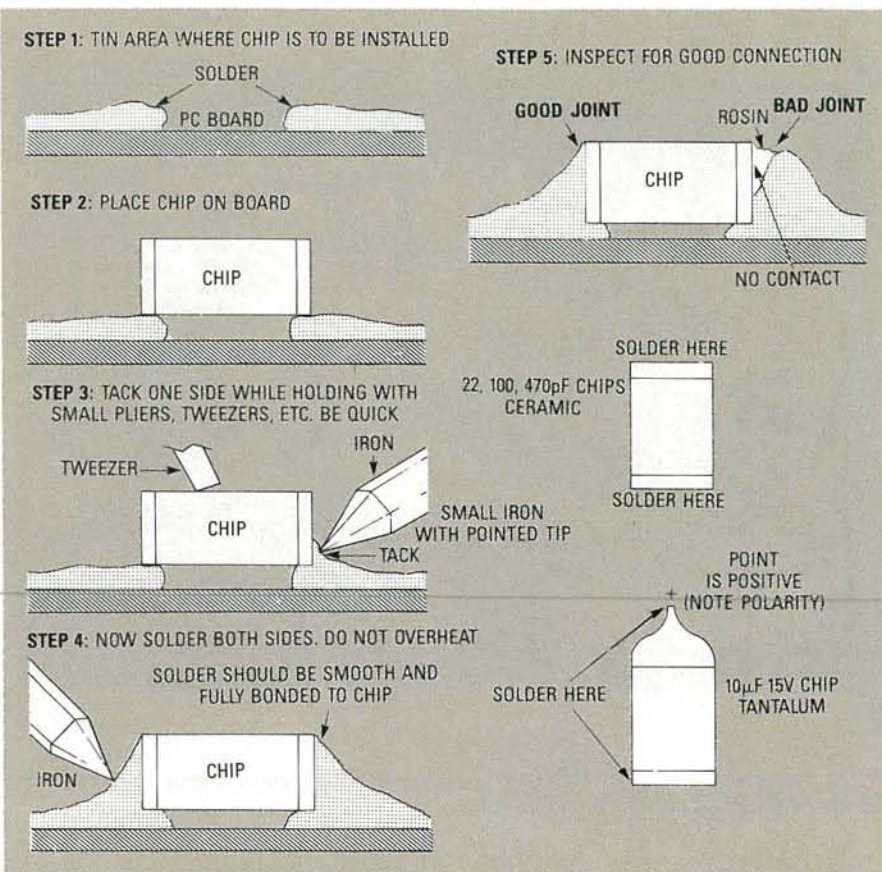


FIG. 6—IF YOU FOLLOW THESE STEPS when soldering the chip components to the PC board, you'll have no problems with them.

Here's how to tune the 2nd and 3rd doublers. Connect an RF probe to the junction of L9 and R19, or to the junction of C25 and L9 if you're building the low-power version. Figure 5 shows you how to build an RF probe if you don't already have one. Adjust C15, C17, C18, C19, C21, and C25 for a maximum reading. You should be able to obtain at least 1.5 volts of RF energy at the junction of R19 and L9 for the high-power version, and about 2 volts at the junction of C25 and L9 for the low-power version. If everything looks good, that checks out stages Q1 through Q5.

To adjust the RF output for the low-power version connect a 47-ohm resistor to J2A (Alternate). Adjust C25 and the position of L9A (Alternate) with respect to L9 for maximum output. Don't couple L9A too close to L9—just enough for about 1 volt across the 47-ohm resistor.

Final assembly

If you're building the 2-watt version, now is the time to install Q6 and Q7, and then L10 through L13. You may now install the chip capacitors C26, C28, C29, C30, and C31, but

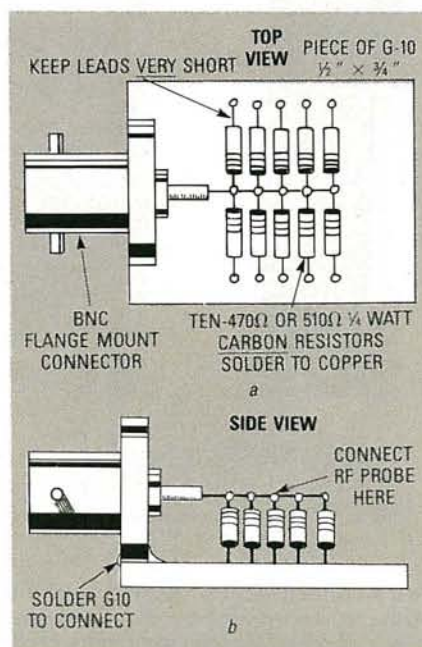


FIG. 7—A DUMMY LOAD SHOULD BE USED while adjusting the power output.

don't overheat them! Make sure that the PC board is tinned in the areas where chips are installed. The best way to install them is to first tack-solder one side to hold it down, solder the other side, and then go back and

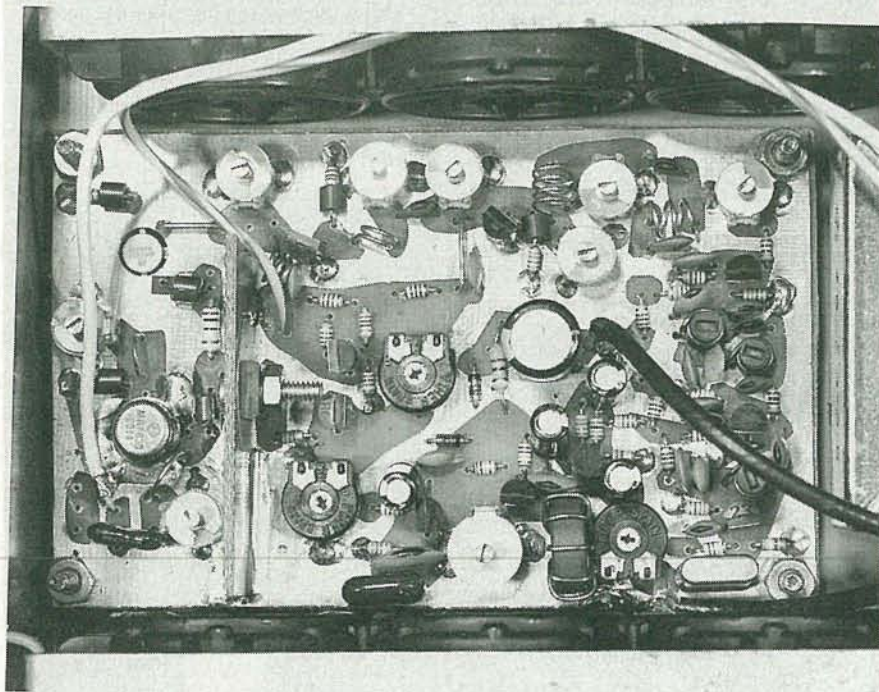


FIG. 8—THE FINISHED PC BOARD has a neat, clean appearance. Sloppy workmanship can not be tolerated on this circuit layout.

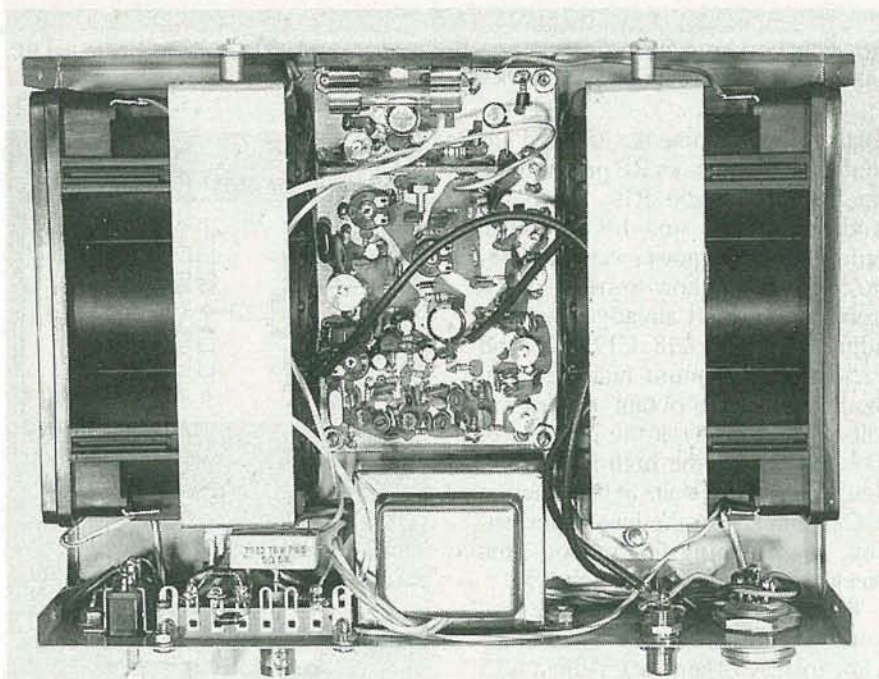


FIG. 9—The AUTHOR'S PROTOTYPE USED 2-Ni-Cd BATTERY PACKS, one on either side of the PC board, which makes the transmitter portable. You'll also notice a power transformer and associated circuitry used for running the transmitter off household AC-line voltage.

resolder the first (tack-soldered) side.

Figure 6 shows you how to solder chip components. Use a 25-watt iron with a pointed tip. Fine-point needle-nose pliers or tweezers should be used to manipulate the chip capacitors.

Finally, install C34 and a suitable

length of small-diameter 50-ohm coax to J2. Check all joints for solder bridges. Make sure that the metal case of Q7 is soldered to the ground plane (top side), and connect its leads to the PC-board underside using as little lead length as possible.

Apply power and quickly adjust C25, C27, and C33 for maximum power into a 50-ohm load connected to J2. You can use a 47-ohm, 2-watt carbon resistor, or the dummy load which can be assembled as shown in Fig. 7. An RF probe can be connected to the hot side of the resistors (center conductor of connector) to read the RF voltage, but an RF power meter is nice to have.

You should get at least 1.5 watts (about 8.5-volts RMS) into the 50-ohm load, which should become warm when operating. Power-supply current will be about 500 mA. Now adjust R33 for an output voltage about half that, or a quarter the power as read on the power meter, if used. Leave the RF load connected as you proceed to the next step.

For either the low- or high-power unit, adjust R33 for about +6 volts at point A (emitter of Q12). Connect a frequency counter to point A, and adjust C40 for exactly 4.500 MHz. Now apply video and audio signals to J3 and J1, respectively. Watch the transmitted image on a TV receiver tuned to the transmitter frequency; adjust the video gain (R32) for best picture contrast and stability, then adjust the audio level (R22) until its level is comparable to a commercial station. Now alternately adjust R32 and R33 for maximum video contrast without seeing any side effects such as instability, audio buzz, or other evidence of clipping. You may also wish to go over all tuning adjustments again for best results. The finished PC board is shown in Fig. 8

Enclosure

Mount the PC board in a shielded metal-case, as shown in Fig. 9, and connect leads from the board to suitable jacks for J1, J2, or J2A, and J3. Also provide a suitable connector for the 12-volt supply, if desired. The transmitter case can house an AC supply, or batteries for portable operation. Use the right size *Ni-Cd* batteries to handle the 100-mA drain (low power), or 500-mA drain (2-watt unit). Use a BNC-type fitting for the antenna jack, J2.

A suitable antenna would be a 6-inch whip or a center-fed dipole, 12-inches long. For amateur TV, a linear amplifier may be installed between J2 and the antenna for greater power output. For the low-power version, use the 6-inch whip antenna. **R-E**

OP-AMP OSCILLATORS

RAY MARSTON

OP-AMPS CAN BE USED TO GENERATE SINE-wave, triangular-wave, and square-wave signals. We'll start by discussing the theory behind designing op-amp oscillators. Then we'll examine methods to stabilize oscillator circuits using thermistors, diodes, and small incandescent lamps. Finally, our discussion will round off with designing bi-stable op-amp switching circuits.

Sine-wave oscillator

In Fig. 1, an op-amp can be made to oscillate by feeding a portion of the output back to the input via a frequency-selective network, and controlling the overall voltage gain.

For optimum sine-wave generation, the frequency-selective network must feed back an overall phase shift of zero degrees, while the gain network provides unity amplification at the desired oscillation frequency. The frequency network often has a negative gain, which must be compensated for by additional amplification in the gain network, so that the total gain is unity. If the overall gain is less than unity, the circuit will not oscillate; if the overall gain is greater than unity, the output waveform will be distorted.

As Fig. 2 shows, a Wien-bridge network is a practical way of implementing a sine-wave oscillator. The frequency-selective Wien-bridge is constructed from the R1-C1 and R2-C2 networks. Normally, the Wien bridge is symmetrical, so that $C1 = C2 = C$ and $R1 = R2 = R$. When that condition is met, the phase relationship between the output and input signals varies from -90° to $+90^\circ$, and is precisely 0° at a center frequency, f_0 , which can be calculated using this formula:

$$f_0 = 1/(2\pi CR)$$

Op-amp oscillators give good vibrations.

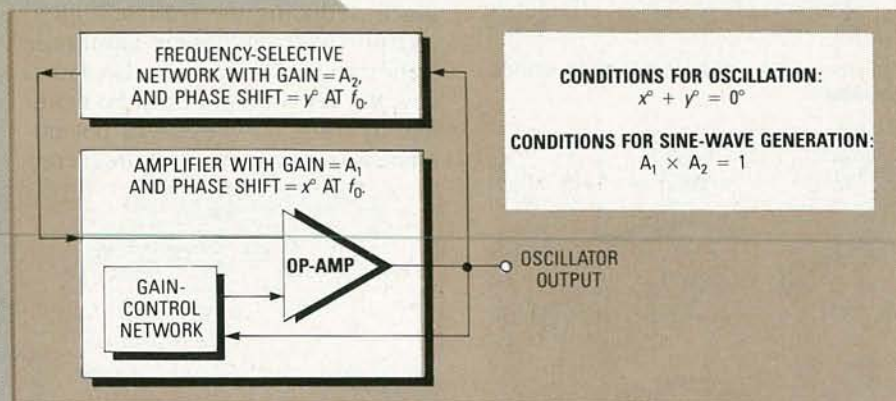


FIG. 1—STABLE SINE-WAVE OSCILLATION requires a zero phase shift between the input and output, and an overall gain of 1.

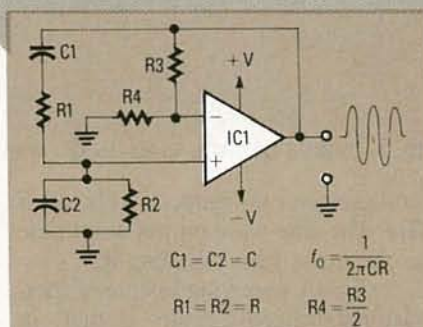


FIG. 2—BASIC WEIN-BRIDGE sine-wave oscillator.

The Wien network is connected between the op-amp's output and the non-inverting input, so that the circuit gives zero overall phase shift at f_0 , where the voltage gain is 0.33; therefore, the op-amp must be given a voltage gain of 3 via feedback network R3-R4, which gives an overall gain of unity. That satisfies the basic requirements for sine-wave oscillation. In practice, however, the ratio of R3 to R4 must be carefully adjusted to give the overall voltage gain of precisely unity, which is necessary for a low-distortion sine wave.

Op-amps are sensitive to temperature variations, supply-voltage fluctuations, and other conditions that cause the op-amp's output voltage to vary. Those voltage fluctuations across components R3-R4 will also

cause the voltage gain to vary. The feedback network can be modified to give automatic gain adjustment (to increase amplifier stability) by replacing the passive R3-R4 gain-determining network with a gain-stabilizing circuit. Figures 3 through 7 show practical versions of Wien-bridge oscillators having automatic amplitude stabilization.

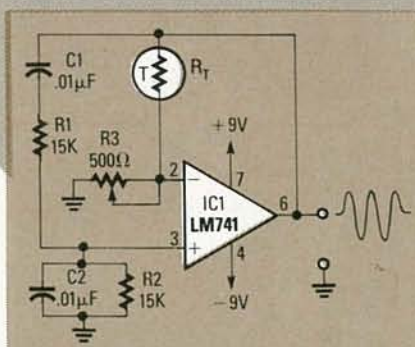


FIG. 3—THERMISTOR-STABILIZED 1-kHz Wien-bridge oscillator.

Thermistor stabilization

Figure 3 shows a 1-kHz fixed-frequency oscillator. The output amplitude is stabilized by a Negative Temperature Coefficient (NTC) thermistor R_T which, together with R3 forms a gain-determining feedback network. The thermistor is heated by the mean power output of the op-amp.

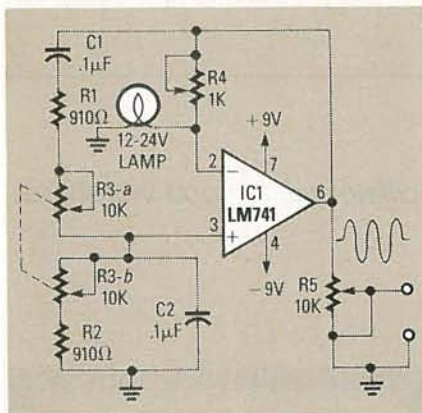


FIG. 4—LAMP-STABILIZED Wien-bridge oscillator.

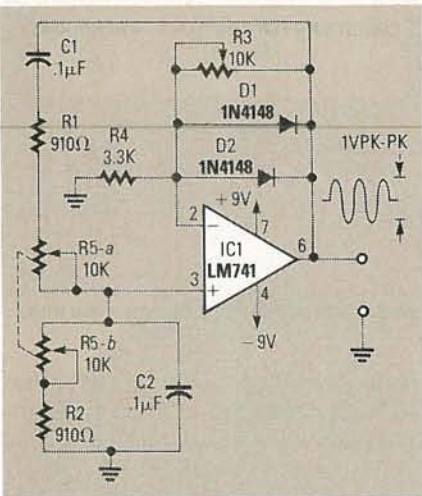


FIG. 5—DIODE-REGULATED Wien-bridge oscillator.

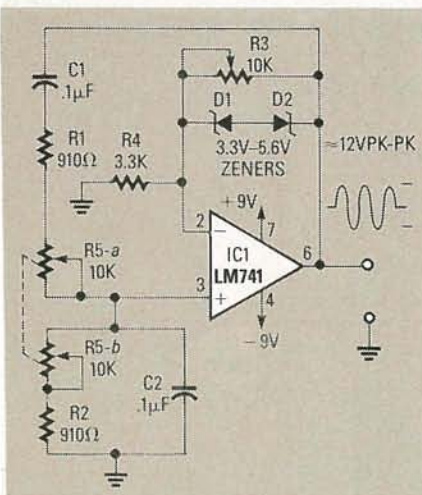


FIG. 6—ZENER-REGULATED Wien-bridge oscillator.

The desired feedback thermistor resistance value is triple that of R3, so the feedback gain is $\times 3$. When the feedback gain is multiplied by the frequency network's gain of 0.33, the overall gain becomes unity. If the oscillator output amplitude starts to rise, R_T heats up and reduces its resistance, thereby automatically reducing

the gain of the circuit, which stabilizes the amplitude of the output signal.

An alternative method of thermistor stabilization is shown in Fig. 4. In that case, a low-current lamp is used as a Positive Temperature Coefficient (PTC) thermistor, and is placed in the lower part of the gain-determining feedback network. If the output amplitude increases, the lamp heats up thereby increasing its resistance, reducing the feedback gain, and providing automatic amplitude stabilization. That circuit also shows how the Wien network can be modified by using a twin-ganged potentiometer to make a variable-frequency

peak-to-peak output of each circuit is roughly double the breakdown voltage of its diode regulator element.

In Fig. 5, the diodes start to conduct at 500 mV, so the circuit gives an output of about 1-volt peak-to-peak. In Fig. 6, the Zener diodes D1 and D2 are connected back-to-back, and may have values as high as 5 to 6 volts, giving a p-p (peak-to-peak) output of about 12 volts. Each circuit is set up by adjusting R3 for the maximum value (minimum distortion) at which oscillation can be maintained across the frequency band.

The frequency range of Wien-bridge oscillators can be altered by changing the C1 and C2 values; in-

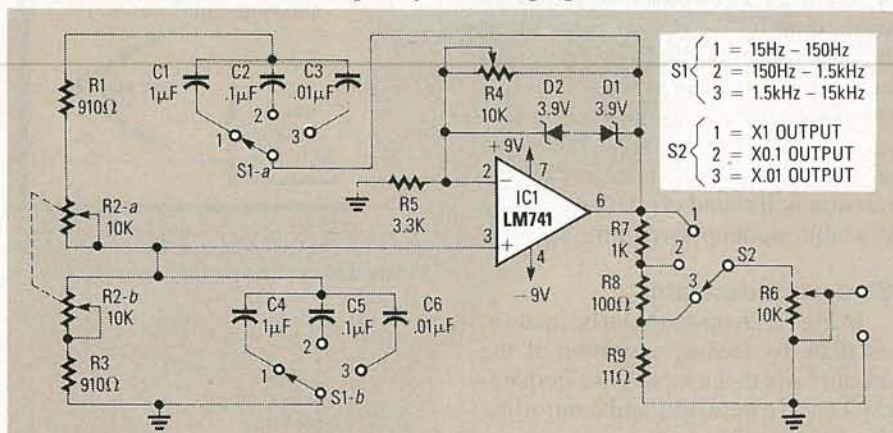


FIG. 7—THREE DECADE 15 Hz-15 kHz Wien-bridge oscillator.

oscillator over the range 150 Hz to 1.5 kHz. The sine-wave output amplitude can be made variable using R5.

A slightly annoying feature of thermistor-stabilized circuits is that, in variable-frequency applications, the output amplitude of the sine wave tends to "jitter" or "bounce" as the frequency control potentiometer is swept up and down its range.

Diode stabilization

The jitter problem of variable-frequency circuits can be minimized by using the circuits of Figs. 5 or 6, which rely on the onset of diode or Zener conduction for automatic gain control. In essence, R3 is for a circuit gain slightly greater than unity when the output is close to zero, causing the circuit to oscillate; as each half-cycle nears the desired peak value, one of the diodes starts to conduct, which reduces the circuit gain, automatically stabilizing the peak amplitude of the output signal. That "limiting" technique typically results in the generation of 1% to 2% distortion on the sine-wave output. The maximum

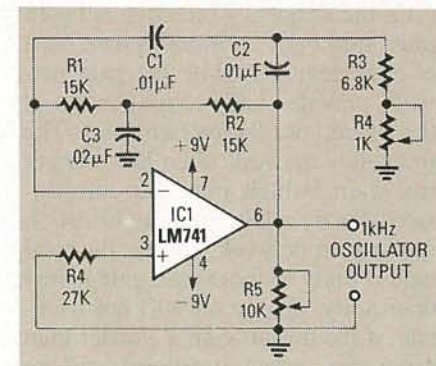


FIG. 8—1-kHz TWIN-T oscillator.

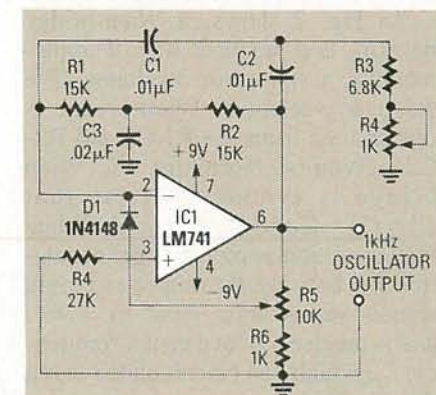


FIG. 9—DIODE-REGULATED 1-kHz twin-T oscillator.

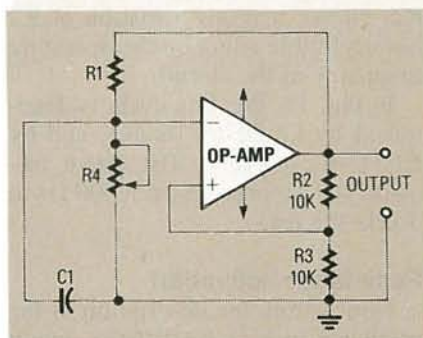


FIG. 10—RELAXATION SQUARE-WAVE oscillator.

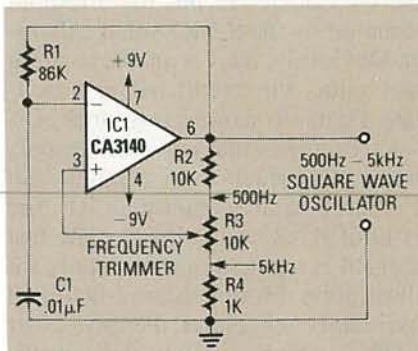


FIG. 11—500 Hz-5 kHz SQUARE-WAVE oscillator.

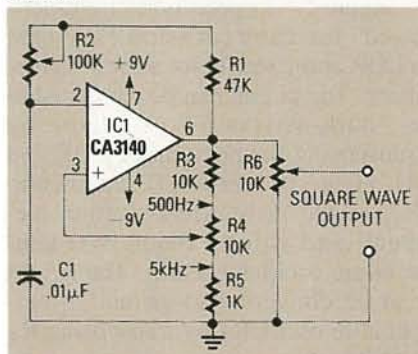


FIG. 12—IMPROVED 500 Hz-5 kHz square-wave oscillator.

creasing C1 and C2 by a decade reduces the output frequency by a decade. Figure 7 shows the circuit of a variable-frequency Wien oscillator that covers the range 15 Hz to 15 kHz in three switched-decade ranges. The circuit uses Zener-diode amplitude regulation, and its output is adjustable by both switched and fully-variable attenuators. Notice that the maximum useful operating frequency is restricted by the slew-rate limitations of the op-amp. The limit is about 25 kHz using a LM741 op-amp, or about 70 kHz using a CA3140.

Twin-T oscillators

Another way of designing a sine-wave oscillator is to wire a twin-T network between the output and input of an inverting op-amp, as shown in Fig. 8. The twin-T network comprises

R1-R2-R3-R4 and C1-C2-C3. In a "balanced" circuit, those components are in the ratios $R1 = R2 = 2(R3 + R4)$, and $C1 = C2 = C3/2$. When the network is perfectly balanced, it acts as a notch filter that gives zero output at a center frequency (f_0), a finite output at all other frequencies, and the phase of the output is 180° inverted. When the network is slightly unbalanced by ad-

operation due to the difficulties of varying three or four network components simultaneously.

Square-wave generator

An op-amp can be used to generate square-waves by using the relaxation oscillator configuration of Fig. 10. The circuit uses dual power supplies, and the op-amp output switches alternately between positive and negative

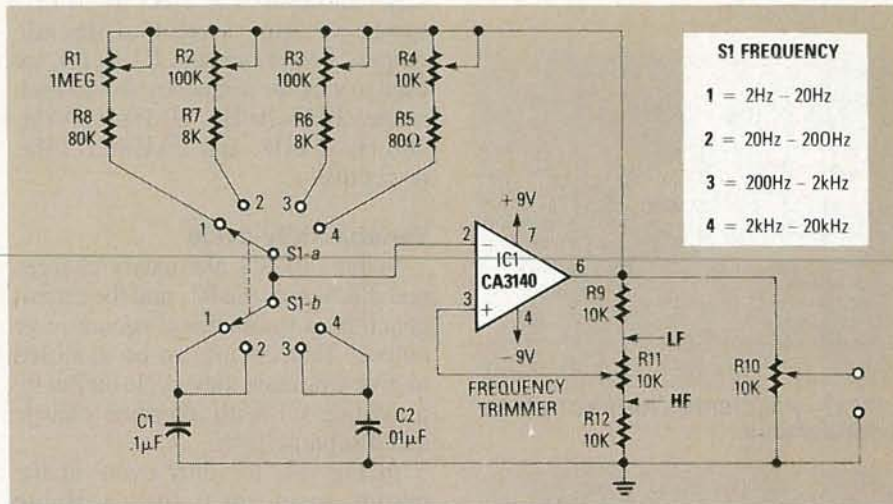


FIG. 13—FOUR DECADE 2 Hz-20 kHz SQUARE-WAVE generator.

justing R4, the network will give a minimal output at f_0 .

By critically adjusting R4 to slightly unbalance the network, the twin-T gives a 180° inverted phase shift with a small-signal f_0 . Because the inverting op-amp also causes a 180° input-to-output phase shift, there is zero overall phase inversion as seen at the inverting op-amp input, and the circuit oscillates at a center frequency of 1 kHz. In practice, R4 is adjusted so that oscillation is barely sustained, and under that condition the sine wave has less than 1% distortion.

Figure 9 shows an alternative method of amplitude control, which results in slightly less distortion. Here, D1 provides a feedback signal via potentiometer R5. That diode reduces the circuit gain when its forward voltage exceeds 500 mV. To set up the circuit, first set R5 for maximum resistance to ground, then adjust R4 so that oscillation is just sustained. Under those conditions, the output signal has an amplitude of about 500 mV p-p. Further R5 adjustment enables the output signal to be varied between 170 mV and 300-mV RMS.

Note that twin-T circuits make good fixed-frequency oscillators, but are not suitable for variable-frequency

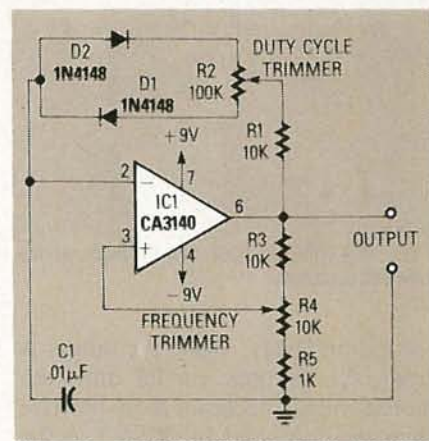


FIG. 14—SQUARE-WAVE GENERATOR with variable duty-cycle, and frequency.

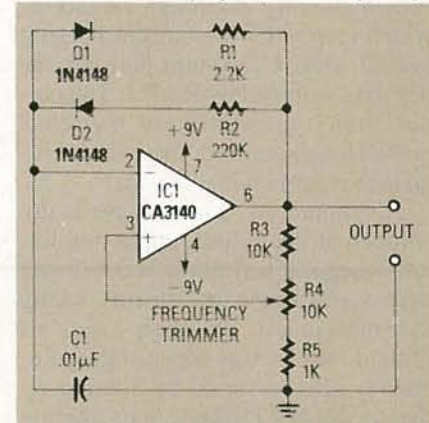


FIG. 15—VARIABLE FREQUENCY narrow-pulse generator.

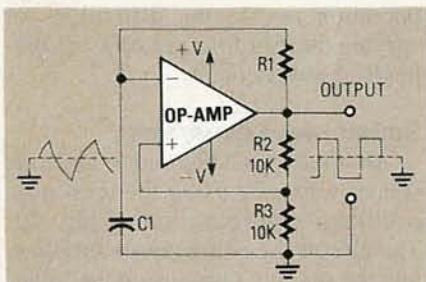


FIG. 16—RESISTANCE-ACTIVATED relaxation oscillator.

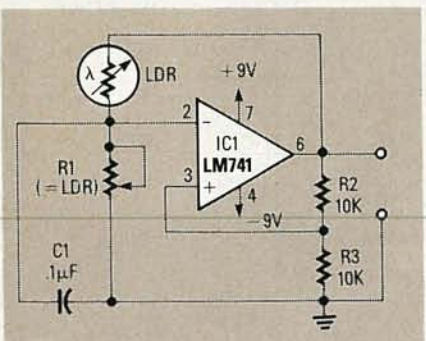


FIG. 17—PRECISION LIGHT-ACTIVATED oscillator/alarms.

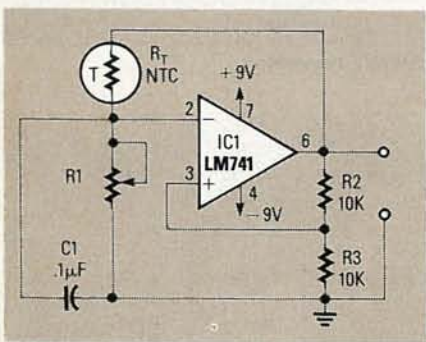


FIG. 18—PRECISION over-temperature oscillator/alarms

saturation levels. When the output is high, C1 charges via R1 until the stored voltage becomes more positive than the value set by R2-R3 at the non-inverting input. The output then regeneratively switches negative, which causes C1 to start discharging via R1 until C1 voltage falls to the negative value set by R2-R3. The output then regeneratively switches positive again, and the whole sequence repeats *ad infinitum*.

A symmetrical square wave is developed at the output, and a non-linear triangular waveform is developed across C1; those waveforms swing symmetrically on both sides of ground. Notice that the operating frequency can be varied by altering either the R1 or C1 values, or by altering the R2-R3 ratios, which makes that circuit quite versatile.

Figure 11 shows how to design a practical 500 Hz to 5-kHz square-wave generator, with frequency variations obtained by altering the attenuation ratio of R2-R3-R4. Figure 12 shows how to improve Fig. 11 by using R2 to preset the range of frequency control R4, and by using R6 as an output amplitude control.

Figure 13 shows how to design a general purpose square-wave generator that covers the 2 Hz to 20-kHz range in four switched-decade ranges. Potentiometers R1 to R4 are used to vary the frequency within each range: 2 Hz–20 Hz, 20 Hz–200 Hz, 200 Hz–2 kHz, and 2 kHz–20 kHz, respectively.

Variable duty-cycle

In Fig. 10, C1 alternately charges and discharges via R1, and the circuit generates a symmetrical square-wave output. That circuit can be modified to give a variable duty-cycle output by providing C1 with alternate charge and discharge paths.

In Fig. 14, the duty cycle of the output waveform is fully variable from 11:1 to 1:11 via R2, and the frequency is variable from 650 Hz to 6.5 kHz via R4. The circuit action is such that C1 alternately charges through R1-D1 and the bottom of R2, and discharges through R1-D2 and the top of

R2. Notice that any variation of R2 has negligible effect on the operating frequency of the circuit.

In Fig. 15, the duty cycle is determined by C1-D1-R1 (mark), and by C1-D2-R2 (space). The pulse frequency is variable between 300 Hz to 3 kHz via R4.

Resistance activation

Notice from the description of the oscillator in Fig. 10 that the output changes state at each half cycle when the C1 voltage reaches the threshold value set by the R2-R3 voltage divider. Obviously, if C1 is unable to attain that value, the circuit will not oscillate. Figure 16 shows a resistance activated oscillator that will oscillate *only* when R4, which is in parallel with C1, has a value greater than R1. The ratio of R2:R3 must be 1:1. The fact that R4 is a potentiometer is only for illustration. Most resistance-activated oscillators use either thermistors or LDR's, which simulate the potentiometer action.

Figure 17 is a precision "light-activated" oscillator (or alarm), and uses a LDR as the resistance activating element. The circuit can be converted to a "dark-activated" oscillator by transposing the position of LDR and R1. Figure 18 uses a NTC thermistor, R_T, as the resistance-activating element, and is a precision over-temperature oscillator/alarms. The circuit can be converted to an under-temperature oscillator by transposing R_T and R1.

The LDR or R_T can have any resistance in the range from 2000 ohms to 2 megohms at the required trigger level, and R1 must have the same value as the activating element at the desired trigger level. R1 sets the trigger level; the C1 value can be altered to change the oscillation frequency.

Triangle/square generation

Figure 19 shows a function generator that simultaneously produces a

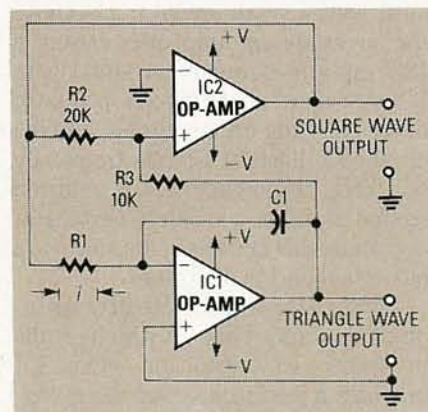


FIG. 19—BASIC FUNCTION GENERATOR for both triangular, and square waves.

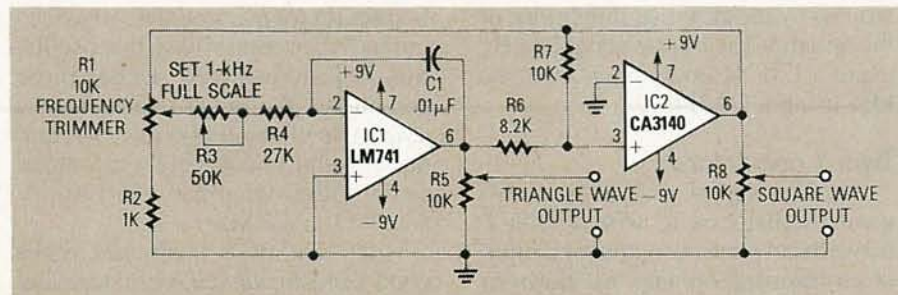


FIG. 20—100 Hz-1 kHz FUNCTION GENERATOR for both triangular, and square waves.

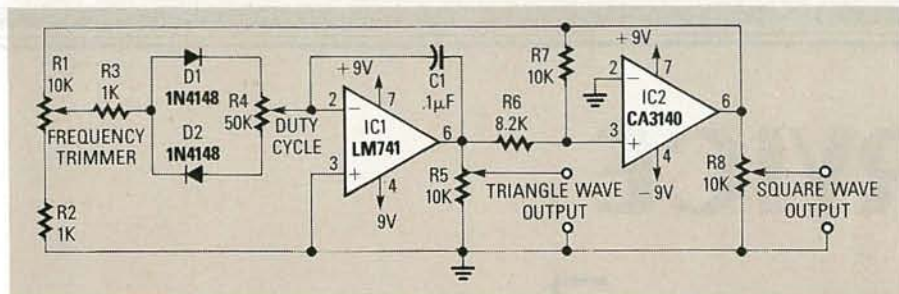


FIG. 21—100 Hz–1 kHz FUNCTION GENERATOR with variable slope and duty cycle.

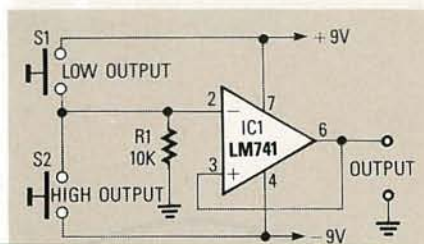


FIG. 22—BI-STABLE with simple manual triggering.

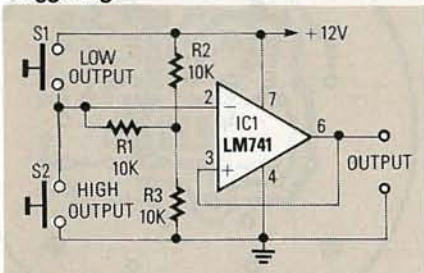


FIG. 23—SINGLE SUPPLY BI-STABLE.


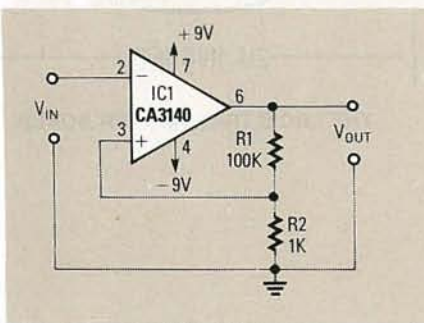


FIG. 24—SCHMITT TRIGGER prevents output oscillations caused by triggering off a slow sine-wave.

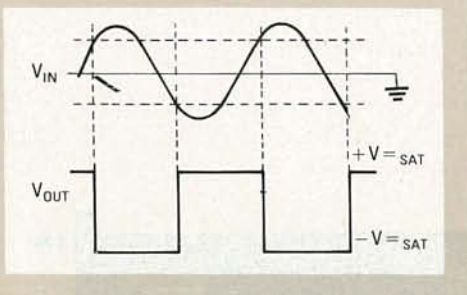

linear triangular wave and a square wave using two op-amps. Integrator IC1 is driven from the output of IC2, where IC2 is wired as a voltage comparator that's driven from the output of IC1 via voltage divider R2-R3. The square-wave output of IC2 switches alternately between positive and negative saturation levels.

Suppose, initially, that the output of IC1 is positive, and that the output of IC2 has just switched to positive saturation. The inverting input of IC1 is at virtual ground, so a current I_{R1} equals $+V_{SAT}/R1$. Because R1 and C1 are in series, I_{R1} and I_{C1} are equal.

Yet, in order to maintain a constant current through a capacitor, the voltage across that capacitor must change linearly at a constant rate. A linear voltage ramp therefore appears across C1, causing the output of IC1 to start to swing down linearly at a rate of 1/C1 volts per second. That output is fed via the R2-R3 divider to the non-inverting input of IC2.

Consequently, the output of IC1 swings linearly to a negative value until the R2-R3 junction voltage falls to zero volts (ground), at which point IC2 enters a regenerative switching phase where its output abruptly goes to the negative saturation level. That reverses the inputs of IC1 and IC2, so IC1 output starts to rise linearly until it reaches a positive value that causes the R2-R3 junction voltage to reach

the zero-volt reference value, which initiates another switching action.

The peak-to-peak amplitude of the linear triangular-waveform is controlled by the R2-R3 ratio. The frequency can be altered by changing either the ratios of R2-R3, the values of R1 or C1, or by feeding R1 from the output of IC2 through a voltage divider rather than directly from op-amp IC2 output.

In Fig. 20, the current input to C1 (obtained from R3-R4) can be varied over a 10:1 range via R1, enabling the frequency to be varied from 100 Hz to 1 kHz; resistor R3 enables the full-

scale frequency to be set to precisely 1 kHz. The amplitude of the triangular waveform is fully variable via R5, and the square wave via R8. The output generates symmetric waveforms, since C1 alternately charges and discharges at equal current values determined by R3-R4.

Figure 21 shows how to modify Fig. 20 to make a variable symmetry ramp/rectangular generator, where the slope of the ramp and duty cycle is variable via R4. C1 alternately charges through R3-D1 and the upper half of R4, and discharges through R3-D2 and the lower half of R4.

Switching circuits


Figure 22 shows the connections for making a manually triggered bi-stable circuit. Notice that the inverting terminal of the op-amp is tied to ground via R1, and the non-inverting terminal is tied directly to the output. Switches S1 and S2 are normally open. If switch S1 is briefly closed, the op-amp inverting terminal is momentarily pulled high, and the output is driven to negative saturation; consequently, when S1 is released again, the inverting terminal returns to zero volts, but the output and the non-inverting terminal remains in negative saturation. The output remains in that state until S2 is briefly closed; that switches the output to a stable positive saturation state until S1 is closed again.

Figure 23 shows how Fig. 22 can be modified for operation from a single-ended power supply.


Finally, Fig. 24 shows how to connect an op-amp as a Schmitt trigger, which can be used to convert a sine wave into a square wave. Suppose, initially, that the op-amp's output is at a positive saturation value of 8 volts. Under that condition the R1-R2 divider feeds a positive reference voltage about 80 mV to the non-inverting input. Consequently, the output remains in that state until the input voltage rises to a value equal to 80 mV. The op-amp's output will then switch regeneratively to a negative saturation level of -8 volts, thereby feeding a reference voltage of -80 mV's to the non-inverting input. The output remains in that state until the input falls to -80 mV; at that point, the output regeneratively switches back to the positive saturation level. The switching levels can be altered by changing the R1 value.

R-E


PC SERVICE

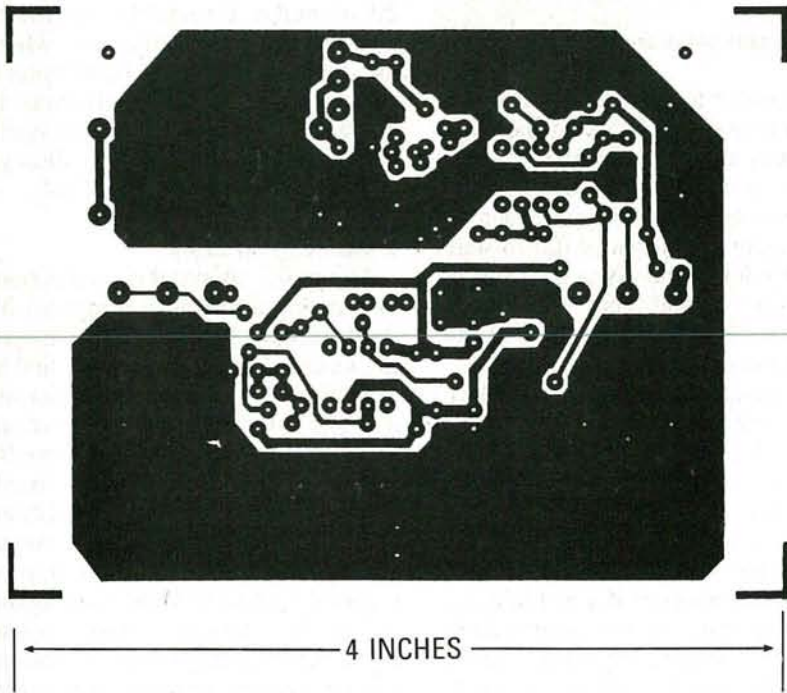

THE LBC'S RECEIVER BOARD.

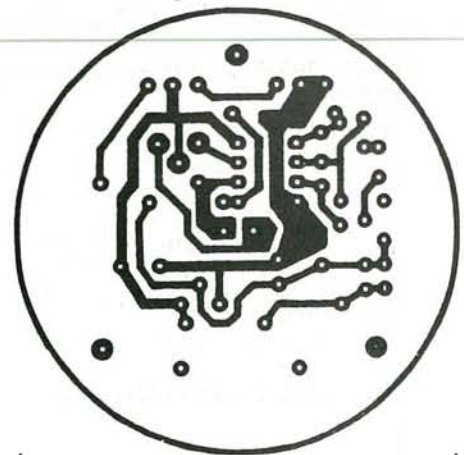

THE LBC'S TRANSMITTER BOARD.

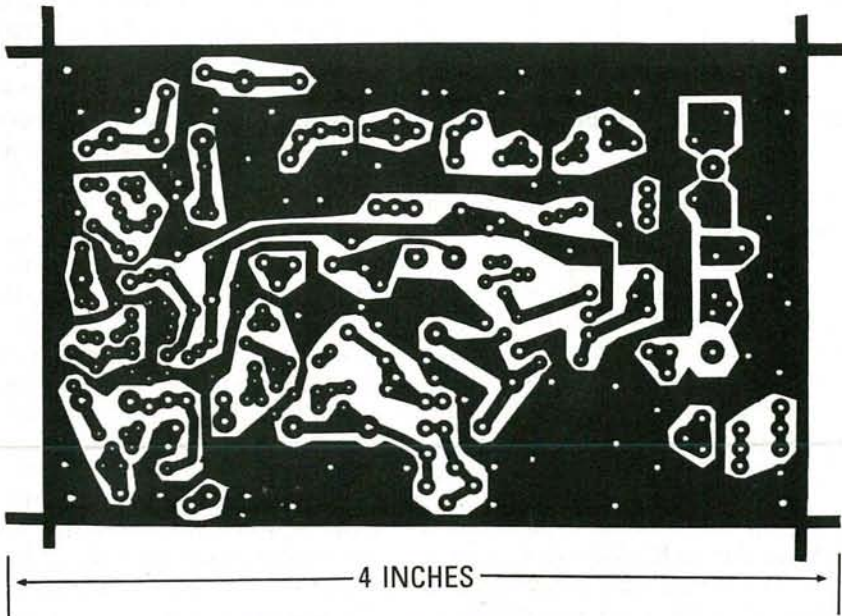

FOIL SIDE OF TV TRANSMITTER.

MORE PC SERVICE ON PAGE 84

SERVICING

REPAIRING SICK AM/FM receivers is generally an easy, straightforward job; that can all change when tackling the newer digitally tuned models. It's bad enough having to work with densely packed circuitry sprouting unfamiliar components, no product documentation, and a matchbook-size schematic; now you have to cope with fixing digitally tuned (synthesized) radios, too.


But don't despair; we'll get you started in servicing those radios. You'll learn about synthesizer circuitry and the most commonly used IC's. We'll also take a look at some troubleshooting techniques that might be new to you.

Synthesizer blues

A lot of technicians have sung the synthesizer blues. Here are some real-life reasons why: One receiver had an annoying whine in the audio on AM. The sound got louder when a station was tuned in. Power-supply problem? Not quite; it turned out to be an open capacitor in the loop filter. Another radio worked on AM but not on FM. Bad FM circuitry? Nope, a dead prescaler IC. And finally a third receiver was dead except for a rushing noise on both AM and FM. Bad power supply or any part in the synthesizer circuitry? You're getting close. That radio had a bad voltage regulator, which powered the synthesizer's controller IC. Let's examine the parts just mentioned a little closer, along with their typical

symptoms when they fail.

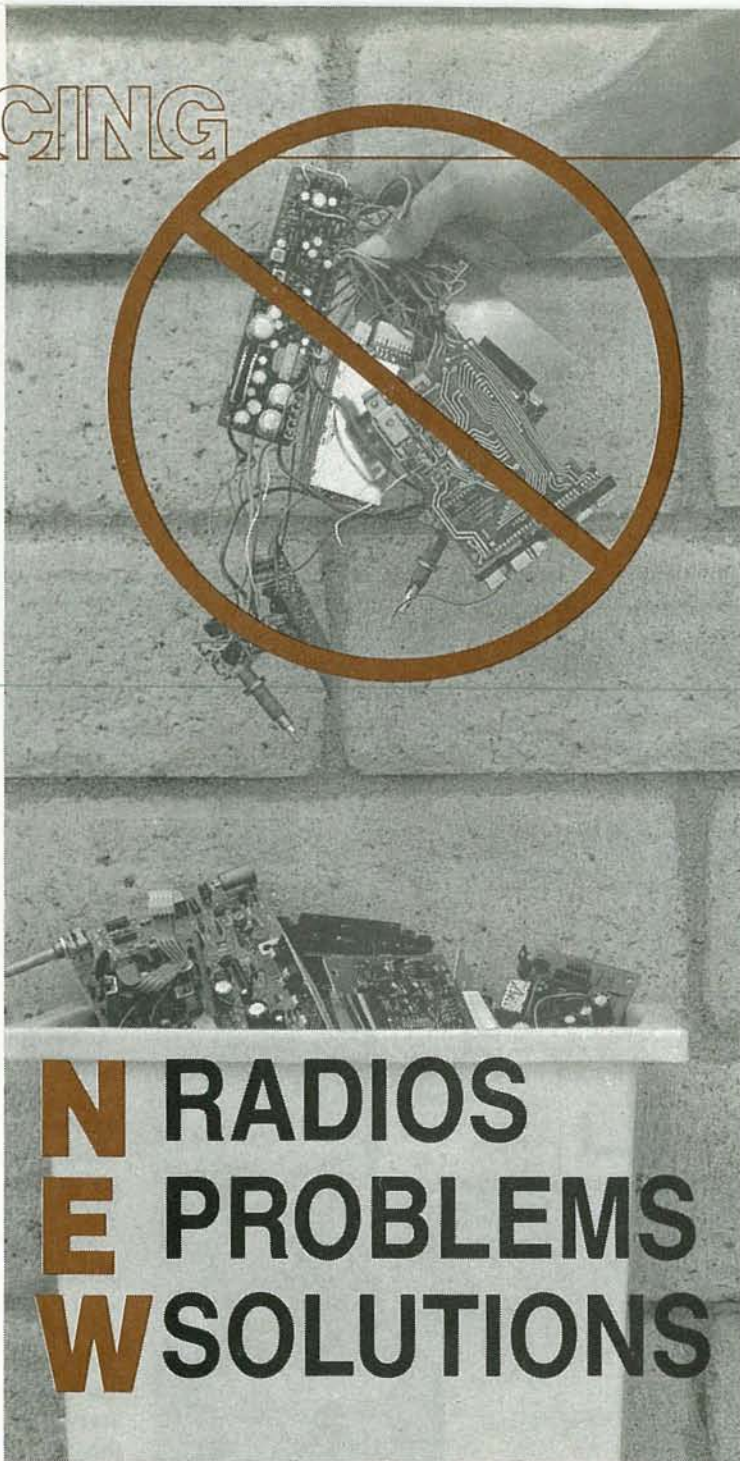Actually, the toughest symptom to troubleshoot is the "receives no AM or FM stations," because that fault could be in the synthesizer, the tuner, or even the power supply. Good news! Since the early 1970's, synthesizer ra-



NEW RADIOS PROBLEMS WITH SOLUTIONS

*Stop! Don't throw out that radio.
We'll show you how to fix the new
digitally tuned receivers.*

GARY McCLELLAN

dios have gone from PC boards loaded with IC's to a four-IC set. That means that troubleshooting today's circuits will be a lot easier than with the earlier monsters, although the broken-radio symptoms remain the same.

Radio circuitry

Digital tuning offers the advantage of drift-free reception along with such features as station presets and signal-seeking tuning. That makes radios easier for consumers to use, and highly profitable for the manufacturers. Modern car radios are a perfect example of synthesizer radios using presets; that's when you just push a button and the station you preset is automatically tuned in. Of course, the old-fashioned pushbutton car radios worked fine, but the manufacturer had the added costs of manually installing the mechanical pushbuttons along with its pulleys and sliding pointer. Quality control then depended on how the assembler felt that day. Now a machine just picks up an IC and solders it in place

Figure 1 shows a typical synthesized AM/FM stereo receiver. Notice that the AM/FM front end uses conventional super-hetodyne circuitry—but with a few modifications. Instead of the familiar mechanical tuning capacitor, a set of varactor (variable capacitor) diodes control the tuning frequency. Varactors change their capacitance in direct proportion to the driving voltage. The

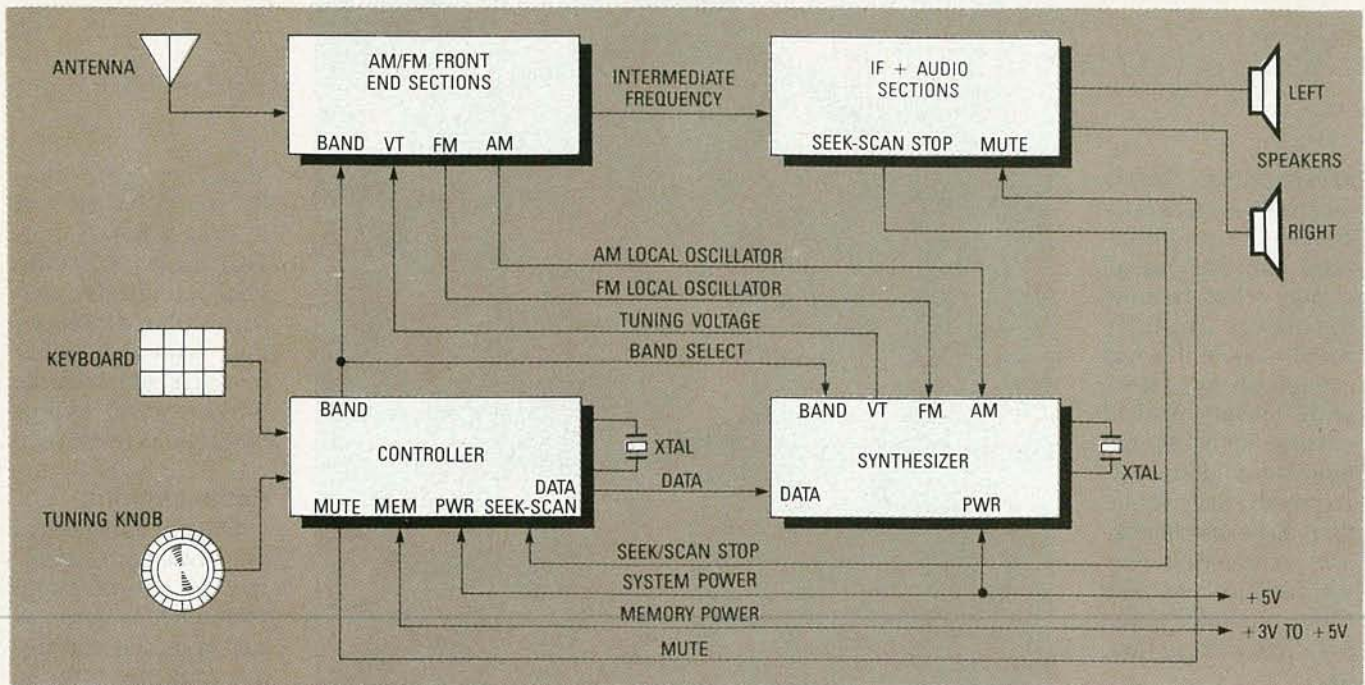


FIG. 1—DIGITALLY TUNED RADIO showing the control lines between the AM/FM front end, controller, prescaler, synthesizer, IF and audio sections, LED display, and keyboard.

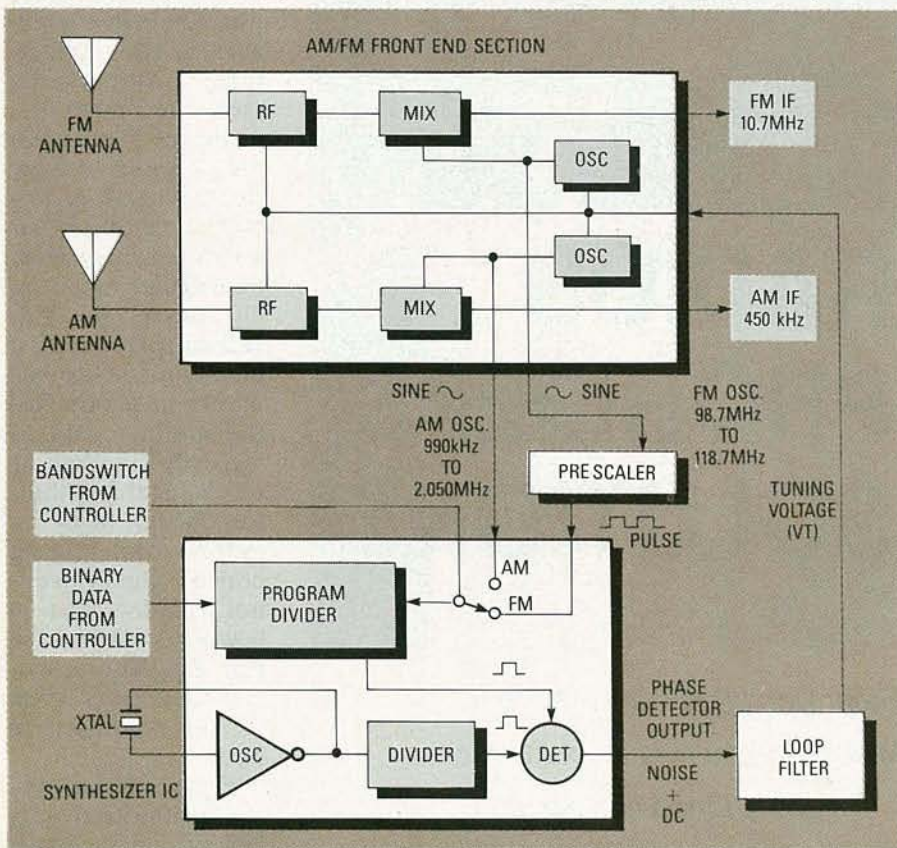


FIG. 2—THE RADIO'S SYNTHESIZER works closely with the AM/FM front end.

stand that the digital display does *not* read the frequency that the receiver is tuned to; it is the frequency entered into the controller. That's an important fact to know when it comes to radio-tuning problems. The **BAND-SELECT** output selects AM or FM operation. Incidentally, if the receiver contains a clock, that function is also performed by the controller. Last, the controller also includes a **MUTE** output, which silences the radio during the tuning interval.

Deluxe receivers may contain an additional pushbutton called seek/scan stop tuning; when depressed, the controller forces the receiver to scan the radio band until a station is found. The radio's IF section then drives the **SEEK/SCAN STOP** line low, which stops the controller at the received station.

Two power sources are used to run the controller. Memory power is derived from batteries, or a large-value capacitor charged by receiver operation. System power (usually a 5-volt supply) runs the rest of the controller circuitry while the receiver is operating, including the display.

As shown in Fig. 2, the synthesizer IC accepts AM and FM local-oscillator signals from the front end. After receiving a divided-down signal from either local oscillator, a phase detector compares it with a signal derived from a crystal oscillator whose frequency is typically 10 kHz. The phase-detector output is an analog

synthesizer monitors the AM- or FM-local oscillator and varies V_T , the tuning voltage that drives the varactor diodes, thereby controlling the receiver frequency.

Unique to digitally tuned receivers is the controller, which accepts inputs from the keyboard (presets, AM, FM,

Seek, Scan) or the tuner switch. The inputs are converted into a binary code that drives the synthesizer IC via the data lines—essentially, it tells the synthesizer what to do. Notice that the **DATA** output from the controller drives the synthesizer, and is also decoded for the digital display. Under-

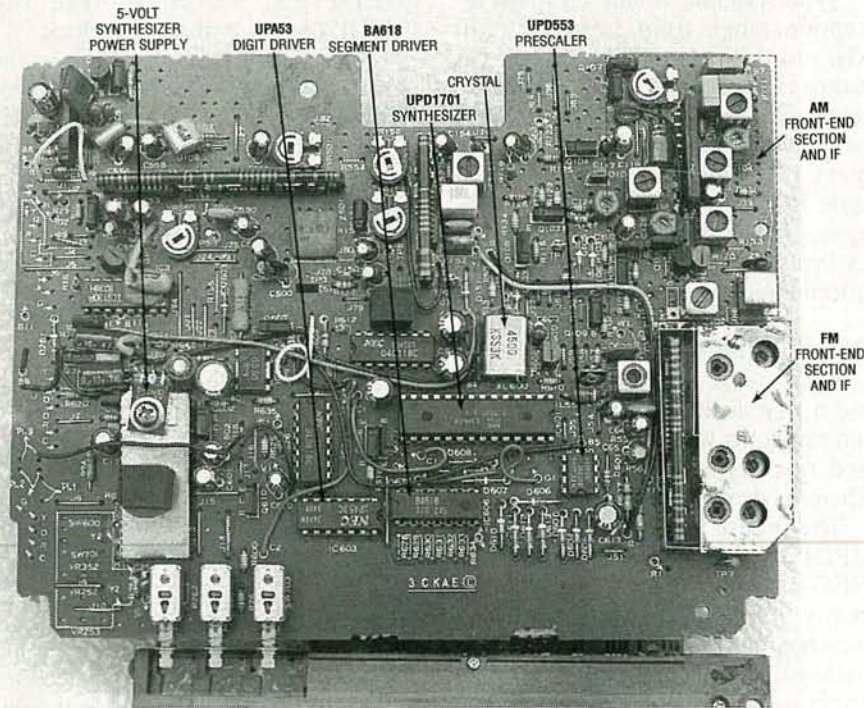


FIG. 4—THIS IS WHAT THE INSIDE of a digitally tuned radio looks like.

tuning feature found in car radios connects exactly like the keyboard. The tuning assembly uses two cam-driven SPST switches. One switch closes momentarily to tune down, and the other closes momentarily to tune up—a simple, but clever device.

The phase-detector output is taken from pin 1 of IC1, through a loop filter consisting of a Darlington transistor, and a few capacitors and resistors. Sometimes you'll find a FET transistor combination used instead. Some high-end receivers substitute op-amps, in their loop filters, for supposedly better results.

The AM/FM tuner may be a collection of discrete components on the board, or more likely a module from Alps or Mitsumi Corporation. It provides buffered local-oscillator outputs on the order of 100–400 mV, and accepts the tuning voltage. Some tuner modules also include IF circuitry; in that case, they can have a seek/scan stop output, and audio-muting provisions.

The increased desire for more presets has forced receiver manufacturers to return to separate controller and synthesizer IC combinations. Chrysler, for example, uses a National COP-series controller and a DS8908 synthesizer-IC set in their recent-model car radios. Headphone

portables use a single IC for controller, synthesizer, and display driver functions—available from Sharp or NEC. Should one of those parts fail, you can buy it *only* from the receiver manufacturer, and that often makes repairs uneconomical.

Troubleshooting techniques

Now let's look at some winning troubleshooting procedures. Well, OK, nothing can replace good ol' factory training, full service data, plus five-years experience, but these tips will get you off to a good start. Figure 4 is a typical digitally tuned receiver that you might come across in any repair shop.

Here's the *test* procedure, which is simple enough. Before you do anything else, try all receiver controls and functions to verify and duplicate the customer's complaints. Doing that will help you avoid those problems caused by customers who have trouble using electronic equipment and may simply be confused. Other problems you want to immediately rule out include the obvious: wiring disconnected, blown fuses, and tinkering by Saturday mechanics.

Just trying the controls can uncover digital-tuning defects like stuck keyboards and intermittent switches. Clean or replace the bad part and your

work is done. Suffice to say, "Always fix the obvious problems first."

Now let's evaluate receiver problems to isolate a bad power supply or dead amplifier. Only when everything else is working should you turn your attention to the digital tuner. Many times, you'll find fixing the simple problems clears up over half of the "it won't get any stations" problems.

As you might expect, to service the digital tuner, it helps to obtain the radio's service manual from the manufacturer; at least then you'll know what voltages to expect, and can identify the parts on the board.

To troubleshoot down to the component level in a digital tuner, the following tips should be helpful:

- **The AM/FM front-end** is good if you hear a rushing sound with the volume turned up. That can be verified by connecting an antenna, and listening for any stations near 540-kHz AM or 88.1-MHz FM. If you have no local stations, try a signal generator.

- **The controller** is probably good if all keys work, and it stores the frequencies you enter. If you observe one or more bad keys, the keyboard is likely to be at fault—bridging the connections behind the bad key with a screwdriver blade will show that fault.

- **The display** has common problems like missing segments, and are usually caused by an open connection between the display and driver. Look for an unsoldered connection or broken wire.

- **The synthesizer IC** is good if you can tune in AM or FM stations. If you can't get FM, check the prescaler circuit. If you can't get AM, suspect either the local oscillator output from the AM/FM front end, or the synthesizer IC itself.

- **The loop filter** is good if you can tune in AM stations across the entire band, without a whine in the sound.

- **The prescaler** is good if you can tune in FM stations—either it works or it doesn't.

- **The power supply** is a common trouble spot. Typically that defect is obvious because the display is not lit.

- Test or substitute the major components in the area you isolated. Look out for the little things like broken parts and unsoldered connections.

Next time we'll dig deeper into receiver problems. And we'll top that off with tips on where to obtain those tough-to-find parts. R-E

CHOOSING THE RIGHT SHORTWAVE ANTENNA

Boost your shortwave reception using a wire antenna—and a little know-how.

JOSEPH J. CARR

MOST ARTICLES ON HIGH-FREQUENCY antennas are about transmitting, but there's also a body of knowledge purely about receiving antennas. Who can benefit from knowing about receiving antennas? On top of the list is the shortwave listener (SWL); a close second is the amateur radio operator who wants a separate receiving antenna to pull in those weak DX (distant) stations.

Reciprocity

Antennas possess a property called *reciprocity*. That's a fancy way of saying that antennas work as well on receive as they do on transmit; that's usually taken for granted. For example, many hams use transceivers, which commonly use the same antenna for both transmitting and receiving. A half-wavelength dipole that works well as a transmitting antenna on 20 meters works equally well as a receiving antenna on 20 meters. Antenna properties like directivity, gain, angle of radiation, and polarization do not vary between transmit and receive at a given frequency. (Bear in mind, however, that simple wire an-



tennas suitable for reception of shortwave signals are not necessarily suitable for transmitting.)

Antenna properties

Assuming that you want more than a simple longwire antenna (which will be discussed shortly), you will want to explore the antenna properties best suited to your monitoring application. Is the antenna to be fixed or rotatable? Do you want omnidirectional or directional reception? In which polarized plane? What about gain?

Because receiving antennas exhibit the same properties as transmitting antennas, any directional transmitting antennas are directional while receiving, too. Therefore, any specifications given for an antenna's transmitting characteristics can be applied

toward receiving characteristics. The common terms you'll come up against when reading antenna specifications are gain, directivity, and angle of radiation. Let's look at each.

Antenna gain stems from the fact that the directional antenna can focus energy. Gain is expressed as the ratio in decibels of the power radiated in a given direction by a test antenna to the power radiated in the same direction by a reference. The two commonly used reference antennas are a dipole (which has a figure-8 radiation pattern) and a spherical point source (which is an isotropic radiator that has an omnidirectional radiation pattern). If an antenna gain is listed as 8 dB over isotropic then, in the direction specified, the radiated signal is 8 dB higher than that radiated by an isotropic antenna.

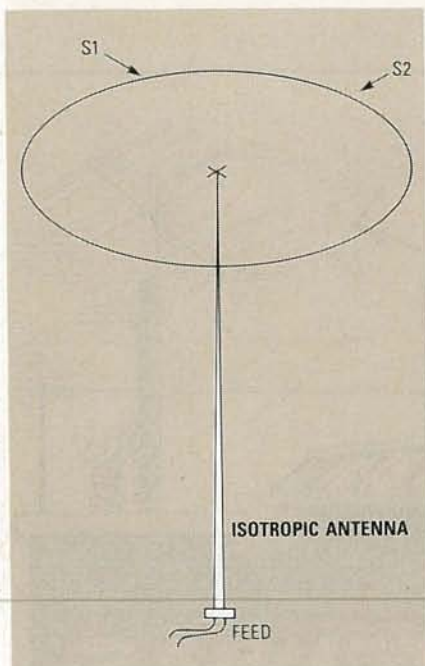


FIG. 1—AN ISOTROPIC ANTENNA is a theoretical construct that receives equally well in all directions.

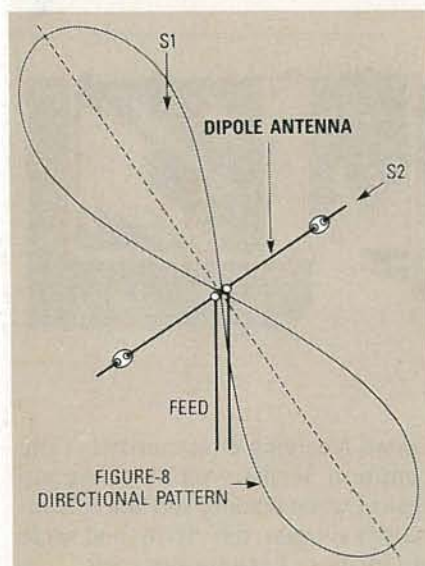


FIG. 2—A DIPOLE ANTENNA has a figure-8 directivity pattern.

So what good is antenna gain? By accumulating more signal, the apparent receiver sensitivity is increased. Note that the antenna gain does *not* create a higher powered signal, but merely increases the *apparent* signal power by focusing energy—like an electromagnetic lens—from a given direction. Note that antenna gain implies directivity.

Directivity is often taken to mean horizontal directivity. But all antennas radiate in three dimensions, so both azimuth and elevation angle of

radiation are important. Certain VHF/UHF vertical antennas are listed as “gain antennas”, yet the pattern in the horizontal direction is 360 degrees, implying omnidirectional behavior. In the vertical plane, however, lost energy is compressed into a smaller range of elevation angles, so gain occurs by refocusing energy that would have been radiated at a higher-than-useful angle.

A second application of directivity is to suppress interfering signals. On the regular AM- and FM-broadcast bands, each station is allowed a channel (called channelization), permitting receiver selectivity to overcome adjacent channel interference. But in the *high frequency* (HF) amateur radio and international broadcast bands, channelization is either nonexistent, poorly defined, or ignored altogether. In those cases, interference from adjacent channel signals can wipe out a weaker desired station.

A similar circumstance occurs in co-channel interference when both stations are on the same frequency. In Fig. 1, two 9540-kHz signals, S1 and S2, arrive at the same omnidirectional vertical antenna; both will be heard, or the stronger will drown out the weaker. In Fig. 2, a dipole is used as the receive antenna, so a little directivity is obtained. The main lobes of the dipole are wide enough to provide decent reception of S1 even though the antenna is positioned in such a way that S1 is not along the maxima line (dotted). Better yet, the position-

ing places interfering co-channel S2 in the null (off the ends of the dipole), weakening response to S2. The result is enhanced S1 reception.

The idea is not to exploit the antenna's gain to increase the response to S1, but rather to place the unwanted signal S2 into the null. Note that the notch is sharper than the peak of the main lobe. If the dipole is placed on a mast with an antenna rotator, the ability to place undesired signals in the null is increased even more.

Another antenna parameter of considerable interest is angle of radiation, which also means angle of reception. Because long-distance HF propagation is caused by skip, the angle of incidence for the signal with the ionosphere becomes extremely important. Figure 3 shows two-skip conditions from the same transmitting station. Here S1 has a high angle of incidence a_1 , so skip distance D1 is relatively short. For S2, however, the angle incidence a_2 is low, so the skip distance D2 is much longer than D1.

The angular range of effective radiation of an antenna is fixed by its design. The angle of refraction in the ionosphere is a function of ionospheric properties at the time and frequency of interest. For that reason, some well-equipped radio hobbyists use several different antennas. The radiation angle can vary with antenna height as well.

Receiver connection

It's rather naive to state, I suppose,

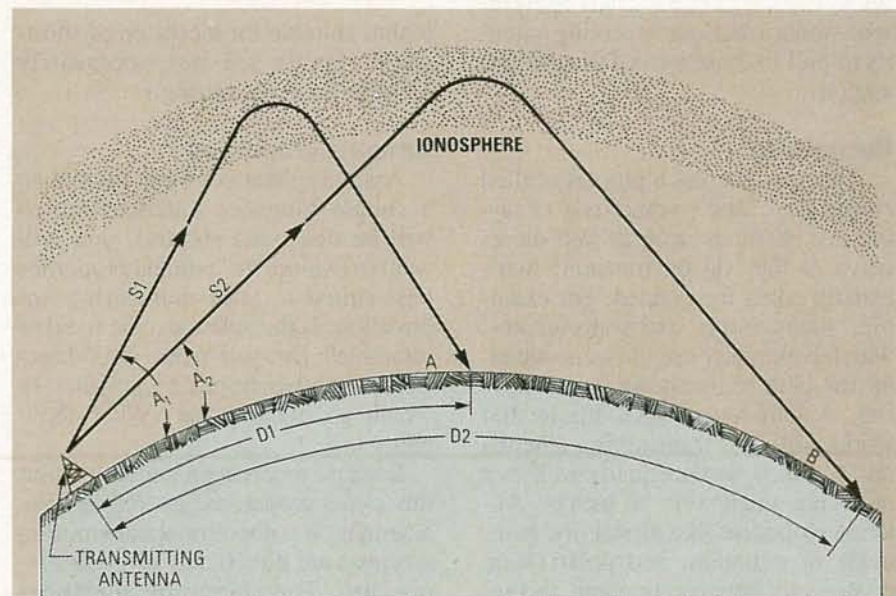


FIG. 3—THE SKIP DISTANCE OF A RADIO WAVE depends upon the angle of elevation at which it's transmitted.

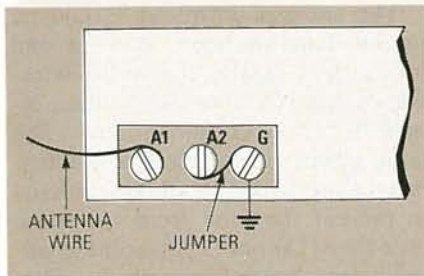


FIG. 4—A RECEIVER'S BALANCED antenna input can be converted to an unbalanced input by connecting A2 and G (ground) together.

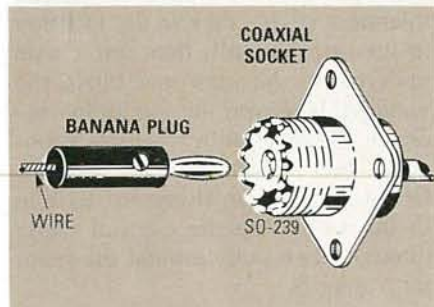


FIG. 5—USE A MINIATURE banana plug to connect your antenna's downlead wire to a standard SO-239 coaxial connector.

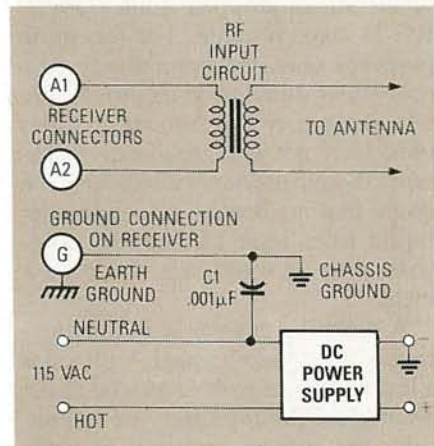


FIG. 6—MANY OLDER VACUUM-TUBE receivers use power supplies that are not isolated from the AC power line. When working on such units, *always* use a 1:1 isolation transformer—for safety.

but let's do it anyway: An antenna must be properly connected to a receiver to be effective. If your antenna uses coax, and the receiver accepts coax, simply attach the proper connector; however, in other cases, non-coaxial cable antennas are used.

There are two major forms of antenna connectors used on shortwave receivers. One uses two or three screws for wrapped wire leads or spade lugs, while the other uses some type of coaxial connector. Consider first the screw-type connector (Fig. 4).

If only two screws are found, then one is for the antenna and the other is for the ground. Those screws will be marked something like "A/G" or "ANT/GND," or with the schematic symbols for antenna and ground.

Three-screw designs are intended to accommodate balanced transmission lines such as twin-lead or ladder line. When balanced parallel lines are used, connect one lead to A1 and the other to A2. Of course, the ground terminal G is connected to Earth ground. On the other hand, for single-lead antennas, connect a jumper wire or bar (a short piece of bare No.22

also serves as the RF common. However, on older AC/DC models the neutral AC power-line wire serves as both DC common and RF-signal ground. In Fig. 6, C1 sets the chassis at RF ground potential, while isolating the DC common from the 60-Hz AC. A danger exists if either the AC plug is installed backwards, or someone wired the socket in the wall incorrectly (which often happens)!

Even if C1 is intact, you can get a nasty shock by touching the antenna ground (G or GND) terminal. The capacitive reactance of C1 is about 2.7 megohms for 60-Hz AC, so you'll get

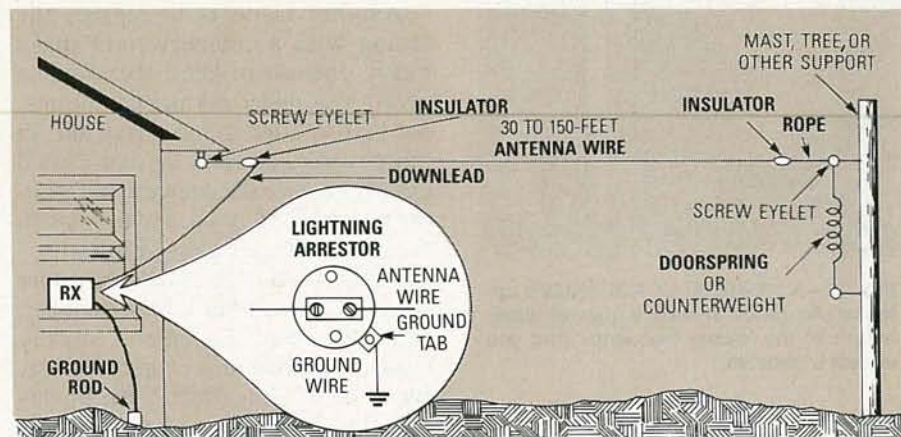


FIG. 7—HERE'S A TYPICAL LONG-WIRE INSTALLATION. Notice the insulator, rope, and spring mechanism, which helps hold the antenna steady when the wind is blowing.

solid hook-up wire) between A2 and G to convert a balanced input to unbalanced. As an interesting aside, shortwave listeners sometimes use ordinary AC-line cord (called zipcord) as a twin-lead transmission line. Zipcord has an impedance that approximates the 75-ohm impedance of a dipole.

On receivers that use an SO-239 coaxial connector, there are two techniques to connect a single-lead antenna. First, using a PL-259 mating plug, solder the antenna lead to the center conductor pin, and then screw the connectors together. An alternative that's easy enough, as shown in Fig. 5, is to attach a (miniature) banana plug to the downlead wire, and then firmly to insert that banana plug into the SO-239 receptacle.

Grounds that bite

Danger! Certain low-cost receivers, especially older vacuum-tube models, have a so called AC/DC (transformerless) internal DC power supply. On most modern receivers the DC common is the chassis, which

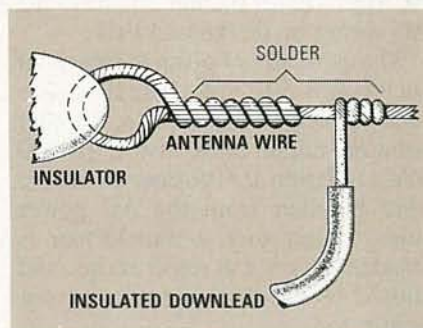


FIG. 8—A GOOD MECHANICAL connection will keep your antenna from falling down prematurely. Solder will keep the electrical connection from corroding to quickly.

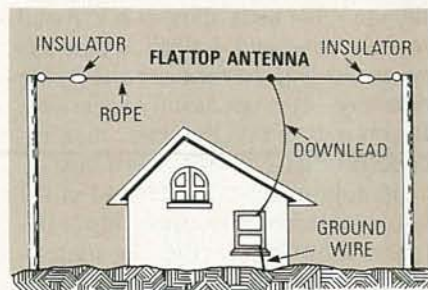


FIG. 9—A FLATTOP ANTENNA is a long wire tapped in the center.

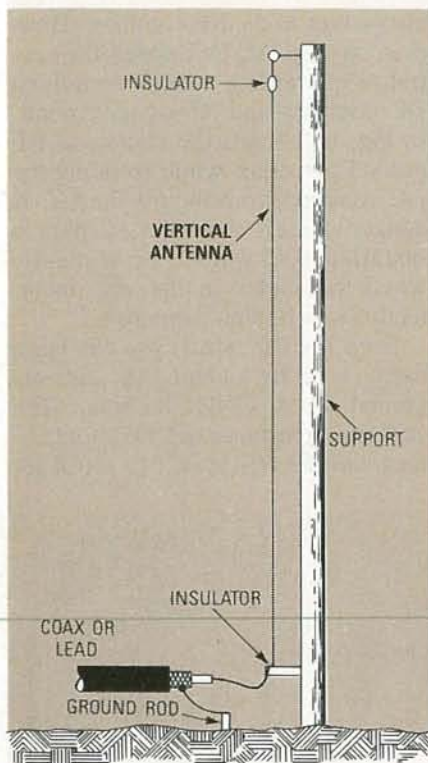


FIG. 10—A VERTICALLY POLARIZED antenna should be at least a quarter wavelength of the lowest frequency that you expect to receive.

a “bite.” But if that capacitor is shorted, as is likely on older receivers, then the bite might prove *fatal*. The problem is that a reversed polarity AC-line will set the hot line from the AC socket on the ground lead.

The usual advice given to owners of such radios is to make sure that C1 is intact before using the radio. A better solution might be to use a 110:110 VAC isolation transformer to isolate your receiver from the AC power lines. Using such a transformer is standard practice in repair shops, and should be standard practice in your house, too.

Wire antennas

Figure 7 shows the common receiving longwire. The antenna element should be 150 to 300-feet long. Although most texts show it horizontal to the ground and, indeed, a case can be made that performance is better that way—it is not strictly necessary. If you must slope the wire, then it's doubtful that you will notice any reception problems. The far end of the wire is attached to a supporting structure—a building, tree, or mast—through an insulator and rope.

Wind will cause motion in the antenna wire, and its supporting struc-

ture. Over time, the wind movement will fatigue the antenna wire and cause it to break. Also, if a big enough gust or a sustained storm comes along, then even a new antenna will either sag badly or break altogether. You can do either of two things to reduce the problem. First, as in Fig. 7, a door spring can be used to provide some variable wire slack. The spring tension is selected to be only partially expanded under normal conditions. When the wind begins to blow, the wire's tension will increase, thereby stretching the spring. Make sure that the spring does not become over-stretched, or it won't work.

Another tactic is to replace the spring with a counterweight that's heavy enough to keep the antenna nearly taut under normal conditions, but light enough to move in wind. In other words, antenna tension should exactly balance the counterweight under normal conditions, and not stretch the antenna wire excessively.

The antenna wire should be either No.12 or No.14 hard-drawn copper, or stranded wire. The latter is actually steel-core wire with a copper coating. Because of “skin effect,” RF signals only flow in the outer copper coating. Soft drawn copper wire will stretch and break prematurely, and should be avoided.

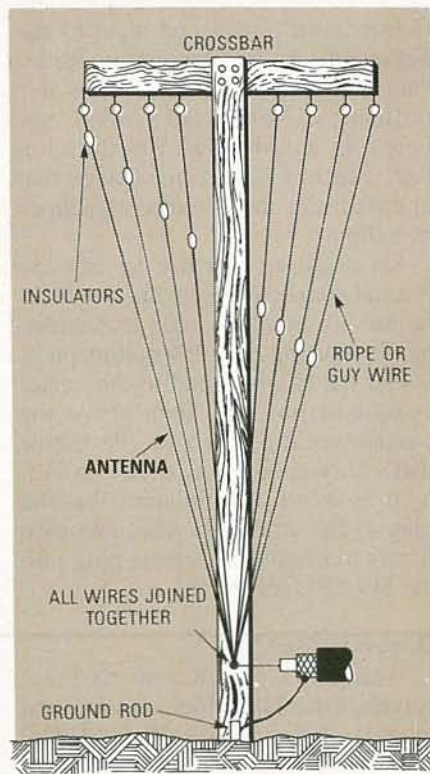


FIG. 11—TUNE IN THE WORLD with eight antennas in one.

The antenna downlead should be insulated and stranded; stranded wire breaks less easily than solid wire. Again, use No.12 or No.14 wire, although No.16 could be used. The point where the downlead and antenna wire are joined should be soldered to prevent the joint from corroding over time. Do not depend on the solder for mechanical strength, for it has very little. Instead, as shown in Fig 8, mechanical strength is provided by proper splicing technique.

There are several ways to bring a downlead into a building. If you can tolerate a slight crack in the junction of the sash and sill, then run a wire underneath the sash and close the window. However, the job looks mechanically nicer with a flat strap connector that passes under the window. Of course, you can always drill a hole in the wall, slip the coaxial cable through, then putty around the seam for a snug fit.

Grounding

The ground lead should be a heavy conductor, such as heavy wire, braid, or the shield stripped from RG-8 or RG-11 coaxial cable. For reception purposes only, the ground may be a cold-water pipe inside the house. Do not use either the hot-water pipes (which are not well grounded), or gas pipes (which are dangerous). Also, be aware that residential air-conditioner liquid lines look like copper cold-water pipes in some cases—don't use them.

A lightning arrester is a safety precaution, and *must* be used. It provides a low resistance path to ground in the event of a lightning strike. Don't consider the arrester optional—it isn't. Besides the obvious safety reasons (which are reason enough), there may be legal and economic reasons for using the arrester. Your local government building and fire codes may require one. Also, your insurance company may not honor your homeowner's policy if the lightning arrester required by local code is not used.

Warning! Do not ever attempt to install an antenna by crossing a power line! No matter what you believe or what your friends tell you, it's never safe—and it may very well kill you.

What about antennas other than the receiver longwire? The flattop antenna is shown in Fig. 9. That antenna is a close relative of the longwire, with

the exception that the downlead is in the approximate center of the antenna section. The flattop antenna should be at least a half wavelength ($492/f\text{MHz}$) at the lowest operating frequency. The advantage of the flattop antenna over other designs is that it allows maximum use of available space in the configuration shown.

It is also possible to build vertically polarized shortwave receiving antennas; Fig. 10 shows one such version. The support structure (a tree or building) should be at least a quarter-wavelength high on the lowest operating frequency. The vertically polarized antenna is fed at the base with coaxial cable. The center conductor goes to the antenna element, while the coaxial cable's shield gets connected to the ground rod at the base of the support structure.

It's possible to install the wire (or

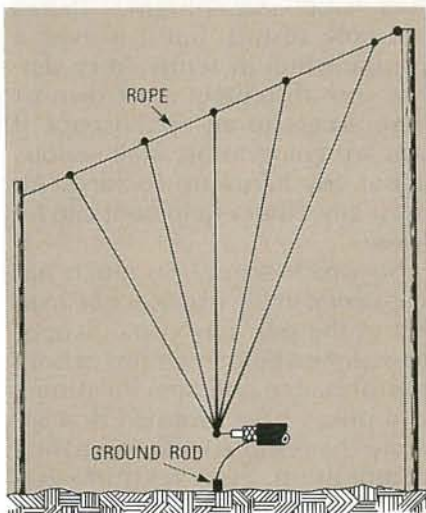


FIG. 12—BY USING A SLANTED ROPE, you can tie together any number of antennas tuned to different wavelengths.

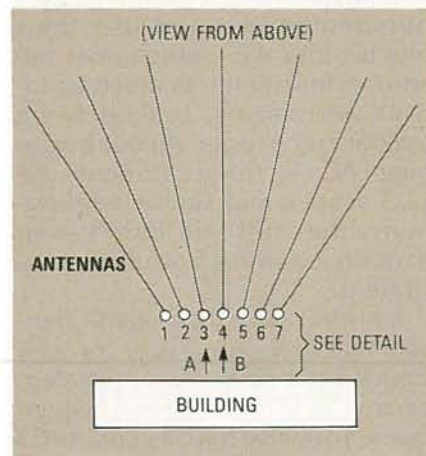


FIG. 13—SELECT THE DIRECTIONAL pattern of the antenna system by interchanging antenna elements of different wavelengths and position.

multiple wires of different lengths) inside a length of PVC plumbing pipe. The pipe serves as the support, and the conductors go inside. If you use a heavy pipe gauges of PVC, then the antenna support can be disguised as a flag pole (townhouse dwellers take note)!

Different conductor lengths ($L = 246/f\text{MHz}$) are required for different operating bands. In Fig. 11, several bands are accommodated from the same feedline using the same support. In fact, eight different antenna elements are supported from the same tee-bar. Be sure that you insulate them from each other, as well as from the support; again, PVC piping can be used for the support structure. Figure 12 shows a method for accommodating several bands by tying the upper ends of each antenna wire to a sloping rope.

Directional wire antenna

A directional antenna has the ability to enhance reception of desired signals, while rejecting undesired signals arriving from slightly different directions. Although directivity normally means a yagi beam, a wire-quad beam, or at least a rotatable dipole, certain designs and techniques allow fixed antennas to be more or less directive. One crude but effective approach uses pin plugs or a rotary switch to select the direction of the antenna's reception.

Figure 13 shows a number of quarter-wavelength radiators fanned out from a common feedpoint at various angles from a building. At the near end of each element is a female banana-jack. A pair of balanced feedlines from the receiver (300-ohm twin-lead, or similar) are brought to where the antenna elements terminate. Each wire in the twin-lead has a banana plug attached. By selecting which banana jack is mated to which banana plug, you can select the directional pattern. If the receiver has a balanced antenna input, then connect the other end of the twin-lead directly to the receiver; for receivers with unbalanced inputs, you will have to use a balanced-to-unbalanced (balun) antenna coupler.

Figure 14-a shows a balun antenna coupler tuned to the receiving frequency. The coil is resonantly tuned by the interaction of the inductor and capacitor. Antenna impedance is matched by selecting the inductor

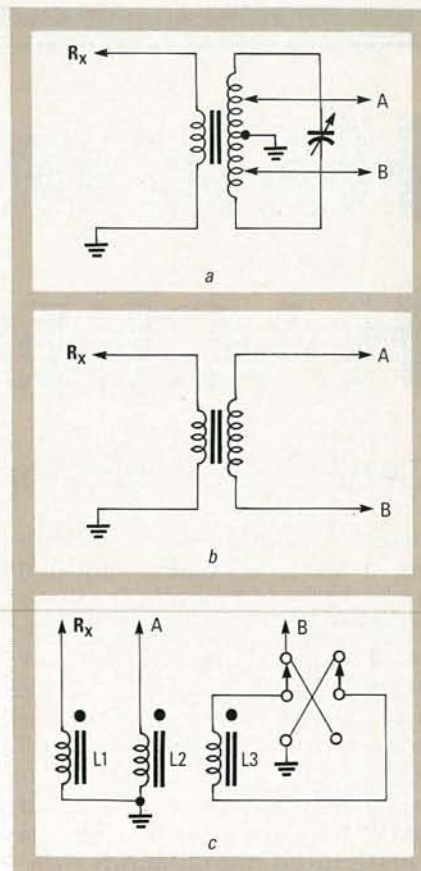


FIG. 14—MATCH A BALANCED ANTENNA with an unbalanced receiver input using any of three methods, (a), (b), or (c).

taps to which the feedline is attached. A simple RF broadband coupler is shown in Fig. 14-b. The transformer is wound over a ferrite core using 12 to 24 turns of No.26 enameled wire, with more turns for lower frequencies, and fewer turns for the higher frequencies. Experiment with the number of turns to determine the correct value.

By combining the right antenna and matching network, the best of both worlds can be had. For example, the antenna in Fig. 13 works by phasing the elements so as to null or enhance the reception in certain directions.

The nulling operation becomes a little more flexible if you build a phasing transformer, like the one in Fig. 14-c. Windings L1, L2, and L3 are wound trifilar style on a ferrite toroidal core using 14 turns of No.26 enameled wire. The idea is to feed one element from coil L2 (the A port), the same way all the time; that port becomes the 0-degree phase reference. Port B is fed from a reversible winding, so it can either be in-phase, or 180-degree out-of-phase with port A.

R-E

HARDWARE HACKER

Getting an oscilloscope

THERE SURE WAS QUITE A BIT OF INTEREST in the digital audio front end we looked at last month. For those of you that missed it, Crystal Semiconductor has a few reasonably priced A/D converters and evaluation boards which can give you everything you will need to input full 16-bit stereo digital audio into your personal computer or other digital recording system—in short, a plug-and-go digital audio front end.

One possible recording device is a plain old SCSI hard-disk drive. In fact, they are approaching a gigabyte in storage capacity, which means that any old personal computer can record several hours of first-rate CD-quality stereo audio. That also means that the so-called "DAT controversy" is now totally moot, since there is now an installed user base of several tens of millions of computer systems that can, at least in theory, do a compact-disc-quality digital audiophile recording.

It should also be easy to adapt the digital-audio front end to an ordinary VCR. That would make probably a very interesting construction project.

What about the playback? Getting from digital to analog isn't nearly the hassle as going the other way. One obvious route is to use any old CD player and intercept and override the bits halfway through. Otherwise, the needed D/A chips are readily available from Analog Devices, Sony, or from Burr-Brown.

Naturally, we've opened up some golden new opportunities here. All of the folks at **Radio-Elec-**

tronics would be most interested in publishing some workable construction projects that you can come up with.

As usual, this is your column, and you can get technical help and off-the-wall networking per that "Need Help?" box. Best calling times are 8-5 weekdays, Mountain Standard Time.

We seem to have a mixed bag this month...

Getting an oscilloscope

I have long been a great fan of doing things on the cheap. The whole purpose of hacking is to get all the effects that you are after to show up reasonably well using the minimum possible time, cost, and effort. And I have seen countless projects ruined or changed into something entirely different and totally out of control by throwing far too much money at them far too soon.

On the other hand, there are one or two essential tools to any endeavor that are best done on a positively first-rate and top-notch basis.

As an obvious example, no photo-journalist would ever try to operate without a camera. And his or her camera choice will almost al-

Toner reloading tools
More on digital audio
Getting an oscilloscope
Simple CMOS oscillators
Some bar code resources

DON LANCASTER

ways be a Nikon. Instamatics need not apply.

It amazes me how many hardware hackers out there do not own a personal oscilloscope or have no reasonable access to one. That is not only absurd, but it is even a contradiction in terms. Very simply, you absolutely *must* own or have access to an oscilloscope if you are going to be at all serious about any hardware hacking. Almost any other equipment can be faked.

So which scope? So much has happened in the oscilloscope market in the past few years. Scopes have gotten better in terms of both performance and specifications, and prices have dropped dramatically thanks in part to increasing competition. Even Tektronix has some bargains.

For instance, outstanding hacker choices would be either their \$695 model 2205 or their somewhat fancier model 2225. I personally own and use their much older 455, which cost me around four times as much as today's instruments, besides being bulkier and heavier. All our beginning EAC electronics students use 2225 scopes and similar workstations, the stuff you didn't even dare dream of back when I was a student.

Tektronix does have some freebies that make life easier for you. Check out their *Tek Direct* catalog, or any of their many free videotapes. They also have a good *ABC's of Oscilloscopes* experimenter book available. It's supposed to cost \$3, but you can often talk them out of a free copy or two.

NEED HELP?

Phone or write your **Hardware Hacker** questions directly to:
Don Lancaster
Synergetics
Box 809
Thatcher, AZ 85552
(602) 428-4073

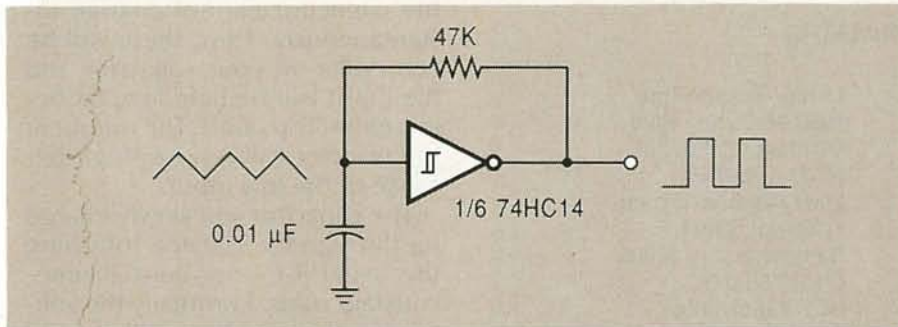


FIG. 1—AN ELEGANTLY SIMPLE OSCILLATOR can be built using nothing but one resistor, one capacitor, and 1/6th of a CMOS hex Schmitt trigger. Your output is a full-supply square wave, while the input is a triangular wave that "saws" between the trigger's upper and lower trip points.

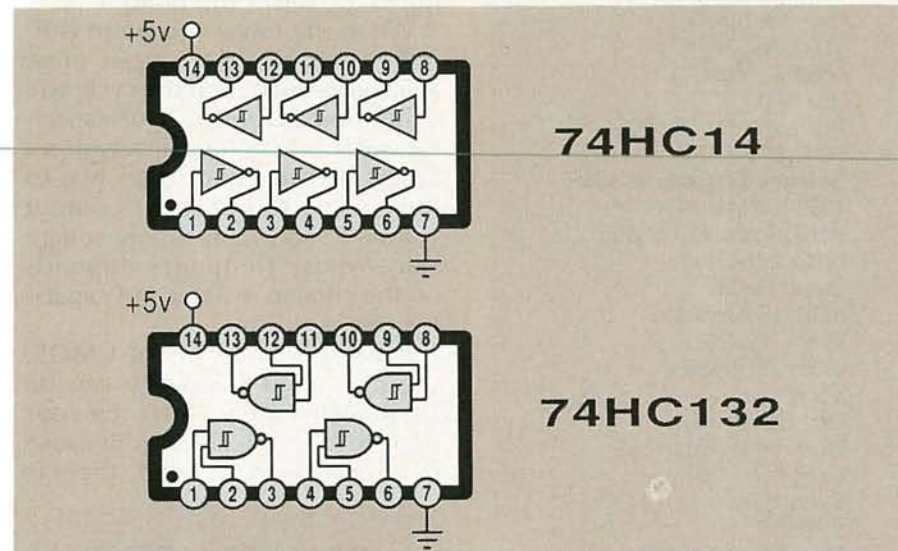


FIG. 2—THE PINOUTS for the two most popular CMOS Schmitt chips include the hex inverting 74HC14 and the quad NAND 74HC132. While intended for +5-volt use, they will work over a +2- to +6-volt range. For higher voltages, use the older 4093 or 4584 devices instead. The chips are shown top view.

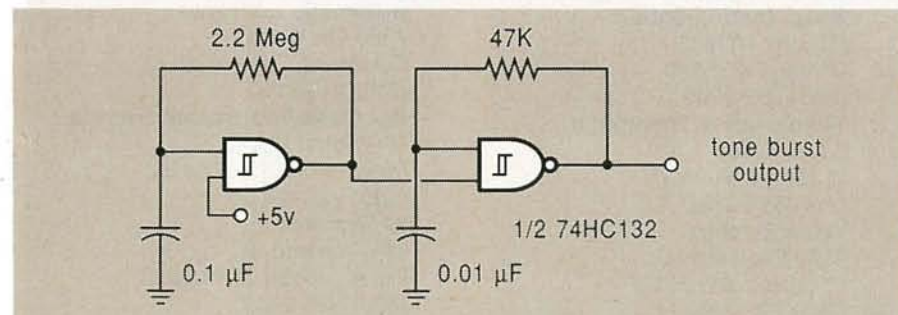


FIG. 3—A GATED OSCILLATOR produces repeated tone bursts. The RC values on the right side set the frequency, while the ones on the left determine the repeat rate.

My favorite circuit

One recent hacker helpline caller needed a tunable 10- to 15-megahertz square-wave generator—preferably in the next ten minutes. I got to thinking about it for a while, and realized that a favorite circuit of mine could easily do the job, and then some.

I always have liked elegant simplicity—any stuff that can do

more with less at lower cost. And I know of no better circuit than this one to use as an example.

Figure 1 shows you an oscillator that uses only 2½ components. One resistor, one capacitor, and one-sixth of a hex CMOS Schmitt trigger.

Let's review a bit here. A CMOS Schmitt trigger is a digital-logic device that will output a "1" when

you input a "0," and vice versa. If you are using the usual +5-volt supply, then the output "1" state will normally be +5 volts, and the output "0" state will normally be ground.

Now, if we used an ordinary inverter, any logic level above 2.5 volts would be considered a "1" and will drive the output low. And any logic level below 2.5 volts would be considered a "0" and would drive the output high. As this is a CMOS device, essentially zero input current is needed, so you can treat the input as an open circuit.

But, a Schmitt trigger has a built-in snap-action or *hysteresis*. A *rising* input level has to exceed an *upper trip point*, typically around +3 volts, before the output will suddenly snap low. Similarly, any falling input level has to go *below* a *lower trip point*, usually around +2 volts, before your output will once again suddenly snap high. We can say that the device has a

NEW FROM DON LANCASTER

HANDS-ON BOOKS

Hardware Hacker Reprints II	24.50
Ask The Guru Reprints I or II	24.50
CMOS Cookbook	18.50
TTL Cookbook	16.50
Active Filter Cookbook	15.50
Micro Cookbook vol I or II	16.50
Enhancing your Apple I or II	17.50
AppleWriter Cookbook	19.50
Apple Assembly Cookbook	21.50
Incredible Secret Money Machine	10.50
LaserWriter Reference (Apple)	19.50
PostScript Cookbook (Adobe)	16.50
PostScript Ref. Man. (Adobe)	22.50
PostScript Prog. Design (Adobe)	22.50

UNLOCKED SOFTWARE

PostScript Show & Tell (Ile/Mac/PC)	39.50
Intro to PostScript VHS Video	39.50
PostScript Perspective Draw	39.50
PostScript Beginner Stuff	39.50
PostScript Technical Illustrations	39.50
PostScript Work in Progress	39.50
PostScript BBS stuff	19.50
Absolute Reset Ile & Ilc	19.50
AppleWriter/Laserwriter Utilities	49.50
Enhance I or II Companion Disk	19.50
AppleWriter CB or Assy CB Disk	24.50

FREE VOICE HELPLINE

VISA/MC

SYNERGETICS

Box 809-RE
Thatcher, AZ 85552
(602) 428-4073

CIRCLE 83 ON FREE INFORMATION CARD

JULY 1989

NAMES AND NUMBERS

Analog Devices

One Technology Way
Norwood, MA 02062
(617) 329-4700

AT&T Microelectronics

961 Macon Blvd
Allentown, PA 18103
(800) 372-2447

Burr-Brown

6730 S Tucson Blvd
Tucson, AZ 85734
(602) 746-1111

Caplugs

2150 Elmwood Ave
Buffalo, NY 14207
(716) 876-9855

Computer Shopper

5211 S. Washington
Titusville, FL 32780
(470) 269-3211

Crystal Semiconductor

4210 S Industrial Drive
Austin, TX 78744
(512) 445-7222

Custom Technology

192 Lakeshore
Texarkana, TX 75501
(214) 838-0243

EVCO

3451 Lorna Lane
Birmingham, AL 35236
(205) 822-5381

Fair Radio Sales

1016 E Eureka St
Lima, OH 45802
(419) 227-6573

Hewlett-Packard Manuals

1320 Kifer Road
Sunnyvale, CA 94086
(415) 857-1501

Jensen Tools Inc

7815 South 46th Street
Phoenix, AZ 85044
(602) 968-6231

Jerryco

601 Linden Place
Evanston, IL 60202
(312) 475-8440

Lazer Products

12741 E Caley Ave #130
Englewood, CO 80111
(303) 792-5277

Lindsay Publications

PO Box 12
Bradley, IL 60915
(815) 468-3668

Linear Technology

1630 McCarthy Blvd
Milpitas, CA 95035
(408) 432-1900

Merryweather Foam

11 Brown Street
Barberton, OH 44203
(216) 753-0353

NEC Electronics

401 Ellis Street
Mountain View, CA 94039
(800) 632-3531

Niagara Plastics

7090 Edinboro Road
Erie, PA 16509
(814) 868-3671

Nuts & Volts

Box 1111
Placentia, CA 92670
(714) 632-7721

Science Magazine/AAAS

1333 H Street NW
Washington, DC 20005
(202) 326-6400

Small Parts

6891 NE Third Ave
Miami, FL 31238
(305) 751-0856

Sony

One Sony Ridge
Park Ridge, NJ 07656
(201) 930-1000

Synergetics

Box 809
Thatcher, AZ 85552
(602) 428-4073

Tektronix

PO Box 500
Beaverton, OR 97077
(800) 426-2200

Texas Instruments

PO Box 809066
Dallas, TX 75380
(800) 232-3200

Thompson & Thompson

23072 Mullin
El Toro, CA 92630
(714) 855-3838

Value Plastics

3350 Eastbrook Dr
Ft Collins, CO 80525
(303) 233-8306

Vortec

10125 Carver Road
Cincinnati, OH 45242
(800) 441-7475

the capacitor cannot change instantaneously. Thus, there will be zero volts on your capacitor and the input will be held low, far below either trip point. The output of the inverter will now go high because of the low input.

The capacitor will slowly charge up through the resistor, following the usual R-C exponential time-constant rules. Eventually the voltage on the capacitor will exceed the upper trip point. That snaps the inverter output low, and the capacitor will now start discharging to the lower trip point.

When the lower trip point is finally reached, the output once again goes high, and the cycle will continuously repeat. Your capacitor will have a triangular waveform across it that ranges from two to three volts. Your inverter's output will be a sharp, full-supply square wave whose frequency depends on the chosen resistor and capacitor values.

Because you are using CMOS, the oscillation frequency can be anything from just a few cycles per hour to beyond 20 MHz. Because of the open-circuit input, there is

BAR CODE RESOURCES

A.I.M.

1326 Freeport Rd
Pittsburgh, PA 15238
(412) 963-8588

Automatic I.D. News

7500 Old Oak Blvd
Cleveland, OH 44130
(216) 243-8100

Bar Code Information Service

500 South Fourth St
Minneapolis, MN 55415
(800) 328-4960

ID Systems

174 Concord St
Peterborough, NH 03458
(603) 924-9631

Identification Journal

2640 N Halsted St
Chicago, IL 60614
(312) 528-6600

UPC Council

8163 Old Yankee Rd #J
Dayton, OH 45458
(513) 435-3870

MacBarCoda

ComputaLabel Ltd
18a Regent St
Narborough, Leicester
England LE95DJ
011-44-533-750131

one-volt hysteresis, or dead band. If you are sitting inside the dead band, you will not cause the output to change—unless you exceed your upper trip point or go below the lower one.

The intended use of CMOS Schmitt triggers is to clean up a

sloppy, noisy, or slowly changing input waveform. It is often a good idea to use them for almost any real-world input going into a hacker's circuit.

So how does our oscillator work? Let us assume that we have just applied power. The charge on

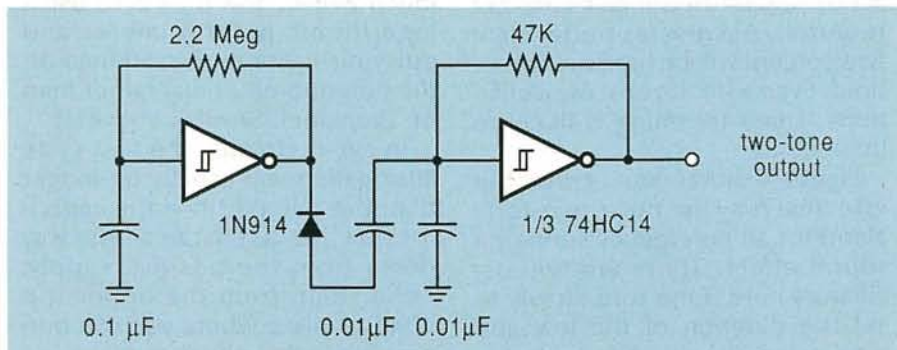


FIG. 4—THIS TWO-TONE ALARM produces a distinctive "twee-dell" output. The spread between the high and low pitch is set by the ratio of the two timing capacitors on the right side. Experiment to get the best-sounding results.

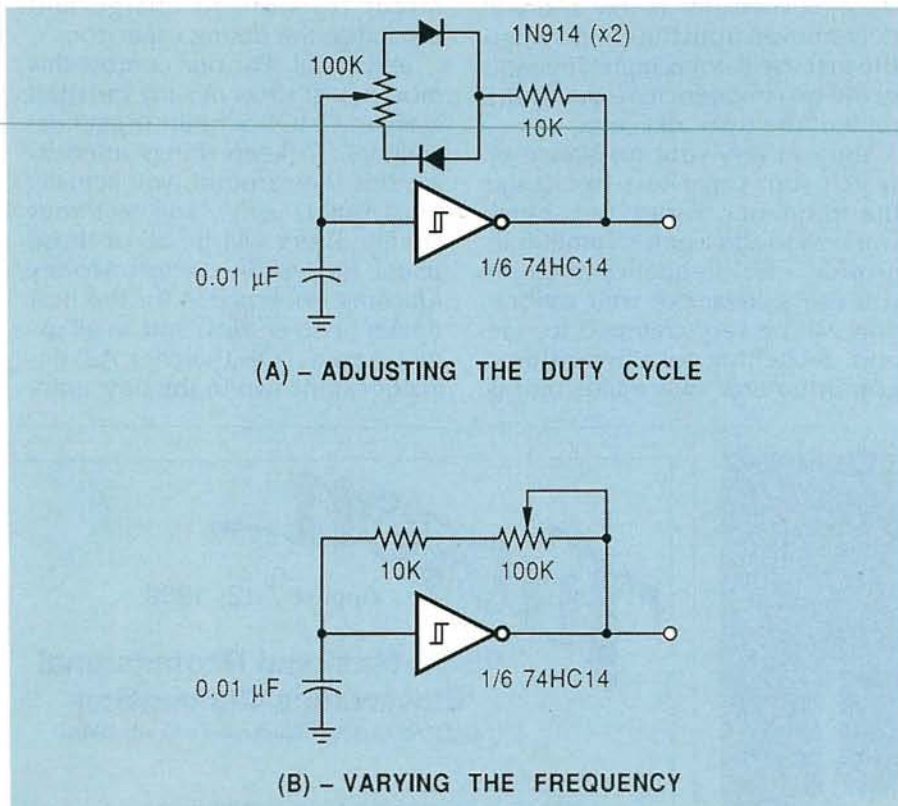


FIG. 5—ORDINARY VOLUME CONTROLS can be used to vary either the duty cycle or the frequency as shown here.

virtually zero loading on the R-C network.

Two obvious chip choices are the hex 74HC14 or else the quad NAND 74HC132. Pinouts for them are shown in Fig. 2. The pricing should be around a quarter or so.

Some older and traditional CMOS devices that also work quite well here would include the 4093 and the 4584. They can be used with a 9-volt battery or power supplies as high as 15 volts, while the '14 and the '132 are intended for use with supplies in the 2- to 6-volt range. Don't try to use HC devices above 6 volts or you will de-

stroy them!

What can you do with all the other inverters or gates in the package? One obvious thing to do is take all five remaining inverters and put them in parallel for use as an output buffer. That isolates your RC timing from any changes in loading. Yes, you can even audibly power a speaker that way. No, it is not very loud. But it does give you an instant cable or continuity checker, a simple logic probe, or even a burglar alarm. The NAND chips can be gated, or turned on and off with an external signal. The rule is that a +5-volt input will run

NEW SUPER LONG PLAY TAPE RECORDERS

12 Hour Model — \$119.00*
USES D-120 TAPE

Modified Panasonic Slimline, high quality, AC-DC Recorders provide 6 continuous hours of quality recording & playback on each side of 12 hours. Built-in features include:
• Voice level control, • Digital counter, etc. TDK DC 120 Cassette Furnished.



PHONE RECORDING ADAPTER

Records calls automatically. All Solid state connects to your telephone jack and tape recorder. Starts recording when phone is lifted. Stops when you hang up.

\$24.95*
FCC APPROVED

VOX VOICE ACTIVATED CONTROL SWITCH

Solid state. Self contained. Adjustable sensitivity. Voices or other sounds automatically activate and control recorder. Uses either recorder or remote mike.

\$28.50*

* Add for ship & hdlg. Phone Adapter & Vox \$1.50 ea. Recorders \$4.00 ea. Cal. Res. add tax. Mail order, VISA, M/C, COD's OK. Money Back Guarantee. Qty. disc. avail... Dealer Inquiries invited, Free data. © AMC SALES INC. Dept A9335 Lubec St., Box 928, Downey, CA 90241 Phone (213) 869-8519

CIRCLE 108 ON FREE INFORMATION CARD

Get A Complete Course In

ELECTRONIC ENGINEERING

8 volumes, over 2000 pages, including all necessary math and physics. 29 examinations to help you gauge your personal progress. A truly great learning experience.

Prepare now to take advantage of the growing demand for people able to work at the engineering level.

Ask for our brochure giving complete details of content. Use your free information card number, or write us directly. \$99.95, Postage Included. Satisfaction guaranteed or money refunded.



Banner Technical Books, Inc.

1203 Grant Ave.
Rockford, IL 61103

CIRCLE 67 ON FREE INFORMATION CARD

the oscillator, while a grounded input stops oscillation. Figure 3 shows you a gated alarm that beeps at a selected rate.

Once again, you set the frequency with either your resistor or capacitor. Recommended resistor values range from 10K to 10 megohms for most of the lower frequencies. Its simplest to experiment with component values to get the best-sounding results or the most-useful range.

Otherwise, you can calculate your charging current by using Ohm's law and the 2.5 volts that is the average across the resistor. There is a formula that says:

$$C = i\Delta t / \Delta v$$

where C is the capacitance in picofarads, Δt is the half time period in microseconds, i is the charging current in microamps and Δv is 1 for the one-volt triangular amplitude. The same formula will also work if C is in microfarads, i is in milliamps, and Δt is in milliseconds.

Naturally, Fig. 3 is a rather sloppy circuit, to be used only where ex-

act or precise frequencies are not required. Accuracies better than five percent will be hard to keep or hold. Even with the best of calculations, some trimming is likely to be needed.

Figure 4 shows you a crude but effective way to do a two-tone alarm for an emergency siren or a sound effect. There are two oscillators here. One runs slowly to set the duration of the low and high notes. The second runs fast to create the actual tones. That second timing capacitor will get switched into the circuit whenever the first oscillator is low and will get removed from the circuit when the first oscillator is high. The ratio of the two frequencies is set by the ratio of the two capacitors.

You can vary your resistance or switch your capacitors to change the frequency. Figure 5-a shows you how to add a potentiometer to provide a 10:1 frequency range. If you use a linear pot your calibration will be very cramped to one end. Switching to a logarithmic potentiometer will make things

much worse. The trick is to use a logarithmic potentiometer and put your calibration markings on the potentiometer dial rather than on the panel. Sneaky, eh what?

In gated circuits, the first cycle after gating will usually be longer than the others, since the capacitor now has to charge all the way down from the positive supply, rather than from the upper trip point. A place where you can purposely use that effect might be in a keyboard auto-repeat circuit.

Figure 5-b shows you how to adjust the duty cycle by using different resistors to charge and discharge the timing capacitor.

Tellyawhat. For our contest this month, just show me any variation at all on CMOS Schmitt-trigger oscillators. To keep things interesting this time around, you actually must build, verify, and test your circuit. There will be all of those usual *Incredible Secret Money Machine* book prizes for the best dozen or so entries, and an all expense paid (FOB Thatcher, AZ) tinaja quest for two to the best entry



OZONE SAFE ULTRAJET® Only from Chemtronics

High-powered (120 psi) precision dust remover made without ozone-depleting CFCs. New E-Series Ultrajet is filtered to <0.2 microns for maximum purity, and packaged in seamless 12 oz. aluminum cans. Available with disposable pushbutton valve, as well as complete reusable system with chrome trigger valve.

Call or write for more information today.



681 Old Willets Path Hauppauge, NY 11788
800-645-5244 516-582-3322

CIRCLE 54 ON FREE INFORMATION CARD

Tucson

August 7-12, 1989

1989 National Professional Electronics Convention and Professional Electronics Trade Show

- For Consumer Service Dealers and Technicians
- Management and Business Seminars
- Technical Seminars and Certification
- Meetings with Major Manufacturers' Reps
- Trade Show and Association Meetings
- Instructors Conference
- Sponsored by the National Electronics Sales & Service Dealers Assn. and the International Society of Certified Electronics Technicians
- Special room and transportation rates provided by Loews Ventana Canyon Resort, Tucson AZ



For more information, call or write to NPEC '89, 2708 West Berry Street, Fort Worth, TX 76109; (817) 921-9061.

Name _____
Address _____
City _____ State _____ Zip _____
Phone _____

of all.

As usual, send your entries directly to me per the "Need Help?" box, rather than to **Radio-Electronics'** editors.

Toner refilling tools

In the past issues, as well as in all the Hardware Hacker reprints, we've seen how the Canon toner cartridges widely used in lots of popular laser printers and copiers can be reloaded many times. That can either be done as a rather profitable sideline service for others, or else to reduce your own per-page toner costs down into the jiffy printing range.

Since there's two brand new toner-cartridge reloading tools available this month, I thought it might be a good time to review all of those top-secret reloading tools and sources.

But first, the new stuff. A great SX cartridge pin puller is now available from Thompson and Thompson as their model AXP43-007.09R GlompenStractor. It neatly and cleanly pulls the pins

with zero damage. The older techniques included traverse cutting pliers, screw extractors, wood-working screw starters, or an obscure craftsman tool known as a #8 gimlet.

The really big news, though, is that it looks as if SX-drum hard recoating is now a reality. In theory, that could greatly extend SX-cartridge life and might eventually reduce or even eliminate the 15:1 per-page toner-cost penalty of the LaserJet II or either the LaserWriter NT or NTX.

One source of recoating drums and services is Arlin Shepard from Lazer Products. Their projected recoating costs are in the \$8 range. It will be rather interesting to see how effective drum recoating actually becomes.

Let's go back to the old stuff. The best source for detailed maintenance and repair manuals on the CX and SX engines is Hewlett Packard. In fact, it is pretty near impossible to intelligently apply any Apple LaserWriter without owning the related HP manual that will

cover it. The older CX engine (LaserJet, LaserWriter, LaserWriter Plus) manual is #02686-90904, while the newer SX engine (LaserJet II, LaserWriter NT and NTX) manual is part number #33440-90904.

HP has traditionally been a great source for the repair and replacement parts for all of the Apple machines, but lately they have been selling the major assemblies only. If the part you want is not individually available from HP, try Custom Technology or Thompson and Thompson.

As I've mentioned a time or two before, there are two reloading methods, the *punch and go* and the *total teardown*. I overwhelmingly prefer punch and go since it delivers far and away the lowest per-page toner costs to the end user. We charge \$24 for local CX and SX reloads. I can still get away with such an outrageously high price since I live in a rather remote rural area.

At any rate, if you insist on a total teardown of a CX cartridge, the

CABLE - TV band - stop filters

- FOR ELIMINATION OF SEVERE INTERFERENCE
- FOR "CENSORING" OF ADULT BROADCASTS



- ATTENUATION - 45 dB TYPICAL
- BANDWIDTH - 4 MHz AT 5 dB POINTS
- INSERTION LOSS - 2 dB

MODEL	TUNING RANGE	FOR CHANNELS	PASSBAND	PRICE	SHIPPING/HANDLING
23H	50-66 MHz	2,3 (or 6 meter ham)	50-300 MHz	\$30	FREE
46FM	66-108 MHz	4,5,6 (or any FM)	50-300 MHz	\$30	FREE
1417	120-144 MHz	14(A) 15(B) 16(C) 17(D)	50-400 MHz	\$30	FREE
1822	144-174 MHz	18(E) 19(F) 20(G) 21(H) 22(I)	50-400 MHz	\$30	FREE
713	174-216 MHz	7,8,9,10,11,12,13	50-400 MHz	\$30	FREE

3 for \$72 - 10 for \$180 - mix & match

Call Toll Free For C.O.D. or Send Check To Order
No Shipping Charges

- Shipped Within 3 Days
- 30 Day Money Back Guarantee

FACTORY DIRECT FROM

Star Circuits

P.O. Box 8067

Pembroke Pines, FL 33084

1-800-433-6319

NOISE REDUCTION FOR UNDER \$10.

MIXING CONSOLES
SWITCHES

MICROPHONE
CONNECTORS

SNAKE CABLES

BATTERY CONTACTS

PLUGS & JACKS
PATCHBAYS

FADERS, POTS

TERMINAL STRIPS

SPEAKER TERMINALS



CRAMOLIN®

Even the finest equipment in the world cannot guarantee noise-free operation. One "dirty" connection anywhere in the electrical path can cause unwanted noise or signal loss.

"MORE THAN A CONTACT CLEANER"

CRAMOLIN® is a fast-acting, anti-oxidizing lubricant that cleans and preserves all metal surfaces, including gold.

When applied to metal contacts and connectors, **CRAMOLIN®** removes resistive oxides as it forms a protective molecular layer that adheres to the metal surfaces and maintains maximum electrical conductivity.

CRAMOLIN® - USED BY THOSE WHO DEMAND THE BEST:

Bell & Howell	Hewlett Packard	MCI(Sony)	Nakamichi
Boeing	John Fluke Mfg.	Motorola	RCA
Capitol Records	McIntosh Labs	NASA	Switchcraft
			SINCE 1956

CAIG LABORATORIES INC

1175-O Industrial Ave., (P.O. Box J) - Escondido, CA 92025-0051 U.S.A. • (619) 743-7143

CIRCLE 50 ON FREE INFORMATION CARD

magic T-10 tamperproof Torx bit you will need is manufactured by Evco in their 945B700 set, and can be gotten through Jensen Tools.

For punch and go, the best way to produce smooth and truly round reloading and draining holes is to use a #3 Unibit from ViseGrip, or one of their imitators. Those are once again available from Jensen Tools or almost any of the large electrical contracting supply houses. One rather good way to replug the holes is with the tapered plastic closures from either Caplugs or Niagara Plastics.

Fusion-roller wiper pads should be replaced each time you reload. One source of the custom-manufactured peel-and-stick and silicon pressure-lubricated Nomex felt strips is Lazer Products. They are normally included free with each bottle of their reload toner. A plain old 5/16-inch wood chisel is often the best way to remove the old wiper pad.

Note that washing and reusing a wiper pad is a no-no. Their purpose is to deliver a very precisely metered amount of silicon fusion oil. Improperly redone wiper pads might rather dramatically shorten the life of the rather expensive fuser assemblies.

A good drum lubricant is essential to a proper reload. You can get drum lubricant in bulk from those larger copier repair houses, while smaller quantities are available as Pixie Dust from Lazer Products.

Several plastic strips are useful as well. A twelve-mil-thick piece of the clear butyrate plastic is useful as the feeler gauge for regapping cartridges that have heavy streaking problems. Similar plastic strips can be used for sealing the fresh toner in reloads that have to be shipped somewhere else or stored for long periods of time. Further details on all of this appear in the Hardware Hacker II reprints.

Bar-code resources

There's a lot of recent hacker interest in bar codes. So, in continuing our series of hacker resources, all of the needed insider information appears in our Bar-Code Resources sidebar.

While there are lots of different bar codes today, far and away the most popular is called the UPC

code, otherwise known as the Uniform Product Code. A complete set of standards is available from The UPC Council.

The leading bar-code trade association is called the AIM, short for the Association of Identification Manufacturers. Among other things, they provide a free list of most major bar-code sources.

There are around a dozen free bar-code trade journals. Those that I am the most familiar with include *I.D. Systems*, *Automatic I.D. News*, and the *Identification Journal*.

One interesting resource is called The Bar Code Information Service. They supply a \$4.95 *Bar Code Film Masters* book and a \$19.95 *Technical Reference Guide*.

Generating your own bar codes by using the PostScript language along with your favorite word processor is simple, and also turns out to be a very good initial project in PostScript programming. Surprising as it may sound, there just are not that many plug and go PostScript bar-code font packages out there on the market just yet, although dozens of low-cost versions are almost certain to shortly appear. As of this writing, the only PostScript bar-code product that I do know about is an English one called MacBarCoda.

For more on PostScript in general, see my "Ask The Guru" column in *Computer Shopper*, or my "Ask The Guru" reprints.

New tech literature

Let us quickly review five of my favorite hacking resources. For "old line" or traditional military-surplus electronics, its real hard to beat Fair Radio Sales. For a mind-boggling collection of nearly anything else in surplus, electronics and otherwise, Jerryco has to be the hands-down winner. For anything you can't find at your hardware store, along with the ability to custom cut up small pieces of metal or plastics cheaply, Small Parts is the only way to go.

For unusual publications, ranging the gamut from early machine-shop techniques through antique radios all the way on down to perpetual-motion machines and the free-energy scams, check out *Lindsay Publications*. And for elec-

tronics bargains direct from electronics startups and other hackers, there's the great little *Nuts and Volts* shopper newsletter.

Texas Instruments has a new free PAL Evaluation Kit, which can even get you those sample programmable logic devices programmed for free. From AT&T, a thick new *Communication Devices* data book. And from NEC Electronics, the new *Memory Products* data book. That one includes full details on an improved-definition television front end. It will accept an ordinary NTSC interlaced TV input and doubles the horizontal scan rate, to give you a flicker-free and apparently much sharper solid-scan video output suitable for display on a Multi-Sync monitor or whatever.

One "must read" recent paper on levitation in physics appeared back in the January 20, 1989 *Science* that shows you proven methods to levitate both solids and liquids. Half a dozen viable methods are covered in depth, with a good bibliography.

There's lots of mechanical stuff this month. The Vortec people have all sorts of ultra-simple solid-state cooling devices that use nothing but shop air to produce temperatures as low as -40 degrees Fahrenheit!

Value Plastics has free samples of their ultimate solution to low-cost custom robotics pneumatic connectors—bondable fittings that can be mixed and matched almost any way. And Merryweather Foam now has a free sample card of their urethane- and polyester-foam products.

Turning to my own stuff, if you are at all into Apple computing, you will find autographed copies of my *Enhancing Your Apple IIe*, volumes I & II, my *Apple Assembly Cookbook*, and my *AppleWriter Cookbook*, along with their companion disks available directly from me at Synergetics.

And if you want to get further into PostScript, the magic language that does all of the artwork you see here, using nothing but your favorite word processor, check out my *Intro To PostScript* video or my *PostScript Show and Tell* disks, now available for most personal computers. **R-E**

COMPUTER DIGEST

OMNIVIEW AND A 386

MIKE TOUTONGHI,
SUNNYHILL SOFTWARE

Intel's 80386 microprocessor is taking the world by storm. For some people, speed is the most important aspect of the microprocessor. For others, though, intelligent memory management and the ability to run several programs simultaneously are what make the 386 desirable, if not indispensable.

By itself, the 386 just acts like a faster, more expensive version of the 286. It takes special software to unlock its treasures, and that's where we come in. OmniView is a multi-tasking operating environment written for machines running MS-DOS. Actually, OmniView can run on any 8088/86/286/386 microprocessor. But on a 386, especially in conjunction with 386^{MAX} (pronounced 386-to-the-max), OmniView can make life under DOS much more pleasant.

In this article we'll summarize briefly what OmniView is, what it does, and how to use it. Then we'll go on to show the basics of how it works with the 80386 to increase your computing power. Next time, we'll take an in-depth look at how the program performs its magic, and show how you can write your own programs to take advantage of that magic. In so doing, we'll present a sample multitasking utility program that monitors the state of your PC in real time.

Using OmniView

OmniView works by putting a menu-based "shell" around your DOS environment. Many DOS shell programs do the same thing; however, the typical DOS shell only allows you to run one program at a time, and won't let



Fig. 1. OMNIVIEW'S USER INTERFACE resembles that of a typical DOS shell. The difference is that you can switch among loaded programs instantaneously, and, on the right hardware, they can actually run simultaneously.

you switch among several different programs without closing one before opening another.

Like the typical shell, OmniView lets you create a menu that lists the programs you use (for example, see Fig. 1). To run a program, move the highlight bar to that item and press Enter. To run another program, press a hot key to return to the menu, move the highlight bar, and press Enter. Later, when you've got several applications running, you can hot-key among them at will. The maximum number of applications that you can run at once is ten; each program runs as if it had complete control of the computer, blissfully ignorant of any others.

Depending on the type of microprocessor and memory in your system, two or more programs can seemingly run simultaneously. That's called multitasking. For example, you could download data from your favorite BBS while simultaneously working in your word processor. On a

continued on page 78

CeBIT

JANET ENDRIJONAS

Topping its own reputation as the greatest computer show in the world, this year's CeBIT—World Center for Bureau (office), Information and Telecommunications Technology—exposition in Hannover, West Germany was the largest ever. Multiple technologies abounded—computers, telecommunications, connectivity, security—you name it. If it pertained to information movement or management, it was at CeBIT.

Over half a million people pushed their sore feet and tired legs through some 3,125 exhibits from 37 countries spread over 14 buildings. They viewed the latest in state-of-the-art technology, stopping only to attend symposia, conference workshops, and industry presentations during the eight-day event. Both prototypes and working models of products developed around the world were on display. As usual, many of those items will not be seen in the United States for several years, and some may never get here. At the same time, the 197 United States exhibitors' booths were crowded with people anxious to see the latest in American innovation.

A quieter show

To veteran CeBIT goers, at first glance the 1989 show appeared tame—no flashy new technology, noisy international rivalries, or juicy scandals surfaced. The show seemed carefully orchestrated with special "pavilions" dedicated to specific interests such as networking, telecommunications, computer security, and doing business with India, CeBIT's first "international business partner."

One noticeable trend involved

Japanese manufacturers rushing to comply with new requirements pertaining to putting "Made in Europe" or, more specifically, "Made in Germany" labels on their products. Last year, the Common Market countries raised the tariffs on imported technology while also establishing minimum percentages for the amount of local content required to earn the coveted labels, putting outsiders in a difficult situation.

CeBIT's overall atmosphere seemed geared toward promoting the harmony that will become reality in 1992 when the European Common Market drops trade barriers within its domain and becomes the European Economic Community, often referred to as the "Untied States of Europe."

Developments such as those, however, could not represent the major excitement—there had to be more going on at CeBIT. You can't have a show this big with nothing new and unexpected to report. Macintosh Apples or Does the Recipe Call for Jonathans?

Last year we reported that there was a rumor floating around CeBIT of "MacClones" being developed in the Orient. Enter Jonathan, a working Macintosh clone developed by a small company, Akkord, in Taiwan who contracted with a friendly West German distributor, Jonathan Computers Deutschland, to display the machine at CeBIT.

The literature made no mention of Apple compatibility. It expressly referred to "tomato compatibility" in an international play on words. The editor of the monthly German Macintosh publication, MacUP, spent three days during CeBIT putting Jonathan through its paces and declared that there could be no question of Macintosh compatibility—every program he tried worked, even the games.

Over the years, several US companies have attempted to clone the Macintosh and wound up losing court cases to Apple. Akkord's legal business consultant insisted that there were no copyright infringements and a spokeswoman for Apple Germany said that to the best of her

knowledge, Jonathan did not violate Apple copyrights. How could that be?

There was a simple explanation. All the previous law suits had been based on infringing the copyrights for the Apple ROM (read only memory) set. So Jonathan is being shipped with ROM sockets but no ROM's. Of course, if you are familiar with US computer-component mail-order opportunities, you know you can buy Mac Plus 128K ROM's for about \$90 from several vendors.

Overall specs indicate that Jonathan is a low-cost Macintosh alternative, more powerful than a Mac Plus thanks to an internal hard disk, but less expensive than a Mac SE. Akkord claims to have showed Jonathan only to prove that a Mac clone is possible. The company will make no specific marketing plans until all legal questions are answered. Hence, there are no price quotes available nor is there word on when (or if) the first Jonathan might turn up in the United States.

Color LCD's—Boom or Bust?

Do consumers really want big LCD screens in monitors or laptops? "They shouldn't until resolution improves," said a spokesman for Casio, one of the manufacturers. Another manufacturer with prototypes on display, Toshiba, agreed that current resolution is only adequate for small-screen television viewing, certainly not for use with computers. Toshiba's spokesperson went so far as to say that his company considered it useless to market an imperfect item just for the sake of selling a product.

So why all the excitement at Hitachi? At their booth, what was said to be the world's first laptop with a color LCD display was being touted as the key product in a hot new market. And at the Sharp booth there was a 386 computer with a 14-inch color LCD that will be available to European consumers by year's end.

Networking

Special pavilions displaying networking and telecommunica-

tions occupied large space in two halls. Here the march toward 1992 resulted in emphasis being placed on internal corporate, external national, and international voice and data communications. ISDN (Integrated Services Digital Networks), which had been the hot topic a year earlier, was somewhat in the background for the moment as European and American companies demonstrated communications solutions that can already be put into place.

The US is the current leader in networking and telecommunications thanks, in part, to the breakup of the Bell system and the growth of smaller, more innovative and competitive telecommunications companies. Telecommunications in most European countries are still controlled nationally. Some change will occur when the new Economic Community becomes a reality in 1992 and, in preparation, the emphasis on importing US telecommunications technology is heavy at the moment.

ISDN wasn't completely ignored during CeBIT. Video conferencing via ISDN lines was a big hit and even enabled Indian Prime Minister Rajib Gandhi to participate in the opening ceremonies from Bombay. The picture phone we've all been joking about and in some cases dreading was available and working much to the dismay of those of us who answer the phone before putting on makeup. And if that wasn't bad enough, one phone not only showed the person on the other end; it also displayed a small inset of you in the corner. It was worse than staring into a mirror.

Hannover Hacker

Just before CeBIT started, newspaper headlines around the world revealed the existence of three computer hackers based in Hannover who had been stealing data from US government computers on behalf of the KGB. The fact that the US claimed that the stolen data was low level didn't lessen the concern for computer security among exhibitors and attendees alike.

This year, an entire floor in one of the exhibit halls was devoted to security solutions. It was a place where hackers could go to attempt to outsmart the experts. The experts didn't always win. Toward the end of the eight-day show, two ten-year-old schoolboys entered a booth at CeBIT and in the process of hacking managed to lock up the booth's entire computer demonstration. They generously offered to undo the damage if the company running the booth would pay them DM 10. The company paid and the boys put the system back in working order.

Calling Moscow

Not everyone was worried about hackers or the KGB. There was evidence of glasnost at work. Deutsche Mailbox, one of Europe's largest electronic-mail (E-Mail) companies announced a link with the Soviet Union. Once hardware, software, and a hotline are installed in Moscow, Deutsche-Mailbox users will be able to send and receive electronic messages from people in the Soviet Union.

As you might expect, there are limitations on the Russian side of that setup. The Soviets will be controlling what their users are allowed to do. The system will not be available to every Igor, Ivan, and Vladimir, and those who are allowed to use it will find themselves unable to access certain functions like data bases.

Right now, the service is restricted to users in Moscow but there are plans to extend it to 30 cities throughout the Soviet Union via the Moscow gateway.

How red is your nose?

Even at CeBIT, technology does not totally supercede humanitarian concerns. One day a year the people of the United Kingdom set aside their self-consciousness and don bulbous red clown noses in support of a charity for needy children organized by Comic Relief, a successor to Band Aid/Live Aid. Since Red Nose Day fell in the middle of CeBIT, one enterprising UK company brought along a supply of red noses and sold them to atten-


dees. By noon, certain areas of CeBIT looked like everyone had enjoyed too much German beer the night before.


Walking shoes before 1990

If you have decided that you want to be a part of the CeBIT excitement in 1990, you had better buy a pair of sturdy walking shoes. CeBIT plans for expansion in 1990 call for at least an additional 200 exhibitors.


Actually, it might be wise to buy two pair. CeBIT has spawned a new little sister, CeNIT, the Asian Center and Conference for Information and Telecommunications, which is to be held in the new Hong Kong Convention and Exhibition Center.

Attendance at CeBIT has always favored European countries. While many products originating in the Orient are introduced to the world at CeBIT, no doubt there are countless other new products being developed in the Far East that none of us, European or American, have ever seen. Now, with CeNIT, the world will get to see what it has been missing.

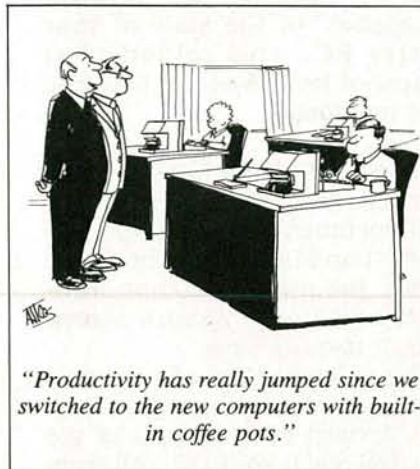It has always taken a world-class exhibit attendee to traverse the length and breadth of CeBIT, enduring blisters and back aches for the sake of seeing new technology as it first appears on the scene. The pain and suffering, sensory overload, and jet lag we have been privileged to endure for CeBIT will now be extended to a new group of technology buffs at CeNIT. We wish them the very best. 



EDITOR'S WORKBENCH

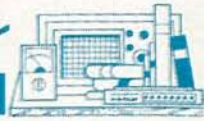

Utility Wars: Mace vs. Norton

What do you do when (accidentally, of course):

- you format your hard disk, or
- you erase a crucial file or directory, or
- you can't boot from your hard disk or even access it, or
- disk operations on certain files seem to be taking longer and longer and longer?

You reach for Mace Gold or Norton 4.5 Advanced—or maybe both. The latest versions of those programs offer several powerful tools for both guarding against disaster and dealing with it when it does occur.

Norton Advanced

Actually, the Norton utilities is a collection of programs designed to make life with PC's easier. Some of those programs have nothing to do with data recovery, but they're useful in their own right. However, the core of the Norton suite has always been NU.EXE. It provides several functions for getting at the data on your disk at various levels. Depending on how you use NU, you can get at physical tracks and sectors, logical (DOS-level) sectors, files, the FAT's (File Allocation Tables), the partition table, and directories.

NU lets you access different structures in different ways: Generally, you can view and edit any structure in hex and ASCII formats; you can also edit higher level structures in an intelligent format. For example, you can change file times and dates without having to compute DOS's packed formats.

One of the most popular uses for NU is to unerase files. The program provides semi-automatic and manual ways of doing so; a separate, fully automated pro-

gram (QU, for Quick UnErase) is also provided. The automatic modes work well on disks whose files are stored in contiguous sectors; with non-contiguous files, some amount of manual intervention is usually required, and NU provides useful tools for doing so. Of course, manual reconstruction is usually only possible with text files, in which you can verify a continuous flow of data.

To help you avoid non-contiguous files, Norton includes a program (SD, Speed Disk) that rearranges your disk so that files are stored contiguously. Other disk and file-oriented utilities include: DS (Directory Sort), which allows you to sort the lists of files in your directories according to time, date, name, and extension, and even to order them manually; DT, which scans the surface of your disk searching for bad sectors, and allows you to lock them out, repair them, move files off of them, etc; SF (Safe Format), a menu-driven replacement for DOS's FORMAT program; and FR (Format Recover), which lets you recover data from an accidentally formatted disk (see Fig. 1).

A number of other utilities are included for listing files and directories, printing files, obtaining information about your system (including the infamous SI rating), wiping files and entire disks completely clean of data (using a government-specified security procedure, if desired), and more. Everything is tied together through an easy to use menu-driven interface (shown in Fig. 1); after learning the programs you can run them from the DOS command line with the proper switches. Invoking a program with a ? (e.g: CSD ?) displays a help screen.

The latest version of the Norton utilities also adds NDD (the Norton Disk Doctor, or NDD), which provides automated recovery from several severe disk problems: a corrupt master boot record, bad partition table, bad FAT, cross-linked files, etc. One really nice feature of NDD is the ability to make any disk bootable; it will rearrange files on disk as necessary to make room for the system files necessary to boot DOS.

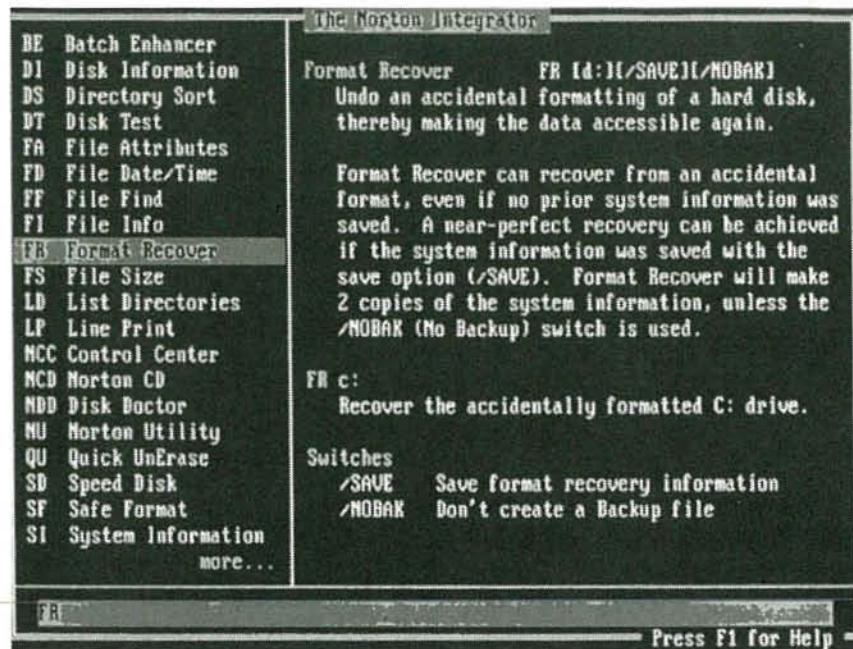


FIG. 1.

The programs all have attractive, easy-to-use screens, and everything is well documented. Now included is *The Norton Troubleshooter*, a 150-page book that contains specific procedures to follow, using various Norton tools, to recover from specific kinds of disasters.

Mace Gold

This package includes programs comparable to the disk-management programs in Norton, skips some of the frillier items, and adds a disk cache, a hard-disk backup program, and programs specifically designed to recover dBASE and text files. Also included is VACCINE, a virus-protection program, and POP, a program like BookMark that allows you to take an occasional "snapshot" of the state of your entire PC, and reload that snapshot later. A sector editor is also included.

Gunfight at the OK Corral

In general, Mace's programs and documentation are less polished than Norton's. In the sector editor, the menus are non-intuitive, and the program's screen output is quite slow.

The real question, of course, is the ability of each to recover data, so I devised several tests to see how well each could do. All tests were run on a generic XT clone

with an ST-225 (20MB) hard disk running PC-DOS 3.30.

Both Mace and Norton offer special programs that save copies of critical system information (boot sector, FAT, and root directory) in a special file with a "signature" that the recovery programs can find even on a disk without directories, FAT's, etc. Normally you run these programs from your AUTOEXEC.BAT file, so at most you'll lose data only since the last time you booted.

Both Mace and Norton offer data-recovery procedures that work both with and without the signature files; each was *much* more successful at restoring data with the signature file than without it.

My first test was to try to restore an accidentally formatted drive. With the signature files present on the disk, Norton's FR (Format Recover) recovered the disk without problem; Mace's UNFORMAT did fairly well, but failed to restore the media descriptor byte in the boot record properly. Norton's NDD, however, was able to correct that fault without manual intervention. Norton gets a slight edge here.

Without the signature file, Norton's format recovery program literally made a mess of the disk. The disk actually contained about 2MB of files, but after running FR, every cluster had been

R-E Computer Admart


Rates: Ads are 2 1/4" x 2 7/8". One insertion \$900. Six insertions \$875. each. Twelve insertions \$845. each. Closing date same as regular rate card. Send order with remittance to **Computer Admart**, Radio Electronics Magazine, 500-B Bi-County Blvd., Farmingdale, NY 11735. Direct telephone inquiries to Arline Fishman, area code-516-293-3000. **Only 100% Computer ads are accepted for this Admart.**

SECRETS OF THE COMMODORE 64



BP135—A beginners guide to the Commodore 64 presents masses of useful data and programming tips, as well as describing how to get the best from the powerful sound and graphics facilities. We look at how the memory is organized, random numbers and ways of generating them, graphics-color-and simple animation, and even a chapter on machine code. Get your copy today. **Send \$5.00 plus \$1.25 for shipping** in the U.S. to **Electronic Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240.**

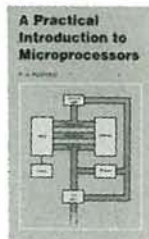A PRACTICAL INTRODUCTION TO MICROPROCESSORS



BP123—Introduces microprocessors by having the reader construct a very simple microprocessor circuit that he can experiment with and thus hopefully gain a clear insight into this complex subject. The completed unit is only intended as an education aid, but can be built inexpensively and many of the parts can be reused for other applications later. Get your copy for **\$5.00 plus \$1.25 for shipping** in the U.S. from **Electronic Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240.**

ICs PROMPT DELIVERY!!!

SAME DAY SHIPPING (USUALLY)
QUANTITY ONE PRICES SHOWN for APRIL 23, 1989

OUTSIDE OKLAHOMA NO SALES TAX

DYNAMIC RAM			
SIMM (1)	256Kx36	80 ns	\$450.00
SIMM	1Mx9	80 ns	265.00
SIMM (2)	1Mx9	85 ns	210.00
SIMM	256Kx9	80 ns	99.00
1Mbit	1Mx1	100 ns	17.95
41256	256Kx1	60 ns	9.95
41256	256Kx1	80 ns	7.95
41256	256Kx1	100 ns	7.95
51258 (3)	256Kx1	100 ns	7.95
41256	256Kx1	120 ns	7.50
41264 (4)	64Kx4	120 ns	9.50
EPROM			
27C1000	128Kx8	200 ns	\$28.50
27C512	64Kx8	200 ns	12.95
27256	32Kx8	150 ns	8.25
27128	16Kx8	250 ns	4.75
STATIC RAM			
62256P-10	32Kx8	100 ns	\$26.50
6264P-12	8Kx8	120 ns	8.50
6116AP-12	2Kx8	120 ns	5.50

OPEN 6 1/2 DAYS, 7:30 AM-10 PM. SHIP VIA FED-EX ON SAT.

SAT DELIVERY INCLUDED ON FED-EX ORDERS RECEIVED BY: The Mid Atk 8:30 PM Fri \$12.25-18

MasterCard/VISA or UPS CASH GOOD.
MICROPROCESSORS UNLIMITED, INC.
24,000 S. Peoria Ave., (918) 267-4961
BEGGS, OK 74421

No minimum order. Please note: prices subject to change! Shipping, insurance extra, up to \$1 for packing materials.

CIRCLE 61 ON FREE INFORMATION CARD

allocated, many files were cross-linked, and the few "recovered" program files I tried to run crashed the machine. Mace did better in the same situation; it found the requisite files and correctly stored them in subdirectories with names UB000, UB001, etc. Files in the root were unrecoverable, but at least the subdirectories and associated files were intact. Score one for Mace.

In another test, I corrupted the first few bytes of the boot record; neither Norton's NDD nor Mace's UNFORMAT was able to properly restore the boot record. Mace=0, Norton=0.

Next I erased (made all bytes 00h) the first copy of the FAT. Without the signature file, NDD claimed to fix the problem, but didn't. I couldn't boot from the disk, and after doing its thing, NDD left both copies of the FAT totally corrupt. With its signature file intact, Mace's UNFORMAT seemed to recover everything, but again left an incorrect media descriptor, which NDD happily fixed. Mace=1, Norton=0.

Other program tests that we ran revealed similar disappointments and inconsistencies.

Conclusions

If you've got anything of value on your hard disk, back it up. Under the best of circumstances,

you may be able to recover some of it; but don't wait until a disaster strikes to buy a copy of either Mace or Norton. Both operate much better with the signature files than without. Norton gets the nod if you're buying pre-disaster; Mace, if you're buying post-disaster. Don't let Norton's NDD loose on a drive with really severe problems.

In case you're wondering, I do weekly backups on an Irwin tape drive, daily backups to floppy, and I often copy on-going projects to temporary disks during the day. Paranoid? You bet! I've lost too many files to the bit bucket.



Duncan's DOS book

If you want to find out how DOS really works, and how to make it work for you, check out Ray Duncan's *Advanced MS-DOS Programming*, second edition. About half the book explains how

DOS loads and controls PC operation thereafter; the second half consists of reference information on BIOS interrupts, DOS function calls, mouse functions, and EMS functions. The book includes numerous example and skeleton programs in both assembler and C. Topics covered include DOS basics, hardware control (keyboard, mouse, and I/O ports), file and disk management, device drivers, and more. OS/2 counterparts of DOS functions are discussed briefly; unfortunately, however, DOS 4.0's new disk structure is not. **CD**

PRODUCTS REVIEWED

- Norton Utilities Advanced Edition Version 4.5 (\$150), Peter Norton Computing, Inc., 2210 Wilshire Boulevard, Santa Monica, CA 90403. (800) 365-1010. (213) 319-2010. **CIRCLE 50 ON FREE INFORMATION CARD**
- Mace Gold (\$149), Paul Mace Software, 400 Williamson Way, Ashland, OR 97520. (800) 523-0258. (503) 488-2322. **CIRCLE 49 ON FREE INFORMATION CARD**
- *Advanced MS-DOS Programming*, second edition (\$24.95), Ray Duncan, Microsoft Press (c. 1988). 16011 NE 36th Way, Box 97017, Redmond, WA 98073-9717. (206) 882-8080. **CIRCLE 48 ON FREE INFORMATION CARD**

OMNIVIEW

continued from page 73

system without a 386 or EMS 4.0 memory, you can only multitask as many programs as will fit in the first 640K of memory simultaneously. But on a 386 (or an 8088 or 80286 with EMS 4.0 memory), you can multitask several large programs.

Even without multi-tasking, OmniView can be useful by letting you switch among several programs quickly. For example, suppose you run a small business from your home, selling microprocessor-based widgets. You use a spreadsheet to track your accounts, a database program to keep your inventory, a word processor to write business letters, and a telephone manager to dial and log your calls. With OmniView and the proper memory, all four could be loaded in memory ready for instant access. So when Mr. Jones calls up wondering where his order of widgets is, you could check his account and your inventory—all while he's on the phone.

After you gain a little experience with OmniView, you can skip loading programs by menu and create a batch file that will load your desired system configuration automatically with just a few keystrokes. You can still hot-key among your programs.

Inside OmniView

What's going on beneath the surface that allows you to do those things? To understand the answer to that question, you must understand the differences between the three types of memory: conventional, extended, and expanded. Briefly, conventional memory is that in the first 640K; extended memory is located above the 1-megabyte boundary, and is addressed linearly by the 80286 and 80386; expanded memory is bank-switched in 16K chunks beneath the 1-megabyte boundary. Expanded memory is available on all three members of the Intel family; with a proper memory manager, extended memory on a 386 can function as expanded memory (see Fig. 2).

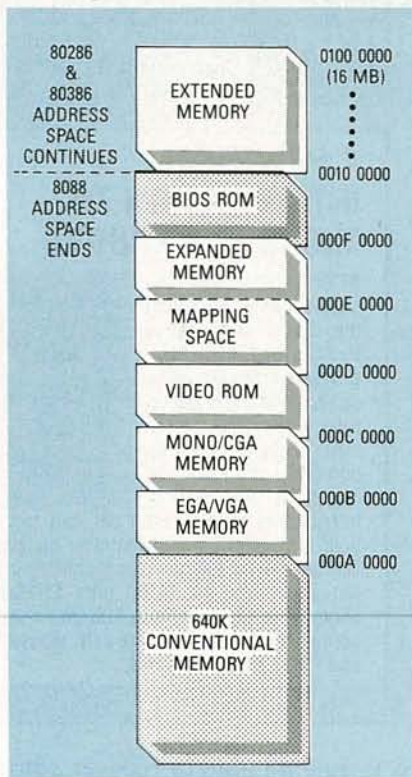


Fig. 2. MEMORY MAP of Intel microprocessors. Expanded memory is available on the 8088/86, the 286, and the 386. Extended memory is available only on 80286 and 80386 microprocessors; on the latter it can function as expanded memory.

Internally, OmniView consists of 5 major modules, as shown in Fig. 3. Basically, the task scheduler determines when each program gets its turn to do its thing. The device-driver module provides control (and emulation, when necessary) of devices including keyboard, screen, mouse, and printer. The message-passing module allows tasks to communicate with each other through a standard mechanism. The memory manager allo-

cates memory both to OmniView itself and to the tasks that it controls. Last, the applications-interface module ties the others together, making OmniView's functions available to external applications programs.

The user interface (i.e., the menu for starting and running programs) is not an integral part of OmniView. Rather, it's simply an applications program that, through the use of the OmniView Applications Program Interface (OAPI), makes OmniView's functions available to the user. As such, it can easily be replaced, and is not necessary at all in some applications.

Although OmniView contains 5 major modules, two of them could easily be broken down into other, more distinct units. For example, the device-driver module actually contains as many parts as there are devices to control: one for the screen, one for the keyboard, etc. In addition, the memory manager delegates much of its work to an EMS 4.0 driver if one is present.

This modular architecture has a number of advantages. Since OmniView supports, but does not require, an 80386, it can be used across a wide range of machines. Other operating environments are designed specifically for, and are therefore limited to running on, the 80386.

Of course, with a proper memory manager, OmniView really shines on a 386, because several features of the 386 simplify the process of building multitasking software: hardware support for task control blocks, segmented and paged memory manage-

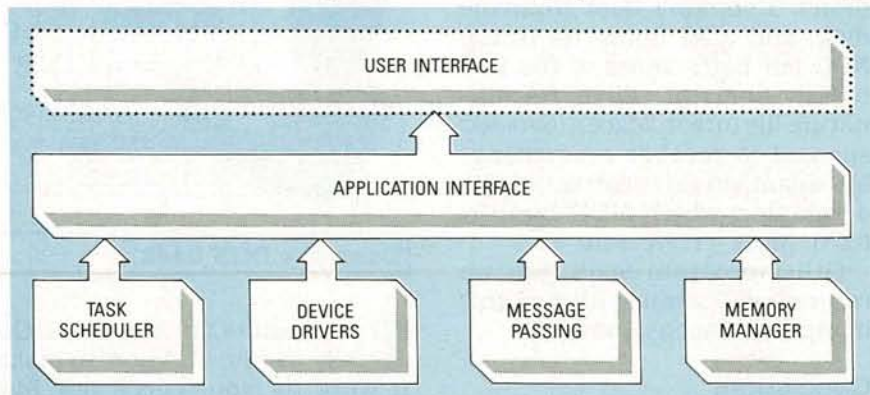


Fig. 3. OMNIVIEW CONSISTS of four modules tied together by an application interface, and an optional user interface.

ment, virtual 8086 (V86) mode, and hardware I/O protection. OmniView uses all of those; let's talk about memory management first.

Memory management

Several 386 memory managers are available commercially, but OmniView has been optimized to work with 386^{MAX}. In addition to emulating EMS 4.0 memory using plain extended memory, 386^{MAX} includes special "hooks" that OmniView uses to virtualize direct screen accesses, to arbitrate between processes that service hardware interrupts, and to allow multitasking with 32-bit protected-mode applications.

For example, by using the EMS 4.0 functions available in 386^{MAX}, OmniView can run multiple programs simultaneously, periodically switching them to conventional memory from extended memory. OmniView does so using the 386's memory paging tables to allocate a desired number of 4K pages, and then mapping those pages in or out of conventional memory as needed. Simply by loading a new value into register CR3, the Page Directory Base Register (PDBR), entire memory-mapped "contexts" can be loaded into conventional memory nearly instantaneously.

386^{MAX} makes that function available to system-level software through the Alternate Mapping Register Set (AMRS) concept, which is part of the EMS 4.0 specification. 386^{MAX} implements that operation very efficiently, so OmniView can switch memory-mapped contexts fast enough to allow programs running in extended memory to service as many as 1000 hardware interrupts per second on a 20-Mhz 80386.

The point is that multiple programs, which would not normally fit together in conventional memory, can service hardware interrupts with no knowledge that OmniView is switching them in and out of memory many times per second.

I/O port virtualization

Since the typical DOS developer designs his program for a

single-tasking operating system, he often assumes (and rightly so) that the program has complete control of the hardware on which it is running. For that reason, many programs access display memory and other hardware directly, without considering that they may be in competition for those resources. Of course, by doing so, programs that would otherwise run sluggishly run much faster. Those programs, labeled "ill-behaved" include the vast majority of most popular commercial applications.

What's so bad about ill-behaved programs? For example, assume two ill-behaved applications are running simultaneously without proper control software. Each can do whatever it wants whenever it wants, so the video display is liable to be visual mishmash, as each writes its data to the screen. Even worse, if both tried to write to disk simultaneously, the FAT (File Allocation Table or directory structure could be corrupted, rendering the disk useless.

However, the 386 provides a number of built-in mechanisms that, when properly used, can help prevent those types of disasters—and the OmniView/386^{MAX} combination takes advantage of those mechanisms to tame most ill-behaved programs.

To facilitate protection, 386^{MAX} provides hooks that OmniView uses to "virtualize" screen and I/O access. Using those hooks, OmniView can control video memory mapping, and it can fool programs running in the background into thinking that they have access to actual video memory. In truth, background programs have access only to a virtual screen storage area, as shown in Fig. 4, which can later be mapped into memory via the 386's paging mechanism to its normal address.

Other hooks can prevent a program from accessing the CRTIC (CRT Controller) hardware, and even from moving the cursor directly. By using the 386's I/O-port privilege map, all accesses to the CRTIC cursor registers can be trapped and simulated without affecting the actual hardware.

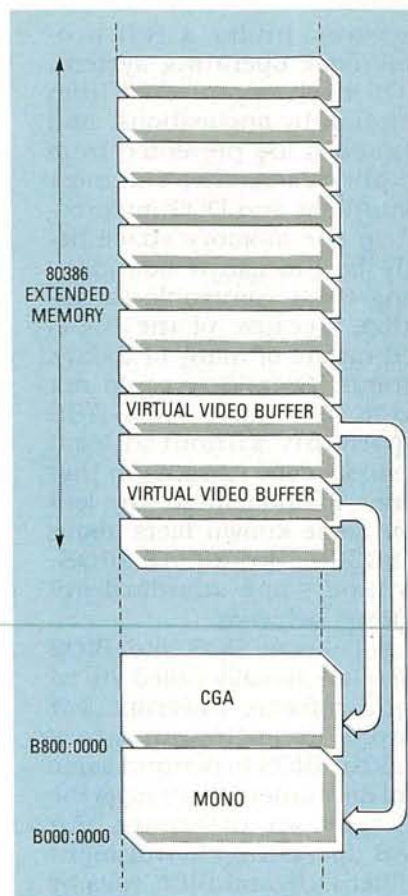


Fig. 4. EXTENDED MEMORY ON AN 80386 can be mapped in 4K chunks anywhere in memory. For example, two programs can write to virtual video buffers, which can be mapped to the normal addresses at the appropriate time.

Again, that allows an invisibly running program to think it is accessing the hardware directly, when in fact it is only modifying or reading its virtual position, as recorded by OmniView.

VCPI

OmniView/386^{MAX} also supports the Virtual Control Program Interface (VCPI), which provides a standard by which 32-bit protected-mode programs and real-mode (DOS) programs can multitask together. The VCPI's chief claim to fame is that it works around the limitation that only one program can control an 80386 in protected mode at a time. By defining a way for protected-mode programs to cooperate with each other, the standard helps bring OmniView/386^{MAX} into the realm of advanced, protected-mode operating systems (UNIX, OS/2).

However, under a full protected-mode operating system, the OS itself is protected from corruption by applications, and applications are prevented from corrupting each other. But most of OmniView and DOS must co-exist in the memory space beneath the 1-megabyte boundary, leaving them vulnerable to corruption. Because of the ill-behaved nature of many of today's programs, OmniView could not provide its almost 100% DOS compatibility without at least some of its code running in that manner. To understand why, let's review some known facts about the 80386, the XT/AT BIOS, DOS, and some standard applications' behavior.

As you know, DOS and BIOS services are usually called via issuing a software interrupt. For example, executing an `INT 13H` causes the BIOS to perform some sort of disk function; `INT 21H` is the DOS services interrupt. An 80386 operating environment can filter DOS and BIOS calls by trapping the software interrupt and determining at that time whether to emulate or pass on the original call.

The problem is that real-life programs often don't use software interrupts to access system services. Rather, many programs actually use `FAR CALL` and `FAR JUMP` instructions to pass control.

For example, a memory-resident TSR (Terminate and Stay Resident) typically "chains" an interrupt. `INT 9` (the keyboard interrupt) might be chained by a keyboard-enhancement utility that would watch for a special hot key. Each time the user presses or releases a key, an `INT 9` is generated. The TSR would check to see if the defined key (or combination) was struck. If so, the program might substitute its own keystroke or perform some other action; otherwise, it would execute a `FAR JUMP` (or `CALL`) to the original BIOS code. Things become even more complicated when several programs "chain" an interrupt in that manner.

The problem is that calls and jumps are not trapped by the 386's support mechanisms when it is running in V86 mode. If the

objective is to filter only the system service, without hampering the application program's filter, then a multitasking system must have V86 code that takes control only at the appropriate time.

Although OmniView must always have some code in the V86 address space (i.e., beneath the 1-megabyte mark), the program occupies only 48K of RAM. And since it can load into EMS memory that is mapped above the screen buffers (refer back to Fig. 2), its affect on the amount of contiguous DOS memory is minimized. And note that that is not a 386-specific feature; 8088/86 and 286 machines with EMS 4.0 memory can also benefit from it.

By way of contrast, other operating environments go to great lengths to keep the environment's own code protected and out of conventional memory. One

Special Discount

SunnyHill Software has arranged special 30% discounts off the list prices of OmniView and 386^{MAX} for readers of **Radio-Electronics**. OmniView normally lists for \$89.95; the discount price is \$62.95. 386^{MAX} normally lists for \$74.95; the discount price is \$52.45.

To order, call the number below. Be sure to mention this article. The discount expires on December 31, 1989. SunnyHill also has separate documentation on the OmniView API; contact the company for details.

For more information on OmniView (formerly called TaskView), see Editor's Workbench, May 1988. For more information on the 386 microprocessor, see the January, February, and March 1989 issues. And stay tuned for an article describing the construction of a low-cost 386SX motherboard.


- OmniView, SunnyHill Software, P.O. Box 33711, Seattle, WA 98133-3711. (800) 367-0651 or (206) 367-0650.
- 386^{MAX}, Qualitas, Inc., 8314 Thoreau Drive, Bethesda, MD 20817-3164. (301) 469-8848. Note that the discount is available only through SunnyHill.

approach, taken by VM/386, executes most of the operating environment in protected mode and loads a separate copy of DOS in its own protected V86 partition for each program running under it. However, there are problems inherent in that approach. Sharing one disk by multiple copies of DOS, each of which maintains a separate FAT, is difficult. Not only does it require a great deal of overhead to arbitrate between the different copies of DOS, but running certain programs together may corrupt disk files.

So, rather than rewrite DOS completely and risk the inevitable incompatibilities that have plagued DOS replacements, OmniView shares one copy of DOS among all programs running under it. Therefore, both OmniView and DOS must remain accessible to the programs that run under them. That means that a program that writes to memory outside that which it has been allocated may be able to crash the entire system. However, on a 386, OmniView is able to prevent a program running in one partition from corrupting the memory space of another program, of DOS, or of OmniView.

Coming attraction

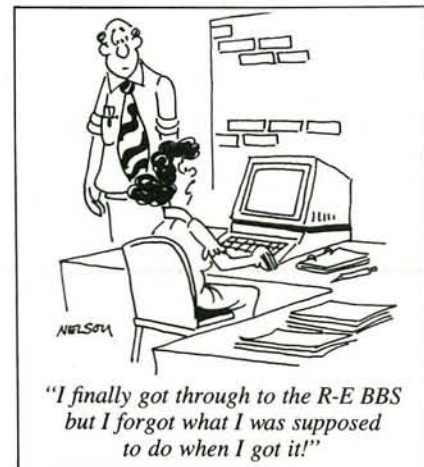
Next time we'll delve deeper into the internal structure of OmniView, and discuss use of the OAPI. In the process, we'll create a program that requests information about presently executing tasks, uses efficient timed delays, and continuously displays the current tasks and available OmniView resources. ♦♦♦



BUILD AN 80386SX MOTHERBOARD

Part II

BERNARD A. McILHANY

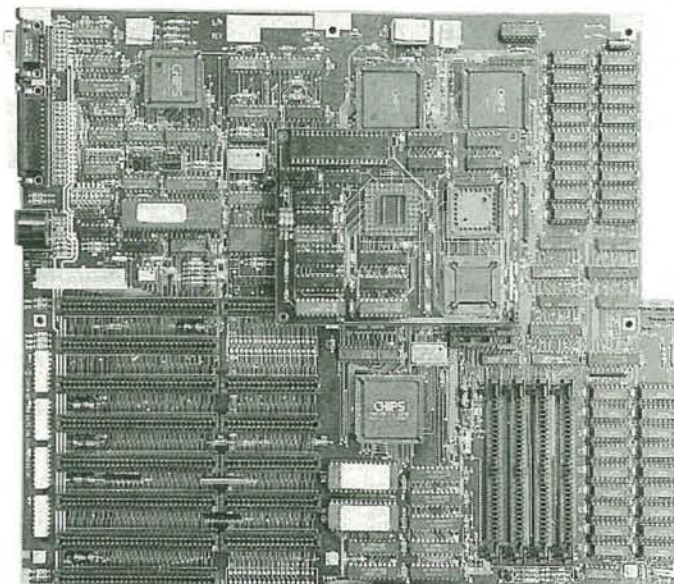

Before starting construction of the PT-386-PLUS, here are a few cautions. The PC board is a four-layer board, and soldering a four-layer board requires a hotter soldering iron than usual. A temperature-controlled iron set at 700° is preferable, but if one is not available, use at least a 50-watt iron. Use of a smaller iron can overheat the board because of the long time required to properly heat the connections. The soldering iron should also have a small tip because of the closely spaced connections on the board. If you have limited soldering experience, we suggest that you get assistance from someone with more experience. Otherwise, buy the assembled board.

Most of the board must be built before any testing can be performed. Use the Parts-Placement diagram (shown in Fig. 1) and the Parts List to locate where each part should be mounted. Figure 2 shows a finished motherboard.

Start construction by installing all resistors, including the DIP and SIP packages. Note that each DIP and SIP pack has a mark that designates pin 1. The board itself has different marks for each type: for the DIP resistors, the board shows a square notch at the pin-1 end, but for the SIP resistors, the pin-1 end is shown on the board with an open square. Make sure that you install the pin-1 ends correctly!

Next, install all of the capacitors, except the variable capacitor (C60). Observe the polarity of the electrolytic and tantalum capacitors as you solder them.

Next, install the IC sockets, including the PGA for the microprocessor (IC57) and the five PLCC sockets (IC43, IC45, IC48, IC61, and IC75). NOTE: No socket is installed at position IC900. When installing the PLCC sockets, be certain the pin-1 designation faces the dot on the board. Although at first glance the PLCC sockets may appear square, they are not. Not only does the socket have orientation (an angled corner and a "1" indicating pin 1), but the IC's themselves also have orientation, indicated by an indented dot or dimple, as well as the angled corner. Of course, the IC's orientation marks will mean nothing if the socket is installed incorrectly!

Install the SIMM sockets next. The sockets should be oriented so that their outlines match the ones on the board.

Now mount and solder the 36- and 62-pin expansion-slot card-edge connectors (J1-J16). Note that nothing is installed in positions J2 and J16; the absence of connectors in those positions leaves space for older 8-bit expansion cards.

Next, install the oscillators and crystals. The oscillators should be soldered directly to the board. Once again, be sure to observe the pin-1 orientation of the oscillators, usually a square corner or a dot (or both).

The transistors and diodes are next: install the flat side of the transistors facing the line marked on the board. The band-

ed end of the diodes should correspond with the line on the board.

Solder the jumper headers (P1-P4, P7-P10), the variable capacitor (C60), the keyboard connector (J17), and the power connector (P6) to the board next. The power connector should be installed with its back side (the high plastic part) toward J15 (an expansion-slot connector).

Using solid wire or scrap left over from cutting off the resistor leads, solder 37 jumper wires in positions CH-1 through CH-37.

At this point, all of the parts on the board that require soldering should have been installed. We suggest that you clean the board of all surplus flux using an aerosol methylene chloride flux remover and cleaner, available from most electronics stores. Now carefully inspect the board for solder bridges and unsoldered pins. Defluxing the board is recommended because excess flux may hide unsoldered connections or hairline solder bridges.

Now insert all IC's into the appropriate sockets. Be careful not to accidentally fold any pin under the IC as you insert it into the socket! Install 512K of DRAM in Bank 0 (near the front left corner of the board); that's the minimum required to test the board.

When we continue next time, we'll discuss how the 80386SX daughterboard is built and installed. Then we'll show you how to configure the system, and finally, we'll power it up and put it to work! ▶◀

Parts List—80286 MOTHERBOARD

Resistors

All resistors are 1/4-watt, 5%.

R1, R2	150 ohms
R3, R46	2 megohms
R4, R15, R17, R22, R29, R32, R35, R37-R40, R42, R43, R48, R51, R902-R904	4700 ohms
R5, R12, R21, R34, R55, R56, R900, R901, R905, R906	10,000 ohms
R6	51,000 ohms
R7, R23, R33, R47	1000 ohms
R8, R13	10 ohms
R9, R10	1 megohm
R11, R14, R16, R18, R19, R24-R28, R41, R44	33 ohms
R20, R50, R907	not used
R30	620 ohms
R31	51 ohms
R36, R45, R52, R57	330 ohms
R49	2200 ohms
R53, R54	470 ohms

Resistor packs

RP1, RP2, RP4, RP5	33 ohms × 8, 16 pins, DIP
RP3	33 ohms × 4, 8 pins, SIP
RP6, RP10	10,000 ohms × 9, 10 pins, SIP
RP7, RP9, RP11, RP13	10,000 ohms × 7, 8 pins, SIP
RP8	150 ohms × 7, 8 pins, SIP
RP12	4700 ohms × 7, 8 pins, SIP
RP14-RP17	330 (or 470) × 14, 16 pins, DIP

Capacitors

C1, C69, C130, C148, C150-C152	22 μF, 16 volts, aluminum electrolytic
C2-C6, C16, C26, C28-C30, C38, C41-C43, C54-C57, C61, C62, C65-C68, C70, C72, C73, C75-C101, C103-C111, C114, C116, C117, C120, C123, C126, C128, C129, C134-C145, C149, C153-C159	0.1 μF, 50 volts, ceramic
C7-C15, C17-C24, C27, C31-C37, C40, C44-C52	0.33 μF, 50 volts, ceramic
C25	22 pF, 5%, 50 volts, mono

C53	4700 pF, 50 volts, ceramic
C58, C59, C63, C64, C112, C113	10 pF, 10%, 50 volts
C60	5-50 pF variable
C71	0.047 μF, 50 volts, ceramic
C74	4.7 μF, 20%, 15 volts, aluminum electrolytic
C102	27 pF, 5%, 50 volts, ceramic
C115, C118, C119, C121, C122, C124, C125, C127, C132, C133	100 pF, 5%, 50 volts, mono
C131	10 μF, 25 volts, tantalum
C146, C147	47 pF, 5%, 50 volts, ceramic

Semiconductors

IC1-IC18, IC21-IC29, IC31-IC39	DRAM, 256K × 1, 100 ns
IC19, IC20, IC41	74F244
IC30	MC14069
IC40, IC42-74F240	
IC43	82C215
IC44	74ALS245
IC45	82C212
IC46	74F00
IC47	32-MHz oscillator
IC48	82C211
IC49, IC901	74F74
IC50	.80287 or cable to daughterboard
IC51	24-MHz oscillator
IC52, IC53	74LS373
IC54, IC55, IC56, IC64, IC65, IC69, IC71, IC77, IC85	74LS245
IC57	.80286 or plug from daughterboard
IC58, IC900	not used
IC59	74F573
IC60	74F543
IC61	82C206
IC62, IC63	27256-17 BIOS EPROMS
IC66, IC73, IC76	74LS244
IC67	74F08
IC68	PAL16L8A
IC70	74LS30
IC72	9.6-MHz oscillator
IC74	WD37C65
IC75	82C605
IC78	.8742AH keyboard controller


IC79	74ALS04
IC80, IC81, IC84	MC1489
IC82, IC90	7407
IC83	TL7705
IC86, IC88	MC1488
IC87	74LS14
IC89	74LS05
IC902	74F02
IC903	74F11
Q1	2N3906
Q2	2N3904
D1, D2	1N4148
DL1	100-ns delay line
SIMMO-SIMM3	DRAM, 30 pins, SIMM, 1024K × 9, 100 ns

Other components

Y1	32.768-kHz crystal
Y2	14.318-MHz crystal
Y3	20-MHz crystal
Y4	1.8432-MHz crystal
J1, J3, J5, J6, J9, J11, J13, J15	2 × 31 edge connector (bus)
J2, J7, J14	not used
J4, J6, J8, J10, J12, J16	2 × 18 edge connector (bus)
J17	5-pin DIN keyboard connector
P1, P2	1 × 4 header strip
P3	1 × 5 header strip
P4, P9	2 × 5 header strip
P5	not used
P6	1 × 12 power connector
P7	2 × 17 header strip
P8	1 × 2 header strip
P10	2 × 13 header strip
W1, W6, W7, W8, W14	1 × 2 header strip
W2, W5, W9, W10	not used
W3, W4, W12, W13, W15, SW1	1 × 3 header strip
W11	2 × 4 header strip

Circuit board



IC Sockets

1 8-pin DIP 18 14-pin DIP 36 16-pin DIP
23 20-pin DIP 1 24-pin skinny DIP 2 28-pin DIP 3 40-pin DIP 1 68-pin PGA 1 68-pin PLCC 4 84-pin PLCC 4 30-pin SIMM (ANGLE). 


ORDERING INFORMATION

Ordering information appeared in the June issue of Computer Digest and will be repeated next month.

PC SERVICE

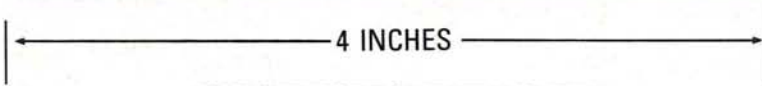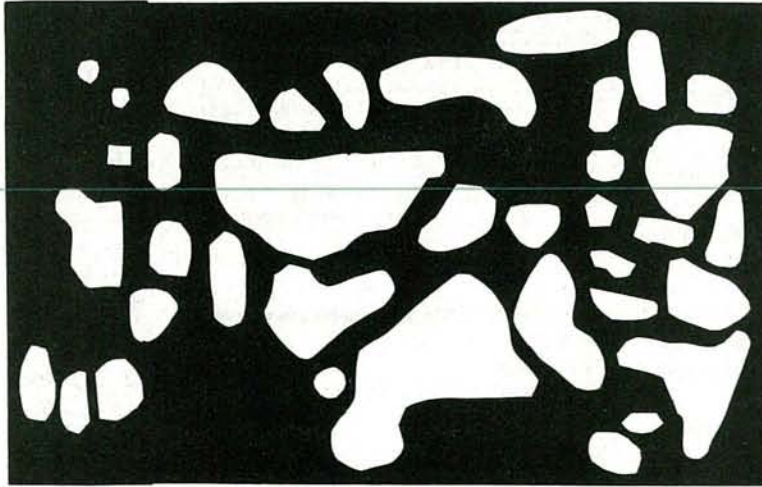

COMPONENT SIDE OF TV TRANSMITTER.

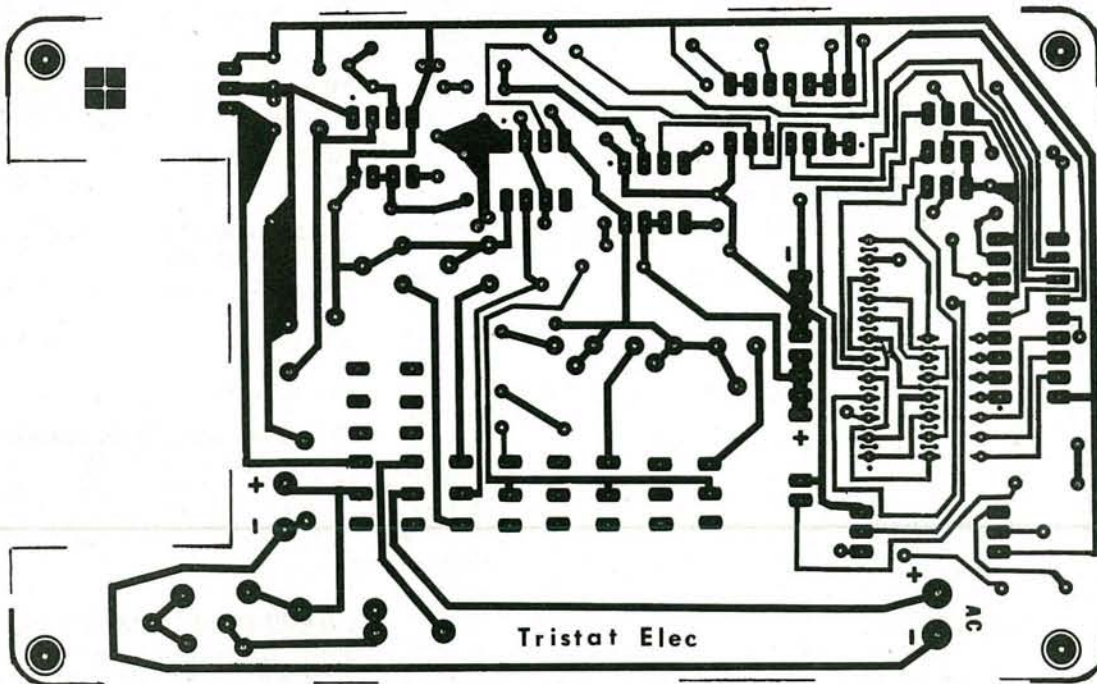

THE CAPACITANCE METER'S FOIL PATTERN.

R-E Engineering Admart

Rates: Ads are 2 1/4" x 2 7/8". One insertion \$900. Six insertions \$875. each. Twelve insertions \$845. each. Closing date same as regular rate card. Send order with remittance to **Engineering Admart**, Radio Electronics Magazine, 500-B Bi-County Blvd., Farmingdale, NY 11735. Direct telephone inquiries to Arline Fishman, area code-516-293-3000. *Only 100% Engineering ads are accepted for this Admart.*

MIDI PROJECTS



BP182—MIDI interfacing enables any so equipped instruments, regardless of the manufacturer, to be easily connected together and used as a system with easy computer control of these music systems. Combine a computer and some MIDI instruments and you can have what is virtually a programmable orchestra. To get your copy send \$6.95 plus \$1.25 for shipping in the U.S. to **Electronic Technology Today Inc.**, P.O. Box 240, Massapequa Park, NY 11762-0240.

FCC LICENSE PREPARATION

The FCC has revised and updated the commercial license exam. The **NEW EXAM** covers updated marine and aviation rules and regulations, transistor and digital circuitry. **THE GENERAL RADIOTELEPHONE OPERATOR LICENSE - STUDY GUIDE** contains vital information. **VIDEO SEMINAR KITS ARE NOW AVAILABLE.**

WPT PUBLICATION
979 Young Street, Suite A
Woodburn, Oregon 97071
Phone (503) 981-5159

CIRCLE 183 ON FREE INFORMATION CARD

Surface Mount Chip Component Prototyping Kits— Only \$49.95



CC-1 Capacitor Kit contains 365 pieces, 5 ea. of every 10% value from 1pf to .33µf. **CR-1 Resistor Kit** contains 1540 pieces; 10 ea. of every 5% value from 10Ω to 10 megΩ. Sizes are 0805 and 1206. Each kit is **ONLY \$49.95** and available for **Immediate One Day Delivery!**

Order by toll-free phone, FAX, or mail. We accept VISA, MC, AMEX, COD, or Pre-paid orders. Company P.O.'s accepted with approved credit. Call for free detailed brochure.

COMMUNICATIONS SPECIALISTS, INC.
426 West Taft Ave. • Orange, CA 92665-4296
Local (714) 998-3021 • FAX (714) 974-3420
Entire USA 1-800-854-0547

CIRCLE 182 ON FREE INFORMATION CARD

DRAWING BOARD

continued from page 29

together through an inverter and eliminate one column in the table. We can tie the two SEL inputs together as well since their state is only important when the chip is enabled. By re-arranging the truth table slightly we'll wind up with the one shown in Fig. 4, and that, as you should realize, is simple to implement because it's just counting up in a plain binary.

Not only that, but we can use a straight binary counter and use the "C" output to toggle the reset. Putting that into practice will produce a circuit like the one shown in Fig. 5. You should work out the logic in your own mind to make sure that you understand what's going on there.

The last part of the control logic is the counter and that can be any binary counter. You can use a 74LS93, 4040, half a 4520 or 4518, half a 74LS393, or just about anything that can count up to four in binary. The 4040 in Fig. 5 is a good choice because it's easy to use and is a mainstream CMOS part, but don't hesitate to use something you happen to have lying around.

The circuit we've come up with

will fill all the design criteria we laid out earlier but it has three sections we still have to go over. The first is the clock, the second is the input latching, and the third is the use of pass transistors to drive the cathodes.

Some time ago we spent several columns talking about the ins and outs of scan oscillators and we found that you can use any frequency as long as it's high enough to eliminate flickering. Anything over 10 kHz or so will fill the bill and any oscillator capable of driving the clock inputs will be as good as any other. I've built mine out of a pair of inverters but if your application has a handy clock line that fills those minimal requirements, you may use that.

Input latches aren't really necessary but they can be useful if the data you want displayed doesn't stay around too long. That would be the case if you want to snatch bus data when a certain pulse shows up elsewhere in the circuit.

I'm using 4508 octal latches but only because I happened to have a bunch of them in the parts box. Notice that I didn't say "junk-box"—the only thing junk parts are good for is building junk. One thing that's nice about 4508's is that they're really two separate four-bit latches in a single package.

The last thing to talk about is the use of pass transistors. If you put together the circuit we showed you in May you probably noticed that the display was rather dim. There's nothing you can do about the scan time, but it is possible to zip more current through a digit when it's selected. That is exactly what the pass transistors are doing.

One disadvantage of that approach is that the brightness of the digit will depend somewhat on how many segments are being lit, but it's not enough of a problem to make the use of individual current-limiting resistors in your circuit an absolute necessity.

Breadboard the circuit of Fig. 5 and feed the sixteen inputs with two cascaded 4040's. You'll see the display count up in true binary, and you'll also know that the circuit works. The circuit is extremely useful and it's well worth the time to generate a PC board for it. The complexity is such that it will more than likely require a double-sided board, but once you've got it done, you can make as many of them as you want. I know it's not easy to produce a double-sided board, but there are some tricks you can use to make the job easier. We'll be looking at that, and some other things as well, next time. **R-E**

MARKET CENTER

CABLE-TV AT ITS BEST

SCIENTIFIC ATLANTA:

Models 8500-8550-8580 ... \$275.00

SA-3 [Add-On Descrambler] ... \$ 99.00

JERROLD:

SB-3 [Inband Gated Sync] ... \$ 74.00

TRI-BI [Trimode/Bistate] ... \$ 95.00

OAK:

M-35B [Combo W/Vari-sync] ... \$ 99.00

N-12 [Add-On W/Vari-sync] ... \$ 89.00

HAMLIN:

MLD-1200 [Add-On] ... \$ 89.00

ZENITH: [Z-TAC Descrambler] ... \$169.00

CONVERTERS: [80-Channels] ... \$ 95.00

N.A.S. INTERNATIONAL
LONG BEACH, CA (213) 631-3552

DEALER DISCOUNT
ON <8> UNITS

DISTRIBUTOR DISCOUNT
ON <10> UNITS

GLOBAL CABLE NETWORK


YOUR cable TV converters and descramblers bargain headquarters: Zenith, Scientific Atlanta, Tocom. Hamlin combo w/remote \$70, Jerrold combo w/remote \$130.00, Oak M35B \$60.00. Visa-M/C-COD. Order yours today (415) 584-1627.

FOR SALE

PHOTOFACT folders, under #1400 \$4.00. Others \$6.00. Postpaid. LOEB, 414 Chestnut Lane, East Meadow, NY 11554.

GREAT buys! Surplus prices, ICs, linears, transformers, PS, stepping motors, vacuum pump, phototransistor, meters, LSASE, FERTIK'S, 5400 Ella, Phila., PA 19120.

CONSOLIDATED ELECTRONICS

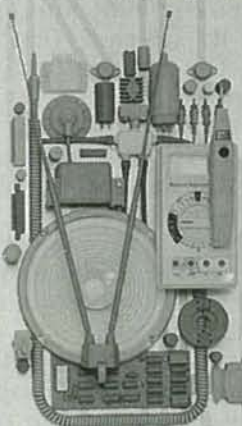

CONSUMER & INDUSTRIAL ELECTRONICS CATALOG • 17TH EDITION

THE ULTIMATE ELECTRONICS CATALOG.

Order your 260 page catalogue packed with over 10,000 money saving electronic parts and equipment. Send \$3.00 check or money order, or call 1-800-543-3568 today and use your MasterCard or Visa.
Consolidated Electronics, Incorporated
705 Watervliet Ave., Dayton, Ohio 45420-2599

NAME

ADDRESS

CITY

STATE

ZIP

CIRCLE 70 ON FREE INFORMATION CARD

DESCRAMBLERS. All brands. Special combo Jerrold 400 and SB3 \$165. Complete cable descrambler kit \$39. Complete satellite descrambler kit \$45.00. Free catalog. **MJM INDUSTRY**, Box 531, Bronx, NY 10461-0531.

BANDSTOP filters — Clear up channels affected by interference. Channels 2, 3, 4, 8, 14, 15, 16, 17, 18, 19, 20, 21 and 22 available. \$20 each. **dB ELECTRONICS**, PO Box 8644, Pembroke Pines, FL 33084.

T.V. tunable notch filters. Free brochure. **D.K. VIDEO**, Box 63/6025, Margate, FL 33063. (305) 752-9202.

CABLE descrambler liquidation. Major makes and models available. Industry pricing! (Example: Hamlin Combo's, \$44 each...minimum 10 orders). **Dealers only!** Call **WEST COAST ELECTRONICS**, (818) 709-1758.

SENIOR Prom — For all your EPROM needs! Duplication, programming, supplies. Great Prices! Write for details. **SENIOR PROM**, 11 Manor Ridge Drive, Princeton Junction, NJ 08550.

REDUCED 75% Diehl Mark V-Scanner \$249. Diehl Mark III \$99. **New. WEEC**, 2805 University Ave., Madison, WI 53705. (608) 233-9741, (608) 238-4629.

COMMUNICATIONS radio, electronic equipment, sales service, FCC licensed, catalog. **RAYS**, 2025 Moline, Ft. Worth, TX 76117. (817) 831-7717.

CB RADIO OWNERS!

We specialize in a wide variety of technical information, parts and services for CB radios. 10-Meter and FM conversion kits, repair books, plans, high-performance accessories. Over 12 years of satisfied customers! Catalog \$2.

CBC INTERNATIONAL
P.O. BOX 31500RE, PHOENIX, AZ 85046

RADIO amateur (HAM) education. Learn at home or in your car. VHS Video or audio cassettes. Easy to obtain license. Free information. **AMATEUR RADIO SCHOOL** 2350 Rosalia Drive, Fullerton, CA 92635.

ALUMINUM image transfer process, your artwork to aluminum. Write: **J & E ENTERPRISES**, 2457 N. Marmora, Chicago, IL 60639.

TEST equipment pre-owned now at affordable prices. Signal generators from \$50. Oscilloscopes from \$50, other equipment, including manuals available. Send for catalog **J.B. ELECTRONICS**, 9518 Grand Ave., Franklin Park, IL 60131. (312) 451-1750.

RENTAL movie stabilizer Connect between VCRs or to monitor. Satisfaction guaranteed. \$69.95, \$4 handling. 1 (800) 367-7909.

TUBES: "oldest," "latest." Parts and schematics. SASE for lists. **STEINMETZ**, 7519 Maplewood Ave., RE, Hammond, IN 46324.

IS it true... Jeeps for \$44 through the government? Call for facts! (312) 742-1142 Ext. 4673.

ELECTRONIC components. Free 192 page catalog including capacitors, resistors, relays, connectors, soldering equipment and supplies. **BOX 699**, Mansfield, TX 76063. 1 (800) 992-9943.

CABLE converters and descramblers. Call or write for free catalog. Includes Jerrold, Oak, Zenith, Hamlin, Scientific Atlanta, many more. **NU-TEK ELECTRONICS**, 5114 Balcones Woods Dr. #307, Suite 298, Austin, TX 78759-5212. (512) 250-5031.

MICROWAVE TV RECEIVERS 1.9 to 2.7 GHz

2 CH Compact Dish System - \$77.95
5 CH Dish System - \$93.95
12 CH Yagi (Rod) System - \$123.95
30 CH Dish System - \$163.90 Yagi - \$183.90
SUN MICROWAVE INT'L. INC. Send \$1.00 for catalog on these and other line video products.
P.O. BOX 34522
PHOENIX, AZ 85067
(602) 230-0640
VISA/MC/COD QUANTITY DISCOUNTS LIFETIME WARRANTY

RARE, dual element, magnetodiodes with flux concentrator; 3 for \$10 with datasheets. Allow 3-4 weeks for postpaid delivery. **PROCTOR**, 1507 Brooks, Rosenberg, TX 77471.

GATED Pulse descrambler as described in December '88 Radio-Electronics article. Partial kit \$25.00. Works on in-band, out-band, AM or FM reference and pilotless systems. Canadian orders add \$2.00 shipping. Cannot accept Ariz. orders. Allow 4 to 6 weeks for delivery. **CYBERNET-WORKS**, Box 41850, Phoenix, AZ 85080.

CABLE descramblers, Tocom, Zenith Z-Tac, Oak RTC 56, Jerrold 400-450, SA 8580, all remote controlled, add ons, MLD 1200, SB 3, SA-3, Pioneer, Tri Bi. Special 5 pak price, 5-Oak M35B \$300.00, 5-TC35 \$300.00, 5 MLD 1200 \$245.00. Full Warranty. **S.A.C.**, (702) 647-3799.

Quality Microwave TV Antennas

Multi-Channel 1.9 to 2.7 GHz. 40dB Gain
30-Channel System complete \$149.95
12-Channel System complete \$104.95
2-Channel System complete \$79.95

Phillips-Tech Electronics

P.O. Box 8533 • Scottsdale, AZ 85262
(602) 947-7700 (\$3.00 Credit all phone orders!)

LIFETIME WARRANTY

MasterCard • Visa • COD's • Quantity Pricing

AUTO alarm module. Exit/Entry delay, on-board siren driver, unlimited inputs. Complete with wiring, hook-up diagram. \$14.95. Remote-controlled alarm kit. Info \$2.5. **CHALKER**, 8 Manor House Lane, Uxbridge, MA 01569.

SURPLUS ELECTRONICS. New giant wholesale catalog. Hundreds of amazing bargains. \$2. Box 840, Champlain, NY 12919.

SOLAR electric systems. Discount prices. **SUN POWER-TEXAS**, PO Box 2788A-R, Freeport, TX 77541. (409) 233-8350.

CABLE TV converters: Jerrold, Oak, Scientific Atlantic, Zenith & many others. "New MTS" stereo add-on: mute & volume. Ideal for 400 and 450 owners! 1 (800) 826-7623, Amex, Visa, M/C accepted. **B & B INC.**, 4030 Beau-D-Rue Drive, Eagan, MN 55122.

LASER Listener II, other projects. Surveillance, descrambling, false identification, information. Plans, kits, other strange stuff. Informational package \$3.00 refundable. **DIRIJO/BOND ELECTRONICS**, Box 212, Lowell, NC 28098.

CABLE TV converters and descramblers. We sell only the best. Low prices. SB-3 \$79.00. We ship C.O.D.. Free catalog. ACE PRODUCTS, PO Box 582, Dept. E, Saco, ME 04072. (207) 967-0726.

RESISTOR cabinet — 5000 quality 1/4w 5% carbon film resistors. 100 per value in 50 labeled drawers. \$79.95 plus \$5.00 shipping (check, MO). **KENTEX INDUSTRIES**, PO Box 1314, St. Charles, MO 63302.

ADD 5 new features to your telephone. Unique product catalog \$1.00. Refundable. **B & M ENGINEERING**, Box 823A, Simi Valley, CA 93062. (Dealers wanted).

SURVEILLANCE telephone \$175.00. Monitor room or telephone conversations. **Range unlimited.** 1 (800) 633-8277. Catalog. \$3.00 to: **LISTEN ELECTRONICS**, 603 Elgin, Muskogee, OK 74401.

LOCKPICKS, explosives, cable TV, bluebox schematics, more revealed in Tap newsletters. Hard to find information — All 91 issues only \$69.95 (sample \$1). **INFOCOM**, Box 1010, Saskatoon, SK S7K 3M7.

CABLE TV descramblers, Jerrold, Scientific Atlanta, Zenith, most major brands. Dealer inquiries welcome. Visa-M/C accepted. **E & O VIDEO**, 9691 E. 265th Street, Elko, MN 55020. 1 (800) 638-6898.



FINALLY!

An interesting and worthwhile project. This **EASY-TO-BUILD** circuit lets you use any regular TV set as a simple **OSCILLOSCOPE**. Build for less than \$10. **NO MODIFICATIONS TO TV!** Single or dual trace. Send for **FREE CATALOG** of other plans and kits.

DETAILED PLANS: \$4.95
TV-SCOPE
PENN RESEARCH,
Box 3543
Williamsport, PA 17701

DESCRAMBLING, new secret manual. Build your own descramblers for cable and subscription TV. Instructions, schematics, for SSAVI, gated sync, sinewave, (HBO, Cinemax, Showtime, UHF, Adult) \$8.95, \$2 postage. **CABLETRONICS**, Box 30502R, Bethesda, MD 20814.

CB tricks booklet. Modifications, tune-ups, channel expansion, clarifier tricks. Send \$19.95 to **MEDICINE MAN CB**, PO Box 37, Clarksville, AR 72830.

FM transmitter 88 to 108 MHz kit \$12.95 **SIERRA ELECTRONICS**, Box 709, Elfers, FL 34680-0709.

ELECTRONIC kits! Transmitters! Recorders! Phone devices! Bug detectors! Surveillance items! More! Catalog \$1.00: **XANDI ELECTRONICS**, Box 25647, 60R, Tempe, AZ 85285-5647.

INVESTIGATORS, experimenters. Quality new plans. Hard to find micro and restricted devices. Free catalog. **SASE KELLEY SECURITY, INC.**, Suite 90, 2531 Sawtelle Blvd., Los Angeles, CA 90064.

WIDE range tunable ultrasonic receiver, cord buster, ear extender, long range listening "TUBE," voice coder/descrambler, bug detector, and other interesting products. Catalog \$1.00. **KRYSTAL KITS**, PO Box 445, Bentonville, AR 72712.

CONVERT 720Kb diskettes to 1.44Mb easily and reliably. Save 60%. Complete process details, \$19.95 CK/MO. **NASH ENGINEERING ENTERPRISES**, Box 514, Mary Esther, FL 32569.

SINGERS! REMOVE VOCALS FROM RECORDS AND CDs!



SING WITH THE WORLD'S BEST BANDS!

An Unlimited supply of Backgrounds from standard stereo records! Record with your voice or perform live with the backgrounds. Used in Professional Performance yet connects easily to a home component stereo. This unique product is manufactured and sold Exclusively by **LT Sound** - Not sold through dealers. Call or write for a Free Brochure and Demo Record.

LT Sound, Dept. R.L-3, 7980 LT Parkway
Lithonia, GA 30058 (404) 482-4724
Manufactured and Sold Exclusively by **LT Sound**
24 HOUR PHONE DEMO LINE: (404) 482-2485

DETECTION - surveillance, debugging. Plans, kits, assembled devices. Latest high-tech catalog \$5. **DETECTION SYSTEMS**, 2515 E. Thomas, #16-864F, Phoenix, AZ 85016.

CATALOG: hobby/broadcasting/HAM/CB: Cable TV, transmitters, amplifiers, surveillance devices, computers, more! **PANAXIS**, Box 130-F3, Paradise, CA 95967.

CB super modulation, make your CB sound super loud. Plans only \$12.95 or kit and plans \$24.95. **MEDICINE MAN CB**, PO Box 37, Clarksville, AR 72830.

CONSTRUCT and package industrial circuits using E-Z Buss prototyping system. Free brochure. **NATIONAL SYSTEMS**, Suite 150, 17 Hammatt Street, Ipswich, MA 01938. (508) 356-1011.

CIRCUIT boards for projects in this magazine (and past issues) about half price. **KLAY-CORPORATION**, 106 Mark Drive, Syracuse, NY 13209-1808.

SURVEILLANCE equipment design gives 58 schematics of Sheffield Electronics' surveillance devices. Circuits explained. Transmitters range from pens to one-mile VOX's including crystal, subcarrier, carrier current, infrared, firefly, automobile. Demodulators given. Cube tap and duplex mains powered transmitters presented. Eighteen telephone transmitters are leech and battery types including crystal and subcarrier. Countermeasures chapter. Much more. This 8 1/2 x 11 inch 110-page book is illustrated with photographs. Price \$30.00 + \$4.00 S & H. First class mail U.S. & Canada. One-day processing, pay with Money Order or Chashiers Check. Send to: **WINSTON ARRINGTON**, 7223 Stony Island Ave., Chicago, IL 60649-2806.

VERSA-AMP amplifier design manual \$2.95. Send specifications for custom schematics \$8.50. Check/ MO. **ERDA**, N87W15625 Belleview Blvd., Menomonee Falls, WI 53051.

TRACKER circuit for your x-y input oscilloscope. Simple transformer/resistive circuit. Test diodes, transistors, IC's. Complete plans \$8.00; kit \$24.95, assembled \$34.95. **TECH CENTER**, 200 North Madison, Edmond, OK 73034.

BUSINESS OPPORTUNITIES

EASY work! Excellent pay! Assemble products at home. Call for information. (504) 641-8003 Ext. 5192.

MECHANICALLY inclined individuals desiring ownership of small electronics manufacturing business-without investment. Write: **BUSINESS-R**, C.S. 9008, Baldwin, NY 11510-9008.

MARK V ELECTRONICS, INC.

8019 E. SLAUSON AVE., MONTEBELLO, CA 90640



- MORE THAN 60 ITEMS IN AUDIO AND DIGITAL INSTRUMENT
- LOW PRICE AND EFFICIENT MANUFACTURING TECHNIQUES

▲ indicates the level of difficulty in the assembling of our Products ▲ Beginner ▲▲ Intermediate ▲▲▲ Advanced ★ Fully Assembled

8-DIGIT 1 GH MULTI-FUNCTION COUNTER FC-1000A ★

Assembled & tested & CAL \$192.00
The FC-1000A is a multi-function 10 hertz to 1ghz dual-range frequency counter. It can measure frequency, period and total events. Readout is a large 0.5" 8-digit 7-segment LED display. It utilizes two crystal oscillators which can be individually calibrated for maximum long term accuracy against a frequency standard such as WWV transmissions.

Additional features include a valuable self-check mode and a two step input attenuator

SPECIFICATIONS
Frequency range: 10hz to 10MHz, 10MHz to 100MHz, 100MHz to 1000MHz
Resolution: 1000hz to 0.1hz depending on range
Accuracy: ±1 digit, ±time base error
Period measurement: 10hz to 10MHz
Period measurement resolution: 10⁻⁷ to 10⁻¹⁰ seconds depending on gate time
Totalization measurement: 10hz to 10MHz
Totalization display: 99999999
Sensitivity: 15mV 10hz to 70MHz, 30mV 70MHz to 100MHz, 15mV 100MHz to 1000MHz
Input impedance: 1 megohm 10hz to 100MHz, 50ohms 100MHz to 1000MHz
Attenuation: X1, X10
Power requirements: 110 to 120VAC, 60hz or 220VAC, 50 to 70hz
Dimension: 7" high, 9" wide, 7.8" deep

120W MOSFET POWER AMPLIFIER (MONO) TA-477 ▲▲

Complete kit \$68.00
Assembled & tested \$85.00
This amplifier is designed specifically for low TIM distortion. It uses parallel MOSFET output transistors. This is a very popular kit because of its superior sound reproducing ability and high power reserve

SPECIFICATIONS
Power output: 120 Watts into 8ohms
Frequency response: 8hz to 20kHz ±0.0 - 0.4 dB
28hz to 65kHz ±0.0 - 1 dB
Sensitivity: 1V
Power requirements: 115VDC @ 8amps
Recommended transformer for a power supply is # 001

PROFESSIONAL COLOR LIGHT CONTROLLER SM-328 ★

Assembled & tested \$165.00
The SM-328 professional color light controller is keyboard programmable for ease of use. It allows full control of intensity and flash rate. It has four separate channels with capacity of 1170 watts per channel. Total wattage capability is 4.68 kilowatts. This is equivalent to 46, 100-watt light bulbs or 936 5-watt colored bulbs and is sufficient for the largest halls and auditoriums.

SPECIFICATIONS
Input sensitivity: 1mV model 100mV
Music program: 2V
Output power: 1170W per channel 4680W total
Power requirement: 105 - 120V, 60hz
Dimensions: 14.32" wide, 9" high, 3.19" deep

300W HI-FI POWER AMPLIFIER (MONO) TA-3600 ▲▲▲

Assembled & tested \$110.00
The TA-3600 is an extremely high power amplifier specifically designed to reproduce the high dynamic range available on compact discs. It has low noise, high stability, low distortion, extended frequency range and high efficiency in a compact package.
Two of these units with appropriate power supply and pre-amplifier are required for stereo reproduction.
Complete kit \$66.00
Assembled & tested \$110.00
Transformer \$38.00
10,000 UF 80V E. Cap \$20.00

80W - 80W PURE DC STEREO MAIN POWER AMPLIFIER TA-802

Complete kit \$45.94
Assembled & tested \$59.72
Modern circuit design utilizes full complementary power output and differential cascode input stage. DC coupling provides superb transient response. A special output circuit guards against short circuits and overload operation.
SPECIFICATIONS
Power output: 80 watts per channel into 8ohms
Total harmonic distortion: Less than 0.5% at rated power
Intermodulation distortion: Less than 0.05% at rated power
Frequency response: DC to 200kHz, 0 dB, -1 dB @ 1 watt
Power requirements: 10VAC x 2 @ 6amp. May use Mark V model 001 transformer
Suggested cabinet is Mark V LC194

HI-FI BI-FET PRE-AMP TA-2800 ▲▲

Complete kit \$48.90
This super low distortion stereo pre-amplifier uses high slew rate wide bandwidth op-amps for 0.005% total harmonic distortion. RIAA curve deviation is 0.2 dB! Tone controls and loudness controls can be switched in and out. Fully regulated power supply. Low, High and Mid tone controls.

SPECIFICATIONS
Frequency response: 10hz to 100kHz, ±0.5 dB
Total harmonic distortion: 0.005% at rated output
Intermodulation distortion: 0.005% at rated output
Sensitivity: 2.5mV @ 47k
Aux and tape: 100mV @ 100k
RIAA deviation: ±0.2 dB, 20hz to 20kHz
Signal to noise ratio: 75 dB
Tuner, aux and tape: 90 dB
Output: 1V
Tone controls:
Bass: ±10 dB at 10hz
Mid: ±5 dB at 1kHz
Treble: ±10 dB at 15kHz
Power requirements: 15V DC @ 0.5 to 1amp
Suggested power transformer for power supply is 15V AC x 2 @ 0.5 to 1amp
This model will match our 120W Mosfet Power Amplifier (TA-120)

4 1/2 DIGIT HI-PRECISION DPM WITH DIN CASE SM-48A

Complete kit \$41.20
Assembled & tested \$52.00
This is essentially our very popular SM-48 digital panel meter but in a standard DIN case. Like the SM-48, it has a large 0.5" LED readout. It is also temperature compensated to 100 PPM / °C. Operating temperature range is 0° to +70° C. This is a sensitive unit. An input of 1.999 volts results in full scale display. The unit operates on 5VDC at 200ma.
SPECIFICATIONS
Rear outputs: BCD data, Busy, Strobe
Range: DC voltage: 1mV to 2000V DC current: 1 microamp to 20amps
Accuracy: ±0.025% ±2 digits
Power requirements: 5 to 6 volts DC at 200ma
Dimensions: 3 1/2" wide x 1 1/2" high x 1 1/2" deep

PHONE AND MAIL ORDER :
TOLL FREE : 1-800-423-3483
(IN CA) : 1-800-521-MARK
FAX : (213) 888-6868

Business and showroom hours :
(Pacific Time)
Mon. - Fri : 9:30 a.m. - 5:00p.m.
Sat. : 10:00 a.m. - 5:00p.m.
Information : (213) 888-8988
Call or write for our FREE Catalog

Terms: \$10 Min. order • \$20 Min. charge card order • We ship UPS ground • Add 10% of total order (min. \$3.00) for shipping outside USA add 20% (min. \$5.00) • Transit Insurance: Add 5% of total (outside USA only). CA residents add sales tax • All merchandise subject to prior sale • Prices are subject to change without notice • We are not responsible for typographical errors.
We accept major credit cards, money orders and checks.
★ Free gift with your order during the months of June and July.

CIRCLE 93 ON FREE INFORMATION CARD

CABLE TV. "BOXES"

Converters—Descramblers
Remote Controls—Accessories

- ★ Guaranteed Best Prices ★
- ★ 1 Year Warranty—C.O.D.'s ★
- ★ Immediate Shipping ★
- ★ FREE CATALOG ★

Call or Write
TRANS-WORLD CABLE CO.
12062 Southwest 117th Court, Suite 126
Miami, Florida 33186
800-442-9333

EARN thousands with your own part time electronics business. I do. Free proof, information. **INDUSTRY**, Box 531, NY 10461-0531.

ASSEMBLE digital car dashboards. Send \$1.00 for details. **MODERN LABS**, Digidash Division, 2900 Ruisseau, Saint-Elizabeth, Quebec, J0K 2J0, Canada.

EDUCATION & INSTRUCTION

IBM PC. Learn assembly language. Spaceship game. Find princess game. \$5 each. Book \$18. **ZIPFAST**, Box 12238, Lexington, KY 40581-2238.

FCC Commercial General Radiotelephone License Prep Course by correspondence. 60 individual lessons, \$89.50. Payment plan. Also **Basic Computers**, \$39.50; certificates. Details free. **AMERICAN TECHNICAL INSTITUTE**, Box 201, Cedar Mountain, NC 28718.

RADIO Broadcasting! How to get started! Complete report by radio professional. Don't fall for worthless mail courses. Take charge yourself! \$10.00. **JON LOCKWOOD**, 405 South State, Davison, MI 48423.

*****PRESENTING***** CABLE TV DESCRAMBLERS *****STARRING***** JERROLD, HAMLIN, OAK AND OTHER FAMOUS MANUFACTURERS

• FINEST WARRANTY PROGRAM AVAILABLE
• LOWEST RETAIL/WHOLESALE PRICES IN U.S.
• ORDERS SHIPPED FROM STOCK WITHIN 24 HOURS
FOR FREE CATALOG ONLY **1-800-345-8927**
FOR ALL INFORMATION 1-818-716-5914

PACIFIC CABLE CO. INC.
7325W RESEDA BLVD., DEPT. RE1/89
RESEDA, CA 91335

PAY TV AND SATELLITE DESCRAMBLING NEW... 1989 EDITION... NEW

The newest systems, parameters, turn-ons, harassment and countermeasures being used by and against cable, wireless and satellite operators. New original information \$15.95. Pay TV Vol. 1 \$14.95. Volume 2 \$12.95. Experiences with VC \$12.95. MDS/MMDS Handbook \$9.95. Build Satellite Systems Under \$600. \$12.95. Any 3/\$28 or 6/\$42. Scrambling News Monthly \$24.95/yr. Sample \$3. Scrambling News Year 1 (200 pages) \$22.95. New Spring Catalog \$1 or call.

Scrambling News, 1552 Hertel Ave., Buffalo, N.Y. 14216 COD's 716-874-2088

SATELLITE TV

CABLE TV secrets — the outlaw publication the cable companies tried to ban. HBO, Movie Channel, Showtime, descramblers, converters, etc. Supplier's list included \$8.95. **CABLE FACTS**, Box 711-R, Pataskala, OH 43062.

DESCRAMBLERS for movies, networks, \$175, video only, \$450 complete. Visa, MC accepted. Catalog \$4. **SKYWATCH**, 238 Davenport Road, Toronto, Canada, M5R 1J6.

3 FOR 1 SPECIAL

ON SUB-MINIATURE VOICE
FM TRANSMITTERS.
KITS CONTAIN PC BOARDS



***FMX-1 LONG RANGE (3 MI) ULTRA SENSITIVE FM VOICE XMTR** with fine tune, range control plus.....\$29.50



***TELX-1 TELEPHONE FM XMTR (3 MI)** automatically operates when phone is used. Crystal clear clarity with fine tune and range control. Non detectable.....\$29.50



***ATR-1 AUTOMATIC TELEPHONE RECORDING DEVICE** tapes telephone conversation all automatically.....\$19.50

ALL THREE OF ABOVE FOR.....\$59.50

CALL OR SEND VISA, MASTER CHARGE, MONEY ORDER, ETC. TO **AMAZING CONCEPTS**, BOX 716, AMHERST, NH 03031. (603) 673-4730.



EMINENCE



MOTOROLA Polydax

1-800-338-0531

PIONEER

3-WAY 100W CROSSOVER

12 dB/octave rolloff.
800Hz, 5000Hz
crossover points. 8
ohm. 100 watts RMS.



#260-210 **\$12.50** **\$9.95**
(1-9) (10-up)

SPEAKER CONTROL PANEL

Panel with 50 watt L-pads
for tweeter and midrange
and built-in LED power
meter. 5" x 2 1/2" 100
watt version available



#260-235 **\$14.50** **\$12.90**
(1-5) (6-up)

12" POLY WOOFER

Super duty, 40 oz. magnet.
100 watts RMS, 145 watts
max. 4 and 8 ohm compat-
ible (6 ohm). 2" voice coil.
fs = 25 Hz. QTS = .166,
VAS = 10.8 cu ft.
Response: 25-1500 Hz. Net
weight: 9 lbs. Pioneer
#A30GU40-51D



#290-125 **\$36.80** **\$34.50**
(1-3) (4-up)

WALNUT SPEAKER CABINET KIT

Super quality,
genuine walnut
veneer cabinet. Kit
includes: routed and
mitred top, sides,
and bottom in
unfinished 3/4"
walnut veneer. Cut
your own custom
holes in the front
and rear to match
your drivers. 15" x
24" x 11". Volume:
1.9 cubic feet.



#260-350 **\$22.50** **\$19.95**
(1-3) (4-up)

PIONEER HORN TWEETER

Mylar dome. 2.93 oz.
barium ferrite magnet. 8
ohm. Response: 1800-
20000 Hz. 35W RMS,
50W max. fs = 2000 Hz,
SPL = 106 dB. Pioneer
#AHE60-51F



#270-050 **\$6.50** **\$5.90**
(1-9) (10-up)

12" SUB WOOFER

Dual voice coil sub woofer.
30 oz. magnet, 2" voice
coils. 100 watts RMS, 145
watts max. fs = 25 Hz. 6 ohm
(4 and 8 ohm compatible).
SPL = 89 dB 1W/1M.
Response: 25-700 Hz.
QTS = .31, VAS = 10.3 cu. ft.
Pioneer #A30GU30-55D.
Net weight: 6 lbs.



#290-145 **\$39.80** **\$36.80**
(1-3) (4-up)

15" THRUSTER WOOFER


Thruster by Eminence.
Made in USA. Poly foam
surround, 86 oz. magnet.
2-1/2", 2 layer voice coil.
150 watts RMS, 210 watts
max. 4 ohm. fs = 23.5
Hz. QTS = .33, VAS = 17.9
cu ft. SPL = 94.8 dB 1W/
1M. Net weight: 15 lbs.


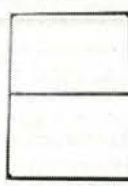
#290-180 **\$43.50** **\$39.80**
(1-3) (4-up)

GRILL FRAME KIT

With this kit you
can make speaker
grill frames up to
30" x 40". Kit
includes 4 corner
pieces, 2 "T"
brackets, and 7
frame bars. Grill
mounting kit
included.



#260-333 **\$8.50** **\$7.80**
(1-9) (10-up)

18" EMINENCE WOOFER

MADE IN USA
100 oz. magnet, 3" voice
coil. 250 watts RMS, 350
watts max. 8 ohm, 30 Hz
resonant frequency. 23-
2700 Hz response.
Efficiency: 95 dB 1W/1M.
Paper cone, treated
accordian surround. Net
weight: 29 lbs.



#290-200 **\$98.90** **\$89.50**
(1-3) (4-up)

TITANIUM COMPOSITE TWEETER

Titanium is deposited on a polymer
dome to combine the advantages of
both hard and soft dome
technologies. 8 ohm. Ferro fluid
cooled voice coil. fs = 1200 Hz.
SPL = 90 dB 1W/1M. 50 watts RMS,
70 watts max. 4" round. Polydax
part #DTW100T125.



#270-047 **\$27.50** **\$24.80**
(1-9) (10-up)



340 E. First St., Dayton, Ohio 45402
Local: 1-513-222-0173
FAX: 513-222-4644

* 15 day money back guarantee *\$15.00 minimum order *We accept
Mastercard, Visa, Discover, and C.O.D. orders *24 hour shipping
*Shipping charge = UFS chart rate +\$1.00 (\$3.00 minimum charge)
*Hours: 8:30 am-6:00 pm EST, Monday - Friday *Mail order
customers, please call for shipping estimate on orders exceeding
5 lbs.

CIRCLE 56 ON FREE INFORMATION CARD

JULY 1989

CABLE TV DESCRAMBLERS

JERROLD™ Tri-Bi Mode	\$105.00	10 Lot \$85.00
JERROLD™ SB-3 OR 2	\$89.00	\$65.00
Hamlin MLD-1200	\$99.95	\$62.00
Oak N-12 W/V.S.	\$99.95	\$62.00
Oak M-35-B W/V.S.	\$99.00	\$78.00
OAK E-13	\$99.95	\$58.00
Zenith SSAVI	\$185.00	\$145.00
Eagle PD-3	\$120.00	\$85.00
Scientific Atlanta	\$129.95	\$105.00
SA-Combo's	CALL	\$Call
Tocom	\$350.00	\$295.00
Oak N-12 W/ Auto	\$140.00	\$105.00
Jerrold Starcom CSV	\$139.95	Call

M.D. ELECTRONICS
WILL MATCH ANY
ADVERTISED PRICE
IN THIS MAGAZINE

*NEW STARGATE 2000 CABLE CONVERTER



1-\$89.00 10-\$69.00 100-Call

Last channel recall-Favorite channel select-75 channel-Channel scan-Manual fine tune-One year warranty-surge protection-HRC & Standard switchable-and much more. **Call Today!**

INFORMATION (402) 554-0417


Orders Call Toll Free
1-800-624-1150

M.D. ELECTRONICS
115 NEW YORK MALL
SUITE 133E
OMAHA, NE. 68114

M.C.
VISA
C.O.D.

CIRCLE 53 ON FREE INFORMATION CARD

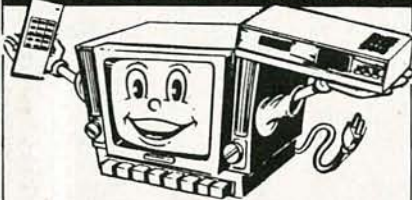CABLE T.V. CONVERTERS WHY PAY A HIGH MONTHLY FEE?



All Jerrold, Oak, Hamlin, Zenith, Scientific Atlanta, Magnavox and all specialized cable equipment available for shipment within 24 hours. For fast service MC / VISA or C.O.D. telephone orders accepted (800) 648-3030 60 Day Guarantee (Quantity Discounts) 8 A.M. to 5 P.M. C.S.T. Monday through Friday. Send self-addressed Stamped envelope (60¢ postage) for Catalog.

MIDWEST
ELECTRONICS INC.

5143 (R) W. Diversey
Chicago, IL 60639

No Illinois Orders Accepted.

DESCRAMBLER MODULE

LATEST technology alternative to Jerrold SB-3 or Radio-Electronics Feb. 1984 project. Featuring electronic tuning, AGC, auto-on/off, AC/DC power, mini-size, A&T, and more. For literature — SOUTHTECH DISTRIBUTING, (813) 527-2190.

ATTENTION CABLE BROKERS

SURPLUS CATV converters at wholesale prices. Unmodified units only. Oak M35B \$30, Hamlin CRX 5000-3M w/remote \$85. (415) 337-8301.

Try the

Radio Electronics

bulletin board
system

(RE-BBS)
516-293-2283

The more you use it the
more useful it becomes.

We support 300 and 1200
baud operation.

Parameters: 8N1 (8 data
bits, no parity, 1 stop bit)
or 7E1 (7 data bits, even
parity, 1 stop bit).

Add yourself to our user
files to increase your
access.

Communicate with other
R-E readers.

Leave your comments on
R-E with the SYSOP.

RE-BBS
516-293-2283

Employers

Willing workers available
now at as little as 1/2
your usual cost.

This is your chance
to get help you've
needed, but thought you
couldn't afford.

No business too large
or too small. Call your
private industry council
or write National
Alliance of Business,
P.O. Box 7207,
Washington, D.C. 20044

A Public Service of
This Publication
**Ad
Council**



This little
part is
just the
beginning...



...of a HUGE assortment of
quality electronic parts you'll
find in the MCM Catalog!

Have you had problems finding the exact part you need? Tired of keeping track of which part is coming from which supplier—and when it's due to arrive? Then, it's time you made the switch to the MCM Electronics Catalog!

For... Test Equipment — Semiconductors — Resistors — Capacitors — Chemicals — Technical Aids — Tools — Computer Equipment — Flybacks — Antennas — Wire & Cable — VCR Tools & Parts — Phono Parts & Styli — Speakers — Alarm Systems & Components — Telephone Accessories — Microwave Oven Parts — Terminals & Connectors — Switches — Batteries — Lamps — Fuses — and lots more... For competitive prices and the friendliest service in the industry; the MCM Electronics Catalog is your best choice!

For Your FREE
ONE-YEAR SUBSCRIPTION
to the MCM
Electronics Catalog...
CALL TOLL-FREE
1-800-543-4330




...or write...



MCM ELECTRONICS
650 CONGRESS PARK DR.
CENTERVILLE, OH 45459-4072
A PREMIER Company

SOURCE NO. RE-59

CIRCLE NO. 87 ON INQUIRY CARD

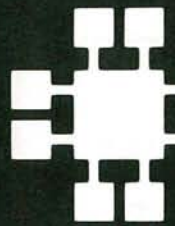

JDR Microdevices®

MMC
MICROCOMPUTER
MARKETING COUNCIL
of the Direct Marketing Association, Inc.

• 30 DAY MONEY BACK GUARANTEE • 1 YEAR WARRANTY ON ALL PRODUCTS • TOLL-FREE TECHNICAL SUPPORT
• COMPLETE CUSTOMER SATISFACTION • SUPERIOR SERVICE • FRIENDLY, KNOWLEDGEABLE SALES STAFF

EPROMS

PART	SIZE	SPEED	V _{pp}	PRICE
2708	1024x8	450ns	25V	4.95
2716	2048x8	450ns	25V	3.49
2716-1	2048x8	350ns	25V	3.95
2732	4096x8	450ns	25V	3.95
2732A	4096x8	250ns	21V	3.95
27C64	8192x8	250ns	12.5V	4.95
2764	8192x8	450ns	12.5V	3.49
2764-250	8192x8	250ns	12.5V	3.69
2764-200	8192x8	200ns	12.5V	4.25
27128	16384x8	250ns	12.5V	4.95
27128A-200	16384x8	200ns	12.5V	5.95
27C256	32768x8	250ns	12.5V	7.95
27256	32768x8	250ns	12.5V	5.95
27256-200	32768x8	200ns	12.5V	7.95
27512	65536x8	250ns	12.5V	11.95
27C512	65536x8	250ns	12.5V	12.95
27C101-20	131072x8	200ns	12.5V	34.95

■ CALL TO CONFIRM CURRENT PRICES ■

STATIC RAMS

PART	SIZE	SPEED	PRICE
2114	1024x4	450ns	.99
2114L-2	1024x4	200ns	1.49
TC5516	2048x8	250ns	3.95
TMM2016-200	2048x8	200ns	3.25
TMM2016-150	2048x8	150ns	3.29
TMM2016-100	2048x8	100ns	4.29
HM6116-4	2048x8	200ns	4.95
HM6116-2	2048x8	150ns	5.95
HM6116-2	2048x8	120ns	6.45
HM6116L-4	2048x8	200ns	5.95
HM6116L-3	2048x8	150ns	6.45
HM6116L-2	2048x8	120ns	6.95
HM6264L-15	8192x8	150ns	9.95
HM6264L-12	8192x8	120ns	10.95
HM43256L-15	32768x8	150ns	17.95
HM43256L-12	32768x8	120ns	19.95
HM43256L-10	32768x8	100ns	24.95

■ CALL TO CONFIRM CURRENT PRICES ■

DYNAMIC RAMS

PART	SIZE	SPEED	PRICE
4116-200	16384x1	200ns	.89
4116-150	16384x1	150ns	.99
4164-150	65536x1	150ns	2.89
4164-100	65536x1	120ns	3.19
4164-120	65536x1	100ns	3.95
TMS4416	16384x4	150ns	8.95
41128-150	131072x1	150ns	5.95
TMS4464-15	65536x4	150ns	14.95
TMS4464-12	65536x4	120ns	15.95
41256-150	262144x1	150ns	7.99
41256-120	262144x1	120ns	8.49
41256-100	262144x1	100ns	8.79
41256-80	262144x1	80ns	9.49
MK4332	32768x1	200ns	6.95
HMS1258-100	262144x1	100ns	13.95
1 MB-120	1048576x1	120ns	24.95
1 MB-100	1048576x1	100ns	27.95

■ CALL TO CONFIRM CURRENT PRICES ■

CO-PROCESSORS

8087	5 MHz	97.95
8087-2	8 MHz	139.95
8087-1	10 MHz	189.95
80287	6 MHz	157.96
80287-8	8 MHz	219.95
80287-10	10 MHz	254.95
80387-16	16 MHz	397.95
80387-SX	16 MHz	389.95
80387-20	20 MHz	469.95
80387-25	25 MHz	589.95

intel
5 YEAR WARRANTY

INCLUDES MANUAL & SOFTWARE GUIDE

EPROM ERASERS

DATARASE II \$39.95

■ SHIRT POCKET SIZE!
■ ERASES MOST EPROMS/
EPLD'S IN 3 MINUTES ■ ALL
SIZES UP TO 4 AT A TIME



Model	Timer	# of Chips	Intensity (uW/Cm ²)	Unit Cost
PE-140	NO	9	8,000	\$ 89
PE-140T	YES	9	8,000	\$139
PE-240T	YES	12	8,500	\$189
PL-265	YES	30	9,600	\$255

SPECTRONICS CORPORATION

HIGH-TECH SPOTLIGHT

NEW! FAST PAGE-MODE DYNAMIC RAMS

THESE NEW CMOS 262144X4 DRAMS ARE IDEAL FOR LARGE CAPACITY MEMORY SYSTEMS REQUIRING HIGH SPEED AND LOW POWER DISSIPATION. HIGHER DENSITY REQUIRES FEWER CHIPS FOR SYSTEM DESIGN. SUPPORTS EXTREMELY LOW POWER STANDBY MODE. 8 MS REFRESH RATE.

PART NUMBER	SPEED	PRICE
414256-100	100 NS	\$28.95
414256-80	80 NS	\$36.95

PARTIAL LISTINGS ONLY! CALL FOR COMPLETE CATALOG

74 SERIES LOGIC

7400		74S	
7400	.19	74LS76	.29
7402	.19	74LS83	.49
7404	.19	74LS85	.49
7405	.25	74LS86	.22
7406	.29	74LS90	.39
7407	.29	74LS92	.49
7408	.24	74LS93	.39
7410	.19	74LS109	.36
7411	.25	74LS112	.29
7414	.49	74LS123	.49
7416	.25	74LS125	.39
7417	.25	74LS132	.39
7420	.19	74LS136	.39
7432	.29	74LS139	.39
7447	.89	74LS151	.39
7473	.34	74LS153	.39
7474	.33	74LS154	1.49
7475	.45	74LS155	.59
7476	.35	74LS156	.49
7588	2.15	74LS157	.35
7489	.39	74LS158	.29
7490	.35	74LS161	.39
7493	.35	74LS163	.39
74121	.29	74LS164	.49
74123	.49	74LS165	.65
74151	.55	74LS166	.95
74154	1.49	74LS175	.39
74157	.55	74LS192	.69
74166	1.00	74LS193	.69
		74LS197	.59
		74LS221	.59
		74LS240	.69
		74LS241	.69
		74LS244	.69
		74LS245	.79
		74LS251	.49
		74LS257	.39
		74LS258	.49
		74LS259	1.29
		74LS260	.49
		74LS273	.79
		74LS279	.39
		74LS322	3.95
		74LS323	2.49
		74LS367	.39
		74LS373	.79
		74LS374	.79
		74LS377	.79
		74LS393	.79
		74LS541	1.49
		74LS670	.89
		74LS682	3.20
		74LS688	2.40

MICROPROCESSORS

6500		8000		8200	
6502	2.25	8031	3.95	8254	2.79
6502A	2.69	8035	1.49	8255	1.99
6502B	4.25	8039	1.95	8255-5	2.49
65C02*	7.95	8052AH		8256	15.95
6522	2.95	BASIC	34.95	8259	1.95
6526	13.95	8080	2.49	8259-5	2.29
6532	5.95	8085	1.95	8272	4.39
6551	2.95	8085A-2	3.75	8274	4.95
6581	14.95	8088	5.99	8275	16.95
		8088-2	7.95	8279	2.49
		8155	2.49	8279-5	2.95
		8155-2	3.95	8282	3.95
		8156	2.95	8283	3.95
		8741	9.95	8284	2.25
		8748	7.95	8286	3.95
		8749	9.95	8287	3.95
		8755	14.95	8288	4.95

6800		8200		Z-80	
6800	1.95	8205	3.29	Z80-CPU	1.25
6802	2.95	8212	1.49	Z80A-CPU	1.29
68B02	3.95	8216	1.49	Z80B-CPU	2.75
6803	3.95	8224	2.25	Z80A-CTC	1.69
6809	2.95	8228	2.25	Z80B-CTC	4.25
68B09	5.99	8237	3.95	Z80A-DART	5.95
6809E	2.95	8237-5	4.75	Z80B-DART	6.95
68B09E	5.49	8238	4.49	Z80A-DMA	5.95
6808	2.49	8243	1.95	Z80A-PIO	1.89
6810	1.95	8250	6.95	Z80B-PIO	4.25
6821	1.25	8251	1.29	Z80A-SIO/0	5.95
68B21	1.85	8251A	1.69	Z80A-SIO/1	5.95
6840	3.95	8253	1.59	Z80A-SIO/2	5.95
6847	4.75	8253-5	1.95	Z8671BASIC	9.95
6850	1.95				
68B50	1.75				
6852	4.95				
6883	22.95				
68000	9.95				
68020	189.95				

SIMM MODULES

41256A8B-15	256K x 8-BIT	FOR MAC	150ns	\$89.00
41256A8B-12	256K x 8-BIT	FOR MAC	120ns	\$95.00
41256A8B-10	256K x 8-BIT	FOR MAC	100ns	\$99.00
41256A9B-15	256K x 9-BIT	FOR PC	150ns	\$94.00
41256A9B-12	256K x 9-BIT	FOR PC	120ns	\$99.00
41256A9B-10	256K x 9-BIT	FOR PC	100ns	\$109.00
41256A9B-80	256K x 9-BIT	FOR PC	80ns	\$119.00
421000A9B-10	1MB x 9-BIT	FOR PC	100ns	\$329.00
421000A9B-80	1MB x 9-BIT	FOR PC	80ns	\$399.00

V-20 SERIES

SPEED UP YOUR PC BY 10% TO 40%
■ HIGH SPEED ADDRESS CALCULATION IN
HARDWARE ■ PIN COMPATIBLE WITH 8088

V20 5 MHz	6.95	V20 8 MHz	8.95
V20 10 MHz	11.95	V30 8 MHz	13.95

PALS

16L8	\$2.95	20R4	\$4.95
16R8	2.95	20R6	4.95
16R6	2.95	20R8	4.95
16R4	2.95	20X8	4.95
20L8	4.95		

STARTER KIT

EASY TO USE PAL
PROGRAMMING KIT
FOR ALL THE PAL
DEVICES AT LEFT.
MCT-PAL-SOFT \$99.95

LINEAR COMPONENTS

TL071	.69	TL497	3.25	MC3487	2.95
TL072	1.09	NE555	.29	LM3900	.49
TL064	1.49	NE556	.49	LM3909	.59
LM301	.34	NE558	.79	LM3914	1.89
LM309K	1.25	LM565	.95	IC7760	1.99
LM311	.59	LM567	.79	7805T	.49
LM311K	3.49	NE570	2.95	7808T	.49
LM317T	.69	NE590	2.50	7812T	.49
LM318	1.49	LM723	.49	7815T	.49
LM319	1.25	LM741	.29	7905T	.59
LM323K	3.49	MC1330	1.69	7912T	.59
LM324	.34	MC1350	1.19	7915T	.59
LM334	1.19	LM1458	.35	MAX232	7.95
LM336	1.75	LM1458	.49	ICL8038	3.95
LM338K	4.49	LM1489	.49	ICM7207A	5.95
LM339	.59	LM1496	.85	ICM7208	15.95
LF353	.59	ULN2003	.79	75150	1.95
LF356	.99	XR2206	3.95	75154	1.95
LM358	.59	XR2211	2.95	75188	1.25
LM380	.89	CA3046	.89	75189	1.25
LM386	.89	CA3146	1.29	75451	.39
LM393	.45	MC3470	1.95	75452	.39

MISC.

ADC0804	2.99
ADC0809	3.85
DAC0800	3.29
DAC0808	1.95
1793	9.95
8272	4.39
COM8116	8.95
UPD765	4.39
1691	6.95
2143	6.95
AY5-3600	11.95
AY5-1015	4.95
AY5-1013	3.95
MC146818	5.95
MMS8167	9.95
MMS5832	2.95
IM6402	3.95
IM6403	9.95
INS8250	6.95
NS16450	10.95

CRYSTALS

32.768 KHz

POWER SUPPLIES



135 WATT POWER SUPPLY
 ■ UL APPROVED
 ■ +5V @15A, +12V @ 4.2A,
 5V @ 5A, -12V @ 5A
PS-135 \$59.95
PS-150 150W SUPPLY \$69.95



200 WATT POWER SUPPLY
 ■ UL APPROVED
 ■ +5V @ 20A, +12V @ 7A,
 -5V @ 5A, -12V @ 5A
PS-200 \$89.95



APPLE TYPE SUPPLY
 ■ WITH APPLE CONNECTOR
 ■ +5V @ 6A, +12V @ 3A,
 -5V @ 1A, -12V @ 1A
PS-A \$49.95



36 WATT POWER SUPPLY
 ■ +5V @2.5A, +12V @1.5A
 ■ 3 PIN INPUT, 6 PIN OUTPUT
 ■ SELECTABLE 110V-220V
PS-3045 \$12.95

SOLDER STATIONS



SOLDER/DESOLDER STATION
 ■ OIL-FREE VACUUM PUMP
 ■ TEMP. ADJUSTS (212° F-900° F)
 & VACUUM (0-60 CMHG)
 ■ WITH GUN-REST, COOLING TRAY,
 WIRE BRUSH & TIP CLEANER ROD
XY999SD \$399.95
XY999D DESOLDER ONLY \$349.99



DELUXE SOLDER STATION
 ■ ROTARY SWITCH TEMP
 CONTROL (200° F-878° F RANGE)
 ■ LED TEMPERATURE READOUTS
 ■ INCLUDES COOLING TRAY
XY9-60L \$79.95



SOLDER STATION
 ■ UL APPROVED
 ■ HEAT SETTING ADJUSTS
 ■ TIP TEMPERATURE READOUT
 ■ REPLACEMENT TIPS @ \$2.95
168-3C \$59.95

WIREWRAP PROTOTYPE CARDS

FR-4 EPOXY GLASS LAMINATE WITH GOLD PLATED
 EDGE CARD FINGERS AND SILK SCREENED LEGENDS




FOR XT
JDR-PR1 WITH +5V AND GROUND PLANE \$27.95
JDR-PR2 ABOVE WITH I/O DECODING LAYOUT \$29.95

FOR AT
JDR-PR10 16 BIT WITH I/O DECODING LAYOUT \$34.95
JDR-PR10PK PARTS KIT FOR JDR-PR10 ABOVE \$12.95

FOR PS/2
JDR-PR32 32 BIT PROTOTYPE CARD \$69.95
JDR-PR16 16 BIT WITH I/O DECODING LAYOUT \$49.95
JDR-PR16PK PARTS KIT FOR JDR-PR16 ABOVE \$15.95
JDR-PR16V 16 BIT FOR VIDEO APPLICATIONS \$39.95

JDR INSTRUMENTS—2 YEAR WARRANTY!

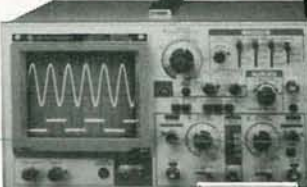35 MHZ DUAL TRACE OSCILLOSCOPE
 ■ WIDE BAND WIDTH ■ VARIABLE HOLDOFF
MODEL-3500 (SHOWN) \$499.95



20 MHZ DUAL TRACE OSCILLOSCOPE
 ■ TV SYNC FILTER ■ COMPONENTS TESTER
MODEL 2000 \$389.95

3.5 DIGIT PROBE TYPE DMM
 ■ AUTORANGING ■ AC/DC 2V - 500V, RESIS. 2K-2M
DPM-1000 (SHOWN) \$54.95

3.5 DIGIT POCKET SIZE DMM
 ■ BASIC DC ACCURACY ±0.5% ■ 14 RANGES
DMM-100 \$29.95

3.5 DIGIT FULL FUNCTION DMM
 ■ BASIC DC ACCURACY ±0.25% ■ 22 RANGES
DMM-200 \$49.95

THE ULTIMATE 3.5 DIGIT DMM
 ■ BASIC DC ACCURACY ±0.25% ■ 34 RANGES
 ■ TEMP, TRANSISTOR & RESISTANCE FEATURES
DMM-300 (SHOWN) \$79.95



RELIABLE,
 HIGH QUALITY
 TEST EQUIPMENT,
 REASONABLY
 PRICED

DATA SWITCH BOXES

TYPE	# OF POS.	PARALL.	SERIAL	PRICE
PUSHBTN.	2-WAY	AB-P	AB-S	39.95
ROTARY	2-WAY	RSP-2	RSS-2	24.95
ROTARY	3-WAY	RSP-3	RSS-3	27.95
ROTARY	4-WAY	RSP-4	RSS-4	29.95

COMPUTER CABLES


GOLD-PLATED CONTACTS; 100% SHIELDED

CBL-PRINTER	PC PRINTER CABLE	9.95
CBL-PRINTER-25	AS ABOVE-25 FT.	15.95
CBL-PRINTER-RA	RT. ANGL. PRINTER	15.95
CBL-DB25-MM	DB25 MALE-MALE	9.95
CBL-DB25-MF	DB25 MALE-FEMALE	9.95
CBL-9-SERIAL	9 PIN-25 PIN SERIAL	6.95
CBL-KBD-EXT	KEYBOARD EXTEN.	7.95
CBL-CNT-MM	36 PIN CENTRON.-MM	14.95
CBL-HD-20	20 PIN HARD DISK	3.95
CBL-HD-34D	34 PIN DUAL HARD DISK	6.95
CBL-FDC-EXT	37 PIN EXT. FLOPPY	9.95
CBL-MNT-9	9 PIN MONITOR EXTEN.	6.95
CBL-MODEM	DB25-DB25 FEMALE	7.95

EXTENDER CARDS


FOR PROTOTYPE DEBUGGING,
 TESTING AND TROUBLESHOOTING

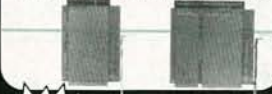EXT-8088 XT COMPATIBLE \$29.95
EXT-80286 AT COMPATIBLE \$39.95
EXT-16 MICROCHANNEL 16-BIT \$69.95
EXT-32 MICROCHANNEL 32-BIT \$99.95



NEW LOW PRICES! SOLDERLESS BREADBOARDS

PDS-100	1360 TIE PTS	\$12.95
PDS-200	1660 TIE PTS	\$19.95
PDS-300	2390 TIE PTS	\$24.95
PDS-400	3220 TIE PTS	\$34.95

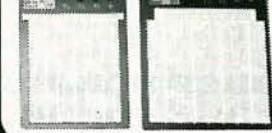

IDC CONNECTORS/RIBBON CABLE

DESCRIPTION	ORDER BY	CONTACTS					
		10	20	26	34	40	50
SOLDER HEADER	IDHxxS	.82	1.29	1.68	2.20	2.58	3.24
RIGHT ANGLE SOLDER HEADER	IDHxxSR	.85	1.35	1.76	2.31	2.72	3.39
WIREWRAP HEADER	IDHxxW	1.86	2.98	3.84	4.50	5.28	6.63
RIGHT ANGLE WIREWRAP HEADER	IDHxxWR	2.05	3.28	4.22	4.45	4.80	7.30
RIBBON HEADER SOCKET	IDSxx	.63	.89	.95	1.29	1.49	1.69
RIBBON HEADER	IDMxx	--	5.50	6.25	7.00	7.50	8.50
RIBBON EDGE CARD	IDExx	.85	1.25	1.35	1.75	2.05	2.45
10' RIBBON CABLE	RCxx	1.60	3.20	4.10	5.40	6.40	7.50

FOR ORDERING INSTRUCTIONS, SEE D-SUBMINIATURE CONNECTORS BELOW

D-SUBMINIATURE CONNECTORS

DESCRIPTION	ORDER BY	CONTACTS						
		9	15	19	25	37	50	
SOLDER CUP	MALE	DBxxP	.45	.59	.69	.69	1.35	1.85
	FEMALE	DBxxS	.49	.69	.75	.75	1.39	2.29
RIGHT ANGLE PC SOLDER	MALE	DBxxPR	.49	.69	--	.79	2.27	--
	FEMALE	DBxxSR	.55	.75	--	.85	2.49	--
WIREWRAP	MALE	DBxxPWW	1.69	2.56	--	3.89	5.60	--
	FEMALE	DBxxSWW	2.76	4.27	--	6.84	9.95	--
IDC RIBBON CABLE	MALE	IDBxxP	1.39	1.99	--	2.25	4.25	--
	FEMALE	IDBxxS	1.45	2.05	--	2.35	4.49	--
HOODS	METAL	MHOODxx	1.05	1.15	1.25	--	--	--
	PLASTIC	HOODxx	.39	.39	--	.39	.69	.75

ORDERING INSTRUCTIONS: INSERT THE NUMBER OF CONTACTS IN THE POSITION MARKED "xx" OF THE "ORDER BY" PART NUMBER LISTED. EXAMPLE: A 15 PIN RIGHT ANGLE MALE PC SOLDER WOULD BE DB15PR MOUNTING HARDWARE .59

IC SOCKETS/DIP CONNECTORS

DESCRIPTION	ORDER BY	CONTACTS								
		8	14	16	18	20	22	24	28	40
SOLDERTAIL SOCKETS	xxST	.11	.11	.12	.15	.18	.15	.20	.22	.30
WIREWRAP SOCKETS	xxWW	.59	.69	.69	.99	1.09	1.39	1.49	1.69	1.99
ZIF SOCKETS	ZIFxx	--	4.95	4.95	--	5.95	--	5.95	6.95	9.95
TOOLED SOCKETS	AUGATxxST	.62	.79	.89	1.09	1.29	1.39	1.49	1.69	2.49
TOOLED WW SOCKETS	AUGATxxWW	1.30	1.80	2.10	2.40	2.50	2.90	3.15	3.70	5.40
COMPONENT CARRIERS	ICCxx	.49	.59	.69	.99	.99	.99	.99	1.09	1.49
DIP PLUGS (IDC)	IDPxx	.95	.49	.59	1.29	1.49	--	.85	1.49	1.59

FOR ORDERING INSTRUCTIONS SEE D-SUBMINIATURE CONNECTORS ABOVE

RS-232 BREAKOUT BOX

FOR TROUBLESHOOTING
 SERIAL COMMUNICATIONS

■ OPEN/CLOSE INDIVIDUAL
 CIRCUITS ■ 20 JUMPERS
 CROSS-CONNECT ANY TWO
 CIRCUITS ■ 10 CIRCUIT
 ACTIVITY LEDs
GENDER-BO \$34.95



SURGE SUPPRESSOR

PROTECTS YOUR EQUIPMENT!

■ SIX 3-PRONG AC OUTLETS
 ■ 15 AMP CIRCUIT BREAKER
 ■ 6' HEAVY DUTY CORD
 ■ 15 AMP MAX LOAD, 1875 WATTS
 ■ UL APPROVED
POWER-SURGE \$12.95
POWER-STRIP W/O SURGE \$9.95



LITHIUM BATTERY

■ 6V FOR 286 AND 386 PCS
 ■ MOTHERBOARD CONNECTOR
 ■ ADHESIVE VELCRO MOUNTING
 STRIP
LITHIUM 6.8V \$11.95



COIN TYPE BATTERY

LONG-LASTING 3V LITHIUM
3V-MHW \$1.95
HOLDER \$1.49



APPLE-COMPATIBLE PRODUCTS

FLOPPY DRIVE FOR APPLE II SERIES
AP-150 (W/CABLE, CONNECTOR) \$99.95

REPLACEMENT KEYBOARD FOR APPLE II & II-
KEYBOARD-AP \$59.95

EPROM PROGRAMMER. NOT REC. FOR CMOS.
RP-525 (NO POWER SUPPLY REQ.) \$89.95

16K RAM CARD BOOSTS 48K APPLE TO 64K
RAM-CARD (2 YEAR WARRANTY) \$39.95

PC BREADBOARD



■ 62 CLEARLY LABELLED BUS LINES
 ■ ACCEPTS UP TO 24 14-PIN ICs
 ■ 1940 TIE POINTS
 ■ EXT FEMALE DB25 D-SUB CONNECT.
PDS-604 \$49.95

GENDER CHANGERS

GENDER-FF FEMALE-FEMALE \$7.95
GENDER-MM MALE-MALE \$7.95
GENDER-MF MALE-FEMALE \$7.95
GENDER-NM NULL MODEM \$8.95
GENDER-JB JUMPER BOX \$8.95
GENDER-MT MINITESTER \$14.95
GENDER-VGA DB9-DB15 \$19.95
GENDER-9-25 DB9-DB25 \$4.95



"SNAPABLE HEADERS"

SNAP APART TO MAKE ANY SIZE
 HEADER, WITH .1" CENTERS

1 X 40	STRAIGHT LEAD	.99
1 X 40	RIGHT ANGLE LEAD	\$1.49
2 X 40	STRAIGHT LEAD	\$2.49
2 X 40	RIGHT ANGLE LEAD	\$2.99



JDR MICRODEVICES, 2233 BRANHAM LANE, SAN JOSE, CA 95124
 LOCAL (408) 866-6200 FAX (408) 559-0250 TELEX 171-110
 RETAIL STORE: 1256 S. BASCOM AVE., SAN JOSE, CA
 (408) 947-8881 HOURS: M-F, 9-7 SAT. 9-5 SUN. 12-4



Terms: Minimum order \$10.00. For shipping & handling include \$3.50 for ground and \$4.50 for air. Orders over 1 lb and foreign orders may require additional shipping charges—contact the sales department for the amount. CA residents must include applicable sales tax. Prices subject to change without notice. We are not responsible for typographical errors. We reserve the right to limit quantities and to substitute manufacturer. All merchandise subject to prior sales. A full copy of our terms is available upon request. Items pictured may only be representative.

ORDER TOLL FREE 800-538-5000

COPYRIGHT 1989 JDR MICRODEVICES

CONTINENTAL U.S.

2400 BAUD MODEM
\$99.95



- HAYES COMPATIBILITY ■ 1/2-CARD ■ AUTO DIAL/ANSWER
- SELF-TEST ON POWER UP ■ FULL AND HALF DUPLEX
- TOUCHTONE OR PULSE DIALING ■ 2ND PHONE JACK
- CALL PROGRESS MONITORING ■ ADJUSTABLE VOLUME

PRO-241
INTERNAL MODEMS (MIRROR II SOFTWARE INCLUDED)
PRO-121 1200 BAUD 1/2 CARD \$69.95
PRO-24M 2400 BAUD FOR PS/2 \$249.95
EXTERNAL MODEMS (REQ. SERIAL PT. CABLE, SOFTWARE)
PRO-24E 2400 BAUD \$169.95
PRO-12E 1200 BAUD \$99.95



DFI HANDY SCANNER

400 DPI \$199.95

- INSTANTLY SCANS UP TO 4.1" WIDE IMAGES ■ 100, 200, 300, 400 DPI BOTH DIRECTIONS ■ 88W & 3 HALF-TONE MODES ■ 32 LEVELS OF GRAY SCALE ■ HERCULES, CGA, EGA AND VGA COMPATIBLE
- INCLUDES HALO DPE AND IMAGE EDITOR SOFTWARE



UPRIGHT CASE \$299.95

- SPACESAVING DESIGN HOLDS ALL SIZES OF MOTHERBOARDS. INCLUDES:
 - 250W POWER SUPPLY ■ MOUNTS FOR 3 FLOPPY & 4 HARD DRIVES
 - TURBO & RESET SWITCH ■ LED SPEED DISPLAY ■ POWER & DISK LED'S
 - ALL HARDWARE, FACEPLATES & SPEAKER



LOGITECH HIREZ MOUSE

\$89.95

- HIGH RESOLUTION BUS MOUSE. IDEAL FOR CAD WORK ■ 320 DPI ■ WITH DRIVER, TEXT EDITOR & POP-UP MENUS
- NO PAD, POWER SUPPLY OR PORT REQ.



LOGITECH 3 BUTTON MOUSE
PC MAGAZINE EDITORS CHOICE! ALL MODELS HAVE SERIAL SUPPORT (COM1/COM2), 200 D.P.I. RESOLUTION, LOTUS 1-2-3 SHELL, SELF-INSTALLING SOFTWARE AND "POINT EDITOR"

LMOUSE \$74.95
LMOUSE-P SERIAL MOUSE W/LOGIPAIN \$89.95
LMOUSE-BP BUS MOUSE W/LOGIPAIN \$89.95
LMOUSE-BPBL BUS MOUSE W/PUBLISHER PKG \$129.95
LMOUSE-BPC BUS MOUSE W/LOGIPAIN/CAD \$139.95

MODULAR PROGRAMMING SYSTEM

INTEGRATED MODULAR SYSTEM EASILY EXPANDS! ALL MODULES USE A COMMON HOST ADAPTOR CARD—USE JUST ONE SLOT TO PROGRAM EPROMS, PROMS, PALS & MORE

HOST ADAPTOR CARD \$29.95

- UNIVERSAL INTERFACE FOR ALL THE PROGRAMMING MODULES!
- SELECTABLE ADDRESSES PREVENTS CONFLICTS
- MOLDED CABLE



UNIVERSAL MODULE \$499.95

- PROGRAMS EPROMS, EEPROMS, PALS, BI-POLAR PROMS, 8748 & 8751 SERIES DEVICES, 16V8 AND 20V8 GALS (GENERIC ARRAY LOGIC) FROM LATTICE, NS, SGS ■ TESTS TTL, CMOS, DYNAMIC & STATIC RAMS ■ LOAD DISK, SAVE DISK, EDIT, BLANK CHECK, PROGRAM, AUTO, READ MASTER, VERIFY AND COMPARE
- TEXT TOOL SOCKET FOR .3" TO .6" IC'S (8-40 PINS)



VGA COMPATIBLE PACKAGE \$549.95



- 800 X 560 MAX. RESOLUTION ■ 640 X 480 IN 16 COLORS
- 320 X 200 IN 256 COLORS ■ IBM STYLE MONITOR
- VGA, EGA, CGA, HERCULES, MONOCHROME COMPATIBLE

VGA-PKG (INCLUDES ATI CARD AND MONITOR)
NEC MULTISYNC II MONITOR \$599.95
■ AUTO FREQ ADJUSTMENT ■ RESOLUTION TO 800 X560
■ IDEAL FOR CAD, CAM, WINDOWS ■ 9-15 PIN ADAPTER
NEC-MULTI

JDR MULTI \$499.95
■ FULL FEATURED MULTISCAN MONITOR WITH UNLIMITED COLORS ■ HIGH RESOLUTION, 14" NON-GLARE DISPLAY
■ AUTO SWITCHING ■ TTL/ANALOG VIDEO INPUT
JDR-MULTI
JDR-MONO (12" MONOCHROME MONITOR) \$69.95

EGA MONITOR \$399.95
■ 640 X 200/350 RESOLUTION ■ 31 MM DOT PITCH ■ 14" BLACK MATRIX SCREEN ■ 16 COLOR DISPLAY ■ 9-PIN CABLE
EGA-MONITOR

SAVE \$50! EGA CARD & MONITOR—JUST \$499

KEYBOARDS

101 KEY ENHANCED, W/SEPARATE CURSOR PAD:
BTC-5339 AUTOSENSE FOR XT/AT, AUTOREPEAT \$79.95
K103-A AUDIBLE "CLICK" STYLE \$84.95
MAX-5339 MAXI-SWITCH W/TACTILE FEEDBACK \$84.95

84 KEY STYLES:
BTC-5060 AUTOSENSE FOR XT/AT \$59.95
MAX-5060 MAXI-SWITCH W/TACTILE FEEDBACK \$64.95

MODULAR CIRCUIT TECHNOLOGY

NEW LOW PRICES!

MOTHERBOARDS:
MCT-XMB STANDARD 8088 MOTHERBOARD \$87.95
MCT-TURBO 4.77/10 MHZ 8088 MOTHERBOARD \$95.95
MCT-TURBO-10 4.77/10 MHZ SINGLE CHIP 8088 \$99.95
MCT-M286 6/10 MHZ MINI-286 \$269.95
MCT-M286-12 6/12 MHZ MINI-286 \$299.95

DRIVE CONTROLLERS:
MCT-FDC FLOPPY DISK CONTROLLER \$29.95
MCT-FDC-1.2 1.2 MB FLOPPY CONTROLLER \$49.95
MCT-HDC HARD DISK CONTROLLER \$79.95
MCT-RLL RLL CONTROLLER \$89.95
MCT-FH FLOPPY/HARD CONTROLLER \$139.95
MCT-AFH 286/386 FLOPPY/HARD \$149.95
MCT-AFH-RLL 286/386 RLL CONTROLLER \$199.95

DISPLAY ADAPTOR CARDS:
MCT-MGP MONOCHROME GRAPHICS \$59.95
MCT-CG COLOR GRAPHICS ADAPTOR \$49.95
MCT-EGA ENHANCED GRAPHICS ADAPTOR \$149.95
MCT-MGMA MONOGRAMPHICS MULTI I/O \$119.75
MCT-MGMAIO 286/386 MONOGRAMPHICS, I/O \$99.95

MULTIFUNCTION CARDS:
MCT-MIO MULTI I/O FLOPPY CONTROLLER \$79.95
MCT-IO MULTI I/O CARD \$59.95
MCT-AMF 286/386 MULTIFUNCTION \$139.95
MCT-AIO 286/386 MULTI I/O CARD \$59.95

MEMORY CARDS:
MCT-RAM 576K RAM CARD \$59.95
MCT-EMS EXPANDED MEMORY CARD \$129.95
MCT-AEMS 286/386 EMS CARD \$139.95

20 MB \$269
30 MB \$299



KITS INCLUDE A SEAGATE HARD DISK DRIVE, DRIVE CONTROLLER, CABLES AND INSTRUCTIONS.
HDKIT20 20 MB SYSTEM KIT
HDKIT30 30 MB SYSTEM KIT



FAST, RELIABLE SEAGATE HARD DISKS:

DISK SIZE	MODEL	AVG. SPD.	SIZE	PRICE
20MB	ST-125	65 MS	3-1/2"	\$259
20MB	ST-225	65 MS	5-1/4"	\$225
30MB RLL	ST-238	65 MS	5-1/4"	\$249
40MB	ST-251	40 MS	5-1/4"	\$379
40MB	ST-251-1	28 MS	5-1/4"	\$469
60MB RLL	ST-277	40 MS	5-1/4"	\$449
80MB	ST-4096	28 MS	5-1/4"	\$629

1 Mb 3 1/2" DRIVE \$99.95



- ULTRA HIGH DENSITY
- READ/WRITE 720K DISKS, TOO
- FDD-1.44X BLACK FACEPLATE
- FDD-1.44A BEIGE FACEPLATE
- FDD-1.44 SOFT SOFTWARE DRIVER \$19.95

1/2 HEIGHT FLOPPY DISK DRIVES:

FD-55B 5-1/4" TEAC DS/DD 360K \$99.95
FD-55G 5-1/4" TEAC DS/HD 1.2M \$129.95
FDD-360 5-1/4" DS/DD 360K \$69.95
FDD-1.2 5-1/4" DS/HD 1.2M \$95.95
FDD-3.5X 3-1/2" 720K (BLACK) \$97.95
FDD-3.5A 3-1/2" 720K (BEIGE) \$97.95

NASHUA DISKETTES (BOXES OF 10):

N-MD2D 360K DS/DD \$6.95
N-MD2D BULK (MULTIPLES OF 50 DISKS) EACH .49
N-MD2H 1.2 MB DS/HD \$13.95
N-3.5HD 1.44 MB 3-1/2" DS/HD \$49.95
N-3.5DS 720K 3-1/2" DD/DS \$16.95

BUILD YOUR OWN SYSTEM!

OVER 25,000 JDR SYSTEMS HAVE BEEN BUILT. OUR DETAILED INSTRUCTIONS MAKE IT VERY EASY—ALL YOU NEED IS ABOUT 2 HOURS AND A SCREWDRIVER!



VIDEO INSTRUCTIONS \$4.95 WITH SYSTEM

OUR 20 MINUTE VIDEO SHOWS YOU STEP-BY-STEP HOW TO BUILD AN XT-COMPATIBLE SYSTEM. SPECIFY VHS OR BETA. VIDEO WITH SYSTEM KIT, \$4.95 VIDEO ALONE, 19.95

10 MHz TURBO 8088 SYSTEM \$595.86

- SERIAL /PARALLEL PORTS, CLOCK/CALENDAR & GAME ADAPTOR ■ RUNS COLOR GRAPHICS SOFTWARE ON ITS MONOCHROME MONITOR ■ MOTHERBOARD ■ 256K RAM MEMORY ■ 135W POWER SUPPLY ■ FLIPTOP CASE
- 84 KEY KEYBOARD ■ 360K FLOPPY DRIVE
- MONOGRAMPHICS I/O CARD

12 MHz MINI-286 SYSTEM \$1038.47

- 12 MHZ MINI-286 MOTHERBOARD ■ 512K RAM MEMORY
- MINI-AT CASE W/POWER SUPPLY ■ 84 KEY KEYBOARD
- MONOCHROME MONITOR ■ 1.2 MB FLOPPY DRIVE
- FLOPPY/HARD CONTROL ■ MONOGRAMPHICS CARD

EPROM PROGRAMMER \$129.95

- PROGRAMS 27XX AND 27XXX EPROMS UP TO 27512
- SUPPORTS VARIOUS PROGRAMMING FORMATS & VOLTAGES ■ SPLIT OR COMBINE CONTENTS OF SEVERAL EPROMS OF DIFFERENT SIZES
- READ, WRITE, COPY, ERASE, CHECK & VERIFY
- SOFTWARE FOR HEX AND INTEL HEX FORMATS



JDR MICRODEVICES, 2233 BRANHAM LANE, SAN JOSE, CA 95124
LOCAL (408) 866-6200 FAX (408) 559-0250 TELEX 171-110
RETAIL STORE: 1256 S. BASCOM AVE., SAN JOSE, CA
(408) 947-8881 HOURS: M-F, 9-7 SAT. 9-5 SUN. 12-4



Terms: Minimum order \$10.00. For shipping & handling include \$3.50 for ground and \$4.50 for air. Orders over 1 lb and foreign orders may require additional shipping charges—please contact the sales department for the amount. CA residents must include applicable sales tax. Prices subject to change without notice. We are not responsible for typographical errors. We reserve the right to limit quantities and to substitute manufacturer. All merchandise subject to prior sales. A full copy of our terms is available upon request. Items pictured may only be representative.

ORDER TOLL FREE 800-538-5000

COPYRIGHT 1989 JDR MICRODEVICES

CONTINENTAL US

NEC V20 & V30 CHIPS

Replace the 8086 or 8088 in Your IBM PC and Increase its Speed by up to 30%
 Part No. Price
 UPD70108-5 (5MHz) V20 Chip.....\$7.49 \$6.49
 UPD70108-8 (8MHz) V20 Chip.....\$9.49 \$7.95
 UPD70108-10 (10MHz) V20 Chip.....\$12.26 \$10.95
 UPD70116-8 (8MHz) V30 Chip.....\$9.96 \$7.95
 UPD70116-10 (10MHz) V30 Chip.....\$14.96 \$15.49

7400

Part No.	1-9	10+	Part No.	1-9	10+
7400	SALE	.15	7474	SALE	.25
7402	29	19	7475	49	39
7404	SALE	.15	7476	45	35
7405	35	25	7483	69	59
7406	39	29	7485	SALE	.45
7407	SALE	.25	7486	SALE	.29
7408	35	25	7489	1.95	1.85
7410	SALE	.15	7490	49	39
7411	35	25	7493	49	35
7414	SALE	.25	7495	59	49
7416	SALE	.19	74107	25	15
7417	SALE	.19	74121	SALE	.25
7420	29	19	74123	SALE	.35
7427	29	19	74125	SALE	.35
7430	SALE	.15	74147	1.79	1.69
7432	39	29	74150	SALE	1.10
7438	SALE	.25	74151	25	15
7442	SALE	.29	74154	1.35	1.25
7445	SALE	.59	74161	69	59
7446	89	79	74173	SALE	.59
7447	89	79	74174	SALE	.35
7448	1.95	1.85	74175	SALE	.35
7473	39	29	74193	79	69

74LS

Part No.	1-9	10+	Part No.	1-9	10+
74LS00	SALE	.15	74LS139	SALE	.29
74LS02	SALE	.15	74LS151	49	39
74LS03	28	18	74LS153	49	39
74LS04	SALE	.16	74LS154	1.19	1.09
74LS05	SALE	.16	74LS157	45	35
74LS06	59	49	74LS161	49	39
74LS07	59	49	74LS163	SALE	.35
74LS08	28	18	74LS164	SALE	.35
74LS09	28	18	74LS165	.75	.65
74LS10	SALE	.15	74LS166	SALE	.69
74LS11	29	19	74LS173	SALE	.25
74LS14	29	19	74LS174	SALE	.25
74LS20	SALE	.28	74LS175	SALE	.25
74LS21	35	25	74LS191	SALE	.39
74LS27	SALE	.19	74LS192	69	59
74LS30	SALE	.15	74LS193	69	59
74LS32	SALE	.19	74LS194	69	59
74LS38	35	25	74LS221	SALE	.49
74LS42	49	39	74LS240	SALE	.45
74LS47	89	79	74LS241	59	49
74LS73	SALE	.25	74LS244	SALE	.49
74LS74	SALE	.19	74LS245	SALE	.59
74LS75	SALE	.25	74LS257	49	39
74LS76	39	29	74LS259	99	89
74LS83	59	49	74LS261	89	79
74LS85	59	49	74LS279	49	39
74LS86	29	19	74LS367	SALE	.29
74LS90	SALE	.29	74LS373	SALE	.59
74LS93	SALE	.29	74LS374	SALE	.49
74LS123	SALE	.35	74LS393	SALE	.69
74LS125	49	39	74LS411	1.29	1.19
74LS132	49	39	74LS590	5.95	5.85
74LS138	49	39	74LS688	2.39	2.29

74S/PROMS*

Part No.	1-9	10+	Part No.	1-9	10+
74S00	SALE	.19	74S188*	1.49	
74S04	SALE	.19	74S189	1.49	
74S32	SALE	.19	74S240	1.39	
74S74	SALE	.19	74S244	SALE	.75
74S12	1.25	1.15	74S288*	1.49	
74S124	SALE	1.25	74S288*	1.49	
74S138	59	49	74S373	SALE	.99
74S153	39	29	74S374	SALE	.99
74S163	99	89	74S387*	1.29	
74S174	SALE	.25	74S472*	SALE	2.49
74S175	SALE	.25	74S571*	2.49	

CD-CMOS

Part No.	1-9	10+	Part No.	1-9	10+
CD4001	19	9	CD4051	59	49
CD4002	19	9	CD4052	59	49
CD4007	25	15	CD4053	59	49
CD4011	19	9	CD4060	65	55
CD4012	25	15	CD4066	29	19
CD4013	29	19	CD4069	19	9
CD4015	49	39	CD4070	29	19
CD4016	29	19	CD4071	22	12
CD4017	49	39	CD4072	22	12
CD4018	59	49	CD4073	22	12
CD4020	59	49	CD4081	22	12
CD4021	59	49	CD4093	35	25
CD4024	45	35	CD4094	89	79
CD4027	35	25	CD4503	39	29
CD4028	49	39	CD4511	69	59
CD4029	69	59	CD4518	75	65
CD4030	35	25	CD4520	75	65
CD4040	65	55	CD4522	79	69
CD4042	59	49	CD4528	79	69
CD4043	59	49	CD4538	79	69
CD4046	65	55	CD4543	79	69
CD4047	65	55	CD4584	49	39
CD4049	29	19	CD4585	69	59
CD4050	29	19			

EEPROMS

Part No.	1-9	10+	Part No.	1-9	10+
2816A	2048x8	350ns (BV-15V) 5V Read/Write	5	25	15
2816A	2048x8	250ns (BV-15V) 5V Read/Write	5	25	15
2817A	2048x8	350ns 5V Read/Write	6	26	16
2864A	8192x8	250ns 5V Read/Write (Pin 1 No R) B13.95			
2864A	8192x8	300ns 5V Read/Write (Pin 1 No R) B12.95			
2865A	3019x8	300ns 5V Read/Write	9	35	25
52B13	2048x8	350ns (21V) 5V Read Only	1	49	39

MICROPROCESSOR COMPONENTS

Z80, Z80A, Z80B, SERIES			8000 SERIES Continued			8000 SERIES Continued		
Part No.	Price		Part No.	Price		Part No.	Price	
Z80	1.19		8155-2	3.49		8286	2.29	
Z80A	1.29		81C55	3.95		8741	9.95	
Z80A-CTC	1.65		8156	2.95		8742	19.95	17.95
Z80A-DART	4.95	3.95	8205	10.95		8748 (25V)	7.95	
Z80A-PIO	1.89	1.49	82C11	6.95		8748H (HMOS)(21V)	9.95	9.95
Z80A-SIO-OC	2.95	2.95	8212	2.29		8749	9.95	
Z80B	2.75		8216	1.39		8751H (3.5-12MHz)	39.95	
Z80B-CTC	2.95	3.25	8224	2.95	1.95	8755	19.95	12.95
Z80B-PIO	3.35	1.49	8228	1.65	1.49	80287-3 (5MHz)	1.69	95
Z8681B1	8.95	6.95	8237-5	4.95	3.95	80287-8 (8MHz)	209.95	
			8243	1.75		80287-10 (10MHz)	259.95	
			8250A	4.95	3.95	80386-16 PGA	279.95	
			8250B (For IBM)	6.95	4.95	80387-16 (16MHz)	395.95	
			8251A	1.69		80387-20 (20MHz)	459.95	
			8039	1.95	1.59	80387-25 (25MHz)	569.95	
			8052AH-BASIC	24.95		80387-SX (16MHz)	369.95	
			8080A	2.25	1.49	82284 (8MHz)	9.49	
			8085A	2.49	5.95	82288 (8MHz)	9.95	
			8085A-2	3.59	2.95			
			8087 (5MHz)	99.95	94.95			
			8087-1 (10MHz)	184.95				
			8087-2 (8MHz)	134.95				
			8088 (5MHz)	4.95	3.49			
			8088-2 (8MHz)	6.95	5.95			
			8116	4.95	3.95			
			8155	2.49	8284	1.29		

STATIC RAMS

Part No.	Function	Price
2016-12	2048x8 120ns	3-75 2.95
2102	1024x1 350ns MOS	.89
2112	256x4 450ns MOS	2-49 1.95
2114N	1024x4 450ns	.79
2114N-2L	1024x4 200ns Low Power	1.49
21C14	1024x4 200ns (CMOS)	.49
5101	256x4 450ns (CMOS)	2.95 2.49
6116P-1	2048x8 100ns (16K) CMOS	3.95 3.19
6116P-3	2048x8 150ns (16K) CMOS	3.49 2.79
6116LP-1	2048x8 100ns (16K) LP CMOS	4.99 3.59
6116LP-3	2048x8 150ns (16K) LP CMOS	2.95 3.09
6264P-10	8192x8 100ns (64K) CMOS	9.95 9.49
6264P-15	8192x8 150ns (64K) CMOS	9.25 7.49
6264LP-10	8192x8 100ns (64K) LP CMOS	10.95 10.25
6264LP-15	8192x8 120ns (64K) LP CMOS	10.49 8.95
6264LP-15	8192x8 150ns (64K) LP CMOS	10.25 7.95
6514	1024x4 350ns CMOS	3-49 3.75
43256-10L	32.768x8 100ns (256K) Low Power	23.95
43256-15L	32.768x8 150ns (256K) Low Power	22.95
62256LP-85	32.768x8 85ns (256K) LP CMOS	26.95
62256LP-10	32.768x8 100ns (256K) LP CMOS	24.95
62256LP-12	32.768x8 120ns (256K) LP CMOS	24.25

DYNAMIC RAMS

Part No.	Function	Price
TM91000L-10	1.048.576x9 100ns 1MEGx9 SIP	399.95 329.95
TM91000S-10	1.048.576x9 80ns 1MEGx9 SIP	399.95 299.95
TM91000L-80	1.048.576x9 80ms 1MEGx9 SIP	449.95 349.95
TM91000S-80	1.048.576x9 80ms 1MEGx9 SIP	449.95 309.95
TMS4416-12	16.384x4 120ns	6-25 5.49
TMS4416-15	16.384x4 150ns	6-25 5.49
4116-15	16.384x4 150ns (MMS290N-2)	1-39 1.25
4128-15	131.072x1 150ns (Piggyback)	5.29
4164-100	65.536x1 100ns	3.49
4164-120	65.536x1 120ns	2.95
4164-150	65.536x1 150ns	2.59
41256-60	262.144x1 60ns	14-99 10.95
41256-80	262.144x1 80ns	10-19 8.95
41256-100	262.144x1 100ns	9-75 8.49
41256-120	262.144x1 120ns	8-95 7.95
41256-150	262.144x1 150ns	8-49 7.49
41464-120	64Kx4 120ns Video RAM	11.95
41464-100	65.536x4 100ns	14-49 11.95
41464-12	65.536x4 120ns	11-95 9.95
41464-15	65.536x4 150ns	10-95 8.95
51258-10	262.144x1 100ns Static Column	10-95 11.95
85227-10PL	262.144x9 100ns 256x9 SIP	149.95 105.95
85227-10PS	262.144x9 100ns 256x9 SIM	149.95 105.95
51100P-80	1.048.576x1 (1 Meg)	25.95 21.95
51100P-80	1.048.576x1 (80ns 1 Meg)	34.95 24.95
514256P-10	262.144x4 100ns (1 Meg)	24.95 29.95
514256P-10	262.144x4 100ns Static Column	31.95

EPROMS

Part No.	Function	Price
TMS2516	2048x8 450ns (25V)	6-95 5.95
TMS2532	4096x8 450ns (25V)	5-95 4.95
TMS2532A	4096x8 450ns (12.5V)	4-49 3.25
TMS2564	8192x8 450ns (25V)	6-95 4.95
TMS2716	2048x8 450ns (-5V, +12V)	6-95 4.49
1702A	256x8 (1µs)	4.95
2708	1024x8 450ns	6.95
2716	2048x8 450ns (25V)	3.75
2716-1	2048x8 350ns (25V)	4-25 3.95
27C16	2048x8 450ns (25V) CMOS	4-25 3.75
27C16-1	2048x8 350ns (25V) CMOS	4-25 3.95
2732A-20	4096x8 200ns (21V)	4.25
2732A-25	4096x8 250ns (21V)	3.95
27C32	4096x8 450ns (25V) CMOS	4-95 4.25
2764-20	8192x8 200ns (21V)	4.25
2764-25	8192x8 250ns (21V)	3.59

Worldwide • Since 1974
QUALITY COMPONENTS • COMPETITIVE PRICING
• PROMPT DELIVERY

15th ANNIVERSARY
YEAR
1974 - 1989

TEST EQUIPMENT

Metex Digital Multimeters

Metex General Specs:
 • Handheld, high accuracy
 • AC/DC Voltage, AC/DC Current, Resistance, Diodes, Continuity, Transistor hFE • Manual ranging w/overload protection
M3650/B & M4650 only:
 • Also measures frequency and capacitance
M4650 only:
 • Data Hold Switch
 • 4.5 Digit



M4650 Pictured

M3610	3.5 Digit Multimeter.....	\$49.95
M3650	3.5 Digit w/Freq. & Capacitance.....	\$69.95
M3650B	Same as M3650 w/Bargraph.....	\$79.95
M4650	4.5 Dig. w/Freq., Capacitance and Data Hold Switch.....	\$99.95

Metex Autoranging Jumbo Readout DMM

• AC/DC Voltage, AC/DC Current, Resistance, Diodes, Continuity and Frequency
 • 3.75 Digit (.8" High)
 • Ruggedized, Water-resistant case
 • Easy-to-use pushbutton switches



M80.....\$59.95

A.R.T. EPROM Programmer

• Programs all current EPROMs in the 2716 to 27512 range plus the X2864 EEPROM • May be operated by any RS232 port w/terminal emulation • Fully intelligent • ASCII command driven • Menu driven software included
EPP.....\$179.95



Oscilloscope Probes


• Attenuation: x1 / x10
 • Capacitance (LF180): 180pF / 22pF; (LF210): 40pF / 17pF



LF180 Pictured

LF180	40MHz Oscilloscope Probe.....	\$19.95
LF210	100MHz Oscilloscope Probe.....	\$29.95

Digital Logic Probes and Logic Pulser

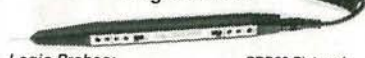

Logic Probes: PRB20 Pictured

• High, low and pulse indication • 20MHz and 50MHz versions available • Circuit powered w/over/undervoltage indicators

Logic Pulser (LP540):

• Generates "one-shot" pulse or continuous 5Hz pulse train • Audible tone • Compatible with: TTL, DTL, RTL, HTL, HINIL, MOS and CMOS ICs
PRB20 20MHz Logic Probe.....\$26.95
PRB20A 20MHz Audible Logic Probe.....\$33.95
PRB50 50MHz Logic Probe.....\$47.95
LP540 Logic Pulser.....\$19.95

RS232 Tester and Breakout Box
Make Your Own Custom Cables!

• Complete cable breakout and reconfiguration exists with 24 in-line switches and 54 in-line machine tool sockets • Bi-color LEDs tell you if a line is hi, low or off • Male to female DB25 pin connectors • Includes device wiring chart
MLA1.....\$29.95



JAMECO IBM PC/XT 8MHz Turbo Compatible Kit With 256K RAM

- Free! QAPLUS Diagnostic Software Included!
- Free! PC Write Word Processing Software Included!
- 256K RAM Included, Expandable to 640K
- AMI BIOS ROMs Included
- 4.77 or 8MHz Operation
- Regular \$592.01 value for only \$479.95!
- Flip-Top Case w/150 Watt Power Supply
- 360K Disk Drive
- Parallel Printer Port
- 84-Key Keyboard
- Monochrome Amber Monitor



JE3002	IBM Compatible PC/XT 8MHz Turbo Kit	\$499.95	\$479.95
EZDOS	Digital Research MS/PC-DOS Comp. Operating System.....	\$49.95	
EZDOSP	Same as above with TrueBASIC.....	\$69.95	

IBM COMPATIBLE DISPLAY MONITORS

AMBER	12" Amber Mono	\$99.95
HD55H	14" RGB 640x240	\$249.95
TM5154	EGA 14" 720x350	\$399.95 \$369.95
JE1059	EGA Monitor & Card	\$619.95 \$499.95
TM5155	14" Multiscan 800x560	\$649.95 \$499.95
QC1478	14" VGA 720x480	\$449.95 \$399.95
JE2055	VGA Monitor & Card	\$649.95 \$599.95



QC1478 Pictured

JAMECO IBM PC/XT/AT COMPATIBLE CARDS

JE1050	Monochrome Graphics Card w/Parallel Printer Port (PC/XT/AT).....	\$59.95
JE1052	Color Graphics Card w/Parallel Printer Port (PC/XT/AT).....	\$49.95
JE1055	EGA Card w/256K Video RAM (PC/XT/AT).....	\$159.95
JE1071	Multi I/O Card w/Controller & Monochrome Graphics (PC/XT).....	\$119.95
JE1060	I/O Card w/Serial, Game, Printer Port & Real Time Clock (PC/XT).....	\$59.95
JE1061	RS232 Serial Half Card (PC/XT).....	\$29.95
JE1062	RS232 Serial Half Card (AT).....	\$34.95
JE1065	I/O Card w/Serial, Game and Parallel Printer Port (AT).....	\$59.95
JE1081	2MB Expanded or Extended Memory Card (zero-K on-board) (AT).....	\$119.95
JE1041	20/40MB Hard Disk Controller Card (PC/XT).....	\$79.95
JE1043	360K/720K/1.2MB/1.44MB Floppy Disk Controller Card (PC/XT/AT).....	\$49.95
JE1044	360K Floppy/Hard Disk Controller Card (PC/XT).....	\$129.95
JE1045	360K/720K/1.2MB/1.44MB Floppy/Hard Disk Controller Card (AT).....	\$149.95

SEAGATE HALF-HEIGHT HARD DISK DRIVES

ST225	20MB Drive only (PC/XT/AT)	\$224.95
ST225XT	20MB w/Controller (PC/XT)	\$269.95
ST225AT	20MB w/Controller (AT)	\$339.95
ST238	30MB Drive only (PC/XT/AT)	\$249.95
ST238XT	30MB w/Controller (PC/XT)	\$299.95
ST238AT	30MB w/Controller (AT)	\$389.95




ST225XT Pictured

Seagate 40MB and 60MB Hard Disk Drives Also Available!

IBM PC/XT/AT COMPATIBLE MOTHERBOARDS

JE1001	4.77/8MHz (PC/XT)	\$89.95
JE1002	4.77/10MHz (PC/XT)	\$109.95 \$99.95
JE3005	Baby 8/12MHz (AT)	\$329.95 \$299.95
JE3010	Baby 8/16MHz NEAT (AT)	\$469.95 \$399.95
JE3020	Baby 16MHz 80386 (AT)	\$1199.95
JE3025	Baby 20MHz 80386 (AT)	\$1499.95
JE3026	Full-Size 25MHz 80386 (AT)	\$2299.95

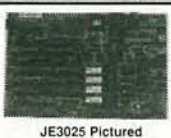

JE3025 Pictured

IBM PC/XT/AT COMPATIBLE 3.5"/5.25" DISK DRIVES

352KU	3.5" 720KB (PC/XT/AT)	\$109.95
356KU	3.5" 1.44MB (PC/XT/AT)	\$129.95
JE1020	5.25" 360KB (PC/XT/AT) Black	\$89.95
JE1021	5.25" 360KB (PC/XT/AT) Beige	\$89.95
JE1022	5.25" 1.2MB (PC/XT/AT) Beige	\$99.95



JE1022 Pictured


IBM PC/XT/AT COMPATIBLE INTERNAL MODEMS

1200H	1200/300 Baud Internal Modem w/MaxiMite Comm. Software (PC/XT/AT)	\$69.95
2400H	2400/1200/300 Baud Internal Modem w/MaxiMite Comm. Stwr. (PC/XT/AT)	\$129.95

External Modems and Pocket-Size Modem Also Available!

PROTOTYPING PRODUCTS

Jameco Solderless Breadboards

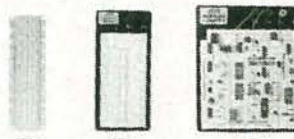

Part No.	Dim. L" x W"	Contact Points	Binding Posts	Price
JE20	6.5x.75	200	0	\$1.95
JE21	3.25x2.125	400	0	\$4.95
JE22	6.5x1.325	630	0	\$5.95
JE23	6.5x2.125	830	0	\$7.95
JE24	6.5x3.125	1,360	2	\$12.95
JE25	6.5x4.25	1,660	3	\$19.95
JE26	6.875x5.75	2,390	4	\$24.95
JE27	7.25x5.75	3,220	4	\$34.95

DATAK Photo Etch PCB Kit
Make your own circuit boards!

The ER4 photo etch kit contains all the chemicals necessary for any hobbyist, engineer or student to create professional circuit boards. Contains: Print frame, photo copy film, resist developer, etch resist, 2 copper circuit boards, concentrated etchant, film developer and fixer, resist patterns and complete instructions.



ER4 Photo Etch PCB Kit.....\$34.95

Jameco Prototype PC Boards

Specs: Laminated glass epoxy .062" thick 2 oz. copper clad with solder tin finish. All holes are .042" dia. on .10" x .10" grid pattern.



JE401 Pictured


JE401	4.5"x6.5" 1-sided 3-hole pad pattern	\$9.95
JE403	4.5"x6.5" 1-sided pwr & gnd busses	\$9.95
JE405	4.5"x6.5" 1-sided general purpose	\$9.95
JE407	5"x13.25" 2-sided general purpose	\$19.95
JE417	4.2"x6.5" PC/XT 1/2 card proto board	\$19.95
JE421	4.75"x3.7" IBM PC/XT Card Extender	\$19.95

ENGINEERING/DATA BOOKS

21035	Sams TTL Cookbook (88)	\$14.95
21398	Sams CMOS Cookbook (88)	\$19.95
22453	Sams Op-Amp Cookbook (88)	\$21.95
270645	Intel 8-bit Controller Hndbk. (89)	\$19.95
270646	Intel 16-bit Controller Hndbk. (89)	\$19.95
270647	Intel 32-bit Controller Hndbk. (89)	\$19.95
400041	NSC Linear Data Book Vol. 1 (88)	\$14.95
400042	NSC Linear Data Book Vol. 2 (88)	\$9.95
400043	NSC Linear Data Book Vol. 3 (88)	\$9.95
ICM89	1989 IC Master (3 Volume Set)	\$129.95

EDUCATIONAL KITS

JE310/315:	Fiber optics kits demonstrate the principles of fiber optic system design. Complete step-by-step instructions, theory of operation and tutorial info. incl.	
JE2206:	Function generator kit provides three basic waveforms: sine, triangle and square wave. Frequency range: 1Hz to 100kHz	
JE310	Fiber Optics Experimenter Kit.	\$19.95
JE315	Advanced Fiber Optics Kit.....	\$29.95
JE2206	Function Generator Kit.....	\$19.95

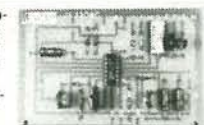

JE2206 Pictured

1355 Shoreway Road
 Belmont, CA 94002
24 Hour Order Hotline (415) 592-8097
 FAX's (415) 592-2503 or (415) 595-2664
 Telex 176043 - Ans. Back: Jameco Blmt
 Data Sheets - 50c each
Send \$2.00 Postage for a FREE 1989 CATALOG
 © 1989 Jameco Electronics 7/89
 IBM is a registered trademark of International Business Machines



\$20.00 Minimum Order - U.S. Funds Only
 CA Residents Add 6%, 6.5% or 7% Sales Tax
 Shipping - Add 5% plus \$1.50 Insurance
 (May vary according to weight)
 Terms: Prices subject to change without notice.
 We are not responsible for typographical errors.
 We reserve the right to substitute manufacturers.
 Items subject to availability and prior sale.
 Products pictured may only be representative.
 Complete list of terms/warranties is available upon request.

24-Hour Order Hotline (415) 592-8097 • The Following Phone Lines Are Available From 7AM - 5PM P.S.T.:

• Customer Service (415) 592-8121 • Technical Assistance (415) 592-9990 • Credit Department (415) 592-9983 • All Other Inquiries (415) 592-7108

DIGI-KEY CORPORATION

1-800-344-4539

AK, Puerto Rico - 218-681-674 Telex - 62827814 FAX - 218-681-3360 TWX - 910350882 DIGI KEY CORP

INTEGRATED CIRCUITS

Part	Price	Part	Price
7400 TTL		7400 TTL	
7401	1.00	7401	1.00
7402	1.00	7402	1.00
7403	1.00	7403	1.00
7404	1.00	7404	1.00
7405	1.00	7405	1.00
7406	1.00	7406	1.00
7407	1.00	7407	1.00
7408	1.00	7408	1.00
7409	1.00	7409	1.00
7410	1.00	7410	1.00
7411	1.00	7411	1.00
7412	1.00	7412	1.00
7413	1.00	7413	1.00
7414	1.00	7414	1.00
7415	1.00	7415	1.00
7416	1.00	7416	1.00
7417	1.00	7417	1.00
7418	1.00	7418	1.00
7419	1.00	7419	1.00
7420	1.00	7420	1.00

INTEGRATED CIRCUITS

Part	Price	Part	Price
7421	1.00	7421	1.00
7422	1.00	7422	1.00
7423	1.00	7423	1.00
7424	1.00	7424	1.00
7425	1.00	7425	1.00
7426	1.00	7426	1.00
7427	1.00	7427	1.00
7428	1.00	7428	1.00
7429	1.00	7429	1.00
7430	1.00	7430	1.00
7431	1.00	7431	1.00
7432	1.00	7432	1.00
7433	1.00	7433	1.00
7434	1.00	7434	1.00
7435	1.00	7435	1.00
7436	1.00	7436	1.00
7437	1.00	7437	1.00
7438	1.00	7438	1.00
7439	1.00	7439	1.00
7440	1.00	7440	1.00

SILICON TRANSISTORS

Part	Price	Part	Price
2N4350	1.00	2N4350	1.00
2N4351	1.00	2N4351	1.00
2N4352	1.00	2N4352	1.00
2N4353	1.00	2N4353	1.00
2N4354	1.00	2N4354	1.00
2N4355	1.00	2N4355	1.00
2N4356	1.00	2N4356	1.00
2N4357	1.00	2N4357	1.00
2N4358	1.00	2N4358	1.00
2N4359	1.00	2N4359	1.00
2N4360	1.00	2N4360	1.00
2N4361	1.00	2N4361	1.00
2N4362	1.00	2N4362	1.00
2N4363	1.00	2N4363	1.00
2N4364	1.00	2N4364	1.00
2N4365	1.00	2N4365	1.00
2N4366	1.00	2N4366	1.00
2N4367	1.00	2N4367	1.00
2N4368	1.00	2N4368	1.00
2N4369	1.00	2N4369	1.00
2N4370	1.00	2N4370	1.00

1% METAL OXIDE FILM RESISTORS

Part	Price	Part	Price
1000	1.00	1000	1.00
1001	1.00	1001	1.00
1002	1.00	1002	1.00
1003	1.00	1003	1.00
1004	1.00	1004	1.00
1005	1.00	1005	1.00
1006	1.00	1006	1.00
1007	1.00	1007	1.00
1008	1.00	1008	1.00
1009	1.00	1009	1.00
1010	1.00	1010	1.00
1011	1.00	1011	1.00
1012	1.00	1012	1.00
1013	1.00	1013	1.00
1014	1.00	1014	1.00
1015	1.00	1015	1.00
1016	1.00	1016	1.00
1017	1.00	1017	1.00
1018	1.00	1018	1.00
1019	1.00	1019	1.00
1020	1.00	1020	1.00

DISC CAPACITORS

Part	Price	Part	Price
1000	1.00	1000	1.00
1001	1.00	1001	1.00
1002	1.00	1002	1.00
1003	1.00	1003	1.00
1004	1.00	1004	1.00
1005	1.00	1005	1.00
1006	1.00	1006	1.00
1007	1.00	1007	1.00
1008	1.00	1008	1.00
1009	1.00	1009	1.00
1010	1.00	1010	1.00
1011	1.00	1011	1.00
1012	1.00	1012	1.00
1013	1.00	1013	1.00
1014	1.00	1014	1.00
1015	1.00	1015	1.00
1016	1.00	1016	1.00
1017	1.00	1017	1.00
1018	1.00	1018	1.00
1019	1.00	1019	1.00
1020	1.00	1020	1.00

Standard Metallized Film Resistors

Part	Price	Part	Price
1000	1.00	1000	1.00
1001	1.00	1001	1.00
1002	1.00	1002	1.00
1003	1.00	1003	1.00
1004	1.00	1004	1.00
1005	1.00	1005	1.00
1006	1.00	1006	1.00
1007	1.00	1007	1.00
1008	1.00	1008	1.00
1009	1.00	1009	1.00
1010	1.00	1010	1.00
1011	1.00	1011	1.00
1012	1.00	1012	1.00
1013	1.00	1013	1.00
1014	1.00	1014	1.00
1015	1.00	1015	1.00
1016	1.00	1016	1.00
1017	1.00	1017	1.00
1018	1.00	1018	1.00
1019	1.00	1019	1.00
1020	1.00	1020	1.00

PANASONIC B-SERIES Polyester Capacitors

Part	Price	Part	Price
1000	1.00	1000	1.00
1001	1.00	1001	1.00
1002	1.00	1002	1.00
1003	1.00	1003	1.00
1004	1.00	1004	1.00
1005	1.00	1005	1.00
1006	1.00	1006	1.00
1007	1.00	1007	1.00
1008	1.00	1008	1.00
1009	1.00	1009	1.00
1010	1.00	1010	1.00
1011	1.00	1011	1.00
1012	1.00	1012	1.00
1013	1.00	1013	1.00
1014	1.00	1014	1.00
1015	1.00	1015	1.00
1016	1.00	1016	1.00
1017	1.00	1017	1.00
1018	1.00	1018	1.00
1019	1.00	1019	1.00
1020	1.00	1020	1.00

4000 CMOS

Part	Price	Part	Price
7400	1.00	7400	1.00
7401	1.00	7401	1.00
7402	1.00	7402	1.00
7403	1.00	7403	1.00
7404	1.00	7404	1.00
7405	1.00	7405	1.00
7406	1.00	7406	1.00
7407	1.00	7407	1.00
7408	1.00	7408	1.00
7409	1.00	7409	1.00
7410	1.00	7410	1.00
7411	1.00	7411	1.00
7412	1.00	7412	1.00
7413	1.00	7413	1.00
7414	1.00	7414	1.00
7415	1.00	7415	1.00
7416	1.00	7416	1.00
7417	1.00	7417	1.00
7418	1.00	7418	1.00
7419	1.00	7419	1.00
7420	1.00	7420	1.00

A/D & D/A

Part	Price	Part	Price
7400	1.00	7400	1.00
7401	1.00	7401	1.00
7402	1.00	7402	1.00
7403	1.00	7403	1.00
7404	1.00	7404	1.00
7405	1.00	7405	1.00
7406	1.00	7406	1.00
7407	1.00	7407	1.00
7408	1.00	7408	1.00
7409	1.00	7409	1.00
7410	1.00	7410	1.00
7411	1.00	7411	1.00
7412	1.00	7412	1.00
7413	1.00	7413	1.00
7414	1.00	7414	1.00
7415	1.00	7415	1.00
7416	1.00	7416	1.00
7417	1.00	7417	1.00
7418	1.00	7418	1.00
7419	1.00	7419	1.00
7420	1.00	7420	1.00

Memory

Part	Price	Part	Price
7400	1.00	7400	1.00
7401	1.00	7401	1.00
7402	1.00	7402	1.00
7403	1.00	7403	1.00
7404	1.00	7404	1.00
7405	1.00	7405	1.00
7406	1.00	7406	1.00
7407	1.00	7407	1.00
7408	1.00	7408	1.00
7409	1.00	7409	1.00
7410	1.00	7410	1.00
7411	1.00	7411	1.00
7412	1.00	7412	1.00
7413	1.00	7413	1.00
7414	1.00	7414	1.00
7415	1.00	7415	1.00
7416	1.00	7416	1.00
7417	1.00	7417	1.00
7418	1.00	7418	1.00
7419	1.00	7419	1.00
7420	1.00	7420	1.00

TRANSFORMERS

Part	Price	Part	Price
7400	1.00	7400	1.00
7401	1.00	7401	1.00
7402	1.00	7402	1.00
7403	1.00	7403	1.00
7404	1.00	7404	1.00
7405	1.00	7405	1.00
7406	1.00	7406	1.00
7407	1.00	7407	1.00
7408	1.00	7408	1.00
7409	1.00	7409	1.00
7410	1.00	7410	1.00
7411	1.00	7411	1.00
7412	1.00	7412	1.00
7413	1.00	7413	1.00
7414	1.00	7414	1.00
7415	1.00	7415	1.00
7416	1.00	7416	1.00
7417	1.00	7417	1.00
7418	1.00	7418	1.00
7419	1.00	7419	1.00
7420	1.00	7420	1.00

PANASONIC LS SERIES

Part	Price	Part	Price
1000	1.00	1000	1.00
1001	1.00	1001	1.00
1002	1.00	1002	1.00
1003	1.00	1003	1.00
1004	1.00	1004	1.00
1005	1.00	1005	1.00
1006	1.00	1006	1.00
1007	1.00	1007	1.00
1008	1.00	1008	1.00
1009	1.00	1009	1.00
1010	1.00	1010	1.00
1011	1.00	1011	1.00
1012	1.00	1012	1.00
1013	1.00	1013	1.00
1014	1.00	1014	1.00
1015	1.00	1015	1.00
1016	1.00	1016	1.00
1017	1.00	1017	1.00
1018	1.00	1018	1.00
1019	1.00	1019	1.00
1020	1.00	1020	1.00

MINIATURE ALUMINUM ELECTROLYTIC CAPACITORS


Part	Price	Part	Price
1000	1.00	1000	1.00
1001	1.00	1001	

★ **QUALITY PARTS** ★ **DISCOUNT PRICES** ★ **FAST SHIPPING**

ALL ELECTRONICS CORP.

3 to 6 Vdc MOTOR with GEARBOX

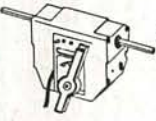Probably designed for child's toy. Lever selects 2 forward and one reverse speed. 1st gear approx. 120 rpm/6vdc, 2nd gear approx. 300 rpm/6vdc, Reverse approx. 120 rpm/6vdc.



3.35" X 1.75" X 3.25"
CAT# DCM-10 \$6.00

CASSETTE MECHANISM

Alpine cassette transport mechanism. Includes stereo tape head, Mitsubishi # MET-3RF2B 13.2 Vdc motor, belt, pulleys, capstan, fast-forward, rewind and eject actuator. Does not include amplifier section. 6 1/2" X 5 1/4" X 1 3/4".



CAT# CMEC-5 \$7.50 each
10 for \$65.00

6 VOLT D.C. 9.5 AMP/HOUR GEL-CELL


Elpower# 695
6 volt, 9.5 amp/hour rechargeable gel-cell battery. 4.25" X 2.75" X 5.5". Quick connect terminals.



CAT# GC-695 \$15.00 each

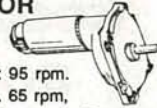12-36 VDC GEAR-HEAD MOTOR

Brevet# 780-953075
Rated for 36 Vdc: 95 rpm. 0.5 amps no load. 65 rpm, 1.5 amp @ 12 lb/in torque. Gearbox is 3 1/4" X 3 1/4" X 1 15/16" deep. Motor is 1 1/2" diameter X 3 1/2" long with double flattened 5/16" X 1" shaft. Ideal for pumps, lift mechanisms, robotics and other high torque applications. CAT# MOTG-11 \$15.00 each • 2 for \$25.00



WALL TRANSFORMERS

ALL PLUG DIRECTLY INTO 120 VAC OUTLET
6 Vdc @ 200 ma. CAT# DCTX-620 \$2.25
6 Vdc @ 750 ma. CAT# DCTX-675 \$3.50
9 Vdc @ 250 ma. CAT# DCTX-925 \$2.50
12 Vdc @ 900 ma. CAT# ACTX-1293 \$3.50
18 Vdc @ 1 amp. CAT# ACTX-1885 \$3.50

SWITCHES

ITT PUSH BUTTON
ITT MDPL series. 3/4" X 1/2" gray rectangular key cap. S.P.S.T. N.O.
Push to close. RATED: 0.1 amp switching, 0.25 amp carry current. P.C. mount. CAT# PB-8 \$6.00 each • 10 for \$50.00



10 POSITION MINI-ROTARY
Grayhill# 56P96-01-1-10N-C
Mini rotary switch. Non-shorting. 1 deck, 10 positions. .125" dia. shaft X .375" long. .377" behind the panel depth. P.C. pins. CAT# MRS-10 WAS \$2.50 NOW \$1.50 each



SPDT PUSHBUTTON
Marquard# 1843
Rated 6 amps @ 125/250 Vac. Black plastic pushbutton. Switch body: .92" X .94" X .65". CAT# PB-18 \$1.65 each • 10 for \$15.00 each



S.P.S.T. (ON-OFF)
All plastic body. Standard size toggle. 7/16" threaded mounting bushing. Copper contacts. Rated: 10 amp @ 125 Vac. CAT# STS-1 \$1.00 each
10 for \$8.50 • 100 for \$75.00



LED'S

STANDARD JUMBO DIFFUSED T-1-3/4 size
RED CAT# LED-1 10 for \$1.50 • 100 for \$13.00
GREEN CAT# LED-2 10 for \$2.00 • 100 for \$17.00
YELLOW CAT# LED-3 10 for \$2.00 • 100 for \$17.00

FLASHING LED with built in flashing circuit operates on 5 volts...
RED \$1.00 each
CAT# LED-4 10 for \$9.50
GREEN \$1.00 each
CAT# LED-4G 10 for \$9.50

BI-POLAR LED
Lights RED one direction, GREEN the other. Two leads. CAT# LED-6 2 for \$1.70

LED HOLDER
Two piece holder. CAT# HLED 10 for 65c

RELAYS

12 VOLT D.C. COIL S.P.D.T.
Omron# G2E-184P 4 Amp contacts 335 ohm coil. Sugar cube size. .61" X .42" X .44" high. P.C. mount with pins on DIP spacing. CAT# RLY-787 \$1.50 each

5 VOLT DC SIP RELAY
Gould, Allied Control# SR-1A-5VDC
SPST-normally open SIP reed relay. 95 ohm coil. 2 amp contacts. .59" X .29" X .39" high. Housing resists flasks fluorocarbon and chlorinated commercial solvents. CAT# RLY-SIP6 \$1.00 each • 10 for \$8.50

10 AMP SOLID STATE RELAY


ELECTROL# S2181 CONTROL
Rated 5.5 to 10 Vdc (will operate on 3-32 Vdc). LOAD: 10 amp @ 240 Vac 2 1/4" X 1 3/4" X 7/8"
CAT# SSRLY-10B \$9.50 each
QUANTITY DISCOUNT
10 for \$85.00 • 25 for \$175.00
50 for \$300.00 • 100 for \$500.00

XENON TUBE

1" long flashtube prepped with 3 1/2" red and black leads. Ideal for electronic flash or strobe projects. CAT# FLT-3 2 for \$1.00

MINIATURE BCD THUMBWHEEL SWITCHES

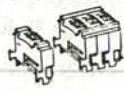SMK# J-D0001 #01
Each switch has digits 0-9. Snap together to make up any necessary configuration. Designed to mount directly to P.C. board. Pins on .1" centers. Each switch is .64" high X .59" wide X .235" thick.
CAT# SWTH-5 2 for \$1.00
10 for \$4.50 • 100 for \$40.00




SOUND AND VIDEO MODULATOR

TM UM1381-1. Designed for use with T.L. computers. Can be used with video cameras, games or other audio/video source. Built in A/B switch enables user to switch from T.V. antenna without disconnection. Operates on channel 3 or 4. Requires 12 Vdc. Hook up diagram included.
CAT# AVMOD \$5.00 each



LIGHT ACTIVATED MOTION SENSOR

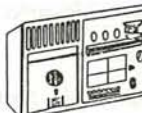This device contains a photo cell which senses sudden change in ambient light. Could be used as a door annunciator or modified to trigger other devices. 5 1/2" X 4" X 1". Operates on 6 Vdc. Requires 4 AA batteries (not included)
CAT# LSMD \$5.75 per unit



1/4 WATT RESISTOR KIT

Ideal for the workshop, this 1/4 watt resistor kit contains 10 pieces each of 42 of the most popular values (420 pieces total), includes a divided box and a parts locator.



VALUES in this kit are:
1 ohm, 10 ohm, 39 ohm, 47 ohm, 51 ohm, 68 ohm, 100 ohm, 130 ohm, 150 ohm, 180 ohm, 220 ohm, 330 ohm, 470 ohm, 560 ohm, 680 ohm, 1K, 1.2K, 1.5K, 2K, 2.2K, 2.7K, 3K, 4.7K, 5.1K, 5.6K, 10K, 15K, 22K, 30K, 33K, 39K, 47K, 56K, 68K, 100K, 120K, 150K, 220K, 470K, 1 MEG, 5.1 MEG, 10 MEG
The resistors alone would sell for \$21.00.
Complete kit • CAT# REKIT-14 \$17.00

PIEZO WARNING DEVICE

Murata Erie # PK8B-4A0
High pitched audible alarm. Operates on 3 - 20 Vdc @ 20 ma. 1" high x 7/8" dia. P.C. board mount.
CAT# PBZ-84 \$1.75 each



NICKEL-CAD BATTERIES (RECHARGEABLE)

SPECIAL!! AAA SIZE
Panasonic# P-18AAA
1.2 volt @ 180 MAh
CAT# NCB-AAAX \$1.50 each
10 for \$13.50 • 100 for \$125.00

AA SIZE \$2.00 each
1.25 volts 500 mA
CAT# NCB-AA

AA SIZE \$2.20 each
WITH SOLDER TABS
CAT# NCB-SAA

C SIZE \$4.25 EACH
1.2 volts 1200 mA
CAT# NCB-C

D SIZE \$4.50 each
1.2 volts 1200 mA
CAT# NCB-D

TRANSISTORS

ORDER BY PART #
PN2222 NPN TO-92 5 for 75c
PN2907 PNP TO-92 5 for 75c
2N3055 NPN TO-3 \$1.00 each
MJ2955 PNP TO-3 \$1.50 each
MJE2955T PNP TO-220 75c each
MJE3055T NPN TO-220 75c each
TIP31 NPN TO-220 75c each
TIP32 PNP TO-220 75c each
TIP220 75c each
TIP121 NPN TO-220 75c each
TIP126 PNP TO-220 75c each

WIDE BAND AMPLIFIER

NEC# UPC1651G. 1200 Mhz @ 3 db. Gain: 19db @ 1-500 hz. 5 volt operation. Small package 4mm dia. X 2.5 mm thick.
CAT# UPC-1651 2 for \$1.00
10 for \$4.50 • 100 for \$35.00

N-CHANNEL MOSFET

IRF-511 TO-220 case
CAT# IRF 511 \$1.00 each • 10 for \$9.00
LARGE QUANTITY AVAILABLE

STROBE KIT

Variable rate strobe kit, flashes between 60 to 120 times per minute. Will operate on either 6 or 12 Vdc depending upon how you wire the circuit. Comes complete with P.C. board and instructions for easy assembly. CAT# STROBE-1 \$7.50 each

TELEPHONE COUPLING TRANSFORMER

Multi Products International# A19N-HO-1D/1
Primary 600 ohm
Secondary: 600/600 ohm
.77" X .61" X .83" high.
6 p.c. pins on .187" centers.
Primary inductance: 300 mH min., at 1kHz, 1 volt.
CAT# TCTX-1 \$1.25 each
10 for \$11.00 • 100 for \$95.00

OPTO SENSOR

U shaped package with mounting ears. 1/8" opening. 3/4" mounting holes. CAT# OSU-6 50c each
10 for \$4.50 • 100 for \$40.00

12 VOLT DC SOLID STATE BUZZER

Star# CMB-12 fits 14 pin DIP socket. CMOS compatible. Operates on 7 - 17 Vdc @ 1 ma. PC pins. Has trigger terminal. 70 dB @ 20 cm. 0.886" X 0.63" X .575" high.
CAT# CMB-12 \$1.25 each

14.7 VOLT TRANSFORMER

Sprite Industries# CS-510A. 14.7 volt, 60 hz, 8.82 Va. 1.61" high X 1.95" X 1.47". Mounting holes on 2.32" centers.
CAT# TX-147 \$3.00 each
10 for \$27.00 • 100 for \$250.00

CALL OR WRITE FOR OUR FREE CATALOG OVER 4000 PARTS!



Now 60 pages!

MAIL ORDERS TO:
ALL ELECTRONICS
P.O. BOX 567
VAN NUYS, CA 91408
TWX-5101010163 (ALL ELECTRONIC)

OUTSIDE THE U.S.A. SEND \$2.00 POSTAGE FOR A CATALOG!!

ORDER TOLL FREE
800-826-5432
INFO: (818)904-0524
FAX: (818)781-2653
MINIMUM ORDER \$10.00
QUANTITIES LIMITED
CALIF. ADD SALES TAX
USA: \$3.00 SHIPPING
FOREIGN ORDERS INCLUDE SUFFICIENT SHIPPING. NO C.O.D.



Active keeps you active!



Whether you are in an "after-hour emergency" or are a dedicated "do-it-yourselfer", **Active** can help you! Visit one of our conveniently located stores, or refer to our catalogue. Call toll-free to access North America's largest and best selection of electronic components and accessories! **Active**, an affiliate of **Future Electronics** has over 12,000 first grade, industrial items in stock ready for **immediate delivery**.

You can count on us!

Locations Nearest You

Westborough, MA 508-366-8899	Chicago, IL 312-593-6655
Woburn, MA 617-932-4616	Seattle, WA 206-881-8191
Long Island, NY 516-471-5400	Santa Clara, CA 408-727-4550
Mt. Laurel, N.J. 609-273-2700	Baltimore, MD 301-536-5400
Detroit, MI 313-689-8000	BY PHONE 1-800-ACTIVE-4




**TOLL-FREE
1-800-ACTIVE-4**

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

Free Information Number	Page	—	Page	—	Page
108	AMC Sales	69	56	Pacific Cable	87, 89
178	Ace Communications	26	193	Parts Express	89
75	Ace Products	15	—	SCO Electronics	11
52	Active Electronics	100	176,177	Scope Electronics	CV4
107	All Electronics	99	—	Sencore	CV3, 25
—	Amazing Concepts	89, 90	186	Star Circuits	71
106	American Design Components	95	83	Star Test	24
84	Appliance Service	15	73	Synergetics	67
67	Banner Technical Books	69	92	T S M	90
109	C & S Sales	30	184	Tektronix	13
70	CEI	86	123	Tentel	27
60	CIE	37, 44	64	Test Probes	14
50	Caig Laboratories	71	181	Video-Link	24
54	Chemtronics	70	183	Viejo Publications	27
191	Chenesko Products	24	—	WPT Publications	85
—	Command Productions	26	Gernsback Publications, Inc. 500-B Bi-County Blvd. Farmingdale, NY 11735 1-516-293-3000 Fax 1-516-293-3115 President: Larry Steckler Vice President: Cathy Steckler		
182	Communications Specialists	85	For Advertising ONLY 1-516-293-3000 Fax 1-516-293-3115 Larry Steckler publisher Arline Fishman advertising director Shelli Weinman advertising associate Lisa Strassman credit manager Christina Estrada advertising assistant		
58	Cook's Institute	11	SALES OFFICES EAST/SOUTHEAST Stanley Levitan Eastern Sales Manager Radio-Electronics 259-23 57th Avenue Little Neck, NY 11362 1-718-428-6037, 1-516-293-3000		
69	Crystek	9	MIDWEST/Texas/Arkansas/ Okla. Ralph Bergen Midwest Sales Manager Radio-Electronics 540 Frontage Road—Suite 339 Northfield, IL 60093 1-312-446-1444 Fax 1-312-446-8451		
189	DX Tele Labs	24	PACIFIC COAST/ Mountain States Marvin Green Pacific Sales Manager Radio-Electronics 5430 Van Nuys Blvd. Suite 316 Van Nuys, CA 91401 1-818-986-2001 Fax 1-818-986-2009		
127	Deco Industries	24, 15			
82	Digi-Key	98			
185,192	Electronica Book Club	5, 23			
121	Fluke Manufacturing	CV2			
180	Goldstar Precision	3			
—	Grantham College	12			
86	Heathkit	11			
65	J & W	7			
113	JDR Microdevices	92			
170,171	JDR Microdevices	93, 94			
114	Jameco	96			
115	Jensen Tools	24			
87	MCM Electronics	91			
53	MD Electronics	91			
93,190	Mark V. Electronics	88, 15			
61	Microprocessors Unltd	77			
188	Ming Engineering	24			
—	NESDA	70			
—	NRI	16			
187	Opto Electronics	21			

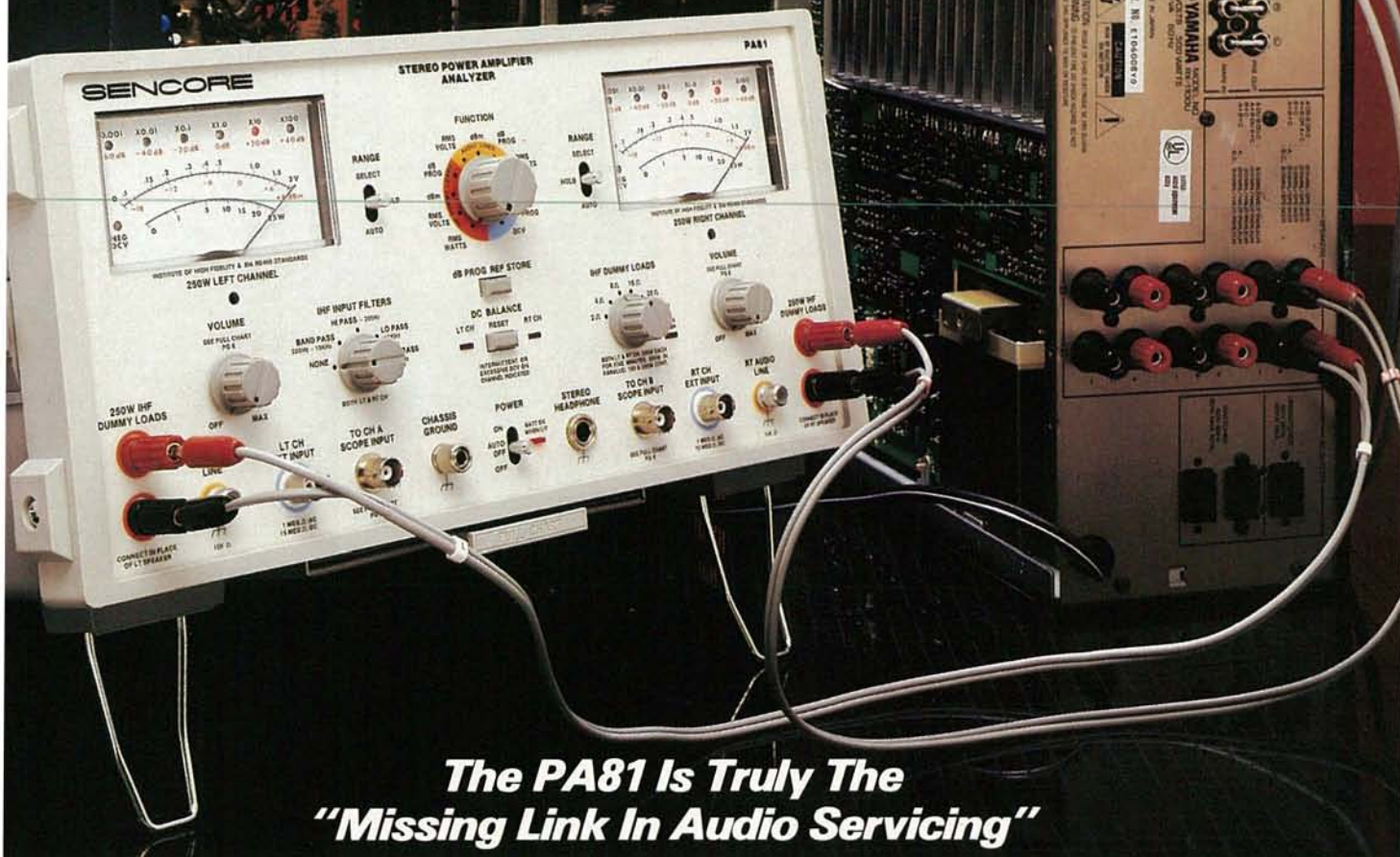Dynamically Analyze Stereo Audio Power Amplifiers To A Full 500 Watts To IHF/EIA* Specifications In Less Than 1/2 The Time It Now Takes




The PA81 Is Truly The "Missing Link In Audio Servicing"

Introducing the "Missing Link In Audio Servicing," with the NEW PA81 Stereo Power Amplifier Analyzer™ from Sencore Electronics. The PA81 provides everything you need for power amplifier analyzing integrated into one complete package, with:

- **Twin Frequency Compensated Autoranged Wattmeters:** 250 watts per channel (500 watts if paralleled), and listen to audio clarity with built-in volume control.
- **Built-in IHF/EIA Testing Components At Your Fingertips:** 2, 4, 8, 16, and 32 ohm-zero reactance loads, and all specified bandpass audio filters.
- **Measure RMS Volts And dB As You Trace Through Circuits:** Plus, programmable dB to measure stage gain.
- **Test Intermittents To Prevent Amplifier Damage:** Built-in DC balance test, automatically opens loads.

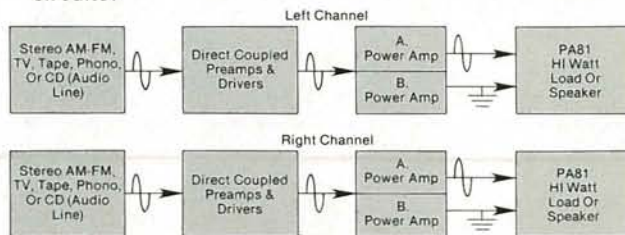- **Test Audio Line Levels To Make Sure The Driver Input Signal Is Correct:** Check turntables, AM tuners, FM tuners, TV stereo demodulator outputs, CD players, etc. for standard line levels.
- **Monitor Stereo Separation To 126 dB:** Monitor, troubleshoot, or align AM-FM or TV Stereo separation circuits.



Walk troubles out of any power amplifier stage, step by step, with the PA81.

SENCORE
3200 Sencore Drive, Sioux Falls, South Dakota 57107

*IHF—Institute of High Fidelity
EIA—Electronics Industry Association

Call 1-800-SENCORE
In Canada Call
1-800-851-8866

CIRCLE 176 ON FREE INFORMATION CARD

Ask About
A 10 Day
Video Preview



QUICK FIX

Super values on the tools and instruments you need to identify problems, get to them quickly and make repairs easily!

PRECISION HAND-HELD INSTRUMENTS

- Lightweight convenience. Easy to read
- Fast, precise results

B & K Precision Test Bench™

- 41 range voltmeter • Ammeter
- Ohmmeter • Frequency counter
- Capacitance meter
- Logic probe
- Transistor and diode tester
- Extra-large LCD display



Model 388-HD
Reg. \$129.95
Our Price **\$119.00**

SCOPE Digital Multimeter

- 11 function, 38 ranges including: Logic Level Detector, Audible and Visual Continuity, Capacitance & Conductance measurements.



Model DVM-638
Reg. \$87.50
Our Price **\$79.95**

CA-92 Deluxe Padded Case for DVM meters \$9.95
TL-216 Transistor and Capacitance Test Leads \$9.90

ALL-PURPOSE 92-PC. TOOL CASE

- Complete kit for home, workshop and auto
- Includes 52-pc. socket set with extenders • 2 tool pallets with roomy rear storage compartments • Attractive, rugged carry case.



Model FTK-28
Reg. \$169.95
Our Price **\$129.95**

DUAL TRACE OSCILLOSCOPES

A.W. SPERRY 20 MHz OSCILLOSCOPE

- Built-in component checker • Z-axis input
- Low power consumption • TV Video sync filter • High-sensitivity X-Y mode • Front panel trace rotator • Includes 2 test probes



Model 620C
Our Price **\$349.95**
Special Price

HITACHI 35 MHz OSCILLOSCOPE

- 19 calibrated sweeps
- 6" CRT with internal graticule, scale illumination & photographic bezel • Auto focus • X-Y operation
- TV sync separation
- Includes 2 probes (10:1 and 1:1)



Model V-355
Reg. \$899.95
Our Price **\$598.00**

ASK FOR YOUR FREE CATALOG

SCOPE ELECTRONICS

260 Motor Parkway
Hauppauge, New York 11788

TOLL FREE 800-648-2626

(In NY State 800-832-1446 Ext. 242)

TELEPHONE
ORDERS
NOW!



Service & Shipping Charge Schedule Continental U.S.A.

FOR ORDERS	ADD
\$25-50	\$4.50
\$51-100	\$5.50
\$101-200	\$7.00
\$201-300	\$8.00
\$301-400	\$9.00
\$401-500	\$10.00
\$501-750	\$12.50
\$751-1000	\$15.00
\$1,001-1,250	\$17.50
\$1,251-1,500	\$20.00
\$1,501-2000	\$25.00
\$2,001 and Up	\$30.00